

Build A Microcomputer

Chapter I Computer Architecture

Advanced Micro Devices



Copyright © 1978 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-1

PREFACE

In this introductory Chapter we intend to:

- 1). develop a common terminology for future chapters.
- 2). introduce several stored-program-computer design topics.
- 3). define some of the computer architect's problems (which will be solved in the subsequent chapters).

In order to achieve these goals, we will start with computer basics. It should be stressed that approaches and solutions can be chosen which are different from the ones described in this and the subsequent chapters. However, the general ideas described will be appropriate to gain familiarity with the micro-programmable bit-slice devices in order to use them in any design configuration.

BACK TO THE BASICS...

A STORED-PROGRAM-COMPUTER is defined as a machine capable of manipulating data according to predefined rules (instructions), where the program (collection of instructions) and data are stored in its memory (Fig. 1). Without some means of communication with the external world, the program and the data cannot be loaded into the memory nor can the results be read out. Therefore, an input/output device is required as shown in Fig. 2.

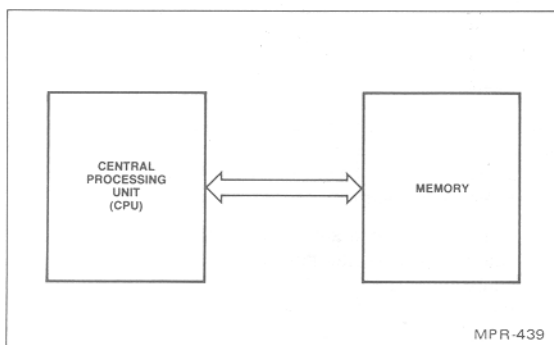


Figure 1. Basic Definition of a Stored-Program-Computer.

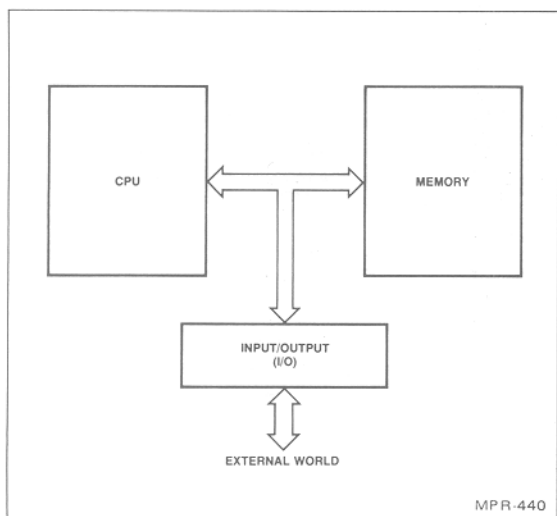


Figure 2. I/O Added to the Basic Stored-Program Computer.

The memory is usually organized in words, each containing N bits of information. A unique address is allocated for each word which defines its position relative to other words. The Central Processor Unit (CPU) usually reads or writes one word at a time by addressing the memory and then when the memory is ready, reading the contents of the word or writing new contents into that word. To perform this operation, two registers are usually used: The Memory Address Register (MAR), which contains the address and the Memory Data Register (MDR) which contains the data (Fig. 3).

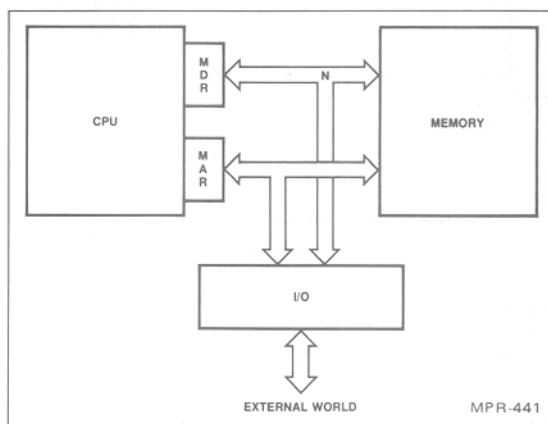


Figure 3. MAR and MDR Depicted for a Stored-Program Computer.

Since accessing a memory (reading from it or writing into it) is usually a relatively slow procedure, it is advantageous to have a few memory locations inside the CPU which can be read from or written into very fast. These locations are usually called Accumulators or Working Registers. Having these fast access registers inside the CPU (Fig. 4) enables many operations to be carried out without referring to the memory (through the MAR and the MDR) and therefore these operations are executed faster.

The unit which actually performs the data manipulation is called the Arithmetic & Logic Unit (ALU). It has two inputs for operands and one output for the result. It usually operates on all the bits of a word in parallel. The ALU can perform all or part of the following operations:

Arithmetic	Logical
Add	OR
Complement	AND
Subtract	XOR
Increment	NAND
Decrement	NOR
	XNOR
	Complement

In some architectures, one of the operands must always be in a special register (accumulator) and the result of the ALU operation is always transferred to this register. In a more general CPU, any two of the internal registers can contain the operands and the result of the ALU operation can be transferred to any one of them.

Another very useful feature of a CPU is the ability to shift the contents of a register or the output of the ALU one or more bits in either direction as shown in Fig. 5.

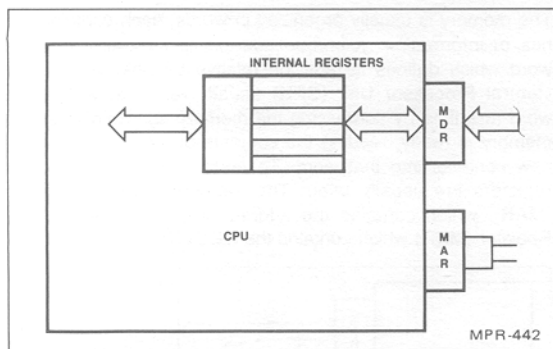


Figure 4. CPU with Internal High Speed Registers.

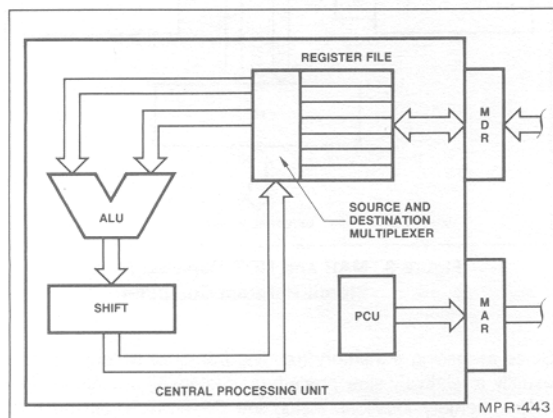


Figure 5. ALU and Shifter Added to the CPU Design.

We now have the elements to do any data manipulation required but we still need a unit which can properly set the MAR in order to find the next instruction of the program in the memory and to find its associated data. This unit is called the Program Control Unit (PCU) and its role is to load the MAR with the correct address in order to find the next instruction or data item or to point to a memory location where a data word should be written.

Often, the program steps (instructions, data) are written in the memory in consecutive locations, starting at address zero or at any other predefined address. The PCU can simply be incremented after each memory access thereby pointing to the address of the next instruction or data item. This counter-type PCU has very little flexibility. Sometimes we wish to change the "normal" flow of the instructions, particularly if we want to enable our computer to "make decisions" according to conditions prevailing at the current execution point. For example, we may want to execute one of two different sequences of instructions depending upon the result of the last operation performed. This is accomplished by loading the MAR with a new value (the address of the next instruction to be executed) rather than incrementing it. This operation is called a BRANCH or JUMP and can be unconditional (which allows execution of a non-contiguous string of instructions) or conditional (depending, for example, on whether the last operation's result was zero or not, was negative or positive, true or false, etc.).

Even more flexibility can be achieved by using a stack (a group of temporary internal or external memory locations) to store vital data. A stack pointer is used to address the memory location currently at the top of the stack. Indirect and relative addressing and other sophisticated addressing modes (all of which can be handled by the PCU) will be discussed later. Meanwhile, Fig. 5 shows the PCU as a part of the CPU.

Executing an instruction in our computer now requires the following steps:

- The PCU loads the address of the next instruction to the MAR and signals to the memory that a Read is requested. Incidentally, the PCU may be as simple as a Program Counter equal to the address width. The memory loads the MDR with the contents of the location addressed.
- The CPU decodes the instruction: i.e., (assuming operands are in internal registers) selects the proper registers to feed the ALU, selects the proper function to be performed by the ALU, sets up the shifter to displace the result, if required, and selects the register in which the result should be stored.
- The ALU performs the function desired.
- The result is loaded into the destination register.
- The result is also examined to determine whether a BRANCH is to be performed.
- The PCU calculates the address of the next instruction, (usually called a "FETCH").

This procedure becomes more complicated if the operands are not stored in the internal registers or if the result is not to be stored in one of them. Let's take an example instruction using relative addressing:

"Take the first operand from the location specified by the sum of the word after this instruction (immediate) and the contents of register R1; take the second operand from the location specified by the sum of the second word after this instruction and the contents of R2; add the two operands and place the result in the location specified by the sum of the third word after this instruction and the contents of register R3. Then execute the instruction located at the address, which is the sum of the fourth word after this instruction and the contents of register R4 if there is a carry resulting from the addition. Otherwise continue sequentially".

The steps required to execute this instruction are as follows:

- The PCU loads the address of the next instruction to the MAR, signalling to the memory that a Read is requested. The memory loads the MDR with the contents of the location addressed.
- The CPU decodes the instruction, i.e., initiates the following steps.
- The PCU is incremented and the next word is read from the memory.
- Register R1 and the MDR are selected as source registers, MAR is the destination register.
- The ALU performs "ADD" and the result is placed in the MAR.
- The first operand is fetched from the memory and placed, for example, in R5.
- The PCU is incremented and the next word is read from the memory.
- Register R2 and the MDR are selected again as source registers and MAR as the destination.

- i). The ALU performs "ADD" and the result is placed in MAR.
- j). The second operand is fetched from the memory and is placed, for example, in R6.
- k). The PCU is incremented, the next word is read from the memory.
- l). Register R3 and the MDR are selected as source registers, the MAR as destination.
- m). The ALU performs "ADD" and the result is placed in the MAR, which now points to the location where the sum of the operands should be stored.
- n). Registers R5 and R6 are selected as sources (they contain the operands), MDR is now the destination.
- o). The ALU performs "ADD" and the result is placed in MDR.
- p). A memory write cycle takes place and the contents of the MDR is stored at the desired address.
- q). The carry is examined to determine the next step to be performed. Assume there is no carry.
- r). The PCU is incremented twice (in order to skip the fifth word of the present instruction). It now points to the address of the next instruction.

As can be seen, 18 steps were used to perform a single addition using this complex relative addressing scheme. Obviously, our CPU needs some kind of "coordinator" which can:

- 1). Decode an instruction fetched from the memory.
- 2). Initiate the proper cycle of steps to be performed.
- 3). Set up the various controls for each step.
- 4). Execute the steps in an orderly sequence.
- 5). Make decisions according to the state of various signals (conditions).

We will call this coordinator the Computer Control Unit (CCU) and it is depicted in Fig. 6. Our CPU is now complete (more or less) and we will go into more detail later.

THE MEMORY

Let's now discuss the memory. The information stored in the memory is organized in words, where each word consists of N bits. N may be as small as 8 for very simple processors or as large as 64 in more powerful machines. The most common memory width for minicomputers is 16 bits. The number N is called the width of the memory and the number of bits in the MDR is obviously also N; equal to the width of the memory.

The depth of a memory is the number of words it contains. With a MAR having k bits, 2^k consecutive memory locations can be addressed. The addresses start from zero and range through 2^k-1 .

The read access time of a memory directly accessible by the CPU is the time needed from stable address at the memory until the data is properly stored in the MDR. This access time depends on the type of memory used and can be as low as a few tens of nanoseconds and as large as several microseconds. Using high speed memory improves the performance of the computer as less time is wasted waiting for the memory to respond. In general, faster memories are costly, take more PC board area and use more power which results in more heat. A 32 bit wide, 2K (2048) word memory with 50 nanosecond access time may need 10 amps from the +5V power supply and may require a board area of 10" x 6". Yet this is a very small memory space.

It is usually not justified to have very large high-speed memories. Not all the programs and associated data need to reside in this memory at once. We may have the current program (or only a part of it) in the memory while other programs or data files can reside elsewhere and be brought into memory during the appropriate part of the program when needed.

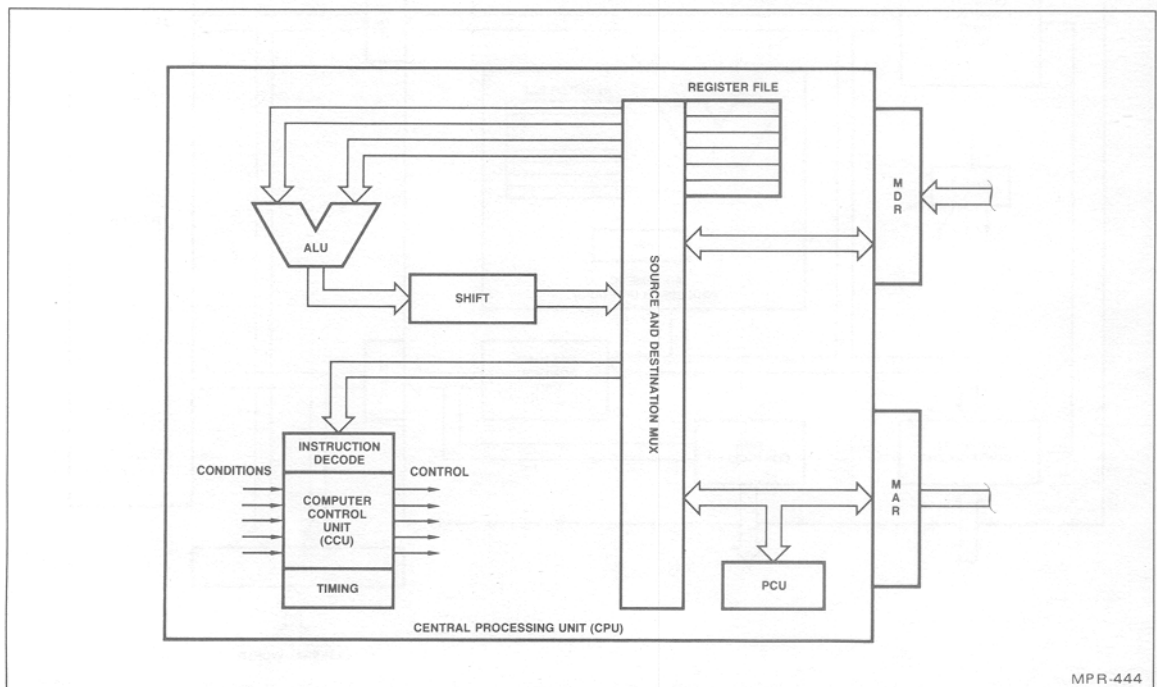


Figure 6. A Computer Control Unit (CCU) Included in a CPU.

This "elsewhere" may be a magnetic tape, cassette, disk, diskette, etc. and we will call it Bulk Memory. The distinctive characteristics of Bulk Memory are:

- 1). very large capacity
- 2). non-volatile (retains the information when not in use)
- 3). not randomly accessible
- 4). long access time
- 5). inexpensive (per bit)

Usually, Bulk Memory devices are serially accessible, i.e., the access time for the first word is large, but then consecutive words can be accessed relatively fast.

In a later chapter the most efficient process of communication between the main and the bulk memory, called the Direct Memory Access (DMA), will be discussed in detail.

THE EXTERNAL WORLD

In any useful machine, some means of communicating with the external world is needed. It may be a keyboard, a CRT, a card reader, a paper tape punch or, in a process controller, reading sensors or positioning actuators. The common denominator of almost all of the input/output devices is that they are much slower than the CPU and therefore a timing problem arises; the CPU must know when the I/O device is ready for data transfer. Usually, a signal is sent by the device to the CPU in order to draw its attention. The CPU now can do one of two things:

- 1). Test this signal periodically and when it is present, jump to a program which handles the data transfer. This type of operation is called "Polling". This technique has two

major drawbacks: First, appreciable computer time is spent performing these periodic tests where most of them will fail (no "Ready" signal present). Second, the recognition by the computer CPU of the appearance of a signal is delayed until the CPU arrives at this device in its polling sequence.

Imagine what will happen if there are a large number of I/O devices. Long latency times (delays) will occur if many I/O devices are busy simultaneously.

- 2). Include some hardware in the CPU which can sense the presence of a "Ready" signal and interrupt the normal flow of the instructions and force the computer to "Jump" to the I/O service program whenever there is a request. It can even send the CPU to different programs according to the I/O device whose "Ready" flag was detected and even establish priority among the different devices if more than one device would like to have the CPU's attention at the same time. Moreover, under program control, this circuitry can ignore some or all of the signals if the computer CPU must not be interrupted at that time. Obviously by paying the price of very little hardware, we gain enormously in computer performance. We will call this hardware the "Interrupt Controller" and will discuss it thoroughly later.

Our computer is now depicted in Fig. 7. We have included the ALU, the internal register file and the shift circuit in one block, which we call the "Arithmetic Processor Unit."

In the following pages and in the subsequent chapters, we will deal in more detail with each area of the machine.

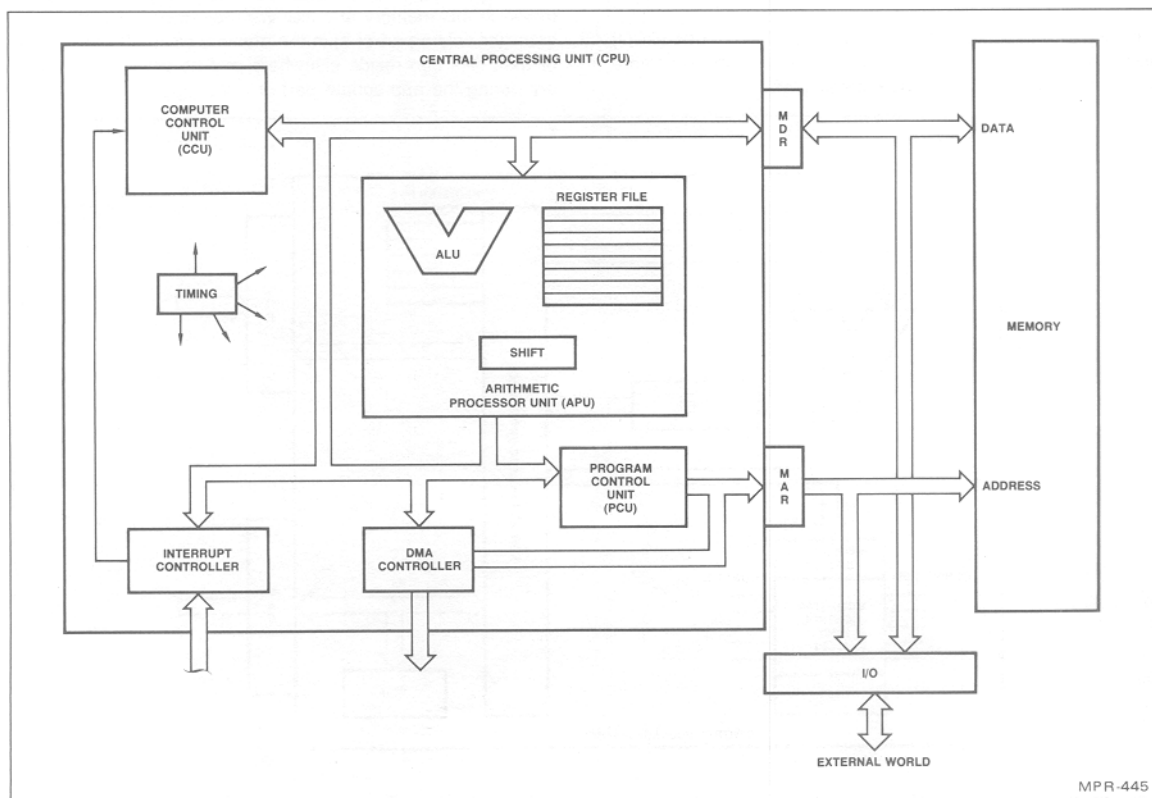


Figure 7. The Stored-Program-Computer with DMA and Interrupt Control Added.

A WORD ABOUT THE INSTRUCTION SET

The internal architecture of the CPU depends to some extent on the instruction set the computer is to execute. If the instruction set is large, some of the instructions usually are more complicated and the computer is more powerful, faster and more efficient. On the other hand, the internal circuitry is also more complicated. Some examples of these tradeoffs are as follows.

ALU Processing Capability:

Although with three basic functions (add, complement, and OR/AND) all the arithmetic and logic operations can be performed, most processors are built to perform subtract, NAND, XOR, etc. This is perhaps the most outstanding example of how performance and speed can be gained with little penalty on the complexity of the machine. With the added features an XOR operation can be performed in one instruction instead of 5.

Data Movement:

Let us assume 4 different computers whose data movement capabilities are described below:

Machine A). A word can be read from the memory and loaded into Register A only. The contents of Register A can be written into the memory, or can be moved into any other register. The contents of any register can be copied into Register A.

Machine B). The contents of any register can be copied into any other register or it can be written into the memory. A word read from the memory can be loaded into any register.

Machine C). As B above but with the added capability to read from one location in memory, to write that word into another location in memory.

Machine D). As C above and also the memory-to-memory operation can be performed on consecutive addresses repetitively. The number of word transfers (or upper and lower address limits) are specified by the instruction.

Machine A has very limited data movement capability. In order to perform an operation on two operands residing in the memory, we have to:

- 1). Bring the first operand from the memory into Register A.
- 2). Copy it into another register.
- 3). Bring the second operand into Register A.
- 4). Perform the operation required (result in A).
- 5). Store the contents of Register A into the memory.

If consecutive operations are required with several partial results, the drawbacks of machine A become more annoying, especially if the number of internal registers is small.

Moving a data block from one location in the memory to another location can be performed by one instruction in computer D, but requires the transfer of each word first to an internal register then to the new memory location in machines A, B (two instructions for each word transferred).

Obviously the decoding, multiplexing and sequencing of the computers grow in complexity as we proceed from machine A to machine D. We trade the complexity of hardware versus the software (programming), speed and performance.

Addressing:

The operands for an operation can be found in several ways:

- The operand is an explicit part of the instruction (Immediate)
- The address of the operand is an explicit part of the instruction. (Direct)
- The address of the operand is in an internal register; the register itself is specified by the instruction. (RR)
- The address of the operand is the sum of the contents of an internal register (specified by the instruction) and a number (called the displacement) which is an explicit part of the instruction. (RX)
- The contents of an internal register are added to a number found in an address specified by the instruction. The sum is the address of the operand. (Indirect)
- The contents of an internal register are added to a number which is an explicit part of the instruction. The sum points to the location where the address of the operand is written. (Indirect)
- The contents of an internal register are added to a number which can be found at the location explicitly specified by the instruction. The sum thus formed points to a location where the address of the operand is written.
- Etc.

Many other schemes can be formed by combining the above operations or by chaining them. In every case an "Effective Address" must be found by calculations and/or memory references. Again, we can gain performance by using more sophisticated addressing schemes but we will pay for it by adding complexity to our machine, especially in its control portion.

TIMING, SEQUENCING, CONTROLLING

In the previous paragraphs we have shown that we can gain performance in our computer by having a more complicated instruction set but more complex hardware is required, usually in the CCU. We have also shown an example for an "Add" operation which required 18 precisely controlled steps. Even if we assume that some of them can be performed simultaneously, we will need a multiphase clock to control these steps – something like that shown in Fig. 8. We can now load an instruction register at the beginning of an instruction with the first word of the instruction (the OP CODE) as is shown in Fig. 9. Using the outputs of the Instruction Register (IR_0 to IR_{n-1}), the different phases of the clock and the various condition inputs to the CCU, we can now try to write the logical equations which should satisfy all of the steps of all the instructions of our instruction set. Then use Karnaugh maps or other techniques to reduce these equations and finally realize them using AND, OR, INVERT gates and Flip Flops. Simple, isn't it? Imagine the complexity of a sophisticated computer and the debugging process it needs!

The question posed immediately is: Isn't there a more organized and more easily understandable way to do that? Or, perhaps, can we have some processor do the job for us? Can't we have some kind of "micro-machine" which can take care of all the timing, sequencing and controlling jobs of our computer – a computer inside the computer? With the advent of the Am2900 family – new Bipolar LSI devices – the answer is: Yes, we can!

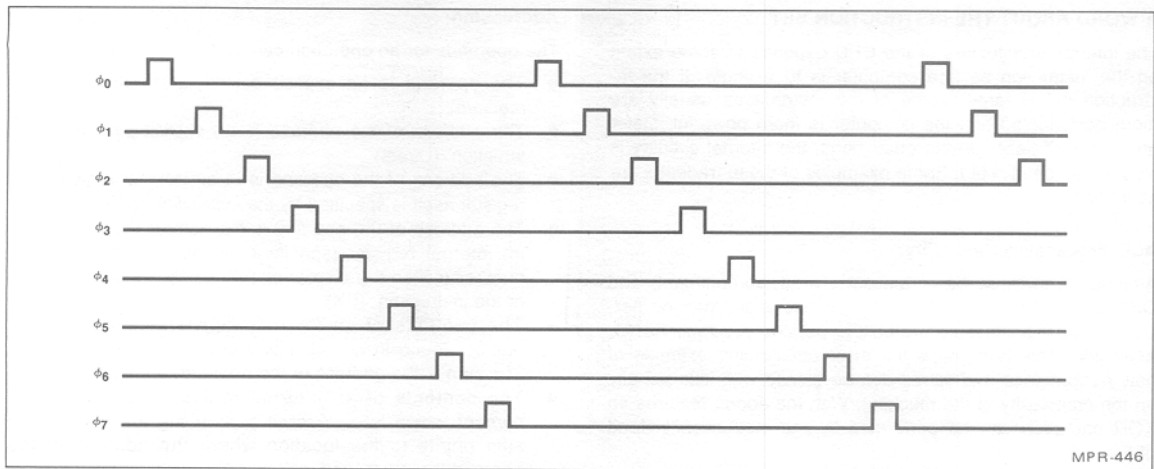


Figure 8. An 8-Phase Clock.

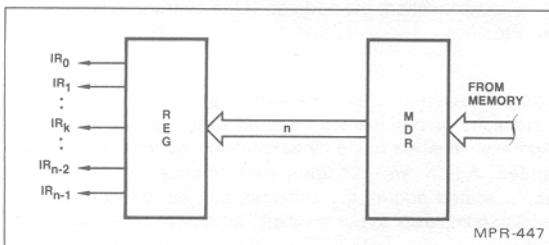


Figure 9. The Instruction Register Bits.

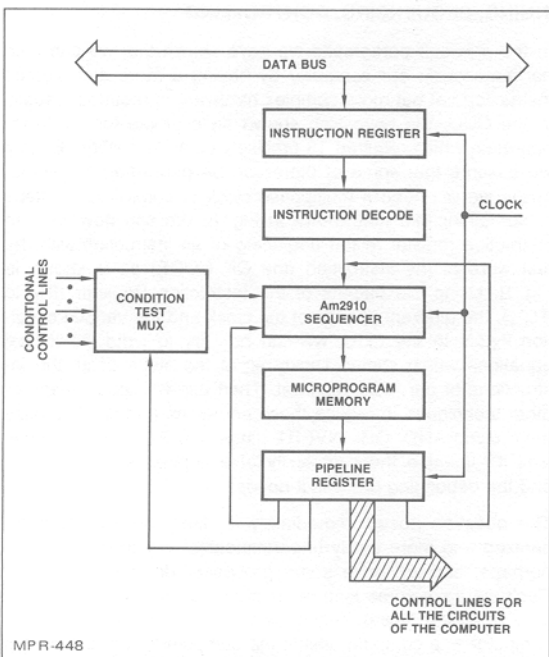


Figure 10. The Micromachine.

THE MICRO-MACHINE

What we need is essentially a machine which can execute a number of well defined sequences. But, remember that this is exactly the purpose of a stored program computer. The only difference between our micro-machine and a general purpose computer is that in the general purpose computer the program to be executed is changed from task to task, while in our micro-machine it is fixed. This allows the use of PROM for its memory instead of the RAM needed in the general purpose (GP) computer. Our Computer Control Unit (CCU) using this micro-machine may now look like Figure 10.

Basically, a microprogrammed machine is one in which a coherent sequence of microinstructions is used to execute various commands required by the machine. If the machine is a computer, each sequence of microinstructions can be made to execute a machine instruction. All of the little elemental tasks performed by the machine in executing the machine instruction are called microinstructions. The storage area for these microinstructions is usually called the microprogram memory.

A microinstruction usually has two primary parts. These are: (1) the definition and control of all elemental micro-operations to be carried out and (2) the definition and control of the address of the next microinstruction to be executed.

The definition of the various micro-operations to be carried out usually includes such things as ALU source operand selection, ALU function, ALU destination, carry control, shift control, interrupt control, data-in and data-out control, and so forth. The definition of the next microinstruction function usually includes identifying the source selection of the next microinstruction address and, in some cases, supplying the actual value of that microinstruction address.

Microprogrammed machines are usually distinguished from non-microprogrammed machines in the following manner. Older, non-microprogrammed machines implemented the control function by using combinations of gates and flip-flops connected in a somewhat random fashion in order to generate the required timing and control signals for the machine. Microprogrammed machines, on the other hand, are normally

considered highly ordered and more organized with regard to the control function field. In its simplest definition, a microprogram control unit consists of the microprogram memory and the structure required to determine the address of the next microinstruction.

The OP-CODE (type of instruction to be executed by the computer) is loaded into the Instruction Register and the Instruction Decoder decodes it. Actually, it generates the microaddress where the first step of the execution sequence for that instruction resides in the microprogram memory. The Am2910 sequencer then generates the microaddress of the next microinstruction. The microprogram data supplies the control signals we need to control all the parts of the com-

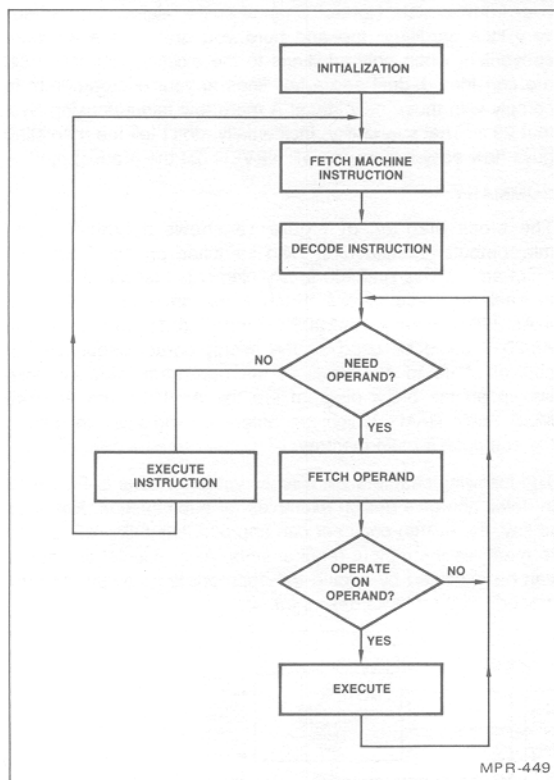


Figure 11. Computer Control Function Flow Diagram.

puter (and there are a lot of them), including the sequencer itself. When all the steps of a machine instruction are executed, the microprogram will cause the reading (fetch) of the next machine instruction from the computer main memory. Typically, the Computer Control Unit is used to fetch instructions and decode them using a PROM for mapping the op code to the initial address of the sequence of microinstructions used to execute this particular instruction. It will also fetch all of the operands needed by the machine instruction and deliver them to the ALU for processing. An example of the flow of a typical Computer Control Unit is shown in Figure 11.

Assume the OP-CODE of the machine instruction that we fetch is 8 bits wide. This allows us to execute a minimum of 256 different instructions. Assume also that an average of 6 steps are needed to execute these instructions. Even if separate microprogram memory locations are used, a depth of this microprogram memory is only 1-1/2K ($K = 1024$). But in that case, the sequencer can almost be replaced by a simple counter. Usually we would like to share some micro-routines among different instructions. With very little effort, we can shrink the depth of the microprogram memory of Figure 10 to less than 1/2K. Of course the sequencer will be a little more sophisticated; it will perform conditional Branch and micro-subroutine CALL's; but we still don't need the complicated addressing schemes for microprogram control as were described earlier as a part of the machine instruction set.

On the other hand, the width of our microprogram memory may be large — maybe 60 to 100 bits. This will depend on the number of control lines needed in our computer. This is of no great disadvantage since the price of PROM devices is dropping constantly. In a future chapter we will discuss techniques to reduce the depth and width of the microprogram memory to save cost.

It is important to understand the distinction between machine level instructions and microprogram instructions. Figure 12 shows a typical machine instruction for a 16 bit minicomputer that has an 8-bit opcode to identify one of 256 instructions; a 4-bit source register specification to identify one of 16 source registers and a 4-bit destination register specification to identify one of 16 destination registers. The microprogram instruction of Figure 12 may contain from 32 to 128 bits in a typical design; or even more bits in a very fast, highly parallel microcoded machine. This microinstruction word usually will contain fields for the ALU source operand, ALU function, ALU destination, status load enable, shift multiplexer control, bus

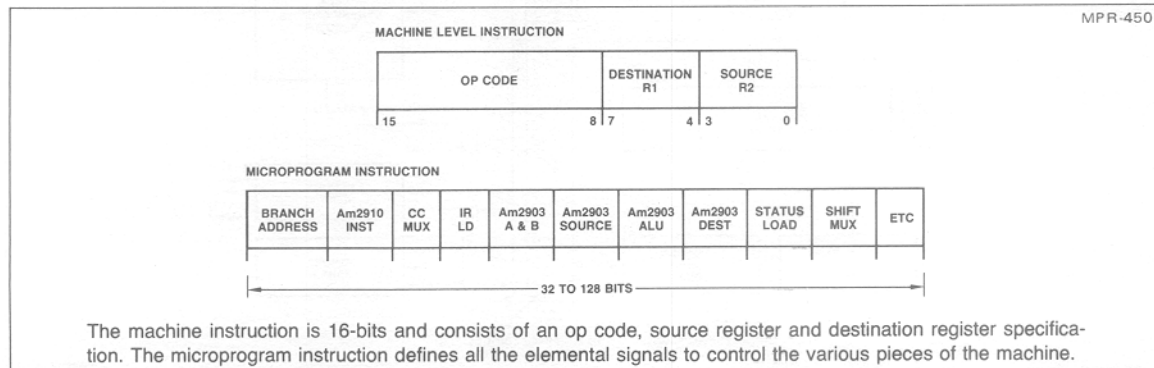


Figure 12.

cycle control, etc. These fields are used to control the various devices within the machine so that its execution is as desired on each clock cycle. This is more straightforward than using combinatorial logic and yields a more organized design.

Let us now compare the depth-over-width (d/w) ratio of the computer's main memory to that of our microprogram memory.

In the Am9080A type microprocessor, the data field is 8 bits and the address field is 16 bits, allowing direct addressing of 64K locations. The ratio d/w is 8K. In some minicomputers, the data width is 16-32 bits and the addressing capability is 64-128K. The d/w ratio is about the same. In larger computers with 32-64 bit data width, we find 256-512K deep memories or even deeper ones. The d/w ratio again is 8K at least.

On the other hand, the d/w ratio in microprogram memories is seldom greater than a few tens. Even if we assume that it is 2K deep and only 64 bits wide, we arrive at a d/w ratio of only 32; usually it will be around 10. It is much easier to control a machine with a d/w ratio of 10 to 20 than to control one with d/w = 8K.

ONE MORE WORD

We have suggested a replacement of the "random logic" realization of the CCU by a micro-machine. We call this a "Microprogrammed Architecture". Perhaps the biggest advantage of this type of architecture is the ease of structuring the control sequence. We allocate a bit or a group of bits in the microprogram memory to control a certain function (e.g.: ALU source register selection, ALU function, ALU destination selection, condition selection, next address calculation selection, MDR destination selection, MAR source selection, etc., etc.) and for each microstep we write the appropriate state for these bits (LOW-HIGH) into this memory field. Later we will see that automated and sophisticated tools are available to perform this microprogram writing. One such tool is AMDASM™ as available on System 29. But, this is not the only advantage of the microprogrammed architecture.

As nobody is perfect, some "bugs" may inadvertently slip into the design. In a random logic architecture, we will have to re-design and usually rebuild the whole computer. On the other hand, in a microprogrammed machine it is usually sufficient to change a couple of bits in the microprogram to rectify the problem. This is even easier if a RAM instead of a PROM is used during the development and debugging phases. Of course, we must be able to load this memory with the microprogram by some external means. Again, a powerful tool is available: AMD's System/29™.

Finally, let's face the reality: The marketing guys usually change their requirements (i.e., the instruction set) when you are 80% through your logic design. Now you have to start over from scratch. Not so! Change some microcode, perhaps very little hardware too and here you are! It is even more convenient when only additions to the existing instruction set are considered. Just add a few lines to your microprogram to comply with those new ideas! A mere few minutes using System 29 - That's flexibility! Incidentally, don't tell the marketing guys how easy it is or you will NEVER get the product out!!

SUMMARY

The block diagram of Figure 13 shows a typical 16-bit minicomputer architecture. Also identified on this block diagram are various Am2900 family elements that might be used in each of these blocks. Such a design might use either 4-Am2901A's or 4-Am2903's for the data path ALU. An Am2910 could be used as the microprogram sequencer for control of up to 4K words of microprogram memory. Also shown on the block diagram are the Am9130 and Am9140 MOS Static RAM's which are potential candidates for use in the computer's main memory.

The following chapters will discuss various blocks of Figure 13 in detail and give design examples for each section. Needless to say, the design engineer can appropriately tailor any design to meet his throughput requirements. Also, special algorithms can be executed by adding the appropriate hardware and microcode to the blocks described.


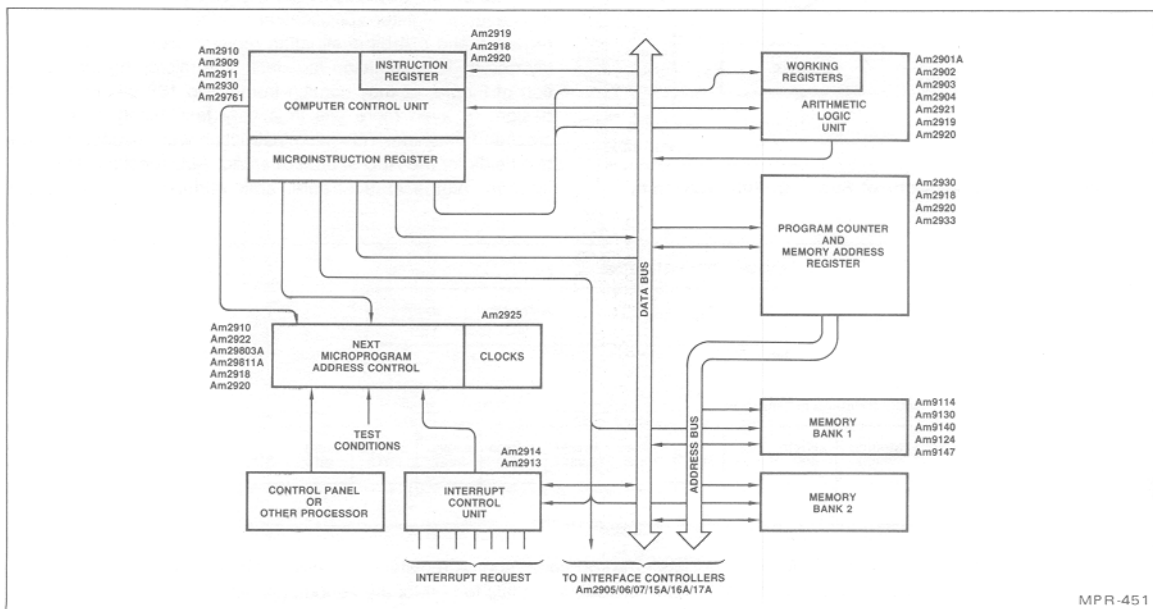


Figure 13. A Generalized Computer Architecture.

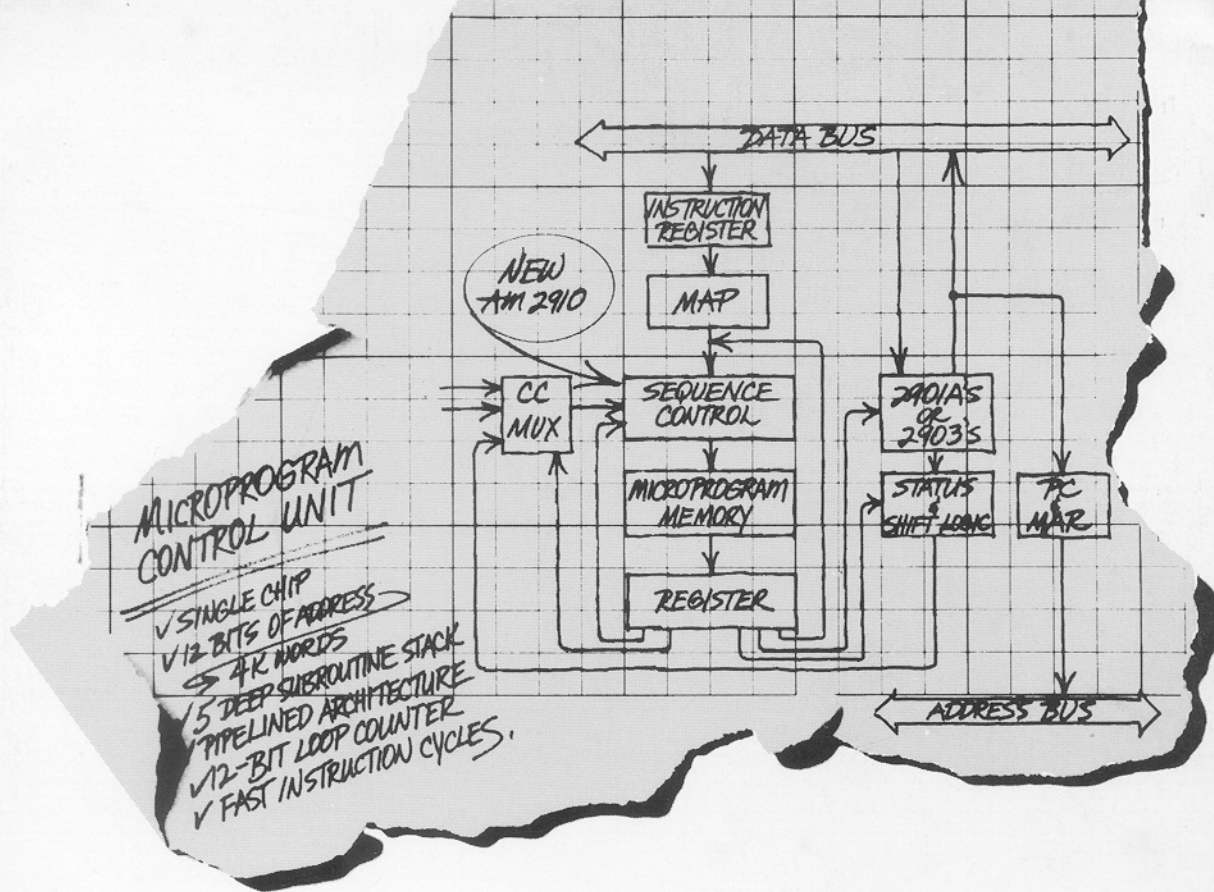AMDASM is a trademark of Advanced Micro Devices.
System 29 is a trademark of Advanced Micro Devices.



**ADVANCED
MICRO
DEVICES, INC.**
901 Thompson Place
Sunnyvale
California 94086
(408) 732-2400
TWX: 910-339-9280
TELEX: 34-6306
TOLL FREE
(800) 538-8450



Build a Microcomputer

Chapter II Microprogrammed Design

Advanced Micro Devices



Copyright © 1978 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-2

CHAPTER II MICROPROGRAMMED DESIGN

INTRODUCTION

A microprogrammed machine is one in which a coherent sequence of microinstructions is used to execute various commands required by the machine. If the machine is a computer, each sequence of microinstructions can be made to execute a machine instruction. All of the little elemental tasks performed by the machine in executing the machine instruction are called microinstructions. The storage area for these microinstructions is usually called the microprogram memory. This technique was identified by Wilkes in the 1950's as a structured approach to the random control logic in a computer.

A microinstruction usually has two primary parts. These are: (1) the definition and control of all elemental micro-operations to be carried out and (2) the definition and control of the address of the next microinstruction to be executed.

The definition of the various micro-operations to be carried out usually includes such things as ALU source operand selection, ALU function, ALU destination, carry control, shift control, interrupt control, data-in and data-out control and so forth. The definition of the next microinstruction function usually includes identifying the source selection of the next microinstruction address, and in some cases, supplying the actual value of that microinstruction address.

Microprogrammed machines are usually distinguished from non-microprogrammed machines in the following manner. Older, non-microprogrammed machines implemented the control function by using combinations of gates and flip-flops connected in a somewhat random fashion in order to generate the required timing and control signals for the machine. Microprogrammed machines, on the other hand, are normally considered highly ordered and more organized with regard to the control function field. In its simplest definition, a microprogram control unit consists of the microprogram memory and the structure required to determine the address of the next microinstruction.

Microprogramming is normally selected by the design engineer as a control technique for finite state machines because it improves flexibility, performance, and LSI utilization. Several additional key features of microprogrammed designs are listed below:

- More structured organization
- Diagnostics can be implemented easily
- Design changes are simple
- Field updates are easy
- Adaptations are straightforward
- System definition can be expanded to include new features
- Documentation and Service are easier
- Design aids are available
- Cost and design time are reduced

THE MICROPROGRAM MEMORY

The microprogram memory is simply an N word by M bit memory used to hold the various microinstructions. For an N word memory, the address locations are usually defined as location 0 through N-1. For example, a 256-word microprogram memory will have address locations 0 through 255. Each word of the microprogram memory consists of M bits. These M bits are usually broken into various field definitions and the fields can consist of various numbers of bits. It is the definition of the various fields of a microprogram word that is usually referred to as **FORMATTING**.

An example of how microinstruction fields are defined in a typical machine microprogram memory word is as follows:

- Field 1 – General purpose
- Field 2 – Branch address
- Field 3 – Next microinstruction address control
- Field 4 – Condition code multiplexer control
- Field 5 – Interrupt control
- Field 6 – Fast clock/slow clock select
- Field 7 – Carry control
- Field 8 – ALU source operand control
- Field 9 – ALU function control
- Field 10 – ALU destination control
- Field 11 – Shift multiplexer control
- Field 12 – etc.

EXECUTING MICROINSTRUCTIONS

Once the microprogram format has been defined, it is necessary to execute sequences of these microinstructions if the machine is to perform any real function. In its simplest form, all that is required to sequence through a series of microinstructions is a microprogram address counter. The microprogram address counter simply increments by one on each clock cycle to select the address of the next microinstruction. For example, if the microprogram address counter contains address 23, the next clock cycle will increment the counter and it will select address 24. The counter will continue to increment on each clock cycle thereby selecting address 25, address 26, address 27, and so forth. If this were the only control available, the machine would not be very flexible and it would be able to execute only a fixed pattern of microinstructions.

The technique of continuing from one microinstruction to the next sequential microinstruction is usually referred to as **CONTINUE**. Thus, in microprogram control definition, we will use the **CONTINUE (CONT)** statement to mean simply incrementing to the next microinstruction.

MICROPROGRAM JUMPING

If the microprogram control unit is to have the ability to select other than the next microinstruction, the control unit must be able to load a **JUMP** address. The load control of a counter can be a single bit field within the microprogram word format. Let us call this one-bit field the microprogram address counter load enable bit. When this bit is at logic 0, a load will be inhibited and when this bit is a logic 1, a load will be enabled. If the load is enabled, the **JUMP** address contained within the microprogram memory will be parallel loaded into the microprogram address counter. This results in the ability to perform an N-way branch. For example, if the branch address field is eight bits wide, a **JUMP** to any address in the memory space from word 0 through word 255 can be performed.

This simple branching control feature allows a microprogram memory controller to execute sequential microinstructions or perform a **JUMP (JMP)** to any address either before or after the address currently contained in the microprogram address counter.

CONDITIONAL JUMPING

While the **JUMP** instruction has added some flexibility to the sequencing of microprogram instructions, the controller still lacks any decision-making capability. This decision-making capability is provided by the **CONDITIONAL JUMP (COND JMP)** instruction. Figure 1 shows a functional block diagram of a microprogram memory/address controller providing the capability to jump on either of two different conditions. In this example, the load select control is a two-bit field used to control a

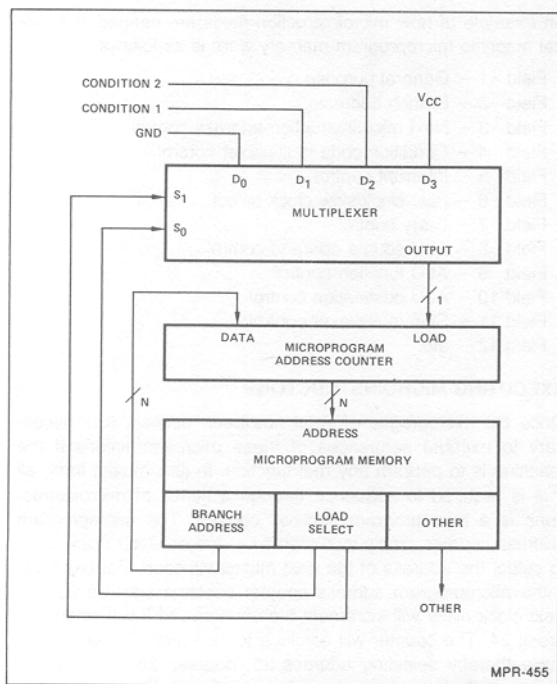


Figure 1. A Two-Bit Control Field Can be Used to Select CONTINUE, BRANCH, or CONDITIONAL BRANCH.

four-input multiplexer. When the two-bit field is equivalent to binary zero, the multiplexer selects the zero input which forces the load control inactive. Thus, the CONTINUE microprogram control instruction is executed. When the two-bit load select field contains binary one, the D₁ input of the multiplexer is selected. Now, the load control is a function of the Condition 1 input. If Condition 1 is logic 0, the microprogram address counter increments and if Condition 1 is logic 1, the jump address will be parallel loaded in the next clock cycle. This operation is defined as a CONDITIONAL JUMP. If the load select input contains binary 2, the D₂ input is selected and the same conditional function is performed with respect to the Condition 2 input. If the load select field contains binary 3, the D₃ input of the multiplexer is selected. Since the D₃ input is tied to logic HIGH, this forces the microprogram address counter to the load mode independent of anything else. Thus, the jump address is loaded into the microprogram address counter on the next clock cycle and an UNCONDITIONAL JUMP is executed. This load select control function definition is shown in Table 1.

TABLE 1.
LOAD SELECT CONTROL FUNCTION.

S ₁ S ₀	Function
0 0	Continue
0 1	Jump Condition 1 True
1 0	Jump Condition 2 True
1 1	Jump Unconditional

OVERLAPPING THE MICROPROGRAM INSTRUCTION FETCH

Now that a few basic microprogram address control instructions have been defined, let us examine the control instructions used in a microprogram control unit featuring the overlap fetching of the next microinstruction. This technique is also known as "pipelining". The block diagram for such a microprogram control unit is shown in Figure 2. The key difference when compared with previous microprogrammed architectures is the existence of the "pipeline register" at the output of the microprogram memory. By definition, the pipeline register (or microword register) contains the microinstruction currently being executed by the machine. Simultaneously, while this microinstruction is being executed, the address of the next microinstruction is applied to the microprogram memory and the contents of that memory word are being fetched and set-up at the inputs to the pipeline register. This technique of pipelining can be used to improve the performance of the microprogram control unit. This results because the contents of the microprogram memory word required for the next cycle are being fetched on an overlapping basis with the actual execution of the current microprogram word. It should be realized that when the pipeline approach is used, the design engineer must be aware of the fact that some registers contain the results of the previous microinstruction executed, some registers contain the current microinstruction being executed, and some registers contain data for the next microinstruction to be executed.

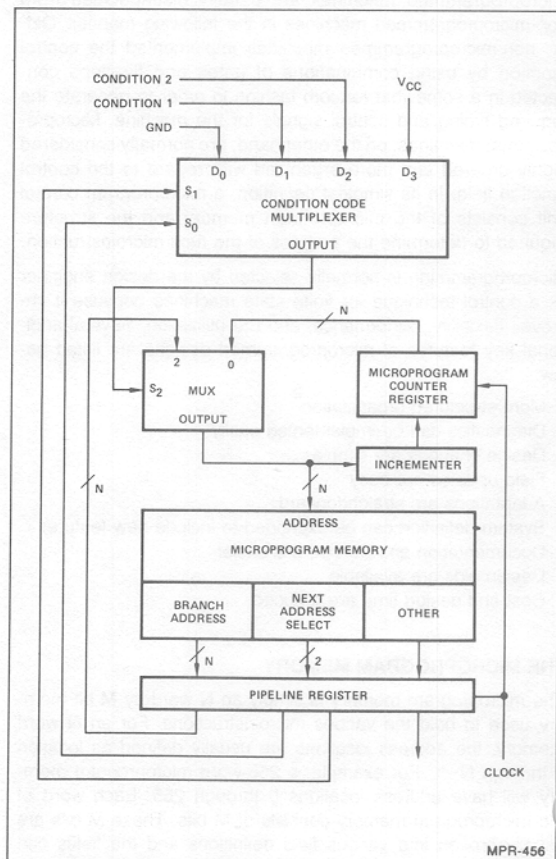


Figure 2. Overlapping (or Pipelining) the Fetch of the Next Microinstruction.

Let us now compare the block diagram of Figure 2 with that shown in Figure 1. The major difference, of course, is the addition of the pipeline register at the output of the microprogram control memory. Also, notice the addition of the address multiplexer at the source of the microprogram memory address. This address multiplexer is used to select the microprogram counter register or the pipeline register as the source of the next address for the microprogram memory. The condition code multiplexer is used to control the address multiplexer in this address selection. By placing an incrementer at the output of the address multiplexer, it is possible to always generate the current microprogram address "plus one" at the input of the microprogram counter register.

In Figure 1, the microprogram address counter was described as a counter and could be a device such as the Am25LS161 counter. In the implementation as shown in Figure 2, the Am25LS161 counter is not appropriate. Instead, an incrementer and register are used to give the equivalent effect of a counter.

The key difference between using a true binary counter and the incrementer register described here is as follows. When the jump address from the pipeline register is selected by the multiplexer, the incrementer will combinatorially prepare that address plus one for entry into the microprogram counter register. This entry will occur on the LOW-to-HIGH transition of the clock. Thus, the microprogram counter register can always be made to contain address plus one, independent of the selection of the next microinstruction address. When the address multiplexer is switched so that the microprogram counter register is selected as the source of the microprogram memory address, the incrementer will again set-up address plus one for entry into the microprogram counter register. Thus, when the address multiplexer selects the microprogram counter register, the address multiplexer, incrementer and microprogram counter register appear to operate as a normal binary counter.

The condition code multiplexer S_0S_1 operates in exactly the same fashion as described for the condition code multiplexer of Figure 1. That is, binary zero in the pipeline register (the current microinstruction being executed) forces an unconditional selection of the microprogram register via D_0 . Binary one or binary two in the next address select control bits of the pipeline register cause a conditional selection at the address multiplexer via D_1 or D_2 . Thus, a CONDITIONAL JUMP can be executed. Binary three in the next address select portion of the pipeline register causes an UNCONDITIONAL JUMP instruction to be executed via D_3 .

When the overall machine timing is studied, it will be observed that the key difference between overlap fetching and non-overlap fetching involves the propagation delay of the microprogram memory. In the non-pipelined architecture, the microprogram memory propagation delay must be added to the propagation delay of all the other elements of the machine. In the overlap fetch architecture, the propagation delay associated with the next microprogram memory address fetch is a separate loop independent of the other portion of the machine.

SUBROUTINING IN MICROPROGRAMMING CONTROL

Thus far, we have examined the CONTINUE instruction as well as the CONDITIONAL and UNCONDITIONAL JUMP instructions for overlap fetch. Just as in the programming of minicomputers and microcomputers, the advantages of SUBROUTINING can be realized in microprogramming. The idea here, of course, is that the same block of microcode (or even a single microinstruction) can be shared by several microinstruction sequences. This results in an overall reduction in the total

number of microprogram memory words required by the design. If we are to jump to a subroutine, what is required is the ability to store an address to which the subroutine should return when it has completed its execution. Examining the block diagram of Figure 3, we see the addition of a subroutine and loop (push/pop) stack (also called the file) and its associated stack pointer. The control signals required by the stack are an enable stack signal (FILE ENABLE = FE) which will be used to tell the file whenever we wish to perform a push or a pop, and a push/pop control (PUP) used to control the direction of the stack pointer (push or pop).

In this architecture, the stack pointer always points to the address of the last microinstruction written on the stack. This allows the "next address multiplexer" to read the stack at any time via port F. When this selection is performed, the last word written on the stack will be the word applied to the microprogram memory. The condition code multiplexer of the previous example has also been replaced by a next address control unit. This next address control unit (Am29811A) can execute 16 different next address control functions where most of these functions are conditional. Thus, the device has four instruction inputs as well as one condition code test input which is connected to the condition code multiplexer. Note also that the next address control field of the microprogram word has been expanded to a four-bit field. Outputs from the Am29811A next address control block are used to control the stack pointer and the next address multiplexer of the Am2911. In addition, the device has outputs to control the three-state enable of the pipeline register and the three-state enable of the starting address decode PROM. Also, the architecture has a counter that can be used as a loop-counter or event counter.

The 16 instructions associated with the Am29811A are listed in Table 2. As is easily seen by referring to Table 2, three of the instructions in this set are associated with subroutines in microprogram memory. The first instruction of this set, is a simple conditional JUMP-TO-SUBROUTINE where the source of the subroutine address is in the pipeline register. The RETURN-FROM-SUBROUTINE instruction is also conditional and is used to return to the next microinstruction following the JUMP-TO-SUBROUTINE instruction. There is also a conditional JUMP-TO-ONE-OF-TWO-SUBROUTINES, where the subroutine address is either in the PIPELINE register or in the internal REGISTER in the Am2911. This instruction will be explained in more detail later.

TYPICAL COMPUTER CONTROL UNIT ARCHITECTURE USING THE Am2911 AND Am29811A

The microprogram memory control unit block diagram of Figure 3 is easily implemented using the Am2911 and Am29811A. This architecture provides a structured state machine design capable of executing many highly sophisticated next address control instructions. The Am2911 contains a next address multiplexer that provides four different inputs from which the address of the next microinstruction can be selected. These are the direct input (D), the register input (R), the program counter (PC), and the file (F). The starting address decoder (mapping PROM) output and the pipeline register output are connected together at the D input to the Am2911 and are operated in the three-state mode.

The architecture of Figure 3 shows an instruction register capable of being loaded with a machine instruction word from the data bus. The op code portion of the instruction is decoded using a mapping PROM to arrive at a starting address for the

TABLE 2. FUNCTIONAL DESCRIPTION OF Am29811A INSTRUCTION SET.

MNEMONIC	INPUTS				OUTPUTS				
	INSTRUCTION I ₃ I ₂ I ₁ I ₀	FUNCTION	TEST INPUT	NEXT ADDR SOURCE	FILE	COUNTER	MAP-E	PL-E	
JZ	L L L L	JUMP ZERO	X	D	HOLD	L L	H	L	
CJS	L L L H	COND JSB PL	L H	PC D	HOLD PUSH	HOLD HOLD	H H	L L	
JMAP	L L H L	JUMP MAP	X	D	HOLD	HOLD	L	H	
CJP	L L H H	COND JUMP PL	L H	PC D	HOLD HOLD	HOLD HOLD	H H	L L	
PUSH	L H L L	PUSH/COND LD CNTR	L H	PC PC	PUSH PUSH	HOLD LOAD	H H	L L	
JSRP	L H L H	COND JSB R/PL	L H	R D	PUSH PUSH	HOLD HOLD	H H	L L	
CJV	L H H L	COND JUMP VECTOR	L H	PC D	HOLD HOLD	HOLD HOLD	H H	H H	
JRP	L H H H	COND JUMP R/PL	L H	R D	HOLD HOLD	HOLD HOLD	H H	L L	
RFCT	H L L L	REPEAT LOOP, CNTR ≠ 0	L H	F PC	HOLD POP	DEC HOLD	H H	L L	
RPCT	H L L H	REPEAT PL, CNTR ≠ 0	L H	D PC	HOLD HOLD	DEC HOLD	H H	L L	
CRTN	H L H L	COND RTN	L H	PC F	HOLD POP	HOLD HOLD	H H	L L	
CJPP	H L H H	COND JUMP PL & POP	L H	PC D	HOLD POP	HOLD HOLD	H H	L L	
LDCT	H H L L	LOAD CNTR & CONTINUE	X	PC	HOLD	LOAD	H	L	
LOOP	H H L H	TEST END LOOP	L H	F PC	HOLD POP	HOLD HOLD	H H	L L	
CONT	H H H L	CONTINUE	X	PC	HOLD	HOLD	H	L	
JP	H H H H	JUMP PL	X	D	HOLD	HOLD	H	L	

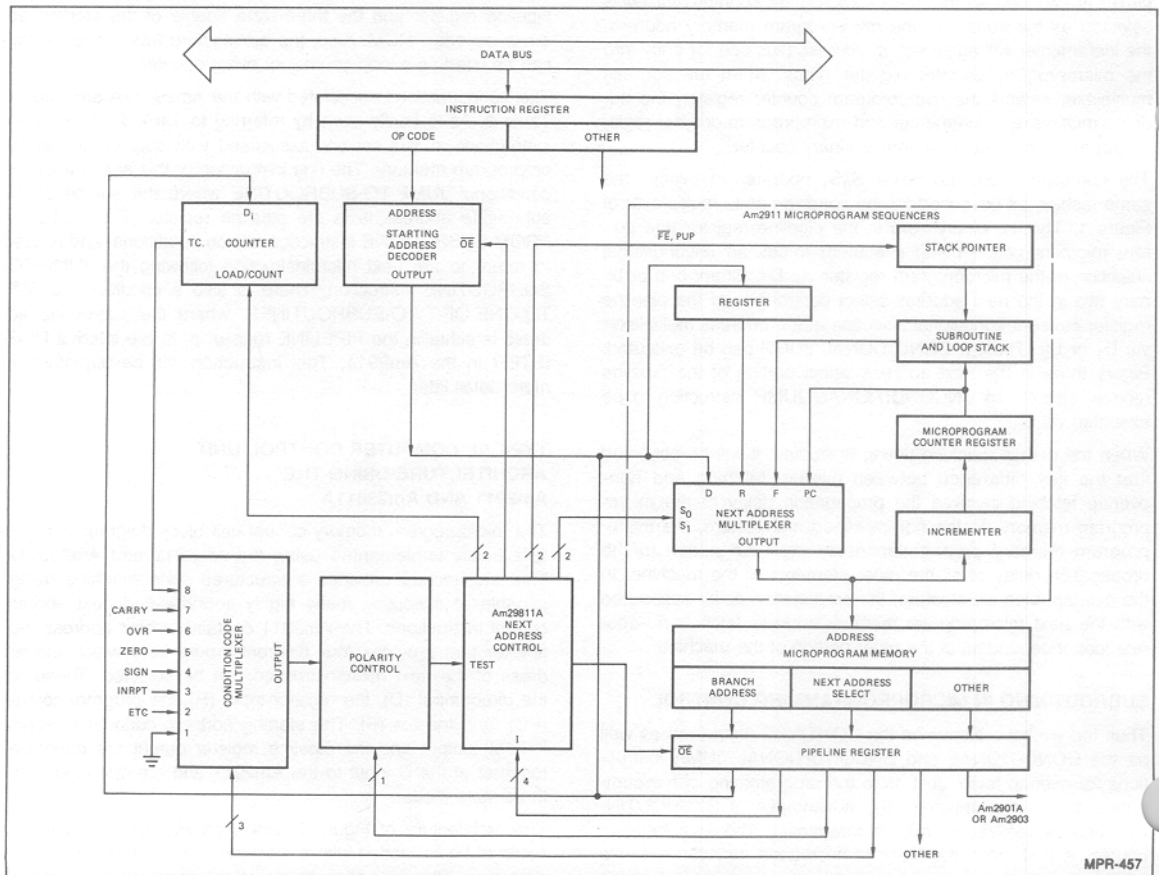


Figure 3. A Typical Computer Control Unit Using the Am2911 and Am29811A.

TABLE 3. PIN FUNCTIONS.

Abbreviation	Name	Function
D_i	Direct Input Bit i	Direct input to register/counter and multiplexer. D_0 is LSB
I_i	Instruction Bit i	Selects one-of-sixteen instructions for the Am2910
\overline{CC}	Condition Code	Used as test criterion. Pass test is a LOW on \overline{CC} .
\overline{CCEN}	Condition Code Enable	Whenever the signal is HIGH, \overline{CC} is ignored and the part operates as though \overline{CC} were true (LOW).
Ci	Carry-In	Low order carry input to incrementer for microprogram counter
\overline{RLD}	Register Load	When LOW forces loading of register/counter regardless of instruction or condition
\overline{OE}	Output Enable	Three-state control of Y_i outputs
CP	Clock Pulse	Triggers all internal state changes at LOW-to-HIGH edge
V_{CC}	+5 Volts	
GND	Ground	
Y_i	Microprogram Address Bit i	Address to microprogram memory. Y_0 is LSB, Y_{11} is MSB
\overline{FULL}	Full	Indicates that five items are on the stack
PL	Pipeline Address Enable	Can select #1 source (usually Pipeline Register) as direct input source
\overline{MAP}	Map Address Enable	Can select #2 source (usually Mapping PROM or PLA) as direct input source
\overline{VECT}	Vector Address Enable	Can select #3 source (for example, Interrupt Starting Address) as direct input source

microinstruction sequence required to execute the machine instruction. When the microprogram memory address is to be the first microinstruction of the machine instruction sequence, the Am29811A next address control unit selects the multiplexer D input and enables the three-state output from the mapping PROM. When the current microinstruction being executed is selecting the next microinstruction address as a JUMP function, the JUMP address will be available at the multiplexer D input. This is accomplished by having the Am29811A select the next address multiplexer D input and also enabling the three-state output of the pipeline register branch address field. The register enable input to the Am2911 is connected to ground so that this register will always load the value at the Am2911 D input. The value at D is clocked into the Am2911's register (R) at the end of the current microcycle, which makes the D value of *this* microcycle available as the R value of the *next* microcycle. Thus, by using the branch address field of two sequential microinstructions, a conditional JUMP-TO-ONE-OF-TWO-SUBROUTINES or a conditional JUMP-TO-ONE-OF-TWO-BRANCH-ADDRESSES can be executed by either selecting the D input or the R input of the next address multiplexer.

When sequencing through continuous microinstructions in microprogram memory, the program counter in the Am2911 is used. Here, the Am29811A simply selects the PC input of the next address multiplexer. In addition, most of these instructions enable the three-state outputs of the pipeline register associated with the branch address field, which allows the register within the Am2911 to be loaded.

The 4 x 4 stack in the Am2911 is used for looping and subroutines in microprogram operations. Up to four levels of subroutines or loops can be nested. Also, loops and subroutines can be intermixed as long as the four-word depth of the stack is not exceeded.

ARCHITECTURE OF THE Am2910

The Am2910 is a bipolar microprogram controller intended for use in high-speed microprocessor applications. It allows addressing of up to 4K words of microprogram. A block diagram is shown in Figure 4.

The controller contains a four-input multiplexer that is used to select either the register/counter, direct input, microprogram counter, or stack as the source of the next microinstruction address.

The register/counter consists of 12 D-type, edge-triggered flip-flops, with a common clock enable. When its load control, \overline{RLD} , is LOW, new data is loaded on a positive clock transition. A few instructions include load; in most systems, these instructions will be sufficient, simplifying the microcode. The output of the register/counter is available to the multiplexer as a source for the next microinstruction address. The direct input furnishes a source of data for loading the register/counter.

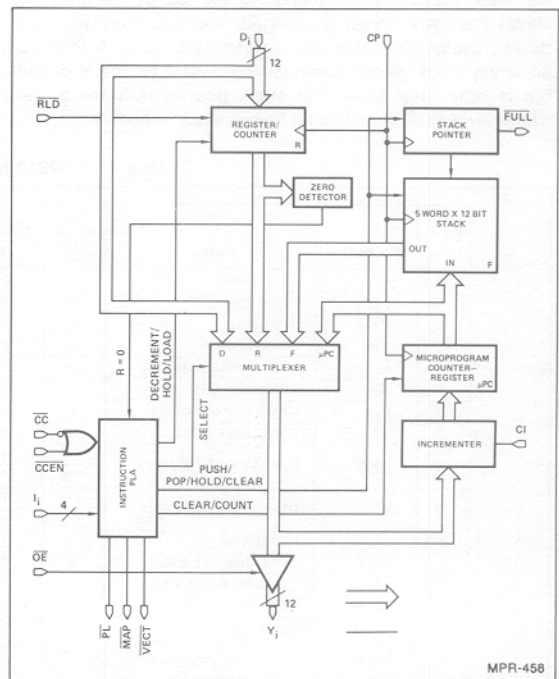


Figure 4. Am2910 Block Diagram.

The Am2910 contains a microprogram counter (μ PC) that is composed of a 12-bit incrementer followed by a 12-bit register. The μ PC can be used in either of two ways. When the carry-in to the incrementer is HIGH, the microprogram register is loaded on the next clock cycle with the current Y output word plus one ($Y+1 \rightarrow \mu$ PC). Sequential microinstructions are thus executed. When the carry-in is LOW, the incrementer passes the Y output word unmodified so that μ PC is reloaded with the same Y word on the next clock cycle ($Y \rightarrow \mu$ PC). The same microinstruction is thus executed any number of times.

The third source for the multiplexer is the direct (D) inputs. This source is used for branching.

The fourth source available at the multiplexer input is a 5-word by 12-bit stack (file). The stack is used to provide return address linkage when executing microsubroutines or loops. The stack contains a build-in stack pointer (SP) which always points to the last file word written. This allows stack reference operations (looping) to be performed without a pop. The stack pointer operates as an up/down counter. During microinstructions 2, 4 and 5, the PUSH operation is performed. This causes the stack pointer to increment and the file to be written with the required return linkage. On the cycle following the PUSH, the return data is at the new location pointed to by the stack pointer.

During six other microinstructions, a POP operation occurs. This places the information at the top of the stack onto the Y outputs. The stack pointer decrements at the next rising clock edge following a POP, effectively removing old information from the top of the stack.

The stack pointer linkage is such that any sequence of pushes, pops or stack references can be achieved. At RESET (Instruction 0), the depth of nesting becomes zero. For each PUSH, the nesting depth increases by one; for each POP, the depth decreases by one. The depth can grow to five. After a depth of five is reached, FULL goes LOW. Any further PUSHes onto a full stack overwrites information at the top of the stack, but leaves the stack pointer unchanged. This operation will usually destroy useful information and is normally avoided. A POP from an empty stack places non-meaningful data on the Y outputs, but is otherwise safe. The stack pointer remains at zero whenever a POP is attempted from a stack already empty.

The register/counter is operated during three microinstructions (8, 9, 15) as a 12-bit down counter, with result = zero available as a microinstruction branch test criterion. This provides efficient iteration of microinstructions. The register/counter is arranged such that if it is preloaded with a number N and then used as a loop termination counter, the sequence will be executed exactly N+1 times. During instruction 15, a three-way branch under combined control of the loop counter and the condition code is available.

The device provides three-state Y outputs. These can be particularly useful in designs requiring automatic checkout of the processor. The microprogram controller outputs can be forced into the high-impedance state, and pre-programmed sequences of microinstructions can be executed via external access to the address lines.

OPERATION

Table 4 shows the result of each instruction in controlling the multiplexer which determines the Y outputs, and in controlling the three enable signals $\overline{\text{PL}}$, $\overline{\text{MAP}}$ and $\overline{\text{VECT}}$. The effect on the μ PC, the register/counter, and the stack after the next positive-going clock edge is also shown. The multiplexer determines which internal source drives the Y outputs. The value loaded into μ PC is either identical to the Y output, or else one greater, as determined by CI. For each instruction, one and only one of the three outputs $\overline{\text{PL}}$, $\overline{\text{MAP}}$ and $\overline{\text{VECT}}$ is LOW. If these outputs control three-state enables for the primary source of microprogram jumps (usually part of a pipeline register), a PROM which maps the instruction to a microinstruction starting location, and an optional third source (often a vector from a DMA or interrupt source), respectively, the three-state sources can drive the D inputs without further logic.

Several inputs, as shown in Table 4 can modify instruction execution. The combination $\overline{\text{CC}}$ HIGH and $\overline{\text{CCEN}}$ LOW is used as a test in 10 of the 16 instructions. $\overline{\text{RLD}}$, when LOW, causes the D input to be loaded into the register/counter, overriding any HOLD or DEC operation specified in the instruction. $\overline{\text{OE}}$, normally LOW, may be forced HIGH to remove the Am2910 Y outputs from a three-state bus.

TABLE 4. Am2910 MICROINSTRUCTION SET.

HEX I ₃₋₁₀	MNEMONIC	NAME	REG/ CNTR CON- TENTS	FAIL $\overline{\text{CCEN}} = \text{LOW}$ and $\overline{\text{CC}} = \text{HIGH}$		PASS $\overline{\text{CCEN}} = \text{HIGH}$ or $\overline{\text{CC}} = \text{LOW}$		REG/ CNTR	ENABLE
				Y	STACK	Y	STACK		
0	JZ	JUMP ZERO	X	0	CLEAR	0	CLEAR	HOLD	PL
1	CJS	COND JSB PL	X	PC	HOLD	D	PUSH	HOLD	PL
2	JMAP	JUMP MAP	X	D	HOLD	D	HOLD	HOLD	MAP
3	CJP	COND JUMP PL	X	PC	HOLD	D	HOLD	HOLD	PL
4	PUSH	PUSH/COND LD CNTR	X	PC	PUSH	PC	PUSH	Note 1	PL
5	JSRP	COND JSB R/PL	X	R	PUSH	D	PUSH	HOLD	PL
6	CJV	COND JUMP VECTOR	X	PC	HOLD	D	HOLD	HOLD	VECT
7	JRP	COND JUMP R/PL	X	R	HOLD	D	HOLD	HOLD	PL
8	RFCT	REPEAT LOOP, CNTR \neq 0	\neq 0	F	HOLD	F	HOLD	DEC	PL
			= 0	PC	POP	PC	POP	HOLD	PL
			\neq 0	D	HOLD	D	HOLD	DEC	PL
9	RPCT	REPEAT PL, CNTR \neq 0	\neq 0	D	HOLD	PC	HOLD	HOLD	PL
			= 0	PC	HOLD	PC	HOLD	HOLD	PL
A	CRTN	COND RTN	X	PC	HOLD	F	POP	HOLD	PL
B	CJPP	COND JUMP PL & POP	X	PC	HOLD	D	POP	HOLD	PL
C	LDCT	LD CNTR & CONTINUE	X	PC	HOLD	PC	HOLD	LOAD	PL
D	LOOP	TEST END LOOP	X	F	HOLD	PC	POP	HOLD	PL
E	CONT	CONTINUE	X	PC	HOLD	PC	HOLD	HOLD	PL
F	TWB	THREE-WAY BRANCH	\neq 0	F	HOLD	PC	POP	DEC	PL
			= 0	D	POP	PC	POP	HOLD	PL

Note: If $\overline{\text{CCEN}} = \text{LOW}$ and $\overline{\text{CC}} = \text{HIGH}$, hold; else load. X = Don't Care.

The stack, a five-word last-in, first-out 12-bit memory, has a pointer which addresses the value presently on the top of the stack. Explicit control of the stack pointer occurs during instruction 0 (RESET), which makes the stack empty by resetting the SP to zero. After a RESET, and whenever else the stack is empty, the content of the top of stack is undefined until a PUSH occurs. Any POPs performed while the stack is empty put undefined data on the F outputs and leave the stack pointer at zero. Any time the stack is full (five more PUSHes than POPs have occurred since the stack was last empty), the FULL warning output occurs. No additional PUSH should be attempted onto a full stack; if tried, information at the top of the stack will be overwritten and lost.

THE Am2910 INSTRUCTION SET

The Am2910 provides 16 instructions which select the address of the next microinstruction to be executed. Four of the instructions are unconditional — their effect depends only on the instruction. Ten of the instructions have an effect which is partially controlled by an external, data-dependent condition. Three of the instructions have an effect which is partially controlled by the contents of the internal register/counter. The instruction set is shown in Table 4. In this discussion it is assumed that CI is tied HIGH.

In the ten conditional instructions, the result of the data-dependent test is applied to \overline{CC} . If the \overline{CC} input is LOW, the test is considered to have been passed, and the action specified in the name occurs; otherwise, the test has failed and an alternate (often simply the execution of the next sequential microinstruction) occurs. Testing of \overline{CC} may be disabled for a specific microinstruction by setting \overline{CCEN} HIGH, which unconditionally forces the action specified in the name; that is, it forces a pass. Other ways of using \overline{CCEN} include (1) tying it HIGH, which is useful if no microinstruction is data-dependent; (2) tying it LOW if data-dependent instructions are never forced unconditionally; or (3) tying it to the source of Am2910 instruction bit I_6 , which leaves instructions 4, 6 and 10 as data-dependent but makes others unconditional. All of these tricks save one bit of microcode width.

The effect of three instructions depends on the contents of the register/counter. Unless the counter holds a value of zero, it is decremented; if it does hold zero, it is held and a different microprogram next address is selected. These instructions are useful for executing a microinstruction loop a known number of times. Instruction 15 is affected both by the external condition code and the internal register/counter.

Perhaps the best technique for understanding the Am2910 is to simply take each instruction and review its operation. In order to provide some feel for the actual execution of these instructions, Figure 5 is included and depicts examples of all 16 instructions.

The examples given in Figure 5 should be interpreted in the following manner: The intent is to show microprogram flow as various microprogram memory words are executed. For example, the CONTINUE instruction, instruction number 14, as shown in Figure 5, simply means that the contents of microprogram memory word 50 is executed, then the contents of word 51 is executed. This is followed by the contents of microprogram memory word 52 and the contents of microprogram memory word 53. The microprogram addresses used in the examples were arbitrarily chosen and have no meaning other than to show instruction flow. The exception to this is the first example, JUMP ZERO, which forces the microprogram location counter to address ZERO. Each dot refers to the time that the contents of the microprogram memory word is in the pipeline register. While no special symbology is used for the conditional instructions, the text to follow will explain what the conditional choices are in each example.

It might be appropriate at this time to mention that AMD has a microprogram assembler called AMDASM, which has the capability of using the Am2910 instructions in symbolic representation. AMDASM's Am2910 instruction symbolics (or mnemonics) are given in Figure 5 for each instruction and are also shown in Table 4.

Instruction 0, JZ (JUMP and ZERO, or RESET) unconditionally specifies that the address of the next microinstruction is zero. Many designs use this feature for power-up sequences and provide the power-up firmware beginning at microprogram memory word location 0.

Instruction 1 is a CONDITIONAL JUMP-TO-SUBROUTINE via the address provided in the pipeline register. As shown in Figure 5, the machine might have executed words at address 50, 51 and 52. When the contents of address 52 is in the pipeline register, the next address control function is the CONDITIONAL JUMP-TO-SUBROUTINE. Here, if the test is passed, the next instruction executed will be the contents of microprogram memory location 90. If the test failed, the JUMP-TO-SUBROUTINE will not be executed; the contents of microprogram memory location 53 will be executed instead. Thus, the CONDITIONAL JUMP-TO-SUBROUTINE instruction at location 52 will cause the instruction either in location 90 or in location 53 to be executed next. If the TEST input is such that location 90 is selected, value 53 will be pushed onto the internal stack. This provides the return linkage for the machine when the subroutine beginning at location 90 is completed. In this example, the subroutine was completed at location 93 and a RETURN-FROM-SUBROUTINE would be found at location 93.

Instruction 2 is the JUMP MAP instruction. This is an unconditional instruction which causes the MAP output to be enabled so that the next microinstruction location is determined by the address supplied via the mapping PROMs. Normally the JUMP MAP instruction is used at the end of the instruction fetch sequence for the machine. In the example of Figure 5, microinstructions at locations 50, 51, 52 and 53 might have been the fetch sequence and at its completion at location 53, the jump map function would be contained in the pipeline register. This example shows the mapping PROM outputs to be 90; therefore, an unconditional jump to microprogram memory address 90 is performed.

Instruction 3, CONDITIONAL JUMP PIPELINE, derives its branch address from the pipeline register branch address value (BR_0 - BR_{11} in Figure 6). This instruction provides a technique for branching to various microprogram sequences depending upon the test condition inputs. Quite often, state machines are designed which simply execute tests on various inputs waiting for the condition to come true. When the true condition is reached, the machine then branches and executes a set of microinstructions to perform some function. This usually has the effect of resetting the input being tested until some point in the future. Figure 5 shows the conditional jump via the pipeline register address at location 52. When the contents of microprogram memory word 52 are in the pipeline register, the next address will be either location 53 or location 30 in this example. If the test is passed, the value currently in the pipeline register (3) will be selected. If the test fails, the next address selected will be contained in the microprogram counter which, in this example, is 53.

Instruction 4 is the PUSH/CONDITIONAL LOAD COUNTER instruction and is used primarily for setting up loops in microprogram firmware. In Figure 5, when instruction 52 is in the pipeline register, a PUSH will be made onto the stack and the counter will be loaded based on the condition. When a PUSH occurs, the value pushed is always the next sequential instruction address. In this case, the address is 53. If the test fails, the counter is not

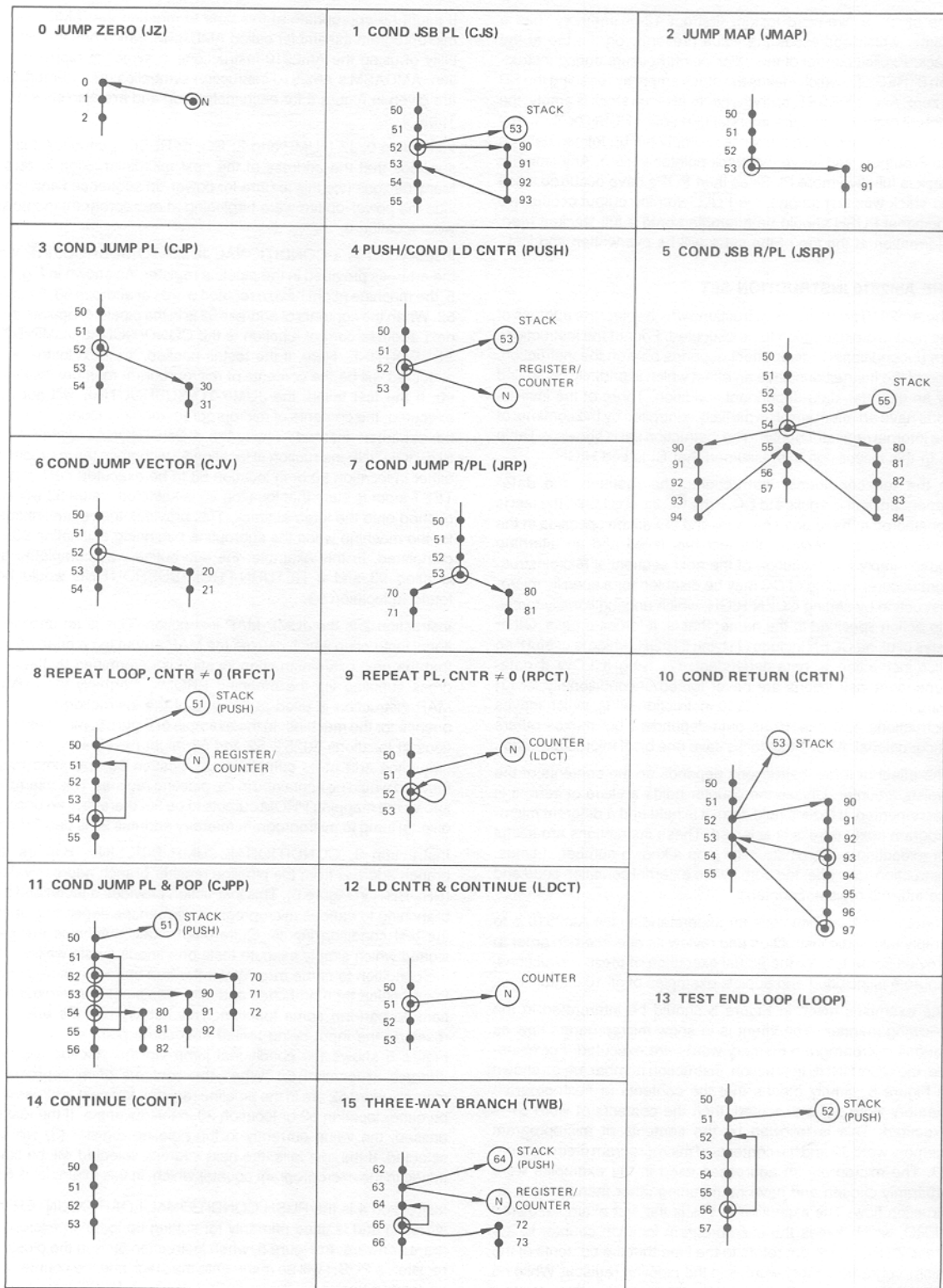


Figure 5. Am2910 Execution Examples.

loaded; if it is passed, the counter is loaded with the value contained in the pipeline register branch address field. Thus, a single microinstruction can be used to set up a loop to be executed a specific number of times. Instruction 8 will describe how to use the pushed value and the register/counter for looping.

Instruction 5 is a **CONDITIONAL JUMP-TO-SUBROUTINE** via the register/counter or the contents of the PIPELINE register. As shown in Figure 5, a PUSH is always performed and one of two subroutines executed. In this example, either the subroutine beginning at address 80 or the subroutine beginning at address 90 will be performed. A return-from-subroutine (instruction number 10) returns the microprogram flow to address 55. In order for this microinstruction control sequence to operate correctly, both the next address fields of instruction 53 and the next address fields of instruction 54 would have to contain the proper value. Let's assume that the branch address fields of instruction 53 contain the value 90 so that it will be in the Am2910 register/counter when the contents of address 54 are in the pipeline register. This requires that instruction at address 53 load the register/counter. Now, during the execution of instruction 5 (at address 54), if the test failed, the contents of the register (value = 90) will select the address of the next microinstruction. If the test input passes, the pipeline register contents (value = 80) will determine the address of the next microinstruction. Therefore, this instruction provides the ability to select one of two subroutines to be executed based on a test condition.

Instruction 6 is a **CONDITIONAL JUMP VECTOR** instruction which provides the capability to take the branch address from a third source heretofore not discussed. In order for this instruction to be useful, the Am2910 output, **VECT**, is used to control a three-state control input of a register, buffer, or PROM containing the next microprogram address. This instruction provides one technique for performing interrupt type branching at the microprogram level. Since this instruction is conditional, a pass causes the next address to be taken from the vector source, while failure causes the next address to be taken from the microprogram counter. In the example of Figure 5, if the **CONDITIONAL JUMP VECTOR** instruction is contained at location 52, execution will continue at vector address 20 if the TEST input is HIGH and the microinstruction at address 53 will be executed if the TEST input is LOW.

Instruction 7 is a **CONDITIONAL JUMP** via the contents of the Am2910 REGISTER/COUNTER or the contents of the PIPELINE register. This instruction is very similar to instruction 5; the conditional jump-to-subroutine via R or PL. The major difference between instruction 5 and instruction 7 is that no push onto the stack is performed with 7. Figure 5 depicts this instruction as a branch to one of two locations depending on the test condition. The example assumes the pipeline register contains the value 70 when the contents of address 52 is being executed. As the contents of address 53 is clocked into the pipeline register, the value 70 is loaded into the register/counter in the Am2910. The value 80 is available when the contents of address 53 is in the pipeline register. Thus, control is transferred to either address 70 or address 80 depending on the test condition.

Instruction 8 is the **REPEAT LOOP, COUNTER \neq ZERO** instruction. This microinstruction makes use of the decrementing capability of the register/counter. To be useful, some previous instruction, such as 4, must have loaded a count value into the register/counter. This instruction checks to see whether the register/counter contains a non-zero value. If so, the register/counter is decremented, and the address of the next microinstruction is taken from the top of the stack. If the register counter contains zero, the loop exit condition is occurring; control falls through to

the next sequential microinstruction by selecting μ PC; the stack is POP'd by decrementing the stack pointer, but the contents of the top of the stack are thrown away.

An example of the **REPEAT LOOP, COUNTER \neq ZERO** instruction is shown in Figure 5. In this example, location 50 most likely would contain a **PUSH/CONDITIONAL LOAD COUNTER** instruction which would have caused address 51 to be PUSHed on the stack and the counter to be loaded with the proper value for looping the desired number of times.

In this example, since the loop test is made at the end of the instructions to be repeated (microaddress 54), the proper value to be loaded by the instruction at address 50 is one less than the desired number of passes through the loop. This method allows a loop to be executed from 0 to 4095 times.

Single-microinstruction loops provide a highly efficient capability for executing a specific microinstruction a fixed number of times. Examples include fixed rotates, byte swap, fixed point multiply, and fixed point divide.

Instruction 9 is the **REPEAT PIPELINE REGISTER, COUNTER \neq ZERO** instruction. This instruction is similar to instruction 8 except that the branch address now comes from the pipeline register rather than the file. In some cases, this instruction may be thought of as a one-word file extension; that is, by using this instruction, a loop with the counter can still be performed when subroutines are nested five deep. This instruction's operation is very similar to that of instruction 8. The differences are that on this instruction, a failed test condition causes the source of the next microinstruction address to be the D inputs; and, when the test condition is passed, this instruction does not perform a POP because the stack is not being used.

In the example of Figure 5, the **REPEAT PIPELINE, COUNTER \neq ZERO** instruction is instruction 52 and is shown as a single microinstruction loop. The address in the pipeline register would be 52. Instruction 51 in this example could be the **LOAD COUNTER AND CONTINUE** instruction (number 12). While the example shows a single microinstruction loop, by simply changing the address in a pipeline register, multi-instruction loops can be performed in this manner for a fixed number of times as determined by the counter.

Instruction 10 is the conditional **RETURN-FROM-SUBROUTINE** instruction. As the name implies, this instruction is used to branch from the subroutine back to the next microinstruction address following the subroutine call. Since this instruction is conditional, the return is performed only if the test is passed. If the test is failed, the next sequential microinstruction is performed. The example in Figure 5 depicts the use of the conditional **RETURN-FROM-SUBROUTINE** instruction in both the conditional and the unconditional modes. This example first shows a jump-to-subroutine at instruction location 52 where control is transferred to location 90. At location 93, a conditional **RETURN-FROM-SUBROUTINE** instruction is performed. If the test is passed, the stack is accessed and the program will transfer to the next instruction at address 53. If the test is failed, the next microinstruction at address 94 will be executed. The program will continue to address 97 where the subroutine is complete. To perform an unconditional **RETURN-FROM-SUBROUTINE**, the conditional **RETURN-FROM-SUBROUTINE** instruction is executed unconditionally; the microinstruction at address 97 is programmed to force **CEN HIGH**, disabling the test and the forced PASS causes an unconditional return.

Instruction 11 is the **CONDITIONAL JUMP PIPELINE register address and POP stack** instruction. This instruction provides another technique for loop termination and stack maintenance.

The example in Figure 5 shows a loop being performed from address 55 back to address 51. The instructions at locations 52, 53 and 54 are all conditional JUMP and POP instructions. At address 52, if the TEST input is passed, a branch will be made to address 70 and the stack will be properly maintained via a POP. Should the test fail, the instruction at location 53 (the next sequential instruction) will be executed. Likewise, at address 53, either the instruction at 90 or 54 will be subsequently executed, respective to the test being passed or failed. The instruction at 54 follows the same rules, going to either 80 or 55. An instruction sequence as described here, using the CONDITIONAL JUMP PIPELINE and POP instruction, is very useful when several inputs are being tested and the microprogram is looping waiting for any of the inputs being tested to occur before proceeding to another sequence of instructions. This provides the powerful jump-table programming technique at the firmware level.

Instruction 12 is the LOAD COUNTER AND CONTINUE instruction, which simply enables the counter to be loaded with the value at its parallel inputs. These inputs are normally connected to the pipeline branch address field which (in the architecture being described here) serves to supply either a branch address or a counter value depending upon the microinstruction being executed. There are altogether three ways of loading the counter — the explicit load by this instruction 12; the conditional load included as part of instruction 4; and the use of the RLD input along with any instruction. The use of RLD with any instruction overrides any counting or decrementation specified in the instruction, calling for a load instead. Its use provides additional microinstruction power, at the expense of one bit of microinstruction width. This instruction 12 is exactly equivalent to the combination of instruction 14 and RLD LOW. Its purpose is to provide a simple capability to load the register/counter in those implementations which do not provide microprogrammed control for RLD.

Instruction 13 is the TEST END-OF-LOOP instruction, which provides the capability of conditionally exiting a loop at the bottom; that is, this is a conditional instruction that will cause the microprogram to loop, via the file, if the test is failed else to continue to the next sequential instruction. The example in Figure 5 shows the TEST END-OF-LOOP microinstruction at address 56. If the test fails, the microprogram will branch to address 52. Address 52 is on the stack because a PUSH instruction had been executed at address 51. If the test is passed at instruction 56, the loop is terminated and the next sequential microinstruction at address 57 is being executed, which also causes the stack to be POP'd; thus, accomplishing the required stack maintenance.

Instruction 14 is the CONTINUE instruction, which simply causes the microprogram counter to increment so that the next sequential microinstruction is executed. This is the simplest microinstruction of all and should be the default instruction which the firmware requests whenever there is nothing better to do.

Instruction 15, THREE-WAY BRANCH, is the most complex. It provides for testing of both a data-dependent condition and the counter during one microinstruction and provides for selecting among one of three microinstruction addresses as the next microinstruction to be performed. Like instruction 8, a previous instruction will have loaded a count into the register/counter while pushing a microbranch address onto the stack. Instruction 15 performs a decrement-and-branch-until-zero function similar to instruction 8. The next address is taken from the top of the stack until the count reaches zero; then the next address comes from the pipeline register. The above action continues as long as the test condition fails. If at any execution of instruction 15 the test condition is passed, no branch is taken; the microprogram counter register furnishes the next address. When the loop is

ended, either by the count becoming zero, or by passing the conditional test, the stack is POP'd by decrementing the stack pointer, since interest in the value contained at the top of the stack is then complete.

The application of instruction 15 can enhance performance of a variety of machine-level instructions. For instance, (1) a memory search instruction to be terminated either by finding a desired memory content or by reaching the search limit; (2) variable-field-length arithmetic terminated early upon finding that the content of the portion of the field still unprocessed is all zeroes; (3) key search in a disc controller processing variable length records; (4) normalization of a floating point number.

As one example, consider the case of a memory search instruction. As shown in Figure 5, the instruction at microprogram address 63 can be Instruction 4 (PUSH), which will push the value 64 onto the microprogram stack and load the number N, which is one less than the number of memory locations to be searched before giving up. Location 64 contains a microinstruction which fetches the next operand from the memory area to be searched and compares it with the search key. Location 65 contains a microinstruction which tests the result of the comparison and also is a THREE-WAY BRANCH for microprogram control. If no match is found, the test fails and the microprogram goes back to location 64 for the next operand address. When the count becomes zero, the microprogram branches to location 72, which does whatever is necessary if no match is found. If a match occurs on any execution of the THREE-WAY BRANCH at location 65, control falls through to location 66 which handles this case. Whether the instruction ends by finding a match or not, the stack will have been POP'd once, removing the value 64 from the top of the stack.

Am29811A Instruction Set Difference

The Am29811A instruction set is identical to the Am2910 except for instruction number 15. In the Am29811A, instruction number 15 is an unconditional JUMP PIPELINE REGISTER instruction. This provides the ability to unconditionally branch to any address contained in the branch address field of the microprogram. Thus, an unconditional N-way branch can be performed. Use of this instruction as opposed to a forced conditional jump pipeline instruction simply allows the condition code multiplexer select field to be shared (formatted) with other functions.

TYPICAL COMPUTER CONTROL UNIT ARCHITECTURE USING THE Am2910

The microprogram memory control unit block diagram of Figure 6 is easily implemented using the Am2910. This architecture provides a structured state machine design capable of executing many highly sophisticated next address control instructions.

The architecture of Figure 6 shows an instruction register capable of being loaded with a machine instruction word from the data bus. The op code portion of the instruction is decoded using a mapping PROM to arrive at a starting address for the microinstruction sequence required to execute the machine instruction. When the microprogram memory address is to be the first microinstruction of the machine instruction sequence, the Am2910 next address control selects the multiplexer D input and enables the three-state output from the mapping PROM. When the current microinstruction being executed is selecting the next microinstruction address as a JUMP function, the JUMP address will be available at the multiplexer D input. This is accomplished by having the Am2910 select the next address multiplexer D input and also enabling the three-state output of the pipeline register branch address field. The register enable input to the Am2910 can be grounded so that this register will load the value at the

Am2910 D input. The value at D is clocked into the Am2910's register (R) at the end of the current microcycle, which makes the D value of this microcycle available as the R value of the next microcycle. Thus, by using the branch address field of two sequential microinstructions, a conditional JUMP-TO-ONE-OF-TWO-SUBROUTINES or a conditional JUMP-TO-ONE-OF-TWO-BRANCH-ADDRESSES can be executed by either selecting the D input or the R input of the next address multiplexer.

When sequencing through continuous microinstructions in microprogram memory, the program counter in the Am2910 is used. Here, the control logic simply selects the PC input of the next address multiplexer. In addition, most of these instructions enable the three-state outputs of the pipeline register associated with the branch address field, which allows the register within the Am2910 to be loaded. The 5 x 12 stack in the Am2910 is used for

looping and subroutines in microprogram operations. Up to five levels of subroutines or loops can be nested. Also, loops and subroutines can be intermixed as long as the five word depth of the stack is not exceeded.

CCU TIMING

The minimum clock cycle that can be used in a CCU design is usually determined by the component delays along the longest "pipeline-register-clock to logic to pipeline-register-clock" path. At the beginning of any given clock cycle, data available at the output of the microprogram memory, counter status, and any other data and/or status fields, are latched into their associated pipeline registers. At this point, all delay paths begin. Visual inspection will not always point out the longest signal delay path.

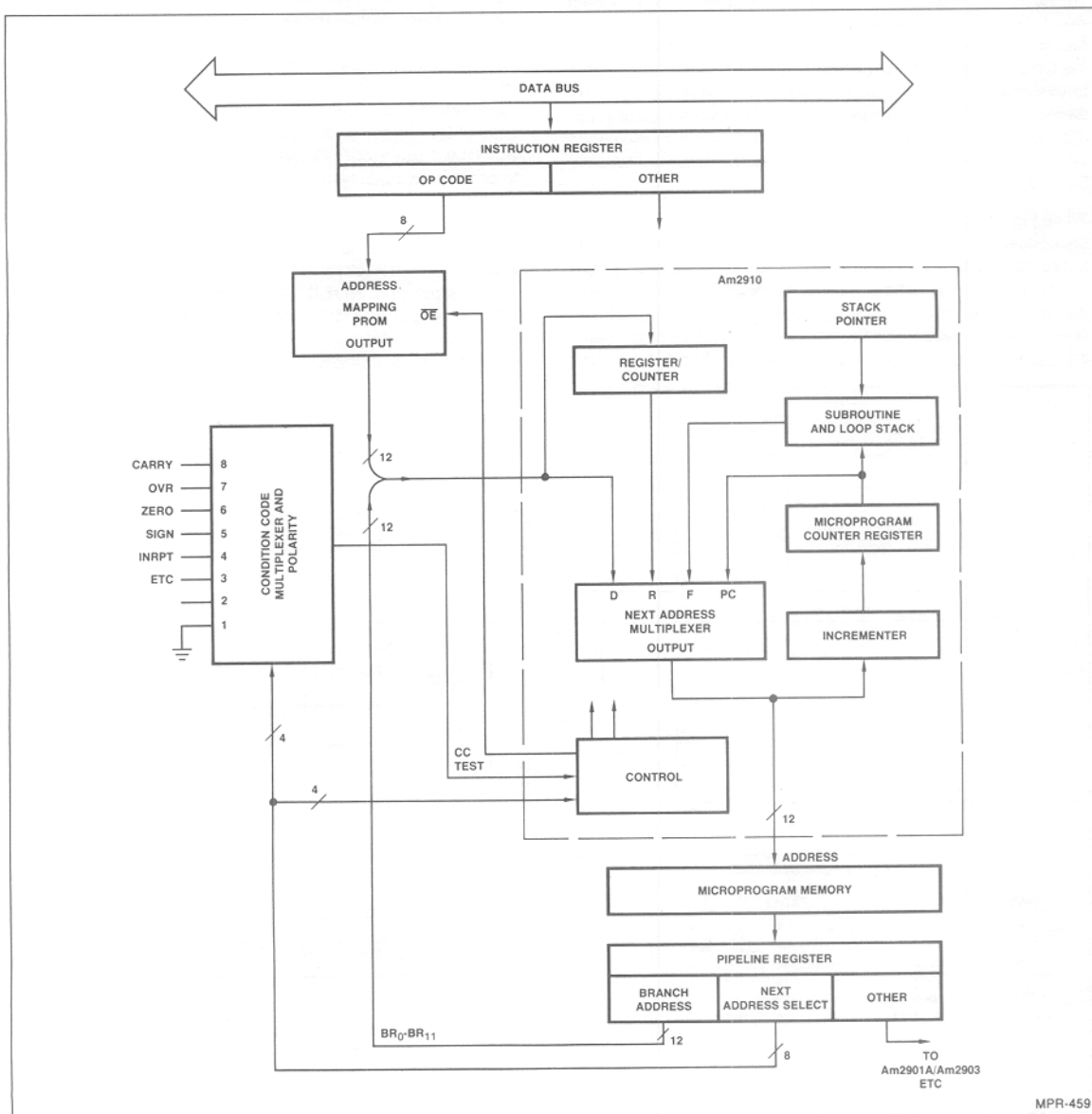


Figure 6. A Typical Computer Control Unit Using the Am2910.

The obviously long paths are a good place to start, but each definable path should be calculated on a component by component basis until the truly longest logic signal path is found.

Referring to Figure 6, a number of potentially long paths can be identified. These include the instruction register to pipeline register time, the pipeline register to pipeline register time via the condition code multiplexer and the status to pipeline register time. In order to demonstrate the technique for calculating the AC performance of the Am2910 state machine design, the timing diagrams of Figure 7 are presented. Here, a number of propagation delay paths are evaluated such that the reader can learn the technique for performing these computations.

All of the propagation delays have been calculated using typical propagation delays because at the time of this writing, the characterization of the Am2910 has not been completed. When the final data sheet is published, the user need only select the appropriate worst case specifications and he can compute the desired maximum propagation delays for his design. Also, by looking at the typical propagation delay numbers, the designer will be able to evaluate the design margin in the system after he has completed all of the worst case calculations. These typical propagation delays represent the expected values if a system were set up on the bench and actual measurements would be taken at 5V and 25°C operating temperature.

While Figure 6 and Figure 7 deal with the Am2910 microprogram sequencer, it is also instructive to evaluate the AC performance of a typical computer control unit using the Am2911 and Am29811A. Figure 3 shows such a connection and will be used as the basis for performing the propagation delay path calculations. The calculations for the various propagation delay paths are demonstrated in Figure 8 and are intended to show the

technique for computing these delays. As before, the typical propagation delays have been used in the computation for comparison purposes. The user can derive the maximum numbers at 25°C and 5V, commercial temperature range and power supply variations or military temperature range and power supply variations as required for his design.

When Figure 7 and Figure 8 are reviewed in detail, the reader will recognize that the longest propagation delay paths in the case of the Am2910 as well as the Am2911 and Am29811A involve the three-state enables on the map PROM or the pipeline register for the branch address. If absolute maximum speed is desired, these paths can be eliminated by using one of several techniques. One technique is to simply allocate one or more bits in the pipeline register to control the three-state enables of the various devices connected to the D input of the Am2910. For the example of Figure 6, one bit would be sufficient and the pipeline register could be implemented using an Am74S175 register. This would allow the true and complement outputs to be used to drive the pipeline register branch address output enable and the mapping PROM output enable. Thus, these longest paths would be eliminated and an improvement of about 30ns would be achieved. A second technique for eliminating these propagation delay paths would be to use a four input NAND gate and a four input NOR gate to encode the equivalent function of the $\overline{\text{MAP}}$ enable and the $\overline{\text{PL}}$ enable. This technique is demonstrated in Figure 9. Again, an Am74S175 register would be used as the pipeline register to provide the instruction inputs to the Am2910 sequencer. This would allow instruction 2 to be decoded to provide the MAP enable signal and "NOT INSTRUCTION 2" to be decoded as the pipeline enable signal. This technique can be applied as well to the computer control unit of Figure 3 to accomplish the same longest path elimination.


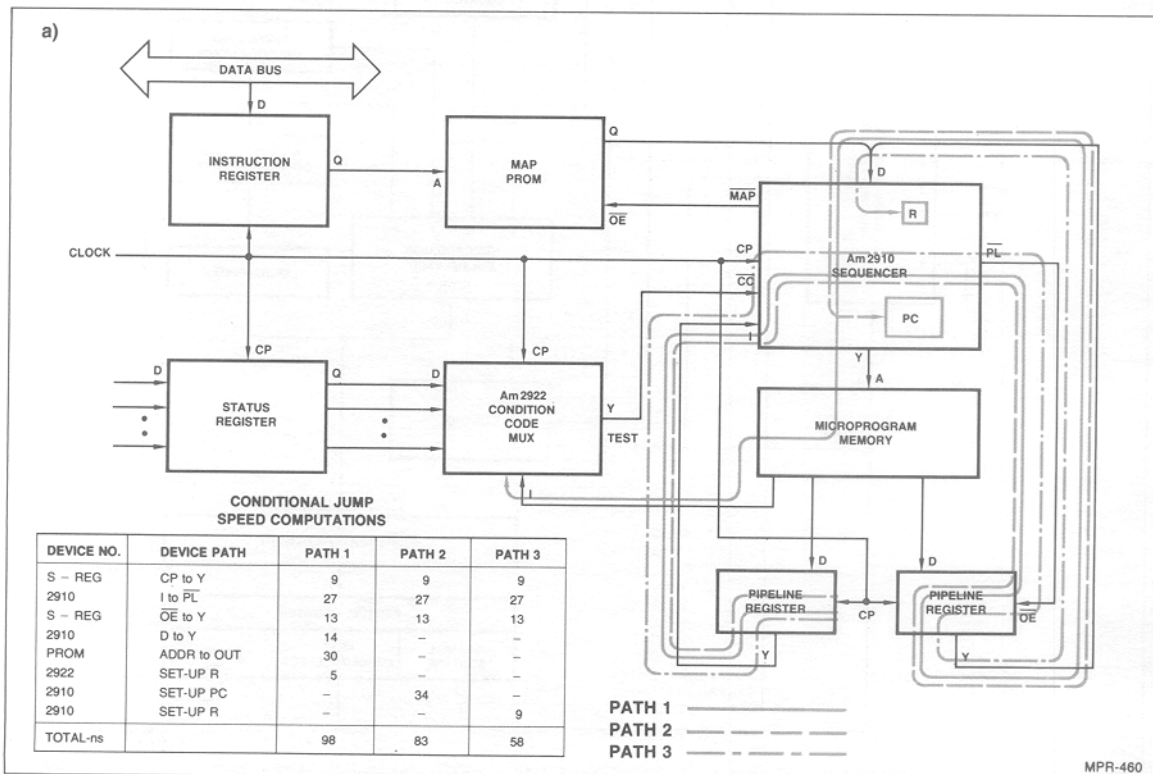



Figure 7. Propagation Delay Calculations on the Am2910 Microprogram Sequencer.

b)

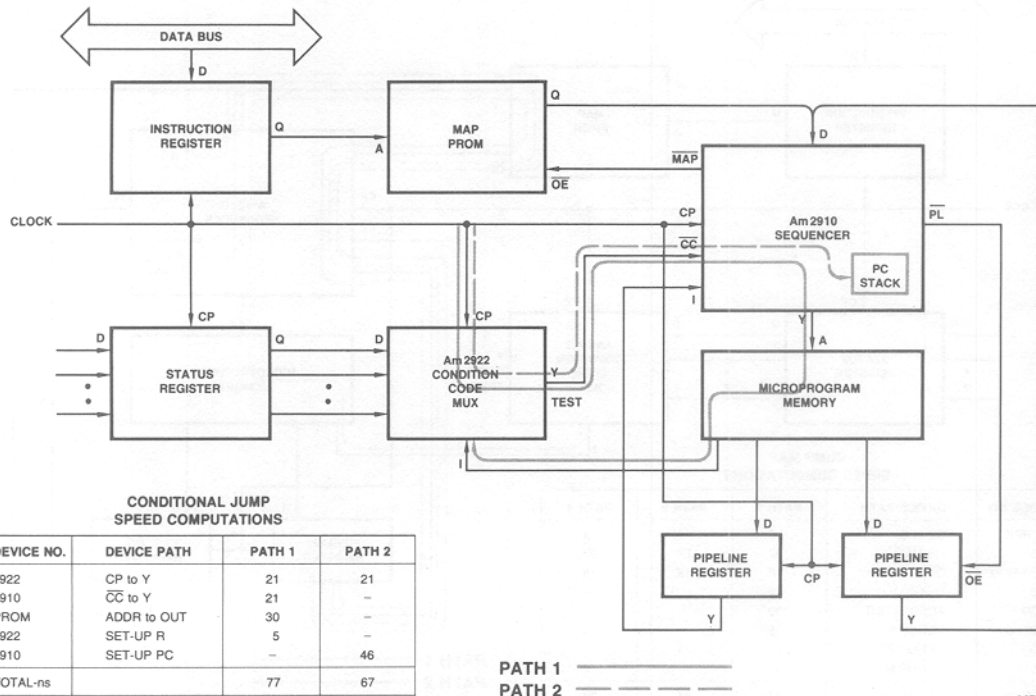

MPR-461


c)

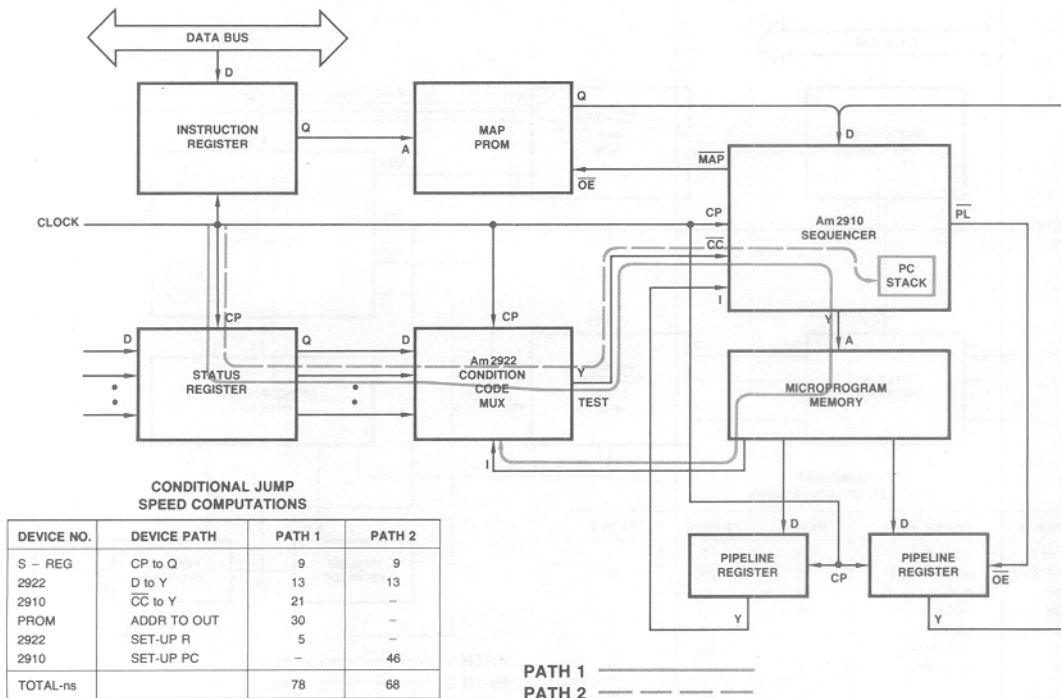

MPR-462

Figure 7. Propagation Delay Calculations on the Am2910 Microprogram Sequencer (Cont.).

d)

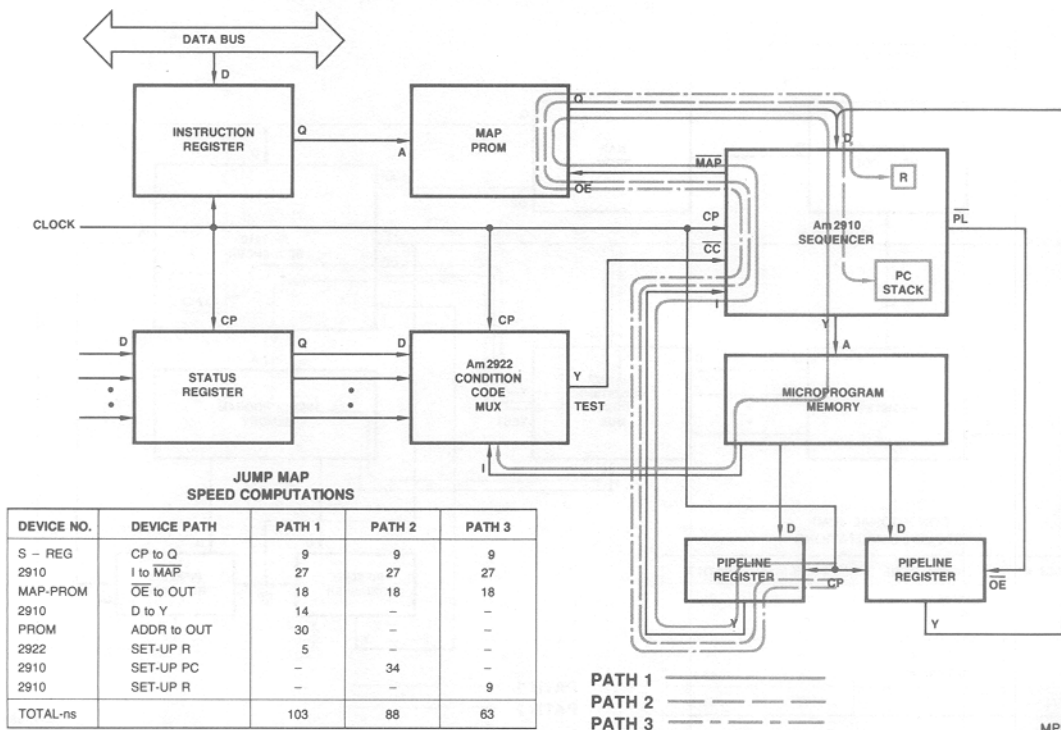

e)


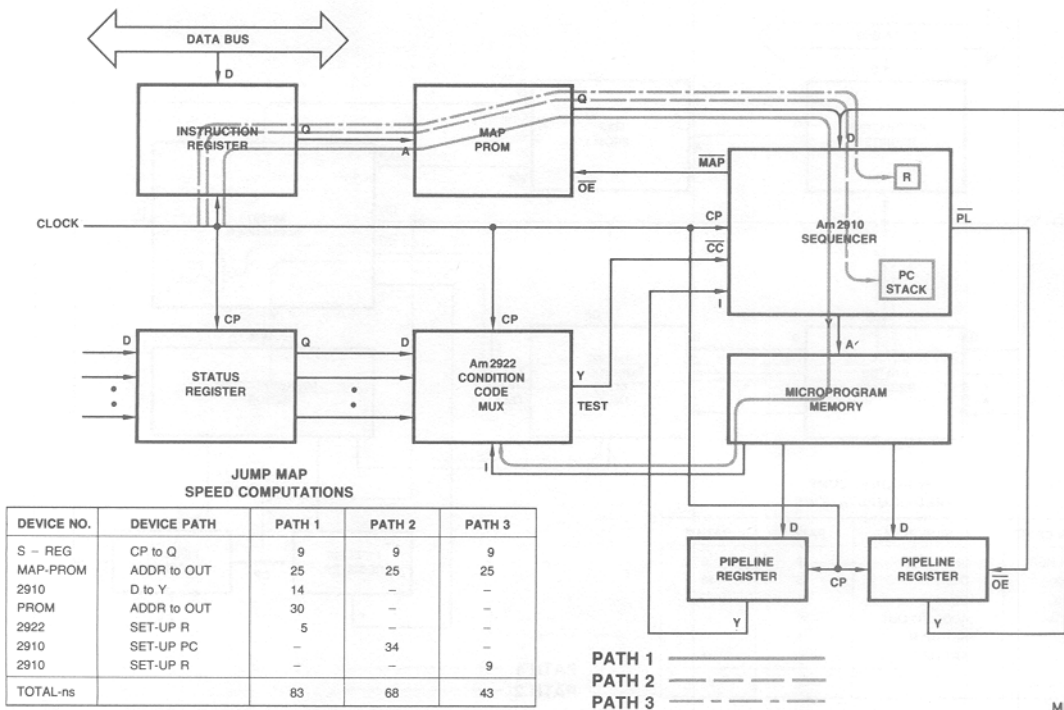



Figure 7. Propagation Delay Calculations on the Am2910 Microprogram Sequencer (Cont.).

f)

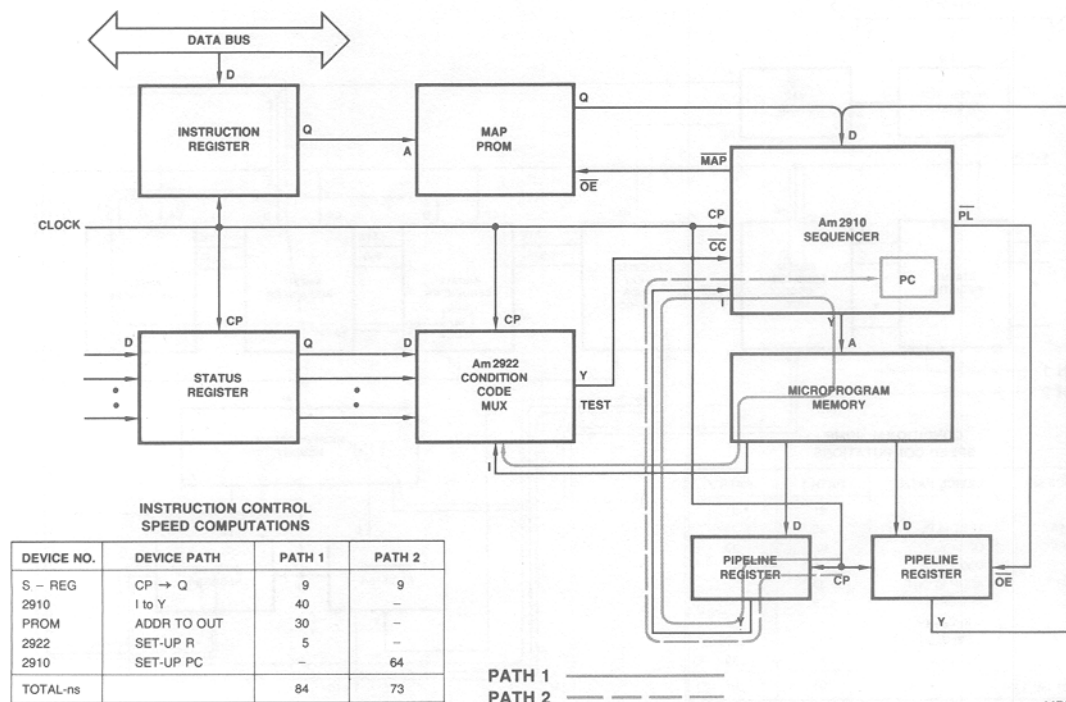

MPR-465


g)

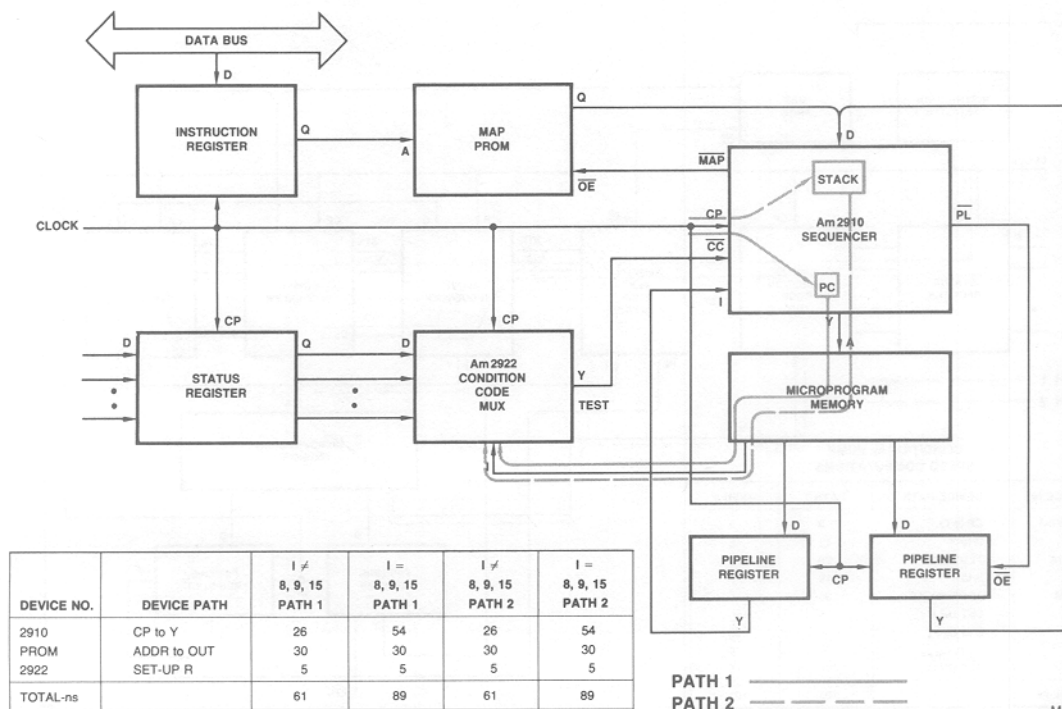

MPR-466


Figure 7. Propagation Delay Calculations on the Am2910 Microprogram Sequencer (Cont.).

a)

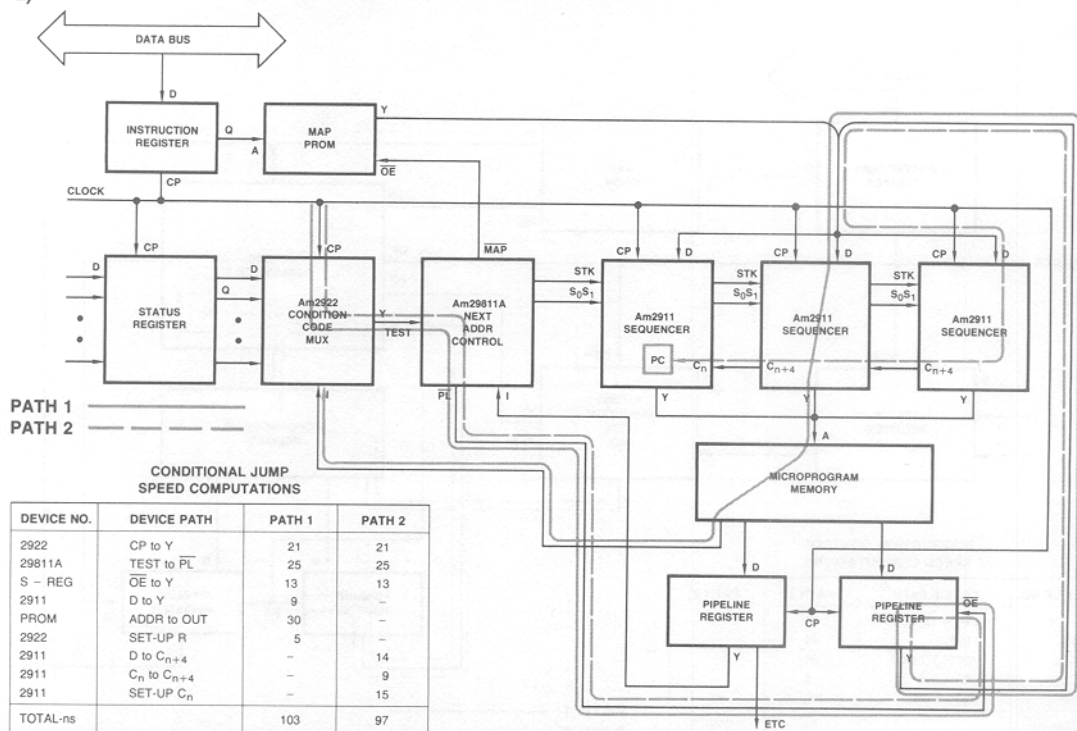

MPR-467


b)

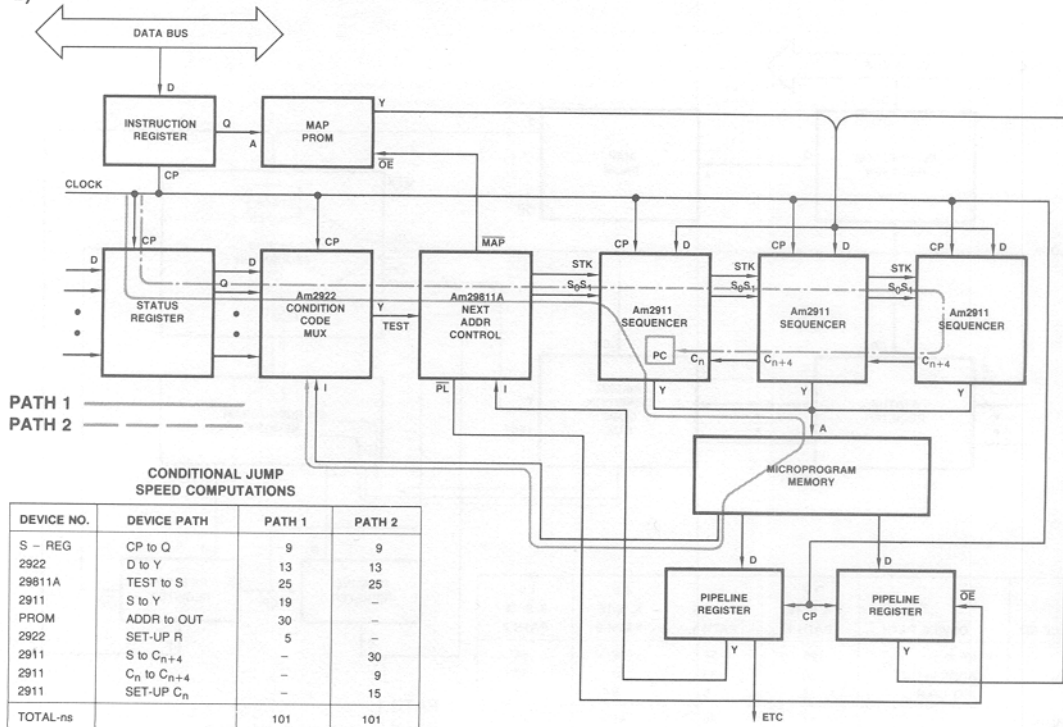

MPR-468


Figure 8. Propagation Delay Calculations for the Am2911 and Am29811A Design.

c)

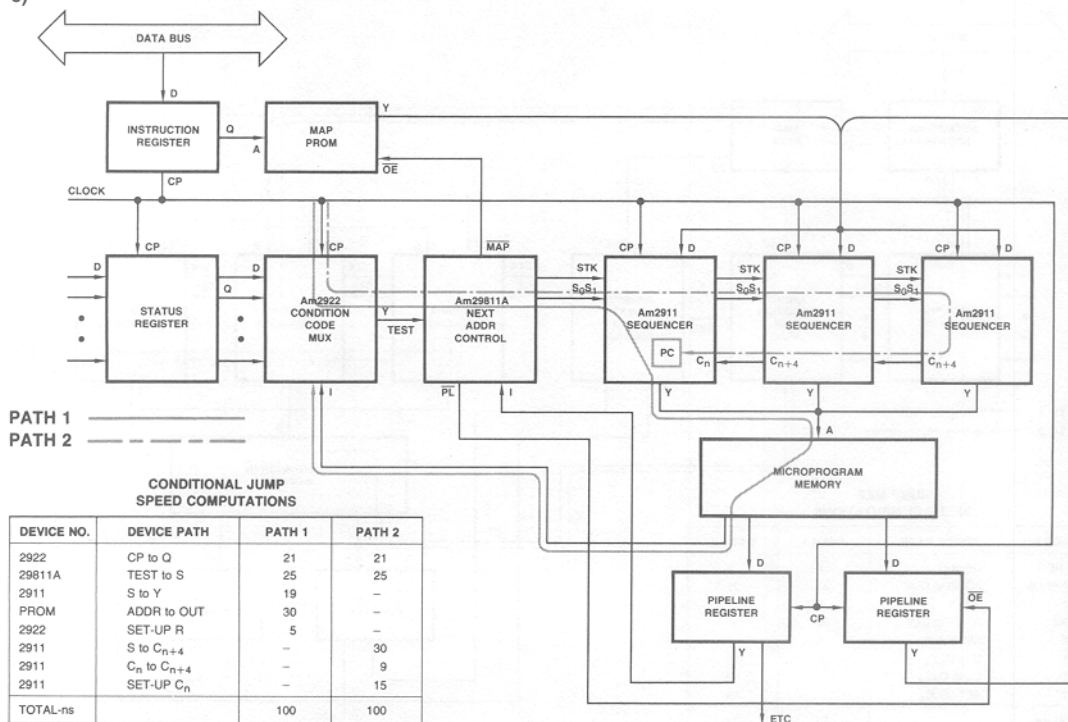

MPR-469


d)

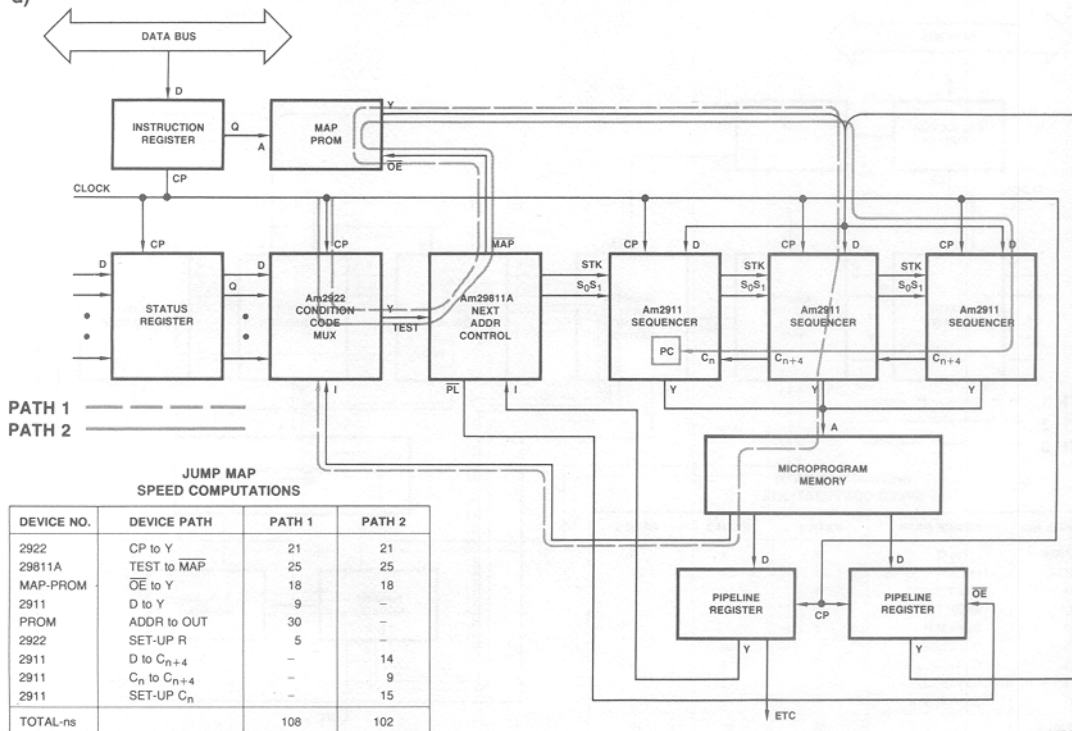

MPR-470


Figure 8. Propagation Delay Calculations for the Am2911 and Am29811A Design (Cont.).

e)

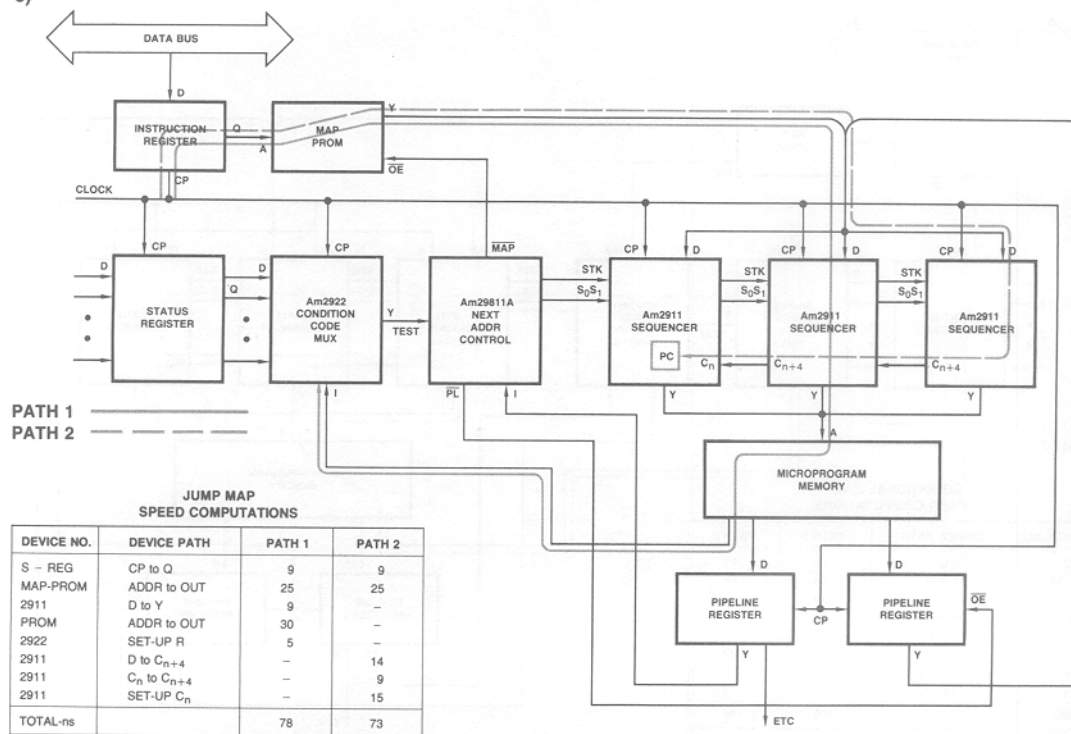

MPR-471


f)

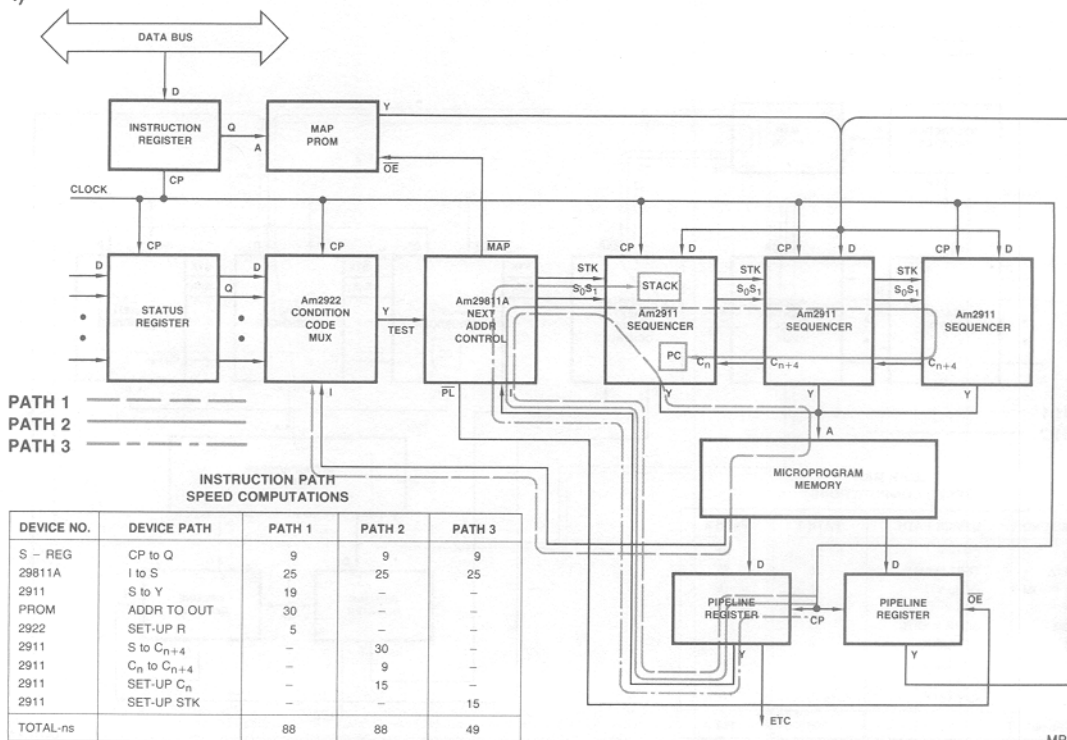

MPR-472


Figure 8. Propagation Delay Calculations for the Am2911 and Am29811A Design (Cont.).

g)

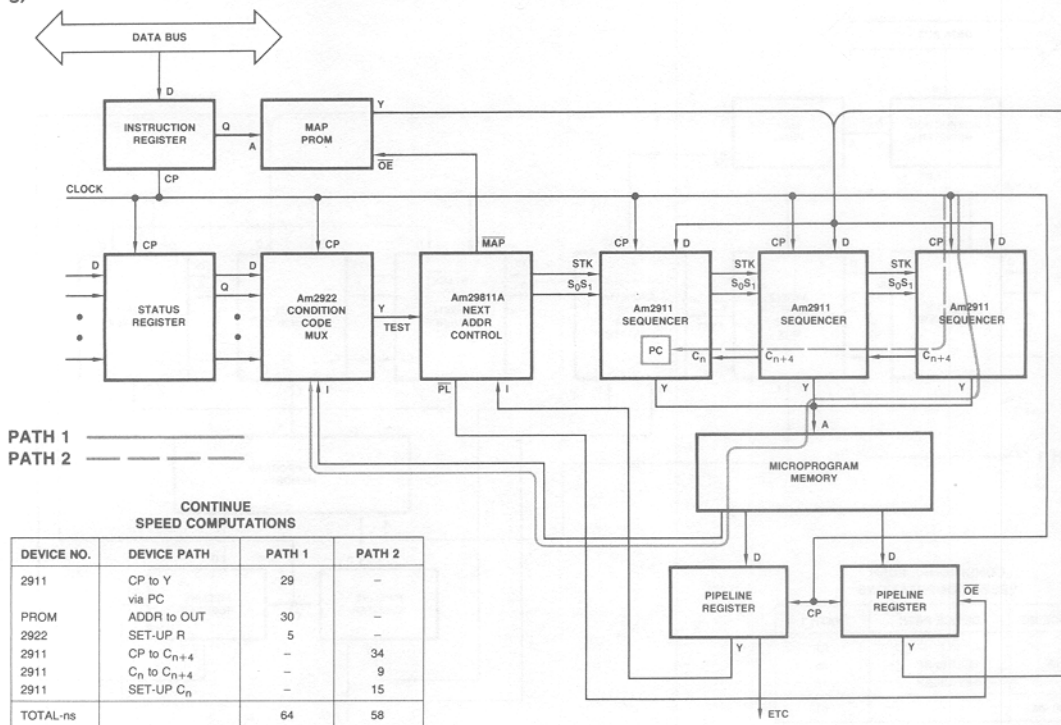

MPR-473

h)

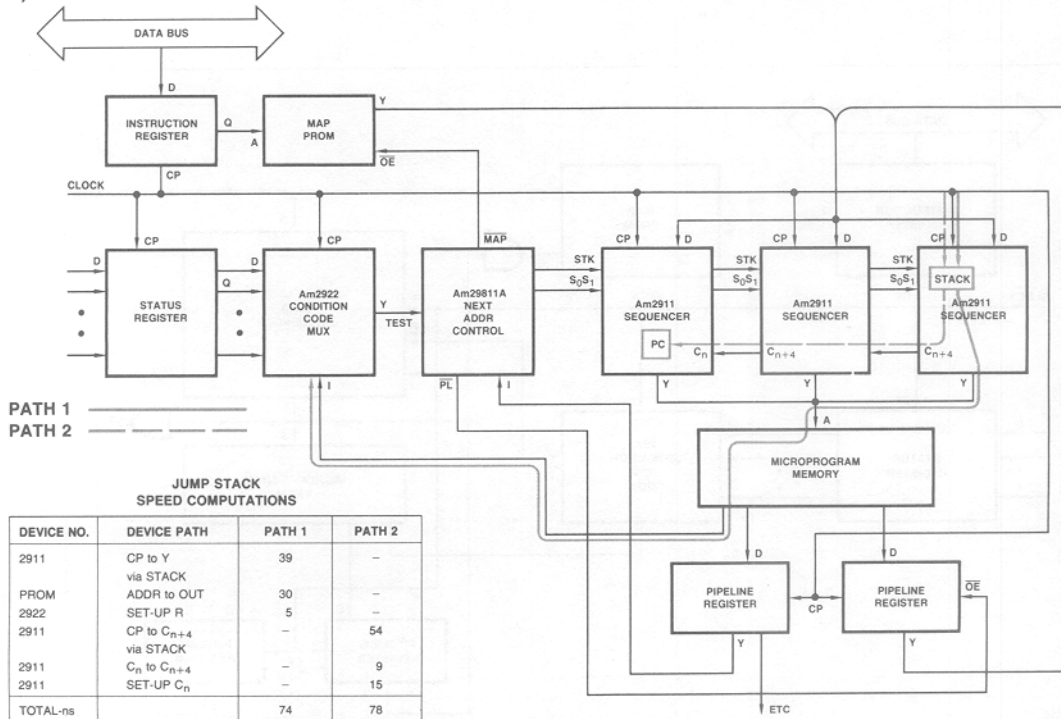

MPR-474

Figure 8. Propagation Delay Calculations for the Am2911 and Am29811A Design (Cont.).

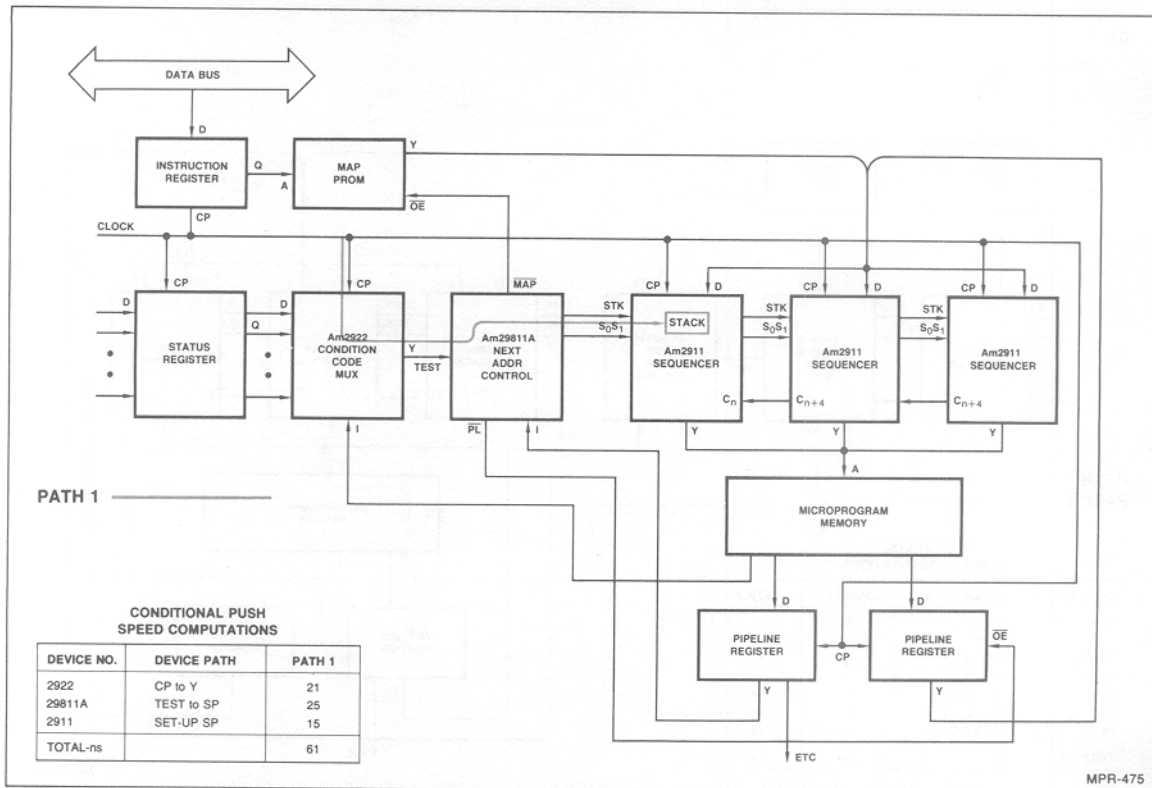


Figure 8. Propagation Delay Calculations for the Am2911 and Am29811A Design (Cont.).

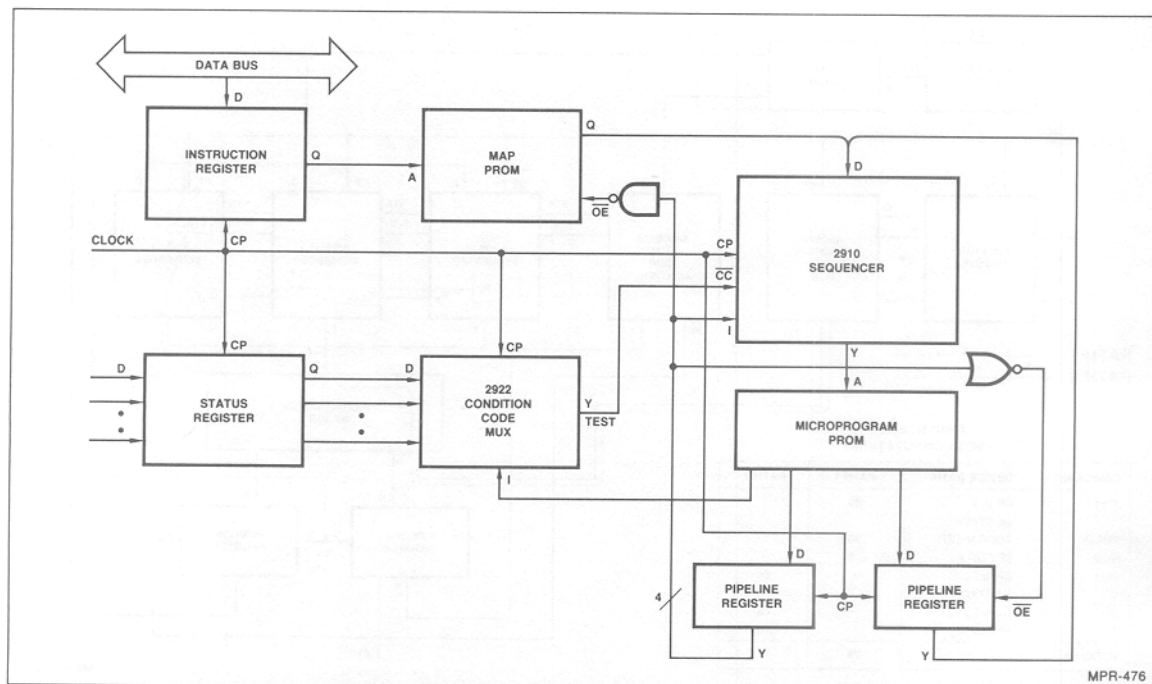


Figure 9. Using NAND and NOR Gates to Improve Am2910 Speed.

In order to compare the performance of the Am2910 with the Am2911 and Am29811A, Table 5 is presented. Here the propagation delays for the Am2911 and Am29811A are for a 12-bit wide microprogram sequencer configuration. If a wider configuration is used, only one additional carry input to carry output delay must be added to the appropriate paths of these calculations. A 12-bit wide Am2911/29811A configuration has been evaluated so that an "apples to apples" comparison can be made.

As is shown in Table 5, a number of combinations are possible for the longest AC propagation delay paths for these microprogram sequencers. First, the continue instruction can be executed the fastest of any of the microprogram instructions if the continues are sequential. That is, from the second continue on, the typical microcycle can be either 61 or 64ns respectively. To achieve this speed, it is required that various signals throughout the architecture be stable such that the only paths that enter into the propagation delay calculation are the clock-to-output of the microprogram counter, the microprogram memory and the pipeline register setup.

The second group of instructions shown in Table 5 show some examples of instruction execution and jumping. These examples assume that the MAP and OE outputs are not used as described earlier. These calculations apply to several of the instructions but not to all the instructions. For the Am2910 sequencer all of the propagation delays are around 80 to 85ns; while for the Am2911/Am29811A combination, the propagation delays range from about 80ns to 100ns, depending on the instruction. It should be noted that certain other instructions such as push and conditional load counter should be evaluated to determine the speed at which they can be executed.

The last two instructions shown in Table 5 are for jumps where the output enable of the field supplying the address to the D inputs of the microprogram sequencers are controlled by either the Am2910 or Am29811A. Notice that for Am2910 configuration, the jump map represents the longest propagation delay path and is 103ns typical. Also, for the Am2911/Am29811A combination, the jump map instruction also represents the longest propagation delay path and is 109ns typical.

It is not the purpose of this exercise to show every possible propagation delay path; but rather, to show the reader the technique for computing propagation delays such that any design can be evaluated and the worst case path derived. Even here, not all of the worst case numbers shown in Table 5 have been derived in Figures 7 and 8. This was done intentionally and is left as an exercise for the student.

If the Am2909 or Am2911 and the Am29811A are combined into microprogram sequencers of either 8 bits in width or 16 bits in width, the calculations need only be modified slightly to determine

the microcycle times. Obviously, if two Am2911s are used, the worst case propagation delay paths do not change. However, if four Am2911s are used, the carry path will become the longer propagation delay path on several of the computations. This may be offset however since larger microprogram PROMs may be used if 64K of microcode is actually being addressed or high power buffers may be placed between the Am2911 outputs and the microprogram memory to provide sufficient drive for such a large microprogram store.

In addition, the Am2909 and Am2911 may be used without the Am29811A where the user wishes to generate a special purpose instruction set or very high speed control of the internal multiplexer and push pop stack. In some designs as much as 25 to 30ns, typical, can be removed from the longest propagation delay paths of the design by using high speed Schottky SSI. While this has not been the typical case, some designers have used it to provide a performance improvement not achievable with a standard Schottky condition code multiplexer and the Am29811A next address control unit.

APPLICATIONS

It should be understood that the microprogram state machine built using either the Am2910 or the Am2911/29811A represents a general purpose state machine controller. Applications for this type of microprogrammed control include uses in minicomputers, communications, instrumentation, controllers and peripherals as well as special purpose processors. Typically, the microprogrammed approach provides a more structured organization to the design and allows the design engineer the greatest flexibility in implementation.

It is important to understand that microprogrammed machines need not be part of a typical minicomputer type structure. That is, a general purpose minicomputer usually has a machine instruction set that is totally different from its microprogram instruction control. As such, it is essential that the designer new to computer design and microprogram design understand the difference between a machine instruction and a microprogram instruction. This differentiation is shown in Figure 10 where a typical 16-bit machine level instruction is demonstrated as compared with a typical microprogram instruction. The machine level instruction usually consists of 16 bits and in this example, these bits are used to provide the op code, source register definition and destination register definition. The microprogram instruction on the other hand usually consists of anywhere from 32 to 128 bits in a typical minicomputer type design. Here, the bits are used to control the elemental functions of a machine such as the Am2910 instruction control and condition code multiplexer, the Am2903 source, ALU function and destination control and so forth. For purposes of this explanation, let us assume that the machine level instruction is available to the machine programmer while the microprogram

TABLE 5. SUMMARY OF LONGEST AC PATHS FOR MICROPROGRAM SEQUENCERS.

Instruction	Am2910	Am2911 Am29811A	Comments
Continue	61	64	The fastest instruction. Assumes sequential continues!
Instruction Execute	84	88	If the MAP and PL outputs are not used.
Jump Map (no OE)	83	78	
Jump PL (No OE)	78	101	
Jump Map (via OE)	103	109	If the MAP and PL outputs are used.
Jump PL (via OE)	98	104	

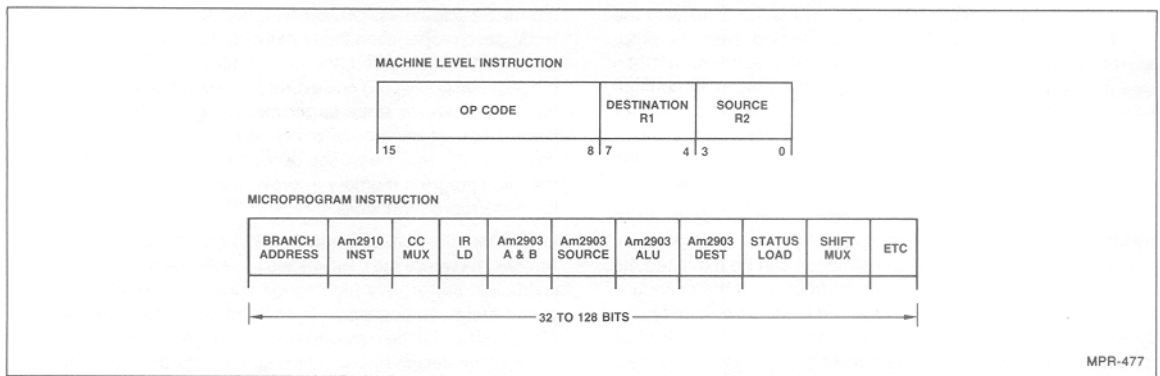


Figure 10. Understanding Machine and Microprogram Instructions.

instruction is not available to the machine programmer at the assembly language level. Let it suffice to say that this assumption is not necessarily valid in machines being designed today.

Perhaps one of the most typical applications of the microprogrammed computer control unit state machine design is as the controller for a minicomputer. Here, the function of the microprogrammed controller is to fetch and execute machine level instructions. The flow required to perform this function is depicted in Figure 11 which should be representative for all general purpose type machines. Figure 11 shows that after initialization, the computer control unit simply fetches machine instructions, decodes these instructions and then fetches the required operands such that the original instruction can be executed. This cycle of fetching and executing instructions is performed without end. Such things as hardware halts or resets are ignored and should be assumed to only cause re-initialization.

Once the flow of a typical computer control unit is understood, it is possible to evaluate a number of architectures using the Am2910 or Am2911/Am29811A such that the flow diagram of Figure 11 can be implemented.

STATE MACHINE ARCHITECTURES

After a machine instruction is fetched from memory, it is normally placed in the machine instruction register as described in Figure 6. Then the op code portion of the instruction is decoded so that a sequence of microinstructions in the microprogram memory can be selected for execution. Each microinstruction is fetched and its contents placed in the pipeline register as shown in Figure 6 for execution.

While the architecture of Figure 6 is recommended and has been used throughout the preceding portion of this chapter, it should be understood that a number of architectures are possible using these microprogram sequencers. The normal flow in fetching microinstructions is to determine the address of the next microinstruction, fetch the contents at that address and set up this data at the input of the pipeline register such that it can be clocked into the pipeline register for execution. If we assume that a clock is being used to clock the pipeline register, the Am2910, the machine instruction register and the Am2903 microprocessor bit slices, it is possible to define a number of computer control unit designs where the relationship between the clock edges is different.

There seem to be a minimum of seven different architectures that can be defined based on placing registers in the appropriate signal paths and storing data on the low-to-high transition of the

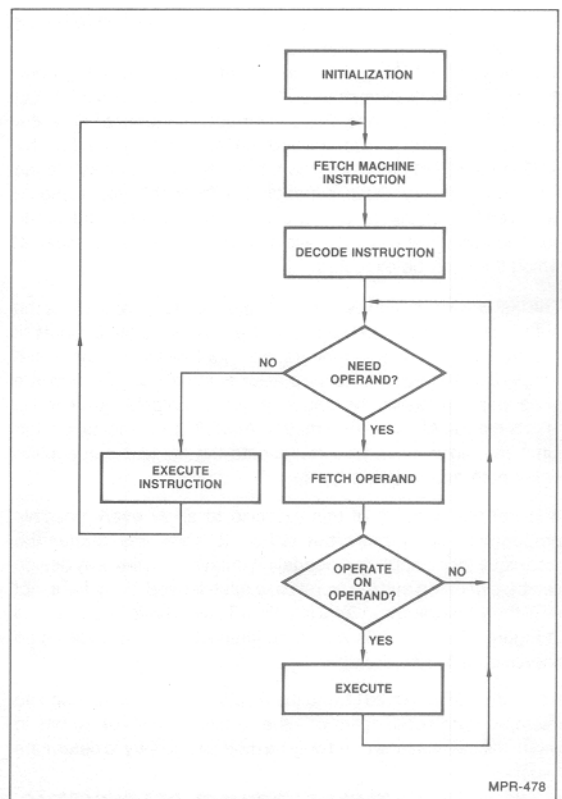


Figure 11. Computer Control Flow Diagram.

clock. For purposes of this discussion, we will assume that all clocked devices will operate using the same clock such that changes will occur on the LOW-to-HIGH transition of the clock. While it is possible to use multiphase clocks and tie different clock phases to different devices, that type of system operation will not be described here. In all cases, we will be talking about the flow of signals between LOW-to-HIGH transitions of the clock. Typically, a cycle is started by a clock edge at a device and the signals begin to flow from one device to the next until a set-up time to a clock edge results. Then, the next microinstruction is executed in

exactly the same manner. There are three different identifiable types of microinstruction sequences where only one register is in the signal flow loop. The first of these we shall call an Address-Based microinstruction cycle. It usually starts with the address of a microprogram memory word being stored in a register by the clock. This address has been determined by the previous microinstruction. This address then accesses the microprogram memory to fetch its contents which are presented at its outputs to control the Arithmetic Logic Unit and the results of the Arithmetic Logic Unit function may be used to determine the next address selected that will be stored in this microprogram address register. This is shown as Figure 12a. The second type of microprogram architecture is called Instruction-Based. Here, the register is placed at the output of the microprogram memory as shown in Figure 12b. Again, the cycle consists of executing the microinstruction in the ALU; perhaps using the results of the operation to determine the address of the next microinstruction and then fetching the contents of that microinstruction and setting this new data up at the input to the register. The third basic architecture for microprogram control is called Data-Based. Here, a register is used to hold the status data from the ALU and this is the determining clock point for the cycle. Here, the status register initiates the selection of the next address from which the microprogrammed data is fetched and this microprogram instruction is used to execute a new function in the ALU thereby setting up the results for the status register. This scheme is shown in Figure 12c. Note that this scheme requires an additional register at the output of the microprogram memory to hold a portion of the microprogram instruction for controlling the condition code multiplexer and Am2910 instruction set. These primitive architectures for microprogrammed control demonstrate the three points at which a register can be placed to provide a start and an end for the microcycle. In a general sense, each of these three architec-

tures is one level pipelined. This, however, is not the definition normally associated with pipelining of microprogram control.

If combinations of the above described architectures are implemented, an improvement in performance will be realized. In each of the three architectures thus described (address-based, instruction-based, and data-based), all of the signal paths are in series and must be transcended before a microcycle can be completed. They are quite easy to program, however, since all of the tasks are completed in the loop before proceeding to the next microinstruction. As stated earlier, these tend to be the slowest of the possible architectures for microprogram control. This disadvantage can be overcome by using a technique referred to as pipelining in microprogram control. In a pipeline architecture, we overlap the fetch of the next microinstruction while we are executing the current microinstruction. This is achieved by inserting additional registers in the overall path such that we can hold the signals step-by-step. There are three possible combinations of the above mentioned architectures that can be utilized in microprogram control. These are address-instruction-based, address-data-based, and instruction-data-based. While each of these represent two stages of pipelining, we normally refer to these as the pipelined architectures. These are shown in Figure 12d, 12e and 12f. It is the instruction-data based architecture that is recommended for the Am2910 and provides the overall best trade-off in cost versus performance.

The last possible architecture using registers in the signal path is a combination of all three architectures and is called address-instruction-data-based microprogram control and is shown in Figure 12g. Here, three stages of pipeline are involved and we normally refer to this as two-level pipelined architecture. Needless to say, if no pipelining were involved at all, we would have a ring oscillator.


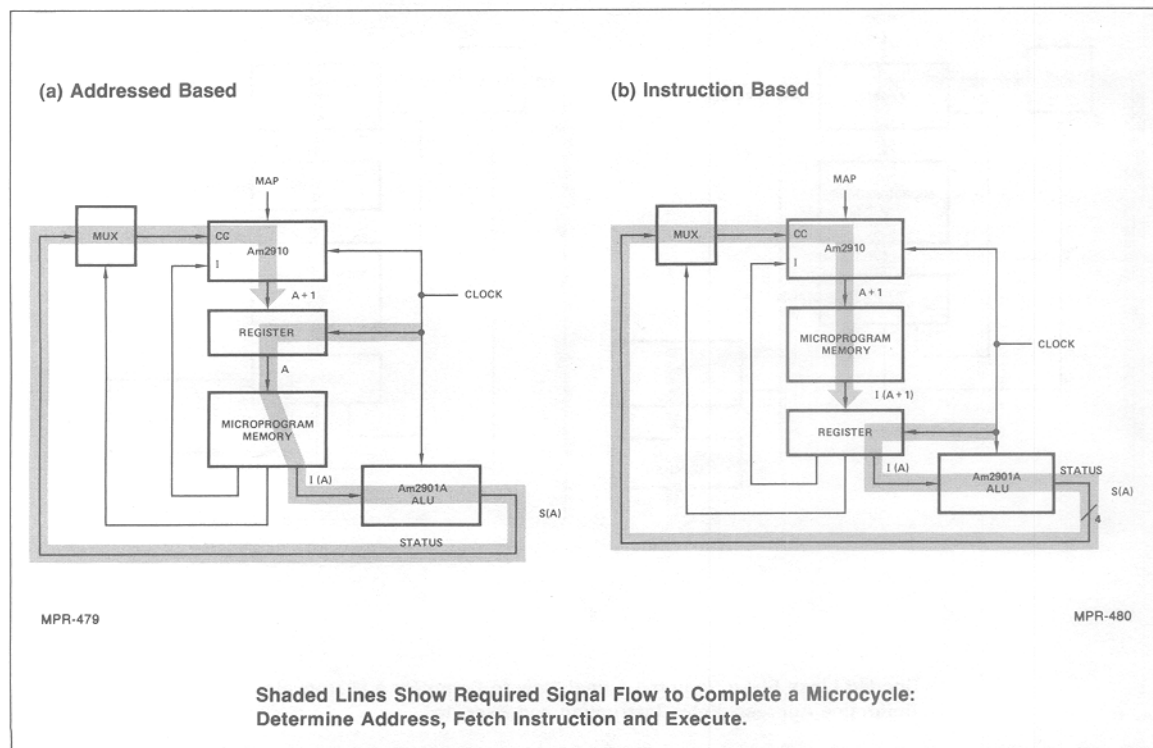



Figure 12. Standard Microprogram Control Architectures.

(c) Data Based

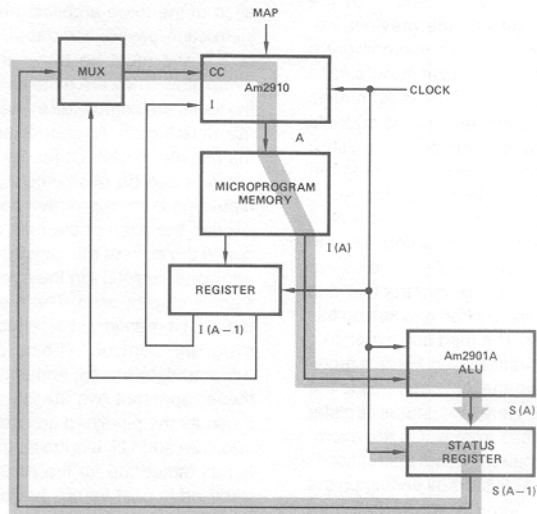


MPR-481

(d) Instruction-Data Based

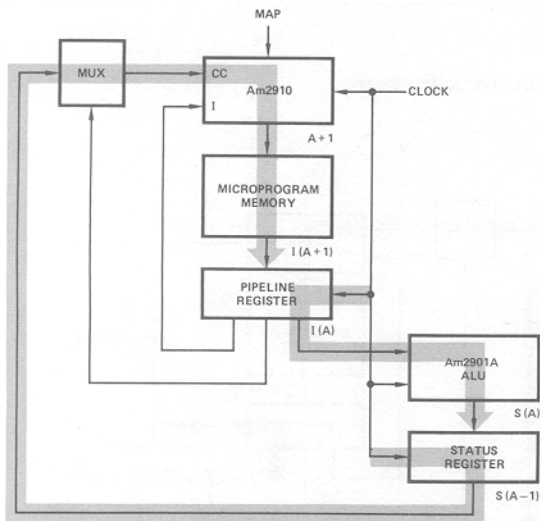

MPR-482

(e) Instruction-Address Based

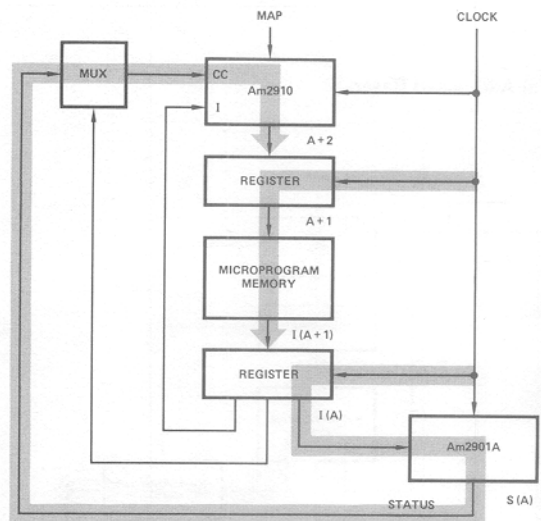

MPR-483

Shaded Lines Show Required Signal Flow to Complete a Microcycle:
Determine Address, Fetch Instruction and Execute.

Figure 12. Standard Microprogram Control Architectures (Cont.).

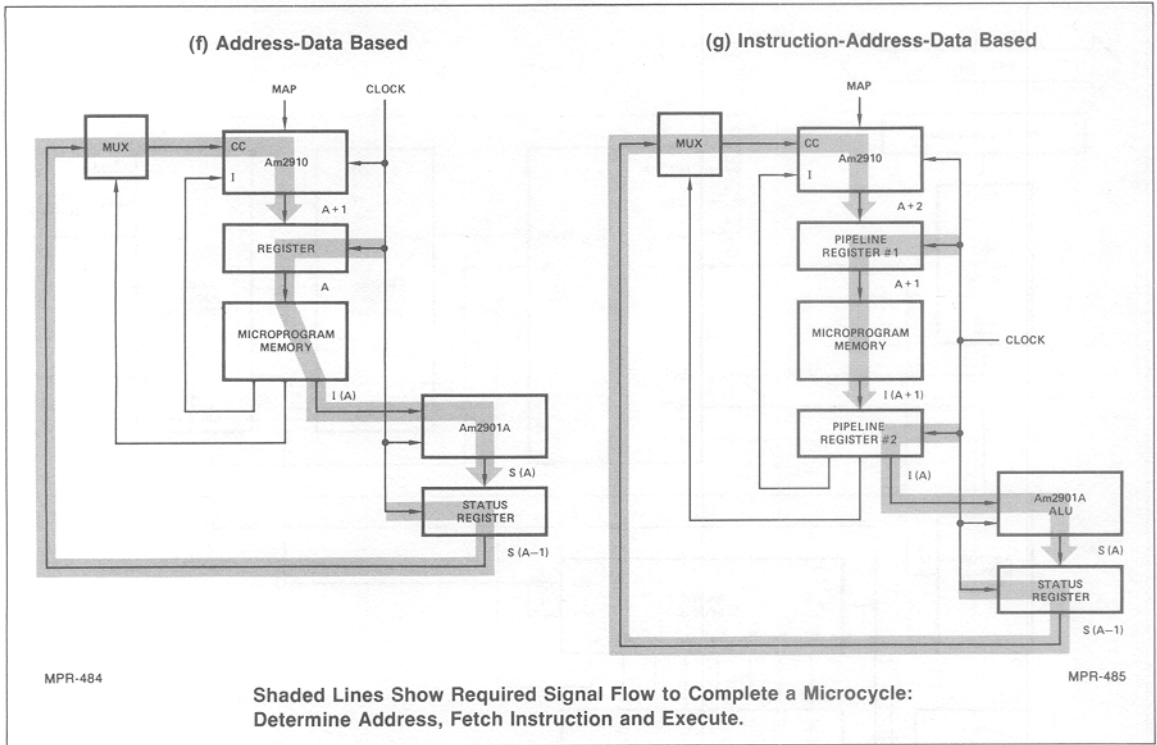


Figure 12. Standard Microprogram Control Architectures (Cont.).

The advantage of the instruction-data-based architecture is that the address and contents of the next microinstruction are being fetched while the current microinstruction in the pipeline register is being executed. This allows a shorter microcycle since the microprogram memory fetch and ALU execution can be operated in parallel. The results of this type operation are demonstrated in Figure 13 where we see a typical timing diagram of the microprogram execution of the address-data-based instruction architecture. It should be noted that when the computational aspects of a microinstruction are not completed in the same microcycle, they obviously cannot be used to determine the address of another microcycle until the computation has been completed and stored in the status register. Thus, this pipelined architecture offers significant speed improvement except in the case of certain conditional jumps. In other words, the conditional jump may not use the status register information of the im-

mediately preceding microinstruction because the computation is just being performed. For this architecture, the conditional jump fetch must be executed on the cycle after the status register contains the proper execution results. This can be seen by studying Figure 13. In most microprogram designs this is not a disadvantage because other housekeeping and ALU operations can be performed while the address of the next microinstruction is being determined using the current contents of the status register. While it is not directly pertinent to the discussion at this time, let us point out that the Am2904 has been designed such that the machine architect can utilize both instruction-data-based architecture as well as instruction-based architecture if no housekeeping is required. Thus, the Am2910 and Am2904 can be used in a variable architecture cycle to achieve maximum performance for the machine.

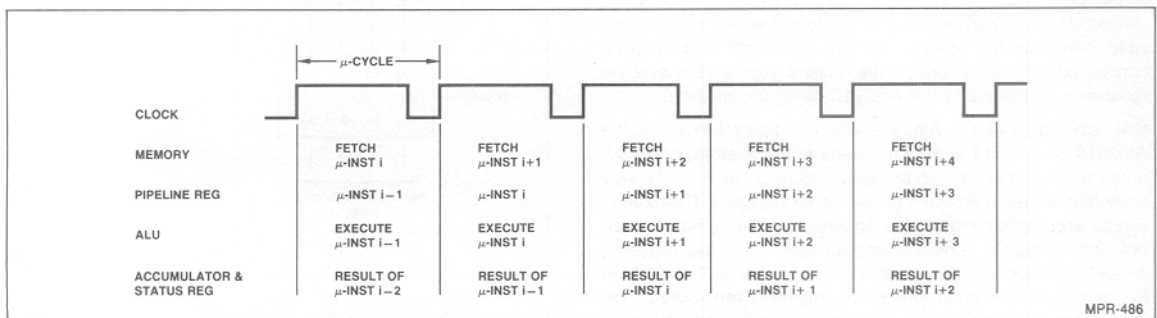


Figure 13. Timing Diagram of Microprogram Execution.

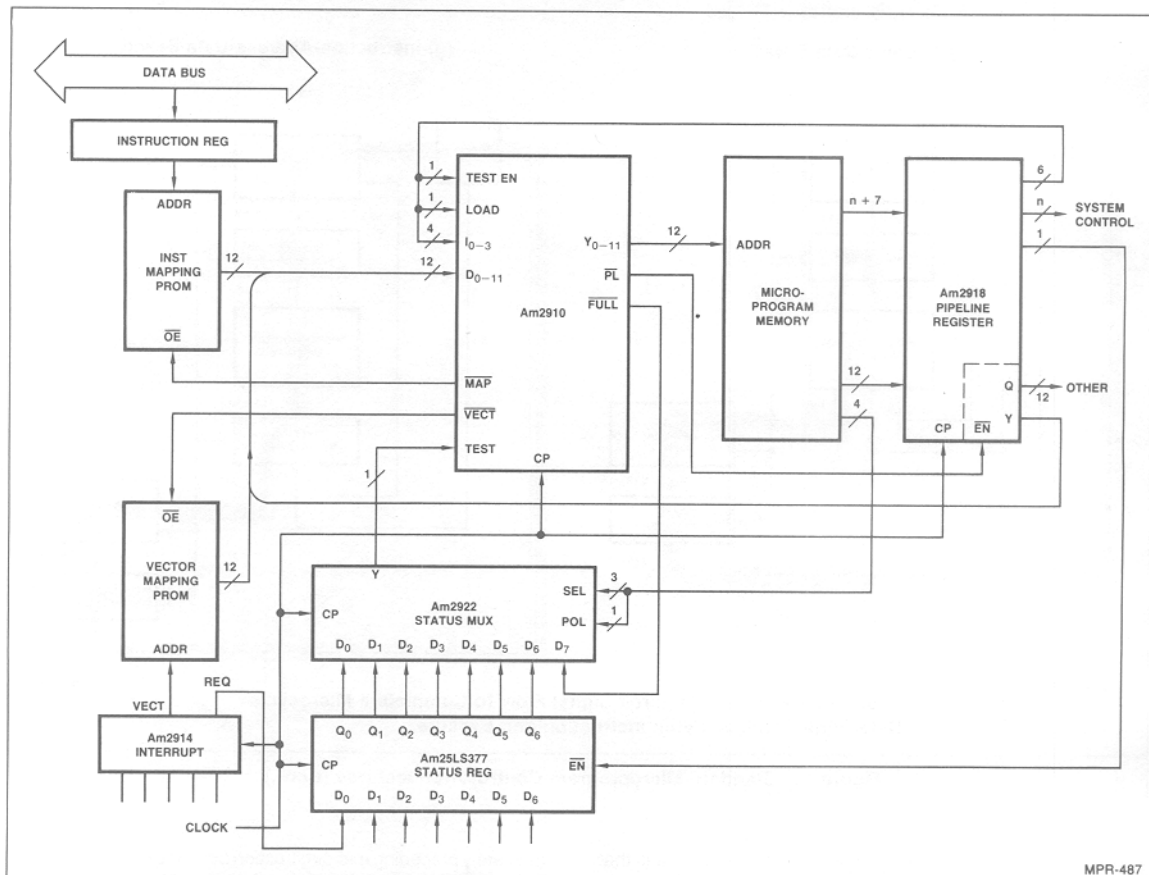


Figure 14. Typical Am2910 Microprogram Control Unit.

The Am2910 in Computer Control

A general state machine design using the Am2910 is shown in Figure 14. Here, all three output enables are used to advantage in order to control the mapping PROM, pipeline register and vector PROM in this design. This design is very straightforward and in fact is identical to that shown earlier.

One area that should not be overlooked is that of initializing the Am2910 at power up. One technique for accomplishing this is to use a pipeline register with a clear input to provide all LOWs to the instruction inputs of the Am2910. This will cause a reset of the stack in the Am2910 and force the outputs to the zero word and microcode which can be used for the initialization routine. Typically, power up will result in the firing of a timer which can be connected to the clear input of the register. Figure 15 shows the technique for initializing the Am2910 using this method.

One advantage of the Am2909 when compared to either the Am2910 or Am2911 is the OR inputs to the microprogram address field. These OR inputs allow two, four, eight or 16-way branching for each device if proper control is used. This control can be accomplished using the Am29803A, 16-way branch control unit. A typical computer control unit using the Am2909, Am2911, Am29803A and Am29811A is shown in Figure 16. In this example, the least significant microprogram control sequencer is an Am2909 and the two more significant sequencers are Am2911s.

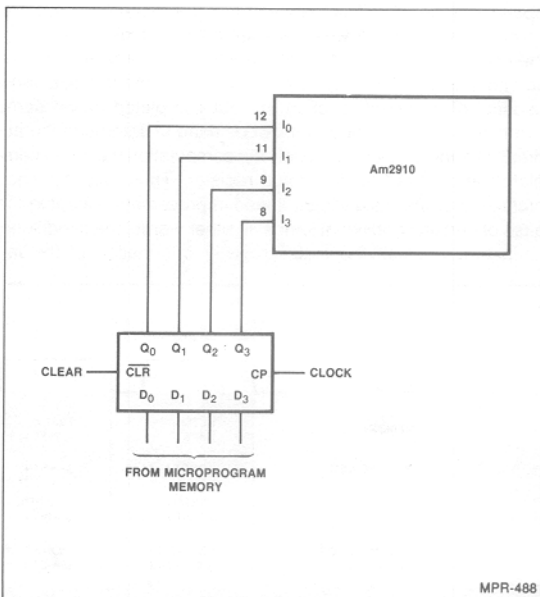


Figure 15. Initializing the Am2910.

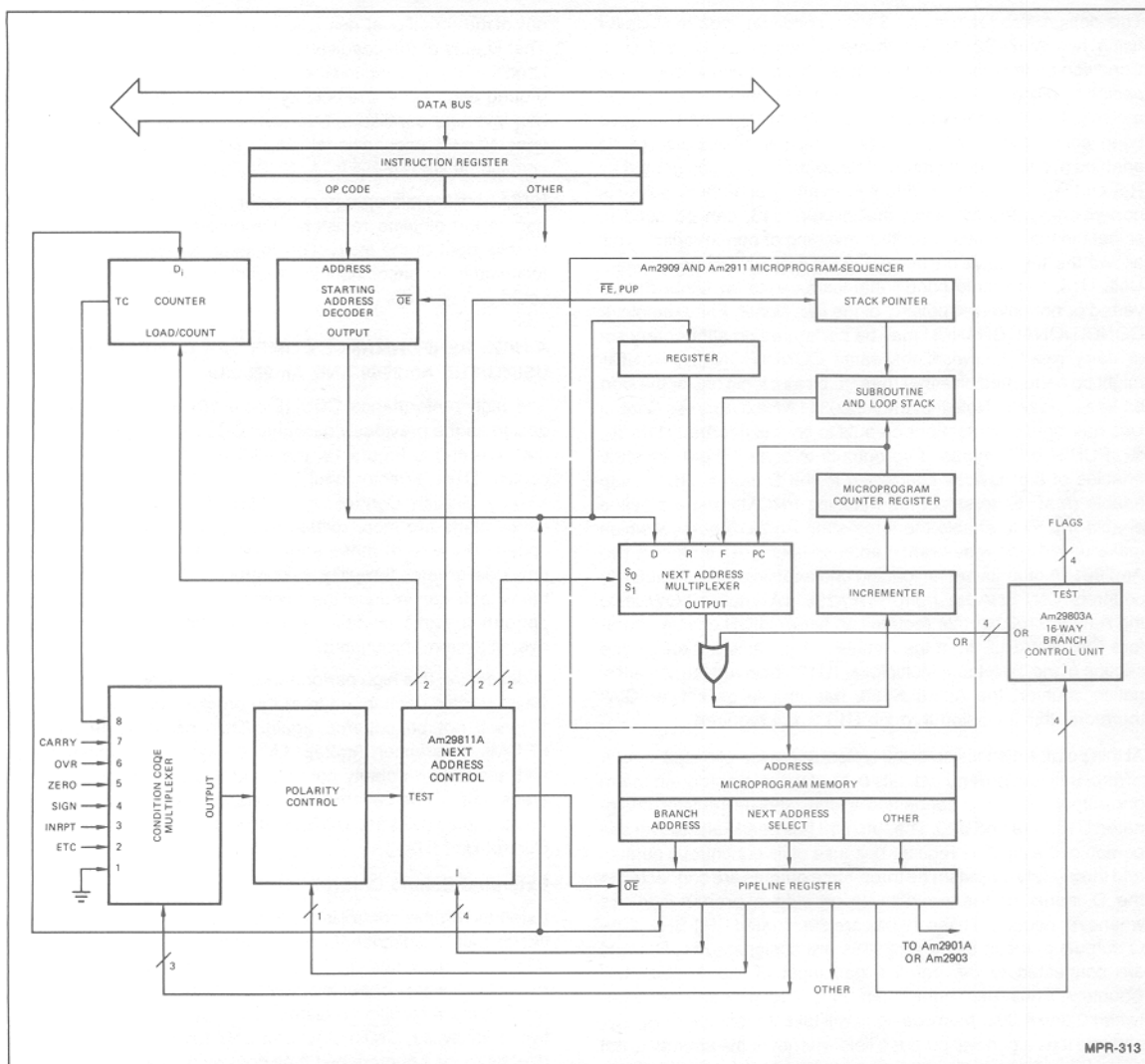


Figure 16. A High Performance Microprogram Controller Using the Am2909, Am29811A and Am29803A.

DETAILED DESCRIPTION OF THE Am2911 AND Am29811A IN A COMPUTER CONTROL UNIT

The detailed connection diagram of a straight-forward computer control unit is shown in Figure 17. This design features all of the next address control functions described previously and a few features have also been added.

Referring to Figure 17, the instruction register consists of two Am25LS377 Eight-Bit Registers with Clock Enable. These registers are designated as U1 and U2 and provide ability to selectively load a 16-bit instruction. This particular design assumes that the instruction word consists of an eight-bit op code as well as eight bits of other data. Therefore, the op code is decoded using three 256-word by 4-bit PROMs. The Am29761 has been selected for this function and is shown in Figure 17 as U3, U4 and U5.

The basic control function for the microprogram memory is provided by the Am2911s. In this design, three Am2911s (U6, U7,

and U8) are used so that up to 4K words of microprogram memory can be addressed. The microprogram memory can consist of PROMs, ROMs, or RAMs, depending on the particular design and the point of its development. This particular design shows the capability of a 64-bit microword; however, the actual number of bits used will vary from design to design.

The pipeline register associated with the computer control unit consists of five integrated circuits designated U16, U17, U18, U19 and U20.

One of the features of the architecture depicted in Figure 17 is the event counter shown as U9, U10 and U11. This event counter consists of three Am25LS163s connected as a 12-bit counter. The counter can be parallel loaded with a 12-bit word from pipeline registers U18, U19 and U20. The multiplexer and D-type flip-flop (U21 and U22) at the counter overflow output (U9) is present to improve system cycle time and will be described in detail later.

This design also features a 16-input condition code multiplexer using two Am74S251s, which are designated U12 and U14. Condition code polarity control capability has been added to the design by using an Am74S158 Two-Input Multiplexer designated as U13. The W outputs and Y outputs from U12 and U14 have been connected together but only one set of outputs will be enabled at a time via the three-state control signal designated as R_{20} and \overline{R}_{20} . Since the Y output is inverting and the W output is non-inverting, the two-input multiplexer, U13, can be used to select the test condition as either inverting or non-inverting. This allows the test input on the Am29811A Next Address Control Unit, U15, to execute conditional instructions on either the inverted or non-inverted polarity of the test signal. For example, a CONDITIONAL BRANCH may be performed on either carry set or carry reset. Likewise, the same CONDITIONAL BRANCH might be performed on either the *sign* bit as a logic one or the *sign* bit as a logic zero. Note that the Am29811A Next Address Control Unit has eight outputs. Four outputs to control the Am2911's S_0 , S_1 , PUP and \overline{FE} inputs. Two outputs to control the three-state enables of the devices connected to the D inputs, i.e., a map enable ($\overline{MAP E}$) to select the mapping PROMs and a pipeline enable ($\overline{PL E}$) to enable the three-state Am2918 outputs which make up a 12-bit wide branch address field. The remaining two Am29811A outputs are for loading and enabling the Am25LS163 counters. CNT ENABLE from the Am29811A is active-LOW while the Am25LS163 counter requires an active-HIGH enable, therefore CNT ENABLE from the Am29811A is passed through one section of the Two-Input Multiplexer (U13) for inversion. An alternative counter, the Am25LS169, has enable as active-LOW; therefore, this inversion through U13 is not required.

At this point, a discussion of the typical operation of this computer control unit is in order. First, bits 0-11 of the microprogram memory output word, are connected to the pipeline register designated U18, U19 and U20. The Am2918 has been selected for this portion of the pipeline register because of its continuous outputs and three-state outputs. The three-state outputs are connected to the D inputs of the Am2911 to provide a branch address whenever needed. These 12 bits are designated BR_0 - BR_{11} . The Q outputs of these same Am2918s are designated R_0 - R_{11} and are connected to the parallel load input of the Am25LS163 Counters. Thus, the counter can be loaded with any value between 0 and 4,095. Many designs will take advantage of R_0 - R_{11} and use it as a general purpose field whenever the counter is not being loaded or a jump pipeline is not being performed. Using a microprogram memory field for more than one function (branch address and counter load value in this example) is called FORMATTING and will be covered in greater detail later. The other two devices in the pipeline register shown on the architecture of Figure 17 are U16 and U17. First, U17 receives four bits (12, 13, 14 and 15) from the microprogram memory to provide four-bit instruction field to the Am29811A. This four-bit field, designated R_{12} - R_{15} , provides the actual next address control instruction for the computer control unit. R_{16} is the polarity control bit for the test input and is connected to the select input of the Am74S158 Two-Input Multiplexer. When R_{16} is LOW, the signal at the Am29811A test input will be inverted, but when R_{16} is HIGH, the test input will be non-inverted.

The Am74S175 has been used as part of the pipeline register (U16) because it has both inverting and non-inverting outputs. Signals R_{17} , R_{18} and R_{19} are used to control the One-of-Eight Multiplexer (U12 and U14) A, B and C inputs. Pipeline register output R_{20} and \overline{R}_{20} are used to enable either the U12 outputs or the U14 outputs such that a one-of-sixteen multiplexer function is implemented. In this design, the TEST 0 input of U14 is connected to ground. This provides a convenient path for converting

any of the conditional instructions to non-conditional instructions. That is, any of the conditional instructions can be executed unconditionally by selecting the TEST 0 input which is connected to ground and forcing the polarity control to either the inverting or non-inverting condition. This allows the execution of unconditional JUMP, unconditional JUMP-TO-SUBROUTINE, and unconditional RETURN-FROM-SUBROUTINE instructions.

Bit 21 from the microprogram memory utilizes a flip-flop in U17 as part of the pipeline register. This output, R_{21} , is used as the enable input to the instruction register. Needless to say, other techniques for encoding this enable function in a formatted field could be provided.

A HIGH PERFORMANCE COMPUTER CONTROL UNIT USING THE Am2909 AND Am29803A

The high performance CCU (Figure 18) is of a similar basic design as the previously described CCU. The major differences are, referring to Figure 18, the addition of an extended enable control (U16), a vector input (U24 and U25), and an Am29803A 16-way Branch Control Unit (U23). These performance enhancements are more related to function than to actual circuit speed. The use of these enhancements by the microprogram provides greater flexibility in controlling a machine's environment, and can reduce the microinstruction count required to perform a particular task, which has the effect of increasing overall system throughput.

In describing this high performance CCU design, those sections which remain unchanged from the previous description (Figure 17), will not be covered again. This includes the mapping PROMs, sequencer, Am29811A, counter, condition test inputs and associated polarity control, and the pipeline register. The areas that will be covered are: extended enable control (U16), Vector inputs (U24 and U25), and the Am29803A 16-way Branch Control Unit (U23).

Extended Enable Control

Extended enable control is accomplished via an Am74S139 dual two-to-four line decoder in conjunction with the Am29811A next address control unit. In Figure 17, $\overline{PL E}$ and $\overline{MAP E}$ of the Am29811A were connected directly to the components that they are to control (pipeline registers and mapping PROMs, respectively). Likewise, CNT LOAD and CNT ENABLE are connected directly to the counters that they control (with the exception that CNT ENABLE requires inversion when using Am25LS163 counters). In Figure 18, $\overline{PL E}$, $\overline{MAP E}$, CNT LOAD and CNT ENABLE go to the inputs of the Am74S139 two-to-four line decoder (U16). When either $\overline{PL E}$ or $\overline{MAP E}$ is LOW, then either $2Y_1$ or $2Y_2$ of U16 is LOW and either the pipeline branch address registers or mapping PROMs are enabled. If both $\overline{PL E}$ and $\overline{MAP E}$ are HIGH, then output $2Y_3$ of U16 is LOW enabling the three-state outputs of U24 and U25 which are alternate microprogram starting address decoders (alternate mapping PROMs), and called VECTOR INPUT in this design. Likewise, CNT LOAD and CNT ENABLE follow the same rules, enabling the counter to load or count via $1Y_1$ and $1Y_2$ of U16.

Vector Input

The "Vector Input" provides the system designer with a powerful next starting address control. For example, one possible use might be as an interrupt vector. For instance, use the "Interrupt Request" output of an Am2914 Vectored Priority Interrupt Controller (or group of Am2914s) as an input to one of the conditional test inputs of multiplexers (U12 or U14). Then connect the Am2914 Vector Out lines to the vector mapping PROMs (Vector input U24 and U25). The microprogram then could, at the appro-

appropriate time, test for a pending interrupt and if present, jump in microprogram memory directly to the routine which handles the specific interrupt as requested via the Am2914 Vector Output lines. This routine will take the proper steps to preserve the status of the interrupt system, and then will service the interrupt. This is one of many possible uses for the Vector Input. Other possible uses include both hardware and software "TRAP" routines and so forth. As can be seen, the design presented here uses the Vector Enable line (output 2Y₃ or U16) to enable an alternate starting address input at the Am2911. This, however, does not preclude the use of other devices in place of mapping PROMs as the D-input vector source.

It should be understood that this does not accomplish a "micro-interrupt" function in that it is not a random possibility. Instead a microprogrammed test is made and an alternate microroutine is performed. A true "microprogram interrupt" is one that could occur at any microinstruction. The Am2910 does not handle this case internally.

Am29803A 16-Way Branch Control Unit

The Am29803A provides 16-way branch control when used in conjunction with the Am2909 bipolar microprocessor sequencer, and is shown as U23 in Figure 18 with its pipeline register U22. The Am29803A has four TEST-inputs, four INSTRUCTION-inputs, four OR-outputs, and an enable control. The four OR-outputs connect directly to the Am2909 OR-inputs (U8 in Figure 18). The four INSTRUCTION-inputs to the Am29803A provide control over the TEST-inputs and OR-outputs, and are provided by the microprogram via the pipeline register U22 (Figure 18).

Basically, the INSTRUCTION-inputs (I₀-I₃) provide sixteen instructions (O-F₁₆) which can select sixteen possible combinations of the TEST-inputs and provide a specific output on the OR-outputs depending upon the state of the inputs being tested. (The subscript 16 refers to basic 16.) All possible combinations of instruction-inputs, TEST-inputs and OR-outputs are shown in Figure 19.

Note that instruction zero does not test any inputs (a disable instruction). Instructions 1, 2, 4 and 8 test one input and can cause a branch to one of two words. Instructions 3, 5, 6, 9, 10 and 12 test two inputs and can jump to one of four words (a 4-word page). Instructions 7, 11, 13 and 14 test three inputs and can jump on an eight word page. Instruction number 15 tests all four inputs and the result can jump to any word on a sixteen word page.

USING THE Am29803A

In the architecture of Figure 18, the Am29803A allows 2-way, 4-way, 8-way or 16-way branching as determined by selectable combinations of the TEST-inputs. Referring to Figure 19, the ZERO instruction (all instruction bits LOW) inhibits the testing of any TEST-inputs, thus providing LOW OR-outputs. Any single TEST-input selected (T₀, T₁, T₂ or T₃) will result in OR₀ being HIGH or LOW in correspondence with the polarity of the selected TEST-input. Selecting any combination of two TEST inputs results in the outputs OR₀ and/or OR₁ being HIGH or LOW, following a mapped one-to-one relationship, i.e., OR₀ and OR₁ will follow the TEST-inputs, but no matter which pair of TEST-inputs are selected, their HIGH/LOW condition is mapped to the OR₀ and OR₁ outputs. Likewise, selecting any three TEST inputs, will map their HIGH/LOW condition to the OR₀, OR₁ and OR₂ outputs. Selecting all four TEST-inputs, of course, causes a one-to-one relationship to exist between the HIGH/LOW conditions of the TEST-inputs and the corresponding OR-outputs. Refer to Figure 19 to verify the relationships between INSTRUCTION-inputs, TEST-input, and OR-output. It is very important that the

mapping relationship between these signals be completely understood. When using the Am29803A TEST-OR capability as shown in Figure 18, the microprogrammer must position the applicable microcode within microprogram memory so that the low-order address bits are available for ORing. Sequencer instructions using the Am2909/2911 D-inputs (JRP, JSRP, JP and CJS in particular) are ideally suited for the Am29803A TEST-OR capability. The jump-to-location, available via pipeline BR₀-BR₁₁ or the Am2909/2911 register, can contain the address of a branch table. A branch table is merely a sequential series of unconditional jump instructions. The particular jump instruction executed is determined by the low-order address bits; that is, the first jump instruction in a branch table must start at a location in microprogram memory whose low-order address bit (or bits) is zero. If a single Am29803A TEST-input is selected (2-way branching) then only the least significant bit in the beginning branch table address needs to be zero. Two Am29803A TEST-inputs selected (4-way branching) requires that the branch table start on an address with the low-order two bits equal to zero; 8-way branching requires three low-order zero bits, and 16-way branching requires four low-order zero address bits. Understanding this branch control concept is really quite simple. The branch table is located in microprogram memory beginning at a location whose address has sufficient low-order zero bits to accommodate the number of selected Am29803A TEST-inputs. If, for instance, three TEST-inputs were selected, the first jump instruction in the branch table must be at an address whose low-order three bits are zero, such as address 0F8₁₆. The second jump instruction in the branch table would begin in microprogram memory address 0F9₁₆. The third jump at location 0FA₁₆, the fourth at 0FB₁₆, etc. Through all eight locations (0F8₁₆-0FF₁₆). Assume the following pipeline instruction (referring to Figure 18): (1) U22 selects three Am29803A TEST-inputs, (2) U18 instructs the Am29811A Next Address Controller to select the Am2909/2911 D-inputs, (3) U16 enables the pipeline branch address as the D source, and (4) U19, U20 and U21 supplies the address 0F8₁₆ as the branch address. The Am29803A TEST-inputs will be ORed into the low-order three bit positions, thus providing a jump entry into the branch table indexed by the value of the OR bits. Each instruction in the branch table is usually a jump instruction, which allows the selection of a particular microcode routine determined by the value presented at the Am29803A TEST-inputs. These jump instructions are the first instruction of the particular sequence. There are, of course, many other ways to use the Am29803A 16-way Branch Control Unit.

The microprogram memory address supplied via an Am2909 sequencer can be modified by the Am29803A 16-way Branch Control Unit. Remember, however, that the microcode associated with this address modification relies on certain address bits being zero, therefore this microcode is not arbitrarily relocatable. The above discussion describes using the D-input and branching to provide low-order zeroes to use the OR inputs. Through proper design, the Register, PC Counter, or File can be used equally well.

THE COMPLETE COMPUTER CONTROL UNIT USING THE Am2910

A detailed connection diagram for a straightforward computer control unit using the Am2910 is shown in Figure 20. This design utilizes the Am25LS377 as U1 and U2 to implement a 16-bit instruction register. The op code outputs from the instruction register drive three Am29761 PROMs to perform the op code decoding function. These are shown in the diagram of Figure 20 as U3, U4 and U5. The Am2910 sequencer (U6) is used to perform the basic microprogram sequencing function.

Function	I ₃	I ₂	I ₁	I ₀	T ₃	T ₂	T ₁	T ₀	OR ₃	OR ₂	OR ₁	OR ₀
No Test	L	L	L	L	X	X	X	X	L	L	L	L
Test T ₀	L	L	L	H	X	X	X	L	L	L	L	H
Test T ₁	L	L	H	L	X	X	L	X	L	L	L	L
Test T ₀ & T ₁	L	L	H	H	X	X	L	L	L	L	L	L
Test T ₂	L	H	L	L	X	L	X	X	L	L	L	L
Test T ₀ & T ₂	L	H	L	H	X	L	X	L	L	L	L	L
Test T ₁ & T ₂	L	H	H	L	X	L	L	X	L	L	L	L
Test T ₀ , T ₁ & T ₂	L	H	H	H	X	L	L	L	L	L	L	L
Test T ₃	H	L	L	L	L	X	X	X	L	L	L	L
Test T ₀ & T ₃	H	L	L	H	L	X	X	L	L	L	L	L
Test T ₁ & T ₃	H	L	H	L	L	X	L	X	L	L	L	L
Test T ₀ , T ₁ & T ₃	H	L	H	H	L	X	L	L	L	L	L	L
Test T ₂ & T ₃	H	H	L	L	L	L	X	X	L	L	L	L
Test T ₀ , T ₂ & T ₃	H	H	L	H	L	L	X	L	L	L	L	L
Test T ₁ , T ₂ & T ₃	H	H	H	L	L	L	L	X	L	L	L	L
Test T ₀ , T ₁ , T ₂ & T ₃	H	H	H	H	L	L	L	L	L	L	L	L

L = LOW, H = HIGH, X = Don't care

Figure 19. Function Table.

A 16 input condition code multiplexer function is provided by using two Am2922s as U7 and U8. These devices allow one of sixteen inputs to be tested and the polarity of the test can also be determined. The pipeline register consists of U9, U10, U11, U12 and U13. These devices are edge triggered D type registers and have been selected to provide unique functions as required depending on their bit positions in the pipeline register. An Am74S175 was selected for U9 because both a true and complement output were desired to provide control to the condition code multiplexer three state enables. An Am74S174 register was selected as U10 because it provides a clear input for initializing the Am2910 microprogram sequencer. Three Am2918s were selected for U11, U12 and U13 because they have a three state output that can be used to provide the branch address field to the D inputs of the Am2910 and they also have a set of outputs that can be used to provide other control signals via this field when it does not contain a branch address. No specific devices are shown for the microprogram memory as the user should select the desired width and depth depending on his design.

ANOTHER DESIGN EXAMPLE

The Am2909, Am2910, Am2911, Am29811A and Am29803A have been designed to operate in the microprogram sequencing section of any digital state machine. Typically, the examples shown are for performing the computer control unit function of a typical minicomputer class machine. The design engineer should not limit his thinking for the use of these devices simply to that of microprogram sequencing in a computer control unit. These devices can be successfully used in other areas of designing such as memory control, DMA control, interrupt control and special purpose microprogrammed machine architectures. In order to provide an example of a design using these devices in something other than a typical computer control unit, a microprogrammed CRT controller is described in the following.

In order to provide some basis for the design of a CRT controller, the requirements of this controller must be spelled out. These are given as follows:

- A) Character size: 5 x 7 dot matrix. The character field will be 7 dots by 10 horizontal lines thereby providing ample space for the 5 x 7 character and the intervening space between characters and lines of characters.
- B) 80 characters per line. A standard 80 character per line display will be utilized and there will be 18 character periods allowed for horizontal retrace time.
- C) 24 lines of characters per frame. This provides a total of 240 visible lines per frame (24 lines of characters by 10 horizontal lines per character). There are a total of 24 lines provided for vertical retrace bringing the total number of lines per frame to 264.
- D) Refresh rate: 60 frames per second. Therefore, the horizontal line rate will be $264 \times 60 = 15,840\text{Hz}$. As there are a total of $80 + 18 = 98$ character periods in a line, the character rate will be $98 \times 15.84 = 1,552.32\text{KHz}$, and the dot rate will be $7 \times 1.5288 = 10.86624\text{MHz}$. (Note: No interlace is used.)
- E) It is assumed that there is a 2K word deep x 8-bit wide character RAM available to the host computer in which it can write the ASCII equivalent of the characters to be displayed. If scrolling is to be used, the host computer must also write the first visible character's address divided by 16_{10} into the Am25LS374 "First Address Register".
- F) This CRT controller must generate an 11-bit character address that is used by the 2K word deep character RAM. It must also generate the required video enable signals and the horizontal and vertical blanking signals.

Principle of Operation

A detailed block diagram of the CRT controller is shown in Figure 21. The block diagram shows an interface to an SBC-80/10 data bus, address bus and control bus. The outputs of the CRT controller are connected to a CRT monitor on the block diagram. Otherwise the block diagram shows a straightforward use of the Am2910 and three Am2911s to implement the CRT control function using microprogrammed techniques. The SBC-80/10 was selected for this example since it is well known.


A logic diagram of the CRT controller is shown in Figure 22. Three Am29775 512-word x 8-bit registered PROMs are used to contain the 23-bit wide microprogram. While only a minimum number of words are used in the design as shown, many additional words can be used to add various options (as described later). The address for these Am29775 registered PROMs is provided by an Am2910 microprogram sequencer. Three Am2911 sequencers are used to generate the character address for the character RAM. The least significant Am2911 sequencer is connected as a divide by 16 counter. This RAM address is compared with the desired last character address ($80 \times 24 = 1920$) value using an Am25LS2521 8-bit equal to detector. When the last address is detected, it can be sensed at the condition code multiplexer (Am25LS153) that is used to select the condition code for the Am2910 sequencer.

The data derived from the 2K word character RAM is decoded by a character generator (6061) in this design and the character output is parallel loaded into an Am25LS23 shift register. This shift register is used to provide the video signal from its Q_0 output to eventually drive the display via an Am74S240 buffer. The diagram of Figure 22 depicts an oscillator input source to supply the dot frequency. In this design, a 10.86624MHz oscillator should be connected to this oscillator input point. This oscillator input signal is used to clock the shift register containing the individual dot bits (dot-on or dot-off) and also drives an Am25LS169 counter which divides this frequency by 7 to generate the character rate clock. This character rate clock is used throughout the controller to provide a timing signal for the state machine design.

An Am25LS168 decade counter is used to generate the line inputs for the character generator and to count 10 horizontal lines per character space. This counter is clocked by the horizontal blanking signal (HB) and its \overline{RCO} output is used as one of the condition code multiplexer inputs. The \overline{RCO} output can be tested to determine when 10 counts have been executed by the counter and it is also used to enable the last address comparator during the 10th horizontal line time.

When the host computer accesses the character RAM, the HOST-ACCESS line is pulled LOW. This removes the Am2911 outputs from the character RAM address bus. When this access occurs, improper data may be present at the shift register inputs. Thus, the character generator PROM output is disabled by the HOST-ACCESS signal during this time.

When power is applied to this CRT controller or whenever it is reset, the RESET line is driven LOW. This signal is inverted through an Am25LS240 and then disables a part of the pipeline register outputs as well as enabling one half of an Am25LS241. This Am25LS241 inserts LOWs onto the instruction (I) inputs of the Am2910 sequencer. Then, the next character rate clock will force the microprogram address outputs to zero and the microprogram for the CRT controller as shown in Figure 23 will be executed starting at address zero.

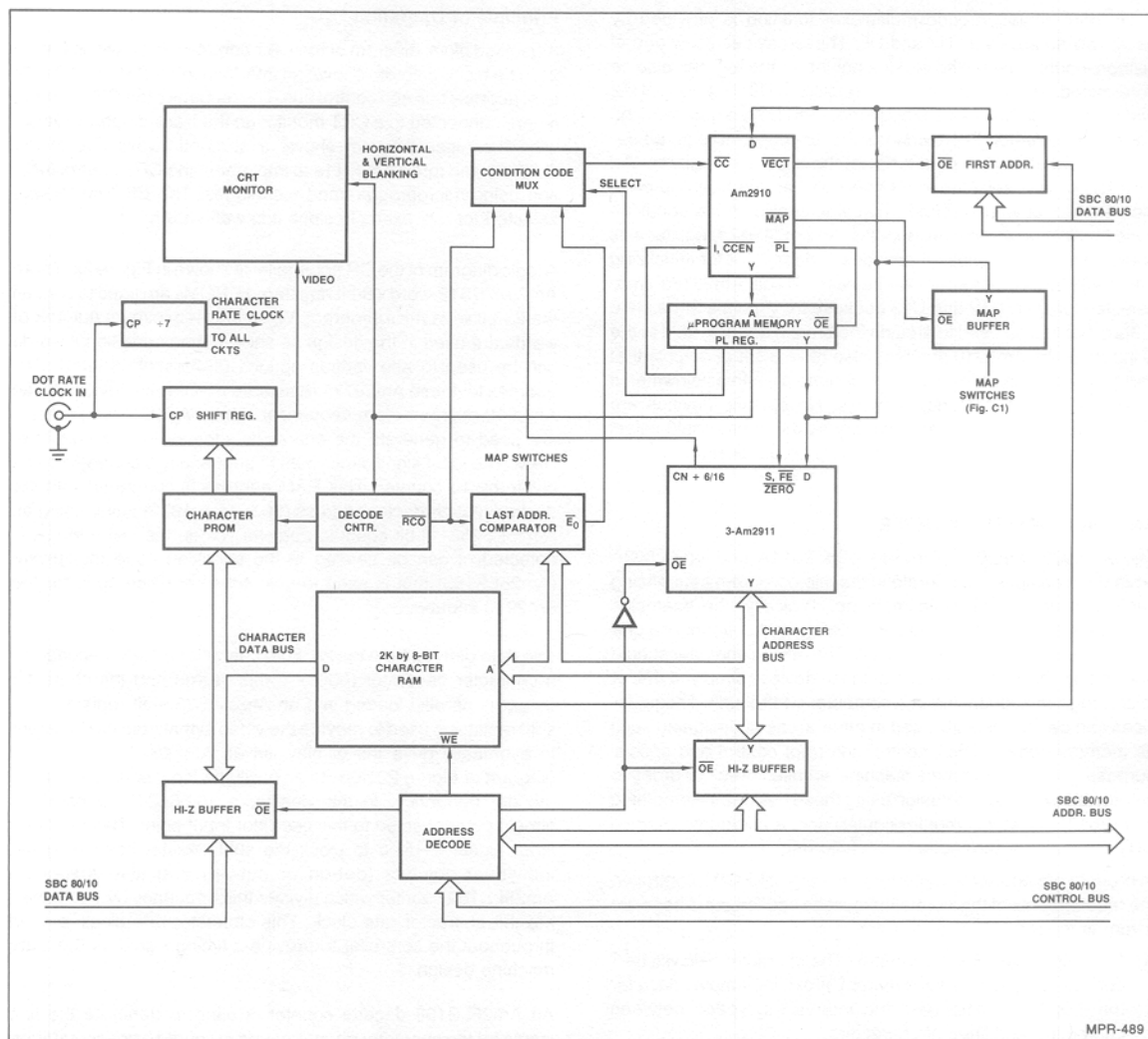

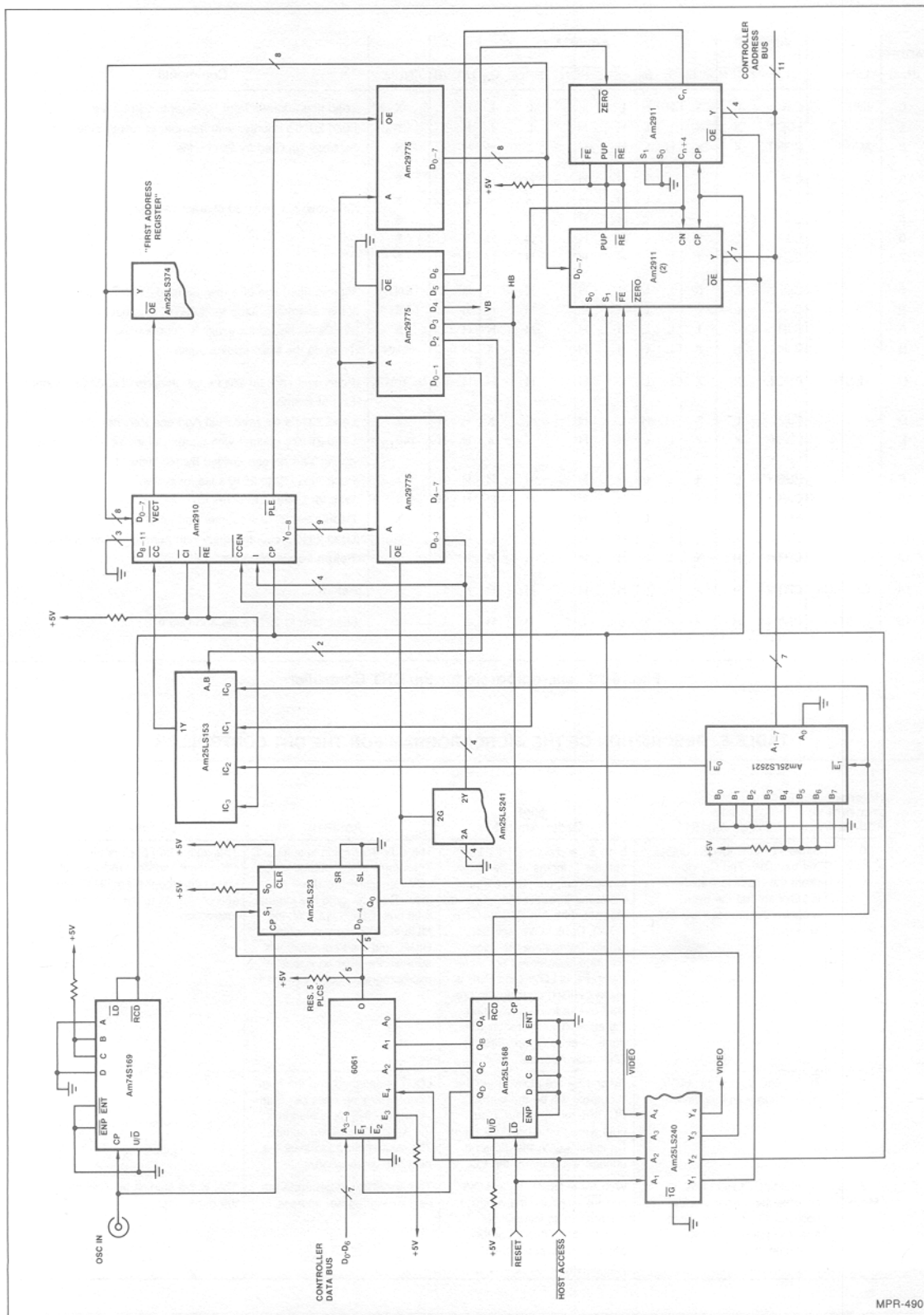


Figure 22. CRT Controller.

ADDR (Hex)	Label	Am2910			Am2911								NUM	Comments
		I	CCEN	MUX	S ₁	S ₀	FE	ZEROH	ZEROL	C _n	HB	VB		
0	INIT	CJV	L	3	H	H	L	H	L	L	H	L	X	;Load first address from Register to 2911's file ;Load 2910's counter with member of rows/frame - 1 ;Address supplied by 2911's file
1	MAIN	LDCT	X	X	L	L	H	H	L	L	H	L	23 ₁₀	
2		CONT	X	X	H	L	H	H	L	H	H	L	X	
3		CJP	L	1	L	L	H	H	H	H	L	L	\$;One row: 5 x 16 = 80 characters
4		CJP	L	1	L	L	H	H	H	H	L	L	\$	
5		CJP	L	1	L	L	H	H	H	H	L	L	\$	
6		CJP	L	1	L	L	H	H	H	H	L	L	\$	
7		CJP	L	1	L	L	H	H	H	H	L	L	\$	
8		CJS	L	0	L	L	H	H	H	H	H	L	TENTH	
9	TENTH	CJS	L	2	L	L	H	H	H	H	H	L	LASTA	;If tenth (last) line of a row: jump to "TENTH" subroutine ;If last character: jump to "LASTA" subroutine ;Wait, until horizontal invisible counts done ;Then do the Main routine again
A		CJP	L	1	L	L	H	H	H	H	H	L	\$	
B		CJP	H	X	L	L	H	H	X	X	H	L	MAIN	
C		RPCT	X	X	L	L	L	H	H	H	H	L	GOBACK	
D		CJV	L	3	H	H	L	H	L	X	H	H	X	
E		LDCT	X	Y	L	L	H	H	X	X	H	H	146 ₁₀	
F		PUSH	L	3	L	L	H	H	H	H	H	H	X	
10	GOBACK	CJP	L	1	L	L	H	H	H	H	H	H	\$;Push next PC to 2910's file for double ;Wait for LS2911 to count 16 ;Decrement 2910's counter and jump one line back if = 0 ;Load 2910's counter again with number of rows/frame - 1 ;Return from subroutine
11		RFCT	X	X	L	L	H	H	H	H	H	H	X	
12		LDCT	X	X	L	L	H	H	H	H	H	H	23 ₁₀	
13		CRTN	H	X	L	L	H	H	H	H	H	H	X	
14		CRTN	H	X	L	L	H	H	H	H	H	L	X	
15		LASTA	H	X	X	X	L	L	H	H	H	L	X	
														;Load zero to 2911's file and return.

Figure 23. Microprogram for the CRT Controller.

TABLE 6. DESCRIPTION OF THE MICROPROGRAM FOR THE CRT CONTROLLER.

Micro-program Address	Low Order Am2911	High Order Am2911s	Am2910	Comments
0	Since ZERO is low, its output will be LOW. The C _n input (from the Pipeline Register) is LOW so that the micro-program incremter will not increment.	Both S ₁ and S ₀ are HIGH so that the D inputs will be routed to the Y outputs. These inputs will come from the First Address Register (the Am2910 VECT is LOW). C _n is LOW (see left column); therefore the micro-program counter will not increment. FE is LOW (and PUP is always HIGH) causing the present output to be pushed on the stack. The character address is already the "First Character Address".	The CJV instruction is selected. Therefore, VECT output will be LOW, enabling the "First Address Register onto the internal 8-bit bus. CCEN is LOW; the MUX is selecting a constant HIGH, and the sequencer will address the next consecutive microprogram address (word 1).	This instruction pushes the "First Character Address" more significant bits onto the Am2911's file, and continues to the next micro-instruction.
1	ZERO and C _n are still LOW, so no change in this device.	S ₁ and S ₂ are LOW; thus, the Y outputs will be the current PC, (the same as the Y outputs were in the previous step). C _n is still LOW, therefore no change will occur in the PC.	LDCT is selected and the number of character-rows per frame minus 1 (23 ₁₀) is loaded into the Am2910 register/counter. The sequencer addresses the next microinstruction.	
2 "MAIN"	Maintaining ZERO LOW assures the proper starting address. C _n is HIGH; therefore, the internal PC will be incremented.	With S ₁ = HIGH, S ₀ = LOW and FE = HIGH, the Am2911 will refer to its internal file (the starting address of this particular character-row) without popping.	The Am2910 will generate the next microprogram address.	This is the starting location for the main loop.

Note: Figure 24 is at back of the book.

TABLE 6. DESCRIPTION OF THE MICROPROGRAM FOR THE CRT CONTROLLER (Cont.).


Micro-program Address	Low Order Am2911	High Order Am2911s	Am2910	Comments
3	This Am2911 now counts up using its PC incrementer. At the final count (moving from F_{16} to 0) its C_{n+4} output will be HIGH.	Initially these two Am2911s will not change their Y outputs since their C_n input is LOW. However, when the C_n input goes HIGH, the internal PC will increment	With the MUX selecting the C_{n+4} output from the least significant Am2911 slice, the CC input to the Am2910 sequencer will be LOW until the Am2911 counts 16. CC = LOW will cause the next microprogram address to be the pipeline register contents; this is also the current microprogram address (word 3). When C_{n+4} goes HIGH, CC will go HIGH and together with \overline{CCEN} = LOW, will force the Am2910 to address the next consecutive microprogram address (4).	This microstep will be executed 16 times. (Note that $80 = 5 \times 16$.)
4 through 7	Same as 3.	Same as 3.	Same as 3, except that at each address, the current microprogram address is written.	The microprogram itself is used as a counter in this application since the count is only 5, the microprogram is relatively short versus the memory's depth and this is a convenient means to economize on chip count.
8	Continues to count (note that it enters this line with an output of zero).	Since C_n is LOW (see left column) no change occurs in these devices. Note that the Y outputs contain the more significant bits of the address of the first character of the next character row.	The MUX selects the Am25LS168 ten-line-counters RCO as the condition code input to the Am2910 (CC). If the line count is less than 10, CC will be HIGH and the next microinstruction will be addressed. If the tenth line of a character row is executed, CC will be LOW and a JUMP-TO-SUB-ROUTINE to an address, supplied by the pipeline register ("TENTH") will be executed.	We are now at the end of a TV line. Therefore, the Horizontal Blanking Signal (HB) is HIGH. The least significant Am2911 slice now counts the invisible characters during the horizontal retrace.
9	Continues to count through the internal PC incrementer.	No change.	The MUX now selects the Last Address Comparator output for CC. If the current more significant bits of the character-address coincide with the last address + 1 ($1920_{10}/16$) a subroutine call will be performed to "LASTA". Otherwise, the microprogram will continue consecutively.	Note that 80 characters/row and 24 rows/frame requires a 1920_{10} word memory. When the last memory location (1920_{10}) is read out, the scan will begin at 0.
A	Continues to count. At count 15, C_{n+4} goes HIGH.	No change until C_n goes HIGH, then count.	Same as at address 3.	Waiting for the least significant Am2911 to count to 15. This microstep will be executed as many times as necessary to accomplish this.
B	It doesn't matter what this device does at this microstep because at the next microstep it will receive LOW on its ZERO input.	No change.	Unconditionally (\overline{CCEN} = HIGH) steers the microprogram to the address supplied by the pipeline register ("MAIN" = 2).	Performing a JUMP to the beginning of the main-loop (address 2).
C "TENTH"	Continues to count.	No change.	If internal counter is equal to zero, it means that 24 character rows were already displayed and we are at the bottom of the CRT display. A vertical retrace period is needed and the microprogram will continue sequentially. If the counter is not yet zero, we do not need to execute the vertical retrace routine and the next address will be supplied by the pipe-register ("GOBACK" = 14_{16}) while the internal counter is decremented.	The decision whether the bottom of the CRT (End of Frame) is reached or not is made internally in the Am2910, using its counter.

TABLE 6. DESCRIPTION OF THE MICROPROGRAM FOR THE CRT CONTROLLER (Cont.).

Micro-program Address	Low Order Am2911	High Order Am2911s	Am2910	Comments
D	$\overline{\text{ZERO}} = \text{LOW}$, therefore, output $Y = 0$. This is necessary to assure that C_{n+4} is LOW.	Same as at address 0.	Same as at address 0.	As we are at the End of Frame, the "First-Address-Register" contents (enabled by the Am2910's VECT output) is pushed onto the Am2911's file. Note that the Vertical Blanking Signal (VB) goes HIGH.
E	Same as at address B.	No change.	The internal counter is loaded with 146_{10} , supplied by the pipeline register. The next consecutive microstep is addressed.	$(146_{10} + 1) \times 16_{10} = 2352_{10}$ equals the number of character-periods during vertical retrace. Loading 2352_{10} directly into the Am2910's counter would require 7 bits. Using this scheme we reduce the microprogram width.
F	Counts.	No change.	With $\overline{\text{CCEN}} = \text{LOW}$ and $\overline{\text{CC}} = \text{HIGH}$ (supplied from a constant HIGH by the MUX), the next address (10_{16}) will be pushed onto the Am2910 file, the counter will not be affected and the next consecutive microstep will be addressed.	This is a preparatory step for the 2 step "Vertical Retrace" double-nested loop.
10_H	Counts. When final count is reached, $C_{n+4} = \text{HIGH}$.	No change with $C_n = \text{LOW}$; increments with $C_n = \text{HIGH}$. This has no practical affect as the HB signal is HIGH, and at the beginning of the next visible line, the correct address will be fetched from the file (address 2).	The MUX supplies the C_{n+4} output of the less significant Am2911 slice to the Am2910 $\overline{\text{CC}}$ input. While this signal is low, the Am2910 will select the pipeline register as the source of the next microinstruction address. The current address (10_H) being written there, this instruction will be executed until $\overline{\text{CC}}$ goes HIGH. Then the next consecutive instruction will be selected through the Am2910 internal PC.	Again, this is a possible way to dwell on a certain microstep waiting a condition to change its status (like address 3 through 7). This is the internal loop of a double-nested loop system.
11_H	Counts.	No change.	If the final count has been reached, the next microinstruction will be addressed and the internal stack will be popped (adjusted). Otherwise, the next microinstruction address will be the one residing on the top of the stack (which is 10_{16}).	This is the external loop of the double-nested loop system, which counts the vertical retrace interval. By adding a single microinstruction the chip count was reduced.
12_H	Counts.	No change.	Same as at address 1.	Reinitializes the Am2910 internal counter with the number of character rows per frame.
13_H	Counts.	No change.	Unconditional return from subroutine. ($\overline{\text{CCEN}} = \text{HIGH}$).	End of "TENTH" subroutine at End of Frame (with vertical retrace).
14_H "GOBACK"	Counts.	No change.	Unconditional return from subroutine.	End of "TENTH" subroutine without vertical retrace.
15_H "LASTA"	Counts.	Pushes zero into file.	Unconditional return from subroutine.	A one-line subroutine to reinitialize character address to zero.

a)


DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3	PATH 4
29775	CP to D	15	15	15	15
2911 (A)	C_n to C_{n+4}	9	—	—	—
2911 (A)	ZERO to C_{n+4}	—	30	—	—
2911 (B)	C_n to C_{n+4}	9	9	—	—
2911 (C)	C_n (t_S)	15	15	—	—
2911 (B, C)	FE (t_S)	—	—	14	—
2911 (B)	S_0, S_1 to C_{n+4}	—	—	—	30
2911 (C)	C_n (t_S)	—	—	—	15
TOTAL-ns		48	69	29	60

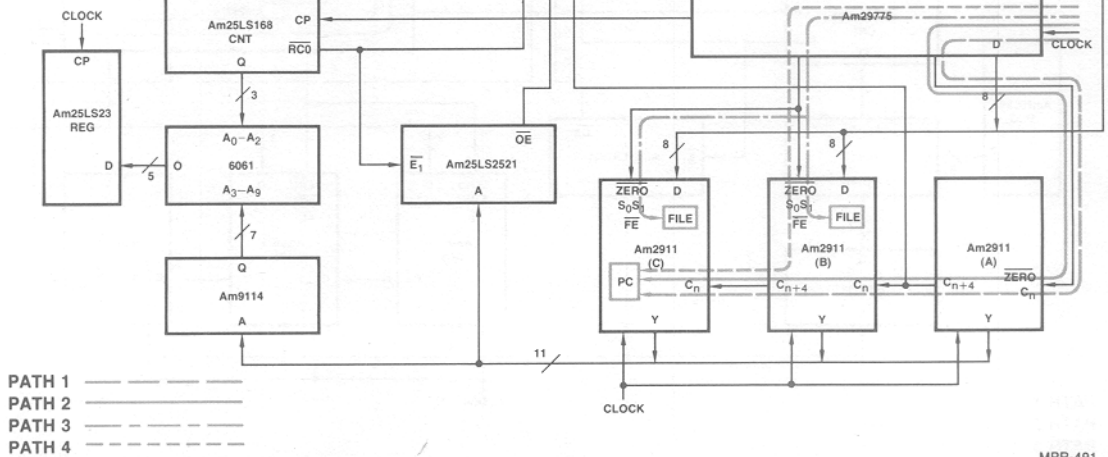

MPR-491

b)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
29775	CP to D	15	15	15
2911 (A)	ZERO to Y	19	—	—
2911 (B, C)	ZERO to Y	—	19	—
2911 (B, C)	S_0, S_1 to Y	—	—	19
9114	A to D	150	150	150
6061	A to Out	70	70	70
25LS23	D to CP (t_S)	23	23	23
TOTAL-ns		277	277	277

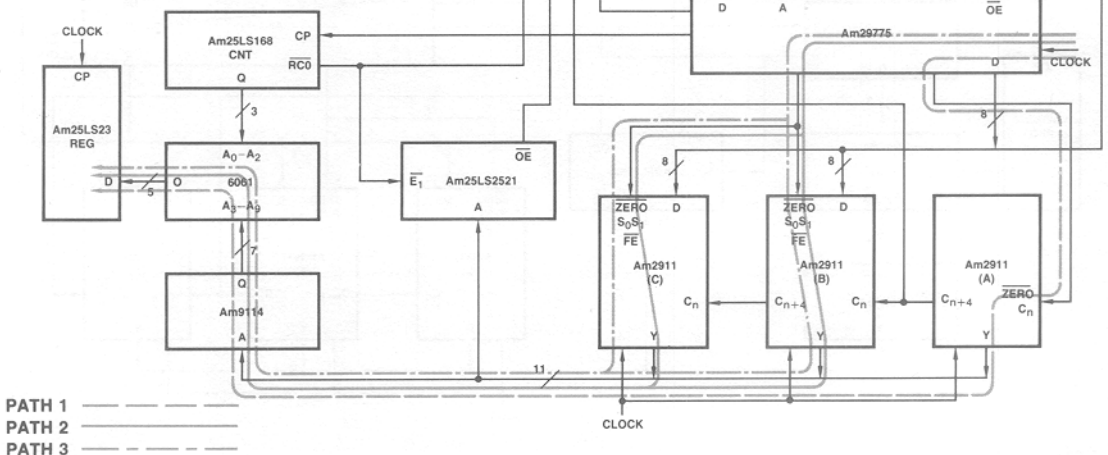


MPR-492

Figure 25.

c)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
29775	CP to D	15	15	—
2910	I to Y	40	—	—
2910	CCEN to Y	—	23	—
2910	CP to Y	—	—	54
29775	A (t ₅)	40	40	40
TOTAL-ns		95	78	94

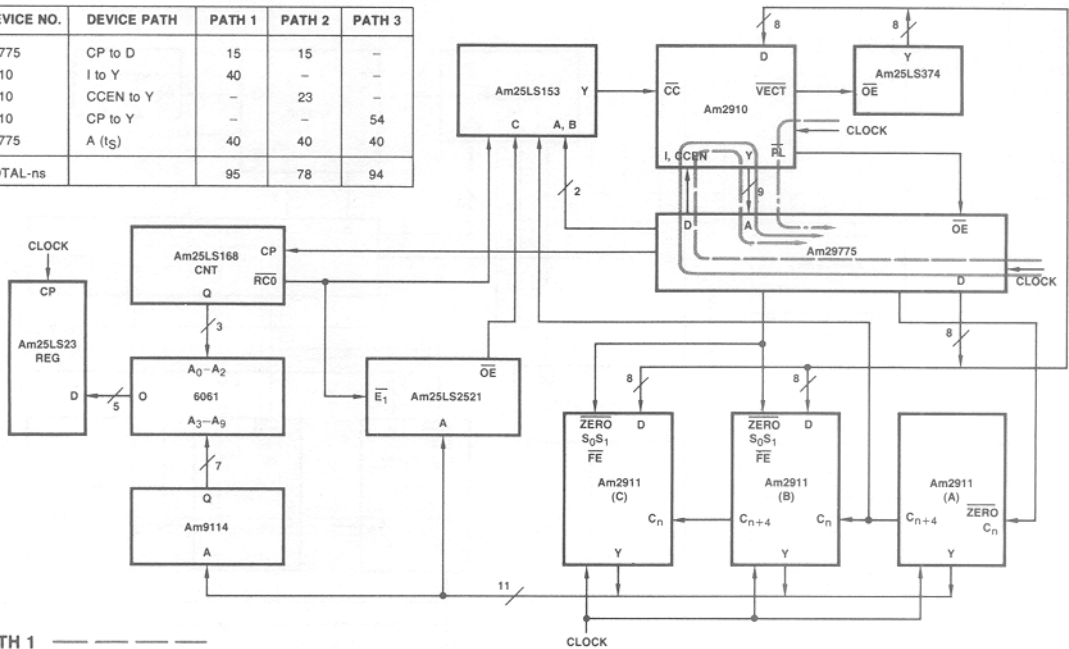


PATH 1 _____
PATH 2 _____
PATH 3 _____

MPR-493

d)

DEVICE NO.	DEVICE PATH	PATH 1
29775	CP to D	15
25LS153	A, B to Y	19
2910	CC to Y	21
29775	A (t ₅)	40
TOTAL-ns		95

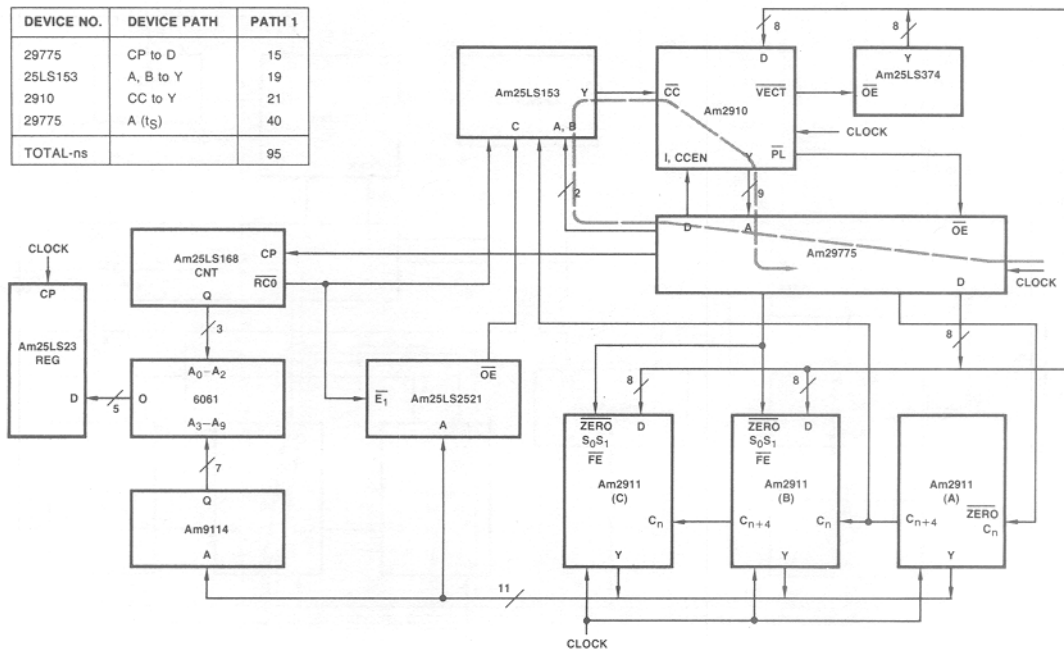


PATH 1 —————

MPR-494

Figure 25. (Cont.)

e)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2
29775	CP to D	15	15
2910	I to PL, VECT	27	27
29775	E ₁ to D	—	15
25LS374	OE to Y	14	—
2910	PC (t _S)	—	34
2911	D (t _S)	17	—
TOTAL-ns		73	91

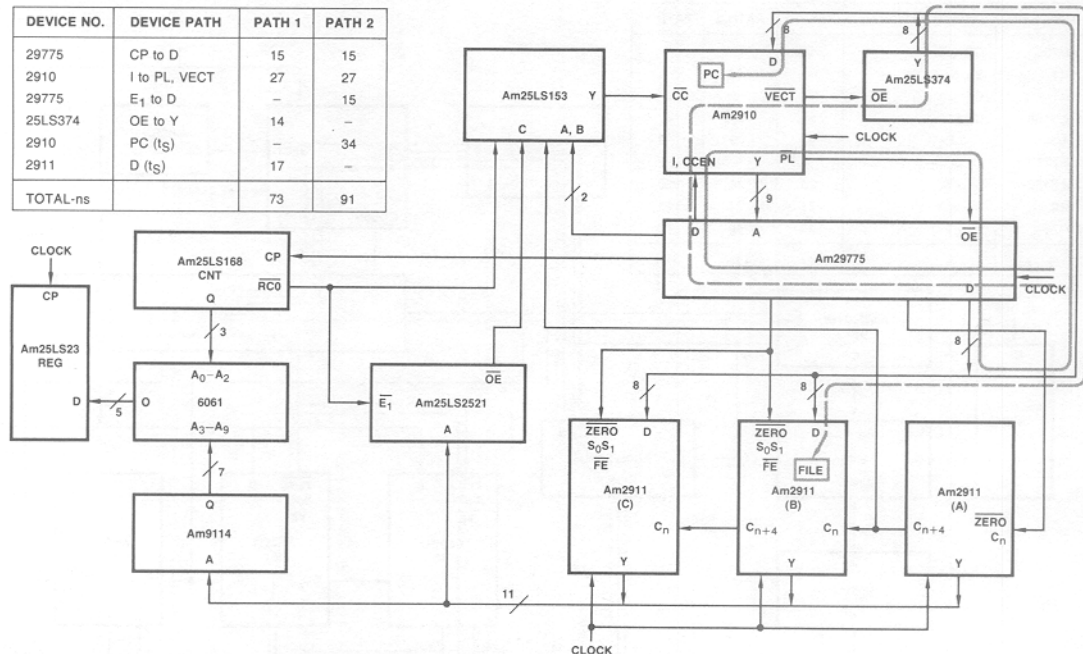


PATH 1 _____
PATH 2 _____

MPR-495

f)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
29775	CP to D	15	15	15
2911	ZERO to C_{n+4}	—	—	30
2911	C_n to C_{n+4}	—	9	—
25LS168	CP to RCO	19	—	—
25LS153	D to Y	20	20	20
2910	CC to Y	21	21	21
29775	A (I_S)	40	40	40
TOTAL-ns		115	105	126

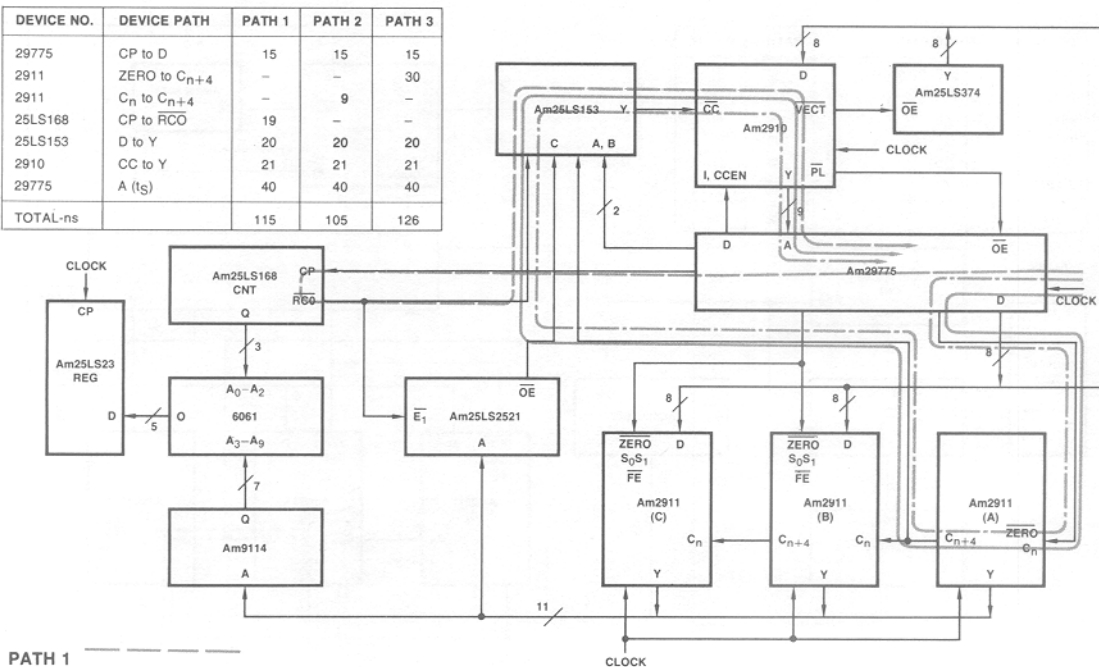

PATH 1 _____

PATH 2 _____


PATH 3 _____

MPR-496

Figure 25. (Cont.)

g)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
29775	CP to D	15	15	—
2911	S ₀ , S ₁ to Y	—	19	—
2911	CP to Y (S ₁ S ₀ = HL)	—	—	54
25LS168	CP to RCO	19	—	—
25LS2521	A to E ₀	—	9	9
25LS2521	E ₁ to E ₀	6	—	—
25LS153	D to Y	20	20	20
2910	CC to Y	21	21	21
29775	A (t _S)	40	40	40
TOTAL-ns		121	124	144

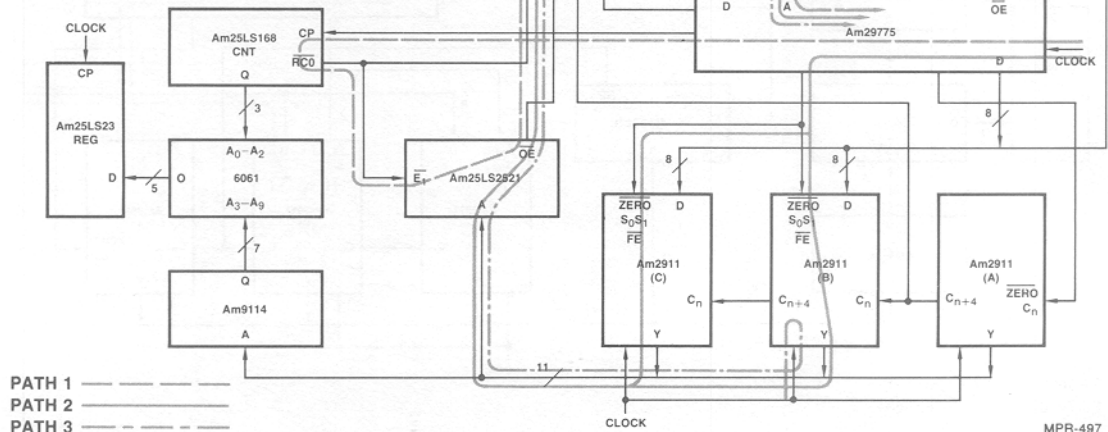

h)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2
2911	CP to Y (S ₁ S ₀ = HL)	39	—
2911	CP to C _{n+4} (S ₁ S ₀ = HL)	—	54
2911	C _n (t _S)	—	15
9114	A to D	150	—
6061	A to OUT	70	—
25LS23	D (t _S)	23	—
TOTAL-ns		282	69

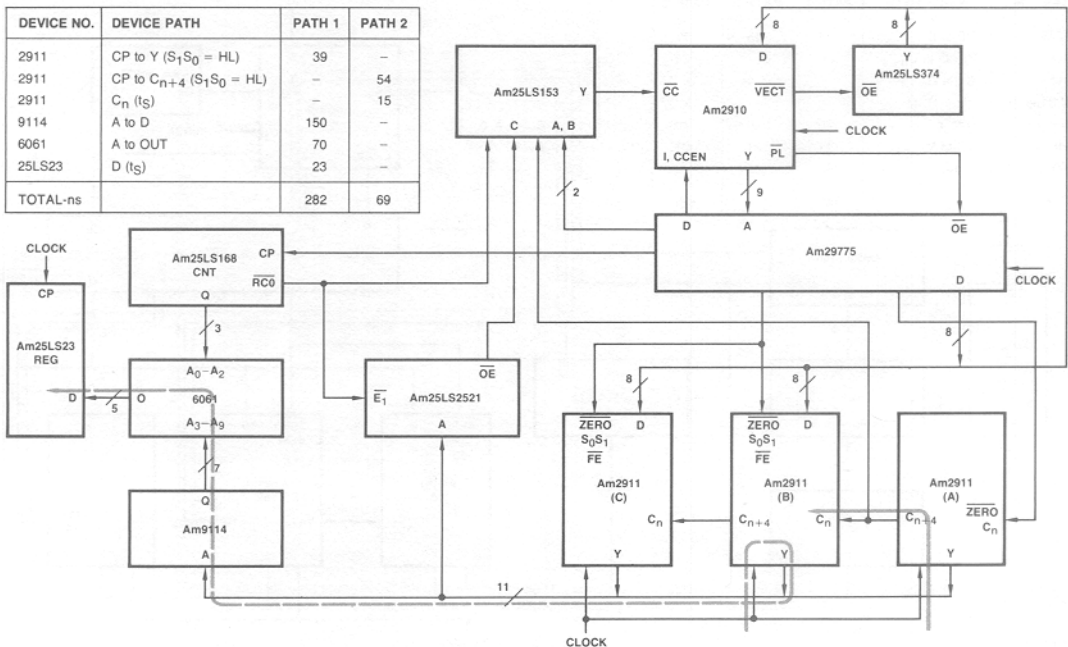


Figure 25. (Cont.)

i)

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
29775	CP to D	15	15	15
2910	I to PL	36	36	36
29775	E ₁ to D	15	—	—
25LS374	OE to Y	—	14	14
2911	D to Y	9	9	—
9114	A to D	150	150	—
6061	A to D	70	70	—
25LS23	t _S (D)	23	23	—
2911	t _S (D)	—	—	17
TOTAL-ns		318	317	82

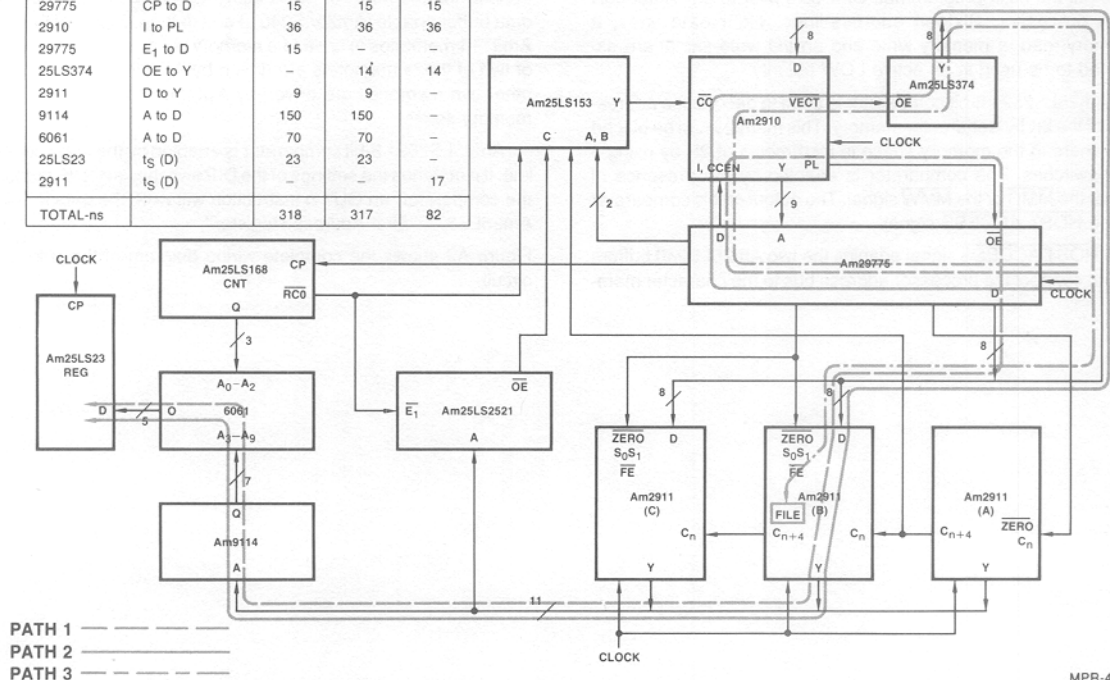


Figure 25. (Cont.)

SUMMARY

The Am2910 provides a powerful solution to the microprogram memory sequence control problem. The Am2910 is a fixed instruction set, 12-bit wide microprogram sequencer. In addition, the Am2909, Am2911, Am29811A and Am29803A provide another solution to the microprogram sequencing problem. These devices are bit slice oriented and provide more potential flexibility to the microprogram sequencing solution. All of these devices are particularly well suited for the high performance computer control unit and structured state machine designs using overlap fetch of the next microinstruction — also referred to as instruction-data-based microprogram architecture.

These Am2900 family microprogram control devices offer the highest performance LSI solution to the problem of microprogram control. They provide a number of conditional-branch source addresses as well as conditional jump-to-subroutine and conditional-return instructions. In addition, several techniques for timed and untimed looping are provided such that loops from one to several microinstructions can be executed. All of the devices described in this chapter are competitively priced and currently available. In addition, all of these devices are available with specifications guaranteed over the full commercial temperature range and power supply tolerance as well as the full military temperature range and power supply tolerance. All of these devices undergo 100% reliability assurance testing in compliance with MIL-STD-883.

APPENDIX A

Figure A1 shows the logic diagram of an interface circuit used to connect the microprogrammed CRT controller to any Am9080A type processor. Sixteen address-lines, eight data lines, a memory-read, a memory write and an I/O write signal are assumed to be used in an active LOW polarity.

An Am25LS2521 8-bit comparator is used to decode the addresses of the 2K by 8 character memory. This memory can be placed anywhere in the memory space in increments of 2K by using 5 DIP-switches. The comparator is enabled by the presence of either the $\overline{\text{MMR}}$ or the $\overline{\text{MMW}}$ signal. The output of this comparator is the $\overline{\text{HOST ACCESS}}$ signal.

The $\overline{\text{HOST ACCESS}}$ signal enables the two Am25LS240 buffers which connect the processor address bus to the character mem-

ory address bus. It also enables one half of an Am25LS241 buffer transferring the $\overline{\text{MMR}}$ or $\overline{\text{MMW}}$ active LOW signal to the proper data buffer enable (Am25LS240's) and to the $\overline{\text{WE}}$ pins of the four Am9114 memories in case of a memory write operation. The $\overline{\text{CS}}$ of two of these memories are driven by A_{10} while the $\overline{\text{CS}}$ of the other two memories are driven by A_{10} , thus forming a 2K by 8 memory space.

An Am25LS2521 8-bit comparator is enabled by the $\overline{\text{I/OW}}$ control line. If n matches the settings of the DIP switches at the B inputs of the comparator, an OUT n instruction will write the data into the Am25LS374 "First Address Register".

Figure A2 shows the complete wiring diagram of this interface circuit.

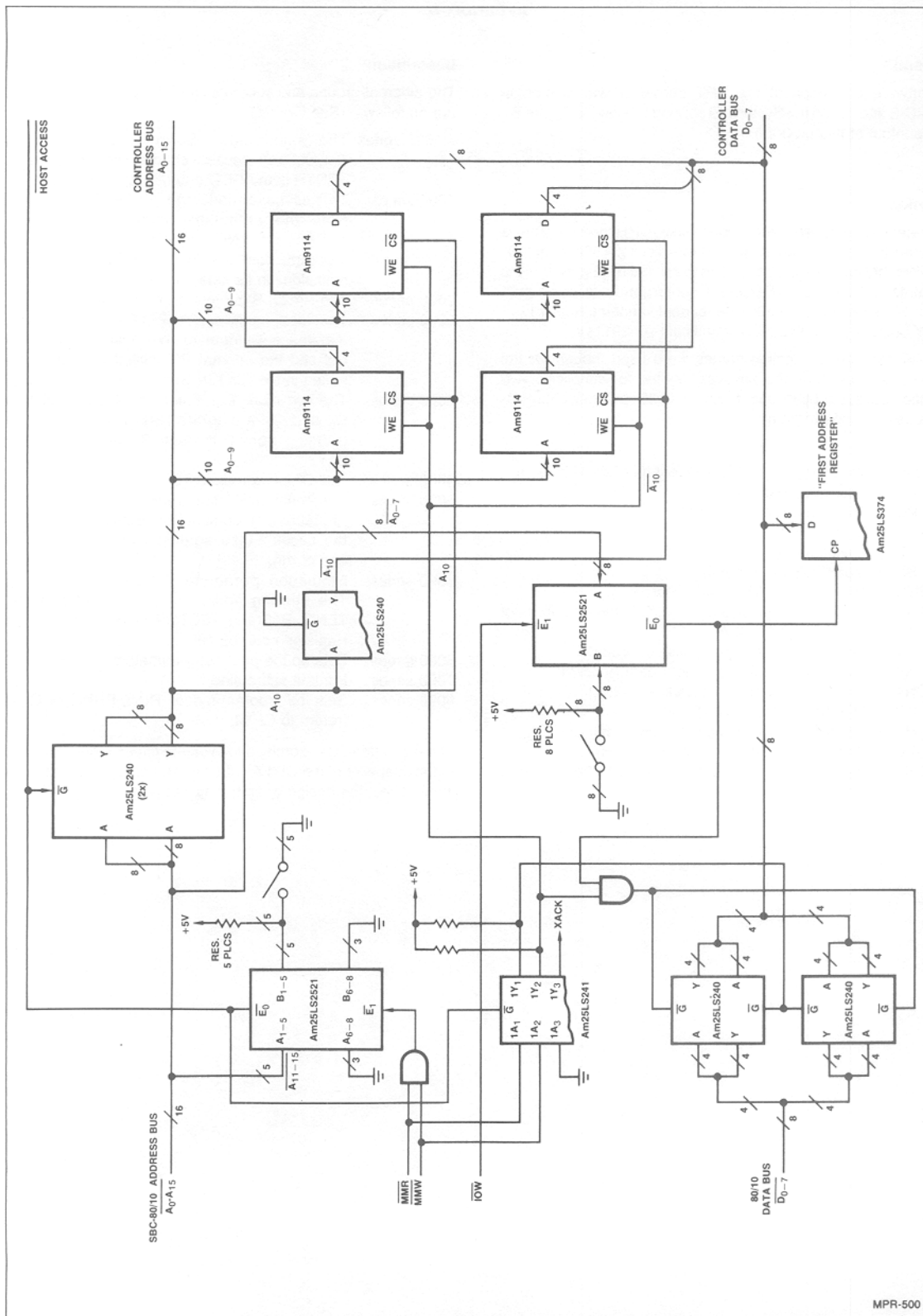


Figure A1. CRT Controller.

APPENDIX B

General

A software emulation of the CRT controller was written in BASIC-E and run on the System 29 support processor. Figure B1 is a printout of this program.

Notations

For reference purposes, each clock pulse (CP) in the program is numbered. The clocks are character-rate clocks. A subscript "10" signifies that this variable belongs to the Am2910 (e.g. R10 = the contents of the Am2910 Register Counter) and similarly a subscript 11 signifies the Am2911 dependent variables (e.g. Y11 = the Y outputs of the two more significant Am2911s).

Usually the normal function names were used though for the active LOW functions the bar was deleted for simplicity. A 0 signifies always a LOW and 1 signifies HIGH. Other abbreviations used in the program:

- MA = Microprogram Address (Y output of the Am2910)
- CA = Character Address
- PC = Program Counter (internal)
- R = Register (internal)
- F = File (internal)
- SP = Stack Pointer (internal)
- TENC = The Am25LS168 decade counter
- L4B = The 4 least significant bits of CA (the Y outputs of the less significant Am2911)
- CN = Carry-in into the less significant Am2911
- CN4 = Carry-out from the less significant Am2911
- CN4 = Carry-in to the next significant Am2911
- I10 = The Am2910 instruction
- HB = Horizontal Blanking signal (active HIGH)
- VB = Vertical Blanking signal (active HIGH)
- CPM = Maximum Clock Pulse (at which the program stops)

Description

The different groups and subroutines of the emulation program are as follows: (See Figure B1).

- <1000 series: The microcode. Subroutine 50 is the Am25LS168 decade counter clocking routine. TENTH is the RCO output of this device.
- 1000 series: This is essentially the Am2910 emulation. Note the definition of the two functions FNFAIL and FNPASS at the beginning of the program, compare to the Am2910 instruction definitions in its data sheet.
- 2000 series: The Am25LS153 multiplexer emulation.
- 2500 series: The less significant Am2911 emulation. Note that the only input to this device is ZEROL. CN and the internal PC (called L4B) are controlled in the CLOCK Subroutine (4000 series).
- 3000 series: The two more significant Am2911's emulation, S₀ and S₁ are treated as a single number (ranging from 0 through 3) and denoted by S11.
- 4000 series: The Clocking routine.
- 5000 series: The main emulation routine. It includes the Am25LS2521 comparator routine and checks the Clock Pulse against CPM to determine end of run.
- 5500 series: Emulation parameter setup (initialization). The starting and ending CP numbers, MA, TENC, R10 and VECTOR (The "First Address Register") can be set.
- 6000 series: Sets up the print-out parameters
- 7000 series: Printout subroutine
- 9000 series: Sets the program mode: RUN, PRINT or QUIT (return to CP/M)

The emulation was exercised to evaluate fifteen different performance aspects of the CRT Controller. The results indicated that in all cases, the design operated as desired.

```

REM
REV=12
PRINT REV
9000 REM      HEADER
      PRINT
      PRINT
      PRINT " *****"
      PRINT
      PRINT "      A MICROPROGRAMMED CRT CONTROLLER EMULATION"
      PRINT
      PRINT " *****"
      PRINT
      PRINT "
      PRINT "      BY MOSHE M. SHAVIT"
      PRINT "      ADVANCED MICRO DEVICES"
      PRINT "      FEBRUARY 27, 1978"
      PRINT
      PRINT
REM
      DIM F10(6)
      DEF      FNFAIL=CCEN=0 AND CC=1
      DEF      FNPASS=CCEN=1 OR CC=0
REM
REM
      GOTO 6000 REM      PROGRAM PARAMETERS (REMOVED REV 6)
REM
REM      <--REV 6
REM
9100 PRINT
      PRINT
      PRINT
      INPUT "R-UN, P-PRINT OR Q-UIT ";MODE$
      IF LEN(MODE$)=0 THEN GOTO 9100
      MODE=ASC(MODE$)-79
      IF MODE<1 OR MODE > 3 \
          THEN PRINT MODE$; " IS INVALID";\
              GOTO 9100
      ON MODE GOTO 9110,9120,9130
REM
9120 RETURN
REM
9130 REM      RUN
      PRINT
      INPUT "PUT RESULTS ON FILE (0 IF DIRECT PRINTOUT)= ";WFILES
      PRINT "CP= ";CP;"MA= ";MA;"VECTOR= ";VECTOR;\
          "CPM= ";CPM;"ROW= ";24-R10
      INPUT "INITIALIZE (Y OR N; CP,MA=0 IF N)";S$
      IF S$="Y" \
          THEN GOSUB 5500 \ REM      INIT.
          ELSE CP=0 : MA=0
      IF WFILES="0" \
          THEN GOTO 6010 \ REM DIRECT PRINTOUT
          ELSE FILE WFILES : GOTO 5000 REM MAIN
REM
9110 REM      PRINT
      PRINT
      INPUT "GET RESULTS FROM FILE=";RFILES
      FILE RFILES
REM
6000 REM PRINT PARAMETERS
      PRINT
6010 PRINT "OUTPUT FORMATS:"

```

Figure B1.

```

PRINT "      A=CP AND CA ONLY"
PRINT "      B=CP,CA,HB,VB,MA"
PRINT "      C=CP,CA,MA,TENC,R10"
PRINT "      D=ALL"
PRINT
INPUT "FORMAT=";FORMAT$
IF LEN(FORMAT$)=0 THEN GOTO 6010
IF ASC(FORMAT$)<65 OR ASC(FORMAT$)>68 \
    THEN PRINT FORMAT$;" IS ILLEGAL" : \
        GOTO 6010
PRINT

REM
6020 REM
IF WFILES NE "0" \
    THEN CONTROL$="A" : \
        GOTO 6030
PRINT "CLOCK CONTROL"
PRINT "      A=CONTINUOUS"
PRINT "      B=STEP"
INPUT "CONTROL=";CONTROL$
IF LEN(CONTROL$)=0 THEN GOTO 6020
IF ASC(CONTROL$)<65 OR ASC(CONTROL$)>66 \
    THEN PRINT CONTROL$;" IS ILLEGAL" : \
        GOTO 6020
PRINT

REM
6030 PRINT "OUTPUT CONTROL"
PRINT "      A=AT EACH CP"
PRINT "      B=AT EVERY N-TH CP"
PRINT "      C=MANUAL CONTROL"
PRINT "      D=STARTING AT CPS AT EVERY CP"
PRINT "      E=STARTING AT CPS AT EVERY N-TH CP"
INPUT "OUTPUT=";OUTPUT$
IF LEN(OUTPUT$)=0 THEN GOTO 6030
IF ASC(OUTPUT$)<65 OR ASC(OUTPUT$)>69 \
    THEN PRINT OUTPUT$;" IS ILLEGAL" : \
        GOTO 6030
O.CTL=ASC(OUTPUT$)-64
ON O.CTL GOTO 6090,6032,6090,6034,6036
6032 INPUT "N=";N
M=0
GOTO 6090
6034 INPUT "CPS=";CPS
GOTO 6090
6036 INPUT "CPS=";CPS
INPUT "N=";N
M=0
GOTO 6090

REM
6090 FORMAT = ASC(FORMAT$)-64
ON FORMAT GOSUB 6190,6300,6200,6100
IF WFILES="0" THEN GOTO 5000 REM MAIN

REM
6900 PRINT
IF END #1 THEN 6910
FOR I=1 TO 2 STEP 0 REM DO UNTIL END OF FILE
READ #1; CP,R10,F1,SP10,PC10,CA,MUX,CC,CCEN,MA,TENC,\
    CN4,F11,HB,VB
F10(SP10)=F1
GOSUB 7000 REM PRINT
GOSUB 5200 REM ESCAPE (REV 7)
IF S=155 THEN PRINT:PRINT "ABORTED AT ";CP : GOTO 6910
NEXT I

```

Figure B1 (Cont.)

```

REM
6910      CLOSE 1
          OUT 100,12      REM      PRINTER PAGE EJECT (REV 7)
          GOTO 9100

REM
6100      PRINT
          PRINT "CP","R10","F10","SP10","PC10"
          PRINT "CA","MUX","CC","CCEN","MA"
          PRINT "TENC","CN4","F11","HB","VB"
          PRINT
6190      RETURN

REM
6200      PRINT
          PRINT "CLOCK","CHAR.ADDR","2910 REG.","LINE CNTR.","NEXT MA"
          RETURN

REM
6300      PRINT
          PRINT "CLOCK","CHAR.ADDR","H.BLANKING","V.BLANKING","NEXT MA"
          RETURN

REM
REM
7000      REM      PRINT SUBROUTINE
          ON O.CTL GOTO 7010,7005,7002,7003,7004

REM
7002      INPUT "OUTPUT (Y OR N)";S$
          IF S$="Y" \
              THEN      GOTO 7010 \
              ELSE      RETURN

REM
7003      IF CP<CPS THEN RETURN ELSE GOTO 7010

REM
7004      IF CP<CPS THEN RETURN ELSE GOTO 7005

REM
7005      M=M+1
          IF M=N THEN M=0 : GOTO 7010 ELSE RETURN

REM
7010      ON FORMAT GOTO 7100,7200,7300,7400

REM
7100      PRINT "CP= ";CP,"CA= ";CA
          RETURN

REM
7200      IF HB=0 THEN HB$="L" ELSE HB$="      H"
          IF VB=0 THEN VB$="L" ELSE VB$="      H"
          PRINT CP,CA,HB$,VB$,MA
          RETURN

REM
7300      PRINT
          PRINT CP,CA,R10,TENC,MA
          RETURN

REM
7400      PRINT
          PRINT CP,R10,F10(SP10),SP10,PC10
          PRINT CA,MUX,CC,CCEN,MA
          PRINT TENC,CN4,F11,HB,VB
          RETURN

REM
REM
5000      REM      MAIN ROUTINE
          REM
          GOSUB 4000      REM      CLOCK
          REM      FETCH MICROCODE
          ON MA+1 GOSUB 30,2,3,4,5,6,7,8,9,10,11,12,13,14,15,16,17,18,19,20,21,22
          GOSUB 2500      REM      2911L
          GOSUB 3000      REM      2911H

```

Figure B1 (Cont.)

```

CA=Y11*16+L4B      REM      CHARACTER ADDRESS
                    REM      COMPARATOR NEXT
IF Y11=120 AND TENTH=0 \      REM REV 8
    THEN      COMP=0 \
    ELSE      COMP=1
GOSUB 2000      REM      MUX
GOSUB 1000      REM      2910
REM
REV 6
IF WFILE$="0" THEN GOSUB 7000 \ REM DIRECT PRINTOUT
    ELSE PRINT #1;CP,R10,F10(SP10),SP10,PC10,CA,MUX,\
        CC,CCEN,MA,TENC,CN4,F11,HB,VB
IF CONTROL$="B" THEN INPUT S$      REM      SINGLE STEP
REM      CHECK END OF RUN
GOSUB 5200      REM      ESCAPE (REV 7)
IF S=155 THEN PRINT:PRINT "ABORTED AT ";CP : GOTO 5100
IF CP<CPM THEN GOTO 5000      REM      REPEAT MAIN

REM
5100      IF WFILE$ NE "0" THEN CLOSE (1)
OUT 100,12      REM PRINTER PAGE EJECT (REV 7)
GOTO 9100

REM
REM      5200 SUB REV 7
5200      REM      ESCAPE SUBROUTINE
S=INP(97)
S=INT(S/2)
S=S/2-INT(S/2)
IF S NE 0 THEN S = INP(96)
RETURN

REM
5500      REM      INITIALIZATION
PRINT
SP10=1
PRINT "MA= ";MA
5505      INPUT "NEW MA (Y OR N)";S$
IF S$="N" THEN GOTO 5510
INPUT "MA=(0<=MA<22)";MA
MA=INT(MA)
IF MA<0 OR MA>21 \
    THEN      PRINT MA;" IS ILLEGAL" : \
        GOTO 5505
IF MA=0 THEN TENC=0 : HB=1 : TENTH=1

REM
5510      PRINT
PRINT "VECTOR= ";VECTOR
5515      INPUT "NEW VECTOR (Y OR N)";S$
IF S$="N" THEN GOTO 5520
INPUT "VECTOR=(0<=VECTOR<120)";VECTOR
VECTOR=INT(VECTOR)
IF VECTOR<0 OR VECTOR>119 \
    THEN      PRINT VECTOR;" IS ILLEGAL" : \
        GOTO 5515

REM
5520      PRINT
PRINT "CP= ";CP
INPUT "NEW CP (Y OR N) ";S$
IF S$="N" THEN GOTO 5530
5525      INPUT "CP(>=0)= ";CP
CP=INT(CP)
IF CP<0 THEN PRINT CP;" IS ILLEGAL" : GOTO 5525

REM
5530      PRINT
PRINT "CPM= ";CPM
5535      INPUT "NEW CPM (Y OR N)";S$
IF S$="N" THEN GOTO 5540

```

Figure B1. (Cont.)

```

INPUT "CPM=(CP+1<CPM)";CPM
CPM=INT(CPM)
IF CPM<CP+1 THEN PRINT CPM;" IS ILLEGAL";"CP= ";CP :GOTO 5535

REM
5540 PRINT
PRINT "TENC= ";TENC
IF MA=0 THEN GOTO 5550
5545 INPUT "NEW TENC (Y OR N)";S$
IF S$="N" THEN GOTO 5550
INPUT "TENC=(0<=TENC<10)";TENC
TENC=INT(TENC)
IF TENC<0 OR TENC>9 \
    THEN PRINT TENC;" IS ILLEGAL" :\
        GOTO 5545
IF TENC=9 THEN TENTH=0 ELSE TENTH=1

REM
5550 PRINT
PRINT "R10= ";R10
5555 INPUT "NEW R10 (Y OR N)";S$
IF S$="N" THEN GOTO 5560
INPUT "R10 (0<=R10<25)";R10
R10=INT(R10)
IF R10<0 OR R10>24 THEN PRINT R10;" IS ILLEGAL" : GOTO 5555

REM
5560 REM
RETURN

REM
REM
REM
30 I10=6
CCEN=0
MUX=3
S11=3
FE=0
ZEROH=1
ZEROL=0
CN=0
HB=1 REM REV 2
VB=0
PL=0
RETURN

REM
2 I10=12
S11=0
FE=1
ZEROH=1
ZEROL=0
CN=0
HB=1 REM REV 2
VB=0
PL=23
RETURN

REM
3 I10=14
S11=2
FE=1
ZEROH=1
ZEROL=0
CN=1
HB=1 REM REV 2
VB=0
RETURN

REM
4 I10=3

```

Figure B1 (Cont.)

	CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 HB=0 VB=0 PL=3 RETURN	REM 9	I10=1 CCEN=0 MUX=0 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 GOSUB 50 REM TENC VB=0 PL=12 RETURN	
REM 5	I10=3 CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 HB=0 VB=0 PL=4 RETURN	REM 10	I10=1 CCEN=0 MUX=2 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 GOSUB 50 VB=0 PL=21 RETURN	
REM 6	I10=3 CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 HB=0 VB=0 PL=5 RETURN	REM 11	I10=3 CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 GOSUB 50 VB=0 PL=10 RETURN	
REM 7	I10=3 CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 HB=0 VB=0 PL=6 RETURN	REM 12	I10=3 CCEN=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 GOSUB 50 VB=0 PL=2 RETURN	
REM 8	I10=3 CCEN=0 MUX=1 S11=0 FE=1 ZEROH=1 ZEROL=1 CN=1 HB=0 VB=0 PL=7 RETURN	REM 13	I10=9 S11=0 FE=0 ZEROH=1 ZEROL=1 CN=1 GOSUB 50 VB=0 PL=20 RETURN	REM REV 5
		REM 14	I10=6 CCEN=0 MUX=3 S11=3	

Figure B1 (Cont.)

	FE=0	REM	REV 10
	ZEROH=1		
	ZEROL=0		
	GOSUB 50		
	VB=1		
	RETURN		
REM 15	I10=12		
	S11=0	REM	REV 10
	FE=1	REM	REV 10
REM	ZEROH=1		
	ZEROL=1	REM	REMOVED REV 10
	GOSUB 50		
	VB=1		
	PL=119		
	RETURN		
REM 16	I10=4		
	CCEN=0		
	MUX=3		
	S11=0		
	FE=1		
	ZEROH=1		
	ZEROL=1		
	CN=1		
	GOSUB 50		
	VB=1		
	RETURN		
REM 17	I10=3		
	CCEN=0		
	MUX=1		
	S11=0		
	FE=1		
	ZEROH=1		
	ZEROL=1		
	CN=1		
	GOSUB 50		
	VB=1		
	PL=16		
	RETURN		
REM 18	I10=8		
	S11=0		
	FE=1		
	ZEROH=1		
	ZEROL=1		
	CN=1		
	GOSUB 50		
	VB=1		
	RETURN		
REM 19	I10=12		
	S11=0		
	FE=1		
	ZEROH=1		
	ZEROL=1		
	CN=1		
	GOSUB 50		
	VB=1		
	PL=23		
	RETURN		
REM 20	I10=10		

Figure B1 (Cont.)

```

CCEN=1
S11=0
FE=1
ZEROH=1
ZEROL=1
CN=1
GOSUB 50
VB=1
RETURN

REM
21    I10=10
      CCEN=1
      S11=0
      FE=1
      ZEROH=1
      ZEROL=1
      CN=1
      GOSUB 50
      VB=0
      RETURN

REM
22    I10=10
      CCEN=1
      FE=0          REM      REV 9
      ZEROH=0
      ZEROL=1      REM      REV 9
      CN=1
      GOSUB 50
      VB=0
      RETURN

REM
50    REM TEN-LINE-COUNTER CLOCKING SUBROUTINE
      IF HB=1 THEN RETURN
      HB=1
      TENC=TENC+1
      IF TENC=9 THEN TENTH=0 ELSE TENTH=1
      IF TENC=10 THEN TENC=0
      RETURN

REM
1000  PUSH AND POP SUBROUTINES REMOVED REV 3
      REM      2910 INSTRUCTIONS SUBROUTINE
      ON I10+1 GOTO 1100,1110,1120,1130,1140,1150,1160,1170,1180, \
      1190,1200,1210,1220,1230,1240,1250

REM
1100  REM      JZ
      MA=0          REM      2910 Y
      SP10=0        REM      2910 STACK POINTER (=0 REV 3)
      RETURN

REM
1110  REM      CJS
      IF FNFAIL \
      THEN          MA=PC10 \
      ELSE          MA=PL : \
      PUSH=1        REM      REV 3

      RETURN

REM
1120  REM      JMAP
      PRINT "JMAP NOT PROGRAMMED"
      RETURN

REM
1130  REM      CJP
      IF FNFAIL \
      THEN          MA=PC10 \
      ELSE          MA=PL

      RETURN

```

Figure B1 (Cont.)

```

REM
1140 REM      PUSH
      IF FNPASS THEN R10=PL      REM      LOAD COUNTER
      MA=PC10
      PUSH=1                     REM      REV 3
      RETURN

REM
1150 REM      JSRP
      PRINT "JSRP NOT PROGRAMMED"
      RETURN

REM
1160 REM      CJV
      IF FNFAIL \
          THEN      MA=PC10 \
          ELSE      MA=VECTOR
      RETURN

REM
1170 REM      JRP
      IF FNFAIL \
          THEN MA=R10 \
          ELSE MA=PL
      RETURN

REM
1180 REM      RFCT
      IF R10=0 \
          THEN      MA=PC10 :\
                   POP=1 \
          ELSE      MA=F10(SP10) :\
                   R10=R10-1
      RETURN

REM
1190 REM      RPCT
      IF R10=0 \
          THEN      MA=PC10 \
          ELSE      MA=PL :\
                   R10=R10-1
      RETURN

REM
1200 REM      CRTN
      IF FNFAIL \
          THEN      MA=PC10 \
          ELSE      MA=F10(SP10) :\
                   POP=1
      RETURN
      REM      REV 3

REM
1210 REM      CJPP
      PRINT "CJPP NOT PROGRAMMED"
      RETURN

REM
1220 REM      LDCT
      R10=PL
      MA=PC10
      RETURN

REM
1230 REM      LOOP
      IF FNFAIL \
          THEN      MA=F10(SP10) \
          ELSE      MA=PC10 :\
                   POP=1
      RETURN
      REM REV 3

REM
1240 REM      CONT
      MA=PC10
      RETURN

```

Figure B1. (Cont.)

```

REM
1250 REM      TWB
PRINT "TWB NOT PROGRAMMED"
RETURN

REM
REM
2000 REM      MUX SUBROUTINE
ON MUX+1 GOTO 2100,2200,2300,2400

REM
2100 IF TENTH=0 \
      THEN CC=0 \
      ELSE CC=1
RETURN

REM
2200 IF CN4=0 \
      THEN CC=0 \
      ELSE CC=1
RETURN

REM
2300 IF COMP=0 \
      THEN CC=0 \
      ELSE CC=1
RETURN

REM
2400 CC=1
RETURN

REM
REM
2500 REM      LEAST SIGNIFICANT 2911 (2911L) SUBROUTINE
IF ZEROL=0 THEN L4B=0
RETURN

REM
REM
REM
REM
3000 REM      MORE SIGNIFICANT 2911S (2911H) SUBROUTINE
ON S11+1 GOSUB 3100,3200,3300,3400
IF ZEROH=0 THEN Y11=0
RETURN

REM
3100 Y11=PC11
RETURN

REM
3200 Y11=R11
RETURN

REM
3300 Y11=F11
RETURN

REM
3400 IF I10=6 \
      THEN Y11=VECTOR \
      ELSE Y11=PL
RETURN

REM
REM
4000 REM      CLOCK SUBROUTINE
PC10=MA+1 REMOVED REV 4
IF CN=1 THEN L4B=L4B+1
IF L4B>15 THEN L4B=0 : CN4=1 ELSE CN4=0
IF CN4=1 \
      THEN PC11=Y11+1 \
      ELSE PC11=Y11
IF FE=0 THEN F11=PC11
REM
<--REV 3

```

Figure B1 (Cont.)

```

IF PUSH=1 \
    THEN SP10=SP10+1 :\
          F10(SP10)=PC10 :\
          PUSH=0
IF SP10>4 \
    THEN PRINT "2910 STACK FULL " :\
          SP10=3
IF POP=1 \
    THEN SP10=SP10-1 :\
          POP=0
IF SP10<0 \
    THEN PRINT "POP EMPTY FILE? ";CP :\
          SP10=0
REM REV 3 -->
PC10=MA+1 REM REV 4
CP=CP+1
RETURN
REM
REM

```

Figure B1 (Cont.)

APPENDIX C

A simple circuit was designed to accommodate five different display formats and also to comply with the European 50Hz TV standard. Figure C1 is the circuit diagram of this additional circuit.

The following parameters change when the format is changed:

- 1) The number of characters/line.
- 2) The number of lines/frame.
- 3) The number of characters to display (i.e., the address of the last character).
- 4) The line frequency and therefore the dot frequency.

The number of characters/line is counted by the least significant Am2911 sequencer via the microcode. Therefore, the microcode can be changed to change the number of characters/line. The number of lines/frame is counted by a constant, loaded into the

Am2910 internal counter by the microcode. The microcode can be changed to vary the number of lines/frame.

The scan is reinitialized to zero when the last address +1 is attained. U₉ (Am25LS2521) detects this address by comparing bits A₄ through A₁₀ of the character address bus to a constant supplied to its B inputs. A table listing these constants is shown in Figure C1. By setting the DIP switches according to that table, the character scan will reinitialize correctly. The same constant is routed through one half of an Am25LS240 (U₂₄) to the internal data bus. At microprogram address zero, a JUMP MAP instruction enables these outputs thereby putting a starting address on the bus according to the table in Figure C1.

The microprogram is shown on Figure C2.

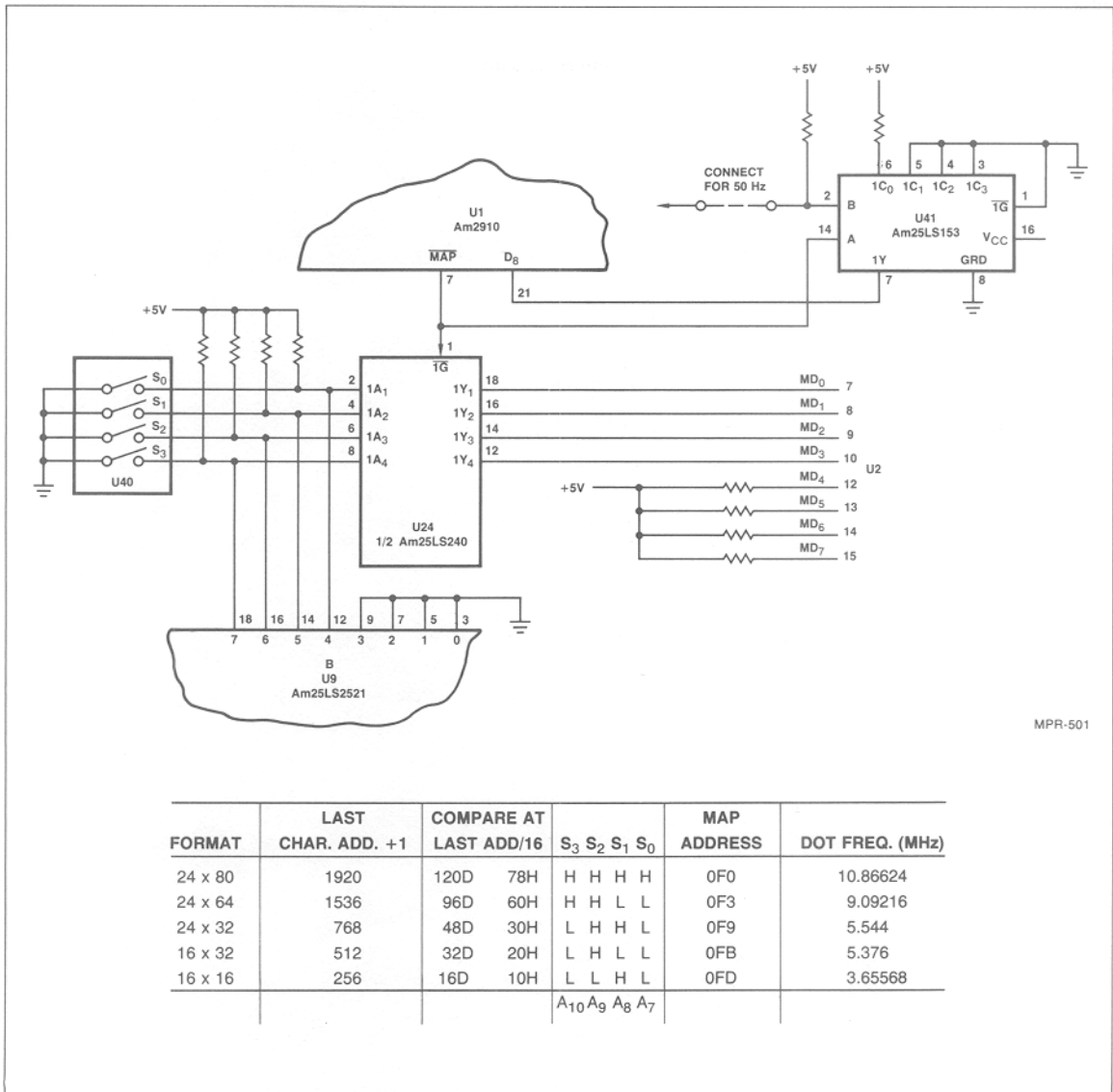


Figure C1.

```

A>TYPE CRT.DEF
;
;CRT DEFINITION FILE
;BY MCSHE M. SHAVIT
;REV 0 3/6/78
;
TITLE    CRT CONTRLLER --DEFINITIONS
WORD     24
;
FE:      DEF      1VB#1,23X
ZEROH:   DEF      1X,1VB#1,22X
S11:     DEF      2X,2V%:Q#,20X
I10:     DEF      4X,4VH#,16X
CN:      DEF      9X,1VB#1,14X
ZERCI:   DEF      10X,1VB#1,13X
VB:      DEF      11X,1VB#0,12X
HB:      DEF      12X,1VB#0,11X
CCEN:    DEF      13X,1VB#,10X
MUX0:    DEF      14X,B#00,8X
MUX1:    DEF      14X,B#10,8X
MUX2:    DEF      14X,B#01,8X
MUX3:    DEF      14X,B#11,8X
PL:      DEF      16X,8V%:
;
L:       EQU      B#0
H:       EQU      B#1
;
COUNT:  DEF      B#1,B#1,B#00,5X,B#1,B#1,B#0,B#0,1X,2X,8X
COUNTH:  DEF      B#1,B#1,B#00,5X,B#1,B#1,B#0,B#1,1X,2X,8X
COUNTV: DEF      B#1,B#1,B#00,5X,B#1,B#1,B#1,B#1,1X,2X,8X
;
END

A>

```

Figure C2. AMDASM Definition and Assembly Files for the CRT Controller.

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

;CPT CONTROLLER MICROPROGRAM
;
;BY MOSHE M. SHAVIT
;REV 2 5/3/78
;
;
0000      I10 H#2 ;JUMP MAP
;
;      24 ROWS 80 CHARACTERS 60 F/S
;
;
0001 S2480: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0002      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
0003 M2480: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0004      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0005      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0006      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0007      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0008      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0009      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2480
000A      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
000B      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
000C      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2480
000D T2480: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOP
ACK
000E      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
000F      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#146
0010      I10 H#4 & CCEN L & MUX3 & COUNTV
0011      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0012      I10 H#8 & COUNTV
0013      I10 H#C & COUNTV & PL D#23
0014      I10 H#A & CCEN H & COUNTV
;
0015 GOBACK: I10 H#A & CCEN H & COUNTH
0016 LASTA: I10 H#A & CCEN H & FE L & ZEROH L & ZEROL & CN H & HB H & VB
;
;
;      24 ROWS 64 CHARACTERS 60 F/S
;
;
0017 S2464: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0018      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
0019 M2464: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
001A      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
001B      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
001C      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
001D      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
001E      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2464
001F      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0020      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
0021      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2464
0022 T2464: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOP
ACK
0023      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
0024      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#122
0025      I10 H#4 & CCEN L & MUX3 & COUNTV
0026      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0027      I10 H#8 & COUNTV

```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```
002E      I10 H#C & COUNTV & PL D#23
0029      I10 H#A & CCEN H & COUNTV
```

```
24 ROWS 32 CHARACTERS 60 F/S
```

```
002A S2432: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
002B      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
002C M2432: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
002D      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
002E      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
002F      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2432
0030      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0031      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
0032      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2432
0033 T2432: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
0034      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
0035      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#74
0036      I10 H#4 & CCEN L & MUX3 & COUNTV
0037      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0038      I10 H#8 & COUNTV
0039      I10 H#C & COUNTV & PL D#23
003A      I10 H#A & CCEN H & COUNTV
```

```
16 ROWS 32 CHARACTERS 60 F/S
```

```
003B S1632: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
003C      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#15
003D M1632: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
003E      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
003F      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0040      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T1632
0041      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0042      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
0043      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M1632
0044 T1632: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
0045      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
0046      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#250
0047      I10 H#4 & CCEN L & MUX3 & COUNTV
0048      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0049      I10 H#8 & COUNTV
004A      I10 H#C & COUNTV & PL D#48
004B      I10 H#4 & CCEN L & MUX3 & COUNTV
004C      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
004D      I10 H#E & COUNTV
004E      I10 H#C & COUNTV & PL D#15
004F      I10 H#A & CCEN H & COUNTV
```

```
16 ROWS 16 CHARACTERS 60 F/S
```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

0050 S1616: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0051 I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#15
0052 M1616: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0053 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0054 I10 H#1 & CCEN L & MUX0 & COUNTH & PL T1616
0055 I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0056 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0057 I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M1616
0058 T1616: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
0059 I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
005A I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#203
005B I10 H#4 & CCEN L & MUX3 & COUNTV
005C I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
005D I10 H#8 & COUNTV
005E I10 H#C & COUNTV & PL D#15
005F I10 H#A & CCEN H & COUNTV
;
00F0 ORG H#0F0 ;24*80
00F0 I10 H#3 & CCEN H & PL S2480
;
;
00F3 ORG H#0F3 ;24*64
00F3 I10 H#3 & CCEN H & PL S2464
;
;
00F9 ORG H#0F9 ;24*32
00F9 I10 H#3 & CCEN H & PL S2432
;
;
00FB ORG H#0FB ;16*32
00FB I10 H#3 & CCEN H & PL S1632
;
;
00FD ORG H#0FD ;16*16
00FD I10 H#3 & CCEN H & PL S1616
;
;
;
;50 F/S ROUTINES
;
0100 ORG H#100
;
;
; 24 ROWS 80 CHARACTERS 50 F/S
;
;
0100 S2480E: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0101 I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
0102 M2480E: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0103 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0104 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0105 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0106 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0107 I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0108 I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2480E
0109 I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
010A I10 H#3 & CCEN L & MUX1 & COUNT & PL $
010B I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2480E
010C T2480E: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK

```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

010D      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
010E      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#200 ;ITERATES
201 TIMES
010F      I10 H#4 & CCEN L & MUX3 & COUNTV
0110      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0111      I10 H#8 & COUNTV
;
0112      I10 H#C & COUNTV & PL D#239
0113      I10 H#4 & CCEN L & MUX3 & COUNTV
0114      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0115      I10 H#8 & COUNTV
;
0116      I10 H#C & COUNTV & PL D#23
0117      I10 H#A & CCEN H & COUNTV
;
;
;
;
24 ROWS 64 CHARACTERS 50 F/S
;
;
;
;
0118 S2464E: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0119      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
011A M2464E: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
011B      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
011C      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
011D      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
011E      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
011F      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2464E
0120      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0121      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
0122      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2464E
0123 T2464E: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
0124      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
0125      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#200
0126      I10 H#4 & CCEN L & MUX3 & COUNTV
0127      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0128      I10 H#8 & COUNTV
;
0129      I10 H#C & COUNTV & PL D#167 ;369
012A      I10 H#4 & CCEN L & MUX3 & COUNTV
012B      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
012C      I10 H#8 & COUNTV
;
012D      I10 H#C & COUNTV & PL D#23
012E      I10 H#A & CCEN H & COUNTV
;
;
;
;
24 ROWS 32 CHARACTERS 50 F/S
;
;
;
;
012F S2432E: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0130      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#23
0131 M2432E: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0132      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0133      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0134      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T2432E
0135      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0136      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $

```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

0137      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M2432E
0138 T2432E: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
0139      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
013A      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#224
013B      I10 H#4 & CCEN L & MUX3 & COUNTV
013C      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
013D      I10 H#8 & COUNTV
013E      I10 H#C & COUNTV & PL D#23
013F      I10 H#A & CCEN H & COUNTV
;
;
;
;
16 ROWS 32 CHARACTERS 50 F/S
;
;
;
;
0140 S1632E: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0141      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#15
0142 M1632E: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0143      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0144      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0145      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T1632E
0146      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
0147      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
0148      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M1632E
0149 T1632E: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
014A      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
014B      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#250
014C      I10 H#4 & CCEN L & MUX3 & COUNTV
014D      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
014E      I10 H#8 & COUNTV
014F      I10 H#C & COUNTV & PL D#223 ;475
0150      I10 H#4 & CCEN L & MUX3 & COUNTV
0151      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0152      I10 H#8 & COUNTV
0153      I10 H#C & COUNTV & PL D#15
0154      I10 H#A & CCEN H & COUNTV
;
;
;
;
16 ROWS 16 CHARACTERS 50 F/S
;
;
;
;
0155 S1616E: I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ CN L & HB H & VB
0156      I10 H#C & S11 0 & FE & ZEROH & ZEROL L & CN L & HB H &
/VB & PL D#15
0157 M1616E: I10 H#E & S11 2 & FE & ZEROH & ZEROL L & CN & HB H & VB
0158      I10 H#3 & CCEN L & MUX1 & COUNT & PL $
0159      I10 H#1 & CCEN L & MUX0 & COUNTH & PL T1616E
015A      I10 H#1 & CCEN L & MUX2 & COUNTH & PL LASTA
015B      I10 H#3 & CCEN L & MUX1 & COUNTH & PL $
015C      I10 H#3 & CCEN H & S11 0 & FE & ZEROH & HB H & VB & PL M1616E
015D T1616E: I10 H#9 & S11 0 & FE L & ZEROH & ZEROL & CN H & HB H & VB & PL GOB
ACK
015E      I10 H#6 & CCEN L & MUX3 & S11 3 & FE L & ZEROH & ZEROL L &
/ HB H & VB H
015F      I10 H#C & S11 0 & FE & ZEROH & HB H & VB H & PL D#200
0160      I10 H#4 & CCEN L & MUX3 & COUNTV
0161      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0162      I10 H#8 & COUNTV

```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

;
0163      I10 H#C & COUNTV & PL D#121      ;323
0164      I10 H#4 & CCEN L & MUX3 & COUNTV
0165      I10 H#3 & CCEN L & MUX1 & COUNTV & PL $
0166      I10 H#8 & COUNTV
;
0167      I10 H#C & COUNTV & PL D#15
0168      I10 H#A & CCEN H & COUNTV
;
01F0      ORG      H#1F0      ;24*80
01F0      I10 H#3 & CCEN H & PL S2480E
;
;
01F3      ORG      H#1F3      ;24*64
01F3      I10 H#3 & CCEN H & PL S2464E
;
;
01F9      ORG      H#1F9      ;24*32
01F9      I10 H#3 & CCEN H & PL S2432E
;
;
01FB      ORG      H#1FB      ;16*32
01FB      I10 H#3 & CCEN H & PL S1632E
;
;
01FD      ORG      H#1FD      ;16*16
01FD      I10 H#3 & CCEN H & PL S1616E
;
;
END

```

```

0000 XXXX0010XXXXXXXX XXXXXXXX 0022 01001001X1101XXX 00010101
0001 01110110X0001011 XXXXXXXX 0023 01110110XX011011 XXXXXXXX
0002 11001100X0001XXX 00010111 0024 11001100XXX11XXX 01111010
0003 11101110X1001XXX XXXXXXXX 0025 11000100X1111011 XXXXXXXX
0004 11000011X1100010 00000100 0026 11000011X1111010 00100110
0005 11000011X1100010 00000101 0027 11001000X1111XXX XXXXXXXX
0006 11000011X1100010 00000110 0028 11001100X1111XXX 00010111
0007 11000011X1100010 00000111 0029 11001010X11111XX XXXXXXXX
0008 11000011X1100010 00001000 002A 01110110X0001011 XXXXXXXX
0009 11000001X1101000 00001101 002B 11001100X0001XXX 00010111
000A 11000001X1101001 00010110 002C 11101110X1001XXX XXXXXXXX
000B 11000011X1101010 00001011 002D 11000011X1100010 00101101
000C 11000011XXX011XX 00000011 002E 11000011X1100010 00101110
000D 01001001X1101XXX 00010101 002F 11000001X1101000 00110011
000E 01110110XX011011 XXXXXXXX 0030 11000001X1101001 00010110
000F 11001100XXX11XXX 10010010 0031 11000011X1101010 00110001
0010 11000100X1111011 XXXXXXXX 0032 11000011XXX011XX 00101100
0011 11000011X1111010 00010001 0033 01001001X1101XXX 00010101
0012 11001000X1111XXX XXXXXXXX 0034 01110110XX011011 XXXXXXXX
0013 11001100X1111XXX 00010111 0035 11001100XXX11XXX 01001010
0014 11001010X11111XX XXXXXXXX 0036 11000100X1111011 XXXXXXXX
0015 11001010X11011XX XXXXXXXX 0037 11000011X1111010 00110111
0016 00XX1010X11011XX XXXXXXXX 0038 11001000X1111XXX XXXXXXXX
0017 01110110X0001011 XXXXXXXX 0039 11001100X1111XXX 00010111
0018 11001100X0001XXX 00010111 003A 11001010X11111XX XXXXXXXX
0019 11101110X1001XXX XXXXXXXX 003B 01110110X0001011 XXXXXXXX
001A 11000011X1100010 00011010 003C 11001100X0001XXX 00001111
001B 11000011X1100010 00011011 003D 11101110X1001XXX XXXXXXXX
001C 11000011X1100010 00011100 003E 11000011X1100010 00111110
001D 11000011X1100010 00011101 003F 11000011X1100010 00111111
001E 11000001X1101000 00100010 0040 11000001X1101000 01000100
001F 11000001X1101001 00010110 0041 11000001X1101001 00010110
0020 11000011X1101010 00100000 0042 11000011X1101010 01000010
0021 11000011XXX011XX 00011001 0043 11000011XXX011XX 00111101

```

Figure C2 (Cont.)

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

0044	01001001X1101XXX	00010101	011E	11000011X1100010	00011110
0045	01110110XX011011	XXXXXXXX	011F	11000001X1101000	00100011
0046	11001100XX11XXX	11111010	0120	11000001X1101001	00010110
0047	11000100X1111011	XXXXXXXX	0121	11000011X1101010	00100001
0048	11000011X1111010	01001000	0122	11000011XXX011XX	00011010
0049	11001000X1111XXX	XXXXXXXX	0123	01001001X1101XXX	00010101
004A	11001100X1111XXX	00110000	0124	01110110XX011011	XXXXXXXX
004B	11000100X1111011	XXXXXXXX	0125	11001100XXX11XXX	11001000
004C	11000011X1111010	01001100	0126	11000100X1111011	XXXXXXXX
004D	11001000X1111XXX	XXXXXXXX	0127	11000011X1111010	00100111
004E	11001100X1111XXX	00001111	0128	11001000X1111XXX	XXXXXXXX
004F	11001010X11111XX	XXXXXXXX	0129	11001100X1111XXX	10100111
0050	01110110X0001011	XXXXXXXX	012A	11000100X1111011	XXXXXXXX
0051	11001100X0001XXX	00001111	012B	11000011X1111010	00101011
0052	11101110X1001XXX	XXXXXXXX	012C	11001000X1111XXX	XXXXXXXX
0053	11000011X1100010	01010011	012D	11001100X1111XXX	00010111
0054	11000001X1101000	01011000	012E	11001010X11111XX	XXXXXXXX
0055	11000001X1101001	00010110	012F	01110110X0001011	XXXXXXXX
0056	11000011X1101010	01010110	0130	11001100X0001XXX	00010111
0057	11000011XXX011XX	01010010	0131	11101110X1001XXX	XXXXXXXX
0058	01001001X1101XXX	00010101	0132	11000011X1100010	00110010
0059	01110110XX011011	XXXXXXXX	0133	11000011X1100010	00110011
005A	11001100XXX11XXX	11001011	0134	11000001X1101000	00111000
005B	11000100X1111011	XXXXXXXX	0135	11000001X1101001	00010110
005C	11000011X1111010	01011100	0136	11000011X1101010	00110110
005D	11001000X1111XXX	XXXXXXXX	0137	11000011XXX011XX	00110001
005E	11001100X1111XXX	00001111	0138	01001001X1101XXX	00010101
005F	11001010X11111XX	XXXXXXXX	0139	01110110XX011011	XXXXXXXX
00F0	XXXX0011XXXXX1XX	00000001	013A	11001100XXX11XXX	11100000
00F3	XXXX0011XXXXX1XX	00010111	013B	11000100X1111011	XXXXXXXX
00F9	XXXX0011XXXXX1XX	00101010	013C	11000011X1111010	00111100
00FB	XXXX0011XXXXX1XX	00111011	013D	11001000X1111XXX	XXXXXXXX
00FD	XXXX0011XXXXX1XX	01010000	013E	11001100X1111XXX	00010111
0100	01110110X0001011	XXXXXXXX	013F	11001010X11111XX	XXXXXXXX
0101	11001100X0001XXX	00010111	0140	01110110X0001011	XXXXXXXX
0102	11101110X1001XXX	XXXXXXXX	0141	11001100X0001XXX	00001111
0103	11000011X1100010	00000011	0142	11101110X1001XXX	XXXXXXXX
0104	11000011X1100010	00000100	0143	11000011X1100010	01000011
0105	11000011X1100010	00000101	0144	11000011X1100010	01000100
0106	11000011X1100010	00000110	0145	11000001X1101000	01001001
0107	11000011X1100010	00000111	0146	11000001X1101001	00010110
0108	11000001X1101000	00001100	0147	11000011X1101010	01000111
0109	11000001X1101001	00010110	0148	11000011XXX011XX	01000010
010A	11000011X1101010	00001010	0149	01001001X1101XXX	00010101
010B	11000011XXX011XX	00000010	014A	01110110XX011011	XXXXXXXX
010C	01001001X1101XXX	00010101	014B	11001100XXX11XXX	11111010
010D	01110110XX011011	XXXXXXXX	014C	11000100X1111011	XXXXXXXX
010E	11001100XXX11XXX	11001000	014D	11000011X1111010	01001101
010F	11000100X1111011	XXXXXXXX	014E	11001000X1111XXX	XXXXXXXX
0110	11000011X1111010	00010000	014F	11001100X1111XXX	11011111
0111	11001000X1111XXX	XXXXXXXX	0150	11000100X1111011	XXXXXXXX
0112	11001100X1111XXX	11101111	0151	11000011X1111010	01010001
0113	11000100X1111011	XXXXXXXX	0152	11001000X1111XXX	XXXXXXXX
0114	11000011X1111010	00010100	0153	11001100X1111XXX	00001111
0115	11001000X1111XXX	XXXXXXXX	0154	11001010X11111XX	XXXXXXXX
0116	11001100X1111XXX	00010111	0155	01110110X0001011	XXXXXXXX
0117	11001010X11111XX	XXXXXXXX	0156	11001100X0001XXX	00001111
0118	01110110X0001011	XXXXXXXX	0157	11101110X1001XXX	XXXXXXXX
0119	11001100X0001XXX	00010111	0158	11000011X1100010	01011000
011A	11101110X1001XXX	XXXXXXXX	0159	11000001X1101000	01011101
011B	11000011X1100010	00010110	015A	11000001X1101001	00010110
011C	11000011X1100010	00011100	015B	11000011X1101010	01011011
011D	11000011X1100010	00011101	015C	11000011XXX011XX	01010111

Figure C2 (Cont.)

AMIOS/29 AMDASM MICRO ASSEMBLER, V1.1
CRT CONTROLLER

```

015D 01001001X1101XXX 00010101
015E 01110110XX011011 XXXXXXXX
015F 11001100XX11XXX 11001000
0160 11000100X1111011 XXXXXXXX
0161 11000011X1111010 01100001
0162 11001000X1111XXX XXXXXXXX
0163 11001100X1111XXX 01111001
0164 11000100X1111011 XXXXXXXX
0165 11000011X1111010 01100101
0166 11001000X1111XXX XXXXXXXX
0167 11001100X1111XXX 00001111
0168 11001010X11111XX XXXXXXXX
01F0 XXXX0011XXXXX1XX 00000000
01F3 XXXX0011XXXXX1XX 00011000
01F9 XXXX0011XXXXX1XX 00101111
01FB XXXX0011XXXXX1XX 01000000
01FD XXXX0011XXXXX1XX 01010101

```

ENTRY POINTS

SYMBOLS

```

GOBACK 0015
H 0001
L 0000
LASTA 0016
M1616 0052
M1616E 0157
M1632 003D
M1632E 0142
M2432 002C
M2432E 0131
M2464 0019
M2464E 011A
M2480 0003
M2480E 0102
S1616 0050
S1616E 0155
S1632 003B
S1632E 0140
S2432 002A
S2432E 012F
S2464 0017
S2464E 011E
S2480 0001
S2480E 0100
T1616 0058
T1616E 015D
T1632 0044
T1632E 0149
T2432 0033
T2432E 0138
T2464 0022
T2464E 0123
T2480 000D
T2480E 010C

```

TOTAL PHASE 2 ERRORS = 0

APPENDIX D

The Microprogrammed CRT Controller was built on a System 29 universal card and exercised by the System 29 support processor. An Am9080A program was written to fill the character memory. Figure D1 is the listing of this program. In order to observe the

correct output of the controller, an oscilloscope or CRT monitor can be connected through an adaptation circuit shown in Figure D2.

```

;
;PROGRAMM TO WRITE INTO CHARACTER MEMORY
;BY MOSHE M. SHAVIT
;REV 0 3/6/78
;
01FF =      STACK EQU      1FFH      ;STACK POINTER
00FF =      FAR   EQU      0FFH      ;FIRST ADDRESS REGISTER O/P PORT
8000 =      CHARAD EQU      8000H     ;CHARACTER MEMORY STARTS HERE
;
0200          ORG      STACK+1 ;WORKING SPACE ABOVE STACK
0200          FA      DS      1      ;FIRST ADDRESS
0201          CURAD   DS      2      ;CURRENT ADDRESS
0203          FIL     DS      2      ;A(FIRST CHARACTER IN LINE)
;
0100          ORG      100H        ;PROGRAM STARTS HERE
0100 31FF01    LXI      SP,STACK
0103 213087    LXI      H,730H+CHARAD ;LAST LINE, FIRST CHARACTER
0106 220302    SHLD    FIL         ;IN "FIRST CHARACTER IN LINE" BUFFER
0109 220102    SHLD    CURAD        ;AND IN CURRENT ADDRESS BUFFER
010C AF        XRA      A          ;CLEAR A
010D D3FF      OUT     FAR         ;START ADDRESS=0
010F 320002    STA     FA          ;SAVE IN BUFFER
0112 CD1B01    CALL    CLEAR        ;CLEAR ALL CHAR. MEMORY
0115 CD2C01    MAIN    CALL    CHARIN ;READ CHARACTER AND PUT IN CHAR. MEMORY
0118 C31501    JMP     MAIN         ;DO IT AGAIN
;
011B 0600      CLEAR    MVI      B,0 ;DATA=0
011D 210080    LXI      H,CHARAD     ;FIRST CHARACTER ADDRESS
0120 110008    LXI      D,2048D      ;COUNTER
0123 70        CLEAR1  MOV      M,B  ;CLEAR THAT ADDRESS
0124 1B        DCX      D           ;COUNT
0125 23        INX      H           ;NEXT ADDRESS
0126 7A        MOV      A,D         ;CHECK
0127 B3        ORA      E           ; IF DONE
0128 C22301    JNZ     CLEAR1       ;NO. CONTINUE
012B C9        RET                ;YES. BACK TO CALLER
;
012C 0E01      CHARIN  MVI      C,1 ;CP/M READ CODE
012E CD0500    CALL    5           ;CP/M READ ROUTINE
0131 FE1A      CPI     1AH         ;CTL-Z?
0133 CA0000    JZ      0           ;RETURN TO CPM IF YES
0136 2A0102    LHLD    CURAD        ;FETCH CURRENT ADDRESS
0139 FE0D      CPI     0DH         ;CR?
013B CA4401    JZ      CRLF        ;YES.
013E 77        MOV      M,A         ;WRITE CHARACTER
013F 23        INX      H           ;INCREMENT
0140 220102    SHLD    CURAD        ;STORE IN BUFFER
0143 C9        RET                ;BACK TO CALLER
;
0144 E5        CRLF    PUSH     H
0145 D5        PUSH     D
0146 C5        PUSH     B
0147 F5        PUSH     PSW
0148 1E0A      MVI     E,0AH
014A 0E02      MVI     C,2
014C CD0500    CALL    5
014F F1        POP      PSW
0150 C1        POP      B
0151 D1        POP      D
0152 E1        POP      H          ;ROUTINE TO ECHO LF
0153 EB        XCHG              ;SAVE CURRENT ADDRESS IN DE

```

Figure D1

```

0154 015000      LXI      B,80D      ;80 CHARACTERS/LINE
0157 2A0302      LHLD     FIL        ;FETCH FIRST CH. IN LINE ADDRESS
015A 09          DAD      B          ;HL= A(NEXT LINE'S FIRST CH. ADD.)
015B EB          XCHG             ;HL=CURRENT ADDR.,DE=A(NEXT LINE FIRST CH. ADDR)
015C 0600      MVI      B,0        ;DATA=0
015E 7C          CRLF2    MOV      A,H      ;MORE SIGNIFICANT CURRENT ADDRESS
015F BA          CMP      D          ;=NEXT LINE FIRST ADDRESS?
0160 C26801      JNZ      CRLF3         ;NO
0163 7D          MOV      A,L          ;LESS SIGNIFICANT CURRENT ADDRESS
0164 BB          CMP      E          ;IS CURRENT LINE FULL?
0165 CA6D01      JZ       CRLF4         ;YES
0168 70          CRLF3    MOV      M,B      ;STORE 0 AT THAT ADDRESS
0169 23          INX      H          ;INCREMENT ADDRESS
016A C35E01      JMP      CRLF2         ;GO CHECK AGAIN
016D 7C          CRLF4    MOV      A,H      ;MORE SIGNIFICANT PART OF ADDRESS
016E E607      ANI      7          ;ONLY 3 LESS SIGNIFICANT BITS
0170 FE07      CPI      7          ;LAST LINE PASSED?
0172 C27E01      JNZ      CRLF5         ;NOT YET
0175 7D          MOV      A,L          ;LESS SIGNIFICANT BYTE OF ADDRESS
0176 FE80      CPI      80H        ;ARE WE AT 780H=1920D?
0178 C27E01      JNZ      CRLF5         ;NOT YET, SKIP
017B 210080      LXI      H,CHARAD    ;YES, START WRITING AT BEGINNING OF CH. MEM.
017E 220302      CRLF5    SHLD     FIL        ;STORE IN FIRST CH. IN LINE BUFFER
0181 220102      SHLD     CURAD        ;AND IN CURRENT ADDRESS BUFFER
0184 3A0002      LDA      FA          ;FETCH FIRST VISIIBLE CHARACTER ADDRESS
0187 C605      ADI      5          ;SCROLL
0189 FE78      CPI      120D        ;TOO MUCH?
018B CC9401      CZ       CRLF0        ;YES
018E 320002      STA      FA          ;STORE IN FIRST ADDRESS BUFFER
0191 D3FF      OUT     FAR          ;LOAD REGISTER
0193 C9          RET              ;RETURN TO CALLER

;
;
0194 AF          CRLF0    XRA      A          ;FIRST ADDRESS=0
0195 C9          RET
;
;

```

Figure D1 (Cont.)

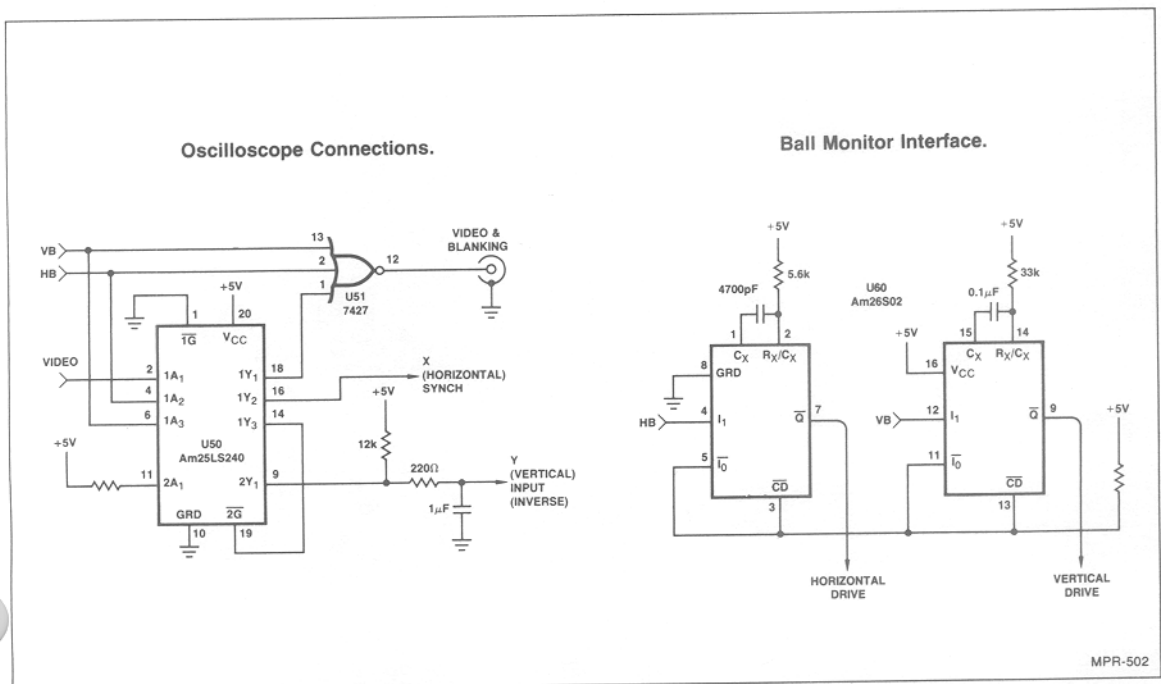


Figure D2.

THE UNIVERSITY OF CHICAGO
DIVISION OF THE PHYSICAL SCIENCES
DEPARTMENT OF CHEMISTRY

RESEARCH REPORT NO. 1000

BY J. H. GOLDSTEIN

1955

RECEIVED BY THE
LIBRARY OF THE UNIVERSITY OF CHICAGO

APRIL 15 1955

THIS REPORT IS THE PROPERTY OF THE
UNIVERSITY OF CHICAGO. IT IS TO BE
REPRODUCED IN WHOLE OR IN PART
FOR PRIVATE USE ONLY. IT IS NOT TO
BE REPRODUCED FOR OTHER THAN
PRIVATE USE WITHOUT THE WRITTEN
CONSENT OF THE UNIVERSITY OF CHICAGO.

1955

RESEARCH REPORT NO. 1000

1955

RESEARCH REPORT NO. 1000



1955

MULTIPLEXER SELECT

R20	R19	R18	R17	SELECT
0	0	0	0	TEST 0
0	0	0	1	TEST 1
0	0	1	0	TEST 2
		⋮		⋮
1	1	1	1	TEST 15

POLARITY CONTROL

R16	OUTPUT
0	COMPLEMENT OF TEST
1	TRUE TEST

NEXT ADDRESS CONTROL

R15	R14	R13	R12	FUNCTION
X	X	X	X	NEXT INSTRUCTION

MACHINE INSTRUCTION REGISTER


R21	FUNCTION
0	LOAD
1	HOLD

CONTROL VALUE


R11-R0	FUNCTION
XXX---XXX	VALUE

JUMP ADDRESS

BR11-BR0	FUNCTION
XXX---XXX	JUMP ADDRESS

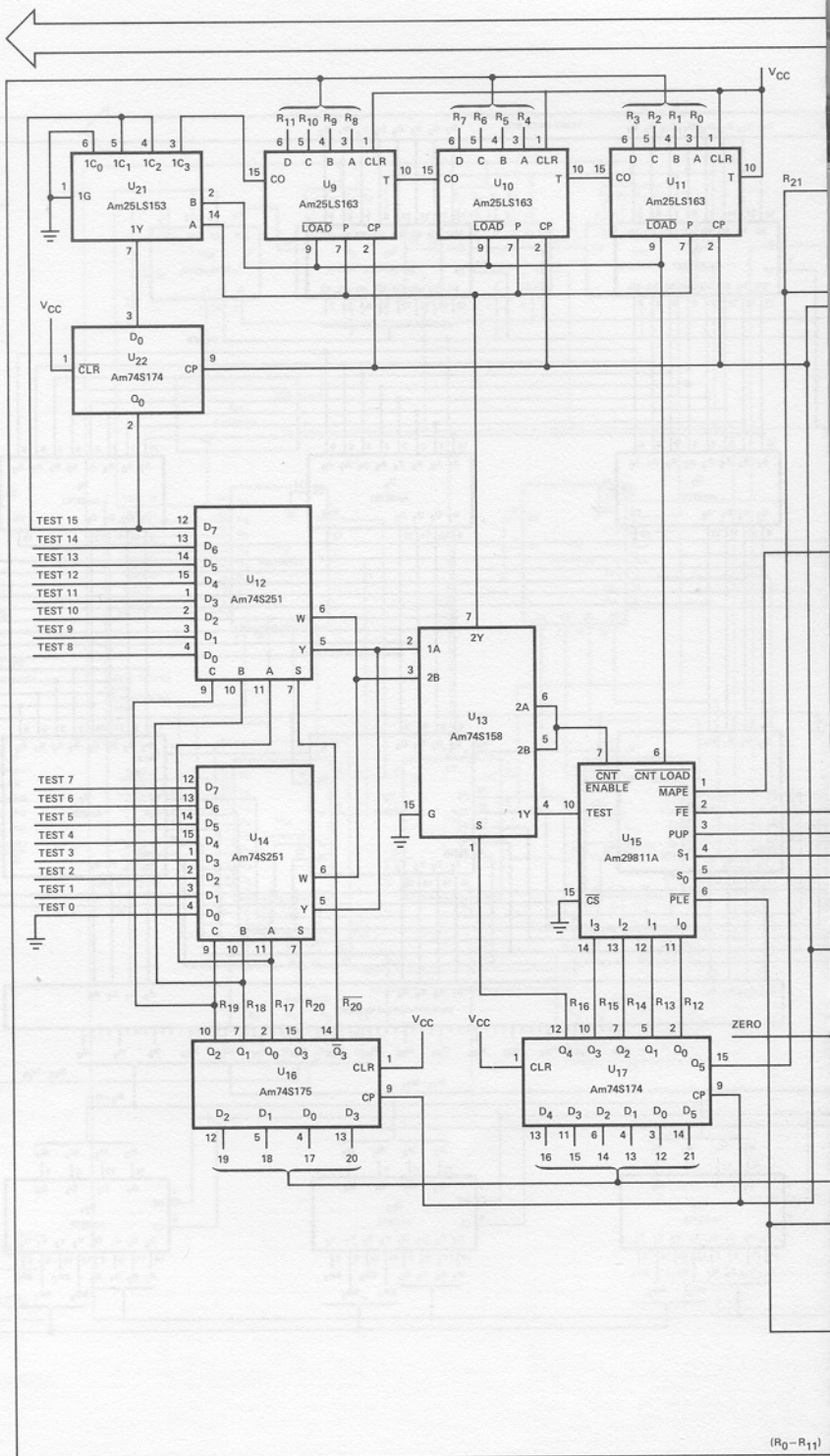

(R0-R11)

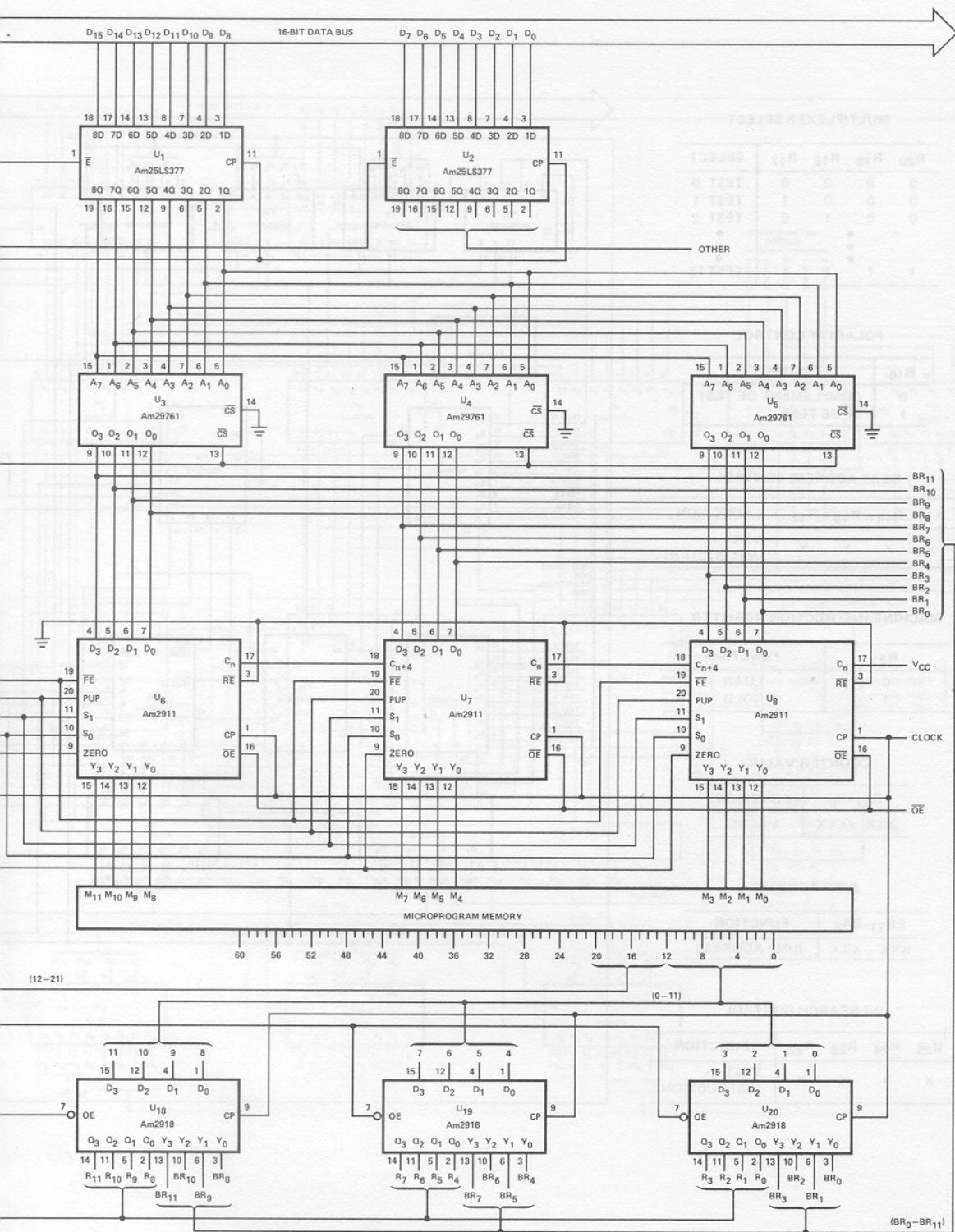

R20	R19	R18	R17	SELECT
0	0	0	0	TEST 0
0	0	0	1	TEST 1
0	0	1	0	TEST 2
		•		•
		•		•
		•		•
1	1	1	1	TEST 15

R ₁₆	OUTPUT
0	COMPLEMENT OF TEST
1	TRUE TEST

R15	R14	R13	R12	FUNCTION
X	X	X	X	NEXT INSTRUCTION

R21	FUNCTION
0	LOAD
1	HOLD

R ₁₁ -R ₀	FUNCTION
XXX...XXX	VALUE

BR ₁₁ -BR ₀	FUNCTION
XXX...XXX	JUMP ADDRESS

R25	R24	R23	R22	FUNCTION
X	X	X	X	TEST INSTRUCTION





MULTIPLEXER SELECT

R ₂₀	R ₁₉	R ₁₈	R ₁₇	SELECT
0	0	0	0	TEST 0
0	0	0	1	TEST 1
0	0	1	0	TEST 2
		⋮		⋮
		⋮		⋮
1	1	1	1	TEST 15

NEXT ADDRESS CONTROL

R ₁₅	R ₁₄	R ₁₃	R ₁₂	FUNCTION
X	X	X	X	NEXT INSTRUCTION

CONTROL VALUE

R ₁₁ ·R ₀	FUNCTION
XXX - - - XXX	VALUE

POLARITY CONTROL

R ₁₆	OUTPUT
0	COMPLEMENT TEST
1	TRUE TEST

MACHINE INSTRUCTION REGISTER

R ₂₁	FUNCTION
0	LOAD
1	HOLD

JUMP ADDRESS

BR ₁₁ ·BR ₀	FUNCTION
XXX - - - XXX	JUMP ADDRESS



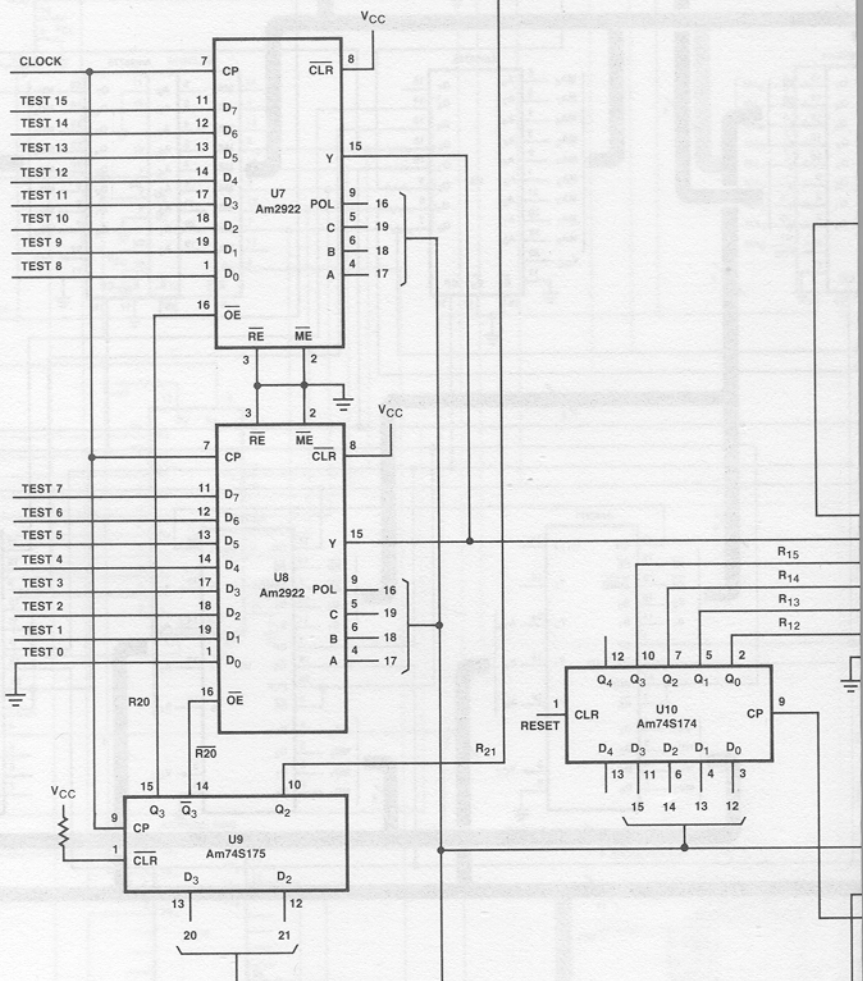


Figure 20. Con

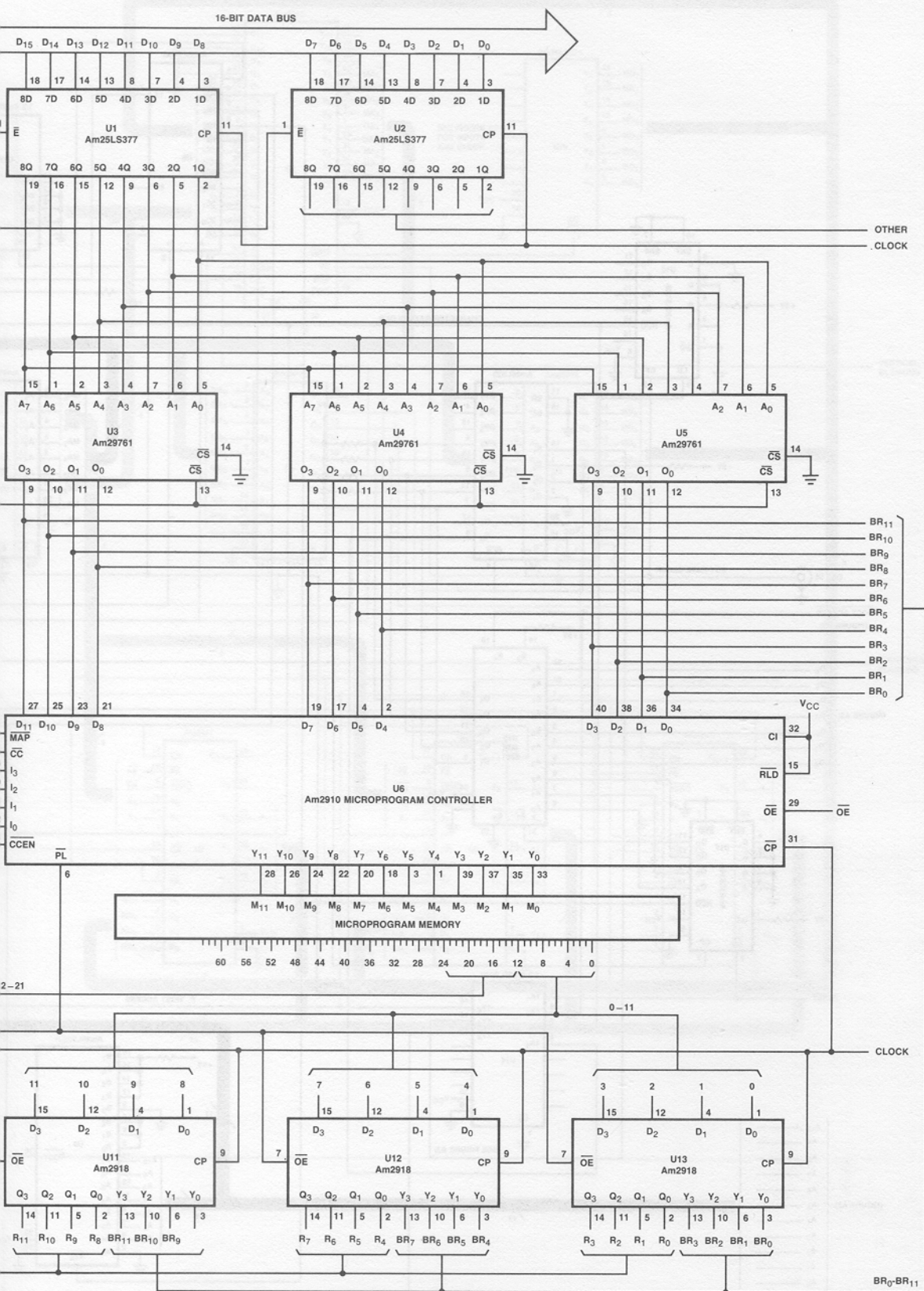

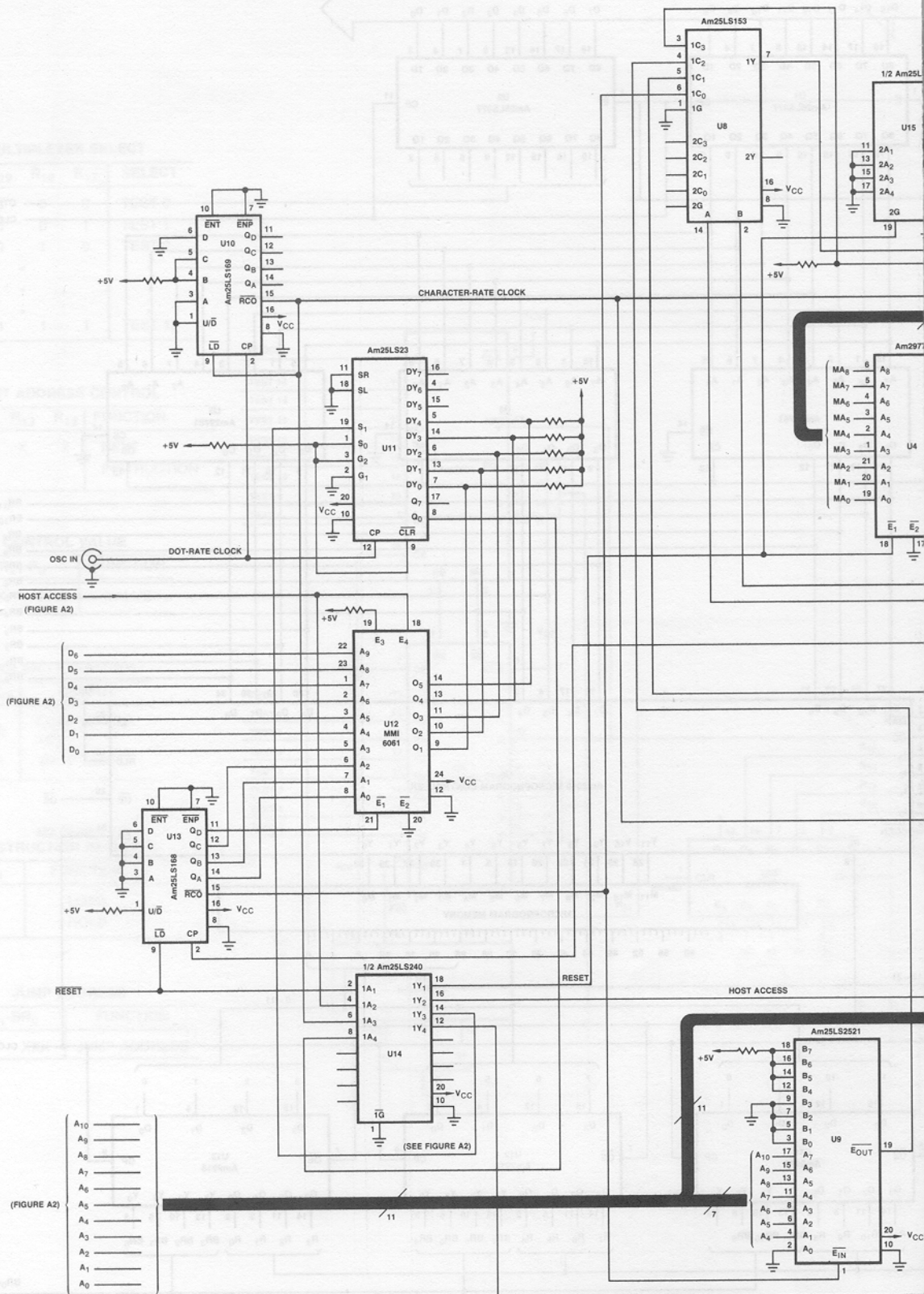




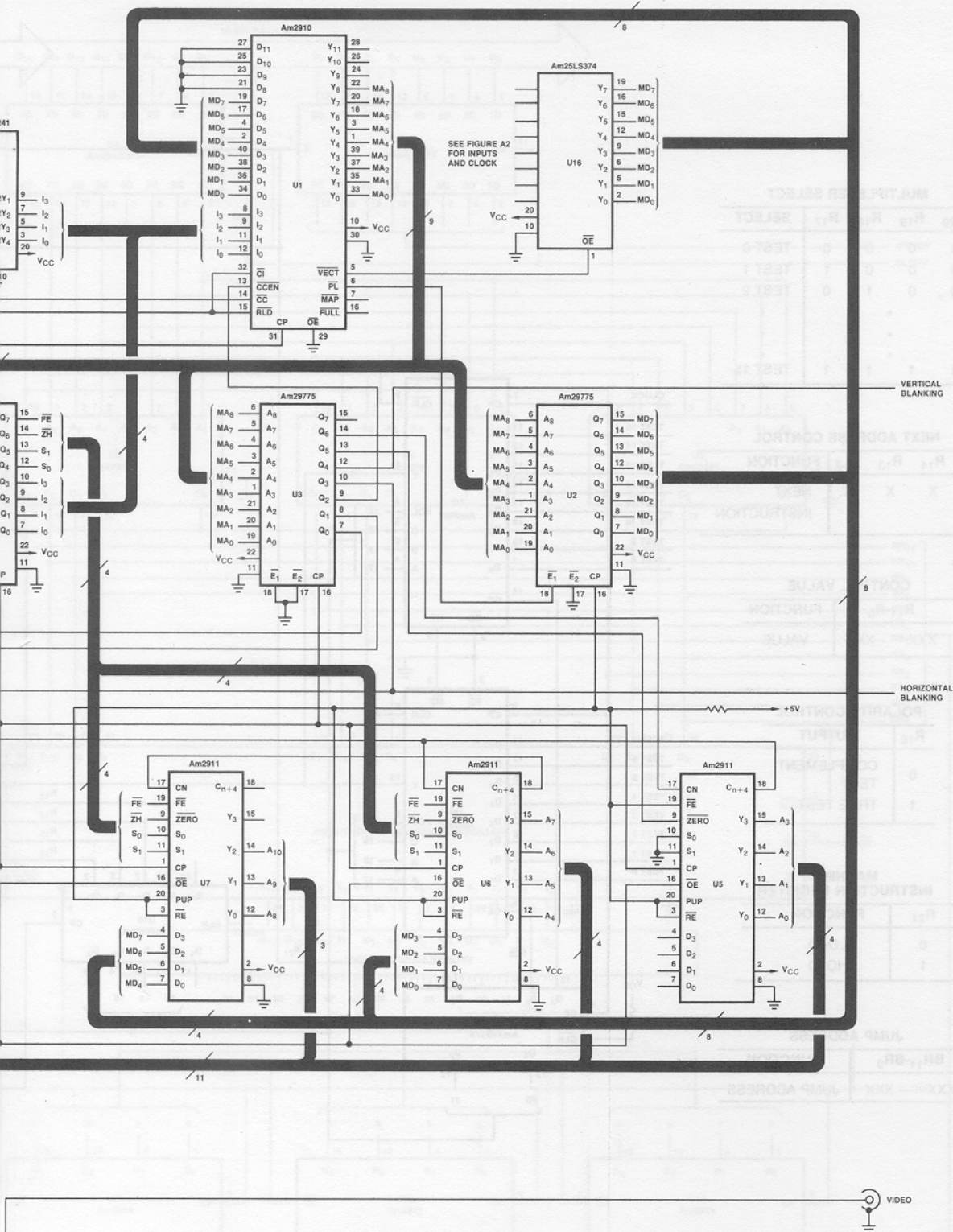


Figure 24. CRT Controller.

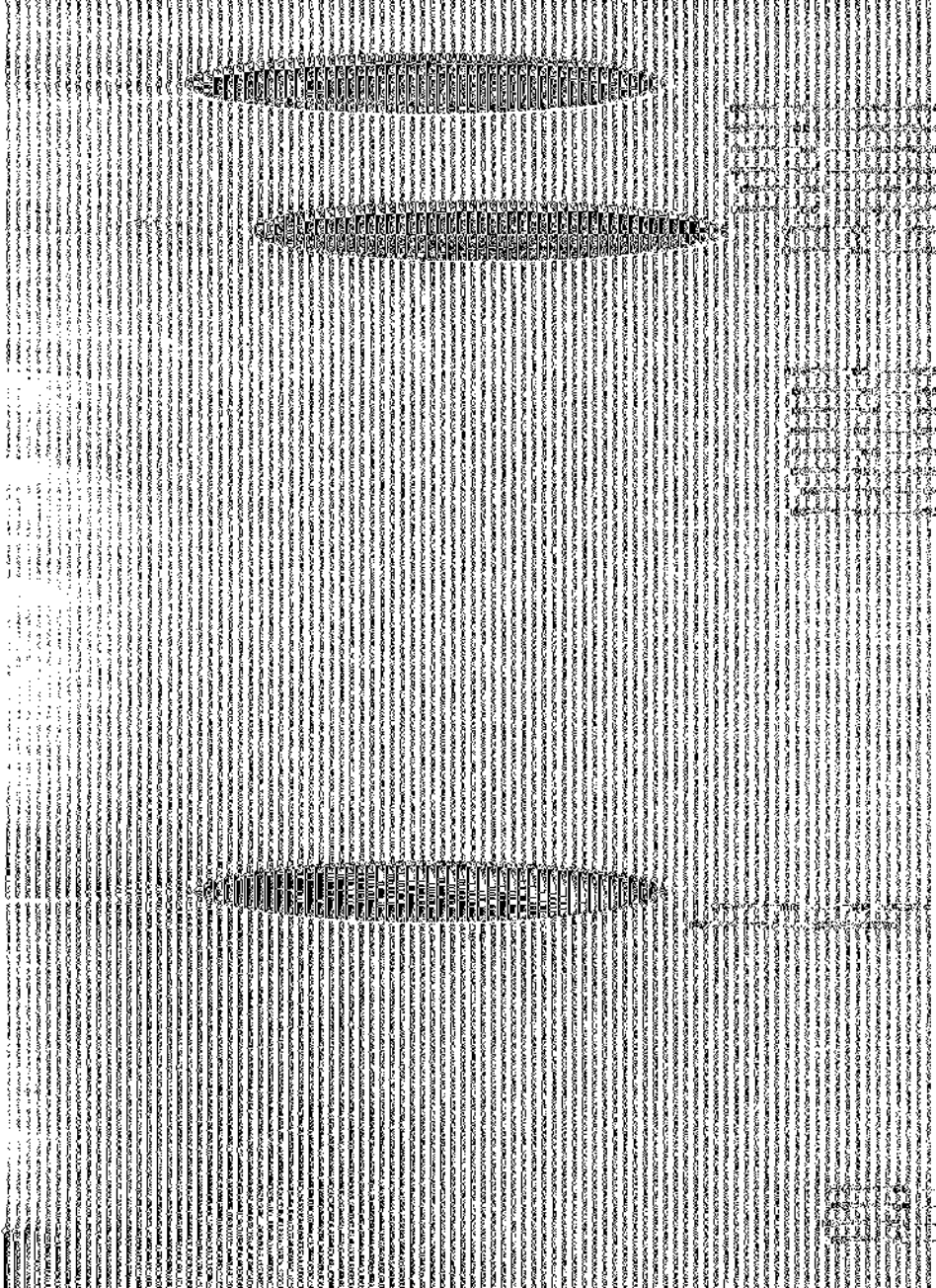

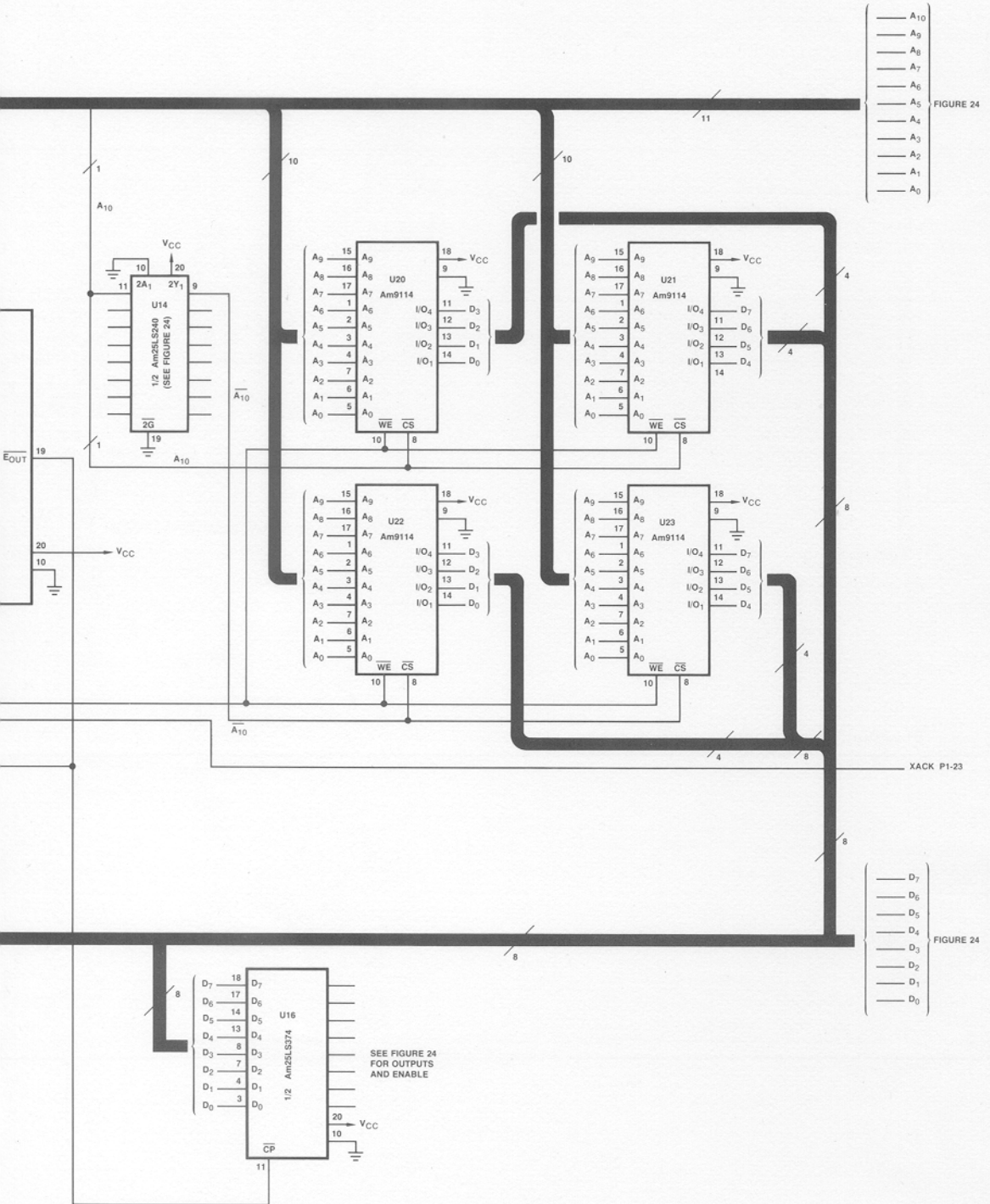

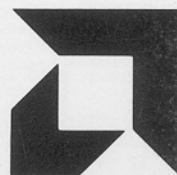

**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
Sunnyvale

California 94086

(408) 732-2400

TWX: 910-339-9280

TELEX: 34-6306


TOLL FREE

(800) 538-8450

THE COMPLETE 16-BIT CPU TAKES
ONLY 8 Am 2900 PARTS & A
HANDFUL OF MSI & SSI.

REPLACE THE SSI/MSI
WITH THE Am2904
LATER.

MIL-STD-883
FOR FREE.

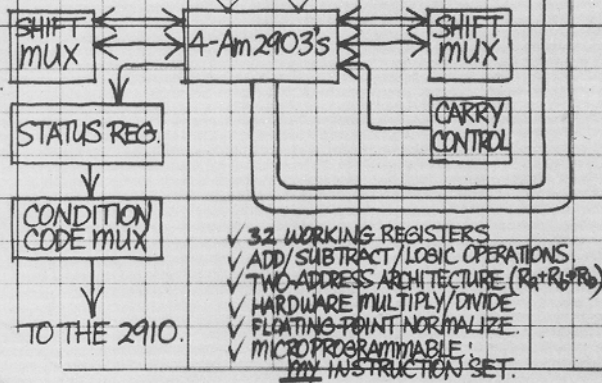

Build A Microcomputer

Chapter III The Data Path

Advanced Micro Devices



Copyright © 1978 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-3

INTRODUCTION

The heart of most digital arithmetic processors is the arithmetic logic unit (ALU). The ALU can be thought of as a digital subsystem that performs various arithmetic and logic operations on two digital input variables. The Am2901A and Am2903 are Low Power Schottky TTL arithmetic logic unit/function generators that perform arithmetic/logic operations on two four-bit input variables. In most ALUs, speed is generally a key ingredient. Therefore, as much parallelism in the operation of the arithmetic logic unit as possible is desired.

The Am2901A and Am2903 ALUs are designed to operate with an Am2902A carry lookahead generator to perform multi-level full carry lookahead over any number of bits. Therefore, the devices have both the carry generate and carry propagate outputs required by the Am2902A carry lookahead generator. The devices also have the carry output (C_{n+4}) and a two's complement overflow detection signal (OVR) available at the output. The net result is that a very high-speed 16-bit arithmetic logic unit/function generator can be designed and assembled using four of these bit slice devices and one Am2902A (the Am2902A is a high-speed version of the '182 carry lookahead generator). In addition, the Am2901A and Am2903 provide a minimum of 16 working registers for providing source operands to the ALU.

UNDERSTANDING THE BASIC FULL ADDER

The results of an arithmetic operation in any position in a word depends not only on the two-input operand bits at that position, but also on all the lesser significant operand bits of the two input variables. The final result for any bit, therefore, is not available until the carries of all the previous bits have rippled through the logic array starting from the least significant bit and propagating through to the most significant bit. A full adder is a device that accepts two individual operand bits at the same binary weight, and also accepts a carry input bit from the next lesser significant weight full adder. The full adder then produces the sum bit for this bit position and also produces a carry bit to be used in the next more significant weight full adder carry input. The truth table for a full adder is shown in Figure 1. From this truth table, the equations for the full adder:

$$S = A \oplus B \oplus C$$

$$C_0 = AB + BC + AC,$$

where A and B are the input operands to the full adder and C is the carry input into the adder.

Inputs			Outputs	
A	B	C	S	C ₀
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 1. Full Adder Truth Table.

The sum output, S, represents the sum of the A and B operand inputs and the carry input. The carry output, C₀, represents the carry out of this cell and can be used in the next more significant cell of the adder. Full adder cells can be cascaded as depicted in Figure 2 to form a four-bit ripple carry parallel adder.

Note that once we have cascaded devices as shown in Figure 2, we may wish to discuss the equations for the i-th bit of the adder. In so doing, we might describe the equations of the full adder as follows:

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = A_i B_i + B_i C_i + A_i C_i$$

where the A_i and B_i are the input operands at the i-th bit, and the C_i is the carry input to the i-th bit. (Note that the equations for this adder are iterative in nature and each depends on the result of the previous lesser significant bits of the adder array.)

The connection scheme shown in Figure 2 requires a ripple propagation time through each full adder cell. If a 16-bit adder is to be assembled, the carry will have to propagate through all 16 full adder cells. What is desired is some technique for anticipating the carry such that we will not have to wait for a ripple carry to propagate through the entire network. By using some additional logic, such an adder array can be constructed. This type of adder is usually called a carry lookahead adder.

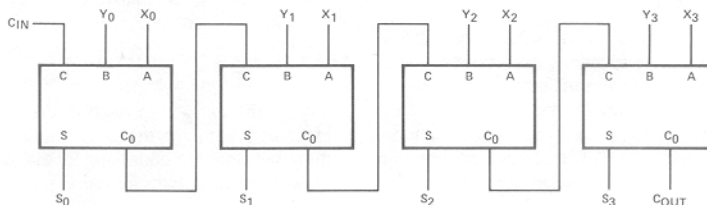


Figure 2. Cascaded Full Adder Cells Connected as a Four-Bit Ripple-Carry Full Adder.

A FOUR-BIT CARRY LOOKAHEAD ADDER

Looking back to the equations developed for i -th bit of an adder, let us now rewrite the carry equation in a slightly different form. When we factor the C_i in this equation, the new equation becomes:

$$C_{i+1} = A_i B_i + C_i(A_i + B_i)$$

From the above equation, let us now define two additional equations. These are:

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

With these two new auxiliary equations, we can now rewrite the carry equation for the i -th bit as follows:

$$C_{i+1} = G_i + P_i C_i$$

Note that we have now developed two terms: the P_i term is known as carry propagate and the G_i term is known as carry generate. An anticipated carry can be generated at any stage of the adder by implementing the above equations and using the auxiliary functions P_i and G_i as required.

It is interesting to note that the sum equation can also be written in terms of these two auxiliary equations, P_i and G_i . For this case, the equation is:

$$S_i = (A_i + B_i)(\bar{A}_i \bar{B}_i) \oplus C_i$$

The auxiliary function G_i is called carry generate, because if it is true, then a carry is immediately produced for the next adder stage. The function P_i is called carry propagate because it implies there will be a carry into the next stage of the adder if there is a carry into this stage of the adder. That is, G_i causes a carry signal at the i -th stage of the adder to be generated and presented to the next stage of the adder while P_i causes an existing carry at the input to the i -th stage of the adder to propagate to the next stage of the adder.

Let us now write all of the sum and carry equations required for a full four-bit lookahead carry adder.

$$\begin{aligned} S_0 &= A_0 \oplus B_0 \oplus C_0 \\ S_1 &= A_1 \oplus B_1 \oplus (G_0 + P_0 C_0) \\ S_2 &= A_2 \oplus B_2 \oplus (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ S_3 &= A_3 \oplus B_3 \oplus (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ C_{i+4} &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

An important point to note is that ALL of the sum equations and the final carry output equation, C_{i+4} , can be written in terms of the A_i , B_i , and C_0 inputs to the four-bit adder. The configuration as described above is shown in Figure 3. This figure is divided into two parts – the upper blocks show the auxiliary function generator circuitry required to implement the P_i and G_i equations while the lower block implements the logic required to generate the sum output at each bit position.

A serious drawback to the lookahead carry adder is that as the word length is increased, the carry functions become more and more complex, eventually becoming impractical due to the large number of interconnections and heavy loading of the G_i and P_i functions. The auxiliary function concept can be extended, however, by dividing the word length into fairly small increments and defining blocks of auxiliary functions G and P .

It is possible for a given block to define a function G as the carry out generated with the block; and P can be defined as the carry propagate over the block. If the block size is set at four bits, then the functions for G and P for this block can be defined as follows:

$$\begin{aligned} G &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 \\ P &= P_3 P_2 P_1 P_0 \end{aligned}$$

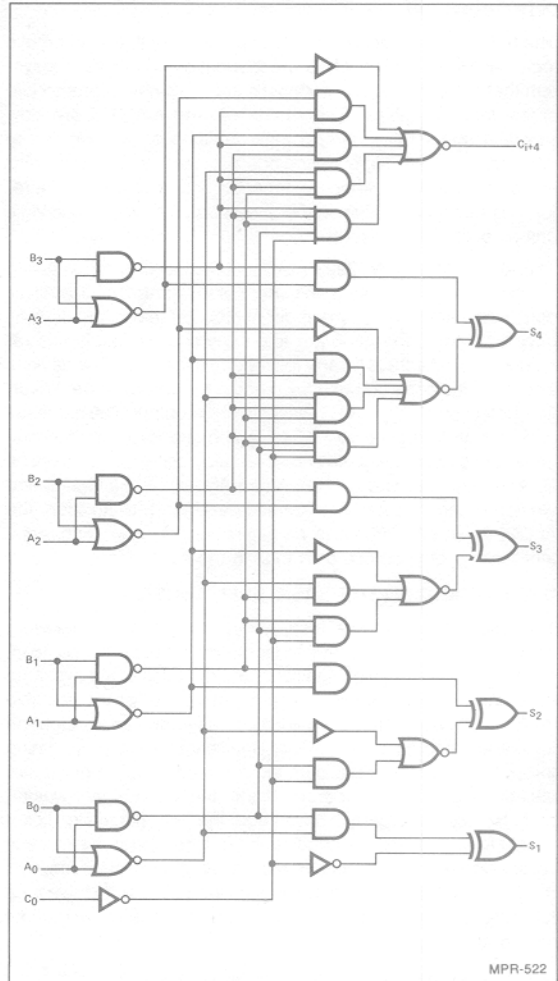


Figure 3. Full Four-Bit Carry-Lookahead Adder.

It is important to note that neither of these terms involves a carry-in (C_0) to the block, so no matter how many blocks are tied in an adder, all the blocks have stable G and P functions available in a minimum number of gate delays.

The G and P functions can be gated to produce a carry-in to each four-bit block, as a function of the lesser significant blocks. The carry-in to a block is therefore:

$$C_n = G_{n-1} + P_{n-1}G_{n-2} + P_{n-1}P_{n-2}G_{n-3} + \dots + P_{n-1}P_{n-2}P_{n-3} \dots P_2P_1P_0C_0$$

Finally, the carry-in to each of the bits in a four-bit block must include a term for the actual least significant carry-in; note, therefore, that the equations for the four-bit full adder presented above include a term for carry-in at each bit position.

Figure 4 shows the technique for cascading typical bit slice ALUs such as the Am2901A or Am2903 and one Am2902A in a full 16-bit high-speed carry lookahead connection. Figure 5 shows a connection scheme using only four bit slices in a 16-bit arithmetic logic unit connection where the carries are rippled between the devices. Each bit slice does use internal carry lookahead over the four-bit block.

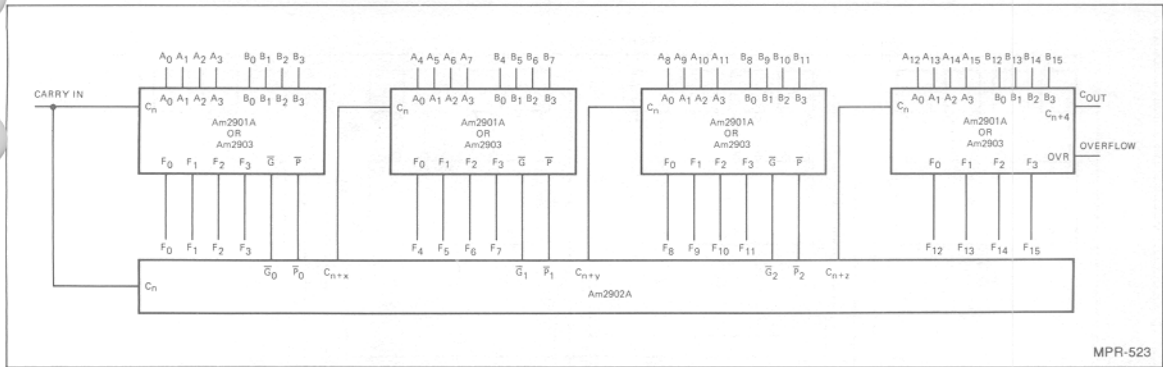


Figure 4. Full Lookahead Carry 16-Bit Adder.

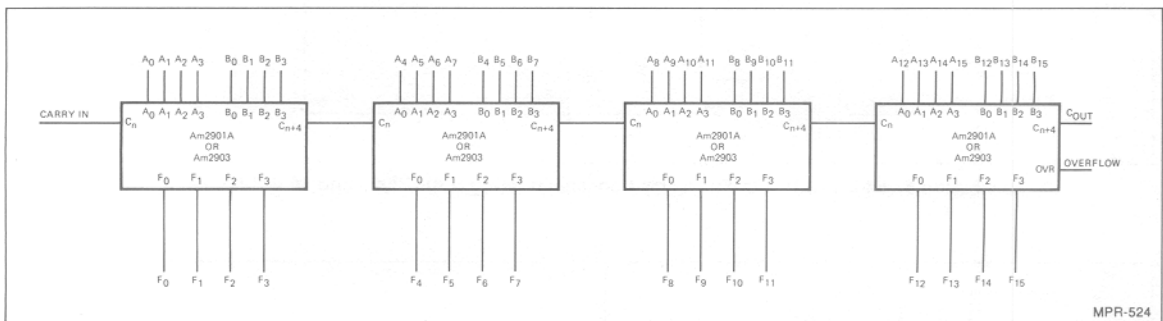


Figure 5. Connection of 16-Bit ALU Using Ripple Carry.

In summary, the ripple carry method can be used in conjunction with the lookahead technique in several ways.

1. Lookahead carry over sections of the adder and ripple carry between these sections of the adder can be used. This method is often the most efficient in terms of hardware for a given speed requirement. It does not require the use of a lookahead carry generator such as the Am2902A.
2. Lookahead carry across 16-bit blocks with a ripple carry between 16-bit blocks can be used. This technique is usually called two-level carry lookahead addition. This technique results in very high-speed arithmetic function generation and makes a reasonable tradeoff between the speed and hardware for word lengths greater than 16 bits.
3. Full lookahead carry across all levels and all block sizes can be used. This is the highest speed arithmetic logic unit connection scheme. For word sizes up to 64 bits, it is referred to as three-level lookahead carry addition. Such a 64-bit ALU requires the use of five Am2902A carry lookahead generator units in addition to the 16 bit slice ALU devices as shown in Figure 6.

OVERFLOW

When two's complement numbers are added or subtracted, the result must lie within the range of the numbers that can be handled by the operand word length. Numbers are normally represented either as fractions with a binary point between the sign bit and the rest of the word, or as integers where the binary point is after the least significant bit. The actual choice for the location of the binary point is really up to the design engineer, as

the hardware configuration required for either technique is identical. It is also possible to use number notations that include both integer and fractional representations in the same numbering scheme. Overflow is defined as the situation in which the result of an arithmetic operation lies outside of the number range that can be represented by the number of bits in the word. For example, if two eight-bit numbers are added and the result does not lie within the number range that can be represented by an eight-bit word, we say that an overflow has occurred. This can happen at either the positive end of the number range or at the negative end of the number range. The logic function that indicates that the result of an operation is outside of the representable number range is:

$$OVR = C_s \oplus C_{s+1}$$

where C_s is the carry-in to the sign bit and C_{s+1} is the carry-out of the sign bit.

Thus, for a four-bit ALU with the sign bit in the most significant bit position, the two's complement overflow can be defined as the C_{n+4} term exclusive OR'ed with the C_{n+3} term.

Putting the ALU in the Data Path of a Simple Computer

Once the Design Engineer understands the basic configuration and operation of a simple high speed carry lookahead adder, he can begin to understand the configuration required to implement the data handling section of a typical computing machine. The simplest architecture for the data handling path of a minicomputer is shown in Figure 7. Here, an accumulator is used in conjunction with an ALU to perform a basic arithmetic/storage capability for data handling. The computer control unit of Figure 7 can be a simple or sophisticated state machine as described in Chapter 2.

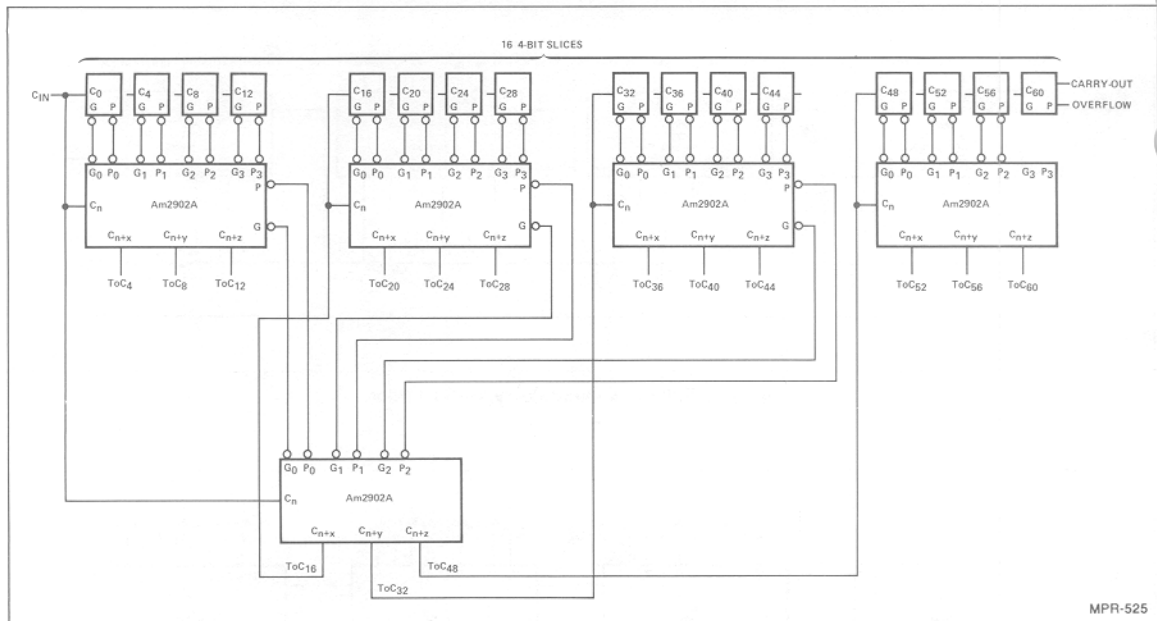


Figure 6. 64-Bit ALU with Full Carry Lookahead Using 5 Am2902s and 16 4-Bit Slices.

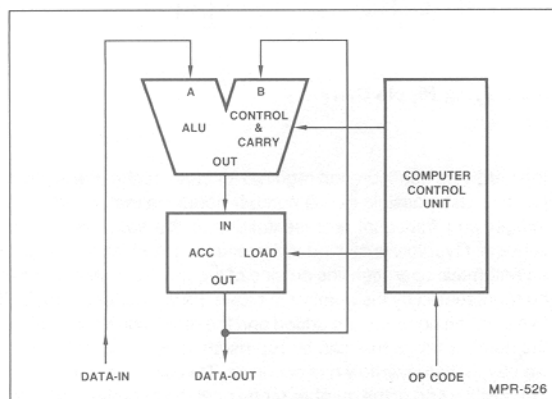


Figure 7. Basic Computer Data Path.

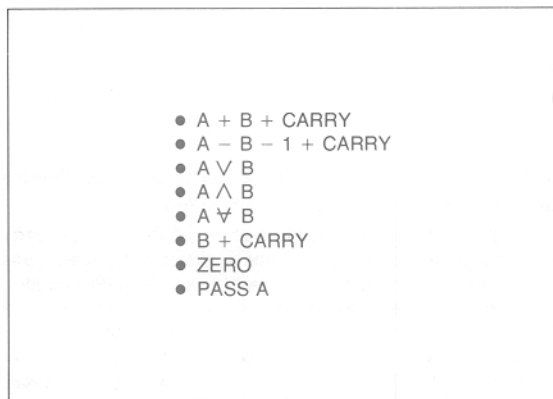


Figure 8. Basic ALU Instructions.

While the introductory material of this chapter concentrated on full adders, it should be understood that more ALU functions than addition are required if we are in to implement the data path of a typical minicomputer. Typically, some or all of the functions shown in Figure 8 are needed if we are to implement a powerful data handling capability.

The operation of the ALU/accumulator configuration shown in Figure 7 can be described as follows. The accumulator can be loaded by bringing data in from the data-in port through the A input of the ALU, passed through the ALU and loaded into the accumulator. A second word of data can be presented at the data-in port to the A input of the ALU and the ALU can be used to perform an operation such as $A + B$, $A \text{ OR } B$, $A \text{ AND } B$, $A - B$ and so forth. The results of this ALU operation can then be placed into the accumulator. The accumulator output is available at the data-out port for use elsewhere. Additional ALU functions such as

those shown in Figure 8 are easily implemented by adding some additional circuitry to the four-bit carry look ahead adder shown in Figure 3. If this circuitry is added, we will arrive at a logic diagram as shown in Figure 9. This diagram certainly is familiar to most CPU designers and is the well known Am74S181 four-bit arithmetic logic unit/function generator.

Once the operation of the simple computer data path as shown in Figure 7 is understood, the Design Engineer will soon recognize the need for additional registers if our machine is to be general purpose and execute instructions. Very rapidly the need arises for a register to hold a program counter (PC) and a memory address register (MAR). The purpose of the program counter is to point to the address of the next instruction in main memory. Typically it is loaded into the memory address register which actually provides the address on to the address bus of the machine. Then, the program counter is incremented through the ALU and stored until

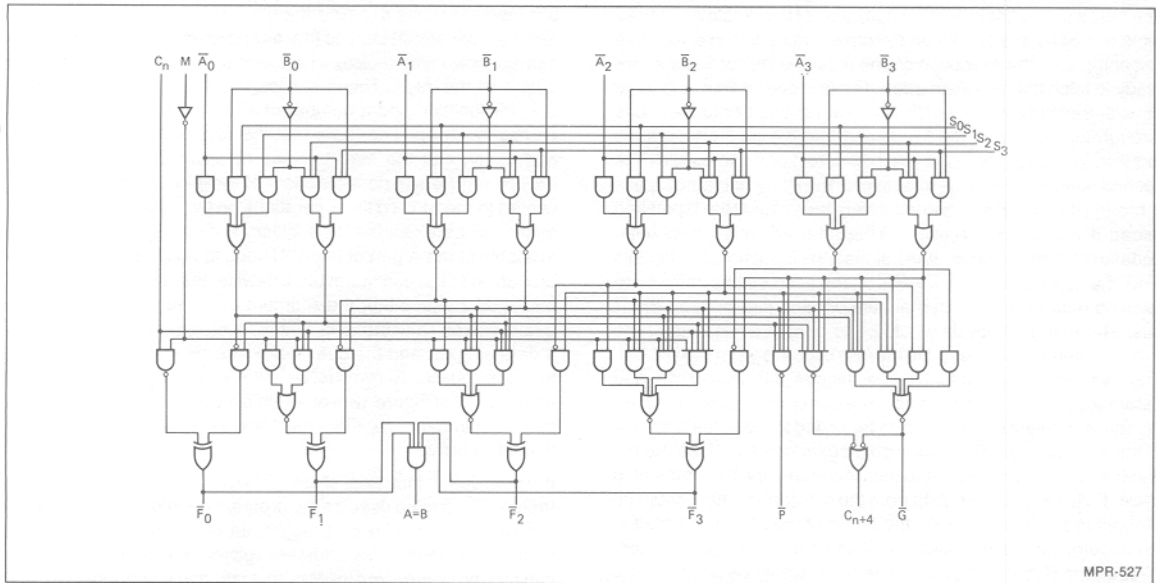


Figure 9. Logic Diagram for Am25LS181.

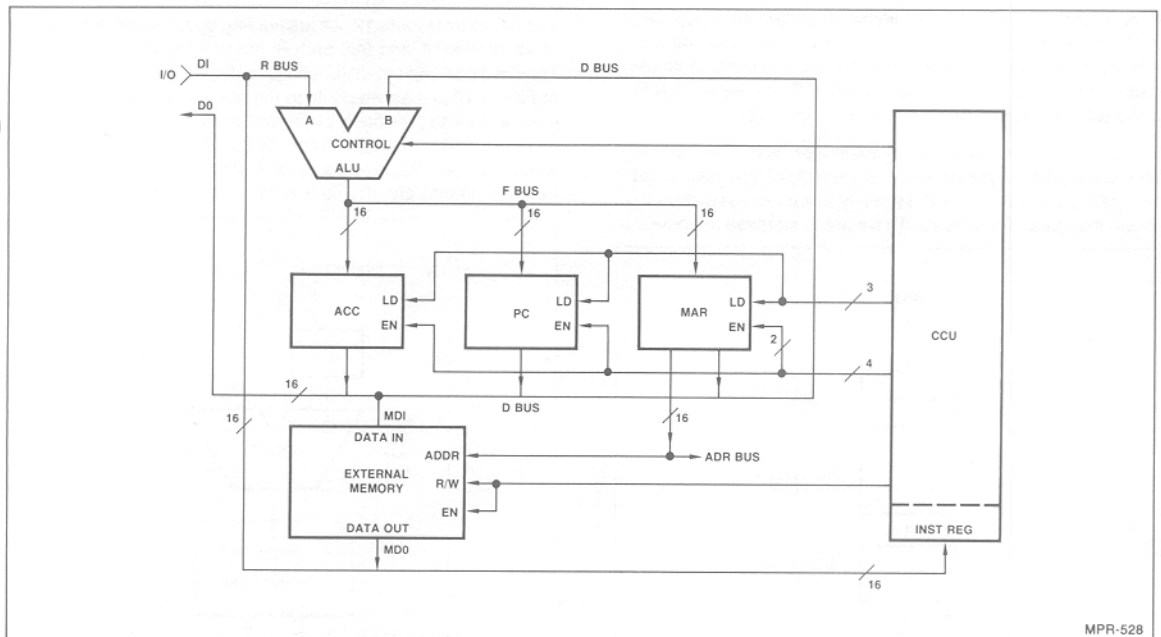


Figure 10. Three Register Computer Data Path.

it is needed again. The block diagram of Figure 10 shows these additional registers connected in parallel at the output of the ALU. This ALU output is called the F bus. Each of these registers (the accumulator, the PC, and the MAR) has an enable input from the CCU so that they can selectively be loaded with data from the ALU. In addition, each of these registers has an output enable such that they can be selectively enabled onto the D bus. The D bus represents the data output path from the basic computer data

path and also is used as one of the inputs to the actual ALU/function generator. The other input in this example is called the R bus and comes directly from the main memory data output as well as from the I/O data input. As shown in Figure 10, the memory address register (MAR) has a second output that is used to drive the address bus. In this example, this register always contains the address to be applied to the external memory whether it be the address of data or the address of an instruction.

The best way to understand the operation of this single ALU/three register machine is to take an example. Let us assume we have just completed the execution of one machine instruction and are ready to fetch the next instruction. The first operation would be to transfer the current value of the program counter onto the D bus through the ALU onto the F bus and into the memory address register. This might be accomplished during one microcycle. The second operation might be to again put the PC on the D bus, pass it through the ALU B port and increment the value at the B port and reload it into the PC register. Thus, the PC has again been updated to point to the address of the next instruction. During this time, the address from the MAR is on the address bus and we are fetching data from the external memory and placing it on the R bus. The third microcycle would be to bring the data out of the external memory and pass it to the instruction register in the CCU. The next microcycle might be to decode this instruction and determine that the next word after the current instruction in memory (an immediate operation) is to be added to the value currently in the accumulator. Thus, we would again need to place the PC into the MAR on one cycle and then increment the PC on the next cycle. Following this, the data from the external memory could be brought to the R bus through the A port of the ALU and added to the accumulator value which is placed on the D bus and brought through the B port of the ALU. The result would be placed in the accumulator. This operation would complete the example and we would be ready to fetch the next instruction. As can be seen, a number of microcycles are required to fetch the instruction, decode it, fetch the data and execute the instruction. One of the best ways to understand the flow needed to implement a typical instruction set is shown in Figure 11. Here, we see the basic instruction fetch and decode operation followed by the path used to execute each of the various instructions. Then, we see a return to the fetch operation to fetch the next instruction.

Certainly from this discussion we can see how three registers have enhanced the performance of the simple ALU/accumulator data path shown in Figure 7. Typically, even more registers than shown in Figure 10 are needed if we are to increase the power of

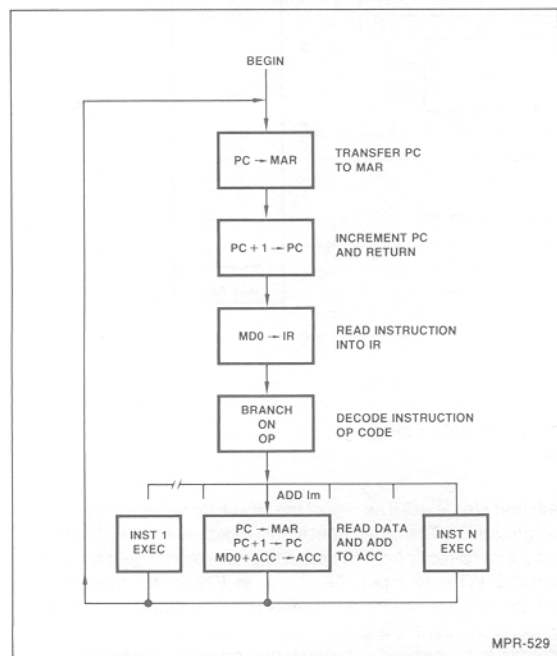


Figure 11. Steps for ADD Instruction.

our machine. If we examine the block diagram of Figure 12, we see a similar architecture to that as shown in Figure 10. Here, the number of working registers has been expanded to sixteen at the output of the ALU. These can be used to provide a program counter function and a number of accumulator functions simultaneously. In addition, note that the registers have two output ports such that the simultaneous selection of any two of the sixteen registers is possible. Both of these registers can be presented to the ALU so that operations on two registers simultaneously can be executed. In addition, a data input multiplexer is available at the A port of the ALU such that external data can be brought in to the configuration. Likewise, there is an output multiplexer such that either the A output of the registers or the ALU output can be selected. This output multiplexer is used to provide a data out port and the output can also be loaded into memory address register to provide an address as required. Thus, the architecture of Figure 12 is quite similar to that of Figure 10 except that the number of registers has been increased to provide additional flexibility.

If we assume that one of the sixteen registers inside of this register file is to be used as the program counter, we see that the program counter can be brought out of the A output port and loaded into the memory address register and at the same time it can also be brought out the B output port and incremented in ALU and reloaded into the register file. In this architecture it appears the A output of the register stack can also be brought to the input multiplexer and the A port of the ALU and incremented via that path and reloaded into the registers. While this is possible in the architecture of Figure 12, we are leading up to the implementation of an Am2901A and this path is not needed in the Am2901A. Thus, we can implement functions and operations in the diagram of Figure 12 just as we could in the diagram of Figure 10. However, what was previously performed in two microcycles can now be performed in one microcycle. That is, the MAR can be loaded with the current value of the PC and at the same time the PC can be incremented and the new value restored in the PC register.

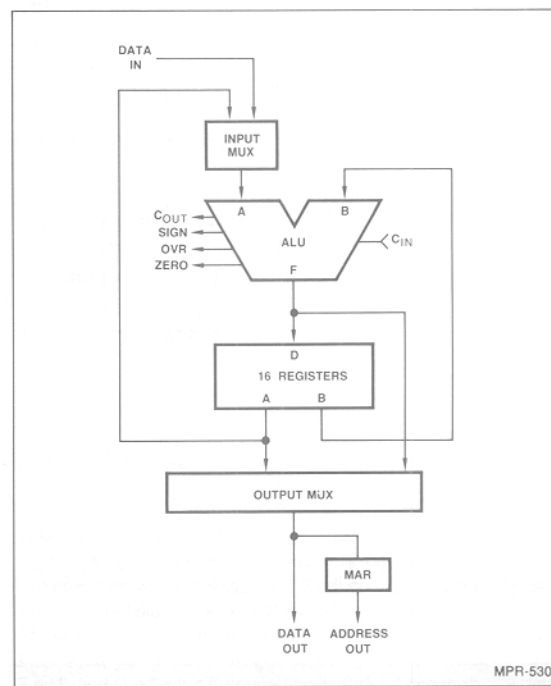


Figure 12. Multi-Register ALU.

Another feature of the block diagram of Figure 12 is the depiction of the carry in bit to the ALU and the four output flags associated with the ALU. Here, carry in is the normal carry in as needed in any adder such that the device is cascadable. In addition, certain kinds of arithmetic functions such two's complement arithmetic also need the ability to provide a carry in for certain operations. The most common is two's complement subtract which is usually performed by complementing the operand to be subtracted, adding and adding one at the carry in. Also, the ALU shows the four output flags usually associated with a typical minicomputer. These are the carry output, the sign bit, the overflow detect, and the zero detect. These four status flags are used to determine various things about the operation being performed. The carry out flag and overflow flag are as described in the previous sections of this chapter. They provide the carry and overflow information about the addition.

The sign bit is simply the most significant bit of the ALU and represents the sign of a two's complement number. That is, when the sign bit is LOW, we assume the two's complement number is positive and when the sign bit is HIGH, we assume the two's complement number is negative. Thus, the sign bit is active HIGH and carries negative weight as we assume in any standard two's complement number representation. If the reader is unfamiliar with two's complement number notations, a discussion of this topic can be found in an application note entitled "The Am25S05, Am2505 and Am25L05 Schottky, Standard and Low Power TTL Two's Complement Digital Multipliers" as found in Advanced Micro Devices' Schottky and Low Power Schottky Data Book dated 10/77. This application note begins on page 5-49 and fully details two's complement number notation and gives examples.

The fourth status flag is called the zero flag and again is just what the name implies. This flag represents the fact that all of the ALU outputs are at logic zero. In this design, a logic zero means that all of the ALU output bits are LOW.

If the architecture of Figure 12 is extended a little more, we will arrive at the Am2901A as depicted in Figure 13. Here, we have redrawn the structure so that the registers are placed above the ALU; however, the function is identical. Two new functions have been added to this block diagram that have not previously been discussed. These are the RAM shift matrix located directly above the sixteen registers now described as a 16 x 4 dual port RAM. The purpose of the RAM shift network is to allow the ability of shifting the data word to be written into the register either up one bit position or down one bit position. The second function added to the block diagram is that of the Q register and shift network. Here, the Q register is used as an auxiliary register such that double length operations can be performed and it is also used in the multiply and divide algorithms. In addition, the shift network allows the Q register contents to be shifted up one bit position or shifted down one bit position. In addition, it should be pointed out that the memory address register is not part of the Am2901A. This is because there were not enough pins on the package to implement the function and the additional power required by the output buffers would have reduced the performance of the ALU and register stack. Instead, this function is being designed into other 2900 family products.

Am2901A ARCHITECTURE

A detailed block diagram of the Am2901A bipolar microprogrammable microprocessor structure is shown in Figure 14. The circuit is a four-bit slice cascadable to any number of bits. Therefore, all data paths within the circuit are four bits wide. The two key elements in the Figure 14 block diagram are the 16-word by 4-bit 2-port RAM and the high-speed ALU.

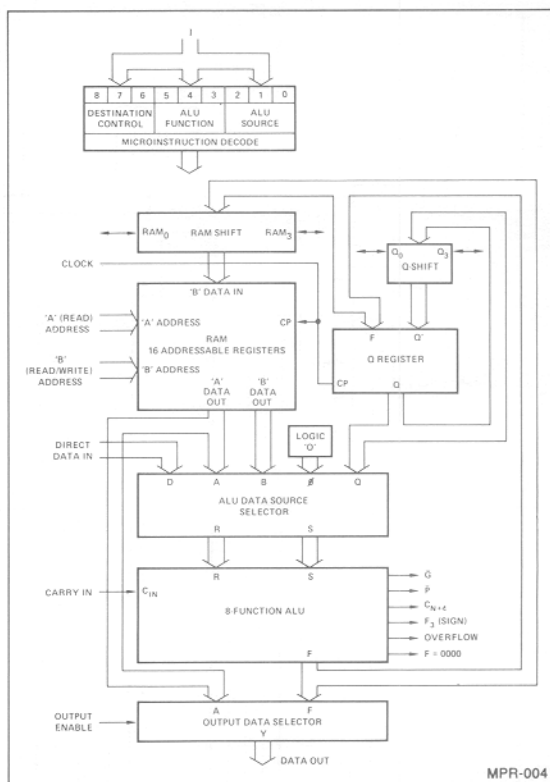


Figure 13. Am2901A Block Diagram.

Data in any of the 16 words of the Random Access Memory (RAM) can be read from the A-port of the RAM as controlled by the 4-bit A address field input. Likewise, data in any of the 16 words of the RAM as defined by the B address field input can be simultaneously read from the B-port of the RAM. The same code can be applied to the A select field and B select field in which case the identical file data will appear at both the RAM A-port and B-port outputs simultaneously.

When enabled by the RAM write enable (RAM EN), new data is always written into the file (word) defined by the B address field of the RAM. The RAM data input field is driven by a 3-input multiplexer. This configuration is used to shift the ALU output data (F) if desired. This three-input multiplexer scheme allows the data to be shifted up one bit position, shifted down one bit position, or not shifted in either direction.

The RAM A-port data outputs and RAM B-port data outputs drive separate 4-bit latches. These latches hold the RAM data while the clock input is LOW. This eliminates any possible race conditions that could occur while new data is being written into the RAM.

The high-speed Arithmetic Logic Unit (ALU) can perform three binary arithmetic and five logic operations on the two 4-bit input words R and S. The R input field is driven from a 2-input multiplexer, while the S input field is driven from a 3-input multiplexer. Both multiplexers also have an inhibit capability; that is, no data is passed. This is equivalent to a "zero" source operand.

Referring to Figure 14, the ALU R-input multiplexer has the RAM A-port and the direct data inputs (D) connected as inputs. Likewise, the ALU S-input multiplexer has the RAM A-port, the RAM B-port and the Q register connected as inputs.



MPR-005

This multiplexer scheme gives the capability of selecting various pairs of the A, B, D, Q and "0" inputs as source operands to the ALU. These five inputs, when taken two at a time, result in ten possible combinations of source operand pairs. These combinations include AB, AD, AQ, A0, BD, BQ, B0, DQ, D0 and Q0. It is apparent that AD, AQ and A0 are somewhat redundant with BD, BQ and B0 in that if the A address and B address are the same, the identical function results. Thus, there are only seven completely non-redundant source operand pairs for the ALU. The Am2901A microprocessor implements eight of these pairs. The microinstruction inputs used to select the ALU source operands are the I_0 , I_1 and I_2 inputs.

The two source operands not fully described as yet are the D input and Q input. The D input is the four-bit wide direct data field input. This port is used to insert all data into the working registers inside the device. Likewise, this input can be used in the ALU to modify any of the internal data files. The Q register is a separate 4-bit file intended primarily for multiplication and division routines but it can also be used as an accumulator or holding register for some applications.

The ALU itself is a high-speed arithmetic/logic operator capable of performing three binary arithmetic and five logic functions. The I_3 , I_4 and I_5 microinstruction inputs are used to select the ALU function. The definition of these functions is shown in Figure 15. The normal technique for cascading the ALU of several devices is in a look-ahead carry mode. Carry generate, \bar{G} , and carry propagate, \bar{P} , are outputs of the device for use with a carry-look-ahead-generator such as the Am2902A ('182). A carry-out, C_{n+4} , is also generated and is available as an output for use as the carry flag in a status register. Both carry-in (C_n) and carry-out (C_{n+4}) are active HIGH.

SOURCE OPERANDS		DESTINATION		
A, B	B, 0	SHIFT	LOAD	Y-OUT
A, D	D, 0	UP	RAM	F
A, Q	Q, 0	UP	RAM & Q	F
A, 0	D, Q	DOWN	RAM	F
		DOWN	RAM & Q	F
		NONE	NONE	F
		NONE	Q	F
		NONE	RAM	F
		NONE	RAM	A
ALU FUNCTIONS				
R+S	R OR S			
R-S	R AND S			
S-R	R EXOR S			
	R EXNOR S			
	R AND S			

Figure 15. Am2901A Microinstruction Control.

The ALU has three other status-oriented outputs. These are F_3 , $F = 0$, and overflow (OVR). The F_3 output is the most significant (sign) bit of the ALU and can be used to determine positive or negative results without enabling the three-state data outputs. F_3 is non-inverted with respect to the sign bit output Y_3 . The $F = 0$ output is used for zero detect. It is an open-collector output and can be wire OR'ed between microprocessor slices. $F = 0$ is HIGH when all F outputs are LOW. The overflow output (OVR) is used to flag arithmetic operations that exceed the available two's complement number range. The overflow output (OVR) is HIGH when overflow exists; that is, when C_{n+3} and C_{n+4} are not the same polarity.

The ALU data output is routed to several destinations. It can be a data output of the device and it can also be stored in the RAM or the Q register. Eight possible combinations of ALU destination functions are available as defined by the I_6 , I_7 and I_8 microinstruction inputs. These combinations are shown in Figure 15.

The four-bit data output field (Y) features three-state outputs and can be directly bus organized. An output control (\bar{OE}) is used to enable the three-state outputs. When \bar{OE} is HIGH, the Y outputs are in the high-impedance state.

A two-input multiplexer is also used at the data output such that either the A-port of the RAM or the ALU outputs (F) are selected at the device Y outputs. This selection is controlled by the I_6 , I_7 and I_8 microinstruction inputs.

As was discussed previously, the RAM inputs are driven from a three-input multiplexer. This allows the ALU outputs to be entered non-shifted, shifted up one position ($\times 2$) or shifted down one position ($\div 2$). The shifter has two ports; one is labeled RAM_0 and the other is labeled RAM_3 . Both of these ports consist of a buffer-driver with a three-state output and an input to the multiplexer. Thus, in the shift up mode, the RAM_3 buffer is enabled and the RAM_0 multiplexer input is enabled. Likewise, in the shift down mode, the RAM_0 buffer and RAM_3 input are enabled. In the no-shift mode, both buffers are in the high-impedance state and the multiplexer inputs are not selected. This shifter is controlled from the I_6 , I_7 and I_8 microinstruction inputs.

Similarly, the Q register is driven from a 3-input multiplexer. In the no-shift mode, the multiplexer enters the ALU data into the Q register. In either the shift-up or shift-down mode, the multiplexer selects the Q register data appropriately shifted up or down. The Q shifter also has two ports; one is labeled Q_0 and the other is Q_3 . The operation of these two ports is similar to the RAM shifter and is also controlled from I_6 , I_7 and I_8 .

The clock input to the Am2901A controls the RAM, the Q register, and the A and B data latches. When enabled, data is clocked into the Q register on the LOW-to-HIGH transition of the clock. When the clock input is HIGH, the A and B latches are open and will pass whatever data is present at the RAM outputs. When the clock input is LOW, the latches are closed and will retain the last data entered. If the RAM-EN is enabled, new data will be written into the RAM file (word) defined by the B address field when the clock input is LOW.

Am2903 GENERAL DESCRIPTION

The Am2903 is a four-bit expandable bipolar microprocessor slice that performs all functions performed by the industry standard Am2901A. In addition, it provides a number of significant enhancements that are especially useful in arithmetic oriented processors. The Am2903 contains sixteen internal working registers arranged in a two address architecture and it also provides all of the necessary signals to expand the register file externally using the Am29705 register stack. Any number of registers can be cascaded to the Am2903 using this technique. In addition to its complete arithmetic and logic instruction set, the Am2903 provides a special set of instructions which facilitate the implementation of multiplication, division, normalization and other previously time consuming operations such as parity generation and sign extension. A block diagram of the Am2903 is shown in Figure 16.

ARCHITECTURE OF THE Am2903

The Am2903 is a high-performance, cascadable, four-bit bipolar microprocessor slice designed for use in CPU's, peripheral controllers, microprogrammable machines, and numerous other applications. The microinstruction flexibility of the Am2903 allows the efficient emulation of almost any digital computing machine.

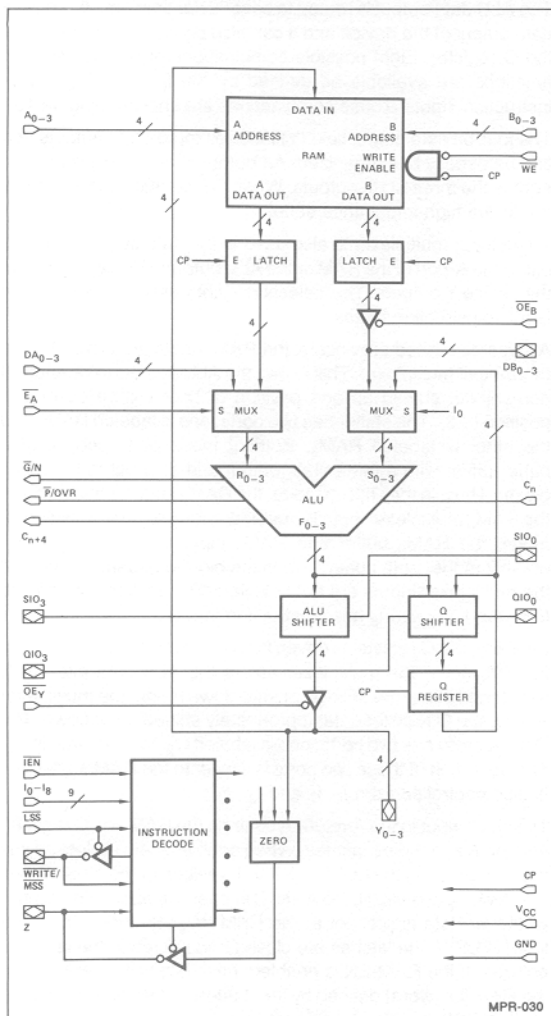


Figure 16. Basic Am2903 Block Diagram.

The nine-bit microinstruction selects the ALU sources, function, and destination. The Am2903 is cascadable with full lookahead or ripple carry, has three-state outputs, and provides various ALU status flag outputs. Advanced Low-Power Schottky processing is used to fabricate this 48-pin LSI circuit.

All data paths within the device are four bits wide. As shown in the block diagram of Figure 16, the device consists of a 16-word by 4-bit, two-port RAM with latches on both output ports, a high-performance ALU and shifter, a multi-purpose Q Register with shifter input, and a nine-bit instruction decoder.

Two-Port RAM

Any two RAM words addressed at the A and B address ports can be read simultaneously at the respective RAM A and B output ports. Identical data appear at the two output ports when the same address is applied to both address ports. The latches at the RAM output ports are transparent when the clock input, CP, is HIGH and they hold the RAM output data when CP is LOW. Under control of the \overline{OE}_B three-state output enable, RAM data can be read directly at the Am2903 DB I/O port.

External data at the Am2903 Y I/O port can be written directly into the RAM, or ALU shifter output data can be enabled onto the Y I/O port and entered into the RAM. Data is written into the RAM at the B address when the write enable input, \overline{WE} , is LOW and the clock input, CP, is LOW.

Arithmetic Logic Unit

The Am2903 high-performance ALU can perform seven arithmetic and nine logic operations on two 4-bit operands. Multiplexers at the ALU inputs provide the capability to select various pairs of ALU source operands. The \overline{E}_A input selects either the DA external data input or RAM output port A for use as one ALU operand and the \overline{OE}_B and I_0 inputs select RAM output port B, DB external data input, or the Q Register content for use as the second ALU operand. Also, during some ALU operations, zeros are forced at the ALU operand inputs. Thus, the Am2903 ALU can operate on data from two external sources, from an internal and external source, or from two internal sources.

When instruction bits I_4 , I_3 , I_2 , I_1 and I_0 are LOW, the Am2903 executes special functions. Figure 17 defines these special functions and the operation which the ALU performs for each. When the Am2903 executes instructions other than the nine special functions, the ALU operation is determined by instruction bits I_4 , I_3 , I_2 and I_1 . Figure 18 defines the ALU operation as a function of these four instruction bits.

Am2903s may be cascaded in either a ripple carry or lookahead carry fashion. When a number of Am2903s are cascaded, each slice must be programmed to be a most significant slice (MSS), intermediate slice (IS), or least significant slice (LSS) of the array. The carry generate, \overline{G} , and carry propagate, \overline{P} , signals required for a lookahead carry scheme are generated by the Am2903 and are available as outputs of the least significant and intermediate slices.

The Am2903 also generates a carry-out signal, C_{n+4} , which is generally available as an output of each slice. Both the carry-in, C_n , and carry-out, C_{n+4} , signals are active HIGH. The ALU generates two other status outputs. These are negative, N, and overflow, OVR. The N output is generally the most significant (sign) bit of the ALU output and can be used to determine positive or negative results. The OVR output indicates that the arithmetic operation being performed exceeds the available two's complement number range. The N and OVR signals are available as outputs of the most significant slice. Thus, the multi-purpose \overline{G}/N and \overline{P}/OVR outputs indicate \overline{G} and \overline{P} at the least significant and intermediate slices, and sign and overflow at the most significant slice. To some extent, the meaning of the C_{n+4} , \overline{P}/OVR , and \overline{G}/N signals vary with the ALU function being performed.

ALU Shifter

Under instruction control, the ALU shifter passes the ALU output (F) non-shifted, shifts it up one bit position (2F), or shifts it down one bit position (F/2). Both arithmetic and logical shift operations are possible. An arithmetic shift operation shifts data around the most significant (sign) bit position of the most significant slice, and a logical shift operation shifts data through this bit position (see Figure 19). SIO_0 and SIO_3 are bidirectional serial shift inputs/outputs. During a shift-up operation, SIO_0 is generally a serial shift input and SIO_3 a serial shift output. During a shift-down operation, SIO_3 is generally a serial shift input and SIO_0 a serial shift output.

The ALU shifter also provides the capability to sign extend at slice boundaries. Under instruction control, the SIO_0 (sign) input can be extended through Y_0 , Y_1 , Y_2 , Y_3 and propagated to the SIO_3 output.

I ₈	I ₇	I ₆	I ₅	Hex Code	Special Function	ALU Function	ALU Shifter Function	SIO ₃		SIO ₀	Q Reg & Shifter Function	QIO ₃	QIO ₀	WRITE
								Most Sig. Slice	Other Slices					
L	L	L	L	0	Unsigned Multiply	$F = S + C_n$ if $Z = L$ $F = R + S + C_n$ if $Z = H$	Log. F/2→Y (Note 1)	Hi-Z	Input	F ₀	Log. Q/2→Q	Input	Q ₀	L
L	L	H	L	2	Two's Complement Multiply	$F = S + C_n$ if $Z = L$ $F = R + S + C_n$ if $Z = H$	Log. F/2→Y (Note 2)	Hi-Z	Input	F ₀	Log. Q/2→Q	Input	Q ₀	L
L	H	L	L	4	Increment by One or Two	$F = S + 1 + C_n$	$F \rightarrow Y$	Input	Input	Parity	Hold	Hi-Z	Hi-Z	L
L	H	L	H	5	Sign/Magnitude-Two's Complement	$F = S + C_n$ if $Z = L$ $F = S + C_n$ if $Z = H$	$F \rightarrow Y$ (Note 3)	Input	Input	Parity	Hold	Hi-Z	Hi-Z	L
L	H	H	L	6	Two's Complement Multiply, Last Cycle	$F = S + C_n$ if $Z = L$ $F = S - R - 1 + C_n$ if $Z = H$	Log. F/2→Y (Note 2)	Hi-Z	Input	F ₀	Log. Q/2→Q	Input	Q ₀	L
H	L	L	L	8	Single Length Normalize	$F = S + C_n$	$F \rightarrow Y$	F ₃	F ₃	Hi-Z	Log. 2Q→Q	Q ₃	Input	L
H	L	H	L	A	Double Length Normalize and First Divide Op.	$F = S + C_n$	Log 2F→Y	$R_3 \nabla F_3$	F ₃	Input	Log. 2Q→Q	Q ₃	Input	L
H	H	L	L	C	Two's Complement Divide	$F = S + R + C_n$ if $Z = L$ $F = S - R - 1 + C_n$ if $Z = H$	Log. 2F→Y	$R_3 \nabla F_3$	F ₃	Input	Log. 2Q→Q	Q ₃	Input	L
H	H	H	L	E	Two's Complement Divide, Correction and Remainder	$F = S + R + C_n$ if $Z = L$ $F = S - R - 1 + C_n$ if $Z = H$	$F \rightarrow Y$	F ₃	F ₃	Hi-Z	Log. 2Q→Q	Q ₃	Input	L

NOTES: 1. At the most significant slice only, the C_{n+4} signal is internally gated to the Y₃ output.
2. At the most significant slice only, $F_3 \nabla OVR$ is internally gated to the Y₃ output.
3. At the most significant slice only, $S_3 \nabla F_3$ is generated at the Y₃ output.
4. Op codes 1, 3, 7, 9, B, D, and F are reserved for future use.

L = LOW
H = HIGH
X = Don't Care

Hi-Z = High Impedance
 ∇ = Exclusive OR
Parity = $SIO_3 \nabla F_3 \nabla F_2 \nabla F_1 \nabla F_0$

Figure 17. Special Functions: $I_0 = I_1 = I_2 = I_3 = I_4 = \text{LOW}$, $\overline{IEN} = \text{LOW}$.

I ₄	I ₃	I ₂	I ₁	Hex Code	ALU Functions
L	L	L	L	0	$I_0 = L$ Special Functions $I_0 = H$ $F_i = \text{HIGH}$
L	L	L	H	1	$F = S \text{ Minus } R \text{ Minus } 1 \text{ Plus } C_n$
L	L	H	L	2	$F = R \text{ Minus } S \text{ Minus } 1 \text{ Plus } C_n$
L	L	H	H	3	$F = R \text{ Plus } S \text{ Plus } C_n$
L	H	L	L	4	$F = S \text{ Plus } C_n$
L	H	L	H	5	$F = \overline{S} \text{ Plus } C_n$
L	H	H	L	6	$F = R \text{ Plus } C_n$
L	H	H	H	7	$F = \overline{R} \text{ Plus } C_n$
H	L	L	L	8	$F_i = \text{LOW}$
H	L	L	H	9	$F_i = \overline{R}_i \text{ AND } S_i$
H	L	H	L	A	$F_i = R_i \text{ EXCLUSIVE NOR } S_i$
H	L	H	H	B	$F_i = R_i \text{ EXCLUSIVE OR } S_i$
H	H	L	L	C	$F_i = R_i \text{ AND } S_i$
H	H	L	H	D	$F_i = R_i \text{ NOR } S_i$
H	H	H	L	E	$F_i = R_i \text{ NAND } S_i$
H	H	H	H	F	$F_i = R_i \text{ OR } S_i$

L = LOW

H = HIGH

i = 0 to 3

Figure 18. ALU Functions.

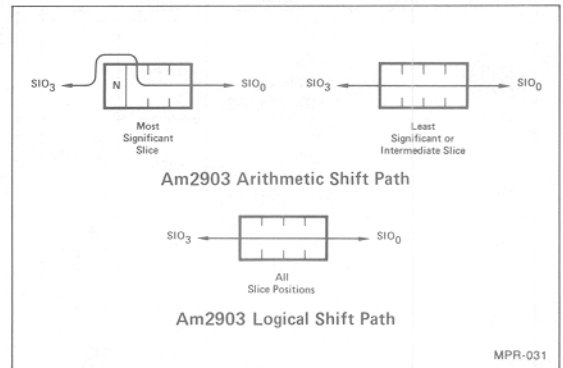


Figure 19.

The instruction inputs determine the ALU shifter operation. Figure 17 defines the special functions and the operation the ALU shifter performs for each. When the Am2903 executes instructions other than the nine special functions, the ALU shifter operation is determined by instruction bits $I_8 I_7 I_6 I_5$. Figure 20 defines the ALU shifter operation as a function of these four bits.

Q Register

The Q Register is an auxiliary four-bit register which is clocked on the LOW-to-HIGH transition of the CP input. It is intended primarily for use in multiplication and division operations; however, it can also be used as an accumulator or holding register for some applications. The ALU output, F, can be loaded into the Q Register, and/or the Q Register can be selected as the source for the ALU S operand. The shifter at the input to the Q Register provides

A cascadable, five-bit parity generator/checker is designed into the Am2903 ALU shifter and provides ALU error detection capability. Parity for the F₀, F₁, F₂, F₃ ALU outputs and SIO₃ input is generated and, under instruction control, is made available at the SIO₀ output.

I ₈	I ₇	I ₆	I ₅	Hex Code	ALU Shifter Function	SIO ₃		Y ₃		Y ₂		Y ₁	Y ₀	SIO ₀	Write	Q Reg & Shifter Function	QIO ₃	QIO ₀
						Most Sig. Slice	Other Slices	Most Sig. Slice	Other Slices	Most Sig. Slice	Other Slices							
L	L	L	L	0	Arith. F/2→Y	Input	Input	F ₃	SIO ₃	SIO ₃	F ₃	F ₂	F ₁	F ₀	L	Hold	Hi-Z	Hi-Z
L	L	L	H	1	Log. F/2→Y	Input	Input	SIO ₃	SIO ₃	F ₃	F ₃	F ₂	F ₁	F ₀	L	Hold	Hi-Z	Hi-Z
L	L	H	L	2	Arith. F/2→Y	Input	Input	F ₃	SIO ₃	SIO ₃	F ₃	F ₂	F ₁	F ₀	L	Log. Q/2→Q	Input	Q ₀
L	L	H	H	3	Log. F/2→Y	Input	Input	SIO ₃	SIO ₃	F ₃	F ₃	F ₂	F ₁	F ₀	L	Log. Q/2→Q	Input	Q ₀
L	H	L	L	4	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	L	Hold	Hi-Z	Hi-Z
L	H	L	H	5	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	H	Log. Q/2→Q	Input	Q ₀
L	H	H	L	6	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	H	F→Q	Hi-Z	Hi-Z
L	H	H	H	7	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	L	F→Q	Hi-Z	Hi-Z
H	L	L	L	8	Arith. 2F→Y	F ₂	F ₃	F ₃	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	L	L	H	9	Log. 2F→Y	F ₃	F ₃	F ₂	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	L	H	L	A	Arith. 2F→Y	F ₂	F ₃	F ₃	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Log. 2Q→Q	Q ₃	Input
H	L	H	H	B	Log. 2F→Y	F ₃	F ₃	F ₂	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Log. 2Q→Q	Q ₃	Input
H	H	L	L	C	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	H	Hold	Hi-Z	Hi-Z
H	H	L	H	D	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	H	Log. 2Q→Q	Q ₃	Input
H	H	H	L	E	SIO ₀ →Y ₀ , Y ₁ , Y ₂ , Y ₃	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	H	H	H	F	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	L	Hold	Hi-Z	Hi-Z

Parity = $F_3 \nabla F_2 \nabla F_1 \nabla F_0 \nabla SIO_3$
 ∇ = Exclusive OR

L = LOW
H = HIGH

Hi-Z = High Impedance

Figure 20a. ALU Destination Control for I₀ or I₁ or I₂ or I₃ or I₄ = HIGH, \overline{IEN} = LOW.

OPERATION		ALU SHIFTER	RAM WRITE	Q
SINGLE LENGTH SHIFT		UP DOWN ARITH UP ARITH DOWN	YES	NC
DOUBLE LENGTH SHIFT		UP DOWN ARITH UP ARITH DOWN	YES	UP DOWN UP DOWN
Q-SHIFT		PASS	NO	UP DOWN
LOAD	RAM	PASS	YES	NC
	RAM & Q		YES	LOAD
	Q		NO	LOAD
	NONE		NO	NC
SIGN EXTEND		SIO ₀	YES	NC

NC = No Change

Figure 20b. Am2903 ALU Destination Control Summary.

the capability to shift the Q Register contents up one bit position (2Q) or down one bit position (Q/2). Only logical shifts are performed. QIO₀ and QIO₃ are bidirectional shift serial inputs/outputs. During a Q Register shift-up operation, QIO₀ is a serial shift input and QIO₃ is a serial shift output. During a shift-down operation, QIO₃ is a serial shift input and QIO₀ is a serial shift output.

Double-length arithmetic and logical shifting capability is provided by the Am2903. The double-length shift is performed by connecting QIO₃ of the most significant slice to SIO₀ of the least significant slice, and executing an instruction which shifts both the ALU output and the Q Register.

The Q Register and shifter operation is controlled by instruction bits I₈I₇I₆I₅. Figures 17 and 20 define the Q Register and shifter operation as a function of these four bits.

Output Buffers

The DB and Y ports are bidirectional I/O ports driven by three-state output buffers with external output enable controls. The Y output buffers are enabled when the \overline{OE}_Y input is LOW and are in the high-impedance state when \overline{OE}_Y is HIGH. Likewise, the DB output buffers are enabled when the \overline{OE}_B input is LOW and in the high-impedance state when \overline{OE}_B is HIGH.

The zero, Z, pin is an open collector input/output that can be wire-OR'ed between slices. As an output it can be used as a zero detect status flag and generally indicates that the Y₀₋₃ pins are all LOW, whether they are driven from the Y output buffers or from an external source connected to the Y₀₋₃ pins. To some extent the meaning of this signal varies with the instruction being performed.


Instruction Decoder

The Instruction Decoder generates required internal control signals as a function of the nine Instruction inputs, I₀₋₈; the Instruction Enable input, \overline{IEN} ; the LSS input; and the WRITE/MSS input/output. The \overline{WRITE} output is LOW when an instruction which writes data into the RAM is being executed.

When \overline{IEN} is LOW, the \overline{WRITE} output is enabled and the Q Register and Sign Compare Flip-Flop can be written according to the Am2903 instruction. The Sign Compare Flip-Flop is an on-chip flip-flop which is used during an Am2903 divide operation.

Programming the Am2903 Slice Position

Tying the LSS input LOW programs the slice to operate as a least significant slice (LSS) and enables the \overline{WRITE} output signal onto the \overline{WRITE}/MSS bidirectional I/O pin. When LSS is tied HIGH, the \overline{WRITE}/MSS pin becomes an input pin; tying the \overline{WRITE}/MSS pin HIGH programs the slice to operate as an intermediate slice (IS) and tying it LOW programs the slice to operate as a most significant slice (MSS). This is shown in Figure 21.

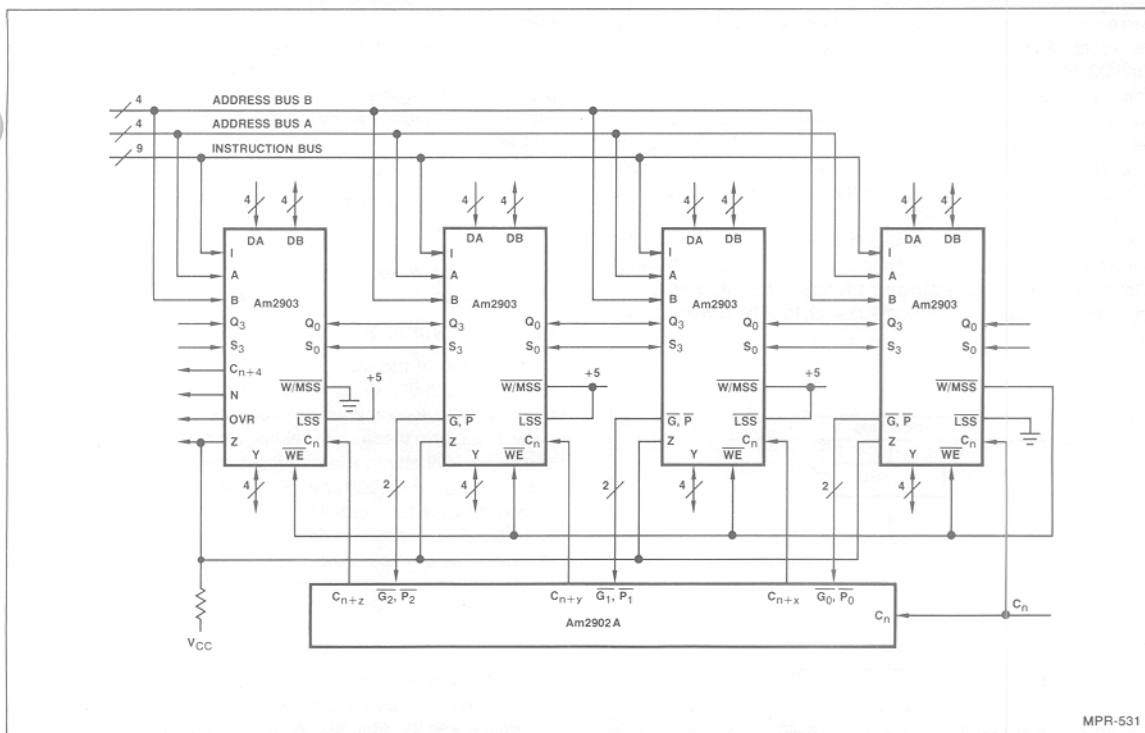


MPR-531

Figure 21. Am2903 - 16-Bit CPU with Carry Look Ahead.

EXPANDING THE NUMBER OF Am2903 REGISTERS

The Am2903 contains 16 internal working registers configured in a standard two port architecture. The number of working registers in the ALU configuration can be increased by utilizing the Am29705 16-word by 4-bit two-port RAM. Any number of Am29705's can be connected to the Am2903 to increase the number of working registers. Figure 22 shows a block diagram of the basic Am29705. As is seen, the device consists of a 16 word by 4 bit two port RAM with latches at the A and B outputs similar to the RAM contained within the Am2903. Each of the latch outputs has three state drivers capable of driving the DA and DB inputs of the Am2903. The Am29705 is a non-inverting device. That is, data presented at the inputs is stored in the RAM and when brought to the RAM outputs, it is non-inverted from when it was originally brought into the device.

The technique for using the Am29705 to expand the number of registers in the Am2903 can best be visualized by referring to Figures 23 and 24 simultaneously. In Figure 23, the data bus connections are shown such that the Am2903 Y output is used to drive the Am29705 inputs. Here, we also assume this bus may be tied to a data bus through a bi-directional buffer. In Figure 23, the A outputs of the Am29705 are connected together and also connected to the DA input of the Am2903. Likewise, the B outputs of the Am29705 are also shown connected to the DB inputs of the Am2903. In all cases, we are assuming 16-bit data busses. Thus, four Am2903's are assumed and eight Am29705's are assumed. As shown in Figure 23, one of the write enable inputs to the Am29705 is tied to the latch enable input of the Am2903 and these pins are also tied to the clock input of the Am2903. This allows the latches in the Am29705 to perform identically to those in the Am2903.

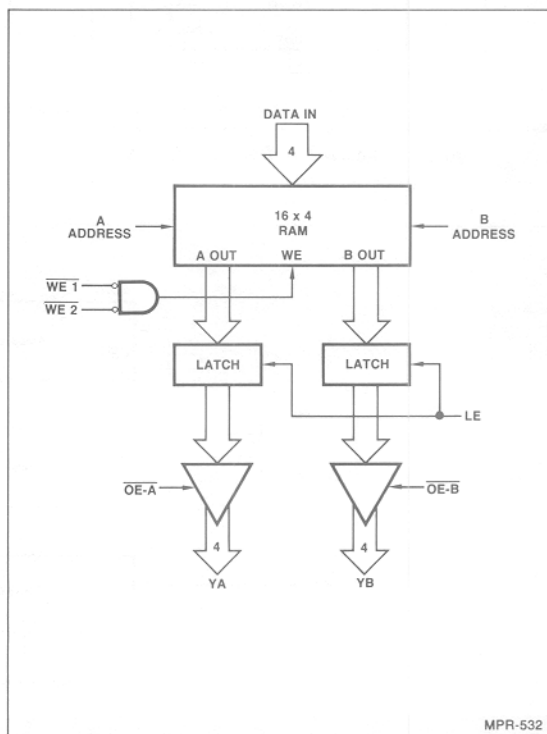

MPR-532

Figure 22. Am29705 Block Diagram.

If we refer to Figure 24, we see the connections required to set up the addressing for additional registers associated with the Am2903. Here, three two-line to four-line decoders are used to properly control the A address, B address and write enable signals to the devices. As shown in Figure 24, the four A address lines are all tied in parallel between the Am2903 and the Am29705's. The two-line to four-line decoder is used to enable the appropriate output enable from the Am29705's or switch the EA MUX inside the Am2903 such that the proper register is selected. The B address operates in a similar fashion in that the four B address lines are also all tied together. Likewise, a two-line to four-line decoder is used to properly select the output enable of either the Am29705's or the Am2903 such that the correct source

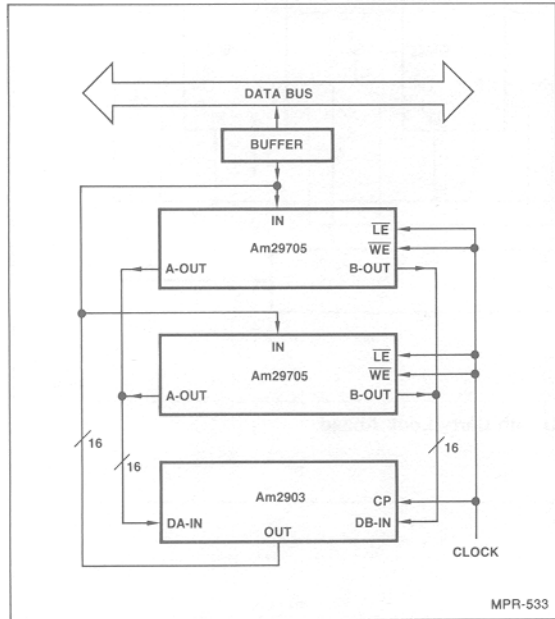


Figure 23. Am2903 - Data Bus Cascading.

operand register is selected. In addition, a two-line to four-line decoder is used to control the write enable signal such that only one register is written into as a destination. This is controlled by properly selecting the write enable of either the Am2903 or the Am29705 as determined by the two most significant bits of the B address.

If this technique is used properly, any number of Am29705's can be used in conjunction with the Am2903. It may be necessary to use either a three-line to eight-line decoder or perhaps even a larger circuit to decode the more significant bits of the A and B addresses. Likewise, the write enable signal must be controlled so that the correct destination register will be written.

UNDERSTANDING BIT SLICE TIMING

Perhaps one of the most important aspects of designing with either the Am2901A or the Am2903 is understanding the calculations required to compute the worst case AC performance. In order to perform these calculations, we have selected a number of standard Schottky devices and assigned minimum, typical and maximum speeds at 25°C and 5V for use in these calculations as shown in Figure 25. Certainly the design engineer should use the exact specifications of the devices he has selected for his design in order to perform the worst case calculations. What is intended here is an understanding of the technique to perform these calculations and some method to allow a comparison of the Am2901A and Am2903 in terms of their AC performance. Since at the time of this writing the Am2903 is still being characterized, only the typical AC data is currently available. Thus, all calculations will be made using the typical AC times such that we can compare the Am2901A with the Am2903. When final characterization data on the Am2903 is available, the designer can then compute its performance by selecting the appropriate temperature range and power supply variations as required by his design.

Figure 26 shows the typical AC calculations for the functions usually considered in an Am2901A design. These functions are usually the speed for a logic operation, arithmetic operation, logic operation with shift and arithmetic operation with shift. In each case, we are computing speeds from the LOW-to-HIGH transition of a clock through an entire microcycle to the next LOW-to-HIGH transition of a clock.

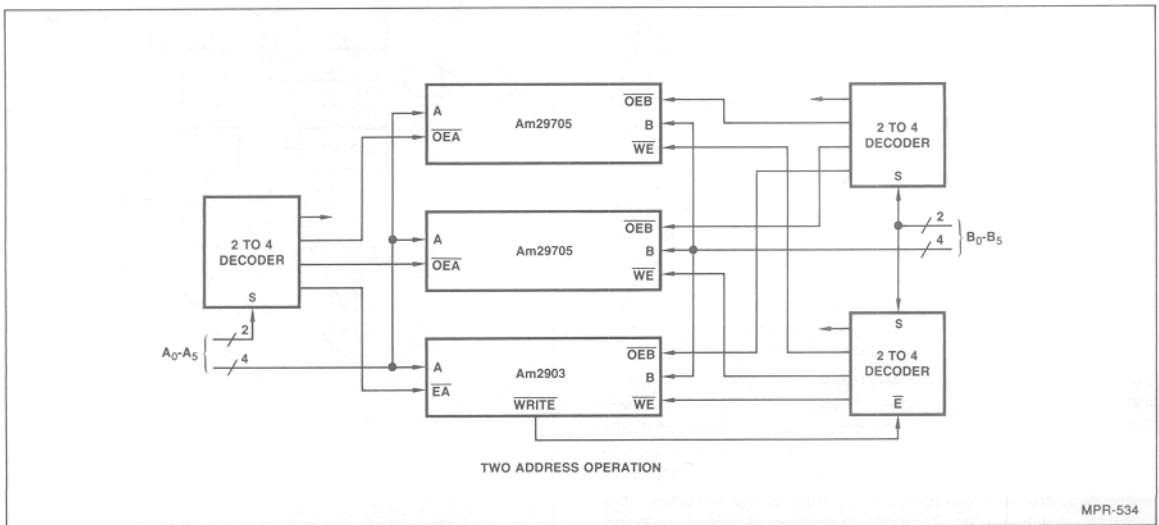


Figure 24. Am2903 - RAM Address Cascading.

DEVICE & PATH	MIN.	TYP.	MAX.
S Register			
Clock to Output		9	15
OE to Output		13	20
Set-Up	5	2	
S MUX			
Data to Output		5	8
Select to Output		12	18
OE to Output		13	20
Microprogram PROM			
Address to Output		30	50
OE to Output		18	25
Mapping PROM			
Address to Output		25	45
OE to Output		18	25
Decoder			
Select to Output		8	12
Counter			
Clock to Q		9	13
Clock to TC		12	18
CET to TC		8	12
Data Set-Up	8	4	
Load Set-Up	16	10	
CEP or CET Set-Up	12	7	
S-EXOR			
IN to OUT		7	11
Am2922			
Clock to Output		21	32
Data to Output		13	19
OE to Output		10	17
Data Set-Up	10	5	
Am29811A			
Input to Output		25	35
Am29803A			
Input to Output		25	35
Am2902A			
C_n to $C_{n+x,y,z}$		7	11
G, P to G, P		7	10
G, P to $C_{n+x,y,z}$		5	7


Figure 25. Standard Device Schottky Speeds.

Similarly, Figure 27 shows the same type of computations for an Am2903 system. There is one very important distinction that should be made in computing the timing of an Am2903 16-bit ALU when compared with an Am2901A ALU in that in the Am2903, the shifter is at the output of the ALU and is followed by the zero detector. Thus, in an Am2903 design, the flags are no longer

independent of the shift operation. This is easily seen in Figure 27.

By way of comparison, Figure 28 shows speeds for the four types of operations for the Am2901A 16-bit system as compared with the Am2903 16-bit system.

a)

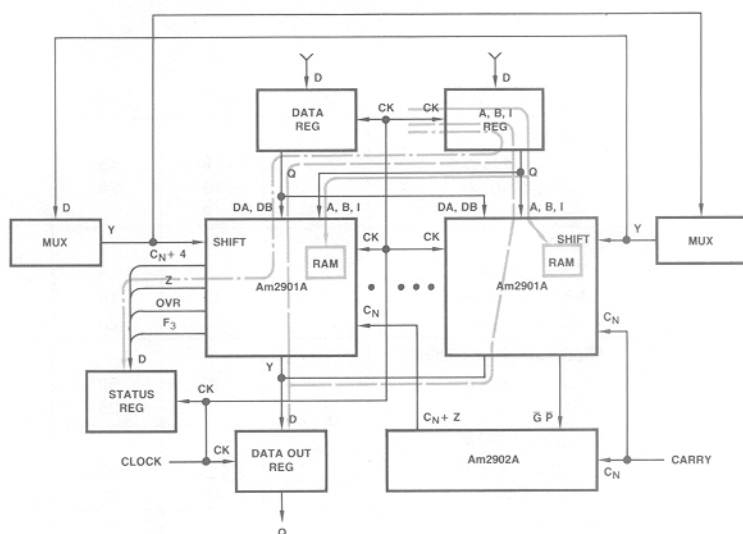


LOGIC OPERATION SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2901A	READ-MODIFY-WRITE	55	-	-
2901A	AB - Y	-	45	-
2901A	AB - Zero	-	-	65
S-REG	SET-UP D	-	2	2
TOTAL-ns		64	56	76

PATH 1 —————
 PATH 2 - - - - -
 PATH 3 - - - - -

MPR-535

b)

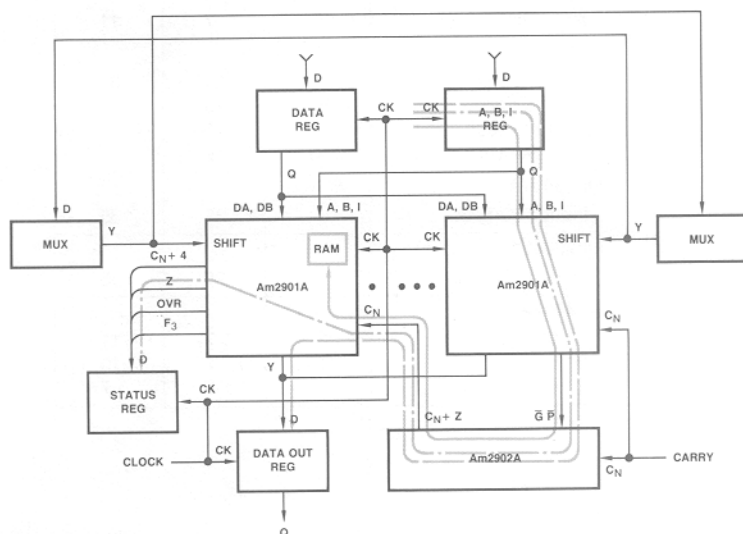

ARITHMETIC OPERATION SPEED COMPUTATIONS


DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S-REG	CP to Q	9	9	9
2901A	AB to GP	40	40	40
2902A	GP to $C_N + xyz$	5	5	5
2901A	SET-UP C_N	40	-	-
2901A	C_N to Y	-	20	-
2901A	C_N to Zero	-	-	35
S-REG	SET-UP D	-	2	2
TOTAL-ns		94	76	91

PATH 1 —————
 PATH 2 - - - - -
 PATH 3 - - - - -

MPR-536

Figure 26. Typical AC Calculations for the Am2901A.

c)

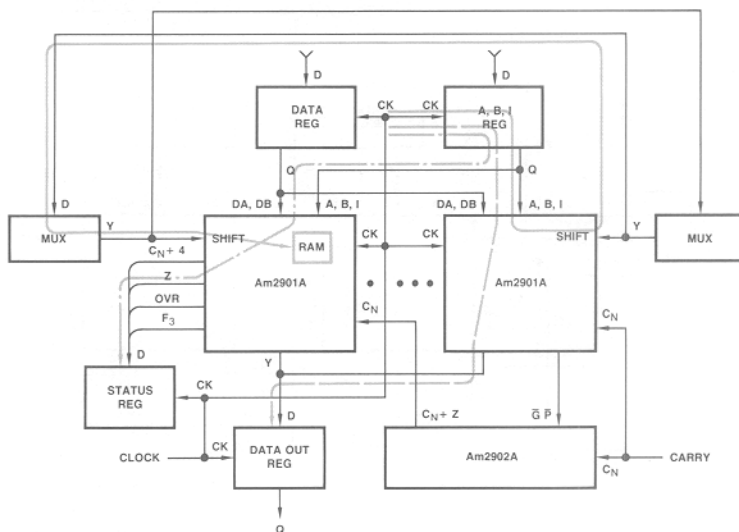


LOGIC OPERATION WITH SHIFT
SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2901A	AB to RAM ₀₃	60	-	-
S-MUX	D to Y	5	-	-
2901A	SET-UP RAM ₀₃	15	-	-
2901A	AB to Y	-	45	-
2901A	AB to Z	-	-	65
S-REG	SET-UP D	-	2	2
TOTAL-ns		89	56	76

PATH 1 —————
PATH 2 - - - - -
PATH 3 - - - - -

MPR-537

d)

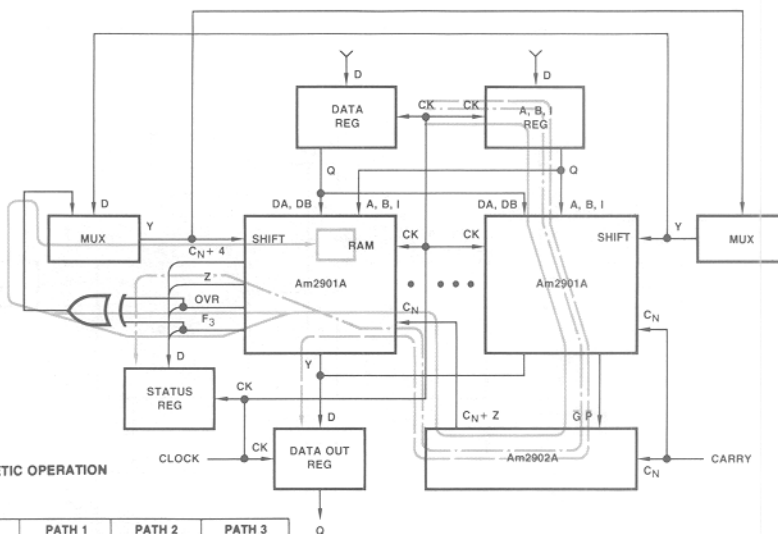

TWO'S COMPLEMENT ARITHMETIC OPERATION
WITH SHIFT DOWN
SPEED COMPUTATIONS


DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2901A	AB to GP	40	40	40
2902A	GP to C _N +xyz	5	5	5
2901A	C _N to F ₃ , OVR	20	-	-
S-EXOR	IN - OUT	7	-	-
S-MUX	D to Y	5	-	-
2901A	SET-UP RAM ₃	15	-	-
2901A	C _N to Y	-	20	-
2901A	C _N to Zero	-	-	35
S-REG	SET-UP D	-	2	2
TOTAL-ns		101	76	91

PATH 1 —————
PATH 2 - - - - -
PATH 3 - - - - -

MPR-538

Figure 26. (Cont.)

e)

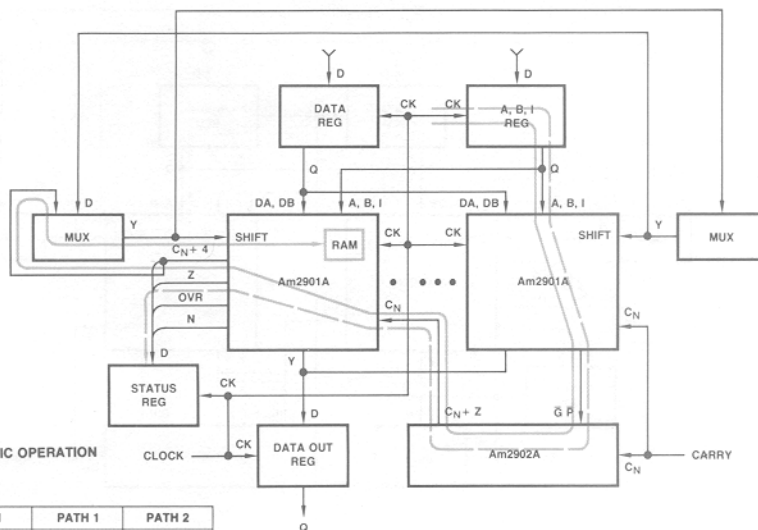

MAGNITUDE ONLY ARITHMETIC OPERATION
WITH SHIFT DOWN
SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2
S - REG	CP to Q	9	9
2901A	AB to GP	40	40
2902A	GP to $C_N + xyz$	5	5
2901A	C_N to $C_N + 4$	10	-
S-MUX	D to Y	5	-
2901A	SET-UP RAM_3	15	-
2901A	C_N to Zero	-	35
S-REG	SET-UP D	-	2
TOTAL-ns		84	91


PATH 1

PATH 2

MPR-539

Figure 26. (Cont.)

a)

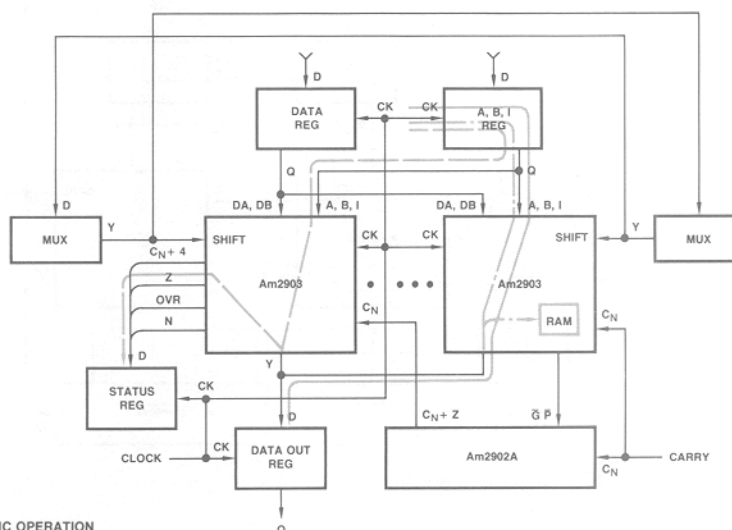

LOGIC OPERATION
SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2903	A, B to Y	56	56	56
2903	Y to Z	-	16	-
S-REG	SET-UP D	2	2	-
2903	SET-UP Y	-	-	9
TOTAL-ns		67	83	74

PATH 1


PATH 2

PATH 3

MPR-540

Figure 27. Typical AC Calculations for the Am2903.

b)

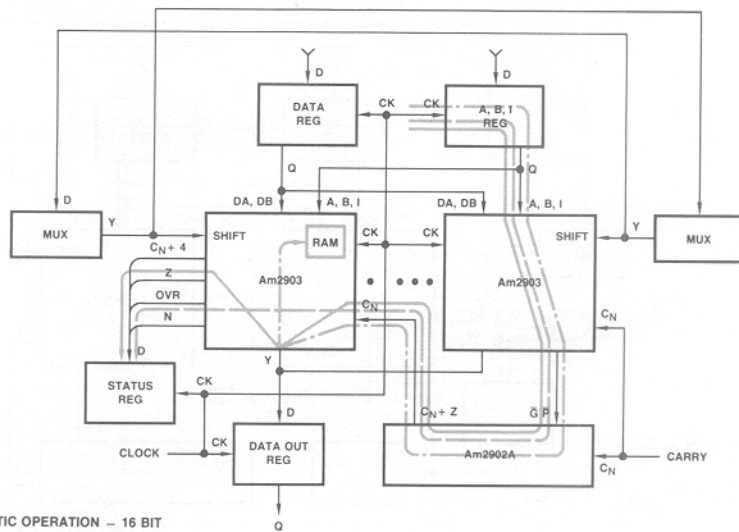


ARITHMETIC OPERATION - 16 BIT
SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S-REG	CP to Q	9	9	9
2903	A, B to G, P	56	56	56
2902A	G, P to C_{n+xyz}	5	5	5
2903	C_n to Y	25	-	25
2903	C_n to FLAG	-	38	-
2903	Y to Z	16	-	-
S-REG	SET-UP D	2	2	-
2903	SET-UP Y	-	-	9
TOTAL-ns		113	110	104

PATH 1 _____
PATH 2 _____
PATH 3 _____

MPR-541

c)

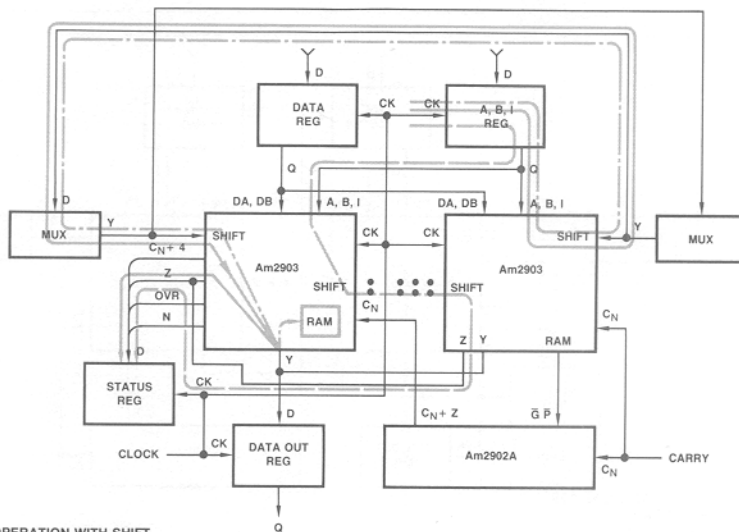

LOGIC OPERATION WITH SHIFT
SPEED COMPUTATIONS

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2903	A, B to S_0	64	64	64
MUX	D to Y	5	-	5
2903	S_3 to Y	13	13	13
2903	Y to Z	16	16	-
S-REG	SET-UP D	2	2	-
2903	SET-UP Y	-	-	9
TOTAL-ns		109	104	100

PATH 1 _____
PATH 2 _____
PATH 3 _____

MPR-542

Figure 27. (Cont.)

d)

**TWO'S COMPLEMENT ARITHMETIC OPERATION
WITH SHIFT DOWN - 16 BIT
SPEED COMPUTATIONS**

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2	PATH 3
S - REG	CP to Q	9	9	9
2903	A, B to G, P	56	56	56
2902A	GP to $C_n + xyz$	5	5	5
2903	C_n to SiO_0	21	-	-
2903	SiO_3 to Y	13	-	-
2903	C_n to N, OVR	-	38	38
S-EXOR	IN to OUT	-	7	7
S-MUX	D to Y	-	5	5
2903	SiO_3 to Y	-	13	13
2903	Y to Z	16	16	-
2903	SET-UP Y	-	-	9
S-REG	SET-UP D	2	2	-
TOTAL-ns		122	151	142

PATH 1 _____
PATH 2 _____
PATH 3 _____

MPR-543

e)

**MAGNITUDE ONLY ARITHMETIC OPERATION
WITH SHIFT DOWN
SPEED COMPUTATIONS**

DEVICE NO.	DEVICE PATH	PATH 1	PATH 2
S - REG	CP to Q	9	9
2903	A, B to G, P	56	56
2902A	GP to $C_n + xyz$	5	5
2903	C_n to $C_n + 4$	21	21
S-MUX	D to Y	5	5
2903	SiO_3 to Y	13	13
2903	Y to Z	16	-
S-REG	SET-UP D	2	-
2903	SET-UP Y	-	9
TOTAL-ns		127	118

PATH 1 _____
PATH 2 _____

MPR-544

Figure 27. (Cont.)

Functional Operation	Am2901A	Am2903
Logic	76	83
Arithmetic	94	113
Logic with Shift	89	109
Two's Complement Arithmetic with Shift Down	101	151
Magnitude Only Arithmetic with Shift Down	91	127

Figure 28. Summary of Am2901A and Am2903 AC Performance in a 16-Bit Configuration.

USING THE Am2903 IN A 16-BIT DESIGN

Perhaps the best technique for understanding the design of the 16-bit ALU is to simply take an example. Figure 29 shows a block diagram overview of four Am2903's with the appropriate shift matrix control, status register, MAR and the usual interface to a CCU and main memory. This block diagram represents the normal data handling path associated with a simple 16-bit minicomputer. If we expand this block diagram to show what would normally be considered to be the complete 16-bit central processing unit, the block diagram of Figure 30 results. Here, we see the Am2903's surrounded by a typical set of MSI support chips. In addition, the block diagram shows a typical computer control unit as described in Chapter 2 of this series. Thus, all of the blocks are

now in place to show a simple 16-bit microcomputer built using the Am2900 family devices. The full design for such a machine is shown in Figure 31.

Figures 31A, Figure 31B and Figure 31C detail the connection of each IC used in this design. Quite simply, the design can be described as follows. Figure 31A represents the microprogram sequencer portion of the design. U1, U2 and U3 are the instruction register that receive a 16-bit instruction from main memory. U4, U5 and U6 are the mapping PROMs used to decode the OP code portion of the instruction to arrive at a starting address for the microprogram sequencer. The microprogram sequencer is the Am2910 and is shown as U7. The branch address pipeline register is U8, U9 and U10 and can be enabled to the D inputs of the Am2910 sequencer to provide the jump address from microcode. The pipeline register for the instruction inputs to the Am2910 is U14. This machine also has the ability to select the A and B addresses for the Am2903 devices from the microprogram as well as the instruction register and U11 and U12 provide this capability as a part of the pipeline register. U13 is a two line to four line decoder used as part of the control for the A and B address select for the Am2903's. U15 is part of the pipeline register and provides both true and complement outputs for bit 11. U16 and U17 represent a one of sixteen decoder whose output can be applied to the DA bus to allow the implementation of all the bit operations. These include bit set, bit clear, bit toggle and bit test. U18 and U19 are PROM's that provide the ability to enter one of thirty-two preprogrammed constants onto the DA bus.

Figure 31B is predominately the data handling portion of the design. Here, U20 and U21 represent a data register that receives data from the data bus. U26, U27, U28 and U29 are the four Am2903's that form a 16-bit register/ALU combination. U30 is the carry look ahead generator for the ALU section. U22, U23


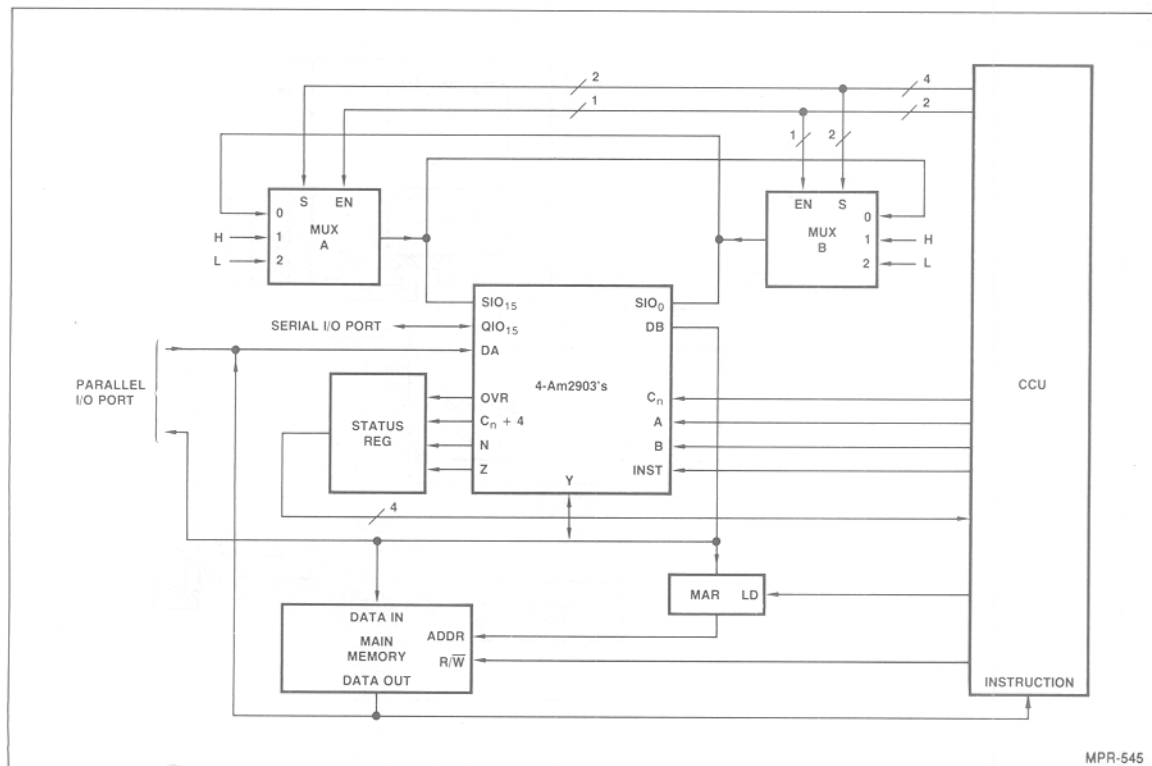


Figure 29. Am2903 with Shift Mux and Status Register.

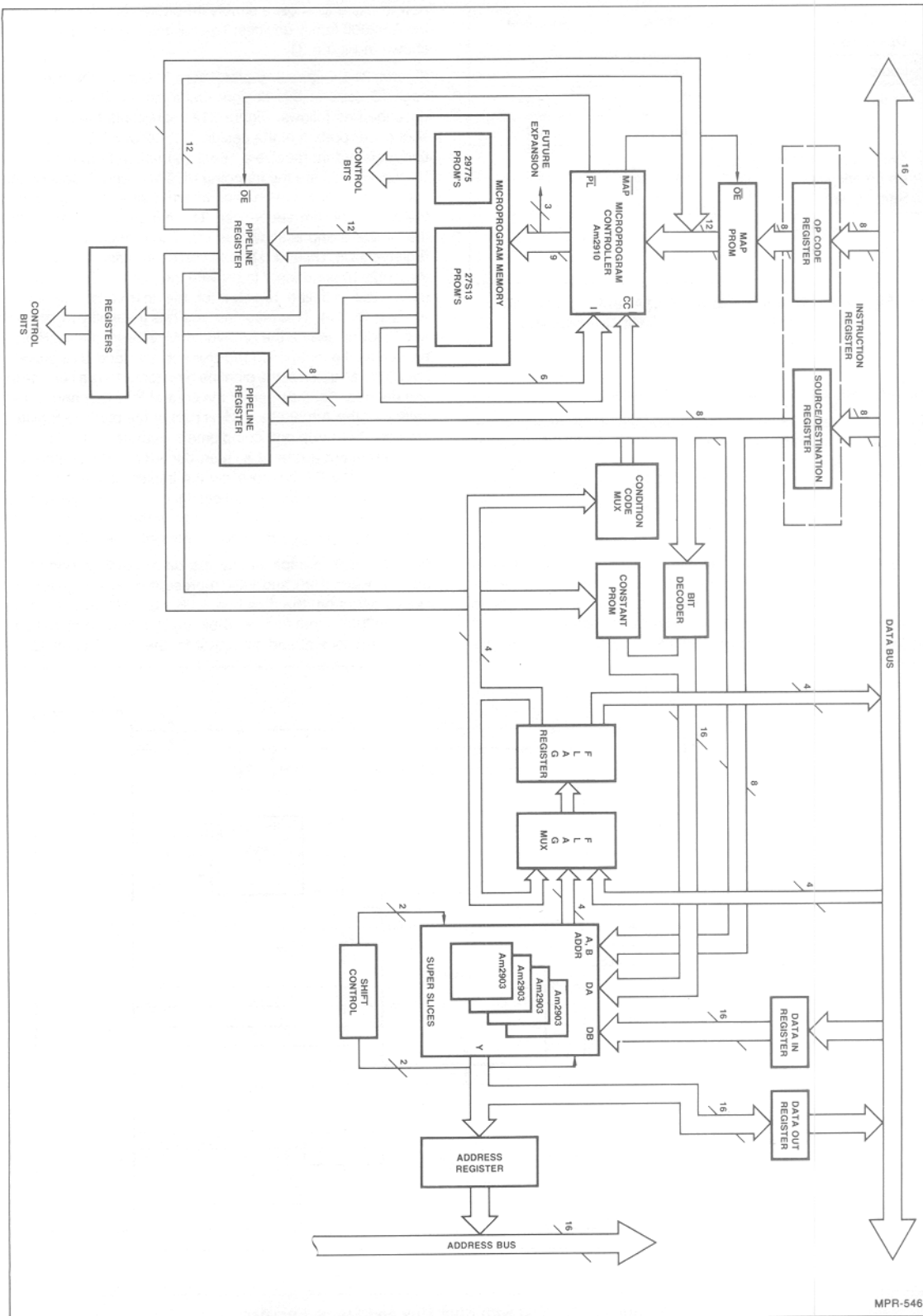

MPR-546

Figure 30.

and U24 represent the status register with the ability to save and restore the flags in main memory. U25 is the condition code multiplexer for the microprogram sequencer. U33, U34, U35 and U36 represent the shift linkage multiplexers that tie together the internal shifters within the Am2903's. U37 is part of the pipeline register and provides both true and complement outputs of a number of the microprogram bits. U38 is part of the carry in logic control such that double length arithmetic operations can be performed. U31 and U32 are the data out register that can be used to accept data from the Am2903s and enable this data onto the data bus. U39 and U40 represent the memory address register and are used to hold the address provided from the CPU to main memory.

The microprogram store is shown in Figure 31C. Here, we have used both the 512 x 8 registered PROM's and 512 x 4 non-registered PROM's in this design. A total of 68 microprogram bits have been depicted in this design. These are shown so that maximum flexibility is achieved. In most typical designs some 10 to 20 of these bits would not be used. Figure 31C shows four 512-word by 8-bit registered PROM's (U41, U42, U43 and U44). It also shows nine 512-word by 4-bit PROM's represented as U45 through U53.

Perhaps the best way to review the design is to simply understand the function of each of the microprogram control bits. If the purpose of each of these bits is well understood, the design engineer will be well along in understanding the design of the simple minicomputer CPU presented here.

The Microprogram Structure

The microprogram for the design shown in Figure 31 is 68 bits wide. The functions of the microprogram control bits are as follows:

Bits PL0 through PL8	The 9 instruction bits of the Am2903 superslices.
Bits PL9, PL10, PL11	The \overline{IEN} , \overline{EA} , \overline{OEB} control inputs of the Am2903 superslices, respectively. PL11 is also connected to the data-in registers (U20 and U21) output-enable. This connection assures that there will be no conflict on the DB pins.
Bits PL12 through PL14 ($\mu 12$ through $\mu 14$)	Select the source for SIO of the Am2903, both for shift-up and for shift-down operations. The following table summarizes the functions of these bits.

Microprogram Bits			SIO _n (Shift-down)		SIO _o (Shift-up)	
14	13	12				
L	L	L	0		0	
L	L	H	SIO _o		SIO _n	
L	H	L	QIO _o		QIO _n	
L	H	H	Carry		Carry	
H	L	L	Zero		Zero	
H	L	H	Sign		Sign	
H	H	L	Not allocated		Not allocated	
H	H	H	1		1	

Bits PL15 through PL17 ($\mu 15$ through $\mu 17$)	Select the source for QIO of the Am2903, both for shift-up and shift-down operations. The following table summarizes the functions of these bits.
--	---

Microprogram Bits			QIO _n (Shift-down)		QIO _o (Shift-up)	
17	16	15				
L	L	L	0		0	
L	L	H	SIO _o		SIO _n	
L	H	L	QIO _o		QIO _n	
L	H	H	Carry		Carry	
H	L	L	Zero		Zero	
H	L	H	Sign		Sign	
H	H	L	Not allocated		Not allocated	
H	H	H	1		1	

Bit PL18	When LOW, enables the MAR clock input, i.e. the data appearing on the Y output pins of the Am2903 Superslices™ will be clocked into the MAR at the LOW-to-HIGH transition of the clock pulse.
Bit PL19	When LOW, enables the MAR output onto the Memory Address Bus.
Bit PL20	When LOW, enables the data output register clock, i.e. the data appearing in the Y output pins of the Am2903 Superslices™ will be clocked into the data output registers (U31 and U32) at the LOW-to-HIGH transition of the clock pulse.
Bit PL21	When LOW, enables the data output registers onto the Data Bus.
Bit PL22	When LOW, enables the data-in register clock, i.e. the data appearing in the Data-Bus will be clocked into the data-in registers at the LOW-to-HIGH transition of the clock pulse.
Bit PL23	This is the CI input of the Am2910 microprogram sequencer.
Bits PL24 through PL27	This is a 4-bit wide field which can be used either for the A-address, for the B-address or for both A and B addresses of the Am2903 superslices.
Bits PL28 through PL31	This is a 4-bit wide field, which can be used for either the A-address of the Am2903 superslice or to designate one of sixteen bits to the DA inputs of the Am2903 superslice via the Am2921's ($\mu 16$ and $\mu 17$).
Bits PL32 and PL33	Select the source for the Am2903 A-address, according to the table below:

Bits		A-Address Source
33	32	
L	L	Data Bus bits 0 through 3
L	H	Microprogram bits 28 through 31
H	L	Data Bus bits 4 through 7
H	H	Microprogram bits 24 through 27

Bit PL34	Selects the source of the Am2903 B-address, according to the table below:
----------	---

Bit 34	B-Address Source
L	Data Bus bits 4 through 7
H	Microprogram bits 24 through 27

- Bit PL35 Is the C_n input of the least significant Am2903 via an Am74S157 mux (μ 38).
- Bits PL36 and PL37 Affect the status register input signals, according to the table below:

Bits		Next Carry	Next Zero, Sign, Overflow
37	36		
L	L	Previous Carry	Previous Zero, Sign, Overflow
L	H	Previous SIO ₁₅	Previous Zero, Sign, Overflow
H	L	Am2903 superslices' Output Data Bus bits 0 through 3	
H	H		

- Bit PL38 Selects either the carry flip-flop or the PL35 bit for carry in.
- Bit PL39 When LOW, enables the status register output to the data bus bits 0 through 3.
- Bit PL40 Controls the output polarity of the one-of-sixteen bit select logic.
- Bit PL41 When LOW, enables the Instruction register (U1, U2, U3) clock. The data present at bits 0 through 15 of the Data-Bus will be latched into the Instruction register at the next LOW-to-HIGH transition of the clock pulse.
- Bit PL42 This is an output signal. When HIGH, it signals the main memory that a memory read is requested.
- Bit PL43 This is an output signal. When HIGH, it signals to the main memory that a memory write is requested.
- Bit PL44 Selects the source of the one of sixteen bit decoders (U16 and U17). When LOW, the output of the Am2919 register (U12) containing the previously latched microprogram bits 28 through 31 will be applied to the decoders. When HIGH, the output of the Am2919 register (U3) containing the previously latched Data-Bus bits 0 through 3 will be applied to the decoders.
- Bit PL45 Selects the Am2903 Superslices™ DA port source. When LOW, the output of the one of sixteen bit decoder (U16 and U17) will be applied to that port. When HIGH, the output of the Am29771 PROM's (U18 and U19) will be applied to the Am2903 DA ports.
- Bit PL46 and PL47 These are the \overline{RLD} and \overline{CCEN} control inputs of the Am2910 sequencer, respectively.
- Bits PL48 through PL50 These select the condition code according to the following table:

Bits			Condition Code Selected
50	49	48	
L	L	L	Carry Sign Zero Overflow
L	L	H	
L	H	L	
L	H	H	
H	L	L	Not Allocated
H	L	H	
H	H	L	
H	H	H	

- Bit PL51 Is the condition code polarity control. When HIGH, the condition code selected will pass non-inverted. When LOW, the selected condition code will be complemented.

- Bits PL52 through PL55 Are the I inputs of the Am2910 sequencer.

- Bits PL56 through PL67 This is a 12-bit wide field and it serves, usually as the next microprogram address. However, the 5 least significant bits of this field (bits 56-60) serve also as an address field of the Am29771 "constant" PROM's (U18 and U19).

Some Sample Microroutines

Figure 32 shows the microprogram code for a few sample microroutines. Different addressing schemes are demonstrated with the "ADD" operation. All the other arithmetic or logic operations can be easily programmed by substituting the I₁-I₄ field of the Am2903 with the appropriate function. Since the main memory address is generated by the Am2903 superslices, the internal register No. 15 serves as the program counter.

The following is a description of some sample microroutines. The reader should refer to the description of the microprogram bits given earlier in this chapter and to the data sheets of the Am2910 sequencer and of the Am2903 superslice.

Microword INIT.

This microword should be at address 0 and when the machine is reset, the Am2910 will start executing from here. The purpose of this location is to reset the machine program counter (Register 15) to zero. Ultimately more microinstructions can be added, should the necessity of other reset functions arise.

Bits 1-4 (Am2903 I₁-I₄) being 8_H will cause the superslices to generate all zeroes at the F-points (internal). Bits 5-8 (Am2903 I₅-I₈) being F_H will cause this data (all zeroes) to appear on the Y outputs. Bit 9 (\overline{IEN}) is LOW and therefore, WRITE will be LOW and this data will be written into the internal register selected by the B-address inputs. Bit 34 is HIGH; therefore, microprogram bits 24-27 will be selected as B address source. Since F_H is in these bits, all zeroes will be written into the program counter (Register 15). Bit 18 is LOW; therefore, the data at the Y outputs (all zeroes) will be latched into the MAR at the next clock pulse. Bits 36 and 37 are set such that the flags will be updated, namely CY=N=OVF=0, Z=1.

Bits 42, 43 are both LOW so no memory reference signal is sent to the main memory (the MAR is still in an undetermined state). Bits 52-55 (Am2910 I) are set to E_H which will force the sequencer to continue to the next sequential address (1) as the CI (bit 23) is HIGH.

Bits 21 and 39 are both HIGH to ensure that there is no conflict on the data bus though in this case one of them could be a DON'T-CARE. Bit 38 could also be a DON'T-CARE as the carry is zeroed by the ALU. Making a HIGH in bit 46 enables executing this microstep without disturbing the Am2910 sequencer's internal register which at power-up has no significance but may be important, should a software restart be issued.

All the other bits are DON'T-CAREs.

Microword FETCH

This is the first step in the machine instruction fetch routine. In this step, the main memory is addressed by the MAR, a read signal is issued (bit 42 = HIGH), and the machine instruction (macroinstruction) is placed on the data bus by the memory. It is

	PL	2910					DA		MMW		MMR		IRE		POL		FDOE		CY=0		Flags
		I	CCP	CC	CLEN	RLD	CONS	BIT													
Number of Bits	12	4	1	3	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	2	
Bit No.	56-67	52-55	51	48-50	47	46	45	44	43	42	41	40	39	38	36-37						
INIT	X	E	X	X	X	1	X	X	0	0	X	X	1	0	2						
FETCH	X	E	X	X	X	1	X	X	0	1	0	X	1	0	0						
FETCH + 1	X	2	X	X	X	1	X	X	0	0	1	X	1	0	0						
ADD	FETCH + 1	7	X	X	1	1	X	X	0	1	0	X	1	0	2						
ADDIMM	X	E	X	X	X	1	X	X	0	1	1	X	1	0	0						
ADDIMM + 1	FETCH + 1	7	X	X	1	1	X	X	0	1	0	X	1	0	2						
ADD DIR	X	E	X	X	X	1	X	X	0	1	1	X	1	0	0						
ADD DIR + 1	X	E	X	X	X	1	X	X	0	0	1	X	1	0	0						
ADD DIR + 2	ADDIMM + 1	7	X	X	1	1	X	X	0	1	1	X	1	0	0						
ADD RR1	X	E	X	X	X	1	X	X	0	0	1	X	1	0	0						
ADD RR1 + 1	X	E	X	X	X	1	X	X	0	1	1	X	1	0	0						
ADD RR1 + 2	FETCH + 1	7	X	X	1	1	X	X	0	1	0	X	1	0	2						

	2903					2910	Y-D			MAR		2903									
	C _n	B	A	R ₂	R ₁		DDBE	OE	E	OE	E	Q	S	OE	EA	IEN	I ₅₋₈	I ₁₋₄	I ₀		
Number of Bits	1	1	2	4	4	1	1	1	1	1	1	3	3	1	1	1	4	4	1		
Bit No.	35	34	32-33	28-31	24-27	23	22	21	20	19	18	15-17	12-14	11	10	9	5-8	1-4	0		
INIT	X	1	X	X	F	1	X	1	X	X	0	X	X	X	X	0	F	8	X		
FETCH	X	X	X	X	X	1	1	1	1	0	1	X	X	0	X	1	X	X	X		
FETCH + 1	1	1	X	X	F	1	1	1	1	0	0	X	X	0	X	0	F	4	0		
ADD	0	0	0	X	X	1	1	1	1	0	1	X	X	0	0	0	F	3	0		
ADDIMM	1	1	X	X	F	1	0	1	1	0	0	X	X	0	X	0	F	4	0		
ADDIMM + 1	0	0	0	X	X	1	1	1	1	0	1	X	X	1	0	0	F	3	0		
ADD DIR	1	1	X	X	F	1	0	1	1	0	X	X	X	0	X	0	F	4	0		
ADD DIR + 1	0	X	X	X	X	1	1	1	1	X	0	X	X	1	X	1	X	4	0		
ADD DIR + 2	0	X	3	X	F	1	0	1	1	0	0	X	X	X	0	1	F	6	X		
ADD RR1	0	X	0	X	X	1	X	1	1	X	0	X	X	X	0	1	F	6	X		
ADD RR1 + 1	0	X	3	X	F	1	0	1	1	0	0	X	X	X	0	1	F	6	X		
ADD RR1 + 2	0	0	2	X	X	1	1	1	1	0	1	X	X	1	0	0	F	3	0		

1. 4-bit fields in hex, others in octal.
2. X = Don't Care.

Figure 32. Example Microcode for Figure 31 Design.

latched into the instruction register (U1, U2, and U3) at the next clock LOW-to-HIGH transition (bit 41 = LOW). It is assumed that if a relatively slow main memory is used, the clock is halted until the data is stable on the data bus and the register set up times are met. We will see in a later chapter how easy it is to implement this requirement using the Am2925 clock generator. The same assumption will also be made in a memory write cycle.

Bit 9 (Am2903 \overline{IEN}) is HIGH; thus, we don't care what the ALU does during this microstep. We prevent the flags from changing by setting bits 36-38 LOW. Also, the registers at the Y output have the \overline{E} input HIGH (bits 18, 20). Bits 21 and 39 are both HIGH; thus, the data bus is free to accept data from the main memory (bit 42 is HIGH, signaling memory read request). The MAR is enabled to the address bus (bit 19 = LOW) and at the next clock, the macroinstruction will be latched into the instruction registers (bit 41 = LOW). The Am2910 sequencer will continue to the next instruction (bits 52-55 = E_H).

Microword FETCH + 1

This is the second step in the macroinstruction fetch routine. The instruction already resides in the instruction registers U1, U2 and U3).


The Am2910 sequencer receives a JUMP MAP instruction (bits 52 though 55 = 2). The next microinstruction will begin to execute the present macroinstruction – according to the mapping PROM.

We use this microstep to update (increment) the program counter (Register 15). Bit 34 being HIGH, microprogram bits 24-27 (= F_H) will be the B address. The Am2903 OEB and I_0 are LOW, therefore, the contents of Register 15 will serve as the S operand for the ALU. C_n being HIGH, a 4 in the I_1 - I_4 field will increment this value. \overline{IEN} = LOW with I_5 - I_8 = F will write this (incremented) value into the same register (R15). At the same time, the MAR is also updated (bit 18 = LOW).

We could update the program counter and the MAR in the previous microstep (location FETCH), but then we had to leave the ALU idle during this microcycle. By adopting the present scheme, we can overlap the first step of the macroinstruction fetch routine (the memory-read cycle) with the execution of the last step of the previous macroinstruction – provided the memory and the data bus are free to perform it. The JUMP MAP cycle is always necessary – and that is why we prefer to update the PC at this step.

Microword ADD

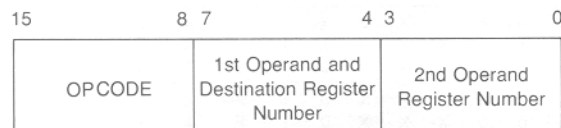This is a sample register-to-register operation. The two operands reside in the internal registers pointed to by the two 4-bit fields of the macroinstruction:



Bits 32-33 are set LOW, instruction register bits 0-3 are selected as A address. Bit 34 = LOW selects instruction register bits 4-7 as B address (see Fig. above). Bit 1 (I_0), bit 10 (\overline{EA}) and bit 11 (\overline{OEB}) are also LOW; therefore, the contents of the selected registers will be presented to the ALU's R and S inputs. Bits 1-4 (I_1 - I_4) = 3, the ALU will perform:

$$F = R \text{ plus } S \text{ plus } C_n.$$

Note that bit 35 and 38 are LOW. With I_5 - I_8 (bits 5-8) = F_H and \overline{IEN} (bit 0) = LOW, the result will be written into the internal register pointed at by the B address lines.


Bits 18 and 20 are HIGH and inhibit the MAR and the data out registers from being affected, while bits 36, 37 (= 2) allow the flags to assume values according to the result of the operation.

During the execution of the function required (ADD in this example) we fetch the next OP CODE from the main memory. The MAR is enabled to the address bus (bit 19 = LOW) and a memory read is requested (bit 42 = HIGH). At the end of this microstep the next macroinstruction will be latched into the instruction registers (bit 41 = LOW).


The Am2910 sequencer is instructed to select the pipeline register bits 56-67 as the next microprogram address (bits 52-57 = 7, bit 47 = HIGH) where the location of FETCH + 1 (2 in this example) is written. The next step will be JUMP MAP and update PC.

Microword ADD IMMEDIATE

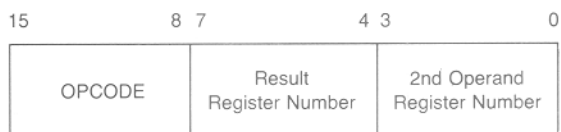This 2 step microroutine adds the contents of an internal register, pointed at by bits 0-3 of the macroinstruction with its second word, placing the result into the internal register pointed at by bits 4-7 of the OPCODE.



First word of the macroinstruction

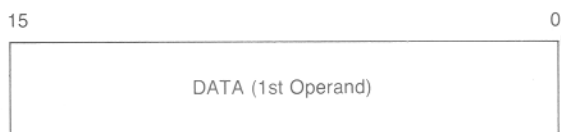


Second (next consecutive) word of the macroinstruction

The first step is to read the first operand from the memory (bit 19 = LOW, bit 42 = HIGH) and to latch it into the data-in register (U20 and U21) (bit 22 = LOW). At the same time the ALU updates (increments) the program counter (register 15) and the MAR (bit 18 = LOW). (Compare the location FETCH + 1). The Am2910 sequencer will continue to the next microprogram address (compare to location FETCH).

Location ADDIMM + 1 is the second step of this macroinstruction. It is very similar to location ADD, the only difference is that bit 11 (\overline{OEB}) is HIGH, selecting the Data-in register as source for the ALU's S operand. The same macroinstruction fetch overlap technique is used again.

Microword ADD DiRect

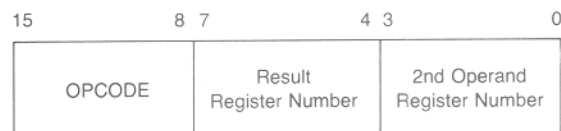This is the starting location to execute a macroinstruction where the second word is the address of the operand:



First word of the macroinstruction

Address of the 1st operand

Second (next consecutive) word of the macroinstruction

The first step is to read the second word of the macroinstruction into the Data-in register. This microword is identical to the one written at location ADDIMM.

Microword ADD DIR + 1

The Data-in register now contains the address of the operand. We have to transfer it into the MAR.

With I_0 (bit 0) LOW and \overline{OEB} (bit 11) HIGH, the ALU's operand will be the DB bus, i.e., the Data-in register. I_1 - I_4 (bits 1-4) = 4 will pass this input to its output, as C_n (bit 3) is LOW. With \overline{IEN} (bit 9) = HIGH, the WRITE line will be HIGH too, assuring that the internal registers maintain their contents. Since I_5 - I_8 (bits 5-8) = F_H , the ALU output will appear on the Am2903 Y pins. This data which is actually the operand address and will be transferred into the MAR at the next clock cycle. The Am2910 sequencer continues to the next consecutive microstep.

Microword ADD DIR + 2

Now we read in the operand from the main memory. The MAR is enabled to address bus (bit 19 = LOW), a memory read signal is issued (bit 42 = HIGH) and the data-in register's clock is enabled (bit 22 = LOW). At the next LOW-to-HIGH transition of the clock, the operand will be placed in the data-in register.

Meanwhile, we need to restore the address of the next macroinstruction in the MAR. Bits 32-33 = 3 select microprogram bits 24-27 as the A address (an F_H is written there); therefore, the internal program counter will be addressed, as \overline{EA} (bit 10) = LOW. The ALU performs an $F = R + C_n$ with C_n (bit 35) LOW, thus passing the program counter contents to the output. \overline{IEN} (bit 9) = HIGH prevents disturbance of internal Am2903 registers and bit 18 will enable the MAR to receive the next macroinstruction address.

Note that the situation now is exactly the same as after the first step of ADD IMMEDIATE. The operand is in the data register and the MAR points to the next macroinstruction. Therefore, the Am2910 sequencer will address, as the next microstep, location ADDIMM + 1. The step after this will, of course, be FETCH + 1. A total of 5 microsteps were needed to execute this macroinstruction but it occupies only 3 microprogram locations.

It is worthwhile to note here that by adding two more Am2920 registers between the Data-bus and the Address-bus and a couple of control-bits in the microprogram, we could shorten the microprogram by one step. In this design we chose not to do so in order to demonstrate the Data-bus to Address-bus path through the ALU.

Microword ADD RR1

The macroinstruction to be executed here points to the register in which the first operand is written, and also into which the result should be written. The second 4-bit field of the OP-CODE (bits 0-3) points to the register in which the address of the second operand is stored.

15 8 7 4 3 0

OPCODE	1st Operand and Result Register Number	2nd Operand's Address Register Number
--------	--	---------------------------------------

Bits 32 and 33 are LOW. Therefore, instruction register bits 0-3 will form the A-address. Now we take the contents of this register and place it in the MAR exactly the same way as we did in location ADD DIR + 2 with the program counter. The Am2910 continues.

Microword ADD RR1 + 1

Here we fetch the operand and place it in the Data-in register. At the same time, we restore the program counter into the MAR.

Microword ADD RR1 + 2

Bits 32, 33 = 2 and instruction register bits 4-7 serve as the A-address. Bit 34 = LOW; the same instruction register bits serve as B-address, too. Note, that \overline{OEB} (bit 11) is HIGH; therefore, the ALU R-source will be the Data-in register and the S-source will be the register addressed by A-address. The result (sum), however, will be written to the correct register, as \overline{IEN} (bit 9) is LOW.

At the same time, the next macroinstruction is fetched in the usual overlapping way and the next microinstruction to be executed will be at location FETCH + 1.

Summary

In this design shown in Figure 31, we have demonstrated some of the addressing schemes mentioned in Chapter 1. We used the ADD instruction throughout these examples, but any other arithmetic or logic instruction can be executed, in *exactly* the same manner by changing the microcode bits 1-4 to the appropriate ALU code.

The reader is encouraged to write several microcode-lines to execute the other addressing modes mentioned in Chapter 1. He will discover that when the result of the macroinstruction is to be written into main memory, the overlapping instruction-fetch is not feasible. In some cases, when the MAR no longer contains the Program Counter value, an additional microstep is needed in order to restore the Program Counter into the MAR. The reader is again encouraged to modify location FETCH in order to save this additional microstep.

Appendix

Throughout Chapter 3, a number of AC calculations have been made to show typical speeds for an Am2901A and Am2903 16-bit ALU configuration. This Appendix shows the latest SWITCHING CHARACTERISTICS for the Am2901A and Am2903.

The typical data on the Am2901A shown in this Appendix supersedes that shown on page 2-12 of the Am2900 Family Data Book dated 4-78 (AM-PUB003). The only difference between the data shown in the typical column of the switching characteristic and this Appendix appears in Table 3. The typical carry in set-up time should be 40ns.

The typical switching characteristic data for the Am2903 as shown in this Appendix supersedes the data presented in the Am2903 Bipolar Microprocessor Slice/Am2910 Microprogram Controller Data Booklet dated 3-78. Here, a number changes have been made to the table for both the combinatorial propagation delays and the set-up and hold times.

Should any questions arise concerning the switching characteristics for either the Am2901A or Am2903, please do not hesitate to contact the AMD factory and ask for Bipolar Microprocessor Marketing or Bipolar Microprocessor Applications.

ROOM TEMPERATURE SWITCHING CHARACTERISTICS

(See next page for AC Characteristics over operating range.)

Tables I, II, and III below define the timing characteristics of the Am2901A at 25°C. The tables are divided into three types of parameters; clock characteristics, combinational delays from inputs to outputs, and set-up and hold time requirements. The latter table defines the time prior to the end of the cycle (i.e., clock LOW-to-HIGH transition) that each input must be stable to guarantee that the correct data is written into one of the internal registers.

All values are at 25°C and 5.0V. Measurements are made at 1.5V with $V_{IL} = 0V$ and $V_{IH} = 3.0V$. For three-state disable tests, $C_L = 5.0pF$ and measurement is to 0.5V change on output voltage level. All outputs fully loaded.


TABLE I

CYCLE TIME AND CLOCK CHARACTERISTICS

TIME	TYPICAL	GUARANTEED
Read-Modify-Write Cycle (time from selection of A, B registers to end of cycle)	55ns	93ns
Maximum Clock Frequency to Shift Q Register (50% duty cycle)	40MHz	20MHz
Minimum Clock LOW Time	30ns	30ns
Minimum Clock HIGH Time	30ns	30ns
Minimum Clock Period	75ns	93ns

TABLE II

COMBINATIONAL PROPAGATION DELAYS (all in ns, $C_L = 50pF$ (except output disable tests))

From Input	To Output	TYPICAL 25°C, 5.0V								GUARANTEED 25°C, 5.0V							
		Y	F ₃	C _{n+4}	$\overline{G}, \overline{P}$	F=0 R _L = 270	OVR	Shift Outputs		Y	F ₃	C _{n+4}	$\overline{G}, \overline{P}$	F=0 R _L = 270	OVR	Shift Outputs	
								RAM ₀ RAM ₃	Q ₀ Q ₃							RAM ₀ RAM ₃	Q ₀ Q ₃
A, B		45	45	45	40	65	50	60	—	75	75	70	59	85	76	90	—
D (arithmetic mode)		30	30	30	25	45	30	40	—	39	37	41	31	55	45	59	—
D (I = X37) (Note 5)		30	30	—	—	45	—	40	—	36	34	—	—	51	—	53	—
C _n		20	20	10	—	35	20	30	—	27	24	20	—	46	26	45	—
I ₀₁₂		35	35	35	25	50	40	45	—	50	50	46	41	65	57	70	—
I ₃₄₅		35	35	35	25	45	35	45	—	50	50	50	42	65	59	70	—
I ₆₇₈		15	—	—	—	—	—	20	20	26	—	—	—	—	—	26	26
OE Enable/Disable		20/20	—	—	—	—	—	—	—	30/33	—	—	—	—	—	—	—
A bypassing ALU (I = 2xx)		30	—	—	—	—	—	—	—	35	—	—	—	—	—	—	—
Clock  (Note 6)		40	40	40	30	55	40	55	20	52	52	52	41	70	57	71	30

SET-UP AND HOLD TIMES (all in ns) (Note 1)

TABLE III

From Input	Notes	TYPICAL 25°C, 5.0V		GUARANTEED 25°C, 5.0V	
		Set-Up Time	Hold Time	Set-Up Time	Hold Time
A, B	2, 4	40	0	93	0
Source	3, 5	$t_{pwL} + 15$	0	$t_{pwL} + 25$	0
B Dest.	2, 4	$t_{pwL} + 15$	0	$t_{pwL} + 15$	0
D (arithmetic mode)		25	0	70	0
D (I = X37) (Note 5)		25	0	60	0
C _n		40	0	55	0
I ₀₁₂		30	0	64	0
I ₃₄₅		30	0	70	0
I ₆₇₈	4	$t_{pwL} + 15$	0	$t_{pwL} + 25$	0
RAM _{0, 3} , Q _{0, 3}		15	0	20	0

Notes: 1. See next page.

2. If the B address is used as a source operand, allow for the "A, B source" set-up time; if it is used only for the destination address, use the "B dest." set-up time.

3. Where two numbers are shown, both must be met.

4. " t_{pwL} " is the clock LOW time.

5. DVO is the fastest way to load the RAM from the D inputs. This function is obtained with I = 337.

6. Using Q register as source operand in arithmetic mode. Clock is not normally in critical speed path when Q is not a source.

A. Am2903 SWITCHING CHARACTERISTICS (TYPICAL ROOM TEMPERATURE PERFORMANCE) – (MAY 18, 1978)

Tables IA, IIA, and IIIA define the nominal timing characteristics of the Am2903 at 25°C and 5.0V. The Tables divide the parameters into three types: pulse characteristics for the clock and write enable, combinational delays from input to output, and set-up and hold times relative to the clock and write pulse.

Measurements are made at 1.5V with $V_{IL} = 0V$ and $V_{IH} = 3.0V$. For three-state disable tests, $C_L = 5.0pF$ and measurement is to 0.5V change on output voltage level.

TABLE IA – Write Pulse and Clock Characteristics

Time	
Minimum Time CP and \overline{WE} both LOW to write	15ns
Minimum Clock LOW Time	15ns
Minimum Clock HIGH Time	35ns

**TABLE IIA – Combinational Propagation Delays (All in ns)
Outputs Fully Loaded. $C_L = 50pF$ (except output disable tests)**

To Output From Input	Y	C_{n+4}	$\overline{G}, \overline{P}$	(S) Z	N	OVR	DB	\overline{WRITE}	QIO_0, QIO_3	SIO_0	SIO_3	SIO_0 (Parity)
A, B Addresses (Arith. Mode)	65	60	56	–	64	70	33	–	–	65	69	87
A, B Addresses (Logic Mode)	56	–	46	–	56	–	33	–	–	55	64	81
DA, DB Inputs	39	38	30	–	40	56	–	–	–	39	47	60
\overline{EA}	38	33	26	–	36	41	–	–	–	36	41	58
C_n	25	21	–	–	20	38	–	–	–	21	25	48
I_0	40	31	24	–	37	42	–	15(1)	–	41	39	63
I_{4321}	45	45	32	–	44	52	–	17(1)	–	45	51	68
I_{8765}	25	–	–	–	–	–	–	21	22/29(2)	24/17(2)	27/17(2)	24/17(2)
\overline{IEN}	–	–	–	–	–	–	–	10	–	–	–	–
\overline{OEB} Enable/Disable	–	–	–	–	–	–	12/15(2)	–	–	–	–	–
\overline{OEY} Enable/Disable	14/14(2)	–	–	–	–	–	–	–	–	–	–	–
SIO_0, SIO_3	13	–	–	–	–	–	–	–	–	–	19	20
Clock	58	57	40	–	56	72	24	–	28	56	63	76
Y	–	–	–	16	–	–	–	–	–	–	–	–
\overline{MSS}	25	–	25	–	25	25	–	–	–	24	27	24

Notes: 1. Applies only when leaving special functions.

2. Enable/Disable. Enable is defined as output active and correct. Disable is a three-state output turning off.

3. For delay from any input to Z, use input to Y plus Y to Z.

TABLE IIIA – Set-Up and Hold Times (All in ns)

CAUTION: READ NOTES TO TABLE III. NA = Note Applicable; no timing constraint.

Input	With Respect to to this Signal	HIGH-to-LOW		LOW-to-HIGH		Comment
		Set-up	Hold	Set-up	Hold	
Y	Clock	NA	NA	9	–3	To store Y in RAM or Q
\overline{WE} HIGH	Clock	5	Note 2	Note 2	0	To Prevent Writing
\overline{WE} LOW	Clock	NA	NA	15	0	To Write into RAM
A,B as Sources	Clock	19	–3	NA	NA	See Note 3
B as a Destination	Clock and \overline{WE} both LOW	–4	Note 4	Note 4	–3	To Write Data only into the Correct B Address
QIO_0, QIO_3	Clock	NA	NA	10	–4	To Shift Q
I_{8765}	Clock	2	Note 5	Note 5	–18	
\overline{IEN} HIGH	Clock	10	Note 2	Note 2	0	To Prevent Writing into Q
\overline{IEN} LOW	Clock	NA	NA	10	–5	To Write into Q



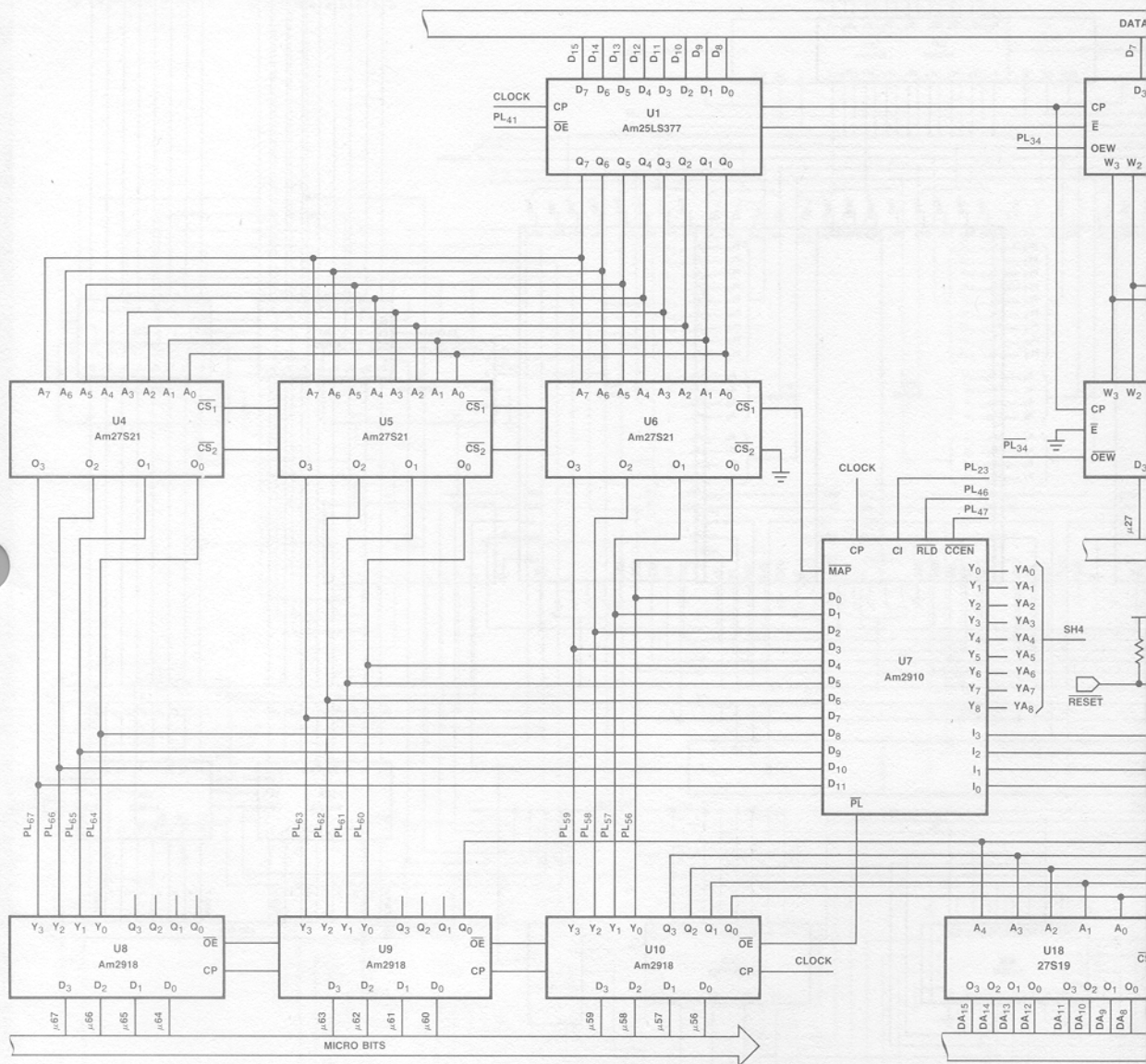


Figure 31

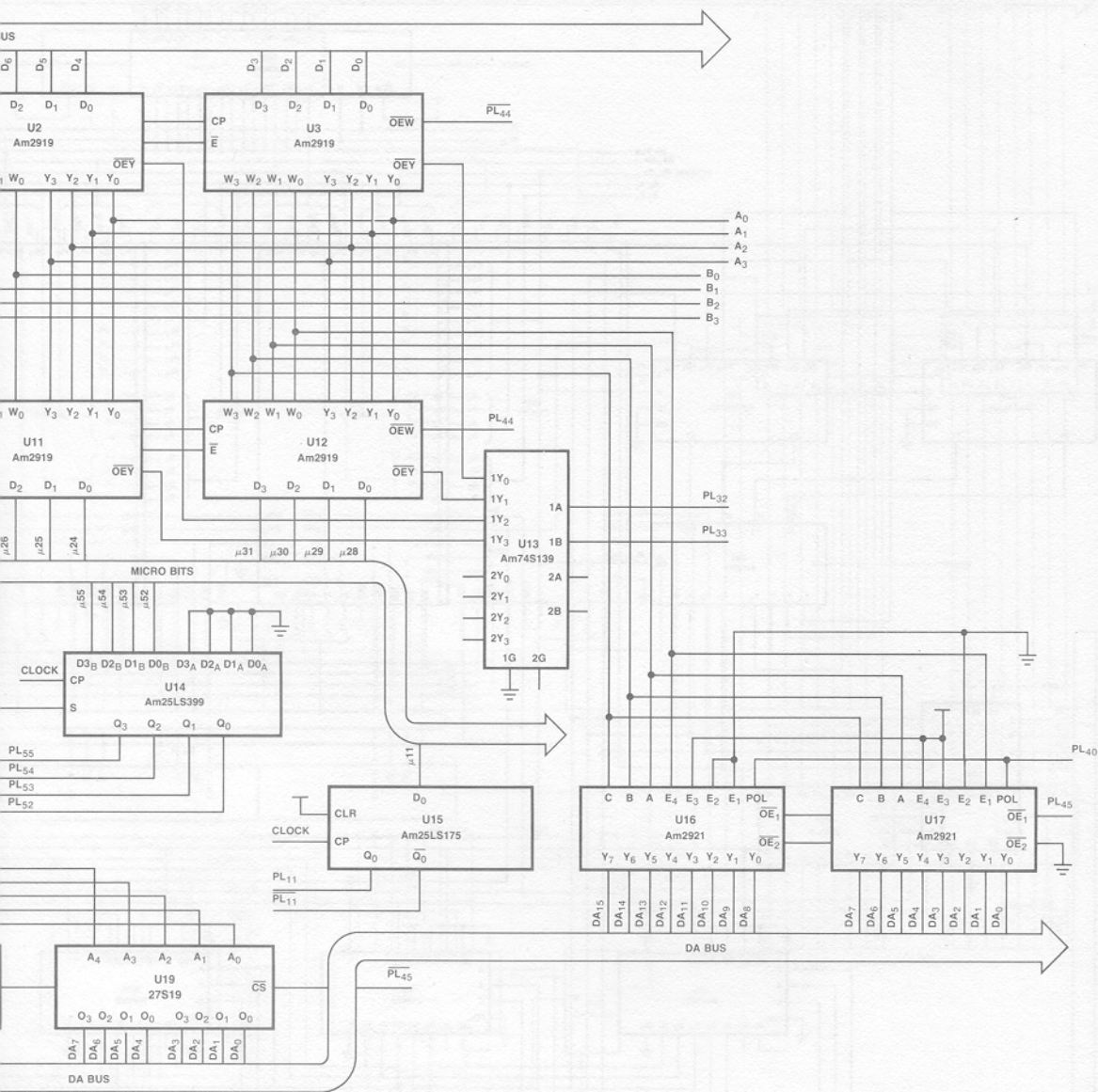

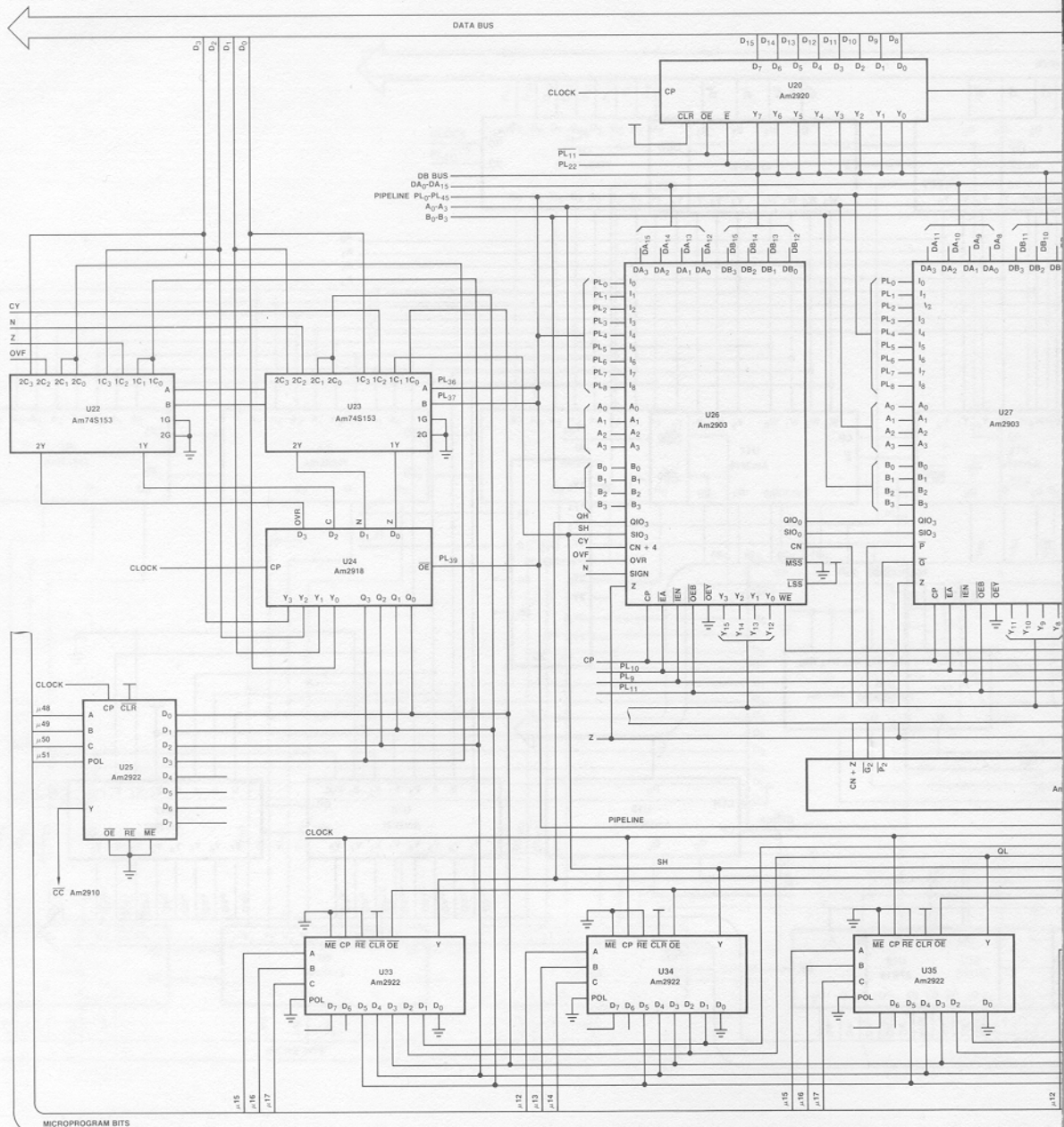

MICROPROGRAM BITS


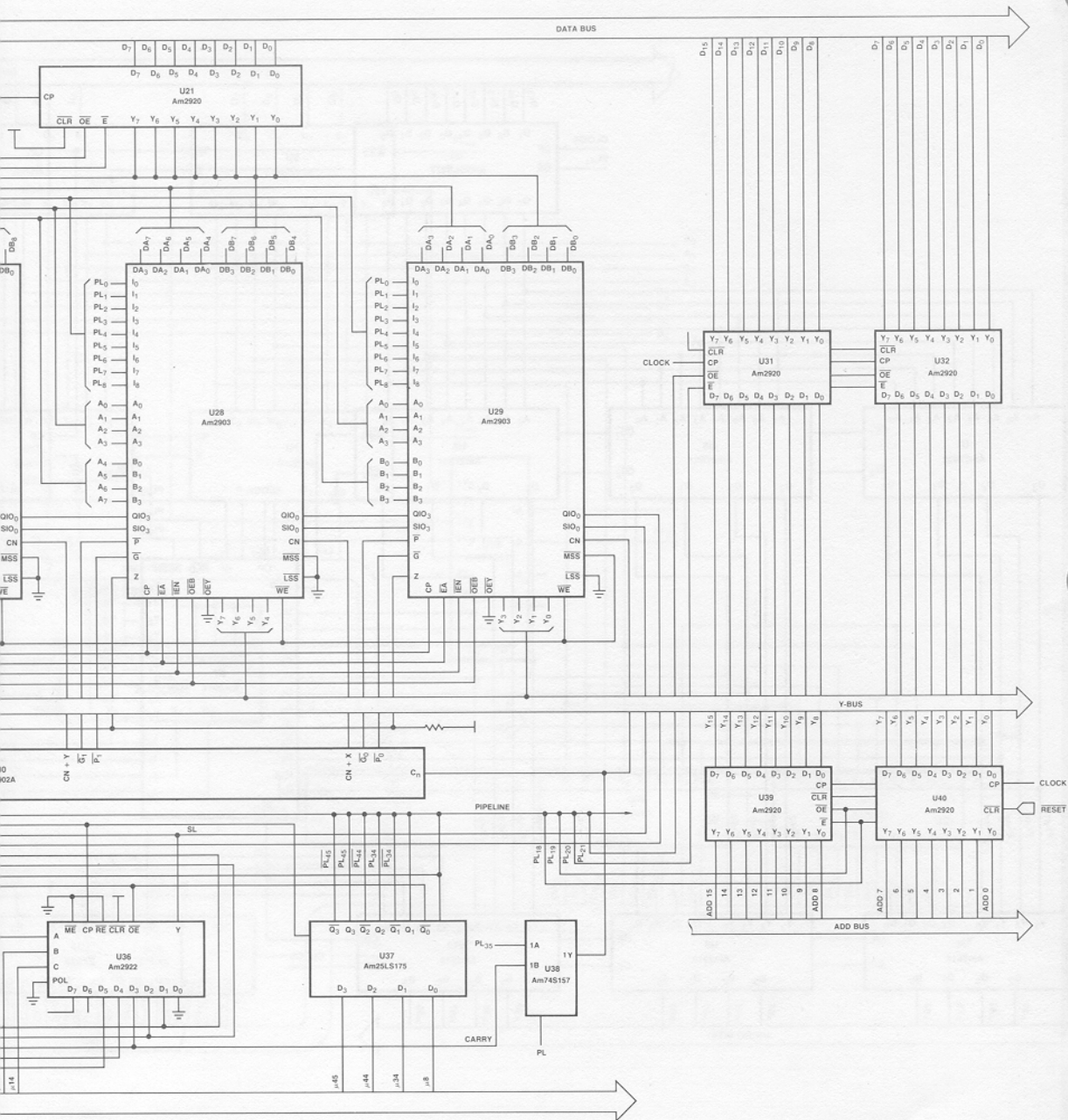
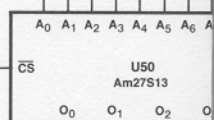
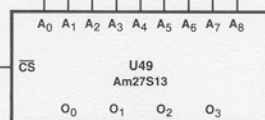
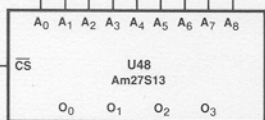
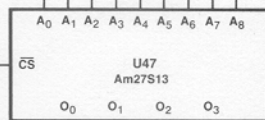
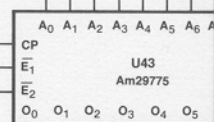
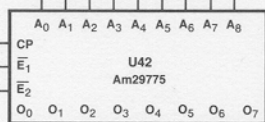


Figure 31b.


YA₈
YA₇
YA₆
YA₅
YA₄
YA₃
YA₂
YA₁
YA₀

CLOCK
CP
E₁
E₂
O₀

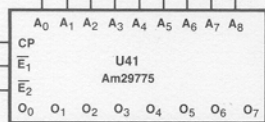

MICROPROGRAM

Figure 31c

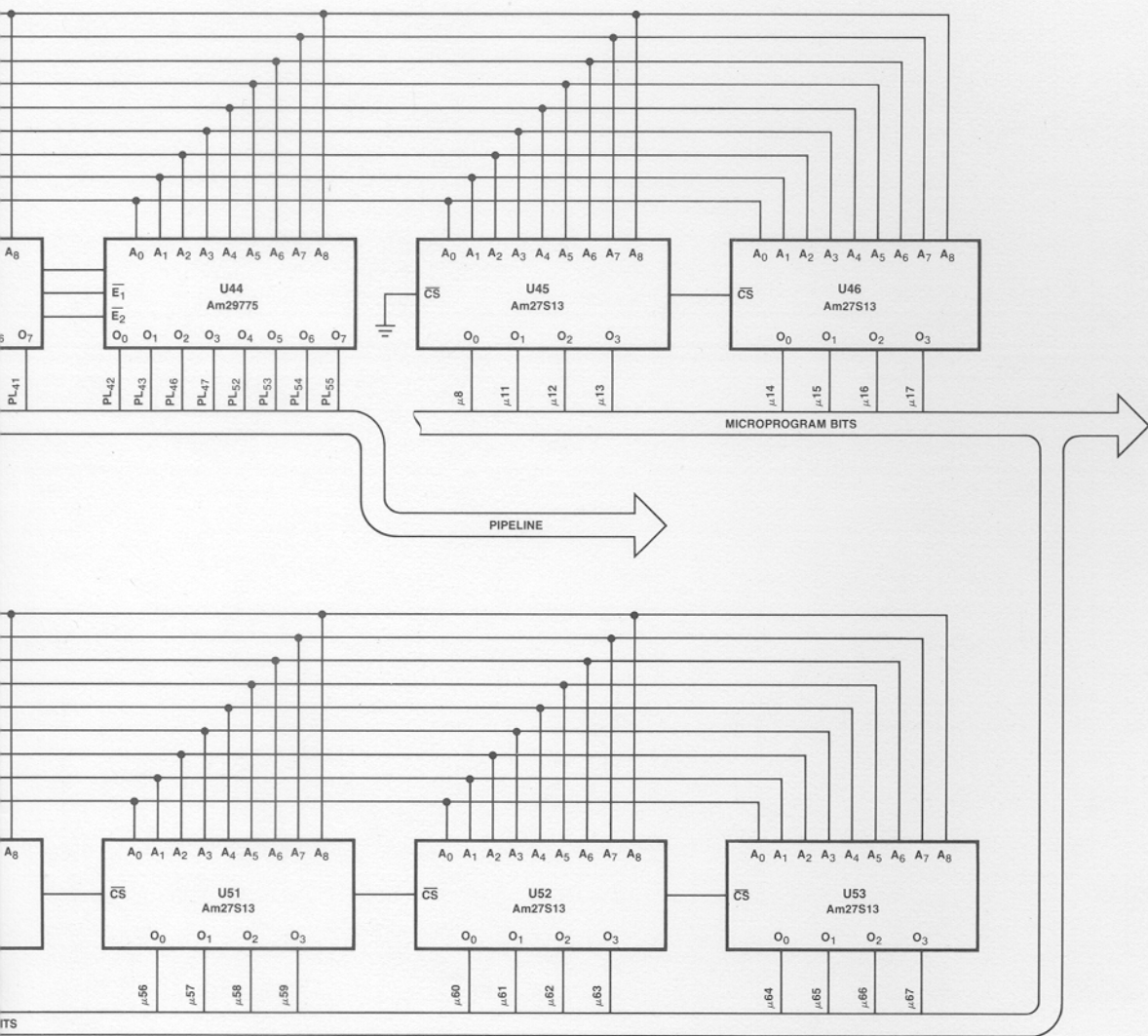



**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
Sunnyvale

California 94086


(408) 732-2400

TWX: 910-339-9280

TELEX: 34-6306

TOLL FREE


(800) 538-8450

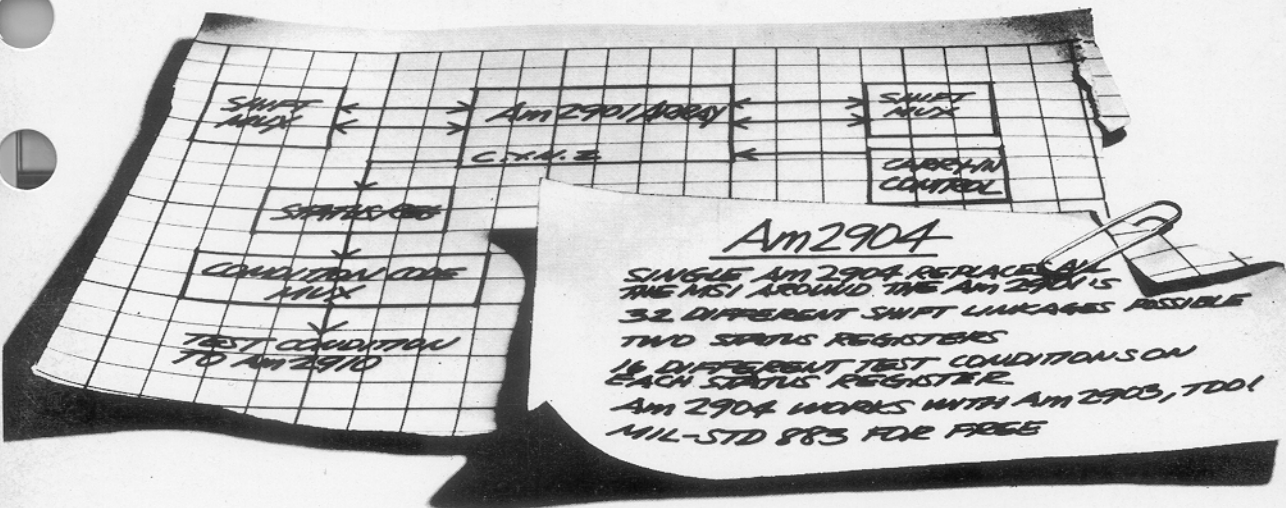


Build A Microcomputer

Chapter IV The Data Path — Part II

Advanced Micro Devices

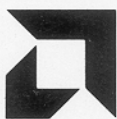

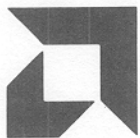

Advanced Micro Devices

Build A Microcomputer

Chapter IV The Data Path — Part II

Copyright © 1979 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-4

Micro Devices

Microcomp II

Part IV
Part II

Microcomp II

Microcomp II

Microcomp II

CHAPTER IV THE DATA PATH

The previous CPU example (See Chapter III) utilized SSI and MSI components to accomplish the shift-linkage, carry control, and status register functions associated with the ALU. These functions can all be implemented with the Am2904 status and shift control unit.

The Am2904 is an LSI device that contains all the logic necessary to perform the shift and status control operations associated with the ALU portion of a microcomputer. These operations include storage for ALU status flags; carry-in generation and selection; data-path, carry bit linkage for shift/rotate instructions; and status condition code generation and selection. The ALU status flags: carry, zero, negative, and overflow; may be stored in either of two registers, a machine status register or a micro status register. The carry-in multiplexer can select the true or complement of the microstatus carry flag or machine status carry flag, as well as an external carry, a logical one, or a logical zero. The shift linkage multiplexers provide paths to rotate/shift single and double length words up, down, around the carry flag, and through the carry flag. The status condition code multiplexer provides tests on the true or complement of any status flag, as well as more complicated logical combinations of these flags to facilitate magnitude comparisons on unsigned and two's complement numbers, and normalization operations.

STATUS REGISTERS

The status registers contained in the Am2904 are shown in the upper portion of Figure 1. Each register is independently controlled by a combination of instruction signals and enable signals.

MICRO STATUS REGISTER (μ SR)

The μ SR is enabled when the \overline{CE}_{μ} signal is low. When \overline{CE}_{μ} is low the instruction present on I_5 through I_0 will be executed on the LOW to HIGH transition of the Clock input. These instructions fall into three main categories: Bit Operations, Register Operations and Load Operations.

The bit operations allow individual bits of the μ SR to be set or reset. (See Table 1.1).

The register operations allow the μ SR to be loaded from the machine status register, to be set to all one's, reset to all zero's, or swapped with the machine status register. (See Table 1.2).

The load operations allow the μ SR to be loaded from the I inputs directly, from the I inputs with I_C complemented, or from the I inputs with overflow retained, $I_{OVR} + \mu_{OVR} \rightarrow \mu_{OVR}$ (See Table 1.3). The load operation with I_C complemented can be used to emulate machines which use direct subtraction and thus need to complement the carry to obtain a borrow. The load with overflow retained allows a series of arithmetic instructions to be executed without the need for a check for overflow after each instruction. If an overflow occurred at any time during the series it will be "trapped." Thus a single test for overflow, at the end of the series, is all that is required.

MACHINE STATUS REGISTER (MSR)

The MSR is enabled when \overline{CE}_M is low. If \overline{CE}_M is low the instruction present on I_5 through I_0 will be executed on the LOW to HIGH transition of the Clock input. Additionally the individual bits of the MSR may be selectively enabled through the use of the Enable inputs \overline{E}_Z , \overline{E}_C , \overline{E}_N and \overline{E}_{OVR} (See Figure 1). This allows all possible combinations of the four status flags to be selectively operated on for maximum flexibility. Thus the instruction specified by I_5 - I_0 only effect the enabled status flags.

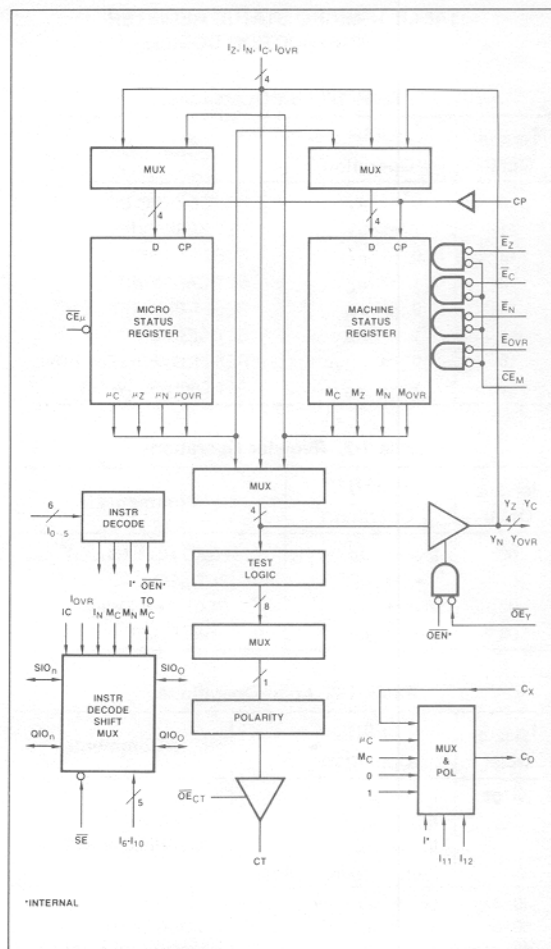


Figure 1. Am2904 Block Diagram.

The MSR instructions fall into two main categories: register operations and load operations (bit operations can be implemented through the use of the selective enable control lines).

The register operations allow the MSR to be loaded from the bi-directional Y port, or the μ SR. Additionally the MSR may be set, reset, or complemented (See Table 2.1). These three instructions, combined with the selective enables, allow any combination of MSR bits to be set, reset, or complemented.

The load operations allow the MSR to be loaded directly from the I inputs, from the I inputs with I_C complemented, or from the I inputs for shift through overflow (See Table 2.2). The load with I_C complemented can be used to produce a borrow. The load for shift through overflow loads the zero flag and the negative flag from the I inputs while swapping the overflow and carry flags. This allows the shift through overflow operation to be easily implemented.

SHIFT LINKAGE MULTIPLEXERS

The shift linkage multiplexers control bi-directional shift lines SIO_n , SIO_0 (RAM shifter on the Am2903) and QIO_n , QIO_0 (Q register shifter on the Am2903). To enable the shift linkage multiplexers the shift enable line \overline{SE} must be low. When \overline{SE} is low the

TABLE 1. MICRO STATUS REGISTER INSTRUCTION CODES.

Table 1-1. Bit Operations.

I ₅₄₃₂₁₀ Octal	μ SR Operation	Comments
10	0 \rightarrow μ Z	RESET ZERO BIT
11	1 \rightarrow μ Z	SET ZERO BIT
12	0 \rightarrow μ C	RESET CARRY BIT
13	1 \rightarrow μ C	SET CARRY BIT
14	0 \rightarrow μ N	RESET SIGN BIT
15	1 \rightarrow μ N	SET SIGN BIT
16	0 \rightarrow μ OVR	RESET OVERFLOW BIT
17	1 \rightarrow μ OVR	SET OVERFLOW BIT

Table 1-2. Register Operations.

I ₅₄₃₂₁₀ Octal	μ SR Operation	Comments
00	M _X \rightarrow μ X	LOAD MSR TO μ SR
01	1 \rightarrow μ X	SET μ SR
02	M _X \rightarrow μ X	REGISTER SWAP
03	0 \rightarrow μ X	RESET μ SR

Table 1-3. Load Operations.

I ₅₄₃₂₁₀ Octal	μ SR Operation	Comments
06, 07	I _Z \rightarrow μ Z I _C \rightarrow μ C I _N \rightarrow μ N I _{OVR} \rightarrow μ OVR	LOAD WITH OVERFLOW RETAIN
30, 31 50, 51 70, 71	I _Z \rightarrow μ Z I _C \rightarrow μ C I _N \rightarrow μ N I _{OVR} \rightarrow μ OVR	LOAD WITH CARRY INVERT
04, 05 20-27 32-47 52-67 72-77	I _Z \rightarrow μ Z I _C \rightarrow μ C I _N \rightarrow μ N I _{OVR} \rightarrow μ OVR	LOAD DIRECTLY FROM I _Z , I _C , I _N , I _{OVR}

Note: The above tables assume \overline{CE} is LOW.

shift linkage data path will be set-up depending on the state of instruction lines I₁₀ through I₆ (See Table 3). These instructions allow single length or double length shifts/rotates either up, or down. Additionally shifts/rotates may be done through or around the MSR carry and negative flag. Special operations exist to provide support for add and shift (multiply) instructions. These instructions select the present carry I_C (for unsigned multiply), or the Exclusive-OR of the sign flag I_N with the overflow flag I_{OVR} (for two's complement multiplication).

CONDITION CODE MULTIPLEXER

The condition code multiplier selects one of sixteen possible logical combinations of the μ SR, MSR or I inputs, depending on the state of the I₅-I₀ input lines. These combinations include the true or complement form of any individual bit in the μ SR, MSR or I inputs. Additionally several more complicated logical operations may be performed to provide magnitude tests on both two's

complement numbers and unsigned numbers. Table 5 lists the conditional test outputs (CT) corresponding to the state of the I₅-I₀ instruction lines. Table 6 lists the possible relations between two unsigned or two's complement numbers and the corresponding status and instruction codes. The three-state conditional test output CT is active only if \overline{OE}_{CT} is low.

CARRY IN MULTIPLEXER

The Carry output can be selected from one of seven different sources depending on the state of instruction input lines. The seven possible sources are: logical zero, logical one, the μ SR carry flag, the complement of the μ SR carry flag, the MSR carry flag, the complement of the MSR carry flag, or the external carry input C_X (See Table 4).

TABLE 2. MACHINE STATUS REGISTER INSTRUCTION CODES.

Table 2-1. Register Operations.

I ₅₄₃₂₁₀ Octal	MSR Operation	Comments
00	Y _X \rightarrow M _X	LOAD Y _Z , Y _C , Y _N , Y _{OVR} TO MSR
01	1 \rightarrow M _X	SET MSR
02	μ X \rightarrow M _X	REGISTER SWAP
03	0 \rightarrow M _X	RESET MSR
05	$\overline{M}_X \rightarrow M_X$	INVERT MSR

Table 2-2. Load Operations.

I ₅₄₃₂₁₀ Octal	MSR Operation	Comments
04	I _Z \rightarrow M _Z M _{OVR} \rightarrow M _C I _N \rightarrow M _N M _C \rightarrow M _{OVR}	LOAD FOR SHIFT THROUGH OVERFLOW OPERATION
10, 11 30, 31 50, 51 70, 71	I _Z \rightarrow M _Z I _C \rightarrow M _C I _N \rightarrow M _N I _{OVR} \rightarrow M _{OVR}	LOAD WITH CARRY INVERT
06, 07 12-17 20-27 32-37 40-47 52-67 72-77	I _Z \rightarrow M _Z I _C \rightarrow M _C I _N \rightarrow M _N I _{OVR} \rightarrow M _{OVR}	LOAD DIRECTLY FROM I _Z , I _C I _N , I _{OVR}

Note: 1. The above tables assume \overline{CE}_M , \overline{E}_Z , \overline{E}_C , \overline{E}_N , \overline{E}_{OVR} are LOW.

Y INPUT/OUTPUT LINES

The bi-directional Y data lines may be used for extra data input lines when the Y output buffer is disabled (\overline{OE}_Y high). Additionally, when I₅-I₀ are low, the Y buffer is disabled, irrespective of the \overline{OE}_Y signal. When the Y buffer is enabled (\overline{OE}_Y is low) the Y data lines are selected from the MSR, μ SR, or I input lines depending on the state of instruction lines I₅ and I₄ (See Table 7).

TABLE 3. SHIFT LINKAGE MULTIPLEXER INSTRUCTION CODES.

I_{10}	I_9	I_8	I_7	I_6	M_C	RAM	Q	SIO_0	SIO_n	QIO_0	QIO_n	Loaded into M_C
0	0	0	0	0				Z	0	Z	0	
0	0	0	0	1				Z	1	Z	1	
0	0	0	1	0				Z	0	Z	M_N	SIO_0
0	0	0	1	1				Z	1	Z	SIO_0	
0	0	1	0	0				Z	M_C	Z	SIO_0	
0	0	1	0	1				Z	M_N	Z	SIO_0	
0	0	1	1	0				Z	0	Z	SIO_0	
0	0	1	1	1				Z	0	Z	SIO_0	QIO_0
0	1	0	0	0				Z	SIO_0	Z	QIO_0	SIO_0
0	1	0	0	1				Z	M_C	Z	QIO_0	SIO_0
0	1	0	1	0				Z	SIO_0	Z	QIO_0	
0	1	0	1	1				Z	I_C	Z	SIO_0	
0	1	1	0	0				Z	M_C	Z	SIO_0	QIO_0
0	1	1	0	1				Z	QIO_0	Z	SIO_0	QIO_0
0	1	1	1	0				Z	$I_N \oplus I_{OVR}$	Z	SIO_0	
0	1	1	1	1				Z	QIO_0	Z	SIO_0	
1	0	0	0	0				0	Z	0	Z	SIO_n
1	0	0	0	1				1	Z	1	Z	SIO_n
1	0	0	1	0				0	Z	0	Z	
1	0	0	1	1				1	Z	1	Z	
1	0	1	0	0				QIO_n	Z	0	Z	SIO_n
1	0	1	0	1				QIO_n	Z	1	Z	SIO_n
1	0	1	1	0				QIO_n	Z	0	Z	
1	0	1	1	1				QIO_n	Z	1	Z	
1	1	0	0	0				SIO_n	Z	QIO_n	Z	SIO_n
1	1	0	0	1				M_C	Z	QIO_n	Z	SIO_n
1	1	0	1	0				SIO_n	Z	QIO_n	Z	
1	1	0	1	1				M_C	Z	0	Z	
1	1	1	0	0				QIO_n	Z	M_C	Z	SIO_n
1	1	1	0	1				QIO_n	Z	SIO_n	Z	SIO_n
1	1	1	1	0				QIO_n	Z	M_C	Z	
1	1	1	1	1				QIO_n	Z	SIO_n	Z	

Notes: 1. Z = High impedance (outputs off) state.

2. Outputs enabled and M_C loaded only if \overline{SE} is LOW.

3. Loading of M_C from I_{10-6} overrides control from I_{5-0} , \overline{CE}_M , \overline{E}_C .

TABLE 4. CARRY-IN CONTROL MULTIPLEXER INSTRUCTION CODES.

I ₁₂	I ₁₁	I ₅	I ₃	I ₂	I ₁	C ₀
0	0	X	X	X	X	0
0	1	X	X	X	X	1
1	0	X	X	X	X	C _X
1	1	0	0	X	X	μ _C
1	1	0	X	1	X	μ _C
1	1	0	X	X	1	μ _C
1	1	0	1	0	0	μ̄ _C
1	1	1	0	X	X	M _C
1	1	1	X	1	X	M _C
1	1	1	X	X	1	M _C
1	1	1	1	0	0	M̄ _C

TABLE 5. CONDITION CODE OUTPUT (CT) INSTRUCTION CODES.

I ₃₋₀ HEX	I ₃	I ₂	I ₁	I ₀	I ₅ = I ₄ = 0	I ₅ = 0, I ₄ = 1	I ₅ = 1, I ₄ = 0	I ₅ = I ₄ = 1
0	0	0	0	0	(μ _N ⊕ μ _{OVR}) + μ _Z	(μ _N ⊕ μ _{OVR}) + μ _Z	(M _N ⊕ M _{OVR}) + M _Z	(I _N ⊕ I _{OVR}) + I _Z
1	0	0	0	1	(μ _N ⊙ μ _{OVR}) • μ _Z	(μ _N ⊙ μ _{OVR}) • μ _Z	(M _N ⊙ M _{OVR}) • M _Z	(I _N ⊙ I _{OVR}) • I _Z
2	0	0	1	0	μ _N ⊕ μ _{OVR}	μ _N ⊕ μ _{OVR}	M _N ⊕ M _{OVR}	I _N ⊕ I _{OVR}
3	0	0	1	1	μ _N ⊙ μ _{OVR}	μ _N ⊙ μ _{OVR}	M _N ⊙ M _{OVR}	I _N ⊙ I _{OVR}
4	0	1	0	0	μ _Z	μ _Z	M _Z	I _Z
5	0	1	0	1	μ̄ _Z	μ̄ _Z	M̄ _Z	Ī _Z
6	0	1	1	0	μ _{OVR}	μ _{OVR}	M _{OVR}	I _{OVR}
7	0	1	1	1	μ̄ _{OVR}	μ̄ _{OVR}	M̄ _{OVR}	Ī _{OVR}
8	1	0	0	0	μ _C + μ _Z	μ _C + μ _Z	M _C + M _Z	I _C + I _Z
9	1	0	0	1	μ̄ _C • μ̄ _Z	μ̄ _C • μ̄ _Z	M̄ _C • M̄ _Z	Ī _C • Ī _Z
A	1	0	1	0	μ _C	μ _C	M _C	I _C
B	1	0	1	1	μ̄ _C	μ̄ _C	M̄ _C	Ī _C
C	1	1	0	0	μ̄ _C + μ _Z	μ̄ _C + μ _Z	M̄ _C + M _Z	Ī _C + I _Z
D	1	1	0	1	μ _C • μ̄ _Z	μ _C • μ̄ _Z	M _C • M̄ _Z	I _C • Ī _Z
E	1	1	1	0	I _N ⊕ M _N	μ _N	M _N	I _N
F	1	1	1	1	I _N ⊙ M _N	μ̄ _N	M̄ _N	Ī _N

Notes: 1. ⊕ Represents EXCLUSIVE-OR

⊙ Represents EXCLUSIVE-NOR or coincidence.

TABLE 6. CRITERIA FOR COMPARING TWO NUMBERS FOLLOWING "A MINUS B" OPERATIONS.

Relation	For Unsigned Numbers			For 2's Complement Numbers		
	Status	I ₃₋₀		Status	I ₃₋₀	
		CT = H	CT = L		CT = H	CT = L
A = B	Z = 1	4	5	Z = 1	4	5
A ≠ B	Z = 0	5	4	Z = 0	5	4
A ≥ B	C = 1	A	B	N ⊙ OVR = 1	3	2
A < B	C = 0	B	A	N ⊕ OVR = 1	2	3
A > B	C • Z̄ = 1	D	C	(N ⊙ OVR) • Z̄ = 1	1	0
A ≤ B	C̄ + Z = 1	C	D	(N ⊕ OVR) + Z = 1	0	1

⊕ = Exclusive OR
⊙ = Exclusive NORH = HIGH
L = LOWNote: For Am2910, the CC input is active LOW, so use I₃₋₀ code to produce CT = L for the desired test.

TABLE 7. Y OUTPUT INSTRUCTION CODES.

\overline{OE}_Y	I_5	I_4	Y Output	Comment
1	X	X	Z	Output Off High Impedance
O	O	X	$\mu_i \rightarrow Y_i$	See Note 1
O	1	O	$M_i \rightarrow Y_i$	
O	1	1	$I_i \rightarrow Y_i$	

Notes: 1. For the conditions:

$I_5, I_4, I_3, I_2, I_1, I_0$ are LOW, Y is an input.

\overline{OE}_Y is "Don't Care" for this condition.

2. X is "Don't Care" condition.

TIMING ANALYSIS

In the previous chapter a timing analysis was presented with the shift-linkage, carry-control, and status registers implemented in SSI and MSI. This timing analysis will be repeated with the SSI and MSI logic replaced with the Am2904. Tables 8.1, 8.2, 8.4 and 8.5 list the typical AC characteristics of the registers, Am2902A, Am2901A, Am2903, and Am2904 used in these calculations. Table 8.3 lists the assumed AC characteristics for the set-up time of the Am2904.

Figure 2 illustrates the timing analysis for an Am2901A based design. The analysis begins with the LOW to HIGH transition of the system clock. All signals must be valid for the next LOW to HIGH transition of the system clock, i.e. one-microcycle later.

Figure 3 illustrates a similar timing analysis for the Am2903. The results of both analysis are listed in Table 9.

USING THE Am2904 IN A 16-BIT DESIGN

Perhaps the best technique for understanding the Am2904 is to simply compare 16-bit ALU designs with and without the Am2904. The first design, Figure 4a, is an example of a 16-bit CPU design using SSI/MSI parts instead of the Am2904. In Figure 4b, the second 16-bit CPU design, the Am2904 is shown replacing the SSI/MSI. The Am2904 substitutes for the appropriate shift matrix control and status registers. A more detailed comparison may be obtained by referring to the 16-bit ALU designs in Chapter III and the one in Appendix C of this chapter. To understand the Am2904 further, the usage of the Am2904 is described through the microprogram bits in the microprogram structure and shown later in the actual microprograms.

TABLE 8-1. STANDARD DEVICE SCHOTTKY SPEEDS.

Device and Path	Min.	Typ.	Max.
S-REGISTER Clock to Output \overline{OE} to Output Set-up		9 13 2	15 20
Am2902A Cn to Cn+x, Y, Z G, P to G, P G, P to Cn+x, Y, Z		7 7 5	11 10 7

TABLE 8-2.
PRELIMINARY SWITCHING CHARACTERISTICS.

Combinational Delays (ns)

From (Input)	To (Output)	t_{pd}
I_Z I_C I_N I_{OVR}	Y_Z Y_C Y_N Y_{OVR}	20
CP	Y_Z, Y_C, Y_N, Y_{OVR}	30
I_4, I_5	Y_Z, Y_C, Y_N, Y_{OVR}	23
I_Z, I_C, I_N, I_{OVR}	CT	30
CP	CT	30
I_0-I_5	CT	30
C_X	C_O	12
CP	C_O	20
$I_{1,2,3,5,11,12}$	C_O	24
SIO_n, QIO_n	SIO_o	16
SIO_o, QIO_o	SIO_n	16
I_C, I_N, I_{OVR}	SIO_n	20
SIO_n, QIO_n	QIO_o	16
SIO_o, QIO_o	QIO_n	16
CP	SIO_o, SIO_n QIO_o, QIO_n	21
I_6-I_{10}	SIO_o, SIO_n QIO_o, QIO_n	19

TABLE 8-3. ASSUMED SET-UP TIME.*

Input	TS
I_{OVR}, I_Z, I_N, I_C	20ns

*The actual set-up times were not available at the time this was written. See current data sheets for correct timing on these signals.

Am2901A — (MAY 18, 1978)

ROOM TEMPERATURE SWITCHING CHARACTERISTICS

Tables I, II, and III below define the timing characteristics of the Am2901A at 25°C. The tables are divided into three types of parameters; clock characteristics, combinational delays from inputs to outputs, and set-up and hold time requirements. The latter table defines the time prior to the end of the cycle (i.e., clock LOW-to-HIGH transition) that each input must be stable to guarantee that the correct data is written into one of the internal registers.

All values are at 25°C and 5.0V. Measurements are made at 1.5V with $V_{IL} = 0V$ and $V_{IH} = 3.0V$. For three-state disable tests, $C_L = 5.0pF$ and measurement is to 0.5V change on output voltage level. All outputs fully loaded.

TABLE 8-4.

TABLE I

CYCLE TIME AND CLOCK CHARACTERISTICS

TIME	TYPICAL	GUARANTEED
Read-Modify-Write Cycle (time from selection of A, B registers to end of cycle)	55ns	93ns
Maximum Clock Frequency to Shift Q Register (50% duty cycle)	40MHz	20MHz
Minimum Clock LOW Time	30ns	30ns
Minimum Clock HIGH Time	30ns	30ns
Minimum Clock Period	75ns	93ns

TABLE II

COMBINATIONAL PROPAGATION DELAYS (all in ns, $C_L = 50pF$ (except output disable tests))


From Input \ To Output	TYPICAL 25°C, 5.0V								GUARANTEED 25°C, 5.0V							
	Y	F ₃	C _{n+4}	$\overline{G}, \overline{P}$	F=0 R _L = 270	OVR	Shift Outputs		Y	F ₃	C _{n+4}	$\overline{G}, \overline{P}$	F=0 R _L = 270	OVR	Shift Outputs	
							RAM ₀ RAM ₃	Q ₀ Q ₃							RAM ₀ RAM ₃	Q ₀ Q ₃
A, B	45	45	45	40	65	50	60	—	75	75	70	59	85	76	90	—
D (arithmetic mode)	30	30	30	25	45	30	40	—	39	37	41	31	55	45	59	—
D (I = X37) (Note 5)	30	30	—	—	45	—	40	—	36	34	—	—	51	—	53	—
C _n	20	20	10	—	35	20	30	—	27	24	20	—	46	26	45	—
I ₀₁₂	35	35	35	25	50	40	45	—	50	50	46	41	65	57	70	—
I ₃₄₅	35	35	35	25	45	35	45	—	50	50	50	42	65	59	70	—
I ₆₇₈	15	—	—	—	—	—	20	20	26	—	—	—	—	—	26	26
OE Enable/Disable	20/20	—	—	—	—	—	—	—	30/33	—	—	—	—	—	—	—
A bypassing ALU (I = 2xx)	30	—	—	—	—	—	—	—	35	—	—	—	—	—	—	—
Clock  (Note 6)	40	40	40	30	55	40	55	20	52	52	52	41	70	57	71	30

TABLE III

SET-UP AND HOLD TIMES (all in ns) (Note 1)

From Input	Notes	TYPICAL 25°C, 5.0V		GUARANTEED 25°C, 5.0V	
		Set-Up Time	Hold Time	Set-Up Time	Hold Time
A, B Source	2, 4 3, 5	40 $t_{pwL} + 15$	0	93 $t_{pwL} + 25$	0
B Dest.	2, 4	$t_{pwL} + 15$	0	$t_{pwL} + 15$	0
D (arithmetic mode)		25	0	70	0
D (I = X37) (Note 5)		25	0	60	0
C _n		40	0	55	0
I ₀₁₂		30	0	64	0
I ₃₄₅		30	0	70	0
I ₆₇₈	4	$t_{pwL} + 15$	0	$t_{pwL} + 25$	0
RAM _{0, 3} , Q _{0, 3}		15	0	20	0

Notes: 1. See next page.

2. If the B address is used as a source operand, allow for the "A, B source" set-up time; if it is used only for the destination address, use the "B dest." set-up time.

3. Where two numbers are shown, both must be met.

4. " t_{pwL} " is the clock LOW time.

5. DVO is the fastest way to load the RAM from the D inputs. This function is obtained with I = 337.

6. Using Q register as source operand in arithmetic mode. Clock is not normally in critical speed path when Q is not a source.

TABLE 8-5.

A. Am2903 SWITCHING CHARACTERISTICS (TYPICAL ROOM TEMPERATURE PERFORMANCE) – (MAY 18, 1978)

Tables IA, IIA, and IIIA define the nominal timing characteristics of the Am2903 at 25°C and 5.0V. The Tables divide the parameters into three types: pulse characteristics for the clock and write enable, combinational delays from input to output, and set-up and hold times relative to the clock and write pulse.

Measurements are made at 1.5V with $V_{IL} = 0V$ and $V_{IH} = 3.0V$. For three-state disable tests, $C_L = 5.0pF$ and measurement is to 0.5V change on output voltage level.

TABLE IA – Write Pulse and Clock Characteristics

Time	
Minimum Time CP and \overline{WE} both LOW to write	15ns
Minimum Clock LOW Time	15ns
Minimum Clock HIGH Time	35ns

TABLE IIA – Combinational Propagation Delays (All in ns)
Outputs Fully Loaded. $CL = 50pF$ (except output disable tests)

To Output From Input	Y	C_{n+4}	$\overline{G}, \overline{P}$	(S) Z	N	OVR	DB	WRITE	QIO_0, QIO_3	SIO_0	SIO_3	SIO_0 (Parity)
A, B Addresses (Arith. Mode)	65	60	56	—	64	70	33	—	—	65	69	87
A, B Addresses (Logic Mode)	56	—	46	—	56	—	33	—	—	55	64	81
DA, DB Inputs	39	38	30	—	40	56	—	—	—	39	47	60
\overline{EA}	38	33	26	—	36	41	—	—	—	36	41	58
C_n	25	21	—	—	20	38	—	—	—	21	25	48
I_0	40	31	24	—	37	42	—	15(1)	—	41	39	63
I_{4321}	45	45	32	—	44	52	—	17(1)	—	45	51	68
I_{8765}	25	—	—	—	—	—	—	21	22/29(2)	24/17(2)	27/17(2)	24/17(2)
\overline{IEN}	—	—	—	—	—	—	—	10	—	—	—	—
\overline{OEB} Enable/Disable	—	—	—	—	—	—	12/15(2)	—	—	—	—	—
\overline{OEY} Enable/Disable	14/14(2)	—	—	—	—	—	—	—	—	—	—	—
SIO_0, SIO_3	13	—	—	—	—	—	—	—	—	—	19	20
Clock	58	57	40	—	56	72	24	—	28	56	63	76
Y	—	—	—	16	—	—	—	—	—	—	—	—
\overline{MSS}	25	—	25	—	25	25	—	—	—	24	27	24

Notes: 1. Applies only when leaving special functions.

2. Enable/Disable. Enable is defined as output active and correct. Disable is a three-state output turning off.

3. For delay from any input to Z, use input to Y plus Y to Z.

TABLE IIIA – Set-Up and Hold Times (All in ns)

CAUTION: READ NOTES TO TABLE III. NA = Note Applicable; no timing constraint.

Input	With Respect to to this Signal	HIGH-to-LOW		LOW-to-HIGH		Comment
		Set-up	Hold	Set-up	Hold	
Y	Clock	NA	NA	9	-3	To store Y in RAM or Q
\overline{WE} HIGH	Clock	5	Note 2	Note 2	0	To Prevent Writing
\overline{WE} LOW	Clock	NA	NA	15	0	To Write into RAM
A,B as Sources	Clock	19	-3	NA	NA	See Note 3
B as a Destination	Clock and \overline{WE} both LOW	-4	Note 4	Note 4	-3	To Write Data only into the Correct B Address
QIO_0, QIO_3	Clock	NA	NA	10	-4	To Shift Q
I_{8765}	Clock	2	Note 5	Note 5	-18	
\overline{IEN} HIGH	Clock	10	Note 2	Note 2	0	To Prevent Writing into Q
\overline{IEN} LOW	Clock	NA	NA	10	-5	To Write into Q

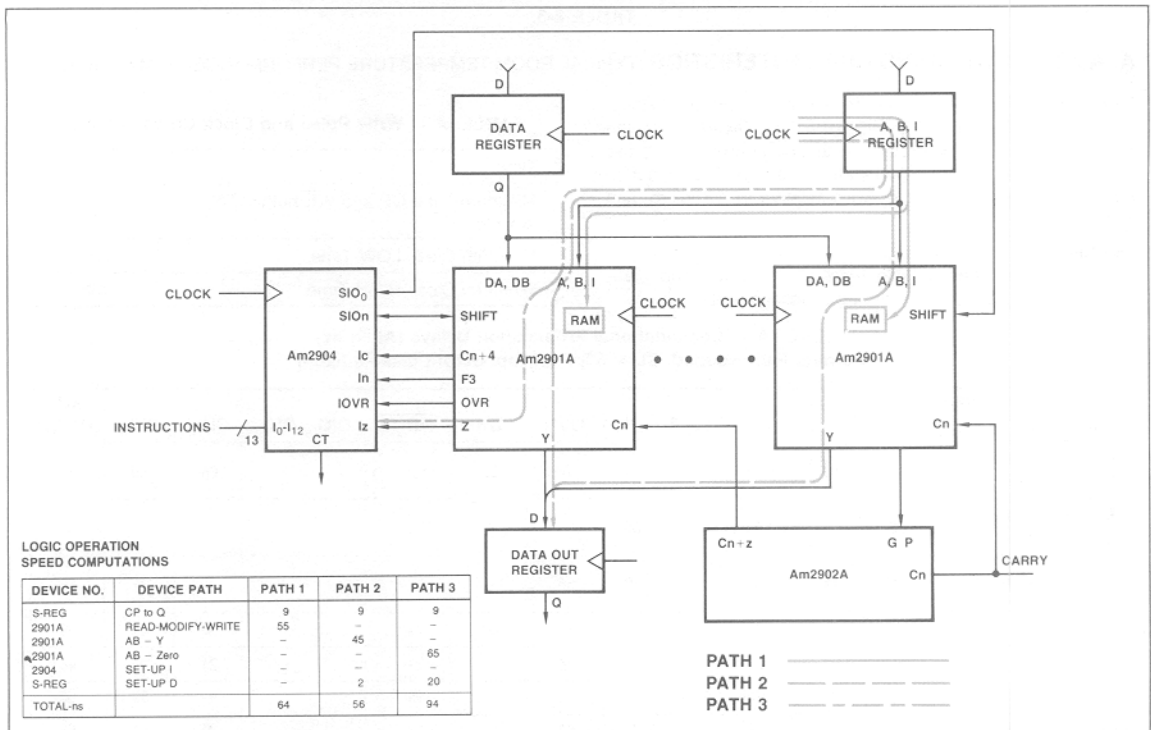


Figure 2-1.

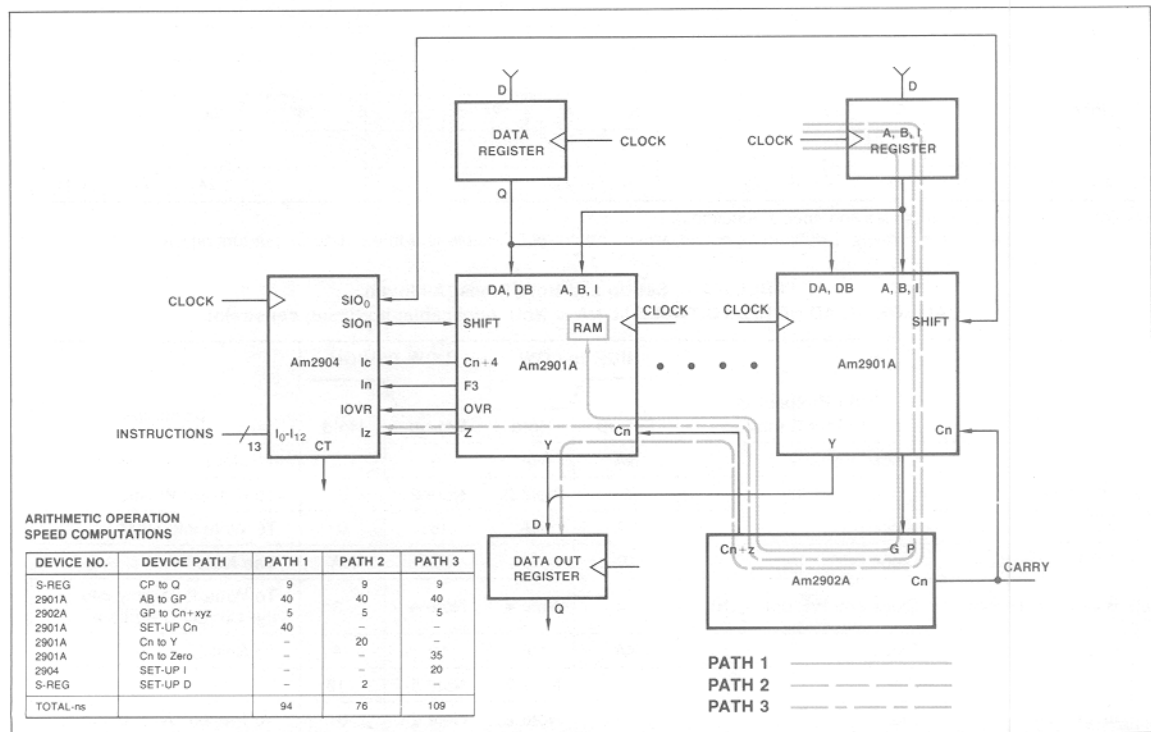


Figure 2-2.

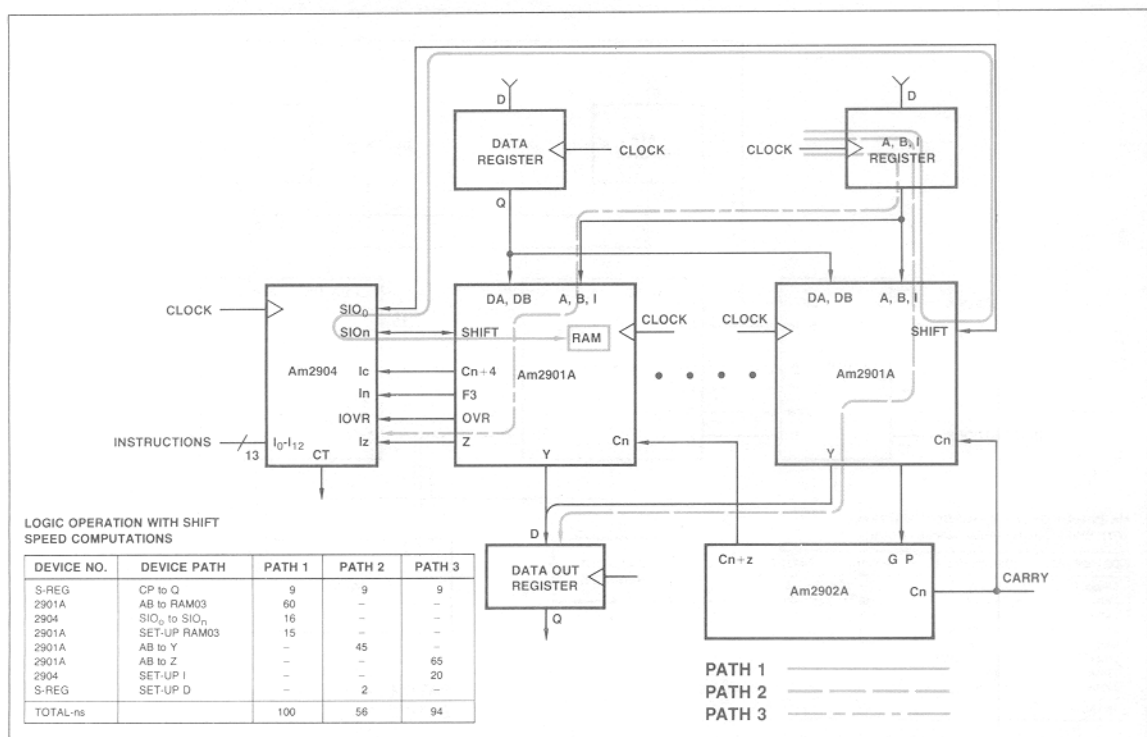


Figure 2-3.

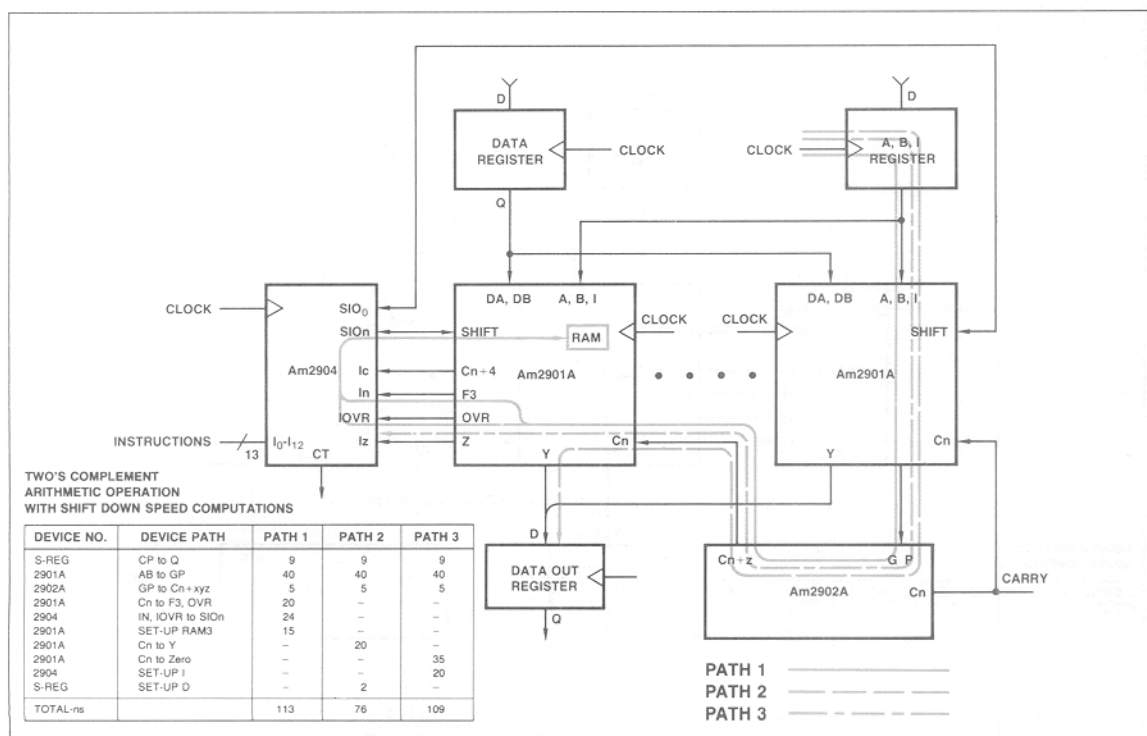


Figure 2-4.

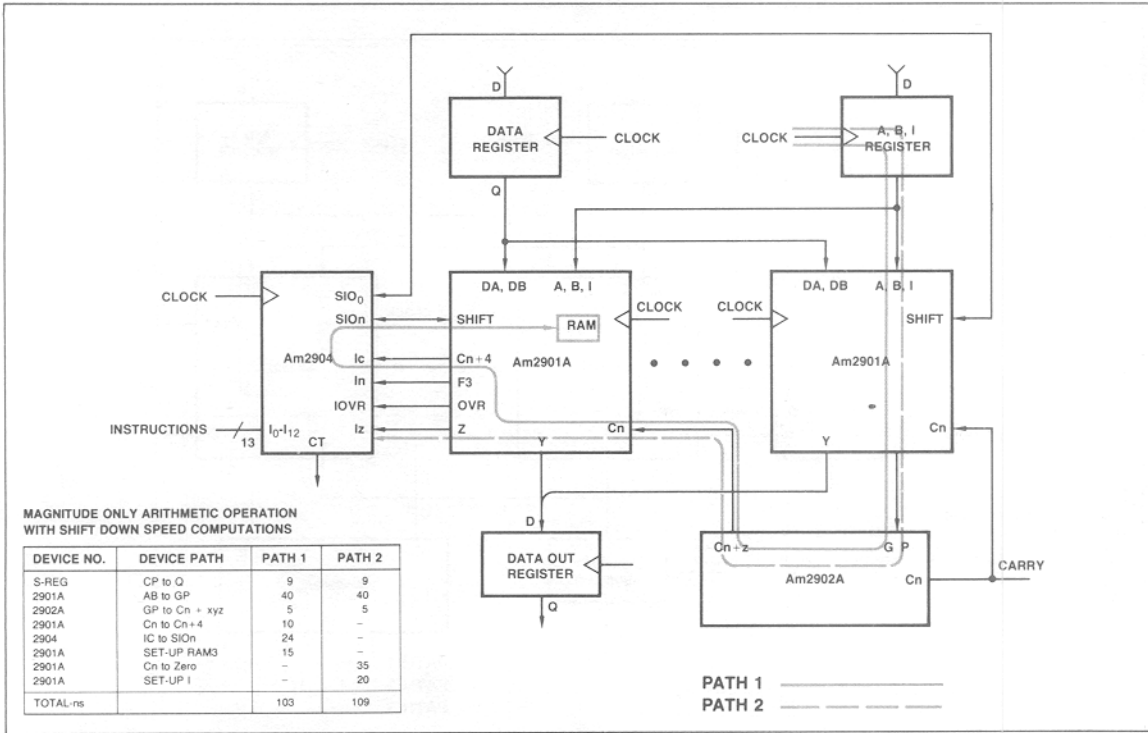


Figure 2-5.

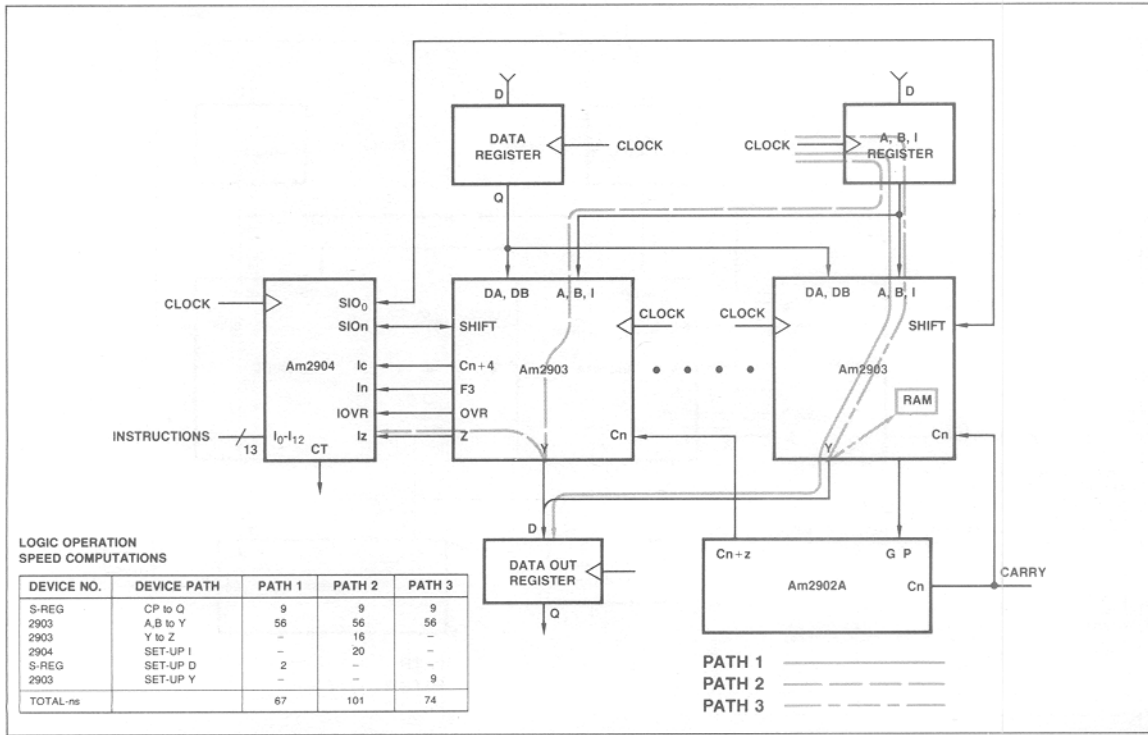


Figure 3-1.

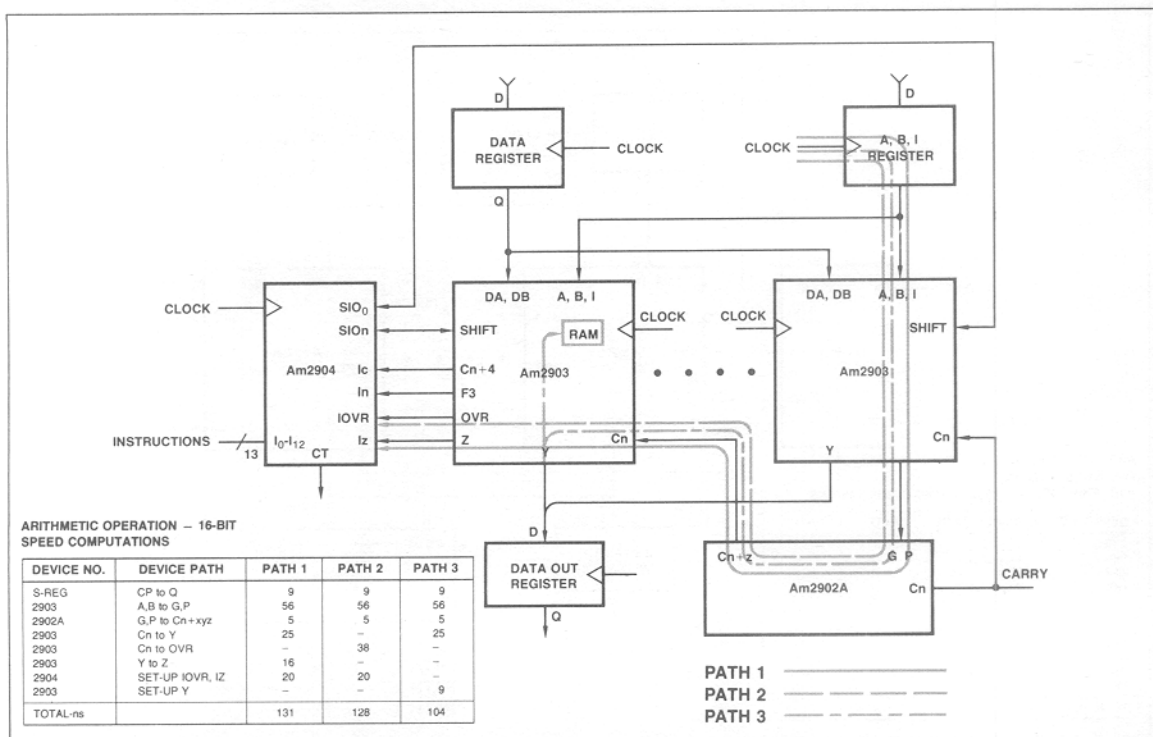


Figure 3-2.

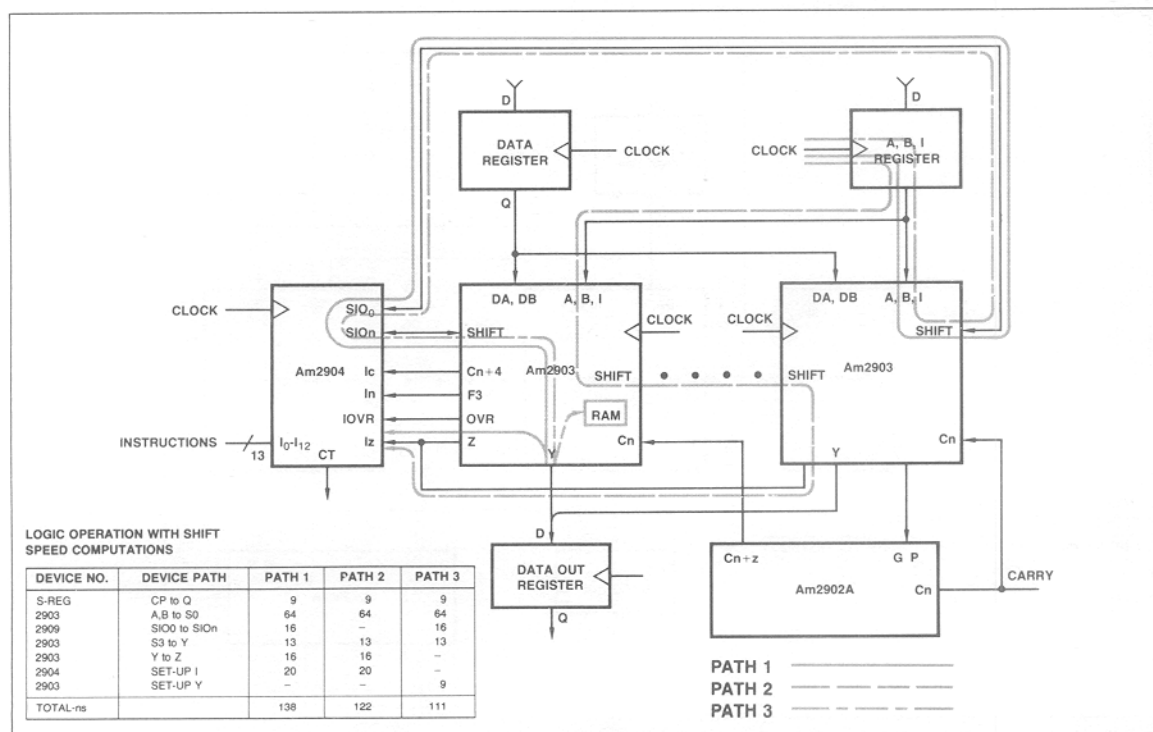


Figure 3-3.

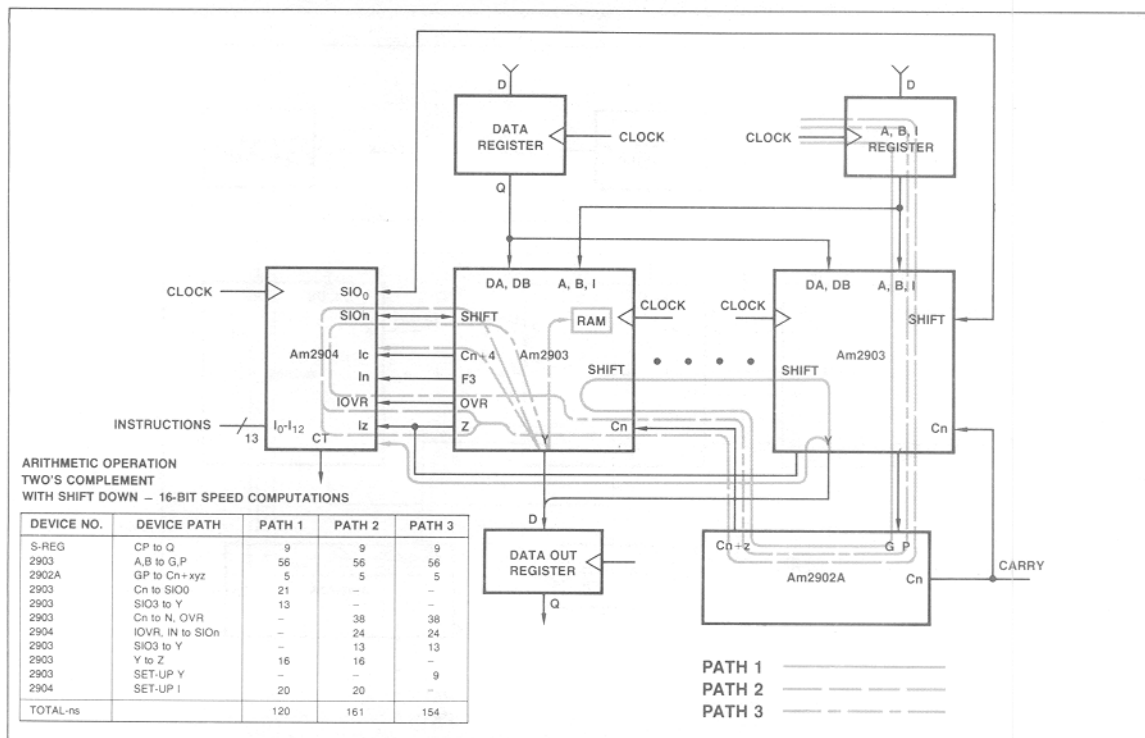


Figure 3-4.


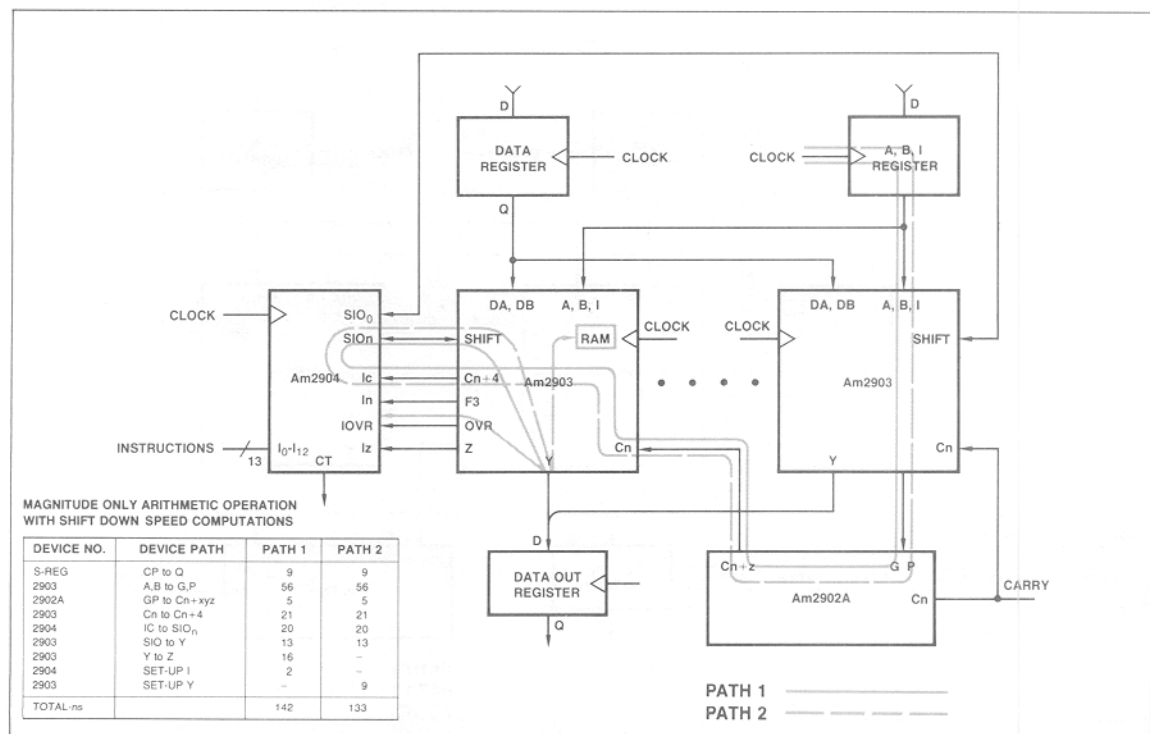


Figure 3-5.

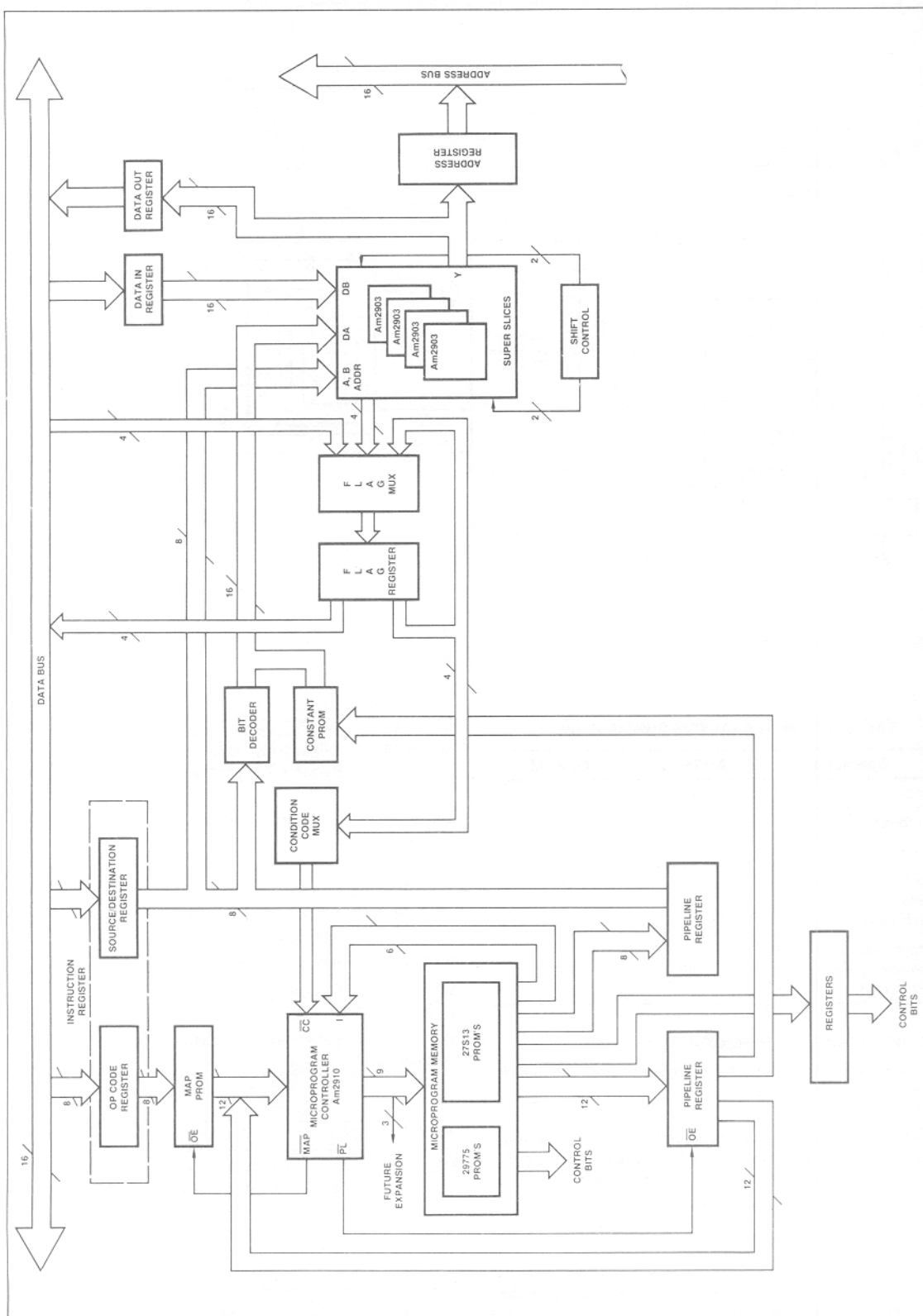

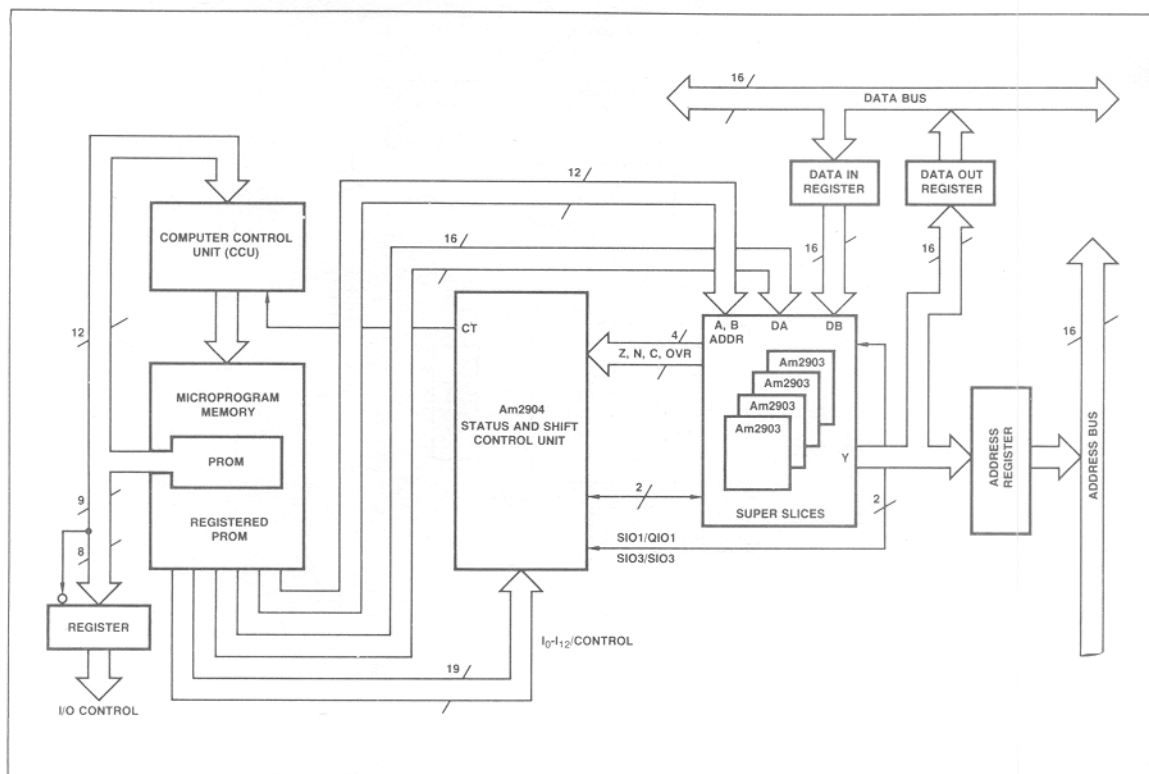


Figure 4b.

TABLE 9. TIMING ANALYSIS SUMMARY (ns).

Operation	Am2901A	Am2903
Logic	94	101
Arithmetic	109	131
Logic w/Shift	100	138
Two's Complement Arithmetic with Shift Down	113	161
Magnitude only Arithmetic with Shift Down	109	142

THE MICROPROGRAM STRUCTURE

The functions of the pipelined (PL) microprogram bits are illustrated in Figure 5 and as follows:

- Bits PL0 through PL11 This is a shared control field. The field is used for branching to a microprogram address or to load the CCU counter or control bits for I/O.
- Bit PL12 The shared control field is determined by PL12, LOW for branching and counting or HIGH for I/O control.
- Bit PL13 When LOW, enables the \overline{WRITE} output and allows the Q Register and Sign Compare flip-flop to be written into.

- Bits PL14 and PL15 The $\overline{CE\mu}$ and \overline{SE} control inputs of the Am2904, respectively. $\overline{CE\mu}$ enables the Micro Status Register. \overline{SE} enables the Am2904 shift operations.
- Bits PL16 through PL19 CCU Next Address.
- Bits PL20 through PL23 CCU Multiplex test select.
- Bit PL24 This bit determines the polarity of the incoming test signal to the CCU.
- Bit PL25 Active LOW Instruction Register enable.
- Bits PL26 through PL29 CCU multi-way branching select.
- Bits PL30 through PL32 Selects the ALU operand sources.

PL30	PL31	PL32	ALU Operand R	ALU Operand S
L	L	L	RAM Output A	RAM Output B
L	L	H	RAM Output A	DB ₀₋₃
L	H	X	RAM Output A	Q Register
H	L	L	DA ₀₋₃	RAM Output B
H	L	H	DA ₀₋₃	DB ₀₋₃
H	H	X	DA ₀₋₃	Q Register

L = LOW

H = HIGH

X = Don't Care

Bits PL33 Selects the ALU functions.
through PL36

I ₄	I ₃	I ₂	I ₁	Hex Code	ALU Functions
L	L	L	L	0	I ₀ = L Special Functions I ₀ = H F _i = HIGH
L	L	L	H	1	F = S Minus R Minus 1 Plus C _n
L	L	H	L	2	F = R Minus S Minus 1 Plus C _n
L	L	H	H	3	F = R Plus S Plus C _n
L	H	L	L	4	F = S Plus C _n
L	H	L	H	5	F = \overline{S} Plus C _n
L	H	H	L	6	F = R Plus C _n
L	H	H	H	7	F = \overline{R} Plus C _n
H	L	L	L	8	F _i = LOW
H	L	L	H	9	F _i = $\overline{R_i}$ AND S _i
H	L	H	L	A	F _i = R _i EXCLUSIVE NOR S _i
H	L	H	H	B	F _i = R _i EXCLUSIVE OR S _i
H	H	L	L	C	F _i = R _i AND S _i
H	H	L	H	D	F _i = R _i NOR S _i
H	H	H	L	E	F _i = R _i NAND S _i
H	H	H	H	F	F _i = R _i OR S _i

L = LOW

H = HIGH

i = 0 to 3

Bits PL37 Selects the ALU destination controls.
through PL40

I ₈	I ₇	I ₆	I ₅	Hex Code	Special Function
L	L	L	L	0	Unsigned Multiply
L	L	H	L	2	Two's Complement Multiply
L	H	L	L	4	Increment by One or Two
L	H	L	H	5	Sign/Magnitude-Two's Complement
L	H	H	L	6	Two's Complement Multiply, Last Cycle
H	L	L	L	8	Single Length Normalize
H	L	H	L	A	Double Length Normalize and First Divide Op.
H	H	L	L	C	Two's Complement Divide
H	H	H	L	E	Two's Complement Divide, Correction and Remainder

Bits PL41 This 4-bit wide field is used for the A-address
through PL44 source.

Bits PL45 This 4-bit wide field is used for the B-address
through PL48 source.

Bits PL49 This 4-bit wide field is the B destination ad-
through PL52 dress into which new data is written.

Bit PL53 Am2903 control input $\overline{OE_Y}$. When LOW enables
the ALU shifter output data onto the Y bus.

Bits PL54 Am2904 instruction code field.
through PL59

Bits PL60 Am2904 shift linkage multiplexer instruction
through PL63 code field.

Bits PL64 Am2904 "carry-in" control multiplexer field.
and PL65

Bits PL66 The $\overline{CE_M}$, $\overline{OE_{CT}}$, $\overline{OE_Y}$ control inputs of the
through PL68 Am2904, respectively.

Bit PL69 This bit when LOW, enables bits PL74 through
PL89 onto the Am2903 DA Bus.

Bit PL70 When LOW, zeros the carry in's to the Am2903
slices.

Bit PL71 When HIGH, enables a status register used in
BCD calculations.

Bit PL72 When LOW, clears the status register.

Bit PL73 When LOW, enables Am2909/11 registers.

Bits PL74 This field contains a 16-bit constant from mi-
through PL89 crocode that is passed to the Am2903's via
the DA bus. Constant is enabled by PL69.

I₀ OR I₁ OR I₂ OR I₄ = HIGH, $\overline{I_{EN}}$ = LOW

I ₈	I ₇	I ₆	I ₅	Hex Code	ALU Shifter Function	SIO ₃		Y ₃		Y ₂		Y ₁	Y ₀	SIO ₀	Write	Q Reg & Shifter Function	QIO ₃	QIO ₀
						Most Sig. Slice	Other Slices	Most Sig. Slice	Other Slices	Most Sig. Slice	Other Slices							
L	L	L	L	0	Arith. F/2→Y	Input	Input	F ₃	SIO ₃	SIO ₃	F ₃	F ₂	F ₁	F ₀	L	Hold	Hi-Z	Hi-Z
L	L	L	H	1	Log. F/2→Y	Input	Input	SIO ₃	SIO ₃	F ₃	F ₂	F ₁	F ₀	F ₀	L	Hold	Hi-Z	Hi-Z
L	L	H	L	2	Arith. F/2→Y	Input	Input	F ₃	SIO ₃	SIO ₃	F ₃	F ₂	F ₁	F ₀	L	Log. Q/2→Q	Input	Q ₀
L	L	H	H	3	Log. F/2→Y	Input	Input	SIO ₃	SIO ₃	F ₃	F ₃	F ₂	F ₁	F ₀	L	Log. Q/2→Q	Input	Q ₀
L	H	L	L	4	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	L	Hold	Hi-Z	Hi-Z
L	H	L	H	5	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	H	Log. Q/2→Q	Input	Q ₀
L	H	H	L	6	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	H	F→Q	Hi-Z	Hi-Z
L	H	H	H	7	F→Y	Input	Input	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Parity	L	F→Q	Hi-Z	Hi-Z
H	L	L	L	8	Arith. 2F→Y	F ₂	F ₃	F ₃	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	L	L	H	9	Log. 2F→Y	F ₃	F ₃	F ₂	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	L	H	L	A	Arith. 2F→Y	F ₂	F ₃	F ₃	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Log. 2Q→Q	Q ₃	Input
H	L	H	H	B	Log. 2F→Y	F ₃	F ₃	F ₂	F ₂	F ₁	F ₁	F ₀	SIO ₀	Input	L	Log. 2Q→Q	Q ₃	Input
H	H	L	L	C	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	H	Hold	Hi-Z	Hi-Z
H	H	L	H	D	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	H	Log. 2Q→Q	Q ₃	Input
H	H	H	L	E	SIO ₀ →Y ₀ , Y ₁ , Y ₂ , Y ₃	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	SIO ₀	Input	L	Hold	Hi-Z	Hi-Z
H	H	H	H	F	F→Y	F ₃	F ₃	F ₃	F ₃	F ₂	F ₂	F ₁	F ₀	Hi-Z	L	Hold	Hi-Z	Hi-Z

The Am2903 special functions can be selected by the following conditions: I₀ = I₁ = I₂ = I₃ = I₄ = LOW, $\overline{I_{EN}}$ = LOW

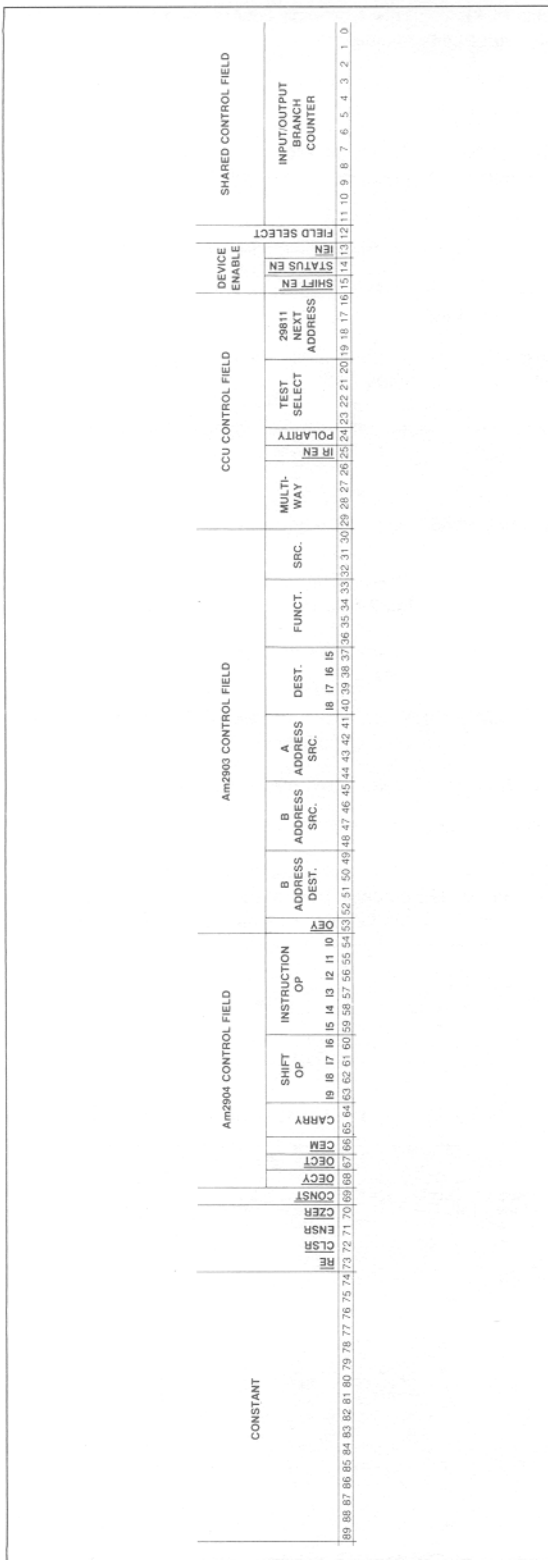


Figure 5.

SOME SAMPLE MICROROUTINES

The following algorithms are implemented using the Am2903 Superslices™ and Am2904 status and shift control unit. The algorithms were developed with the aid of AMDASM on System 29. All algorithms assume values and constants to be initialized prior to the entrance of the algorithms. Appendix A relates the actual microcode to the microword fields. Appendix B is the AMDASM Phase 1 and Phase 2 listings of the microprograms and the definitions of mnemonics. Figure 4b is a block diagram of the CPU hardware including the Am2904 Status and Shift Control Unit from which the microroutines were developed. A detailed diagram of the CPU hardware is in Appendix C.

Normalization, Single- and Double-Length

Normalization is used as a means of referencing a number to a fixed radix point. Normalization strips out all leading sign bits such that the two bits immediately adjacent to the radix point are of opposite polarity.

Normalization is commonly used in such operations as fixed-to-floating point conversion and division. The Am2903 provides for normalization by using the Single-Length and Double-Length Normalize commands. Figure 6a represents the Q Register of a 16-bit processor which contains a positive number. When the Single-Length Normalize command is applied, each positive edge of the clock will cause the bits to shift toward the most significant bit (bit 15) of the Q Register. Zeros are shifted in via the QIO0 port. When the bits on either side of the radix point (bits 14 and 15) are of opposite value, the number is considered to be normalized as shown in Figure 6b. The event of normalization is externally indicated by a HIGH level on the Cn+4 pin of the most significant slice ($Cn+4 \text{ MSS} = Q3 \text{ MSS} \vee Q2 \text{ MSS}$).

There are also provisions made for a normalization indication via the OVR pin one microcycle before the same indication is available on the Cn+4 pin ($OVR = Q2 \text{ MSS} \vee Q1 \text{ MSS}$). This is for use in applications that require a stage of register buffering of the normalization indication.

Since a number comprised of all zeros is not considered for normalization, the Am2903 indicates when such a condition arises. If the Q Register is zero and the Single-Length Normalize command is given, a HIGH level will be present on the Z line.

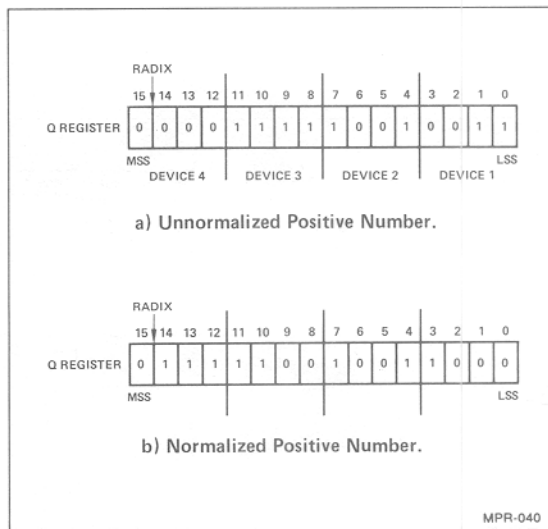


Figure 6.

Normalizing a double-length word can be done with the Double-Length Normalize command which assumes that a user-selected

When double-length normalization is being performed, shift counting is done either with an extra microcycle or with an external counter. Figure 13 illustrates the double-length normalize flowchart and Figure 14 shows the microcode.



Figure 7.



Figure 8. Single Length Normalize.

This Special Function allows for easy implementation of unsigned multiplication. Figure 15 is the unsigned multiply flow chart. The algorithm requires that initially the RAM word addressed by Address port B be zero, that the multiplier be in the Q Register, and that the multiplicand be in the register addressed by Address port A. The initial conditions for the execution of the algorithm are that: 1) register R₁ be reset to zero; 2) the multiplicand be in R₀ and 3) the multiplier be in R₁. The first operation transfers the

When the unsigned Multiply command is given, the Z pin of device 1 becomes an output while the Z pins of the remaining devices are specified as inputs as shown in Figure 18. The Z output of device 1 is the same state as the least significant bit of the multiplier in the Q Register. The Z output of device 1 informs

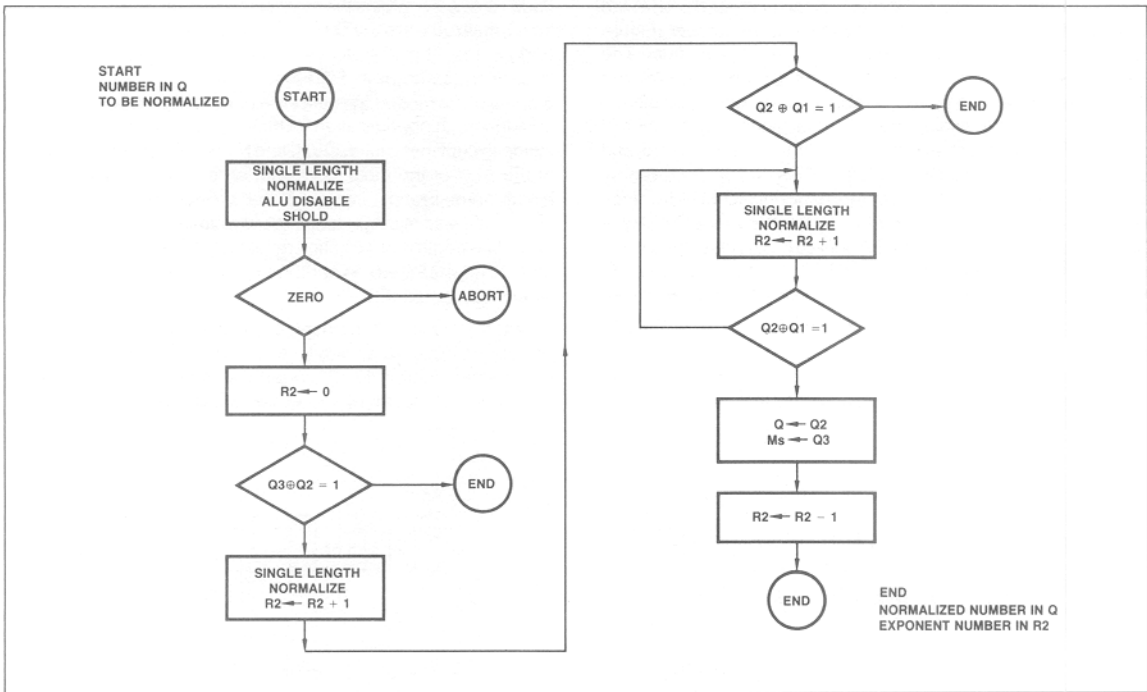


Figure 9. Single Length Normalize.

013C SLN R2,R2,OFF & CONT & SHOLD
013D MAZ & T & CJP & GOTO ABORT
013E MAC & T & LOW R0 & CJP & GOTO END
013F SLN R2,R2 & MAO & T & CJP ONE & GOTO END & SUL
0140 AGAIN: SLN R2,R2 & MIO & T & CJP ONE & GOTO AGAIN & SUL
0141 SDQP & SMS & CONT
0142 SRS R2,R2,R0 & CONT

Figure 10.

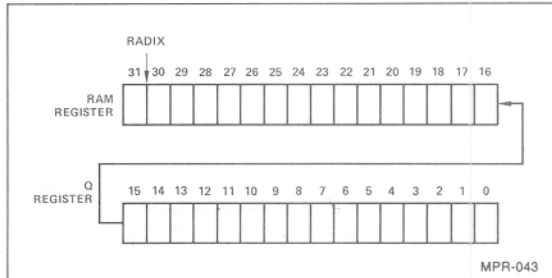


Figure 11. Double Length Word.

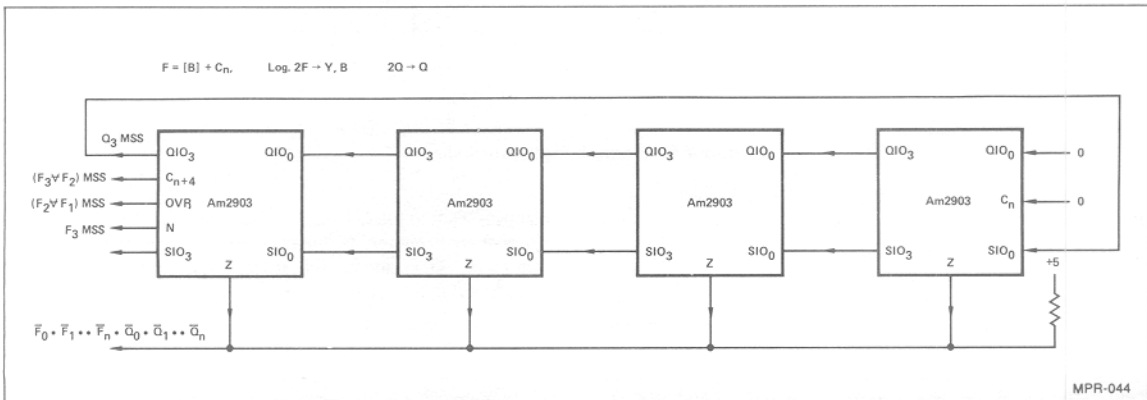


Figure 12. Double Length Normalize.

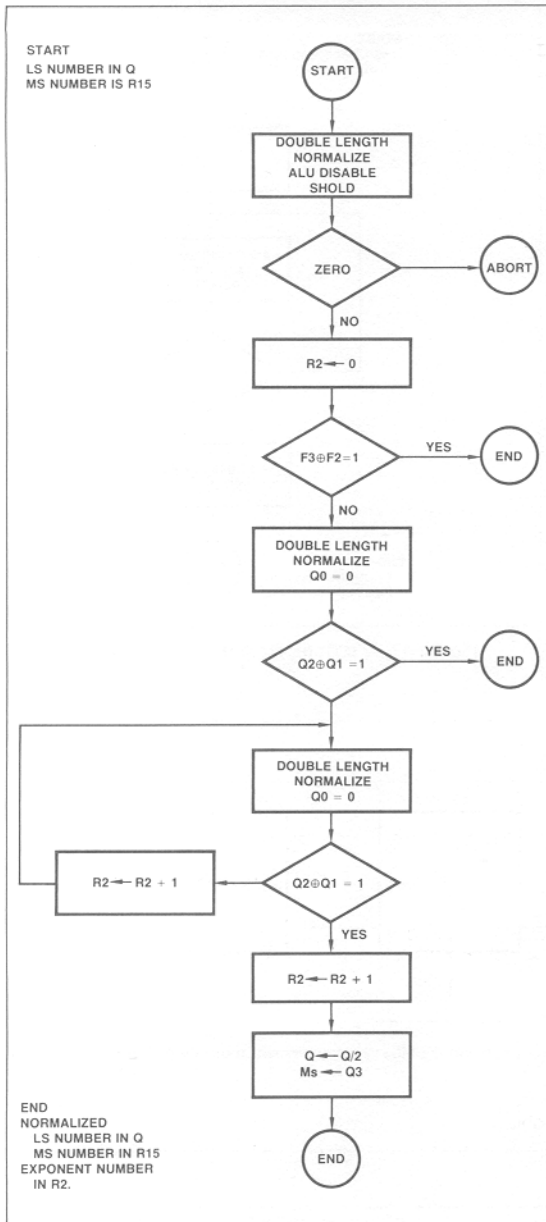


Figure 13. Double Length Normalize.

0148	DLN R15,R15,OFF & CONT & SHOLD
0149	MAZ & T & CJP & GOTO ABORT
014A	LOW R2 & MAC & T & CJP & GOTO END2
014B	DLN R15,R15 & SDUL & MAO & T & CJP & GOTO JUMP1
014C	LOOP4: DLN R15,R15 & SDUL & MIO & T & CJP & GOTO JUMP1
014D	PAR R2,R2 & JP ONE & GOTO LOOP4
014E	JUMP1: PAR R2,R2 & CONT ONE
014F	SDRQ R15, R15 & SDMS & END

Figure 14.

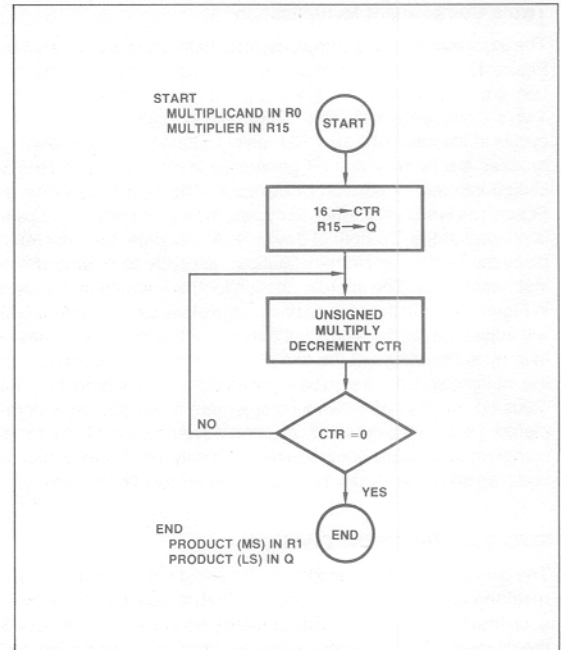


Figure 15. Unsigned 16 X 16 Multiply.

the ALUs of all the slices, via their Z pins, to add the partial product (referenced by the B address port) to the multiplicand (referenced by the A address port) if Z = 1. If Z = 0, the output of the ALU is simply the partial product (referenced by the B address port). Since Cn is held LOW, it is not a factor in the computation. Each positive-going edge of the clock will internally shift the ALU outputs toward the least significant bit and simultaneously store the shifted results in the register selected by the B address port, thus becoming the new partial sum. During the down shifting process, the Cn+4 generated in device 4 is internally shifted into the Y₃ position of device 4. At this time, one bit of the multiplier will down shift out of the QIO₀ ports of each device into the QIO₃ port of the next less significant slice. The partial product is shifted down between chips in a like manner, between the SIO₀ and SIO₃ ports, with SIO₀ of device 1 being connected to QIO₃ of device 4 for purposes of constructing a 32-bit long register to hold the 32-bit product. Shifting of the partial product between the B address and Q registers are accomplished via the Am2904. At the finish of the 16 x 16 multiply, the most significant 16 bits of the product will be found in the register referenced by the B address lines while the least significant 16 bits are stored in the Q Register. Using a typical Computer Control Unit (CCU), as shown in Appendix C, the unsigned multiply operation requires only two lines of microcode, as shown in Figure 16, and is executed in 17 microcycles.

010C	LQPT R15 & F & GRD & PUSH & COUNT 00E
010D	UMUL R1,R1,R0 & F & CNT & SDDL & RFCT

Figure 16.

Two's Complement Multiplication

The algorithm for two's complement multiplication is illustrated by Figure 17. The initial conditions for two's complement multiplication are the same as for the unsigned multiply operation. The Two's Complement Multiply Command is applied for 15 clock cycles in the case of a 16 x 16 multiply. During the down shifting process the term $N \nabla OVR$ generated in device 4 is internally shifted into the Y_3 position of device 4. The data flow shown in Figure 18a is still valid. After 15 cycles, the sign bit of the multiplier is present at the Z output of device 1. At this time, the user must place the Two's Complement Multiply Last cycle command on the instruction lines. The interconnection for this instruction is shown in Figure 18b. On the next positive edge of the clock, the Am2903 will adjust the partial product, if the sign of the multiplier is negative, by subtracting out the two's complement representation of the multiplicand. If the sign bit is positive, the partial product is not adjusted. At this point, two's complement multiplication is completed. Using a typical CCU, as shown in Appendix C, the two's complement multiply operation requires only three lines of microcode, as shown in Figure 19, and is executed in 17 microcycles.

TWO'S COMPLEMENT DIVISION

The division process is accomplished using a four quadrant non-restoring algorithm which yields an algebraically correct answer such that the divisor times the quotient plus the remainder equals the dividend. The algorithm works for both single precision and

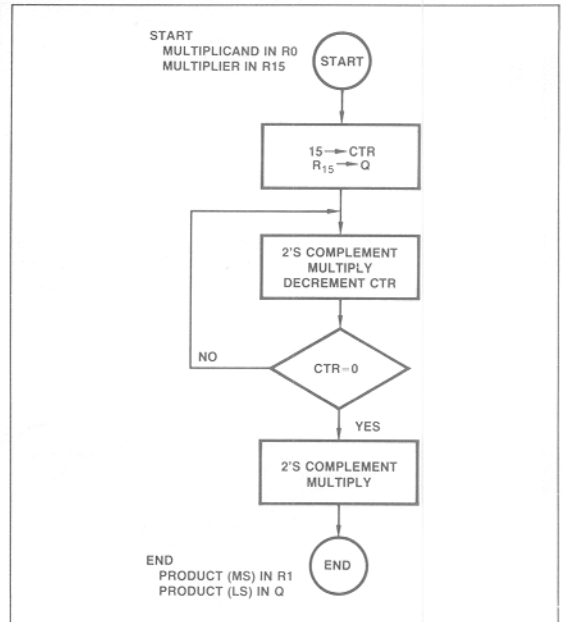


Figure 17. 2's Complement 16 X 16 Multiply.

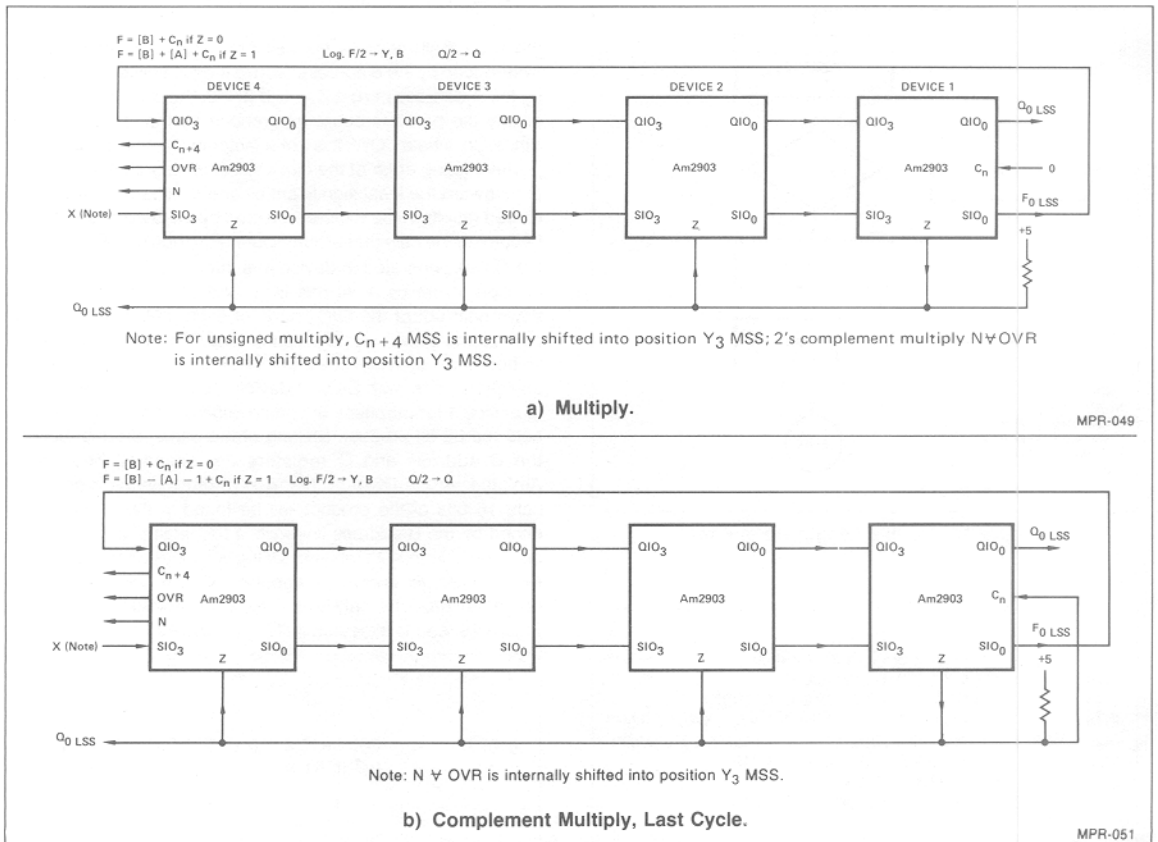


Figure 18.

0113	LQPT R15 & F & GRD & PUSH & COUNT 00D
0114	TCM R1,R1,R0 & F & CNT & SDDL & RFCT
0115	TCMC R1,R1,R0 & SDDL & CONT CZ

Figure 19.

multi-precision divide operations. The only condition that needs to be met is that the absolute magnitude of the divisor be greater than the absolute magnitude of the dividend. For multi-precision divide operations the least significant bit of the dividend is truncated. This is necessary if the answer is to be algebraically correct. Bias correction is automatically provided by forcing the least significant bit of the quotient to a one, yet an algebraically correct answer is still maintained. Once the algorithm is completed, the answer may be modified to meet the user's format requirements, such as rounding off or converting the remainder

so that its sign is the same as the dividend. These format modifications are accomplished using the standard Am2903 instructions.

The true value of the remainder is equal to the value stored in the working register times 2^{n-1} when n is the number of quotient digits.

The following paragraphs describe a double precision divide operator.

Referring to the flow chart outlined in Figure 20, we begin the algorithm with the assumption that the divisor is contained in R_0 , while the most significant and least significant halves of the dividend reside in R_1 and R_4 respectively. The first step is to duplicate the divisor by copying the contents of R_0 into R_3 . Next the most significant half of the dividend is copied by transferring the contents of R_1 into R_2 while simultaneously checking to ascertain if the divisor (R_0) is zero. If the divisor is zero then division is aborted. If the divisor is not zero, the copy of the most significant half of the dividend in R_2 is converted from its two's complement to its sign magnitude representation. The divisor in R_3 is converted in like manner in

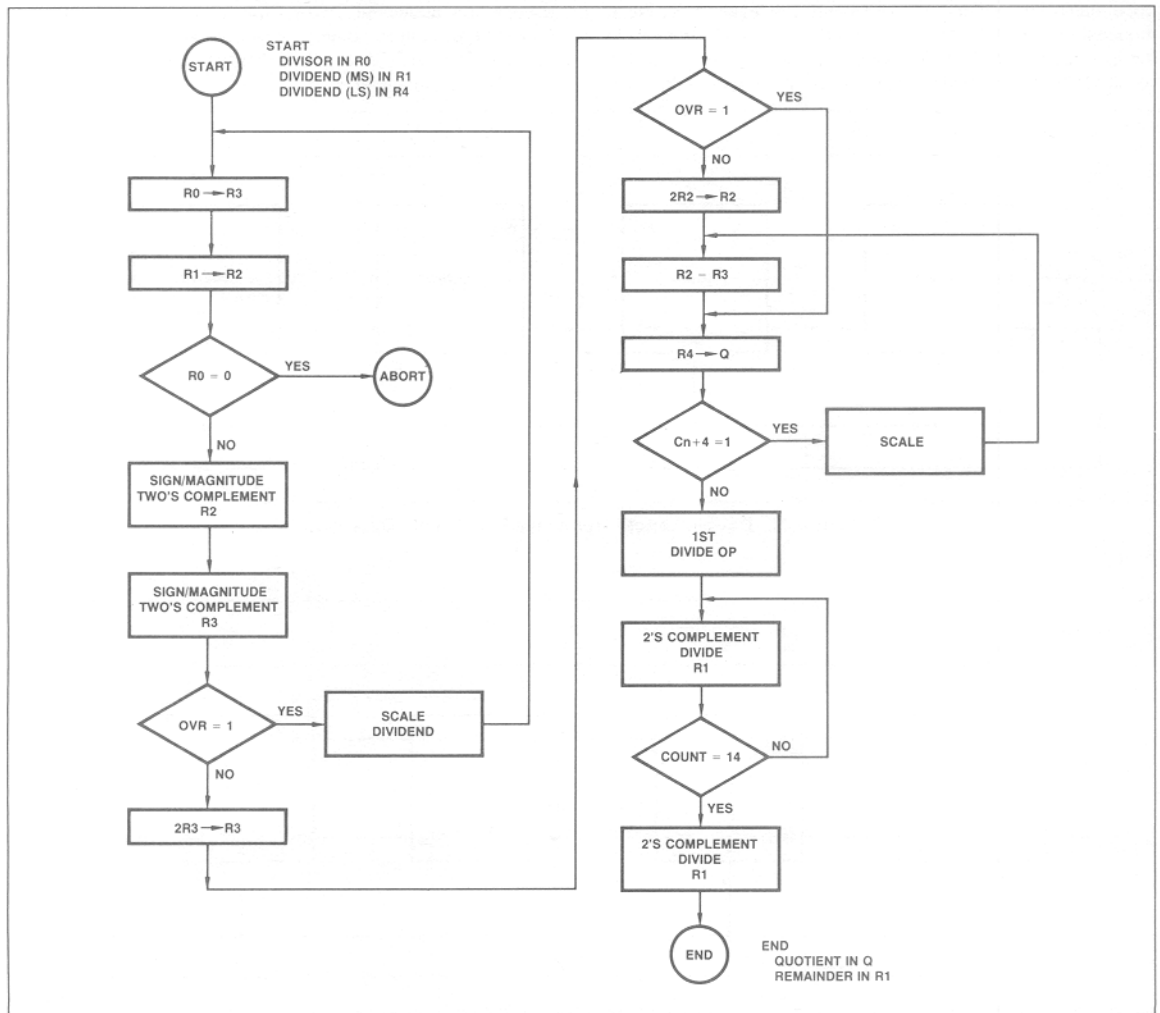


Figure 20. Two's Complement Division.

the next step, while testing to see if the results of the dividend conversion yielded an indication on the overflow pin of the Am2903. If the output of the overflow pin is 'one' then the dividend is -2^n and hence is the largest possible number, meaning that it cannot be less than the divisor. What must be done in this case is to scale the dividend by down shifting the upper and lower halves stored in R_1 and R_4 respectively. After scaling, the routine requires that the algorithm be reinitiated at the beginning.

Conversely, if the output of the overflow pin is not a one, the sign magnitude representation of the divisor (R_3) is shifted up in the Am2903, removing the sign while at the same time testing the results of two's complement to sign magnitude conversion of the divisor in the Am2910. If the results of the test indicate that the divisor is -2^n i.e., overflow equals one, then the lower half of the dividend is placed in the Q register and division may proceed. This is possible because the divisor is now guaranteed to be greater than the dividend. If overflow is not a one then we must proceed by shifting out the sign of the sign magnitude representation of the dividend stored in R_2 . At this point we are able to check if the divisor is greater than the dividend by subtracting the absolute value of the divisor (R_3) from the absolute value of the upper half of the dividend (R_2) and storing the results in R_3 . Next, the least significant half of the dividend is transferred from R_4 to the Q register while simultaneously testing the carry from the result of the divisor/dividend subtraction. If the carry (C_{n+4}) is

one, indicating the divisor is not greater than the dividend then a scaling operation must occur. This involves either shifting up the divisor or shifting down the dividend. If the carry is not one then the divisor is greater than the dividend and division may now begin.

The first divide operation is used to ascertain the sign bit of the quotient. The two's complement divide instruction is then executed repetitively, fourteen times in the case of a sixteen bit divisor and a thirty-two bit dividend. The final step is the two's complement correction command which adjusts the quotient by allowing the least significant bit of the quotient to be set to one. At the end of the division algorithm the sixteen bit quotient is found in the Q register while the remainder now replaces the most significant half of the dividend in R_1 . It should be noted that the remainder must be shifted down fifteen places to represent its true value. The interconnections for these instructions are shown in Figures 21, 22, 23. Using a typical CCU as shown in Appendix C, the double precision divide operation microcode, is shown in Figure 24.

For those applications that require truncation instead of bias correction, the same algorithm as above should be implemented except one additional Two's Complement Divide instruction should be used in lieu of the Two's Complement Divide Correction and Remainder instruction. However, this technique results in an invalid remainder.

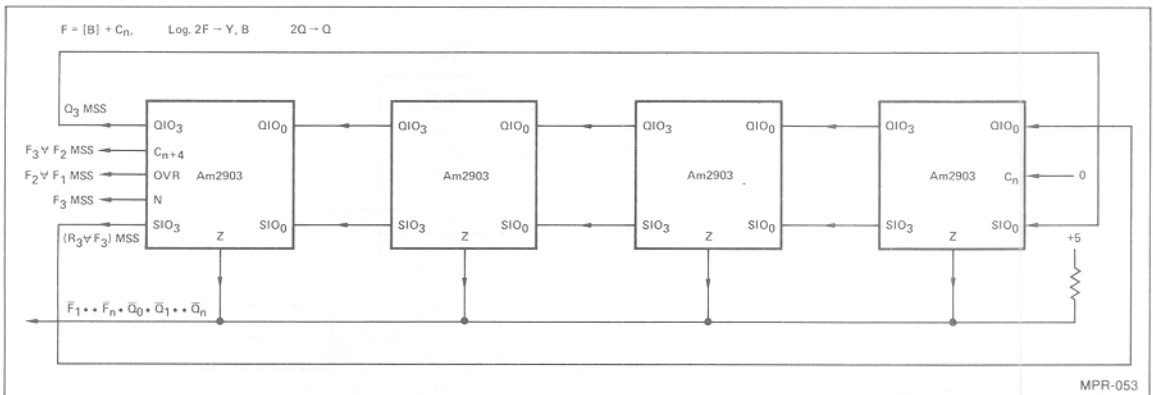


Figure 21. Double Length Normalize/First Divide Operation.

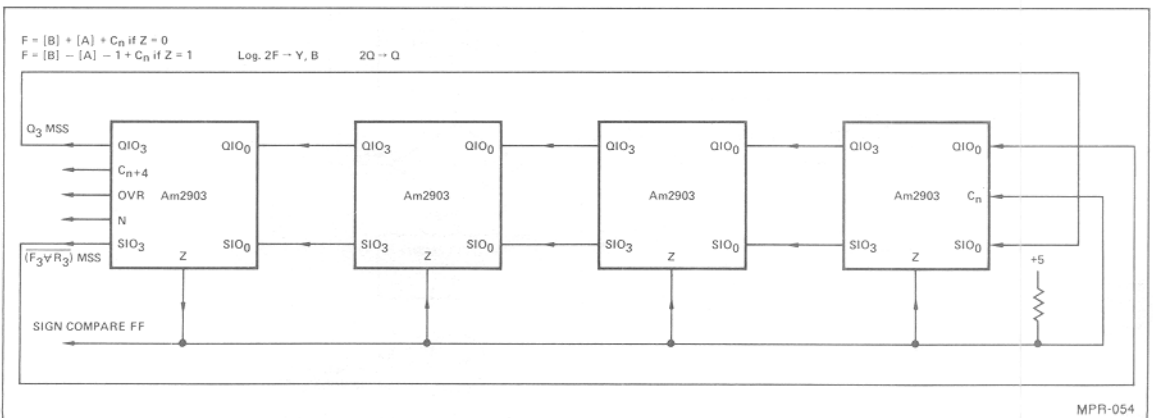


Figure 22. 2's Complement Divide.

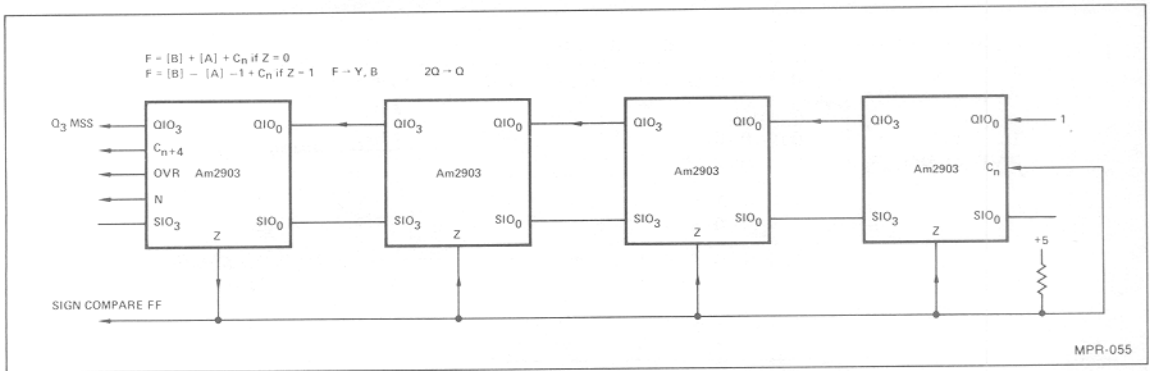


Figure 23. 2's Complement Divide Correction.

```

0119 DIV:      LOW R10 & JSR & GOTO INP
011A          PAR R7,R15 & JSR & GOTO INP
011B          PAR R1,R15, & JSR & GOTO INP
011C          PAR R4,R15 & CONT
011D LOOP1:   PAR R3,R7 & CONT
011E          PAR R2,R1 & T & MIZ & CJP & GOTO ABORT
011F          SMT C R2,R2 & CONT Z
0120          SMT C R3,R3 & T & MIO & CJP CZ & GOTO SCALE1
0121          ALUOFF & T & MIO & CJP & GOTO SKIP6
0122          SURL R3,R3 & SUL & CONT
0123          SURL R2,R2 & SUL & CONT
0124          ALUOFF & JP & GOTO LOOP2
0125 SCALE1:  LQPT R4 & JSR & GOTO SDIVD
0126          ALUOFF & JP LOOP1
0127 LOOP2:   SSR R3,R2,YBUS & CONT ONE
0128 SKIP6:   LQPT R4 & F & MIC & CJP & GOTO SKIP3
0129          ALUOFF & JSR & GOTO SDIVD
012A          SURL R2,R2 & SDL & CONT
012B          ALUOFF & JP & GOTO LOOP2
012C SKIP3:   ALUOFF & F & GRD & LDCT & COUNT 00C
012D          DLN R1,R1,R7 & T & GRD & SDUL & PUSH
012E          TDIV R1,R1,R7 & F & CNT & SDUL & RFCT CZ
012F          TDC R1,R1,R7 & SUH & CONT CZ
0130          QMOV R15 & JSR & GOTO OUTP
0131          PAR R15,R1 & JSR & GOTO OUTP
0132          ALUOFF & JP & GOTO DIV
0133 SDIVD:   PAR R1,R1 & CONT
0134          ALUOFF & T & MIS & CJP & GOTO NEG
0135          PAR R1,R1,ADRQ & SDDL & CONT
0136          ALUOFF & JP & GOTO RET
0137 NEG:     PAR R1,R1,ADRQ & SDDL & CONT
0138 RET:     QMOV R4 & CONT
0139          PAR R10,R10 & RTN ONE
  
```

Figure 24.

NON-RESTORING BINARY ROOTS

The algorithm for Non-Restoring Binary Roots is illustrated in Figure 25. The initial conditions required are: 1) the non-negative number to be rooted in the radicand register, R_1 ; 2) R_2 has the positive append bits 101_B ; 3) R_3 has the negative append bits 011_B ; 4) R_4 is the mask register with $BFFF_H$; 5) R_5 is the partial register with 4000_H ; and 6) the counter register, R_6 , with the value 08_H .

An example of the Non-Restoring Binary Root algorithm is shown in Figure 26. Starting at the binary point, the number to be rooted is partitioned into pairs. The partial value is subtracted from the first pair. An intermediate remainder and sign are then produced.

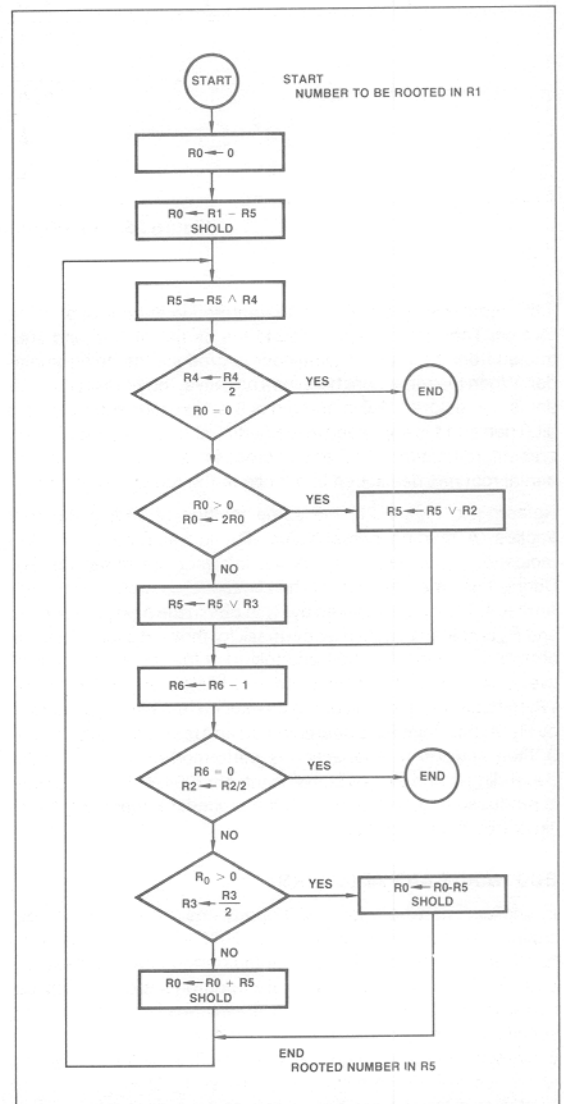


Figure 25. Non-Restoring Binary Root.

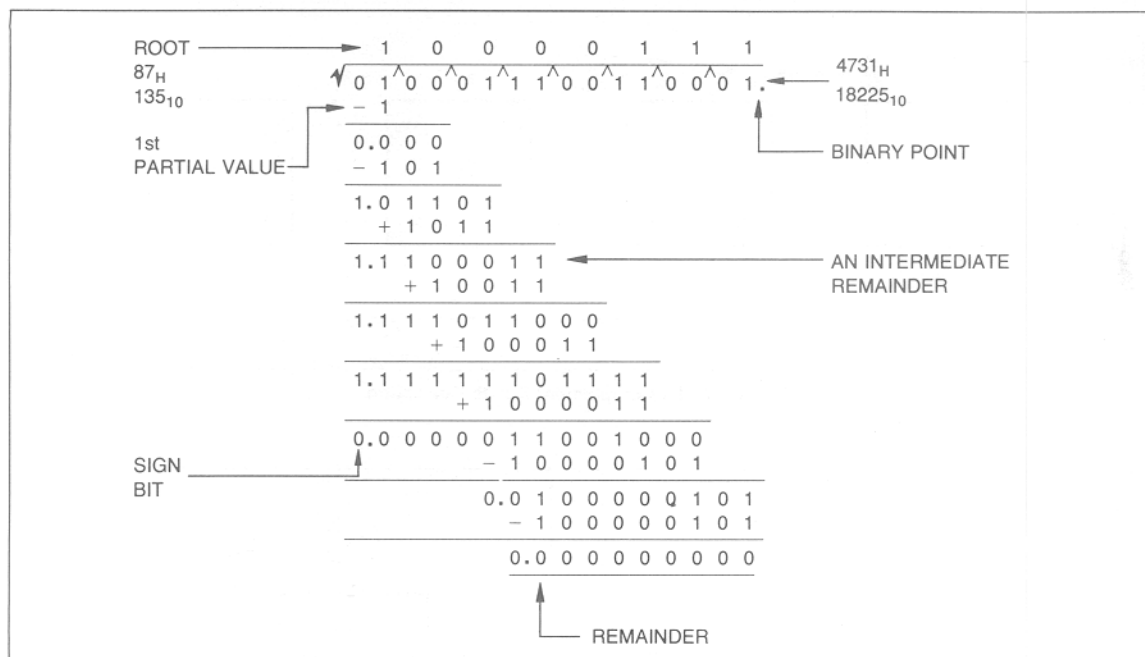


Figure 26. Non-Restoring Binary Root Example.

If the remainder is positive, a 1 is entered in the corresponding root bit. Then a 01 is appended to the partial, shifted and subtracted from the present remainder to produce the next remainder. When the remainder becomes negative, the present remainder is not restored. A 0 is entered in the next corresponding root bit. Then an 11 is appended to the partial, shifted and added to the present remainder. The entire process is repeated until the partial root has developed into 8 bits or the remainder is zero.

Referring to Figure 26, the same method of finding the root applies. A starting partial value, R_5 , is subtracted from the radicand, R_1 , which produces the intermediate remainder R_0 . During this time, the sign of the remainder is stored within the Am2904. Then R_5 is masked by R_4 to obtain the next partial value and R_4 is shifted to obtain a new mask for the next cycle. Status is obtained from the Am2904 and tested. If the remainder is positive, a root bit of 1 is developed and bits 01 appended by R_2 . When negative, a root bit of 0 is developed and bits 11 appended by R_3 . At this point R_6 is decremented and tested for zero. If $R_6 \neq 0$, then addition or subtraction is performed on the remainder depending on the sign bit stored in the Am2904. A new remainder is produced and cycled through the procedure again. Figure 27 illustrates the microcode.

BCD HARDWARE ADDITIONS

In applications where fast BCD operations are needed the designer has the option of using a slight amount of additional hardware to dramatically increase the performance of these operations. These firmware/hardware trade-offs are very application sensitive. The hardware-firmware examples given below are specifically for an intensive BCD system with a large fraction of conventional logic-arithmetic operations. The designer is willing to reduce cycle time slightly to increase BCD throughput. Small hardware additions are acceptable as long as flexibility is retained.

```


0152  SQRT:  LOW R10 & CONT
0153          LOW R0 & CONT
0154          PAR R1,R15 & CONT
0155          PAR R2,R0,,DARB & CONST 0005 & CONT
0156          PAR R3,R0,,DARB & CONST 0003 & CONT
0157          PAR R4,R0,,DARB & CONST H#BFFF & CONT
0158          PAR R4,R0,,DARB & CONST 4000 & CONT
0159          PAR R6,R0,,DARB & CONST 0008 & CONT
015A          SRS R0,R1,R5 & CONT & SHOLD
015B  CYCLE:  AND R5,R5,R4 & CONT
015C          SDRL R4,R4 & MAS & CJP & GOTO END3
015D          SDRL R0,R0, & T & MAS & CJP & GOTO POS
015E          OR R5,R3 & JP & GOTO CNT
015F  POS:    OR R5,R2 & CONT
0160  CNT:    SRS R6,R6,R10 & CONT
0161          SDRL R2,R2, & T & MIZ & CJP & GOTO END3
0162          SDRL R3,R3 & T & MAS & CJP & GOTO SUB
0163          ADD R0,R0,R5 & JP & GOTO CYCLE & SHOLD
0164  SUB:    SRS R0,R0,R5 & JP & GOTO CYCLE & SHOLD
0165  END3:   JP & GOTO SQRT

```

Figure 27.

The hardware additions finally decided on were chosen to increase the performance of BCD to binary conversion, binary to BCD conversion and BCD addition. The performance increases were approximately an order of magnitude in the first two cases, and a factor of 4 or 5 in the last case. A diagram of the additions (3¼ ICs) is given in Figure 28.

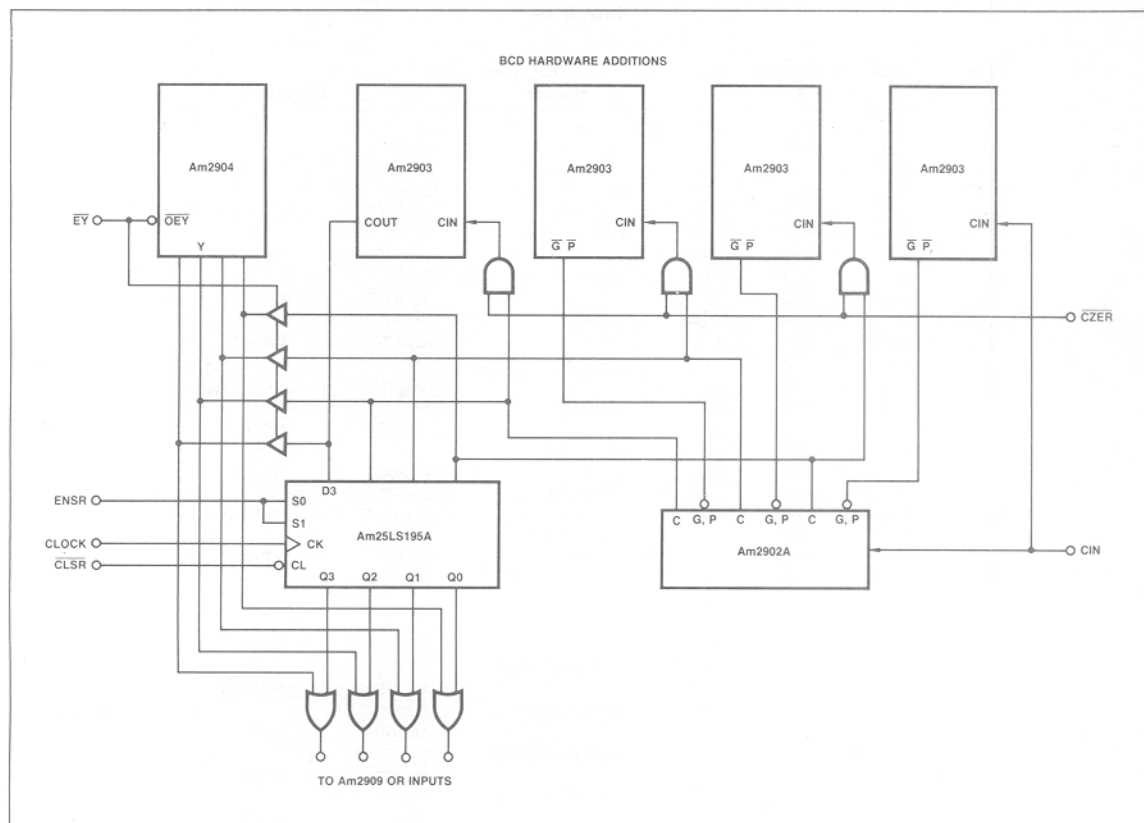The 74S08 AND gates normally pass the carry from the Am2902A to the Am2903s. When microbit CZER is low the Carries-in are forced to zero. This is used to "disconnect" the carry so that a test may be done on each slice simultaneously. For example if a test for 5 or greater is desired a HEX B is added and



the carry out of each slice will indicate the result of the test. This allows simultaneous tests on each individual slice and greatly increases thru-put. This addition increases the performance of BCD to binary conversion and binary to BCD conversion by at least an order of magnitude. The drawback to this addition is that the AND-gates introduce an extra gate delay in a critical path. The machine cycle time may be increased by about 8ns. The increase in BCD performance will more than offset this delay for BCD intensive systems.

Another hardware addition is the Am25LS241 three-state buffer. This buffer allows the Am2904 to be used to store the carry-out status bits via the bi-directional Y bus.

The 25LS195A is wired as a 4-bit register with clear and enable. This register is used to store the carry-out bits from a test cycle. The outputs of the 25LS195A are ORed with the output of the Am2904 Y-bus and connected to the Am2909 OR inputs in the CCU. This allows a multi-way branch on the OR of two test cycles, greatly increasing the performance of BCD addition.

BCD TO BINARY CONVERSION

The usual method of BCD to binary conversion is to divide the BCD number by 2. The 1-bit remainder will indicate if a 1 existed in the BCD number. The previous division result is divided by 2 again and the remainder will indicate if a 2 existed in the BCD number. In general the remainder from a division by 2^n will indicate if a 2^{n-1} existed in the BCD number.

These remainders can be used to construct the binary representation, $b_n 2^n + b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_1 2^1 + b_0 2^0$. The b_n bit is thus the remainder from division step $n + 1$. The binary representation may thus be created by shifting the remainders down until the m -bit BCD number has been divided by 2 m times.

To divide a BCD number by 2 a down shift is executed. The 4, 2 and 1-bit positions will contain the correct result, but the 8-bit position is incorrect. Its value has changed from 10 to 8 instead of from 10 to 5. This means the resulting BCD number will have a value 3 greater than it should for the division by 2 to be correct. A 3 must be subtracted from any digit in which a 1 entered its 8-bit.

A sample conversion is given in Table 10. The BCD number is gradually shifted down and corrected when necessary. The binary number is finally correct after 16 cycles.

A flow diagram for the algorithm is given in Figure 29. The BCD input, A, is shifted down to the binary output B, to start the loop. The constant 0888 is added to A with the carries-in forced to zero. The resulting carries-out will indicate if A contained a 1 in any of the 8-bit positions. These carries are saved in status register SR1. A multi-way branch is then executed to enter the adjust table. The digits are adjusted depending on the previous test. At the same time a shift can be executed to prepare for the next test instruction. A test for end of loop is also done in this cycle to provide an exit if 16 iterations of the loop are complete. Finally a shift up of B is needed to cancel the extra right shift when the loop is exited. The microcode for this algorithm is given in Figure 30.

TABLE 10.

Digit 3	Digit 2	Digit 1	Digit 0	BCD → Binary Result	Operation
0010	1001	0000	0100		
0001	0100	1000	0010	0	SHIFT
0001	0100	0101	0010		ADJUST DIGIT 1
0000	1010	0010	1001	00	SHIFT
0000	0111	0010	0110		ADJUST DIGITS 2, 0
0000	0011	1001	0011	000	SHIFT
0000	0011	0110	0011		ADJUST DIGIT 1
0000	0001	1011	0001	1000	SHIFT
0000	0001	1000	0001		ADJUST DIGIT 1
0000	0000	1100	0000	11000	SHIFT
0000	0000	1001	0000		ADJUST DIGIT 1
0000	0000	0100	1000	011000	SHIFT
0000	0000	0100	0101		ADJUST DIGIT 0
0000	0000	0010	0010	1011000	SHIFT
0000	0000	0010	0010		ADJUST NONE
0000	0000	0001	0001	01011000	SHIFT
0000	0000	0001	0001		ADJUST NONE
0000	0000	0000	1000	101011000	SHIFT
0000	0000	0000	0101		ADJUST DIGIT 0
0000	0000	0000	0010	1101011000	SHIFT
0000	0000	0000	0010		ADJUST NONE
0000	0000	0000	0001	01101011000	SHIFT
			0001		ADJUST NONE
			0000	101101011000	SHIFT
			0000		ADJUST NONE
			000	0101101011000	SHIFT
			000		ADJUST NONE
			00	00101101011000	SHIFT
			00		ADJUST NONE
			0	000101101011000	SHIFT
			0		ADJUST NONE
				0000101101011000	SHIFT
					ADJUST NONE

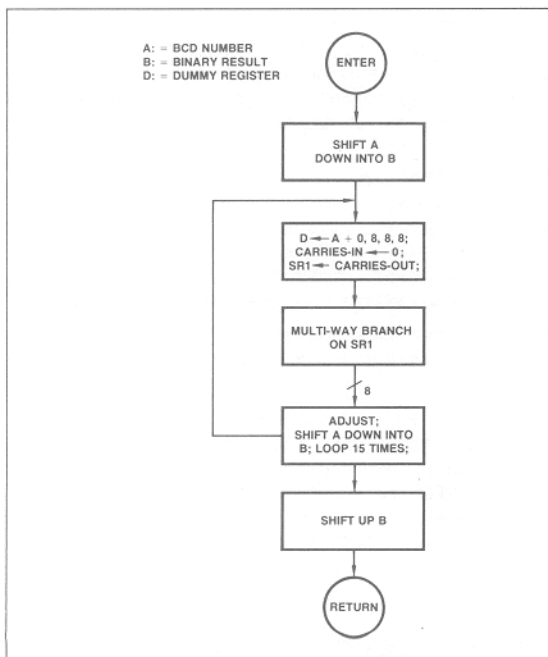


Figure 29. BCD to Binary Conversion (16 Bits to 14 Bits).

BINARY TO BCD CONVERSION

A method very similar to the one used for BCD to binary conversion may be used for binary to BCD conversion. The BCD number is created by shifting the binary number up, into a partial BCD result. The BCD number is adjusted to provide a multiplication by 2. The shift adjust process continues until the least significant binary bit is shifted into the BCD result.

The adjustment is needed when a 1 is shifted from the 8-bit position to the 1-bit position of the next digit. The value has increased from 8 to 10, instead of from 8 to 16. To correct this a 6 must be added to any digit that has a 1 shifted out of its 8-bit position. Alternately a 3 could be added before the shift to any digit that has a 1 in its 8-bit position.

Another correction is needed whenever an invalid BCD digit is encountered. If a number greater than 9 is detected in any digit a 10 must be subtracted from that digit and a 1 added to the next highest digit. The same correction can be accomplished if a 6 is added to the invalid digit after the shift. To correct before the shift a 3 is added to any digit which contains a 5, 6 or 7. These adjustments are summarized in Table 11. Both adjustments may be accomplished by adding a 3 to any digit which is greater than 4.

Table 12 shows an example conversion. The binary number is gradually shifted up and the BCD partial result adjusted. After 14 iterations the conversion is complete. A flow diagram for the algorithm is given in Figure 31.

A: = R0
B: = Q

```

1  ENR & COUNT LOOP & CONT
2  PAS R0, R0 LDRQ & SDDL & LDCT & CONST 15
LOOP: 3  ADD R1, R0, R0, DARB & ALUOFF & CONST 0888 & CZERO & ENSUR1 & CLSR2 & RPCT
4  ALUOFF & MULTI 8WAY
      ALIGN 8
5  ALUOFF & CJRP & CNTR & GOTO EXIT
6  SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
7  SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
8  SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
9  SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
10 SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
11 SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
12 SUB R0, R0, R0, LDRQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
EXIT: 13 PAS R0, R0, R0, LURQ & SDUL & RTN

```

Figure 30.

TABLE 11.

Present #	Adjustment Before Shift	Reason
0000	NONE	—
0001	NONE	—
0010	NONE	—
0011	NONE	—
0100	NONE	—
0101	+3	Illegal BCD
0110	+3	
0111	+3	
1000	+3	Shift Thru Correction
1001	+3	
1010	+3	
1011	+3	
1100	+3	
1101	+3	
1110	+3	
1111	+3	

Initially the 14-bit binary number is left justified by two shift up operations. To start the loop the binary input, B, is shifted up, into the partial BCD result, A. The constant BBBB is added to A, with the carries-in forced to zero. The resulting carries-out are stored in status register SR1. A multi-way branch is used to enter the adjust table. The digits are adjusted depending on the result of the previous test. In the same instruction a shift is executed to prepare for the next test cycle. Additionally an end of loop test is used to provide an exit if 16 iterations of the loop are complete. Before the exit a fix-up cycle is used to cancel the extra shift executed in the loop. The microcode for this algorithm is given in Figure 32.

BCD ADD

One method of performing a 4-digit BCD add is to do a 16-bit binary add, with the carries-in forced to zero, and adjust the resulting sum. The adjustments are necessary to change invalid BCD digits to valid BCD digits. When an invalid digit is modified a carry to the next highest digit is generated. This could cause a

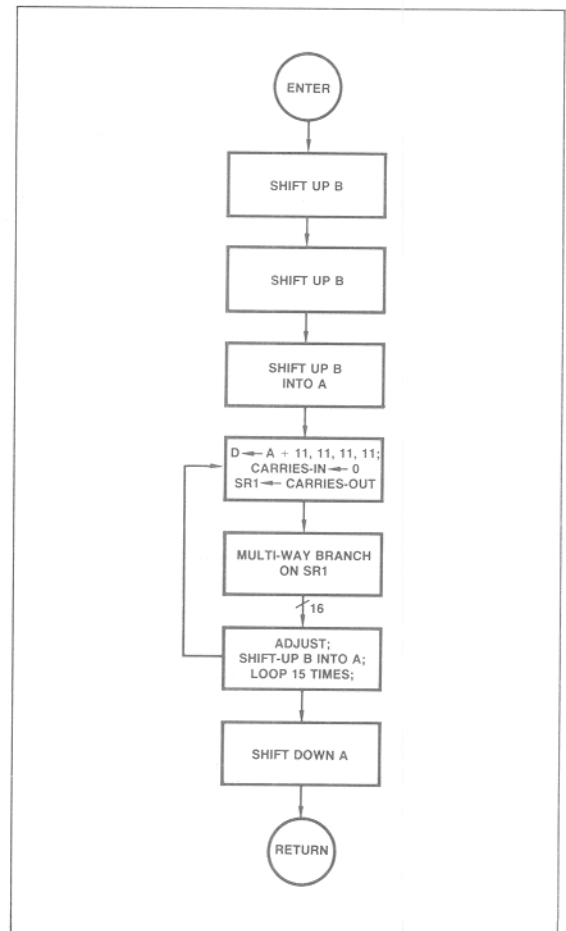


Figure 31. Binary to BCD Conversion (14 Bits to 16 Bits).

Q: = Binary Input

R0: = BCD Result

```

1  SURL R0, R0 & SUL & CONT
2  SURL R0, R0, & SUL & ENR & COUNT LOOP & CONT
3  PAS R0, R0, ,LURQ & SDUL & LDCT & COUNT 15
LOOP:
4  ADD R1,R0, R0, DARB & ALUOFF & CONST BBBB & CZERO & ENSR1 & CLSR2 & RPCT
5  ALUOFF & MULTI 16WAY
   ALIGN 16
6  ALUOFF & CJRP & GOTO EXIT
7  ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
8  ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
9  ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
10 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
11 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
12 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
13 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
14 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
15 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
16 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
17 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
18 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
19 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
20 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
21 ADD R1, R0, R0, LURQ,DARB & CONST 0003 & CJRP & CNTR & GOTO EXIT
EXIT:
22 SDRL R0, R0, & SDL & RTN

```

Figure 32. Binary to BCD Conversion Microcode (14 Bits to 16 Bits).

TABLE 12.

Result				Binary → BCD Conversion	Operation
Digit 3	Digit 2	Digit 1	Digit 0		
			0	00101101011000	SHIFT
			0	0101101011000	ADJUST NONE
			00	101101011000	SHIFT
			00		ADJUST NONE
			001	01101011000	SHIFT
			001		ADJUST NONE
			0010	1101011000	SHIFT
			0010		ADJUST NONE
		0	0101	101011000	SHIFT
		0	1000		ADJUST DIGIT 0
		01	0001	01011000	SHIFT
		01	0001		ADJUST NONE
		010	0010	1011000	SHIFT
		010	0010		ADJUST NONE
		0100	0101	011000	SHIFT
		0100	1000		ADJUST DIGIT 0
	0	1001	0000	11000	SHIFT
	0	1100	0000		ADJUST DIGIT 1
	01	1000	0001	1000	SHIFT
	01	1011	0001		ADJUST DIGIT 1
	011	0110	0011	000	SHIFT
	011	1001	0011		ADJUST DIGIT 1
	0111	0010	0110	00	SHIFT
	1010	0010	1001		ADJUST DIGIT 2
1	0100	0101	0010	0	SHIFT
1	0100	1000	0010		ADJUST DIGIT 1
10	1001	0000	0100		SHIFT
10	1001	0000	0100		ADJUST NONE
2	9	0	4		

previously valid digit to become invalid. The word must be checked and modified until all digits are valid (up to four modification cycles could be necessary).

Initially the two BCD numbers are added with the carries-in to each digit forced to zero. The carries out are saved. Next the hex number 6666 is added to the sum, with the carries-in forced to zero, and the resulting carries out are saved. This tests each digit for validity, a carry-out indicating an invalid BCD digit

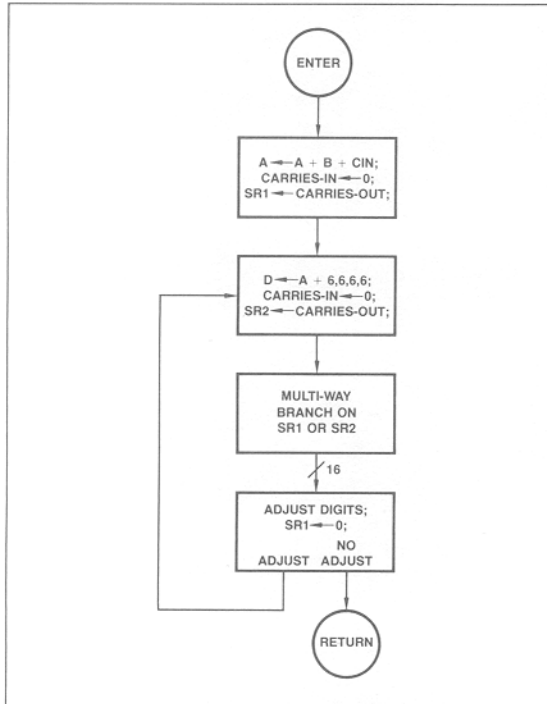


Figure 33. BCD Add.

(greater than 9). If a carry was generated in either cycle a 6 is added to the invalid digit, with carries-in forced to zero, to create the valid BCD digit. Additionally a 1 must be added to the next highest digit to provide the BCD carry-out. Each time a digit is adjusted the carry-out may invalidate the next highest digit. Thus adjustment cycles must be followed by validity tests until all digits are valid. A flow diagram for this algorithm is given in Figure 33. The microcode for this algorithm is given in Figure 34.

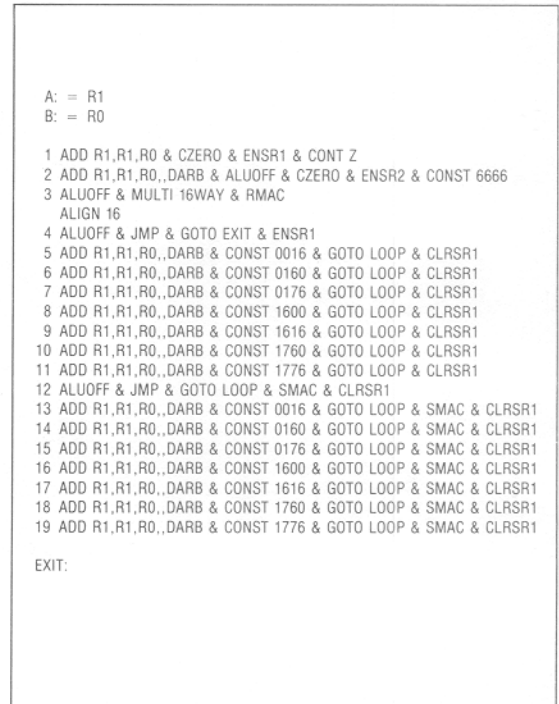


Figure 34. BCD Add Microcode.

SUMMARY

In this chapter, a detailed description of the Am2904 was presented, along with an example timing analysis. Several microcode algorithms were discussed to show how the Am2904 operates in a 2903 based CPU. As can be seen, the Am2904 provides a powerful, single-chip LSI solution to the shift multiplexer, status register, and carry multiplexer design portion of a CPU using either the Am2901B or the Am2903.

The Appendix includes a full microcode listing. The interested reader is encouraged to study these listings to gain a better understanding of the hardware organization (Appendix C). An additional microcode listing (Appendix B) gives the AMDASM™ definition file and source file for the microcode. The reader should study these listings while referring to the AMDASM Manual. (The Am2900 Family Data Book contains an AMDASM Reference Manual, document AM-PUB003, 4-78 FRODO.)

APPENDIX A

COMMENTS			CONSTANT																																			
	ADDRESS	LABEL																	89	88	87	86	85	84	83	82	81	80	79	78	77	76	75	74	73	72	71	70
SINGLE LENGTH NORMALIZE	0 1 3 C	AGAIN:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 3 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 3 E		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 3 F		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 0.		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 1		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 4 2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
DOUBLE LENGTH NORMALIZE	0 1 4 8	LOOP4:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 9		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 4 A		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 B		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 C		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 4 E	JUMP1:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 4 F		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
BINARY ROOTS																																						
	0 1 5 2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 3		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 4		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 5		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
	0 1 5 6		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
	0 1 5 7		1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1		
	0 1 5 8		0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
	0 1 5 9		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
	0 1 5 A		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 B	CYCLE:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 C		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 5 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 E		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 F	POS: CNT:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 6 0		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 6 1		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 6 2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 6 3		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
	0 1 6 4	SUB:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		

APPENDIX A

COMMENTS			CONSTANT																					
	ADDRESS	LABEL																						
			89	88	87	86	85	84	83	82	81	80	79	78	77	76	75	74	73	72	71	70	69	
SINGLE LENGTH NORMALIZE	0 1 3 C	AGAIN:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 3 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 3 E		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 3 F		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 0		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 1		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 4 2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
DOUBLE LENGTH NORMALIZE	0 1 4 8	LOOP4:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 9		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 A		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 B		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 C		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 4 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 4 E	JUMP1:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
0 1 4 F	X		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
BINARY ROOTS																								
	0 1 5 2	CYCLE:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 3		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 4		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 5		0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	X	X	X	X	
	0 1 5 6		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	X	X	X	X	
	0 1 5 7		1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	X	X	X	X	
	0 1 5 8		0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	X	X	X	X	
	0 1 5 9		0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	X	X	X	X	
	0 1 5 A		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 B		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 C		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 D		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 E		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 5 F		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	
	0 1 6 0		CNT:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 6 1			X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 6 2		SUB:	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	0 1 6 3			X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
0 1 6 4	X	X		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		

				CCU CONTROL FIELD												DEVICE ENABLE				SHARED CONTROL FIELD																		
CT.	SRC.			MULTI- WAY				IR EN	POLARITY	TEST SELECT				29811 NEXT ADDRESS				SHIFT EN	STATUS EN		IEN	FIELD SELECT	INPUT/OUTPUT BRANCH COUNTER															
																			STATUS EN	IEN																		
34 33	32	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0					
1 0	0 0	0 0	0 0	0 0	0 0	0 0	0 0	1 1	0 0	0 1	0 1	0 1	0 1	0 1	0 0	0 0	0 0	X 0	0 0	0 0	1 X	0 X	0 X	0 X	0 X	0 X	0 X	0 X	0 X	0 X	1 X	1 X	1 X	0 X				
1 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 1 1	0 1 1	0 1 1	0 1 1	0 1 1	0 0 0	0 0 0	0 0 0	X 0 0	0 0 0	0 0 0	1 X X	0 X X	0 X X	0 X X	0 X X	0 X X	0 X X	0 X X	0 X X	0 X X	1 X X	1 X X	0 X X	1 X X				
0 0 0	X X X	X X X	X X X	0 0 0	0 0 0	0 0 0	0 0 0	1 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 X X	0 0 0	0 0 0	1 X X	0 0 0	1 X X	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0				
0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	0 0 0	1 1 X	0 0 0	0 0 0	0 0 0																											

Am2904 CONTROL FIELD																				Am2903 CONTROL FIELD																			
ENSR		CZER	CONST	OEY	OECT	CEM	CARRY	SHIFT OP				INSTRUCTION OP							OEY	B ADDRESS DEST.				B ADDRESS SRC.				A ADDRESS SRC.				DEST.				FUN			
2	71	70	69	68	67	66	65	64	63	62	61	60	59	58	57	56	55	54	53	52	51	50	49	48	47	46	45	44	43	42	41	40	39	38	37	36	35	34	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	1	1	1	1	0	1	1	0	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0		
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	1	1	1	1	0	1	1	0	0	1		
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	0	0	1	0	0	0		
X	X	X	X	X	X	X	1	1	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	0	0	1	1	0	0		
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	1	0	1	0	X	X	X	X	X	X	X	X	1	1	1	1	1	0		
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	1	1	X	X	X	X	0	1	1	1	1	1	1	1	1	0		
X	X	X	X	X	X	X	1	0	X	X	X	X	X	X	X	X	X	X	0	0	0	1	0	0	0	1	0	X	X	X	X	0	1	0	1	0	0		
X	X	X	X	X	X	X	0	0	X	X	X	X	0	1	0	1	1	0	0	0	0	1	0	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	1	1	X	X	X	X	X	X	X	X	1	0	0	1	0	1		
X	X	X	X	X	X	X	0	0	0	0	1	0	X	X	X	X	X	X	0	0	0	1	0	0	0	1	0	X	X	X	X	1	0	0	1	0	1		
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
X	X	X	X	X	X	X	0	0	0	0	1	0	X	X	X	X	X	X	0	0	0	1	1	X	X	X	X	X	X	X	X	1	0	0	1	0	1		
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
X	X	X	X	X	X	X	0	0	0	0	1	0	X	X	X	X	X	X	0	0	0	1	1	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	1	1	1	1	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	0	0	0	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	1	1	1	1	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	1	1	1	1	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	0	0	0	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X		
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	0	0	0	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	1	1	1	1	X	X	X	X	0	0	0	1	1	1	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0	0	1	1	0	X	X	X	X	X	X	0	0	0	0	1	X	X	X	X	0	0	0	1	0	0	1	1	1	0	1	
X	X	X	X	X	X	X	0	0</																															

CONSTANT

[illegible]

CONSTANT

	ADDRESS	LABEL																	ENR	
			89	88	87	86	85	84	83	82	81	80	79	78	77	76	75	74	73	72
BCD TO BINARY CONVERSION ROUTINE	0	ENTER	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	0
	1		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
	2		0	0	0	0	1	0	0	0	1	0	0	0	1	0	0	0	0	1
	3	LOOP	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
BRANCH TABLE	8		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
	9		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1
	10		0	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	1
	11		0	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	1	1
	12		0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	1
	13		0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	1	1	1
	14		0	0	0	0	0	0	1	1	0	0	1	1	0	0	0	0	0	1
	15		0	0	0	0	0	0	1	1	0	0	1	1	0	0	1	1	1	1
16	EXIT	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	
BINARY TO BCD CONVERSION ROUTINE	0	ENTER	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
	1		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	0
	2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
	3	LOOP	1	0	1	1	1	0	1	1	1	0	1	1	1	0	1	1	1	1
4		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
BRANCH TABLE	16		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
	17		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1
	18		0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	1
	19		0	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	1	1
	20		0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	1
	21		0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	1	1	1
	22		0	0	0	0	0	0	1	1	0	0	1	1	0	0	0	0	0	1
	23		0	0	0	0	0	0	1	1	0	0	1	1	0	0	1	1	1	1
	24		0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1
	25		0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	1	1	1
	26		0	0	1	1	0	0	0	0	0	0	1	1	0	0	0	0	0	1
	27		0	0	1	1	0	0	0	0	0	0	1	1	0	0	1	1	1	1
	28		0	0	1	1	0	0	1	1	0	0	0	0	0	0	0	0	0	1
	29		0	0	1	1	0	0	1	1	0	0	0	0	0	0	1	1	1	1
	30		0	0	1	1	0	0	1	1	0	0	1	1	0	0	0	0	0	1
	31		0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1	1
32	EXIT	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	

Am2904 CONTROL FIELD																		Am2903 CONTROL FIELD																									
ENSR		CLRSR		CONST		OEY		OECT		CEM		CARRY		SHIFT OP				INSTRUCTION OP						OEY		B ADDRESS DEST.				B ADDRESS SRC.				A ADDRESS SRC.				DEST.				FUN	
71	70	69	68	67	66	65	64	63	62	61	60	59	58	57	56	55	54	53	52	51	50	49	48	47	46	45	44	43	42	41	40	39	38	37	36	35							
0	1	1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X							
0	1	1	0	1	1	X	X	0	1	1	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1								
0	0	0	1	1	0	0	0	X	X	X	X	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0								
0	1	1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X								
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0								
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	0	0	1	1	0	1	0	1	1	1	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0							
0	1	1	0	1	1	X	X	1	1	1	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	1							
0	1	1	0	1	1	0	0	0	0	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	1	0	1							
0	1	1	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	1							
0	0	0	1	1	0	0	0	X	X	X	X	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0							
0	1	1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	0	0	1	1	0	0	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	0							
0	1	1	0	1	1	X	X	0	1	0	0	X	X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1							

				CCU CONTROL FIELD												DEVICE ENABLE			SHARED CONTROL FIELD																					
CT.	SRC.			MULTI- WAY				IR EN	POLARITY	TEST SELECT				29811 NEXT ADDRESS				SHIFT EN	STATUS EN		IEN	FIELD SELECT	INPUT/OUTPUT BRANCH COUNTER																	
14	33	32	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0						
X	X	X	X	X	0	0	0	0	1	X	X	X	X	X	1	1	1	0	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	1	1					
1	0	0	0	0	0	0	0	0	1	X	X	X	X	X	1	1	0	0	0	1	0	1	0	0	0	0	0	0	0	0	1	1	1	1						
1	1	1	0	0	0	0	0	0	1	X	X	X	X	X	1	0	0	1	1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X						
X	X	X	X	X	0	1	1	1	1	X	X	X	X	X	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0						
0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X						
1	0	0	0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	0	0	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X						
1	0	0	0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	0	0	1	1	1	0	0	0	0	0	0	0	0	0	0	1	1						
1	0	0	0	0	0	0	0	0	1	X	X	X	X	X	1	1	0	0	0	1	0	1	0	0	0	0	0	0	0	1	1	1	1	1						
1	1	1	0	0	0	0	0	0	1	X	X	X	X	X	1	0	0	1	1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X						
X	X	X	X	X	1	1	1	1	1	X	X	X	X	X	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	1	1	0	0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	0	0	0	1	0	0	0	0	0						
1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X						

APPENDIX A

COMMENTS			CONSTANT																								ENR	CZERO	ENSR	CLRSR	CONST		
	ADDRESS	LABEL	89	88	87	86	85	84	83	82	81	80	79	78	77	76	75	74	73	72	71	70	69	68	67	66	65	64	63	62	61	60	
BCD ADD ROUTINE	0	ENTER	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	0	0	1	1										
	1		0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	0	1	1	0										
	2		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	1	0	1	1									
ADJUST TABLE	16	TAB	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0										
	17		0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	1	0	0	0										
	18		0	0	0	0	0	0	0	0	1	0	1	1	0	0	0	0	0	1	1	0	0	0									
	19		0	0	0	0	0	0	0	0	1	0	1	1	1	0	1	1	0	1	1	0	0	0									
	20		0	0	0	1	0	1	1	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0									
	21		0	0	0	1	0	1	1	0	0	0	0	0	1	0	1	1	0	1	1	0	0	0									
	22		0	0	0	1	0	1	1	1	0	1	1	0	0	0	0	0	0	1	1	0	0	0									
	23		0	0	0	1	0	1	1	1	0	1	1	1	0	1	1	0	1	1	0	0	0	0									
	24		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0									
	25		0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	0	1	1	0	0									
	26		0	0	0	0	0	0	0	0	1	0	1	1	0	0	0	0	0	0	1	1	0	0	0								
	27		0	0	0	0	0	0	0	0	1	0	1	1	1	0	1	1	0	1	1	0	0	0									
	28		0	0	0	1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0								
	29		0	0	0	1	0	1	1	0	0	0	0	0	1	0	1	1	0	1	1	0	0	0									
	30		0	0	0	1	0	1	1	1	0	1	1	1	0	0	0	0	0	0	1	1	0	0	0								
	31		0	0	0	1	0	1	1	1	1	0	1	1	1	0	1	1	0	1	1	0	0	0									
		EXIT																															

Am2904 CONTROL FIELD

Am2903 CONTROL FIELD

OEY	OECT	CEM	CARRY	SHIFT OP				INSTRUCTION OP							OEY	B ADDRESS DEST.				B ADDRESS SRC.				A ADDRESS SRC.				DEST.					FUNCT.				SR	
				I ₉	I ₈	I ₇	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀	I ₈		I ₇	I ₆	I ₅	I ₈	I ₇	I ₆	I ₅	I ₈	I ₇	I ₆	I ₅	I ₈	I ₇	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀			
68	67	66	65	64	63	62	61	60	59	58	57	56	55	54	53	52	51	50	49	48	47	46	45	44	43	42	41	40	39	38	37	36	35	34	33	32	31	
1	1	0	1	1	X	X	X	X	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	0	0
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X	1	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	1	0
0	1	0	X	X	X	X	X	X	0	0	0	0	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	1	0
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	1	0
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	1	0
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X	0	0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1	1	0	0	1	1	1	0

SHARED CONTROL FIELD

C.	MULTI-WAY					IR EN	POLARITY	TEST SELECT	29811 NEXT ADDRESS					SHIFT EN	STATUS EN	IEN	FIELD SELECT	INPUT/OUTPUT BRANCH COUNTER															
	29	28	27	26	25				24	23	22	21	20					19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	0	1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X	
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	0	1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X		
X	1	1	1	1	1	1	X	X	X	X	X	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0		
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	1	1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0		
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1		
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1		
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1		
0	0	0	0	0	0	1	X	X	X	X	X	1	1	1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1		
0	0	0	0	0	0																												

APPENDIX B

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1 CPUII DEFINITIONS

```
;ADVANCE MICRO DEVICES  
; AM2903 AND AM2904 DEFINITION FILE FOR CPUII  
;  
;REV. OCTOBER 17, 1978
```

WORD 90

;EQUATES

```
MEM:    EQU H#F  
SPF:    EQU H#0  
OFF:    EQU B#1
```

;2903 DESTINATION MODIFIERS

```
ADR:    EQU H#0  
LDR:    EQU H#1  
ADRQ:   EQU H#2  
LDRQ:   EQU H#3  
RPT:    EQU H#4  
LDQP:   EQU H#5  
QPT:    EQU H#6  
RQPT:   EQU H#7  
AUR:    EQU H#8  
LUR:    EQU H#9  
AURQ:   EQU H#A  
LURQ:   EQU H#B  
YBUS:   EQU H#C  
LUQ:    EQU H#D  
SINX:   EQU H#E
```

;CONSTANTS

```
R0:     EQU H#0  
R1:     EQU H#1  
R2:     EQU H#2  
R3:     EQU H#3  
R4:     EQU H#4  
R5:     EQU H#5  
R6:     EQU H#6  
R7:     EQU H#7  
R8:     EQU H#8  
R9:     EQU H#9  
R10:    EQU H#A  
R11:    EQU H#B  
R12:    EQU H#C  
R13:    EQU H#D  
R14:    EQU H#E  
R15:    EQU H#F
```

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CPU11 DEFINITIONS

;2903 SOURCE MODIFIERS

RADB: EQU 3B#001
RAQ: EQU 3B#010
DARB: EQU 3B#100
DADE: EQU 3B#101
DAQ: EQU 3B#110

;I/O

IOIN: EQU 12H#01
BIN: EQU 12H#10
BOUT: EQU 12H#08
LMAR: EQU 12H#10
YREG: EQU 12H#02
AOUT: EQU 12H#40
IOUT: EQU 12H#04

;CARRY SELECT

ONE: EQU 2B#01
CZ: EQU 2B#10

;SUB DEFINITIONS

SUB0: SUB 36X,1B#0,4VX,4VX,4VX
SUB1: SUB 36X,1B#0,4VX,4VX,4VX,4VH#F
SUB2: SUB 36X,1B#0,4VX,4VX,4Y,4VH#F
SUB3: SUB 3VB#000,16X,1B#0,13X
SUB4: SUB 36X,1B#0,12X
SUB5: SUB 44X,1B#0,15X
SUB6: SUB 44X,1B#0,15X
SUB7: SUB 26X
SUB8: SUB 36X,1B#0,4VX,8X,4VH#F
SUB9: SUB 36X,1B#0,4VX,4X,4VX,4VH#F
SUB10: SUB 36X,1B#0,4VX,4VX,4X
SUB11: SUB 24X,2VF#00,34X,4B#0000,1B#1,5X
SUB12: SUB 77X,1B#1,12VXH#0%
SUB13: SUB SPF,3VB#000,16X,1B#0,13X
SUB14: SUB 24X,2VF#00,34X,4B#0000,2B#10
SUB15: SUB 23X,1B#0,6X
SUB16: SUB SPF,3B#000,16X,1VB#0,13X
SUB17: SUB 54X
SUB18: SUB 22X,1B#0,7X
SUB19: SUB 16X,1B#0,13X
SUB20: SUB 1X,1VB#0,14X
SUB21: SUB 30X,H#B,20X

;CCU CONTRCL

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CPU11 DEFINITIONS

```
ACK:    DEF 66X,H#9,20X
OBF:    DEF 66X,H#A,20X
CNT:    DEF 66X,H#F,20X
GRD:    DEF 66X,H#0,20X
JZ:     DEF SUB11,H#0,SUB20
CJS:    DEF SUB11,H#1,SUB20
JMAP:   DEF SUB11,H#2,SUB20
CJP:    DEF SUB11,H#3,SUB20
PUSH:   DEF SUB11,H#4,SUB20
JSRP:   DEF SUB11,H#5,SUB20
CJV:    DEF SUB11,H#6,SUB20
JRP:    DEF SUB11,H#7,SUB20
RFCT:   DEF SUB11,H#8,SUB20
RPCT:   DEF SUB11,H#9,SUB20
CRTN:   DEF SUB11,H#A,SUB20
CJPP:   DEF SUB11,H#B,SUB20
LDCT:   DEF SUB11,H#C,SUB20
LOCP:   DEF SUB11,H#D,SUB20
CONT:   DEF SUB11,H#E,SUB20
JP:     DEF SUB11,H#F,SUB20
JSR:    DEF SUB14,H#01,SUB20
RTN:    DEF SUB14,H#0A,SUB20
```

;SHARED CONTROL FIELD

```
GOTC:   DEF SUB12
COUNT: DEF SUB12
PUT:    DEF 77X,1B#0,12VXH#0%
```

;POLARITY CONTROL

```
T:      DEF 65X,1B#1,24X
F:      DEF 65X,1B#0,24X
```

;2903 CONTROL/FUNCTIONS

```
IN:     DEF 36X,1B#1,H#F,8X,H#F,H#0,19X,1B#0,13X
OUT:    DEF 36X,1B#0,8X,H#F,H#C,H#6,SUB3
YOFF:   DEF 36X,1B#1,53X
HIGH:   DEF SUB8,H#0,3B#010,SUB19
SRS:    DEF SUB1,H#1,SUB3
SSR:    DEF SUB1,H#2,SUB3
ADD:    DEF SUB1,H#3,SUB3
PAS:    DEF SUB2,H#4,SUB3
COMS:   DEF SUB2,H#5,SUB3
PAR:    DEF SUB9,H#6,SUB3
COMR:   DEF SUB9,H#7,SUB3
LOW:    DEF SUB8,H#8,3X,SUB19
CRAS:   DEF SUB1,H#9,SUB3
XNRS:   DEF SUB1,H#A,SUB3
XOR:    DEF SUB1,H#B,SUB3
AND:    DEF SUB1,H#C,SUB3
NOR:    DEF SUB1,H#D,SUB3
NAND:   DEF SUB1,H#E,SUB3
OR:     DEF SUB1,H#F,SUB3
```

;2903 SPECIAL FUNCTIONS

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CPUII DEFINITIONS

```

UMUL:  DEF SUB0,H#0,SUB16
TCM:   DEF SUB0,H#2,SUB16
SMTC:  DEF SUB10,H#5,SUB16
TCMC:  DEF SUB0,H#6,SUB16
SLN:   DEF SUB10,H#8,SUB16
DLN:   DEF SUB0,H#A,SUB16
TDIV:  DEF SUB0,H#C,SUB16
TDC:   DEF SUB0,H#E,SUB16
INC:   DEF SUB10,H#4,SUB16
SDQP:  DEF SUB4,H#5,4X,SUB3
SUQP:  DEF SUB4,H#D,4X,SUB3
LQPT:  DEF 36X,1B#0,8X,4VX,H#6,H#6,SUB3
RMOV:  DEF SUB2,H#4,SUB3
QMOV:  DEF 36X,1B#0,4VX,8X,MEM,H#4,3B#010,SUB19
SDRL:  DEF SUB10,H#1,H#4,SUB3
SURL:  DEF SUB10,H#9,H#4,SUB3

```

;2904 SHIFT CONTROL

```

SDDH:  DEF SUB7,H#3,SUB6
SDUH:  DEF SUB7,H#7,SUB5
SDDL:  DEF SUB7,H#6,SUB6
SDUL:  DEF SUB7,H#6,SUB5
RDD:   DEF SUB7,H#F,SUB6
RDU:   DEF SUB7,H#F,SUB5
SSXO:  DEF SUB7,H#E,SUB6
RSD:   DEF SUB7,H#A,SUB6
RSU:   DEF SUB7,H#A,SUB5
SUL:   DEF SUB7,H#2,SUB5
SUH:   DEF SUB7,H#3,SUB5
SDL:   DEF SUB7,H#0,SUB6
SDH:   DEF SUB7,H#1,SUB6
SDMS:  DEF SUB7,H#5,SUB6
SMS:   DEF SUB7,H#2,SUB6
SDDC:  DEF SUB7,H#7,SUB6
SDUC:  DEF SUB7,H#4,SUB5

```

;2904 MICRO INSTRUCTION CODES

```

RSTI:  DEF 30X,6B#0000011,SUB17
SWAP:  DEF 3 X,6B#0000010,SUB17
SHLD:  EQU 1B#1

```

;2904 MACHINE INSTRUCTION CODES

```

LMA:   DEF SUB15,6B#0000000,SUB17
RSTA:  DEF SUB15,6B#0000011,SUB17
SHOLD: DEF 23X,1B#0,66X

```

;2904 MICRO STATUS SELECT

AMDOS/29 AMDASM MICRO ASSEMBLER, V1.1
CPU11 DEFINITICNS

MIZ: DEF SUB18,6B#010100,SUB21
MIO: DEF SUB18,6B#010110,SUB21
MIC: DEF SUB18,6B#011010,SUB21
MIS: DEF SUB18,6B#011110,SUB21

;2904 MACHINE STATUS SELECT

MAZ: DEF SUB18,6B#100100,SUB21
MAO: DEF SUB18,6B#100110,SUB21
MAC: DEF SUB18,6B#101010,SUB21
MAS: DEF SUB18,6B#101110,SUB21

;DEVICE DISABLE

ALUCFF: DEF 7 X,1B#1,13X
ALLOFF: DEF 7 X,3B#111,13X

;LOAD CONSTANT

CONST: DEF 16 VXH#0%,4X,1B#0,69X

;BCD STATUS REGISTER CONTROL

ENR: DEF 16X,1B#0,73X
CLSR2: DEF 17X,1B#0,72X
ENSR1: DEF 18X,1B#1,71X
CZERO: DEF 19X,1B#0,70X

END

TOTAL PHASE 1 ERRORS = 0

;ADVANCE MICRO DEVICES
; AM2903 AND AM2904 CPUII SOURCE FILE

```

0100      ORG H#100
0100 INP:  ALUOFF & T & OBF & CJP & GOTO INP
0101      ALUOFF & PUSH
0102      IN & T & OBF & LOOP & PUT ICIN
0103      ALUOFF & RTN

0104 OUTP:  OUT & CONT & PUT YREG
0105      ALUOFF & PUSH
0106      ALUOFF & F & ACK & LOOP & PUT IOOUT
0107      ALUOFF & PUSH
0108      ALUOFF & T & ACK & LOOP
0109      ALUOFF & RTN

010A USM:  LOW R1 & JSR & GOTO INP
010B      PAR R0,R15 & JSR & GOTO INP
010C      LQPT R15 & F & GRD & PUSH & COUNT 00E
010D      UMUL R1,R1,R0 & F & CNT & SDDL & RFCT
010E      PAR R15,R1 & JSR & GOTO OUTP
010F      QMOV R15 & JSR & GOTO OUTP
0110      JP & GOTO USM

0111 SM:   LOW R1 & JSR & GOTO INP
0112      PAR R0,R15 & JSR & GOTO INP
0113      LQPT R15 & F & GRD & PUSH & COUNT 00D
0114      TCM R1,R1,R0 & F & CNT & SDDL & RFCT
0115      TCMC R1,R1,R0 & SDDL & CNT CZ
0116      PAR R15,R1 & JSR & GOTO OUTP
0117      QMOV R15 & JSR & GOTO OUTP
0118      ALUOFF & JP & GOTO SM

0119 DIV:  LOW R10 & JSR & GOTO INP
011A      PAR R7,R15 & JSR & GOTO INP
011B      PAR R1,R15 & JSR & GOTO INP
011C      PAR R4,R15 & CONT
011D LOOP1: PAR R3,R7 & CONT
011E      PAR R2,R1 & T & MIZ & CJP & GOTO ABORT
011F      SMTC R2,R2 & CONT CZ
0120      SMTC R3,R3 & T & MIO & CJP CZ & GOTO SCALE1
0121      ALUOFF & T & MIO & CJP & GOTO SKIP6
0122      SURL R3,R3 & SUL & CONT
0123      SURL R2,R2 & SUL & CONT
0124      ALUOFF & JP & GOTO LOOP2
0125 SCALE1: LQPT R4 & JSR & GOTO SDIVD
0126      ALUOFF & JP LOOP1
0127 LOOP2:  SSR R15,R3,R2,YBUS & CONT ONE
0128 SKIP6:  LQPT R4 & F & MIC & CJP & GOTO SKIP3
0129      ALUOFF & JSR & GOTO SDIVD
012A      SDRL R2,R2 & SDL & CONT
012B      ALUOFF & JP & GOTO LOOP2
012C SKIP3:  ALUOFF & F & GRD & LDCT & COUNT 00C
012D      DLN R1,R1,R7 & T & GRD & RDU & PUSH
012E      TDIV R1,R1,R7 & F & CNT & RDU & RFCT CZ
012F      TDC R1,R1,R7 & SUH & CONT CZ
0130      QMOV R15 & JSR & GOTO OUTP
    
```

```

0131      PAR R15,R1 & JSR & GOTO OUTP
0132      ALUOFF & JP & GOTO DIV
0133 SDIVD: PAR R1,R1 & CONT
0134      ALUOFF & T & MIS & CJP & GOTO NEG
0135      PAR R1,R1,ADRQ & SDDL & CONT
0136      ALUOFF & JP & GOTO RET
0137 NEG:  PAR R1,R1,ADRQ & SDDL & CONT
0138 RET:  QMOV R4 & CONT
0139      PAR R10,R10 & RTN ONE

013A SLNORM: JSR & GOTO INP
013B      LQPT R15 & CONT
013C      SLN R2,R2,OFF & CONT & SHOLD
013D      MAZ & T & CJP & GOTO ABORT
013E      MAC & T & LOW R0 & CJP & GOTO END
013F      SLN R2,R2 & MAC & T & CJP ONE & GOTO END & SUL
0140 AGAIN: SIN R2,R2 & MIO & F & CJP ONE & GOTO AGAIN & SUL
0141      SDQP & SMS & CONT
0142      SRS R2,R2,R0 & CONT
0143      QMOV R15 & JSR & GOTO OUTP
0144      PAR R15,R2 & JSR & GOTO OUTP
0145 END:  JP & GOTO SLNORM

0146 DLNORM: JSR & GOTO INP
0147      LQPT R15 & JSR & GOTO INP
0148      DLN R15,R15,R15,OFF & CONT & SHOLD
0149      MAZ & T & CJP & GOTO ABORT
014A      LOW R2 & MAC & T & CJP & GOTO END2
014B      DLN R15,R15,R15 & SDUL & MAO & T & CJP & GOTO JUMP1
014C LOOP4: DLN R15,R15,R15 & SDUL & MIO & T & CJP & GOTO JUMP1
014D      PAR R2,R2 & JP ONE & GOTO LOOP4
014E JUMP1: PAR R2,R2 & CONT ONE
014F      SDRQ R15,R15 & SDMS & JSR & GOTO OUTP
0150      QMOV R15 & JSR & GOTO OUTP
0151 END2:  JP & GOTO DLNORM

0152 SQRT:  LOW R10 & CONT
0153      LOW R0 & JSR & GOTO INP
0154      PAR R1,R15 & CONT
0155      PAR R2,R0,,DARB & CONST 0005 & CONT
0156      PAR R3,R0,,DARB & CONST 0003 & CONT
0157      PAR R4,R0,,DARB & CONST F#BEFF & CONT
0158      PAR R5,R0,,DARB & CONST 4000 & CONT
0159      PAR R6,R0,,DARB & CONST 0008 & CONT
015A      SRS R0,R1,R5 & CONT & SHOLD
015B CYCLE: AND R5,R5,R4 & CONT
015C      SDR1 R4,R4 & MAS & CJP & GOTO END3
015D      SURI R0,R0 & T & MAS & CJP & GOTO POS
015E      OR R5,R3 & JP & GOTO CNT
015F POS:  CR R5,R2 & CONT
0160 CNT:  SRS R6,R6,R10 & CONT
0161      SDR1 R2,R2 & T & MIZ & CJP ,SHLD & GOTO END3
0162      SDR1 R3,R3 & T & MAS & CJP & GOTO SUB
0163      ADD R0,R0,R5 & JP & GOTO CYCLE & SHOLD
0164 SUB:  SRS R0,R0,R5 & JP & GOTO CYCLE & SHOLD
0165 END3:  JP & GOTO SQRT

```

AMDCS/29 AMDASM MICRO ASSEMBLER, V1.1

0166 ABORT: ALUOFF & JP & GOTO ABORT
0167 JP & GOTO DIV

END

```

0100 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX
    1110100011X01100 0100000000
0101 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX
    1XXXXX0100X01XXX XXXXXXXXXXXX
0102 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX111111X1XXXXX X11110000XXX0000
    1110101101X00000 0000000001
0103 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX
    10000001010X01XXX XXXXXXXXXXXX
0104 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX0XXXXXXX111 1110001100000000
    1XXXXX1110X00000 0000000010
0105 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX
    1XXXXX0100X01XXX XXXXXXXXXXXX
0106 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXX XXXXXX XXXXXXXXXXXXXXX0000
    1010011101X01000 0000000100
0107 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
    1XXXXX0100X01XXX XXXXXXXXXXXX
0108 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX000
    1110011101X01XXX XXXXXXXXXXXX
0109 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXX XXXXXX XXXXXXXXXXXXXXX0000
    10000001010X01XXX XXXXXXXXXXXX
010A XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00001XXXXXXX X11111000XXX0000
    1000000001X00100 0100000000
010B XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00000XXXX111 1111011000000000
    1000000001X00100 0100000000
010C XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX0XXXXXXX111 1011001100000000
    1000000100X0100 000000110
010D XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX000010001000 0000000000000000
    1011111000000XXX XXXXXXXXXXXX
010E XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXX000 1111101100000000
    1000000001X00100 0100000100
010F XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXXXXX X111101000100000
    1000000001X00100 0100000100
0110 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
    1XXXXX1111X0X100 0100001010
0111 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00001XXXXXXX X11111000XXX0000
    1000000001X00100 0100000000
0112 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00000XXXX111 1111101100000000
    1000000001X00100 0100000000
0113 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX0XXXXXXX111 1011001100000000
    1000000100X00100 0000001101
0114 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX000010001000 0001000000000000
    1011111000000XXX XXXXXXXXXXXX
0115 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX000010001000 0011000000000000
    1XXXXX1110000XXX XXXXXXXXXXXX
0116 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXX000 1111101100000000
    1000000001X00100 0100000100
0117 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXXXXX X111101000100000
    1000000001X00100 0100000100
0118 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
    1XXXXX1111X01100 0100010001
0119 XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01010XXXXXXX X11111000XXX0000
    1000000001X00100 0100000000
011A XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00111XXXX111 1111101100000000
    1000000001X00100 0100000000
011B XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00001XXXX111 1111101100000000
    1000000001X00100 0100000000
011C XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX02100XXXX111 1111101100000000
    1XXXXX1110X0XXX XXXXXXXXXXXX

```

```

011D XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00011XXXX011 1111101100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
011E XXXXXXXXXXXXXXXX XXXXX0X00XXXXX01 010000010XXXX000 1111101100000000
1110110011X00100 0101100110
011F XXXXXXXXXXXXXXXX XXXXXXXXXXX10XXXXXX XXXX000100010XXX X0101000000000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0120 XXXXXXXXXXXXXXXX XXXXX0X10XXXXX01 0110000110011XXX X0101000000000000
1110110011X00100 0100100101
0121 XXXXXXXXXXXXXXXX XXXXX0X00XXXXX01 0110XXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1110110011X01100 0100101000
0122 XXXXXXXXXXXXXXXX XXXXXXXXXXX000010XX XXXX000110011XXX X1001010000000000
1XXXXX1110000XXX XXXXXXXXXXXX
0123 XXXXXXXXXXXXXXXX XXXXXXXXXXX000010XX XXXX000100010XXX X1001010000000000
1XXXXX1110000XXX XXXXXXXXXXXX
0124 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01100 0100100111
0125 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXX0XXXXXXXXXX010 0011001100000000
1000000001X00100 0100110011
0126 XXXXXXXXXXXXXXXX XXXXXXXXXXX01XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01XXX XXXXXXXXXXXX
0127 XXXXXXXXXXXXXXXX XXXXXXXXXXX01XXXXXX XXXX011110011001 0110000100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0128 XXXXXXXXXXXXXXXX XXXXX0X00XXXXX01 10100XXXXXXX010 0011001100000000
1010110011X00100 0100101100
0129 XXXXXXXXXXXXXXXX XXXXXXXXXXX0XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
10000000001X01100 0100110011
012A XXXXXXXXXXXXXXXX XXXXXXXXXXX000000XX XXXX000100010XXX X0001010000000000
1XXXXX1110000XXX XXXXXXXXXXXX
012B XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01100 0100100111
012C XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1000001100X01100 00000001100
012D XXXXXXXXXXXXXXXX XXXXXXXXXXX001111XX XXXX000010001211 1101000000000000
1100000100000XXX XXXXXXXXXXXX
012E XXXXXXXXXXXXXXXX XXXXX0X101111XX XXXX000010001011 1110000000000000
1011111000000XXX XXXXXXXXXXXX
012F XXXXXXXXXXXXXXXX XXXXXXXXXXX100011XX XXXX000010001011 1111000000000000
1XXXXX1110000XXX XXXXXXXXXXXX
0130 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXX01111XXXXXXX X1111010001000000
1000000001X00100 0100000100
0131 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXX01111XXXX000 1111101100000000
1000000001X00100 0100000100
0132 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01100 0100011001
0133 XXXXXXXXXXXXXXXX XXXXX0X00XXXXXX XXXX00001XXXX000 1111101100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0134 XXXXXXXXXXXXXXXX XXXXX0X00XXXXX01 1110XXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1110110011X01100 0100110111
0135 XXXXXXXXXXXXXXXX XXXXXXXXXXX000110XX XXXX00001XXXX000 1001001100000000
1XXXXX1110000XXX XXXXXXXXXXXX
0136 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01100 0100111000
0137 XXXXXXXXXXXXXXXX XXXXXXXXXXX000110XX XXXX00001XXXX000 1001001100000000
1XXXXX1110000XXX XXXXXXXXXXXX
0138 XXXXXXXXXXXXXXXX XXXXXXXXXXX00XXXXXX XXXX00100XXXXXXX X1111010001000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0139 XXXXXXXXXXXXXXXX XXXXXXXXXXX01XXXXXX XXXX01010XXXX01 0111101100000000
1000001010X00XXX XXXXXXXXXXXX

```

```

013A XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX
100000000100100 0100000000
013B XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 111 1011001100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
013C XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX000100010XXX X100000000000000
1XXXXX1110X01XXX XXXXXXXXXXXX
013D XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 0100XXXXXXXXXXXXX XXXXXXXXXXXXXXX000
1110110011X0X100 0101100110
013E XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 101000000XXXXXXXXX X11111000XXX0000
1110110011X00100 0101000101
013F XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 0110000100010XXX X100000000000000
1110110011000100 0101000101
0140 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 0110000100010XXX X100000000000000
1010110011000100 0101000000
0141 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX0XXXXXXXXXXXXX X0101XXXX000000
1XXXXX1110000XXX XXXXXXXXXXXX
0142 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX000100010000 0111100010000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0143 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXXXXX X11110100010000
1000000001X00100 0100000100
0144 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXX001 0111101100000000
1000000001X00100 0100000100
0145 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX000
1XXXXX1111X0X100 0100111010
0146 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX000
1000000001X0X100 0100000000
0147 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX0XXXXXXXXXXXXX 111 1011001100000000
1200000001X00100 0100000000
0148 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111111111 1101000000000000
1XXXXX1110X01XXX XXXXXXXXXXXX
0149 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 0100XXXXXXXXXXXXX XXXXXXXXXXXXXXX000
1110110011X0X100 0101100110
014A XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 101000010XXXXXXXXX X11111000XXX0000
1110110011X00100 0101010001
014B XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 011001111111111 1101000000000000
1110110011000100 0101001110
014C XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX 10 011001111111111 1101000000000000
1110110011000100 0101001110
014D XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00010XXXX001 0111101100000000
1XXXXX1111X00100 0101001100
014E XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00010XXXX001 0111101100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
014F XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX011111111XXX X0011010000000000
1000000001000100 0100000100
0150 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01111XXXXXXX X1111010001000000
1000000001X00100 0100000100
0151 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX000
1XXXXX1111X0X100 0101000110
0152 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX01010XXXXXXX X11111000XXX0000
1XXXXX1110X00XXX XXXXXXXXXXXX
0153 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00000XXXXXXXXX X11111000XXX0000
1000000001X00100 0100000000
0154 XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXXXXXX XXXX00001XXXX111 1111101100000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0155 0000000000000101 XXXX0XXXXXXXXXXXXX XXXX00010XXXX000 0111101101000000
1XXXXX1110X00XXX XXXXXXXXXXXX
0156 000000000000011 XXXX0XXXXXXXXXXXXX XXXX00011XXXX000 0111101101000000
1XXXXX1110X00XXX XXXXXXXXXXXX

```

```

0157 101111111111111111 XXXX0XX00XXXXXXX XXXX00100XXXXX000 0111101101000000
1XXXXX1110X00XXX XXXXXXXXXX
0158 0100000000000000 XXXX0XX00XXXXXXX XXXX00101XXXXX000 0111101101000000
1XXXXX1110X00XXX XXXXXXXXXX
0159 0000000000001000 XXXX0XX00XXXXXXX XXXX00110XXXXX000 0111101101000000
1XXXXX1110X00XXX XXXXXXXXXX
015A XXXXXXXXXXXXXXXXXX XXXXXY000XXXXXXX XXXX000000001010 1111100010000000
1XXXXX1110X00XXX XXXXXXXXXX
015B XXXXXXXXXXXXXXXXXX XXXXXY000XXXXXXX XXXX001010101010 0111111000000000
1XXXXX1110X00XXX XXXXXXXXXX
015C XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXX10 1110001000100XXX X0001010000000000
1X10110011X00100 0101100101
015D XXXXXYYXXXXXXXXX XXXXX0X00XXXXX10 11100000000000XXX X1001010000000000
1110110011X00100 0101011111
015E XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXX001010011XXX X1111111100000000
1XXXXX1111X00100 0101100000
015F XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXX001010010XXX X1111111100000000
1XXXXX1110X00XXX XXXXXXXXXX
0160 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXX001100110101 0111100010000000
1XXXXX1110X00XXX XXXXXXXXXX
0161 XXXXXXXXXXXXXXXX XXXXX0X00XXXXX01 0100000100010XXX X0001010000000000
1110110011X10100 0101100101
0162 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXX10 1110000110011XXX X0001010000000000
1110110011X00100 0101100100
0163 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXX0000000000010 1111100110000000
1XXXXX1111X00100 0101011011
0164 XXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXX0000000000010 1111100010000000
1XXXXX1111X00100 0101011011
0165 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X0X100 0101010010
0166 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X01100 0101100110
0167 XXXXXXXXXXXXXXXXXX XXXXX0X00XXXXXXX XXXXXXXXXXXXXXXXXXXX XXXXXXXXXXXXXXX0000
1XXXXX1111X0X100 0100011001

```

Am2903 MNEMONICS

I₀ FUNCTION

RAMB	RAM B – OUTPUT
Q	Q REGISTER
SPF	SPECIAL FUNCTIONS

ALU Functions

SPF	Special Functions	
HIGH	Fi = HIGH	HIGHS
SRS	Subtract R from S	$S - R - 1 + C_n$
SSR	Subtract S from R	$R - S - 1 + C_n$
ADD	Add R and S	$R + S + C_n$
PAS	Pass S	$S + C_n$
COMS	2's Complement S	$\bar{S} + C_n$
PAR	Pass R	$R + C_n$
COMR	2's Complement R	$\bar{R} + C_n$
LOW	Fi = LOW	LOW'S
CRAS	Complement R AND with S	\overline{RAS}
XNRS	Exclusive NOR R with S	\overline{RVS}
XOR	Exclusive OR R with S	RVS
AND	AND R with S	RAS
NOR	NOR R with S	\overline{RVS}
NAND	NAND R with S	\overline{RAS}
OR	OR R with S	RVS

ALU Destination Control

ADR	Arithmetic Shift Down, Results Into RAM
LDR	Logical Shift Down, Results Into RAM
ADRQ	Arithmetic Shift Down, Results Into RAM and Q Register
LDRQ	Logical Shift Down, Results Into RAM and Q Register
RPT	Results Into RAM, Generate Parity
* LDQP	Logical Shift Down Contents of Q Register, Generate Parity
* QPT	Results Into Q Register, Generate Parity
RQPT	Results Into RAM and Q Register, Generate Parity
AUR	Arithmetic Shift Up, Results Into RAM
LUR	Logical Shift Up, Results Into RAM
AURQ	Arithmetic Shift Up, Results Into RAM and Q Register
LURQ	Arithmetic Shift Up, Results Into RAM and Q Register
* YBUS	Results to Y BUS Only
* LUQ	Logical Shift Up the Contents of the Q Register
SINX	Sign Extend
REG	Results to RAM, Sign Extend

* = $\overline{\text{WRITE}} = H$

Special Functions

UMUL	Unsigned Multiply
TCM	Two's Complement Multiply
INC	Increment by One or Two
SMTC	Sign Magnitude \leftrightarrow Two's Complement
TCMC	Two's Complement Multiply Last Step
SLN	Single Length Normalize
DLN	Double Length Normalize
TDN	Two's Complement Multiply Division
TDC	Two Complement Division Correction

Am2904 Mnemonics

SHIFT INSTRUCTIONS

	I ₁₀	I ₉	I ₈	I ₇	I ₆	M _C	RAM	Q	SIO ₀	SIO _n	QIO ₀	QIO _n	Loaded into M _C
SDL	0	0	0	0	0				Z	0	Z	0	
SUH	0	0	0	0	1				Z	1	Z	1	
SUL	1	0	0	1	0				0	Z	0	Z	
SUH	1	0	0	1	1				1	Z	1	Z	
SDDH	0	0	0	1	1				Z	1	Z	SIO ₀	
SDDL	0	0	1	1	0				Z	0	Z	SIO ₀	
SDUL	1	0	1	1	0				QIO _n	Z	0	Z	
SDUH	1	0	1	1	1				QIO _n	Z	1	Z	
RSD	0	1	0	1	0				Z	SIO ₀	Z	QIO ₀	
RSU	1	1	0	1	0				SIO _n	Z	QIO _n	Z	
SSXO	0	1	1	1	0				Z	I _N ⊕ I _{OVR}	Z	SIO ₀	
RDD	0	1	1	1	1				Z	QIO ₀	Z	SIO ₀	
RDU	1	1	1	1	1				QIO _n	Z	SIO _n	Z	
SDMS	0	0	1	0	1				Z	M _N	Z	SIO ₀	
SMS	0	0	0	1	0				Z	0	Z	M _N	SIO ₀
SDDC	0	0	1	1	1				Z	0	Z	SIO ₀	QIO ₀
SDUC	1	0	1	0	0				QIO _n	Z	0	Z	SIO _n

Microstatus Register Instruction Codes

RSTI	Reset μ SR	$0 \rightarrow \mu_X$
SWAP	Register Swap	$M_X \rightarrow \mu_X$
SHLD	Hold Status	

Microregister Condition Code Output (CT)


MIZ	Zero	$\mu_Z \rightarrow C_T$
MIO	Overflow	$\mu_{OVR} \rightarrow C_T$
MIC	Carry	$\mu_C \rightarrow C_T$
MIS	Sign	$\mu_N \rightarrow C_T$


Machine Status Register Instruction Codes

LMA	Load Y_Z, Y_C, Y_N, Y_{OVR}	$Y_X \rightarrow M_X$
	To MSR	
RSTA	Reset MSR	$0 \rightarrow M_X$
SHOLD	Hold Status	


Machine Register Condition Code Output (CT)

MAZ	Zero	$M_Z \rightarrow C_T$
MAO	Overflow	$M_{OVR} \rightarrow C_T$
MAC	Carry	$M_C \rightarrow C_T$
MAS	Sign	$M_N \rightarrow C_T$

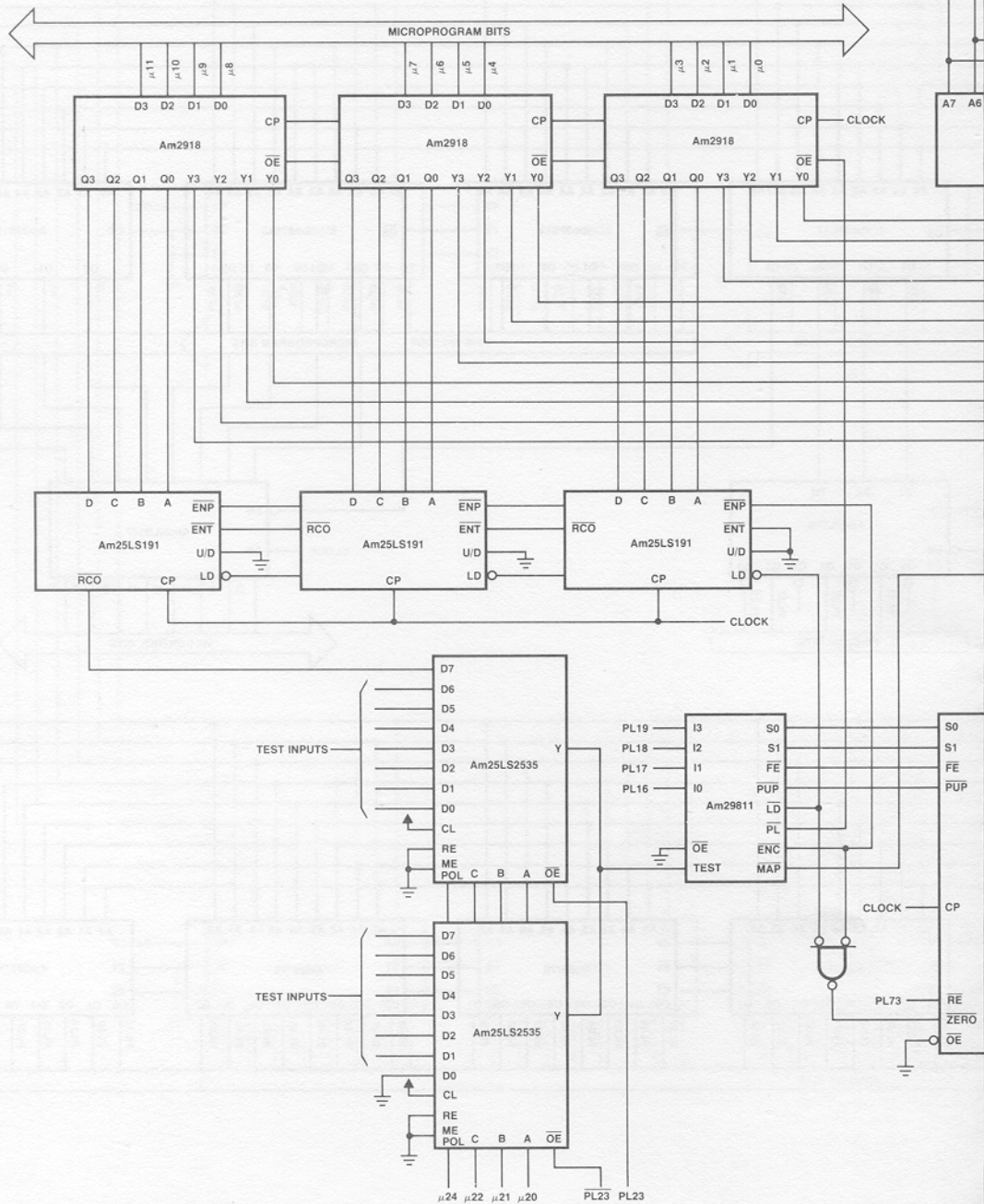


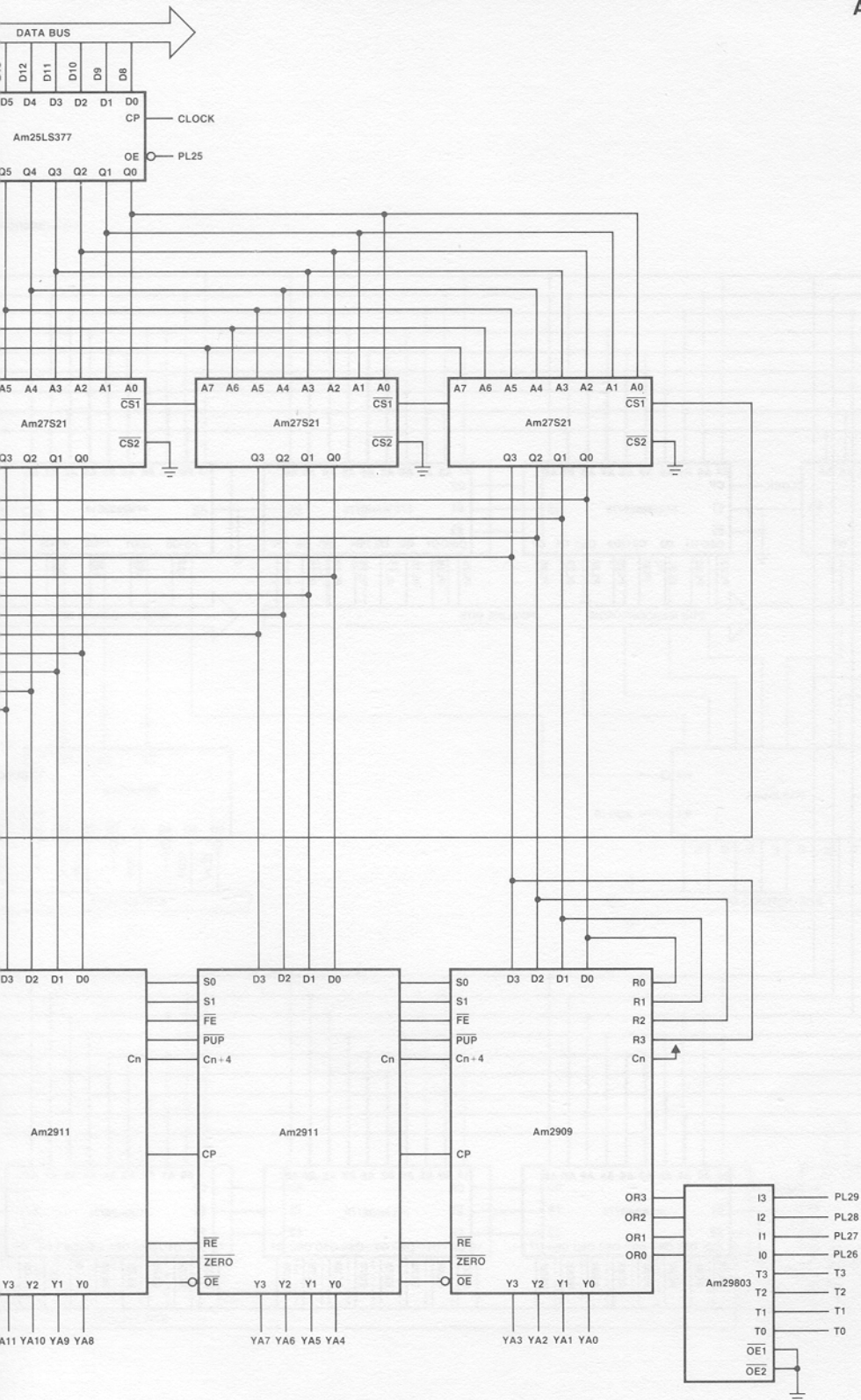


APPENDIX C

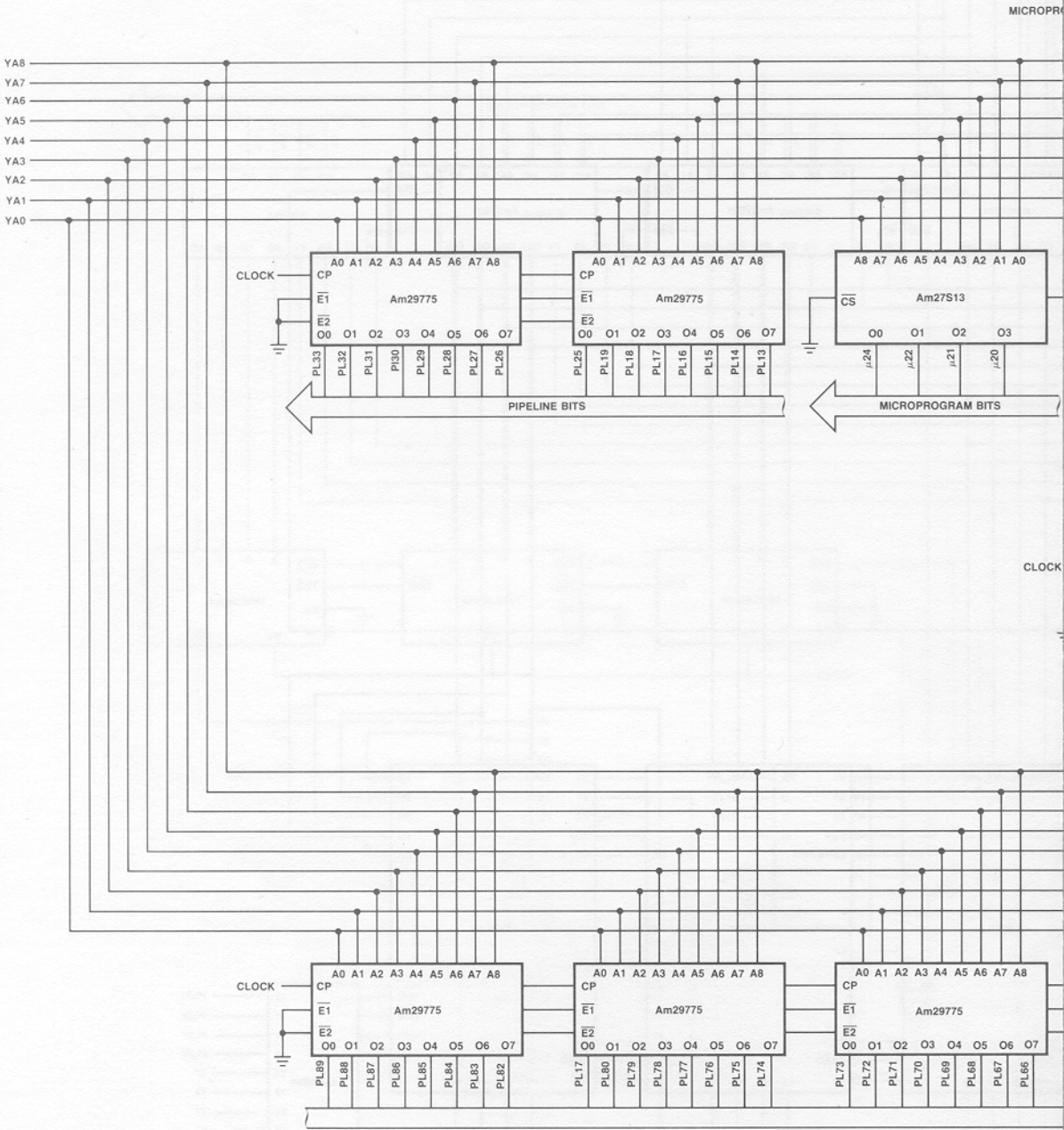


GRAM MEMORY

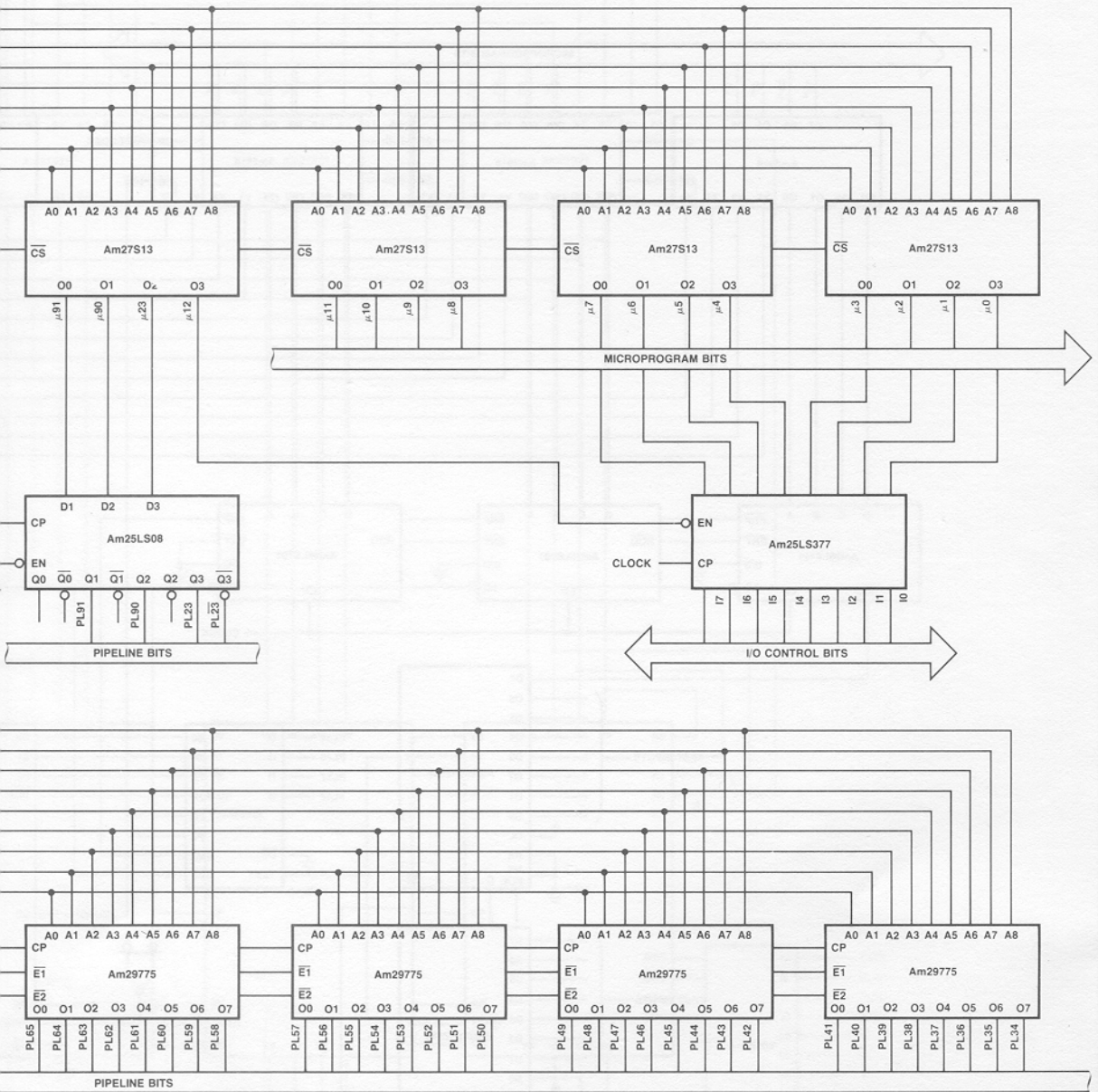

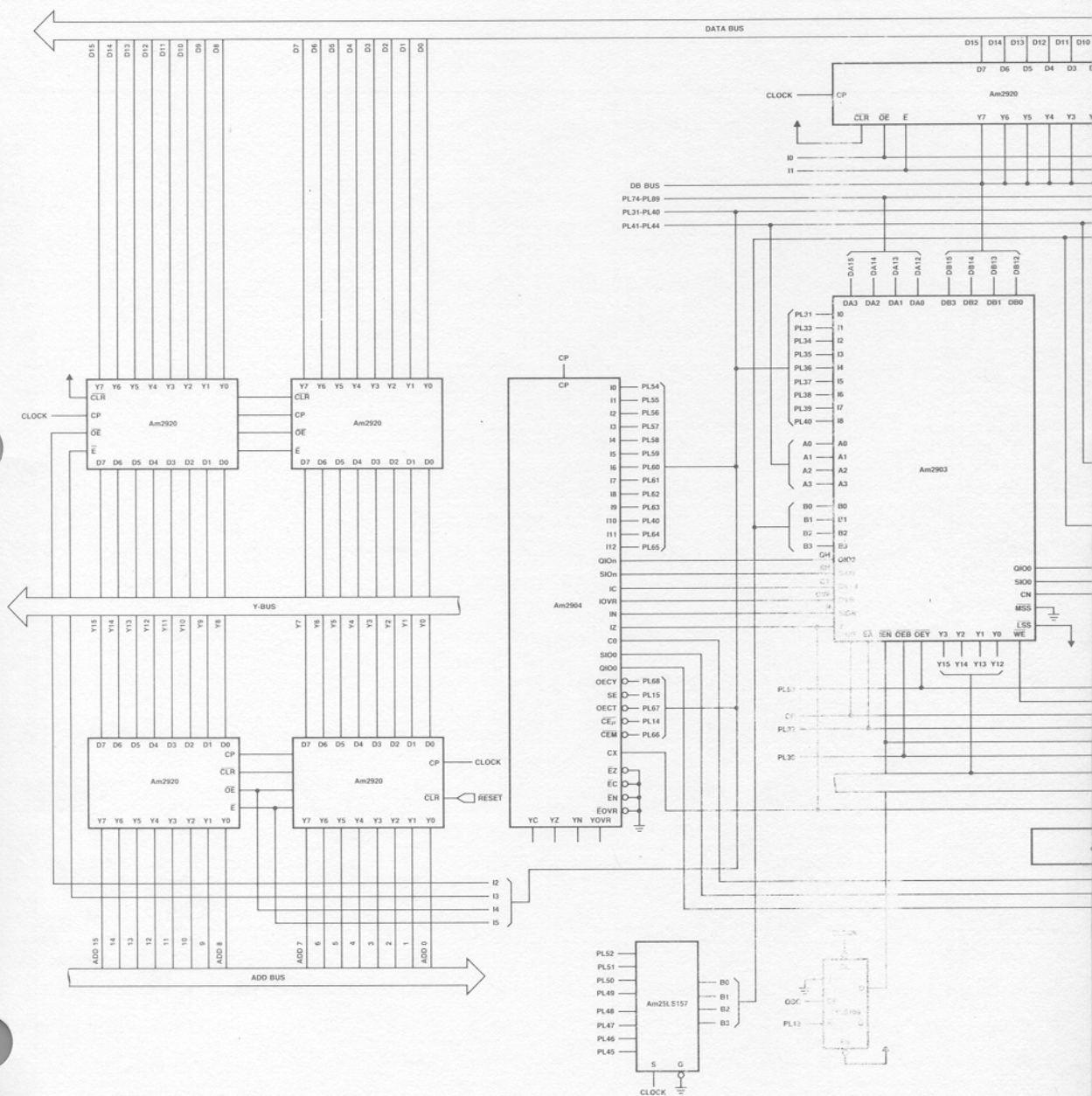

Central Processing Unit

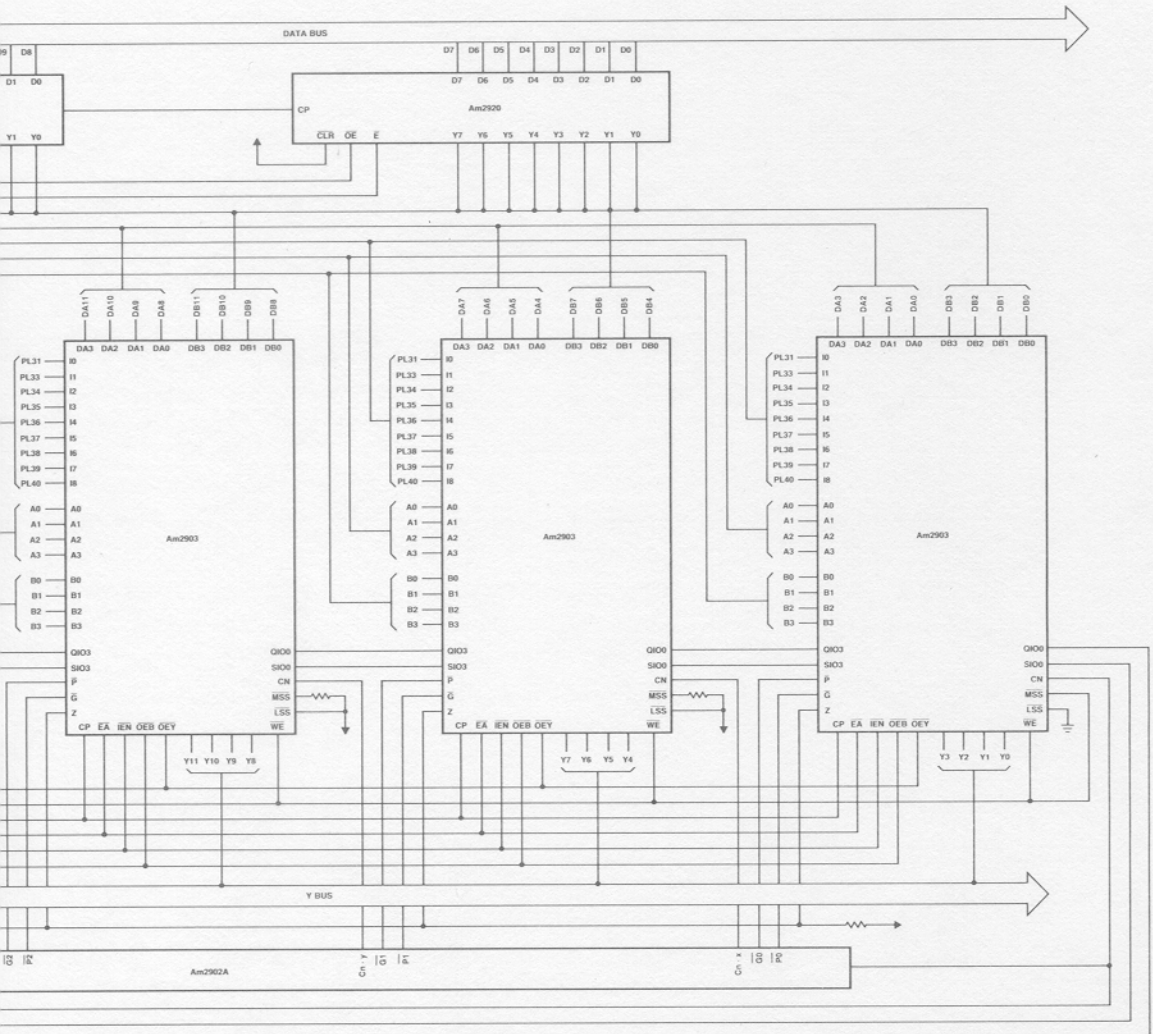



**ADVANCED
MICRO
DEVICES, INC.**


901 Thompson Place
Sunnyvale
California 94086
(408) 732-2400

TWX: 910-339-9280

TELEX: 34-6306

TOLL FREE

(800) 538-8450

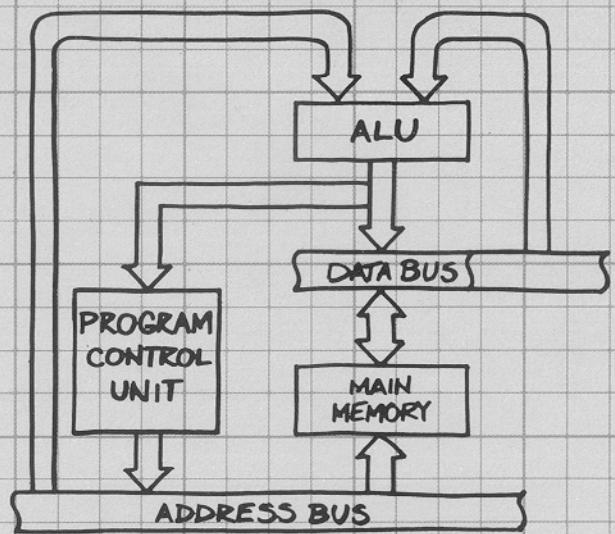


Build A Microcomputer

Chapter V Program Control Unit

Advanced
Micro Devices



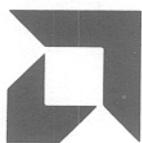

Advanced Micro Devices

Build A Microcomputer

Chapter V Program Control Unit

Copyright © 1978 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-5



Advanced Micro Devices

Build A Microcomputer

Chapter V Program Control Unit

Copyright © 1980 Advanced Micro Devices, Inc.

Advanced Micro Devices, Inc. is a registered trademark of Advanced Micro Devices, Inc. All other trademarks are the property of their respective owners.

Introduction

In order to access instructions and data in an orderly manner within a computer, a Program Control Unit is usually used to provide the most efficient mechanism for program control. A program is a set of instructions which direct the processor to perform a specific task. Ordinarily, program instructions are stored in sequential memory locations. During the normal processing of a program, an instruction is fetched from the location specified by the program counter, the instruction is executed, the program counter is incremented, and another fetch and execute cycle begins. The addressing mechanisms that such control unit might employ are various. Indeed there are some machines that literally use dozens of addressing modes to fetch instructions and data. In this discussion of program control units, several of the addressing modes and their common implementation techniques will be discussed. The addressing modes used commonly in today's machines include register, immediate, direct, indirect, index, and relative and various combinations thereof.

Data Formats

Technically, an instruction set manipulates data of various length words. Generally speaking, most 16 bit minicomputers can manipulate data of three different word lengths: 8-bit bytes, 16-bit words and 32-bit double words. This data may represent fixed point numbers, floating point numbers, or logical data. The data is used as operands for the instructions, and is manipulated as indicated by the particular instruction being executed.

Typically, fixed point data is treated as signed 15-bit integers in the 16-bit representation or as signed 31-bit integers in the 32-bit double length notation. Positive and negative numbers are represented in the ordinary 2's complement notation with the sign bit carrying negative weight. Positive numbers have a sign bit of zero and negative numbers have a sign of one. The numerical value of zero is always represented with all bits LOW.

Floating point numbers consist of a signed exponent and a signed fraction. Many different formats are used by manufacturers in expressing floating point data and these variations will not be described here. Let it simply suffice to say that the floating point number represents a quantity expressed as the product of a fraction times the number 2 raised to the power of the exponent. In some cases, the number 16 is raised to the power of the exponent. Typically, all floating point numbers are assumed to be normalized prior to their use as operands. No pre-normalization is performed and all results are post-normalized. Usually, the floating point instruction set will normalize un-normalized floating point numbers.

Logical operations are used to manipulate 8-bit bytes, 16-bit words or 32-bit double words. All bits participate in the logical operations.

Instruction Formats

Various minicomputers use different types of instruction formats ranging from the very simple straight forward formats to the more complicated difficult to decode formats. For example, a register to register format can consist of a simple 8-bit opcode and two 4-bit source operand specifiers. On the other hand, it may consist of a byte or word specifier, an opcode specifier, source and destination register specifiers, and mode specifiers for each of the source and destination register selections. Again, it is not the purpose of this application note to describe all of the trade-offs in selecting instruction formats but rather to select a simple format such that the student of bipolar microprogrammed microprocessors can understand the techniques used by instructions for operating the machine.

Thus, we will use a few 16-bit and 32-bit formats in this application note to demonstrate the function of the program control unit in various types of instruction execution.

Instruction Types

For purposes of this application note, we will define nine different instruction types using various addressing modes. As we define these instruction types, we will use the basic ADD instruction as the example in all cases. It should be recognized that the operations of the instructions are similar for all the arithmetic as well as logical type operations. However, by using the ADD instruction it will be easier to describe the operation of each of these instructions rather than to try to be very general in their description. Figure 1 shows all nine instruction types with their appropriate names. As is seen, four of the instruction types are single 16-bit word instructions while five of the instruction types are double word or 32-bit, instructions. The advantage of the double word instructions is that a second word can be used as an address whereby it provides an index value or a second word can be used for data which is used as an immediate value.

Register-to-Register Instructions

When the register-to-register (RR) instruction is executed, it is simply a technique for selecting two of the machine's internal working registers in order to execute the desired operation. The instruction is fetched from memory and placed in the instruction register and the source register R2 and second source register R1 are selected as the two source operands for the ALU. Register R1 is the destination register in addition to being a source register and the results of the ALU operation will be placed in the register specified by the R1 field. In the instruction format shown in Figure 1 for the register-to-register instruction, the 8-bit opcode field specifies the machine operation to be performed. The next 4-bit field, R1, in the instruction format specifies the address of the first operand. In most machines, the R1 field is normally the address of a general register. The 4-bit R2 field in the register-to-register instruction format specifies the address of the second operand; this also is normally the address of a general register. In most machines, the R1 field also in addition to being a source operand is the destination general register select. Thus, the results of the operation are stored in the register selected by the R1 field.

The RR instructions are used for operations between registers. We are assuming in this discussion that the machine contains 16 general registers which function as accumulators or index registers in all arithmetic and logical operations. Each general register contains a 16-bit word consisting of two 8-bit bytes. For arithmetic operations, the most significant bit is considered the sign bit using 2's complement representation. The general registers of the machine are usually numbered from 0 to 15 (decimal) and written in hexadecimal notation as 0 through F. In this example, the general registers have not been given specific functional assignments. However, in some machines certain registers are assumed to perform specific functions. These can include specific stack pointer registers and program counter registers. Figure 2 depicts the typical signal path for executing the RR instruction in a bit-slice system.

The actual operation of the Register-to-Register Instruction is as follows. First, the instruction is fetched and placed in the instruction register as shown in Figure 2. This is part of the fetch routine. Next, the instruction is decoded via the mapping PROM and the appropriate microinstruction in the microprogram memory selected and placed in the pipeline register. Then, the instruction is executed where the two registers in the general purpose registers of the Am2903 are selected by the contents of the R1 and R2 fields of the instruction register. The actual microcode required to

Register-to-Register

0	7	8	11	12	15
OP		R1		R2	

ADD INSTRUCTION

$$(R1) \leftarrow (R1) + (R2)$$

Register-to-Memory Reference

0				15
OP		R1		X2

$$(R1) \leftarrow (R1) + [(X2)]$$

Memory-to-Memory

0				15
OP		X1		X2

$$[(X1)] \leftarrow [(X1)] + [(X2)]$$

Register Short Immediate

0				15
OP		R1		DATA

$$(R1) \leftarrow (R1) + DATA$$

Register-to-Indexed Memory

0			15	16		31
OP		R1		X2		ADDRESS

$$(R1) \leftarrow (R1) + [(X2) + A]$$

Register-to-Memory Immediate

0			15	16		31
OP		R1		X2		DATA

$$(R1) \leftarrow (R1) + DATA + [(X2)]$$

Memory-to-Memory Indexed

0			15	16		31
OP		X1		X2		ADDRESS

$$[(X1)] \leftarrow [(X1)] + [(X2) + A]$$

Register Immediate

0			15	16		31
OP		R1				DATA

$$(R1) \leftarrow (R1) + DATA$$

Memory Immediate


0			15	16		31
OP		X1				DATA

$$[(X1)] \leftarrow [(X1)] + DATA$$

Note: (R1) means the contents of register 1.

[(X1)] means the contents of the word whose address is in R1.

Figure 1. Various Instruction Types for the ADD operation.

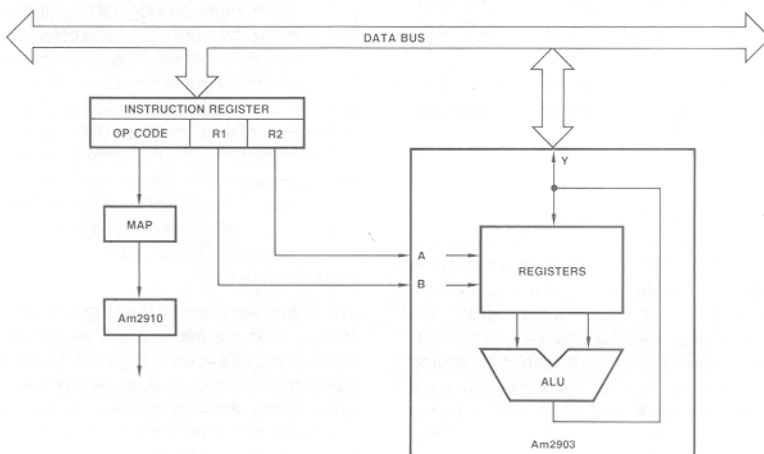

MPR-562

Figure 2. Register-to-Register Instructions Select Two Registers in the Am2903 Array for Instruction Execution.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC \rightarrow MAR; PC + 1 \rightarrow PC	X												
Fetch Inst to IR		X											
Decode			X										
(X2) \rightarrow MAR				X									
MEM + R1 \rightarrow R2					X								

Figure 5. Register to Memory Reference Instruction Microcode.

Next, the instruction is fetched from memory and placed in the instruction register within the CCU. Thirdly, the instruction is decoded via the mapping PROM and the appropriate microinstruction selected and placed in the pipeline register. To execute this particular register-to-memory-reference instruction, it is necessary to place the contents of the register specified by the X2 field into the memory address register. Then the contents of memory can be fetched and the operand added to the value currently contained in the register specified by the R1 field. The result of this operation is placed in the register specified by the R1 field. All totaled, the execution of this register to memory reference instruction requires five microcycles as depicted in this example.

Memory to Memory

This instruction is one whereby the memory location pointed to by the contents of the register specified in the X2 field is fetched and the memory location pointed to by the contents of the register locations specified in the X1 is fetched and these two operands are added together. At the completion of the instruction, the resultant is placed in the memory location as defined by the contents of the register specified in the X1 field.

The Memory to Memory Instruction operation is also depicted by the block diagram shown in Figure 4. In fact, all of the next six instructions to be defined utilize the block diagram of Figure 4 to represent the hardware required for implementing these instructions.

The microcode required for the memory to memory instruction is detailed in Figure 6. The first three microinstructions represent the fetch routine. In the fourth microinstruction, the contents of the register specified by the X2 field are placed in the memory address register. Then, in the fifth microinstruction the contents of

this memory location is loaded into the Q register within the Am2903. This value is temporarily held for use later. In the sixth microinstruction, the contents of the register specified by the X1 field in the instruction is placed in the memory address register. On the seventh microinstruction, this operand is fetched from memory and added to the contents of the Q register with the result being placed in the Q register. In the eighth microinstruction, the current contents of the Q register is returned to the memory location. This memory location is specified by the contents of the register specified by the X1 field and is still in the memory address register. Thus, we have used the Q register as a temporary holding register for the data used in this instruction.

Register with Short-Immediate

This instruction is a technique whereby a 4-bit field is added to the contents of the register specified by the R1 field. Thus, short jumps or branches can be executed within a range of zero to fifteen memory locations. The more significant 12-bits of the word are zero filled.

The register with short immediate instruction operates very similar to the register-to-register instruction. The microcode for this instruction is shown in Figure 7. The only difference between the register-to-register instruction and the register short-immediate instruction is that instead of adding operands specified by the R1 and R2 fields, we take a data value contained in a four-bit field in the instruction as depicted in Figure 1 and add it to the contents of the register specified in the R1 field. The results of the operation are returned to the register specified by the R1 field. This addition is performed by taking the 4-bit data value shown in Figure 1 as the DATA and zero filling the twelve most significant bits. This gives us a 16-bit word ranging in value between zero and fifteen. Thus, short jumps can be implemented using this technique.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC \rightarrow MAR; PC + 1 \rightarrow PC	X												
Fetch Inst to IR		X											
Decode			X										
(X2) \rightarrow MAR				X									
MEM \rightarrow Q					X								
(X1) \rightarrow MAR						X							
MEM + Q \rightarrow Q							X						
Q \rightarrow MEM								X					

Figure 6. Memory to Memory Instruction Microcode.

Microinstruction Operation	Microcycle Time													
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12	
PC \rightarrow MAR; PC + 1 \rightarrow PC	X													
Fetch Inst to IR		X												
Decode			X											
R1 + Data \rightarrow R1				X										

Figure 7. Register Short Immediate Instruction Microcode.

Register to Indexed Memory

The 16-bit word in the register defined by X2 in the instruction is added to the address that is the second word of memory. Then, this address is used to fetch an operand from memory which is added to the contents of the register pointed to by R1. The results of this operation are then placed in R1. The instruction format for this instruction was shown in Figure 1.

The Register to Indexed Memory Instruction is shown in Figure 8 and executed in the following manner. First, the current PC value is placed in the MAR and PC + 1 is returned to the PC register. Next, the instruction at this memory location is fetched and placed in the instruction register. On the third cycle this instruction is decoded and the contents of the microprogram memory placed in the pipeline register. On the fourth microinstruction, the PC value is again placed in the MAR and PC + 1 is returned to the PC register. On the fifth microinstruction, the value at this location in memory is fetched and added to the contents of the X2 register

with the result being placed in the MAR. And on the sixth microinstruction, the operand pointed to by this address is fetched and added to the contents of R1 with the result being placed in the register pointed to by the R1 field of the instruction.

Register to Memory Immediate

In the register to memory immediate instruction, the contents of the memory location pointed to by the register specified in the X2 field is fetched from the memory and the data value which is in the second word of the instruction is also fetched from memory and added to it. This result is then added to the contents of the R1 register and the final result replaces the value currently in R1.

The register to memory immediate instruction as shown in Figure 1 is implemented using the microcode shown in Figure 9. Again, the first three microinstructions are the fetch routine. The fourth microinstruction is used to take the contents of the register specified by the X2 field and place it in the memory address

Microinstruction Operation	Microcycle Time													
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12	
PC \rightarrow MAR; PC + 1 \rightarrow PC	X													
Fetch Inst to IR		X												
Decode			X											
PC \rightarrow MAR; PC + 1 \rightarrow PC				X										
MEM + X2 \rightarrow MAR					X									
MEM + R1 \rightarrow R1						X								

Figure 8. Register to Indexed Memory Instruction Microcode.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC \rightarrow MAR; PC + 1 \rightarrow PC	X												
Fetch Inst to IR		X											
Decode			X										
(X2) \rightarrow MAR				X									
MEM + R1 \rightarrow R1					X								
PC \rightarrow MAR; PC + 1 \rightarrow PC						X							
MEM + R1 \rightarrow R1							X						

Figure 9. Register to Memory Immediate Instruction Microcode.

register. Next, the operand at this memory location is brought into the Am2903's and added to the contents of the register specified by the R1 field with the results returned to that register. The sixth microinstruction is used to set up the memory address register to fetch the second word of the instruction. The seventh microinstruction brings this data value into the Am2903 ALU via the data bus and adds this value to the contents of the register specified by the R1 field. The result of the operation is placed into the register specified by the R1 field.

Memory to Memory Indexed

The memory to memory indexed instruction is one whereby the contents of the register specified in the X2 field are added to the second word of the instruction to form a new address. This address is then used to fetch an operand which is added to the operand selected by taking the contents of the register specified in the R1 field and using that as a memory address to fetch an operand. The result of this addition is then replaced in the memory location pointed to by the contents of the register specified in the X1 field.

The memory to memory indexed instruction is probably the most complicated of the instruction formats described in the application note. In all, nine microinstructions are required for its implementation. Basically, the first three microinstructions are used to fetch the instruction from memory, place it in the instruction register, and decode the instruction for initial operation. Again, the basic fetch routine. Microinstruction number 4 sets up the memory address register to fetch the second word of the instruction and microinstruction number 5 is used to bring this value from mem-

ory into the Am2903 ALU where it is added to the X2 register. The results of the addition are placed into the memory address register during this microinstruction. This value is used to fetch a value from memory which is placed in the Q register using microinstruction number 6. In the seventh microinstruction, the contents of the register pointed to by the X1 field are placed in the memory address register so that microinstruction eight can be utilized to bring this memory value into the Am2903s where it is added to the contents of the Q register with the result being placed into the Q register. Microinstruction number 9 is used to place this value back into the memory location as specified by the contents of the register pointed to by the X1 field. This memory address is still contained in the memory address register so that no updating is required. The total microcode required to implement this instruction routine is shown in Figure 10.

Register Immediate

The register immediate instruction is a very useful instruction which allows data to be added to the contents of the register. In this example, the second word of the instruction is fetched and added to the contents of the register specified in the R1 field.

Figure 11 depicts the microcode used to implement the register immediate instruction. Here, the first three microinstructions are the fetch routine for the instruction. The fourth microinstruction of this routine sets up the MAR to fetch the second word of the two word instruction. The contents of this memory location is brought into the Am2903 ALU and added to the contents of the register specified by the R1 field. The result of this operation is placed in the register specified by the R1 field.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
PC → MAR; PC + 1 → PC				X									
MEM + X2 → MAR					X								
MEM → Q						X							
(X1) → MAR							X						
MEM + Q → Q								X					
Q → MEM									X				

Figure 10. Memory to Memory Indexed Instruction Microcode.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
PC → MAR; PC + 1 → PC				X									
MEM + R1 → R1					X								

Figure 11. Register Immediate Instruction Microcode.

Memory Immediate

The memory immediate instruction is used to add immediate data contained in the second word of the instruction to a location in memory. The memory location is contained in the register specified in the X1 field of the instruction.

The memory immediate instruction is similar to the register immediate instruction except that an indirect addressing scheme is used. Again, the first three microinstructions fetch and decode the memory immediate instruction. The fourth and fifth microinstructions are used to fetch the data value which is the second word of this memory immediate instruction. Microinstruction number 4 sets up the memory address register and microinstruction number 5 brings the data into the Am2903 Q register. Microinstruction number 6 places the contents of the register specified by the X1 field into the memory address register so that the contents of this memory location can be brought into the Am2903 during microinstruction number 7. Here, during microinstruction 7 the contents of the Q register are added to this value and returned to the Q register. At microinstruction 8, the Q register is written back to the memory location as specified by the contents of the register pointed to by the X1 field. This value was already in the memory address register because it was used to fetch the operand originally at this location. The microcode for this instruction is detailed in Figure 12.

Improving Program Control Unit Performance

If we examine the microcode as shown for the various instruction types depicted in Figure 1, we find that all of these microroutines have several things in common. First, the very first microinstruction simply sets up the memory address register with the current value of the program counter. In addition, this microinstruction increments the current program counter value. The second microinstruction simply fetches the contents of memory and places it in the instruction register. The third microinstruction is used to decode the microinstruction, select the appropriate micromemory word and set it into the pipeline register. Finally, the fourth microinstruction begins actual execution of the desired instruction. In all of these examples and using the block diagram of Figure 4, we find that a bottle neck occurs in the ALU because of our need to be operating on program counter data and operand data intermixed. We can improve the performance of the program control unit by making the program counter an external register and using a multiplexer to select either the program counter or the Am2903 output to load the memory address register. This is depicted in block diagram form in Figure 13.

The first effect of implementing a program control unit with this architecture is that one of the instruction types is shortened by one microcycle. This is the register-to-memory-immediate instruction. The new microcode flowcharts for this instruction is

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
PC → MAR; PC + 1 → PC				X									
MEM → Q					X								
(X1) → MAR						X							
MEM + Q → Q							X						
Q → MEM								X					

Figure 12. Memory Immediate Instruction Microcode.

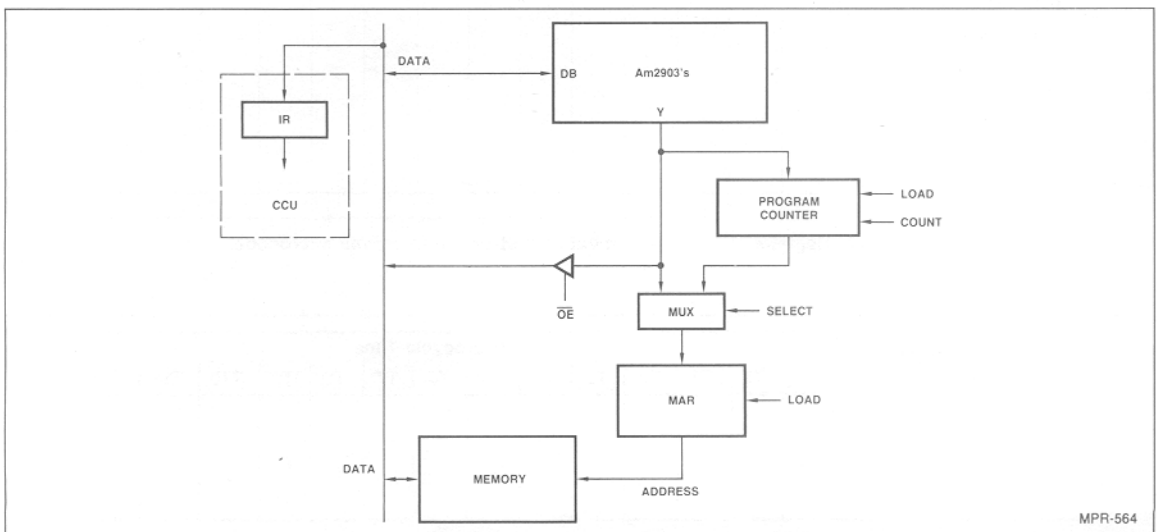


Figure 13. Memory Addressing Scheme with PC Outside of the ALU.

shown in Figure 14. In this case, we see that a PC value can be placed into the memory address register and the PC incremented while the ALU within the Am2903 is being used to perform either a pass or an addition. Thus, this architectural change has made some improvement in the thru-put of our machine.

The most important improvement in thru-put realized by the architecture shown in Figure 13 can be seen by evaluating the timing for sequential instructions. That is, what happens when several instructions are executed sequentially?

To keep the examples simple, let's visualize the microcycle timing chart for three register-to-register instructions executed sequentially. The most obvious timing chart would simply be to take the register-to-register microinstruction flows as shown in Figure 3 and concatenate three examples of this timing chart. If we do this, we will see that the final execution of the values of $R1 + R2$ return to $R1$ utilize the ALU, but the program counter is not in operation. However, the next microcycle requires placing the program counter into the memory address register. Thus, the architecture of Figure 13 allows us to do these two micro-operations during the same microinstruction. If we assume three register-to-register instructions in sequence in memory; let's call them instruction A, B and C; the timing chart of Figure 15 results. What we see in this diagram is that the execution of instruction A can be overlapped with the set up the program counter in memory address register for fetching instruction B. Thus, instead of instruction B starting at time T_4 , it may be started at time T_3 . This can be accomplished by simply having the execution microinstruction also load the MAR with the current PC value and increment the PC. From this discussion, we can see that instead of twelve microcycle times being required to execute three register-to-register instructions, only nine microcycle times will be required. We should caution that if the reader counts the microcycles in Figure 15, he will arrive at 10 microcycle times being required. This leads us to our next point.

If we examine all of the instructions described earlier in this application note, we will find that in all cases, the execution of the instruction (the last microcycle) can be overlapped with the first

microinstruction of the fetch routine. Thus, the architectural change shown in Figure 13 not only allows three of the instructions to execute faster during their total microcode, but in fact all microinstructions can be executed at least one microcycle faster because of the ability to overlap the first microcycle of the fetch routine with the execution of the instruction. This architectural change therefore saves one or two microcycles depending on the instruction.

In Chapter 9 we will show how further overlapping at the machine instruction level can allow us to execute a register-to-register instruction during every microcycle, effectively; rather than every three microcycles as shown in Figure 15. At the present time, let us simply leave the discussion at this point.

Subroutining

An implementation technique that is common to the different addressing modes is the subroutine (also called stack and link). The subroutine allows sections of main program to access a common subsection of the program. The general effect is to allow less lines of machine code to be written for any given program that employs subroutines.

Figure 16 shows an example of a subroutine within the program. The main program executes instructions until it gets to instruction 52 which is a call to subroutine. This instruction puts address 80 in the program counter while saving address 53 in a separate register called Return Register. The program continues on from address 80 to address 85 where it encounters the return from subroutine command. The return-from-subroutine command takes a value out of the return register and puts that into the program counter. At that point the program counter continues down in the main body of the program until it reaches address 57. At this time, another call to subroutine may occur forcing the program counter back to the value of 80 while putting the value 58 into the return address. The subroutine is executed and at address 85 the return command is again encountered. At this point,

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
(X2) → MAR				X									
MEM + R1 → R1					X								
PC → MAR; PC + 1 → PC					X								
MEM + R1 → R1						X							

Figure 14. Register to Memory Immediate Instruction Improved Microcode.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	A			B			C						
Fetch Inst to IR		A			B			C					
Decode			A			B			C				
R1 + R2 → R1				A			B			C			

Figure 15. Register to Register Instruction with Overlap of Execute and PC Control.

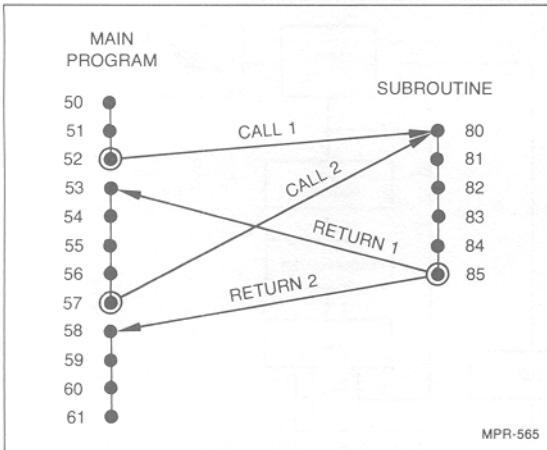


Figure 16. Subroutine Execution.

the subroutine will return control of the program to address 58 of the instruction stream and the main program continues to sequence through its instructions.

In many systems, one subroutine may very well call another subroutine which may in turn call yet another subroutine and so on. To accomplish this the return address linkage must now be "nested" using a last-in first-out (LIFO) stacking arrangement. Figure 17 illustrates subroutine nesting. In this example, the main program contains a subroutine call or jump-to-subroutine command (JSB) at address 53. Program control is passed to the first subroutine at address 88, while the return address 54 is placed in the stack. At address 89 of the subroutine 1 another JSB command is encountered passing the program control to Subroutine 2 at address 502. The return address value 90 is pushed onto the top of the stack. This continues in like fashion for calls to Subroutine 3 and 4 with return address 506 and 723 being placed on the stack. At address 785 of Subroutine 4, a Return from Subroutine (RTS) command is decoded causing the return address 723 on the top of the stack to be placed in the program counter and the contents of the stack are "popped" up one place.

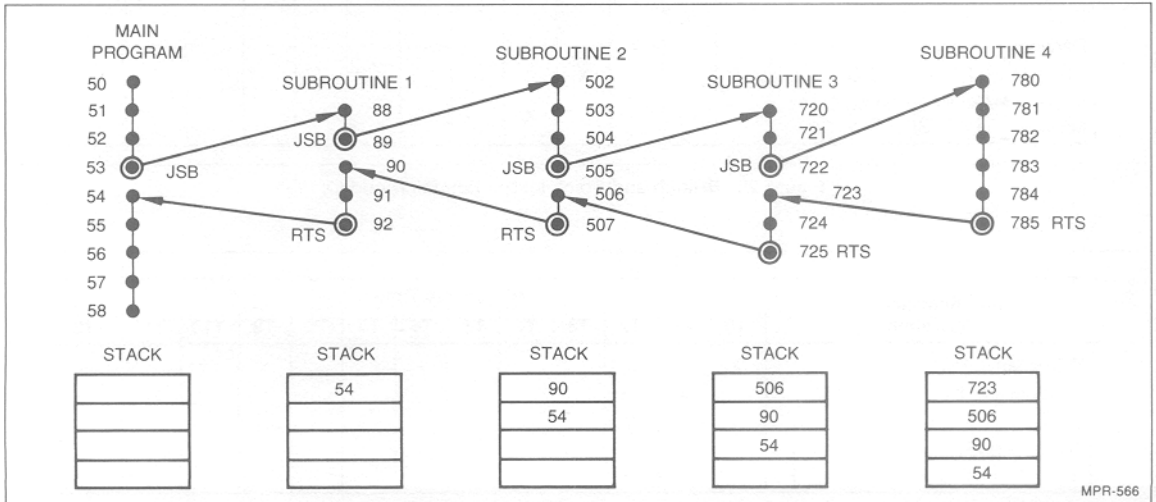


Figure 17. Nested Subroutine Example.

At address 725 another RTS command is found, causing the top of the stack, address 506, to be placed in the program counter and the stack is popped. The identical action occurs for the RTS commands at address 507 and 92 such that control is eventually returned to the main program and the stack is empty.

The LIFO or subroutine stack in the program control hardware is shown in Figure 18. When the call from subroutine command is decoded by the computer control unit, the pipeline register outputs cause the stack control to accept the output of the program counter register and place it at the top of the stack. Next the subroutine address is brought in from the memory passed through the multiplexer and placed in the MAR. The subroutine address is also brought through the multiplexer incrementer, through the incrementer and placed in the program counter register to be used as a possible next source of address. The subroutine return address is recovered from the stack when the pipeline register instructs the stack control logic to place the return address at the multiplexer. The return address is passed through the multiplexer and clocked into the MAR. The return address is also clocked into the PC register via the incrementer multiplexer and the incrementer, for use as the next sequential address. Figure 19 shows the jump to subroutine instruction and Figure 20 shows the microcycles that are used in a typical call to subroutine command using the program control hardware shown in Figure 18. At T0 the program counter is placed into the MAR and updated. Time T1 finds the MAR accessing the subroutine call instruction, with the instruction being placed into the instruction register. At T2 the opcode is decoded by the CCU, and the first instruction microcode bits are clocked into the pipeline register. At time T3, the PC is placed in the MAR. At T4 the starting address of the subroutine is being fetched and placed into the MAR; the stack pointer is incremented; the current program counter is placed on the LIFO stack; and the starting address of the Subroutine plus one is placed into the program counter.

Figure 21 details the microcycle timing for a return-from-subroutine execution. At time zero the current program counter is placed into the MAR, then incremented by one. During time one the contents of the MAR fetches the return from subroutine command, which is then clocked into the instruction register at the end of the microcycle. At time 2 the contents of the instruction register is decoded in the CCU with the control bits being clocked into the pipeline register. During time 3 the return address on the top of

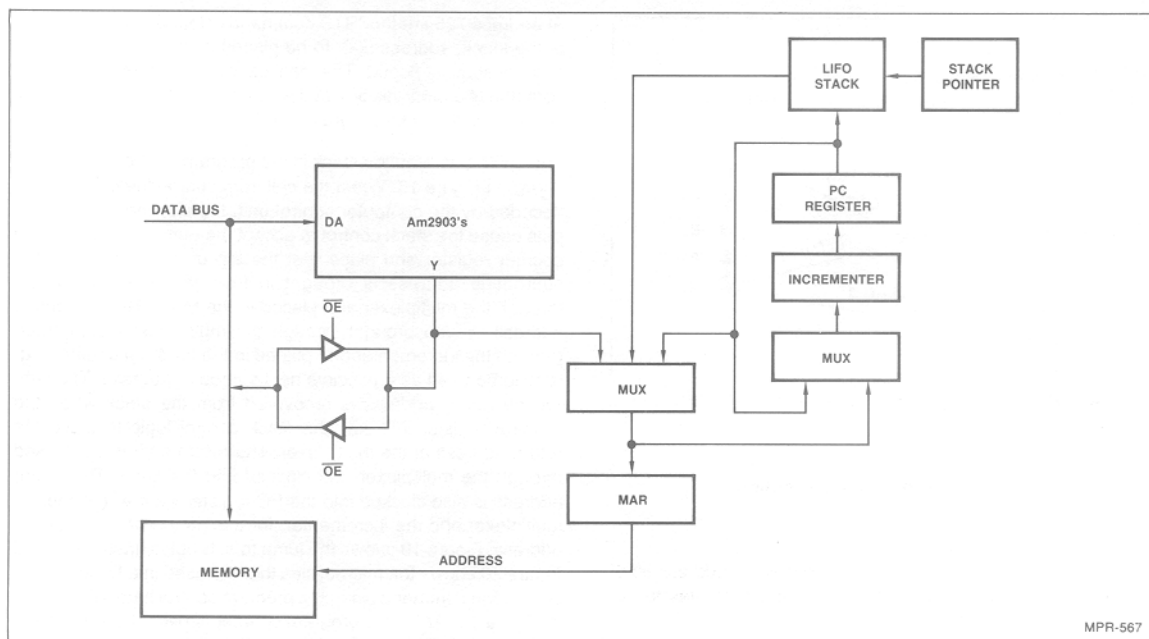


Figure 18. Subroutine Stack Architecture.



Figure 19. Jump to Subroutine (Branch and Stack) Instruction.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
PC → MAR; PC + 1 → PC				X									
{ MEM → MAR; PC → STACK }					X								
{ MEM + 1 → PC; SP + 1 → SP }													

Figure 20. Branch and Stack Instruction Microcode.

Microinstruction Operation	Microcycle Time												
	T0	T1	T2	T3	T4	T5	T6	T7	T8	T9	T10	T11	T12
PC → MAR; PC + 1 → PC	X												
Fetch Inst to IR		X											
Decode			X										
{ Stack → MAR; Stack + 1 → SP }				X									
{ SP - 1 → SP }													

Figure 21. Return from Subroutine Instruction Microcode.

the LIFO stack is placed into the MAR, while that value plus one is stored into program counter. The stack pointer is then decremented.

The basic program control hardware thus developed with some embellishments added are contained within the Am2930 program control unit as shown in Figure 22. The Am2930 is a 4-bit slice of the program control unit. It therefore easily allows the address bus to be virtually independent of the data bus in terms of width. The Am2930 has a general purpose auxiliary register which has two sources and two destinations. One source being the D inputs which flow through the R multiplexer and hence into the auxiliary register and the other source being the output of the full adder which is the second input to the R multiplexer. The two outputs of the auxiliary register go to the A and B multiplexers which in turn source the A and B inputs to the full adder. The register enable pin (\overline{RE}) allows the auxiliary register to be unconditionally loaded from the D Inputs of the Am2930. The A multiplexer selects as its sources a logical zero, the output of the auxiliary register, or the D inputs. The B multiplexer accepts the outputs of the auxiliary register, a logical zero, the output of the subroutine stack file, or the output of the program counter register as its sources.

In the Am2930 design the LIFO stack is 17 words deep, allowing up to seventeen levels of subroutine. The LIFO stack is controlled by the stack pointer logic which gives a FULL indication when the

stack is full and an EMPTY indication when the stack has emptied. The input to the LIFO stack is fed through a stack multiplexer whose inputs may be D inputs or the output of the program counter. Thus, depending upon the application, the stack may be used as either a subroutine stack or a general purpose LIFO stack which resides on the D bus. The incrementer and the full adder are controlled by the Ci and Cn carry-in bits respectively. Figure 23 details the ripple carry connections between Am2930s in a 16-bit array. The Ci input of the least significant slice (LSS) is controlled from the pipeline register.

The Ci signal is internally propagated through the incrementer of each device using carry look ahead logic. The microprogram memory, using the Ci input may now cause the Am2930s to repeatedly access the same main memory instruction if so desired. The full adder has its Cn input tied to ground for the LSS device of the Am2930 array. The Cn signal is propagated in parallel through the Am2930s.

For a faster propagation of the Cn signal the interconnection shown in Figure 24 should be employed. The generate and propagate pins (\overline{G} , \overline{P}) of the Am2902A carry look ahead generator. The look ahead carries ($Cn + x, y, z$) are connected to the Cn inputs of their respective devices. The output of the Am2930 is three-state and is controlled by the output enable pin

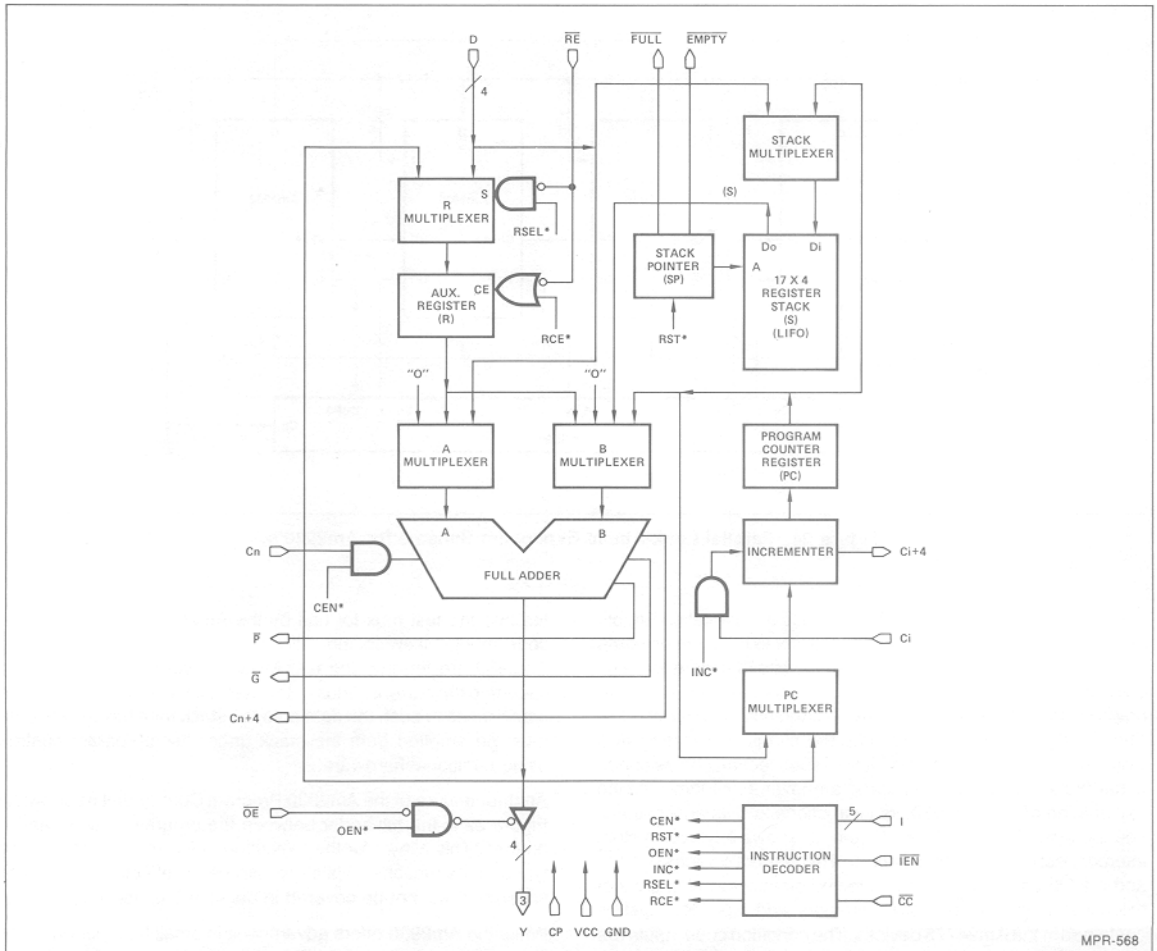


Figure 22. Am2930 Block Diagram.

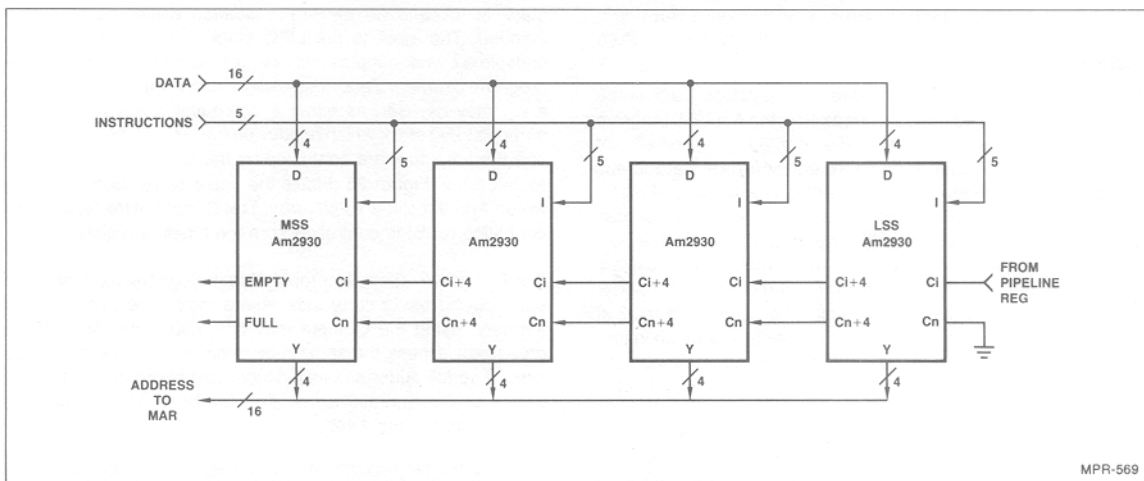


Figure 23. Ripple Expansion Scheme for Am2930's.

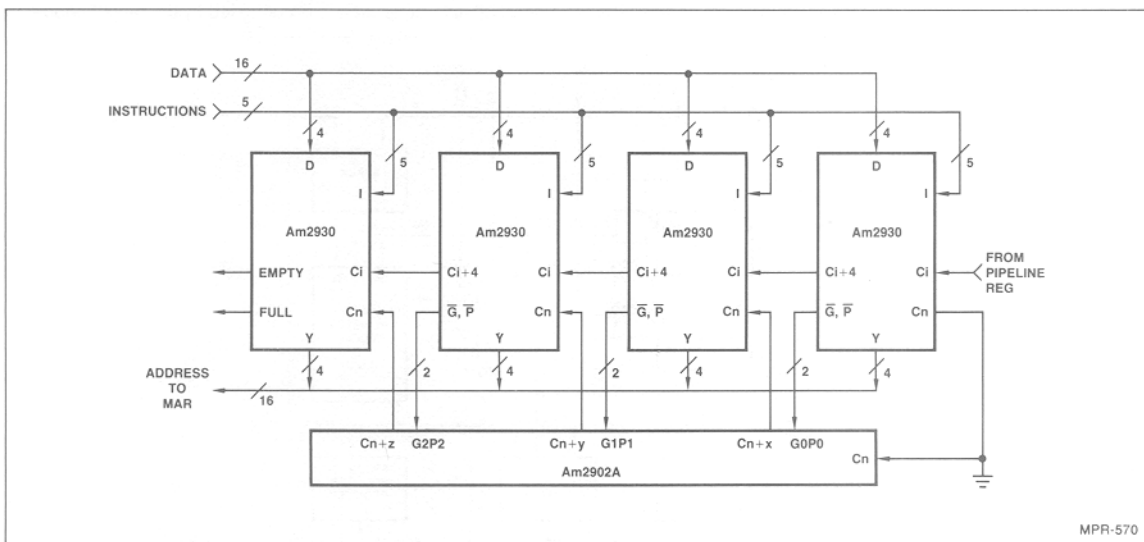


Figure 24. Parallel Look-Ahead Expansion Scheme for Am2930's.

(\overline{OE}). Other features of the Am2930 include an Instruction Enable pin (\overline{IEN}). This pin allows the Am2930 array to be taken off of the microprogram data bus thus allowing the bits that were formerly committed to the Am2930 to be used in conjunction with other devices. The Am2930 also includes a condition code input (\overline{CC}). The Condition Code input permits the conditional testing of a single bit. This allows the feasibility of such techniques as conditional branching at the macroprogram level. For more detailed explanation of the Am2930, its instructions and its applications, see the Am2930 Data Sheet. Figure 25 shows a typical system interconnection using the Am2930. The instruction lines, Ci , RE and the \overline{OE} control pins are connected directly to the outputs of the combination microprogram memory and pipeline registers contained in the Am24775 devices. The condition code inputs are obtained from the Am2904 status and control device, thus allowing conditional jumps on status. Status from the Am2904 is also

fed into the test mux for use by the Am2910 for its conditional code input. Likewise the full and empty indications from the Am2930 are fed into the test MUX for use by the Am2910 to ascertain the current status of the stack. If the stack is full and the user wishes to push the data onto the stack then the current data must be emptied from the stack under microprogram control, using additional hardware.

Another feature of the Am2930 Program Control Unit as shown in Figure 22 is the full adder between the program counter and Y outputs. This allows for the execution of PC relative addressing types of instructions. While this can be an effective addressing scheme, it will not be covered in detail in this application note.

While the Am2930 offers advantages in small high performance systems requiring a small LIFO stack, it is not intended to be the solution for all program counter requirements.

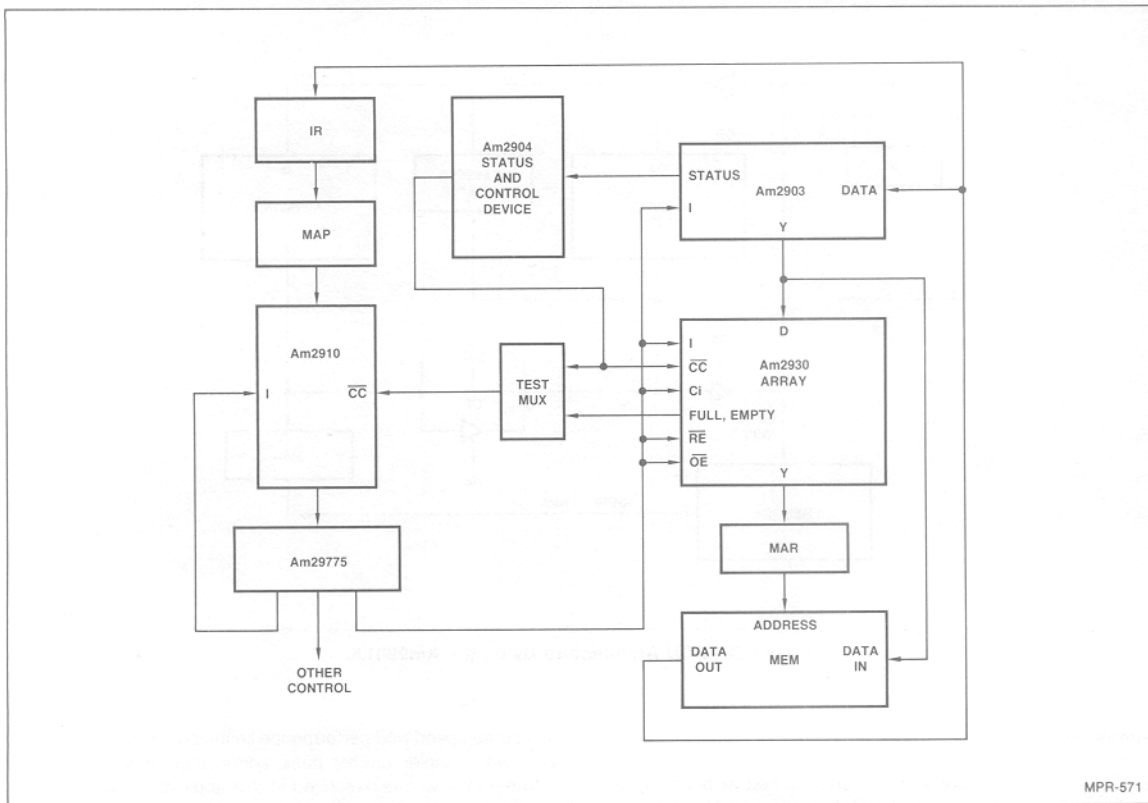


Figure 25. System Interconnection Using the Am2930.

Using the Am2901A as a Program Control Unit

Up to this point, the discussion has concerned a general architecture which includes 16 general registers in the ALU section and the LIFO stack is a program control section as shown in Figure 18. An alternative architecture and that used by most general purpose machines, is to place the LIFO stack in main memory. The stack pointer for the main memory LIFO stack can be contained in the program control unit to be described in this section. If the program control unit is built using Am2901A's it now has the capability of using its internal registers as the program counter, stack pointer, upper stack bound pointer, lower stack bound pointer, and internal temporary registers. This of course provides considerable flexibility in the architecture and also allows for a much greater repertoire of instructions to be executed. Particularly, several stack instructions can be included in the instruction set, most of which will use the form of the register-to-indexed-memory instruction format as shown in Figure 1.

Another advantage of the architecture shown in Figure 25 is speed. The Am2901A's slightly surpass the Am2903 in speed.

Thus, a 16-bit Am2901A program control unit architecture can be implemented and it will perform well within the microcycle times budgeted for the system.

Looking at Figure 26 which shows the Am2901A used as a program control unit and the Am2903 used for the general register stacks/ALU section, we see a three-state buffer on the Y outputs of the Am2903 connected to the data bus as well as a three-state buffer at the input of the Am2903's from the data bus. This provides isolation and buffering for the bus as well as allowing appropriate disconnects so that certain microcycles can be combined to improve the overall performance of the machine. In addition a transfer register is used between the Am2903's and Am2901s to allow a microcycle to be terminated if an ALU operation is taking place within the Am2903's. This provides higher performance operation for the machine. In addition, a bi-directional buffer (such as the Am8304B) is used between the Am2901A Y-outputs and the Am2903 Y-outputs. This gives the ability to push the program counter contained in the Am2901A on the stack for interrupt handling. In addition, values coming from the Am2903 can be placed in the memory address register.

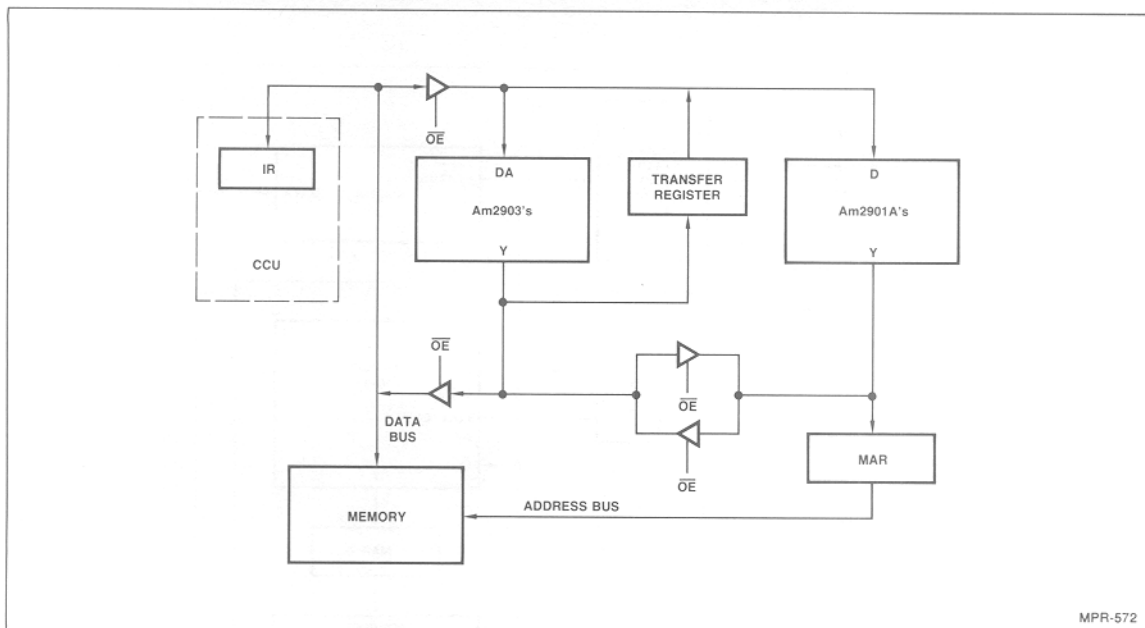



Figure 26. PCU Architecture Using the Am2901A.

Summary

The thrust of this discussion has been aimed at defining and implementing hardware to accomplish addressing of main memory. We have shown that a speed advantage is realized if the program counter is kept separate from the main general purpose register stack/ALU hardware. The most general purpose program control unit is the Am2901A. It offers several advantages in terms of program control, stack pointer control, and stack pointer boundary conditions. The Am2930 can be used in program control units occupying less space and including a built-in stack, but

has some speed and performance limitations. Both devices can be used to implement the basic addressing modes associated with the instructions described in this application note.

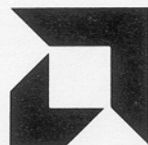Another purpose of this application note is to set the stage for Chapter 9 where we will overlap machine instructions such that register to register instructions can be executed in a single 200ns microcycle and the memory reference instructions can be executed in 600ns (3 microcycles) as the effective execution time. Also, we will expand on the use of the Am2901A as a Program Control Unit.



**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
Sunnyvale

California 94086
(408) 732-2400


TWX: 910-339-9280

TELEX: 34-6306

TOLL FREE

(800) 538-8450

11-78

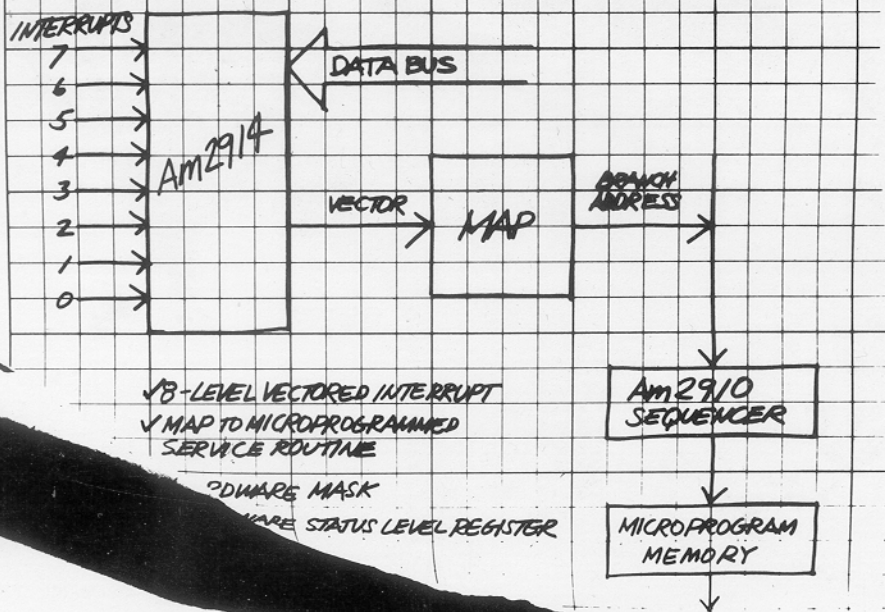

Build A Microcomputer

Chapter VI Interrupt

Advanced
Micro Devices



Copyright © 1979 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-6

INTRODUCTION

A digital computer can be viewed as a finite state machine that moves from state to state via the execution of a program. Interrupt mechanisms provide a well-defined way of altering the flow of states in response to outside asynchronous events (interrupts). There is a wide variety of ways of handling interrupts depending upon the system requirements. The choice of a particular interrupt mechanism can have a large impact on the throughput and flexibility of a system. Therefore, time should be spent carefully defining the interrupt mechanism of a new computer design.

POLLING VS. NON-POLLING

One of the simplest ways to handle asynchronous events is the polling method. With each possible event there is an associated flag that can be accessed by the program. The processor then interrogates each flag in order to determine if service is required. This method trades simple hardware for software. This not only uses memory space but also uses time for polling the flags when no service is required. The polling method has low system throughput, high real time overhead and slow response time.

In non-polling systems, the asynchronous event generates an interrupt request signal which is passed to the processor. The processor in turn suspends the execution of the current process and starts execution of an interrupt service routine. When the interrupt routine is completed, the processor resumes execution of the suspended process. This system is called an interrupt driven system because it executes interrupt service routines that are initiated by interrupt requests.

Although the non-polling method requires more hardware, it has many advantages. Because the execution of interrupt service routines is transparent to the current process, less thought and time is required of the programmer of the current process. The response time is faster because no time is spent interrogating the other non-active interrupts, which in turn increases the system throughput. There is less real time overhead and less memory space required because only the service routine exists in memory and no polling routine is required.

MACHINE VS. MICROPROGRAM LEVEL INTERRUPTS

There are two levels on which interrupts may be handled. The first and most common is the machine level interrupt. In this method possible interrupt requests are checked for during the machine instruction fetch cycle. This guarantees that an interrupt can only happen when a machine instruction is complete and before a new instruction starts.

The second level of handling interrupts is on the microprogram level. In the machine level interrupt system, the microprogram has complete control of when to recognize an interrupt but in the microprogram level system the microprogram can be interrupted at any time. This method has a smaller response time for servicing interrupt requests but requires that restrictions may be placed on the microprogram and the interrupt mechanism. These restrictions come from setting aside space on the finite microprogram stack in the sequencer for possible interrupt requests. Special consideration may also have to be given to loop counters.

TYPES OF INTERRUPTS

There are basically four types of interrupts based on the relationship of the source of the interrupt to the processor: within the processor, within the system, between software, and between processors. A multiprocessor has to be able to handle all four levels of interrupts. Therefore, the interrupt structure that is picked will have these design tradeoffs to consider.

- A. *Intrprocessor* interrupts are those asynchronous events that happen within the processor during the execution of a machine instruction. This group includes such things as zero divide, overflow, accessing restricted memory, execution of a privileged instruction, machine failure, etc.
- B. *Intrasystem* interrupts are interrupts created by system peripherals such as disks, CRT's and printers that require service.
- C. *Executive* interrupts are those interrupts caused by the current program that is executing. This provides a way for the current program to make a request of the executive (operating system) program. These requests might include such things as starting new tasks, allocating hardware resources (disks, line printers), communication with other tasks, etc. A good example would be the supervisor call (SVC) in the IBM 360/370 computers.
- D. *Interprocessor* interrupts include those interrupts between two intelligent processors. For example, this class of interrupts would be used to initiate data and status transfer between a local processor and a processor at a remote site.

SEQUENCE OF EVENTS FOR INTERRUPT HANDLING

When an interrupt occurs there is a sequence of six events that happen. These events, which can be implemented in microcode or machine code, integrated together with the hardware comprise the interrupt mechanism. The sequence of events describes the steps that occur to provide for a smooth transfer from the current process environment to an interrupt servicing environment and back again. The sequence ensures that the processor status will be the same immediately after an interrupt is serviced as immediately before the interrupt occurred. The events listed in the next few paragraphs may differ in order or overlap depending upon the machine design and application.

Interrupt Recognition

This step consists of the recognition of an interrupt request by the processor via an interrupt request line. In this step the processor can determine which device made the request. The method that is used to determine which device to service is directly related to the interrupt structure of the machine. The different types of interrupt structures will be discussed in more detail below.

Save Status

The goal of this step is to make the interrupt sequence transparent to the interrupted process. Therefore, the processor saves a minimum set of flags and registers that may be changed by the interrupt service routine, so that after the service routine is finished they may be restored.

The minimum set of flags and registers would be those which will be destroyed in the transfer of control from the current process to the interrupt service routine. It is then the responsibility of the service routine to save any other registers which it might change. The minimum set of flags and registers might include the Program Counter, Overflow Flag, Sign Flag, Interrupt Mask, etc. The minimum set also includes any register or flag that needs to be saved that the interrupt service routine cannot access.

Interrupt Masking

This step can overlap some of the other steps. For the first few steps of the sequence all interrupts are masked out so that no interrupt may occur before the processor status is saved. The mask is then usually set to accept interrupts of higher priority.

Some machines allow the service routine to selectively enable or disable interrupts also. There may be different variations to this step depending upon the application.

Interrupt Acknowledge

At some point the processor must acknowledge the interrupt being serviced so that the interrupting device knows that it is free to continue its task. The processor can acknowledge several different ways. One of the ways is to have a line devoted to interrupt acknowledge. Another method relies upon the interrupting device recognizing an acknowledge when the cause of the interrupt is serviced.

Some processor designs also use this signal as a request for the interrupting device to send an I.D. down the data bus. This aspect will be discussed in more detail below.

Interrupt Service Routine

At this point the processor can call the interrupt service routine. The address of the routine can be obtained several ways depending upon the system architecture. The most trivial is when there is only one routine which polls each device to find out which one interrupted. Some designs require that the interrupting device put an address on the data bus so that the processor can store it in its program counter and branch to it. Other designs use an I.D. number derived from the priority of the interrupt and put it through a mapping PROM or look-up table in memory in order to obtain the address of the service routine.

Restore and Return

After the interrupt service routine has returned via some variation of an Interrupt Return instruction, the processor should re-

store all the registers and flags that were saved previous to the interrupt routine. If this is done correctly, the processor should have the same status as before the interrupt was recognized.

INTERRUPT STRUCTURES

There are several interrupt structures that can be implemented. As usual there is a trade-off between hardware and software (or firmware). Listed below are some of the more common structures used. The particular structures vary in the way that the processor determines which device made the interrupt request.

Single Request, Multiple Poll

In this structure there is one request line which is shared among all interrupting devices. When the processor recognizes an interrupt request it polls all the devices to find the interrupting device (see Figure 1). Priority is introduced via the order in which the devices are polled. This scheme also allows dynamic reallocation of priority.

Single Request, Daisy Chain Acknowledge

In this structure there is one request line which is shared. When the processor receives an interrupt it sends out a signal acknowledging the interrupt. The acknowledge signal is passed from I/O device to I/O device until the interrupting device receives the signal. At this point the interrupting device identifies itself by putting an I.D. number on the data bus (see Figure 2). This structure requires less software, but has a static priority associated with each interrupting device. There is also a time delay associated with daisy chain acknowledge structure because in each device INTA signal has to pass through several gate delays.

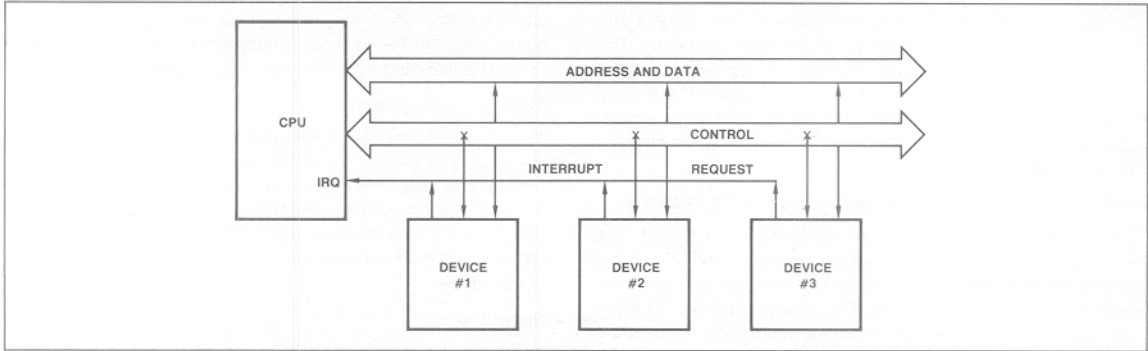


Figure 1. Single Request, Multiple Poll.

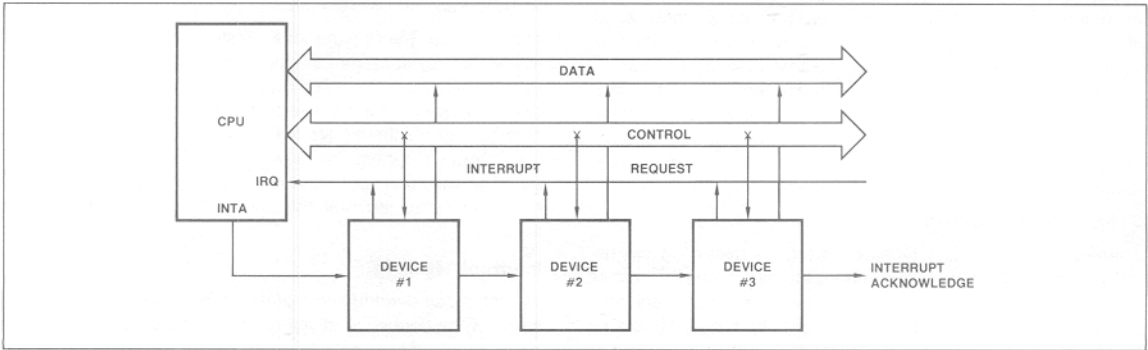


Figure 2. Single Request, Daisy Chain Acknowledge.

Multiple Request

This structure features one line per priority level (see Figure 3). The multiple line structure gives the fastest response time since the interrupting device can be identified immediately. It also results in simpler interfaces in the peripheral units, in general, a single interrupt request flip-flop. This structure allows for the possibility of having a mask bit associated with each priority level (device). The trade-off of this circuit is a wider bus and a limit of one peripheral per priority level.

Multiple Request, Daisy Chain Acknowledge

This structure combines the Single Request/Daisy Chain Acknowledge with the Multiple Request structure (see Figure 4). For each interrupt request line there is an interrupt acknowledge line which is connected to a string of devices in a daisy chain fashion. When the appropriate device receives the interrupt acknowledge, it puts an I.D. number on the data bus.

The advantage of this structure is that a lot (more than available interrupt levels) of devices may be handled by breaking them up

into short daisy chains. This gives a shorter access time than a pure daisy chain with less hardware than an interrupt request line per device. This advantage is that each device must be intelligent to pass on the acknowledge signal which requires more hardware in each device.

PRIORITY SCHEMES

When handling asynchronous requests one must assume that sometimes two or more requests can happen simultaneously. In order to handle this situation, there must be some sort of priority scheme implemented to pick which request is serviced first.

The two most common priority schemes are the static and the rotating structures. In the static structure, all the interrupt levels are ordered from the lowest priority to the highest priority. This can be fixed in software or hardware and is usually permanent.

In the rotating structure the possible interrupt requests are arranged in a circle. There is a pointer which points to the lowest priority interrupt. The priority of each interrupt increases as one travels around the circle, with the highest priority interrupt being

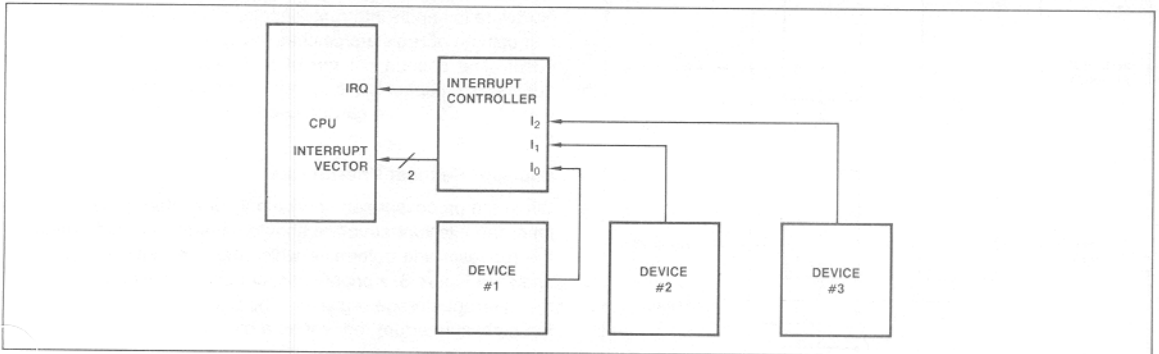


Figure 3. Multiple Request.

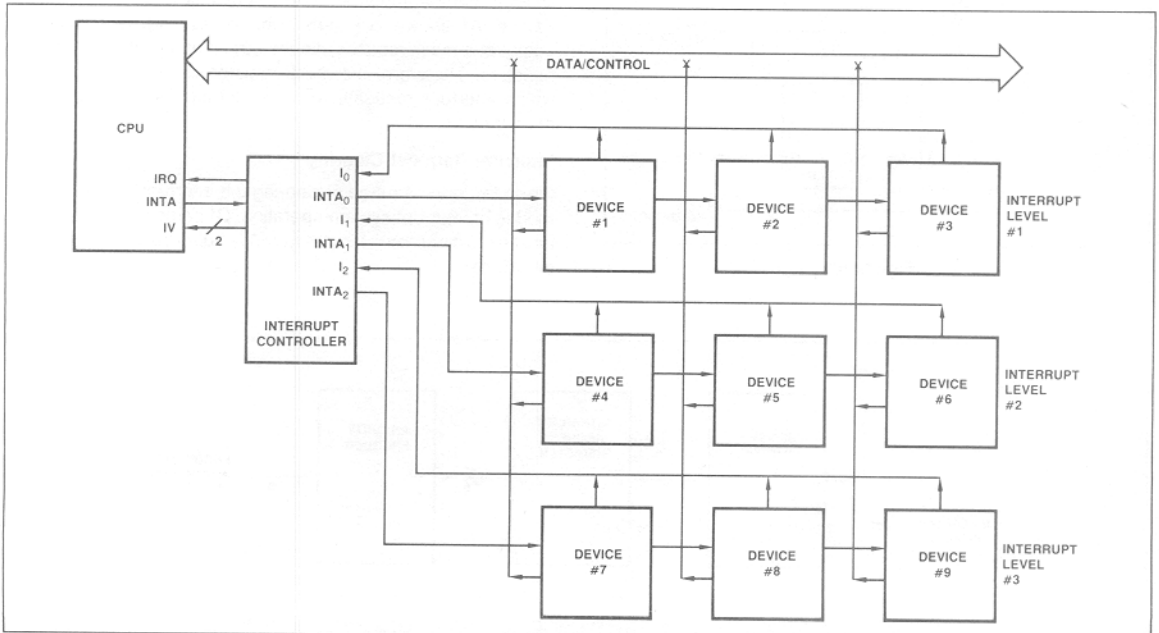


Figure 4. Multiple Requests, Daisy Chain Acknowledge.

adjacent to the lowest priority interrupt. The lowest priority interrupt pointer is changed to point at the interrupt that was just serviced. This structure is advantageous when all interrupts have similar priority and service bandwidth requirements.

NESTING

Nesting allows only higher priority interrupts to interrupt a processing interrupt service routine. Nesting requires fencing off equal and lower level interrupts. Fencing requires that the interrupt structure hold the value of the highest priority interrupt being serviced. This can be implemented with a Status Register that holds the value as a binary encoded number or in other systems as an In-Service Register with a different bit associated with each interrupt.

Whether nesting is performed in microcode or not, all computers must have machine instructions to enable and disable interrupts

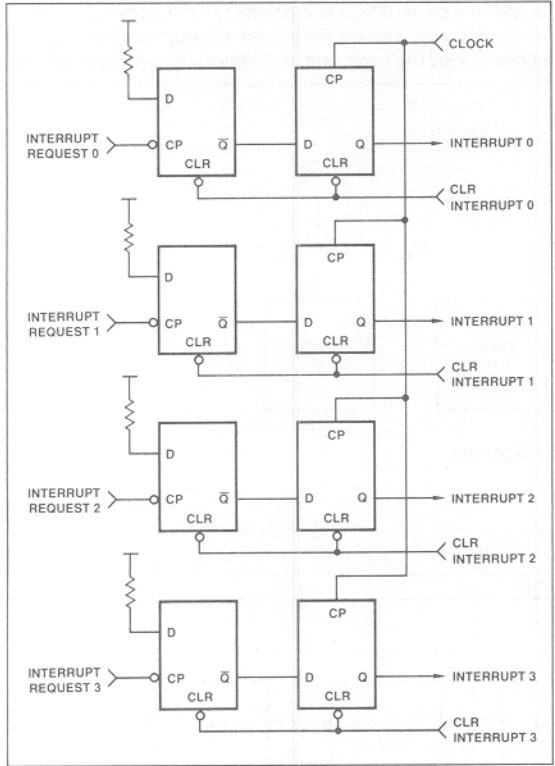


Figure 5.

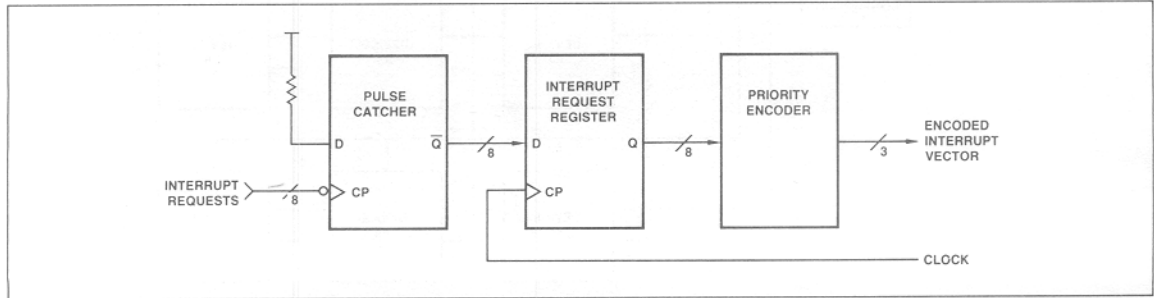


Figure 6.

and set and clear mask bits. With these instructions, interrupt handlers can be written to accomplish nesting of interrupts although less efficiently than when done with microcode and hardware. In low-end computers, the interrupt structure only prioritizes interrupts leaving nesting to the software interrupt handlers.

A UNIVERSAL HARDWARE INTERRUPT STRUCTURE

While designing a hardware interrupt structure, the designer should consider the specific functions that are to be achieved. This provides for system optimization in not only hardware but also software. In the following paragraphs is a step by step development of a general purpose interrupt structure as related to the design concepts involved.

Multiple Interrupt Request Handling

Since interrupt requests are generated from a number of sources, the interrupt structures ability to handle interrupt requests from several sources is important.

As implemented in Figure 5, the register configuration allows the hardware to handle interrupt requests from several sources. The first column of registers catches the asynchronous interrupt request. The second column of registers synchronizes the requests with respect to the system. After the interrupt is serviced, one of the CLR lines can be used to selectively clear the interrupt request.

Interrupt Request Prioritization

Since the processor can service only one interrupt request at a time, the interrupt structure should have the ability to prioritize the requests and determine which has the highest priority. As shown in Figure 6, a priority encoder can be put on the output of the interrupt storage registers. The priority encoder will identify the highest interrupt request as a binary encoded number.

Dynamic Interrupt Request Masking

The ability to selectively inhibit or "mask" individual interrupt requests under program control is desirable. For example at times it may be important to inhibit all interrupts except Power Failure. As shown in Figure 7 this is realized by ANDing the output of a mask register with the output of the interrupt storage registers. Therefore, the mask register can be used to select which interrupt requests will pass through to the rest of the hardware.

Interrupt Request Clearing

Flexibility in the method of clearing the interrupt allows different modes of interrupt system operation. Of particular value are the abilities to clear the interrupt currently being serviced or clear all interrupts.

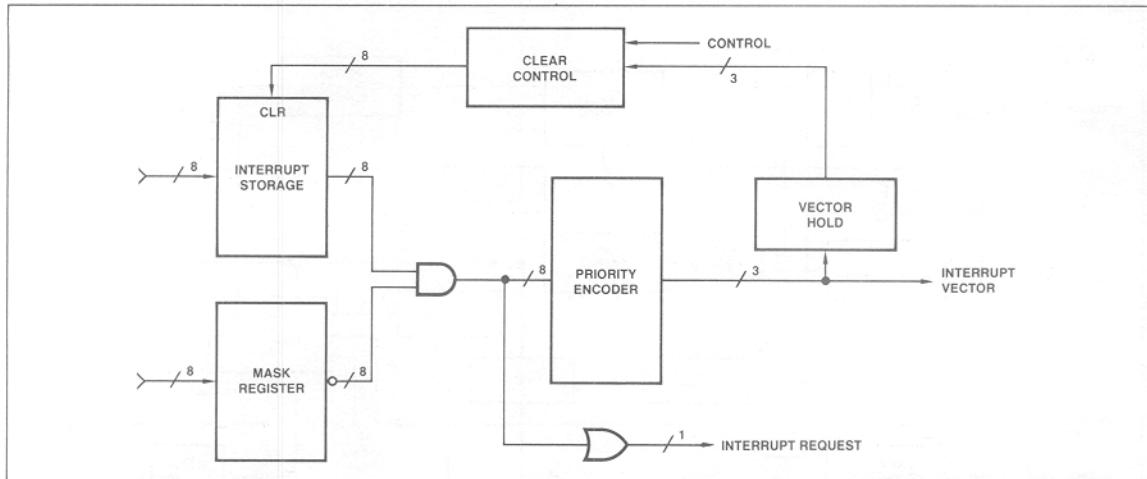


Figure 7.

This is implemented in Figure 8 by use of the Vector Hold register on the output of the Priority Encoder. This register holds the latest interrupt request that was recognized. Before another interrupt request is recognized, the output of the Vector Hold register can be fed through some clear control logic to selectively clear the old interrupt.

Interrupt Request Priority Threshold

The ability to establish a priority threshold is valuable. In this type of operation, only those interrupt requests which have higher priority than a specified threshold priority are accepted. The threshold priority can be defined by microprogram or can be automatically established by hardware at the interrupt currently being serviced plus one. This automatic threshold prevents multiple interrupts from the same source.

This feature is implemented in Figure 8 using an incrementer and status register which is compared with the current request. Each time an interrupt is recognized, the status register is updated with one plus the current level.

Interrupt Service Routine "Nesting"

This feature allows an interrupt service routine for a given priority request to be interrupted in turn by a higher priority interrupt request. This can be achieved by saving the status register before each interrupt is serviced and restoring it afterwards.

Microprogrammability and Hardware Modularity

These last two design concepts bring us to the Vectored Priority Interrupt controller, the Am2914. The Am2914 is a modular interrupt system block which is beneficial in two ways. First,

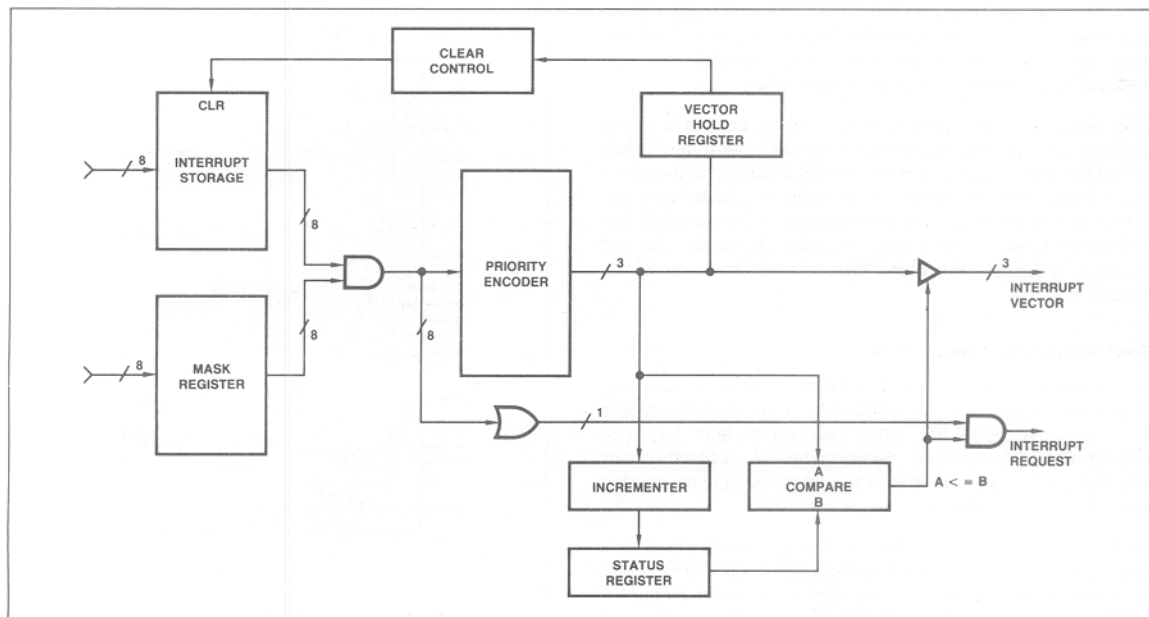


Figure 8.

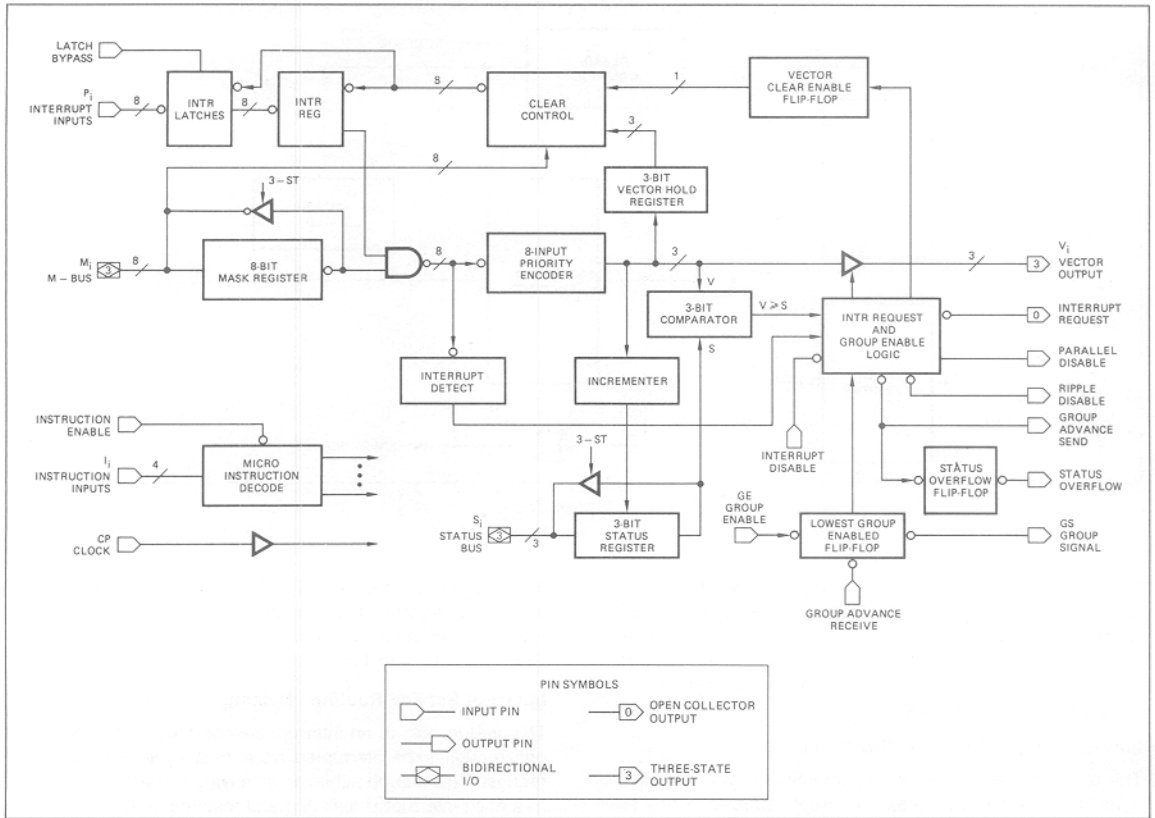


Figure 9. Am2914 Block Diagram.

hardware modularity provides expansion capability. Additional modules may be added as the need to service additional requests arises. Secondly, hardware modularity provides a structural regularity which simplifies the system structure and also reduces the number of hardware part numbers.

The Am2914 is microprogrammable, which permits the construction of a general purpose or "universal" interrupt structure which can be microprogrammed to meet a specific application's requirement. The universality of the structure allows standardization of the hardware and amortization of the hardware development costs across a much broader user base. The end result is a flexible, low cost interrupt structure as shown in Figure 9.

PROGRAMMING THE Am2914

The Am2914 is controlled by a four-bit microinstruction field I_0 - I_3 . The microinstruction is executed if \overline{IE} (Instruction Enable) is LOW and is ignored if \overline{IE} is HIGH, allowing the four I bits to be shared with other functions. Sixteen different microinstructions are executed. Figure 11 shows the microinstructions and the microinstruction codes.

In this microinstruction set, the *Master Clear* microinstruction is selected as binary zero so that during a power-up sequence, the microinstruction register in the microprogram control unit of the central processor can be cleared to all zeros. Thus, on the next clock cycle, the Am2914 will execute the *Master Clear* function.

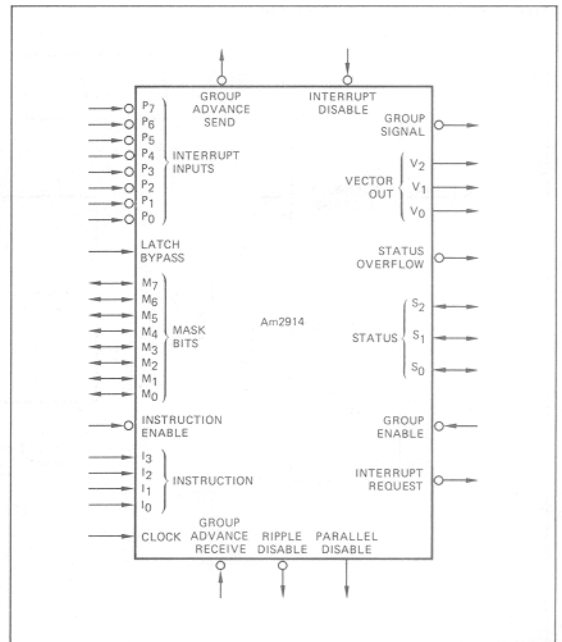


Figure 10. Am2914 Logic Symbol.

MICROINSTRUCTION DESCRIPTION	MICROINSTRUCTION CODE I ₃ I ₂ I ₁ I ₀
MASTER CLEAR	0000
CLEAR ALL INTERRUPTS	0001
CLEAR INTERRUPTS FROM M-BUS	0010
CLEAR INTERRUPTS FROM MASK REGISTER	0011
CLEAR INTERRUPT, LAST VECTOR READ	0100
READ VECTOR	0101
READ STATUS REGISTER	0110
READ MASK REGISTER	0111
SET MASK REGISTER	1000
LOAD STATUS REGISTER	1001
BIT CLEAR MASK REGISTER	1010
BIT SET MASK REGISTER	1011
CLEAR MASK REGISTER	1100
DISABLE INTERRUPT REQUEST	1101
LOAD MASK REGISTER	1110
ENABLE INTERRUPT REQUEST	1111

Figure 11. Am2914 Microinstruction Set.

This includes clearing the Interrupt Latches and Register as well as the Mask Register and Status Register. The LGE flip-flop of the least significant group is set LOW because the Group Advance Receive input is tied LOW. All other Group Advance Receive inputs are tied to Group Advance Send outputs and these are forced HIGH during this instruction. This clear instruction also sets the Interrupt Request Enable flip-flop so that a fully interrupt driven system can be easily initiated from any interrupt.

The *Clear All Interrupts* microinstruction clears the Interrupt Latches and Register.

The *Clear Interrupts from M-Bus* microinstruction clears those Interrupt Latches and Register bits which have corresponding M-Bus bits set equal to one.

The *Clear Interrupts from Mask Register* microinstruction clears those Interrupt Latches and Register bits which have corresponding Mask Register bits set equal to one. The M-Bus is used by the Am2914 during the execution of this microinstruction and must be floating.

The *Clear Interrupt, Last Vector Read* microinstruction clears the Interrupt Latch and Register bit associated with the last vector read.

The *Read Vector* microinstruction is used to read the vector value of the highest priority request causing the interrupt. The vector outputs are three-state drivers that are enabled onto the I bus. This microinstruction also automatically loads the value "vector plus one" into the Status Register. In addition, this instruction sets the Vector Clear Enable flip-flop and loads the current vector value into the Vector Hold Register so that this value can be used by the *Clear Interrupt, Last Vector Read* microinstruction. This allows the user to read the vector associated with the interrupt, and at some later time clear the Interrupt Latch and Register bit associated with the vector read.

During the *Read Status Register* microinstruction, the Status Register outputs are enabled onto the Status Bus (S₀-S₂). The Status Bus is a three-bit, bi-directional, three-state bus.

The *Read Mask Register* microinstruction enables the Mask Register outputs onto the bi-directional, three-state M-Bus.

The *Set Mask Register* microinstruction sets all the bits in the Mask Register to one. This results in all interrupts being inhibited.

The *Load Status Register* microinstruction loads S-Bus data into the Status Register and also loads the LGE flip-flop from the Group Enable input.

The *Bit Clear Mask Register* microinstruction may be used to selectively clear individual Mask Register bits. This microinstruction clears those Mask Register bits which have corresponding M-Bus bits equal to one. Mask Register bits with corresponding M-Bus bits equal to zero are not affected.

The *Bit Set Mask Register* microinstruction sets those Mask Register bits which have corresponding M-Bus bits equal to one. Other Mask Register bits are not affected.

The entire Mask Register is cleared by the *Clear Mask Register* microinstruction. This enables all interrupts subject to the Interrupt Enable flip-flop and the Status Register.

All Interrupt Requests may be disabled by execution of the *Disable Interrupt Request* microinstruction. This microinstruction resets an Interrupt Request Enable flip-flop on the chip.

The *Load Mask Register* microinstruction loads data from the three-state, bi-directional M-Bus into the Mask Register.

The *Enable Interrupt Request* microinstruction sets the Interrupt Enable flip-flop. Thus, Interrupt Requests are enabled subject to the contents of the Mask and Status Registers.

Am2914 BLOCK DIAGRAM DESCRIPTION

The Am2914 block diagram is shown in Figure 9. The Microinstruction Decode circuitry decodes the Interrupt Microinstructions and generates required control signals for the chip.

The Interrupt Register holds the Interrupt Inputs and is an eight-bit, edge-triggered register which is set on the rising edge of the CP Clock signal if the Interrupt Input is LOW.

The Interrupt latches are set/reset latches. When the Latch Bypass signal is LOW, the latches are enabled and act as negative pulse catchers on the inputs to the Interrupt Register. When the Latch Bypass signal is HIGH, the Interrupt latches are transparent.

The Mask Register holds the eight mask bits associated with the eight interrupt levels. The register may be loaded from or read to the M-Bus. Also, the entire register or individual mask bits may be set or cleared.

The Interrupt Detect circuitry detects the presence of any unmasked Interrupt Input. The eight-input Priority Encoder determines the highest priority, non-masked Interrupt Input and forms a binary coded interrupt vector. Following a Vector Read, the three-bit Vector Hold Register holds the binary coded interrupt vector. This stored vector can be used later for clearing interrupts.

The three-bit Status Register holds the status bits and may be loaded from or read to the S-Bus. During a Vector Read, the Incrementer increments the interrupt vector by one, and the result is clocked into the Status Register. Thus, the Status Register points to a level one greater than the vector just read.

The three-bit Comparator compares the Interrupt Vector with the contents of the Status Register and indicates if the Interrupt Vector is greater than or equal to the contents of the Status Register.

The Lowest Group Enabled Flip-Flop is used when a number of Am2914's are cascaded. In a cascaded system, only one Lowest Group Enabled Flip-Flop is LOW at a time. It indicates the eight interrupt group, which contains the lowest priority interrupt level which will be accepted and is used to form the higher order status bits.

The Interrupt Request and Group Enable logic contain various gating to generate the Interrupt Request, Parallel Disable, Ripple Disable, and Group Advance Send signals.

The Status Overflow signal is used to disable all interrupts. It indicates the highest priority interrupt vector has been read and the Status Register has overflowed.

The Clear Control logic generates the eight individual clear signals for the bits in the Interrupt Latches and Register. The Vector Clear Enable Flip-Flop indicates if the last vector read was from this chip. When it is set it enables the Clear Control Logic.

The CP clock signal is used to clock the Interrupt Register, Mask Register, Status Register, Vector Hold Register, and the Lowest Group Enabled, Vector Clear Enable and Status Overflow Flip-Flops, all on the clock LOW-to-HIGH transition.

CASCADING THE Am2914

A number of input/output signals are provided for cascading the Am2914 Vectored Priority Interrupt Encoder. A definition of these I/O signals and their required connections follows:

Group Signal (\overline{GS}) – This signal is the output of the Lowest Group Enabled flip-flop and during a Read Status microinstruction is used to generate the high order bits of the Status word.

Group Enable (\overline{GE}) – This signal is one of the inputs to the Lowest Group Enable flip-flop and is used to load the flip-flop during the Load Status microinstruction.

Group Advance Send (\overline{GAS}) – During a Read Vector microinstruction, this output signal is LOW when the highest priority vector (vector seven) of the group is being read. In a cascaded system Group Advance Send must be tied to the Group Advance Receive input of the next higher group in order to transfer status information.

Group Advance Receive (\overline{GAR}) – During a Master Clear or Read Vector microinstruction, this input signal is used with other internal signals to load the Lowest Group Enabled flip-flop. The Group Advance Receive input of the lowest priority group must be tied to ground.

Status Overflow (\overline{SV}) – This output signal becomes LOW after the highest priority vector (vector seven) of the group has been read and indicates the Status Register has overflowed. It stays LOW until a Master Clear or Load Status microinstruction is executed. The Status Overflow output of the highest priority group should be connected to the Interrupt Disable input of the same group and serves to disable all interrupts until new status is loaded or the system is master cleared. The Status Overflow outputs of lower priority groups should be left open (see Figure 14).

Interrupt Disable (\overline{ID}) – When LOW, this input signal inhibits the Interrupt Request output from the chip and also generates a Ripple Disable output.

Ripple Disable (\overline{RD}) – This output signal is used only in the Ripple Cascade Mode (see below). The Ripple Disable output is LOW when the Interrupt Disable input is LOW, the Lowest Group Enabled flip-flop is LOW, or an Interrupt Request is generated in the group. In the ripple cascade mode, the Ripple Disable output is tied to the Interrupt Disable input of the next lower priority group (see Figure 13).

Parallel Disable (\overline{PD}) – This output is used only in the parallel cascade mode (see below). It is LOW when the Lowest Group Enabled flip-flop is LOW or an Interrupt Request is generated in the group. It is not affected by the Interrupt Disable input.

CASCADING CONFIGURATIONS

A single Am2914 chip may be used to prioritize and encode up to eight interrupt inputs. Figure 12 shows how the above cascade lines should be connected in such a single chip system.

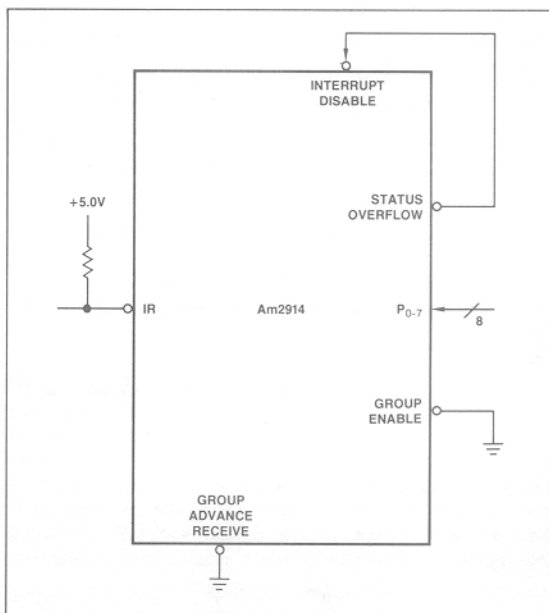


Figure 12. Cascade Lines Connection for Single Chip System.

The Group Advance Receive and Group Enable inputs should be connected to ground so that the Lowest Group Enabled flip-flop is forced LOW during a Master Clear or Load Status microinstruction. Status Overflow should be connected to Interrupt Disable in order to disable interrupts when vector seven is read. The Group Advance Send, Ripple Disable, Group Signal and Parallel Disable pins should be left open.

The Am2914 may be cascaded in either a Ripple Cascade Mode or a Parallel Cascade Mode. In the Ripple Cascade Mode, the Interrupt Disable signal, which disables lower priority interrupts, is allowed to ripple through lower priority groups. Figures 13, 16, and 17 show the cascade connections required for a ripple cascade 32 input interrupt system.

In the parallel cascade mode, a parallel lookahead scheme is employed using the high-speed Am2902 Lookahead Carry Generator. Figures 14, 15, and 17 show the cascade connections required for a parallel cascade 32-input interrupt system. For this application, the Am2902 is used as a lookahead interrupt disable

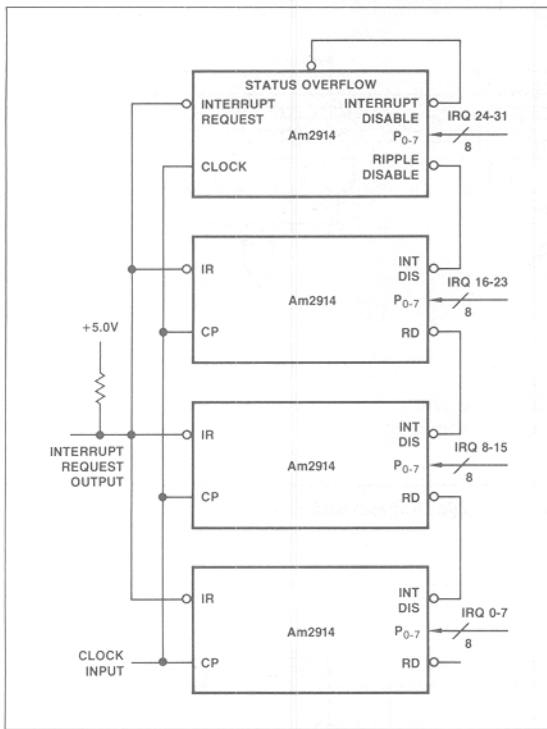


Figure 13. Interrupt Disable Connections for Ripple Cascade Mode.

generator. A Parallel Disable output from any group results in the disabling of all lower priority groups in parallel. Figure 15 shows the Am2902 logic diagram and equations.

In Figures 16 and 17 the Am2913 Priority Interrupt Expander is shown forming the high order bits of the vector and status, respectively. The Am2913 is an eight-line to three-line priority encoder with three-state outputs which are enabled by the five output control signals G1, G2, G3, G4, and G5. In Figure 16, the Am2913 is connected so that its outputs are enabled during a Read Vector instruction, and in Figure 17 the Am2913 is connected to microinstruction bits so that its outputs are enabled during a Read Status Instruction. The Am2913 logic diagram and truth table are shown in Figure 18.

The Am25LS138 three-line to eight-line Decoder also is shown in Figure 17. It is used to decode the three high order status bits during a Load Status instruction. The Am25LS138 logic diagram and truth table are shown in Figure 19.

Am2914 IN THE Am2900 SYSTEM

The block diagram of Figure 20 shows a typical 16-bit mini-computer architecture. The Am2914 is the heart of the Interrupt Control Unit as shown at the bottom of the block diagram. It receives its microinstructions from the Computer Control Unit. The mask, Status and Interrupt vector information are passed on the data bus. The interrupt request line from the Am2914 input into the next microprogram Address Control unit where it can be tested to determine if an interrupt request has been made.

Figures 21 and 22 show the detailed hardware design of two example interrupt control units (ICU's) for an Am2900 Computer

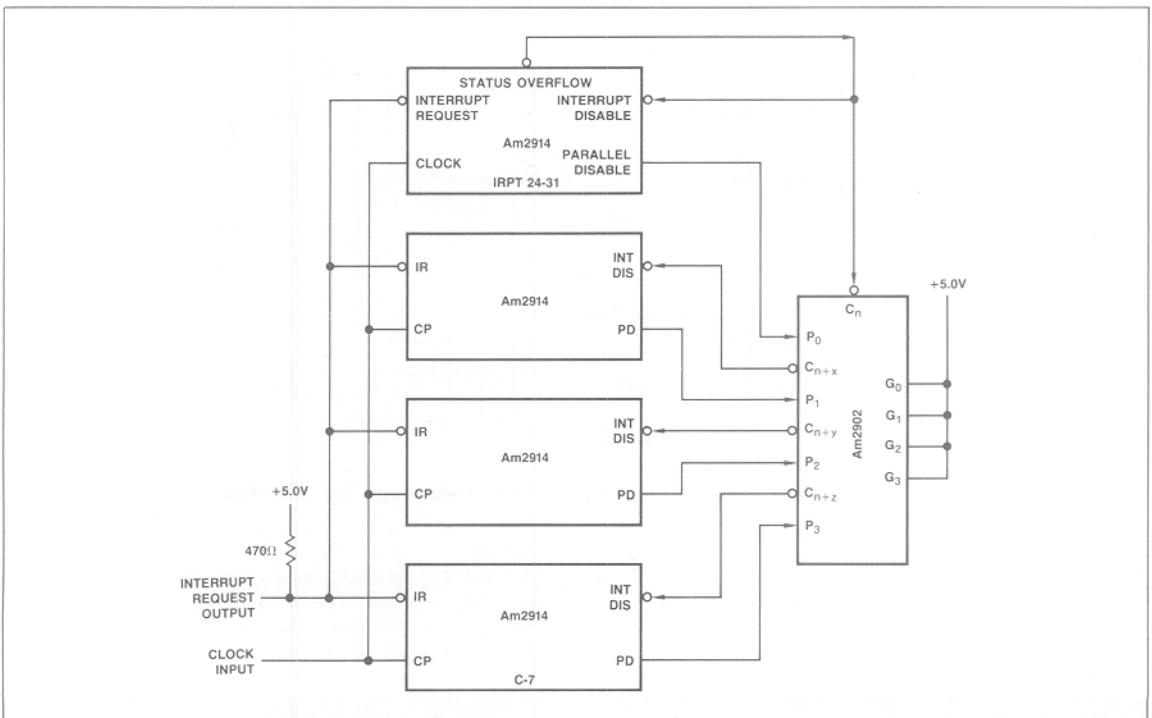


Figure 14. Interrupt Disable Connections for Parallel Cascade Mode.

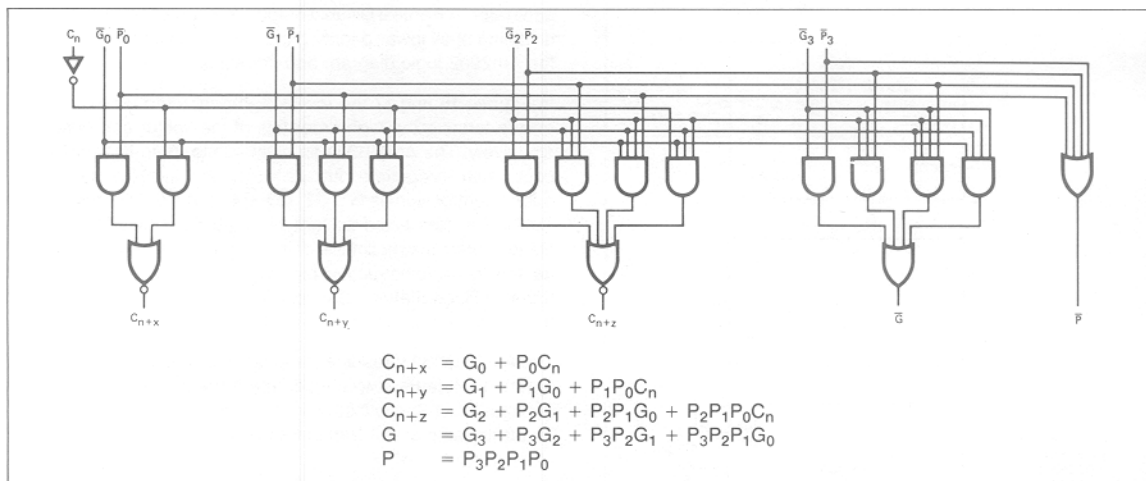


Figure 15. Am2902 Carry Look-Ahead Generator Logic Diagram and Equations.

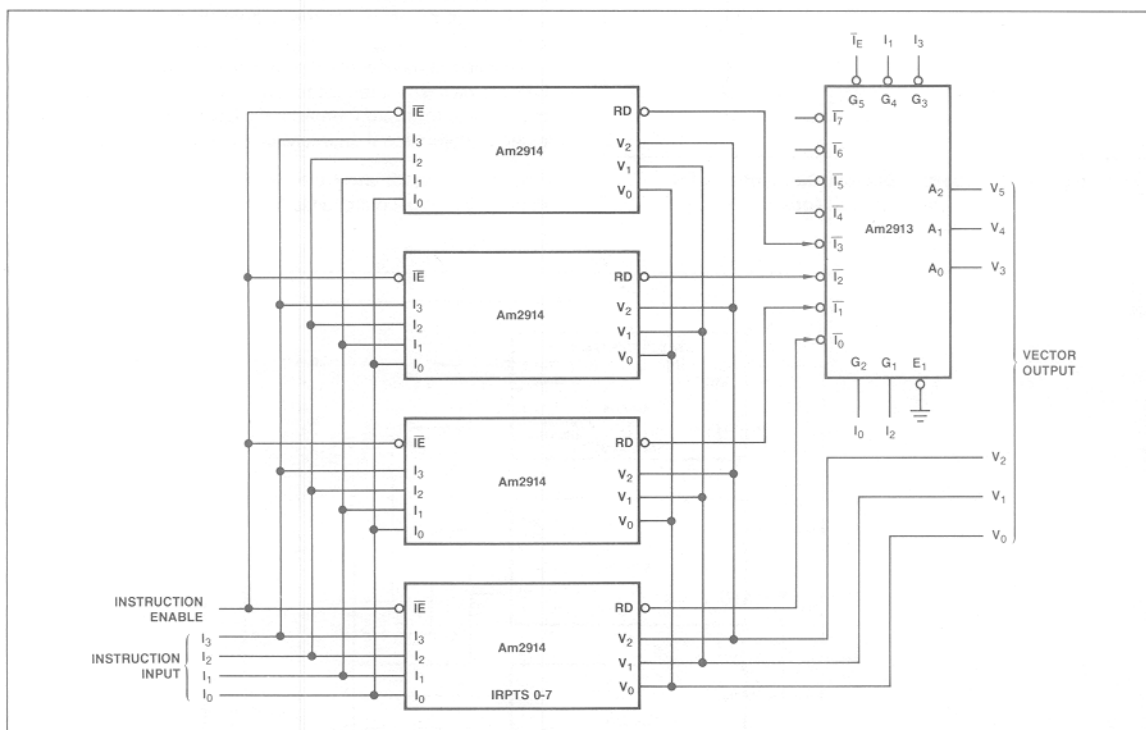


Figure 16. Vector Connections for both the Parallel and Ripple Cascade Modes.

System. Figure 21 shows an eight interrupt level ICU, and Figure 22 shows an ICU which has sixteen levels. In both designs, the Am2914 Instruction inputs and Instruction Enable input are driven by the I_{0-3} field and \overline{IE} bit, respectively, of the Microinstruction Register. Note that Am2914 Instruction inputs are enabled only when the \overline{IE} bit is LOW. Therefore, the I_{0-3} field of the Microinstruction Register may be shared with another functional unit of the computer such as the ALU.

The Latch Bypass input is shown connected to ground so that a Low-going pulse will be detected at any of the Interrupt Inputs. The designer has the option of connecting the Latch Bypass input to a pull up resistor connected to +5 volts. This makes the inputs low level sensitive. They are clocked in by each system clock. It is therefore implied that the processor will have to acknowledge the interrupt so that the interrupting device will know when to release the interrupt request line.


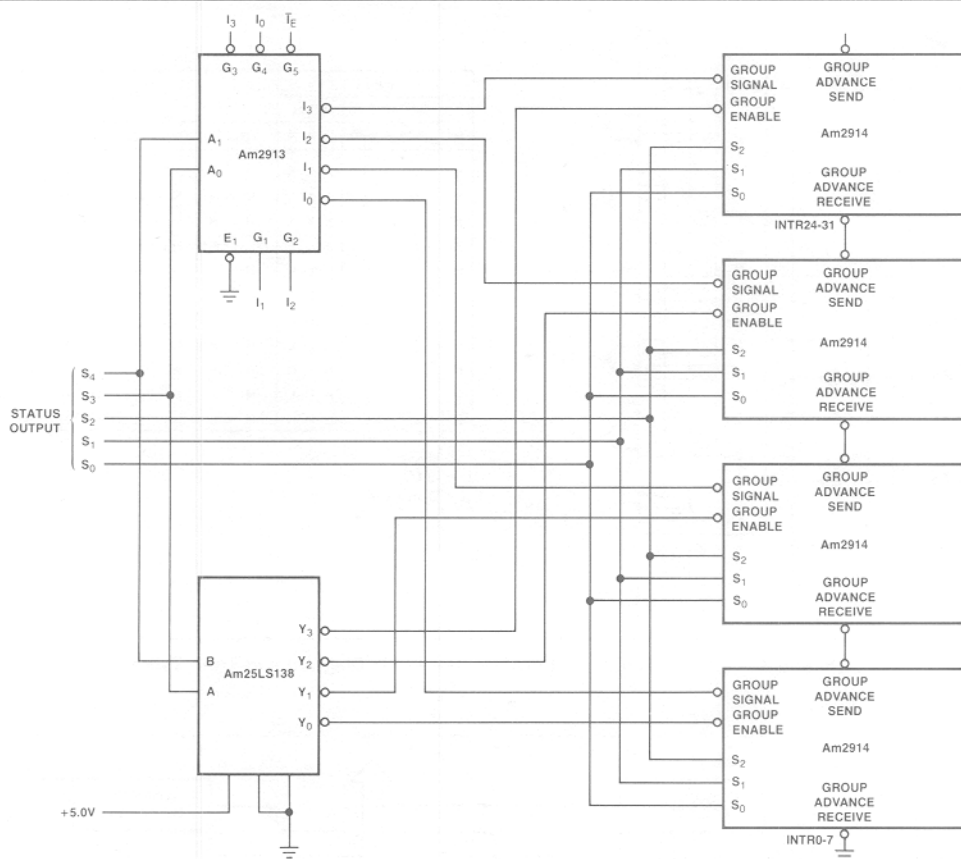


Figure 17. Group Signal, Group Enable, Group Advance Send, Group Advance Receive and Status Connections for Both the Parallel and Ripple Cascade Modes.

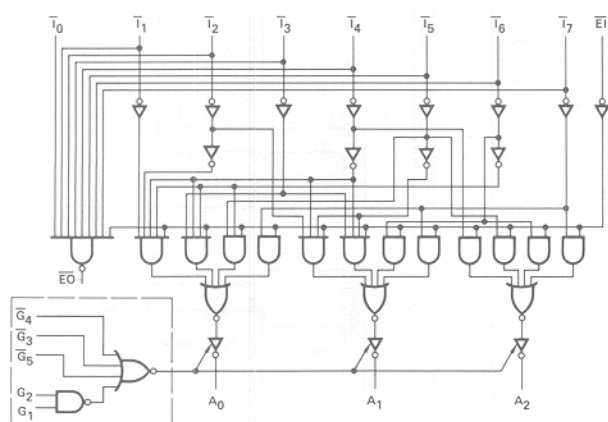

Inputs									Outputs			
EI	T ₀	T ₁	T ₂	T ₃	T ₄	T ₅	T ₆	T ₇	A ₀	A ₁	A ₂	EO
H	X	X	X	X	X	X	X	X	L	L	L	H
L	H	H	H	H	H	H	H	H	L	L	L	H
L	X	X	X	X	X	X	X	L	H	H	H	H
L	X	X	X	X	X	X	L	H	L	H	H	H
L	X	X	X	X	L	H	H	H	H	L	H	H
L	X	X	X	L	H	H	H	H	L	L	H	H
L	X	X	L	H	H	H	H	H	H	H	L	H
L	X	L	H	H	H	H	H	H	L	H	L	H
L	X	L	H	H	H	H	H	H	L	L	L	H
L	L	H	H	H	H	H	H	H	L	L	L	H

H = HIGH Voltage Level

L = LOW Voltage Level

X = Don't Care

For $G_1 = H, G_2 = H, G_3 = L, G_4 = L, G_5 = L$

G1	G2	G3	G4	G5	A ₀	A ₁	A ₂
H	H	L	L	L	Enabled		
L	X	X	X	X	Z	Z	Z
X	L	X	X	X	Z	Z	Z
X	X	H	X	X	Z	Z	Z
X	X	X	H	X	Z	Z	Z
X	X	X	X	H	Z	Z	Z

Z = HIGH Impedance

Figure 18. Am2913 Priority Interrupt Expander Logic Diagram and Truth Table.

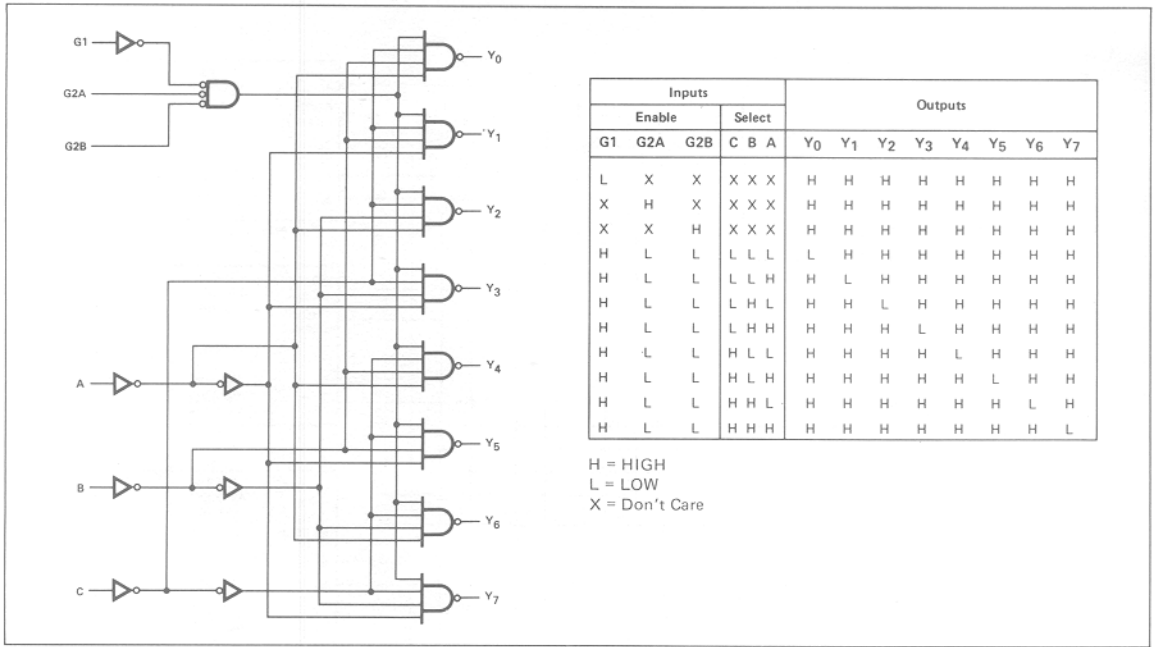


Figure 19. Am25LS138 3 to 8 Line Decoder Logic Diagram and Truth Table.

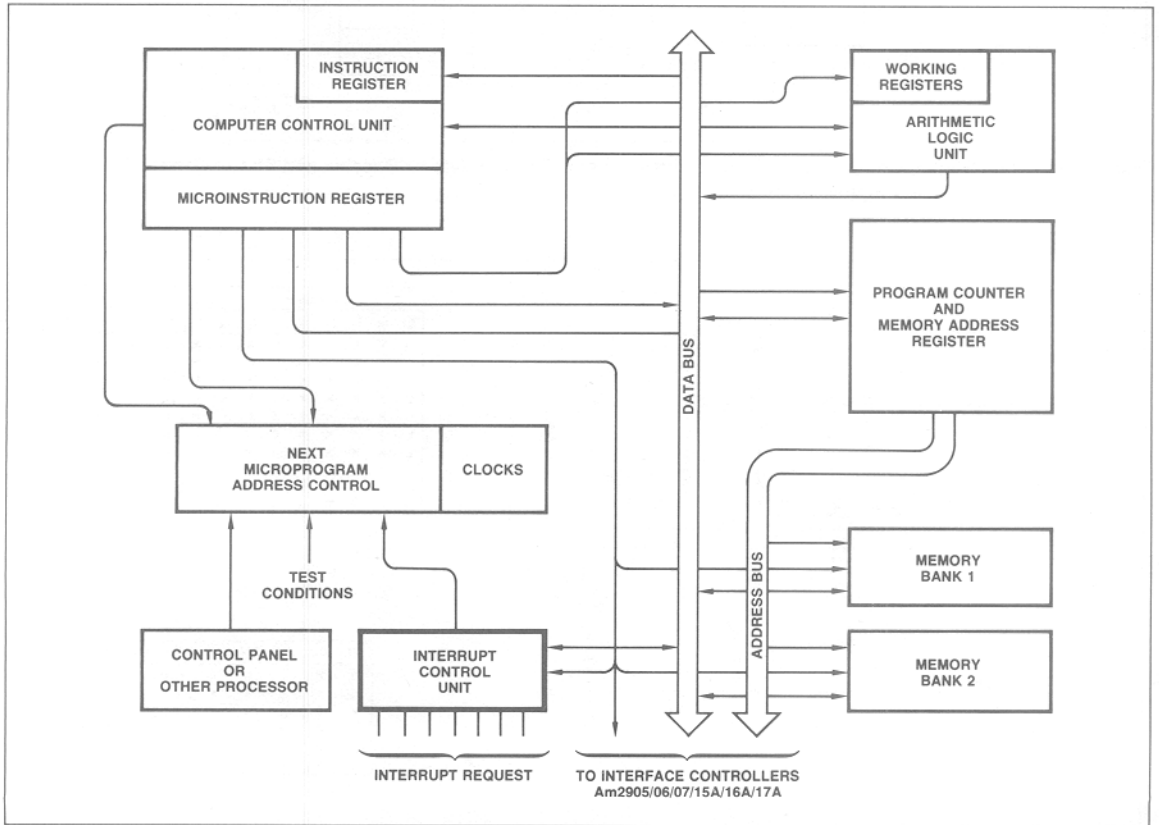


Figure 20. A Generalized Computer Architecture.

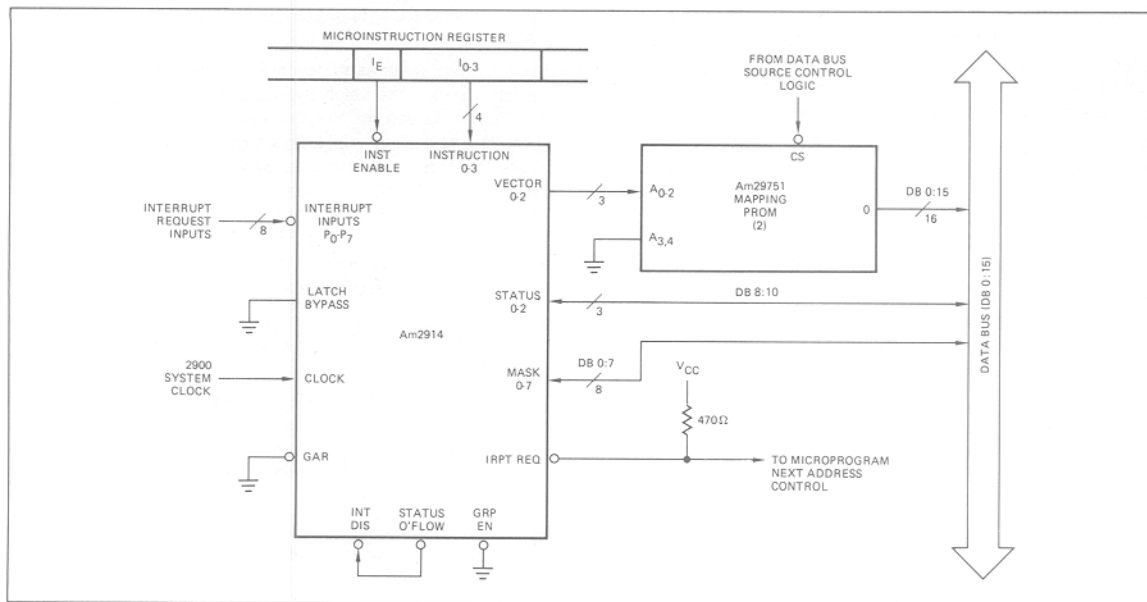


Figure 21. 8 Level Interrupt Control Unit for Am2900 System.

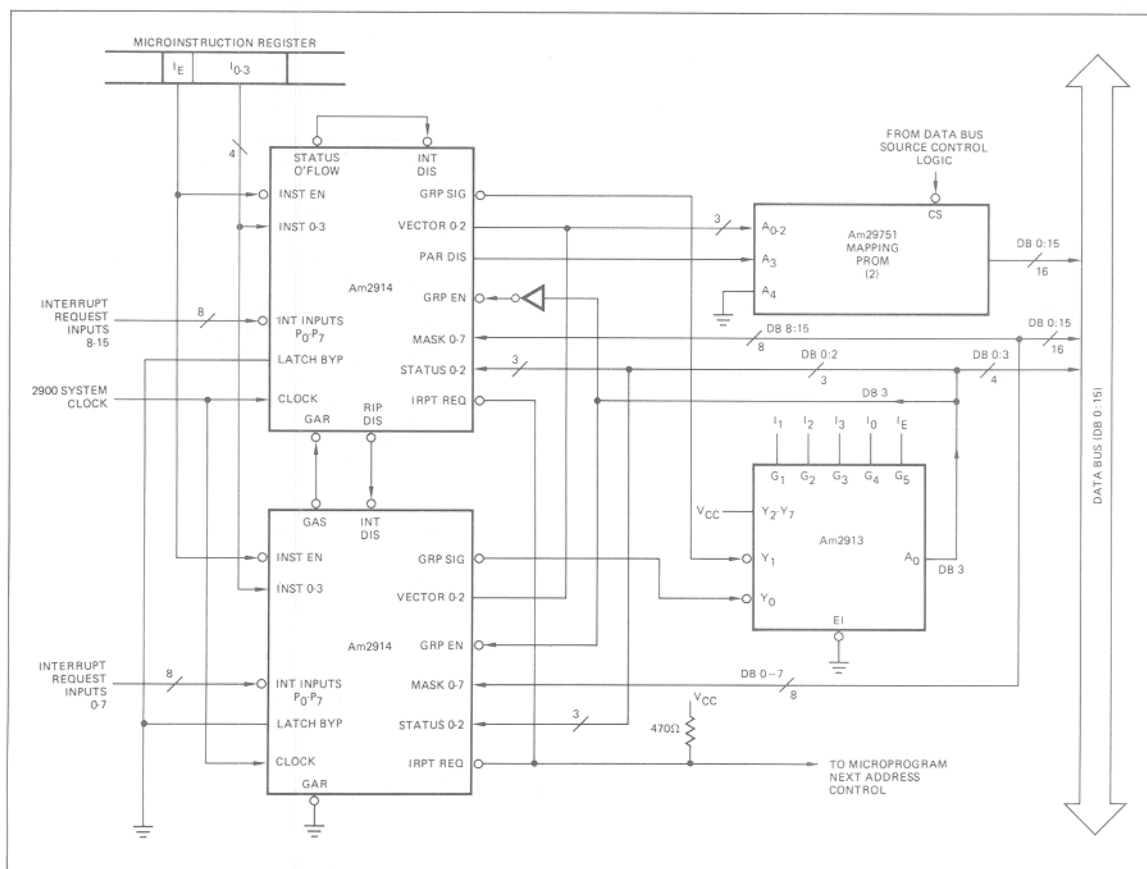


Figure 22. 16 Level Interrupt Control Unit for Am2900 System.

In Figures 21 and 22, the Status and Mask inputs/outputs are connected to the data bus in a bi-directional configuration so that Status and Mask Registers may be loaded from or read to the data bus with appropriate Am2914 instructions. This gives the designer two possibilities which could be very advantageous.

Number one is the ability to store the Status and Mask information on a stack in memory. This is very advantageous when doing nested interrupts. Secondly, it allows the designer to construct machine instruction that can modify these two registers. This is very important to the system programmer who is involved in writing software to manage the interrupts.

For the eight level ICU of Figure 21, the Status Overflow output is connected to the Interrupt Disable input, and the Group Advance Receive and Group Enable inputs are connected to ground, as previously described.

For the 16 interrupt level ICU of Figure 22, the Parallel Disable output of the higher priority group serves as the high order vector bit. An Am2913 Priority Interrupt Expander is gated by the Am2914 instruction lines so that its output is enabled only during a Read Status instruction, and is used to encode the high order bit of the status. An inverter suffices to decode the high order bit of the status bit during a Load Status instruction. As described previously for a ripple cascade system, the Group Advance Receive input of the next higher priority group; the Ripple Disable output is connected to the Interrupt Disable input of the next lower priority group; the Status Overflow output of the highest priority group is connected to the Interrupt Disable input of the same group, and the Group Advance Receive input of the lowest priority group is connected to ground.

In both designs, two Am29751 32-word by 8-bit PROM's with three-state outputs are used to map the Am2914 Vector outputs into a 16-bit address vector. The PROM outputs are connected to the data bus. When a Read Vector Instruction (Am2914) is executed, the address vector is available to be used either as the address of the next instruction or a location to find the address of the next instruction to execute.

Figure 23 shows a design where the address vector from the mapping PROM can be clocked into a register in the Am2903's. The registers in the Am2903's would be split between general purpose, scratch, stack pointers and Program Counter registers.

The address vector also may be gated directly to the "D" inputs of the Am2911 Microprogram Sequencer as shown in Figure 24, and used as the start PROM address of a microinstruction interrupt service routine. This method would be most useful in a controller application. This method would trade faster service for a bigger microprogram that accommodates all the code to service each individual interrupt.

FIRMWARE EXAMPLE FOR Am2914 INTERRUPT SYSTEM

The software for handling interrupt requests is on two levels. The first level to come into play is the microprogram level. This is the level at which the request is recognized and the program counter is manipulated to start execution of a machine level interrupt service routine which is the second level. When the machine level interrupt service routine is finished, some form of a Return Interrupt instruction is executed. The microcode for the return instruction manipulates the program counter so that execution of the current machine program previous to the request is restored as shown in Figure 25.

This example is concerned with the microprogram level. This microcode goes along with the hardware shown in Figure 23. In this example the code is shown in the form of Flow Charts be-

cause the actual microprogram format will vary from machine to machine.

The important features to notice that have a direct relevance to the firmware are the Latch Bypass and where the Mask, Status and Vector busses go. For this example, the Latch Bypass is LOW making the Interrupt Latches latch up on a negative going pulse. The Mask and Status busses go to the data bus allowing the Status and Mask data to be transferred to and from memory. The Vector bus passes through a mapping PROM to the data bus where it can be read into the Program Counter contained in the Am2903's. The PROM contains addresses of service routines which correspond to the different interrupt levels.

Another relevant fact, important to understanding the firmware is that the interrupt mechanism is limited to handle interrupts on the machine level.

As shown in Figure 26a, the first thing that happens in the fetch routine (written in microcode) is a conditional subroutine call that will be taken if an interrupt request is present. This happens before the current machine instruction is fetched and the program counter is incremented.

In the Interrupt routine (shown in Figure 26b) a microprogram subroutine is first called to push the program counter onto the system stack. This is done so that the program counter can be restored in order to resume execution of the machine program after the interrupt service routine is done. The next thing that is saved on the system stack is the contents of the Am2914 Status Register. This is done because the status register which contains the priority level that would be serviced prior to the interrupt, will be restored after the interrupt is serviced. This maintains a nested interrupt structure (fence).


After saving the program counter and status register, the vector is read out of the Am2914 through the mapping PROM to obtain the address of the machine interrupt service routine. The address is then read into the program counter which resides in the Am2903's. When the Vector is read, the interrupt request priority plus one is automatically put into the status register by the Am2914 so that all interrupt requests of lower priority than the one being serviced are ignored. This is often referred to as moving the fence up. Since the vector has been read and the new address is in the program counter, the interrupt request can be cleared from the interrupt register via the Clear Interrupt/Last Vector Read instruction. At this point a jump is made to the Fetch routine which will now fetch the first instruction of the machine Interrupt Service routine.

The last instruction that the machine level interrupt service executes is an Interrupt Return. This will in turn call Return Interrupt microprogram. The status is first popped off the system stack and loaded back into the status register. This restores the Interrupt Fence. The program counter is then popped off the system stack and loaded into the program counter register. This restores the program counter to point to the instruction that was going to be executed when the interrupt request occurred.

TIME DELAY WHEN USING THE Am2914

An aspect that should be covered when using any part is how it will fit into the system timing; because the cycle time of the system will be as long as the longest delay path in the machine. Shown in Figure 27 is the longest delay path through the Am2914 for the previous 16-bit computer example. The calculations were using both typical and worst case values at 25°C and 5.0V.

The longest delay path for the system where the vector from the mapping PROM feeds into the "D" inputs of the Am2910 is

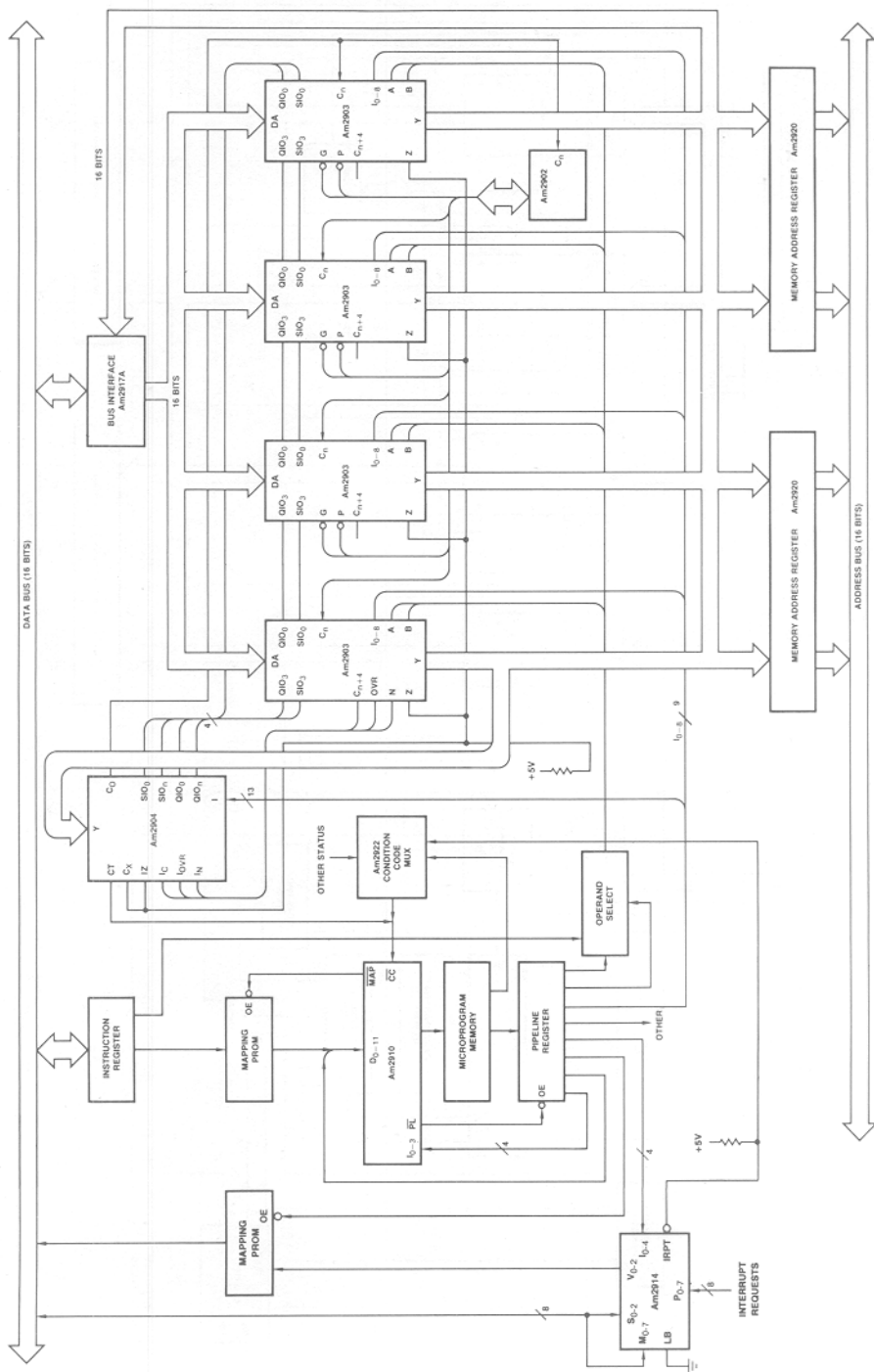

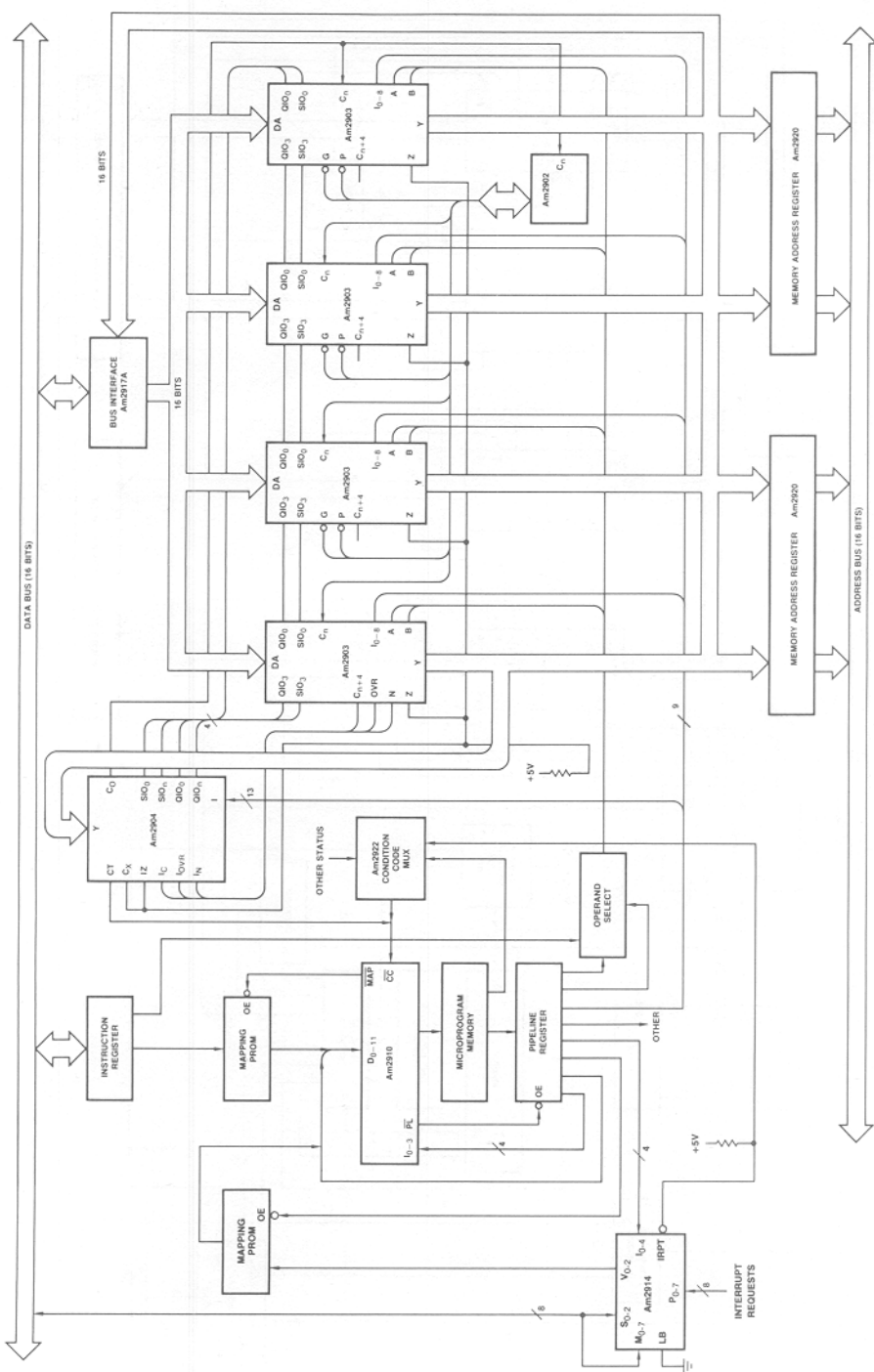


Figure 24.

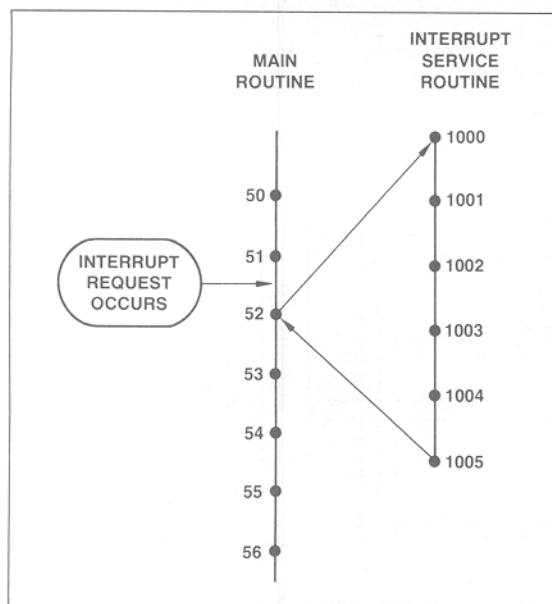


Figure 25. Machine Level Instruction Flow During Interrupt Request.

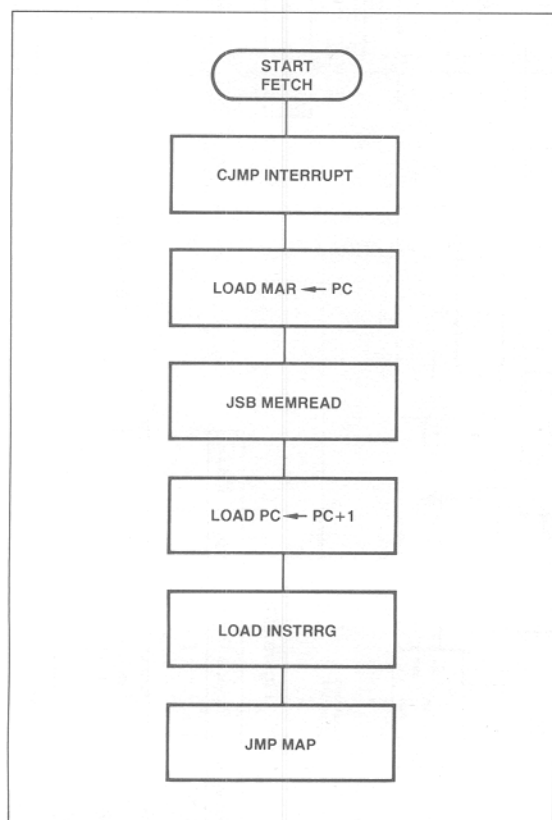


Figure 26a. Flow Chart for a Simplified Microprogram Fetch Routine.

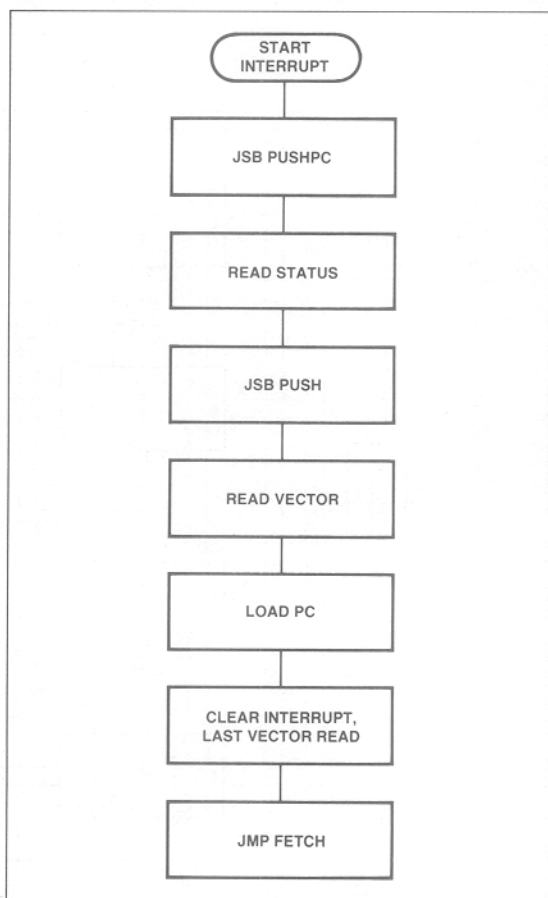


Figure 26b. Call Interrupt Service Routine Microprogram Flow Chart.


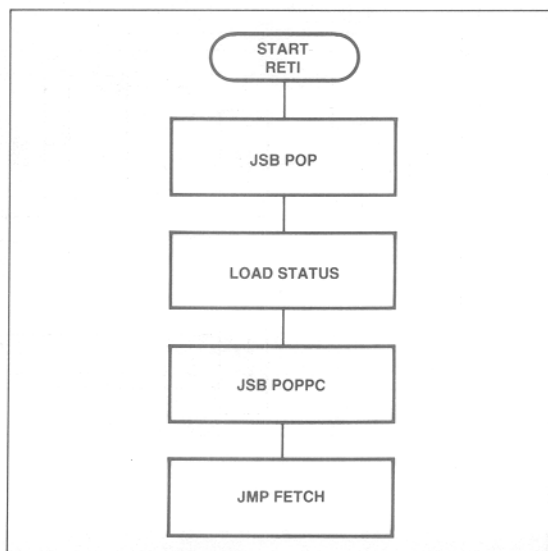


Figure 26c. Return Interrupt Microprogram Flow Chart.

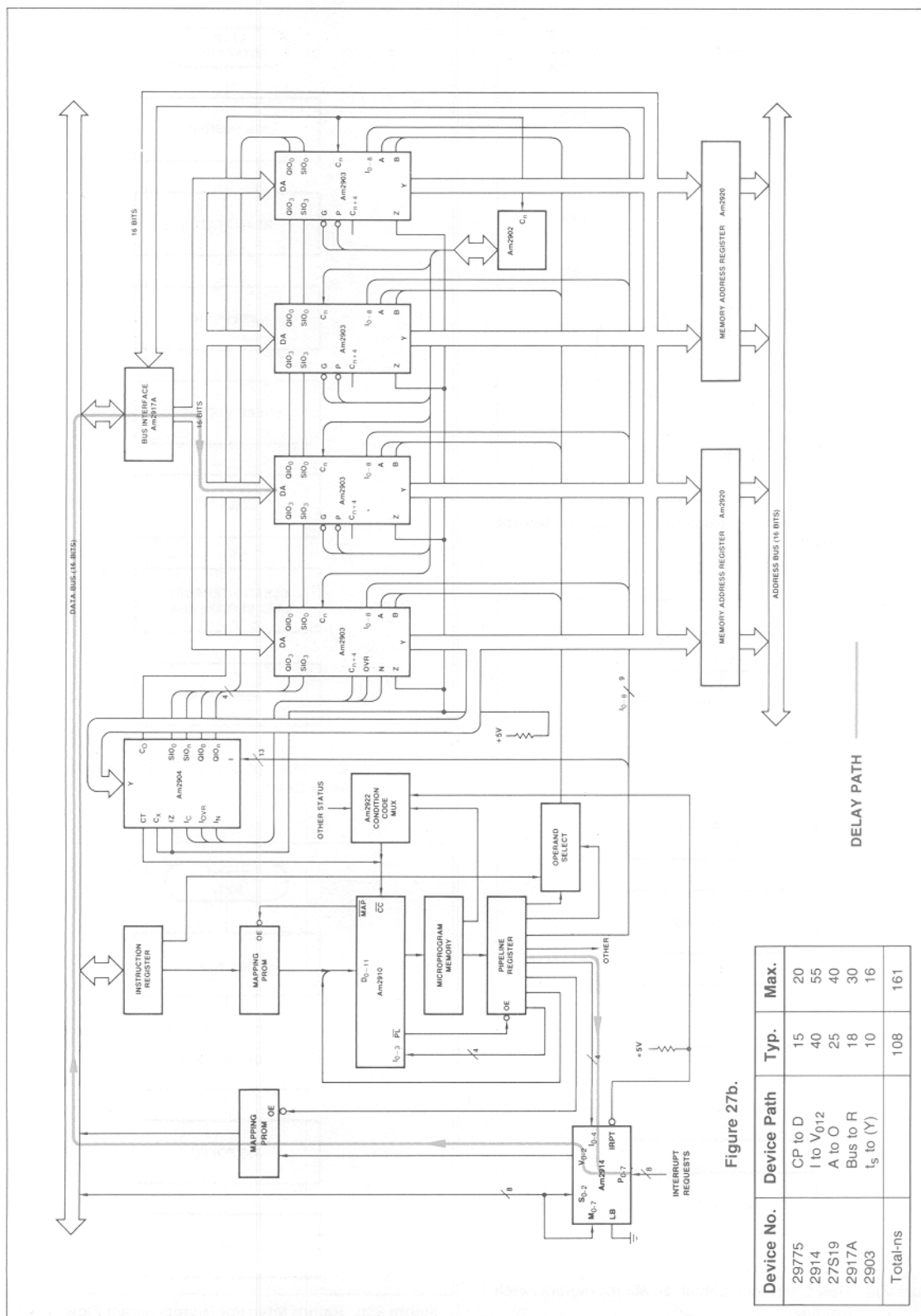

Device No.	Device Path	Typ.	Max.
29775	CP to D	15	20
2914	I to V ₀₁₂	40	55
27S19	A to O	25	40
2917A	Bus to R	18	30
2903	t _s to (Y)	10	16
Total-ns		108	161



Figure 28c.

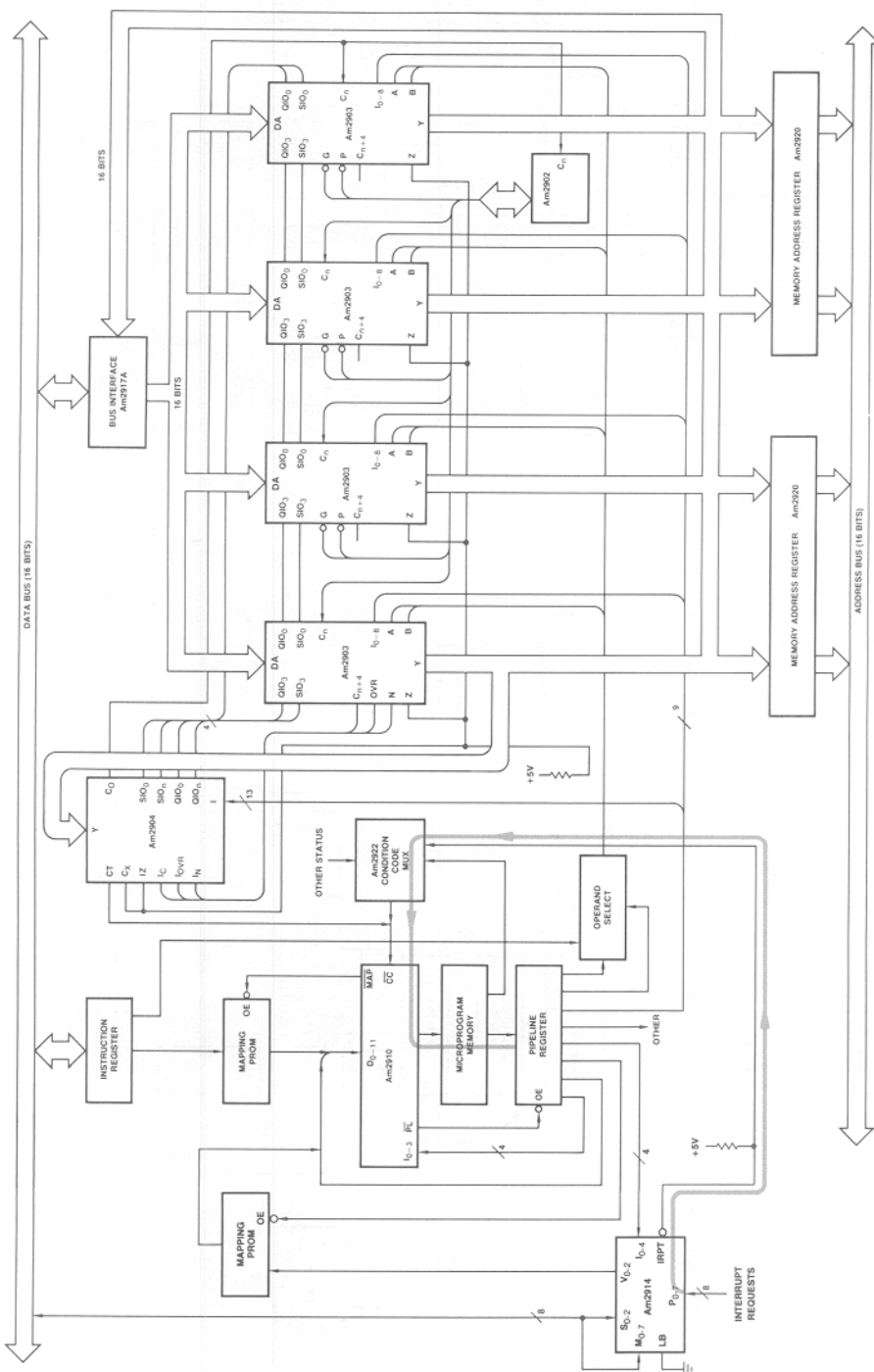




Figure 28e.

Device No.	Device Path	Typ.	Max.
29775	CP to D	15	20
2914	I to V	40	55
2918	t_s (Data)	5	5
Cycle n Total-ns		60	80
2918	CP to Q	8.5	13
27S19	A to O	25	40
2910	D to Y	14	22
29775	t_s (A)	40	50
Cycle n+1 Total-ns		97.5	125

Figure 28f.

Device No.	Device Path	Typ.	Max.
2914	CP to IRQ	65	82
2922	D_n to Y	13	19
2910	\overline{CC} to Y	27	44
29775	t_s (A)	40	50
Total-ns		145	195

Figure 28g.

Device No.	Device Path	Typ.	Max.
2914	CP to IRQ	65	82
74S74	t_s (Data)	3	3
Cycle n Total-ns		68	85
74S74	CP to Q	6	9
2922	D_n to Y	13	19
2910	\overline{CC} to Y	27	44
29775	t_s (A)	40	50
Cycle n+1 Total-ns		86	122

Figure 28h.

shown in Figure 28. This path is much longer because of the two PROM's that have to be accessed. Therefore, there may be a trade-off of slightly longer system cycle time for faster service of interrupts via service routines in microcode.

For some systems the delay time shown in Figure 28b may be too long. Therefore, the designer can split the delay time into parts by putting a register between the Am2914 and the mapping PROM as shown in Figure 28c. When done in two system clock cycles, the delay time will be as shown in Figure 28f.

Figure 28d shows the delay path from the Interrupt Request Register through the Condition Code MUX to the Am2910. The time calculations are shown in Figure 28g. Again, for some systems, this path may be too long. Therefore, as shown above, this path may be broken in two, which is shown in Figure 28e. This will result in two system clock cycles. The delay involved in each cycle is shown in Figure 28h.

ANOTHER EXAMPLE OF Am2900 SYSTEM USING THE Am2914

As shown in Figure 29, this example varies in the way that the interrupt request is recognized by the microprogrammed

machine. In this example the interrupt request line for the Am2914 enables or disables the \overline{MAP} signal going to the mapping PROM. When an interrupt request is present and a Jump Map instruction is executed, the output of the mapping PROM remains tri-stated; and the bus connected to the "D" inputs of the Am2910 is HIGH because of the pull-up resistors. Therefore, the microprogram will start executing at the highest location in microprogram memory when an interrupt request is present. At this location a Jump Instruction to the microprogram interrupt service routine could be placed. The microcode is written so that the only time a Jump Map instruction is executed is at the end of the Fetch microprogram routine as shown in Figure 30a.

In the previous example the interrupt request was recognized before the program counter is incremented after which the Jump Map instruction is executed. When the Jump Map is executed, either the instruction is executed or an interrupt request is serviced. Therefore, when the Return Interrupt machine instruction is executed, the program counter needs to be backed up via microcode, as shown in Figure 30b, in order to refetch the machine instruction which was lost. This also dictates that the program counter have a path to an incrementer/decrementer or ALU, which in this example is handled by putting the program counter in the Am2903's.

MICROPROGRAM LEVEL INTERRUPT EXAMPLE

Some high-speed control applications require extremely fast interrupt response. While it may ordinarily be desirable to complete an entire processing sequence (such as executing a microprogram for a macroinstruction) prior to testing for the interrupt and allowing it to occur, it is not always possible to achieve the required interrupt response time desired. If this is the case, microinstruction level interrupt handling must be employed. The technique described below has a maximum latency of three microcycles which can be 450-600ns total. Implementation is straightforward using the Am2910 Microsequencer, a 40-pin LSI device that can control 4096 words of microprogram at a 150ns cycle time, and a few extra MSI and SSI packages. In this application, the Am2910 is configured in its standard architecture. The additional logic does not influence the normal system cycle time.

If microlevel interrupt handling is to be employed, logic must be provided to generate a substitute microprogram address corresponding to the location of the interrupt service routine. In the event of a microlevel interrupt, the sequencer address outputs are tri-stated and the substitute address is placed on the microprogram address bus, causing the next microinstruction fetch to be determined by the interrupt control vector generator. While this is happening, steps must be taken with the Am2910 to insure that the interrupted routine can be properly restored. To understand this procedure, it will be necessary to examine the Am2910 in more detail.

Referring to Figure 31, the microprogram address bus is driven by the Y outputs of the Am2910 through a tri-state buffer than can be disabled by means of the \overline{OE} input. The address is selected in a multiplexer from a direct input, from a register/counter, from a push/pop stack, or from a microprogram counter register. The microprogram counter register is commonly used as the address source when executing the next microinstruction in sequence. Whenever an address appears at the multiplexer outputs, it is incremented and presented to the microprogram counters inputs. At the rising edge of the clock, this new address that is current address-plus-1 is loaded into the microprogram counter and a microprogram access begins at this address.

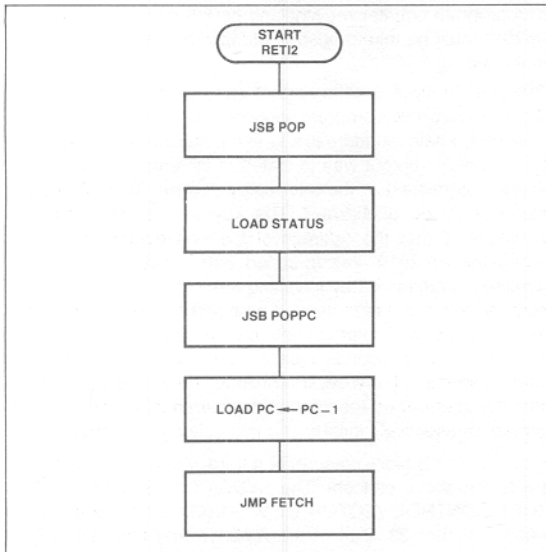


Figure 30a. Return Interrupt Microprogram for Second Example.

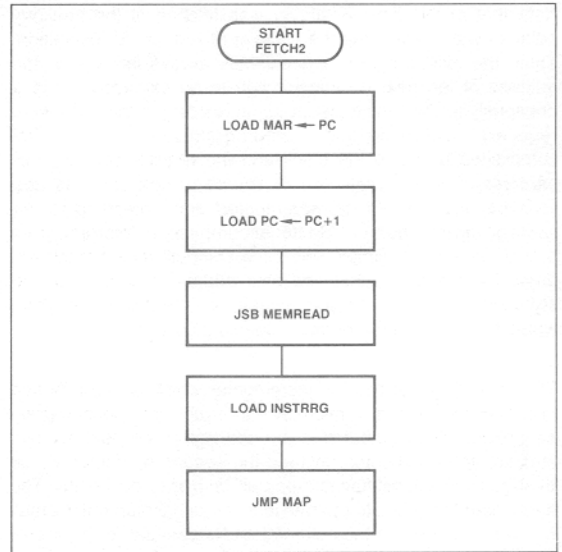


Figure 30b. Fetch Microprogram for the Second Example.

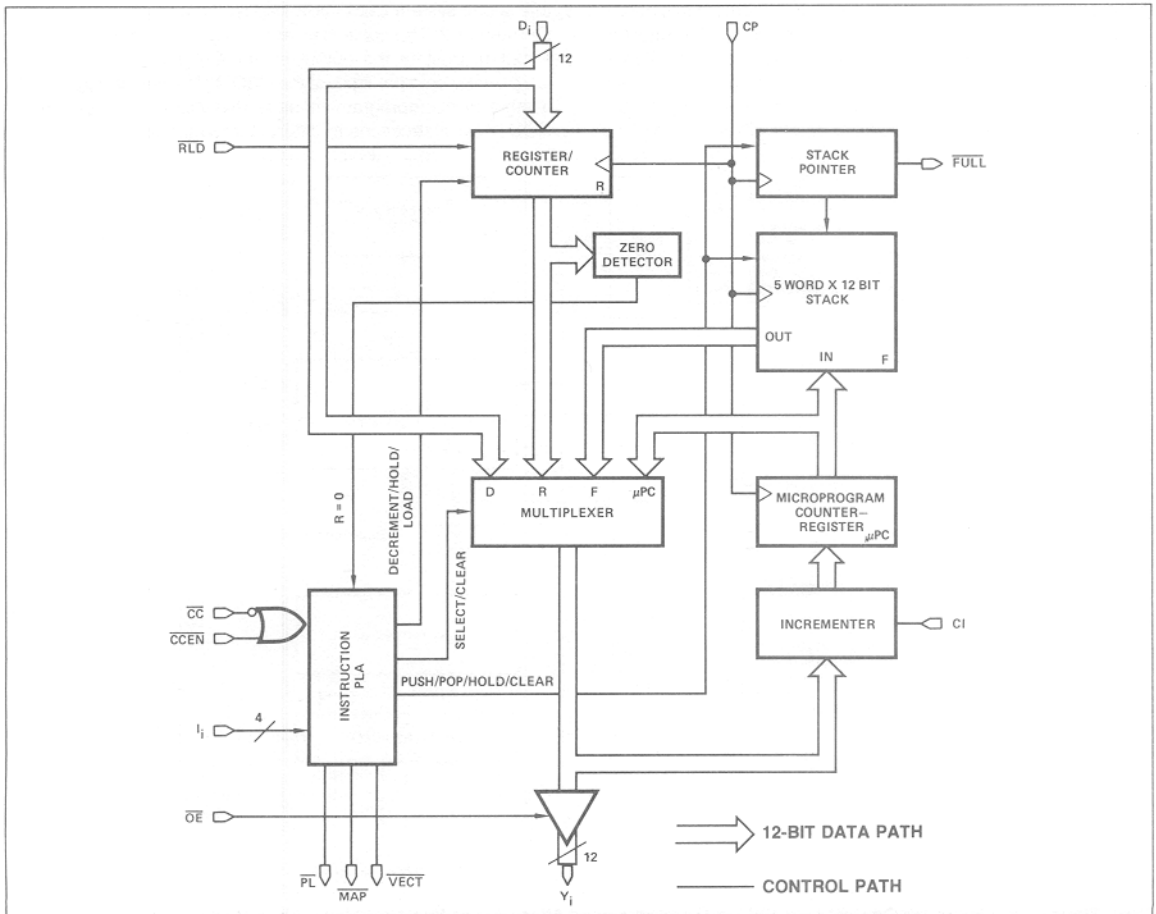


Figure 31. Am2910 Block Diagram.

Note that at this time, whatever was fetched at the previous address was loaded into the microword register for execution. Thus, the microprogram sequencer is always looking for the address of the next microinstruction to be executed (while a previously fetched microinstruction is residing in the microword register). Subroutine and microprogram loops may be accomplished by using the stack and the register counter. *Regardless of what is selected as source of next address, the selected address will be incremented and presented to the microprogram counter.* So to accomplish a microprogram branch, one would simply select the D inputs for a branch address for one cycle, then the next address source could be switched back to the program counter on the next cycle which would then contain the branch address plus 1.

This is a carry input to the incrementer which is normally tied HIGH. In the case of a microlevel interrupt, the microprogram sequencer will not determine the address of the next microinstruction to be executed. Instead the sequencer output will be tri-stated and a substitute address will be placed on the bus. The sequencer continues to operate in a normal fashion with its multiplexer output being incremented and presented to the microprogram counter register. It must now be noted that the instruction located at the address then coming out of the multiplexer outputs *will not be executed* but rather the next microinstruction to be executed will be determined by the interrupt vector generator. It would therefore, be wrong to increment this microprogram address but rather it must be saved intact in order to push it onto the stack for access during interrupt return. This is easily accomplished in the Am2910 by grounding the carry input to the incrementer simultaneously with three-stating the sequencer output. Then the multiplexer output will be stored in the

microprogram counter register and on the next microcycle the Am2910 must be told to push in order to preserve this address on the stack.

This carry-in input is all important and exists on all Advanced Micro Devices' microprogram sequencers. Unless the carry-in is grounded, whatever address was in the multiplexer output when the sequencer output was tri-stated is incremented and an instruction is missed in the interrupted routine. This, of course, would likely be disastrous. The key to this microinterrupt technique is that the address of the unexecuted instruction (when the Am2910 was tri-stated and a substitute address supplied) is preserved by inhibiting the increment via the carry input, so the address is passed on intact to the microprogram counter. If the microinterrupt is to be more than one cycle long, the microprogram counter must be pushed so as to save the return address. Otherwise, a "continue" may be used to return from the interrupt on the very next cycle. In this event the microinterrupt effectively inserts one instruction in the stream.

Figure 32 is the block diagram of a hardware design that implements the above concept. The SYNC/CONTROL and INTERRUPT CONTROL/VECTOR GENERATOR logic are shown in detail in Figure 33. Part of the Am2918 and both 'LS74 Flip-Flops are used to synchronize the recognition of the asynchronous interrupt request as shown in Figure 34. The interrupt request arrives at the interrupt input. On the next clock cycle it is clocked into the Am2918. In the following clock cycle a pulse that is one system clock cycle long is put out by the flip-flop pair FF1 and FF2. The pulse is used to disable the carry input of the Am2910, tri-state the output of the Am2910, and enable the jump vector onto the input of the PROM. The vector indexes into a table in microprogram memory that contains "JUMP SUB-ROUTINE" instructions to different interrupt service routines.

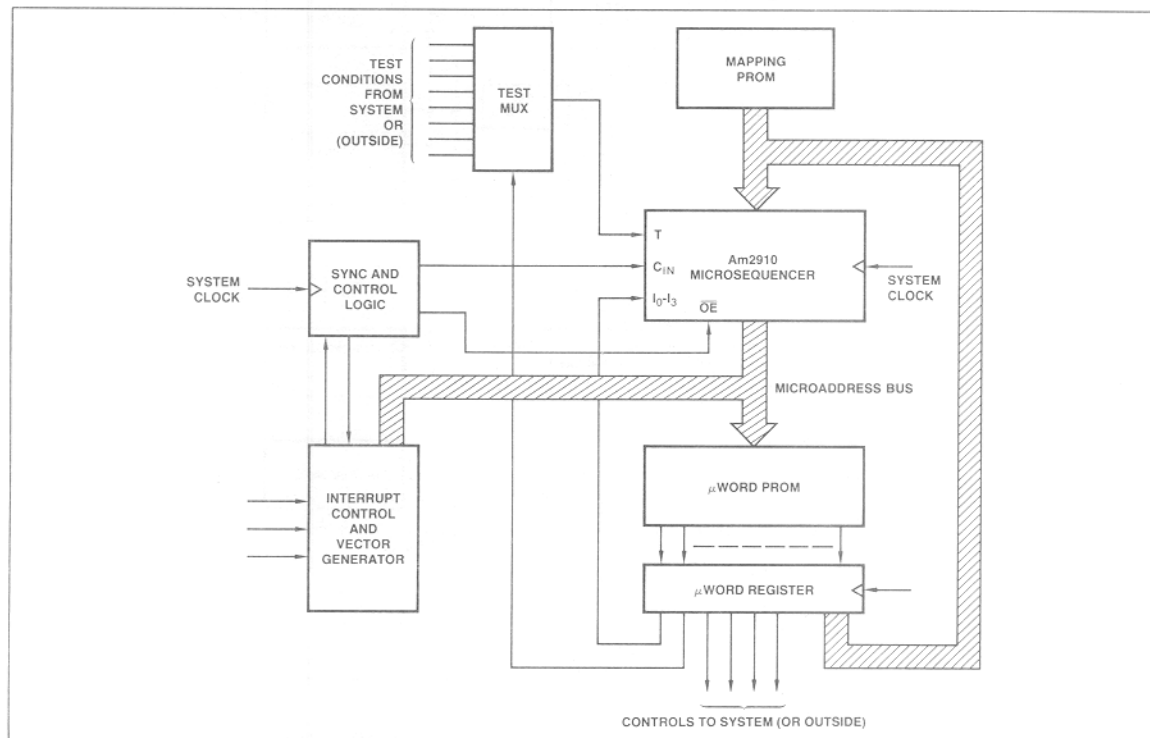


Figure 32. Computer Control Unit Set-up for High-Speed Micro-Level Interrupt Handling. Latency is a Maximum of Two Microcycles (i.e., about 300 to 500ns).

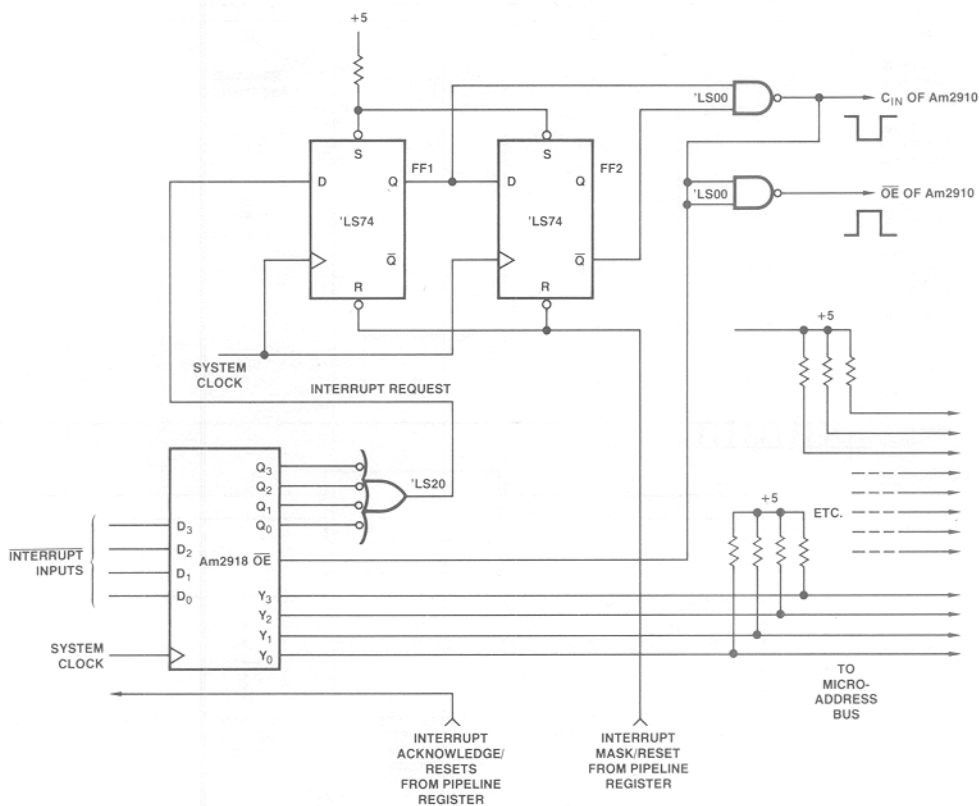


Figure 33. Example of Sync Control Logic and Vector Generator.

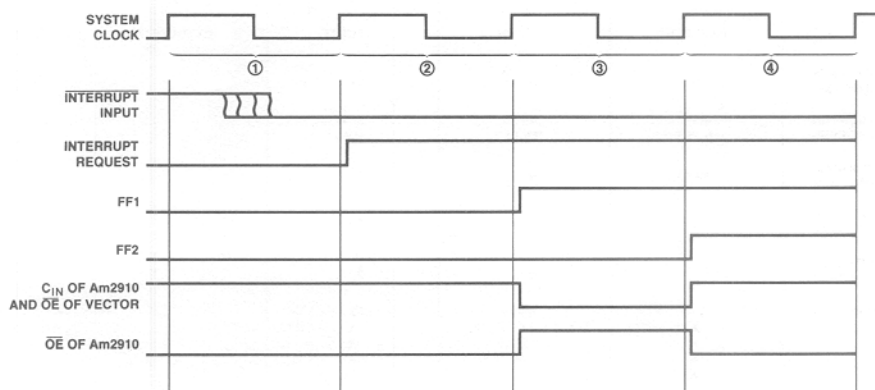


Figure 34. Timing of Vector Generator and Sync Control Logic.

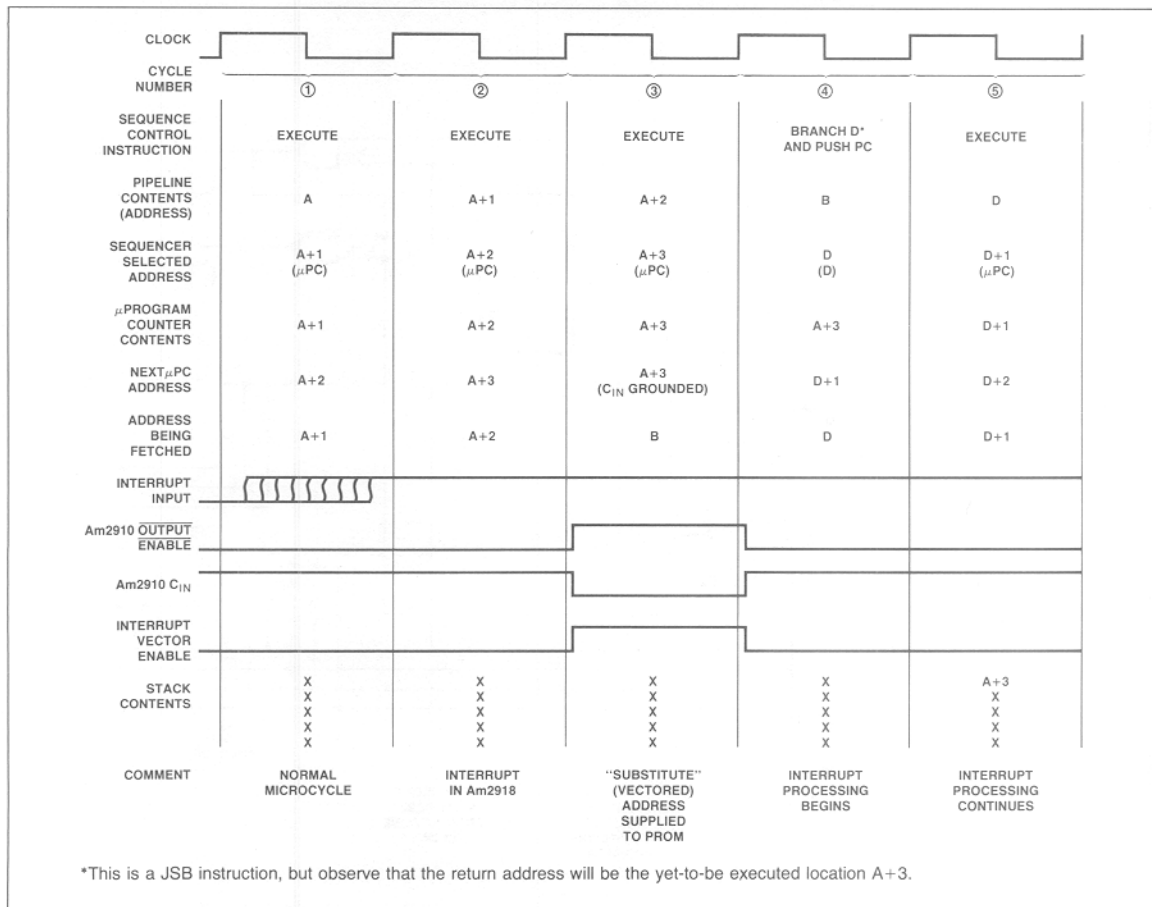


Figure 35. Interrupt Sequence Timing.

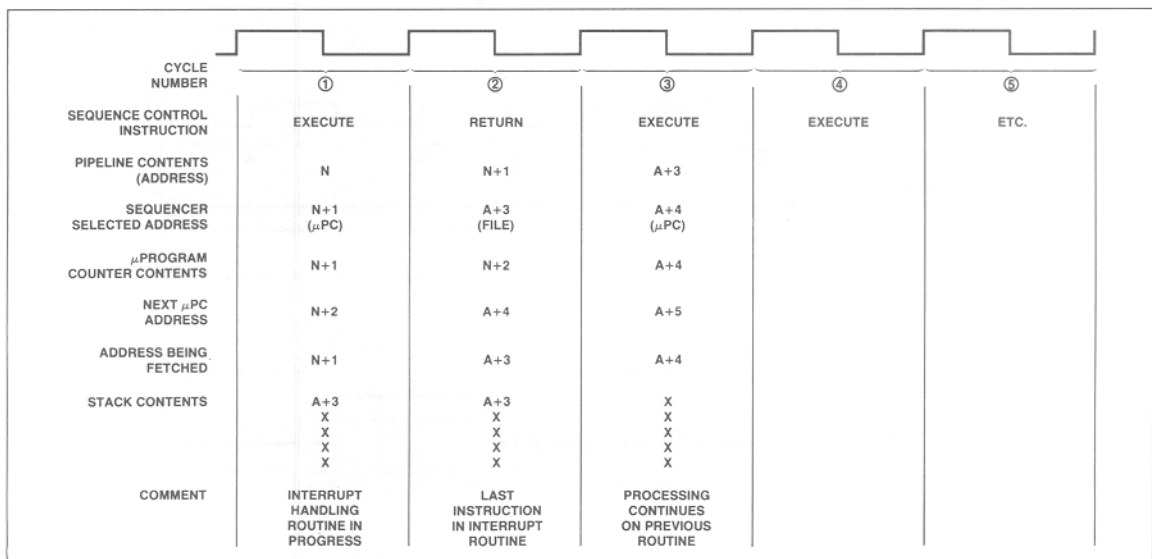


Figure 36. Return-From-Interrupt Sequence Timing.

Figure 35 shows how the interrupt sequence timing fits into the normal flow of microprogram address in the Am2910. Note how the stack is used. This demonstrates the need for always reserving room on the stack to allow for interrupts. This applies to any room that the interrupt service routine may require as well as the return address. This limitation may require that only one interrupt request be serviced at a time.

Figure 36 shows how the return from the interrupt service routine fits into the microprogram flow. Notice that a Return instruction is used to accomplish this.

SUMMARY

In this chapter, Interrupts were discussed beginning with a definition of the Interrupt Mechanism and proceeding to a classification of different interrupts and how they are handled. A dis-

cussion of the concepts that go into designing the "Universal Interrupt" hardware was given which culminated with the Am2914. The chapter ends with several Interrupt Mechanism applications using the Am2914 and Am2910.

In this chapter it was shown how interrupts can be handled using parts from the Am2900 family. Because of their hardware modularity and universal architecture, they may be used in a variety of applications. Since the Am2900 Family parts are microprogrammable, they allow the user's system to grow with time as system requirements change. Together these attributes make the Am2900 Family the flexible cost effective family that it is.



**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
Sunnyvale

California 94086


(408) 732-2400

TWX: 910-339-9280

TELEX: 34-6306

TOLL FREE

(800) 538-8450

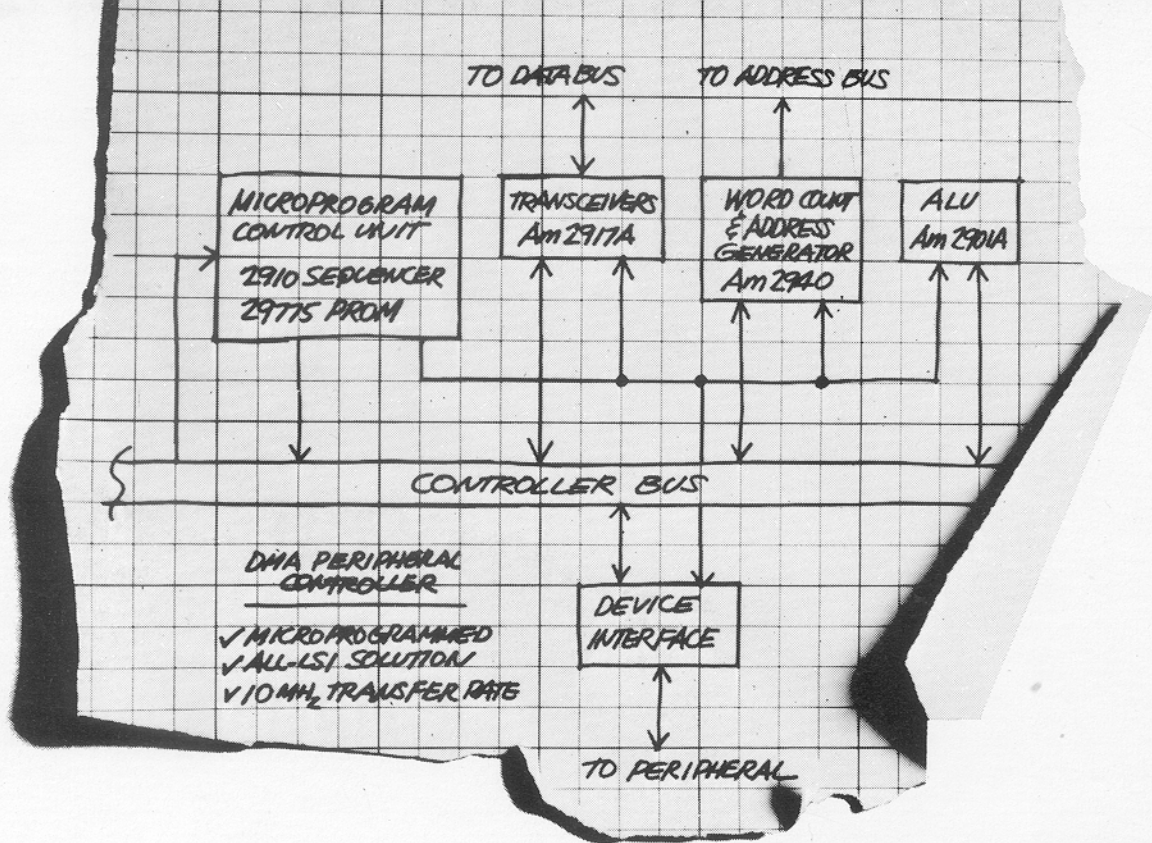

Build A Microcomputer

Chapter VII Direct Memory Access

Advanced Micro Devices





Advanced Micro Devices

Build A Microcomputer

Chapter VII Direct Memory Access

Copyright © 1978 by Advanced Micro Devices, Inc.

Advanced Micro Devices cannot assume responsibility for use of any circuitry described other than circuitry entirely embodied in an Advanced Micro Devices' product.

AM-PUB073-7

Introduction

The transfer of data between the microcomputer and the peripheral devices is generally referred to as Input/Output (I/O). What is desired is a high speed technique of transferring data between the peripherals and the memory. Generally speaking, there is a minimum of three types of I/O. These are, Programmed I/O, Memory Mapped I/O and Direct Memory Access I/O. All of these schemes are common in today's currently available minicomputers. A basic understanding of these I/O techniques is helpful in fully comprehending DMA. The first two of these types of I/O can be interrupt driven. That is, programmed I/O or memory mapped I/O can be initiated by an interrupt from the peripheral device.

Programmed I/O

In this type of I/O, all operations are controlled by the CPU program. In other words, the peripheral device performs the functions of inputting or outputting data as it is controlled by the CPU. Normally, the machine will include a set of I/O instructions which are used to transfer data to or from the peripheral devices via an Input/Output port. All data for the peripheral devices passes through these I/O ports to the CPU and the resources of the CPU must be utilized in order to effect an I/O transfer. Figure 1 shows the Block Diagram of a programmed I/O system used in a typical microcomputer. Figure 2 shows an example of that portion of the program used to output data to the peripheral device.

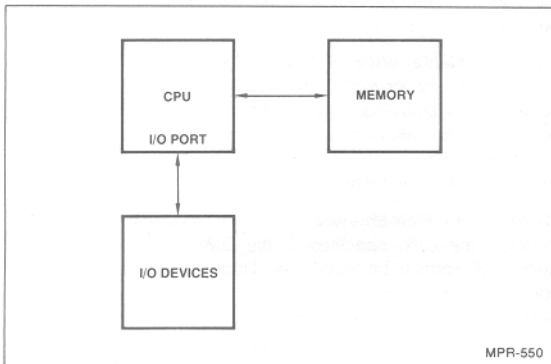


Figure 1. Programmed I/O System.

CPU Program	Comments
—	—
—	—
Load R, M	Load CPU Register R with the Contents of Memory Address M
Out D, R	Transfer the Contents of CPU Register R to I/O Device D via the I/O port.
—	—

Figure 2. Example Output Program — Programmed I/O.

Programmed I/O is simple to implement and does not require the utilization of any memory addresses for its realization. In addition, special instructions are available to the programmer to execute the peripheral data transfers. Programmed I/O is also low cost relative to other types of I/O; however, it has the following disadvantages. Since I/O device operation is asynchronous with re-

spect to CPU operation, the CPU has no way of knowing when a peripheral device is ready to transfer data and must periodically poll the device to determine its readiness. This results in an inefficient I/O transfer. Also, since the CPU must be used to effect the I/O transfer, the CPU resources are tied up during the time of transfer and the time of polling and cannot be used for other tasks. For these reasons, Programmed I/O is generally limited to use with low speed devices.

Perhaps, one of the best known programmed I/O microcomputers in the industry today is the Am9080A. This device features two instructions for either inputting data or outputting data to any one of 256 Input/Output ports.

Memory Mapped I/O

Memory Mapped I/O is a technique whereby the transfer of data to and from peripheral devices is accomplished by using some of the normally available memory space. In this technique, memory addresses are decoded within the peripheral devices and are thus used to determine when a specific device is being addressed. Usually, each type of function within the peripheral device is assigned a memory address and can then be accessed by the CPU. For example, the peripheral device may contain a command register, a status register, a data in register and a data out register. Thus, four memory addresses might be utilized in performing I/O to this peripheral. Figure 1 is also the block diagram for a Memory Mapped I/O scheme.

The chief advantage of Memory Mapped I/O is that all of the memory reference instructions are usually available to perform the I/O function. Consequently, no special I/O instructions are required in the machine. The key disadvantage of this technique is that a block of the memory addressing range must be set aside for assignment to the peripheral devices. Thus, the overall memory addressing range of the machine is reduced by the size of this block. Again, the resources of the CPU are tied up while the I/O is being performed. A well known machine using only Memory Mapped I/O is the PDP 11. In it the upper 4k of memory space is usually used for the I/O devices.

Interrupt Driven I/O

Interrupts are means by which a peripheral device can stop the normal flow of the CPU instruction execution and force the CPU to temporarily suspend its current program. Then, the program "jumps" to a different program which executes an I/O transfer. Typically, this eliminates the need for polling the peripheral devices to determine if an I/O transfer is ready. Thus, the interrupt driven scheme provides a more efficient I/O transfer technique. However, there is an overhead burden associated with interrupts in that the CPU must store away and later restore all of the parameters required to resume the interrupted program. This overhead degrades the CPU performance. Depending on the overall interrupt structure, the CPU still may have to do some polling of devices which may be tied to the same interrupt level.

It should be pointed out that both Programmed I/O and Memory Mapped can take advantage of the interrupt technique. That is, an interrupt can be used to initiate the peripheral data transfer in either type of system. The CPU still must control the transfer of the data between the memory and the peripheral device and the CPU resources are unavailable for executing other instructions during this time.

What is DMA?

DMA is a technique for data transfer which provides a direct path between the I/O device and the memory without CPU intervention. With this path, a peripheral device has "Direct Memory Access" and can transfer data directly to or from the memory. The

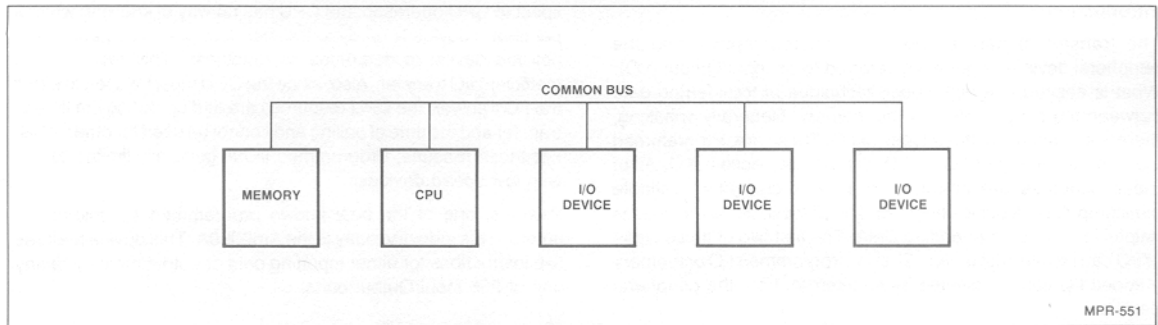


Figure 3. DMA I/O System.

purpose of the DMA is to relieve the CPU of the task of controlling the I/O transfer, thereby freeing it to perform other tasks during this time, and to provide a means by which data can be transferred between an I/O device and memory at very high speed. Figure 3 shows the Block Diagram of a system where several I/O devices can perform DMA transfers into memory. Note that the CPU and peripheral devices share a common bus to the memory and that the CPU and peripheral devices cannot access memory during the same cycle. DMA can also be designed to perform memory-to-memory transfers or I/O-to-I/O transfers.

Several DMA transfer methods exist, such as the CPU halt method, the memory timeslice method, and the "cycle steal" method. In the CPU halt method, the CPU is halted and switched off the bus while a DMA transfer occurs. This is the most straightforward method. However, it takes a relatively long time to switch the CPU on and off the bus, and the CPU cannot do anything during the transfer.

The memory timeslice method works by splitting each memory cycle into two timeslots; one is reserved for the CPU and the other for DMA. This method provides the highest CPU execution rate as well as the highest DMA transfer rate because both the CPU and DMA are guaranteed access to memory during every memory cycle. The disadvantage of this method is that high speed, costly memories must be used.

The "cycle steal" method is a cost/performance compromise between the low cost of the CPU halt method and the high performance of the memory timeslice method. Cycle stealing refers to a DMA device "stealing" a CPU memory cycle in order to execute a DMA transfer. CPU program execution continues during the DMA transfer (the CPU is not halted), resulting in an overlap of CPU program execution with DMA transfer. If the CPU and a DMA device require a memory cycle at the same time, priority is granted to the DMA device and the CPU waits until the DMA cycle is completed. DMA causes CPU performance degradation only in those applications where the CPU uses the entire memory bandwidth. In many applications the CPU is slow relative to memory cycle time and "cycle stealing" provides satisfactory performance at relatively low cost.

How is DMA Implemented?

In order to relieve the CPU of the I/O transfer control task, circuitry external to the CPU must be added. This circuitry is called the DMA Controller and performs the following functions.

Address Line Control – In a DMA system, the memory address lines are driven by either the CPU or a DMA device, depending on which is using the memory during a given cycle. The DMA controller must switch the appropriate address onto the memory address lines.

Data Transfer Control – The DMA Controller must provide the control signals required to transfer data directly between memory and an I/O device. As with the address lines, these control signals must be switched onto and off of the memory control lines appropriately.

Address Maintenance – Just as the CPU has the program counter and one or more other registers for memory address pointers, the DMA controller must also maintain an address pointer that indicates where the next word of data will be read or written in memory. This pointer must be incremented or decremented after each word transfer.

Word Count Maintenance – At the initialization of a DMA transfer, the CPU specifies to the DMA Controller the total number of words to be transferred. During the transfer, the DMA controller must maintain a count of the number of words that have been transferred and terminate the transfer when the specified number of words has been reached.

Mode Control – Certain aspects of a DMA transfer, such as direction of data flow, method of termination, etc., may vary from one DMA transfer to the next. For this reason, a number of DMA modes may be required. Mode control logic contained in the DMA controller, is set by the CPU at the initialization of a DMA transfer.

A DMA Controller can be placed in each I/O device (Distributed DMA) or DMA control circuitry for a number of I/O devices can be placed in a separate unit (Centralized DMA). The former provides the advantage of incremental cost; DMA control circuitry is added only as I/O devices are added. The latter provides the advantages of consolidation.

At DMA initialization, the CPU normally specifies the mode, the starting memory address and the number of words to be transferred (word count) to the DMA controller. In some applications, it is desirable to repeat a DMA transfer over and over again without disturbing the CPU. This capability is called Repetitive DMA, and can be implemented by adding two registers to the DMA controller. One register saves the starting address and the other the starting word count. This allows the DMA Controller to automatically reinitialize itself after the transfer of the data has been completed, thereby eliminating the need for CPU intervention.

The Am2940 DMA ADDRESS GENERATOR

The design of the Address Line Control, Data Transfer Control and Mode Control circuitry of a DMA Controller is dependent upon system architecture and timing; therefore, it varies considerably from system to system. However, the address maintenance and word count maintenance circuitry is independent of these variables, and is common to almost all DMA Controllers. The Am2940 DMA Address Generator is designed for use in DMA Controllers and provides the Address and Word Count maintenance circuitry that is common to most. It combines the advantages of high speed bipolar LSI with the flexibility and general purpose usefulness of microprogrammed control.

Am2940 GENERAL DESCRIPTION

The Am2940, a 28-pin member of Advanced Micro Devices Am2900 family of Low-Power Schottky bipolar LSI chips, is a high-speed, cascadable, eight-bit wide Direct Memory Access Address Generator slice. Any number of Am2940s can be cascaded to form larger addresses.

The primary function of the device is to generate sequential memory addresses for use in the sequential transfer of data to or from a memory. It also maintains a data word count and generates a DONE signal when a programmable terminal count has been reached. The device is designed for use in peripheral controllers with DMA capability or in any other system which transfers data to or from sequential locations of a memory.

The Am2940 can be programmed to increment or decrement the memory address in any of four control modes, and executes eight different instructions. The initial address and word count are saved internally by the Am2940 so that they can be restored later in order to repeat the data transfer operation.

Am2940 ARCHITECTURE

As shown in the Block Diagram of Figure 4, the Am2940 consists of the following:

- A three-bit Control Register.
- An eight-bit Address Counter with input multiplexer.
- An eight-bit Address Register.
- An eight-bit Word Counter with input multiplexer.
- An eight-bit Word Count Register.
- Transfer complete circuitry.
- An eight-bit wide data multiplexer with three-state output buffers.
- Three-state address output buffers with external output enable control.
- An instruction decoder.

Control Register

Under instruction control, the Control Register can be loaded or read from the bidirectional DATA lines D_0-D_7 . Control Register bits 0 and 1 determine the Am2940 Control Mode, and bit 2 determines whether the Address Counter increments or decrements. Figure 5 defines the Control Register format.

Address Counter

The Address Counter, which provides the current memory address, is an eight-bit, binary, up/down counter with full look-ahead carry generation. The Address Carry Input (\overline{ACI}) and Address Carry Output (\overline{ACO}) allow cascading to accommodate larger addresses. Under instruction control, the Address Counter can be enabled, disabled, and loaded from the DATA inputs, D_0-D_7 , or the Address Register. When enabled and the \overline{ACI} input is LOW, the Address Counter increments/decrements on the LOW to HIGH transition of the CLOCK input, CP. The Address Counter output can be enabled onto the three-state ADDRESS outputs A_0-A_7 under control of the Output Enable input, \overline{OE}_A .

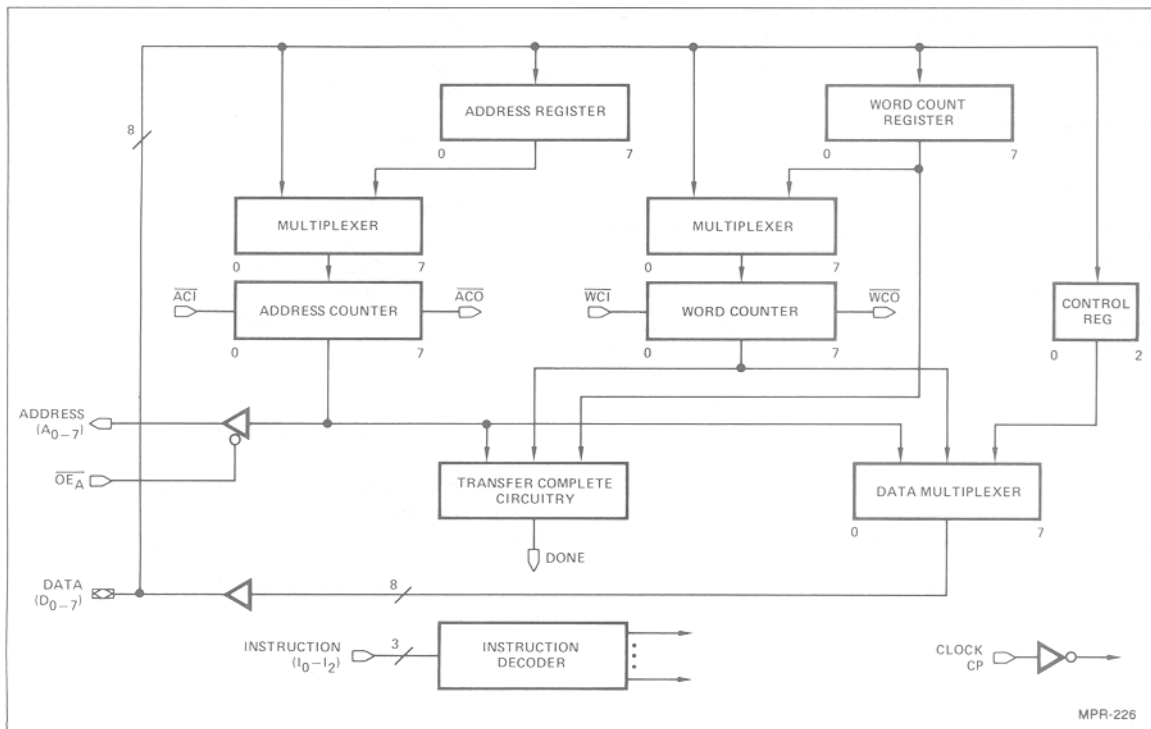


Figure 4. Am2940 DMA Address Generator.

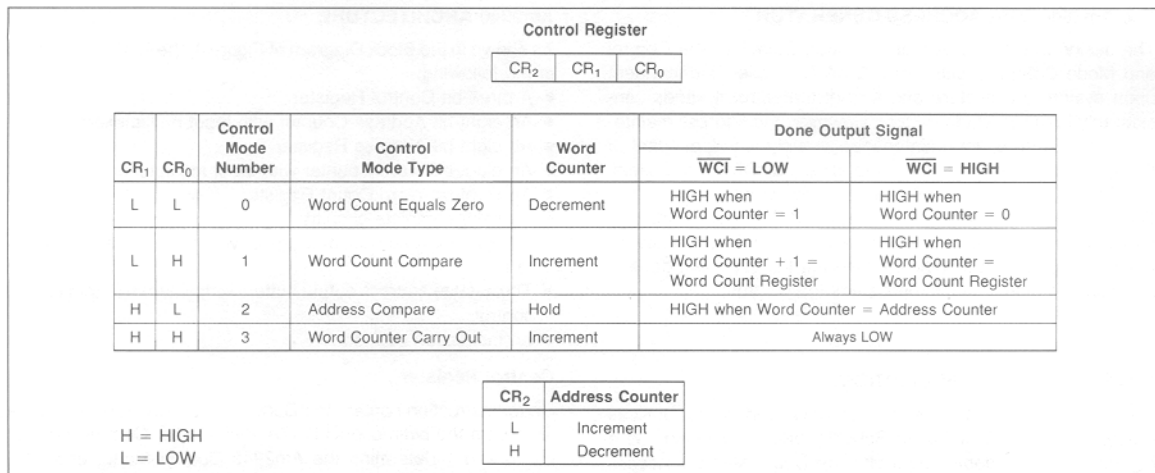


Figure 5. Control Register Format Definition.

Address Register

The eight-bit Address Register saves the initial address so that it can be restored later in order to repeat a transfer operation. When the LOAD ADDRESS instruction is executed, the Address Register and Address Counter are simultaneously loaded from the DATA inputs, D₀-D₇.

Word Counter and Word Count Register

The Word Counter and Word Count Register, which maintain and save a word count, are similar in structure and operation to the Address Counter and Address Register, with the exception that the Word Counter increments in Control Modes 1 and 3, decrements in Control Mode 0, and is disabled in Control Mode 2. The LOAD WORD COUNT instruction simultaneously loads the Word Counter and Word Count Register.

Transfer Complete Circuitry

The Transfer Complete Circuitry is a combinational logic network which detects the completion of the data transfer operation in three Control Modes and generates the DONE output signal. The DONE signal is an open-collector output, which can be dot-anded between chips.

Data Multiplexer

The Data Multiplexer is an eight-bit wide, 3-input multiplexer which allows the Address Counter, Word Counter, and Control Register to be read at the DATA lines, D₀-D₇. The Data Multiplexer and three-state Data output buffers are instruction controlled.

Address Output Buffers

The three-state Address Output Buffers allow the Address Counter output to be enabled onto the ADDRESS lines, A₀-A₇, under external control. When the Output Enable input, \overline{OE}_A , is LOW, the Address output buffers are enabled; when \overline{OE}_A is HIGH, the ADDRESS lines are in the high-impedance state. The address and Data Output Buffers can sink 24mA output current over the commercial operating range.

Instruction Decoder

The Instruction Decoder generates required internal control signals as a function of the INSTRUCTION inputs, I₀-I₂ and Control Register bits 0 and 1.

Clock

The CLOCK input, CP, is used to clock the Address Register, Address Counter, Word Count Register, Word Counter, and Control Register, all on the LOW to HIGH transition of the CP signal.

Am2940 CONTROL MODES

Control Mode 0 — Word Count Equals Zero Mode

In this mode, the LOAD WORD COUNT instruction loads the word count into the Word Count Register and Word Counter. When the Word Counter is enabled and the Word Counter Carry-in, WCI, is LOW, the Word Counter decrements on the LOW to HIGH transition of the CLOCK input, CP. Figure 5 specifies when the DONE signal is generated in this mode.

Control Mode 1 — Word Count Compare Mode.

In this mode the LOAD WORD COUNT instruction loads the word count into the Word Count Register and clears the Word Counter. When the Word Counter is enabled and the Word Counter Carry-in, WCI, is LOW, the Word Counter increments on the LOW to HIGH transition of the clock input, CP. Figure 5 specifies when the DONE signal is generated.

Control Mode 2 — Address Compare Mode

In this mode, only an initial and final memory address need be specified. The initial Memory Address is loaded into the Address Register and Address Counter and the final memory address is loaded into the Word Count Register and Word Counter. The Word Counter is always disabled in this mode and serves as a holding register for the final memory address. When the Address Counter is enabled and the \overline{ACI} input is LOW, the Address Counter increments or decrements (depending on Control Register bit 2) on the LOW to HIGH transition of the CLOCK input, CP. The Transfer Complete Circuitry compares the Address Counter with the Word Counter and generates the DONE signal during the last word transfer, i.e., when the Address Counter equals the Word Counter.

Control Mode 3 – Word Counter Carry Out Mode

For this mode of operation, the user can load the Word Count Register and Word Counter with the two's complement of the number of data words to be transferred. When the Word Counter is enabled and the WCI input is LOW, the Word Counter increments on the LOW to HIGH transition of the CLOCK input, CP. A Word Counter Carry Out signal, WCO, indicates the last data word is being transferred. The DONE signal is not required in this mode and, therefore, is always LOW.

Am2940 INSTRUCTIONS

The Am2940 instruction set consists of eight instructions. Six instructions load and read the Address Counter, Word Counter and Control Register, one instruction enables the Address and Word Counters, and one instruction reinitializes the Address and Word Counters. The function of the REINITIALIZE COUNTERS, LOAD WORD COUNT, and ENABLE COUNTERS instructions vary with the Control Mode being utilized. Table 1 defines the Am2940 Instructions as a function of Instruction inputs I_2 - I_0 and the four Am2940 Control Modes.

The WRITE CONTROL REGISTER instruction writes DATA input D_0 - D_2 into the Control Register; DATA inputs D_3 - D_7 are "don't care" inputs for this instruction. The READ CONTROL REGISTER instruction gates the Control Register outputs to DATA lines, D_0 - D_2 . DATA lines D_3 - D_7 are in the HIGH state during this instruction.

The Word Counter can be read using the READ WORD COUNTER instruction, which gates the Word Counter outputs to DATA lines D_0 - D_7 . The LOAD WORD COUNT instruction is Control Mode dependent. In Control Modes 0, 2, and 3, DATA inputs D_0 - D_7 are written into both the Word Count Register and Word Counter. In Control Mode 1, DATA inputs D_0 - D_7 are written into the Word Count Register and the Word Counter is cleared.

The READ ADDRESS COUNTER instruction gates the Address Counter outputs to DATA lines D_0 - D_7 , and the LOAD ADDRESS instruction writes DATA inputs D_0 - D_7 into both the Address Register and Address Counter.

In Control Modes 0, 1, and 3, the ENABLE COUNTERS instruction enables both the Address and Word Counters; in Control Mode 2, the Address Counter is enabled and the Word Counter holds its contents. When enabled and the carry input is active, the counters increment on the LOW to HIGH transition of the CLOCK input, CP. Thus, with this instruction applied, counting can be controlled by the carry inputs.

The REINITIALIZE COUNTERS instruction also is Control Mode dependent. In Control Modes 0, 2, and 3, the contents of the Address Register and Word Count Register are transferred to the respective Address Counter and Word Counter; in Control Mode 1, the content of the Address Register is transferred to the Address Counter and the Word Counter is cleared. The REINITIALIZE COUNTERS instruction allows a data transfer operation to be repeated without reloading the address and word count from the DATA lines.

Am2940 Timing

Various computations must be performed by the designer to determine how fast the Am2940 can be operated reliably in a given design. The exercises of this section demonstrate how these computations are performed.

Worst case A.C. characteristics, over the full temperature and voltage operating range should be used in these computations. Since, at the time of this writing, the Am2940 is still being characterized, only typical A.C. characteristics are available. These typicals are used here merely to demonstrate how the computations are performed; the designer must use worst-case characteristics. Figure 6 shows the characteristics of a Schottky register and a memory which are assumed for this exercise.

Figures 7A, B, and C show the typical cycle time calculations for the 16-bit Am2940 configuration. The typical delay along the longest path for any of the eight Am2940 instructions determines the typical cycle time. In each case, delays are computed from the LOW to HIGH transition of a clock through an entire microcycle to the next LOW to HIGH transition of a clock. The typical cycle time for a 16-bit Am2940 configuration is 64ns.

TABLE 1. Am2940 INSTRUCTIONS

I_2	I_1	I_0	Octal Code	Function	Mnemonic	Control Mode	Word Reg.	Word Counter	Address Reg.	Address Counter	Control Register	Data D_0 - D_7
L	L	L	0	WRITE CONTROL REGISTER	WRCR	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	D_0 - D_2 →CR	INPUT
L	L	H	1	READ CONTROL REGISTER	RDCR	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	CR→ D_0 - D_2 (Note 1)
L	H	L	2	READ WORD COUNTER	RDWC	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	WC→D
L	H	H	3	READ ADDRESS COUNTER	RDAC	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	AC→D
H	L	L	4	REINITIALIZE COUNTERS	REIN	0, 2, 3 1	HOLD HOLD	WCR→WC ZERO→WC	HOLD	AR→AC AR→AC	HOLD	Z Z
H	L	H	5	LOAD ADDRESS	LDAD	0, 1, 2, 3	HOLD	HOLD	D→AR	D→AC	HOLD	INPUT
H	H	L	6	LOAD WORD COUNT	LDWC	0, 2, 3 1	D→WR D→WR	D→WC ZERO→WC	HOLD	HOLD	HOLD	INPUT INPUT
H	H	H	7	ENABLE COUNTERS	ENCT	0, 1, 3 2	HOLD HOLD	ENABLE COUNT HOLD	HOLD	ENABLE COUNT ENABLE COUNT	HOLD	Z Z

CR = Control Reg.
AR = Address Reg.
AC = Address Counter

WCR = Word Count Reg.
WC = Word Counter
D = Data

L = LOW
H = HIGH
Z = High Impedance

Note 1:
Data Bits D_3 - D_7 are high during this instruction.

	Min.	Typ.	Max.
Schottky Register			
Clock to Output Delay		9	15
Input Set-Up Time	5	2	
Memory			
Address Set-Up Time	20	10	

Figure 6. Assumed AC Characteristics.

Figure 8 shows the address output enable time computations. Since the Am2940 has an asynchronous address output enable control, the address output enable time may not be related to the Am2940 cycle time.

Figure 9 shows the typical cycle time calculation for an 8-bit Am2940 configuration. The path shown is the longest path and determines an 8-bit typical cycle time of 52ns.

The typical cycle time calculation for a 24-bit Am2940 configuration is shown in Figure 10. The path shown is the longest path and determines a 24-bit typical cycle time of 76ns.

Figure 11 is a summary of typical Am2940 cycle times for the 8, 16 and 24-bit configurations.


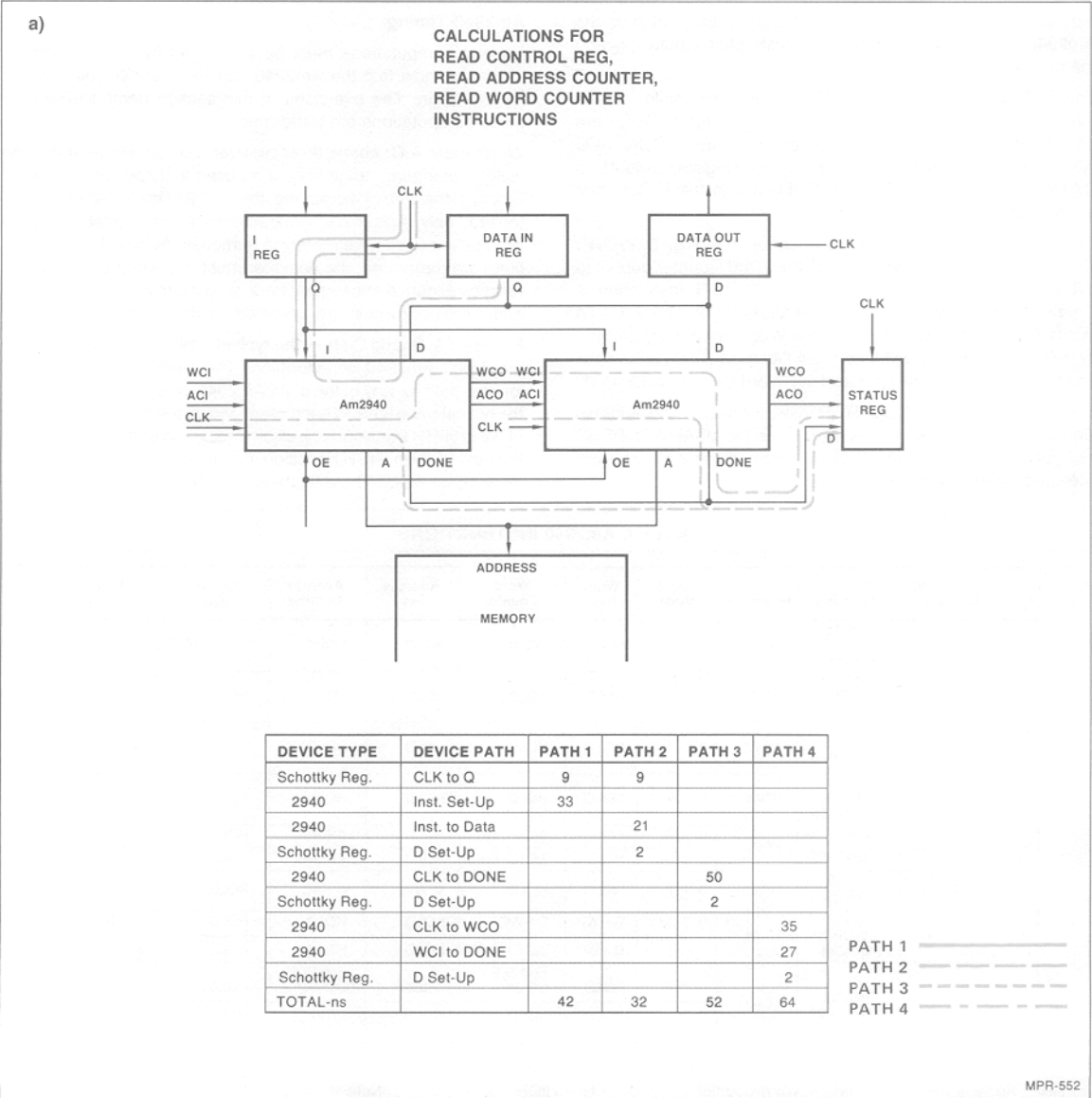


Figure 7. 16-Bit Typical Cycle Time Computations.

b)

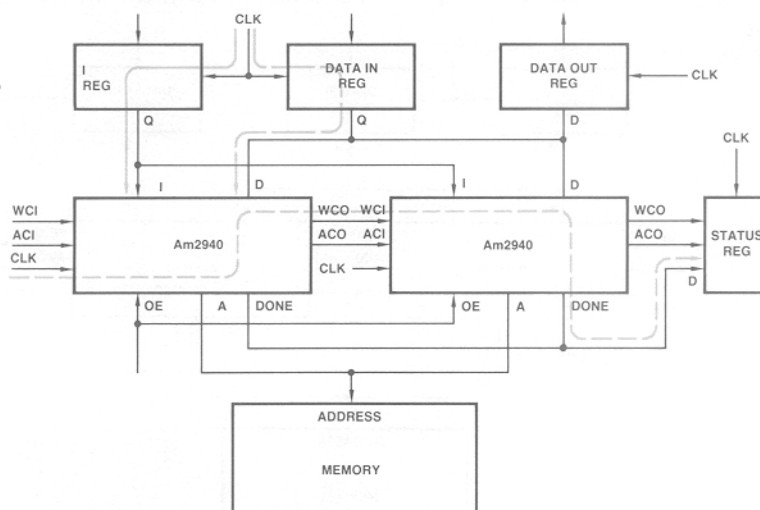CALCULATIONS FOR
WRITE CONTROL REG,
LOAD WORD COUNT,
LOAD ADDRESS
INSTRUCTIONS




MPR-553

DEVICE TYPE	DEVICE PATH	PATH 1	PATH 2	PATH 3
Schottky Reg.	CLK to Q	9	9	
2940	Inst. Set-Up	33		
2940	Data Set-Up		13	
2940	CLK to WCO			35
2940	WCI to DONE			27
Schottky Reg.	D Set-Up			2
TOTAL-ns		42	22	64

PATH 1 _____
PATH 2 _____
PATH 3 _____

c)

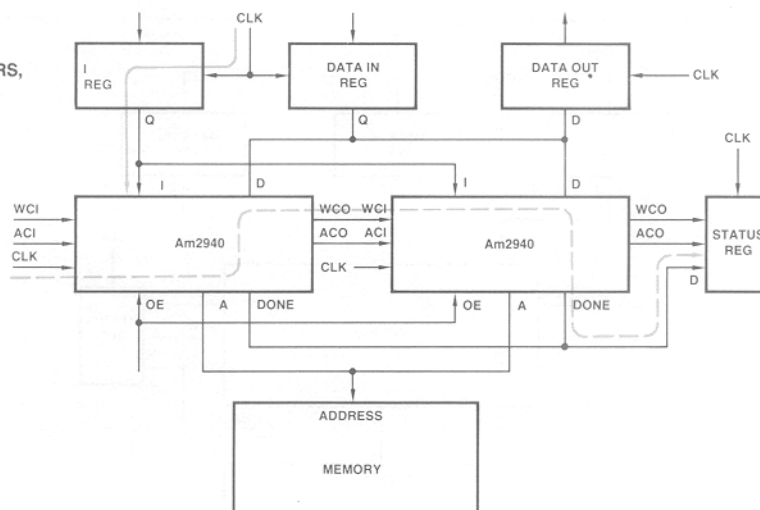CALCULATIONS FOR
REINITIALIZE COUNTERS,
ENABLE COUNTERS
INSTRUCTIONS




DEVICE TYPE	DEVICE PATH	PATH 1	PATH 2
Schottky Reg.	CLK to Q	9	
2940	Inst. Set-Up	33	
2940	CLK to WCO		35
2940	WCI to DONE		27
Schottky Reg.	D Set-Up		2
TOTAL-ns		42	64

PATH 1 _____
PATH 2 _____

MPR-554

Figure 7. 16-Bit Typical Cycle Time Computations. (Cont.)

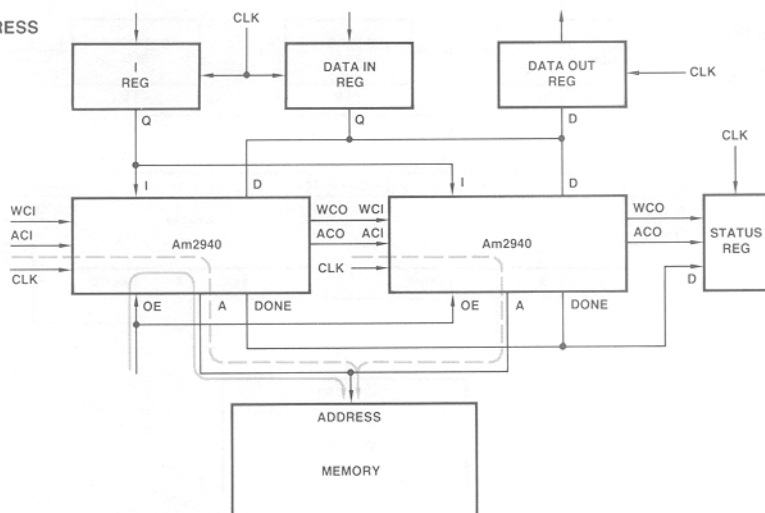**CALCULATIONS FOR
ENABLE MEMORY ADDRESS
(ASYNCHRONOUS)
INSTRUCTIONS**




DEVICE TYPE	DEVICE PATH	PATH 1	PATH 2
2940	OE to A	19	
2940	CLK to A		35
Memory	ADR Set-Up	10	10
TOTAL-ns		29	45

PATH 1 _____
PATH 2 _____

MPR-555

Figure 8. Speed Computations.

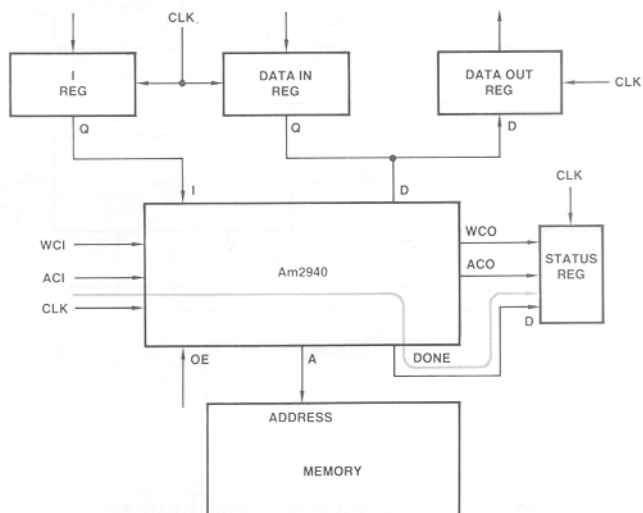


DEVICE TYPE	DEVICE PATH	PATH 1
2940	CLK to DONE	50
Schottky Reg.	D Set-Up	2
TOTAL-ns		52

PATH 1 _____

MPR-556

Figure 9. 8-Bit Typical Cycle Time Computation.

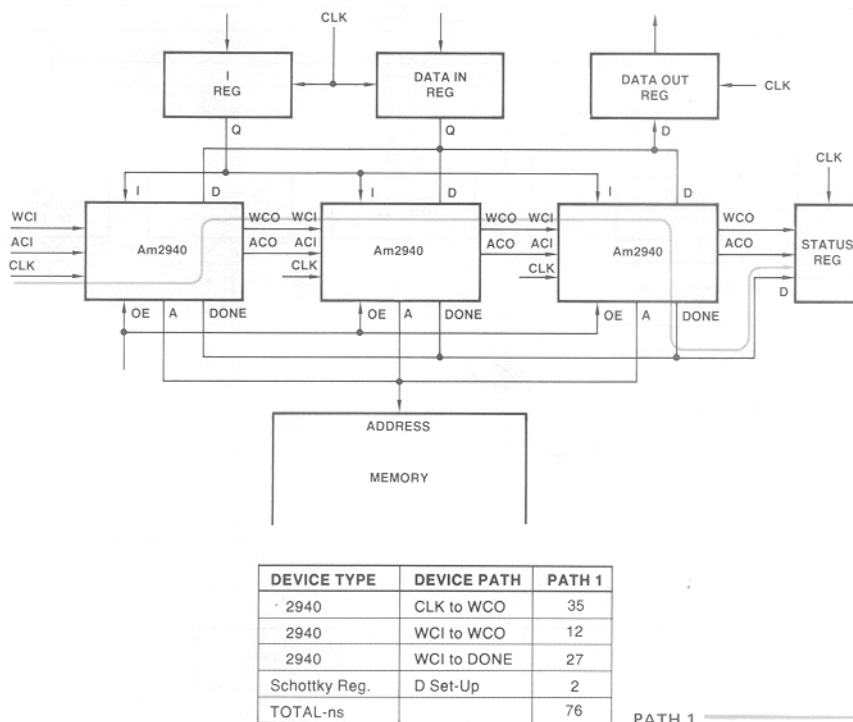

MPR-557

Figure 10. 24-Bit Typical Cycle Time Computation.

	Typical Cycle Time
8-Bit Configuration	52ns
16-Bit Configuration	64ns
24-Bit Configuration	76ns

Figure 11. Summary of Am2940 Cycle Times.

AN EXAMPLE DESIGN

The Am2940 is designed for use in high speed peripheral Controllers using DMA and provides the address and word count maintenance circuitry that is common to most. As indicated previously, DMA Control can be placed in each I/O Controller (Distributed DMA) or DMA Control for a number of I/O devices can be centralized in a separate unit.

Figure 12 shows a block diagram of a microprogrammed I/O Controller which is designed for use in a Distributed DMA system. The Am2910 Microprogram Sequencer, Microprogram Memory and the Microinstruction Register form the microprogram control portion of this I/O Controller. The Am2940 maintains the memory address and word count required for DMA operation. An internal three-state bus provides the communication path between the Microinstruction Register, the Am2917 Data Transceivers, the Am2940, the Am2901A Microprocessor, and the Device Interface

Circuitry. The Address Line Control, Data Transfer Control and Mode Control functions of this DMA Controller are incorporated into the I/O Controller Microprogram and the Asynchronous Interface Control Circuitry. The I/O Controller Microprogram also controls the Am2940.

The Am2940 interconnections are shown in detail in Figure 13. Two Am2940s are cascaded to generate a sixteen-bit address. The Am2940 ADDRESS and DATA output current sink capability is 24mA over the commercial operating range. This allows the Am2940s to drive the System Address Bus and Internal Three-State Bus directly, thereby eliminating the need for separate bus drivers. Three bits in the Microinstruction Register provide the Am2940 Instruction Inputs, I_0 - I_2 . The microprogram clock is used to clock the Am2940s and, when the ENABLE COUNTERS instruction is applied, address and word counting is controlled by the CNT bit of the Microinstruction Register.

Asynchronous interface control circuitry generates System Bus control signals and enables the Am2940 Address onto the System Address Bus at the appropriate time. The open-collector DONE outputs are dot-and-ed and used as a test input to the Am2910 Microprogram Sequencer.

The I/O controller read operation is flowcharted in Figure 14. The CPU initializes the I/O controller by sending a read command, the starting memory address, the word count and any other parameters required to perform the operation. The I/O Controller then obtains a word of data from the I/O device and requests use of the system bus for a DMA transfer. When the bus is granted, the I/O Controller requests a memory data transfer. Upon receipt of the memory acknowledge signal, which indicates the memory trans-

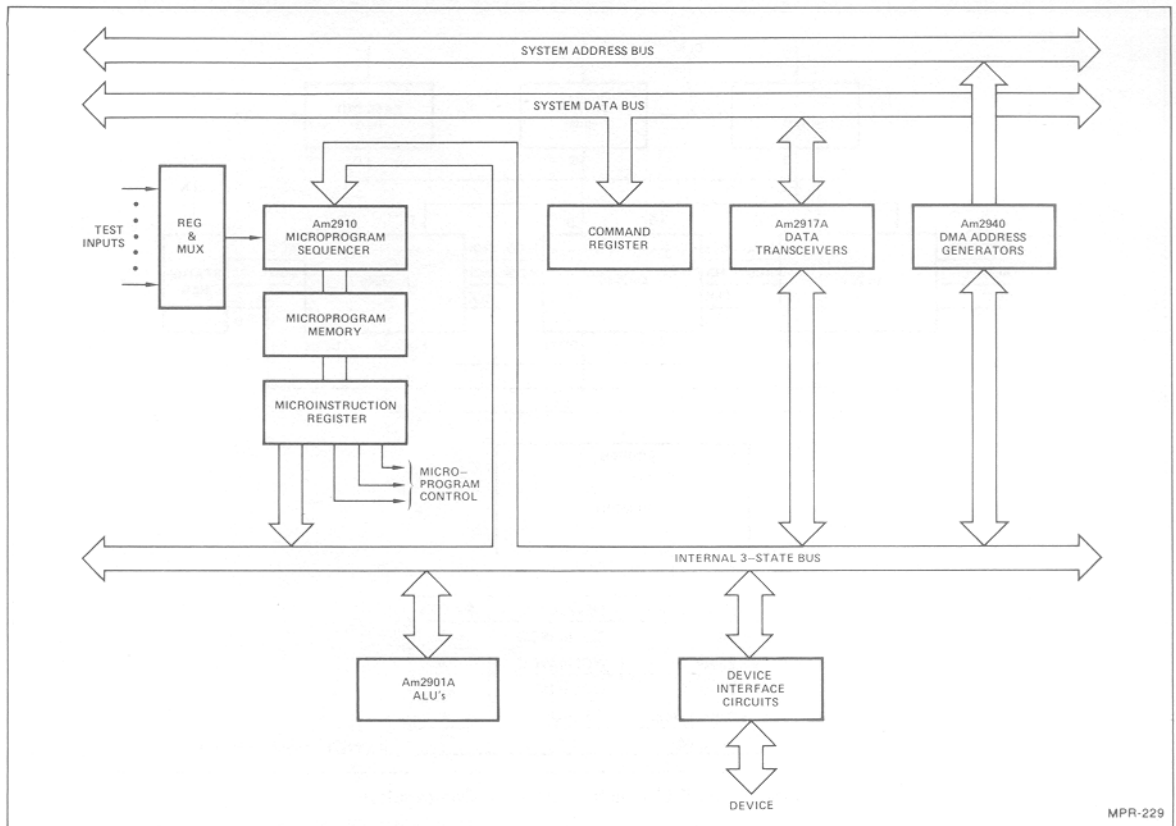


Figure 12. DMA Peripheral Controller Block Diagram.


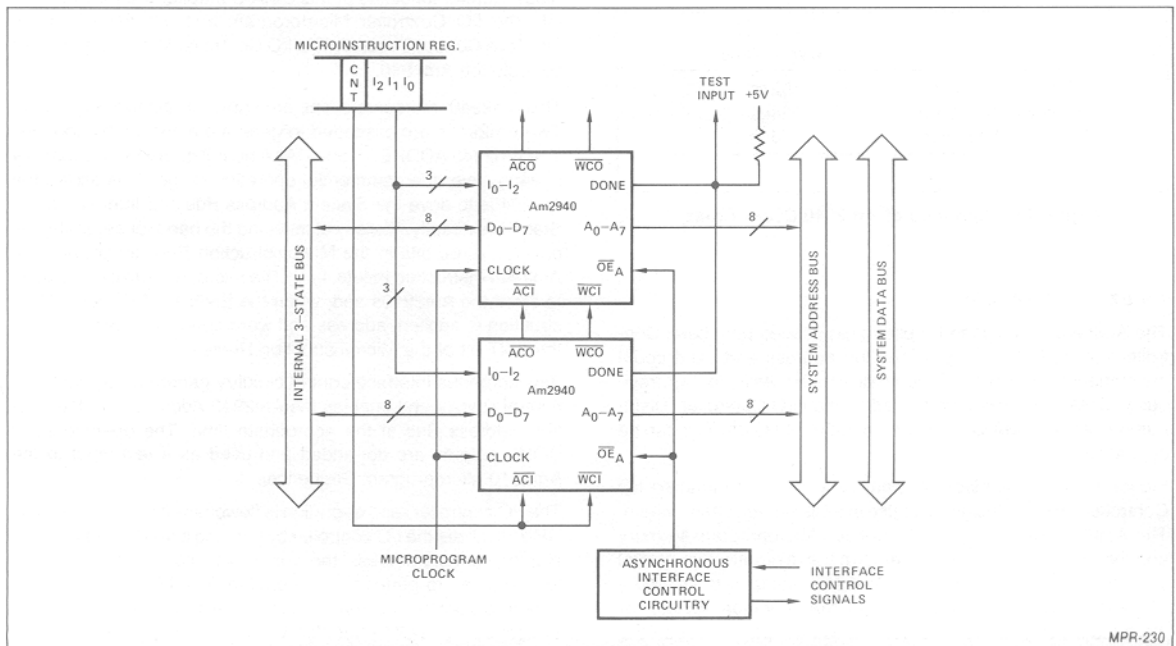


Figure 13. Am2940 Interconnections.

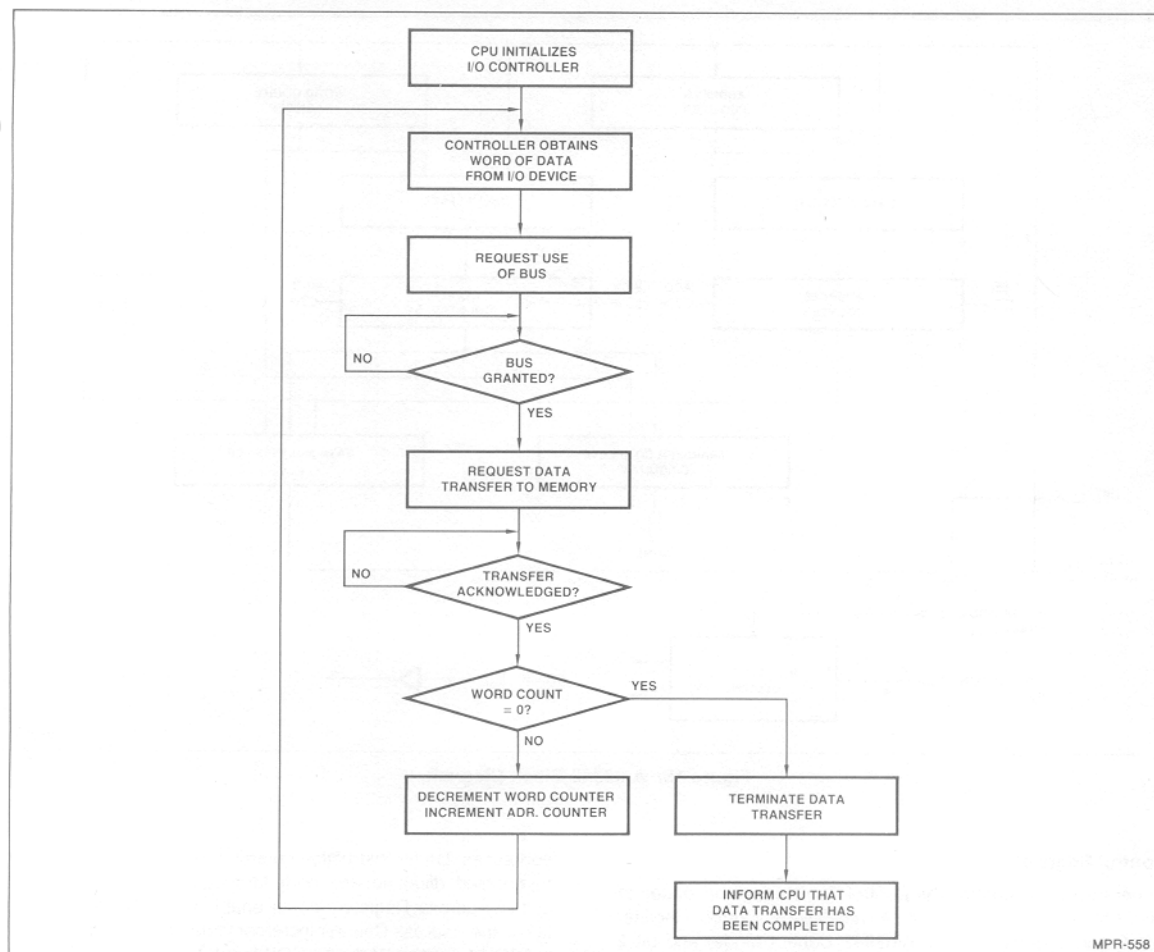

MPR-558

Figure 14. Read Control Flowchart.

fer is complete, the I/O Controller tests the word count. If the word count is not equal to zero, the word counter is decremented, the address counter is incremented and another data word is transferred. When the word count reaches zero, the I/O Controller terminates the data transfer and informs the CPU that the transfer has been completed.

THE Am2942 PROGRAMMABLE TIMER/COUNTER, DMA ADDRESS GENERATOR.

GENERAL DESCRIPTION

The Am2942, a 22-pin version of the Am2940, can be used as a high-speed DMA address Generator or Programmable Timer/Counter. It provides multiplexed Address and Data lines, for use with a common bus, and additional Instruction Input and Instruction Enable pins. The Am2942 executes 16 instructions; eight are the same as the Am2940 instructions, and eight instructions facilitate the use of the Am2942 as a Programmable Timer/Counter. The Instruction Enable input allows the sharing of the Am2942 instruction field with other devices.

When used as a Timer/Counter, the Am2942 provides two independent, programmable, eight-bit, up-down counters in a 22-pin package. The two on-chip counters can be cascaded to form a single chip, 16-bit counter. Also, any number of chips can be cascaded – for example three cascaded Am2942s form a 48-bit timer/counter.

Reinitialization instructions provide the capability to reinitialize the counters from on-chip registers. Am2942 Programmable Control Modes, identical to those of the Am2940, offer four different types of programmable control.

Am2942 ARCHITECTURE

As shown in the Block Diagram, the Am2942 consists of the following:

- A three-bit Control Register.
- An eight-bit Address Counter with input multiplexer.
- An eight-bit Address Register.
- An eight-bit Word Counter with input multiplexer.
- An eight-bit Word Count Register.
- Transfer complete circuitry.
- An eight-bit wide data multiplexer with three-state output buffers.
- An instruction decoder.

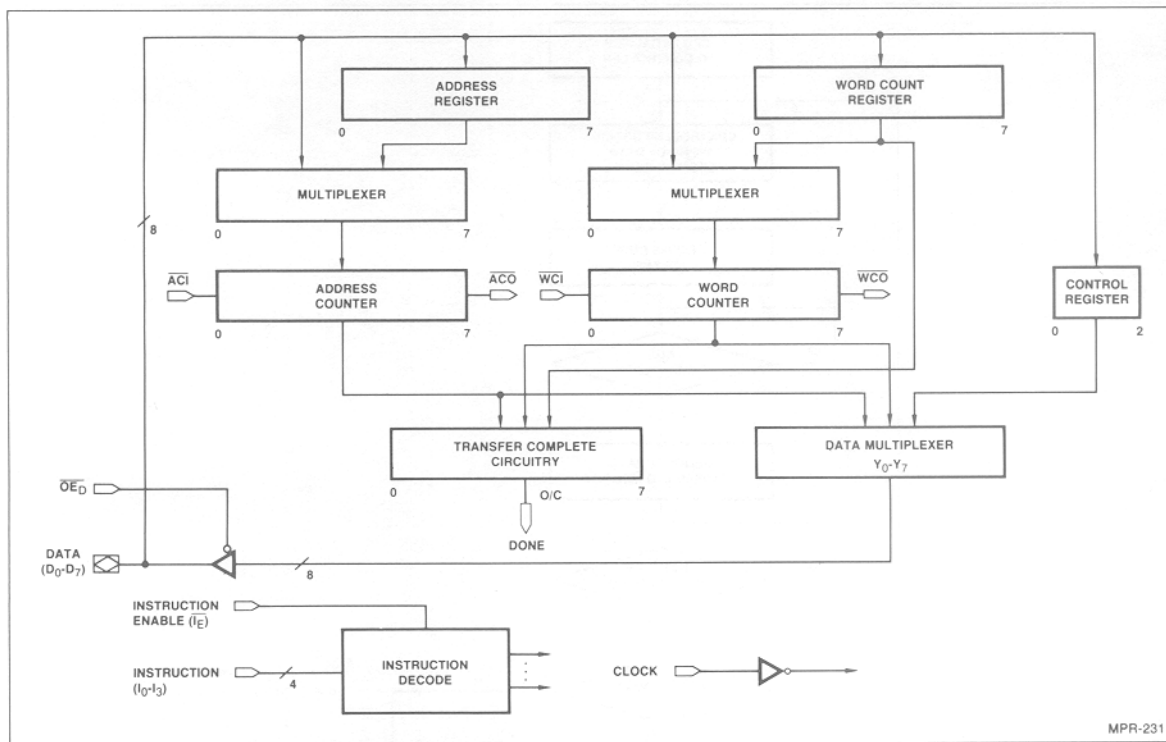


Figure 15. Am2942 Block Diagram.

Control Register

Under instruction control, the Control Register can be loaded or read from the bidirectional DATA lines, D₀-D₇. Control Register bits 0 and 1 determine the Am2942 Control Mode, and bit 2 determines whether the Address Counter increments or decrements. Figure 16 defines the Control Register format.

Address Counter

The Address Counter, which provides the current memory address, is an eight-bit, binary, up/down counter with full look-ahead carry generation. The Address Carry input (ACI) and Address Carry Output (ACO) allow cascading to accommodate larger

addresses. Under instruction control, the Address Counter can be enabled, disabled, and loaded from the DATA inputs, D₀-D₇, or the Address Register. When enabled and the ACI input is LOW, the Address Counter increments/decrements on the LOW to HIGH transition of the CLOCK input, CP.

Address Register

The eight-bit Address Register saves the initial address so that it can be restored later in order to repeat a transfer operation. When the LOAD ADDRESS instruction is executed, the Address Register and Address Counter are simultaneously loaded from the DATA inputs, D₀-D₇.

Control Register						
CR ₂ CR ₁ CR ₀						
CR ₁	CR ₀	Control Mode Number	Control Mode Type	Word Counter	Done Output Signal	
					WCI = LOW	WCI = HIGH
L	L	0	Word Count Equals Zero	Decrement	HIGH when Word Counter = 1	HIGH when Word Counter = 0
L	H	1	Word Count Compare	Increment	HIGH when Word Counter + 1 = Word Count Register	HIGH when Word Counter = Word Count Register
H	L	2	Address Compare	Decrement	HIGH when Word Counter = Address Counter	
H	H	3	Word Counter Carry Out	Increment	Always LOW	

CR ₂	Address Counter
L	Increment
H	Decrement

H = HIGH
L = LOW

Figure 16. Control Register Format Definition.

Word Counter And Word Count Register

The Word Counter and Word Count Register, which maintain and save a word count, are similar in structure and operation to the Address Counter and Address Register, with the exception that the Word Counter increments in Control Modes 1 and 3 and decrements in Control Modes 0 and 2. The LOAD WORD COUNT instruction simultaneously loads the Word Counter and Word Count Register.

Transfer Complete Circuitry

The Transfer Complete Circuitry is a combinational logic network which detects the completion of the data transfer operation in three Control Modes and generates the DONE output signal. The DONE signal is an open-collector output, which can be dot-anded between chips.

Data Multiplexer

The Data Multiplexer is an eight-bit wide, three-input multiplexer which allows the Address Counter, Word Counter and Control Register to be read at DATA lines D_0 - D_7 . The Data Multiplexer output, Y_0 - Y_7 , is enabled onto DATA lines D_0 - D_7 if, and only if, the Output Enable input, OE_D , is LOW. (Refer to Figure 17.)

\overline{OE}_D	D_0 - D_7
L	DATA MULTIPLEXER OUTPUT, Y_0 - Y_7
H	HIGH Z

Figure 17. Data Bus Output Enable Function.

Instruction Decoder

The Instruction Decoder generates required internal control signals as a function of the INSTRUCTION inputs, I_0 - I_3 Control Register bits 0 and 1, and the INSTRUCTION ENABLE input, I_E .

Clock

The clock input, CP, is used to clock the Address Register, Address Counter, Word Count Register, Word Counter, and Control Register, all on the LOW to HIGH transition of the CP signal.

Am2942 CONTROL MODES

Control Mode 0 — Word Count Equals Zero Mode

In this mode, the LOAD WORD COUNT instruction loads the word count into the Word Count Register and Word Counter. When the Word Counter is enabled and the Word Counter Carry-in, WCI , is LOW, the Word Counter decrements on the LOW to HIGH transition of the CLOCK input, CP. Figure 16 specifies when the DONE signal is generated in this mode.

Control Mode 1 — Word Count Compare Mode

In this mode the LOAD WORD COUNT instruction loads the word count into the Word Count Register and clears the Word Counter. When the Word Counter is enabled and the Word Counter Carry-in, WCI , is LOW, the Word Counter increments on the LOW to HIGH transition of the clock input, CP. Figure 16 specifies when the DONE signal is generated.

Control Mode 2 — Address Compare Mode

In this mode, only an initial and final memory address need to be specified. The initial Memory Address is loaded into the Address Register and Address Counter and the final memory address is loaded into the Word Count Register and Word Counter. The Word Counter serves as a holding register for the final memory address. When the Address Counter is enabled and the \overline{ACI} input is LOW, the Address Counter increments or decrements (depending on Control Register bit 2) on the LOW to HIGH transition of the CLOCK input, CP. The Transfer Complete Circuitry compares the Address Counter with the Word Counter and generates the DONE signal during the last word transfer, i.e., when the Address Counter equals the Word Counter.

Control Mode 3 — Word Counter Carry Out Mode

For this mode of operation, the user can load the Word Count Register and Word Counter with the two's complement of the number of data words to be transferred. When the Word Counter is enabled and the \overline{WCI} input is LOW, the Word Counter increments on the LOW to HIGH transition of the CLOCK input, CP. A Word Counter Carry Out signal, WCO , indicates the last data word is being transferred. The DONE signal is not required in this mode and, therefore, is always LOW.

Am2942 INSTRUCTIONS

The Am2942 instruction set consists of sixteen instructions. Eight are DMA instructions and are the same as the Am2940 instructions. The remaining eight instructions are designed to facilitate the use of the Am2942 as a Programmable Timer/Counter. Figures 18 and 19 define the Am2942 Instructions.

Instructions 0-7 are DMA instructions. The WRITE CONTROL REGISTER instruction writes DATA input D_0 - D_2 into the Control Register; DATA inputs D_3 - D_7 are "don't care" inputs for this instruction. The READ CONTROL REGISTER instruction gates the Control Register to Data Multiplexer outputs Y_0 - Y_2 . Outputs Y_3 - Y_7 are HIGH during this instruction.

The Word Counter can be read using the READ WORD COUNTER instruction, which gates the Word Counter to Data Multiplexer outputs, Y_0 - Y_7 . The LOAD WORD COUNT instruction is Control Mode dependent. In Control Modes 0, 2 and 3, DATA inputs D_0 - D_7 are written into both the Word Count Register and Word Counter. In Control Mode 1, DATA inputs D_0 - D_7 are written into the Word Count Register and the Word Counter is cleared.

The READ ADDRESS COUNTER instruction gates the Address Counter to Data Multiplexer outputs, Y_0 - Y_7 , and the LOAD ADDRESS instruction writes DATA inputs D_0 - D_7 into both the Address Register and Address Counter.

In Control Modes 0, 1, and 3, the ENABLE COUNTERS instruction enables both the Address and Word Counters; in Control Mode 2, the Address Counter is enabled and the Word Counter holds its contents. When enabled and the carry input is active, the counters increment on the LOW to HIGH transition of the CLOCK input, CP. Thus, with this instruction applied, counting can be controlled by the carry inputs.

The REINITIALIZE COUNTERS instruction also is Control Mode dependent. In Control Modes 0, 2, and 3, the contents of the Address Register and Word Count Register are transferred to the respective Address Counter and Word Counter; in Control Mode 1, the content of the Address Register is transferred to the Address Counter and the Word Counter is cleared. The REINITIALIZE COUNTERS instruction allows a data transfer operation to be repeated without reloading the address and word count from the DATA lines.

$\overline{I_E}$	I_3	I_2	I_1	I_0	HEX CODE		
0	0	0	0	0	0	WRITE CONTROL REGISTER	DMA INSTRUCTIONS
0	0	0	0	1	1	READ CONTROL REGISTER	
0	0	0	1	0	2	READ WORD COUNTER	
0	0	0	1	1	3	READ ADDRESS COUNTER	
0	0	1	0	0	4	REINITIALIZE COUNTERS	
0	0	1	0	1	5	LOAD ADDRESS	
0	0	1	1	0	6	LOAD WORD COUNT	
0	0	1	1	1	7	ENABLE COUNTERS	
1	0	X	X	X	0-7	INSTRUCTION DISABLE	
0	1	0	0	0	8	WRITE CONTROL REGISTER, T/C	TIMER/COUNTER INSTRUCTIONS
0	1	0	0	1	9	REINITIALIZE ADDRESS COUNTER	
0	1	0	1	0	A	READ WORD COUNTER, T/C	
0	1	0	1	1	B	READ ADDRESS COUNTER, T/C	
0	1	1	0	0	C	REINITIALIZE ADDRESS & WORD COUNTERS	
0	1	1	0	1	D	LOAD ADDRESS, T/C	
0	1	1	1	0	E	LOAD WORD COUNT, T/C	
0	1	1	1	1	F	REINITIALIZE WORD COUNTER	
1	1	X	X	X	8-F	INSTRUCTION DISABLE, T/C	

0 = LOW 1 = HIGH X = DON'T CARE

- Notes: 1. When I_3 is tied LOW, the Am2942 acts as a DMA circuit: When I_3 is tied HIGH, the Am2942 acts as a Timer/Counter circuit.
2. Am2942 instructions 0 through 7 are the same as Am2940 instructions.

Figure 18. Am2942 Instructions

When $\overline{I_E}$ is HIGH, Instruction inputs, I_0 - I_2 , are disabled. If I_3 is LOW, the function performed is identical to that of the ENABLE COUNTERS instruction. Thus, counting can be controlled by the carry inputs with the ENABLE COUNTERS instruction applied or with Instruction Inputs I_0 - I_2 disabled.

Instructions 8-F facilitate the use of the Am2942 as a Programmable Timer/Counter. They differ from instructions 0-7 in that they provide independent control of the Address Counter, Word Counter and Control Register.

The WRITE CONTROL REGISTER, T/C instruction writes DATA input D_0 - D_2 into the Control Register. DATA inputs D_3 - D_7 are "don't care" inputs for this instruction. The Address and Word Counters are enabled, and the Control Register contents appear at the Data Multiplexer output.

The REINITIALIZE ADDRESS COUNTER instruction allows the independent reinitialization of the Address Counter. The Word Counter is enabled and the contents of the Address Counter appear at the Data Multiplexer output.

The Word Counter can be read, using the READ WORD COUNTER, T/C instruction. Both counters are enabled when this instruction is executed.

When the READ ADDRESS COUNTER, T/C instruction is executed, both counters are enabled and the address counter contents appear at the Data Multiplexer output.

The REINITIALIZE ADDRESS and WORD COUNTERS instruction provides the capability to reinitialize both counters at the same time. The Address Counter contents appear at the Data Multiplexer output.

DATA inputs D_0 - D_7 are loaded into both the Address Register and Counter when the LOAD ADDRESS, T/C instruction is executed. The Word Counter is enabled and its contents appear at the Data Multiplexer output.

The LOAD WORD COUNT, T/C instruction is identical to the LOAD WORD COUNT instruction with the exception that Address Counter is enabled.

The Word Counter can be independently reinitialized using the REINITIALIZE WORD COUNTER instruction. The Address Counter is enabled and the Word Counter contents appear at the Data Multiplexer output.

When the $\overline{I_E}$ input is HIGH, Instruction inputs, I_0 - I_2 , are disabled. The function performed when I_3 is HIGH is identical to that performed when I_3 is LOW, with the exception that the Word Counter contents appear at the Data Multiplexer output.

EXAMPLE DESIGNS

Figure 20 shows an Am2942 used as two independent, programmable eight-bit timer/counters. In this example, an Am2910 Microprogram Sequencer provides an address to Am29775 512 x 8 Registered PROMs. The on-chip PROM output register is used as the Microinstruction Register.

The Am2942 Instruction input, I_3 is tied HIGH to select the eight Timer/Counter instructions. The $\overline{I_E}$, I_0 - I_2 , and $\overline{OE_D}$ inputs are provided by the microinstruction, and the D_0 - D_7 data lines are connected to a common Data Bus. GATE WC and GATE AC are separate enable controls for the respective Word Counter and Address Counter. The DONE, ACO and WCO output signals indicate that a pre-programmed time or count has been reached.

\overline{I}_E	$I_3 I_2 I_1 I_0$ (Hex)	Function	Mnemonic	Control Mode	Word Reg.	Word Counter	Adr. Reg.	Adr. Counter	Control Reg.	Data Multiplexer Output
L	0	WRITE CONTROL REGISTER	WRCR	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	$D_{0-2} \rightarrow CR$	FORCED HIGH
L	1	READ CONTROL REGISTER	RDCR	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	CONTROL REG.
L	2	READ WORD COUNTER	RDWC	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	WORD COUNTER
L	3	READ ADDRESS COUNTER	RDAC	0, 1, 2, 3	HOLD	HOLD	HOLD	HOLD	HOLD	ADR. COUNTER
L	4	REINITIALIZE COUNTERS	REIN	0, 2, 3	HOLD	$WR \rightarrow WC$	HOLD	$AR \rightarrow AC$	HOLD	ADR. CNTR.
				1	HOLD	$ZERO \rightarrow WC$	HOLD	$AR \rightarrow AC$	HOLD	ADR. CNTR.
L	5	LOAD ADDRESS	LDAD	0, 1, 2, 3	HOLD	HOLD	$D \rightarrow AR$	$D \rightarrow AC$	HOLD	WORD COUNTER
L	6	LOAD WORD COUNT	LDWC	0, 2, 3	$D \rightarrow WR$	$D \rightarrow WC$	HOLD	HOLD	HOLD	FORCED HIGH
				1	$D \rightarrow WR$	$ZERO \rightarrow WC$	HOLD	HOLD	HOLD	FORCED HIGH
L	7	ENABLE COUNTERS	ENCT	0, 1, 3	HOLD	ENABLE	HOLD	ENABLE	HOLD	ADR. CNTR.
				2	HOLD	HOLD	HOLD	ENABLE	HOLD	ADR. CNTR.
H	0-7	INSTRUCTION DISABLE	-	0, 1, 3	HOLD	ENABLE	HOLD	ENABLE	HOLD	ADR. CNTR.
				2	HOLD	HOLD	HOLD	ENABLE	HOLD	ADR. CNTR.
L	8	WRITE CONTROL REGISTER, T/C	WCRT	0, 1, 2, 3	HOLD	ENABLE	HOLD	ENABLE	$D_{0-2} \rightarrow CR$	CONTROL REG.
L	9	REINITIALIZE ADR. COUNTER	REAC	0, 1, 2, 3	HOLD	ENABLE	HOLD	$AR \rightarrow AC$	HOLD	ADR. COUNTER
L	A	READ WORD COUNTER, TC	RWCT	0, 1, 2, 3	HOLD	ENABLE	HOLD	ENABLE	HOLD	WORD COUNTER
L	B	READ ADDRESS COUNTER, T/C	RACT	0, 1, 2, 3	HOLD	ENABLE	HOLD	ENABLE	HOLD	ADR. COUNTER
L	C	REINITIALIZE ADDRESS AND WORD COUNTERS	RAWC	0, 2, 3	HOLD	$WR \rightarrow WC$	HOLD	$AR \rightarrow AC$	HOLD	ADR. CNTR.
				1	HOLD	$ZERO \rightarrow WC$	HOLD	$AR \rightarrow AC$	HOLD	ADR. CNTR.
L	D	LOAD ADDRESS, T/C	LDAT	0, 1, 2, 3	HOLD	ENABLE	$D \rightarrow AR$	$D \rightarrow AC$	HOLD	WORD COUNTER
L	E	LOAD WORD COUNT, T/C	LWCT	0, 2, 3	$D \rightarrow WR$	$D \rightarrow WC$	HOLD	ENABLE	HOLD	FORCED HIGH
				1	$D \rightarrow WR$	$ZERO \rightarrow WC$	HOLD	ENABLE	HOLD	FORCED HIGH
L	F	REINITIALIZE WORD COUNTER	REWC	0, 2, 3	HOLD	$WR \rightarrow WC$	HOLD	ENABLE	HOLD	WD. CNTR.
				1	HOLD	$ZERO \rightarrow WC$	HOLD	ENABLE	HOLD	WD. CNTR.
H	8-F	INSTRUCTION DISABLE, T/C	-	0, 1, 3	HOLD	ENABLE	HOLD	ENABLE	HOLD	WD. CNTR.
				2	HOLD	HOLD	HOLD	ENABLE	HOLD	WD. CNTR.

WR = WORD REGISTER AC = ADDRESS COUNTER
 WC = WORD COUNTER CR = CONTROL REGISTER
 AR = ADDRESS REGISTER D = DATA

Figure 19. Am2942 Function Table.

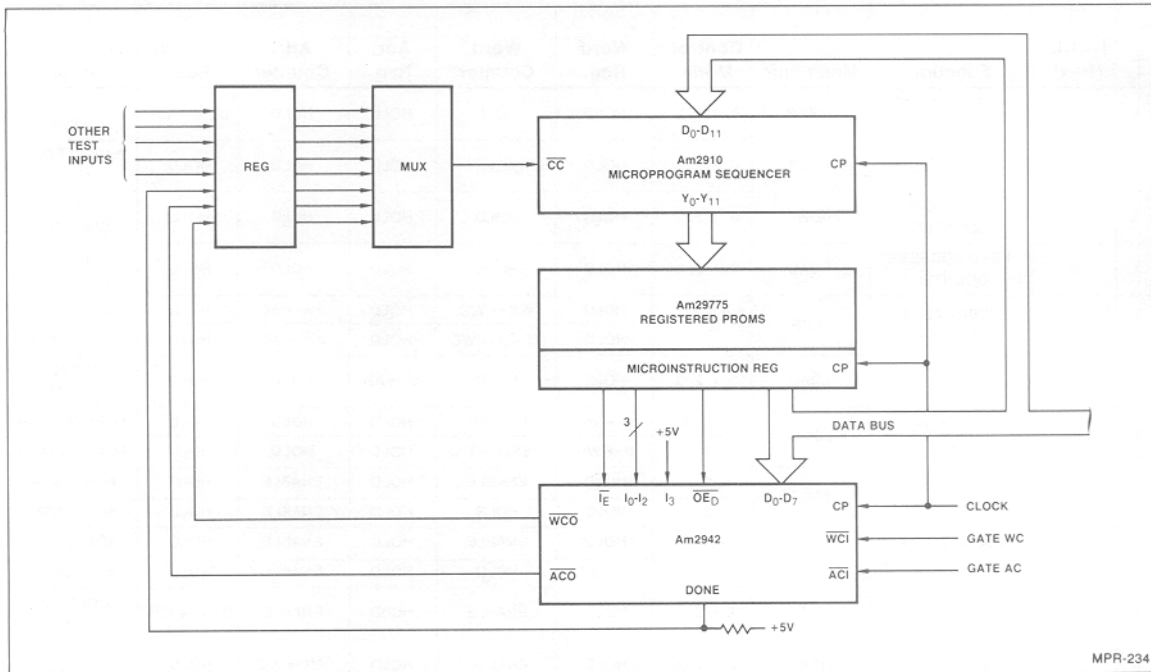


Figure 20. Two 8-Bit Programmable Counters/Timers in a 22-Pin Package.

Figure 21 shows an Am2942 used as a single 16-bit, programmable timer/counter. In this example, the Word Counter carry-out, WCO, is connected to the Address Counter carry-in, ACI, to form a single 16-bit counter which is enabled by the GATE signal.

Figure 22 shows two Am2942s cascaded to form a 32-bit programmable timer/counter. The two Word Counters form the low order 16 bits, and the two Address Counters form the high order bits. This allows the timer/counter to be loaded and read 16 bits at a time.

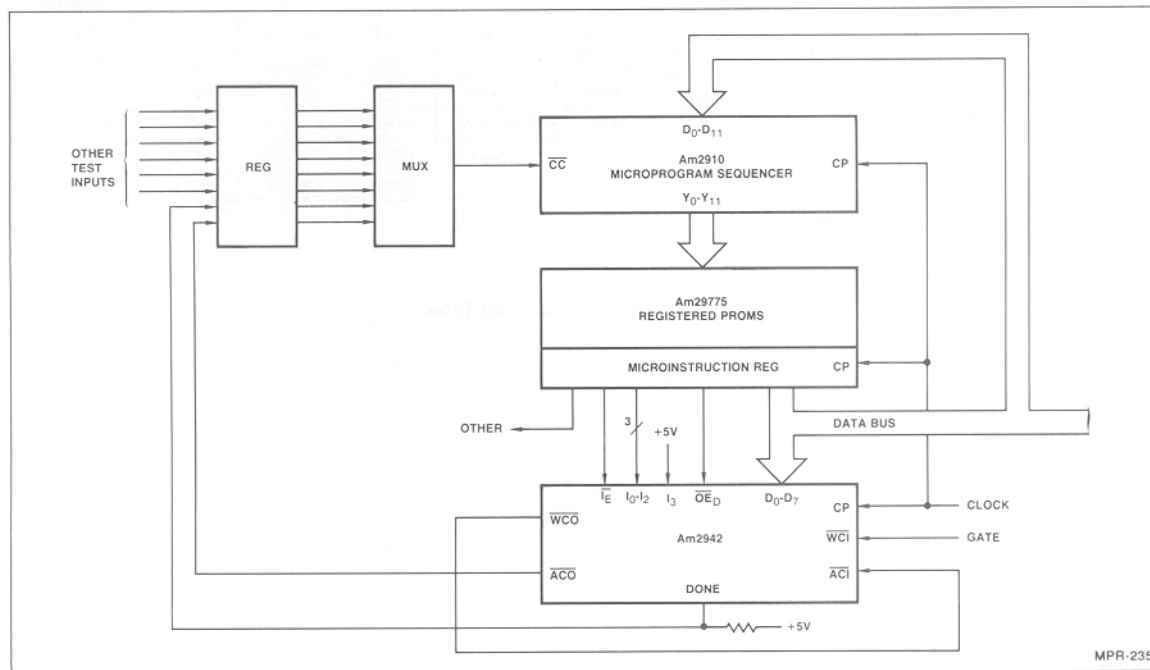


Figure 21. 16-Bit Programmable Counter/Timer Using a Single Am2942.

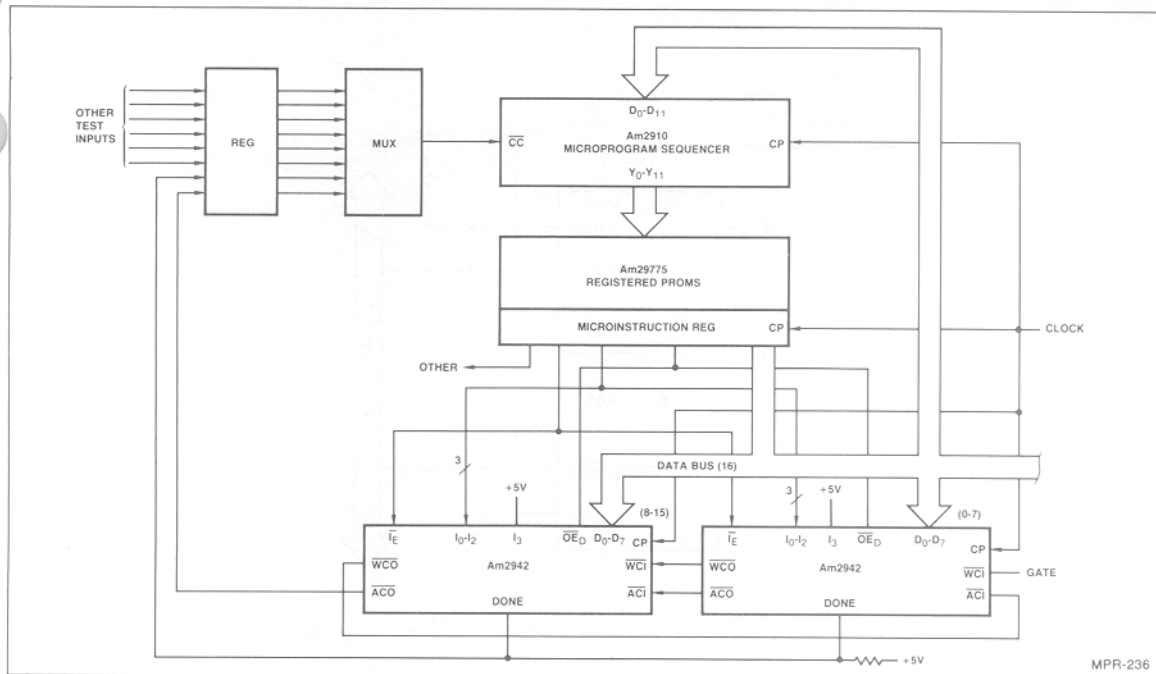


Figure 22. 32-Bit Programmable Counter/Timer Using Two Am2942s.

In Figure 23, two Am2942s are shown cascaded to form dual 16-bit counters/timers. GATE WC and GATE AC are separate enable controls for the respective Word Counter and Address Counter. Using the 16-bit Data Bus, each 16-bit counter can be loaded or read in parallel.

Figure 24 shows two Am2942s used as DMA address Generators on a common DATA/ADDRESS bus. The common bus allows the use of the Am2942 multiplexed data and address pins, D₀-D₇. The Am2942 is in a 22 pin package whereas the Am2940, which has separate address and data pins, requires a 28 pin package.

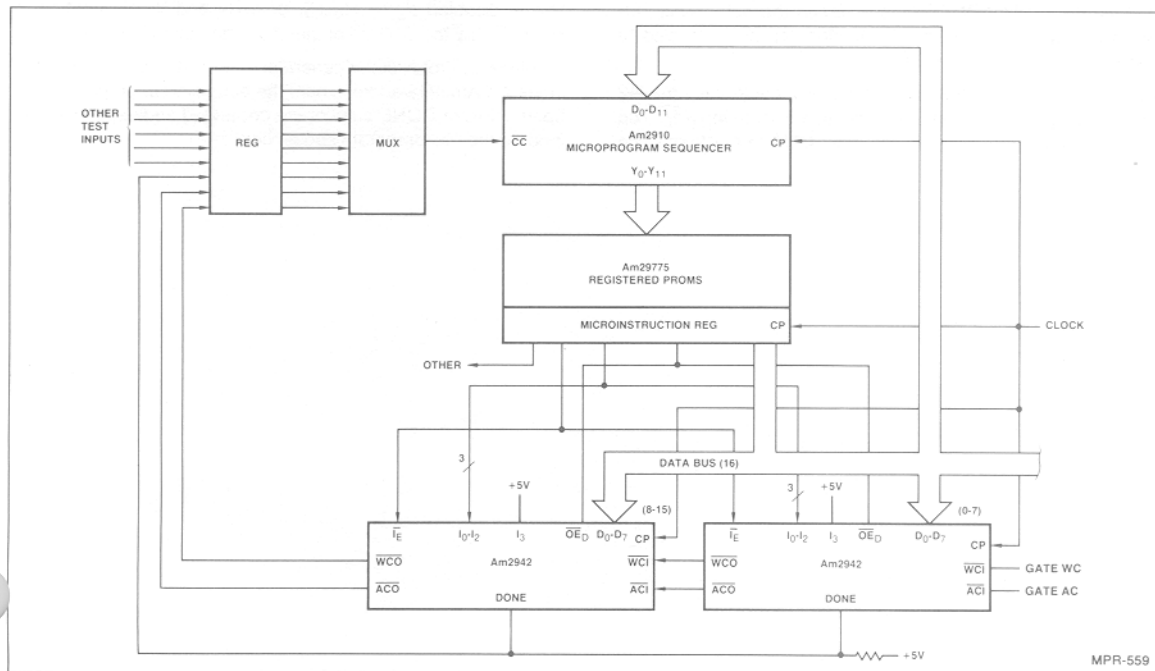


Figure 23. Dual 16-Bit Programmable Counters/Timers.

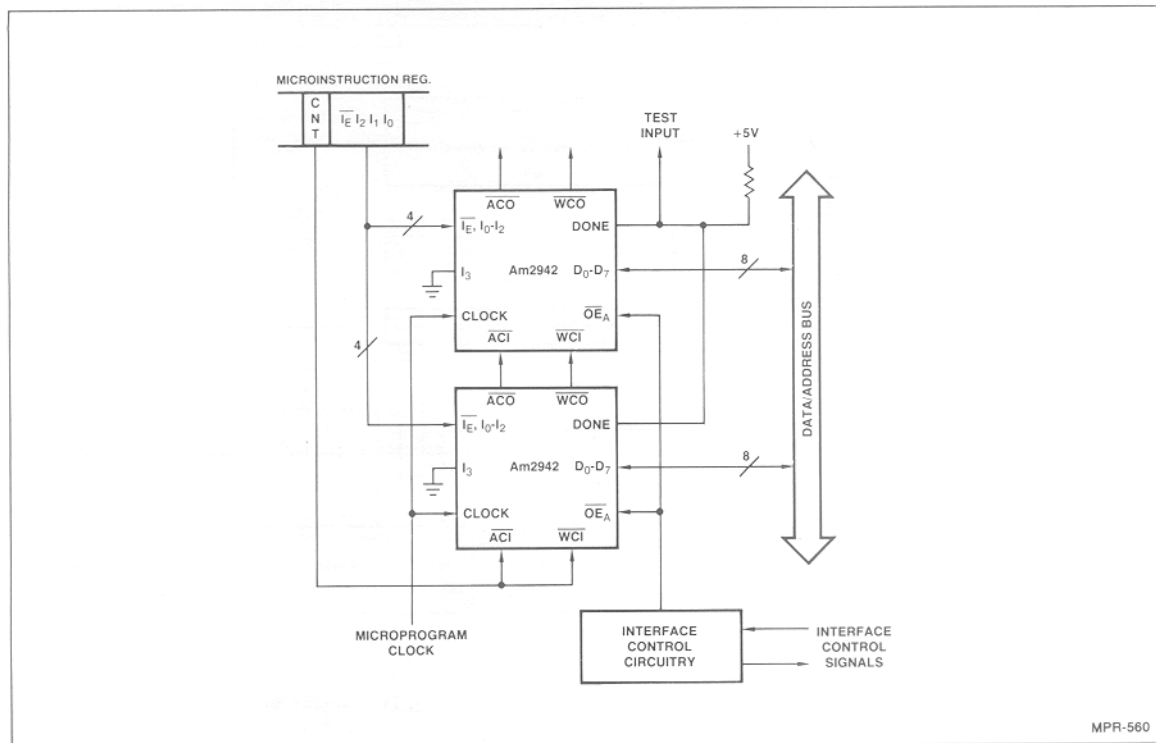



Figure 24. Am2942s Used as DMA Address Generator on Common Bus.

In this example the Am2942 Address Counter, Word Counter and Control Register are loaded and read directly from the CPU via the DATA/ADDRESS bus. Since the bus carries addresses as well as data, the D_0-D_7 pins can be used also to enable the address onto the bus.

Four bits in the Microinstruction Register provide the Am2942 Instruction Inputs, I_0-I_2 and the Instruction Enable input $\overline{I_E}$. The I_4 input is tied LOW, selecting the eight DMA instructions. The

microprogram clock is used to clock the Am2942s, and when the ENABLE COUNTERS instruction is applied or the instruction is disabled ($\overline{I_E} = \text{HIGH}$), address and word counting is controlled by the CNT bit of the Microinstruction Register.

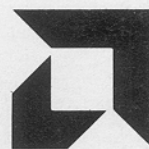Interface control circuitry generates bus control signals and enables the Am2942 address onto the bus at the appropriate. The open-collector DONE outputs are dot-and-ed and used as a test input to the microprogram sequencer.



**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
Sunnyvale

California 94086
(408) 732-2400

TWX: 910-339-928

TELEX: 34-6306

TOLL FREE

(800) 538-8450

11-78