

## APPLICATION NOTE


# 5-Volt Horizontal Clock Drivers

for use with Kodak KAI-2000, KAI-2093,  
KAI-4010 and KAI-4020 interline image  
sensors

October 23, 2002  
Revision 1

This document describes a simple horizontal CCD clock driver for the KAI-2000, KAI-2093, KAI-4010, and KAI-4020 image sensors.

## HCCD Register Operation

 

The horizontal CCD is arranged to allow the entire image to be read out of either video 1 or video 2 (mirror image). For faster read out both video 1 and video 2 may be used simultaneously. The horizontal shift register is designed as a reversible pseudo 2-phase CCD. The direction of charge transfer in the horizontal CCD is controlled by the wiring connections.

To direct all pixels to the video 1 output, make the following HCCD connections:

$\phi H1 = \phi H1SL, \phi H1SR, \phi H1BL, \phi H2BR$   
and  
 $\phi H2 = \phi H2SL, \phi H2SR, \phi H2BL, \phi H1BR$

where  $\phi H1$  is the output of the H1 phase timing generator and  $\phi H2$  is the output of the H2 phase timing generator.

To direct all pixels to the video 2 output, make the following HCCD connections:


$\phi H1 = \phi H1SL, \phi H1SR, \phi H2BL, \phi H1BR$   
and  
 $\phi H2 = \phi H2SL, \phi H2SR, \phi H1BL, \phi H2BR$

For faster image read out, direct the left half of the image to video 1 and the right half of the image to video 2 by making the HCCD connections:

$\phi H1 = \phi H1SL, \phi H1SR, \phi H1BL, \phi H1BR$   
 $\phi H2 = \phi H2SL, \phi H2SR, \phi H2BL, \phi H2BR$
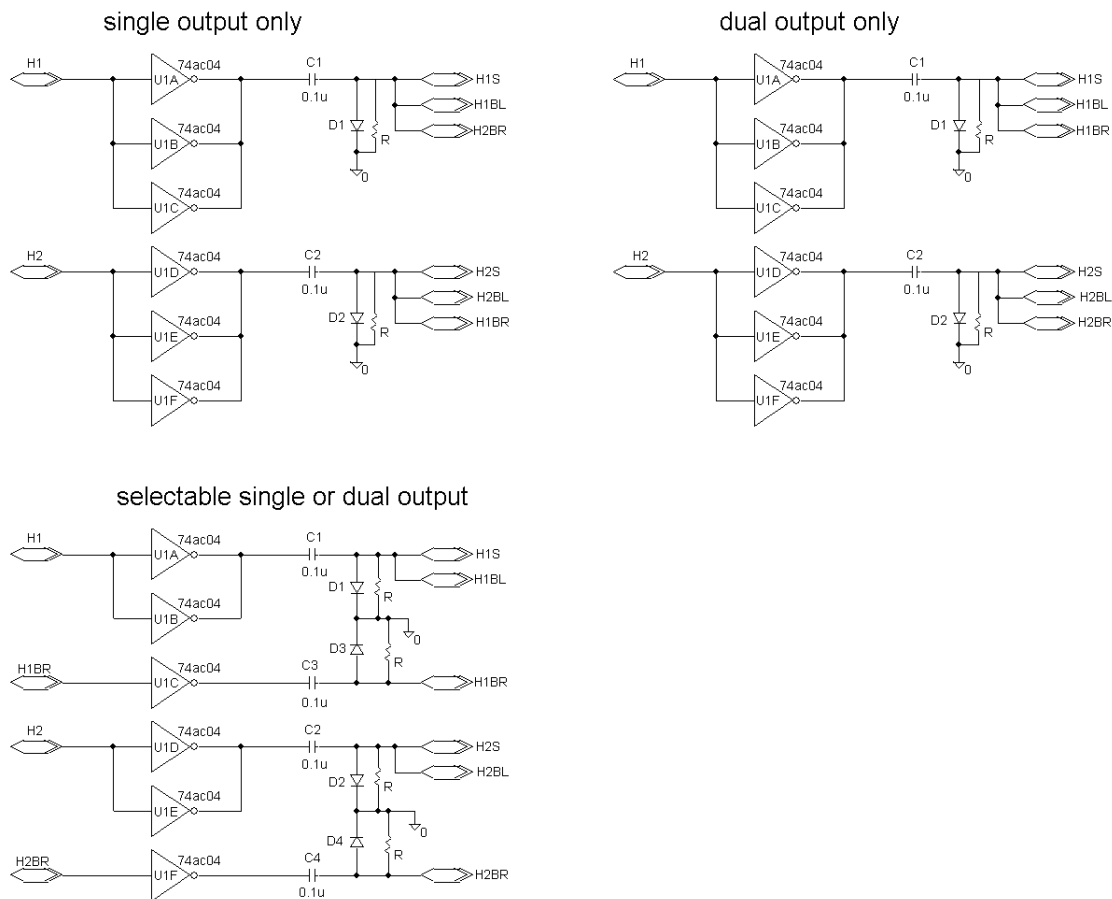
## HCCD Clock Driver

The HCCD clock inputs should be driven by buffers capable of driving the sensor capacitance and having a full voltage swing of at least 4.75V. A 74AC04 or equivalent is recommended to drive the HCCD. The HCCD requires a low-level voltage in the range of  $-5V$  to  $-4V$ . A negative clock level is easily obtained by capacitive coupling and a diode to clamp the high level to GND.



The inputs to the above circuits,  $\phi H1$  and  $\phi H2$ , are 5-V logic from the timing generator (e.g., the Kodak KSC-1000 support chip or a programmable gate array). If the camera is to have selectable single or dual output modes of operation, then the timing logic needs to generate two extra signals for the  $\phi H1BR$  and  $\phi H2BR$  timing. For single output mode, program the timing such that  $\phi H1BR = \phi H2$  and  $\phi H2BR = \phi H1$ . For dual output mode program the timing such that  $\phi H1BR = \phi H1$  and  $\phi H2BR = \phi H2$ .

The resistor in the above circuit, R, is there to ensure the high level of the diode-clamped signal does not start up below zero volts. The value of R should be in the range of  $47k\Omega$  to  $200k\Omega$ . If the timing to the clock driver is stopped in the low level state for more than the horizontal retrace time, then the coupling capacitor will begin to

discharge through the resistor R. If the clocks are stopped during a long integration time, while no image is being read out, then stop both clocks in the high level state to prevent the capacitor from discharging.

To prevent signal cross talk (through clock edge jitter), do not mix the horizontal clock buffers in the same package as other timing signals.