

EDN[®]

VOICE OF THE ENGINEER

APRIL

3

Issue 7/2008
www.edn.com



Apple slashes NAND-flash orders Pg 74

EDN.comment: Hello, EDN readers Pg 10

Signal Integrity:
Designing a split termination Pg 26

Analog Domain:
Honest energy Pg 28

Design Ideas Pg 65

HEADS AND TAILS:
design RF amplifiers for linearity and efficiency

Page 31

Boost efficiency
for low-cost fly-back converters

Page 47

Critical
clock-domain-crossing bugs

Page 55

LAYING
SEAMLESS
WIMAX
FABRIC

page 40

CLICK HERE TO

RENEW

your FREE **magazine**
subscription

CLICK HERE TO

START


a FREE **e-newsletter**
subscription

Picture-Perfect Ultrasound AFE

50% Smaller, 40% Less Noise, 20% Less Power

TI's new **AFE5805** Analog Front End provides low power consumption (122mW/ch) and low noise (0.85nV/ $\sqrt{\text{Hz}}$ at 2 MHz, 20dB) in an ultra-small (15x9mm) BGA package. It is the first device in TI's new AFE58xx family that integrates multiple high-performance analog components providing superior image quality for a wide range of ultrasound equipment. **That's High-Performance Analog >>Your Way™.**

Lowest noise for superior image quality

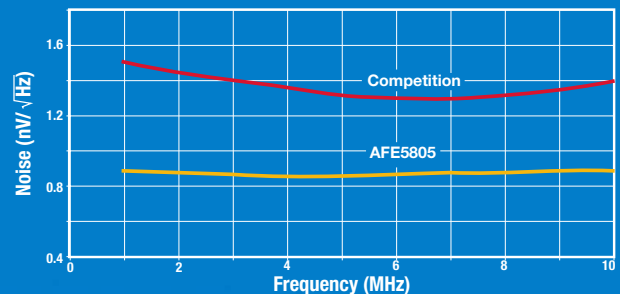

www.ti.com/ultrasound 1.800.477.8924 ext. 14443
Get Samples and Evaluation Modules



WHAT YOU WANT, WHEN YOU NEED IT.



Digi-Key[®]

CORPORATION



**Hundreds-of thousands*
of parts in stock. Visit
www.digikey.com today
to see how many!**

Quality Electronic Components, Superior Service

**Digi-Key Corporation purchases all product
directly from its original manufacturer.**

**www.digikey.com
1.800.344.4539**

*New product added daily.
© 2008 Digi-Key Corporation


701 Brooks Ave. South • Thief River Falls, MN 56701 • USA



Enter the New World of Bourns

Automotive Sensors
Circuit Protection Solutions
Magnetic Products
Microelectronic Modules
Panel Controls & Encoders
Precision Potentiometers
Resistive Products

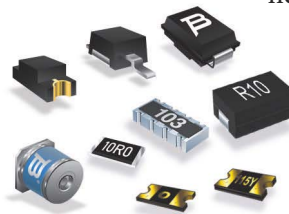The world of Bourns has grown. An expanding world focused on exceeding our customers' needs. New innovative products and technologies. Expanded application solutions. Plus a worldwide team of technical experts to facilitate the design process and solve tough application problems. All provided to help customers shorten design cycles and achieve faster time-to-market.



At Bourns, we have grown to serve you better. Step in – explore the new world of possibilities from Bourns today:

www.bourns.com/newworld

▶ Bourns - the company you have relied on for more than 60 years.

BOURNS®

Built on Trust...Based on Innovation

Energy-Efficient Power Solutions

High-Performance Analog >>Your Way™

At TI, we've been helping our customers design high-performance power conversion products that meet strict efficiency regulations for over 20 years. TI can help you get to market fast with a winning, energy-saving design. **That's High-Performance Analog >>Your Way.**

UCC28600	Green Mode PWM Controller	Enables off-line power supplies to meet light-load efficiency standards
TPS40140	Stackable Multiphase Controller	Improves point-of-load efficiency in power-hungry data centers and telecom equipment
TPS2410	ORing FET Power Rail Controller	Replaces low-efficiency diodes with high-efficiency, high-reliability control and protection solutions
UCC28060	Industry's First Single-Chip Interleaved PFC Controller	Dual phase for high-efficiency, high-power density and easy phase management for light-load efficiency
UCD9112	Digital Controller w/Configurable GUI	Easy-to-use, flexible point-of-load solution for multi-rail power topologies
PTH08T250W	50-A Non-Isolated Power Module w/TurboTrans™ Technology	96%-efficient, stackable, and easy-to-use point-of-load module for servers, wireless infrastructure, datacom and telecom equipment
TMS320F28335	Digital Signal Controller	Highly integrated digital controller improves efficiency of renewable energy systems

www.ti.com/greenpower 1.800.477.8924 ext. 1422


Get Samples, Evaluation Modules and the Power Management Selection Guide



PowerWise® Equalizer Family Features Industry's First Quad 10 Gbps Equalizer

national.com/lvds

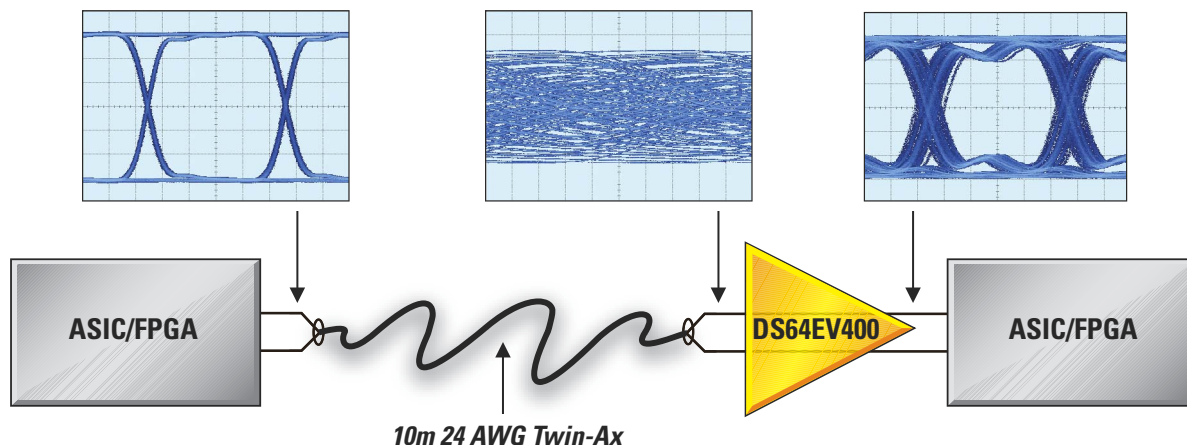Equalizer Family Delivers Lowest Jitter at Lowest Power



	Product ID	Description	Supply Voltage	Channels	Package
NEW	DS32EV400	Quad 1-5 Gbps general purpose CML equalizer	2.5-3.3	4	LLP-48
NEW	DS64EV400	Quad 5-10 Gbps general purpose CML equalizer	2.5-3.3	4	LLP-48
NEW	DS32EV100	Single Channel 1-5 Gbps general purpose CML equalizer	2.5-3.3	1	LLP-14
NEW	DS64EV100	Single Channel 5-10 Gbps general purpose CML equalizer	2.5-3.3	1	LLP-14
NEW	DS50EV401	Quad 2.5-8 Gbps PCI Express equalizer	2.5-3.3	4	LLP-48
	DS16EV5110	HDMI/DVI equalizer supporting 2.25Gbps data rates	3.3	3 + CLK	LLP-48
	DS25BR110	DC to 3.125 Gbps LVDS equalizer	3.3	1	LLP-8
	DS38EP100	1-5 Gbps 7 dB boost, bi-directional Power-saver equalizer	NA	1	LLP-6
	DS80EP100	5-12 Gbps 7 dB boost, bi-directional Power-saver equalizer	NA	1	LLP-6

Applications

Copper Cable Extension, Active Cable Assemblies, FR4 Backplane Extension, HDMI, DVI, Data Center (XAUI, Infiniband, 802.3ap), Storage Area Networks (Fiber Channel, SATA, SAS), and PCI Express

For samples, datasheets, and more information about PowerWise products, visit:

national.com/lvds

Or call: 1-800-272-9959

 **National**
Semiconductor
The Sight & Sound of Information

EDN

contents

4.3.08



Laying seamless WiMax fabric

40 Chip sets are emerging that add WiMax capability to mobile PC and cell-phone applications, while lab and production-test equipment evolves to keep pace.
by Rick Nelson, Editor-in-Chief, and Ron Wilson, Executive Editor



Heads and tails design RF amplifiers for linearity and efficiency

31 Base stations and handsets need RF amplifiers with high linearity and efficiency. With some clever techniques, designers can align these mutually exclusive goals.
by Paul Rako, Technical Editor


Boost efficiency for low-cost flyback converters

47 Many devices employ flyback converters because of their simplicity and low cost—not their stellar efficiency. But don't too quickly eliminate flybacks from your list of options. With a few little-known tricks, you can improve power loss by nearly 10%.
by John Betten and Brian King, Texas Instruments

Critical clock-domain-crossing bugs

55 Awareness of CDC issues, along with the use of good design practices and proven EDA tools for CDC verification, can avoid costly silicon re-spins and significantly improve time to market.
by Shaker Sarwary and Saurabh Verma, Atrenta Inc

DESIGN IDEAS

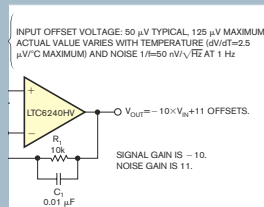

65 Chop the noise gain to measure an op amp's real-time offset voltage

66 Simple analog circuit provides voltage clipping and dc shifting for flash ADC


68 Compact laser-diode driver provides protection for precision-instrument use

70 Current source makes novel Class A buffer

Delta-Sigma ADCs

High Performance, Broad Portfolio—Enable Your Design

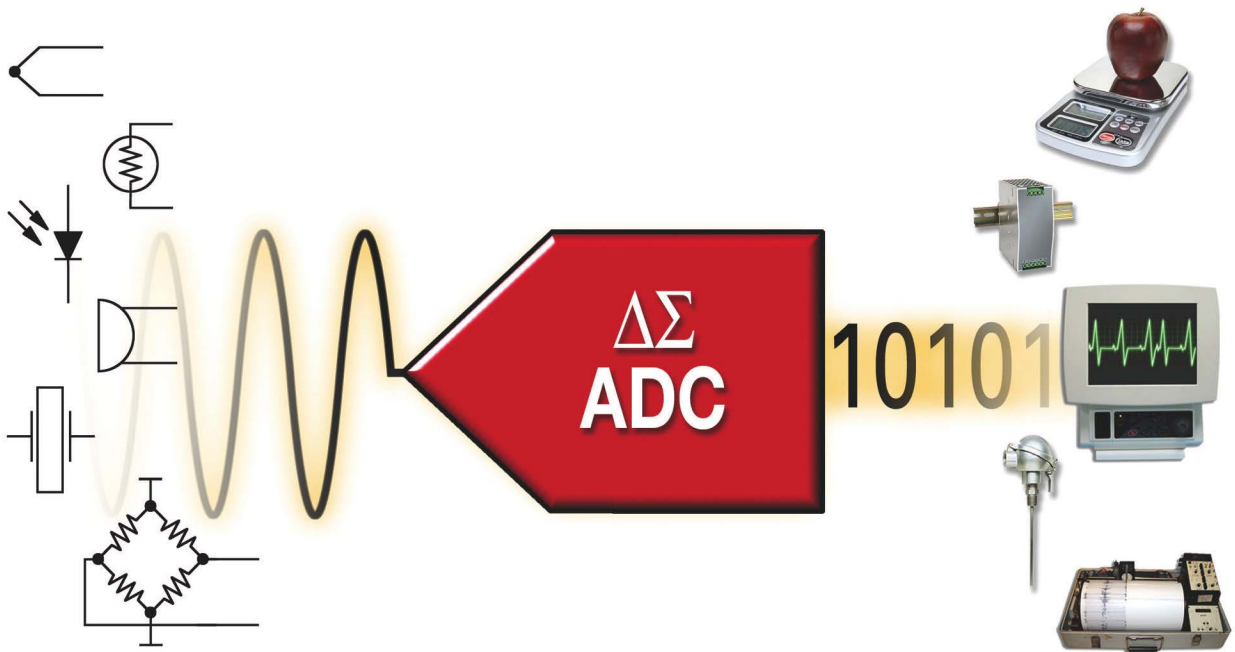High-Performance Analog >>> **Your Way™**



Low noise. Wide bandwidth. High speed. When your design needs best-in-class delta-sigma ADC performance, look to TI for high-performance devices to meet your design challenges.

Device	Description
ADS1110	Tiny, low power, 16-bit $\Delta\Sigma$ ADC with onboard reference and PGA (G=1, 2, 4, 8) in SOT: 2.048V $\pm 0.05\%$ accuracy, 5ppm/°C drift
ADS1226	Low-cost, easy-to-use 24-bit $\Delta\Sigma$ ADC: dedicated START pin, 100SPS data rate, 4 μ V _{RMS} low noise
ADS1232	Ideal for weigh scales: 24-bit $\Delta\Sigma$ ADC, up to 23.5 effective bits, onboard PGA (G = 1, 2, 64, 128), 10SPS or 80SPS data rates
ADS1256	Best-in-class 23-bit, noise-free $\Delta\Sigma$ ADC: 8 channels, 30kSPS and programmable digital filter (averaging)
ADS1258	Fastest channel cycling, 24-bit, 125kSPS $\Delta\Sigma$ ADC: Measure all 16 channels in <675 μ s
ADS1278	Widest bandwidth, simultaneous sampling: 24-bit, 8-channel $\Delta\Sigma$ ADC, 128kSPS, 106dB SNR, $\pm 0.0003\%$ INL
ADS1281	Ultra-low distortion 24-bit $\Delta\Sigma$ ADC: 130dB SNR and -122dB THD while consuming only 12mW of power, $\pm 0.00006\%$ INL
ADS1610	Fastest 16-bit $\Delta\Sigma$ ADC: 10MSPS, 86dB SNR, 5MHz wide and flat bandwidth
DDC232	Highly integrated, current-input 20-bit $\Delta\Sigma$ ADC for measuring photodiodes, X-ray security and CT scanners: 32 channels




www.ti.com/deltasigma 1.800.477.8924 ext. 1434
Get Datasheets, Samples and Evaluation Modules





- 17 Intel launches 45-nm quad- and dual-core processors for embedded-system applications
- 17 Analog-output module extends embedded I/O
- 18 Mixed-signal chip combines audio, power
- 18 LCD controller tackles harsh environments
- 20 Processor combines Cortex-A8 core with graphics and digital-signal processing

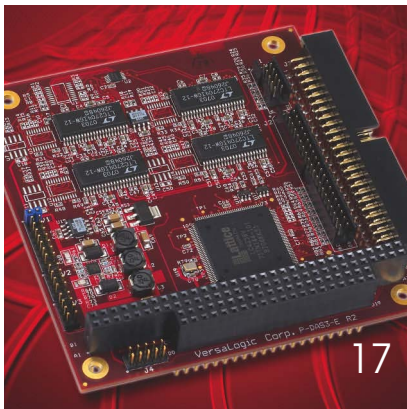
- 20 MOSFETs get their 15 minutes of fame at APEC
- 22 1-μHz to 240-MHz generator produces precision pulses, 14-bit arbitrary waveforms, and more
- 22 Fast Spice simulator targets digital, mixed-signal, and analog designs
- 24 **Research Update:** Stanford tries nanotubes for on-chip interconnect; Georgia Tech studies off-chip-interconnect issues



17



76

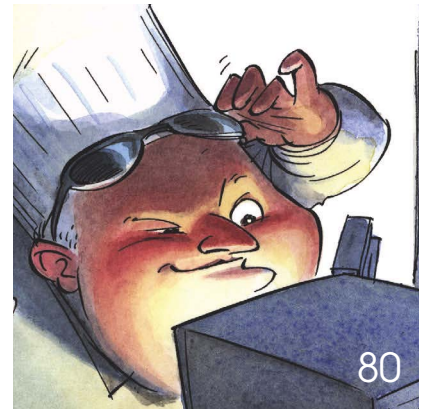

80

DEPARTMENTS & COLUMNS

- 10 **EDN.comment:** Hello, *EDN* readers
- 26 **Signal Integrity:** Designing a split termination
- 28 **Analog Domain:** Honest energy
- 74 **Supply Chain:** Apple sneezes, flash industry gets sick; Sunnier prospects for polysilicon; EPA releases Energy Star guidelines for servers
- 80 **Tales from the Cube:** Contamination: not your usual suspects

PRODUCT ROUNDUP


- 76 **Discrete Semiconductors:** MOSFET/Schottky-barrier-diode devices, insulated-gate-bipolar transistors, power MOSFETs, and more
- 77 **Integrated Circuits:** High-definition-digital-TV platforms, video decoders, triple-core processors, audio-DSP kits, QVGA modules, and more

EDN® (ISSN#0012-7515), (GST#123397457) is published biweekly, 26 times per year, by Reed Business Information, 8878 Barrons Blvd, Highlands Ranch, CO 80129-2345. Reed Business Information, a division of Reed Elsevier Inc, is located at 360 Park Avenue South, New York, NY 10010. Tad Smith, Chief Executive Officer; Mark Finkelstein, President, Boston Division. Periodicals postage paid at Littleton, CO 80126 and additional mailing offices. Circulation records are maintained at Reed Business Information, 8878 S Barrons Blvd, Highlands Ranch, CO 80129-2345. Telephone (303) 470-4445. POSTMASTER: Send address changes to EDN®, PO Box 7500, Highlands Ranch, CO 80163-7500. EDN® copyright 2008 by Reed Elsevier Inc. Rates for nonqualified subscriptions, including all issues: US, \$165 one year; Canada, \$226 one year, (includes 7% GST, GST#123397457); Mexico, \$215 one year; air expedited, \$398 one year. Except for special issues where price changes are indicated, single copies are available for \$10 US and \$15 foreign. Publications Agreement No. 40685520. Return undeliverable Canadian addresses to: RCS International, Box 697 STN A, Windsor Ontario N9A 6N4. E-mail: Subsmail@ReedBusiness.com. Please address all subscription mail to EDN®, 8878 S Barrons Blvd, Highlands Ranch, CO 80129-2345. EDN® is a registered trademark of Reed Elsevier Properties Inc, used under license. A Reed Business Information Publication/Volume 53, Number 7 (Printed in USA).

All the right tools in your hand.

WaveJet® Oscilloscopes

FROM
\$2,950

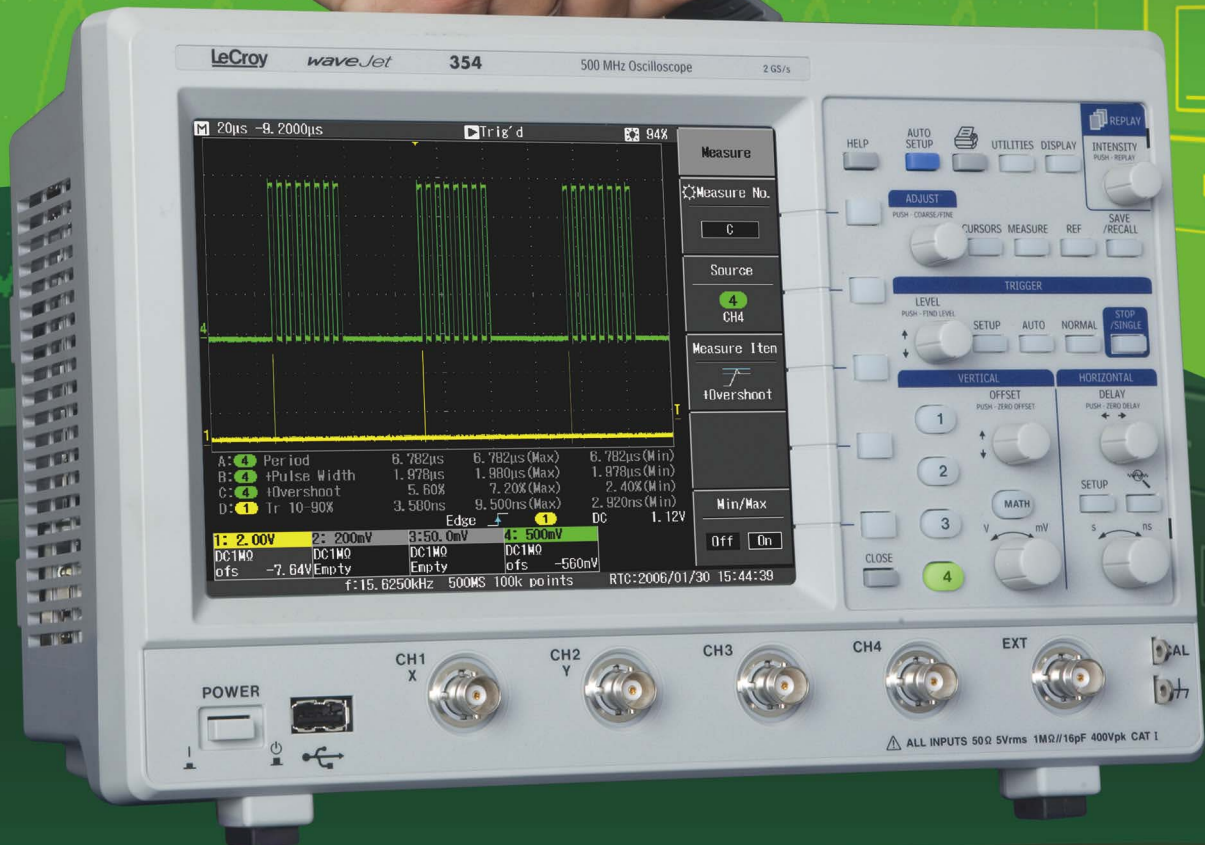

More tools. Better tools. The right tools.


The right tools make debugging faster and easier. The WaveJet 300 Series provides more tools and greater performance than other compact oscilloscopes in the 100 MHz to 500 MHz range.

- Long Memory: 500 k/ch
- Large 7.5" Color Display
- Compact Size, only 4" Deep

- USB Connectivity
- Replay History Mode
- Frequency Counter

www.lecroy.com 1-800-5-LeCroy

LeCroy

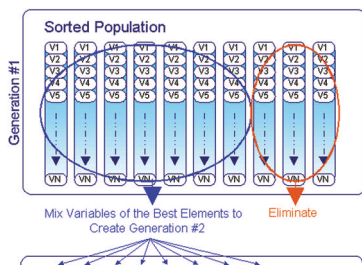

ONLINE ONLY

Check out these Web-exclusive articles:

Genetic algorithm solves thermistor-network-component values

An algorithm employing survival-of-the-fittest principles finds the optimal resistor and NTC thermistor values for applying temperature compensation to an active device.

→ www.edn.com/article/CA6542381

Customizable CPU platform combines DSP, FPGA

→ www.edn.com/article/CA6538964

Intel fleshes out next-gen multicore processors

→ www.edn.com/article/CA6541269

IBM develops tiny nanophotonic switch for optical routing between cores

→ www.edn.com/article/CA6541216

IMEC launches methodology to analyze process variability

→ www.edn.com/article/CA6540826



READERS' CHOICE

A selection of recent articles receiving high traffic on www.edn.com.

Consumer ICs: designing for reliability

Consumers want the latest electronics but only if they'll last longer than the time it takes to take them out of their packages. IC vendors must tackle reliability issues so that their devices will find use in reliable, long-lasting products.

→ www.edn.com/article/CA6535342

LED lighting: Yet more green BS

→ www.edn.com/080403toc1

Audio equalizer features trans-impedance Q-enhancement topology

→ www.edn.com/article/CA6535344

Not so easy to run an LED "bulb" off of a dimmer switch—but here's how

→ www.edn.com/080403toc2

Delta-sigma ADCs in a nutshell, part 3: the digital/decimator filter

→ www.edn.com/article/CA6531581



AWARD WINNER

Congratulations to Senior Technical Editor Brian Dipert, winner of a 54th Annual Jesse H Neal National Business Journalism Award for his blog, *Brian's Brain*. The Neal Awards are among the most prestigious and sought-after editorial honors. The awards committee described *Brian's Brain* as "a rare combination of authoritative tech argument and a clear connection to the business community." Check it out for yourself.

→ www.edn.com/briansbrain

FROM EDN'S BLOGS

Laptop catches fire, but don't blame the battery just yet

From PowerSource, by Margery Conner

Before fingering the lithium-ion chemistry as being faulty, consider that the laptop apparently was sitting on a blanket on an upholstered loveseat, making it likely that the air vents were blocked. Especially for battery-powered designs, this is a good reminder that available ambient air can vary greatly.

→ www.edn.com/080403toc4

DEVmonkey

A new online community featuring development kits, ratings, reviews, news, poll, hands-on videos, and a bunch more resources for design engineers.

APRIL: "Editor's Choice" Series: The DEVmonkey Lab reviews the Renesas Starter Kit for R8C/2D Microcontroller with M16C-Family 16-Bit CPU.

Log on to read the written review, watch the video, and provide your feedback.

www.developmentmonkey.com

Sponsored by:

Electronics Design, Strategy, News

EDN

ElectronicsWeekly

EDN
EUROPE





BY KAREN FIELD, EDITORIAL DIRECTOR

Hello, *EDN* readers!

As a former design engineer at Texas Instruments and, as a reader of this magazine, I can't tell you how excited and proud I am to join the team here at *EDN* as the new editorial director. From the enduringly popular Design Ideas and deep technical articles to new online offerings such as Video Design Ideas and blogs including Senior Technical Editor Brian Dipert's *Brian's Brain* and Technical Editor Paul Rako's

Anablog, it's clear that *EDN*'s editors are committed to delivering the most compelling, useful, and unique content for design engineers. I love that about *EDN*.

In the future, you can expect to continue to get all the things that you love from *EDN*—and more. In my new role, I'll be working with the editorial team to develop innovative content that you won't be able to find anywhere else. Currently, we're exploring different ways to create and present content that's highly relevant and useful to design engineers, including video, flash animation, photo galleries, and searchable databases. We're also committed to in-depth coverage of the topics that you tell us are of highest interest and importance, such as development kits and tools.

In a recent survey of *EDN* readers, 95% of the respondents reported that they bought at least one development kit in the past year. Most bought more than one, with some 10% reporting that they'd purchased five or more kits last year. Development-kit sales in general are up, with some vendors noting increases of 50 to 100% over the past three years. You may wonder why a flurry of interest in development

kits has suddenly occurred. With never-ending pressure to quickly get their designs out the door—and you know this better than I—design engineers increasingly use development kits and boards to prove a concept, learn about software tools, quickly build a prototype, avoid building a PCB (printed-circuit board), and test and evaluate their designs.

In turn, manufacturers and third-party makers have increased their kit offerings, focusing on ease of use, better documentation, and greater performance. And it's no wonder that they're taking these steps: The stakes are huge. They know that there's a high probability that, when engineers have a good experience with a development kit, they'll spec the component into the final design.

The same survey revealed that you not only use a lot of these kits, but also want more information on them, including reviews of kits by engineers who have used them, and an easier way to find information on them. So, I'm pleased to announce that, in response to your wish list, *EDN* has created the *Devmonkey* Web site (www.developmentmonkey.com). We launched it on Feb 1, 2008, and it is

the first Web site to focus exclusively on the latest news and information on development tools for design engineers. Here, you will find the most up-to-date articles on new kits and tools, as well as hands-on reviews of some of the latest kits from our Senior Reviews Editor Jon Titus. A former editor at *EDN*, he's been reviewing kits for years and has unique access to the companies and application engineers who develop them. He also writes the *Devmonkey* blog for the Web site, in which he previews new goodies coming down the pipeline and tips and tricks based on his own experiences with development kits and tools.

A new form of content on the site is our two-minute demo videos, in which Titus reviews kits and describes their key features and capabilities. He also talks about what he's done with a kit that goes beyond the basic documentation. This year, we'll add even more content to the site, including kit reviews from readers and gadgets our readers have designed using a kit. If you have a moment, please check out the *Devmonkey* site. I'd love to get your feedback on the site and on the sorts of features you find most valuable. Please drop me a line at kfield@reedbusiness.com. You can also sign up for the *EDN* e-newsletter on development tools, which brings you the latest *Devmonkey* content each month. To subscribe, go to www.edn.com and click on the "Free e-mail newsletters" button in the upper right corner.

And stay tuned. We have a slew of new ideas in the pipeline that we expect to introduce in the coming year that we hope you're going to like a lot. **EDN**

Contact me at kfield@reedbusiness.com.

MORE AT EDN.COM

 **Go to www.edn.com/080403ed and click on Feedback Loop to post a comment on this column.**

Save more power. Expend less energy.


DATASHEETS, SAMPLES, BUY

TECHNICAL INFORMATION

APPLICATIONS

DESIGN CENTER

SUPPORT

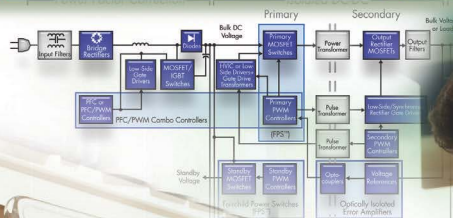

FAEs

AC-DC Conversion

DC-DC Conversion

Evaluation Boards

Online Tools



Your engineering resource for energy-efficient solutions.

Power Factor Correction

PFC Controllers • PFC/PWM Combo Controllers
Low-Side Gate Drivers • MOSFET/IGBT Switches

Isolated DC-DC

PWM Controllers • MOSFETs
Integrated Power Switches (FPS™) • HVICs
Low-Side/Sync Rectifier Gate Drivers
Optically Isolated Error Amplifiers
Integrated Power Modules (SPM™)

Non-Isolated DC-DC

Multi-Phase PWM Controllers • MOSFETs
Integrated Switching Regulators • DrMOS

Energy conservation is a global concern, and power engineers face increasingly difficult design challenges. That's why Fairchild—The Power Franchise®—is committed to providing the industry's most comprehensive portfolio of power components and support services.

From power analog, power discrete, integrated power modules and optoelectronic products to online tools, FAEs and regional centers staffed by experienced power engineers, we have everything you need to minimize energy consumption in power-sensitive applications. Now both your design and your time are energy-efficient.

For more information about Fairchild's energy-efficient solutions, please visit www.fairchildsemi.com/power.

Saving our world, 1mW at a time™

www.fairchildsemi.com

the
power
franchise®

PICO

SPACE SAVING TECHNOLOGY Transformers & Inductors from .19" ht. Over 5000 Standard Thru-Hole Models Surface Mount and

Audio Transformers
Impedance Levels 10 ohms to 250k ohms,
Power Levels to 3 Watts, Frequency
Response $\pm 3\text{db}$ 20Hz to 250Hz. All units
manufactured and tested to MIL-PRF-27.
QPL Units available.

Power & EMI Inductors
Ideal for noise, spike and Power Filtering
Applications in Power Supplies, DC-DC
Converters and Switching Regulators

**Multiplex Data Bus
Pulse Transformers**
Plug-In units meet the requirements
of QPL-MIL-PRF 21038/27
Surface units are electrical equivalents
of QPL-MIL-PRF 21038/27.

Pulse Transformers
10 Nanoseconds to 100 Microseconds. ET
Rating to 150 Volt Microsecond, Manufactured
and tested to MIL-PRF-21038.

**DC-DC Converter
Transformers**
Input voltages of 5V, 12V, 24V And 48V.
Standard Output Voltages to 300V (Special
voltages can be supplied). Can be used as self
saturating or linear switching applications. All
units manufactured and tested to MIL-PRF-27.

**400Hz/800Hz
Power Transformers**
0.4 Watts to 150 Watts. Secondary Voltages 5V
to 300V. Units manufactured to MIL-PRF-27
Grade 5, Class S (Class V, 155°C available).



PICO

Electronics, Inc.

143 Sparks Ave. Pelham, NY 10803 • **Call Toll Free** 800-431-1064 • **Fax:** 914-738-8225

Send for free 180 pg PICO Catalog

See PICO's full Catalog Immediately on the internet

www.picoelectronics.com

E-mail: info@picoelectronics.com



Design Considerations for a Transimpedance Amplifier

Application Note AN-1803

Maithil Pachchigar, Applications Engineer

It's challenging to design a good current-to-voltage (transimpedance) converter using a Voltage-Feedback Amplifier (VFA). By definition, a photodiode produces either a current or voltage output from exposure to light. The Transimpedance Amplifier (TIA) is utilized to convert this low-level current to a usable voltage signal and the TIA often needs to be compensated for proper operation. This article explores a simple TIA design using a 345 MHz rail-to-rail output VFA, such as National's LMH6611. The main goal of this article is to offer necessary information for TIA design, discuss TIA compensation and performance results and analyze the noise at the output of the TIA.

A voltage feedback amplifier modeled as a TIA with photodiode and the internal op amp capacitances is illustrated in *Figure 1*.

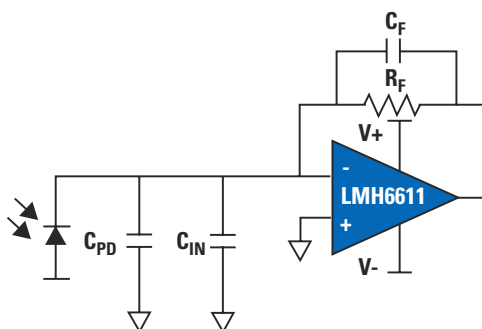


Figure 1. Photodiode Modeled with Capacitive Elements

The LMH6611 allows circuit operation of a low light intensity due to its low-input bias current by using larger values of gain (R_F). The total capacitance (C_T) on the inverting terminal of the op amp includes the photodiode capacitance (C_{PD}) and the input capacitance (C_{IN}). The C_T plays an important role in the stability of the circuit. The Noise Gain (NG) of this circuit determines the stability, and is defined by:

$$NG = \frac{1 + sR_F(C_T + C_F)}{1 + sC_F R_F} \quad \text{Equation 1}$$

$$\text{Where } f_z \approx \frac{1}{2\pi R_F C_T} \quad \text{Equation 2}$$

Figure 2 shows the bode plot of the noise gain intersecting the op amp open-loop gain (A_{OL}). With larger values of gain (R_F), C_T and R_F create a zero in the transfer function. At higher frequencies, transimpedance amplifiers could become inherently unstable as there will be excess phase shift around the loop.

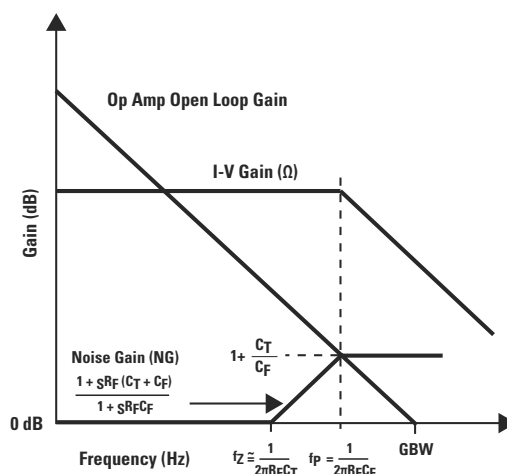


Figure 2. Bode Plot of Noise Gain Intersecting with Op Amp Open-Loop Gain

In order to maintain the stability, a feedback capacitor (C_F) across R_F is placed to create a pole at f_p in the noise gain function. The noise gain slope will be flattened by choosing an appropriate value of C_F for the optimum performance, such that noise gain is equal to the open loop gain of the op amp at f_p . This “flattening” of the noise gain slope beyond the point of intercept of A_{OL} and noise gain will result in a Phase Margin (PM) of 45°. Because at the point of intercept, the noise gain pole at f_p will have a 45° phase lead contribution that gives PM of 45° (assuming f_p and f_z are at least a decade apart).

Equations 3 and 4 theoretically calculate the optimum value of C_F and the expected -3 dB bandwidth:

$$C_F = \sqrt{\frac{C_T}{2\pi R_F(\text{GBW})}} \quad \text{Equation 3}$$

$$f_{-3\text{dB}} = \sqrt{\frac{\text{GBW}}{2\pi C_T R_F}} \quad \text{Equation 4}$$

Equation 4 indicates that the -3 dB bandwidth of the TIA is inversely proportional to the feedback resistor. Therefore, if the bandwidth is important, then the best approach would be to have a moderate transimpedance gain stage followed by a broadband voltage gain stage.

Table 1 shows the measurement results of the LMH6611 with different photodiodes having various capacitances (C_{PD}) at a transimpedance gain (R_F) of 1 k Ω . The C_F and $f_{-3\text{dB}}$ values are calculated from the Equations 3 and 4 respectively.

Table 1. TIA (Figure 1) Compensation and Performance Results

C_{PD} (pf)	C_T (pf)	C_F CAL (pf)	C_F USED (pf)	$f_{-3\text{dB}}$ CAL (MHz)	$f_{-3\text{dB}}$ Meas (MHz)	Peaking (dB)
22	24	5.42	5.6	29.3	27.1	0.5
47	49	7.75	8	20.5	21	0.5
100	102	11.15	12	14.2	15.2	0.5
222	224	20.39	18	9.6	10.7	0.5
330	332	20.2	22	7.9	9	0.8

Note:
 $V_S = \pm 2.5\text{V}$
 $\text{GBW} = 130\text{ MHz}$
 $C_T = C_{PD} + C_{IN}$
 $C_{IN} = 2\text{ pf}$

Figure 3 shows the frequency response for the various photodiodes used in Table 1. The signal-to-noise ratio is improved when all the required gain is placed in the TIA stage, because the noise spectral density produced by R_F increases with the square-root of R_F and the signal increases linearly.

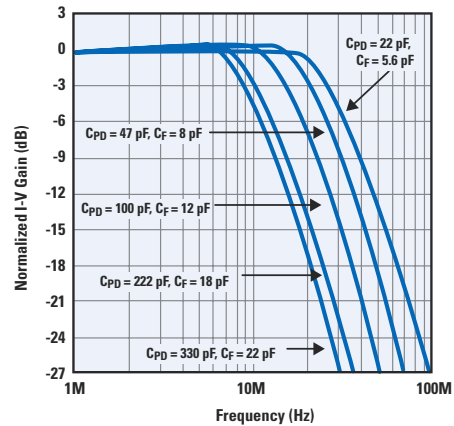


Figure 3. Frequency Response of the LMH6611 for the Various Photodiodes

It is essential to take into account various noise sources. Op amp noise voltage, feedback resistor thermal noise, input noise current, and photodiode noise current do not all operate over the same frequency range while analyzing the noise at the output of the TIA. The op amp noise voltage will be gained up in the region between the noise gain's zero and its pole. The higher the values of R_F and C_T , the sooner the noise gain peaking starts, and therefore its contribution to the total output noise will be larger. An equivalent total-noise voltage is computed by taking the square root of the sum of squared contributing noise voltages at the output of TIA.

To summarize, the total capacitance (C_T) plays an important role in the stability of the TIA and hence it is advantageous to minimize C_T by proper op amp choice, or by applying a reverse bias across the diode at the expense of excess current and noise. This article has also shown that various photodiodes and the compensation method used in the lab confirm a good match between the theory and the bench measurements.

National Semiconductor
 2900 Semiconductor Drive
 Santa Clara, CA 95051
 1 800 272 9959

Mailing Address:
 PO Box 58090
 Santa Clara, CA 95052

National Semiconductor
 The Sight & Sound of Information

For more information, visit:
national.com/analogedge

PRESIDENT, BOSTON DIVISION, REED BUSINESS INFORMATION

Mark Finkelstein, mark.finkelstein@reedbusiness.com
1-781-734-8431

PUBLISHER, EDN WORLDWIDE

Russell E Pratt, 1-781-734-8417;
rpratt@reedbusiness.com

ASSOCIATE PUBLISHER, EDN WORLDWIDE

Judy Hayes, 1-408-345-4437;
judy.hayes@reedbusiness.com

VICE PRESIDENT, EDITORIAL DIRECTOR

Karen Field, 1-781-734-8188;
kfield@reedbusiness.com

EDITOR-IN-CHIEF, EDN WORLDWIDE

Rick Nelson, 1-781-734-8418;
rnelson@reedbusiness.com

EXECUTIVE EDITOR

Ron Wilson, 1-408-345-4427;
ronald.wilson@reedbusiness.com

EDITOR-IN-CHIEF, EDN.COM

Matthew Miller

1-781-734-8446; fax: 1-303-265-3017;
mdmiller@reedbusiness.com

SENIOR ART DIRECTOR

Mike O'Leary

1-781-734-8307; fax: 1-303-265-3021;
moleary@reedbusiness.com

ANALOG

Paul Rako, Technical Editor
1-408-745-1994; paul.rako@reedbusiness.com

EMBEDDED SYSTEMS

Warren Webb, Technical Editor
1-858-513-3713; fax: 1-858-486-3646;
wwebb@edn.com

MASS STORAGE, MULTIMEDIA, PCs AND PERIPHERALS

Brian Dipert, Senior Technical Editor
1-916-760-0159; fax: 1-303-265-3187;
bdipert@edn.com

MICROPROCESSORS, DSPs, TOOLS

Robert Cravotta, Technical Editor
1-661-296-5096; fax: 1-303-265-3116;
rcravotta@edn.com

NEWS

Suzanne Deffree, Managing Editor
1-631-266-3433; sdeffree@reedbusiness.com

POWER SOURCES, ONLINE INITIATIVES

Margery Conner, Technical Editor
1-805-461-8242; fax: 1-805-461-9640;
mconner@reedbusiness.com

SEMICONDUCTOR MANUFACTURING AND DESIGN

Ann Steffora Mutschler, Senior Editor
1-408-345-4436; ann.mutschler@reedbusiness.com

DESIGN IDEAS EDITOR

Charles H Small
edndesignideas@reedbusiness.com

SENIOR ASSOCIATE EDITOR

Frances T Granville, 1-781-734-8439;
fax: 1-303-265-3131;
f.granville@reedbusiness.com

ASSOCIATE EDITOR

Maura Hadro Butler, 1-617-276-6523;
mbutler@reedbusiness.com

EDITORIAL/WEB PRODUCTION MANAGER

Diane Malone, Manager
1-781-734-8445; fax: 1-303-265-3024
Steve Mahoney, Production/Editorial Coordinator
1-781-734-8442; fax: 1-303-265-3198
Melissa Annand, Newsletter/Editorial Coordinator
Contact for contributed technical articles
1-781-734-8443; fax: 1-303-265-3279
Adam Odoardi, Prepress Manager
1-781-734-8325; fax: 1-303-265-3042
CONTRIBUTING TECHNICAL EDITORS
Dan Strassberg, strassberg@edn.off.net
Nicholas Cravotta, editor@nicholascravotta.com

COLUMNISTS

Howard Johnson, PhD; Bonnie Baker;
Joshua Israelsohn; Pollab Chatterjee

PRODUCTION

Dorothy Buchholz, Group Production Director
1-781-734-8329

Kelly Jones, Production Manager
1-781-734-8328; fax: 1-303-265-3164
Linda Leporda, Production Manager
1-781-734-8332; fax: 1-303-265-3015

EDN EUROPE

Graham Prophet, Editor, Reed Publishing
The Quadrant, Sutton, Surrey SM2 5AS
+44 118 935 1650; fax: +44 118 935 1670;
gprophet@reedbusiness.com

EDN ASIA

Raymond Wong, Managing Director/
Publishing Director
raymond.wong@rbi-asia.com
Kirtimaya Varma, Editor-in-Chief
kirti.varma@rbi-asia.com

EDN CHINA

William Zhang, Publisher and Editorial Director
wmzhang@idg-rbi.com.cn
John Mu, Executive Editor
johnmu@idg-rbi.com.cn

EDN JAPAN

Katsuya Watanabe, Publisher
k.watanabe@reedbusiness.jp
Ken Amemoto, Editor-in-Chief
amemoto@reedbusiness.jp



The EDN Editorial Advisory Board serves as an industry touchstone for the editors of EDN worldwide, helping to identify key trends and voicing the concerns of the engineering community.

DENNIS BROPHY

Director of Business Development,
Mentor Graphics

DANIS CARTER

Principal Engineer, Tyco Healthcare

CHARLES CLARK

Technical Fellow, Pratt & Whitney Rocketdyne

DMITRII LOUKIANOV

System Architect, Intel

RON MANCINI

Retired Staff Scientist

GABRIEL PATULEA

Design Engineer, Cisco

DAVE ROBERTSON

Product Line Director, Analog Devices

SCOTT SMYERS

VP Network and System Architecture Division, Sony

TOM SZOLYGA

Program Manager, Hewlett-Packard

JIM WILLIAMS

Staff Scientist, Linear Technology

EDN, 225 Wyman St, Waltham, MA 02451. www.edn.com. Phone 1-781-734-8000. **Address changes or subscription inquiries:** phone 1-800-446-6551; fax 1-303-470-4280; subsmail@reedbusiness.com. For a free subscription, go to www.geffreemag.com/edn. Reed Business Information, 8878 S Barrons Blvd, Highlands Ranch, CO 80129-2345. Include your mailing label.

PICO

**DC-DC Converters
2V to 10,000 VDC Output**

- Over 2500 Std. DC-DC Converters
- Surface Mount
- From 2V to 10,000 VDC Output
- 1-300 Watt Modules
- Isolated/Regulated/Programmable Models Available
- Military Upgrades Available
- Custom Models, Consult Factory

See full Catalog immediately
www.picoelectronics.com

For Engineering Assistance Call Factory or send direct for FREE PICO Catalog
Call toll free 800-431-1064
in NY call 914-738-1400
Fax 914-738-8225

PICO Electronics, Inc.
143 Sparks Ave. Pelham, N.Y. 10803-1889
INDUSTRIAL • COTS • MILITARY

Intersil Analog Solutions

High Performance Analog

intersil
HIGH PERFORMANCE ANALOG

A World of Analog Solutions at Your Fingertips.

Intersil offers a wide selection of power management and mixed signal processing ICs for the consumer, industrial, communication and computing markets.

Intersil continues to innovate with nominations or wins for superior products from EETimes, EDN, and analogZONE during the past year. In power management, Intersil's recognized leadership in computing switching regulation is only a fraction of the story. Intersil has developed a diverse portfolio of PWMs and battery management devices for everything from handhelds, large LCD displays, medical and industrial products.

Go to www.intersil.com for samples, datasheets and support



Analog Mixed Signal:

- Amplifiers
- Communications ICs
- Data Converters
- DCPs
- High Speed Drivers
- Interface ICs
- LCD Drivers
- Light Sensors
- Switches/MUXes/Xpoints
- Timing Circuits
- Video ICs
- Voltage References

Power Management:

- Battery Management
- Bridge Drivers
- Digital Power
- Display Power ICs
- Integrated FET Regulators
- Hot Plug Controllers
- Power MOSFET Drivers
- Power Supply Support
- Supervisors
- Switching Regulators

Intersil – An industry leader in Switching Regulators and Amplifiers.

©2007 Intersil Americas Inc. All rights reserved. The following are trademarks or services marks owned by Intersil Corporation or one of its subsidiaries, and may be registered in the USA and/or other countries: Intersil (and design) and I (and design).


intersil
HIGH PERFORMANCE ANALOG

pulse

INNOVATIONS & INNOVATORS

Intel launches 45-nm quad- and dual-core processors for embedded-system applications

Intel Corp is shipping quad- and dual-core processors that the company based on its high-k-metal-gate-transistor formula and manufactured on its 45-nm process. The new processors, which include the quad-core Xeon 5400 series and the dual-core Xeon 5200 series combine with Intel's power-optimized 5100 memory-controller-hub chip set to create the first 45-nm CPU platforms for thermally constrained, bladed systems, according to the company. When using Intel's 5000P chip set, the 45-nm processors target high-performance, memory-intensive applications, such as storage, routers, security, and medical equipment, as well as communications applications, including IMS (Internet Protocol-

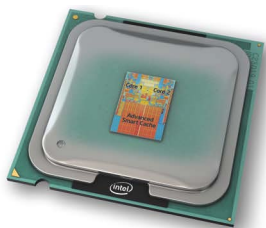

The quad-core Xeon 5400 series and the dual-core Xeon 5200 series combine with Intel's power-optimized 5100 memory-controller-hub chip set to create the first 45-nm CPU platforms for thermally constrained bladed applications.

multimedia) subsystems.

Intel claims that its hafnium-based, high-k-metal-gate-transistor formula reduces power consumption, increases switching speed, and offers greater transistor density than

the company's 65-nm manufacturing technology. The 45-nm CPU-based platforms target a maximum power envelope of 200W, such as those for AdvancedTCA (Advanced Telecommunications Computing Architecture) and for NEBS (network-equipment-building-system) Level 3 requirements. Telecommunications company Ericsson (www.ericsson.com) plans to introduce its quad-core Xeon-processor-based IMS/core network nodes and application servers to allow operators and service providers to host more subscribers in a smaller footprint and to lower the total cost of ownership and environmental impact. The processing head room will also allow the development of the next generation of IMS ser-

vices, according to Magnus Furustam, vice president and head of Ericsson's product-area core and IMS. To accelerate this innovation, Ericsson and Intel are promoting the benefits of IMS to the global communications-developer community.

Intel offers life-cycle support for seven years for the 5200 series, which includes the E5240, E5220, and L5238, and the 5400 series, which comprises the E5440 and L5408. This support represents a two-year increase from the previous minimum. The 45-nm processors with extended-life-cycle support are available now at prices of \$321 to \$690. The dual-core, 35W Xeon L5238 processor is now available, and the 5100 chip set, also available now, sells for \$76.

—by Ann Steffora Mutschler
▷ Intel, www.intel.com.

Analog-output module extends embedded I/O

Targeting applications such as process control, data monitoring and collection, security and medical-equipment design, VersaLogic's new VCM-DAS-3 PC/104 analog-output module offers a convenient and cost-effective method for adding I/O functions in single-board-embedded-computing applications. The ROHS-compliant PC/104 module features 16 channels of 12-bit analog output and 24 digital-I/O lines. In addition, the VCM-DAS-3 operates in an extended-temperature range of -40 to $+85^{\circ}\text{C}$.

Enhanced features include independently programmable output ranges, software calibration, the ability to reset to zero scale on power-up, and readback of DAC and span codes for simplified setup. Legacy features include 8-bit-ISA (industry-standard-architecture)-bus compatibility, jumper-configurable output ranges in groups of eight, and the ability to reset to midscale on power-up. Prices for the DAS-3 start at approximately \$400 (OEM quantities).—by Warren Webb

▷ VersaLogic Corp, www.versalogic.com.



The PC/104 VCM-DAS-3 module features 16 channels of 12-bit analog output and 24 digital-I/O lines to support many embedded-computing applications.

Mixed-signal chip combines audio, power

Wolfson Microelectronics has introduced the AudioPlus product line, which will combine the company's expertise in high-quality audio for portable products with a power-management subsystem. Wolfson has combined functions from both of these domains in a single mixed-signal chip. The WM8350, the first product in the family, comprises an audio codec with a suite of regulators and dc/dc converters that will meet all of the power-management needs of a typical portable product, such as a mobile handset or media player. On the audio side, a high-fidelity audio codec has mixing capabilities, pop and click suppression, and signal/noise performance of 98 dB for its DAC at -84-dB THD (total harmonic distortion). The audio chain's ADC achieves SNR (signal-to-noise ratio) of 95 dB at -80 dB THD.

The chip has six analog inputs, two stereo analog outputs, and two monophonic line outputs; it also features on-chip headphone amplifiers that drive 20 mW into 16 Ω with THD of -70 dB. Power-management functions switch and regulate multiple voltage lines. You can program four 2-MHz dc/dc step-down (buck)

Combining these mixed-signal functions on one chip can save 25% in external-component count and 50% in board area.

converters to provide 0.85 to 3.4V in 25-mV steps. The converters yield peak efficiency of more than 90%, and they need only a small external inductor and capacitor per line. To generate voltage above the battery line—for display backlighting and for the 5V necessary for USB—two 1-MHz boost converters also achieve more than 90% peak efficiency.

You can program four on-chip, 150-mA, low-noise, low-dropout regulators over 0.9 to 3.3V in 50- or 100-mV steps, depending on the version. To handle the lithium battery that typically powers the class of products that Wolfson has in mind for this chip, a single-cell charger—programmable for different cell voltages—has trickle and fast-charging modes. The charger finds its supply from USB or ac/dc source, as avail-

able, and allows product operation while charging an empty battery.

The chip has 13 I/O pins that you can use to control system functions: You can program, either at start-up or during operation, all of the outputs to set power-up and -down sequences using a dedicated onboard controller. The chip occupies a 129-pin, 7 \times 7-mm BGA package with a 0.5-mm ball pitch. Wolfson acknowledges that, if you use all of the regulation functions at rated levels, the chip will dissipate 1 to 2W but says that you can use all of the lines together and stay within the chip's fully protected operating zone.

Combining these mixed-signal functions on one chip can save you 25% in external-component count and 50% in board area, the company says. The chip's designers synchronized audio and dc/dc-converter clocks to avoid on-chip-interference effects, but Wolfson claims that this step turned out to be largely unnecessary. Wolfson's expertise in physical and substrate phenomena on mixed-signal processes minimized unwanted effects.

—by Graham Prophet
▶ Wolfson Microelectronics, www.wolfsonmicro.com.

LCD CONTROLLER TACKLES HARSH ENVIRONMENTS

Digital View recently introduced the HE-1920 COTS (commercial-off-the-shelf) LCD controller. The fully buffered, multisynchronous interface controller provides analog and digital connections for a range of TFT (thin-film-transistor)-LCD panels with resolutions to 1920 \times 1200 pixels. It features full-screen image expansion of lower resolutions, image-flip and -invert functions, and onscreen picture-in-picture functions.

The \$269 (1000) HE-1920 also features a 16-bit bus connector that permits developers to create proprietary hardware interfaces for the controller. The interfaces provide software-managed selection pins to manage multiple input configurations, including optical inputs and additional ports. The ROHS-compliant HE-1920, targeting military and rugged industrial applications, features silicon-resin conformal coatings, an operating-temperature range of -40 to +80°C, and calculated MTBF greater than 100,000 hours.

—by Warren Webb
▶ Digital View, www.digitalview.com.

04.03.08

DILBERT By Scott Adams



The rugged HE-1920 COTS LCD controller supports high-resolution and high-definition formats in military or industrial applications.

ICs that enable world-class diagnostics for any patient, anywhere.



Continua[®]
HEALTH ALLIANCE

ADI is a member of Continua Health Alliance, an international group of technology, medical device, and health and fitness industry leaders, dedicated to making personal telehealth a reality.

Our newest medical innovations



AD9271: 8-Channel Ultrasound Receiver

Combined LNA, VGA, AAF, ADC blocks reduce signal path size by 50%, power by 25%. Enables a new level of patient care with accurate images in battery-powered equipment for nontraditional environments.



AD8339: Doppler Phase Shifter

Replaces crosspoint switches and analog delay lines, saving up to 75% of board space, 30% of power consumption. Allows increased channel density and CW Doppler capabilities in portable equipment.



AD7982: 1 MSPS, 18-Bit, 7 mW ADC

Combines high accuracy, 95% less power, 80% less space than other ADCs. Enables patients to carry their cell-phone sized heart monitor all day long during their hospital recovery.



ADuM240x: iCoupler[®] 4-Channel Digital Isolator

Replaces optocouplers with an integrated solution to reduce costs and space up to 60%. Multiple channels of 5 kV reinforced insulation in a single package simplifies design, improves reliability. Approved for medical grade isolation per IEC 60601-1.

User experience defines the design; ADI defines the possibilities

With Analog Devices ICs inside their designs, medical engineers are dramatically improving the diagnostic experience for patients and practitioners everywhere. That's because ADI offers an industry-leading portfolio of standard and application-tuned amplifiers, data converters, microcontrollers, MEMS, low drop out regulators, and digital isolators with unequalled performance, size, cost, and power advantages. From imaging to monitoring to instrumentation, from medical to consumer to communications—wherever user experience defines the design, ADI is there.

To experience what Analog Devices ICs can do for your designs, visit www.analog.com/medical-ad1.



analog is everywhere.™

www.analog.com/medical-ad1



**ANALOG
DEVICES**

Processor combines Cortex-A8 core with graphics and digital-signal processing

Texas Instruments' latest OMAP (Open Multimedia Applications Platform) processors integrate a superscalar, 600-MHz ARM (www.arm.com) Cortex-A8 core with DSP functions, HD (high-definition)-video acceleration, and 2- and 3-D graphics engines. The devices, which can operate with Windows CE or Linux operating systems, target applications with graphics interfaces and video capabilities for power-constrained products, such as handheld devices for home management and patient monitoring, as well as GUIs for consumer and home appliances.

The entry-level device of the family, the OMAP3503,

is available for sampling and includes USB 2.0 HS (high-speed)-compliant OTG (On-The-Go) controllers with two additional USB-host controllers. It also includes a display subsystem with support for PIP (picture in picture), color-space conversion, rotation, and resizing. All the devices include interface support for LCDs, SDTVs (standard-definition televisions), and HDTVs (high-definition televisions) and support for LPDDR (low-power-double-data-rate), NOR, and NAND memories, along with SRAM and pseudoSRAM. The OMAP3503 is available for \$19.95 (10,000) in a 0.4-mm-pitch package.

The OMAP3515 and 3530

add a 2- and 3-D graphics engine that supports Open GL ES (graphics language for embedded systems) 2.0 graphics based on Imagination Technologies' (www.imgtec.com) PowerVR SGX graphics accelerator that can deliver 10 million polygons/sec. The OMAP3530 adds a 64x+ DSP core and HD-video accelerators that can support performance to MPEG-4 SP with 720p decoding at 30 frames/sec. The OMAP3525 omits the Open GL ES 2.0 engine, but it includes the C64x+ DSP and HD-video accelerator of the OMAP3530 processor.

These processors use TI's SmartReflex technology, which allows the systems to dynami-

cally control the voltage, frequency, and power consumption based on activity. The OMAP35x evaluation module includes an OMAP3503 processor with a Linux board-support package based on the 2.6.22 kernel, peripheral drivers, a U-boot for boot loading, and a Busybox-based root-file system. The \$1499 evaluation module supports Ethernet, USB 2.0, SDIO (secure digital input/output), I²C, JTAG, keypad connectivity, and daughtercards. It sports S-video output via NTSC/PAL (National Television System Committee/phase-alternation-line) and YpbPr/RGB, and it can connect with CompactFlash, SD/MMC (secure-digital/multimedia-card), and DDR memories.


—by Robert Cravotta

► **Texas Instruments**, www.ti.com.

MOSFETs get their 15 minutes of fame at APEC

One thing you can count on at the power-conversion industry's annual APEC (Applied Power Electronics Conference) is that MOSFETs will feature prominently. This year's conference, which took place last month in Austin, TX, was no exception, with new announcements from Infineon, Fairchild, and Toshiba, among others.

Infineon's 900V superjunction MOSFETs target high-efficiency SMPS (switched-mode-power-supply), industrial, and solar-energy applications. Infineon claims that the CoolMOS power-MOSFET family overcomes the "silicon limit," a characteristic of MOSFET semiconductors in which doubling of voltage blocking capability leads to a fivefold increase in on-resistance. In overcoming the silicon limit, the CoolMOS devices achieve the industry's lowest on-resistance per package type: 0.12 Ω in a TO-247 package, 0.34 Ω in a TO-220 package, and 1.2 Ω in a D-Pak. The company claims that these figures are at least 75% lower than those for conventional 900V MOSFETs. The volume price for a 120-m Ω part in a TO-247 package is less than \$3.50.

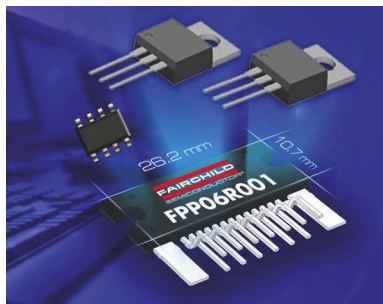

Fairchild's Power-SPM FPP06R001 synchronous-rectifier module offers 10% lower on-resistance and 16% less stray inductance than comparable discrete designs.

Using discrete MOSFETs on a board can increase manufacturing costs and resistance between parts. Fairchild attacks this problem by incorporating two PowerTrench MOSFETs and a high-current gate driver into its EPM15-packaged Power-SPM FPP06R001, which replaces as many as 10 discrete components. Fairchild claims the advanced package accounts for 10% lower on-resistance and 16% lower stray inductance than comparable discrete

approaches. The devices cost \$5.

Toshiba announced a family of high-speed switching MOSFETs, which the company based on its U-MOS VI-H sixth-generation trench process. The new devices enable increased power efficiency by lowering on-resistance and increasing switching speed through lower gate charge and lower gate resistance. The new MOSFETs also feature aluminum-strap connections instead of conventional wire-bond technology to further reduce on-resistance. The devices will find use as low-side MOSFETs in dc/dc-converter applications. Features include a maximum drain-to-source voltage of 30V, a maximum drain current of 50A, and a typical on-resistance of 2 m Ω . Packaging options include a low-profile SOP Advance measuring 5×6×0.95 mm. Prices start at 65 cents.

—by Margery Conner

► **Applied Power Electronics Conference**, www.apec-conf.org.

► **Fairchild**, www.fairchildsemi.com.

► **Infineon**, www.infineon.com.

► **Texas Instruments**, www.ti.com.

► **Toshiba**, www.toshiba.com.

Babies, bouquets, and big events— courtesy of Analog Devices ICs.



Our newest camera innovations



AD9920A: Highly Integrated Analog Front End (AFE)

Low noise image capture helps to deliver higher quality images at higher ISO settings. This high performance AFE consumes 50% less power than competitive AFEs.



SSM2301: Fully Integrated, High Efficiency Class-D Audio Amplifier

Our low power Class-D audio amplifier combines the ability to efficiently deliver more power out, with excellent THD and SNR audio fidelity, for a better remote playback experience.



ADV7520NK: 80 MHz, HDMI Transmitter

This HDMI transmitter enables faithful display of your high resolution photos on HDTV and consumes a fraction of the standby current of competitive solutions.

Digital still cameras are all about the user experience—that's why more than half have ADI inside

Crisp images. Clear remote audio. Long battery life. When the leading manufacturers of digital still cameras (DSCs) seek to deliver the best user experience, they turn to Analog Devices for its proven credentials as an active partner on the design team. Our years of experience and applications expertise help manufacturers bring the newest DSCs to market on time and on budget. But it's not only camera designers and users who benefit from our extensive portfolio of high performance analog and mixed signal ICs—we're also at the forefront of medical, automotive, communications, and industrial technologies. Wherever user experience defines the design, Analog Devices defines the possibilities.

To experience what Analog Devices ICs can do for your designs, call 1-800-AnalogD or visit www.analog.com/digitalcameras.



analog is everywhere.™

www.analog.com/digitalcameras



1- μ Hz to 240-MHz generator produces precision pulses, 14-bit arbitrary waveforms, and more

Design and test engineers are under increasing pressure to quickly bring high-quality products to market and differentiate those products from their competition. Achieving these objectives requires new test protocols and new classes of instruments, says Alois Hauk, vice president and general manager of digital-photonic test at Agilent Technologies, which has introduced what the company calls the industry's first generator to combine superior signal quality with the ability to produce such a wide variety of waveforms over such a broad frequency range.

The 81150A pulse/function/arbitrary-waveform/noise generator employs a 512k-sample/channel arbitrary-waveform memory and a 14-bit DAC that operates as fast as 2G samples/sec. The generator can produce signals with repetition rates as low as 1 μ Hz with modulation at frequencies as high as 10 MHz.

The unit, which produces many waveforms greater than 100 MHz and sine waves to 240 MHz, suits use in general-purpose bench tests and advanced serial-data stress tests.

The 81150A provides versatile generation of pulses with tight control over transition times and other parameters; standard, arbitrary, and modulated waveforms; and noise for stress testing. The generator works well with the manufacturer's 5/6/80000 Infiniium real-time oscilloscopes and DCA-J sampling oscilloscope for serial-data testing. Integration of many functions into one instrument minimizes cabling, space, and test-setup time.

Engineers must create ideal and worst-case signals to obtain rapid, accurate insights into designs for such devices as semiconductor circuits, sensors, and modulators. The 81150A's accurate signals help engineers to test their devices—not the signal source.



With 14-bit resolution and outputs from 1 μ Hz for a variety of signals to 240 MHz for sine waves, the compact 81150A may provide all of the capabilities you need for generating precision pulses, functions, arbitrary waveforms, and noise to well beyond 100 MHz.

"When signal fidelity matters, 'just enough' signal quality isn't enough," says Hauk. "Versatile waveforms and the most precise signals are key contributors to developing quality products within a reduced design cycle. The pulse/function/arbitrary-waveform/noise generator supports engineers through each development phase, and the patented noise generator enables a quantum leap in productivity."

The instrument provides both "random" and calibrated,

deterministic noise for repeatable stress tests. (The random noise is not truly random, but you can set the signals to repeat as infrequently as every six to

12 hours; you can also choose much more frequent repetition.) You can define various stress tests simply by adjusting the crest factor, a measure of signal quality equal to the ratio of peak or peak-to-peak-to-rms voltages.

The 81150A features accurate signals that test the device—not the source—with intrinsic jitter of 8-psec rms at any frequency and has 13 standard functions, modulation capabilities to 10 MHz, and more than 80 measurement types. It also has differential output and high-voltage output amplifiers to test state-of-the-art devices. The 81150A is available in one- and two-channel versions; prices start at \$8900.

—by Dan Strassberg

► **Agilent Technologies**, www.agilent.com/find/81150.

FAST SPICE SIMULATOR TARGETS DIGITAL, MIXED-SIGNAL, AND ANALOG DESIGNS

EDA start-up Nascentric Inc has introduced a Fast Spice simulation tool for analog, mixed-signal, and custom digital designs that claims true Spice accuracy and higher speeds than other commercial Fast Spice simulators.

The OmegaSim tool uses a patented current-based SPICE model and engine. It quickly classifies elements in a design, groups them, and then assigns each group to a simulation engine that the company optimized for a particular operation. "Each

of the engines focuses on what it does best," says Rahm Shastry, Nascentric's president and chief executive officer. "The transistor engine is complex, but you don't need the same complexity for interconnect because interconnect is only RLC [resistance/inductance/capacitance]. Thus, the interconnect engine can be much simpler, and interconnect can simulate fast and accurately. The same goes for SRAM-bit cells, which go to an SRAM engine."

OmegaSim also has

multithreaded engines, further speeding simulation. Users can run the tool in digital or analog mode. The digital mode has a submode for verification or analysis. In digital mode operating on one thread, the tool typically runs 10 times faster than other commercial Fast Spice simulators, Shastry claims.

On a multithread platform, such as an Intel (www.intel.com) CoreDuo, the tool can run two times faster. In digital-verification mode, the tool pro-

vides 2 to 4% the accuracy of Spice, and, in digital-analysis mode, the tool provides 1 to 2% the accuracy of Spice.

Nascentric licenses the tools under a thread-based licensing model. It costs \$1200/thread/month or \$12,000/thread/year for the digital-only version. The company offers the mixed-signal tool for \$500 more per thread/month or \$5000 more per thread/year.

—by Michael Santarini

► **Nascentric**, www.nascentric.com.

04.03.08

Stay ahead of the curve.



Tiny Leadless Modules™ vs. Standard SOT Packages

Central's new Tiny Leadless Modules™ (TLM™)

Designed for today's ultra thin electronic products, Central Semiconductor Corp. introduces the Tiny Leadless Module (TLM™) family. These new package types feature lower profile (height) and reduced board space utilization as compared to industry standard SOT packages. Here are several featured devices from this new family:

Rectifiers

Central Type No.	I _F (A)	V _{RRM} (V)	Description	TLM Size L x W x H (mm)	Package
*CTLSH1-40M621H	1.0	40	Single, Schottky	2 x 1.5 x 0.4	TLM621H
CTLSH1-40M832D	1.0	40	Dual, Schottky	3 x 2 x 0.9	TLM832D
CTLSH2-40M832	2.0	40	Single, Schottky	3 x 2 x 0.9	TLM832
CTLSH3-30M833	3.0	30	Single, Schottky	3 x 3 x 0.9	TLM833
CTLSH5-40M833	5.0	40	Single, Schottky	3 x 3 x 0.9	TLM833

Transistors

Central Type No.	I _C (A)	V _{CEO} (V)	Description	TLM Size L x W x H (mm)	Package
*CTLT3410-M621	1.0	40	Low V _{CE(SAT)} , NPN	2 x 1 x 0.8	TLM621
*CTLT7410-M621	1.0	40	Low V _{CE(SAT)} , PNP	2 x 1 x 0.8	TLM621
CTLT853-M833	6.0	200	High Current, NPN	3 x 3 x 0.9	TLM833
CTLT953-M833	5.0	140	High Current, PNP	3 x 3 x 0.9	TLM833

Combo: Low V_{CE(SAT)} Transistor and Low V_F Schottky Rectifier


Central Type No.	Transistor I _C (A)	Transistor V _{CEO} (V)	Rectifier I _F (A)	Rectifier V _{RRM} (V)	TLM Size L x W x H (mm)	Package
CTLM1034-M832D (NPN)	1.0	40	1.0	40	3 x 2 x 0.8	TLM832D
CTLM1074-M832D (PNP)	1.0	40	1.0	40	3 x 2 x 0.8	TLM832D

Central welcomes the opportunity to explore selected, special, or custom devices, upon request.
* Under Development


The TLM Advantage

Standard SOT Package vs. Bottom Contact TLM™

• Board Space Comparison

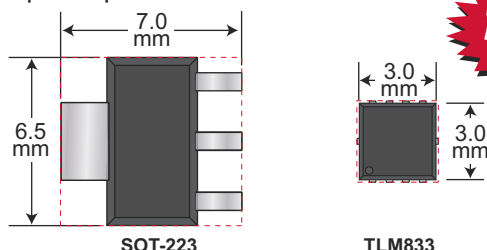

• Low Profile

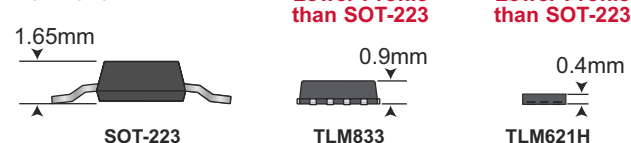

Illustrations of devices are not shown in actual size, but are in proportion to each other. All values are shown as nominal.

Call Today and experience the TLM Advantage.
For Samples visit: www.centrasemi.com/tlm3
or call 631-435-1110



Central Semiconductor Corp.

www.centrasemi.com

TLMs

Small Signal Transistors

Bipolar Power Transistors

Energy Efficient Devices

MDMs

Rectifiers

Diodes

Transient Voltage Suppressors

MOSFETs

RESEARCH UPDATE


BY RON WILSON

Stanford tries nanotubes for on-chip interconnect

A recent paper in *Nano Letters* illustrates both why researchers are so interested in carbon nanotubes as an interconnect medium and why making the nanomaterials a useful reality is such a hurdle. Researchers at Stanford University, working with support from Toshiba (www.toshiba.com) and foundry services from TSMC (Taiwan Semiconductor Manufacturing Co, www.tsmc.com), have successfully connected ring oscillators using nanotubes from a commercial third party. The hit-or-miss results displayed oscillator frequencies as high

as 1 GHz—a first for this new material.

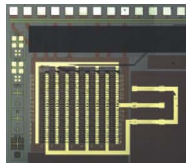TSMC fabricated a die with 256 ring oscillators; one interconnect link was missing from each ring. The Stanford/Toshiba team then attempted to make this one missing connection using commercially manufactured metallic-mode



Carbon nanotubes form connections in ring oscillators in this research die.

nanotubes. They succeeded for 19 of the 256 circuits. Of those 19, 16 of the connections showed impedance low enough to allow the oscillators to operate at frequencies greater than 800 MHz, and one achieved 1.02 GHz. The team used nanotubes measuring 50 to 100 nm in diameter and approximately 5 microns long. HS Phillip Wong, professor of electrical engineering at Stanford and co-author of the paper, observes that significant improvements in both the quality of the nanotube stock and the technology of connecting the tubes to transistor contacts would be necessary before the technique approached production viability. But the experiment shows that the nanotubes can at least achieve reasonable frequencies.

► **Stanford University**, www.stanford.edu.

FEEDBACK LOOP

“There is no one that I trust less to make intelligent economic or engineering decisions than Congress, which, through previous idiotic legislation, is one of the primary contributors to high energy prices by making it nearly impossible to develop new, economically viable sources of energy.”

—Reader Herm Harrison, in *EDN's* Feedback Loop, at www.edn.com/article/CA6531582.


GEORGIA TECH STUDIES OFF-CHIP-INTERCONNECT ISSUES

As chips get faster, off-chip interconnect increasingly looks like a bottleneck to high-frequency signals. This scenario occurs when the signals must traverse not only relatively long distances across a board, but also short hops from the package leads to the board traces. A pair of studies at the Georgia Institute of Technology School of Chemical and Biomolecular Engineering is exploring these challenges.

In the first study, researchers attempted to fabricate an all-copper structure to bond package-lead frames to PCBs (printed-circuit boards), reasoning that such con-

nections should be lower in series resistance than the traditional flow-soldered-bump technology. The team electroplated copper bumps onto both the package pads and the PCB pads. Then, placing the package on the board and aligning the bumps, they immersed the assembly in an aqueous-copper solution, allowing a thin pillar of metallic copper to grow between the bumps.

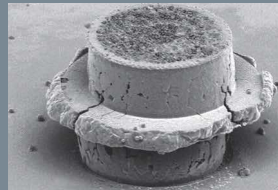The result is too thin to be structurally adequate in that state, so the team then annealed the assembly at 180°C for one hour—not necessarily the most welcome step for process engineers but enough to strengthen the copper pillars. The result



Two copper pillars bond together using a novel fabrication technique. Placing these all-copper connections between computer chips and external circuitry will lead to increased computing speeds (courtesy Tyler Osborn).

is a strong, low-resistance connection.

For board-crossing, the second study experimented with forming conductors with buried air gaps beneath them to reduce parasitic capacitance. The process involves plating copper traces onto an ep-

oxy-fiberglass board and then coating the traces with a layer of sacrificial polymer. A layer of a different polymer then builds up around the traces. A titanium barrier and a top copper layer go over the original traces on top of the sacrificial polymer. The scientists then cook away this sacrificial polymer at 180°C. The result is a multilayer connection of copper, air gap, titanium, and copper.

The team has demonstrated formation of this structure and is working on a version that would in effect form a coaxial cable.

► **Georgia Institute of Technology**, www.gatech.edu.

04.03.08

The Fastest SPI Serial EEPROMs in the Industry



Speed • Quality • Reliability • Availability

Microchip provides SPI serial EEPROMs across a wide memory-density range (1 Kbit - 1 Mbit), which are specified to operate over an extended temperature range (up to 125°C). These devices provide over 1 million erase/write cycles and 200-year data retention.

1 Mb	25AA1024	25LC1024	Up to 20 MHz
512 Kb	25AA512	25LC512	
256 Kb	25AA256	25LC256	
128 Kb	25AA128	25LC128	Up to 10 MHz
64 Kb	25AA640A	25LC640A	
32 Kb	25AA320A	25LC320A	
16 Kb	25AA160A/B	25LC160A/B	
8 Kb	25AA080A/B	25LC080A/B	
4 Kb	25AA040A	25LC040A	
2 Kb	25AA020A	25LC020A	
1 Kb	25AA010A	25LC010A	
	1.8V – 5.5V	2.5V – 5.5V	

Actual Package Sizes!

				
8-SOIC (SN) 5 x 6 mm	8-TSSOP (ST) 3 x 6.5 mm	8-MSOP (MS) 3 x 5 mm	6-SOT (OT) 3 x 3 mm	8-DFN (MC) 2 x 3 mm

microchip
DIRECT
www.microchipdirect.com

Get started today with the
SEEVAL® 32 Serial EEPROM
Designer's Kit (Part Number
DV243002) for only \$99.99!



MICROCHIP

www.microchip.com/SPI

Microcontrollers • Digital Signal Controllers • Analog • Serial EEPROMs



BY HOWARD JOHNSON, PhD

Designing a split termination

My last two articles dealt with the design of the end-terminating structure in **Figure 1a** (references 1 and 2). That structure terminates a transmission line with a single resistor value, R_T (termination resistance), leading to a fixed V_T (terminating voltage). In most cases, the termination resistance equals the characteristic impedance of the transmission line or can be a little higher than that impedance if the driver is weak. The ideal terminating voltage centers

the digital waveform, producing equal voltage margins above and below the required switching levels, V_{OH} (high output voltage) and V_{OL} (low output voltage). That ideal voltage equals the average of the required high- and low-output levels minus a correction term that accounts for asymmetry in the drive capability of the source:

$$V_T = \frac{V_{OH} + V_{OL}}{2} - R_T \frac{I_{OH} + I_{OL}}{2}.$$

This equation assumes that the I_{OH} (high-side source current) is positive and the I_{OL} (sinking current) is neg-

ative. If those two values have equal magnitudes, they sum to zero.

If you have a suitable source of terminating voltage, the structure in **Figure 1a** is easy to understand and uses fewer components than the one in **Figure 1b**. On the other hand, if no suitable voltage source exists, then you have no choice: You must synthesize the Thevenin equivalent from **Figure 1b**.

Given any combination of termination resistance, termination voltage, and V_{CC} (power-supply voltage) with voltage greater than the termination voltage, the following circuit values make the circuit in **Figure 1b** perform, from the transmission line's perspective, just as well as the one in **Figure 1a**.

$$R_2 = R_T \frac{V_{CC}}{V_{CC} - V_T}; \quad R_1 = R_T \frac{V_{CC}}{V_T}.$$

If you carefully follow the equations, you are now almost finished with your design. Next, you will discover that, no matter what values you have just computed, those exact values are never available in your component catalog. The values in the catalog are quantized to the nearest standard value, according to the tolerance

specification for each component.

If you want your circuit to perform over a range of resistor values and over a range of possible values for the power-supply voltage, check the worst-case constraints in **Figure 1**. If resistor R_1 meets these conditions, then the circuit in **Figure 1b** will work under all conditions just as well as the one in **Figure 1a**. Make sure that the minimum and maximum values take into account temperature and aging. Some fiddling with the values will be necessary; there is no straightforward design approach that always works.

If you have difficulty satisfying the constraints, try raising your target for the termination resistance and start again. Although it will not terminate the circuit as well, increasing the termination resistance opens more room for tolerance in the circuit. The tolerance requirements for R_1 and R_2 are somewhat interchangeable. A tighter tolerance for R_2 opens more room for R_1 and vice versa.

I cannot help you further with this aspect of the design. Component selection in analog circuits always involves some last-minute juggling to meet all the tolerance requirements. I can, however, point out that the circuit in **Figure 1a** helps you understand the need for two resistor values and how they work together to meet the impedance and current-drive constraints your driver imposes. **EDN**

REFERENCES

- 1 Johnson, Howard, PhD, "Yao! What a handshake!" *EDN*, Feb 7, 2008, pg 22, www.edn.com/article/CA6526821.
- 2 Johnson, Howard, PhD, " Z_{MIN} , a very special value," *EDN*, March 6, 2008, pg 24, www.edn.com/article/CA6535348.

Howard Johnson, PhD, of Signal Consulting, frequently conducts technical workshops for digital engineers at Oxford University and other sites worldwide. Visit his Web site at www.sigcon.com or e-mail him at howie03@sigcon.com.

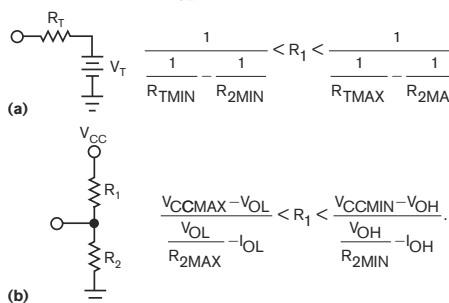


Figure 1 If R_1 meets both the termination-impedance constraints (a) and the drive-current constraints (b), then both termination circuits perform equally well.

Intersil Telecom/Datacom Products

High Performance Analog


intersil
HIGH PERFORMANCE ANALOG

Why Look Anywhere Else?

Intersil has your complete Telecom/Datacom solution, from DC/DC Bus Converters to Point-of-Load DC/DC (and everything in between).



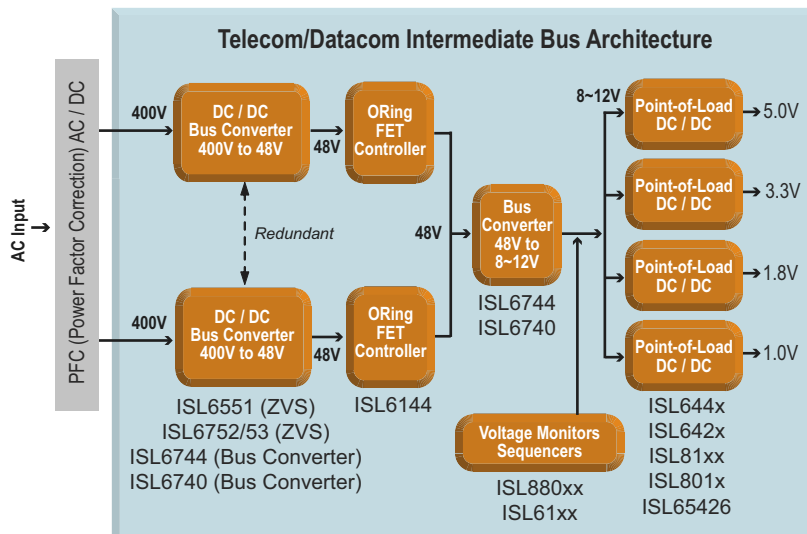Go to www.intersil.com for samples, datasheets and support



Intersil – Switching Regulators for precise power delivery.

©2007 Intersil Americas Inc. All rights reserved. The following are trademarks or services marks owned by Intersil Corporation or one of its subsidiaries, and may be registered in the USA and/or other countries: Intersil (and design) and i (and design).

intersil
HIGH PERFORMANCE ANALOG



BY JOSHUA ISRAELSOHN, CONTRIBUTING TECHNICAL EDITOR

Honest energy

I had the honor and great pleasure of serving as a panelist at an APEC (Applied Power Electronics Conference, www.apec-conf.org) rap session in February in Austin, TX. Although the session's central theme was the power sector's focus on efficiency, I was intrigued to note that all of the panelists agreed on an issue concerning energy use that lies outside a strict definition of efficiency: watts out divided by watts in.

As typical household products become more sophisticated, the power factor of the load they represent decays—a trend that is exacerbating a growing stress on our electric-power infrastructure. The problem with low power-factor loads is that they tie up grid capacity in excess of the energy they use.

An analysis of a load that draws nonsinusoidal current represents the current waveform as a harmonic series with components that are either in phase or in quadrature with the voltage waveform. Because the power grid

must supply all of the current—the in-phase component, which the utility meter measures, and the out-of-phase or reactive component, which the utility meter does not measure—the grid load exceeds the metered load.

The so-called P_A (apparent power) is the product of the rms voltage and rms current—measures that ignore relative phase (Figure 1). P_{REAL} (real power) is the integral of the in-phase voltage-current product over each line cycle. P_{REAC} (reactive power) accounts for the quadrature-current component. The PF (power fac-

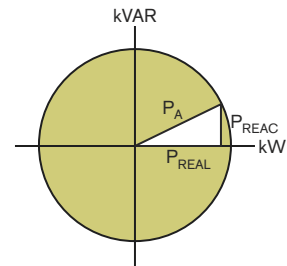


Figure 1 Power factor is the ratio of real-to-apparent power and is a measure of grid-use efficiency.

tor) is a measure of grid-use efficiency, which you can calculate as the ratio of P_{REAL} to P_A , or

$$\frac{P_{\text{REAL}}}{\sqrt{P_{\text{REAL}}^2 + P_{\text{REAC}}^2}}.$$

Conversely, the excess grid capacity that a load uses is

$$\frac{P_A - P_{\text{REAL}}}{P_{\text{REAL}}} = \frac{1}{\text{PF}} - 1.$$

The figure shows a load with a PF of about 0.9, which corresponds to an excess grid use of about 12%. To put numbers to a few real objects, I measured some devices in my home (Table 1). Think of these numbers in the context of the electronic devices your company makes and consider the important role high power factors can play in electric-energy availability. **EDN**


Joshua Israelsohn is a co-founder of JAS Technical Media, where he manages the company's technical-communication consultancy practice. You can find his contact information at www.jas-technical-media.com/Contact.

TABLE 1 POWER FACTORS, EXCESS GRID USE

Device	Power factor	Excess grid use (%)
Home computer	0.65	54
Computer-CRT display	0.65	54
Laser printer	0.73	37
Compact fluorescent lamp	0.56	79
Tungsten-filament lamp	1	0
Refrigerator compressor	0.91	10

MORE AT EDN.COM

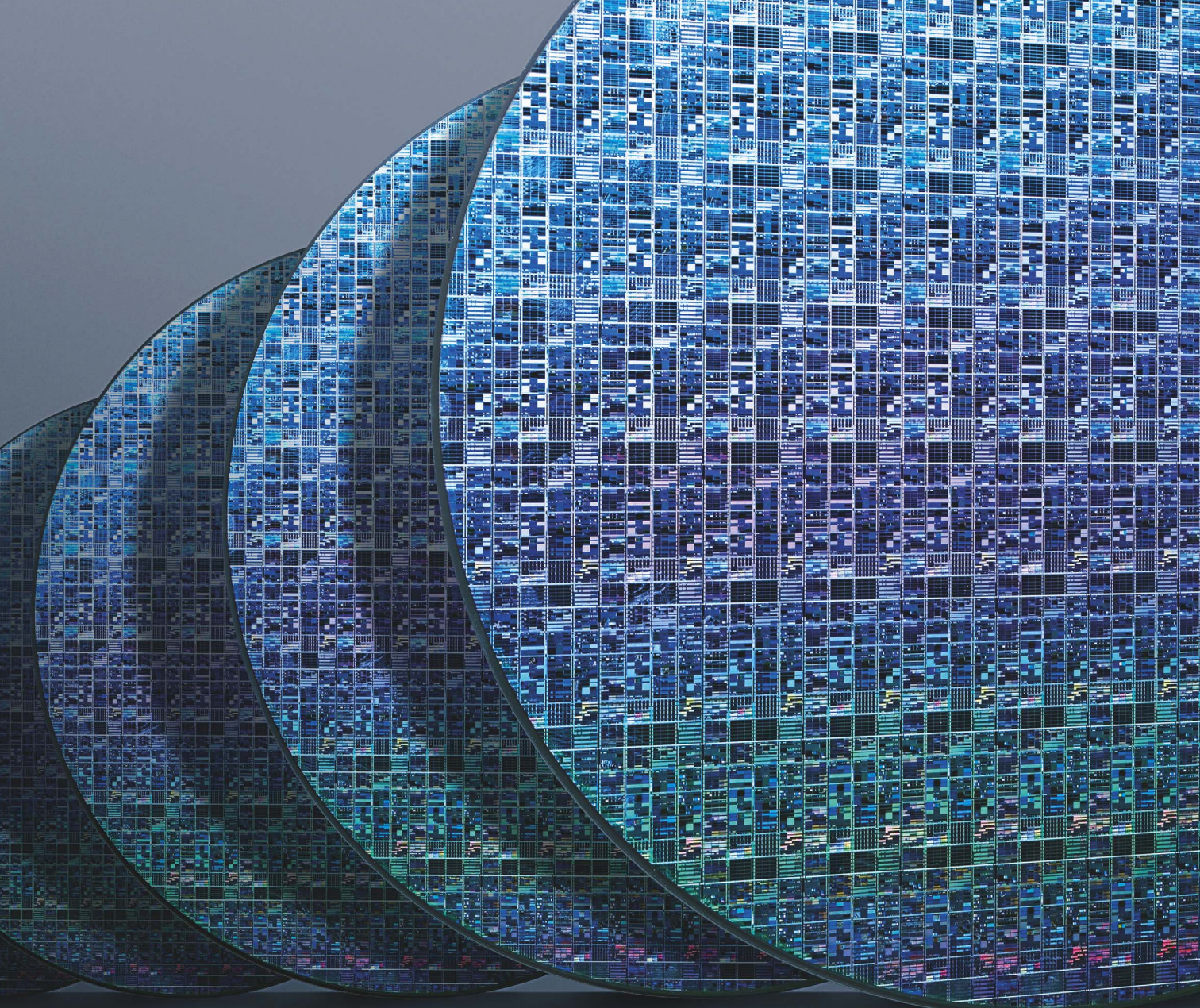Go to www.edn.com/080403ji and click on Feedback Loop to post a comment on this column.



*A CODEC CHIP THAT
ACHIEVED 50% COMPRESSION
IN DEVELOPMENT TIME.*

THAT'S MODEL-BASED DESIGN.

*To be first to market with a
next-generation mixed-signal
chip, the IC design team at
Realtek used system models to
continuously verify their design.
The result: 50% less time to
completion and a 50% market
share. To learn more and to
request the IBS study on Simulink
ROI in Electronic Design, visit
mathworks.com/mbd*

Small things make a big difference.

Melexis' Award-Winning Triaxis™ Hall-Effect ICs Simplify 360° Rotary Position and Joystick Applications

Small Things

At 4mm X 5mm, the MLX90316 and MLX90333 are Award-winning Hall-effect position sensor ICs which were designed specifically for 360 degree rotary position and contactless joystick applications. Both the MLX90316 and the MLX90333 belong to the Triaxis™ family of Hall-effect ICs, which employs patented IMC (Integrated Magnetic Concentrator) technology and standard Mixed Signal CMOS IC fabrication to achieve its outstanding performance.

Triaxis™

The Big Difference

Melexis' Triaxis™ technology senses the position of a common magnet within a 15mm proximity of the chip. This allows accurate and repeatable 3-Dimensional position sensing without the need for exotic magnetic circuits or constant mechanical and electronic calibration.

The MLX90316 and MLX90333 solve the sensing and signal problems so designers can concentrate on making the best rotary controls and joysticks.



Small things make a big difference.

For more information call us at
1 (603) 223 2362
or visit our website:
www.melexis.com



Wireless ICs

Bus ICs

Intelligent Drivers
And Actuators

Automotive ICs

Hall ICs

CMOS Imaging

Silicon MEMS

IR Temperature

Using a Buck Converter in an Inverting Buck-Boost Topology

By John Tucker
Applications Engineer

Introduction

To power some applications, generating a negative voltage from a positive input voltage source may be required. In such instances it is possible to configure the buck converter into an inverting buck-boost topology, where the output voltage is negative with respect to ground.

Basic Buck Topology

To understand the inverting buck-boost circuit operation, first consider the basic topology of the buck converter as shown in Figure 1. The components inside the box with a blue dotted outline are typically integrated into the converter's integrated circuit, while those outside are required external components.

When the FET switch is on, the voltage across the inductor is $V_{IN} - V_{OUT}$, and the current through the inductor increases at a rate of

$$\frac{di}{dt} = \frac{V_{IN} - V_{OUT}}{L}$$

When the switch is off, the inductor voltage reverses to keep the inductor current continuous. Assuming that the voltage drop across the diode is small, the inductor current ramps down at a rate of $di/dt = V_{OUT}/L$. The steady-state load current is always

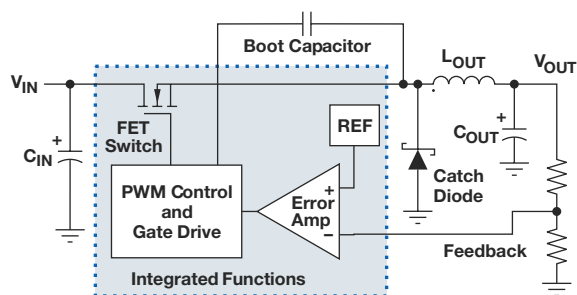


Figure 1. Buck topology

Featured in the latest online issue

- Using a touch-screen controller's auxiliary inputs
- Driving a WLED does not always require 4 V
- Host-side gas-gauge-system design considerations for single-cell handheld applications
- Using a buck converter in an inverting buck-boost topology
- Download your copy now at www.ti.com/aaj

carried by the inductor during both the on and off times of the FET switch. The average inductor current is equal to the load current, and the peak-to-peak inductor ripple current is

$$I_{L(PP)} = \frac{(V_{IN} - V_{OUT}) D}{f_{SW} L},$$

where V_{IN} is the input voltage, V_{OUT} is the output voltage, D is the duty cycle V_{OUT}/V_{IN} , f_{SW} is the switching frequency, and L is the output inductance.

Inverting Buck-Boost Topology

Compare the preceding operation to that of the inverting buck-boost topology shown in Figure 2. The inductor and catch diode have switched places relative to the buck converter of Figure 1; and the output capacitor is reversed in polarity, as the

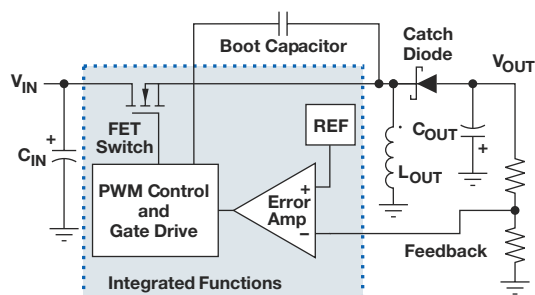


Figure 2. Inverting buck-boost topology

output voltage is negative. During operation, when the FET switch is on, the voltage across the inductor is V_{IN} and the current ramps up at a rate of $di/dt = V_{IN}/L$. While the FET switch is on, the entire load current is supplied by energy stored in the output capacitor. When the FET switch turns off, the inductor reverses polarity to keep the inductor current continuous. The voltage across the inductor is approximately V_{OUT} , and the inductor current decreases at a rate of $di/dt = -V_{OUT}/L$. During the off time, the inductor supplies current both to the load and to replenish the energy lost by the capacitor during the on time. So for the buck-boost circuit, the average inductor current is

$$I_L = \frac{I_{OUT}}{1-D},$$

and the peak-to-peak inductor current is

$$I_{L(PP)} = \frac{V_{IN}D}{f_{SW}L}.$$

The duty cycle, D , is approximately

$$D = \frac{V_{OUT}}{V_{IN} + V_{OUT}}.$$

These basic differences in circuit operation are important when the buck converter is used as a buck-boost converter.

Design Considerations

When a nonsynchronous buck converter is used in an inverting buck-boost configuration, certain considerations must be made. The design equations are presented in simplified form with the semiconductors idealized and other component losses neglected. To implement the buck-boost topology of Figure 2, the buck-converter ground pin is connected to V_{OUT} , and the positive lead of the output capacitor is connected to ground. The voltage across the device's V_{IN} pin to GND is then $V_{IN} - (-V_{OUT})$, rather than just V_{IN} as in the buck converter. This combined voltage must be less than the specified V_{IN} of the chosen device.

Since the average output current cannot exceed the device's rated output, the available load current is reduced by a factor of $1 - D$. So for this design, the maximum available DC load current is $I_{SW} \times (1 - D) = I_{Load}$, where I_{SW} is the average rated current of the high-side switch FET.

Typical Waveforms

To demonstrate some of the performance characteristics of an inverting buck-boost converter, a test circuit was constructed. The circuit used a 24-V input and had a -5-V output at 2 A. Output voltage ripple and switching-node waveforms are shown in Figure 3. Note that the switching-node voltage varies from V_{IN} to V_{OUT} for the inverting buck-boost converter instead of V_{IN} to ground for a buck converter. The

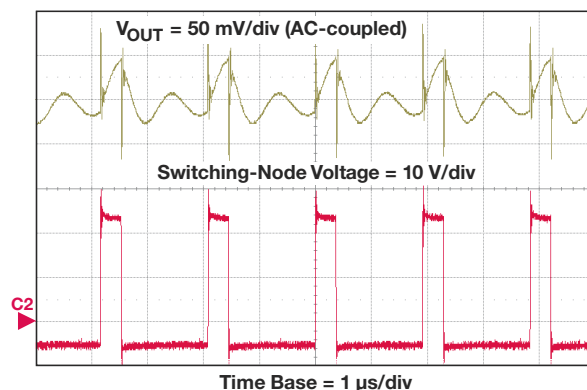


Figure 3. Inverting buck-boost output voltage ripple and switching-node voltage

ground reference line is indicated by the C2 marker at the left edge of the figure. Also observe that the output voltage ripple does not show the linear ramp characteristic typical of the buck converter. The output capacitor supplies the load current during the switch on time and is recharged during the switch off time. This charge-and-discharge cycle is superimposed with the AC ripple current to create a more complex ripple current as shown in the figure. Remember that the output voltage is negative, so the positive portions of the waveform represent the output becoming less negative, or the discharge portion of the cycle.

Conclusion

A buck converter can be used to generate a negative output voltage from a positive input voltage if the circuit is configured as an inverting buck-boost converter. The circuit design is straightforward, but these important points should be remembered. The output current is less than the average inductor current by a factor of $1 - D$, so the available output current will be less than the device rating. The output voltage is negative and is available at the device ground pin, so the effective voltage across the input of the device is $V_{IN} - V_{OUT}$. This difference must not exceed the input-voltage rating of the device. Finally, the ground of the device should not be tied to the system ground.

Please see Reference 1 for the complete version of this article, which provides additional design details and shows waveform comparisons between test circuits for a buck converter and the inverting buck-boost converter.

Reference

1. View the complete article at <http://www-s.ti.com/sc/techlit/slyt286>



BASE STATIONS AND HANDSETS NEED RF AMPLIFIERS WITH HIGH LINEARITY AND EFFICIENCY. WITH SOME CLEVER TECHNIQUES, DESIGNERS CAN ALIGN THESE MUTUALLY EXCLUSIVE GOALS.

Heads ~~and~~ or tails

BY PAUL RAKO • TECHNICAL EDITOR

DESIGN RF AMPLIFIERS FOR LINEARITY AND EFFICIENCY

Cell phones use modern modulation schemes that require linear amplification of the RF signal. A typical way to achieve this linearity is to burn more power in the output stage. This approach reduces efficiency, even though efficiency is one of the most important operating parameters in a phone, a base station, or any other electronic system.

Important efficiency requirements exist on both the handset and the base-station sides of the telecom world. In handsets, efficiency directly translates into battery life. By increasing cell-phone efficiency, you can also increase talk time—a fundamental figure of merit for a handset. On the base-station side,

efficiency results in lower electric bills and, just as important, less heat. Reducing heat and power consumption creates a cascading set of results that provide lower initial costs, lower operation costs, and lower total cost of ownership.

In older cell-phone-modulation designs, the linearity of the output stage was unimportant because the demodulation did not depend on linearity. CW (continuous-wave), FM (frequency-modulation), and GMSK (gaussian minimum-shift keying) for GSM (global-system-for-mobile) communication technologies have a constant envelope and require no linear amplification. To work properly, new modulation schemes, such as EDGE (enhanced data for GSM evolution), require linear amplifiers. You can achieve this linearity by underdriving the RF amplifier and leaving head room between the output signal and the power-supply voltage. The problem with this approach is that it directly decreases the amplifier's efficiency.

Efficiency in single-transistor output stages improves as the output swing approaches the power-supply rails. To improve efficiency, select power-supply voltages and load impedances so that the output stage swings close to the rails.

This approach dissipates less average power in the output transistors because the output transistor always has less voltage across it as the output signal nears the power rail.

Unfortunately, driving the output signal closer to the supply rail also reduces the amplifier's linearity. This reduction occurs just as frequently at RF frequencies as it does at audio frequencies. Any amplifier whose circuit design causes it to swing to values near the power-supply rails has less linearity. The ultimate expression of linearity problems in an amplifier is amplifier clipping, and the power-supply voltage is insufficient to allow the signal excursion to properly represent the amplified input signal (Figure 1).

THE NEED FOR LINEARITY

It may not be immediately apparent, but linearity is not a primary concern in designing many RF systems. The fact that designers use Class C amplifiers should suggest that a perfect representation of the input sine wave might not be critical to the communications

requirements of some types of signals. Imagine the RF signal from an FM-radio station. In FM transmissions, the zero crossings of the waveform contain all the information in the signal. Even if the peaks of the waveform become distorted, the fidelity of the demodulated signal do not. Overdriven FM-radio signals create frequency harmonics of the carrier frequency, and those harmonics may be objectionable from an interference standpoint, but a receiver tuned to an overdriven-FM-radio signal still operates successfully (**Figure 2**).

Over the past decade, the acquisition costs and revenue demands of cell-phone-radio bands have encouraged the

AT A GLANCE

- ▣ New cell-phone standards require linear RF amplifiers.
- ▣ Improving linearity often hinders efficiency.
- ▣ Digital predistortion is one method of achieving linearity and efficiency.
- ▣ The Doherty amplifier implements a hardware method for improving efficiency.
- ▣ Modeling and simulating nonlinear systems are challenges.

design of advanced modulation schemes that allow for more information in a nar-

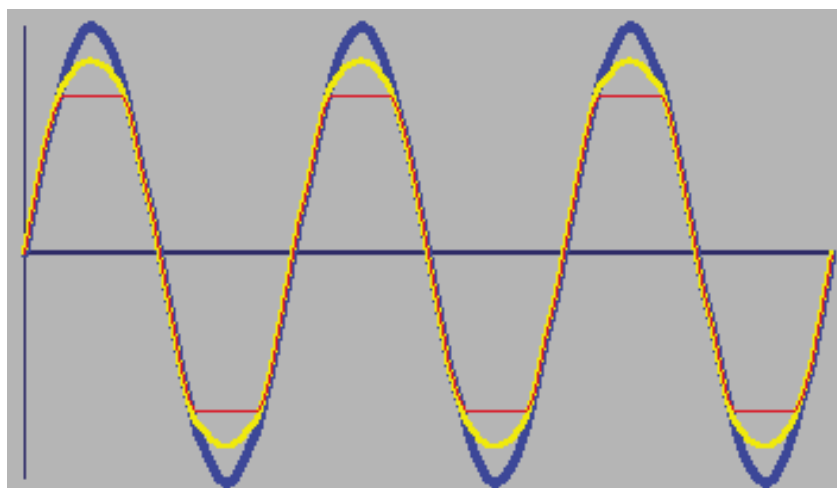


Figure 1 Clipping distortion is apparent when comparing the blue input with the yellow, moderately clipped output waveform or the red, heavily clipped output waveform. Symmetrical clipping such as this one appears as odd harmonics in the frequency domain. Amplifier nonlinearity creates intermodulation distortion that is harmonically unrelated to the two input tones.

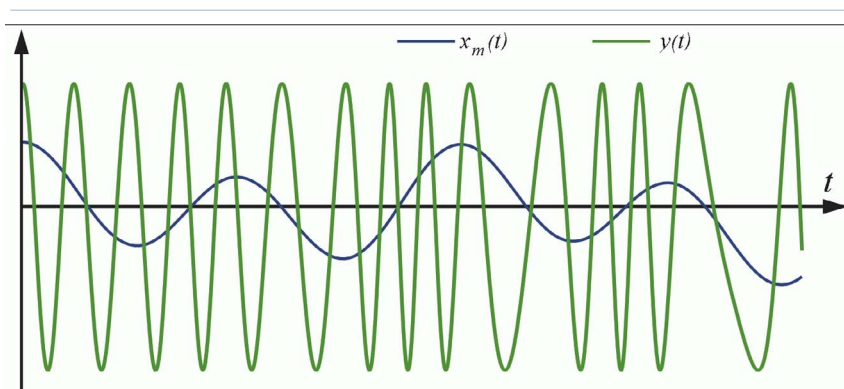


Figure 2 The frequency-modulated signal, $y(t)$, is immune to amplifier nonlinearity. The zero crossings, rather than the amplitude, contain the information, so amplitude distortion in the amplifier causes no problems.

rower frequency band. A figure of merit for these schemes is bandwidth efficiency, which you express in megabits per megahertz or bits per second per hertz. Modern and proposed cell-phone standards, such as EDGE, contain information in far more than the zero crossings of the signal. The new cell-phone-modulation schemes, such as QAM (quadrature-amplitude modulation), carry information in both the phase and the amplitude of the envelope signal on the RF-carrier frequency. Examine the classic 64-QAM (64-state-QAM)-vector constellation (**Figure 3**). The phase and amplitude of the signal use a series of symbol vectors to create the envelope of the RF signal. Because there are 64 vectors, the information that any vector carries can represent 6 bits of digital information, providing the bandwidth efficiency of 64-QAM schemes, which approach 6 Mbps/MHz.

Poor linearity causes problems in such an advanced modulation scheme. Because the demodulator needs an accurate depiction of both the amplitude and the phase of the signal, the instantaneous accuracy of the signal is important, unlike with FM transmissions, in which only the zero crossings matter. If the operating signals drive the RF-power amplifier close to the output rail, the transistor approaches saturation, compounding its inherent logarithmic nonlinearity. Thus, the symbol vector that the amplifier encodes loses the correct amplitude and phase. When the nonlinearity is severe enough, the symbols overlap and lose the information.

A demodulation scheme might account for the inherent nonlinearity of a transistor, but the biasing of that transistor establishes at which point on the logarithmic-transfer function the transistor operates. Thus, coming up with such a demodulation scheme would be difficult. Further, the saturation of the transistor as it approaches the power rails would be difficult to factor into to any demodulation scheme because each RF source has a somewhat arbitrary power-supply voltage. The only approach to correcting poor symbol accuracy is improving the accuracy of the RF-power amplifier.


Class A output stages have inherent nonlinearity due to the transistor's curve, making the positive and the negative excursions of the output sig-

Power That Gives You Best Of Both Technology Worlds

Switcher Efficiency Combined With LDO Noise And Transient Performance




MIC38300
Actual Size 4mm x 6mm

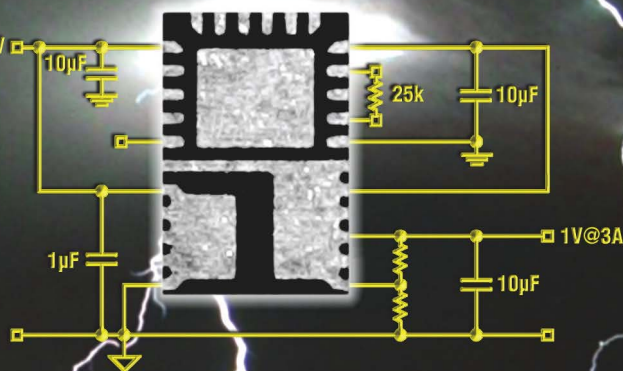

No Power Expertise Required

ASICs/FPGA Requirement

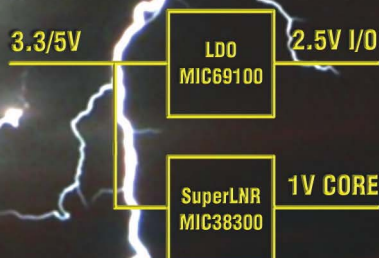

The MIC38300 is a 3A step down converter and the first device in a new generation of SuperLNR™ products providing the benefits of LDOs with respect to ease of use, fast transient performance, high PSRR and low noise while offering the efficiency of a switching regulator.

As output voltages move lower, the output noise and transient response of a switching regulator become an increasing challenge for designers. By combining a switcher whose output is slaved to the input of a high performance LDO, high efficiency is achieved with a clean low-noise output.

For more information, contact your local Micrel sales representative or visit us at: www.micrel.com/ad/mic38300.

Literature: 1 (408) 435-2452 Information: 1 (408) 944-0800

The Good Stuff:

- ◆ 2.2A Continuous operating current
- ◆ Input voltage range: 3.0V to 5.5V
- ◆ Adjustable output voltage down to 1.0V
- ◆ Output noise less than 5mV
- ◆ Ultra fast transient performance
- ◆ Unique Switcher plus LDO architecture
- ◆ Fully integrated MOSFET switches
- ◆ Micro-power shutdown
- ◆ Easy upgrade from LDO as power dissipation becomes an issue
- ◆ Thermal shutdown and current limit protection
- ◆ 4mm x 6mm x 0.9mm MLF® package

MICREL
Innovation Through Technology™
www.micrel.com

nal asymmetrical. At lower frequencies, feedback overcomes this nonlinearity. Transistor amplifiers soon evolved into operational amplifiers that have forward gain that can exceed 120 dB, enabling designers to improve linearity by using a large amount of negative feedback. This feedback combines with Class A-B output stages to produce linearity such as that of the National Semiconductor LME49710, which specifies a linearity of 0.00003%. Note, however, that this linearity spec is for operation at relatively low frequencies. All amplifiers exhibit a roll-off of gain with frequency. Current-feedback-amplifier architectures have less gain loss at high frequencies, but they still roll off at high frequencies.

Remember that the linearity improvement you achieve with large feedback involves also having a large forward gain. Because amplifiers have less forward gain at higher frequencies, they also have less feedback at high frequencies. As a result, RF amplifiers, especially RF power amplifiers, cannot use conventional feedback at the 1-GHz and higher frequencies at which they operate.

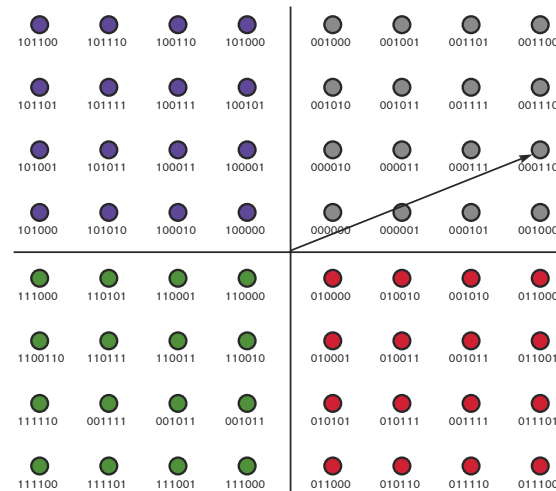


Figure 3 A 64-QAM constellation can encode 6 bits per symbol vector. Some vectors are subject to phase errors, and some vectors are sensitive to amplitude errors. In either case, the accuracy of the waveform envelope is critical, which makes amplifier linearity so important.

Just as daunting, the open-loop nature of most RF amplifiers means that they are subject to power-supply-rejection and output-saturation problems. Because RF amps operate near the frequency limits of the transistors themselves, you cannot practically make them into high-gain operational amplifiers. In this

regard, RF-amplifier design still incurs all the difficulties that designers of tube equipment faced decades ago.

In addition to the linearity problems facing all amplifier designers, other linearity impediments make RF amplifiers even more challenging. For example, the electrical and thermal operation of the amplifier can cause memory effects that in turn introduce time- or data-dependent nonlinearity. Electrical-memory effects are analogous to the memory effects that you can observe in old tube-guitar amplifiers. These amps had cheap power-supply systems—often, open-loop linear supplies comprising a capacitor hanging across a tube-rectified line voltage. A loud power chord would heavily drive the output stage

and pull down the power-supply voltage as the capacitor drained. The line voltage restores the capacitor after the heavy load, but it takes 10s of milliseconds to do so. The sag in the power-supply voltage changes the biasing of the output transistors in the guitar amplifier, creating distinct “data-dependent” nonlinearity. The degree of nonlinearity depends on the previous signal. RF-power amplifiers are subject to the same phenomenon. The sequence of data may require symbols that cause the heavy driving of the amplifier. This situation affects the power supply and biasing of the amplifier and creates time-dependent nonlinearity that changes with the modulation of the RF carrier.

Besides these electrical-memory effects, amplifier designers must also handle thermal-memory effects. Hot and cold transistors have different transfer functions, introducing a time-dependent nonlinearity into the system. If the environment is hot or the data stream heats up the output stage, then the transistor exhibits different nonlinearity from what it would exhibit at a cool temperature. As more CMOS chips are integrating RF-power amplifiers, even more thermal problems emerge.

Figure 4 shows the nonlinearity of RF-power stages. At the core of transistor nonlinearity is the fact that the current-to-voltage transfer function of a

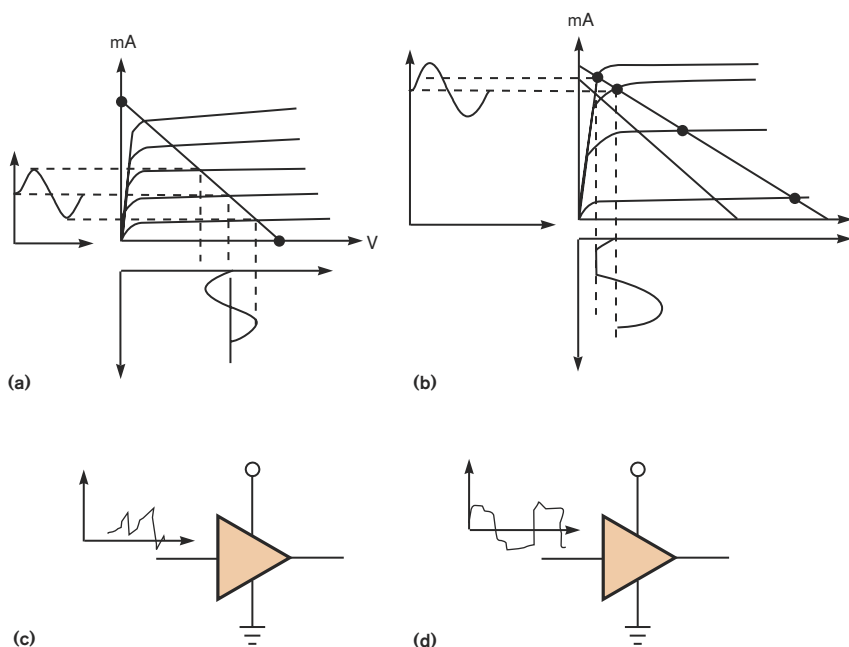


Figure 4 RF-power-amplifier nonlinearity occurs because of the inherent nonlinearity of a transistor amplifier (a), clipping distortion (b), and both electrical-memory (c) and thermal-memory (d) effects.



Looking for a basket full of functionality?

Only Keithley offers a power supply, current source, DMM, ARB waveform and V or I pulse generator, and trigger controller all rolled into one.



Series 2600 SourceMeter® Instruments

- **Boost your test throughput by 2–4×** with our embedded Test Script Processor (TSP™) that blows away GPIB bottlenecks.
- **Integrate and control multiple instruments easily**, economically, and without a chassis with TSP-Link™ high speed trigger and communication bus.
- **Control your cost of ownership** by scaling your channel count precisely for your application.
- **Perform DC and pulse testing from femtoamps and microvolts** with our low current test solutions for semiconductor components.

Go to www.keithley.com/rolled and try a demo.

PICO

**Surface Mount
(Thru-Hole Available)
Transformers and
Inductors**

See Pico's full Catalog immediately
www.picoelectronics.com

Low Profile from
.19" ht.



Audio Transformers

Impedance Levels 10 ohms to 250k ohms.
Power Levels to 3 Watts, Frequency Response
 $\pm 3\text{db}$ 20Hz to 250Hz. All units manufactured
and tested to MIL-PRF-27. QPL Units available.

Power & EMI Inductors

Ideal for noise, spike and Power Filtering
Applications in Power Supplies, DC-DC
Converters and Switching Regulators

Pulse Transformers

10 Nanoseconds to 100 Microseconds. ET
Rating to 150 Volt Microsecond, Manufactured
and tested to MIL-PRF-21038.

Multiplex Data Bus Pulse Transformers

Plug-In units meet the requirements
of QPL-MIL-PRF 21038/27.
Surface units are electrical equivalents
of QPL-MIL-PRF 21038/27.

DC-DC Converter Transformers

Input voltages of 5V, 12V, 24V And 48V.
Standard Output Voltages to 300V (Special
voltages can be supplied). Can be used as self
saturating or linear switching applications. All
units manufactured and tested to MIL-PRF-27.

400Hz/800Hz Power Transformers

0.4 Watts to 150 Watts. Secondary Voltages 5V
to 300V. Units manufactured to MIL-PRF-27
Grade 5, Class S (Class V, 155°C available).

**Delivery—stock to one week
for sample quantities**

See EEM
or send direct
for **FREE** PICO Catalog
Call toll free 800-431-1064
in NY call **914-738-1400**
Fax **914-738-8225**

PICO Electronics, Inc.

143 Sparks Ave, Pelham, N.Y. 10803

E Mail: info@picoelectronics.com
www.picoelectronics.com

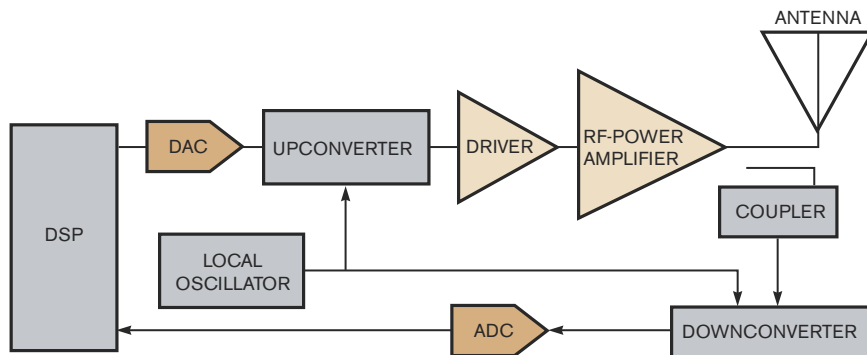


Figure 5 A cell-phone base station uses digital predistortion depending on the components the base station uses. Cartesian feedback also allows dynamic algorithms that can help compensate for memory effects and other nonlinearity.

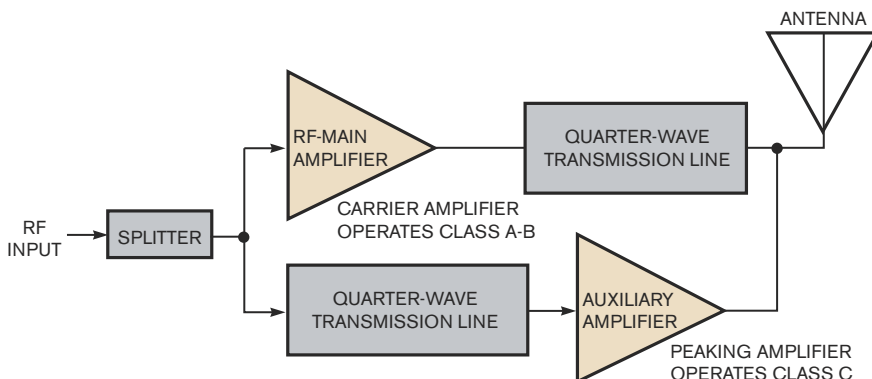


Figure 6 The Doherty RF amplifier achieves better efficiency by using an auxiliary amplifier to vary the load impedance on the primary amplifier. This approach allows the primary amplifier to continue to swing a large signal, dissipating less power in the amplifier. If the auxiliary amp lowers the load impedance on the primary amplifier, the primary amplifier delivers more power.

transistor is a logarithmic curve, not a straight line. The next issue is the saturation of the transistor as it approaches the power-supply rail.

APPROACHES TO LINEARITY

RF designers cannot just swing the output of the amplifier across a smaller range and suffer with the efficiency hit. They can use feedback, feedforward, or predistortion approaches to preserve efficiency for battery life and power savings. The feedback approach suits designs requiring high linearity, narrow bandwidth, and medium efficiency. The feedforward technique also works for designs requiring high linearity but with wide bandwidth and a low-efficiency requirement. Predistortion allows for medium linearity and bandwidth but yields high efficiency. Because RF-power amplifiers operate at such high frequencies, the use of conventional feedback tech-

niques is impractical. In this context, the term “feedback” often refers to Cartesian feedback, in which circuitry converts the RF output back down to baseband, deriving the I (in-phase) and Q (quadrature) signals and feeding those signals back to the input stages. This system can achieve high linearity but only if you don’t overdrive the output stage. The efficiency is lower than you might think. Because feedback amplifiers are subject to oscillation, you cannot use this technique on wideband amplifiers.

To get both acceptable linearity and high bandwidth, RF designers have resorted to predistortion techniques: The I and the Q signals that perform the modulation can compensate for the deterministic nonlinearity of a system. Because a digital system can also use complex algorithms to predict the thermal- and electrical-memory effects, these setups also preserve linearity in the face of

these problems. Note that the inherent linearity of the components in the RF-signal path is still relevant. There is a limit to the corrections that you can apply in the digital domain. The closer the signal path is to ideal, the easier job a digital-system designer will have providing an accurate predistorted signal.

Designers are always cognizant of the inherent linearity of system components, according to James Wong, high-frequency-product-marketing manager at Linear Technology. "An active upconverter with built-in amplification, noise, linearity, and superior isolation results in a superior dynamic range ... compared with a passive upconverter followed by an amplifier," he says. "This [approach] greatly reduces the challenge [for] digital designers ... providing predistortion to the signals." He points out that modern base stations also use Cartesian feedback. Circuitry downconverts and extracts the I and Q components of the output and then feeds them back to the DSP core. This approach allows the system to use sophisticated algorithms that use real-time Cartesian feedback as well as predistortion based on the components the signal chain uses (Figure 5).

Hardware designers need not resort to using digital predistortion to improve linearity, however. Hardware can also improve linearity and efficiency; the better the inherent linearity, the less digital systems must correct. Designers may want to consider the use of a Doherty amplifier, which William H Doherty of Bell Laboratories invented in 1936 (Figure 6 and Reference 1). This amplifier has two RF paths. The RF does not just shuttle between a low-power stage and a high-power stage. The output-voltage swing in an RF amplifier should be close to the power-supply-rail voltage. The Doherty amplifier uses the second amplifier to change the apparent output impedance on the main amplifier. An amplifier feeding a transmission line faces an infinite output impedance if the second amplifier produces an identical signal on the other end of the line (Figure 7). Because both ends of the transmission line are equipotential, no current flows, and the line delivers no power. If you don't drive the secondary amplifier at all, then the output impedance that the first amplifier "sees" is the characteristic impedance of the transmission line. By exten-

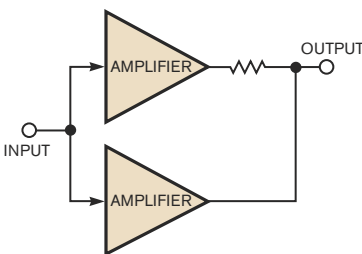


Figure 7 In this circuit, the same signal passes to both sides of a resistor, and the upper amplifier sees an infinite load. The amplifiers drive both sides of the resistor at the same amplitude, so neither amplifier sources any current or delivers power to the resistor. If the signal to each amplifier is 180° out of phase, the load that each amplifier perceives would be twice the resistor value. A Doherty amplifier uses this principle to vary output power and maintain efficiency.


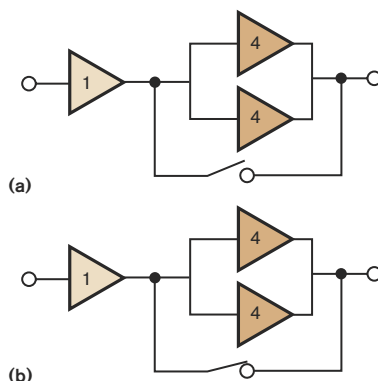


Figure 8 The low cost of handsets encourages the use of straightforward methods to improve efficiency. Avago makes amplifier modules that switch between high-power mode with output power greater than 16 dBm (a) and low-power mode with output power less than 16 dBm (b). The improvement in efficiency can add an hour of talk time.

sion of this principle, if you drive the secondary amplifier 180° out of phase from the first, then you are differentially driving the right side of the transmission line, and the apparent output impedance that the first amplifier sees is half the characteristic line impedance, increasing the delivered power. The main amplifier always swings near the output rails. If the design requires low-power transmission, the secondary amplifier increases the ap-

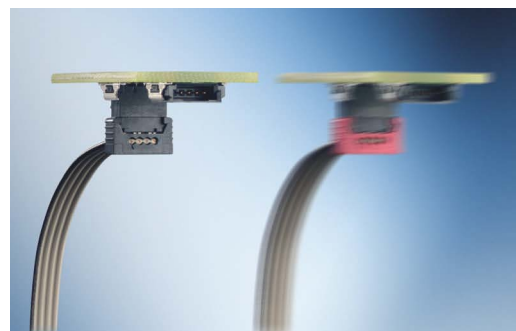

Good, good, good, good Vibrations: ERNI MiniBridge™

Only 10 x 10 x 3 mm in size, but up to 4 amperes of load capacity

The new ERNI MiniBridge 4-pin cable connector – a high performance all-rounder for sensor and actuator systems, data and power transmission in automobiles, machines, computers, consumer electronics, household appliances and medical devices. The MiniBridge is available as a black connector and – for difficult application conditions involving shocks and vibrations – a red connector with locking latch.



In a 1.27 mm grid with all SMC qualities yet smaller and in versions with:

2, 3, 4, 6 or 8 pins, board-to-cable, straight or angled male multipoint connector, cable outlet in 90° or 180°. The MiniBridge can be assembled with existing manufacturing devices. It is also costefficient, yet offers additional extras such as easy mounting of cables, single strand connection and partial loading. The exact technical data and drawings can be downloaded from our website. Exploit our know-how in connector and assembly technology – from design all the way down to the smallest component. Call ERNI for samples, today.

USA: 1-800-296-3764
Europe: +49 7166 500
Asia: +65 6 555 5885
www.erni.com/minibrIDGE



Any Sensor. Any Project. NI Data Loggers



NI C Series Data-Logging Family

- PC-connected or stand-alone deployment
- Expandable I/O from four to 250+ channels
- Rugged devices with long-lasting durability
- Multiple mounting and sensor connectivity options

>> See NI data loggers
in action at
ni.com/dataloggers

800 327 9894



©2007 National Instruments Corporation. All rights reserved. National Instruments, NI, and ni.com are trademarks of National Instruments. Other product and company names listed are trademarks or trade names of their respective companies. 2007-3229-301-101

parent output impedance that the main amplifier sees, and, for a given voltage swing near the rail, the amplifier delivers less current and, hence, less power.

The sophistication of the Doherty amplifier makes it a good fit for use in the base-station side of the cell-phone world. On the handset side, space and cost constraints are far more severe. In this case, you can use RF switches to switch gain blocks as necessary, providing substantial power savings. For example, Avago's CoolPAM (power-amplifier-module) RF devices provide cell-phone designers a way to maintain efficiency over wide output-power levels (**Figure 8**). You can use this straightforward technique instead of feeding the output stage with a dc/dc converter. Using the converters allows the RF-output stage to always operate near saturation and, hence, improve efficiency. However, dc/dc converters consume more space and have efficiency limitations of their own. Using the CoolPAM technology, Avago claims, can increase talk time to more than an hour, a compelling opportunity for cell-phone designers.

THE TROUBLE WITH MODELING

The quest for linearity with efficiency in RF-power amplifiers also affects the EDA tools for developing RF systems. Because these RF systems are inherently nonlinear, they share all the mathematical problems of other nonlinear systems. Using Spice and other circuit-simulation techniques may not apply and may be time-consuming because RF designs often require steady-state operation, a condition that may take billions of signal excursions to achieve. RF designers have typically resorted to black-box-modeling techniques, such as the use of S (scattering) parameters, to design systems. S parameters do not account for nonlinearity and do not model the bias points of the amplifier, however. To solve this problem, Agilent, which popularized S-parameter design, recently introduced X parameters, or polyharmonic-distortion modeling (**Reference 2**). These parameters combine the response of a linear system with the response due to the nonlinear factors. Agilent has provided several papers detailing this technique, and the inclusion of X-parameter simulation in Agilent's RF-design tools and the development of Agilent's test equip-

MORE AT EDN.COM

Go to www.edn.com/080403df
and click on Feedback Loop to post
a comment on this article.

ment that can characterize X parameters are sure to follow.

The design of RF-power amplifiers is becoming increasingly difficult due to the design requirements for new cell-phone-modulation schemes. The RF domain has long been the realm of intuitive design and experienced engineers. The demands on linearity and efficiency in these new designs only further accentuate the need for expertise when creating designs that work properly. The design effort is also spreading across disciplines. RF-, analog-, and digital-system designers all contribute to the performance of the signal chain. With experienced designers now getting access to sophisticated tools and instruments from EDA and test-equipment manufacturers, you can all look forward to even more amazing performance gains, all at significantly lower costs. **EDN**

REFERENCES

- 1 Vani Viswanathan, "Efficiency Enhancement of Base Station Power Amplifiers Using Doherty Technique," Virginia Polytechnic Institute and State University http://scholar.lib.vt.edu/theses/available/etd-05062004-152027/unrestricted/Viswanathan_Thesis.pdf.
- 2 Verspecht, Jan, and David E Root, "Polyharmonic Distortion Modeling," *IEEE Microwave Magazine*, Volume 7, Issue 3, June 2006, pg 44, www.janverspecht.com/pdf/phd_ieemicrowavemagazine.pdf.

FOR MORE INFORMATION

Agilent
www.agilent.com
Avago Technologies
www.avagotech.com

Linear Technology
www.linear.com
National Semiconductor
www.national.com

You can reach
Technical Editor
Paul Rako at
1-408-745-1994
and paul.rako@reedbusiness.com.







Spend up to 19% less



And our 34401A is now even better looking

Agilent's 34401A DMM, the long-held industry standard, now sports a new look along with a 9% price cut. And the high performance 34410A is 19% less than it was before. Take advantage of these new prices today; go to www.agilent.com/find/dmmcompare

Specification

				
	34405A	34401A	34410A	34411A
Resolution	5½ digits	6½ digits	6½ digits dual display	6½ digits dual display
Basic DC Accuracy	250 ppm	35 ppm	30 ppm	30 ppm
Max Readings/s (continuous to PC)	19	1,000	10,000	50,000
Connectivity	USB	GPIB RS-232	GPIB, USB, LAN LXI Class C	GPIB, USB, LAN LXI Class C
Price	\$745*	\$1,172* \$1,070*	\$1,595* \$1,295*	\$1,995*

© Agilent Technologies, Inc. 2008
* Prices in USD and subject to change



Agilent Technologies

Agilent Authorized Distributors



RS ELECTRONICS

888-852-7234

Allied Electronics

800-433-5700

Hensley Technologies

877-595-7447

Instrument Engineers

800-444-6106



BY RICK NELSON, EDITOR-IN-CHIEF • RON WILSON, EXECUTIVE EDITOR

CHIP SETS ARE EMERGING THAT ADD WIMAX CAPABILITY TO MOBILE PC AND CELL-PHONE APPLICATIONS, WHILE LAB AND PRODUCTION-TEST EQUIPMENT EVOLVES TO KEEP PACE.



LAYING SEAMLESS

WIMAX FABRIC

WiMax (worldwide interoperability for microwave access) stands poised to extend coverage in PC networking and mobile-phone communications as semiconductor makers roll out WiMax chip sets and as test-equipment vendors offer the lab instrumentation and production ATE (automatic-test-equipment) systems necessary to test the chip sets and the products they populate. WiMax shows promise as a technology for PC networking as well as a potential cellular technology (see **sidebar** “WiMax markets and opportunities”). Paul Argent of Aeroflex expects WiMax to initially bring broadband-wireless access to laptops despite suggestions from WiMax Forum members that WiMax is a technology for multiple applications, including cellular telephony. Over the next two years, Argent says, WiMax will primarily provide high-speed data access to PCs in coffee shops as well as in moving vehicles.

Jennifer Stark, Agilent’s WiMax business-team leader, cautions that you should not consider WiMax as a replacement for other broadband-wireless-access technologies. She segments wireless technologies by range—with personal-area networks, such as UWB (ultrawideband) and Bluetooth, operating at 10m or less; WLANs (wireless local-area networks) operating at 100m or less;

and WiMax operating at three to 10 miles or more. As for WiMax’s competing with WLANs, she expects them rather to complement each other, with appliances making the most effective connection based on conditions of the moment. For instance, WiMax will be the choice if you’re on a train going 50 mph, she says; if you later find yourself in a stationary situation, WLAN might be the best choice.

WIMAX-CHIP TEST

To test WiMax chips in production volumes, ATE makers are adapting their RF-capable systems to handle WiMax-test requirements, and makers of bench- and rack-mount test equipment are tailoring their instrumentation to handle a potential onslaught of components, modules, and WiMax-compatible appliances. These vendors are also addressing the test needs of service providers that will install and maintain the WiMax infrastructure. Adam Smith, a business-development engineer at Verigy, says that WiMax test represents an evolutionary step from WLAN test, with WiMax imposing stricter requirements as designers try to cram ever more features into a tighter space. “From a test-equipment point of view,” he says, “your equipment needs to have very good noise performance; it needs to be very sensitive.” Agilent’s Stark adds that WiMax’s underlying OFDM (orthogonal-frequency-division-



multiplexing) scheme results in high peak-to-average power levels, putting a premium on highly accurate power-amplifier measurements.

Testing of WiMax silicon presents an instructive bundle of issues to chip designers and test engineers. On one hand, if WiMax is to reach wide acceptance, test costs—including the cost of silicon overhead to support testing—must be as small as possible. Ultimately, says Smith, someone will want to fit WiMax capability within a \$99 mobile device. On the other hand, a number of factors militate against a fast, comprehensive test procedure. The WiMax standard is still not mature. Adjustments are by now small, but they still happen. More important, the standards reach only far enough to attempt to ensure interoperability at the system level. They make no demands on the implementation approach or on the signals passing between functional blocks in the implementation. Even more troubling, you may find that you don't have access to signals between functional blocks. Ken Harvey, senior product technologist at Teradyne, points out that, as WiMax chips become increasingly integrated, you'll find you might not have direct access to I (in-phase) and Q (quadrature) signals. "You'll go straight from RF to bits," he says.

Lacking standards against which to test the signal between the RF mixer and the ADC, and—potentially—access to that signal, you'll have to rely on

AT A GLANCE

WLANs (wireless local-area networks) and WiMax (worldwide interoperability for microwave access) should complement, rather than compete with, each other.

ATE (automatic-test-equipment) makers are adapting their RF-capable systems to handle WiMax-test requirements, and makers of bench- and rack-mount test equipment are tailoring their instruments for an onslaught of components, modules, and WiMax-compatible appliances.

WiMax standards reach only far enough to attempt to ensure interoperability at the system level.

Designers must be aware of component and module EVM (error-vector magnitude) so that they can stay within an overall EVM budget.

High-performance ATE lets you characterize silicon on the ATE itself, smoothing the transition to high-volume production test.

system-level requirements, such as the EVM (error-vector magnitude) of the resolved signal and bit-error rate of the data stream. Agilent's Stark elaborates on this point. She divides the WiMax market into four segments: chips and components; modules, for which chip makers' reference designs sometimes substitute; appliances; and service providers. She concurs that EVM is a system-level spec that requires measurement at the appliance level but cautions that designers must be aware of component and module EVM of a power amplifier, for example, so that they can stay within an overall EVM budget. Ulti-

mately, she says, test will play a key role as vendors try to differentiate their components in features, RF performance, and power consumption as they strive to fit WiMax capability within the tight constraints of appliances. Stark points out that WiMax-appliance vendors fortunately won't create brand-new devices that you've never seen before. The use case for WiMax, she says, is to add WiMax to currently available devices, such as laptops, PDAs (personal digital assistants), and cell phones.

But just how a system, no matter how familiar, reaches adequate system-level performance standards varies depending on the baseband software, system design, and intended operating environment of that system. So, there is no straightforward translation between WiMax's system-performance specifications and testable behaviors on WiMax silicon.

The testing problem is easier in some functional blocks than others, however. The digital baseband, for instance, from a testing point of view, is just another fast signal processor. According to an Intel engineering spokesman, "WiMax silicon is not very different from any other SOC [system-on-chip] testing we perform at Intel. The part goes through Intel's strict product-reliability and qualification guidelines that include wafer testing, ESD [electrostatic-discharge] stressing, burn-in, and analog/mixed-signal testing across a broad range of temperature, environmental, and power-supply variability conditions. WiMax silicon can use the same DFT (design-for-test) techniques and hardware structures that are common in SOC design, such as at-speed scan, ATPG [automatic test-pattern generation], and logic and memory BIST [built-in self-test]. The process also includes package qualification, and silicon performance testing on multiple skew lots, as well as normal silicon lots."

Baseband silicon is a specialized, but still programmable, signal processor. It is either working correctly, or it isn't. Designers must adjust the software to the application, and that challenge is not a testing problem.

ANALOG SPACE

If you talk to a vendor of RF silicon, you get a different view. In the digital world, chip variations don't alter the



The Agilent E6651A WiMax test set supports protocol-conformance test as well as base-station emulation and RF-parametric measurements.

performance of a device until they become so severe as to break the circuit. In the RF and analog domains, variations in the chip are variations in the chip's performance. As one old chestnut has it, you test digital circuits, but you characterize analog ones. This distinction changes the approach test engineers must take to an emerging technology such as WiMax.

"WiMax is all over the place right now," says Tom Gratzek, business director for the WiMax silicon program at Analog Devices. "There are different frequency bands, different bandwidth requirements, different baseband filtering schemes; everyone has an approach." The company offers WiMax front-end silicon, which includes the RF stages, mixers, ADCs, DACs, and some digital filtering. Gratzek says that Analog Devices tests the digital portions of the chips in the same way as it does any other digital circuitry: with scan-based BIST. After that, things get more complex, however.

"We have to examine the analog signal chain for defects," Gratzek says. "That by itself requires hundreds of milliseconds of test time. After that, the only approach we have found to predict how the chip will work in the customer's system is to stimulate the silicon at speed." This testing is not, Gratzek explains, a full characterization. Rather, the test program is an artful compromise that the company bases on the full characterization of skew lots in the engineering lab, on the ability of test engineers to elegantly check many degrees of freedom with a few tests, and on continuous feedback from the company's applications engineers who work on customers' designs. Analog Devices drives the receiver with 2-, 3-, and 4.9- to 5.9-GHz-band test signals and drives the transmitter with corresponding digital vectors. "We sweep three frequencies in each band," Gratzek says. "Unfortunately, that [approach] forces us onto mainframe RF testers, and it adds seconds of test time."

This approach is not unique. Infineon engineers report that they also generally stimulate their WiMax silicon at speed. They use a standard 64-QAM (64-state-quadrature-amplitude modulation) Rate 2/3 of a 3.5-MHz-bandwidth signal at 4 MHz as a starting point. But Infineon is

seeing increasing pressure for customers with video-over-broadband applications to expand the bandwidth to 10 or even 20 MHz, causing changes from the silicon on up through the testing program.

Even moving to mainframe RF ATE isn't the whole solution, though. Gratzek says that Analog Devices has augmented its testers' already-formidable hardware with some custom spectral-analysis gear. That equipment also integrates some proprietary design features in the silicon and the device-under-test card to increase coverage and reduce test time. This allows the test team to sweep frequencies for an end-to-end test on the receiver side, for instance, driving the antenna inputs to the LNA (low-noise amplifier) and analyzing the output stream from the ADC for EVM and noise figures.

These top-line numbers give the company a go/no-go indication and more on

each die. For instance, the engineers can infer the SNR (signal-to-noise ratio) and linearity of the ADC from the end-to-end test. But the test team can extract even more detailed information as well, due to the high degree of digital configurability of the RF design. "We can manually control the automatic-gain-control loop, and we do so during test," Gratzek says. "We can also disembed the digital filters on the output of the chain to examine the raw digital data. And we can force the analog filters to specific characteristics, step through the gain settings on the LNA, and so forth." This approach allows the test team to move, if necessary, from the end-to-end test to an almost diagnostic level of examination while still on the production-test head.

This flexibility comes in handy. "We are delivering WiMax chips to all sorts of customers' evaluation boards, and

WIMAX MARKETS AND OPPORTUNITIES

Embedded mobile WiMax in mobile PCs will drive the emerging WiMax chip set market through 2012, says In-Stat (Reference A). "The market-research company predicts that Intel's combination Mobile WiMax (interoperability for microwave access) and Wi-Fi Echo Peak module, which will launch as an option to the company's Montevina mobile processor platform in 2008, will drive the adoption of embedded WiMax into mobile PCs. WiMax CPE (customer-premises equipment), external clients, and dual-mode cellular/WiMax handsets will also help drive WiMax-chip-set volumes through 2012, the company reports.

"The total WiMax user terminal-chip-set market will reach almost \$500 million in 2012, growing from \$27 million in 2007," says Gemma Tedesco, In-Stat analyst, in a press release. "Furthermore, WiMax base-station-semiconductor revenues are expected to be approximately \$1.4 billion in 2012, compared to \$130 million in 2007"

In a separate report, In-Stat says that, from a mobile operator's perspective, mobile WiMax provides

more of a service complement than a competitive threat (Reference B). The company notes that the mobile standard for WiMax has been the subject of debate since its inception, with debaters falling into two camps.

"One camp led by select equipment vendors with no stake in WiMax has taken an either/or approach to discussing mobile WiMax," says Daryl Schoolar, In-Stat analyst, in a press release. "Any gain by WiMax comes at the expense of other 3G data technologies. In the other camp, infrastructure vendors, such as Alcatel-Lucent, Motorola, and Nokia Siemens, see a world where multiple mobile wireless-broadband technologies will coexist. In-Stat believes that this camp's view will prevail"


REFERENCES

A "WiMax Chipset Market 2006-2012: Faith in Mobile WiMax Drives Expected Volume Growth," In-Stat, www.instat.com.

B "Complement or Threat-WiMax Strategies for Mobile Operators," In-Stat, www.instat.com.



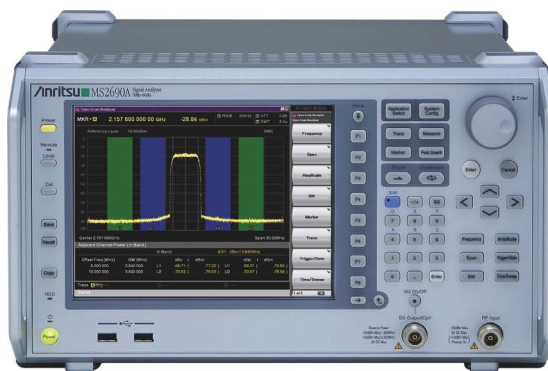The CMU270 single-instrument production tester from Rohde & Schwarz makes signaling and nonsignaling measurements of WiMax mobile stations and customer-premises equipment.



Anritsu M2690A/M2691A signal analyzers operate from 50 Hz to 6 GHz and can measure the transmitting power of mobile-WiMax devices.

they use the silicon in many ways," Gratzek says. "Our applications engineers feed use data back to the test team, and we try to adjust the tests to anticipate the sensitivities of a ... customer application. For instance, many customers change the filter settings to get the EVM they want on a ... board and antenna configuration. We try to adapt to that [configuration]." This approach means that the application-support team reserves time on the test floor for development purposes.

Commercial-test companies are working to streamline WiMax test. ATE vendors including Advantest, Teradyne, and Verigy are tailoring their systems to test WiMax devices in multisite configurations. Verigy's Smith says nothing is magical about WiMax. UWB is dealing with new spectra, but WiMax aims to make more efficient use of the allocated spectrum, he says. WiMax test is well within the capabilities of his company's Port Scale RF instrument, which Verigy introduced last summer for the V93000 system. Similarly, Advantest's 12GWS-GA RF module, which the company introduced last fall for its T2000 test system, and Teradyne's UltraWave, which the company introduced in March, will handle WiMax-chip test.

Semiconductor-ATE systems have typically focused on high throughput without necessarily providing the performance of bench-top and rack-mount instrumentation, but the advent of WiMax is changing that scenario, says Teradyne's Harvey. Measurement requirements are becoming so stringent, he says, that ATE instruments must approach bench and rack versions in measurement capability. He cites an additional advantage of high-performance

ATE: It lets you characterize silicon on the ATE itself, smoothing the transition to high-volume production test.

Companies that provide test equipment for WiMax modules and appliances as well as components include Anritsu, Agilent Technologies, Aeroflex, Tektronix, and Rohde & Schwarz, all of which make general-purpose test and measurement equipment that can perform tests on WiMax systems as well as dedicated WiMax boxes and software.

Tektronix, for example, offers the K1297-G35 WiMax protocol analyzer, which provides protocol simulation, emulation, and monitoring. In addition, Tektronix offers for its real-time spectrum analyzers the RSA-IQWiMax software, which can help detect, diagnose, and resolve WiMax-design errors. Rohde & Schwarz offers the CMU270 single-instrument production tester as well as the TS8970 WiMax-radio-conformance-test system. Anritsu offers bench-top signal-generation and analysis instruments, such as the MS2690A signal analyzer and MG3700A vector-signal generator, as well as the handheld MS2724B spectrum analyzer, which can make fixed- and mobile-WiMax measurements in the field.

Aeroflex offers WiMax-test equipment in PXI (PCI-extensions-for-instrumentation) and traditional rack-and-stack formats for testing WiMax base stations and mobile devices "from birth to death," says Argent of Aeroflex. He notes that, before vendors submit their WiMax devices to WiMax Forum-certification labs, they would benefit from doing their own precertification tests to help ensure that their devices pass the first time. When WiMax Forum labs are charging approximately \$500 per hour,

he says, customers will want to have maximum confidence that their products will pass quickly.

Agilent's offerings extend from the EEsof division's ADS (Advanced Design System) design and simulation software to WiMax-drive-test systems. Along the way, the company offers a complement of signal-generation and -analysis equipment, which can link to ADS through Agilent's Connected Solutions technology, as well as WiMax protocol analyzers and logic analyzers for baseband development and troubleshooting.

Test cost will be paramount—for chips, modules, appliances, and infrastructure installation and maintenance. Gratzek of Analog Devices summarizes the cost issue from a chip maker's perspective: "On our GSM [global-system-for-mobile-communication]-product line, we were able to substantially reduce the test cost as the market matured," he says. "We aren't at that stage yet with WiMax, but we have planned for it. We designed our ATE strategy from the beginning with an end cost point in mind and a path to get there. We may well reduce the test cost by a factor of three as the technology matures." **EDN**

AUTHORS' BIOGRAPHIES

You can reach Editor-in-Chief Rick Nelson at 1-781-734-8418 and melson@reedbusiness.com. You can reach Executive Editor Ron Wilson at 1-408-345-4427 and ronald.wilson@reedbusiness.com.

MORE AT EDN.COM

Go to www.edn.com/080403cs for this article's associated vendor box. At this URL, you can also post a comment on this article.

Green Engineering

Powered by National Instruments

MEASURE IT



Acquire environmental data from thousands of sensors



Analyze power quality and consumption



Present measured data to adhere to regulations

FIX IT



Design and model more energy efficient machines



Prototype next-generation energy technologies



Deploy advanced controllers to optimize existing equipment

For more than 30 years, National Instruments has empowered engineers and scientists to measure, diagnose, and solve some of the world's most complex challenges. Now, through the NI graphical system design platform, engineers and scientists are using modular hardware and flexible software to not only test and measure but also fix inefficient products and processes by rapidly designing, prototyping, and deploying new machines, technologies, and methods. Today, a number of the world's most pressing issues are being addressed through green engineering applications powered by NI products.


>> Download green engineering resources at ni.com/greenengineering

800 890 1345




World's Smallest Battery Charger!

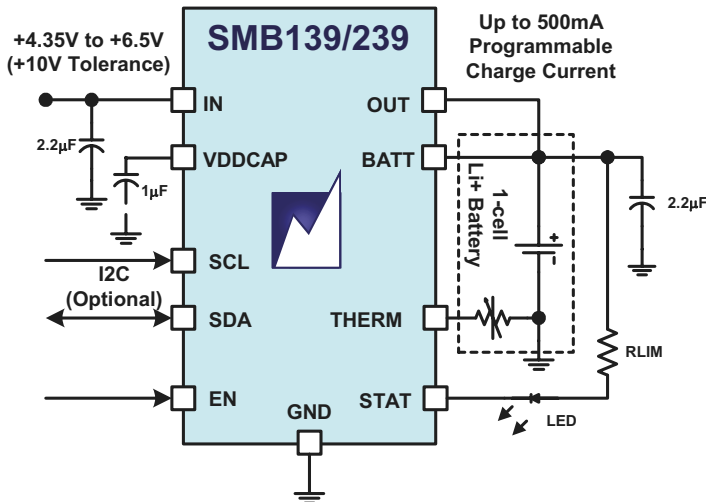Performance and Programmability in Tiny Package
500mA Charging Current - Ideal for Bluetooth™ Devices



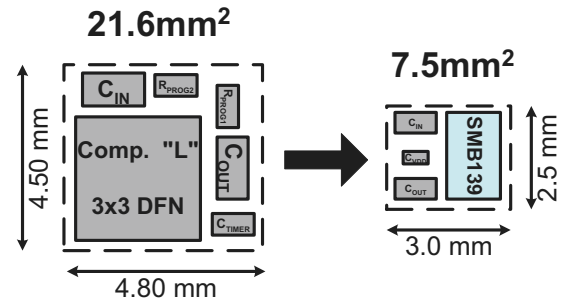Shrink Solution Size by 65% vs. Existing Chargers



SMB139/239 Applications

- Bluetooth™ phone headsets
- Bluetooth™ stereo headphones
- Ultra-thin phones/media players
- Wristwatch GPS/MP3
- Sports/wearable electronics
- Portable biometric monitors



Summit's Family of Programmable Battery Chargers

The Ideal Solution for Your Portable Application

	SMB137	SMB138	SMB135/235	SMB139/239
Topology	Switch-mode	Switch-mode	Switch-mode	Linear-mode
Input Voltage Range (V)*	4.35 to 5.5 (16)	4.35 to 6.0 (16)	4.35 to 6.5 (10)	4.35 to 6.5 (10)
# of Inputs/Outputs	2/2	1/1	1/1	1/1
Maximum Charge Current (mA)	1500	1250	900	210/500
TurboCharge™ Output	Automatic	Automatic	Software/uC	
CurrentPath™ Control	X			
USB On-The-Go Power	X	X		
Low-Battery Recovery Mode	X			
I2C Interface	X	X	X	X
Programmable Float Voltage	X	X	X	X
Programmable Charge/Term. Current	X	X	X	X
Programmable Input Current Limit	X	X		
Input/Battery OV/UV	X	X	X	X
Hardware Safety Timer	X	X	X	X
Software Watchdog Timer	X	X		
Battery Thermal Protection	X		X	X
IC Thermal Protection	X	X	X	X
Package	3.6x3.3 CSP-30	3.1x2.1 CSP-20	2.1x1.3 CSP-15 5x5 QFN-32	2.1x1.3 CSP-15 5x5 QFN-32
Solution Size (mm²)	50	28	31	7.5

* () Indicates overvoltage "holdoff" tolerance

For more information see:
www.summitmicro.com/SMB139

SUMMIT
 MICROELECTRONICS

Programmable Power for a Green Planet™

Boost efficiency for low-cost flyback converters

MANY DEVICES EMPLOY FLYBACK CONVERTERS BECAUSE OF THEIR SIMPLICITY AND LOW COST—NOT THEIR STELLAR EFFICIENCY. BUT DON'T TOO QUICKLY ELIMINATE FLYBACKS FROM YOUR LIST OF OPTIONS. WITH A FEW LITTLE-KNOWN TRICKS, YOU CAN IMPROVE POWER LOSS BY NEARLY 10%.

In a conventional diode-rectified flyback converter, the output diode rectifier is a substantial power-loss contributor. The average current in the output diode is equal to the dc output current, and the peak current can be several times higher, depending on the duty cycle. The forward-voltage drop of the diode is typically 0.5V for Schottky diodes and 0.8V for standard PN-junction diodes. This large forward-voltage drop leads to relatively high losses in the diode and a substantial reduction in efficiency.

Replacing the diode with a synchronous MOSFET significantly reduces these conduction losses. **Figure 1** illustrates how you can convert a standard diode-rectified flyback supply into a self-driven-synchronous-flyback supply.

In the self-driven-synchronous flyback, an N-channel MOSFET replaces the output diode, and you must add a winding to the power transformer to generate the synchronous-gate-drive signal. The low on-resistance of the synchronous MOSFET yields much less conduction loss than the output-diode rectifier, significantly improving the efficiency at high load currents.

There is a fundamental difference between the operation of a diode-rectified flyback and a synchronous flyback. **Figure 2** shows the key waveforms. The output diode in the diode-rectified flyback prevents the transformer secondary current from flowing backward. At light loads, this condition results in DCM (discontinuous-current-mode) operation in which the transformer's secondary current completely discharges into the output at the end of each cycle. The synchronous MOSFET allows current to

continue to flow in the negative direction and forces the synchronous flyback to always operate in CCM (continuous-current mode) regardless of load current. This situation is generally beneficial in that the control loop gain does not decrease as it does when it transitions into DCM operation, thereby maintaining full dynamic performance, even at zero load. The use of synchronous MOSFETs has a negative impact on zero- or light-load efficiency, because relatively large ac cur-

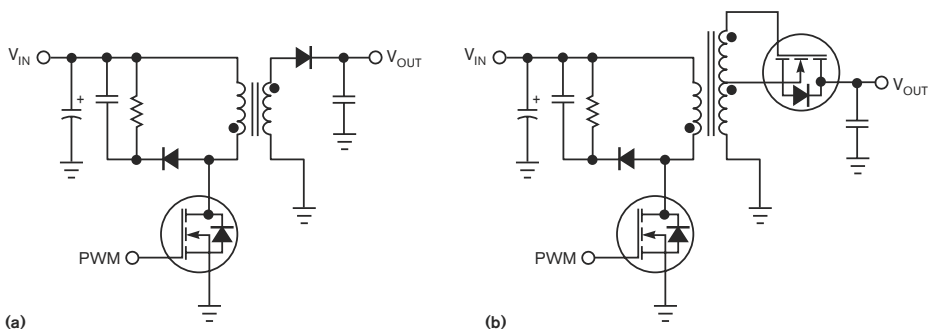


Figure 1 Replacing the output diode with an N-channel MOSFET and adding a winding to the power transformer to generate the synchronous-gate-drive signal can convert a standard diode-rectified flyback supply (a) into a self-driven synchronous-flyback supply (b).

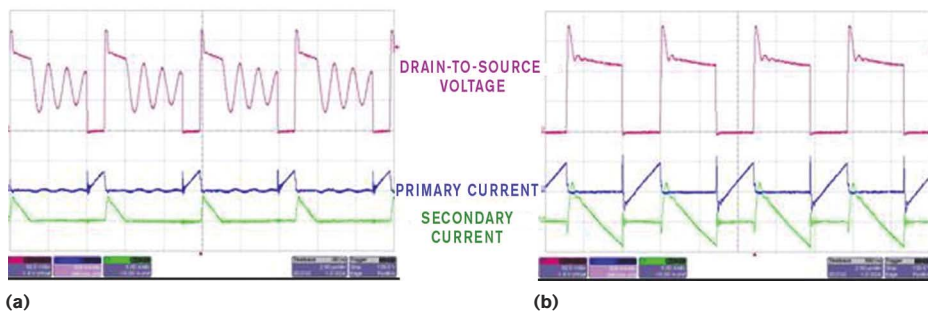


Figure 2 The output diode in the diode-rectified flyback prevents the transformer secondary current from flowing backward. At light loads, this situation results in discontinuous-current-mode operation in which the transformer's secondary current discharges completely into the output at the end of each cycle (a). The synchronous MOSFET allows current to continue to flow in the negative direction and forces the synchronous flyback to always operate in continuous-current mode, regardless of load current (b).

rents flow with little or no net dc-output current. Transformer and primary-MOSFET switching losses associated with these circulating currents are larger than those in the diode-rectified flyback, whose currents decrease in amplitude at light loads.

Although the synchronous MOSFET significantly lowers conduction losses, it introduces gate drive, switching, and shoot-through losses that are not present in the diode-rectified flyback. Gate-drive losses result from the capacitance of the MOSFET gate that charges and discharges during each switching cycle. At the turn-on and turn-off transitions of the MOSFET, switching losses occur as the drain-to-source voltage and the drain current exhibit overlap. Shoot-through occurs because the primary switch must turn on before the secondary FET can start to turn off. This situation places a short circuit across the transformer during switching and can lead to substantial power loss. In the self-driven synchronous flyback, the primary-MOSFET turn-on commands the synchronous-MOSFET turn-off. Hence, it is impossible to eliminate the shoot-through currents when the power transformer directly drives the synchronous MOSFET. A self-driven synchronous MOSFET must have fast-turn-off delay and fall times to minimize shoot-through losses. Although a properly designed synchronous MOSFET introduces additional switching losses, the conduction losses are typically substantially lower than the diode-rectifier-forward-drop losses. This one benefit alone typically outweighs all synchronous MOSFETs' negatives.

Figure 3 shows how you can add an isolated gate-drive signal with programmable delays to the synchronous flyback to eliminate shoot-through losses. The device achieves isolation and level-shifting through a gate-drive transformer. A PWM controller with complementary drive outputs and adjustable delays, such as the UCC2897, is necessary to control the primary- and secondary-side synchronous MOSFETs. The delays must be long enough to ensure that the synchronous

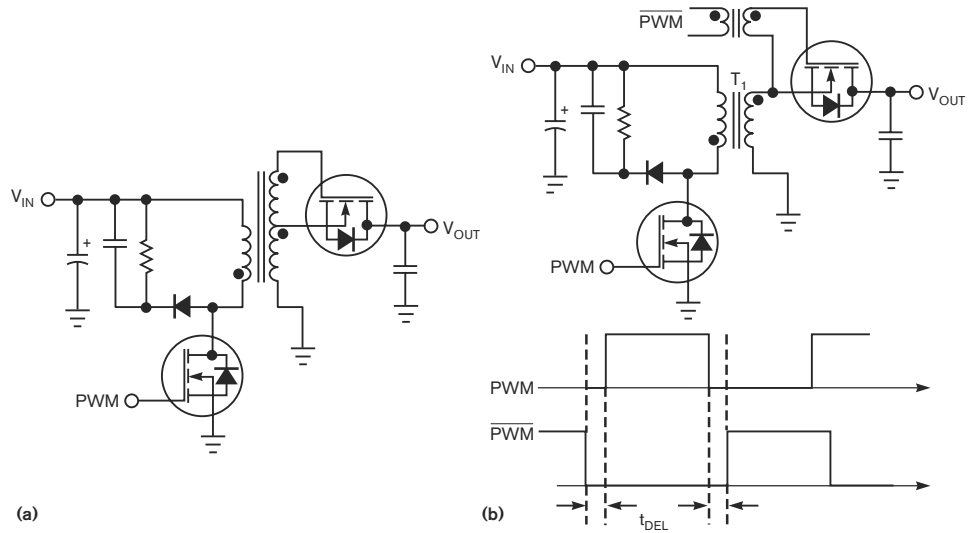


Figure 3 Adding an isolated gate-drive signal with programmable delays to the synchronous flyback (a) can eliminate shoot-through losses (b).

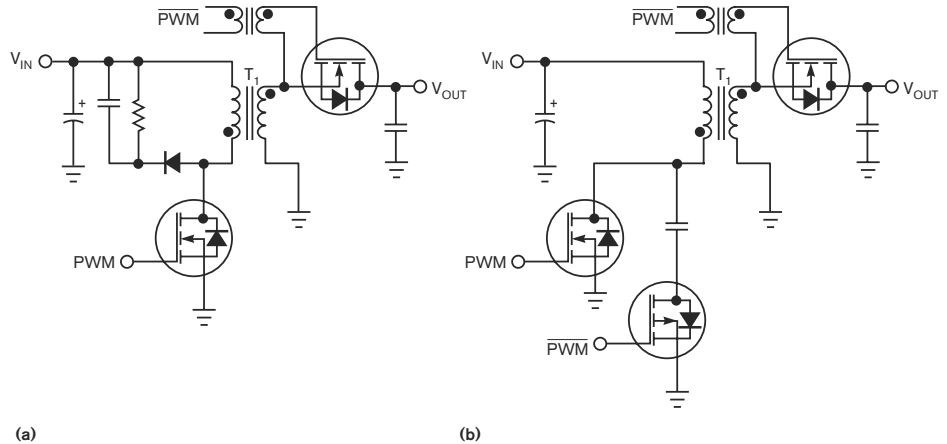


Figure 4 In the active-clamp flyback (a), the clamp capacitor captures the leakage energy, and the system recirculates it to the load and back to the input, resulting in a virtually lossless snubber (b).


MOSFET is fully off before the primary MOSFET switches on. Excessive delay causes body-diode conduction on one or both of the MOSFETs and leads to excess power loss. Because the optimal dead time depends on the primary- and secondary-MOSFET delay, transition speed, power-transformer-leakage inductance, and gate-drive circuit, a controller with adjustable delay is critical to minimizing losses.

Figure 4 illustrates how to further improve the efficiency and take advantage of the synchronous-MOSFET-gate-drive signal to control an active primary snubber. This configuration

■ EMI: Best in Class
■ ESD: > 6 kV



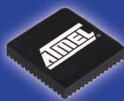Unbeaten! The Best EMC Performance You Can Get



Having difficulty making your designs pass car makers' quality tests? Looking for OEM-approved LIN parts?

Atmel supplies a complete LIN IC family with industry's best EMC performance, ranging from standard LIN transceivers and system basis chips (with voltage regulator, watchdog, output driver) to complete highly integrated SiP solutions incorporating Atmel's famous AVR[®] μ C. All parts are compliant with the LIN2.0 stan-

dard and SAEJ2602-2 and have OEM approval from all major car makers.

Thanks to our proven high-voltage BCD-on-SOI technology, high integration, excellent EMC protection and operation up to 40V go without saying.

Trust the expert! Atmel, an automotive specialist, has 25-plus years of automotive design experience with successful design-ins at all large Tier1s.

Part Number	Function	Description
ATA6662	Standard LIN Transceiver	Including Atmel's 2 nd -generation LIN IP with Excellent EMC Performance
ATA6622, ATA6623, ATA6624, ATA6625, ATA6626	LIN System Basis Chip (SBC)	ATA6662 plus Voltage Regulator and Watchdog
ATA6823	LIN SBC for H-bridge Applications	ATA662x plus H-bridge Gate Driver
ATA6612, ATA6613	LIN System in Package (SiP) Solution	ATA6624 plus 8/16K AVR Microcontroller

Go to www.atmel.com/ad/automotive today to apply for a free LIN demo board.



is often called an active-clamp flyback. In the previous figures, the design employed a snubber to reduce the voltage spike on the drain-to-source voltage of the primary MOSFET. The spike occurs at turn-off of the primary MOSFET and is due to the leakage energy in the primary winding of the transformer. The RCD (resistor-capacitor-diode) snubber dissipates this energy in its snubber resistor. In the active-clamp flyback, the clamp capacitor captures the leakage energy, and the system recirculates it to the load and back to the input, resulting in a virtually lossless snubber. **Figure 5** shows the drain-to-source voltage waveforms of an RCD snubber versus an active clamp. The active clamp eliminates the high-frequency spike. In addition to virtually eliminating the leakage losses, the design significantly reduces switching losses and EMI (electromagnetic interference). In many cases, the active-clamp snubber allows the use of a lower drain-to-source-voltage-rated primary MOSFET, which can further reduce losses and possibly reduce the cost of the MOSFET.

Figure 6 shows how much each upgrade to the diode-rectified flyback improves the efficiency of a real-world design. The power supply converts a telecom 48V-dc input to a 3.3V output with a maximum load current of 3.5A. Converting from a diode rectifier to a self-driven-synchronous-flyback device improves the maximum load efficiency by more than 7% but decreases the light-load efficiency below an output current of 1A. This situation occurs because of the gate-drive, switching, and shoot-through losses that the synchronous MOSFET

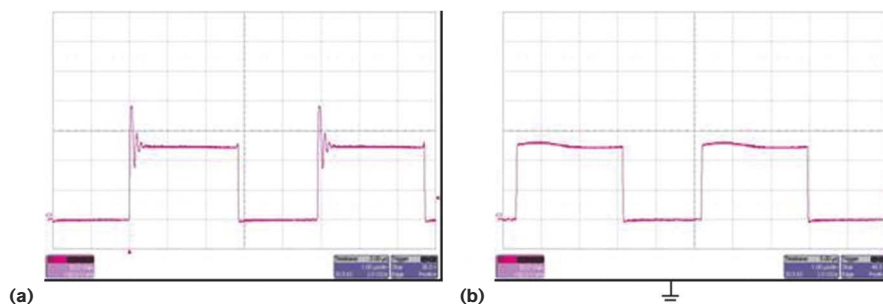


Figure 5 The drain-to-source-voltage waveforms of a programmable dead-time synchronous flyback circuit employ an RCD snubber (a) and an active clamp (b). The active clamp eliminates the high-frequency spike. In addition to virtually eliminating the leakage losses, this approach significantly reduces switching losses and EMI.

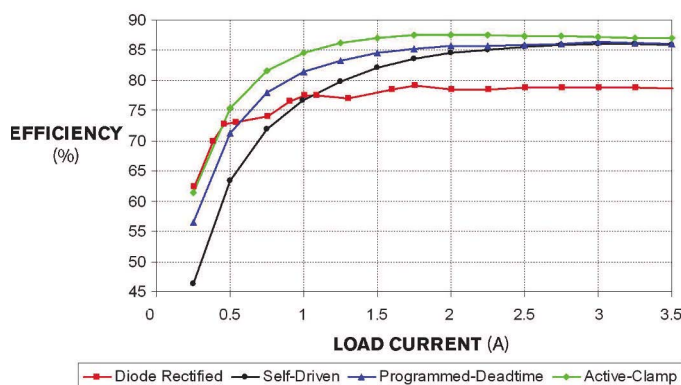


Figure 6 Using a power supply that converts a telecom 48V-dc input to a 3.3V output with a maximum load current of 3.5A as an example, each upgrade to the diode-rectified flyback improves the efficiency on a real-world design.

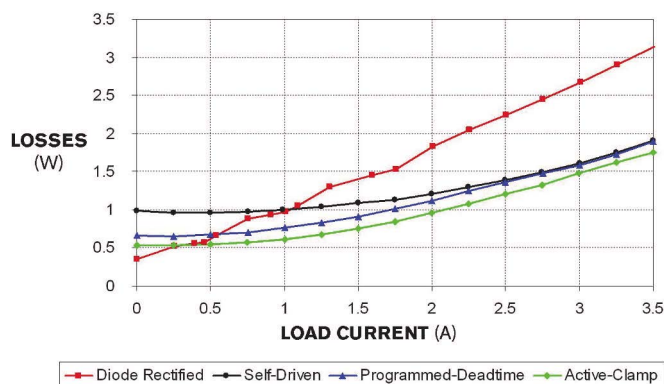


Figure 7 Introducing a programmable dead-time delay increases the light-load efficiency significantly by eliminating the shoot-through losses. The full-load efficiency remains nearly identical, because other circuit losses dominate the synchronous MOSFET losses. Implementing the active clamp increases the efficiency of the 3.3V supply across all loading conditions.


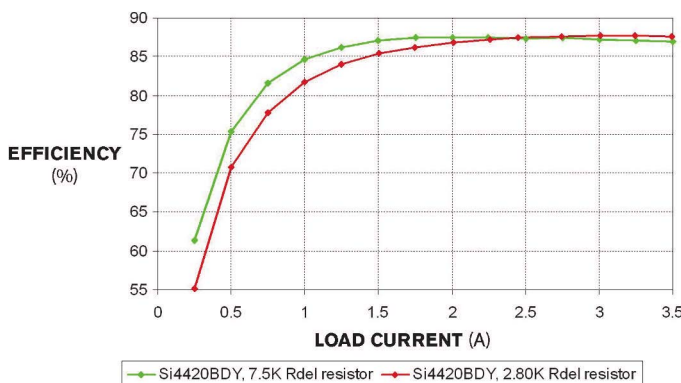


Figure 8 The delay resistor determines the dead time. In some situations, you may have to choose between maximizing efficiency at light loads or maximum load by selecting the appropriate delay-resistance value.

You DESIGN It We BUILD It

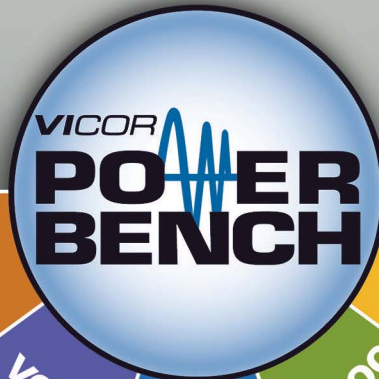Use the Most Comprehensive Power Design Tools Available



Custom Module Design System

Configure a DC-DC converter from hundreds of existing designs for:

- Environmental grade
- Baseplate style
- Pin options
- or....
- Specify your custom design and verify its feasibility in real time with our module design simulator



CMS

VCAD

Product Selector

VSPOC

Design Configurators



Design Configurators

- Select a DC-DC converter from the broadest array of input voltages, output voltages and power levels
- Configure a DC-DC or AC-DC power supply up to three outputs and 600 watts

Vicor Computer Assisted Design

- Configure your design of Vicor's VIPAC and VIPAC Array family
- Specify input voltage, output voltages and power levels, mechanical configurations, thermal and connection options.



- Identifies the Vicor product(s) that meet your requirements
- DC-DC converters, modular filters and front ends, and a broad range of AC-DC and DC-DC configurable power supplies

Vicor Systems Product Online Configurator

- Easy, rapid solutions from Westcor's broad product line of AC-DC supplies
- Configure your specific power supply requirements
 - Outputs 1 to 400 V in 0.1 V steps
 - Up to 20 isolated outputs per supply
- Get your unique model number online and your prototype order can be shipped in 10 days or less

PowerBench gives you the power to specify your own power design solution.

And verify it in real time. All on line.

It's fast, easy, and cost effective!



Visit the Vicor website at www.vicorpower.com/powerbench

Call Vicor Technical Support at 800-927-9474



vicorpower.com/powerbench

introduces. These losses become a larger percentage of the total losses at light loads and consequently decrease light-load efficiency (**Figure 7**). Introducing a programmable dead-time delay significantly boosts the light-load efficiency by eliminating the shoot-through losses. The full load efficiency remains nearly identical, because other circuit losses dominate the synchronous-MOSFET losses. Finally, implementing the

MORE AT EDN.COM ►

Go to www.edn.com/ms4268 and click on Feedback Loop to post a comment on this article.

active clamp increases the efficiency of the 3.3V supply across all loading conditions.

Figure 8 shows two delay settings in the active-clamp circuit and how they affect the efficiency at different loading conditions. A longer delay, which you program on the UCC2897 by using a larger value for

a delay resistor significantly improves the light-load efficiency by decreasing the shoot-through losses at light load. But this longer delay also increases the synchronous MOSFET's body-diode conduction time and, at full load, reduces the efficiency by about 1%. The full-load synchronous-MOSFET body-diode-conduction losses dominate the shoot-through losses when using a lower delay resistance. In some situations, you may have to choose between maximizing efficiency at light loads or maximum load by selecting the appropriate delay-resistance value. **Figure 9** shows the active-clamp-fly-

back-power supply implementing all of the efficiency-improving techniques. This configuration yields nearly a 10% efficiency improvement at maximum load and has nearly the same light-load-efficiency performance as the original diode-rectified design. **EDN**

REFERENCES

1. Betten, John and Brian King, "Benefits of adding an active clamp to a synchronous flyback power supply," *EDN*, Dec 14, 2006, www.edn.com/article/CA6399933.
2. "UCC2897, Current Mode Active Clamp PWM Controller," Texas Instruments, www.ti.com/sc/device/ucc2897.

AUTHORS' BIOGRAPHIES



John Betten is an application engineer and senior member of the group technical staff at Texas Instruments. He has 22 years of ac/dc- and dc/dc-power-conversion-design experience. He received a bachelor's degree in electrical engineering from the University of Pittsburgh and is a member of IEEE.



Brian King is an application engineer and a member of the group technical staff with Texas Instruments. He is a member of IEEE and holds bachelor's and master's degrees in electrical engineering from the University of Arkansas.


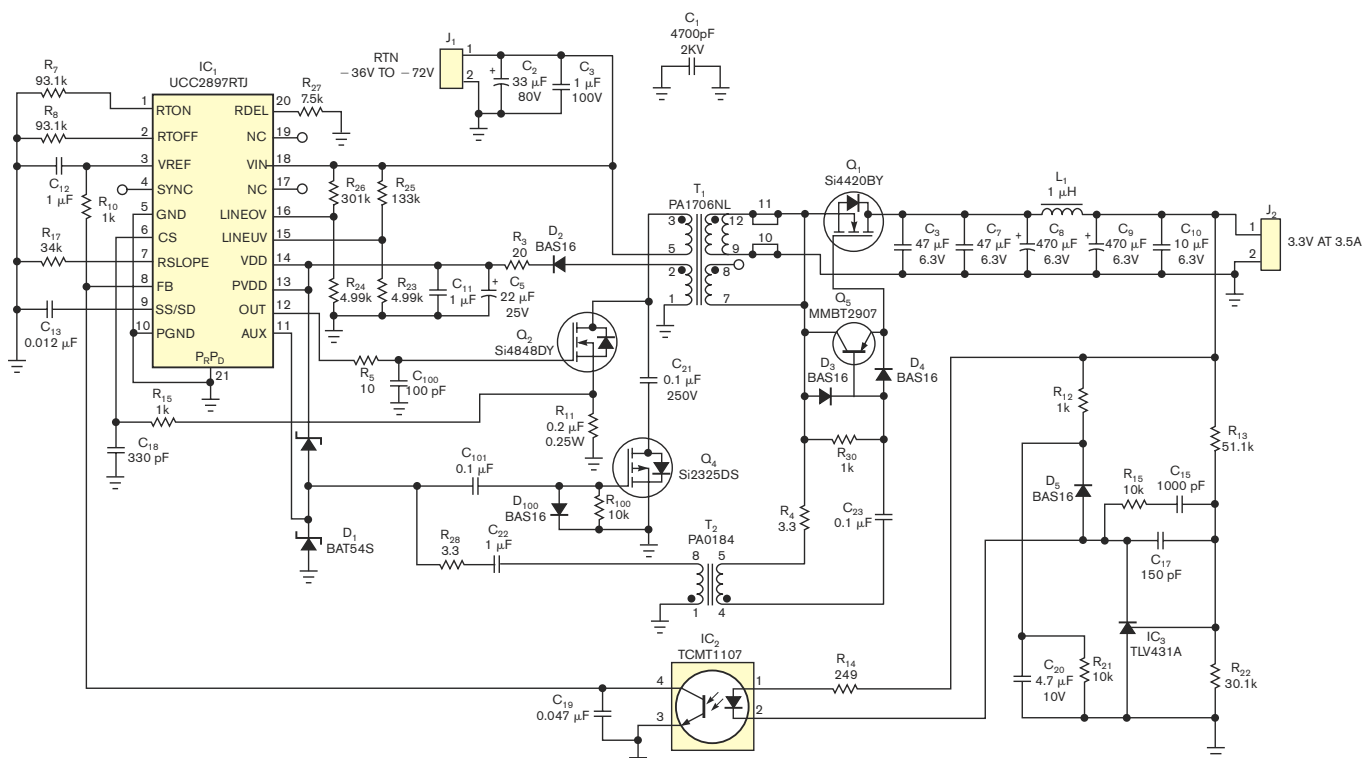


Figure 9 The active-clamp flyback power supply implements all of the efficiency-improving techniques, yields a nearly 10% efficiency improvement at maximum load, and has nearly the same light-load efficiency performance as the original diode-rectified design.

GENIUS KNOWS NO BOUNDARIES

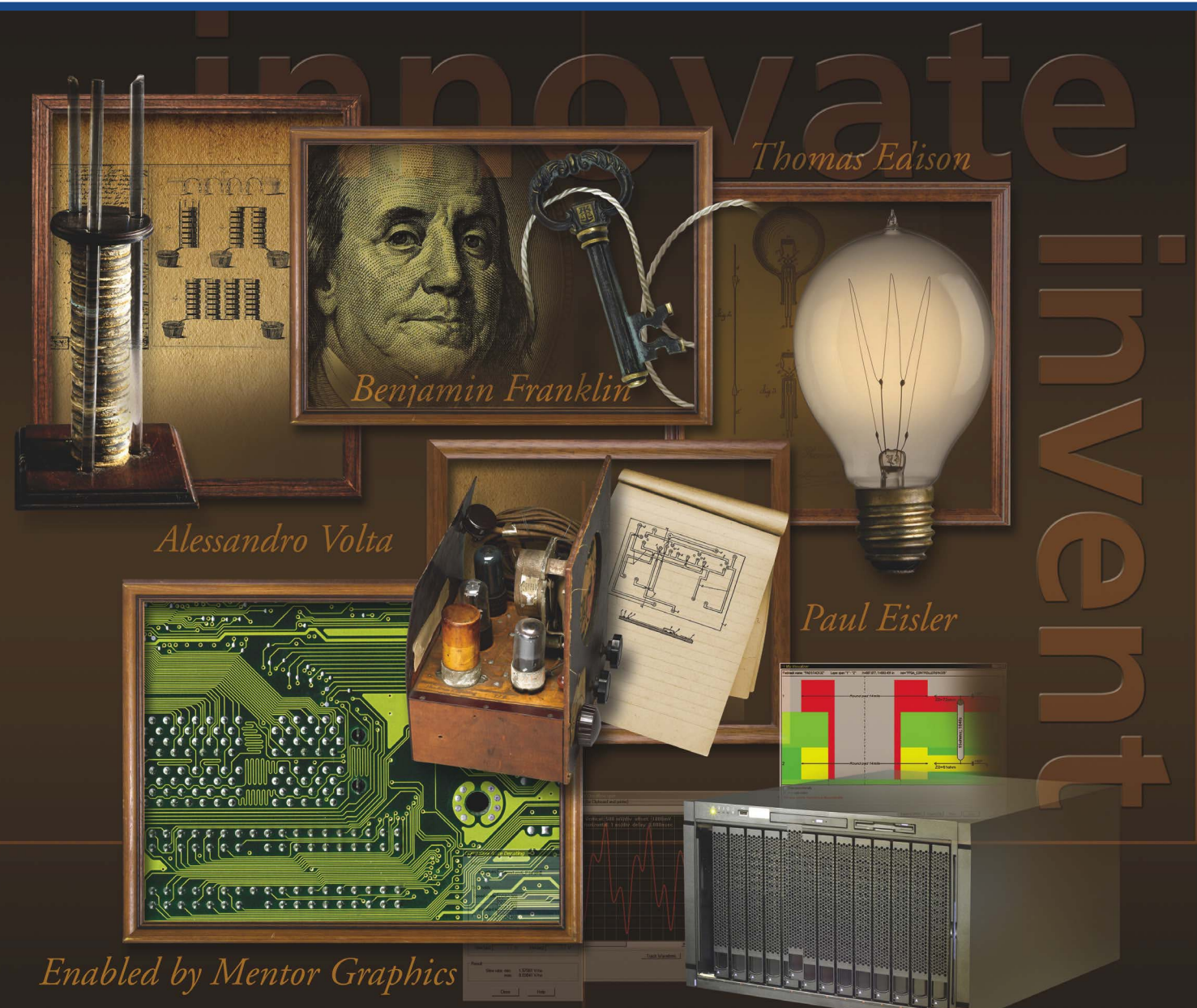

INTEGRATED SYSTEM DESIGN + DESIGN FOR MANUFACTURING + ELECTRONIC SYSTEM LEVEL DESIGN + FUNCTIONAL VERIFICATION

PCB Design Solutions | The great minds of the past were driven by their passion to innovate. Today, the drive to innovate continues with a different set of time, budget and resource constraints. With Mentor Graphics innovative PCB design solutions, teams are free to develop and optimize creative ideas effectively and more efficiently. Release your imagination and realize your greatest potential with Mentor. Visit us at www.mentor.com or call 1-800-547-3000.

**Mentor
Graphics®**
THE EDA TECHNOLOGY LEADER

Intersil Switching Regulators

High Performance Analog



Take Control.

Intersil's ISL65426 dual-channel, synchronous buck regulator has **user-configurable power blocks that enable quick design and reconfiguration of power supply systems** for FPGAs, CPLDs, core processors, and ASICs.




ISL65426 Key Features:

- 180° out-of-phase operation
- Startup in a pre-biased load
- Independent output soft-start
- Stable all ceramic solutions
- High efficiency: 95%
- $\pm 1\%$ system accuracy over temperature

Output Current Configurations

I _{1SET}	I _{2SET}	I _{OUT1}	Channel 1 Connections	I _{OUT2}	Channel 2 Connections
1	1	3A	LX1, LX2, LX3	3A	LX4, LX5, LX6
1	0	4A	LX1, LX2, LX3, LX4	2A	LX5, LX6
0	1	5A	LX1, LX2, LX3, LX4, LX6	1A	LX5
0	0	2A	LX1, LX2, LX3, LX4, LX6	4A	LX3, LX4, LX5, LX6
Invalid LX Configurations: SS Prevented					
X	X	1A	LX2	5A	LX1, LX3, LX4, LX5, LX6

Six Integrated 1A Power Blocks

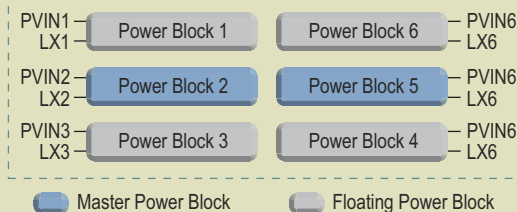

Go to www.intersil.com for samples, datasheets and support



Intersil – Switching Regulators for precise power delivery.

©2007 Intersil Americas Inc. All rights reserved. The following are trademarks or services marks owned by Intersil Corporation or one of its subsidiaries, and may be registered in the USA and/or other countries: Intersil (and design) and i (and design).



Critical clock-domain-crossing bugs

AWARENESS OF CDC ISSUES, ALONG WITH THE USE OF GOOD DESIGN PRACTICES AND PROVEN EDA TOOLS FOR CDC VERIFICATION, CAN AVOID COSTLY SILICON RE-SPINS AND SIGNIFICANTLY IMPROVE TIME TO MARKET.

Today's SOC (system-on-chip) designs have dozens of clocks, many of which are asynchronous. This design approach facilitates the convergence of digital-audio, video, wireless, and networking applications in a single chip. CDCs (clock-domain crossings) can cause difficult-to-detect functional failures in SOCs involving multiple asynchronous clocks. Simulation and static-timing analysis often do not detect issues such as metastability and the coherency of correlated signals' CDCs; as a result, these issues often end up as bugs in silicon. Unfortunately, most relevant literature does not adequately cover some of these critical CDC issues, and designers learn about them only after making costly mistakes. Two of the most common and critical issues involving CDCs are improper sequencing of data/enable in enable-based synchronization and data coherency due to the convergence of signals.

ENABLE-BASED SYNCHRONIZATION

A receiver flip-flop output can become metastable if it violates the data/reset setup-and-hold times. This scenario can arise when the transmitter—the source of data—and the receiver flip-flop are in asynchronous-clock domains. To avoid such issues, designers use synchronizers that isolate metastability and deliver a clean signal to the downstream logic. A

synchronizer can be a simple double flip-flop. Designers commonly use this technique for a control signal's CDCs. In a data transfer across clock domains, the data is first set up; then, a control signal that synchronizes with the destination domain travels to the destination to enable data capture. Although this data-transfer technique across clock domains is a common and proven technique, it involves pitfalls that require special attention. This technique relies on data to be stable when you assert an enable (Figure 1).

Having too low a margin between the data you are setting up and the enable you are asserting may corrupt the data transfer. A good way to prevent such problems is to design a full handshake when you set up the data. In this approach, you assert and synchronize the request in the destination domain and adequately assert an acknowledge to let the next data load occur. This approach might add a few cycles of latency, but it avoids functional failures.

Glitches are other sources of worry across clock domains. Typically, any combinational logic may be subject to short-lived glitches. These issues are generally harmless because they resolve themselves when you activate the next clock edge. Although these issues are not problematic for synchronous transfers, a glitch may occur with asynchronous crossings if you activate a destination clock. The design may therefore receive a glitch as a pulse, causing a functional failure. For this reason, it is important to avoid using any combinational logic that may cause glitches on a CDC path. You

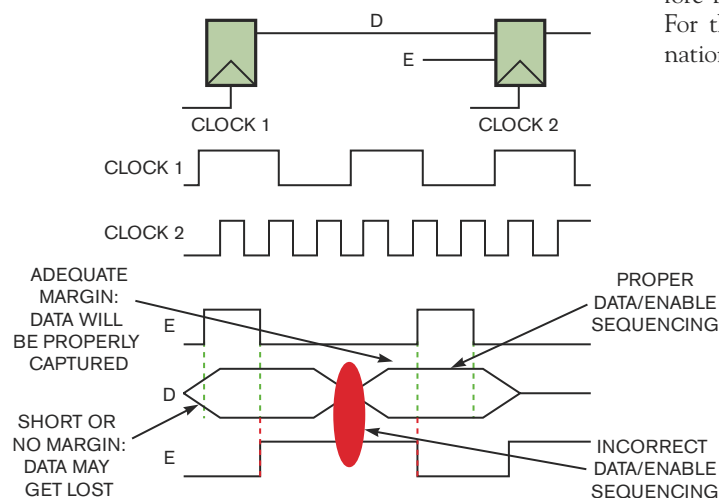


Figure 1 In a data transfer across clock domains, the data must be stable when enable is asserted. Too short of a margin between data setup and enable assertion can result in data corruption.

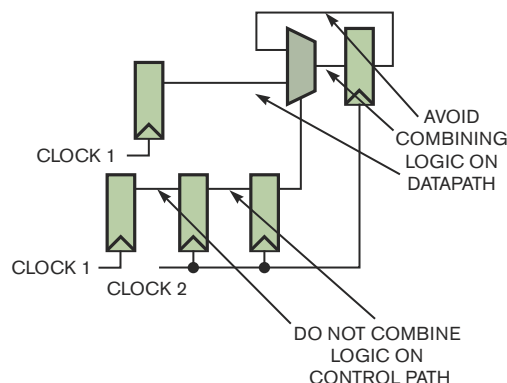


Figure 2 A good design practice is to avoid using any logic, except the recirculation-multiplexer logic, which is part of the enable flip-flop, on the datapath CDCs.

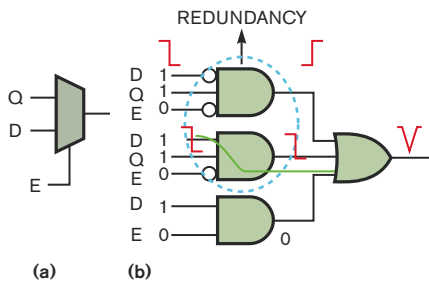


Figure 3 You can map a simple, glitch-free multiplexer (a) with AND and OR gates that can create glitches (b).

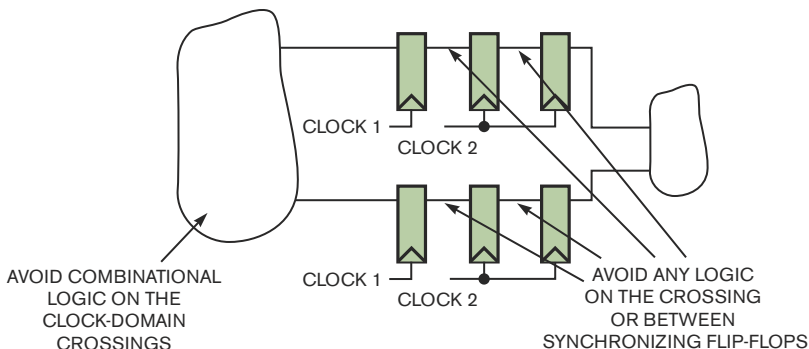


Figure 4 Any glitch in the Gray encoder may cause a functional failure in the design.

should perform any computation either before crossing clock domains or after the destination domain captures the signals.

Glitches may affect both control and data CDCs. In a data transfer, a glitch may affect the enable line or the data line; both present risks affecting safe data transfer. You must synchronize the enable logic in the destination domain and avoid using combinational logic after synchronization. Glitches on the datapath may be harmful, too. A good design practice is to avoid using any logic, except the recirculation-multiplexer logic, which is part of the enable flip-flop, on the datapath CDCs (Figure 2).

Although this data-synchronization scheme is the most common, many variations of enabled-data crossing involve an enable signal with combinational logic. Occasionally, design-

ers use an enabled AND instead of a multiplexer or combine the multiplexer with other combinational logic on the datapath. They rely on the enable signal to ensure that data synchronously transfers to the destination and that glitches do not occur. As designers become more creative and use extra logic in enabled-data crossings, they expose their designs to glitch risks that are difficult to detect. To comprehend these risks, consider a simple example of a glitch-free multiplexer; you can implement this multiplexer so that it can create a glitch. Downstream tools, such as synthesis, optimization, and technology mapping, can transform the circuit and introduce logic that can cause a glitch and thus cause a functional failure. You can map a simple, glitch-free multiplexer with AND and OR gates that can create glitches (Figure 3).



TAITRONICS Taipei International Electronics Show

Oct. 7-11, 2008

Venue:
TWTC Nangang Exhibition Hall

In conjunction with



Taiwan RFID

Taiwan Int'l RFID Applications Show **October 7-11**
Venue: TWTC Nangang Exhibition Hall



Broadband Taiwan

Taiwan Broadband Show **October 7-11**
Venue: TWTC Nangang Exhibition Hall



Photovoltaic Forum & Exhibition Taiwan

Taiwan International Photovoltaic Forum & Exhibition **October 7-8**
Venue: TWTC Exhibition Hall



Featuring

- *Electronic Components & Equipment
- *Meters & Instruments
- *Wires & Cables
- *Electronic Manufacturing Equipment
- *Inspection Equipment
- *Consumer Electronics

- *Security Systems & Products
- *Computers & Peripherals
- *Audio & Video
- *Auto Electronics
- *Stage Technology & Illumination Devices

www.taitronics.org/taipei

Organizers:



Taiwan External Trade Development Council (TAITRA)

www.taiwantrade.com.tw
www.taitra.org.tw
taitronics@taitra.org.tw



Taiwan Electrical & Electronic Manufacturers' Association (TEEMA)
www.teema.org.tw



Sponsor:

Taipei World Trade Center
www.twtc.org.tw

TAIWAN TRADE CENTER, NEW YORK
TAIWAN TRADE CENTER, SAN FRANCISCO

newyork@taitra.org.tw
sf@taitra.org.tw

TAIWAN TRADE CENTER, MIAMI
TAIWAN TRADE CENTER, CHICAGO

miami@taitra.org.tw
chicago@taitra.org.tw

The Heat is Off

High-Efficiency Power Solutions Reduce Heat, Save Energy, and Conserve Space

Power-One's high efficiencies enable some of the industry's greenest power solutions, advantages include:

- Reduced energy consumption.
- Increased power densities.
- Improved performance in elevated ambient-temperature environments.
- Less dissipated heat lowers system and site-level cooling costs.

<i>Products</i>	<i>Applications</i>	<i>Efficiency</i>
Hot-Swap Front Ends	Data Servers/Storage, Industrial, and Communications	91%
DC-DC Bricks	DPA, Bus Converters, RF Amplifiers, DOSA Compliant, and Military	97%
POL Conversion and Management	Z-One® Digital IBA, Analog IBA, and DOSA Compliant	95%
AC-DC Chassis Mount	Industrial, Medical, Datacom, CompactPCI, and PoE	91%
DIN-Rail, PSR, and Cassette	Railway, Communications, Military, and Rugged Industrial	97%



power-one®
Changing the Shape of Power

www.power-one.com

Power-One and Z-One are registered trademarks of Power-One, Inc.

Although this transformation may seem unlikely with a stand-alone multiplexer, it may well occur if you introduce more logic on the datapath. Synthesis and optimization tools may identify opportunities to increase timing performance, reduce area, or decrease power consumption by combining multiplexer logic with other logic on the path; however, these tools may also create a final implementation prone to glitches. To avoid such problems, you should control the use of these tools to avoid such transformations. Unfortunately, designers often fail to consider these details when creating and implementing a design. Furthermore, a glitch is not an easily predictable event; simulation or static-timing verification cannot detect a glitch on an asynchronous crossing. Once the symptom appears in silicon, it is difficult to perform a root-cause analysis. It takes significant effort and time to link silicon failures to a glitch on a CDC. Static-CDC analysis is better for systematically catching and reporting such issues and avoiding costly silicon re-spins.

DATA COHERENCY

Another critical issue involving asynchronous clocks is the coherency problem due to convergence of independently synchronized signals. CDCs introduce latency and cycle-level un-

	BINARY COUNT	GRAY COUNT
0	000	000
1	001	001
2	010	011
3	011	010
4	100	110
5	101	111
6	110	101
7	111	100

Figure 5 A Gray encoder targeting counting from zero to seven for a full 3-bit counter will fail when the pointer moves from five to zero.

BAD GRAY CODE
IF COUNT
GOES TO FIVE


GOOD GRAY CODE
IF COUNT
GOES TO SEVEN

certainly, even with synchronized crossings. Although synchronizers isolate metastability and ensure that a “clean” signal travels to downstream logic, they cannot prevent latency. Coherency problems occur when two correlated, separately synchronized signals cross clock domains; each synchronizer introduces a different latency factor due to the CDC. If one of the signals captures a transition, metastability settles to the correct value in the first cycle, whereas the other signal captures a transition in the next cycle. That is, metastabil-

ity settles to an incorrect value, and you must wait for the next clock cycle to capture the transition. Then, you will observe an incorrect set of values at the destination for at least one cycle. If the signals represent a state variable, then you will observe an unknown or unwanted state at the destination. This unknown state causes a functional failure in the design.

This problem is one of the most common in CDC, and it is becoming more important as designs become larger. Design reuse and IP (intellectual-property) integration may create convergences of which designers may be unaware. To avoid coherency problems—assuming that you know the convergences—you should use correlated signals so that they change values at different times. You must use Gray encoding to correlate signals that are CDCs. This scenario occurs when FIFO point-

Analog ICs for Signal Conditioning

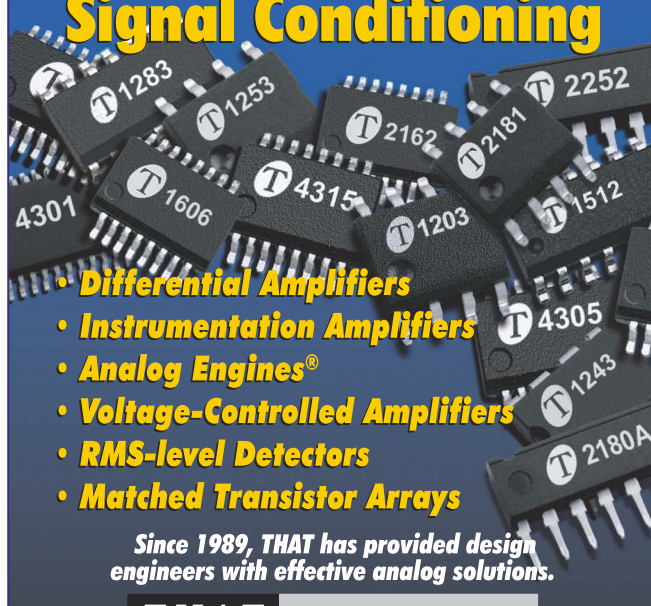

- **Differential Amplifiers**
- **Instrumentation Amplifiers**
- **Analog Engines®**
- **Voltage-Controlled Amplifiers**
- **RMS-level Detectors**
- **Matched Transistor Arrays**


Since 1989, THAT has provided design engineers with effective analog solutions.

THAT Corporation

Analog Circuits Made Easy™

For datasheets and more information visit
www.thatcorp.com or email: info@thatcorp.com

POTS SIGNALLING



The CMX865A DTMF codec and telecom signalling and data combo offers increased flexibility when designing telemetry and telephone based systems.

The low-cost CMX865A offers advanced performance and low power requirements in a small footprint package making it ideal for Wireless Local Terminals (FCT/FWT/FWP), Private Branch Exchanges (PBXs), Alarm and Monitoring applications and more...

- ▶ Integrated FSK Modem
- ▶ DTMF Codec
- ▶ Call Progress Detect/Generate

www.cmlmicro.com/Telecoms/10
A CML Microsystems Plc Company

CML Microcircuits
COMMUNICATION SEMICONDUCTORS

Drive LEDs Your Way



High Efficiency LED Drivers

Part No.	Topology	Dimming Range	Input Voltage Range (V)	Max. Output Voltage (V)	$I_{LED(MAX)}$ (A)*	Package
LT®1618	Buck, Boost, Buck/Boost Mode	DC/PWM	1.6 to 18	36	1.00	3mm x 3mm DFN-10, MSOP-10
LT3466	Dual Boost	DC/PWM	2.7 to 24	39	0.02 x 2	3mm x 3mm DFN-10
LT3474/-1	Buck	400:1 PWM	4 to 36	9/25	1.00	TSSOP-16E
LT3475/-1	Dual Buck	3000:1 PWM	4 to 36 (40 Max.)	9/25	1.50 x 2	TSSOP-20E
LT3476	Quad Buck, Boost, Buck/Boost Mode	1000:1 PWM	2.8 to 16	36	1.00 x 4	5mm x 7mm QFN-38
LT3477	Buck, Boost, Buck/Boost Mode	DC/PWM	2.5 to 25	40	2.00	4mm x 4mm QFN-20, TSSOP-20E
LT3478/-1	Buck, Boost, Buck/Boost Mode	3000:1 PWM	2.8 to 36 (40 Max.)	40	4.00	TSSOP-16E
LT3486	Dual Boost	1000:1 PWM	2.7 to 24	35	0.10 x 2	3mm x 5mm DFN-16
LT3496	Triple Buck, Boost, Buck/Boost Mode	3000:1 PWM	3 to 30 (40 Max.)	45	0.50 x 3	4mm x 5mm QFN-28
LT3517/18	Buck, Boost, Buck/Boost Mode	5000:1 PWM	3 to 30 (40 Max.)	45	1.0/2.0	4mm x 4mm QFN-16
LT3590	Buck Mode	200:1 PWM	4.5 to 55	n/a	0.05	2mm x 2mm DFN-6, SC-70
LT3595	Buck Mode	3000:1 PWM	4.5 to 45	n/a	0.05 x 16	5mm x 9mm QFN-56
LT3755/56	Buck, Boost, Buck/Boost Mode	3000:1 PWM	4.5 to 40/6 to 100	60/100	Ext. FET	3mm x 3mm QFN-16, MSOP-16E
LTC®3783	Buck, Boost, Buck/Boost Mode	3000:1 PWM	3 to 36	40	Ext. FET	4mm x 5mm DFN-16, TSSOP-16E

*Actual output current will depend on V_{IN} , V_{OUT} and topology.

Info & Free Samples

www.linear.com/LEDdrivers

1-800-4-LINEAR



Free Power
Management for
LEDs Brochure

www.linear.com/ledsolutions

LT, LTC and LT are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.



ers cross clock domains to compute empty and full flags. You Gray-encode the binary counters, transfer to the other domain, and then convert the counters back to binary before using them. Occasionally, designers access pointers in a FIFO block to do empty/almost-empty or full/almost-full flag calculations. This practice may create CDCs, convergences, or both that a designer may overlook. Adopting standard practices prevents the introduction of CDC bugs into the design.

Gray-encoding circuitry seems simple; however, errors can easily slip into a design. You must Gray-encode and register the signals before crossing clock domains. Sending Gray-encoded signals directly to the destination domain defies the purpose. Furthermore, any glitch in the Gray encoder may cause a functional failure in the design (**Figure 4**).

Another subtle issue is mismatch between Gray-encoding assumptions and the binary-counter range. Designs sometimes fail when a designer expects a Gray counter targeting the full range of a 4-bit counter to count to lower counts and loop back to zero. For example, a designer can build the write pointer of a six-layer-deep FIFO to count from zero to five and loop back to address zero. A Gray encoder targeting counting from zero to seven for a full 3-bit counter will fail when the pointer moves from five to zero (**Figure 5**).

Designing a Gray encoder may give a false sense of security if you fail to account for these details. Both junior and experienced designers may face such issues. There are a large

MORE AT EDN.COM

Go to www.edn.com/ms4271 and click on Feedback Loop to post a comment on this article.

number of corner-case problems in CDC, and it is difficult for any designer to pay attention to all the details, especially when under tight schedule pressure. The best way to catch these issues is to approach them with a systematic methodology that has concise metrics. Static-CDC verification has recently emerged as an accepted approach to achieve this goal. This approach targets metastability, convergence, and other CDC issues that

traditional verification tools, such as simulation and static-timing verification, do not cover. Static-CDC verification successfully targets corner cases that designers may overlook. Furthermore, it provides a systematic-verification approach that can fit into any design flow as part of the verification-sign-off tool suite. **EDN**

AUTHORS' BIOGRAPHIES

Shaker Sarwary is technology director at Atrenta (San Jose, CA). He has a doctorate from Paris University (France), and he has performed postdoctorate work at the University of California—Berkeley. He has held senior engineering positions in the areas of synthesis and verification at Lattice Semiconductor, Get2Chip, and Cadence. You can reach him at shaker@atrenta.com.

Saurabh Verma is an engineering manager at Atrenta. He has a bachelor's degree from Indian Institute of Technology Kanpur. He has rich experience in formal technology and rule-based-design verification. You can reach him at saurabhv@noida.atrenta.com.

ZigBee Technology, Proprietary Mesh and More

**New Single
Chip with
ZigBee 2006**



Cirronet has it all. ZigBee compliant 2.4 GHz, high power **wireless mesh networking module**, combined with a ZigBee compliant **Modbus or Ethernet gateway** allow seamless integration of networked sensors and devices into existing networks. **Developer's Kit** accelerates the integration process. Don't need ZigBee? How about other options for low cost, low power modules including **proprietary mesh with sleeping routers, 802.15.4, 433MHz and 900MHz?**

Each is FCC Certified for unlicensed operation, saving you even more. All from a name you trust ... Cirronet.

Call or visit our web site today!


+1.678.684.2000
www.cirronet.com



CIRRONET

Fuse Clips

For 2AG, 3AG and 5mm fuses

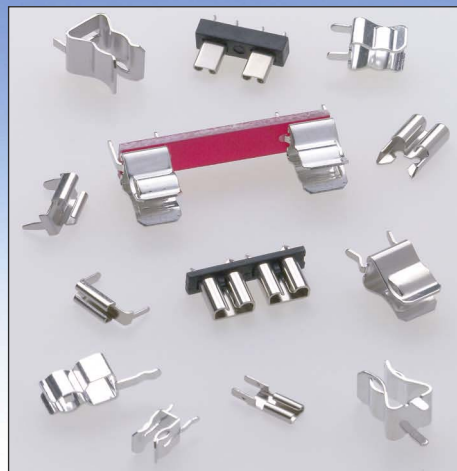

Easy to assemble • Quick ship

For details: write, call, fax or visit our website


MPD

MEMORY PROTECTION DEVICES, INC.

200 BROAD HOLLOW RD., FARMINGDALE, NY 11735
TEL (631) 249-0001 / FAX (631) 249-0002

www.fuseholders.com

36V_{IN} µModule DC/DC Family

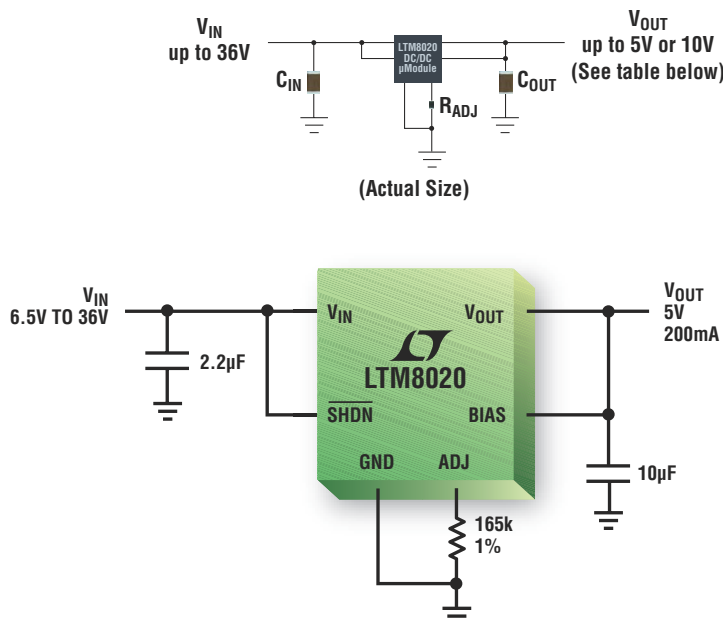

Compact, Low Profile & No Heat Sink

Our new DC/DC µModule™ regulators with up to 36V_{IN}, 200mA to 2A, operate cooler than linear regulators and are simpler than discrete switchmode DC/DC regulators. With onboard inductor, power switches and other circuitry, the LTM®8020, LTM8021, LTM8022 and LTM8023 are complete switchmode DC/DC regulator systems in an IC form factor. Low profile, thermally efficient and compact, they mount on either side of the board, leaving space for digital ICs.

Features

- Onboard inductor, power components, DC/DC regulator, input/output bypass capacitors and compensation circuitry
- Current mode operation for fast short-circuit response, accurate current limiting and precise line and load regulation
- LGA package with gold finished pads allow soldering with Pb and Pb-free solder pastes
- RoHS compliant
- Simple copy-and-paste layout

The New 200mA to 2A DC/DC µModule Family



	LTM8020	LTM8021	LTM8022	LTM8023
V _{IN}	4V to 36V	3V to 36V	3.6V to 36V	3.6V to 36V
V _{OUT}	1.25V to 5V	0.8V to 5V	0.8V to 10V	0.8V to 10V
I _{OUT}	200mA	500mA	1A	2A
Size (mm)	6.25 x 6.25 x 2.3	6.25 x 11.25 x 2.8	11.25 x 9 x 2.8 Pin Compatible	

More Info

www.linear.com/micromodule

1-800-4-LINEAR




Free DC/DC Telecom,
Datacom and
Industrial Brochure

www.linear.com/48vsolutions

L, LTC, LT and LTM are registered trademarks and µModule is a trademark of Linear Technology Corporation. All other trademarks are the property of their respective owners.



Ultra-Tiny 16-Bit ADC

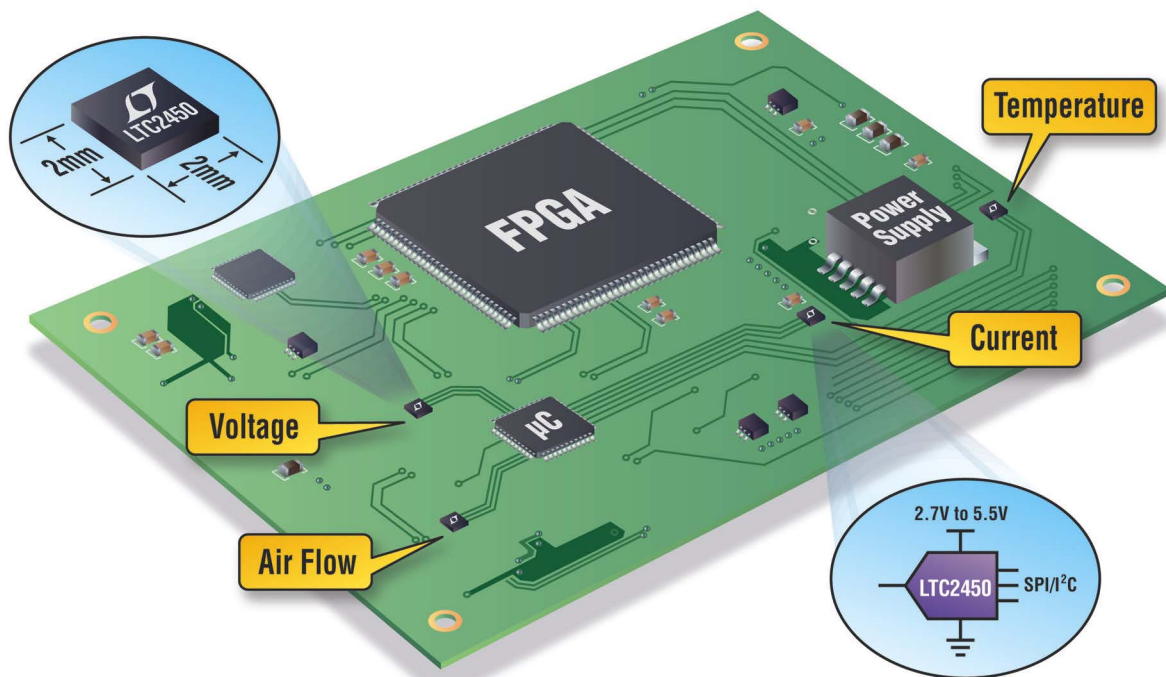


Easy-to-Use ADC Features 16-Bit Performance at a 12-Bit Price

The LTC[®]2450 packs a mighty punch with 16-bits of analog sampling performance and an internal oscillator in just 4mm². The LTC2450 sets a new standard for monitoring system environments in compact, power-conscious applications. Thanks to the flexibility of either I²C or SPI interface, you can measure voltage, current, temperature, airflow or other general purpose analog signals without compromising performance.

▼ Features

- ± 2 LSB INL, 16-Bits No Missing Codes
- Ultra-Tiny 6-Lead, 2mm x 2mm DFN Package
- Low Power: 350 μ A I_Q at 60 Conversions Per Second, 0.5 μ A Sleep Current
- 60Hz (LTC2450-1) & 30Hz (LTC2450) Output Rate Versions
- SPI or I²C Versions, Single-Ended or Differential Versions
- Internal Oscillator – No External Components Required

16-Bit Integral Nonlinearity Error

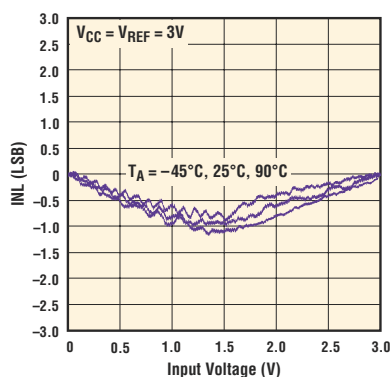

▼ Info & Free Samples

www.linear.com/2450

1-800-4-LINEAR



Free Industrial Signal Chain Brochure

www.linear.com/indsolutions

LT, LTC and LT are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.





DESIGN NOTES

µModule Buck-Boost Regulators Offer a Simple and Efficient Solution for Wide Input and Output Voltage Range Applications

Design Note 438

Jian Yin and Eddie Beville

Introduction

An increasing number of applications require DC/DC converters that produce an output that falls somewhere within the input voltage range. The problem is that conventional buck-boost converter topologies, such as SEPIC or boost followed by buck, are complex, inefficient and consume a relatively large board area. Linear Technology offers 4-switch-topology buck-boost regulators that significantly improve efficiency and save space, but a complete regulator design still requires a number of external components and meticulous board layout decisions related to electrical and thermal considerations. The next clear step to simplify the design is a modular approach—a buck-boost regulator system in an IC form factor. The LTM4605 and LTM4607 µModule™ buck-boost regulators take that approach. Each requires only one external inductor and a single sensing resistor to produce a compact, high performance, high efficiency buck-boost regulator with exceptional thermal performance.

High Efficiency

The LTM4605 and LTM4607 are high efficiency switch mode buck-boost power supply modules. The LTM4605 can operate over an input voltage range of 4.5V to 20V and support any output voltage within the range of 0.8V to 16V, set by a single resistor. As shown in Figure 1, the LTM4607 supports 4.5V to 36V inputs and outputs of 0.8V to 16V. Both can provide 92% to 98% efficiency over the wide input range. This high efficiency design delivers up to 5A continuous current in boost mode (12A in buck mode). Only the inductor, sensing resistor, and bulk input and output capacitors are needed to finish the design. Figure 2 shows a typical LTM4605 application with an output of 12V at 5A. An optional RC snubber is added here to reduce switching noise for applications where radiated EMI noise is a concern.

Low Profile Solution

These power modules are offered in a space saving and thermally enhanced 15mm × 15mm × 2.8mm LGA package. This low profile package can fit the back side of PC boards for many high density point-of-load applications. Their high switching frequency and current mode architecture enable a fast transient response to line and load changes without sacrificing stability. Both can be frequency synchronized with an external clock to reduce undesirable frequency harmonics. Fault protection comes in the form of overvoltage protection and foldback current protection.

Smooth Transition and Circuit Simplicity

Both the LTM4605 and LTM4607 include the switching controller, four power FETs, compensation circuitry and support components. The 4-switch topology provides high efficiency in all three modes of operation—buck, buck-boost and boost—with a smooth transition between each.

LT, LT, LTC and LTM are registered trademarks and µModule is a trademark of Linear Technology Corporation. All other trademarks are the property of their respective owners.

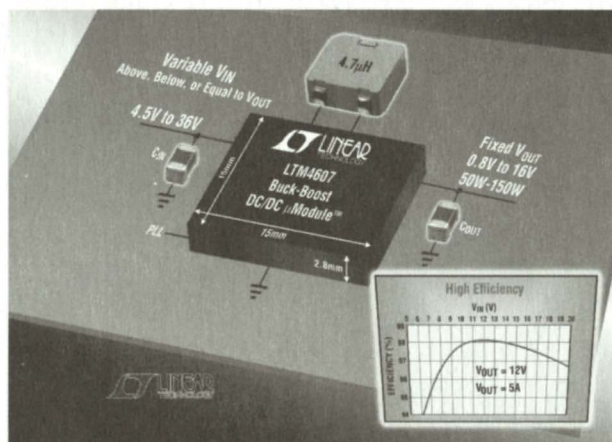


Figure 1. There is No Easier Way to Design a High Efficiency, High Power Density Buck-Boost Regulator than with the LTM4605 or LTM4607

Figure 2 shows an actual buck-boost design with external components chosen to satisfy the boost mode's 5A maximum load current. For buck-only applications, the maximum load current can be 12A at 12V_{OUT} with the same external components. For instance in a buck-only configuration, such as in Figure 3, the load current can be increased up to 7A at 12V_{OUT} for 168W capability. This application can achieve better than 98% efficiency as shown in Figure 4.

Excellent Thermal Performance

The low profile LGA package has a low thermal resistance from junction to pin (4°C/W), thus maintaining an acceptable junction temperature even when satisfying high power requirements. Typically, operation in room temperature ambient conditions requires no special heat sinking or added airflow, but for warmer ambient environments or

high loads, simply add a heat sink to the top of the case for 2-sided cooling and add air flow to significantly lower the thermal resistance from junction to ambient. The data sheet provides more details about adding heat sinks and air flow considerations.

Conclusion

There is no easier way to design an efficient high-density buck-boost converter than with the LTM4605 or LTM4607 μ Module regulator. No design tricks are necessary to achieve efficiencies up to 98%—only one inductor, a single sensing resistor and bulk capacitance are required to complete a design. Low profile LGA packages fit on the back side of PCBs and have good thermal performance, enabling a 168W power output in an 8cm \times 8.4cm 4-layer PCB. These devices are ideal for automotive, telecom, medical, motor drive and battery-powered applications.

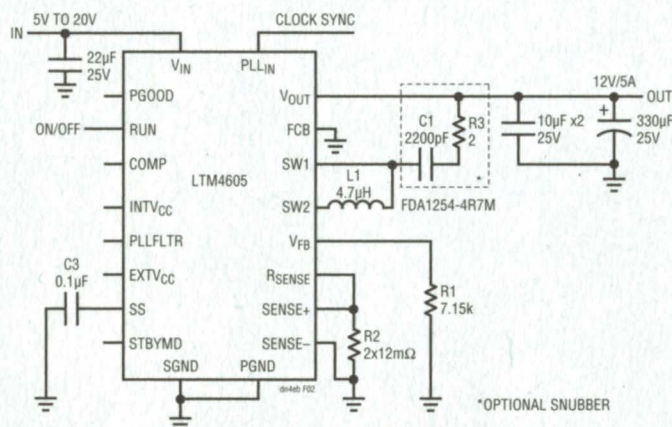


Figure 2. Buck-Boost Converter Produces 12V_{OUT} at 5A from a 5V to 20V Input Range

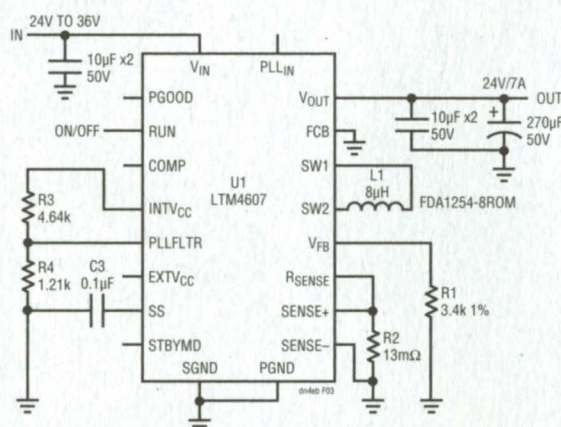


Figure 3. Buck Converter Produces a 24V Output with 168W Capability

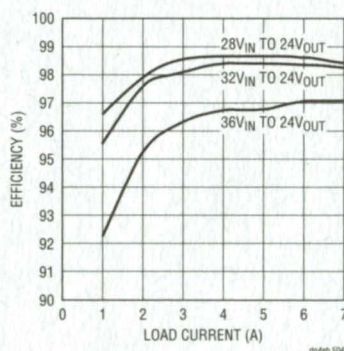


Figure 4. Efficiency for the 24V_{OUT} Converter in Figure 3

Data Sheet Download

www.linear.com/micromodule

For applications help,
call (408) 432-1900, Ext. 2593

Chop the noise gain to measure an op amp's real-time offset voltage

Glen Brisebois, Linear Technology, San Jose, CA

One of the most important specifications of an op amp is its input-offset voltage. You can null out this voltage on many op amps, but the problem with determining the input-offset voltage is that the offset voltage varies with temperature, flicker noise, and long-term drift. Chopping and autozeroing techniques have been around for several years, reducing achievable input offset to microvolts or less. The accuracy is so good that other minuscule effects, such as copper-solder thermocouple junctions, dominate the errors, until, with some effort, you can overcome them, as well. This Design Idea introduces a new type of chopping. "Chopping the noise gain" is a simple way to measure the offset voltage in real time, so that you can subtract it and enhance dc precision.

Figure 1 shows an LTC6240HV op

amp in an inverting gain-of-10 configuration, along with several of its pertinent specifications. All of the input offset arrives at the output with a gain of 11 (called the "noise gain") as an output error. Any downstream circuitry or observer looking at the output voltage cannot distinguish the output error from the desired output signal.

Figure 2 shows the chop-the-noise-gain method. S_1 switches the additional shunt resistor, R_3 , in and out, changing the noise gain without affecting the signal gain or bandwidth. There would normally be some degradation of bandwidth, but C_1 dominates the bandwidth limitation whether the switch is open or closed. Now, you impose a small square wave on the output with an amplitude that is equal to the present dc errors. You can demodulate out the error as with a conventional chop-

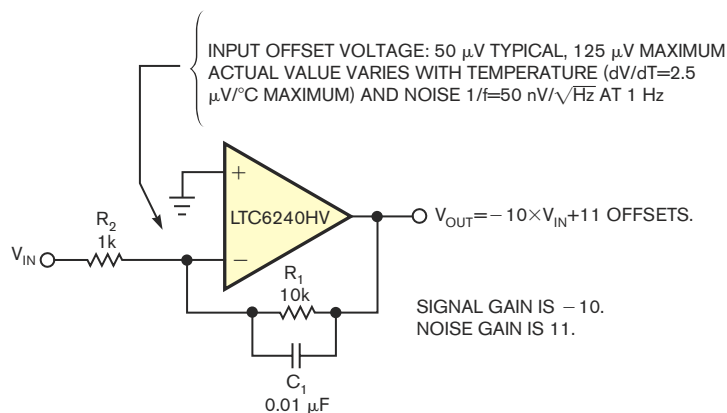


Figure 1 An op amp has a conventional gain of -10 . The noise gain is 11, so all of the input errors appear at the output with a gain of 11. You cannot distinguish the signal from noise just by looking at the output.

DIs Inside

66 Simple analog circuit provides voltage clipping and dc shifting for flash ADC

68 Compact laser-diode driver provides protection for precision-instrument use

70 Current source makes novel Class A buffer

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

per, or you can subtract it in software in a modern ADC-based system.

The circuit in Figure 2 is much like a simple summing amplifier, with one input both connected and disconnected. It is, in that sense, much like a true chopper amplifier. But, in this case, the input voltage being chopped is the amplifier offset, rather than the input signal. Why disconnect your input signal if you don't have to? Also, there is no need for continuous chopping; you need apply it only when you require an offset measurement.

Note that, although this Design Idea shows the inverting case for ease of understanding, the noninverting case is also practicable with a good analog switch for S_1 . Also, as with any sampled system, frequencies at or greater than the clock rate alias into baseband, and you should therefore filter them out before the chopping. Finally, this method does not correct for bias- or leakage-current-induced errors.

Switch S_1 opens and closes, increasing the noise gain and imposing the input errors onto the output with alternating noise gains of 11 and 22. The

resultant square wave now represents an easily measurable “11 errors,” which you can then subtract from the output. This technique is similar to that of conventional chopper amplifiers, except that, in this case, you are chopping the error rather than the signal.

Figure 3 shows the oscillogram of the output of the circuit of **Figure 2**, with an input voltage of 0V (grounded). The top trace is “S,” the control signal applied to S_1 at 750 Hz. The bottom trace is the output error alternating between 1 and 2 mV, indicating 90 μ V of op-amp offset. The output “sees” the effect of doubling the noise gain of the output offset. The difference between the two noise gains is 11, and this difference dictates the amplitude of the square wave that S_1 causes, independently of the input voltage.

Figure 4 is similar to Figure 3, but zoomed out and with a 2-mV-p-p slow-moving sine wave signal at the input

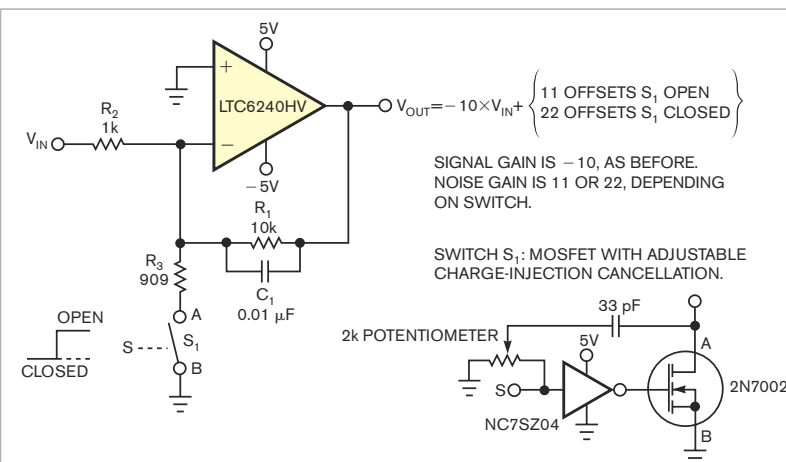


Figure 2 S_1 switches the additional shunt resistor, R_3 , in and out, changing the noise gain without affecting the signal gain or bandwidth.

voltage—that is, 20-mV-p-p output. The 1-mV square wave of **Figure 3** is superimposed upon the slow-moving output signal and still contains the

real-time dc-error information. Just by looking at the output, you can discern that the true value of the signal is 1 mV below the measured value. **EDN**

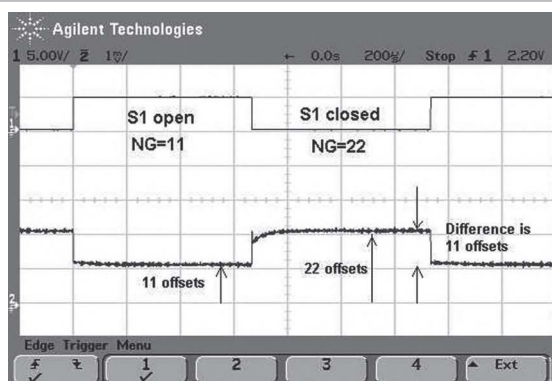


Figure 3 This oscillogram shows the output of the circuit in Figure 2, with an input voltage of 0V (grounded). The top trace is “S,” the control signal applied to S_1 at 750 Hz. The bottom trace is the output error alternating between 1 and 2 mV.

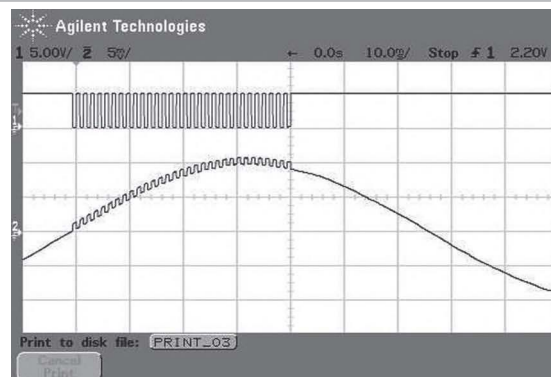



Figure 4 The oscillogram is similar to that in Figure 3, but with a 2-mV-p-p slow-moving sine wave signal applied at the input voltage.

Simple analog circuit provides voltage clipping and dc shifting for flash ADC

Alfredo del Rio, University of Vigo, Spain



 Many flash ADCs, such as National Semiconductor's (www.national.com) ADC1175, have a recommended operating input-voltage range of 0.6 to 2.6V (**Reference 1**).


However, in some applications, you must convert a symmetrical analog-input signal. The circuit in this Design Idea converts a symmetrical input-voltage range of -0.2 to $+0.2\text{V}$ into

the recommended 0.6 to 2.6V range (**Figure 1**). The circuit also prevents the output voltage from going below -0.3V , which would probably damage the ADC.


The circuit uses an Analog Devices (www.analog.com) AD8002 dual-current-feedback operational amplifier to obtain a high bandwidth (**Reference 2**). The first block, noninverting am-



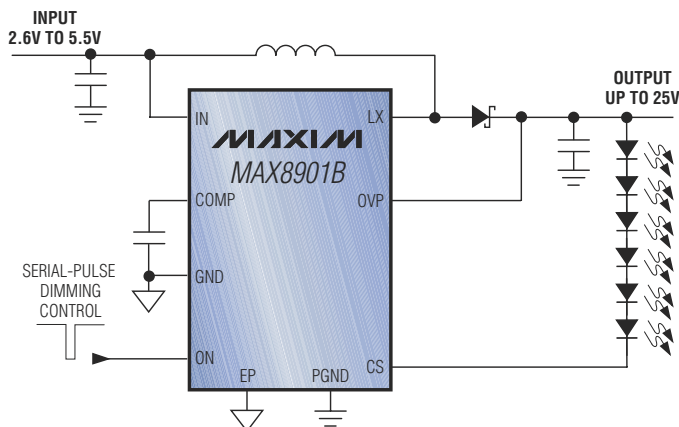Smallest, highest efficiency WLED drivers offer serial or PWM dimming in a tiny, 2mm x 2mm TDFN package



MAX8901B EFFICIENCY vs. DIM STEP

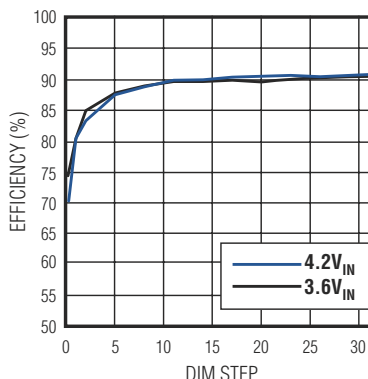

Highest efficiency

- Up to 6 WLEDs with $\pm 1\%$ LED current accuracy
- Flexible dimming control
 - Direct PWM dimming (MAX8901A)
 - 32-step, single-wire serial dimming (MAX8901B)
- 1 μ F input and 0.1 μ F output capacitors
- Input overvoltage lockout (6.3V, max)
- LED overvoltage protection

Longer battery life and smaller size

Specification	Competition	MAX8901A/B
Peak Efficiency (%)	85	> 90
Supply Current (μ A)	800	85
C _{OUT} (μ F)	0.22	0.1
Package (mm x mm)	TDFN (2 x 3)	TDFN (2 x 2)



Smallest footprint



Technical Support

www.maxim-ic.com/support

MAXIM DIRECT

www.maxim-ic.com/shop

AVNET
electronics marketing

www.avnet.com

MAXIM

www.maxim-ic.com/MAX8901-info

Call 1-800-998-8800 for a free sample

Distributed by Maxim Direct and Avnet Electronics Marketing. The Maxim logo is a registered trademark of Maxim Integrated Products, Inc. © 2008 Maxim Integrated Products, Inc. All rights reserved.

plifier IC_{1A} has a voltage gain of five. This block also provides high input impedance and low output impedance, so that the second block, IC_{1B}, operates properly. The second block does most of the work. Starting from a basic inverting amplifier comprising IC_{1B}, R₄, and R₅, you obtain the clipping effect by adding R₃ and D₁. R₃, D₁, R₄, and R₅ determine the clipping level. In addition, adding the I_{DC} current dc-shifts the output voltage. You can trim adjustable potentiometer resistor P₁ to obtain the desired output voltage shift—that is, 1.6V.

If diode D₁'s current is negligible, the output voltage, V_O, is $-(1+R_2/R_1) \times (R_5/(R_3+R_4)) \times V_1 + V_{CC} \times R_5/(R_6+P_1+R_7) = 1.6 - 5 \times V_1$. Given that the diode voltage, V_{DIODE}, is 0.6V_S, $V_O = -(R_5/R_4) \times V_{DIODE} + V_{CC} \times R_5/(R_6+P_1+R_7) = 1.6 - 1.65 = -0.05V$.

The clipping takes place near 0V, protecting the ADC. Raising the clipping level makes the circuit less linear in the nonclipping range. In other words, a design trade-off exists between clipping level and linearity. Resistor R₈ limits the current through the ADC's input pin. Capacitor C₂ is optional; it

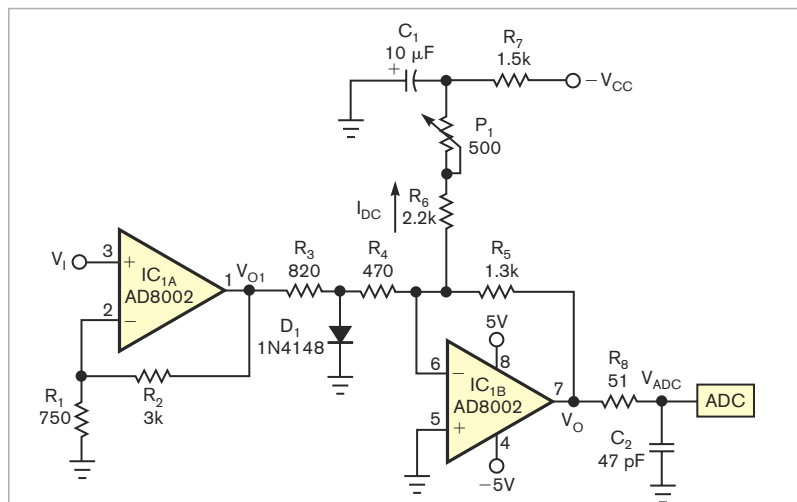


Figure 1 Adding R₃ and D₁ to a conventional op-amp circuit provides clipping. R₃, D₁, R₄, and R₅ determine the clipping level. In addition, adding the I_{DC} current causes dc-shifting of the output voltage.

limits the V_{ADC}/V₁ bandwidth. Capacitor C₁ helps to reduce the voltage noise that might come from the -V_{CC} power supply. **EDN**

REFERENCES

- 1 "ADC1175 - 8-Bit, 20MHz, 60mW A/D Converter," National Semicon-

ductor, www.national.com/mpf/DC/ADC1175.html

- 2 "AD8002 Dual 600 MHz, 50 mW Current Feedback Amplifier," Analog Devices, www.analog.com/en/prod/0%2C2877%2CAD8002%2C00.html.

Compact laser-diode driver provides protection for precision-instrument use

Jiaqi Shen and Xiaoshu Cai,
University of Shanghai for Science & Technology, Shanghai, China

Continuous-wave laser diodes in precision-instrument applications require constant-current sources to drive them. Proper design of such a driver must involve careful tackling of robustness, stability, noise, and other issues and is consequently costly and complicated (Reference 1). Figure 1 shows a compact, cathode-grounded laser-diode driver with protection against ESD (electrostatic-discharge) damage, start-up spikes, overshoot, and possible fluctuation arising from external optical feedback. An op amp, IC₄, with an enable input drives PMOS FET Q₁ and controls the output current. R_S sets the current to the

rated value for a 35-mW HL6738MG laser diode from Opnext (www.opnext.com). To prevent output from Q₁ during start-up, comparator IC_{5A} keeps IC₄ off, and a 10-kΩ pullup resistor keeps Q₁ off by linking Q₁'s gate to the supply of IC₄ until the terminal supply, V_B, reaches the designed value, approximately 6.5V, and opens Q₁ via IC₄.

The key point for protection against ESD damage and overshoot lies in the use of Q₂, a depletion-mode NMOS FET. With power off, Q₂ conducts, shunting any harmful ESD to ground. With power on, comparator IC_{5B} outputs a negative voltage far below the gate-to-source off-state voltage. Hence,

Q₂ is off and has little effect upon the drive current unless the operating voltage at the laser's anode exceeds the maximum rating of 2.8V in the **figure**. In this case, the operating voltage triggers IC_{5B} to output high and thus turns on Q₂, shunting the drive current to ground, as well. The circuit now introduces significant hysteresis to latch off the state of emergency. Considering the low on-resistance of Q₂, this circuit provides better protection than the common method of relying on a paralleled zener diode for overshoot suppression (**Reference 2**).

Despite employing a split supply, this design requires no particular supply sequencing. You must cut off Q₂ only at the beginning of start-up, so it would be better to turn on the -9V external supply before enabling the driver. Despite the availability of substitutes for some ICs in this design, selection



Drive 8Gbps/10Gbps electrical interfaces over 10-meter cables


Optimized for backplanes and active copper-cable assemblies

The MAX3984 cable driver is optimized for 8.25Gbps Fibre Channel and 10.3Gbps Ethernet interconnects up to 10m with 24AWG cables.

Flexibility for FR4, cable applications

- Four selectable preemphasis levels
- Selectable input equalization
- Selectable 1.0V_{p-p} or 1.2V_{p-p} differential output swing

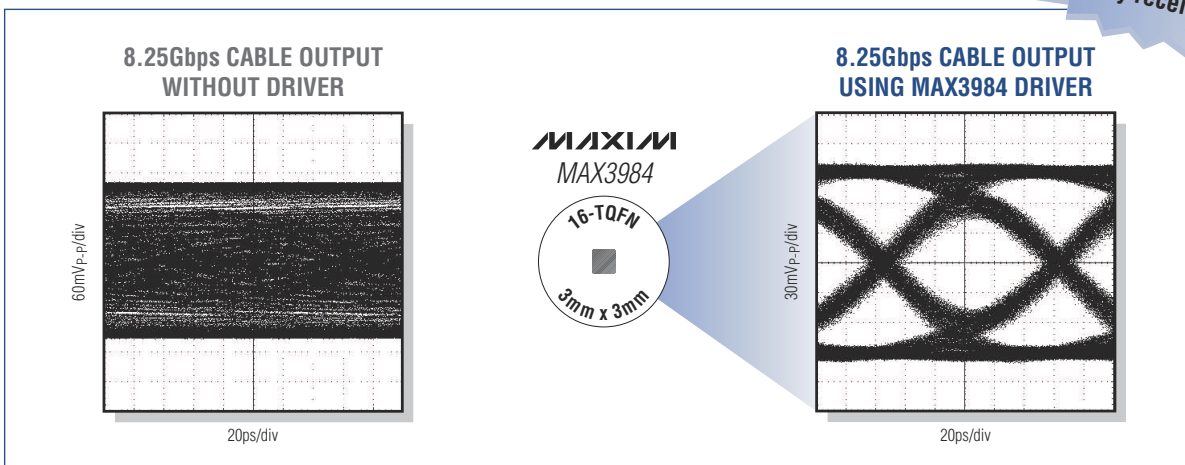Provides plenty of eye opening for any receiver



Free design help for a fully SFP-compliant 8Gbps active copper-cable assembly!

Go to: www.maxim-ic.com/SFPcable

Technical Support
www.maxim-ic.com/support



www.maxim-ic.com/shop



www.avnet.com



www.maxim-ic.com/SFPcable

Call 1-800-998-8800 for a free sample

Distributed by Maxim Direct and Avnet Electronics Marketing. The Maxim logo is a registered trademark of Maxim Integrated Products, Inc. © 2008 Maxim Integrated Products, Inc. All rights reserved.

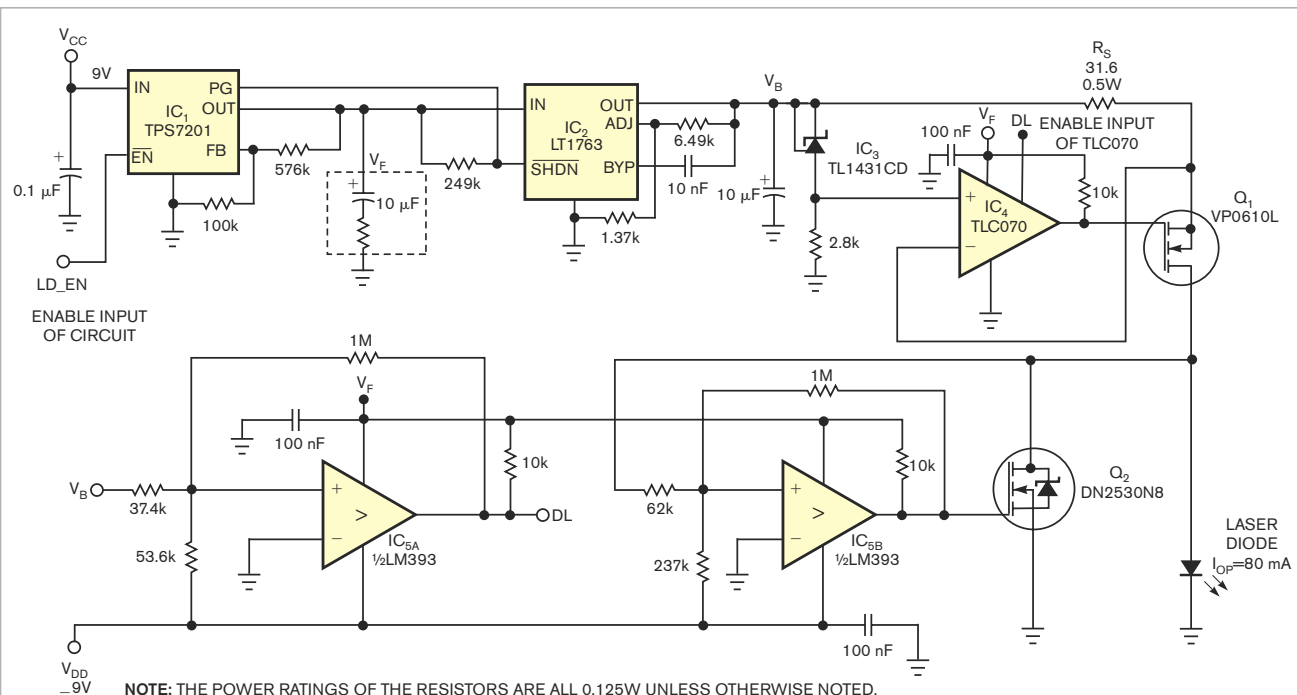


Figure 1 This laser-diode-drive circuit provides a constant current and protection against input overvoltages and start-up transients.

of the proper devices may be troublesome. For example, you can with slight modifications replace the Texas Instruments (www.ti.com) TLC070 with a Linear Technology (www.linear.com) LT1637; the two devices are not pin-compatible. However, the TLC070's superior ac performance, especially higher CMRR (common-mode-rejection ratio) over a wider bandwidth permits more effective protection against

fluctuations in the operating voltage because of external optical feedback under some desired or undesired circumstances (**Reference 3**).**EDN**

REFERENCES

1 Williams Jim, "Current sources for fiber-optic lasers: a compendium of pleasant current events," *EDN*, Aug 22, 2002, pg. 69, www.edn.com/article/CA238417.

2 "DN2530: N-Channel Depletion-Mode Vertical DMOS FETs," Supertex, 2001, www.supertex.com/pdf/datasheets/DN2530.pdf.

3 "TLC070, TLC071, TLC072, TLC073, TLC074, TLC075, TLC07xA: family of wide-bandwidth high-output-drive single supply operational amplifiers," Texas Instruments, September 2006, <http://focus.ti.com/lit/ds/symlink/tlc074.pdf>.

Current source makes novel Class A buffer

Horst Koelzow, Winnipeg, MB, Canada

1 The basis for this Design Idea is a classic two-transistor current source (**Figure 1**). Current through R_1 depends only on the V_{BE} (base-emitter voltage) of Q_2 and on the value of R_1 itself. The V_{BE} of Q_1 has no impact on the output current. Typically, this circuit finds use as a steady current source or as a limiter. The circuit forms the amplifier for the upper,

positive half of the signal. Adding a complementary stage for the lower, negative half of the signal completes the buffer (**Figure 2**). The emitters of Q_2 and Q_3 become the input for the circuit, and the junction of sensing resistors R_1 and R_2 is the output. R_3 is an input-termination resistor that sets the output quiescent voltage. You can replace the bias sources (current



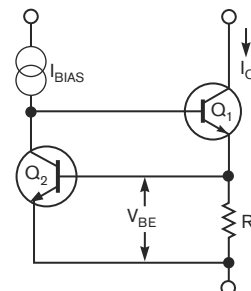


Figure 1 This classic two-transistor current source commonly finds use as a steady source of current or as a limiter.

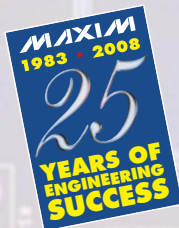


256-tap, SPI or I²C, single or dual, nonvolatile digital potentiometers

The MAX54xx family of digital potentiometers adds **value** to any application by providing 35ppm/°C end-to-end temperature drift and low 1µA (max) supply current. Available in a single or dual resistor configuration, the devices offer a **variety** of resistance values and a choice of I²C or SPI™ interfaces. With such a **versatile** configuration, the MAX54xx devices can be used as voltage-dividers or variable resistors.

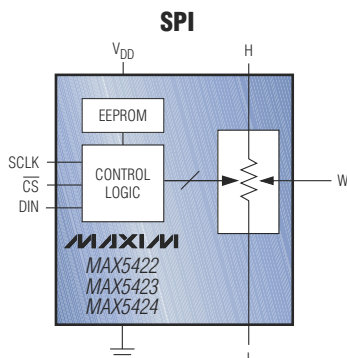


Single

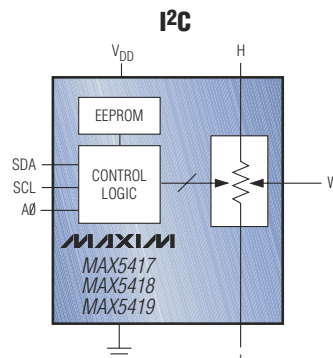- EEPROM stores last position prior to power-down
- Tiny 3mm x 3mm, 8-pin TDFN
- 35ppm/°C end-to-end tempco and 5ppm/°C ratiometric tempco
- Single 2.7V to 5.25V supply
- 1µA (max) standby supply current
- Eight unique I²C addresses per product




I²C

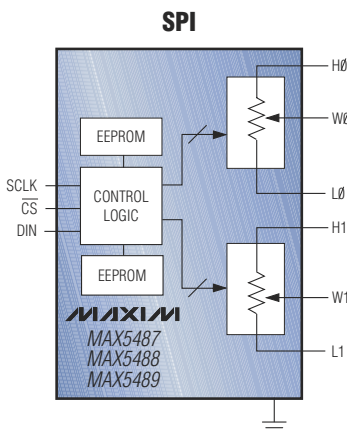

Dual

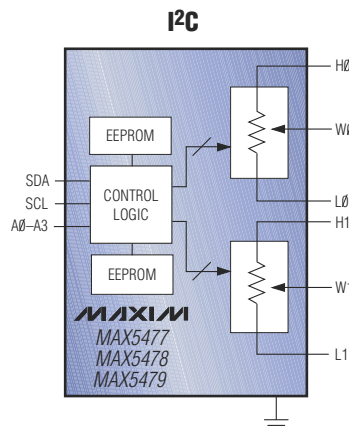- Dual EEPROM stores last position prior to power-down
- Tiny 3mm x 3mm, 16-pin TQFN
- 35ppm/°C end-to-end tempco and 5ppm/°C ratiometric tempco
- Single 2.7V to 5.25V supply
- 1µA (max) standby supply current
- Eight unique I²C addresses per product



I²C

Part	No. of Pots	Interface	End-to-End Resistance (kΩ)	Price† (\$)
MAX5417/MAX5418/MAX5419	1	I ² C	50/100/200	1.25
MAX5422/MAX5423/MAX5424	1	SPI	50/100/200	1.25
MAX5477/MAX5478/MAX5479	2	I ² C	10/50/100	1.60
MAX5487/MAX5488/MAX5489	2	SPI	10/50/100	1.60

**Ideal choices
for contrast
control**

SPI is a trademark of Motorola, Inc.

†1000-up recommended resale. Prices provided are for design guidance and are FOB USA. International prices will differ due to local duties, taxes, and exchange rates. Not all packages are offered in 1k increments, and some may require minimum order quantities.

Technical Support
www.maxim-ic.com/support



www.maxim-ic.com/shop



www.avnet.com

MAXIM
www.maxim-ic.com

Call 1-800-998-8800 for a free sample

Distributed by Maxim Direct and Avnet Electronics Marketing. The Maxim logo is a registered trademark of Maxim Integrated Products, Inc. © 2008 Maxim Integrated Products, Inc. All rights reserved.

sources in the figures) with resistors.

At the quiescent, 0V-input-voltage operating point, both halves of the circuit run at maximum current, and both the input and the output are at the same potential. When you impress a voltage on the input, you inject current into the Q_2 - Q_3 emitter node. From there, current can go up into base of Q_1 or down into base of Q_4 . The output voltage relative to the input voltage determines the direction of the injected current. If the input voltage is positive, it has no effect on the upper half because it is already limiting. It can, however, reduce drive current in the lower half, resulting in a reduction of lower output-drive current. Reduction of lower side output current results in a rise in output voltage. In short, an injected signal current “unlimits” the stage of opposite polarity.

At first glance, the circuit appears to have unity gain. But, because Q_2 and Q_3 sense the tops of R_2 and R_3

AN INJECTED SIGNAL CURRENT “UNLIMITS” THE STAGE OF OPPOSITE POLARITY.

and not circuit output, R_1 and R_2 are effectively in series with the output load. If the load's impedance, R_{LOAD} , is small, the circuit gets significantly loaded down. However, as long as the input stage does not clip, the circuit does not become distorted. The source driving the buffer stage sets $h_{FE}(Q_1) \times (R_1 + R_{LOAD}) \Omega$, where h_{FE} is forward-current gain.

Q_2 and Q_3 are common-base stages. Their purpose is to translate input voltage to the bias voltage that Q_1 and Q_4 require. This voltage-translation action allows direct substitution of other devices, such as MOSFETs or Darlington transistors. **EDN**

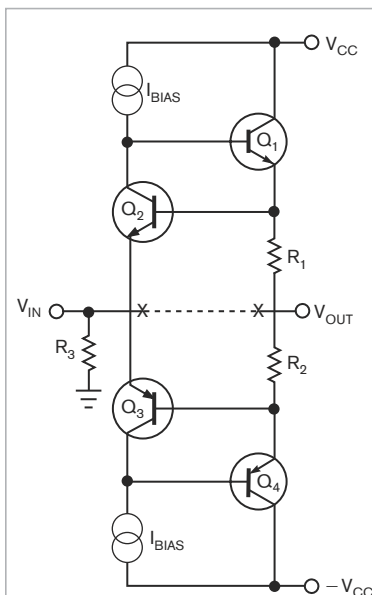


Figure 2 Adding another stage to the current source allows the circuit to function as a buffer.

a leap ahead in automotive

► System Basis Chips

- applications with LIN connection
- features for sensing and actuation

► Magnetic Rotary Encoders


- transmission box applications
- steering wheel positioning

► FlexRay™ Transceivers

- next generation vehicle networks
- reliable and stable bus systems

► Data Acquisition Products

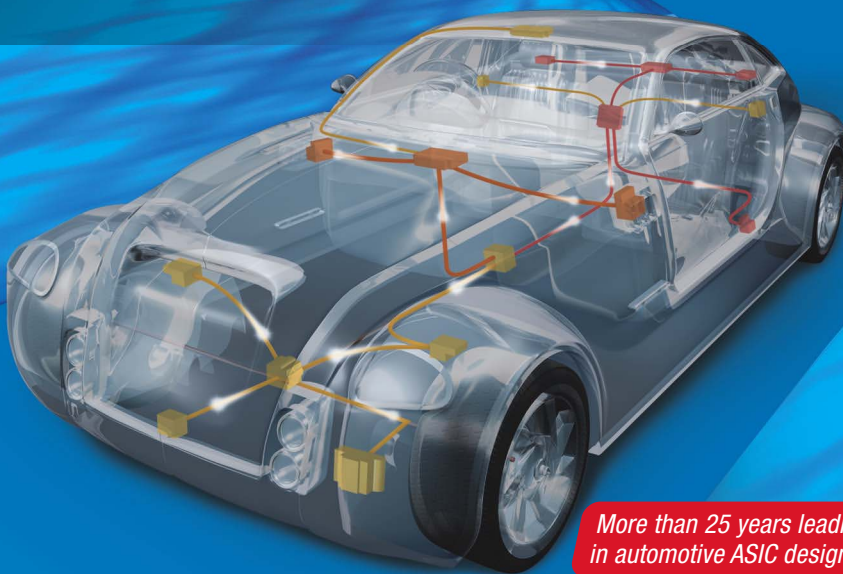- high precision sensing
- battery energy management



More than 25 years leading
in automotive ASIC designs

ae austriamicrosystems


a leap ahead in analog

West Coast (408) 345-1790 · East Coast (919) 676-5292
www.austriamicrosystems.com

PowerWise® 6V to 100V Current-Mode Buck Controller

national.com/power

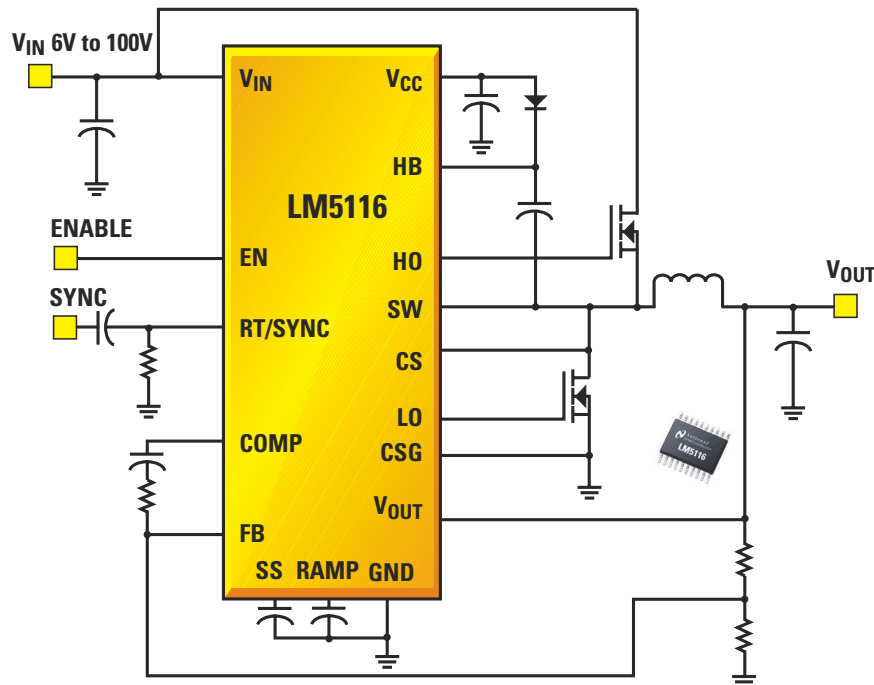LM5116 Synchronous Controller is Energy-Efficient and Features Emulated Current Mode (ECM) Control for High Step-Down Ratio



LM5116 Features

- Ultra-wide input range: 6V to 100V
- Programmable output from 1.215V to 80V
- Less than 10 μA I_Q in sleep mode
- Frequency adjustable to 1 MHz with sync capability
- Programmable soft-start
- Drives standard or logic-level MOSFETs
- $R_{DS(ON)}$ or resistor current sensing
- Controlled start-up into pre-biased load
- Available in thermally enhanced TSSOP-20 packaging

Applications


Telecommunications, automotive, and industrial control

For samples, datasheets, and more information about PowerWise products, visit:

national.com/power

Or call: 1-800-272-9959

Typical Circuit Efficiency

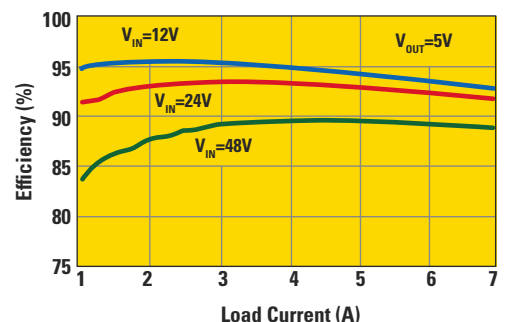

 **National**
Semiconductor
The Sight & Sound of Information

supplychain

LINKING DESIGN AND RESOURCES

Apple sneezes, flash industry gets sick

Demand cuts for NAND-flash memory from Apple Inc (www.apple.com) have driven down total NAND-market estimates for 2008. Reports from iSuppli Corp's (www.isuppli.com) industry sources indicate that the consumer-electronics maker significantly slashed its 2008 NAND-flash orders and has informed suppliers that its demand growth in 2008 will be slower than that of 2007. As a result, iSuppli reduced its outlook for 2008 global NAND-flash revenue growth to the single-digit-percentage range.

Before Apple's warning, iSuppli had predicted the company's NAND-flash purchases would rise by 32.2% this year, helping drive significant market growth. As proof of Apple's considerable impact on the NAND mar-



ket, iSuppli points out that the company was the world's third-largest OEM buyer of NAND-flash memory in 2007, with purchases of \$1.2 billion—13.1% of the global market.

The current economic situation, bearing the influence of the credit crunch and mortgage crisis, has weakened consumer spending. Sales to consumers drive NAND, which finds wide use in consumer-electronics applications, including flash-storage cards, MP3 players, and USB-flash drives.

The research company notes that slower NAND de-

mand will have a major impact on suppliers' financial results. Indeed, capital spending on NAND production should increase by more than 20% this year. Such an increase would guarantee supply of parts and encourage average selling prices to decrease. iSuppli believes that NAND prices now are below suppliers' fully loaded costs.

"In light of these factors, NAND suppliers are likely to go into the red in the first quarter and are not likely to recover in the second," says Nam Hyung Kim (**photo**), director and chief analyst for memory at iSuppli. As 2008 shapes up to be a poor year for NAND, suppliers are likely to look back with nostalgia at 2007, when NAND revenue grew by 12.5% to reach \$13.9 billion, iSuppli says.

SUNNIER PROSPECTS FOR POLYSILICON

OUTLOOK

Frost & Sullivan (www.frost.com) expects the severe shortages and allocations of polysilicon, a key component of most solar panels, to turn around in 2008. The market-research company believes that polysilicon supply should catch up with the demand, offering sunnier prospects for the solar-energy industry. The majority of the new polysilicon quantities will come from four top suppliers that are expanding their production capacities. The big four—Hemlock Semiconductor, Renewable Energy Corp, Wacker, and Tokuyama—should add more than 17,000 tons of capacity in 2008, representing more than a 50% increase over their current capacities.

Frost expects demand from the semiconductor industry to grow at steady single-digit rates and demand for solar-grade polysilicon to reach more than 50% of the total demand for high-purity silicon in 2008/2009. Frost also reports that, in 2005, the global solar-photovoltaic market saw earned revenues of \$6.49 billion. The company expects that figure to reach more than \$16 billion in 2012, basing that prediction on a "huge demand" for polysilicon.

GREEN UPDATE

EPA RELEASES ENERGY STAR GUIDELINES FOR SERVERS

The US EPA (Environmental Protection Agency, www.epa.gov) has released the first draft of its voluntary Energy Star (www.energystar.gov) power-efficiency specifications for computer servers. In doing so, the government agency has established its definitions of eligible server-product categories and laid the groundwork for later establishment of power-supply efficiency, power- and temperature-measurement, and power-management and -virtualization requirements that server manufacturers must meet to qualify their products as Energy Star-rated.

Load points of 10, 20, 50, and 100% are among the few technical points the draft establishes. The draft has so far declared a power factor only for the 100% load, at which the power factor will be 0.9. Although the EPA con-

siders this power factor reasonable, the agency is reviewing whether the level will prove more challenging at lower loading points and will determine over the next few months whether the 10, 20, and 50% loads will need separate power-factor requirements.

The EPA is following its standard "tier" stepping process and will first introduce a Tier 1 set of Energy Star power efficiencies for servers and later increase requirements. The agency plans to work with industry groups over the next several months to test server supplies and create a real-world data set to develop consistent test procedures and efficiency levels. You can find the draft at www.energystar.gov/index.cfm?c=new_specs.enterprise_servers.

Support Across The Board.TM

From Design to DeliveryTM

Now, you can have it all.TM

Faster and easier than ever before. Our commitment to customer service is backed by an extensive product offering combined with our supply chain and design chain services – which can swiftly be tailored to meet your exact needs. We have dedicated employees who have the experience to provide the highest level of customer service with accuracy and efficiency. All of our technical experts are factory certified on the latest technologies, providing you the expertise to move projects forward with speed and confidence.

Avnet offers the best of both worlds: extensive product and supply chain knowledge, and specialized technical skill which translates into faster time to market – and the peace of mind that comes from working with the industry's best. **Avnet is ranked Best-In-Class* for well-informed sales reps and knowledgeable applications engineers. Proof that we consistently deliver:**

- > Industry-recognized Product Expertise
- > Specialized Technical Skills

Ready. Set. Go to Market.TM

Visit the Avnet Design Resource CenterTM at:
www.em.avnet.com/drc



Avnet is a proud sponsor of the Innovation Awards.



Accelerating Your SuccessTM

1 800 332 8638
www.em.avnet.com



*As rated by Hearst Electronics Group, 2006 The Supplier Interface Study.
©Avnet, Inc. 2008. All rights reserved. AVNET is a registered trademark of Avnet, Inc.

productroundup

DISCRETE SEMICONDUCTORS



MOSBD devices integrate MOSFET, Schottky diodes

➡ The TPCA8A02-H and TPCA8A03-H MOSBD (MOSFET/Schottky-barrier-diode) devices eliminate external wiring between the MOSFET and the diodes for increased power efficiency and reduce wiring resistance and inductance. The TPCA8A02-H features a 30V drain-to-source voltage with a maximum 34A drain current, and a 4.8-m Ω on-resistance; the TPCA8A03-H provides a 30V drain-source voltage with a maximum 15A maximum drain current, and a typical 5.1-m Ω on-resistance. The TPCA8A02-H comes in a 5 \times 6 \times 0.95-mm SOP, and the TPCA8A03-H comes in a 5 \times 6 \times 1.6-mm SOP-8. The TPCA8A02-H and TPCA8A03-H cost 55 and 50 cents, respectively.

Toshiba America Electronic Components, www.toshiba.com/taec

MOSFETs tout high efficiency

➡ Suited for dc/dc converters, the STD60N3LH5 and STD85N3LH5 StripFET V Power MOSFET devices claim a superior performance and efficiency due to low on-resistance and lower total gate charge. The 30V devices offer an 8.8-nC gate charge, 7.2-m Ω on-resistance at 10V, and a figure of merit equal to on-resistance times gate charge. The STD85N3LH5 features a 4.2-m Ω on-resistance at 10V, and a 14-nC gate charge. Aiming at notebook-

computer, server, telecom, and networking applications, the STD60N3LH5 and STD85N3LH5 cost 65 cents and 95 cents (2500), respectively.

STMicroelectronics, www.st.com



SOT883 MOSFETs take up 14% of PCB space

➡ Taking up 14% of the PCB (printed-circuit-board) space, the SOT883-packaged MOSFETs claim a comparable power dissipation and performance to that of SOT23-packaged devices. Available in a 1 \times 0.6 \times 0.5-mm footprint, the MOSFET provides 0.65 Ω on-resistance at 2.5V. The series features switching speeds of 12- to 16-nsec turn-on and 17- to 24-nsec turn-off. Prices for the PMZ760SN, PMZ390UN, PMZ250UN, PMZ270XN, and PMZ350XN start at 20 cents (10,000).

NXP Semiconductors, www.nxp.com

600V IGBTs reduce power dissipation

➡ Targeting devices having 20-kHz switching and low short-circuit requirements, the 600V IRGB4059 IGBT (insulated-gate-bipolar-transistor) family reduces power dissipation by as much as 30%, according to the vendor. This reduction allows high-efficiency power conversion in UPS (uninterruptible-power-supply) and solar-inverter applications. With ultrafast soft-recovery diodes, the family provides lower collector-to-emitter saturation voltage and total switching energies than punch-through and non-punch-through IGBTs. The device also features internal ultrafast soft-recovery diodes improving efficiency and reducing EMI. The IRGB4059 IGBTs cost 68 cents.

International Rectifier, www.irf.com


Power MOSFET has low on-resistance

➡ An advanced architecture and package design allow the NP180-

N04TUG power MOSFET to offer a 1.5-m Ω maximum on-resistance. Rated for single- and repetitive-avalanche energy, the power MOSFET operates at 175°C at a 10V gate voltage and a 40V drain-to-source voltage at a drain current of 180A. Available in ROHS (restriction-of-hazardous-substances)-compliant packages, the NP180N04TUG power MOSFET costs \$2.50 (800).

NEC Electronics America, www.am.necel.com

900V superjunction MOSFET has low on-resistance

 The 900V superjunction CoolMOS power MOSFET family suits SMPS (switched-mode-power-supply), industrial, and renewable-energy applications. The devices provide a figure of merit—multiplying the on-state resistance by the gate charge—of 34V nC, resulting in low conduction, driving, and switching losses and in-




creased efficiency. The devices have 120-, 340-, or 1200-m Ω on-resistance and come in TO-246, TO-220, and DPAK packages, respectively; 500-, 800-, and 1000-m Ω devices are available. The 120-m Ω TO-247 package costs \$3.50.

Infineon Technologies, www.infineon.com


INTEGRATED CIRCUITS

High-definition-digital-TV platform has worldwide-standard support

 Based on the vendor's STi1010 single-chip IDTV (integrated-digital-television) processor, the DTV50 single-chip, high-definition decoder-and-processor platform supports worldwide standards. The platform features demodulation, MPEG-2 high-definition- and standard-definition-decoding, high-definition-video-processing, high-quality-audio, and video-switching functions for IDTV sets worldwide. Using STi101X processors, the STi1010 provides high-definition-display capabilities with a picture-in-picture feature, and the STi1011 suits the WXGA (wide-extended-graphics-array) version with no picture-in-picture feature. Available in a 27×27-mm PBGA package, the DTV150 platform with a high-definition configuration costs \$45.

STMicroelectronics, www.st.com


Video decoder has 3-D NTSC/PAL comb filter

 Combining a 12-bit 3-D comb filter with 1080p-high-definition and 150M-sample/sec sampling rate, the ADV7802 video decoder provides 4:4:4 sampling throughout the processing pipeline, including support for RGB SCART (Syn-

d'Appareils Radio et Télévision) inputs. An on-chip interface with SDR (single-data-rate) DRAM reduces system cost, and DDR (double-data-rate) DRAM support enables simultaneous 12-bit NTSC/PAL (National Television System Committee/phase-alternation-line) 3-D comb, DNR (digital-noise reduction), and TBC (timebase correction). Available in a TQFP-176 package, the ADV7802 video decoder costs \$12; the ADV7800 10-bit version costs \$10.

Analog Devices, www.analog.com


Triple-core processor has an audio engine and a security processor

 Aiming at 1024-bit and greater encryption techniques, the DM870 ARM9-based triple-core processor provides a dedicated audio engine, a real-time tamper-resistant security processor, and integrated wireless-Internet support. The 240-MHz ARM926EJ processor core supports Linux, MP3, WMA, AAC, and other audio-decompression standards and offers generous additional processing bandwidth for system control and advanced user-interface operations. Targeting use in complex-audio processing, the audio engine supports real-time MP3 encoding and WMA (Windows-media-audio) lossless decoding. Additional features include support for popular sound-enhance-

ment algorithms; 600-MIPS computational power; and on-chip Ethernet-, wireless-Internet-, and USB-interface connectivity options. The processor integrates 802.11a/b/g MAC (media-access control), an internal color-LCD controller, and onboard stereo-PWM (pulse-width-modulation) outputs. Measuring 17×17-mm in an mBGA-292 package, the DM870 processor costs \$14 (1000) bundled with the JukeBlox SDK (software-development kit). The JukeBlox development platform includes a hardware-reference platform and an SDK and costs \$10,000.

BridgCo, www.bridgco.com

Automotive-contact monitors maintain eight remote switches

 The MAX13037/MAX13038 automotive-contact monitors and level shifters provide an integrated voltage regulator, a watchdog timer, and reset functions. The devices monitor and debounce eight remote mechanical switches and consume 28- μ A typical supply current using programmable polling periods and a programmable scanning period. Aiming at harsh automotive environments, such as body-controller applications, the devices feature a \pm 45V input-voltage range, \pm 8-kV ESD protection on switch inputs, adjustable wetting current, and low dropout. An open-

INTEGRATED CIRCUITS

drain interrupt output is active in the absence of a logic supply and can wake up external microcontrollers from a sleep state. An SPI (serial-peripheral interface) reads the switch status and configures the operating characteristics of each device, and the switch inputs provide programmable wetting current and switching hysteresis. Four inputs allow ground-connected switches, and the other four inputs are programmable in groups of two as battery- or ground-connected switches. The microcontroller-interface pins are configurable to direct-level-shifting outputs for interfacing with PWM (pulse-width-modulation), low-voltage, or other timing signals. Operating over 6 to 26V battery voltage and withstanding a 42V load dump, the contact has a 2.7 to 5.5V logic-supply input that sets the interface voltage. The device has a -40 to +125°C automotive-temperature range. The MAX13037 features a 5V low-dropout regulator, and the MAX13038 has a 3.3V low-dropout regulator; both low-dropout devices provide 150 mA. Available in a 6×6-mm, ROHS (restriction-of-hazardous-substances) TQFN package, the MAX13037/MAX13038 automotive-contact monitor and level shifter cost \$2.16 (1000) each.

Maxim Integrated Products, www.maxim-ic.com

2V-rms audio-line driver operates from 3.3V power supply

Operating from a 3.3V power supply, the DRV601 2V-rms DirectPath audio-line driver adjusts input-gain levels. The device integrates a charge pump and has a 1.8 to 4.5V power-supply range and independent right- and left-channel-shutdown control. The device also includes short-circuit and thermal protection, pop-reduction circuitry, and a 105-dB dynamic range. Available in a 4×4-mm QFN package, the DRV601 audio-line driver costs 90 cents (100).

Texas Instruments, www.ti.com

Audio-DSP kit uses Symphony Studio software

The Symphony Studio software and the Symphony SoundBite audio-DSP kit allow developing, debugging, and simulating applications using an IDE (integrated-development environment). Using the open-source Eclipse platform, Symphony Studio software works with the vendor's audio DSPs, including the multicore DSP5672x devices. The kit suits cost-sensitive applications, independent-design houses,

small development shops, and college laboratories. Shipping with the vendor's Symphony DSPB56371 DSP on a form-factor PCB (printed-circuit board) with a 256-kbyte serial EEPROM, the device also includes a mini-USB interface and DIP switches for user inputs. The kit also includes an evaluation board, a mini-USB cable, and a CD-ROM with software and start-up documentation. Available for downloading from the vendor's Web site, the Symphony SoundBite development kit costs \$150.

Freescale Semiconductor, www.freescale.com

QVGA modules have RO8803 controller

The 5.7-in. monochrome STN (supertwisted-nematic) and FSTN (film-compensated-STN) QVGA modules come in FSTN gray, positive, and transmissive or STN blue, negative, and transmissive configurations. The devices are available with an RO8803 controller with built-in touchscreen controller with CCFL (cold-cathode-fluorescent-lamp) or LED backlighting. The STN negative blue-mode module CCFL backlight costs \$42.50 (1000) or \$39.87 (5000).

Phoenix Display International, www.phoenixdisplay.com



WHEN RECEIVE SIGNALS ARE WEAK, explore the potential of our MMICs in your next RF application. Highly integrated in smallest packages, they come with ESD protection and low power consumption, ideal for battery-operated handheld devices. What's more, our innovative SiGe technology delivers lower noise, hence increased receive sensitivity than silicon alternatives and performance comparable to more expensive GaAs devices.

For more information: www.infineon.com/rfmmic

Scale 2:1 in mm



Never stop thinking

Company	Page
Agilent Technologies	39
Analog Devices Inc	19
	21
Astrodyne	C-3
Atmel Corp	49
austriamicrosystems AG	72
Avnet Electronics Marketing	75
Bourns Inc	2
Central Semiconductor Corp	23
Cirronet	60
CML Microcircuits (UK) Ltd	58
Digi-Key Corp	1
ERNI Electronics	37
Fairchild Semiconductor	11
Infineon Technologies AG	78
Intersil Corp	16
	27
	54
Keithley Instruments Inc	35
Lecroy Corp	8
Linear Technology Corp	59
	61
	62
	63-64
Littelfuse	C-4
MathWorks Inc	29
Maxim Integrated Products	67
	69
	71
Melexis Inc	30
Mentor Graphics Corp	53
Micrel Semiconductor	33
Microchip Technology Inc	25
National Instruments	38
	45
National Semiconductor	4
	13-14
	73
Pico Electronics	12
	15
	36
Power One Inc	57
Radcom Research	79
Summit Microelectronics	46
Taiwan External Trade Dev	56
Tern	79
Texas Instruments	C-2
	3
	6
	30-A-B
That Corp	58
Trilogy Design	79
Vicor Corp	51

EDN provides this index as an additional service. The publisher assumes no liability for errors or omissions.

EDN

productmart

This advertising is for new and current products.

Modem Ease

Embedded Modems

It's Radicom for reliable, high-performance, simple to implement Serial TTL, RS232, USB, PC/104 and RF wireless modems, competitively priced.



Featured -
RJ-11 TinyModem™
Data/Voice/Fax
0.66" x 1.25" x 0.75"
300 bps to 56k bps

Count on Radicom to reduce time-to-market, lower cost, and improve product quality.

Radicom
Affordable Modem Technology

sales@radi.com | www.radi.com 408-383-9006 x112



NEW!
Ver. 6.0

How to keep track of it all?

Easily create and manage multi-level parts lists and specs, calculate costs, generate shopping and kit lists, print labels, generate RFQs and POs and much more...

Parts & Vendors Parts List Manager and Vendor Database

Get the full function DEMO at
www.trilogydesign.com

Trilogy Design / 200 Litton Dr. #330
Grass Valley, CA 95945 / 530-273-1985

ADVERTISE IN

EDN

productmart

For more information
on how to place
your ad
in this section
please contact:

ROSE MURPHY

T: 781-734-8457

E-mail: MurphyS@Reedbusiness.com

FlashCore-B (FB)™

Add embedded mass data storage,
16-bit ADCs to your product



\$79 Qty 1 \$34 OEM

- 2.1" x 2.4", C/C++ programmable.
- CompactFlash interface with FAT file system.
- 16-bit ADCs, DACs, RS232 and TTL I/Os.
- Ultra-low quiescent current for battery power.

50+ Low Cost Controllers with ADC, DAC, 18 UARTs, 300 I/Os, solenoid, relays, CompactFlash, LCD, DSP motion control. Custom board design. Save time and money.

Tern
INC.

1724 Picasso Ave., Suite A
Davis, CA 95616 USA
Tel: 530-758-0180 • Fax: 530-758-0181
www.tern.com
sales@tern.com



Contamination: not your usual suspects



While working in the 1980s for a major semiconductor manufacturer, we had a major yield problem that was baffling the production team. Yields were decreasing on a daily basis because of high leakage failures. The usual suspects in this case are positive ions (so-

dium) or heavy-metal contamination causing leakage in the oxide layers. Sources for these ionic contaminants can range from a

defective dopant bottle to a bag of chips an operator sneaks into the fabrication facility. We applied all the usual approaches to correcting the problem, including changing diffusion sources and cleaning all the glassware, and the yields improved.

We used CV (capacitance-versus-voltage) plots to determine that heavy metal was the source of the decrease in yields and determined that, after cleaning, we had eliminated the source. Unfortunately, only a week later, the problem returned. The CV plots once again confirmed the presence of heavy

metal. The next step was to replace all the large, expensive quartz tubes in the diffusion oven. Wafers sat in these tubes while the oven heated and diffusion gases flowed over the wafers. Replacing these tubes upset the production-team members, but they felt that they had at least cured the contamination problem.

The transistors inside the new quartz tubes were good ones and met all the specifications. Everything was fine for three months. Then the exact same problem developed again. Transistor yields plunged, and it seemed that heavy

metal was again the problem. The team ran many experiments and tried several approaches to determine the source of the contamination. Investigations found that there was gold in the silicon and that it was ruining the electrical properties. When you use gold in high-speed switching transistors, it provides a place for hole-electron pair recombination, speeding transistor switching. For linear transistors, however, the gold just ruins the properties with excessive leakage and poor low-current amplification. But the investigators thought that they had eliminated any and all potential sources of gold contamination.

After some extensive research on what had changed in the fab, they found that the fab had brought in a used diffusion oven from another division. The diffusion oven had come from a line that was making high-speed chips, and that other line had at one point used the oven for gold diffusion. Changing glassware was not permanently solving the problem. If gold could diffuse into the quartz tubes, it could also continue on and contaminate the heating coils. We got a new set of quartz tubes and also changed the heating coils.

Even after three months, the transistors coming out of that furnace were just fine. It turns out that, in the old factory, the gold had continued to diffuse into the quartz. When the gold atoms reached the outside of the quartz tube, they deposited themselves on the nichrome heating coils. It had taken three months for the gold to diffuse from the outside to the inside of the tubes; it then began to ruin the wafers inside the tubes. This fact amazed the production people, but anyone who has worked on semiconductor processes knows that you can never just look at the usual suspects. **EDN**

Martin DeLateur is a consultant who spent 30 years as a product engineer at Fairchild and National Semiconductor. Contact him at delateurm@all2ex.net. Like Martin, you can share your Tales from the Cube and receive \$200. Contact edn.editor@reedbusiness.com.

CUSTOMIZE IT. FAST AND FLEXIBLE POWER SUPPLIES



Astrodyne provides the most Rapid Resolution to your custom power supply challenges. Our experienced engineers will help you to create an efficient modified power solution in both small and large quantities. Tailored to your space and performance needs, Astrodyne delivers all this and more... at the right price:

- Modified Output Voltages
- Specialty I/O Connectors

- Cable/Connector Assemblies
- Full Custom Electrical Design
- Mechanical and Packaging Design
- Label and Package Customization

Call today to find your innovative custom power supply solution. We'll listen and deliver the Rapid Resolution you deserve.

astrodyne.com 800.823.8082




Astrodyne

Rapid Resolutions




Varistors

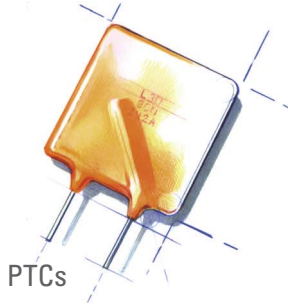

PTCs




GDTs

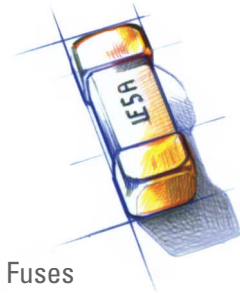


Fuses

CIRCUIT
PROTECTION
COMES
IN MANY
FORMS

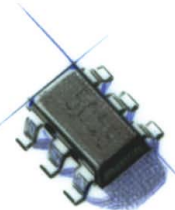


Diodes and Silicon
Protection Arrays

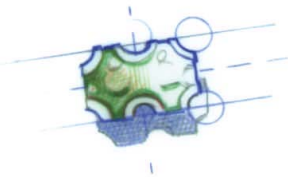

PulseGuard®
ESD Suppressors



Thyristors

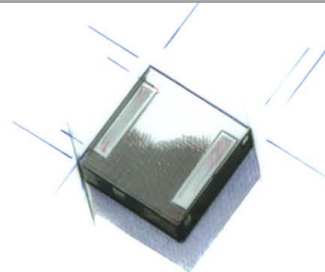

SIDACTor® Devices

AND WE HAVE THEM ALL

**Littelfuse is recognized
around the world as the #1
brand in circuit protection**

With the industry's broadest and deepest portfolio of circuit protection technologies, Littelfuse is the company that engineers trust to answer their most critical circuit protection questions. Whether you need overcurrent or overvoltage products, Littelfuse has the expertise to help you.

Don't take chances when it comes to circuit protection, contact the experts today! Visit www.littelfuse.com for more information.



Expertise Applied | Answers Delivered