

JULY
1963

Practical 2/- **WIRELESS**



ADCOLA

REGISTERED TRADE MARK


SOLDERING INSTRUMENTS

**EQUIPMENT
FOR THE
RADIO AMATEUR**

ILLUSTRATED

List 64.
 $\frac{3}{16}$ DETACHABLE BIT
IN
PROTECTIVE SHIELD
List 700

BRIT. & FOR. PATS.

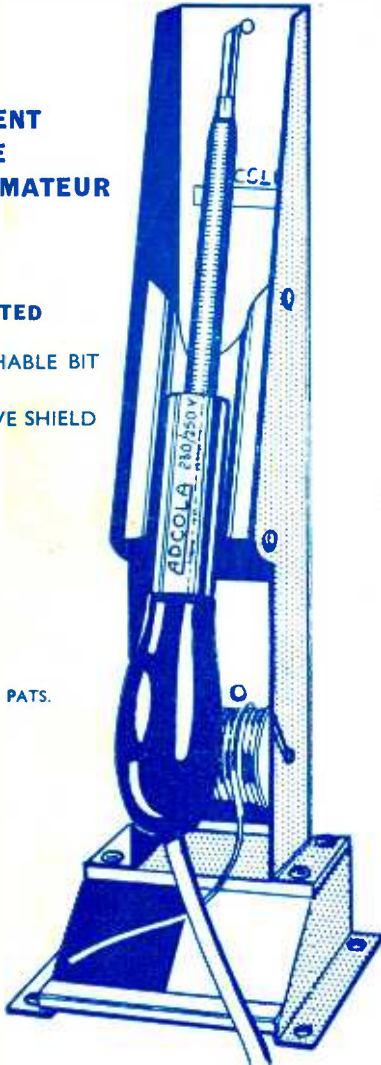

Sales & Service
APPLY DIRECT FOR CATALOGUE
TO

ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD, LONDON, S.W.4

Telephones 774 Cauly 4272 & 3101 Telegrams SOLJOINT LONDON SW4

OSMOR

PRICE LISTS & INFORMATION ON Various Designs in

Practical Wireless	Radio Constructor	Wireless World	R.S.G.B. Bulletin
-----------------------	----------------------	-------------------	----------------------

SEND 6d. POSTAGE FOR




CIRCUITS

OSMOR LTD

418 BRIGHTON ROAD
S. CROYDON SURREY
Telephone CRO 5148

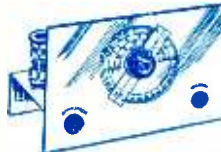LISTEN TO THE WORLD on TELSTAR our 1-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. **Total Building Costs 35/-** P. & P. 2/-.



THE R.C.S. PERSONAL SET For Private Listening

An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 1/2 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. **Total Building Costs (including earpiece) 30/-** P. & P. 2/-.

AMAZING RESULTS from OUR LATEST

5-STAGE TRANSISTOR RECEIVER

A highly sensitive receiver using top grade transistors and components. Fully tunable over medium wave.
★ Can be built in 1 hour. ★ High flux moving coil speaker. ★ Built-in ferrite rod aerial. ★ Specially designed coils for maximum signal strength. ★ Volume on/off control. ★ Eyeletted circuit board. ★ Easy to follow building plans.



Total Building Cost 50/- P. & P. 2/6.

R.C.S. CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components including case. **8/6** P. & P. 1/6.
(Suitable headphones 9/6). Easily converted to 1-transistor or 2-stage transistor receiver.



All parts available separately. Send S.A.E. for free layout plans and parts lists on any of the above sets.

R.C.S. PRODUCTS (RADIO) LTD.
11 OLIVER ROAD, LONDON, E.17
(Mail Order Only)

Tubes

Corr. & Ins. 12/6.

	12in.	14in.	15-17in.	21in.
MOST MULLARD, MAZDA, COSSOR, EMITRON, EMISCOPE, BRIMAR, FERRANTI TYPES.	£2. 0.0	£2.10.0	£3. 5.0	£3.15.0
PROCESSED IN OUR OWN FACTORY	£3. 0.0	£3.10.0	£4. 5.0	£6.0.0

SPECIAL TEMPORARY OFFER
Due to huge Bulk Special Purchase we are offering 6W 31/74 Tubes at the unrepeatable price of 29/-, MW 38/24 ditto, 39/-. P.P. 12/6. The above are guaranteed for 6 months.

P.M. SPEAKERS. 3Ω Top Makes.
6in. 7/6
8in. 7 4in. 8/6

VALUE!

4 watt AMPLIFIERS
excellent amplifier with high gain preamp stage, 100% driver, 10P11 output stage, complete with sin. speaker. In attractive 2-tone case. Tone control, negative feedback, ready for immediate use. Individually tested. Excellent volume and clarity. Ideal for guitars, record players, p.a. in small halls, baby alarms etc. Easily worth £5. Our price whilst stocks last. Carr. 45/- Packing, etc. 7/6.

CO-AX, low loss, 6d. yd., 25 yds., 11/6. 50 yds., 22/-. 100 yds. 42/6.
Co-ax Spig 1/3. Wall outlet boxes 3/6.

ALL WAVE RADIOS

VERDI 55. MAINS & VALVE SUPER-SENSITIVE SUPERHET. Really attractive high quality modernistic panel and gold cabinets. Very compact. Wavebands 18-50m 180-550m, 700-2000m, ferrite aerial and throwout aerial. Smooth slow motion tuning. High dux sin. speaker. **AMAZING S.W. PERFORMANCE, CLARITY, VOLUME.** Standard miniature valves. Easily serviced, standard layout. Truly unusual value and UNR-PEATABLE! Absolutely complete with guarantee and circuit. Tax paid.

Guaranteed 3 Months



7 Gns.

6 Gns. each.

VERDI 54. As above but medium and long wave only.

BBC/ITA 14in. TVs.
With CRM 141 Tubes. Absolutely complete, tested for raster. Famous make, large purchase enables us to offer them at **£4.19.0** Carr. 12/6.

AM/FM RADIOS

Fantastic offer. 7 valves plus 2 diodes. Contemporary Cabinet. Top quality and finish. A.F.C. & V.C. Absolutely complete. Guaranteed 3 months. **£11**

PORTABLE RECORD PLAYERS. Takes all sizes Records, all speeds, amplifier, auto-changer, Garrani new "Nimline" Gram. In two-tone Case. **13 Gns.** All absolutely new.

PORTABLE RADIOGRAMS. As above with 5 valve superhet radio. Med. and Long wave. Fantastic value. 17 gns.

TELEPHONE C.O.D. ORDERS
DISPATCHED THE SAME DAY.

HIGHEST QUALITY—
COMPARE OUR PRICES

	6 Months	12 Months	NEW TYPES
MW 31/74	£2. 0.0	£3. 0.0	£3.15.0
MW 38/24	£2.10.0	£3.10.0	£4.15.0
CRM 172	£3. 5.0	£4. 5.0	£6.0.0
MW 43/64	£3.15.0	£5.15.0	

TRANSISTOR RADIO

Zephyr 6 transistor midset de luxe, superhet 180-550 metres with leather case only. **£4.10.0**

100 RESISTORS 6/6

Excellent. Sizes 1/3 watt.

100 CONDENSERS 10/-

Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER £5.

12 POTS. Popular values. 5K to 2 Meg. Unused, mixed, pre-set, long sp. switched, etc. **4/6**

CONDENSERS. 25 Mixed, Electrolytic. Many popular sizes. List Value £5. Our Price **10/-**

SILICON RECTS.

250V 50mA standard TV replacement. Top quality 8/8 (3 for 24/-)

3 VALVE AMPLIFIERS

Kit of new parts, consisting chassis mains and output transformers, valves (P61, 616G, 6X5N) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feedback, etc. Truly unusual value! **29/-**

29/-

29/-

29/-

29/-

FREE THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

Radiostructor EQUIPMENT-COURSES

A NEW-PRACTICAL WAY of UNDERSTANDING

Radio - Television - Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR...Your Career...Your Own Business...An absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G28)
READING, BERKS.

Please send brochure, without obligation, to:—

★ Name _____

Address _____

7/63

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

CAR OWNERS — LOOK!

SUPER CAR-PORTABLE RADIO OFFER

By Famous British Manufacturer—
Brand New and Unused. Fully
Guaranteed. Original List Price
£26.18.11



A fully transistorised Go-Anywhere portable that automatically becomes a real car radio simply by sliding into the car-holder tray. Full Medium and Long waveband coverage—Press button wavechange—Transistors used: 1—OC44; 2—OC45's; 1—OC82D; 2—OC82's and one diode. Internal ferrite rod aerial—Internal loudspeaker provides ample volume as a portable. Separate 8 x 5in. speaker is used in the car (supplied complete with 8 x 6in. baffle for easy fixing). Battery drain is exceptionally low, the life of the set's self-contained battery is approx. 200 hrs. Attractive finish in two-tone red and grey Vyandite washable material. Carrying handle folds away when not in use. Tuning scale is illuminated when set is operating in the car-tray. Size 9½ x 7½ x 3in. Bracket for padlock provides an effective theft deterrent. Compares with sets costing at least double. Properly installed this set will give you years of pleasure and service—both in and out of your car. Note: As a car radio this receiver operates ONLY from a 12-volt electrical system (positive or negative earth). As a portable it is powered by its own internal battery. All connections to car battery, speaker and aerial are automatically made simply by sliding into car-tray.

WIRECOMP'S **£10.19.6**
PRICE


COMPLETE WITH METAL TRAY, ALL CAR
FITTINGS, 8 x 5in. CAR SPEAKER & FULL
EASY-TO-FOLLOW FIXING INSTRUCTIONS. PP9 Battery 3/9 extra. P. & P. 7/6 extra

LOOK AT OUR NEW PRICES!

THE COROVER '6'

This superb receiver uses the very latest circuitry, 6 transistors and two diodes and is fully tunable over both medium and long wavebands. First stage uses three Mullard AF117 alloy diffused transistors with OA79 and OA91 diodes, output—OC81D and two OC81's in push-pull. I.F. frequency 470 Kc/s. Large internal ferrite rod aerial gives excellent reception over all ranges. 3 inch high flux speaker has a maximum output of 330mW. Operates on four 1.5 v. pen torch batteries. All components are mounted on a single printed circuit board. Attractive plastic case with carrying handle—fitted sockets for personal earpieces, tape recorder and car aerial. Size 6½ x 4 x 1½in.

MAY BE BUILT FOR **£5.7.6** All parts sold separately.
P. & P. 4/- extra. (Data and Instructions 2/6, free if all parts bought.)

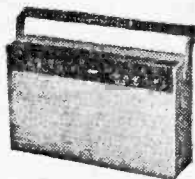

BUILD IT — TODAY!



The SPRITE


A unique Wirecomp offer. The Sprite is a six transistor superbet Miniature Pocket Radio of Commercial Quality—offered to you in three main pre-assembled units—each together with simple wiring—enable you to build it in only one hour!

Fully tunable over Long and Medium wavebands. Uses printed circuit and High sensitivity internal ferrite rod aerial. I.F. frequency 470 Kc/s. Transistors: 3 Philco 2067's, 2 Mullard OC81M's, OC81DM and OA90 diode. 3 inch speaker. Works on single PP9 battery. Supplied with the complete R.F. and I.F. stages. Driver and Output stages, ready built and mounted on the printed circuit; for final assembly you only have to fit the wave-change switch, tuning condenser and drive, volume control, earphone socket and aerial rod. In very attractive plastic case, size 4 x 2½ x 1½in. All parts sold separately.

THE 'REALISTIC 7'

A fully transistorised Portable Receiver made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2OC45's, OC71, OC81D, and 2OC81's plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker—I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. All components mounted on single printed circuit board, size 5½ x 5½in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3½in. with easy to read dial and socket for car aerial. choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions. All parts sold separately.

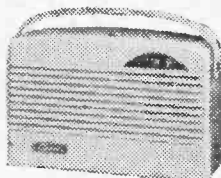WIRECOMP'S **£5.19.6** Battery 3/9 extra.
P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)



WIRECOMP'S
BARGAIN PRICE

79/6

Real Calf Leather Case, wrist strap and Personal Earphone with case and Battery, 12/6 extra.

P. & P. 3/6 extra. (Data and Instructions 2/6, free if all parts bought.)

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W9.

TEL: CUNNINGHAM 9533

Hours of business: 9 a.m. to 6 p.m. Open all day
Saturday, Opposite Paddington General Hospital.

Buses 18B and 36 pass the door.

Stern's

MULLARD DESIGNS

COMPLETE KITS OF PARTS

MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifier requiring input up to 250mV. Incorporates 5 input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 180 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case size 11" x 4" x 4".



KIT OF PARTS **£10.0.0** ASSEMBLED & TESTED **£13.13.0**
(Carr. & Ins. 5/-).

MULLARD "5-10" MAIN AMPLIFIER

For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS AND MULLARD VALVES including PARMEKO MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer.

COMPLETE KIT (Parmeko Output Trans.) **£10.0.0**
ASSEMBLED AND TESTED **£13.10.0**

ABOVE incorporating PARTRIDGE OUTPUT TRANS. **£1.8.0** extra.

THE MULLARD 510/RC AMPLIFIER

The popular complete "5-10" incorporating "Passive Control Unit providing up to 10 watts high quality reproduction with input of 600 mV. Specified components and new MULLARD VALVES. Includes PARMEKO MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus Power available for Tuner.



COMPLETE KIT **£12.0.0**
ASSEMBLED AND TESTED **£16.0.0** With PARTRIDGE OUTPUT TRANS. **£1.8.0** ex.
(Carr. & Ins. 7/6).

THE MULLARD 33/RC

A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

KIT OF PARTS **£8.8.0**
ASSEMBLED AND TESTED **£11.10.0**

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and 45 rpm output. (Carr. & Ins. 3/6)

L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. (Carr. & Ins. 1/6)

THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls and produces up to 3 watts undistorted output. (Carr. & Ins. 3/6)

Kit of Parts **£4.10.0** Assembled and Tested **£6.0.0**

Perfectly suited for Portable Installations for which purpose we offer PORTABLE CASE (£3.10.0) the AMPLIFIER (Kit) and 8" x 5" SPEAKER (£1.0.0). All for Alternately with ASSEMBLED AMPLIFIER **£10.0.0**
(Carr. & Ins. 5/-).

The Case quoted above will accommodate some 4-speed Single Record Units. A larger model is available for extra 10". With this Equipment a COMPLETE PORTABLE RECORD PLAYER can be built for **£14.0.0**

MULLARD FOUR CHANNEL MIXING UNIT


Self powered Cathode follower output. Incorporates two inputs for CRYSTAL MICROPHONES, one for CRYSTAL PICK-UPS and a fourth for Radio or Tape.

KIT OF PARTS **£8.8.0** ASSEMBLED AND TESTED **£11.10.0** (Carr. & Ins. 5/-).
Alternative Model I/L provides for one input matched for moving coil or ribbon mike **£1.17.0** extra.



ARMSTRONG RADIOGRAM CHASSIS

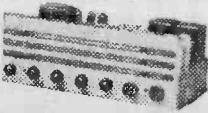We have the full range in stock. Prices range from £20.10.0. Full details are readily available



Send for current price list of all leading recording tapes and accessories.

MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard 2-VALVE PRE-AMPLIFIER but also perfectly suitable for other makes.



- ★ Equalisation for the latest R.I.A.A. characteristics.
- ★ Input for Crystal Pick-ups and variable reluctance magnetic types
- ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls.

KIT OF PARTS **£6.6.0** ASSEMBLED AND TESTED **£9.10.0** (Carr. & Ins. 5/-).

PRICE REDUCTIONS

- (a) THE KIT OF PARTS to build both the "5-10" Amplifier and the 2-Valve Pre-Amplifier... **£15.15.0**
(Carr. & Ins. 8/6).
- (a) Assembled and Tested... **£21.10.0**
- (b) THE KIT OF PARTS to build both the "5-10" Amplifier and the 3-Valve Pre-Amplifier... **£19.10.0**
(Carr. & Ins. 10/-).
- (b) Assembled and Tested... **£25.10.0**

With PARTRIDGE OUTPUT TRANSFORMER **£1.8.0** extra.

HIGH FIDELITY LOUDSPEAKERS

WE STOCK THE COMPLETE RANGE BY GOODMAN'S, WHARFEDALE and W.B. STENTORIAN

A few recommended examples

8 INCH TYPES	
GOODMANS "AXIETTE"	£5.5.7
W.B. HF 818	£5.18.6
WHARFEDALE "SUPER 8/RS/DD"	£6.14.2
10 INCH TYPES	
GOODMANS "AXIOM 10"	£6.5.11
W.B. MODEL HF 1016	£7.0.0
WHARFEDALE "GOLDEN 10/RS/SD"	£7.17.5
12 INCH TYPES	
GOODMANS "AXIOM 20" 15 watts	£10.7.0
GOODMANS "AXIOM 30" 20 watts	£14.10.0
W.B. MODEL HF 1214 15 watts	£10.5.8
WHARFEDALE "W12/RS"	£10.15.0
WHARFEDALE "Super 12/RS/DD"	£17.10.0
Carr. & Ins. on above 5/6 each.	

LEAK AND QUAD AMPLIFIERS IN STOCK

- LEAK "TL12 PLUS" POWER AMPLIFIER with the "POINT ONE PLUS" PRE-AMPLIFIER, 14 watts rated output. **£31.10.0**
- LEAK "TL25 PLUS" with the "POINT ONE PLUS" PRE-AMPLIFIER, 28 watts rated output. **£37.16.0**
- LEAK "STEREO 20" POWER AMPLIFIER with the "VARISLOPE STEREO" PRE-AMPLIFIER, 22 watts (11 watts per channel) **£55.9.0**
- QUAD II POWER AMPLIFIER with QUAD II CONTROL UNIT, 15 watts output. **£42.0.0**
Carr. & Ins. on above Amplifiers, 10/-

RECORD PLAYERS

- THE COLLARO "JUNIOR" 4-speed single player with separate crystal pick-up. **£3.10.0**
- THE NEW GARRARD "AUTOSLIM" 4-speed autochanger with crystal pick-up. **£7.10.0**
- GARRARD "AUTOSLIM DE LUXE" 4-speed autochanger, incorporates transcription pick-up arm. **£11.8.0**
- THE COLLARO "C80" 4-speed autochanger unit with Studio "O" pick-up. **£16.19.6**
- B.S.R. Model UA14, a 4-speed mixer autochanger with crystal pick-up. **£6.10.0**
- The new GARRARD Model HIF High Quality Single Record Player fitted with the latest T.P.A. 12 pick-up arm and G.C.S. crystal Cart-ridge. **£16.17.6**
- GARRARD record S.L.P. 10 single record player fitted with high output crystal pick-up PHILIPS Model AG106. A 4-speed player can be operated both manually and automatically. Suitable for Mono or Stereo operation. **£5.0.0**
Carr. & Ins. on each above 5/6 extra.

Mk. 11 "Fidelity" FM TUNING UNIT


- An attractively presented Unit incorporating MULLARD PERMEABILITY TUNING HEART and corresponding Mullard valve line-up. Very suitable to operate with our Mullard Amplifiers. **£10.10.0**
- KIT OF PARTS **£10.10.0**
- ASSEMBLED AND TESTED **£14.5.0**
(Carr. & Ins. 5/-).

IF YOU ARE PLANNING TO INSTALL "HI-FI" AND UNCERTAIN OF THE TYPE OF EQUIPMENT TO USE—OUR WIDELY EXPERIENCED TECHNICAL STAFF WILL WITH PLEASURE PUT FORWARD RECOMMENDATIONS—STATE TYPE OF INSTALLATION CONTEMPLATED AND APPROX. PRICE LEVEL.
CREDIT SALE TERMS are available on all Equipment over £10.0.0.
FULLY DESCRIPTIVE LEAFLETS are readily available—please advise items of interest and enclose S.A.E.

Stern's

SPECIALISTS IN SOUND EQUIPMENT FOR OVER 25 YEARS

STEREO TAPE PRE-AMPLIFIER

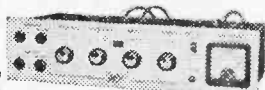

MODEL STP-1. For use with current TRUVOX, BRENNELL, or COLLARO "STUDIO" 1 and 1 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4 speed Equalisation Signal Level Meter and separate Gain Controls. Includes separate Power Unit.
KIT OF PARTS **£22.0.0** (Carr. & Ins. 8/6). **ASSEMBLED £28.0.0**

TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1 track, Mono Tape Decks. Incorporates Ferroxcube Push Pull Oscillator, Treble Inductor and 3-speed Equalisation. Includes Separate Power Unit.
KIT OF PARTS **£14.0.0** **ASSEMBLED £19.10.0**
(Carr. & Ins. 7/6).



MULLARD TAPE AMPLIFIER

Based on Mullard's Type "A" design and suitable for most 1 track Mono Tape Decks. Incorporates Ferroxcube Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit.
KIT OF PARTS **£13.13.0** (Carr. & Ins. 7/6). **ASSEMBLED £19.0.0**



STERN'S "ADD-A-DECK"

A self contained Unit consisting of Garrard Deck and matched Pre-amplifier on one chassis. Provides full tape recording facilities and replays through Pick Up Sockets or standard Radio receiver or Amplifier.
PRICE includes complete Tape Magazine. **£18.18.0**
(Carr. & Ins. 10/-).



and NOW!!! STERN'S OFFER THE "EMPRESS" STEREOSCOPE UNIT

A SPECIAL BULK PURCHASE ENABLES US TO OFFER THIS HIGH GRADE STEREO PRE-AMPLIFIER AT APPROX THE MANUFACTURER'S PRODUCTION COST. IT IS ENGINEERED TO THE VERY HIGHEST TECHNICAL STANDARDS AND REPRESENTS THE ULTIMATE IN PRECISION HIGH FIDELITY EQUIPMENT FOR

EXCEPTIONAL VALUE



Unquestionably the most advanced STEREOPHONIC Pre-amplifier available today, it provides the greatest range of facilities ever offered in a single unit. It incorporates full input facilities for Crystal or Magnetic Pick-Ups and Microphones, Radio Transmissions, Tape Recorders and Replay direct from high impedance Tape Heads. A miniature Cathode Ray Tube provides for VISUAL balancing of the input signals, and also for measuring the frequency response of PICK UPS and the power output in watts. The controls include Scratch and Rumble Filters, Channel reversal and Mixing facilities together with Function Switches, separate Volume and Baxandall Tone Controls. Size 14in. x 10in. x 4in.
OFFERED AT THE SPECIAL PRICE OF £17.10.0
(Carr. & Ins. 8/6).

THE EMPRESS IS PARTICULARLY SUITABLE TO OPERATE WITH OUR MULLARD "10 plus 10" POWER AMPLIFIER, AND WE OFFER THE TWO FOR ONLY **£36.0.0**
(Carr. & Ins. 15/-).

Send S.A.E. for fully descriptive technical leaflets, or call at our showrooms and hear the equipment on demonstration.

Our Technical dept. will be happy to advise on the choice of matching PICK-UPS - Microphones - Loudspeakers.

POSTAL ENQUIRIES and MAIL ORDERS TO

STERN RADIO LTD.

6-12, TUDOR PLACE, TOTTENHAM COURT RD.
LONDON, W1. TEL. MUSEUM 6128/9

DÉMONSTRATION and SHOWROOMS AT ...

STERN RADIO LTD.

109, FLEET ST, LONDON, EC4

TEL. FLEET ST. 5812/3

OPEN... 9 a.m. to 6 p.m. SAT. close 1 p.m.

PREMIER RADIO

23, TOTTENHAM COURT RD.

LONDON, W1. TEL. MUSEUM 6128/9

OPEN... 9 a.m. to 6 p.m. THURS. close 1 p.m.

!! COMBINED PRICE OFFERS !!

Includes small charge for special testing and
**PRECISE MATCHING of the ASSEMBLED
PRE-AMPLIFIER (or Amplifier) to TAPE DECK**

STP-1 (KIT) and "STUDIO" Deck	£38.0.0 Assembled	£48.0.0
STP-1 (KIT) and Brenell Deck	£66.0.0 Assembled	£75.0.0
STP-1 (KIT) and Truvox Deck	£51.0.0 Assembled	£59.0.0
TYPE "C" (KIT) and "STUDIO" Deck	£28.10.0 Assembled	£33.0.0
TYPE "C" (KIT) and BRENNELL Deck	£43.0.0 Assembled	£50.0.0
TYPE "C" Assembled and Wearite Deck	£70.0.0 Inc. Head Lift Trans.	
HF/TR3 (KIT) and "STUDIO" Deck	£28.0.0 Assembled	£33.0.0
HF/TR3 (KIT) and BRENNELL Deck	£43.0.0 Assembled	£50.0.0
HF/TR3 Assembled and Wearite Deck	£70.0.0 Inc. Head Lift Trans.	

To build a complete TAPE RECORDER we offer HF/TR3 AMPLIFIER STUDIO DECK, PORTABLE CASE, ROLA 10 x 8in. SPEAKER MICROPHONE and 1,200ft. TAPE ALL for £35.0.0. ALTERNATIVELY WE OFFER... THE COMPLETELY ASSEMBLED and GUARANTEED PORTABLE RECORDER... (Model CR3/S) .. FOR .. £43.0.0. (Carr & Ins. on above items 15/- each)

MULLARD "10+10" STEREO AMPLIFIER

A high fidelity design providing up to 10 watts (per channel). Superb reproduction frequency response flat to within 3db from 20 c/s to 60 Kc/s at 50 mW. Total Harmonic Distortion at 10 watts 0.1%.

Price (a) ASSEMBLED AMPLIFIER (as illustrated) **£24.0.0**

(b) KIT OF PARTS, **£20.0.0** (Carr. & Ins. 7/6.)
Built to the highest technical standards and presented strictly to MULLARD'S specification. Two specially designed GILSON ULTRA-LINEAR OUTPUT TRANSFORMERS with 20% taps are used. We can also supply the assembled MAIN AMPLIFIER only for operation with our DUAL CHANNEL PRE-AMPLIFIER; this provides a more versatile installation and is essential if a low output pick-up is to be used. When ordering specify loudspeaker impedance.

(a) THE ASSEMBLED MAIN AMPLIFIER and ASSEMBLED DUAL CHANNEL PRE-AMP **£34.0.0**

(b) KIT OF PARTS for both Units **£27.0.0** (Carr. & Ins. 10/6).



MULLARD DUAL-CHANNEL PRE-AMPLIFIER

A four Valve design for both STEREO-PHONIC and MONOPHONIC operation. Operates equally well with any make of amplifier requiring an input of up to 250 mV.
KIT OF PARTS **£12.10.0**



ASSEMBLED AND TESTED **£15.0.0**
(Carr. & Ins. 5/-)

THE "TWIN THREE" STEREO AMPLIFIER

ASSEMBLED AND TESTED
£9.0.0 (Carriage and Insurance 5/- extra)



Based on a recent design by MULLARD LTD., is ideally suited for use in Portable RECORD PLAYERS for which purpose we offer a specially designed Case. Incorporates MULLARD ECL 86 Valves, separate BASS and TREBLE CONTROLS and produces up to 3 watts per channel. Frequency response is 40 c/s to 35 Kc/s, size is only 14in. x 3in. x 5in. To construct a STEREO PORTABLE RECORD PLAYER we offer: Assembled AMPLIFIER with two ROLA 8in. x 5in. LOUD-SPEAKERS and PORTABLE CASE for **£16.10.0**

THE "TUDOR" STEREO AMPLIFIER

PRICE **£15.0.0** (Packing & Carr. 7/6)



A self-contained Shelf-mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate BASS and TREBLE CONTROLS. The Cabinet is finished in Black Crackle. Size 14 x 8 x 4in. Send for full specification.

WHEN ORDERING OR WRITING FOR
LEAFLETS PLEASE STATE DEPT. P.W.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS 38 CHALCOT ROAD, LONDON, N.W.1


Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 3/6 EXTRA. TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE

O82	8/-	6BR7	8/8	6UT6	9/8	25U4GT18/2	AC/8G/12M	EBC3	20/6	E184	8/-	M891	12/8	R17	17/8	U47	10/-	AF116	10/-	
082	17/6	6BR8	9/8	6V6G	4/7	25Y5 8/-	AC/12/12M	EBC4	7/6	E185	9/8	M84	3/8	R18	14/-	U50	5/3	AF117	20/-	
0Z4GT	4/3	6BS7	25/-	6V6GT	6/-	25Y16 19/5	AC/12/12M	EBC5	7/6	E186	13/6	M84D	8/8	R19	9/-	U52	4/6	AF118	8/6	
IA3	3/-	6BW6	10/8	6X1	4/6	25Z40 7/-	AC/12/12M	EBC6	5/-	E191	3/-	M114	7/8	R32	9/-	U78	5/8	AF127	12/-	
IA5	5/-	6BW7	6/-	6X3	4/6	25Z5 8/-	AC/12/12M	EBC9	12/4	E193	6/6	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF128	12/-	
IAC7	9/8	6BX6	4/6	6Y6	10/6	25Z6GT 8/-	AC/12/12M	EBC10	9/8	E194	10/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF129	12/-	
IC2	7/-	6C5	5/-	7B7	7/8	2817 7/8	ATP4	2/6	E195	9/8	E195	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF130	12/-
IC3	6/9	6C6	3/-	7C5	10/-	30C1 7/-	AZ1	1/4	E196	12/8	E196	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF131	12/-
IC5	7/-	6C8	6/-	7C8	7/8	30C15 10/-	AZ1	1/4	E197	12/8	E197	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF132	12/-
IC6	10/6	6C9	11/-	7D3	21/-	30F5 6/-	B36	5/9	E198	12/8	E198	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF133	12/-
ID5	18/2	6C10	8/8	7D5	15/-	30FL1 9/8	BL3	10/6	E200	12/8	E200	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF134	12/-
ID6	9/8	6C11	2/8	7D6	15/-	30FL12 12/6	CL4	12/6	E201	12/8	E201	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF135	12/-
IP1	6/9	6C12	15/8	7D8	15/-	30L 8/6	C1C	12/6	E202	12/8	E202	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF136	12/-
IP2	3/-	6C13	15/8	7D9	15/-	30L15 11/8	CB11	27/2	E203	12/8	E203	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF137	12/-
IP3	2/9	6C14	6/-	7S7	15/-	30P4 12/8	CH35	22/8	E204	12/8	E204	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF138	12/-
IP7	15/-	6C15	24/-	7Y4	5/-	30P12 7/8	CK06	8/6	E205	12/8	E205	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF139	12/-
IPD9	4/3	6D1	1/8	7B1	9/8	30P12 7/8	CL4	23/10	E206	12/8	E206	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF140	12/-
106	8/-	6D3	19/5	8D8	8/6	30P19 12/6	CL3	12/-	E207	12/8	E207	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF141	12/-
115GT	8/9	6D5	3/-	8H6V 14/11	30P11 10/6	CV6	2/6	E208	12/8	E208	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF142	12/-	
11A	3/-	6D6	15/-	8D2	3/-	30P13 9/8	CV6	10/6	E209	12/8	E209	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF143	12/-
11A	18/10	8E5	7/-	9D7	13/7	30P13 12/4	CV6	12/6	E210	12/8	E210	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF144	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E211	12/8	E211	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF145	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E212	12/8	E212	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF146	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E213	12/8	E213	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF147	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E214	12/8	E214	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF148	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E215	12/8	E215	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF149	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E216	12/8	E216	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF150	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E217	12/8	E217	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF151	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E218	12/8	E218	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF152	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E219	12/8	E219	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF153	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E220	12/8	E220	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF154	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E221	12/8	E221	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF155	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E222	12/8	E222	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF156	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E223	12/8	E223	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF157	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E224	12/8	E224	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF158	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E225	12/8	E225	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF159	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E226	12/8	E226	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF160	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E227	12/8	E227	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF161	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E228	12/8	E228	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF162	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E229	12/8	E229	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF163	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E230	12/8	E230	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF164	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E231	12/8	E231	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF165	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E232	12/8	E232	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF166	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E233	12/8	E233	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF167	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E234	12/8	E234	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF168	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E235	12/8	E235	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF169	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E236	12/8	E236	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF170	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E237	12/8	E237	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF171	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E238	12/8	E238	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF172	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E239	12/8	E239	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF173	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E240	12/8	E240	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF174	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E241	12/8	E241	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF175	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E242	12/8	E242	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF176	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E243	12/8	E243	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF177	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E244	12/8	E244	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF178	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E245	12/8	E245	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF179	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E246	12/8	E246	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF180	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E247	12/8	E247	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF181	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E248	12/8	E248	12/8	M114D12/8	R31/24/0	U78	4/6	U84	4/7	AF182	12/-
11D5	4/3	8E1	6/8	10D7	10/-	30P13 12/4	CV6	12/6	E249	12/8	E249	12/8	M114D12/8	R31/241						

Just a few of our **BARGAINS**

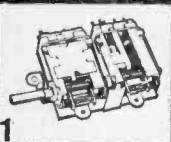

1



2




3



5




4

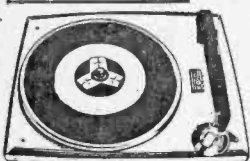

6



7

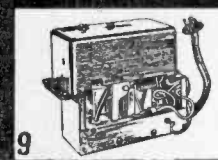

9



8




10



11



12

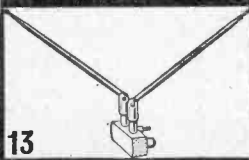

13



14

**RADIO & T.V.
COMPONENTS
[ACTON]
LIMITED**

1. **A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size $2\frac{1}{2} \times 2\frac{1}{2}$ in. approx. By famous manufacturer. A.M.-I.F. 470Kc/s. F.M.-I.F. 10.7Mc/s. A.M. coverage from 1,620 Kc/s-825Kc/s. F.M. coverage 108Mc/s-88Mc/s. Circuit diagram 2/6, FREE with Tuner. 25/-, plus 1/- P. & P.
2. **TRANSISTORISED POCKET RADIO** with printed circuit, mini-circuit, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening. $4\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. Luxembourg in favourable areas. Only 21/- P. & P. 2/6. All parts available separately.
3. **A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter scale, calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamperes 0-10, 0-1000 Ohms ranges 0-10,000 0-100,000, 19/6. P. & P. 2/- Wiring diagrams 1/-, free with parts.
4. **SIGNAL GENERATORS.** Cash 27.5.0, or 30/- deposit and 6 monthly payments of 21/6. P. & P. 6/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case $10 \times 6\frac{1}{2} \times 4\frac{1}{2}$ in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.
5. **SIGNAL GENERATORS.** Cash 25.5.0. P. & P. 6/6. Coverage 120 kc/s to 84 Mc/s. Case $10 \times 6\frac{1}{2} \times 4\frac{1}{2}$ in. Size of scale $6\frac{1}{2} \times 3\frac{1}{2}$ in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.
6. **STAAR 45. 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on/off switch governed motor, attractive two-tone grey finish, 22.9.6. P. & P. 2/-.
7. **CARRYING CASE** for STAAR 45 or COMPLETE KIT beautifully styled in two tone with record compartment. Specially designed to take player and amplifier. Just screw in and connect up. All parts available separately. Case only 22/6. P. & P. 5/- Complete kit, 25.10.0. P. & P. 5/-.
8. **TRANSISTORISED AMPLIFIER,** suitable STAAR 45. Output 1 watt. Size $4\frac{1}{2} \times 2\frac{1}{2}$ in. Printed circuit, tone/volume controls plus 4 transistors Push-pull output complete with 2in. moving coil speaker. Built and tested, 49/6. P. & P. 2/-.
9. **CHANNEL TUNER I.F. 16-19 Mc/s.** Continuously tunable from 174-216 Mc/s. Valves required—PCF90 and POC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 19/- P. & P. 3/-.
10. **B.S.R. MONARCH V414 WITH FUL-FI HEAD.** 4-speed, plays 10 records, 12in., 10in., or 7in. at 16, 33, 45 or 78 r.p.m. Internals 7in., 10in., and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: $12\frac{1}{2} \times 10\frac{1}{2}$ in. Space required above baseboard 4in. below baseboard 2in. Fitted with Ful-Fi turnover crystal head, 25.19.6. P. & P. 6/6.
11. **POCKET MULTI-METER.** Size $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. Meter size $2\frac{1}{2} \times 1\frac{1}{2}$ in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω Complete with test prods, battery and full instructions, 25/- Plus 1/6 P. & P.
12. **8-watt PUSH-PULL 4 VALVE AMPLIFIER** plus METAL RECTIFIER. A.C. mains 200-250 v. Size $10\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$ in. 5 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 dB down all hum. Output transformer tapped for 3 and 16 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, 23.13.6. P. & P. 6/- Crystal mike to suit 15/- P. & P. 2/- 5in. F.M. Speaker to suit, 12/6. P. & P. 2/-.
13. **INDOOR AERIAL** for ITV/BBC/FM. Complete with standard co-axial plug. Heavy chrome extending dipoles—7ft. fully extended. Plugs straight into T.V. or VHF Tuner. Fully directional, 10/6. P. & P. 1/6.
14. **NO MORE FLAT BATTERIES.** Charge your own battery overnight with this wonderful little charger. Output 6 and 12 volts, 2 amps. Input 200-250 v. A.C. mains. Mains fuse incorporated. Attractive silver hammer finished case. $6 \times 3 \times 3\frac{1}{2}$ in. Complete with leads and battery clips only 21/- P. & P. 3/6.

**21b HIGH STREET
ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.
GOODS NOT DESPATCHED OUTSIDE U.K.

WEYRAD

6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500mW OUTPUT

ROD AERIAL—RA2W

6 in. long, $\frac{3}{8}$ in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil 12/6

OSCILLATOR COIL—P50/1AC

M.W. covered with 176pF tuning capacity, L.W. by extra padder 5/4

I.F. TRANSFORMERS


1st and 2nd Stage—P50/2CC 5/7
(2 required)

3rd Stage—P50/3CC 6/-

DRIVER TRANSFORMER—LFDT4 9/6

OUTPUT TRANSFORMER—OPT1 10/6

PRINTED CIRCUIT—PCA1 9/6

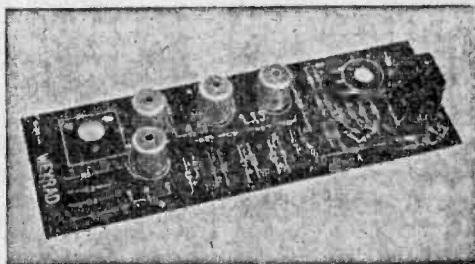

In response to many requests we have redesigned the output stages to give 500mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

CONSTRUCTOR'S BOOKLET WITH FULL DETAILS

2/-

TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL 63/6

WEYMOUTH RADIO MANUFACTURING CO., LTD.

REGENT FACTORY, SCHOOL STREET,
WEYMOUTH, DORSET

EVERY RADIO ENTHUSIAST NEEDS THIS SUPERB COMPONENT CATALOGUE

Latest Reprint No. 7 is now available and has been enlarged to 172 pages, listing over 5,000 components with 600 illustrations.

Beautifully printed on high-grade paper with comprehensive index for easy quick reference.

It will save you hours of time and also money because you will be able to obtain all your components by return from one source.

Many new and interesting lines now included.

Acknowledged to be the best component catalogue available and used as a standard reference book by most designers and writers. All brand new proprietary makes including Eddystone, Heathkit, Armstrong, Lektrokit, plus all the well known component manufacturers.



**SEND
FOR
YOUR
COPY
TODAY**

**OBTAINABLE ONLY
FROM**

HOME RADIO

187 LONDON ROAD, MITCHAM

2/6

PLUS 9d POST

POST
COUPON
TODAY
Write
CATALOGUE
on top left
of envelope

Enclose
P.O. 3/3

NAME

ADDRESS

Home Radio Ltd.(PW) 187 London Rd.Mitcham, Surrey

THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT
FOR VOCAL AND INSTRUMENTALIST GROUPS


Eminently suitable for bass guitar and all other musical instruments

- * Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- * Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- * Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- * For 200-250 v. to 50 c.p.s. A.C. mains operation.
- * Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- * Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- * LEVEL frequency response throughout the audible range.
- * SUPERIOR TO UNITS AT TWICE THE COST.

39½ Gns.

Send S.A.E. for leaflet.

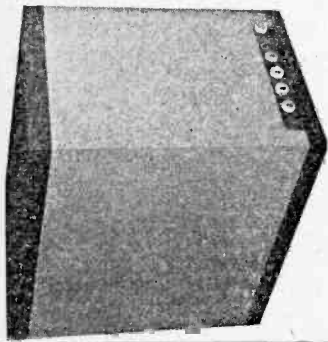OR DEPOSIT of £43.0 and 12 monthly payments of £3.9.11. Carr. 17/6.



R.S.C. JUNIOR GUITAR AMPLIFIER
5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome, strongly made cabinet (size 14 x 14 x 7in. approx.) finished in attractive and durable polychrome. 200-250 A.C. mains operation. **£8.19.6** Or DEPOSIT £1 and 9 monthly payments of £1. Carr. 7/6.

LINEAR TREMOLO/PRE-AMP. UNIT
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket of amplifier. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. Three sockets are for two inputs and Foot Switch. **4 Gns.**

R.S.C. SENIOR Guitar Amplifier
14 watt high-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-up can be used at the same time. Two loudspeakers are incorporated, a 12in. high flux 14 watt bass unit, and a 6 x 4in. elliptical for treble. Cabinet is well made and finished as Junior Model. Size approx. 18 x 18 x 8in. Only **16 Gns.** Carr. 10/-

Send S.A.E. for leaflet.
Or DEPOSIT 37/- and nine monthly payments of 37/-.

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS. Type BG1. Suitable for Bass Guitar. Speaker Unit 15in. High Flux. 15 ohms. 25 watts. Cabinet size approx. 24 x 21 x 13in. Only 19½ gns. Or Deposit 42/- and 12 monthly payments of 34/9. Type BG2. Suitable for Bass Guitar. Super Sensitive. 15in. 15 ohms high flux speaker. Cabinet size approx. 30 x 21 x 14in. Attractive covering of two contrasting tones of Rexine and Vynair. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

Type BG3/2. Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of Grey Vynair and Rexine. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

LARGE REXINE COVERED SPEAKER CABINETS. Heavy block-board construction. Very attractive two tone covering of Rexine and Vynair. Size 30 x 21 x 16in. cut for 15in. or 18in. speaker or for two 12in. 11 gns. Or Deposit 25/9 and nine monthly payments 25/9. Size 30 x 30 x 18in. cut for 15in. or 18in. speaker 13 gns. Or Deposit 30/4 and nine monthly payments 30/4. Suitable speakers available.

FANE ACOUSTICS 15in. HEAVY DUTY LOUDSPEAKER. High flux. 15 ohm 25 watt. Total flux 186,000 lines. Cast chassis. Suitable for Bass Guitar. Only 13 gns. Or Deposit 31/6 and nine monthly payments 31/6.

EXTRA HEAVY DUTY 15in. Type 153. 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm. voice coil. Only 18 gns. Or Deposit 35/- and 12 monthly payments 35/-.

ANNOUNCING THE R.S.C. B20 BASS GUITAR AMPLIFIER



A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains. Send S.A.E. for leaflet.

29½ Gns. Or Deposit £32.0 and 12 monthly payments of 56/10. Carr. 17/6.


EX. GOVERNMENT ACCUMULATORS. Size 7½ x 4 x 2in. 2 v. 16 A.H. brand new. 6/9 each. 3 for 15/6.

EX. GOVT. SMOOTHING CHOKES. 200 mA. 3-5 H. 50 ohms. Parmeko 8/9; 150 mA. 10 H. 50 ohms 9/9; 80 mA. 20 H. 90 ohms 5/9; 120 mA. 12 H. 100 ohms 8/9; 50 mA. 50 H. 1,000 ohms 6/9; 100 mA. 10 H. 100 ohms 6/9; 60 mA. 5-10 H. 250 ohms 2/11.

COMPLETE POWER PACK KIT, 19/11
Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing choke at both units. For 200-250 v. A.C. mains. Outputs 250 v., 60 mA. 6.3 v. 2 A.

R.S.C. POWER PACK, 99/9. Louvred metal case only 8 x 5½ x 2½ins. Stove enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA. fully smoothed and 6.3 v. 2 A. Suitable for power requirements of almost any Pre-amp or Radio Tuner.

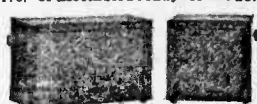R.S.C. BABY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Control at both units. An intercomm. of this class would normally cost £20-£30. Only 79/6, carr. 5/- or assembled ready for use £5.15.0.



EX. GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.W. ONLY 19/9

LEICESTER

BRANCH
NOW
OPEN

TRANSISTOR SALE: Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/9, OC81 4/11, OC171 9/9, Ediswan 5A101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

D.C. SUPPLY KIT: 12 v. 1 A. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

SELENIUM RECTIFIERS

F.W. BRIDGE 24 v. 2 amp. .. 14/9
6/12 v. 1 A. .. 3/11 24 v. 20 amp. .. 89/9
6/12 v. 2 A. .. 6/11 H.T. TYPES H.W.
6/12 v. 3 A. .. 9/9 150 v. 40 mA. .. 3/9
6/12 v. 4 A. .. 12/3 250 v. 50 mA. .. 3/11
6/12 v. 6 A. .. 15/3 250 v. 60 mA. .. 4/11
6/12 v. 10 A. .. 26/9 250 v. 80 mA. .. 5/11
6/12 v. 15 A. .. 35/9 250 v. 250 mA. .. 11/9
(Bridge) 10/11. 250 v. 50 mA. F.W.
(Bridge) 8/11. H.W. 250 v. 60 mA. 5/11.

LINEAR TAPE PRE-AMPLIFIER
Type LPL1. Switched Negative feedback equalisation Positions for Iccord 15in. 3fin., 7in. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 gns. S.A.E. for leaflet.

HUGE PURCHASE OF BRAND NEW 21v. 20 amp. F.W. (BRIDGE) SELENIUM RECTIFIERS, each

49/9

R.S.C. (Manchester) Ltd.

LEICESTER: BIRMINGHAM:

32 High St. 6 Gt. Western

Half-day Thursday No half-day

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

SHEFFIELD: HULL: LIVERPOOL: BRADFORD:

13 Exchange St. 51 Savile 73 Dale St. 56 Morley St.

Half-day Thursday Half-day Wednesday

MANCHESTER: LEEDS:

8-10 Brown St. (Market St.) 5-7 County

No half-day Half-day Wed.

R.S.C. (Manchester)

LEICESTER: BIRMINGHAM:
32 High St. 6 Gt. Western
Arcade
Half-day (Opp Snow Hill
Thursday Sta) No half-day

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied, S.A.E. with all enquiries please.

SHEFFIELD: **HULL:** **LIVERPOOL:** **BRADFORD:** **MANCHESTER:** **LEEDS:**
13 Exchange St. 51 Savile 73 Dale St. 56 Morley St. 8-10 Brown St. 57 County
Castle Market Bldgs, Sheffield Liverpool 2 (above Alhambra Theatre) Bradford Manchester 2 (Market St.) (Mecca) Arcade
Half-day Half-day Half-day Half-day Half-day Half-day

SENSATIONAL STEREO OFFER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 18/9 extra with above only.

R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures comparable with the most expensive amplifiers available. Hum level 70 db down. Frequency response ± 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 307 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 6X7, 6X7, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, CLUBS, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 18/9. The amplifier can be supplied, factory built with 200-250 v. 50 c/s. valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

11 Gns.

Carr. 10/-
riving handles can be supplied for 18/9. The amplifier can be supplied, factory built with 200-250 v. 50 c/s. valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

WE STOCK ARMSTRONG, DULCI LINEAR AND JASON EQUIPMENT GOODMAN'S W.B. AND FANE SPEAKERS

GARRARD AND GOLDRING T/ABLES

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V./C. Controls are Tunings, W/Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7 in. high. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams. 39/9, or ready to use, 46/6.




kit of parts with diagrams and instructions, 49/9, or ready to use, 56/6.

P.M. SPEAKERS. 10in. W.B. "Stentorian" 3 or 15 ohms type HF 1012 10 watts. hi-fidelity type. Recommended for use with our All Amplifier. £4.7.6. 12in. R.A. 3 ohms 10 watts (12,000 lines). 59/6.

TWEETERS. Plessey 30 19/9, 150 25/9.

Jason FMTI V.H.F./F.M. Radio Tuner design. Total costs of parts including valves. Tuning dial, Escutcheon, etc., £8.18.9. Other Jason equipment in stock.

LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for any record playing unit, and most microphones. Negative feedback. Controls for Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E220, ECC83, EL84. Size only 7-5-5 in. high. Guaranteed 12 months. Only £5.16.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

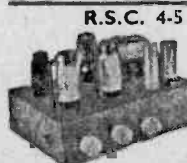**R.S.C. 4.5 WATT A5 HIGH-GAIN AMPLIFIER**

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 30 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes full punched chassis (with associated wiring diagrams and instructions). Exceptional value at only £4.15.0, or assembled ready for use £5/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

NOW AT LEICESTER

R.S.C. GRAM. AMPLIFIER KIT. 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc. supplied. Only 39/9. Carr. 3/9.

THE SKYFOUR T.R.F. RECEIVER
A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, SP61, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and parts list 1/9. maximum building costs £4.10.6. Inc. attractive walnut veneered wood cabinet 12 x 6 1/2 in.


MULTI-METERS. CARY M1. Sensitivity 2,000 ohms per volt. A.C. and D.C. 54/-.

A.10. Basic Meter sensitivity 155 micro-amps A.C. and D.C. ranges £4.17.6.

B.20. Sensitivity up to 10,000 ohms per volt A.C. and D.C. £6.10.0. 30,000 ohms per volt £8.19.8.

R.S.C. JUNIOR HI-FI REPRODUCER. The very latest Goodmans Axlette 8 High Fidelity loudspeaker (retailing at approx. 5 gns.) fitted in a specially designed Bass Reflex cabinet size 12in. x 18in. x 10 in. Acoustically lined and ported and finished in polished walnut veneer. Matching 12 in. speaker. Frequency range 40-15,000 c.p.s. Power handling 6 watts nominal. Ideal for Stereo. Limited number. Carr. 4/6

8 Gns.

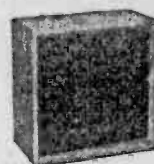12in. 10 WATT HIGH QUALITY LOUDSPEAKER

In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-.

Deposit 11/3 and 9 monthly payments of 11/3.

12in. 20 WATT LOUDSPEAKERS IN CABINETS. Size 18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.

For larger types see page 301.

R.A. 12in. DUAL CONE 3 ohm 8 watt Speakers. Ideal for Stereo. Only 39/9 ea.

R.S.C. BASS REFLEX CABINETS. JUNIOR MODEL. Specially designed or W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.18.6.


STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. For vertical or horizontal use. £5.18.6. Suitable legs with brass ferrules, 19/6 per set of 4.

R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 11 x 8in. for 8 x 5in. or 10 x 6in. speaker. £2.9.9.

STANDARD MODEL. Size 27 x 18 x 12in. for 8 or 10in. speakers. £4.11.9.

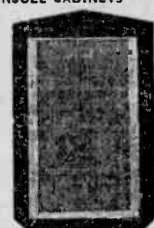SENIOR MODEL. Size 30 x 20 x 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.



AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.18.9. Carr. 5/-.

Or Senior 15 watt, 7 gns. Carr. 7/6.

AUDIOTRINE EQUIPMENT CABINETS. Size 36 x 15 x 18in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Uncut removable baseboard. Depth above Only 12in. gns. baseboard 51". Carr. 15/-.



AUDIOTRON HI-FI TAPE RECORDER KIT


REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR

Incorporating the latest Collaro Studio Tape Transcriber. The audiotone High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish, size 14 1/2 x 15 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. TERMS. Deposit £2.15.9 and 12 monthly payments of 44/- . Cash price if settled in 3 months.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR
OUTPUT "BUILT-IN" TONE
CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A.10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL24, EL34, E281. High Quality sectionally wound output transformer especially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response ± 3 dB. 30-30,000 c/s. Six negative feedback loops. Hum level 60 dB down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STAN-DAIRD OR LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING, BASS, LEAD OR RHYTHM GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 A. For supply of a RADIO FEEDER UNIT. Size approx. 12.9-7in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only 8 Gns. Carr.

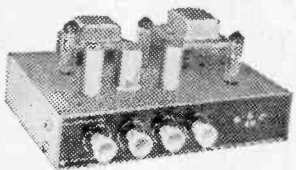


(Or factory built 5/- extra.) If required louvered metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets. Speaker. Microphones, etc., with cash and credit terms.

B.S.R. MONARDECK TAPEDECKS. Speed 3 1/2 in. per sec. With high quality recording heads, £6.19.6. Carr. 5/- . Cabinets to take Deck and amplifier 39/6.

R.S.C. TRANSISTORISED GRAM AMPLIFIER. Output 1 watt, for 30hm speaker. Transistors Mullard OC71, OC81, OC81, OC81. Fitted Vol. Control with switch. Assembled and tested. Suitable for any normal crystal pick-up. Only 59/9.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

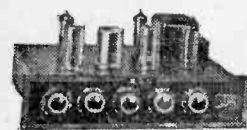

A complete set of parts for the construction of a stereo-phonographic amplifier giving 5 watts high quality output on each channel (Total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL24, EL34, E281. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and full instructions supplied. Send S.A.E. for leaflet. 8 Gns. Carr.

Kit can be supplied assembled ready to use for 59/6 extra.

R.S.C. BATTERY CHARGING EQUIPMENT

HEAVY DUTY CHARGER KIT 6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-250 v. F.W. (Bridge) Selenium Rectifier, Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. 59/9. Carr. 4/6.

CHARGER KIT. 12V. 14 AMP or 24v. 7amp. Consisting of mains trans. 0-200-250 v. F.W. (Bridge) selenium Rectifier, F. Ammeter, Fuses, Variable Resistor and Circuit. Only 6 Gns. Carr. 15/- . Please state if 12v. or 24v. kit required.

SOLDERING IRONS. 230-250 v. 30 watts. First quality. For Radio work. 19/9. Spare elements and bits available.

Assembled 4-5 amps. 6/12 v.



as above. Only 59/9. Carr. 3/6.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finished. Fused and ready for use with mains and output leads. Carr. 5/- . Terms: Deposit 18/3 and 5 monthly payments 13/3. 6/12 v. 3a. All facilities 49/9. Carr. 3/6.

ASSEMBLED 12V. 10 Amp with variable charge rate adjust-ment, ammeter and strong louvered stove enamelled case. Ready for use. Only 7 Gns. Carr. 10/- or in Kit Form 5 Gns.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 250-230-250 v. 50 c/s. Screened TOP SHROUDED DROP THROUGH

250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a 17/9
350-0-350v. 80mA. 6.3v. 2a. 5v. 2a. 18/9
250-2-250v. 100mA. 6.3v. 2a. 6.3v. 1a. 21/9
250-0-250v. 100mA. 6.3v. 3.5a. C.T. 19/9
250-2-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 25/9
300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 310 Amplifier. 29/9
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
425-0-425v. 200mA. 6.3v. 4a. 5v. 3a. 49/9
FULLY SHROUDED UPRIGHT
250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. 17/11
Midget type 21-3-4in. 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 27/9
300-0-300v. 100mA. 6.3v. 4a. 5v. 3a. 27/11
300-0-300v. 130mA. 6.3v. 4a. C.T. 3v. 1a. for Mullard Amplifier 33/9
350-0-350v. 100mA. 6.3v. 4a. 5v. 3a. 27/11
350-0-350v. 150mA. 6.3v. 4a. 5v. 3a. 35/9

FULLY SHROUDED (continued)—
425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 55/-
425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a. 59/9
450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a 69/9
OUTPUT TITANOSOL MERS
Midget Battery Pentode 66 : 1 for 354, etc. 4/6
Small Pentode, 5,000 Ω to 3 Ω 4/6
Small Pentode 7/8,000 Ω to 3 Ω 4/6
Standard Pentode 10,000 Ω to 3 Ω 5/7
Standard Pentode 7,000 Ω to 3 Ω 5/9
10,000 Ω to 3 Ω 5/9
Push-Pull 8 watts. EL34. or 6V6 to 3 Ω or matched to 15 Ω 9/9
Push-Pull 10-12 watts to match 6V6 or EL34 to 3-8 or 15 Ω 10/9
Following types for 1 and 15 Ω speakers:
Push-Pull 10-12 watts 6V6 or EL34. 18/9
Push-Pull 15-18 watts. 6L6, KT66 22/9
Push-Pull Mullard 510 Ultra Linear 29/9
Push-Pull 20 watts, sectionally wound. 6L6, KT66, EL34, etc. 49/9

25 1 GNS.
2 Carr.
17/6



ONLY 3
PAIRS OF
SOLDERED
JOINTS
PLUS
MAINS

SPECIAL NOTE. The Tape Decks we supply are latest models. Where customers already have a Deck or wish to use one of those being offered cheaply we can supply Kit less Deck at 13 Gns. carr. 10/- . Or deposit 2 Gns. and 12 monthly payments 28/9. Also if required we can supply in lieu of portable cabinet and 7 1/2 in. speaker, the Equipment Cabinet illustrated at foot of opp. page and a high flux 8 1/2 x 5 1/2 in. speaker for 8 Gns. extra.

HI-FI CRYSTAL PICK-UP HEADS. (Cartridges.) Acos Standard replacement for Garrard, B.S.R. and Collaro. 16/9. Acos Stereo-Monaural 29/9. Ronette Stereo-Monaural 59/6. B.S.R. Stereo 39/9. AUTOMATIC RECORDING HEADS. High Impedance Record/Playback 22/- . Low Impedance Erase, 12/6.

PICK-UP ARMS. Complete and with latest Acos/hi-fi Turnover Cartridge 28/11. CRYSTAL MICROPHONES. Hand type NP110 14/9. R.T.C. 19/9. Acos Mic 40 25/9. Acos Mic 45 29/9. Stick type Acos 39-1 39/9. BM3 with neck band and heavy table stand 59/9. Lapel type 35/9.

COLLARO JUNCTION speed Single Flyer Unit and Crystal Pick-up with hi-fi Turnover head. Only £3.19.6.

B.S.R. UA14-4-sp'd AUTO-CHANGERS with hi-fi turnover head, £6.19.6. Carr. 4/6.

GARRARD AT-10-SLIM 4-SPEED AUTO-CHANGER with high fidelity pick-up. Latest model For 200-250 v. A.C. mains. 27.19.6. Carr. 4/6.

GARRARD AT-6 AUTO-SLIM DE-LUXE 4-SPEED AUTO-CHANGERS. Turnover GC3 head, for 200-250 v. A.C. mains. 11 Gns.

GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. A.C. mains. Size 11 1/2 x 2 1/2 x 4 1/2 in. Controls: Vol. and Tone with switch. Only 59/6.

All for A.C. Mains 200-250v., 50 c/s. Guaranteed 12 months.

ASSEMBLED 6/12 v. 2 amps.

Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case finished attractive blue. Fused, ready for use with mains and output leads 49/9. Carr. 3/6.

6/12v. Lamp 27/9 Less meter.

BATTERY CHARGER KITS Consisting of Mains Transformer. F.W. Bridge. Metal Rectifier, well ventilated steel case. Fuses. Fuse-holders. Charge Rate Selector Panels, Heavy Duty Clips, circuit. Carr. 3/6 extra.

6v. or 12v. 1 amp. 22/9
As above, with Ammeter 28/9
6 v. 2 amps. 19/9
6v. or 12v. 2 amps. 25/9
6 v. or 12 v. 2 amps, inclusive of Ammeter. 35/9
6 v. or 12 v. 4 amps. 45/9
6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 52/9

CHARGER AMMETERS 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-60 a., 8/9.

MIDGET MAINS Primaries 200-250 v. 50 c/s. 250 v. 60 mA. 6.3 v. 2a. 11/9
250-0-250 v. 80 mA. 6.3 v. 2a. 12/11

Both above size 2 1/2 x 2 1/2 in.

FILAMENT TRANSFORMERS All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5a. 5/9; 6.3 v. 2a. 7/9; 0-4-6.3 v. 2a. 7/9; 1.5a. 1.5a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/8; 12 v. 1.5a. twice 17/8.

SMOOTHING CHOKES 150 mA. 7-10 H 250 ohms 11/9
100 mA. 10 H 250 ohms 8/9
80 mA. 10 H 350 ohms 8/9
60 mA. 10 H 400 ohms 4/11

CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1a. 12/9; 0-9-15 v. 2a. 14/9; 0-9-15v. 3a. 18/9; 0-9-15 v. 5 a. 18/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8a. 28/9.

AUTO (Step up/down) TRANS. 0-110/120-330v. 50-50 watts. 13/9; 250 watts. 39/9; 150 watts. 27/9.

MICROPHONE TRANSFORMERS 120 : 1 high grade, clamped, 6/9; 120 : 1 Plotted, Mu-metal screened, 9/9.

SURBITON PARK RADIO LTD.

FOR POST HASTE—POST FREE SERVICE

MARTIN RECORDAKITS

HALF TRACK

B.S.R. TD2 Monardeck, latest model 5 1/2 in. spool	£9.9.0
Deposit £1.0.0 and 9 monthly	£11.0
Tape Amplifier for B.S.R. deck, printed circuit wired with EX235, RCL22, EM85 and EZ81. Complete with all plugs, sockets, pans, knobs, etc. The whole amplifier mounts on to the deck, making a self-contained unit	£8.8.0
Deposit £1.0.0 and 8 monthly	£11.0
Case with 7 in. x 4 in. speaker, in two tone grey	£4.4.0
Complete Kit as above	£22.0.0
Deposit £2.4.0 and 12 monthly	£16.6
The above recorder can be supplied assembled, tested and complete with tape and microphone for	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.6
Collaro Studio Deck, Very latest model 3 speeds 7 in. spools	£12.10.0
Deposit £1.5.0 and 12 monthly	£10.8
Tape Amplifier for studio deck, with ready wired printed circuit control and input panels, mains and output transformers. Complete with valves, knobs, pans, screws, etc. EF84, EC45, EM84, EZ81, OA81 and EL84, 3 wate output. Magic eye, radio and mic. inputs, EX L/S socket, tone and monitor controls. Can be used as an amplifier	£11.11.0
Deposit £1.4.0 and 12 monthly	19/-
Case for above including 9 in. x 5 in. speaker	£5.5.0
Total Kit as above	£29.0.0
Deposit £2.8.0 and 12 monthly	£23.2
We can offer the above recorder, complete with tape and microphone, in a De Luxe two tone grey cabinet, assembled for	£35.0.0
Deposit £3.10.0 and 12 monthly	£28.2
This Machine is listed at 39 Gas, by makers and is a very good buy. Building Instructions available at 2/6 each kit (refunded if kit bought.)	

QUARTER TRACK

B.S.R. TD2	£11.11.0
Deposit £1.4.0 and 12 monthly	19/-
Tape Amplifier as above, but quarter track	£9.9.0
Deposit £1.0.0 and 9 monthly	£11.0
Case, two tone grey, with speaker	£4.4.0
Complete Kit as above	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.6
Collaro Studio Deck, 4 track	£17.17.0
Deposit £1.17.6 and 12 monthly	£19.5
Tape Amplifier, as above, but 4 track	£12.12.0
Deposit £1.7.0 and 12 monthly	£10.8
Case with 9 in. x 5 in. speaker	£5.5.0
Complete Kit 4 track Collaro	£35.0.0
Deposit £1.10.0 and 12 monthly	£21.6
Tape Pre-amplifier for Collaro deck, with power supplies, EOC83, ECL82, EZ80 and EM85, Radio and Mic. sockets, gives an equalised output of 400 mV/Valts.	
Half Track	£8.8.0
Deposit £1.0.0 and 8 monthly	£11.0
Quarter Track	£9.9.0
Deposit £1.0.0 and 9 monthly	£11.0
Bradmatic R/PB and Erase on Collaro bracket 4 track	£11.9.6
Bradmatic R/PB, Ideal 3rd head Collaro deck 4 track	£12.12.6
Pressure pad (audio deck only)	4/0
Brenell Mk.5 deck, 4 track, 4 speeds	£29.8.0
Deposit £3.1.6 and 12 monthly	£22.7
Brenell Mk. 5 Amplifier, with power	£24.0.0
Deposit £2.9.0 and 12 monthly	£19.10

JASON F.M. TUNERS

FMT1, complete with valves	£6.17.6
Deposit £1.1.0 and 6 monthly	£12.9
FMT2, complete with valves, Less Power	£7.17.6
Deposit £1.0.0 and 7 monthly	£12.6
FMT2, complete with valves, Self powered	£9.15.0
Deposit £1.0.0 and 9 monthly	£11.8
FMT3, complete with valves, Less power	£9.12.6
Deposit £1.0.6 and 9 monthly	£11.4
FMT3, complete with valves, Self powered	£12.0.0
Deposit £1.4.0 and 12 monthly	19/10
Power pack kit ready drilled chassis for FMT1, etc.	£2.12.8
The instruction books are included in all kits but are otherwise 8/6.	
JTV/2, switched F.M. and TV, Sound self powered, All valves	£14.15.0
Deposit £1.9.6 and 12 monthly	£14.5
Mercury 2 as JTV/2 but less power, with all valves	£10.15.0
Deposit £1.1.6 and 12 monthly	17/10

The instruction book is again included but is otherwise 3/6.
All the above units are available ready built and aligned. Price on request.

AMPLIFIERS (MONO)

Linear L45 Three valve amplifier	£5.19.6
Linear Dioniso Five valve, push pull	£12.12.0
Deposit £1.7.0 and 12 monthly	£19.5
Linear Concord 30 watt with case	£18.0.0
Deposit £1.16.0 and 12 monthly	£19.10
Tripletone Hi Fi Major, with Pre-amp	£15.18.9
Deposit £1.15.3 and 12 monthly	£16.1
Pye Mozart, including Pre-amp, 10 watt	£25.4.0
Deposit £2.10.6 and 12 monthly	£21.11
Leak TL 12, Main amp, only 10 watt	£18.18.0
Deposit £2.0.6 and 12 monthly	£11.11
Leak Variotone 111 Pre-amplifier	£15.15.0
Deposit £1.11.6 and 12 monthly	£16.1
Quid Main amp, only 15 watt	£22.10.0
Deposit £2.5.0 and 12 monthly	£17.4

AMPLIFIERS (STEREO)

Dulci AC202, Integrated	£12.12.0
Deposit £1.7.0 and 12 monthly	£10.8
Dulci GA505, Integrated	£18.18.0
Deposit £2.0.6 and 12 monthly	£11.11
Rogers Cadet Mk2, with Pre-amplifier	£26.15.0
Deposit £2.13.6 and 12 monthly	£22.4
Leak Stereo 20 Main amplifier	£30.8.0
Deposit £3.4.6 and 12 monthly	£210.3
Leak Variotone 111 Stereo Pre-amplifier	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.6
Quad 22 Stereo Control unit, Pre-amplifier	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.6

GRAMOPHONE UNITS

Garrard SRP10 with G.08 mono cartridge	£20.0.11
B.S.R. UA14 TC9 cartridge	£26.19.6
Deposit £1.0.0 and 6 monthly	£13.3
Garrard Autoslim Mono	£17.17.0
Deposit £1.0.0 and 7 monthly	£12.6
Garrard Autoslim De Luxe Mono cartridge	£11.9.0
Deposit £1.8.6 and 9 monthly	£14.9
Phillips AQ1016 with stereo cartridge	£12.12.0
Deposit £1.7.0 and 12 monthly	£10.8
Decca Deram Arm only	£5.5.0
Decca Deram Transcription cartridge	£4.14.6
Decca Deram Auto cartridge	£3.13.8
Goldring GL83, with arm, less cartridge	£15.19.8
Deposit £1.12.0 and 12 monthly	£16.6
Goldring '58' Transcription, no pick up	£17.14.0
Deposit £1.19.0 and 12 monthly	£19.0
Goldring GL85 as GL83 but less P.U. arm	£13.1.7
Deposit £1.7.7 and 12 monthly	£11.6
Garrard 4EF with Mono cartridge	£17.0.0
Deposit £1.14.0 and 12 monthly	£12.6
Garrard Lab: Type 'A' Auto-changer, Mono	£19.14.9
Deposit £1.19.6 and 12 monthly	£12.9
Garrard 301	£20.12.2
Deposit £2.3.2 and 12 monthly	£14.0
Garrard 301 Strobe	£22.0.0
Deposit £2.4.0 and 12 monthly	£16.8

LOUDSPEAKERS

Goodmans Ariette 8	£5.5.7
Goodmans Axiom 10	£6.5.11
Goodmans Axiom 201	£10.7.0
Deposit £1.1.0 and 8 monthly	£1.5
Goodmans 512/30 30 watter with cross over	£7.0.0
Wharfedale RS12/DD 12 in. full range	£11.10.0
Deposit £1.7.6 and 9 monthly	£14.9
Whiteley Electrical W.B. H.F. 1012 10 in.	£4.7.6

48 SURBITON ROAD, KINGSTON UPON THAMES, SURREY

Established over 30 years

Telephone KIN 5549

We pay all postage and insurance. All orders despatched same day. Money refund guarantee.
Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday). We do not close for lunch. Open all day Saturday.

"ROAMER-7 MK. II" (5 Wavebands)

PERFORMANCE WILL AMAZE YOU!

★ (7 Transistor plus 2 Diode design)

★ Med/Long Waves, Trawler Band and 2 S.W. to approx. 17 metres.

★ Rich-toned heavy duty 5in. Speaker.

Total cost of parts **£7.9.6** P.P. 5/6.

★ Fine for car radio use.

Less case and dial £5.19.6. P. & P. 3/-

★ Telescopic aerial for S. Waves & T.B.

★ FERRITE ROD AERIAL FOR M/L

★ Push-Pull output for room filling volume.

★ Full After Sales Service.


★ Simulated hide case saddle stitched, with golden trim and with shoulder & hand straps.

★ Air spaced ganged Tuning Condenser.

★ Case size 9 x 7 x 4in. approx.

★ No alignment problems.

★ Parts price list and data 3/-.

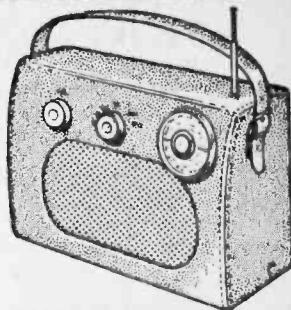

THE SUPER SEVEN

★★ (7 Transistors plus 2 Diodes)

★ 2 R.F. STAGES.

★ Coverage of Medium, Long Waves, Trawler Band.

★ Telescopic aerial for Trawler Band.

★ Use as domestic radio, car radio or fit with strap for carry-about.

★ No aerial required.

★ 3-inch speaker but will drive a larger speaker.

★ Push-Pull Output.



SIZE: 7½ x 5½ x 1½in.

May be built for **£6.5.0** plus 3/6 post, etc.


PARTS PRICE LIST AND EASY BUILD PLANS 2/-

NEW TRANSONA-6

★ (6 Transistors, plus 2 Diodes, 8-Stage)

★ MW/LW

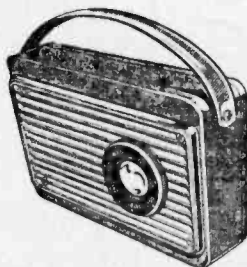Powerful magnet 3in. high grade speaker. Push-pull transformers. This is a top performing receiver. Many stations listed in one evening including Luxembourg loud and clear. A pleasure to listen to. **FERRITE ROD AERIAL.** All parts sold separately, grille in red. Uses 9 volt battery.



Total building cost: **£3.19.6** P.P. 3/- . Size 6½ x 4½ x 1½in.

"Luxembourg as loud as local. Your easy build diagram helped a lot... my first attempt."—H. S., Penzance, Cornwall (poor reception area).

PARTS PRICE LIST AND EASY BUILD PLANS 1/6

All components used in our receivers may be purchased separately if desired.

AFTER SALES SERVICE

Radio Exchange Co.

27 HARPUR STREET, BEDFORD


Phone: 2367

10 a.m.—1 p.m. Sat. Opp. Co-op.

"POCKET-5"

MW/LW and TRAWLER BAND (7 Stages)
(5 Transistors, plus 2 Diodes)

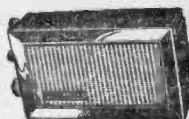Designed round supersensitive **FERRITE ROD AERIAL** and fine tone moving coil speaker. Attractive case in black with speaker grille in red. On test, Home, Light, Radio Luxembourg and many Continental stations were received.



Total cost of all parts required **£2.19.6** P.P. 3/-.

EASY BUILD PLANS AND PARTS PRICE LIST 1/6

PUSH-PULL FIVE

(5 Transistors, plus 2 Diodes, 7 Stage)

★ 2½in. Super-tone Loudspeaker.

★ Ferrite rod aerial.

★ Tuning condenser.


★ Volume control.

★ Case with speaker grille in red.

★ Fully tunable over med/long waves.

★ Simple assembly diagrams.

★ Push-pull output.

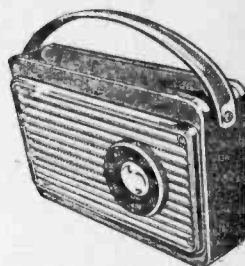

Can be built for **59/6** P.P. 3/-.


★ PARTS PRICE LIST, etc., 2/-.

"Home, Light, AFN, Lux., all at good volume."—G. P., Durham.

"ROAMER-7 MK. I"

5 Wavebands
(M/L, T.B. and 2 S.W.)

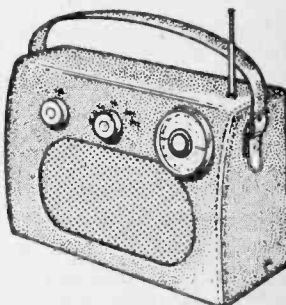Uses 6 top grade transistors plus 2 diodes. 5in. Speaker. Ferrite rod aerial for sensitivity. Telescopic aerial for short waves. Handsome case with gilt fittings size 9 x 7 x 4in. approx. Listen to stations half a world away.



Total cost of parts **£6.19.6** Post & Packing 5/6.

Plans, parts price list 3/-.

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let I.C.S. tuition develop your talents and help you to success.

STUDY IS EASY with I.C.S. guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

Take the right course now . . .

ADVERTISING
Gen. Advertising, Retail & Dept.
Store Copywriting.

ART
Oil & Water Colour
Commercial Illustrating

BUILDING
Architecture, Clerk of Wks., Buildg.
Constr. & Allied Trades, Quantity
Surveys.

CIVIL ENGINEERING
Highway Eng., Struct. Engrg.,
Concrete Engineering.

COMMERCE
Bookkeeping, Accountancy, Office
Training, Costing, Secretaryship,
Storekeeping
Shorthand & Typewriting

DRAFTSMANSHIP
Architectural, Mechanical, Matha.
& Machine Drawing
Drawing Office Practice
Structural Drawing

ELECTRONICS
Industrial Electronics
Computers & Maintenance

FARMING
Arable & Livestock
Farm Machinery Maint.
Pig & Poultry Keeping
Market Gardening

FIRE ENGINEERING
I.F.E. Examinations
Fire Service Promotion

GENERAL EDUCATION
Good Eng., Foreign Langs.
G.C.E. subjects at ordinary or
advanced level.

INTENSIVE COACHING for all principal examinations
including C.I.S., A.C.C.A., I.C.W.A., B.I.M., A.M.I.Mech.E.
Brit.I.R.E., I.Q.S., City & Guilds of London Institute,
R.H.S., P.M.G. Certificates in Radiotelegraphy, etc.
**MEMBER OF THE ASSOCIATION OF BRITISH
CORRESPONDENCE COLLEGES**

HORTICULTURE
Complete Gardening
Flower & Veg. Growing

MANAGEMENT
Business Management
Hotel Management
Office Management
Industrial Management
Personnel Management
Work Study, Foremanship

**MECHANICAL & MOTOR EN-
GINEERING**
Engineering Matha., Weldg.
Diesel Engines and Locos.
Inspection. Workshop Pract.
Refrigeration, Motor Mech.
Running and Maintenance (many
other subjects)

PHOTOGRAPHY
Practical Photography
P.D.A. Examination

POLICE
Police Entrance Exam.

RADIO, T.V. & ELECTRL.
Radio Servicing & Engrs.
Radio Constrn. (with kits)

SELLING
Commercial Travellers
Sales Mangnt, Ret. Selling

WRITING FOR PROFIT
Short Story Writing
Free-Lance Journalism

And many other subjects

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS
(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on . . .

Name . . .

Address . . .

Occupation . . .


7.63

INTERNATIONAL CORRESPONDENCE SCHOOLS

SPECIAL BARGAIN OFFER!

**RECORD
PLAYER
CABINETS**

Cabinet
Price
£33.30
Carr. &
Ins. 5/-

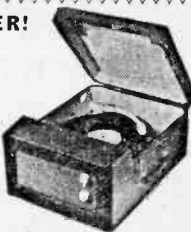

Contemporary style, rexine covered cabinet in Tan and Fawn/ Wine and Cream. Size 18 1/2 x 13 1/2 x 11 1/2 in. fitted with all accessories including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Uncut record player mounting board 14 x 13 in. supplied.

2-VALVE 2-WATT AMPLIFIER. Twin stage ECL82 with vol. and neg. feedback Tone control. A.C. 200/250v. with knobs, etc., ready wired to fit above cabinet, inc. 6 1/2 in. speaker and output transformer. £3.19.6. Carr. 2/6.

Comp. Record Player Kit Ditto Record Player Kit with B.S.R. UA30 Unit. Reduced Price **£12.10.0** Carr. 7/6 **£11.10.6** Carr. 7/6

BARGAIN RECORD PLAYER UNITS

Single Players Carr. 4/6
Garrard SRP10 5 gns.
Collaro "Junior" 65/-
B.S.R. Latest TU12 72/6
E.M.I. Junior "985" 67/6
Auto Changers Carr. 5/-
Collaro "C 60" £8.19.6
B.S.R. (UA14) £8.10.0
Latest Garrard Model A76 with
Transcription Arm. Plug-in
Head. Mono 9 gns.
Stereo 10 gns.
"Autoslim" Model £8.15.0

TRANSISTOR COMPONENTS

Condensers—150V. wgs. 0.01
mfd. to 0.04 mfd. 9d. 0.05 mfd.
0.1 mfd. 1/- 0.25 mfd. 1/3.
0.5 mfd. 1/6. etc.
Tuning Condensers. J.B.
"00" 208+176pF. 8/6. Ditto
with trimmers. 9/6. 385pF
single. 7/8. Sub-min. 1in.
DILEMIN 100pF. 300pF. 500pF
7/-
Midset Vol. Control with
edge control knob. 5kΩ with
switch. 4/9. Ditto less switch.
3/9.
Speakers P.M.—2in. Plessey
73 ohms. 15/6. 2 1/2in. Con-
tinental 8 ohms. 13/6. 7 x 4in.
Plessey 35 ohms. 23/6.
Ear Plug Phones—Min.
Continental type. 3Ct. lead.
jack plug and socket. High
imp. 8/- Low Imp. 7/6.

PRE-SET TV POTS. W/W 25
ohms-50 K. 3/- 50 K-2 Meg.
(Carbon). 3/-.

RECORDING TAPE—Reduced Prices

SYNCHROTAPE—High Fidelity Recording Tape. Bulk buying from a famous British manufacturer has at last made possible the marketing of a superior grade Recording Tape at greatly reduced prices. These new low prices enable us to offer Tape with all the quality and refinements previously found in more expensive brands. Leader and Stop Foils on all types (except 3in. size). Brand new, factory fresh and attractively cartoned. Unconditionally guaranteed.

Standard (PVC base)	Long Play (PVC base)	D'ble Play (Mylar base)
3in. 150ft. 3/9	225ft. 4/9	300ft. 6/6
4in. 600ft. 11/8	450ft. 9/8	600ft. 13/9
5in. 850ft. 14/8	900ft. 15/-	1200ft. 25/-
7in. 1200ft. 17/8	1800ft. 22/8	1800ft. 32/8
		2400ft. 42/8

Post and Packing—3in. Reels, 6d. Each additional Reel, 3d.

4in. to 7in. Reels 1/- Each additional Reel, 6d.

EMPTY TAPE REELS (Plastic): 3in. 1/3. 5in. 2/-. 5 1/2in. 2/-. 7in. 2/3.

PLASTIC REEL CONTAINERS (Cassettes): 5in. 1/8. 5 1/2in. 2/-. 7in. 2/3.

Terms C.W.O. or C.O.D. Post and Packing up to 4 lb. 7d. 1lb. 1/11.
3lb. 1/6. 5lb. 2/- 10lb. 2/9. Hours: 9 a.m. to 6 p.m.; 1 p.m. Weds.




**RADIO COMPONENT
SPECIALISTS**

70 BRIGSTOCK ROAD, THORNTON HEATH
SURREY, Est. 1946. Telephone: THO 2188

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI


- Peak output in excess of 1W.
- All standard British components.
- Built on printed circuit panel, size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET114 or 81 Mullard OC81D and matched pair of OC81 o/p).
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately.

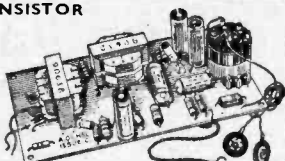

**SPECIAL
PRICE**
45/-
P. & P. 2/6.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded ultra output transformer to match 3-15 ohm speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL34s, 6XQ33, EF86 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).

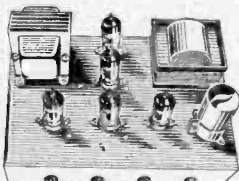

ONLY £6.19.6 P. & P. 6/6.

AMPLIFIER ON PRINTED CIRCUIT BOARD

Two valve, UY85, UL84 O.P. trans. use with 80 volt tap of motor. 38/6. P.P. 2/6 on above. Dropper res. for filaments if required. 2/6.

B.S.R. AUTO UNITS

160 v. Suitable for use with above. (Slightly soiled.) £4.1.0.

LARGE CABINET

Suitable for above two items. Complete with 3 ohm speaker. £3.9.8. Carr. 3/-.

Superior CABINET

Similar to above to take 8 x 5 in. speaker, with motor board will accommodate BSR UA14 or UA16. £3.9.8. Carr. 6/6. Speaker 15/- extra. P. & P. 1/6 extra.

UNREPEATABLE OFFER!
**BRAND NEW 8" x 5" 3 OHM
SPEAKERS**
By well known maker
10/6 each.
P. & P. 1/6 per speaker
A pair of these are ideal for Stereo

SPECIAL BARGAIN OFFERS!

MAINS TRANSFORMERS. Tapped Primary. 1/2 wave or Bridge Rectifier. Secondary 250 v. at 75 mA 6.3 volts at 2 amps. 10/6 each. P. & P. 3/-.

TWO GANG .0005 TUNING CONDENSER. Geared precision reduction ratio. Size 2 1/2 x 2 x 1 1/2 in. Brand new and unused. 3/6 each. P. & P. 1/-.

MAINS TRANSFORMER. Impregnated and fully shrouded. Size 4 1/2 x 2 1/2 in. Weight 6 lbs. Tapped primary 205, 225, 240v. Electrostatic screen. Output 360-0-360 v. at 120 mA D.C. plus 1050 v. half wave at 3 mA D.C. 6.3 v. at 3.5 amps centre tapped 5 v. at 21 amps and 6.3 v. at .6 amps. PRICE ONLY 21/- each. P. & P. 5/-.

CARBON MIKE INSERTS. Brand new, 2 1/2 in. dia., 3/8. P. & P. 9d.

ELECTROSTATIC H.F. TWEETERS. Type L.S.H. 75. Size 3 x 3 in., 2/6 each, plus 9d. P. & P.

MIDGET 2/GANG CONDENSERS. Capacity 195 and 100 pF. Polystyrene case with built-in trimmers. Size 1 1/2 x 1 1/2 x 1/2 in. Not used but removed from P/C Boards. Two for 9/-, plus 1/6 P. & P.

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6.

TSU CRYSTAL STICK MIKE. Listed at 45/-. Our price 18/6. P. & P. 1/6.

TRANSISTOR DRIVER and O/P TRANSFORMERS. (Tapped 3 ohms and 15 ohms output), plus 4 suitable Transistors giving approx. 1 watt output. 30/-. P. & P. 2/6.

3 PUSH-BUTTON TRANSISTOR SWITCH. D.P.—D.T. Each Switch 5/6 and 1/- P. & P.

FURTHER HUGE PURCHASE.
TELEFUNKEN HI-FI STEREO AMPLIFIER. 110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal). Size 12 x 9 x 2 in. Weight 9 lb. Complete with spec. and instructions. Now only £5.9.8. Carr. 5/-.

Also Model 882. Similar specification but with balance control. Now only £5.19.6. Carr. 5/-.

SPECIAL PURCHASE! TURRET TUNERS

by famous maker Brand new and unused. Complete with PC84 and PCF80 valves, 34-38 Mc/s I.F. Biscuits for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P.P. 2/6.

F.M. TUNER HEAD




A permeability tuned tuner head by a famous maker, supplied without valve (EC285) and drum and spindle, 18/6, plus 1/9 P. & P. Valve 8/6 extra. Drum and spindle 3/6 extra.

GÖRLER F.M. TUNER HEADS

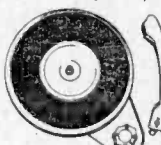10.7 Mc/s I.F. 15/-, plus 1/9 P. & P. (EC285 valve, 8/6 extra.)

E.M.I. 4-speed Player and P.U.

FURTHER HUGE PURCHASE enables us to offer these 67/6 4/6.



Heavy 8 1/2 in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 45 V for amplifier valve filament if required. Turnover LP/78 head.

RECORD PLAYER AMPLIFIER

2 valve (E280, ECL82), A.C. mains, 3 watts output, ready built, tested and complete with valves and output transformer. Size 7 in. w. x 2 1/2 in. d. x 5 1/2 in. h. 55/-. P. & P. 3/6. Suitable speakers: 6 in. 15/- or 10 x 6 in. 25/-. P. & P. 1/6 on each.

4-SPEED PLAYER UNIT BARGAINS


SINGLE PLAYERS
TU12, £3.10.0. Carr. 3/6.
AUTO CHANGERS
B.S.R. K. UA11, £8.2.6.
Latest B.S.R. UA16, £7.2.6.
Latest Garrard "Auto-Slim" £6.17.0. Carr. 5/- on each.

SPEAKER & CABINET FABRICS

Oatmeal fabric for speaker or cabinet or Red velvet for cabinet 6 1/2 in. wide, 13/6 per yard length. P. & P. 1/6.

HARVERSON'S F.M. TUNER Mk.I

● F.M. tuning head by famous maker. ● Guaranteed non-drift. ● Permeability tuning. ● Frequency coverage 88-100 Mc/s. ● OA81 balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3 in. glass). ● Self powered, using a good quality mains transformer and valve rectifier. ● Valves used ECC85, two EF80s, and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2 in. ● All parts sold separately. Set of parts if purchased at one time £5.19.6, plus 8/6 P.P. and ins. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 8/6.

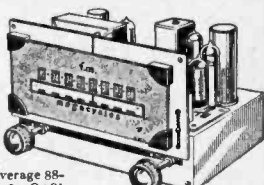

Mark III Version as above but with output stage (ECL82) and tone control. £7.7.0. P. & P. 8/6. Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/-, P. & P. 2/6. To fit Mark II, 17/6, P. & P. 2/6.

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2 in.) ● 3 pre-aligned I.F. transformers. ● High-gain ferrite rod aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions.

All parts sold separately Set of parts if purchased at one time.

ONLY £4.5.0 P. & P. 2/6

35 OHM SPEAKERS

Suitable for use with above. 2 in. Goodmans. Ideal replacement for most pocket portables 8/8; 2 1/2 in. 10/8; 3 in. 12/6; 5 in. 17/8; 7 x 4 in. 21/-.

P. & P. 1/6 per speaker.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 in. speaker. 25/-. P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and aerial coupling), 28/6 complete, post 1/6. 6 transistor printed circuit, board to match. 8/6, post 9d. Circuit diagram 1/6 extra.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (which is used in a 29 gn. record player) employs ECC83, EL84, E280 valves. Bass, treble and volume controls. On/off controls.

PRICE 69/6 P. & P. 3/6

DITTO. Mounted on board with output transformer and 6 in. speaker.

Complete at 89/6, P. & P. 4/6.

TRANSISTORS

GET15 (Matched Pair) 15/-
OC71 5/- FXA101 6/8
OC72 5/- XA103 6/8
OC76 6/- XA109 12/6
Set of Mullard 6 transistors, OC44, 2-OC45, OC81D, matched pair OC81, 25/-, All Post Free.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19. CHERRYWOOD 3985/6

Open all day Saturday.

Early closing Wed., 1 p.m.

A few minutes from South Wimbledon Tube Station.

(Please write clearly)

Please Note: P. & P. charges quoted apply to U.K. only. P. & P. on overseas orders charged extra. (S.A.E. all enquiries).

New 10th Edition Newnes Great Profit Maker!

COMPLETE IN
6 VOLUMES



Radio & TV Servicing

DATA FOR MODELS RIGHT BACK TO 1956

This latest, 10th Edition provides all the technical information you need for quicker repair work now and for years ahead! It gives you full servicing data and specialist repair methods for the popular models marketed by 70 principal makers and companies—current models and back to 1956. It is essential to the shrewd repair man because people are keeping their sets longer. If you have never before examined this famous reference work now is your opportunity. See the latest edition for a week on free examination without obligation to buy.


TELEVISION · RADIO · RADIOGRAMS · CAR RADIOS
TAPE RECORDERS · RECORD REPRODUCERS

DATA FOR ALL THESE MAKES—Alba, Ambassador, Argosy, Armstrong, Baird, Beethoven, Berec, Brayhead, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansetta, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Emerson, E.M.I., Emisonic, English Electric, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphona, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Sony, Sound, Spencer-West, Stella, Stereosound, Strad, Ultra, Vidor, Walter, Webcor. Includes 50-page supplementary section of older models.

PLUS 2 YEARS' FREE POSTAL ADVISORY SERVICE

More than 4,000 Circuits and Component Layout Diagrams · 2,250 Popular Models

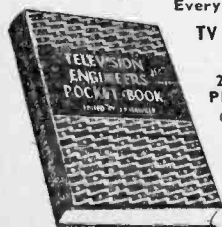Use it **FREE** for 7 days
to prove its value



Every purchaser receives a Free copy of
TV ENGINEERS POCKET BOOK
(Value 12/6)

272 PAGES · OVER 200
PRACTICAL ILLUSTRATIONS

Concise information on installing,
fault-tracing and repairing, ser-
vicing equipment, alignment, etc.

An invaluable companion to
your set for on-the-spot repairs
Hurry - Post Coupon To-day

George Newnes Ltd., 15-17 Long Acre, London, W.C.2.
Send me Newnes RADIO AND TELEVISION SERVICING (in 6 volumes) and TV ENGINEERS POCKET BOOK without obligation to purchase. I will return them in 8 days or send 15/- deposit 8 days after delivery, then twenty monthly subscriptions of 15/-, paying £15. 15s. in all. Cash price in 8 days is £15.

Name and Address in block letters please

Mr., Mrs., Miss _____

Address _____

Occupation _____

Signature _____

Parent's Signature if you are under 21. { Mr. _____
Mrs. _____

Tick V where applicable

The address on left is —

My Property ☐

Rented unfurnished ☐

Parents' Home ☐

Furnished Accom. ☐

Temporary Address ☐


(RV)533/65

SPECIAL OFFER PRINTED CIRCUIT AM-FM CHASSIS AT ONLY £9

A small quantity of Printed Circuit chassis by famous manufacturer Valves UY85, UCH81, UF89, UAB80, UL84 and UOX85. O.n. traps for 2-3 ohm speaker. Chassis 14 x 7 x 7in. Front controls concentric, left—Vol. and Tone; right—W/c and Tuning "Gold" centre knobs provided. 2-dial bulbs. Sockets. A.E. E; Ext. sp; P.U. Mains isolating transformer free. Covers Long, Med., V.H.F. (87-101 Mc/s). Unused, slightly tarnished, but not dirty. New Mullard Valves. Dial in gold and brown, size 13 x 3 1/2in.

THIS SUPERB SET for £9

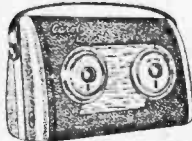6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades, M.W. and L.W. ferrite rod, provision for car aerial, 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7 1/2in. high x 4 1/2in. at base tapering to 2 1/2in. at top. Brand new, fully guaranteed.



SUPERIOR GRAMOPHONE AMPLIFIER

Valves UY85, UF80 and UL84. Mains trans. 200-240 a.c. Covered baffle 13 1/2 x 7 1/2in. (6 1/2in. speaker); 3 front controls bass, treble, on-off/vol. 74/- (post 4/-). Resine cabinet to fit, with carrying handle, and lid (detachable) 14in. 10/- extra.

5 WATT AMPLIFIER

Our price ONLY 56/- (post 4/-); NEW MANUFACTURE; valves EF91 and EL84 with metal rectifier; 8 x 4 x 1 1/2in. high (5in. over EL84). Mains trans. and o.p. with vol. and tone controls; on/off; co-ax input.

COLIARO STUDIO TAPE TRANSCRIBER, 3 MOTORS. 3 SPEED. 1 1/2, 3 1/2 and 7 1/2 I.P.S. Push buttons, £10.7.6 (10/- carr.) inc. spool.

BATTERY ELIMINATOR


For 4 Low Consumption Valves (96 range) 90v. 15mA and 1.4v. 125mA, 45/- (2/6 post). 200-250v. A.C. Also for 250mA, 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries.

BATTERY RADIO

Valves DK96, DF96, DAF96, DL96. Two Short Wavebands 16 to 49 M, and 25 to 75 M. Size 10 1/2 x 4 1/2 x 8in. 24.7.6, carr. paid. M.W. and S.W. £4.11.0, carr. paid.

MAINS OPERATED RADIO CHASSIS AND AMPLIFIER OF FAMOUS MANUFACTURE

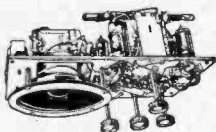Chassis 10 x 5 1/2 x 4in. front to back. Valves: UB41, UCH41, UF89, UL84 with metal rectifier. 8in. speaker. Ferrite rod aerial. Tone, vol. and gram. position. Covers L. and M. waves. Limited quantity at only £8 (5/- carr.) complete with small dial. Unused and in working order.



TRANSISTOR SET BATTERY ELIMINATOR. Converts your 6 transistor receiver to mains operation. With flex lead and battery charging attachment. For Miniature Sets, size 1 1/2 x 1 x 1 1/2in. Price 18/6. For Larger Sets, 3 x 1 1/2 x 1 1/2in. Price 24/6.

TRANSISTOR COMPONENTS

M.W. and L.W. ferrite rod aerial, with car coupling coil. For 200pF condenser, 6/-; One coil, 12/- and 3rd 1/2 P.F., all 4/6 ea.; Driver trans. 6/-; min. 64mF 10v.; 10mF 16v.; 100mF 9v.; all 1/3 ea.; Tuning cond. 208mF +170pF 8/6; post 9d. on all orders.

GRAMOPHONE AMPLIFIER

With 5in. SPEAKER Baffle 12 1/2 x 6in. ECL82 and Rectifier, Tone and Volume On/Off switch. Two Knobs. Ready to play. Useful for Stereo. ONLY 57/-, post 4/-.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIERS




PRINTED CIRCUIT. 5in. x 2in. x 1 1/2in., over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and radio input. 9-12 volt battery required. Frequency range 100 c/s. to 20 Kcs. Push/pull output. Instruction sheet provided. Fully wired ready to use. Two types available, 1W output. 35/-, 1 1/2 watts 41/-, P. & P. 2/6.

TOP QUALITY RECORDING TAPE (Guaranteed)


(1/- per tape, six or more post free)					
4in. ..	600ft. ..	12/8	5 1/2in. ..	1200ft. ..	17/6
5in. ..	600ft. ..	12/8	5 1/2in. ..	1800ft. ..	35/-
5in. ..	900ft. ..	17/-	7in. ..	1200ft. ..	17/8
5in. ..	1200ft. ..	30/-	7in. ..	1800ft. ..	26/6
8 1/2in. ..	850ft. ..	15/-	7in. ..	2400ft. ..	45/-

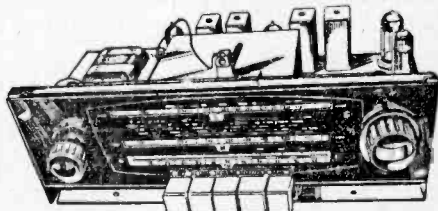BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £12.12.0 (Carriage Paid)




A.C. ONLY. Chassis size 13 x 6 1/2 x 5 1/2in. high. New manufacture. Dial 14 1/2 x 4in. in 2 colours, predominantly gold. Pick-up Ext. Speaker. Ac. E. and Dipole Sockets. Five push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.; 200-500 M.; 88-98 Mc/s. Valves EZ80 rect.; ECH81, EF90, EAB80, EL24, EOX85. Negative feed-back circuit. Speaker and Cabinet to fit chassis (table model). 47/6 (post 8/-). 9 x 6in. ELLIPTICAL SPEAKER, 20/-, to purchasers of this chassis. TERMS: (Chassis) £3.10.0 down and 5 monthly payments of £2. Cheap Room Dipole for V.H.F.. 12/6. Feeder 6d. yd. Circuit diagram 2/6.

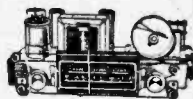SELF-POWERED VHF TUNER CHASSIS. Covering 88-90 Mc/s. Mullard permeability Tuner. Dims. 10 1/2 x 4 1/2 x 5in. high EOX85 and 3—EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.7.0 (carr. paid). Room dipole 12/6 Feeder 6d. yd.



PUSH-PULL AMPLIFIER £5.5.0 (5/- Carr.)

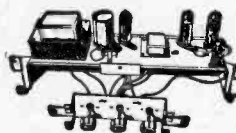

Brand new 200-240 A.C. mains. Bass, treble and vol. controls. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3 1/2 x 4 1/2in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel." Stereo version 2 x 4 w., same price. Fixed panel. Tone & Vol. Controls.

TAPE RECORDER AMPLIFIER




Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1 1/2in. Height 5 1/2in. overall. Front to back 5 1/2in. Vol. and on/off tone. Mike, radio and ext. speaker jacks. Valves ECC83, ECL82, EZ80, plus DM70 (magic eye). Mains trans. Ready to bolt to B.S.R. Deck. Complete with switch water wired. Our Price ONLY £8.15.0 (6/- Packing and Carr.). Also available for Coliario Deck at 5/- extra.

6-TRANSISTOR KITS AND SETS


All brand new parts. Rexine and Vynair Cabinets. Different colours. All holes drilled in printed circuit boards. Full M.W. and L.W. coverage. Car aerial socket. Alignment service, 17/6, inc. return post. All parts supplied separately. Built in 2 1/2 hours. 500 mW. output. Booklets 2/6, refunded on purchase of kit.

THE "SCALA"

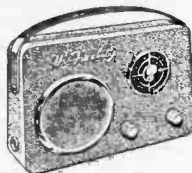

"Scala" Kit £4.19.6. (Post 3/-). Size 8 1/2 x 2 x 5 1/2in. high and 3 1/2in. speaker; or fully built £7.10.6.

THE "MILAN"

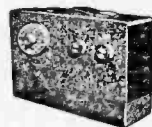

"Milan" Kit £5.17.6. (Post 3/6). Size 9 x 3 1/2 x 7in. with 8 x 2 1/2in. speaker

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH.

Terms Available on Items over £5. Send 6d. (stamps will do) for 20-page illustrated catalogue. Delivered by return C.O.D. 2/- extra.

ALL ITEMS GUARANTEED 12 MONTHS

VALVES 3 MONTHS

GLADSTONE RADIO

"SCALA", CAMP RD., FARNBOROUGH, HANTS.

Farnborough 3371

FARNBOROUGH CLOSED SATS.

Practical Wireless

Vol. XXXIX No 677 JULY, 1963

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House,
Southampton Street, W.C.2.

© George Newnes Ltd., 1963

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland	£1.9.0 per annum
Abroad	£1.7.6 per annum
Canada	£1.5.0 per annum

Contents

	Page
Editorial	213
Round the World of Wireless	214
The Malvern Tape Recorder	216
Local Station F.M. Receiver	220
Switch-tuned Radio/ Amplifier	227
Semiconductors	230
Magnetic Pickup For an Acoustic Guitar	235
Pocket Signal Injector	236
7-Valve Stereogram	240
More About Cathode Followers	244
Test Gear Techniques	249
On Your Wavelength	258
Double Conversion Commu- nications Receiver	261
Trade News	269
Club News	273
Books Reviewed	274
Letters to the Editor	277

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless".

Keys to Success

WHY can Joe Brown construct an elaborate piece of equipment which looks like a professional product, while Jack Smith gets tied up in knots trying to build a simple three valver?

No doubt some have electronic "green fingers", but the reason is usually less fanciful. Also, of course, experience plays its part. And the fact that some learn faster than others. But disregarding the particular for the general, there are several important reasons for the wide divergence in constructional skill and the results obtained.

(1) Tools. There is a bare minimum of tools without which the enthusiast should not embark upon any regular constructional work. These should be maintained in optimum condition, and added to when the need arises and finances permit.

(2) Test Gear. The amateur does not have to equip a laboratory, but he should obtain as early as possible certain basic essentials, such as a reliable test meter. To contemplate serious constructional work without even this indispensable item can only lead to frustration and disappointment.

(3) Theory. It is not necessary to be an academic genius to get fun out of our hobby, but if one is to be versatile and progressive, a good basic working knowledge is essential.

(4) Patience. This attribute is not always easy, when one is keen, but it should be cultivated. It is, for instance, courting trouble to attempt a communications receiver after having only built one or two portables.


(5) Confidence. This may be even more difficult! But with reliable tools, some testing equipment and a working knowledge of theory, the enthusiast is half way home. But the real key is the willingness and ability to *experiment*.

Having built one or two pieces of equipment from the magazine point-to-point wiring diagrams, the newcomer should attempt one or two simple items using only the theoretical circuit diagram.

Mistakes would be made, but mistakes are the food on which knowledge grows and soon the newcomer would gain the confidence to plan his own layouts.

We know that some readers, even after many years of building, still prefer everything planned for them, and we shall continue to cater for them. But for those who wish to progress, the moral is the well used but true phrase: there is no substitute for experience. The keys to success are there—ready to open the doors to advanced construction—for those with the confidence to try.

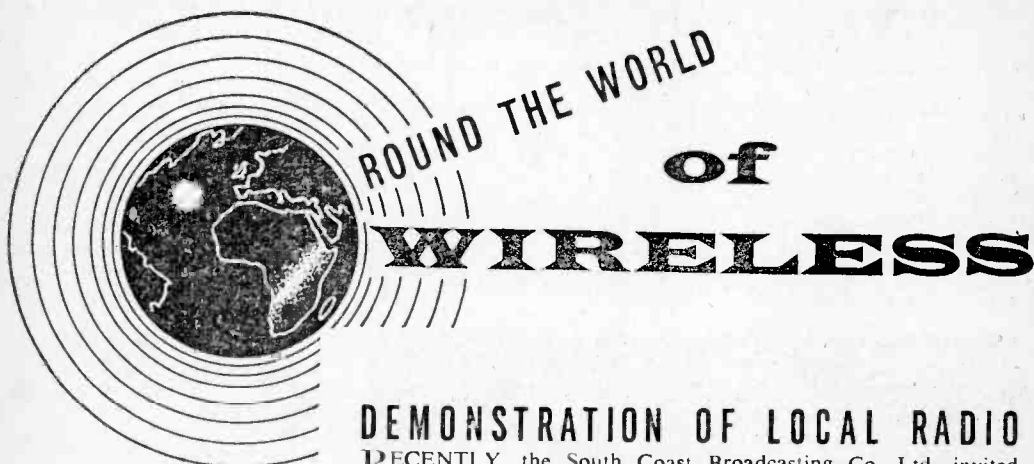Our next issue dated August will be published on July 5th



NEWS AT HOME AND ABROAD

EQUIPMENT AT PARIS AIR SHOW

AT this year's Paris Air Show, Marconi's Wireless Telegraph Company Limited are exhibiting a full range of their products designed for aeronautical use. The Sixty Series radio equipment will be a feature of the display, as will their new "daylight radar display".

The exhibit also includes the type AD722 lightweight radio-compass and a navigation computer and display unit.

Electronics in the Navy

THE growing importance of electronics and the increasing need for electrical specialists, was underlined recently when the Admiralty announced that more electrical officers will be required for each new warship that is commissioned. This is because of the increased complexity of the electrical equipment which is included in the Navy's new ships.

As a result, new regulations are to be introduced governing the entry of electronic specialists into the service and also a system whereby officer entrants will be given seniority "credits", based on their previous experience in outside industry and also for their academic qualifications.

In many new ships now coming into service, electrical and electronic equipment installed may well account for up to 50% of the total cost of the warship, and these ships may now expect to carry three or four times as many electrical officers as earlier vessels.

DEMONSTRATION OF LOCAL RADIO

RECENTLY, the South Coast Broadcasting Co. Ltd. invited the public to a demonstration of local independent radio at its headquarters at Castle Goring, Worthing. For six days features of the demonstration included local news and events, music and record request programmes, weather and traffic information.

When the Pilkington Committee on broadcasting was studying the possibility of the introduction of local commercial radio, S.C.B.C., whose programme controller and managing director is Mr. Ian Collins, was the only independent company to present trial local programmes.

Proposed programmes would be devoted to all local affairs and would include regular school's broadcasts. Also planned by the company is a night service.

Contributions towards the demonstration programmes came from many local bodies, including the police, schools and civic authorities.

Radio Equipment for new Transport Planes

WHEN the Royal Air Force Transport Command has completed its latest re-equipment programme, three new types of aircraft will be seen for the first time in R.A.F. colours. The three types of aircraft—the Vickers VC10, the de Havilland DH125 and the military freighter version of the Avro 748—will all be fitted with the Marconi Sixty Series of aircraft radio equipment.

In both the VC10's and the 748's, dual installations of Marconi v.h.f. communications systems and v.h.f. navigation systems have been specified. In the DH125's, single installations of both systems are required.

The Sixty Series equipment will also be installed in a number of aircraft already in service with the R.A.F.

RECTIFIERS FOR NEW POWER STATION

FOUR sets of silicon rectifier equipments have been ordered from Westinghouse Brake and Signal Company Ltd., for use in the excitation of four 500MW generators which are being built for the Central Electricity Generating Board's Ferrybridge "C" power station. The order, which was placed by C. A. Parsons and Co. Ltd., is worth £64,000.

Westinghouse silicon rectifiers will be used extensively for the large generators recently ordered under the C.E.G.B.'s current plans to expand electric power generation.

SOLID STATE CIRCUITS ON SHOW

FOR years electronic components have been getting smaller and smaller until they can be made no smaller and still remain as single items. The next logical step has been taken already and among other exhibits, Ferranti Ltd. showed some of their developments in silicon solid state integrated circuits, at this year's Radio and Electronic Components Show,

which was held recently in London.


The techniques used in the production of these circuits enables a number of planar silicon transistors (or diodes) and resistors to be contained within one or two tiny pieces of silicon and to be sealed in an encapsulation of reduced dimensions which would normally hold but one transistor! The circuit illustrated,

for example, is a ZLAIA linear amplifier from the "Microlin" range of elements. Contained in this eight-lead encapsulation, which measures only 0.36in. in diameter and 0.18in. in height, is a silicon integrated circuit consisting of six resistors and two transistors.

These integrated circuits are manufactured by producing a number of separate minute regions which function as components (resistors, capacitors, diodes or transistors) within one or more pieces of semiconductor material. The regions are interconnected by evaporated layers in the basic material, and isolated by p-n junctions. Connections to other circuits lead off from the case, and the complete circuit is hermetically sealed in a metal container which provides a stable environment and ensures a high standard of reliability.

Ferranti Ltd., have concentrated on the development of this technique for two separate functions — linear amplification and high speed logic circuitry — and demonstrations of both types of circuits were included on their stand.

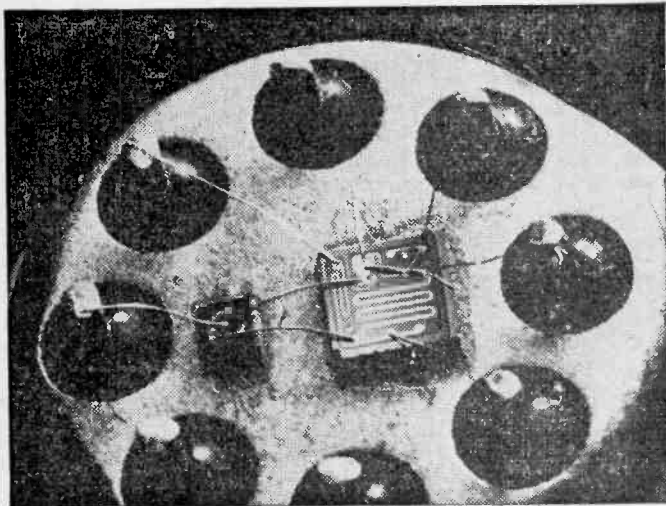This photograph shows a Ferranti silicon integrated circuit magnified 20 times.



Aerials for New Forfar V.H.F. Station

AS a result of their decision to go ahead with the plans for a new transmitting station near Forfar, Angus, the BBC has placed an order with EMI Electronics Ltd. for the supply and erection of the v.h.f. and TV aerials. This station will improve reception and extend the coverage of television and radio programmes in East Scotland.

The v.h.f.-f.m. aerial will be mounted below the television aerial on the mast, and will transmit the Home, Light, Third and Network Three programmes in Band II. This array, which will be horizontally polarized, will include eight stacks of unipoles, mounted on the north-west and south-west corners of the mast.

VENEZUELAN MINISTER TOURS WOOLWICH FACTORY

AS part of his tour of Standard Telephones and Cables, Woolwich factory, Sr. Ingeniero Pablo Miliani, saw the workshop where repeaters for undersea telephone cables are made. In this dust-free, air conditioned workshop, where everyone entering wears special clothing to prevent contamination, the repeaters are constructed to operate continuously for more than 20 years on the sea bed.

Sr. Miliani, who is visiting Britain at the invitation of the President of the Board of Trade, also inspected the production of microwave radio link equipment for carrying large numbers of long-distance telephone circuits and television channels.

Three Brands of Valves on Show



AT this year's R.E.C.M.F. exhibition, Thorn-AEI Radio Valves and Tubes Ltd. made their first ever appearance. On their one stand they exhibited three brands of valves—Mazda, Ediswan and Brimar.

The Brimar valves were mainly of the entertainment equipment type, although range of low power industrial and professional types was also on show.

Entertainment valves and c.r.t.'s were the types exhibited under the Mazda brand-name, and of special interest was the newly developed television valve 30C18 (PCF805).

The Ediswan brand represented the overseas sales of Mazda valves, but also included was a selection of industrial valves.

THE MALVERN TAPE RECORDER

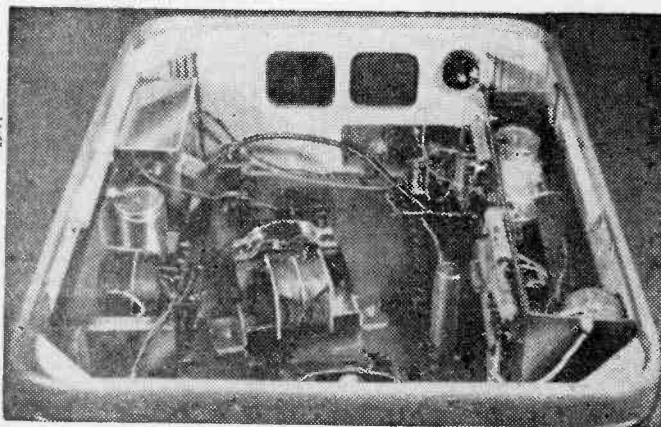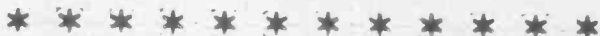

By
T. Snowball

THIS is a mains driven tape recorder using semiconductors throughout and is based on a design by G.E.C. in their application report No. 24.

The design as given here is matched to the small loudspeaker contained within its portable cabinet, but with a few modifications the recorder can be designated Hi-Fi and will drive larger external loudspeakers such as in a permanent installation. The specification gives 2 watts output from a transformerless output stage feeding a 3Ω loudspeaker, with a frequency response of up to 6kc/s at 3½in./sec. using a B.S.R. Tapedeck.

The supply circuits were designed to run from a 12V mains-derived power supply so that if a d.c. motor, or a transistor inverter for the motor, were used the unit could be operated from batteries.

The audio output from a radio tuner can be applied to the input of the recorder—which will then provide high quality amplification with a frequency response from 30c/s to 30kc/s.

The complete circuit diagram is given in Fig. 1. The first pair of transistors (Tr1, Tr2) are in a feedback circuit, the frequency response of which can be readily altered in order to compensate for recording or playback, according to the setting of the function switch S1.

The third transistor Tr3 is used as an additional amplifier with a treble boost network in its collector circuit.

The combined driver/output stage (Tr4-Tr8) delivers 2W to a 3Ω loudspeaker without the use of any transformers, thus giving extremely

good frequency response, with very little phase shift. The output stage also drives the recording head via a transformer (T1) and series resistor.

The erase and bias oscillator is separate and is built in a screened box to prevent radiation. It provides 2 watts at 60kc/s.

The current consumption varies from 12 to 300mA on playback, and from 300 to 500mA on record.

THE MAGNETIC RECORDING PROCESS

A few words on tape recording requirements will probably help some constructors.

The aim of recording on magnetic tape is to record the signal as large as possible without excessive distortion; and constant in amplitude throughout the entire frequency range. This is the condition that gives the largest playback signal and so gives the best signal to noise ratio for the recording process.

So at first look it appears that because the magnetic field is proportional to ampere-turns, the need is a constant current through the record head for all frequencies. This is indeed what is done in the output stage as described below.

As the recording head is an inductor its impedance XL will rise steadily with an increase in frequency.

$$XL = \frac{1}{2\pi fL}$$

So for the head on the B.S.R. deck where L approximately equals 400mH, XL at 50, 500 and 5,000c/s is 100Ω, 1kΩ and 10kΩ respectively. So in order to keep a constant recording current flow-

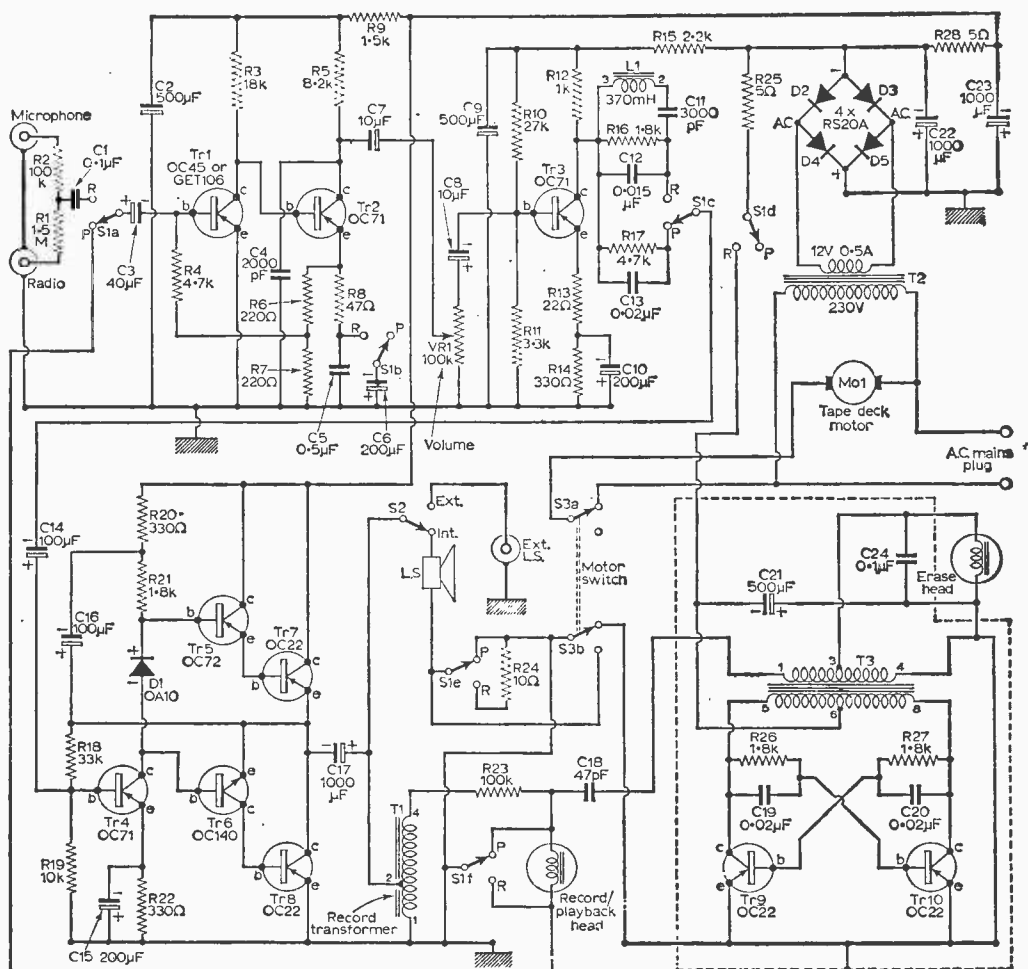


Fig. 1: The complete circuit of the recorder.

ing for, say 15V r.m.s. output at all frequencies, it is normal to feed the head through a large resistor. In this case a 100k Ω resistor is used; thus at 50, 500 and 5,000/s the total impedance is 100,100 Ω , 101,100 Ω and 110,000 Ω , making of course for all practical purposes a constant current of 150 μ A.

Unfortunately this simple expedient is not the whole answer to recording, because as the frequency is raised, the losses in the tape and head increase sharply. So in order to keep the recorded signal constant at the top audio frequencies, the amplifier stages boost these frequencies by as much as four times or 12dB. The exact figures of boost, and the frequency at which it occurs, vary with different types of head and with tape speeds. But with the B.S.R. deck and small loudspeaker this circuit gives 6dB at 5kc/s. The actual response is shown in Fig. 2.

Playback, having once recorded the tape, is also somewhat difficult.

As the recorded signals go past the playback

gap, the voltages induced head are proportional to the number of cycles per sec. that go past. So at low frequencies the output will be much smaller than at high frequencies. If all were perfect then the output would rise linearly all the way; that is, the output should double for each doubling in frequency, or to state this in the more conventional manner, rise at 6dB per octave.

But once again at high frequency the output drops due to eddy currents in the head, spacing between head and tape, head gap width, etc. So instead of rising all the way, after about 1kc/s the output remains constant within 3 or 4dB, up to 5kc/s.

So the required playback response needed is shown in Fig. 3.

The erase and bias oscillator also comes into the recording story, in that as an erase oscillator it saturates the tape with a very strong signal at 60kc/s as it passes under the erase head. And as the tape moves away from the head the field slowly reverses on each half cycle of oscillation,

until it decays away to zero, leaving the tape "empty" and noise free. Considering the function of the bias oscillator, a simple explanation of a complicated subject is that the oscillator moves the point of magnetisation of the tape, so that the audio signals are recorded without distortion.

The final result of all these adjustments would be to give a constant output voltage to the loudspeaker on playback, from 50c/s to 5kc/s, if a constant voltage at all frequencies were fed into the recording amplifier.

The various ways in which these operations are carried out in this tape recorder will now be described.

mum efficiency, types which oscillate easily at 60kc/s, without excessive loss, are necessary. Mullard OC22 or G.E.C. GET116 are most suitable.

Indication that all is well is the existence of approximately 25V r.m.s. across the erase head. Read this on the a.c. range of a good voltmeter with extended h.f. response, such as the *Practical Television Testmeter*, Oct., Nov. '61; or a valve voltmeter. Otherwise, if the current consumption is 300-400mA at 10-12V the circuit is probably working correctly.

The overwind on the transformer for the bias supply gives 400V r.m.s. output and is applied through a small capacitor to the recording head. This is in order to allow variation of bias current by means of varying the capacitor, and at the same time to allow a small value of "C", thus avoiding a heavy load on the oscillator or shunting of the audio signals which are being applied to the head, at the same time.

The usual bias current is normally between 0.4 and 1.2mA, and with the value of C18 at 47pF will give about 1mA, but variations can occur mainly due to the screened leads absorbing the power.

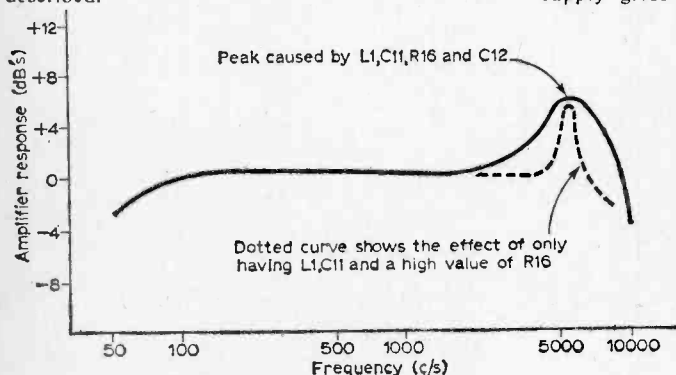


Fig. 2 (above): The record response curve.

Fig. 3 (right): The playback response curve.

THE RECORDING CIRCUIT

Bias and Erase Oscillator


As the tape passes through the recorder it is first erased by the sine wave oscillator consisting of Tr9 and Tr10 which are connected together in a class "C" condition. The transformer T3 connected in the collector circuit of Tr9 and Tr10 has a secondary winding which feeds the erase head and also the recording head (bias) via a small capacitor C18.

The oscillator operates at approximately 60kc/s and the erase head and transformer T3 are tuned by the 0.1μF capacitor C24 to increase the erase current in the head.

As mentioned in the G.E.C. report, the transformer can be purchased from various companies, i.e. Belclere TF2547, Colne Electric 06042, Parmeko P3007. However, it is easy to construct on a Mullard LA2 or G.E.C. GA110B ferrite core, and winding details will be given later.

As this circuit is, effectively, quite a powerful transmitter on 60kc/s, it is suggested that construction is carried out in a screened box: otherwise the main amplifier can be saturated because of stray pick-up.

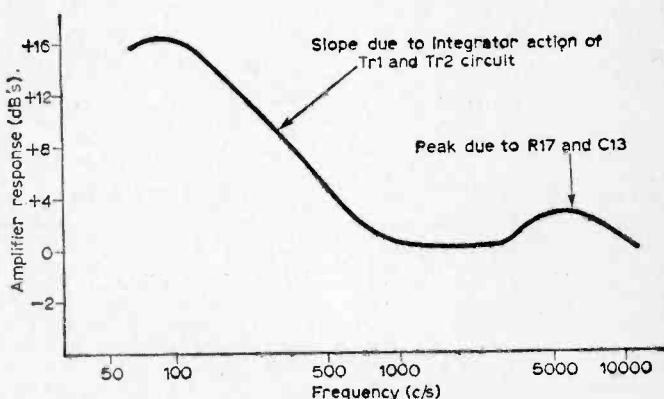Various transistors can be used, but for maxi-



After erasure the tape passes the recording head, when the bias affects it, as previously described. At this point, the audio signal currents are added in via the head transformer T1, and series resistor R23.

Record Head Transformer

This head transformer T1 can be wound on an LA1 or GA110A ferrite core, as will be described later. Alternatively it can be purchased as Belclere TF2550, Colne 06040 or Parmeko P3005. It is best situated near the Record/Playback switch and bias oscillator, in order to ensure that leads with higher voltages are kept short.

COMPONENTS LIST

Resistors:

R1	1.5M Ω	R13	22 Ω
R2	100k Ω	R14	330 Ω
R3	18k Ω 5% H.S.	R15	2.2k
R4	4.7k Ω 5% H.S.	R16	1.8k
R5	8.2k Ω 5% H.S.	R17	4.7k
R6	220 Ω 5% H.S.	R18	33k
R7	220 Ω 5% H.S.	R19	10k
R8	47 Ω	R20	330 Ω
R9	1.5k	R21	1.8k
R10	27k	R22	330 Ω
R11	3.3k	R23	100k
R12	1k	R24	10 Ω
R25	5 Ω $\frac{1}{2}$ W or 2 x 10 Ω in parallel		
R26	1.8k	R27	1.8k
R28	5 Ω or 2 x 10 Ω in parallel		

All $\frac{1}{2}$ W, 10% carbon, unless otherwise stated.
VR1 100k Ω potentiometer

Capacitors:

C1	0.1 μ F paper 200V
C2	500 μ F electrolytic 12V
C3	40 μ F electrolytic 3V
C4	0.002 μ F paper 100V
C5	0.5 μ F paper 100V
C6	200 μ F electrolytic 3V
C7	10 μ F electrolytic 10V
C8	10 μ F electrolytic 10V
C9	500 μ F electrolytic 10V
C10	200 μ F electrolytic 3V
C11	0.003 μ F paper 100V
C12	0.015 μ F paper 100V
C13	0.02 μ F paper 100V
C14	100 μ F electrolytic 10V
C15	200 μ F electrolytic 3V
C16	100 μ F electrolytic 6V
C17	1,000 μ F electrolytic 6V
C18	47 μ F mica or ceramic 350V
C19	0.02 μ F paper 100V
C20	0.02 μ F paper 100V
C21	500 μ F electrolytic 12V
C22	1,000 μ F electrolytic 15V
C23	1,000 μ F electrolytic 15V
C24	0.1 μ F paper 100V

Transformers:

- T1 Recording head autotransformer—see text. Alternatively can be purchased (Belclere TF2550; Colne 06040 or Parmeko P3005).
T2 Mains transformer. Tapped primary. Secondary 13.3V 0.6A (Radiospares).
T3 Bias and erase oscillator transformer—see text. Alternatively can be purchased (Belclere TF2547, Colne 06042 or Parmeko P3007).

Inductor:

- L1 Treble boost coil 370mH, 60 Ω , 1,000 turns of 40 s.w.g. en. wire on ferrite core LA1 or GA110A. Alternatively can be purchased (Belclere TF2549; Colne 06039 or Parmeko P3004).

Switches:

- S1 6-pole 2-way rotary switch. (Two wafers, each 4-pole, 2-way).
S2 Toggle switch 1-pole, 2-way.
S3 Toggle switch 2-pole, 2-way.

Transistors:

- Tr1 OC45, GET106 or NKT246.
Tr2 OC71, GET103, NKT244 or GET114
Tr3 OC71, GET114 or NKT244
Tr4 OC71, GET114 or NKT244
Tr5 OC72, GET104 or NKT243
Tr6 OC140, OC139 or NKT751
Tr7 OC22, GET116 or NKT304
Tr8 OC22, GET116 or NKT304
Tr9 OC22, GET116 or NKT304
Tr10 OC22, GET116 or NKT304

Diodes:

- D1 OA10
D2)
D3 } RS20A, SX641, ZS30B,
D4 } GEX541 or GJ3M
D5 }

Loudspeaker:

- LS Elliptical p.m. unit, 7 x 4in., 3-5 ohms

Tape Deck:

- BSR TDI or TD2
"Veroboard" (see text) is available from Vero Electronics, Regents Park, Southampton.

The transformer has a ratio of 8:1, and as the amplifier will produce 3.8V r.m.s., a maximum output of 30V r.m.s. is available for recording. So with the series resistor of 100k Ω this makes a maximum recording current of 330 μ A; as the normal recording current is only 150 μ A, at which point the output is only 14V r.m.s., it thus allows a good safety margin for peak signals and high frequency boost.

Loudspeaker Monitoring

The internal loudspeaker can be connected across the output when recording, in series with a resistor of approximately 10 Ω , which reduces the volume and loading of the output stage. In this way it is easy to check that the signal being recorded is suitable, and warning is given when recording radio shows, etc, that the item is likely to finish. Also, with some practice, the loudspeaker obviates the necessity of a recording level meter, as one soon becomes quite expert at judging recording

levels. Of course, when using the microphone, the loudspeaker has normally to be switched off in order to avoid audio feedback.

Complementary Pair Output

The output stage, which is used unaltered for playback and record functions, consists of four transistors in Class B output. Actually it is a complementary pair, the OC140 (Tr6) and the OC22 (Tr8) forming one high gain NPN transistor, and the OC72 (Tr5) and the OC22 (Tr7) a large high gain PNP transistor.

The NPN (Tr6, Tr8) takes care of the positive parts of the signal and the PNP (Tr5, Tr7) handles the negative portions. Because of the large current gain and low impedance of this combination the loudspeaker can be driven direct without a transformer and any normal 2 to 5 Ω loudspeaker is suitable, a 7in. x 4in. elliptical one being used in the author's model.

TO BE CONTINUED

Local Station F.M. Receiver

by J. G. Ransome

THIS receiver was designed with three objects in mind, namely that the set should be easy to construct, it should produce reasonable quality sound and that it should be cheap to build. It is felt that this design has satisfied these requirements. Originally the set was designed for the reception of the London transmissions at a range of about ten miles, but later the receiver was modified to receive these transmissions at about 30 miles from the transmitter.

The prototype was constructed in three stages—each a complete entity in itself. Initially only that section shown in Fig. 1 was constructed, this being used to feed a high quality a.f. amplifier, later an extra i.f. stage was added to increase the sensitivity of the set for use at the increased range, and finally the a.f. amplifier was constructed to make the complete receiver. It will be convenient therefore to describe the construction of the set "in historical order".

I. THE F.M. TUNER

R.F. Section

There is nothing unduly special about the r.f. section. The aerial is coupled to the centre of L1 by C1, this capacitor helping to prevent break through at the i.f. frequency (10.7Mc/s). L1 in turn takes the signal to the grid of V1a which is the pentode section of the ECF82. As L1 is extremely heavily damped by the valve the tuning of the coil will be extremely broad and there will be very little advantage in trying to tune the coil manually, so in this case the core of L1 is adjusted for the best results for the centre frequency of the three stations to be received, and sealed in this position. V1a acts as an r.f. amplifier and mixer, the resultant signal at 10.7Mc/s being coupled via IFT1 to the grid of V2.

The Oscillator

The oscillator is constructed around the triode section of the ECF82 (V1b). A very reliable circuit form has been adopted and hence the usual troubles associated with v.h.f. oscillators have been avoided.

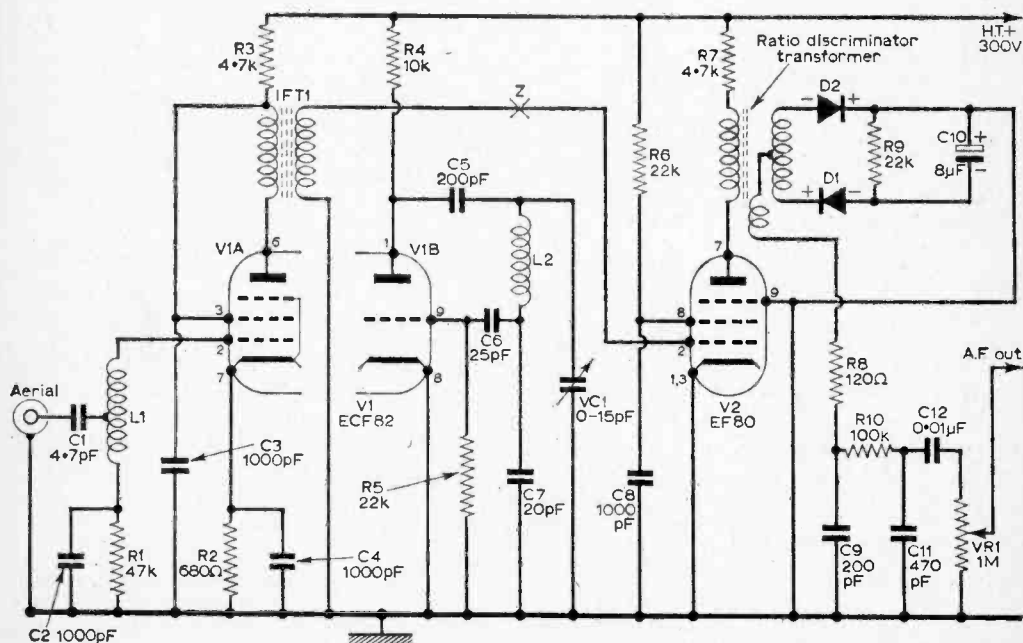


Fig. 1: The main circuit.


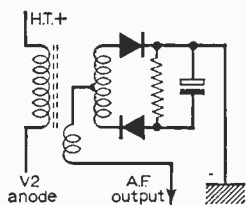


Fig. 2 (left): The basic circuit of the detector.

Right: The finished tuner.

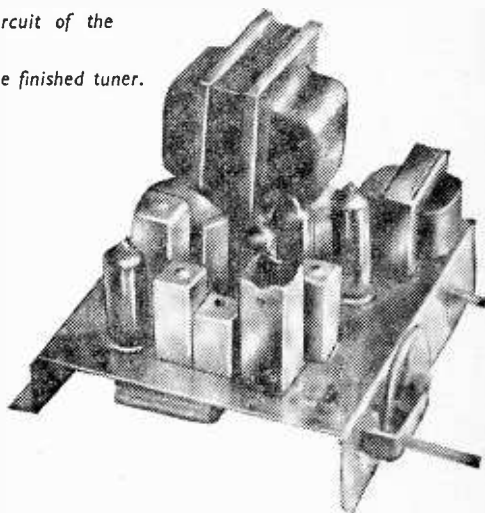

In an attempt to overcome frequency drift, so common in receivers of this type, C7 is specified as a negative temperature co-efficient component. The use of such a capacitor has the advantageous function of counteracting the capacitance changes which take place in the valve as it warms up, which would otherwise tend to cause the set to keep drifting off frequency during the first half hour of the operation, after switching on.

The oscillator contains the only continuously variable tuned circuit in the whole receiver. The oscillator runs at 10.7Mc/s below the signal frequency and so by varying the oscillator frequency we can vary the received r.f. frequency. There is no direct coupling between V1a and V1b as it was found that strong capacitance coupling was more than enough for satisfactory operation. However, should this not prove to be the case (and this is very unlikely) the anode of V1b should be coupled to the grid of V1a by a capacitor having a value of 1-2pF; alternatively a short piece of 20s.w.g. wire (about 1in. long) should be soldered to pin 1 of V1 and a similar piece of wire soldered to pin 2 of V1. These wires should be sleeved completely and twisted together ensuring that they *do not* make

V2 which amplifies the signal and passes it on to the ratio detector for demodulation.

The ratio detector is a little unusual since it is of the unbalanced type rather than the more familiar balanced type. The unbalanced detector has the advantage of using fewer components than its balanced counterpart whilst at the same time being less critical of component tolerances.

The basic unbalanced detector circuit is shown in Fig. 2. Basically the operation of the circuit is as follows:

The capacitor and resistor in parallel constitute a circuit with a large time constant. This circuit is charged with d.c. by the two diodes to a level proportional to that of the i.f. amplitude. On the arrival of a large interference pulse at the circuit the resistor capacitor combination, having a large time constant, takes a long time to charge up to a value equivalent to that of the pulse, and so tends to absorb the pulse with very little change in d.c.

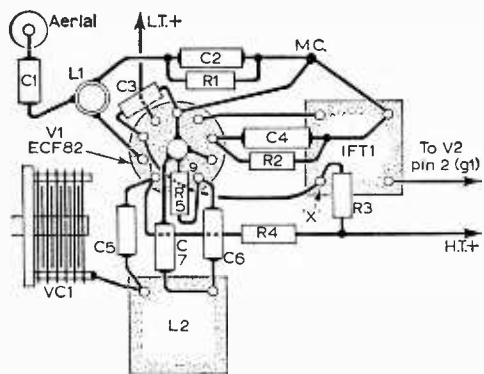


Fig. 3: The wiring of the r.f. and oscillator stages.

electrical contact. This will provide an adequate coupling between the two stages.

I.F. and Demodulation

V2 has two functions as it acts as an i.f. amplifier and partial limiter for the ratio detector stage. As this tuner will be used as a local station receiver very little limiting of interference pulses will be required as the set is quite insensitive to everything but the strongest of signals, and so V2 is allowed to draw more anode current than is usual in this type of circuit, to enhance the i.f. gain at the expense of full limiting action. The i.f. amplifier is otherwise quite straightforward, the i.f. signal from 1ET1 being coupled to the grid of

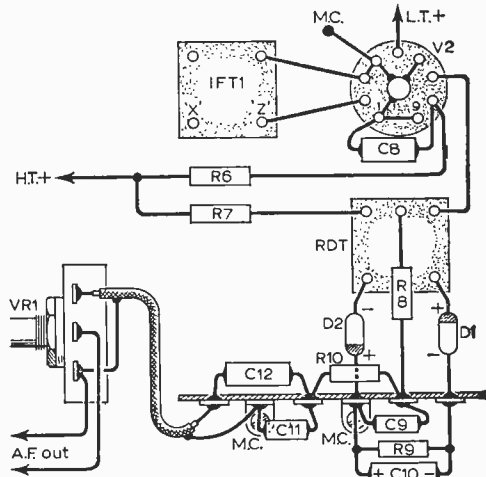


Fig. 4: The i.f. and detector stages wiring diagram.

level across the circuit. Thus the effect of the interference pulse is limited and reduced.

However, as it stands, the circuit of Fig. 2 would not satisfactorily meet our requirements. Firstly the "r.f. output" is not pure r.f., but contains a large measure of i.f. signal which if it were passed on to the a.f. section might have some unfortunate results. We have, therefore, to remove the unwanted i.f. signal whilst preserving the required a.f. component. This is done quite simply by including a capacitor (C9 Fig. 1) which is of such a value as to present a low impedance path to a.f. A suitable value is 200pF.

The second modification which has to be made to the basic circuit is the inclusion of the de-emphasis circuit (R10, C12 Fig. 1). The f.m.

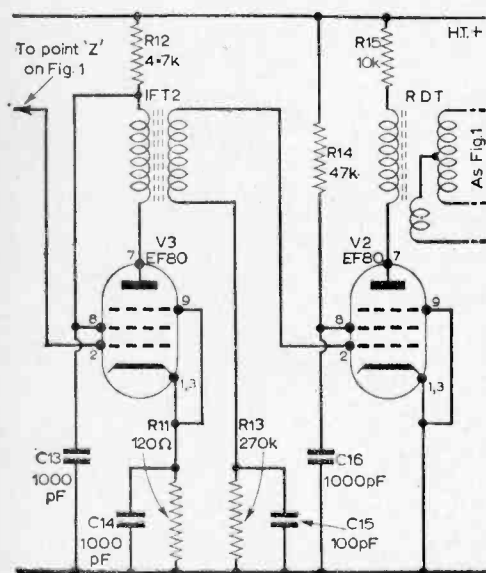


Fig. 5: The circuit employing an additional i.f. stage.

broadcasts in this country are transmitted with a boosted or emphasised treble characteristic and this must be equalised at the receiving end to level the a.f. output of the set. The boosted treble transmission with its subsequent de-emphasis at the receiving end has the advantage, amongst others, of improving the signal to noise ratio of the system. The degree of emphasis given to the treble at the transmitting end is given in terms of a time constant—this being the time constant of the circuit to be used in the receiver to de-emphasise the treble. The BBC quote a figure of 50μsec for this time constant and this is satisfied by making C11 equal 470pF and R10 100kΩ (Fig. 1).

The last modification to be made to the basic circuit is the inclusion of the resistor R8 (Fig. 1) which modifies the limiting action of the ratio detector a little. The inclusion of this resistor enables the detector circuit diodes (D1, D2) to do

COMPONENTS LIST

Resistors:

R1	47kΩ	R11	120Ω
R2	680Ω	R12	4.7kΩ
R3	4.7kΩ	R13	270kΩ
R4	10kΩ 1W	R14	47kΩ
R5	22kΩ	R15	10kΩ 1W
R6	22kΩ	R16	2.2kΩ
R7	4.7kΩ	R17	150kΩ
R8	120Ω	R18	47kΩ
R9	22kΩ	R19	1MΩ
R10	100kΩ	R20	120Ω

(All $\frac{1}{4}$ or $\frac{1}{2}$ W unless otherwise stated)
VR1 1MΩ carbon potentiometer

Capacitors:

C1	4.7pF mica or ceramic
C2	1,000pF ceramic
C3	1,000pF ceramic
C4	1,000pF ceramic
C5	200pF ceramic
C6	25pF mica or ceramic
C7	20pF ceramic (neg. temp. co-efficient)
C8	1,000pF ceramic
C9	200pF ceramic
C10	8μF electrolytic 150V
C11	470pF ceramic
C12	0.01μF paper
C13	1,000pF ceramic
C14	1,000pF ceramic
C15	100pF ceramic
C16	1,000pF ceramic
C17	25μF electrolytic 12V
C18	8μF electrolytic 450V
C19	0.01μF paper
C20	16μF } electrolytic 450V
C21	16μF }
VC1	0-15pF air variable

Inductors:

L1	Aerial coil, see text
L2	Oscillator coil, see text
L3	L.F. choke 10H, 100mA
IFT1, 2	10.7Mc/s i.f. transformer (Denco IFT11/10.7)
RDT	Discriminator transformer (Denco RDT1/10.7)
T1	Output transformer 40 : 1 (for 3Ω loud-speaker)
T2	Mains transformer with tapped primary. Secondaries: 300V 100mA (h-w); 6.3V 2A

Valves:

V1	ECF82	V4	EF86
V2	EF80	V5	EL84
V3	EF80		

Diodes:

D1, 2	OA81 germanium diode (or similar)
D3	3 x RM2 selenium power rectifier

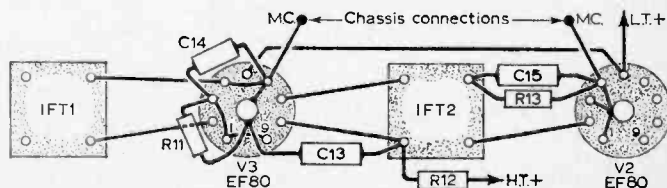


Fig. 6: The wiring of the additional i.f. stage.

their job effectively even when they are working well into the non-linear portions of their characteristics.

The a.f. signal is taken from the junction of R10 and C11 via C12 to VR1 and thence to the a.f. amplifier. The function of C12 is to act as a d.c. blocking device preventing the d.c. which appears at the tertiary winding on the ratio detector, as a result of the rectifying properties of D1 and D2, from appearing across VR1 which would cause the volume control to be noisy in operation.

Construction

The full layout of the prototype is not shown as it was not really a model of its kind! A rough idea of the original layout may be had from the photograph, but that chosen by the reader will undoubtedly reflect his neatness—or otherwise, and the size of the components to hand. The only critical section is the r.f. and oscillator section where the wiring should be short and point to point. No attempt should be made to make the wiring "look pretty".

R.F. and Oscillator Stages

A wiring diagram for these two stages is shown in Fig. 3. It must be emphasised that the wiring must be short and direct. Coil L1 is wound on a $\frac{1}{8}$ in. dia. iron-dust cored former and consists of $5\frac{1}{2}$ turns of 20s.w.g. wire, each turn being spaced from the next by a distance equal to the diameter of the wire. The coil is tapped at exactly its mid-point. The coil is mounted beneath the chassis and may be left unscreened.

Coil L2 consists of six turns of 20s.w.g. wire on a $\frac{1}{8}$ in. dia. iron-dust cored former being wound, as L1, with each turn separated from the next by the diameter of the wire. This coil should be fitted with a screening can.

The wiring may now be undertaken as shown. It is recommended that in these two stages only components of the type specified should be used as the use of inferior components, especially in the by-pass and decoupling circuits, can result in instability or alterations to the response characteristic of the receiver, causing an asymmetrical operation of the detector stage and thus a distorted audio output. To avoid unfortunate capacitance effects VC1 should be mounted as close as possible to L2. (In the original this was not done—this resulted in extremely poor frequency stability which was cured immediately on removing C7 to a point proximate to L2.)

I.F. and Detector

This is a very straightforward piece of construction. It is recommended that the i.f. by-pass and de-emphasis circuits be mounted on a tag strip as shown in Fig. 4 as this makes for a reasonably neat layout and helps to avoid hum pick-up. Screened wire should be used to take the output from the


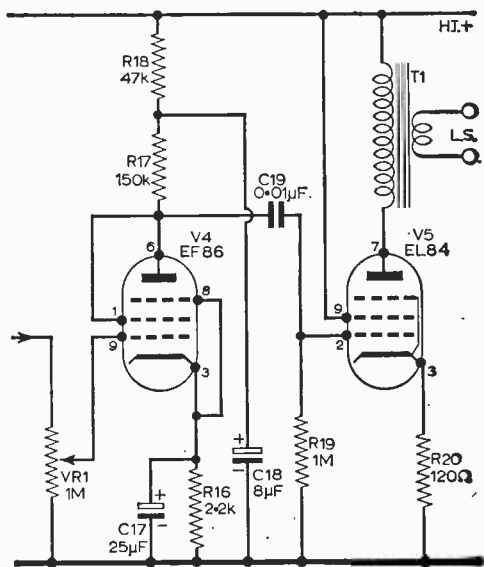


Fig. 7 (above): The a.f. amplifier circuit.

Fig. 8 (below): Wiring of the a.f. amplifier.

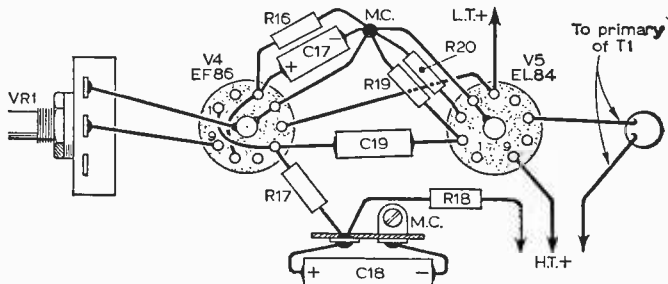

detector stage to the volume control to eliminate 50c/s hum. Another useful precaution in this respect would be to keep the leads carrying the heater current well away from all a.f. points.

The unit now, as it stands, may be used as a local station tuner by connecting it up to a suitable power unit (250-300V d.c. at 25mA and 6.3V at 0.6A). The setting up and test procedure is exactly the same as for the more sensitive receiver (except, of course, that there is one less i.f. coil to align).

However, as stated earlier in this article, it will be found that the set is too insensitive for satisfactory results at a range above that of ten miles from the transmitter and so for areas of weaker signal strength another i.f. stage will have to be added. Also, since the signal strength will be less at this greater range the effect of interference will be greater, and so we shall have to increase the limiting action of the circuit to overcome this difficulty. The improved circuit for increased sensitivity is shown in Fig. 5 where the r.f. and oscillator sections remain intact, the new circuit continuing from point Z in Fig. 1.

2. THE IMPROVED CIRCUIT

It will be seen from Fig. 5 that the improved circuit has several additional features beyond merely that of an additional i.f. stage. Looking first at the detector stage we see that the anode and screen loads of V2 are each doubled in value—R15 (R7 of Fig. 1) becoming 10k Ω and R14 (R6 of Fig. 1) increasing to 47k Ω . This has the effect of lowering the anode and screen voltages of the valve and thus reducing the current that the valve draws, which improves the a.m. limiting properties of the circuit. The rest of V2 circuitry is retained in its original form.

The extra i.f. gain is obtained from V3 and its associated network. The only circuitry of interest here is the combination of C15 and R13. This circuitry has a time constant of 27 μ sec and provides a certain amount of standing bias on the grid of V2. This circuit has a limiting action and thus aids V2 in a.m. interference suppression.

The wiring diagram for the additional i.f. stage is shown in Fig. 6 and indicates only the wiring for V3 (the wiring for V2 is exactly the same as in Fig. 4, save for the change in values of R6 and R7, making them R14 and R15 respectively.) The alignment and testing of the tuner is described under the heading of "Testing and Tuning".

Table 1
TEST VOLTAGES

Pins	V1	V2	V3	V4	V5
1	100	1.5*	1.2*	50	—
2	—	—	—	—	—
3	200	1.5*	1.2*	1.0*	5.5*
4	a.c.†	—	—	—	—
5	—	a.c.†	a.c.†	a.c.†	a.c.†
6	200	—	—	50	—
7	4*	200	110	—	200
8	—	200	120	—	—
9	—4.5*	—	—	—	210

H.T. line 210V †L.T. 6.3V a.c.

All voltages measured with 20,000ohm/volt meter on 1,000V range (* on 10V range).

leads and associated components; otherwise the layout may be as convenient. A wiring diagram for the a.f. stage is given in Fig. 8.

A suitable power pack for use with the completed receiver is shown in Fig. 9. Any power unit capable of giving 250-300V at 80-90mA and 6.3V at 1.5A will, however, be suitable.

4. TESTING AND TUNING

Initially the whole of the wiring should be checked for wrong connections against the diagrams and the h.t. and l.t. leads examined for shorts to the chassis. If available, a milliammeter (0-100mA) should be inserted in the h.t. lead and all valves (except the rectifier—if used) should be removed and the set switched on.

After allowing the set to warm up the milliammeter should indicate that there is no current flowing in the h.t. circuit. Plug in the EL84. About half a minute after doing this the h.t. current should rise to about 50mA ($\pm 10\%$). Next plug in the EF86. The valve should light up (faint heater glow) but there will be little or no noticeable increase in current. There should be a general "liveliness" about the set now with a very faint hum in the loudspeaker. On touching pin 9 of the EF86 with a long-bladed screwdriver there should be a very loud noise from the loudspeaker (make sure that VR1—the gain control—is full up) and the h.t. current should fluctuate. If all is well the a.f. section may now be used as a gramophone amplifier if so desired. The tuner section may now be tested.

If only the tuner section has been constructed it should first be connected to an a.f. amplifier and a suitable power supply with, if at all possible, a milliammeter in series with the h.t. lead. We will

—continued on page 257

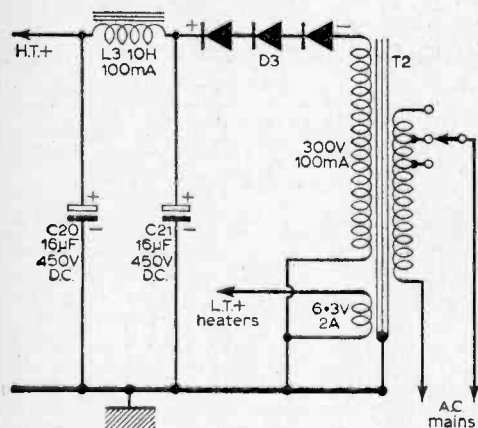


Fig. 9: The power supply circuit.

3. THE A.F. AMPLIFIER

The a.f. amplifier may take several forms. A simple circuit built around a single EC1.82 would be quite satisfactory for ordinary domestic use if a little can be sacrificed in the way of quality. The circuit of the a.f. stage used in the prototype is shown in Fig. 7. It will be seen that this is quite an ordinary circuit form—pre-amplification being given by a triode connected EF86 feeding a single-ended output pentode (EL84). An EF86 was used here as it is intended at a later date to add feedback tone controls, in which case the extra gain given by a pentode configuration for the EF86 will become necessary.

Construction of this stage should follow normal high gain a.f. practice—especially in that heater leads should be kept well away from control grid

**RADIO-AMATEUR GEAR
EDUCATIONAL KITS**

**TEST INSTRUMENTS
HI-FI EQUIPMENT**

With the simple English of our instruction manual, anyone can build any of our models—and save money!



S-33

We guarantee that NO electronic or soldering experience is necessary. Our simple, well illustrated manual guides you step-by-step.

6W STEREO AMPLIFIER. Model S-33. 3 w/chl. Inputs for radio-tape and gram., Stereo/Mono ganged controls. Sensitivity 200 mV. ... £13.76

NEW! 5W HI-FI MONO AMPLIFIER. Model MA-5. A low-priced amplifier based on the S-33. Printed circuit construction... £10.19.6

TAPE RECORDING/PLAYBACK AMPLIFIER. Stereo (TA-1S) £24.10.0 Monaural (TA-1M) ... £19.2.6

STEREO CONTROL UNIT. USC-1. Luxury model with inputs to suit any pick-up or tuner ... £19.10.0

HI-FI AM/FM TUNER. Tuning range: FM 88-108 Mc/s, AM 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.) and I.F. amplifier (£20.13.0). Printed circuit board ... Total £25.6.6



SB-10U



USC-1



TA-1S



S-99



AM/FM Tuner



SSU-1



O-12U

HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. Tuning Unit (FMT-4U) with 10.7 Mc/s I.F. output (£2.15.0 inc. P.T.) I.F. Amplifier (FMA-4U) complete with cabinet and valves (£12.6.0). Total £15.1.0.



F.M. TUNER

NEW! 6W DE LUXE AMPLIFIER. Model S-33H. An inexpensive Stereo-Mono amplifier, with high sensitivity. Suitable for Decca Deram cartridge ... £15.17.6

5in. OSCILLOSCOPE. Model O-12U. Wide band amplifiers essential for TV servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges ... £38.10.0

HI-FI 18W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram., radio and tape recorder inputs. P/B selection ... £27.19.6

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted port bass reflex cabinet "in the white". Two speakers. Legs 14/6 extra. Bookcase model ... £10.17.6

SEND FOR FREE CATALOGUE—OVER 50 MODELS TO CHOOSE FROM

SINGLE SIDE BAND ADAPTOR. Model SB-10U. May be used with most A.M. transmitters. Less than 3W R.F. input power required for 10W output. Operation on 80, 40, 20, 15 and 10 m. bands on USB, LSB, or DSB. £39.5.0

THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Fully Transistorised. Excellent portable or general purpose receiver for the amateur and short-wave listener ... £39.17.6
See full specification leaflet.



GC-1U

SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1. Two short bands, trawler and medium ... £19.17.6

HI-FI EQUIPMENT CABINETS. Large range, in kit form or assembled and finished, available to meet various needs. Details on request ... from £6.19.6 to £29.8.0

PORTABLE SERVICE OSCILLOSCOPE. Model OS-1. Compact portable scope, ideal for servicing and general work. Printed circ. Case 7 1/4 x 4 1/2 x 12 1/2 in. long. Wt. only 10 1/2 lb. £19.19.0



DX-40U

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. CW., 60 w. peak C.C. phone. Output 40 w. to aerial. Provision for V.F.O. ... £33.19.0

INTERNATIONAL MAIL ORDER SCHEME
Covering 250 American Models. Full details and catalogue can be obtained from us for 1/-. Post paid.

BASIC AMATEUR BANDS RECEIVER. Model RA-1. To cover all the Amateur Bands from 160 to 10 m. Many special features incl.: half-lattice crystal filter, 8 valves, signal strength "S" meter, tuned R.F. Amplifier stage. ... £39.6.6

6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers, Printed circuit, 7 x 4 in. high flux speaker. Real hide case ... £12.11.0

VALVE VOLTMETER. Model VTA. Measures up to 1,500 volts (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1% 1,000M2 £13.18.6

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands, 160-10 m. 150 w. D.C. input, self contained with power supply. Modulator, V.F.O. £74.19.0



DX-100U

Send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s).....

NAME

ADDRESS

PW7

Assembled models also available—prices on request
Deferred terms available over £10. Free Delivery U.K.

DAYSTROM LTD.

Dept. P.W.7, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

4 HANDBOOKS FOR ENTHUSIASTS!

**Practical!
Authoritative!
GET
YOURS
TODAY**

* TRANSISTOR RADIO CIRCUITS

Contains full details on the construction of 6 different receivers, plus articles on the basic principles of semi-conductors and practical aspects of servicing.

* TEST GEAR for Amateurs

Principal contents include a wide range of signal generators suitable for a.m. and f.m. receiver alignment and servicing applications, and for audio equipment testing.

* 25 SELECTED CIRCUITS for Amateurs



Divided into 4 sections covering receivers, audio amplifiers, transmitters and test gear. Contains comprehensive instructions and circuit diagrams to build all the popular equipment you are likely to need.

* RADIO CONSTRUCTION for Amateurs

Includes an illustrated guide to components, colour codes and circuit symbols . . . instructions on chassis assembly and soldering . . . circuit diagrams and instructions to build simple receivers, test gear and amplifiers.

3'6 EACH

ON SALE AT ALL NEWSAGENTS AND BOOKSTALLS

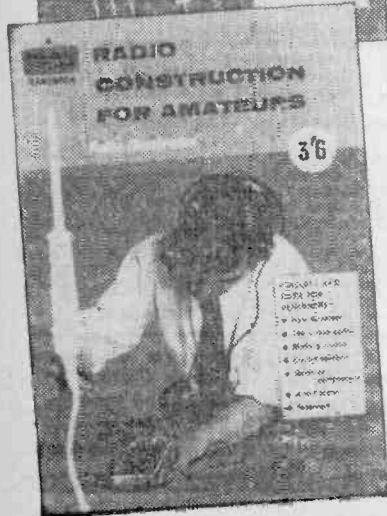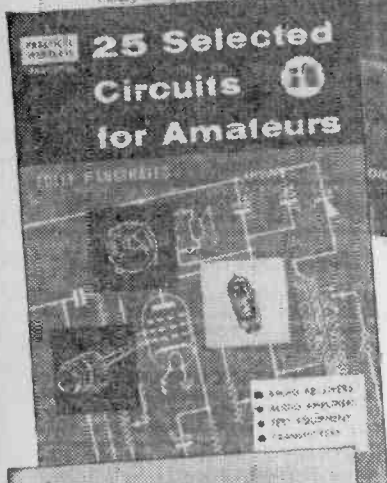

Switch-tuned Radio/Amplifier

BY R. MURRAY-SHELLEY

ALTHOUGH using only two valves together with a rectifier, this unit embodies the functions not only of a switch-tuned local station radio receiver but also of an audio amplifier capable of producing over three watts of power at quite reasonable quality.

At first glance the circuit may appear to be a little complicated, though it is in fact quite straightforward. Provision is made for the reception of two programmes; in the case of the prototype these were the Home Service on the medium wave band, and the Light Programme on long waves. In theory any two selected stations could be received but it should be pointed out that the selectivity and sensitivity of the circuit is necessarily limited to a certain extent—it is essentially a local station instrument. Stations are selected by means of a three-position switch. The third position converts the unit into a two-stage amplifier.

The Radio Circuit

Only one tuned circuit is employed in this design for each channel, therefore the initial alignment of the equipment is greatly simplified. Leaky grid detection together with a measure of positive feedback ensures a reasonable level of sensitivity. This positive feedback is regulated by adjusting the voltage on the screen grid of V1, the cathode of this valve being connected to a tapping on the tuning coil—in this way a very stable adjustment can be achieved.

The value of the grid leak resistor R3 calls for

some comment. It is usual to find a resistor of several MΩ in this position, however in this design the component doubles as the grid leak resistor for the first stage of the audio amplifier, and thus a smaller value of resistance has to be used. In fact it is found that in practice the specified value of 220kΩ is quite suitable.

The operation of the output stage, V2, is the same on both radio and amplifier functions. The volume control VR3 is included in its grid circuit. A measure of tone correction is introduced by the capacitor C7; this together with the slight degree of negative feedback produced over the first stage (in the "amplifier" position) by the elimination of the usual by-pass capacitor for R4, leads to a very satisfactory performance.

The Amplifier Circuit

The input to the amplifier is made via a jack plug and socket. This socket has integral switching contacts whose function can be clearly seen from the circuit diagram (Fig. 1). It should be noticed that in order to convert the unit from a radio receiver to an amplifier it is necessary to switch the selector switch S1 to position three, and then to plug in the jack plug.

This plug must be removed before the unit can again be used as a radio receiver. This slight inconvenience was thought to be justifiable since it avoids complicating further the selector switch connections. Again too much switching of signal circuits always brings with it problems of instab-

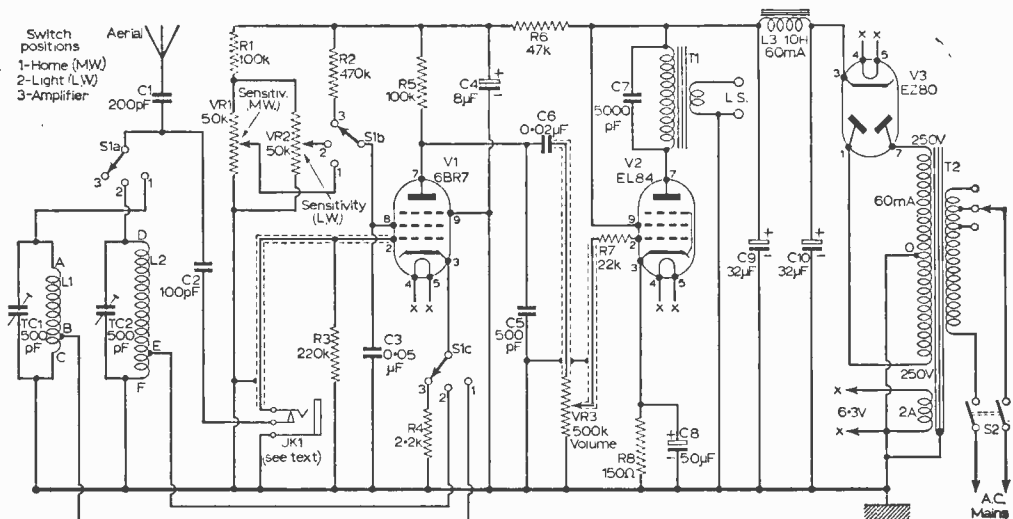


Fig. 1: The circuit.

ility and feedback which might prove difficult to counter. The amplifier input is at high impedance.

Power Supplies

The power-pack is quite conventional. Although the power consumed by the unit is not large (about 50-60mA h.t.) a mains isolating transformer is used in the interests of safety. Full wave rectification, large value smoothing capacitors and a smoothing choke all contribute to a low hum level.

The rectifier valve used is an EZ80 having a 6.3V heater. An EZ81 is equally suitable, though if other valves are used then C10 should be

reduced to 16 μ F capacity. The chassis should be earthed.

Construction

The unit is constructed on an aluminium chassis size 7in. x 5in. x 2in. deep. The drilling details for this chassis are given in Fig. 4. It would not be practicable to use a chassis of smaller dimensions than the one specified.

The valveholders, transformers and smoothing choke are mounted first together with the three variable resistors, group board, and the reservoir and smoothing capacitors (C9 and C10). Earth connections are made to an earth busbar which is connected to the chassis at one point only. This busbar is conveniently made of a length of 16 or 18s.w.g. tinned copper wire, and it is mounted as shown in the wiring diagram (Fig. 3).

The heater wiring and the wiring to the mains switch S2 should be completed next. This wiring which carries alternating current should be twisted together tightly as shown and pressed hard against the chassis. The power supply should now be wired, followed by the output stage and last of all the first stage. The valves should not be inserted into their holders until all the wiring has been completed.

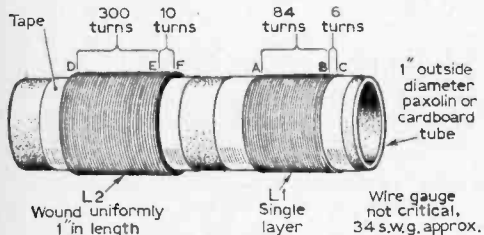


Fig. 2: Details of suitable tuning coils.

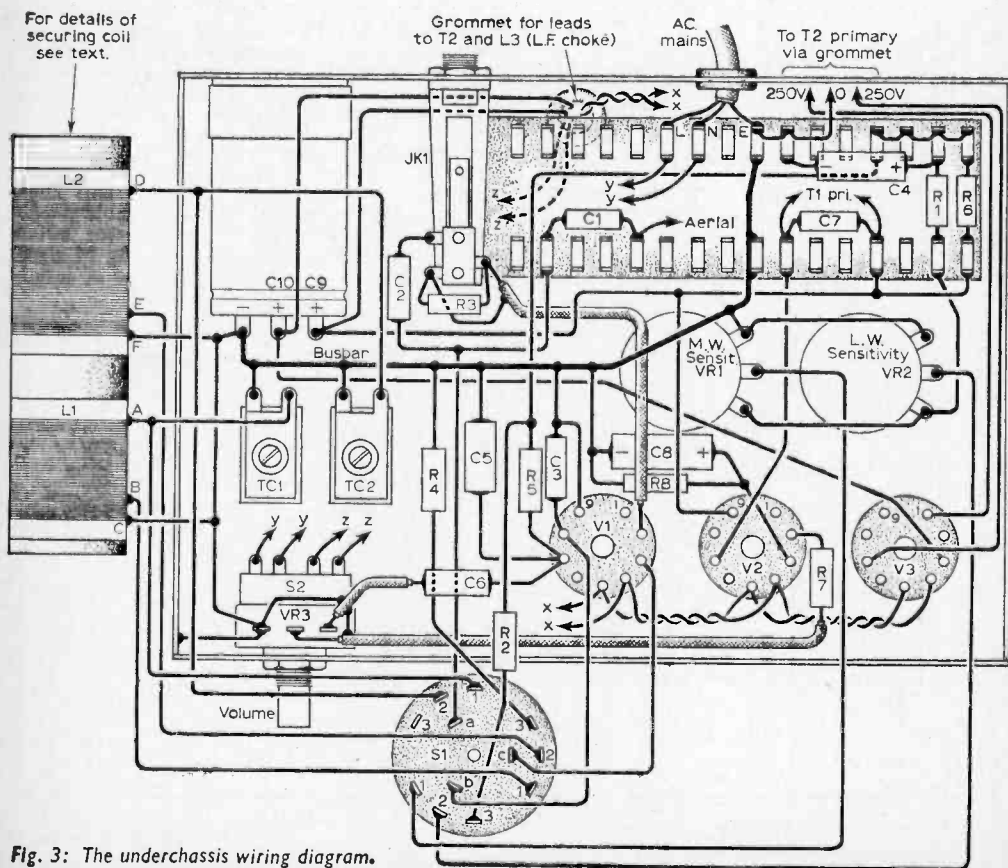



Fig. 3: The underchassis wiring diagram.

Fig. 4: Dimensions and drilling details of the chassis.

Screened lead should be used where it is shown in the circuit diagram. A determined effort should be made to keep all the wiring as short as is practicably possible. This particularly applies to the first stage. This method of construction leads to a less tidy arrangement than might otherwise be possible, but it pays dividends in that less trouble is experienced from instability.

The grid stopper resistor R7 should be connected as close to its appropriate valve pin as possible.

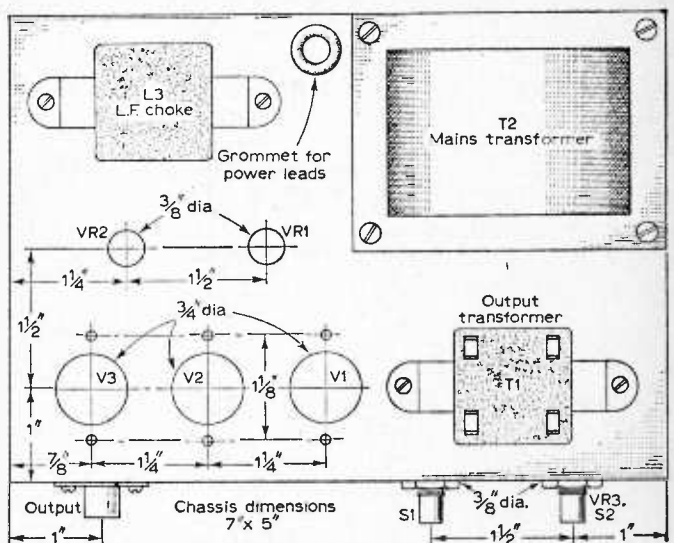A suggested wiring plan is given in Fig. 3. Notice that here the selector switch has been turned through a right angle in order to clarify the wiring. The output from the unit was taken via a coaxial socket since this was to hand. Any other type of loud-speaker socket could, of course,



COMPONENTS LIST

Resistors:

R1 100kΩ	R5 100kΩ
R2 470kΩ	R6 47kΩ 1W
R3 220kΩ	R7 22kΩ
R4 2.2kΩ	R8 150Ω 5W

All 10%, 1/2W unless otherwise stated.

VR1 50kΩ potentiometer, preset, log.

VR2 50kΩ potentiometer, preset, log.

VR3 500kΩ potentiometer, midget type with d.p. switch (S2)

Capacitors:

C1 200pF mica
C2 100pF mica or ceramic
C3 0.05μF paper 350V
C4 8μF electrolytic 350V
C5 500pF ceramic
C6 0.02μF paper 1000V
C7 5,000pF paper 350V
C8 50μF electrolytic 50V
C9 32μF electrolytic 350V
C10 32μF electrolytic 350V
TC1 500pF compression type trimmers
TC2 500pF compression type trimmers

Inductors:

L1, L2 (see text and Fig.2)
L3 Smoothing choke 10H 60mA

Transformers:

T1 Output transformer 3-5W (see text)
T2 Mains transformer tapped primary.
Secondaries: 250-0-250V 60mA; 6.3V 2A
S1 Rotary switch 3-pole, 3-way
S2 Toggle switch s.p. s.t. (see VR3)
JK1 Jack socket, closed-circuit type (Bulgin J12)

Valves:

V1 6BR7	V2 EL84	V3 EZ80
---------	---------	---------

Miscellaneous:

Coaxial socket. Three B9A valveholders.
Screened lead. Wire for coils (see text).
Connecting wire and sleeving.

be used. One side of the output is earthed as is one side of the heater wiring.

The connections to the jack sockets are shown in Fig. 5. The metal ferrule on the socket must make a good contact with the chassis. The trimmers TC1 and TC2 each have one of their tags soldered to the earth busbar which then serves as a mechanical support for these components.

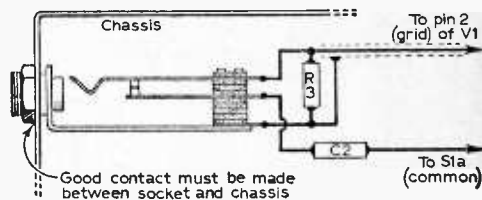


Fig. 5: Connections to the jack socket, JK1.

Construction of the Tuning Coil


The coils used in the prototype equipment were home made. Details of this construction are given in Fig. 2. The former used was a length of 1in. outside diameter paxolin tubing. Cardboard tubing or even a tube made from gummed paper would serve equally well. The wire gauge is not particularly critical, 34s.w.g. enamelled copper wire being suitable. On completion the coils should be varnished or preferably waxed.

The coils were fixed to the chassis in the prototype using a clip made from cardboard reinforced with plastic tape. A metal clip is not suitable. Care should be taken to see that the coil is not placed hard up against the chassis or other metal components.

Commercially made coils could certainly be used in this circuit, but they would have to be modified in order to incorporate the cathode tapping. This is most easily done by winding a few more turns on to the coil in the same direction as

—continued on page 232

by G.M. and E.C.D.

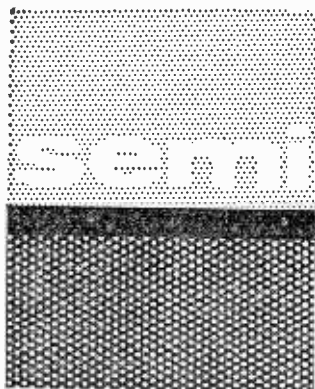

Semiconductors

TALKING POINTS ON CIRCUIT PRACTICE

No. 6—More on R.F. Operation

Continued from page 149 of the June issue

TO predict the behaviour of transistors at radio frequencies without involving oneself in mathematics is extremely difficult. It is more than doubtful if any of the old, well-tried "single-valve" circuits really offers fruitful ground for experimenting with "single-transistor" techniques. Completely new techniques hold the best possibilities of success in this field.

The fact of the low impedance of transistors as compared to valves; the fact that they amplify current rather than voltage, the existence of an internal feedback path which is variable to frequency and which must therefore require a cancellation procedure which is also variable to frequency and which must of necessity upset "reflex" calculations; combined with the difficulty of avoiding "pulling" and therefore the de-tuning of the aerial circuits by the reflex circuits if modern high efficiency solid core inductances are used, all combine to make the design and operation of "freak" circuits at once a challenge and a problem, with transistors, if they are to be tunable over a wide band of frequencies, as must be a receiver intended for broadcast reception.

For single-channel reception the problem would not be so difficult nor the mathematics so involved.

Even with the superhet certain precautions are necessary. There may be feedback in the supply lines, which may require decoupling. The full supply voltage is rarely needed in the early stages, so the decoupling may also drop the supply to a lower voltage than is taken by the output stages.

PRACTICAL ASPECTS

Transistors tend to be noisy, though a mixer-oscillator will demodulate its own noise on signal; resistance and capacitors in the first stages should be of high quality and guaranteed stability whatever may be used in the later stages; and, of course, non-inductive. Decoupling capacitors are normally of some 100 μ F or more as far as the supply line is concerned, and they can vary from 0.1 μ F to as much as 8 μ F according to position elsewhere. Electrolytics with "can negative" must be insulated from deck, of course.

Since these devices, as well as their associated components, are so small it can be quite a job to service a receiver which does not work—more especially so if it is of bird's nest construction. A bold layout, on breadboard lines, will repay the builder . . . it is simple enough to finalise and "box" it after one has made sure it operates successfully.

For work at broadcast frequencies, start with a fully-fledged superheterodyne circuit, you will then "duck" nine tenths of the problems, and get acceptable results into the bargain. For experiments with freak circuits use an outdoor aerial and air-cored inductance coils. This may sound pessimistic advice, but would you expect (if using valves) to operate a "single-valver" on an 8in. frame aerial with much success? It is as well to remember that commercial portables normally use five or more valves, while commercial transistor portables commonly have seven stages: six transistors and a diode.

Remember the low input impedances you will be dealing with, and that matching is normally a step-down; that it is not voltage amplification you require from each stage . . . you are likely to get more of that than you want if you are not to overload the following stage—but *current* swing, which in any case must not be more than the output current of that stage can take, after amplification in the transistor itself, without causing more voltage drop over the collector load than you have volts to drop.

Intelligent use of the published curves and data should make the difference between valve technique and transistor technique understandable.

Transistors are not really difficult—apart from the mathematics and this aspect of their use has probably been done to death—they are just "different". Once they are approached as devices in themselves, and not as substitutes for valves operating much in the same way that valves do, an entire fog of misapprehension and frustration is likely to dissolve.

They are probably most tricky in their high frequency application; if one can obtain a signal

from one's first stage then it can always be amplified afterwards... but the tuning of transistorised aerial stages, other than in superheterodyne circuits, is still a field in which there is much to be done.

We realise that we are likely to be very unpopular for suggesting that freak transistor circuits more often do not work than they do, and we are quite certain that numerous people will reply angrily that they have got Pekin with no trouble

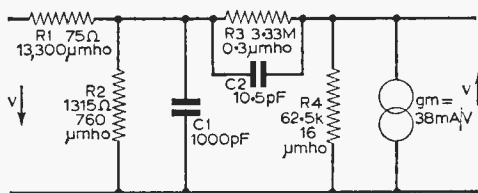


Fig. 1: Hybrid π circuit for OC45 at any frequency.

at all on one transistor and a safety-pin used for an aerial, and on medium waves at that. Nevertheless, we are in company with the professionals when we say that the superheterodyne circuit is the one to be preferred for transistor radio applications at the present state of knowledge. And we hope that we have given sound reasons why in fact this is so. It follows inevitably from the theory of transistors.

We have not considered f.m. applications and a whole host of other possibilities, nor dealt in practical circuits because rather than add to the

BASE POTENTIALS

In the first article of this series, published in February, 1963, it was suggested that in order to obtain a base current of $200\mu A$, the potential required on the base would be $200\mu V$.

This implies that the input resistance (base to emitter) of a transistor is of the order of 1Ω . However, this is not so in practice, since the input resistance of a transistor in the common-emitter mode of operation is likely to range from 500Ω to $1,000\Omega$.

It follows from this that the base potential required to obtain $200\mu A$ base current will range from $100mV$ to $200mV$.

It should now be clear that where $200\mu V$ is mentioned in the text and also in the accompanying diagrams Figs. 2, 3 and 6, this should be amended to read $200mV$ (millivolts NOT microvolts).

The amendment also applies to the second article in the series (March issue) where the base voltage is referred to on pages 1026 and 1029.

One last word in this connection: although evaluation of the voltage on the base was referred to as completing the theoretical picture, if the problem be considered in terms of current as recommended it will be appreciated that the total resistance required to limit the value of I_b to microamperes is such that the resistance of the device itself plays only a very small part in it. The makers' data therefore should, as stated, always be referred to for actual values, or a meter used in the emitter.

legions of circuits already published our aim is to enable the reader to understand those that are. These articles are in the main theoretical. To talk glibly of "Neutralisation", "Unilateralisation" and so on is all very well... but what do these terms mean? And why are the procedures to which they refer necessary? We could write down the formula for K ; the stabilising factor for transistors, for instance; but we would require a book, or a course at a technical college to explain that formula to the non-technical. Even at that we may attempt it some day.

We are very conscious of all the things we have still managed to miss out; but at least with the explanation given above of the peculiarities of transistors and diodes in operation at radio frequency we hope we have supplied the clue which may explain hook-ups that have failed to work and at the same time enable a clearer understanding to be gained of the general principles involved.

NEUTRALISING INTERNAL FEEDBACK

The formulae for calculating the value of internal feedback are rather beyond the scope of these articles. We show in Fig. 1 the equivalent circuit of an OC45 at any frequency working at a V_{ce} of $-6V$ and an I_e of $1mA$. The calculations can be made from the values given, by those with the mathematical knowledge.

If the transistor is only working at one frequency, as in the case of a superhet i.f. stage—say $470kc/s$, then the π equivalent circuit shown in Fig. 2 can be used and it will be seen that the calculation becomes a much simpler proposition.

In the hybrid π circuit of Fig. 1 the values of all the components can be regarded as independent of frequency providing the operating frequency is always considerably lower than that of f_c —the cut-off frequency.

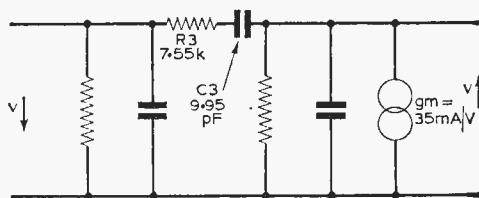


Fig. 2: π circuit for OC45 at $470kc/s$ only.

In the π equivalent circuit of Fig. 2 all the components depend on frequency. We see that the feedback circuit within the transistor itself consists of $R3$ and $C3$ —which Messrs Mullard give as $R3=7.55k\Omega$ in series with $C3=9.95pF$ (micro-microfarads) for the OC45 working at the frequency and conditions stated.

To neutralise this feedback we require an equal and opposite feedback to be erected externally, to cancel it out. At the values given for $R3$ and


C3, then the neutralising values would theoretically be $7.55k\Omega$ and $9.95pF$, similarly. But we must remember that the external feedback has to be connected from the secondary of the interstage coupling transformer in order to reverse its phase in relation to the internal feedback, and this transformer is normally a step-down ratio in order, as we have already seen, to match the high impedance output of the transistor to the low impedance input of the (base of) following stage.

Supposing this transformer to be a ratio $n:1$ then the values for the external feedback elements

The purely practical man can obtain the actual values for individual types of h.f. transistor as applying to the voltages and frequencies at which they will be operated in commonly preferred circuits, by reference to the published data issued by the transistor manufacturers themselves. If he wishes to experiment outside these more or less established circuitry conditions then he will perforce have to work out the answers himself.

The values given here are for the Mullard OC45, which is an h.f. transistor; they would be different again of course for the OC170.

Fig. 3: Equivalent circuit for OC45 at 470kc/s, showing neutralising components.

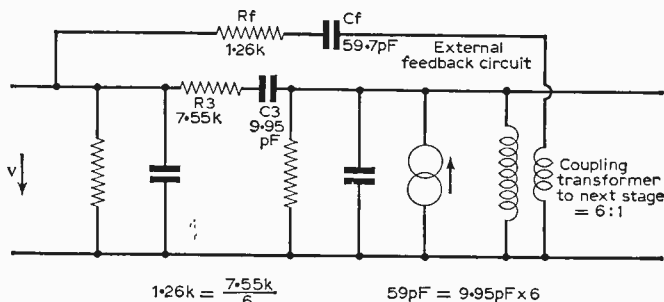

will be nC_3 and R_3/n . At a ratio of $6:1$; $R_F = 1.26k\Omega$ and $C_F = 59.7pF$. The equivalent circuit with both internal and external feedback paths is in Fig. 3.

It will further be realised that the addition of this external neutralising pathway must alter the original values of input and output impedance of the transistor itself and that these changes will also require to be worked out. They will not present any great difficulty to those familiar with evaluating π and hybrid- π equivalent circuits but, as we have said, they are beyond the scope of this article.

If one obtains the basic values for the type of transistor in question, from the maker's published data or from the makers themselves if necessary, the required feedback constants at all frequencies, or at a single preferred frequency, can be worked out from the data given above. From those calculations the final impedance, input and output can then be calculated so that matching can be done with some precision and regeneration applied, if required.

SERIES CONTINUED NEXT MONTH

SWITCH-TUNED RADIO/AMPLIFIER

—continued from page 229

the original winding. The end of the original winding then becomes the cathode tapping. About four or six turns would be required in the case of a medium wave coil and eight to ten turns for a long wave coil.

Components

The valves specified are all miniature B9A based components. Older international octal based types could be used, however. In this case a 6J7G should be substituted for V1 (the 6J7 and 6BR7 are electrically almost identical), and a 6V6G for the EL84. The output obtainable from the unit would be reduced, however, since the 6V6 has a lower slope than the EL84. If a 6V6 is used the value of R8 should be increased to 270Ω . A larger chassis will probably be required if octal valves are employed.

Using the EL84 output valve the output transformer should have a ratio of $40:1$ for a 3Ω loudspeaker, or $15.5:1$ for a 15Ω loudspeaker. (For a 6V6 the ratios are $50:1$ and $23:1$ respectively.)

the transformer should have a power rating of $3.5W$ and the primary should be rated for a d.c. current of at least $40mA$.

All resistors are $\frac{1}{2}W$ rating and 10% tolerance, unless otherwise stated in the components list. The valveholders should preferably be of the nylon loaded type.

Alignment and Testing

On completion, the wiring should be carefully checked. An aerial should then be connected to the receiver. An indoor aerial will suffice in areas of good signal strength, though an outdoor arrangement is of course to be preferred.

The selector switch is then turned to the medium wave band position and the unit switched on. On rotation of the appropriate feedback control (VR1 in this case) a point should be reached where the set starts to oscillate. The control is then turned back until the oscillation just ceases. The trimmer capacitor TC1 is now adjusted to tune in the local Home Service broadcast. VR1 is then re-adjusted for best reception.

The same procedure is repeated for the Light Programme, in this case VR2 and TC2 are adjusted. The amplifier circuit requires no initial adjustment.

New large purchases of components and reductions in purchase tax at the beginning of the year enable you to build your transistor radio at these vastly reduced prices.




P. & P. 3/6 extra

★ Six-Transistor Superhet Miniature Personal Pocket Radio. ★ Tunable over Long and Medium wavebands. ★ Uses PP3 battery. Ferrite Rod aerial. ★ I.F. Frequency 470 Kc/s. Transistors: 3 Philco 2067's, 2 Mullard OC81 M OC81 DM and OA90 diode. ★ 3 inch speaker. ★ Printed circuit 2½ x 2in. ★ Slow Motion Drive. ★ In Plastic Case, size 4 x 2½ x 1in.

In order to ensure perfect results, the SPRITE is supplied to you with R.F. and I.F. stages, Driver and Output stages ready built with all components ready mounted on the printed circuit. To complete assembly you only have to fit the wavechance and the remaining components already mounted on the printed circuit. The remaining components all having been prefitting at the factory for you. The SPRITE is offered as above, pre-assembled, plus cabinet, speaker and all components in a separate box. The cabinet is made of a high quality material. The Data and Instructions separately. 2/6. Refunded if parcel is purchased. Real calf leather case, wriststrap, personal earphone and case for earphone and battery 12/6 the lot extra. Make no mistake this is a SUPERHET receiver of genuine commercial quality. Write to: **THE SPRITE COMPANY, 10, PARKWAY, LONDON, E.C.2.**

TESLA "SONET"

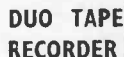


★ Continental manufactured 2-speed tape recorder with 11 x 3 1/2 in. i.p. Twin track recording to inter-level standards. ★ Takes 11 in. spools. ★ Fast forward and fast wind. ★ Record level indicator. ★ Inputs for mic. radio and pick-up. For use on 110 and 200-250 v. 50 c.p.s. mains. ★ Digital position indicator. ★ In attractive wood case with metal top cover fitted with storage compartments and carrying handle. ★ 10 x 7 in. High quality record-replay amplifier with internal loudspeaker provides immediate high quality reproduction. ★ Socket for external speaker. ★ Tone control: Supplied with reel of tape, empty spool, microphone and a selection of interconnecting leads, etc., with canvas waterproof cover. Brand New and Unused. List price 38 Gns.

LASKY'S PRICE 24 gns.
Carr. and Ins. 10/8.

The "REALISTIC" Seven

STAR FEATURES ★★★★★


- ★ 7 Transistor Superhet.
- ★ 350 Milliwatt output into 4-inch high flux speaker.
- ★ All components mounted on a single printed circuit board, size 5½ x 5½in. in one complete assembly.
- ★ Plastic cabinet, with carrying handle size 7 x 10 x 5½in. in choice of colours.
- ★ Red/Grey, Blue/Grey, all Grey.
- ★ Easy to read Dial.
- ★ External Socket for car aerial.
- ★ I.F. frequency 470 Kc/s.
- ★ Ferrite Rod Internal aerial.
- ★ Operates from PP9 or similar battery.
- ★ Full comprehensive data supplied with each Receiver.
- ★ All coils and I.F.'s etc., fully wound ready for immediate assembly.

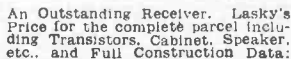

£5.19.6 Postage and Packing 4/6
PP9 Battery 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel.

The COROVER '6'


- * A 6-transistor plus 2-diode superhet receiver using the latest circuitry. * Three Mullard AP17 alloy diffused transistors are used with OA79 and OA91 diodes followed by OC81d and two OC81s in push-pull. * I.F. frequency 455 Kc/s. * 100% test checked. * 100% guaranteed. * Earbuds. * Sockets provided for personal earpiece or tape recorder, and car radio aerial. * Large internal ferrite rod aerial gives high sensitivity. * Uses four 1.5 v. pen torch batteries. * All parts new. * Simple to assemble. * Painted cabinet. * Simple stake by stage instructions. * Cabinet size 6 1/2 x 4 1/4 in. * With carrying handle. * All coils and I.F. ready wound. **ALL COMPONENTS AVAILABLE SEPARATELY.** * **Prices are listed separately 2/6. Refunded if you purchase the parcel.**

 

£5.7.6

Post and packing 4/- extra.
Batteries 1/4.

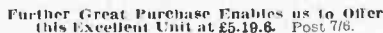TELEFUNKEN STEREO HI-FI AMPLIFIERS MODEL S82



5.19.6 A complete stereo amplifier of unsurpassed quality, with inputs for radio, tape recorder, F.M. tuner or any other hi-fi source, either monaural or stereo. Output power 5 watts total (2½ watts each channel). With balance control. New and unused. listed at 16 gm.

LASKY'S PRICE £5.19.6

CRYSTAL PICK-UP CARTRIDGES

Lowest Prices Ever!

Some at Less than Half List Price
All complete with Styl. L.P. and Stand-
ard (and Stereo where shown). Fully
guaranteed. standard fitting. will fit
most P.U. arms and heads.
Postage 1/- each extra.

Postage 1/- each extra.

MONO Type C.T.I.

By well known manufacturer. With two sapphire styl	9/6
Garrard Ceramic GOE 4	15/-
Garrard Magnetic T.O.M.2.	15/-
Acos GP.59	14/-
Acos GP.65/3	15/-
Acos GP.65/1	17/-
Acos 67/1	14/-

STEREO


Acostereo 73/1 with two sapphires.	25/-
Acostereo 73/2 with Diamond L.P./Stereo and sapphire Std.	29/6
Collaro type C. Turnover. with 2 sapphires	19/11
Collaro S.C.I. Turnover with 2 sapphires	10/11
Collaro S.C.I. Turnover with Diamond L.P./Stereo and sapphire Std.	25/-
Ronette Stereo O.V. Turnover. with 2 sapphires.	25/-
Ronette Stereo type 105 & 106 with 2 sapphires	35/6
Ronette Stereo type 105 & 106 with Diamond L.P./Stereo and sapphire Std.	39/6

CAR PORTABLE RADIO last few left
\$10.95. Battery 2/8 B. & B. 7/6

207 EDGWARE ROAD, LONDON, W.2. | 33 TOTTENHAM COURT ROAD, W.1
Near Praeger St. PADLINGTON 3271/2 | Nearest to Goudge St. MUSEUM 4603
BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd.

152/3 FLEET STREET, LONDON, E.C.4
Telephone: Fleet Street 2833.
Open all day Thursday. Early closing Sat.

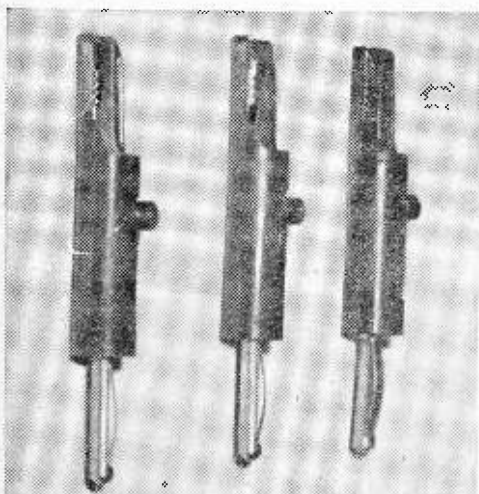HIRSCHMANN PLUG CROCODILE CLIPS & PANEL SOCKETS



The HIRSCHMANN AGS 10 Plug Crocodile Clips and BIL 20 Panel Sockets used on the AUDITRON described in this journal recently, may be obtained as follows: 3 of each AGS 10 (Red or Black) and BIL 20 (Red or Black) for 11/-, post free, cash with order, from

NEOFLEX LTD.,
115a, Cricklewood Broadway, London, N.W.2.

SOLDERING EQUIPMENT

by



PRECISION SOLDERING for the ELECTRONICS INDUSTRY

Comprehensive range—Robust & reliable
- Light weight - Rapid heating - Bit sizes
3/32in. to 3/8in. - 'Permabit' or Copper
bits - All voltage ranges 6/7v. to 230/
250v. - Prices from 21/-.

Also

- Plastic Cable Strippers
- Miniature Solder Pots
- Heat Guards
- Long Life Bits

Illustrated is the 25w. 3/16in. replaceable
bit model with safety shield.

ADAMIN— new range of pre-
cision micro-soldering instruments—
Have you had details?

Brochure No. S10 sent free on request.
Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LTD.
28 Sydenham Road, Croydon, Surrey
Phone: CROYdon 8589 Grams: Litesold Croydon



THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

ATTENDING COURSE

Full-time One-Year Course in Radio and Television. College course in basic principles for prospective servicing engineers.

Next course commences 3rd September, 1963. This course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations. Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:
The Pembridge College of Electronics (Dept. P11)
34a, Hereford Road, London, W.2

Please send, without obligation, details of the One-Year Course.

Name _____

Address _____

Magnetic Pickup

FOR AN ACOUSTIC GUITAR

incorporating a
transistor pre-amplifier

by J. Banthorpe

THE electric guitar has gained much popularity of late owing to its prominence in popular music. Many people, who already play a conventional acoustic guitar, would like to change to an electric guitar, for greater versatility, but are deterred by the cost.




The alternative is to modify the acoustic guitar by the addition of a pick-up. The magnetic pick-up described here has none of the following disadvantages associated with the more usual contact microphone type of pick-up.

1. Acoustic feedback if used too close to the loudspeaker.
2. Sensitivity to extraneous noises.
3. Inadequate frequency response.

It is essential however that steel strings be used on the guitar.

Construction

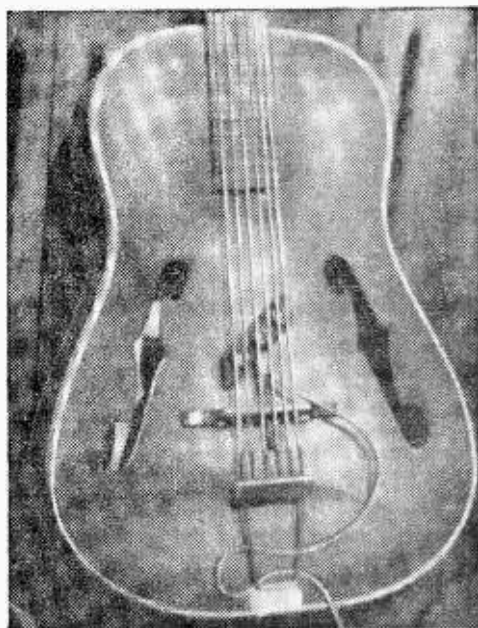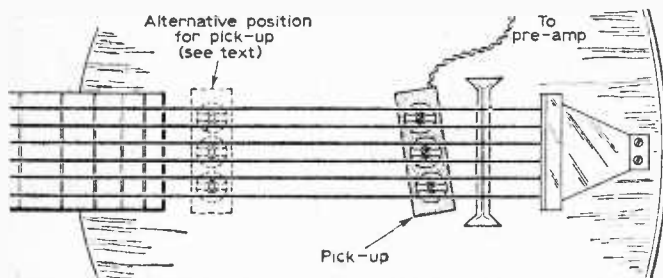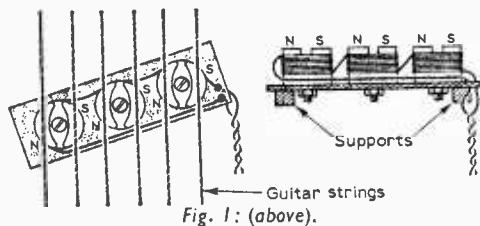Three small button magnets,* each drilled to take a small screw, are required. These are bolted to a paxolin board so that one magnetic pole lies under each string, as shown in Fig. 1.



The pick-up in place on a guitar

Each magnet is wound with 20-30 turns of 32s.w.g. enamelled wire. The gauge of wire is not critical. The pick-up is mounted on the guitar body as shown in Fig. 2. With the pick-up mounted near the fret-board a mellow sound is produced.

If, however, it is mounted near the bridge, several harmonics of the original note are picked up and produce the popular "twangy" sound.

The steel strings are magnetised by the underlying magnets and when plucked, the resultant change of magnetic flux induces an e.m.f. in the surrounding coils.

The pick-up is connected to an amplifier via a matching transformer. A small pentode output transformer is suitable for this purpose. It is advisable to keep the matching transformer well away from the amplifier since it is sensitive to "hum" radiated by mains transformers.

The pick-up may be connected to the transformer by up to 5yd of twin flex with negligible hum pick-up. If greater lengths are required screened cable should be used. Screened cable should also be used from the transformer to the amplifier.

Extra Gain

The output from the matching transformer is some 5-10mV. It is therefore not possible for those not possessing a high-gain amplifier, to connect the transformer output directly to the gram sockets of a radio receiver or to a gramophone amplifier.

In order to use the pick-up in conjunction with a gram amplifier,

*Suitable button magnets are manufactured by Eclipse Ltd. and are on sale in many tool and hardware shops.

—continued on page 274

pocket SIGNAL INJECTOR

BY R. W. KNEESHAW

NO claim is made by the author with respect to the originality of the circuitry, as this is purely a free running multivibrator (collector coupled). The circuit diagram is shown in Fig. 1.

All the author claims is, perhaps, some originality in the novelty of constructing such a multivibrator in a small penlight torch container, which is readily obtainable at 1s. 10d. from Woolworths. This container is readily adaptable without any physical modification, especially since it has a shaped plastic "nose cone" which allows neat professional streamlining of the probe tip to be obtained.

The whole unit costs about 25s. to construct, and is as professional in appearance as those signal injectors which are available on the market costing about £4.

The output is of square wave form at a fundamental frequency of about 2kc/s and thus is rich in harmonics, and so provides a continuous note when injected into any receiver, up to about 25Mc/s.

Holes A, B and C are of $\frac{3}{32}$ in. diameter and should be bored using a twist drill, all the other holes however are quite small and in fact were pierced by means of a red-hot sewing needle, in the positions indicated.

Next cut a piece of spring brass or phosphor bronze of about $\frac{1}{32}$ in. thickness to the dimensions shown in Fig. 3. Such a piece of spring brass is easily obtainable from the brass terminal strips found on some 4.5V torch batteries.

Now bend this brass strip in a gentle curve and attach it to the paxolin chassis by pushing the thin tongue at the end of the strip through hole B and bending it over. Also attach two paper clips to the chassis i.e. one at either end. This is done by snipping off about half of the length of the "legs" of the paper clips and bending the remaining part of the legs through the holes A and B.

The "legs" of the paper clips after bending should be tightly squeezed to the chassis by means of pliers, and then soldered so that the clips remain firmly attached and do not work loose. The attachment of the paper clips and brass "leaf spring" is shown in Fig. 4.

Wiring

Take resistors, R1, R2, R3 and R4 and cut all their connecting wires until in each case the wires left are about $\frac{1}{16}$ in. long. Tin these remaining wires very lightly. All resistors should be of the miniature $\frac{1}{4}$ W type in order that they will not impede the chassis when it is finally pushed inside the penlight casing.

The resistors should have their leads bent and passed through certain specific holes in the chassis and should be so disposed as shown in Fig. 5.

The first thing to be soldered is the lead of R2 to paper clip "A" (see also Fig. 6). Solder next the emitter leads of both Tr1 and Tr2 to the bent-over tongue of the previously mentioned brass strip. A heat sink *must* be used when soldering all connecting wires of transistors and the author found that a pair of metal tweezers with pointed ends were sufficient in soldering the transistor leads on this tiny chassis. The tweezers, of course, should always grip the wire between the transistor and the point of soldering.

Next the base and collector wires must be fed through the correct holes in the chassis (as shown in Fig. 5) and soldered lightly and quickly to their respective resistors (the soldering being done under the chassis, of course).

C1 must now be soldered in place. It is placed in position across the chassis in the space now existing between the two transistors. The leads of

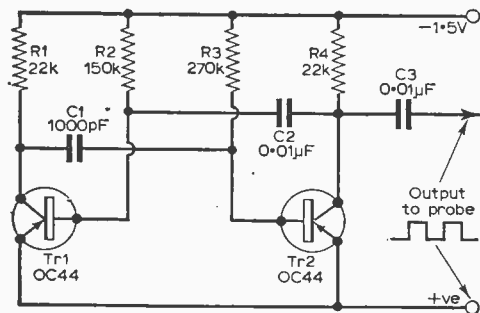


Fig. 1: The circuit of the instrument.

The power supply is entirely self-contained and is very inexpensive comprising of a single 1.5V leak-proof U7 penlight cell, the life of which is probably only determined by its deterioration with time.

Construction

The complete multivibrator is constructed on a small rectangular chassis of paxolin $1\frac{1}{2}$ in. long and $\frac{1}{8}$ in. wide, and $\frac{1}{32}$ in. thick. Celluloid or Perspex or similar material is not suitable since during the construction this would more than likely become twisted or burnt by the heat of the soldering iron. This chassis must have a number of holes bored in it at specific points, as in Fig. 2.

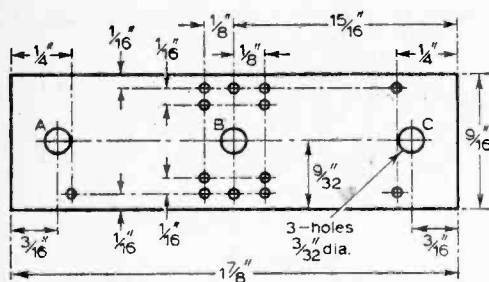


Fig. 2

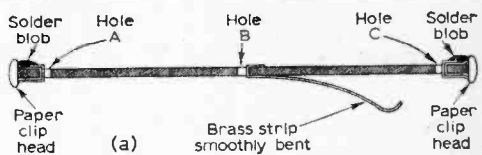


Fig. 4

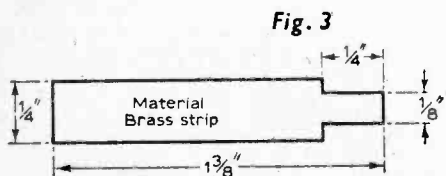
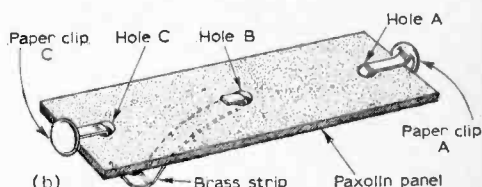


Fig. 3

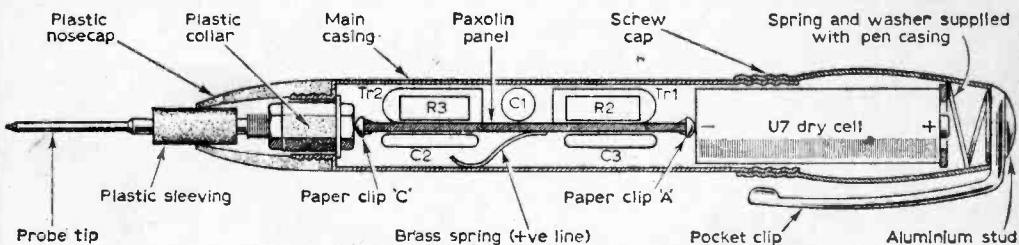


Fig. 5



Sectional view of the completed signal injector.

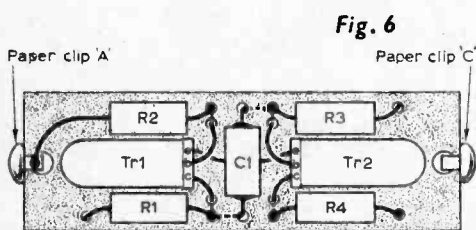


Fig. 6

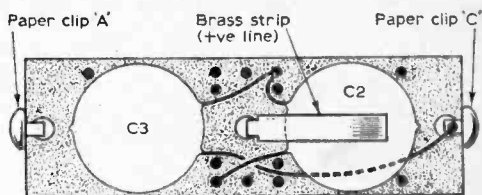


Fig. 8

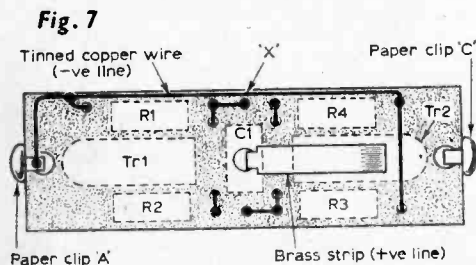


Fig. 7



Fig. 9

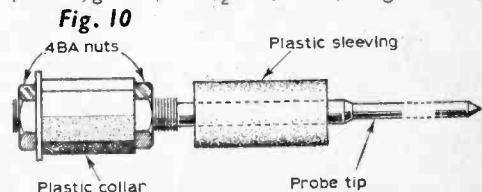


Fig. 10

C1 must be threaded through the two remaining holes in the chassis and one lead soldered underneath the chassis to the junction of R3 and the base of Tr2, the other lead being connected to the junction of Tr1 collector and R1. The mounting and connecting of C1 is shown in Fig. 6.

Now the underchassis wiring must be completed. A piece of thin gauge tinned copper wire (the -ve battery line) must be run along the underside of the chassis as shown in Fig. 7. It must first be soldered at paper clip "A" and terminated at the underside connection to R3 and, as seen in Fig. 7, during its run it is soldered to R1 and R4 (to the ends of these resistors, which are as yet unconnected). In the region of "X3" (Fig. 7) this copper lead must be bent outwards slightly to prevent it from touching the other underchassis connections to R1 and R4 so that it does not short out these two resistors.

All that remains to be done now is to wire in capacitors C2 and C3. These are both of the "disc" type and must be as small as possible. Such capacitors were found to be more suitable, since the tubular type will probably be too large and prevent the chassis from being pushed into the penlight casing.

The connecting wires of C2 and C3 should first be lightly "tinned" and then insulating sleeving slipped over them. Fig. 8 shows how C2 and C3 are connected. These of necessity must be laid flat against the underside of the chassis. One wire from C3 and one from C2 are both connected to R4 at the point shown and the other lead of C2 is connected to R2. The other lead of C3 is soldered to paper clip "C".

The chassis is now completely wired together.

Fitting the Chassis into the Casing

The penlight casing actually forms the connection from the battery positive terminal to the chassis via the brass spring fixed to the chassis. It is therefore imperative that the inside of the case must be clean to ensure good contact between it and the brass spring. To ensure this, scrape the inside of the "bulbholder"-half of the penlight case with a small round file, especially at the point where the brass spring contacts the casing.

In the "bulbholder"-part of the casing is a small spring. This should be extracted and placed inside the screw cap instead.

The chassis may now be pushed inside the "bulbholder"-part of the casing and if the chassis dimensions have been carefully adhered to it should make an easy but rigid fit.

Paper clip "C" should be made to enter first, and care should be taken to ensure that the brass strip enters the casing properly. The chassis should then be pushed right down to the end of the casing by means of a pencil pushing against paper clip "A". The U7 penlight cell must now be pushed into the casing until its -ve terminal (the bottom of the zinc container) is hard against paper clip "A". The penlight cap may then be screwed over the lower casing.

Preliminary testing

Although the probe tip has not yet been built

the injector should now be working and, to ensure that it is, place a piece of wire into the aerial terminal of any available radio receiver and touch the other end of the wire on to paper clip "C", which may be exposed at the bottom of the casing if the plastic "nose cone" is unscrewed.

A continuous note should then be heard in the radio receiver. If no note is heard, probably the screw cap is not screwed on far enough and should be screwed on further. If this is done and a note is still not heard in the receiver it is quite likely that the brass strip is not making good contact with the inside of the casing. To cure this the chassis should be removed (by pushing on paper clip "C" with a pencil) and the inside of the casing scraped some more with a small, round file or sandpaper. Also bend the brass strip very gently out a bit further.

If this still doesn't produce a note in the receiver then there must be a mistake or bad connection in the chassis wiring, which should be rechecked.

The next job is to construct the probe tip.

Making the Probe Tip

The probe tip is made from a piece of 4B.A. brass screwed rod which is easily obtainable from a local "hobbies" shop. Alternatively a long 4B.A. bolt (longer than 2in.) may be used.

A 2in. length was sawn off the brass screw rod and placed in the chuck of a hand drill, which was clamped in a vice. The hand drill was used as a crude type of lathe and, apart from doing the job on an actual lathe, an electric drill would make this part of the operation a little easier. However, the brass rod was fairly soft and even using the hand drill the probe tip was correctly fashioned in about half an hour.

The brass rod was thus filed to the correct shape while being turned as fast as possible in the chuck of the hand drill. The shape to which the rod is turned is shown in Fig. 9.

The original 4B.A. thread is left on for $\frac{1}{4}$ in. of length (this part was in the chuck of the drill). The next $\frac{1}{4}$ in. is turned down to $\frac{3}{16}$ in. diameter and the next $\frac{1}{4}$ in. is turned down to $\frac{1}{8}$ in. diameter.

Next obtain a standard type aerial plug. These are readily obtainable from any radio shop. Saw the plastic screw cap portion of this aerial plug about $\frac{1}{4}$ in. from the top (cable entry end). Fix this portion of the plug cap over the probe tip by means of two 4B.A. nuts as shown in Fig. 10.

Strip about $\frac{1}{2}$ in. of plastic sleeving off a piece of thick plastic-covered wire (such as is used to take the e.h.t. to the tube in TV sets) and slip this sleeving over the probe tip to the position shown.

Alternatively, obtain a polystyrene ink cartridge of the type used in certain types of fountain pen these days. These are readily obtainable from any stationery shop for 4d. Puncture both ends of this cartridge and empty it of ink and then cut off a portion $\frac{7}{10}$ in. long from the "stepped" end. Slip this portion over the constructed probe tip.

Assembling the Injector

The probe tip is now complete and the chassis should now be removed from the casing and the probe tip dropped in point first until it protrudes

through the original "bulbholder" section. The chassis may now be replaced inside the casing (paper clip "C" entering first), the battery then being correctly positioned and the screw cap replaced.

The plastic "nose cone" may now also be screwed in place, being threaded over the protruding probe tip. The probe tip and plastic "nose cone", both correctly positioned, are shown in the illustration on page 237.

The finished signal injector is extremely small and light and may be easily clipped into a pocket. The injector is switched on by screwing the penlight cap fully on and the instrument is switched off by unscrewing this cap half a turn or so.

Warning

One point must always be remembered. *Never insert the battery the wrong way round, otherwise damage to the transistors will result. The battery must always be inserted such that its positive terminal enters the screw cap of the container first.*

It must also be understood that the squarewave output from the injection appears across the output

However, this injector may also be employed as a fault-finding aid in mains operated equipment, where quite often it is found that the chassis of such equipment is live. The user of the injector should thus remember that if he then connects the penlight casing to the chassis of the equipment under test he is in danger of obtaining a shock from the injector.

This danger can be alleviated in such circumstances if, for the purposes of testing on such live equipment, the user completely wraps or binds the injector with insulation tape, which can quite easily be peeled off later when the job is completed.

USING THE SIGNAL INJECTOR FOR FAULT FINDING

It is not claimed that the injector is infallible as a fault finder as, for instance, it probably will be of no use if the fault is a transistor that has for some reason lost its gain but is not in any way open circuit. When this occurs the signal from the injector would still pass through the faulty transistor, although it would not be amplified by

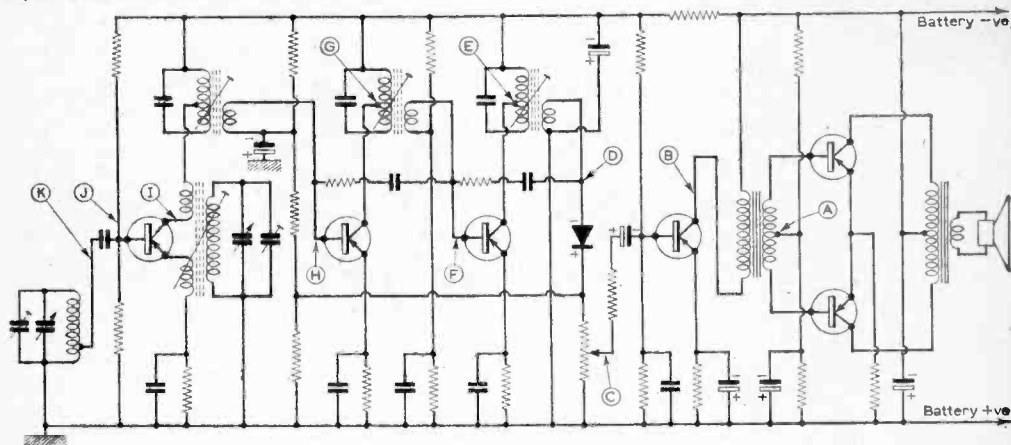


Fig. 11: A typical transistor superhet circuit.

probe tip and the -ve battery line (the penlight casing) and so, when injecting the signal into a receiver or other piece of apparatus, it is not sufficient for the probe to be placed on the point of investigation. The penlight casing must be connected also to the -ve or earthing chassis of the equipment being tested. To facilitate this a small connecting lead must be constructed which is merely a piece of plastic-covered flex (about 18in. long) with a crocodile clip (of the miniature type which are readily available these days) fixed to each end.

When testing circuitry one end of this lead must be clipped to the -ve line or chassis of the equipment under test and the other end should be clipped on to the metal pocket clip attached to the screw cap of the penlight casing.

This injector was primarily constructed for use as an aid to servicing transistorised equipment where in a majority of cases no voltage exists which make it dangerous for the main casing of the injector to be connected directly to the chassis of the equipment being repaired.

The reason is, of course, that such a faulty transistor is still a good electrical connection between its preceding stage and its succeeding stage (unlike a valve which, when it has lost its emission completely, would isolate the two stages by virtue of the non-conducting vacuum existing between its anode and cathode).

However, the device is very useful for faults which are of the "broken circuit" nature (i.e. open circuit resistors or capacitors or poor connection on to a printed circuit board) and in such cases can be used to isolate the stage in which the fault is present very quickly. How it may be used to do this is described below.

Consider the fault to exist on a typical transistor superhet receiver the circuit of which is shown in Fig. 11. Assume that the obvious initial precaution of checking the battery voltage has been carried out with a voltmeter and shown the battery to be satisfactory.

Then clip the wander lead of the injector on to the +ve battery line of the set and place the probe

—continued on page 270

7 VALVE STEREOGRAPH

By J. B. Willmott


THIS is a reasonably simple receiver capable of reliable reception of the long and medium wavebands, and having a good standard of reproduction from gramophone records (both mono and stereo), yet without a multiplicity of variable controls. In order to keep costs down, "single ended" a.f. amplifiers are used on both channels, and, as an output of 3W per channel is more than adequate for domestic listening, low h.t. consumption output pentodes of the EL32 type (now readily obtainable at very low prices from advertisers in this magazine) were chosen, and the total h.t. consumption of the receiver was found to be just under 100mA, and therefore within the limitations of a mains transformer of modest size and cost. The first stage of a.f. amplification on each channel is provided by one half of a 6SL7 valve; a dual-gang potentiometer in the grid circuits provides simultaneous control of the volume of both channels, whilst a further dual-gang potentiometer, one half of which is connected "in reverse", controls the input to the EL32s and thus acts as a balance control. Fixed tone correction is provided by a simple resistor/capacitor combination across the primary of each output transformer, thus reducing the number of panel controls, and this has been found perfectly satisfactory in practice. With the moderate amount of stage gain available in the simple a.f. amplification circuits used, there is insufficient to spare for more elaborate tone correction methods. Intending constructors should not be deterred by this

seemingly ultra-simplified audio circuitry—the results on both radio and gram are quite pleasing; well up to the standard provided by the average commercially produced radiogram in the medium price range.


Radio Circuit

The radio section has been accommodated on the same chassis as the audio amplifier circuits. Simplicity is again the keynote. The first valve, an ECH35, is used in a conventional frequency changer circuit; in order to simplify switching arrangements, and to select long or medium wave radio, or changeover to gram reproduction, yet use only a single wafer 4-pole 3-way switch, a certain amount of ingenuity in design was needed. The aerial is bottom-capacity coupled to the tuned windings of the long and medium wave aerial coils L1 and L2 (see Fig. 1), which dispenses with the need for switching the aerial to the respective primary coupling windings. In order to eliminate modulation hum, often troublesome in bottom-capacity coupled circuits, the resistor R1 is provided. Note that C2, 0.0025 μ F, is a critical component as it acts both as bottom-capacity coupler to the coils and also as the decoupling component for the a.g.c. line. Hence, the value specified must be used.

The tuned windings of L1 and L2 are selected by the first section of the switch, S1a, for application to the mixer grid of V1. Note that in the "gram" position of the switch, the mixer grid is connected direct to earth in order to silence any incoming radio signals. In the oscillator section of V1, only a single oscillator coil, L3, is used on both wavebands, by virtue of the fact that when S1b is set to the long wave position, the additional capacitor PC2 is brought into play in parallel with the main tuning capacitor (VC1b). This provides correct tracking over both wavebands. A value of 390pF was found suitable in the prototype, but this may require slight variation to compensate for stray circuit capacities in individual units. Note that the medium wave fixed padder capacitor PC1 (470pF) remains in circuit on both wavebands. As in the "mixer" section, with the switch in the "gram" position, earthing of the grid (in this case the oscillator grid, of

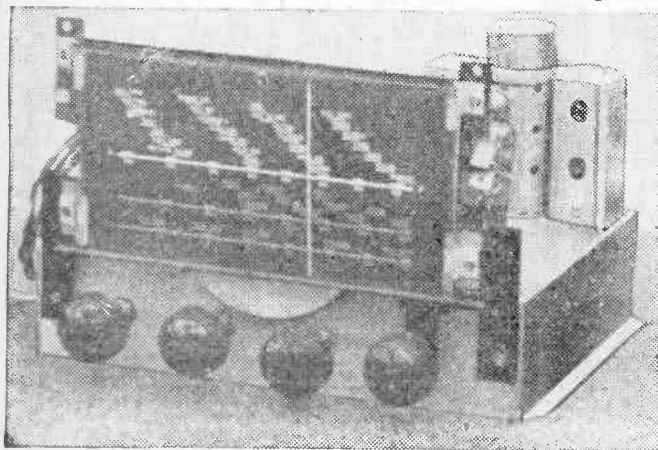

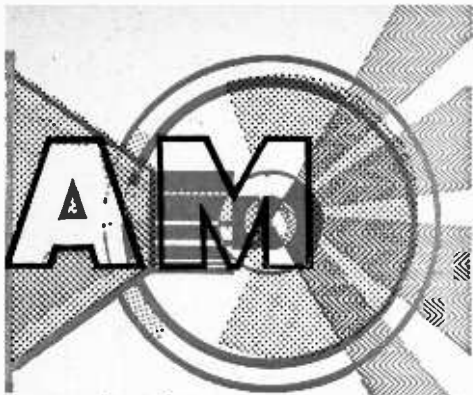The finished tuner and amplifier chassis.



course) is carried out to prevent any danger of radio break-through.

'Common' Resistors

Standard iron-core tuner IFT's designed for 465kc/s operation are used for i.f. coupling—V2 is an EF39 valve acting as a conventional i.f. amplifier. It will be noticed that certain economies of components have been made by using "common" resistors and decoupling capacitors for screen grid and cathode circuits of V1 and V2; this considerably simplifies the wiring up of these stages and in no way detracts from the performance. At the anode of V2, part of the signal is tapped off by C7, and applied to one of the diode anodes of V3 (which is a 6H6 valve) to produce a.g.c. voltage across R8, which is then applied to the control grids of V2 and V1. As the cathode of V3 is connected direct to chassis, a.g.c. is of the non-delayed type, which is quite satisfactory for l.w. and m.w. reception conditions.

The second half of V3 acts as signal demodulator, the resultant a.f. voltage being filtered by R9 in conjunction with C9 and C10, developed across R10 and fed via the d.c. blocking capacitor C20 to the "radio/gram" changeover portion of the switch. The two remaining poles, S1c and S1d, are used for this purpose, and are so wired that on "radio" (long or medium wavebands) both a.f. amplifier channels are connected in parallel and mono reproduction of radio signals is given by the two loudspeakers. In the "gram" position, each channel is fed separately from the left-hand and right-hand socket of the stereo pick-up input panel, and stereo reproduction of records is achieved. Ordinary "mono" records can, of course, be played using the same pick-up, in which case both channels will carry equal and identical signals, giving balanced mono reproduction from the two loudspeakers.

Components and Layout of Chassis

The entire radio tuner section and twin channel audio amplifier is easily accommodated on an aluminium chassis measuring 12in. x 9in. x 2½in. (this being a standard size obtainable ready made from a number of advertisers in this magazine); the power supply components are mounted on a separate chassis, measuring 11in. x 6in. x 2½in., and this can conveniently stand on the "floor" of the cabinet which houses the completed instrument. Power supplies are taken via an octal plug and socket mounted on the latter chassis, and a colour coded 4-way cable conveys h.t. and l.t. supplies to the main chassis.

It will be observed that no "on-off" switch is

positioned on the receiver chassis; instead, a separate switch of the toggle type is inserted in one of the mains leads and mounted at a convenient point, either adjacent to the receiver controls, or, as in the author's case, on the rear cover of the cabinet. Isolation of the function of "on-off" switching from all other controls, enables volume and balance controls to remain undisturbed when switching the receiver on and off, and this considerably reduces wear of the volume control. Care should be taken to see that the mains supply to the gram motor is taken off "after" the toggle switch, so that the latter is entirely disconnected from the mains when the receiver is switched "off".

Potentiometers

There were no specialised components used in the prototype, and there is no reason why components of any reputable make should not prove satisfactory. It is, however, emphasised that the correctly matched dual-ganged potentiometers specified for VR1 and VR2 positions, designed for stereo amplifier circuits, must be used. VR1 should be a dual 1M log/log component, whilst VR2 should be of the 500k log/antilog type. Suitable alternative valve types for V1, V2 and V3 are suggested in the components list. For the remaining valves the specified types should be used, except if a mains transformer having a rectifier heater winding giving 4V is used, an MU14 (VU39A) can be used instead of the 5Z4. Any reliable make of mains transformer rated at 250-0-250V 100mA h.t., and 6.3V at 2.1A (or more), plus 5V (or 4V) at 2A, will suffice. In the prototype, a component of the totally shrouded top chassis mounting pattern was used. All resistors and capacitors should be within the ratings shown on the components list,* and, of course, it cannot be too strongly emphasised that all capacitors must be in first-class condition. Use of dubious components stripped from long-stored government surplus units should be avoided. It is far wiser to pay a few coppers extra for new capacitors in the first place, than to face hours of tedious fault tracing later.

The tuning coils specified are small in size, and easy to mount (a single 6BA screw), and their connections are clearly colour coded. The coupling windings, connected to the green and black tags, are not used on the aerial circuit coils, and are ignored. Adjustable trimmers of 0-50pF are wired across the tuned winding of each coil, and if a "triple bank" (i.e., three trimmers mounted side by side) is obtainable, as was used in the original, these are easily and neatly mounted adjacent to the coils. Actual mounting positions are not shown in Fig. 2, as this will depend on the component(s) used. It is absolutely essential that the oscillator coil, L3, be correctly wired into the circuit, together with its associated trimmer and padder capacitors. An error here will almost certainly prevent signals of any kind from being received.

Chassis

The layout and drilling dimensions of the main chassis are given in Fig. 2. Note especially the orientation of the valvoholders as given by the position of the locating spigots. The diagram

* The Components List will appear in the following issue.


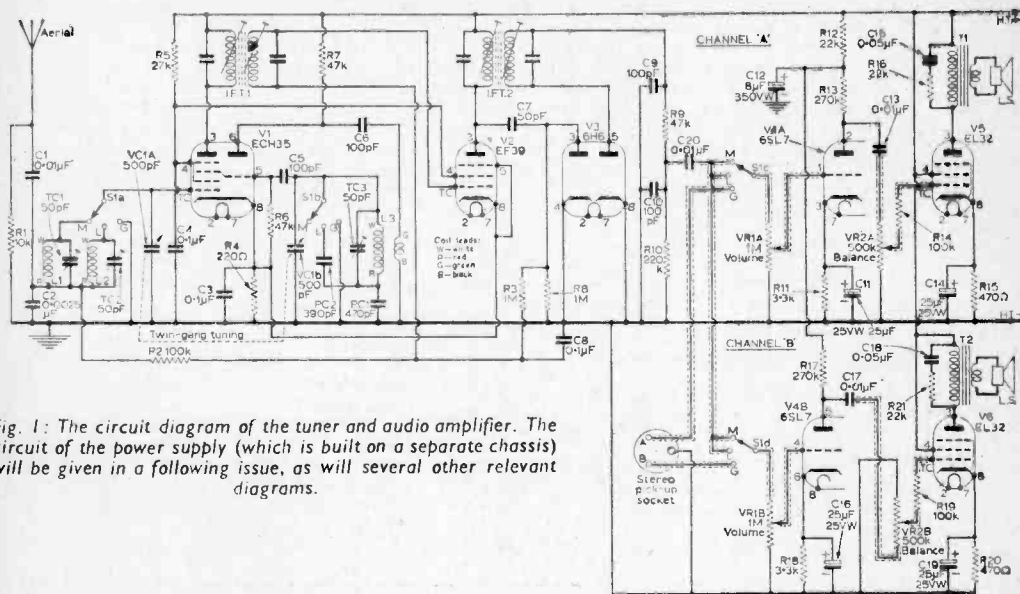


Fig. 1: The circuit diagram of the tuner and audio amplifier. The circuit of the power supply (which is built on a separate chassis) will be given in a following issue, as will several other relevant diagrams.

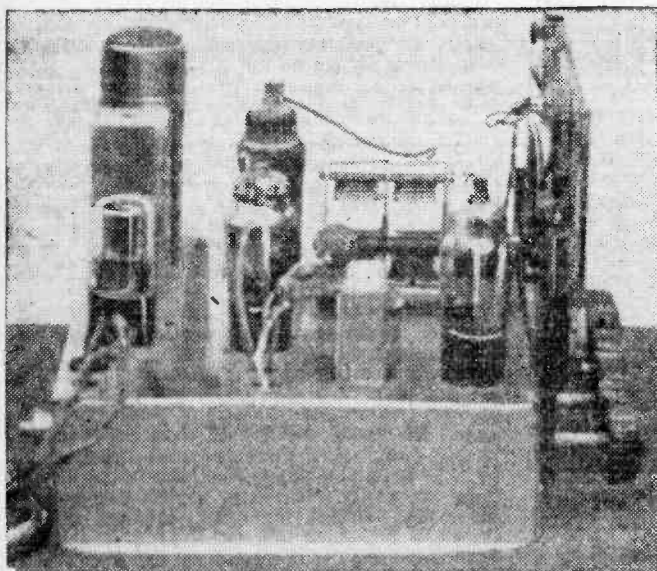

A side view of the 'main' chassis.

represents the top view of the chassis, and should be consulted when mounting the components, but it is often advisable to use the actual components as templates for marking the exact position of fixing holes on the chassis. The drilling size of the principal holes is clearly shown, except in the case of the valveholder fixing holes, which are all of 6B.A. clearance, but for clarity, size has been omitted from the diagram.

Dial Assembly

When satisfied that all holes have been drilled, the mounting of components may proceed. There is no hard and fast rule as to the order in which this should be carried out, but it is suggested that the valveholders be fixed in position first; a single 6B.A. soldering tag is attached to the fixing bolt nearest the locating spigot in each case, to form a convenient anchoring point for earth connections. This can be followed by mounting the various socket panels on the rear chassis runner, and the balance, volume and wavechange controls on the front runner. The dial assembly is then fixed in position, by first removing the flywheel from its drive spindle, in order that the spindle may pass through the hole provided in the chassis runner. The flywheel is then remounted on the inside of the chassis. The dial used has waveband markings for the short waveband (16-50m) in addition to the long and medium wavebands. But it is a simple matter to remove the s.w. markings from the glass dial—a gentle rub with a coarse cloth soaked in detergent will be found quickly to remove the lettering without scratching the glass. There is, of course, no reason why the markings should not remain if the constructor prefers.

The 2-gang tuning capacitor should next be bolted down, making sure that its spindle engages with the hole provided in the drive drum on the dial assembly without straining. The dial should be so adjusted that with the pointer opposite the 550m mark, the plates of the variable tuning capacitor are fully closed. Mounting of the remaining components may now proceed, noting that the output transformer for Channel A is mounted below chassis towards the rear, and that

for Channel B is mounted above the chassis towards the front. Rubber grommets should be inserted in the hole providing access for the power supply and in the three holes through which pass the leads to Channel B output transformer, and the top cap (grid) connections of V5 and V7. The two tagboards, which are used in the construction, should not be mounted until the associated resistors and capacitors have been soldered to them.

TO BE CONTINUED

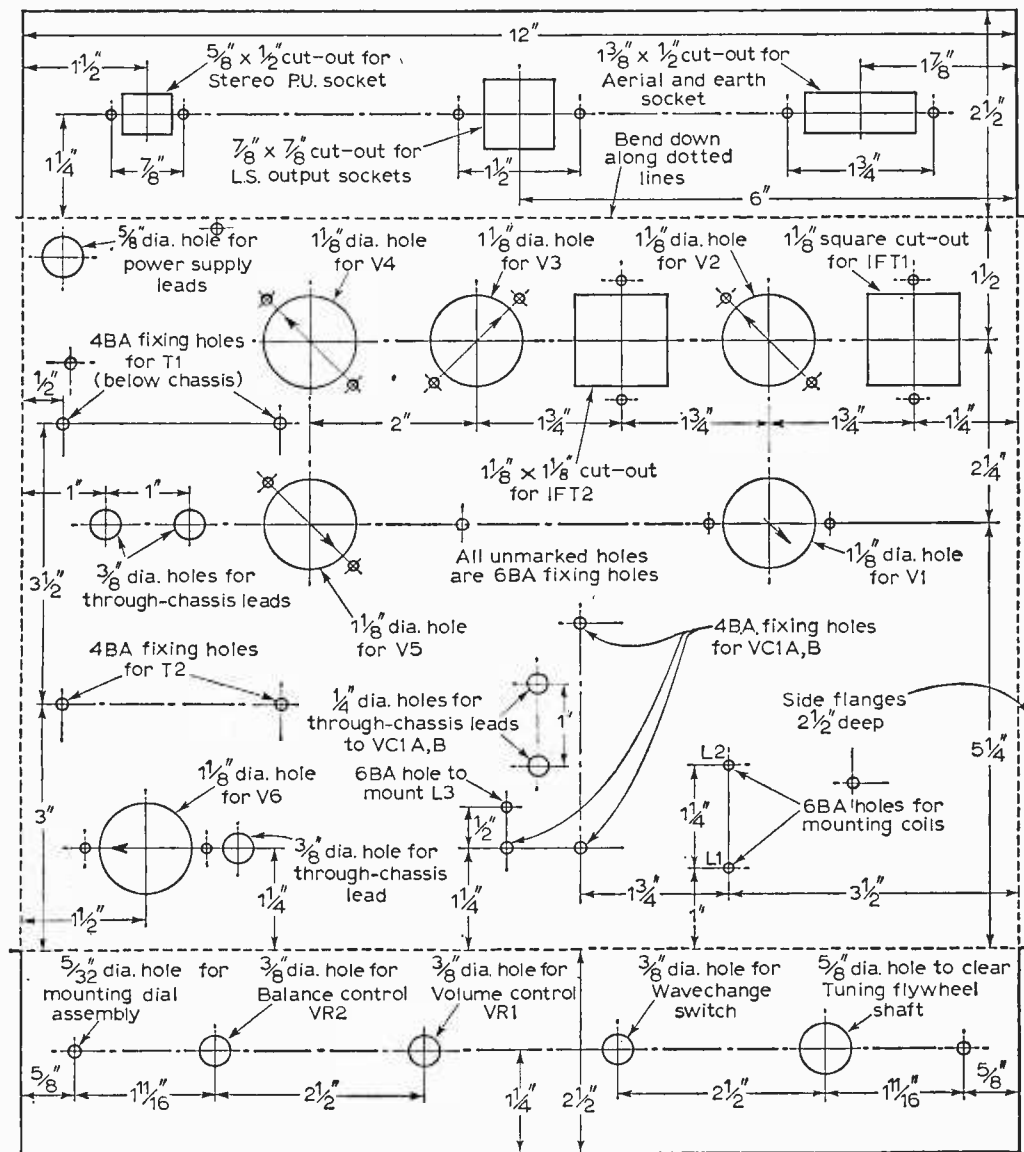


Fig. 2: The dimensions and drilling details of the main chassis.

more about

CATHODE FOLLOWERS

SOME NOTES ON USING CATHODE FOLLOWERS AS AUDIO OUTPUT STAGES AND AS SIGNAL STAGES FEEDING LONG RUNS OF SCREENED OR COAXIAL CABLE

by E. McLoughlin

IN the series of articles on Cathode Followers (Jan-March, 1962) it was stated, quite correctly, that the effective output impedance of a cathode follower is $1/g_m$. It was then further stated that, accordingly, maximum power output into a consumer load is obtained when this load has an impedance also equal to $1/g_m$ of the cathode follower valve, in common with the same rule for power generators of any kind.

As some readers pointed out, this statement should have been amplified to read, in the case of the cathode follower, that maximum power-output for a given input-signal drive at the grid is obtained when the load impedance is $1/g_m$, provided also that the applied drive does not lead to excursions beyond the linear portion of the valve characteristic.

Now it is in practice a fact that, for normal valves, the acceptable grid-drive is very small in a cathode follower using such small output-loads as $1/g_m$. Some considerably higher load may thus give more realisable total output power, even though the power developed per volt of input drive is much less than in the matched condition. The much greater acceptable drive voltage then more than compensates. Thus (Fig. 1) one finds loads of several thousand ohms or thereabouts "ideal" for cathode follower audio-output stages, instead of a few hundred ohms, as would be dictated by the matched-load condition $R=1/g_m$.

These facts were, of course, correctly embodied in the practical circuits of the original articles mentioned. A practical circuit as shown in Fig. 1 can thus be arrived at simply by moving the normal output transformer from the anode circuit of a conventional output stage (Fig. 2) to the cathode circuit. Some adjustment of primary tapings may be required for optimum results, and the d.c. resistance of the transformer primary should be about equal to the normal cathode resistor, to set the normal d.c. operating point of the valve.

Normal Loading Law

It is not difficult to see why a cathode follower apparently disobeys the "normal law" for maximum power loading. The basic function of the cathode follower—basic circuit Fig. 3—is to attempt to reproduce a voltage change across R_k about equal to the voltage change applied across R_g . Now if R_k is extremely small, as it would be if it is equal to $1/g_m$ (reciprocal of the slope of the valve), a very large current change is needed through it to produce a voltage drop change across it equal to even a moderate grid voltage drive. Such huge current excursions rapidly drive the valve beyond its linear range, unless the input drive is kept very small. If, however, the value of R_k is large, only small current excursions are required through it to follow even large grid drives, so that operation remains within the linear portion of the characteristic even for large drives.

The ultimate reason, therefore, why a cathode follower departs from the usual law for extracting maximum power from a generator is that it does not obey Ohm's Law for all conditions of operation. Ohm's Law simply requires that an electrical component have a constant effective resistance, given by the ratio of applied voltage and resulting current under all circumstances. This is true for a valve only as long as the operating point does not run beyond the linear range of the characteristic.

When one looks at the matter even more closely, one finds that the simple matching law for maximum power output in fact hardly ever applies for valve circuits. Thus a pentode output valve has an anode impedance much greater than the optimum anode load for maximum achievable output power in a conventional circuit. Beyond the normal linear portion of the pentode characteristic the anode impedance is very much less; we would thus expect a "mean" to indicate lower loading impedance for optimum power output—as is also in fact the case. However, this way of looking at it is rather pedantic; consultation of the characteristics in conjunction with load lines for proposed load values, in the normal manner, is always the simplest practical design-method.

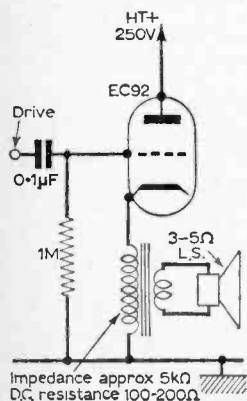


Fig. 1: A typical low-power cathode follower output stage for use in audio frequency applications.

The Transistor Equivalent

It is interesting to point out that, in the case of the Emitter Follower, which is the rough transistor equivalent of the cathode follower (Fig. 4), the effective output impedance is given by the impedance of the base drive generator G_b divided by the current gain of the transistor in earthed emitter arrangement (about 10 to 50 for most normal transistors). Provided that the impedance of G_b is not too low, there may certainly be enough linear current excursion within the characteristic of a high-current transistor to make the matched load (G_b divided by current gain) also about equal to the optimum achievable power load. These facts led to the unusual possibilities with emitter followers as exemplified in our recent constructional article "A Central Control Amplifier" (Nov. 1962—Jan. 1963).

A matched cathode follower or emitter follower always generates a total output e.m.f. equal to the input drive. This is distributed in direct proportion between the effective internal output impedance and the actual output load. In the matched condition, when both impedances are equal, the voltage across the output load is naturally exactly one half of the input drive voltage.

In the case of a cathode follower load with a very much higher output load, to give maximum achievable power, the drop across the internal impedance is negligible, and the output voltage is virtually equal to the input drive voltage. If the normal d.c. anode current rating of the valve is 1mA and the load resistor is R kilohm, much greater than $1/g_m$, then the acceptable linear drive will allow, very roughly, excursions from zero anode current to double the standing value. The peak-to-peak voltage excursion across the output load is thus $2 \times IR$ volts, which is also the required grid-input drive. This can be very considerable for example, if $I=10mA$ and $R=5k\Omega$ the peak-to-peak grid drive required for full undistorted output comes out as about 100V on these considerations. If the drive is a sinewave,


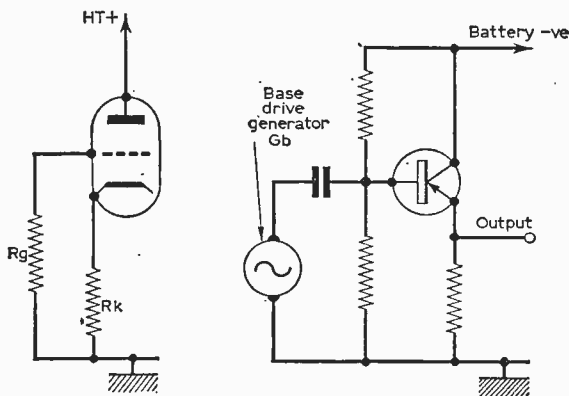


Fig. 3 (left): Basic circuit of a cathode follower circuit.
Fig. 4 (right): Basic circuit of an emitter follower circuit.

Fig. 2: A conventional anode-loaded output stage for comparison with Fig. 1.

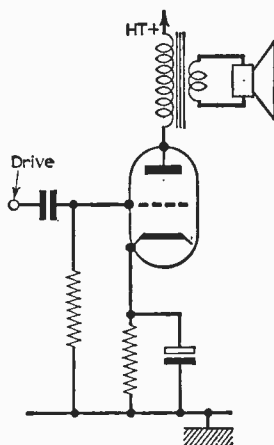

the r.m.s. current swing thereby represented is, as always, about a third of the peak-to-peak swing, i.e. some 6mA in our example. We know that 6mA flowing in $5k\Omega$, develops some 180 milliwatts of power, which is therefore roughly the actual power output to be expected in our example. This example corresponds roughly to that which would be achievable with a EC92 valve, and shows in general how to calculate expected power output in designing such cathode followers.

Capacitive Loading

A reader raised the further important question of the effect of large capacities in parallel with the output load of a cathode follower, such as present with long runs of coaxial or screened cable carrying the output signal to distant apparatus. The reader maintained that loads of this nature cause severe distortion unless the drive is drastically reduced. This statement, as it stands, cannot be correct, because it is well known that the cathode follower is an *ideal* output stage for feeding long runs of cable having considerable capacity.

If we desire to pass a signal through a load afflicted with large parallel capacity, yet maintain all rapid transients of the signal waveform across the load, then clearly the signal source must have *very low output impedance*, so that it can deliver the huge surge currents needed to *force* the voltage on the parallel capacity to follow sufficiently rapidly.

It is thus obvious that the cathode follower, with its essentially low output impedance, is eminently suitable for this purpose, within limits. And these limits are now clearly seen to be an imposition of a maximum frequency of permissible operation, not a primary limitation of the usable input drive. The signal frequency must not exceed the value where the parallel capacity

charging time becomes an appreciable fraction, say more than a tenth, of one cycle.

Now this characteristic charging time, or time constant as it is more usually called, is given as usual by the product of resistance and capacity in the charging circuit—here the product of cathode follower output impedance ($1/g_m$) and capacity parallel to the load.

These considerations, expressed as a simple practical formula, lead to the result that the signal frequency must not exceed $gm/10C$ kc/s, where gm is the slope of the valve in mA/volt and C is the capacity parallel to the output load, expressed in microfarads. One can use this formula to determine the maximum tolerable capacity for a given proposed signal frequency or vice versa. Taking a typical value of 10mA/volt for gm , and 50kc/s as uppermost frequency limit for a hi-fi audio amplifier, some $0.02\mu F$ is tolerable in parallel with the output load of such a valve used as a cathode follower stage. Using screened cable of capacity about 1pF per inch, about a quarter of a mile thereof is quite tolerable!

When using cathode followers for r.f., however, conditions could be more critical. Here the "White Cathode Follower" is sometimes used (Fig. 5), where another valve is used as cathode load in place of a resistor, this valve being also driven from a small anode load on the main valve giving an anode-gain of A times. The output impedance is then only $1/A$ of $1/g_m$, so that A times as much parallel capacity is tolerable in the output load.

If, however, one does go beyond the imposed limits, i.e. applies any signals with transients equal to or faster than the cathode time constant, then such transients act *in full* at the grid, without the negative feedback characteristic of all cathode followers. If positive, they then drive the valve momentarily up to huge anode and grid currents (unless the drive voltage is kept very small); the grid current can then cause a subsequent lengthy blockage on the grid drive input blocking capacitor and associated gridleak time constant. If the impermissible transients are negative, they can momentarily cut the valve off, without any after-effects, in general.

If the cathode follower stage is intentionally an audio output stage, and design considerations have been correctly applied for such frequencies, it is nevertheless clearly most important to watch that unwanted higher frequencies cannot inadvertently stray in! These could cause severe cross modulation distortion on the wanted signal, by methods as just described. Note, for example, that for this reason a top-cut filter was placed between the Y-amplifier and the cathode follower output stage of our recently published "Auditron" circuit.

Cable Impedance

We have thus seen that it is, in fact, one of the *principal advantages* of cathode followers that they are capable of driving loads afflicted with quite appreciable stray capacities, such as long coaxial cable runs.

However, it must be remembered that another solution to the problem of sending a signal down

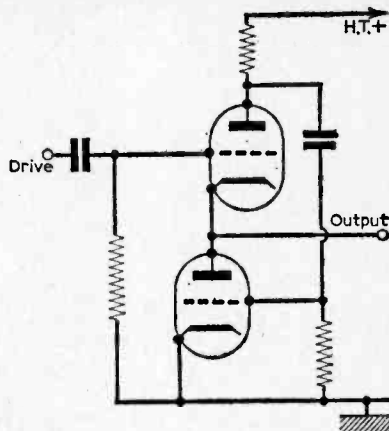


Fig. 5: Basic circuit of a white cathode follower which achieves output impedances much less than the reciprocal mutual conductance of the upper valve. The drawing is basic only—biasing components have been omitted for clarity.

a long run of coaxial cable exists at very high frequencies. Such a cable will, namely, have not only distributed capacity along its length, but also distributed inductance. These, in fact, work together at any frequency to compensate each other mutually, leaving merely the effect of a characteristic impedance (around 80Ω for common types of coaxial cable) which is purely resistive in character. Such a cable, terminated with a purely resistive load equal to the characteristic impedance, situated at the far end, will make the input end behave as a pure resistive load of value equal to the characteristic impedance, whatever the frequency and whatever the length of the cable. The generator feeding the cable then sees neither capacity nor inductance in its load, but just a pure resistance. However, we are tied to one particular load value—the characteristic impedance. This form of cable matching is quite essential when the frequency is so high that the length of cable involved is an appreciable fraction, say more than about a twentieth, of the wavelength involved, as otherwise interference between main and reflected signal waves at the points of mismatch would appear.

At lower frequencies one could use characteristic impedance matching, except that the characteristic impedance is generally so low that the usable drive and resulting signal transfer are rather small. It is then better to run the cable unmatched, relying on the tolerance shown by cathode followers for the resulting high capacities "seen" then on long cable runs. Even for the highest audio frequencies the electromagnetic wavelength is so large that at least a mile of cable run is tolerable before this becomes an appreciable fraction of the wavelength and would dictate characteristic impedance matching to avoid interference of main and reflected signal waves travelling down the cable.

EVENWith the **NEW**
MARK 8**BETTER
PERFORMANCE****PARISIENNE!!**THE "TEN STAR" TRANSISTOR
POCKET RADIO**NOW
ONLY
£3.19.6***All components supplied separately if required*

- ★ No external aerial or earth required.
- ★ Free 9-volt transistor battery.
- ★ Built-in wave change switch not pre-set. Dial graduated, L. and M. waves.
- ★ Printed circuit for easy assembly including high "Q" ferrite rod aerial.
- ★ High sensitivity carpiece if required, 5/-.
- ★ Cream Polystyrene case with carrying handle.
- ★ Hi-Fi 3-inch moving coil speaker.
- ★ All new components plainly marked, including best Mullard transistors.
- ★ Fully illustrated 30-page booklet with step by step instructions, 2/9.
- ★ Comprehensive speedy after-sales service.

*Money refunded
if not satisfied*PLEASE SEND FOLLOWING ITEMS
TICK BOX BELOW AS REQUIRED☐ FULL SET OF PARISIENNE
COMPONENTS £3-19-6☐ EARPIECE 5/-☐ BOOKLET 2/9 POST FREE

NAME _____

ADDRESS _____

I ENCLOSE CHEQUE P.O. MONEY ORDER INCLUDING
2/6 P. & P. FOR £. s. d.**POST
NOW!****WOLVERHAMPTON
RADIO AND TV SUPPLIES**42, DARLINGTON STREET, WOLVERHAMPTON
Telephone No. 20315

P.W.2.

IMPROVED

STANDARDS OF

ACCURACY AND RELIABILITY

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.



Mk 4

MULTIMINOR

D.C. Current: 100μA f.s.d. — 1A f.s.d. in 5 ranges
A.C. Voltage: 10V f.s.d. — 1,000V f.s.d. in 5 ranges
D.C. Voltage: 2.5V f.s.d. — 1,000V f.s.d. in 6 ranges
D.C. Millivolt range: 0 — 100mV f.s.d.

Resistance: 0-2MΩ in ranges using 1.5V cell.
Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
1,000Ω/V on a.c. Voltage ranges.

For full details of this great new pocket size instrument, write for descriptive leaflet.

AVO LTD

AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD • LONDON, S.W.1 • Tel.: VICTORIA 3404

M GROUP

MM17

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1S5, 1T4, 354, 3V4, DAF91, DF91, DK91, DL92, DL94 ... Set of 4 for 18/6
DAF96, DF96, DK96, DL96 ... 4 for 26/6

1A7GT 7/8	6QT7 8/-	50L6GT 8/3	ECC83 7/-	KT32 6/6	U52 4/6
1D5 9/8	6Q7GT 8/-	1B5BT 19/6	ECC84 7/-	KT61 9/-	U191 11/-
1H5GT 9/-	6SL7GT 5/9	AC1TH1 19/6	ECC85 7/6	MU14 6/6	U281 9/6
1N5GT 9/-	6SN7GT 4/9	AZ1 12/6	ECCF90 7/-	MX40 13/6	U282 15/-
1R5 5/6	6U4GT 9/9	CB11 12/-	ECCF92 8/6	N18 7/-	U291 11/-
1S4 8/6	6V6 4/3	CC835 13/6	ECH38 7/3	N37 10/-	U301 13/9
1S5 4/9	8V6GT 7/3	CL33 8/6	ECH42 5/9	PC95 9/-	U801 19/-
1T4 3/-	6X4 5/-	CY1 12/6	ECH81 7/3	PC97 9/-	UABC80 6/6
3A5 9/-	6X5GT 6/9	CY31 5/9	ECL80 7/-	PCC84 7/-	UAF42 8/-
3Q4 7/-	6X30L2 8/6	DAC32 9/-	ECL82 8/-	PCC85 8/-	UBC41 7/8
354 5/9	7B7 8/-	DAF91 4/9	ECL88 9/-	PCC88 12/6	UBF90 7/9
3V4 6/9	7C5 7/9	DAF96 7/3	EF37A 6/9	PCC89 8/-	UBF89 7/3
5U4G 4/6	7C6 7/6	DCC90 9/-	EF39 3/11	PCF90 6/9	UBL21 13/6
5V4G 4/6	7H7 5/9	DF33 9/-	EF40 11/6	PCF82 7/-	UCB84 11/6
5Y3GT 9/-	7S7 9/-	DF91 7/3	EF41 7/9	PCF86 8/6	UCC85 13/-
5Z4G 8/9	7Y4 6/-	DF96 6/9	EP42 6/9	PCL82 8/6	UCF90 12/-
6A15 3/6	10C1 12/-	DH76 4/9	EP80 4/9	PCL83 9/8	UCH21 13/6
6A6S 3/6	10C2 16/6	DH77 5/3	EP85 5/-	PCL84 8/6	UCH42 8/-
6A05 6/3	10LD11 11/6	DK32 9/6	EP86 7/6	PCL85 8/6	UCH81 7/6
6A76 5/3	12A76 6/6	DK91 5/6	EP89 6/3	PEN A4 11/6	UCL82 9/3
6B46 5/9	12A7T 4/9	DK92 7/6	EP91 3/6	PEN38C 8/-	UCL83 12/3
6B88 5/6	12A07 4/9	DK95 7/3	EP183 10/3	PL36 10/-	UF41 7/8
6B06G 13/6	12AX7 4/9	DL33 8/-	EP184 10/3	PL81 8/6	UF89 6/3
6B88 6/-	12K7GT 4/9	DL35 9/6	EL33 9/6	PL82 7/-	UL41 7/8
6B36 5/9	12K8GT 9/6	DL92 5/9	EL41 8/6	PL83 7/-	UL44 10/6
6B78 8/-	12Q7GT 4/9	DL94 6/9	EL42 8/6	PL84 7/6	UL46 9/6
6CD8G 26/6	14S7 14/6	DL96 7/3	EL84 6/3	PLX4 10/6	UL84 6/3
6F1 9/6	19BC6G 13/6	EAB8C3 6/6	EM34 7/3	PX25 8/6	URIC 7/3
6F13 9/6	20L1 17/6	EAF42 8/6	EM80 8/6	PY32 11/-	UUT 8/6
6F14 9/6	20P4 17/-	EB01 3/9	EN81 8/-	PY80 6/8	UY21 11/-
6G4G 8/9	20P5 15/-	EBC3 5/-	EN82 9/-	PY81 7/-	UY41 5/9
6KGT 4/9	25L6GT 7/-	EBC41 7/9	EN85 9/9	PY82 6/-	UY85 5/9
6K8G 4/9	27SU 17/6	EBF90 7/9	EY51 7/-	PY83 7/-	VP48 9/6
6K8GT 9/-	30L15 10/3	EBF89 8/-	EY86 6/6	R16 17/-	VP41 5/-
6L9G 6/6	30P4 12/6	EEL21 13/6	EZ40 6/-	TH21C 15/6	W76 4/9
6L19 10/-	30P19 13/-	EEL31 17/-	EZ41 7/6	U25 10/6	W77 3/9
6LD20 5/6	35A5 14/-	ECC40 8/6	EZ80 5/6	U26 8/6	W79 14/-
6P25 8/-	35L6GT 8/3	ECCU1 4/9	EZ81 5/6	U47 10/6	Z77 3/8
6P28 11/6	35Z4GT 5/6	ECC82 4/9	GZ32 8/6	U50 5/6	

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL.
LONDON N.16 STA. 4587

NEW 1963 EDITION RADIO AMATEUR HANDBOOK

by A.R.R.L.

- 36/- Postage 2/6.
- TRANSISTOR RADIOS, CIRCUITRY & SERVICING**, by Mullard. 5/-. Postage 6d.
- R. SIGNALS HANDBOOK OF LINE COMMUNICATION**. Vol. I, by H.M.S.O. 30/-. Postage 1/6.
- RADIO SERVICING POCKET BOOK**, by J. P. Hawker. 12/6. Postage 8d.
- RADIO & TELEVISION TEST INSTRUMENTS**, by G. J. King. 25/-. Postage 1/-.
- PRINCIPLES OF COLOUR TELEVISION**, by G. N. Patchett. 16/-. Postage 8d.
- RADIO DATA REFERENCE BOOK**, an R.S.G.B. Publication. 12/6. Postage 1/-.
- THE ELECTRONIC MUSICAL INSTRUMENT MANUAL**, by A. Douglas. 37/6. Postage 1/6.
- REFERENCE MANUAL OF TRANSISTOR CIRCUITS**, by Mullard. 12/6. Postage 1/-.
- COMPLETE CATALOGUE** 1/-.
- THE MODERN BOOK CO.**
BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books
19-21 PRAED STREET
LONDON, W.2
Phone: PADdington 4185
Open 6 days 9-6 p.m.

TEST GEAR techniques

PART 5 - F.M. SIGNAL GENERATORS

H. W. Hellyer

THE farther this series of articles progresses, the more evident does it become that space is going to beat us. Several readers have suggested that explanations of principles require expansion, or that circuits need more explicit description, and others ask for less of the foregoing but an expansion of "techniques".

It is impossible to please everybody, but at the risk of repeating information that will be already familiar to many readers, this section must begin with a brief resumé of frequency modulation, and the specifications of the transmissions in this country.

However, it should be understood that the f.m. signal generator, or "wobbulator", as it is called for reasons that will become apparent, is not restricted to the alignment of f.m. receivers. The method of varying the applied frequency at a controlled rate and by a regular amount, enables visual inspection of the response curves of the receiver's tuned circuits to be made on the screen of an oscilloscope, and greatly eases the procedure of adjustment.

This technique is widely used by television service engineers, and more details of this can be found in the expansion to this present series which appeared in the May and June issues of our companion journal, *Practical Television*.

Frequency Modulation

When a carrier frequency is varied about its nominal mean, plus and minus so many cycles, at a regular rate of variation, by a regular amount and with the amplitude of the basic signal remaining constant, the resultant can be considered as a carrier being modulated by a frequency which is the rate of variation, and the amplitude of the modulating signal is represented by the amount of the variation. As an example, if a carrier of 90Mc/s is modulated by a pure tone of constant amplitude and a frequency of 1,000c/s, then the frequency modulated signal becomes a variation above and below 90Mc/s, a thousand times a second. Now, if we fix a limit to the amount we need to "swing" the carrier for 100% depth of modulation, we can work out the actual bands of frequencies that will be transmitted in terms of sidebands. This "swing", which is known as the *deviation* of the signal, is fixed at 75kc/s for 100% modulation by the broadcast engineers.

Thus, if the modulation depth is to be 50%, the carrier will have to swing between 89.9625 and 90.0375Mc/s, a thousand times per second. Increasing the amplitude of the modulation (the loudness of the tone) by a further 50%, but keeping the pitch of the tone as it was before, brings the modulation to full depth (100%) and swings the

carrier between the 75kc/s limits, i.e., between 89.925Mc/s and 90.075Mc/s. But again, this swing is at the rate of 1,000 times per second, which is the modulation frequency. Raising the tone an octave but retaining the same loudness, now swings the carrier between the same limits at *twice the rate*.

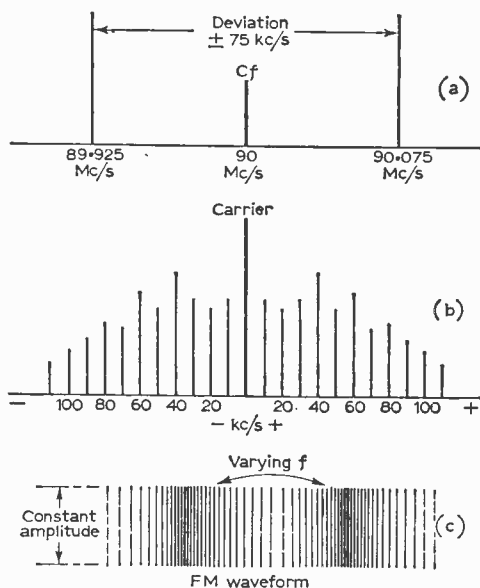


Fig. 1: Basic features of the f.m. waveform as described in the text.

Modulation Index

The ratio between the amount of fluctuation (depth of modulation) and frequency of modulation is known as the *modulation index*. The larger this ratio, the greater the extent of the sideband coverage. A signal varying about a mean frequency sets up pairs of sidebands, as shown in Fig. 1. Here, it can be seen that a 200kc/s bandwidth has been used, but the sidebands towards the outer limits tail off considerably. Remember that these sidebands are not, as with amplitude modulation, simply plus or minus the modulation frequency, but are multiples of the modulation frequency.

Even though the upper audio limit can be taken to be about 15kc/s, and we have a deviation of 75kc/s for 100%, a bandwidth of more than 200kc/s is needed to embrace the sidebands greater than $1\frac{1}{2}\%$ of the unmodulated carrier. It is

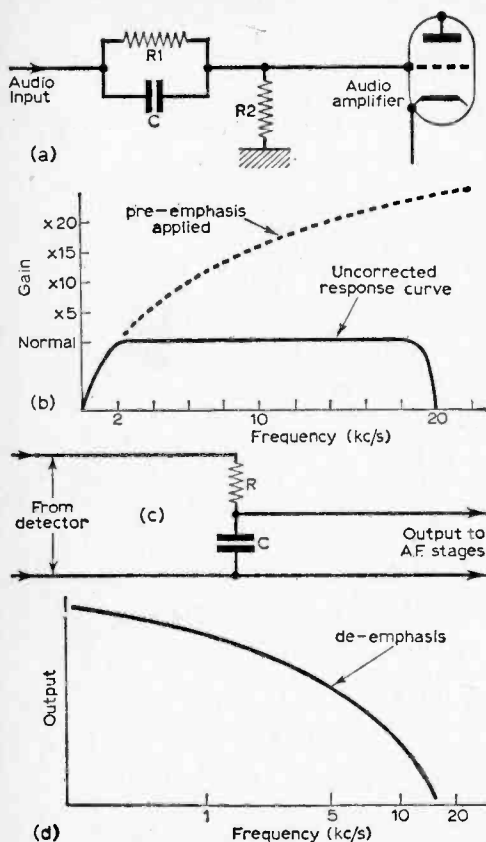


Fig. 2: Pre-emphasis networks and curves.

for this reason that frequency modulated signals are transmitted in the v.h.f. bands. Band II is divided into a number of channels of 220kc/s bandwidth, between 87.5 and 100Mc/s.

Because of the bandwidth available, it is possible to transmit signals with modulating frequencies up to the useful limits of the audio range—although it should be noted that the frequency limitations of land-lines, etc., very often means that full advantage of this extended bandwidth is not gained. However, the upper frequency ranges of the modulating frequencies, which contain the all-important harmonics that we need to retain for high-fidelity, are lower in amplitude.

Pre-emphasis

To overcome this, a measure of *pre-emphasis* is used. This consists of a "distortion" of the response curve at the transmitter, by arranging the circuits so that the amplifier gain increases by a regulated amount as the frequency rises. (This is somewhat similar to the pre-emphasis given to recordings—the purpose being to boost those weaker signals above the inherent noise level of the system, de-emphasising them again at the reproducing end.)

The pre-emphasis is measured in time-constant of a simple RC network, and in the British f.m. system, this is 50 μ sec. Fig. 2 shows the curves and

basic circuits at the transmitter and receiver, with the time-constant determined by R and C at the receiver, and by R_1 and C and R_2 and C at the transmitter end. (At low frequencies, the high impedance of C has little effect on R_1 and the two resistors are effectively in series. At high frequencies, C has a low impedance, shunts R_1 and is effectively in series with R_2 .)

Note that the time constant components are not necessarily as shown in Fig. 2(c). In practice, allowance has to be made for the self-capacitance of connecting leads, especially screened leads, and other circuit parameters that alter the overall impedance.

From all this it can be seen that the shape of the response curve of an f.m. receiver is important, if the advantages of the extended frequency coverage are to be gained.

Typical Response Curve

Fig. 3(a) shows the response curve of a typical a.m. receiver that is tuned to receive a 10kc/s signal with an "ideal" curve superimposed. Fig. 3(b) has an f.m. curve also passing 10kc/s, and it is immediately apparent that the bandwidth is much greater in proportion, almost 170kc/s, in fact.

In general, it can be stated that the bandwidth

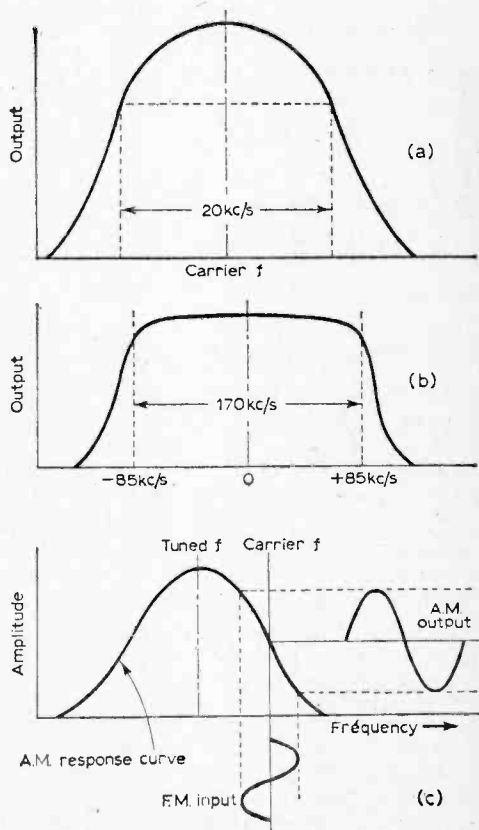


Fig. 3: Response curves of a.m. and f.m. receivers.

EASY TO BUILD




AMATEUR RADIO EQUIPMENT

CR 66 COMMUNICATIONS RECEIVER ★ A CODAR KIT TRIUMPH

NOW... THE FINEST KIT EVER OFFERED!

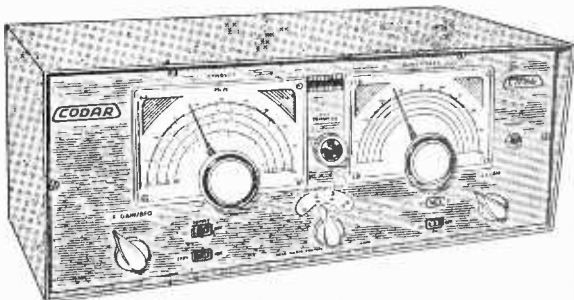This completely new Communications Receiver with its many design features and handsome styling offers more in performance and quality than many higher priced units.




Frequency Range 540 Kc/s to 30 Mc/s in four Band-switched ranges. Separate Main Tuning and Electrical Bandspread. Entirely new design High "Q" ferrite cored Coils. Oscillator Coils fitted temperature compensated trimmers for stability. Coil Unit is wired and assembled, and with the I.F. Transformers is supplied factory aligned and tested. Low loss Trollex glass alkyl switch wafers. Controlled regenerative I.F. amp. for maximum gain and B.F.O. Panel Ant. Trimmer. Delayed A.V.C. Cathode follower output for tape recorder, etc. 3 watts output for external 2/3 ohm speaker. For panel slider switches. On-Off/Standby-Receiver/A.V.C. On-Off/Speaker On-Off Front Panel Silver and Black, control knobs Grey with Silver trim. Provision for EM 84 Signal strength indicator. Panel phone iack. Heavy gauge steel chassis, cadmium plated. Valve line-up: ECH81/EBF89/ECC81/EL84/EZ80. Instruction Manual, 17 pages. Cabinet size 16 x 6½ x 8½ins. Silver Grey. For AC 200-250 volts. (Export and Marine Model 115 volts). Total cost of complete Kit, less Cabinet and Indicator **£16.10.0** carr. 6/.

CR 66 Cabinet **£11.50** Signal strength indicator with EM84 **17/6**

H.P. Terms available. Details on request.

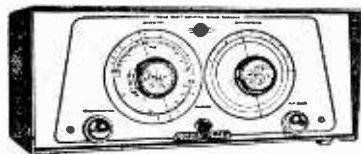THE NEW CR 45 ★ NEW STYLING TOP PERFORMANCE



- ★ Tunes 10-2000 metres (5 Coils).
- ★ Separate electrical bandspread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb styling. World-wide reception. Total building cost, with 2 Coils, 25-75 and 60-175 metres. Instruction Manual 11 pages, less Cabinet

£6.19.6 carr. 3/6.

CR 45 Cabinet Silver Grey, 12 x 5½ x 7in. sliding door for easy coil changing

27/6 Extra coils, all ranges **4/9** each.

ALL PARTS AVAILABLE SEPARATELY

★ THE MINI-CLIPPER

- ★ Tunes 10-2000 metres (5 coils).
- ★ Miniature 1 valve, all band receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.



Can be built in an evening, will receive Amateur and Broad cast stations from all parts of the world. Total building cost with one coil 25-75 metres, Instruction Manual 4 pages, 36/6, carr. 2/6. Extra coils, all ranges, 4/9 each. Electrical bandspread available. All parts available separately.

36/6

★ THE SUPER CLIPPER

- ★ Tunes 10-2000 metres (5 coils).
- ★ Large precision dial, dual slow motion drives.
- ★ Bandspread on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

88/6



Easy to assemble, this top performing All Band Receiver brings a new world of listening pleasure to your finger-tips at low cost. Total building cost with 2 Coils, 20-60 and 55-190 metres, Instruction Manual 7 pages, 88/6, carr. 2/6. Extra Coils, all ranges, 4/9 each. Front Panel, Silver Grey, 10 x 7½in., 6/9.

Please note NEW address. We have now acquired new modern premises, combining all depts., offices and laboratories. New equipment under development will be announced in due course. Now available P.R.30 R.F. Preselector 1.5/30 Mc/s, greatly improves performance of any superhet receiver. CODAR Equipment is famous for Top Quality, Peak Performance and Easy-to-Follow Instructions—no guesswork. 6d. in stamps brings illustrated leaflets. Coming shortly, 70 watt 5 Band Transmitter Model No. CT80.

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX

G3IRE

Canadian Distributors: JAYCO ELECTRONICS, TWEED, ONT.

G3IPA

INTRODUCING!!


THE BRILLIANT NEW

"NORCOL NOMAD"

SEVEN TRANSISTOR TWO WAVEBAND SUPERHET RADIO UNIT

BRAND NEW DESIGN FOR CAR RADIO AND GENERAL PURPOSE GIVING ONE WATT OUTPUT WHEN CONNECTED TO ANY STANDARD 3 ohm SPEAKER

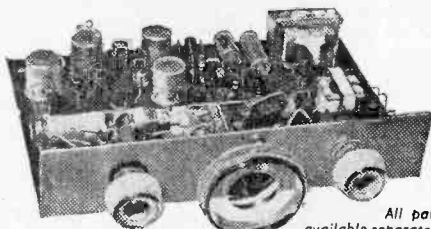This versatile unit has been designed to fit into a variety of cases and all components, down to control knobs and battery clips, are supplied together with clear illustrated plans. It gives a superb performance with dozens of stations including Luxembourg when connected to a 9 volt battery and speaker.



Size: 7 x 5 x 1 1/2 in. Building Plans 2/6 (Free with kit).

FEATURES

- NEW PRINTED CIRCUIT OF OUR OWN DESIGN
- LARGE OUTPUT TRANSFORMER
- SEVEN FIRST GRADE TRANSISTORS
- INTERNAL HIGH "Q" FERRITE AERIAL
- CAR AERIAL COUPLING COIL

We are offering the above for **THE AMAZING PRICE OF £6.19.6** P.P. 2/-

or at NO EXTRA COST in 3 Stages (A, B and C) of 46/6 each plus P.P. 1/6.

ALIGNMENT SERVICE:

This unit is covered by our Test and Alignment Service which also handles the **PW-6 Pocket Superhet** and **Mercury-6 Mk. II**, for which we stock all components. The charge is 12/6 plus P.P. for Test and Alignment and where fault finding and broken component replacement is required a small service charge is added. (Cases and Speakers should not be included.)

NORCOL LTD. 147 LONDON ROAD, YORKTOWN, ELECTRONIC COMPONENTS CAMBERLEY, SURREY Phone: CAMBERLEY 3743

RADIO UPKEEP AND REPAIRS

A. T. Witts, A.M.I.E.E.

Ninth Edition

In the latest edition of this established work new information has been added on Transistor and F.M. receivers and there is now a separate chapter devoted to the alignment of receivers. The chapters on meters, aeriels, and feeders have also been re-written. 18/- net.

FROM ALL
BOOKSELLERS


PITMAN

Parker St., Kingsway,
London, W.C.2

CRYSTALS & COMPONENTS LTD.

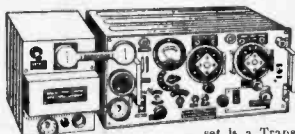2-4 EARLHAM ST. W.C.2. Tel. TEM. 1189

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations. Hours of Business: 9 to 6. Saturdays 9 to 1. Open All Day Thurs.



WIRELESS SET NO. 19

No. 19 Mk. II Wireless Sets complete with power supply unit for 12 volts D.C. and connecting lead to net. This

set is a Trans/Receiver covering 2-8 Mc/s using 6 valve superhet receiver with 1.F. of 465 kc/s and a 6-valve transmitter. For voice and C.W. operation. Incorporates 500 microammeter for tuning voltages, aerial loading, etc. Panel controls, frequency tuning, gain control, P.A. tuning M.C.W. C.W. R/T switch, hot tone netting, off/on, quench aerial AVC-RT-LT Drive test. Complete with valves. In clean, serviceable condition. £4.17.6, plus carr. & packing £1. Variometers in new cond. 15/- each. P. & P. 2/6.

AR 88 LF RECEIVERS. 75-550 kc/s. and 1.5 to 30 Mc/s. 110/240 v. A.C. input. Price from £27.10.0 (slightly soiled exterior) to £30 (as new). Carriage and packing 35/-.

VIBRATOR POWER SUPPLY UNIT 6 volts D.C. input. 230 volts 100 mA A.C. output and 6 v. L.T. out. Fully assembled, with OZ4 rectifier valve. Brand new in steel case with pilot light, on/off switch and Sylvania fuse on front panel. Measures 8 1/2 x 6 x 5 1/2 in. 38/8. plus 6/6 P. & P.

SPECIAL OFFER — TYPE 46 SETS From 4.4-7.4 Mc/s. Complete with valves, crystals and coil box but having had the original send/receive switch removed. Without other accessories. This set is supplied with a substitute switch and full instructions and diagram for wiring in. At 18/6 each or 35/- per pair. P. & P. 5/6.

FIELD STRENGTH METERS 100-150 Mc/s. Contains 0-1 mA meter, 152 valve, chrome telescope aerial, etc. New condition in black crackle case. Operates on 1.5 v. and 90 v. batteries. Dimensions 7 x 7 x 7 in. 45/-, P.P. 2/6.

for an f.m. receiver has to be twice the deviation plus twice the modulation frequency.

We are approaching the point when we can consider that required specifications of the instruments needed to test the f.m. receiver, but first it should be stated that frequency modulation of an a.m. signal and amplitude modulation of an f.m. signal both give rise to distortion. (Readers are referred to an excellent article touching on this subject by my colleague, Gordon J. King, in the March 1963 issue of PRACTICAL WIRELESS.)

It is not necessary to go into the details of limiters, detectors and associated circuits, but it is worth remembering at this point that the most careful alignment of a receiver can be nullified by faulty limiting and detection. As an example, consider the diagram of the response curve of an a.m. receiver operating at v.h.f., which has an f.m. signal applied so that the mean carrier falls on the slope of the r.m. response curve (Fig. 3c). If the a.m. receiver is a superhet, and the carrier of the f.m. signal fluctuates by $\pm 50\text{kc/s}$, the resultant output from the receiver's tuned stages will be an a.m. signal corresponding to the f.m. modulation frequency—which explains why some viewers are annoyed by "breakthrough" of public-service f.m. broadcasts on a.m. television receivers. The remedy is to increase the selectivity of the set, either by re-alignment to make the sides of the response curve steeper, or enhancing the sensitivity of the receiver, and aerial system.

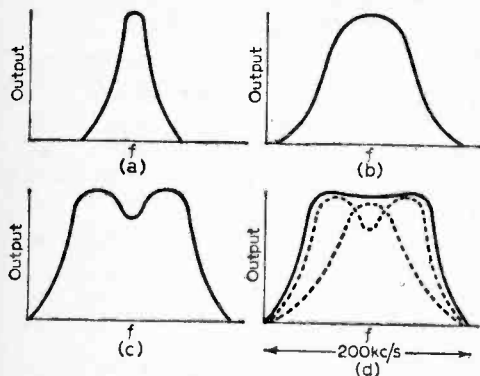


Fig. 4: Effects of coil couplings.

The actual frequency of the modern f.m. receiver i.f. circuits is tuned to a 200kc/s passband around a basic 10.7Mc/s. Some manufacturers have chosen to use a rather higher frequency of 19.5Mc/s.

The choice of frequency is determined partly by the need to keep the second-channel or image frequency outside the acceptance of the aerial and i.f. circuits. For example, taking a transmitted signal of 90Mc/s, and an oscillator tuned to the signal frequency plus the i.f. (which is normal practice for engineering reasons that need not concern us here), if we had a low i.f., such as the 470kc/s used by the a.m. set, the second channel would occur at 90.94Mc/s. This is the signal frequency plus twice the i.f., and such a frequency would fall well within the acceptance range of the "front-end" circuits. By choosing a higher i.f., of 10.7Mc/s, the image frequency is at 110.14Mc/s,

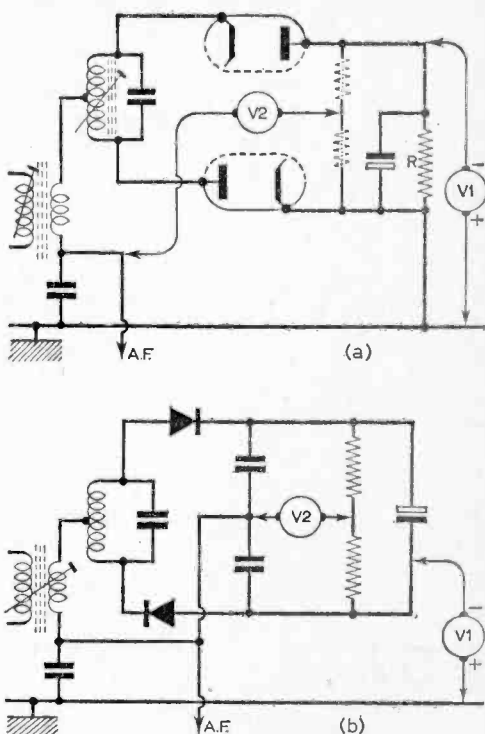


Fig. 5: Unbalanced (a) and balanced (b) ratio detector circuits.

where a good degree of attenuation can be afforded by correct pre-oscillator alignment.

This is aided by the "capture effect" of f.m. reception, where a set will tend to tune to a signal that has an aerial strength more than double the unwanted signal. This exact frequency of 10.7Mc/s was decided by an international conference after protracted and exhaustive consideration of the whole interference problem.

One secondary advantage is that its distance (in frequency) from the 470kc/s intermediate frequency of the a.m. circuits allows the tuned coils of each to be wound in series on the receivers that are designed for a.m./f.m. signals, without the one having adverse effect upon the other.

Coil Coupling

Alignment is affected by the coupling factors of the i.f. coils, and the need to maintain a good, wide, symmetric response curve in order to retain the advantage of the full frequency coverage available. For this reason, the coils may be varied in coupling to produce differing curves, the summation of these giving the desired effect, as seen in Fig. 4. Curve (a) represents a loosely coupled transformer, (b) shows the "normal", intermediate curve, often found in a.m. receiver circuitry, (c) shows the effect of tight coupling and (d) illustrates the principle of combining the familiar "double-humped curve" of a tightly coupled transformer with the peak of a loosely coupled transformer to

obtain a response that is wide, level and symmetrical. This is not quite the same thing as the "stagger-tuned" circuit met with in television receivers, where an i.f. of 35Mc/s and a pass band of 3Mc/s may be encountered.

The last i.f. transformer, the discriminator circuit, is the most critical. The coupling factor has to be carefully adjusted and tuning must be precise for distortionless output.

I.F. Alignment

Instruments used in i.f. alignment can be the ones described previously: an amplitude modulated signal generator with a frequency coverage taking in the 10-7Mc/s i.f. and the receiver band of 80-100Mc/s, plus a high resistance voltmeter. With the signal generator connected to the grid of the final i.f. valve, and tuned to the centre frequency, i.e., 10-7Mc/s, the circuits can be tuned for resonance. But to obtain a correct indication it may be first necessary to *detune* the discriminator transformer secondary, returning to this section of the circuit after the i.f.'s have been aligned. Simply unscrew the core of the secondary winding of the discriminator transformer a few turns.

Fig. 5(a) and (b) shows the points to which the high resistance voltmeter should be connected for the ensuing tests.

Unbalanced Ratio Detector

In Fig. 5(a), an unbalanced ratio detector circuit is illustrated. The voltmeter V1 is connected across the load R, with the positive probe connected to chassis. As is normal practice, both signal generator and receiver must be allowed to warm up to obtain stable conditions, and a period of 15 minutes may

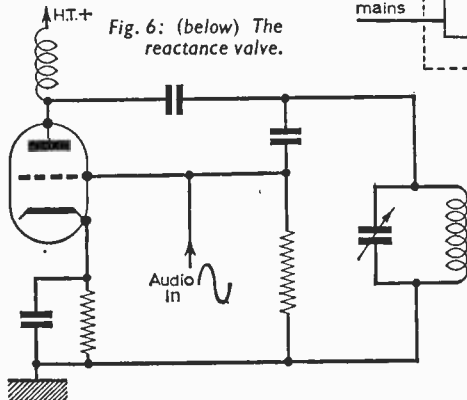


Fig. 6: (below) The reactance valve.

be necessary, particularly if the receiver chassis is removed from the cabinet for bench testing.

An unmodulated signal should then be applied from the generator and the primary of the discriminator transformer, then the primary and secondary of the output transformer of the last i.f. adjusted for maximum reading on the voltmeter. The signal generator is then transferred to

the mixer, and the first i.f. aligned.

To couple to the mixer, make a loop of stiff copper wire and loosely couple the signal by pushing the loop over the envelope of the valve, or, where a slide-fit screening can be used, connect a crocodile clip to this and slide it up until its chassis connection is open-circuited. Note that where tightly coupled transformers are employed, it will be necessary to damp the winding which is not being adjusted, to reduce interaction. The maker's instructions should be followed closely in these cases.

The discriminator secondary is re-adjusted by connecting a voltmeter V2 between an artificial balancing point formed by the junction of the two resistors shown dotted in Fig. 5(a) and the a.f. take-off point, then tuning for zero reading.

Balanced Ratio Detector

Where a balanced ratio detector is used, as in Fig. 5(b), the connections are as shown, and adjustments are similar: V1 for maximum negative swing and V2 for zero or minimum reading. Note that, in all cases, limiting action should be avoided by keeping the input signal as low as can be employed

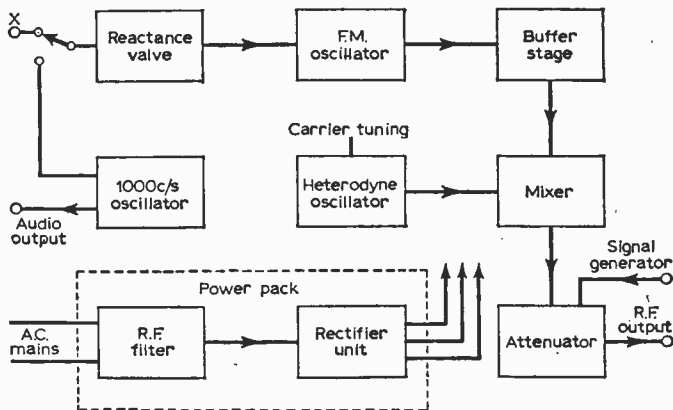


Fig. 7: Block diagram of the Cossor 1324 f.m. alignment generator.

for adequate output readings. Where circuit details are not known, it is a good general rule to tune the i.f. transformers with a damping resistor of about 39,000Ω across the secondary of the final i.f. transformer, removing this before tuning the discriminator secondary.

Foster-Seeley Circuit

A Foster-Seeley circuit can be aligned with an a.m. signal generator by applying the modulated signal and connecting an output meter to the loudspeaker feed, adjusting as before. If, after alignment, the sound appears to lack "top", it may be that the response curve has been narrowed by peaking, and careful detuning of the i.f. circuits may be needed.

Although much can be done without the aid of an f.m. signal generator with sweep facilities, there is no doubt that this instrument, in conjunction with an oscilloscope, gives by far the better, quicker, and more trustworthy results. We shall be

—continued on page 257

radiohistory.com

COMPREHENSIVE TECHNICAL HANDBOOK SERVICE


For complete data on Mullard Valves, Tubes, Semiconductors and Components

The Mullard Technical Handbook is a loose-leaf publication, issued on a subscription basis and containing data sheets on Mullard valves, tubes, semiconductor devices and components in current production. From one to twenty pages are devoted to each valve, tube or semiconductor type, data including the maximum ratings and performance figures for various applications. Subscribers automatically receive revised sheets and supplementary data on new types, as they are introduced.


Please write for details to:

Mullard

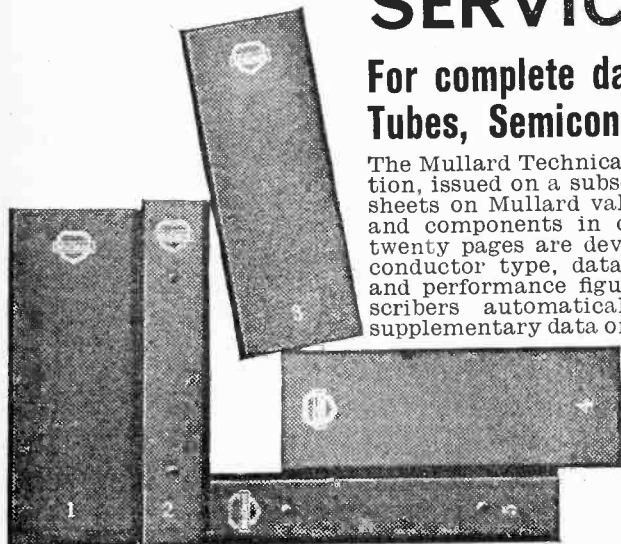MULLARD LIMITED,
TECHNICAL INFORMATION DEPARTMENT,
MULLARD HOUSE, TORRINGTON PLACE,
LONDON, W.C.1. MVM 1276



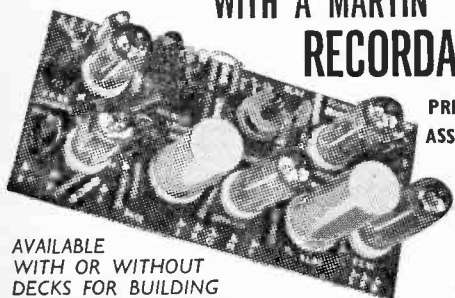ADD TAPE TO YOUR HI-FI WITH A MARTIN RECORDAKIT



PRE-AMP
ASSEMBLY

Money
Saving
tool

AVAILABLE
WITH OR WITHOUT
DECKS FOR BUILDING
IN 3 DIFFERENT WAYS

MARTIN RECORDAKIT PRE-AMP ASSEMBLIES are available for 2 or 4 track use with Collaro Studio Deck or B.S.R. Monardeck. Amplifying portions are supplied assembled with valves on printed circuit boards. Kits may be bought for pre-amp alone, with deck for mounting into existing cabinet, or with deck and modern polished wood cabinet. Whichever way suits you, these Recordakits provide a wonderful way to add tape to existing installations for very little expense, and give wonderful quality.

2 Track
Pre-Amp
Kit alone 8 gns
4 Track
Pre-Amp
Kit alone 9 gns
Kit with
polished wood
Cabinet and
Deck
from 17 gns

**MARTIN
RECORDAKITS**

From Radio Stockists
or direct in cases of
difficulty write or
phone
ISLeworth 5885/1161


MARTIN ELECTRONICS LTD.
155 High St., Brentford, Middx.
Latest Recordakits leaflets please!

NAME _____
ADDRESS _____
PP.7 _____

READY BUILT - READY TO GO

Listen in comfort, to your favourite
stars without annoying others with our
"PERSONAL TRANSISTOR
POCKET PORTABLE"

Designed exclusively for personal use
and supplied complete with miniature
earpiece and battery. Works anywhere,
any time—our special circuit with built
in ferrite rod aerial ensures wonderful
reception over the full medium wave
band, B.B.C. Home, Light, Luxembourg
and many Continental stations. Com-
pletely portable, compact size, only
2½ x 3½ x 1 in., slips into pocket. NO
EXTERNAL AERIAL OR EARTH
REQUIRED. Condenser tuning and
with "exclusive" separate fine tuning
control for "spot on" station selection.
Complete station separation makes
this ideal for use as Tape Jack for
recording or tuner unit for amplifier.

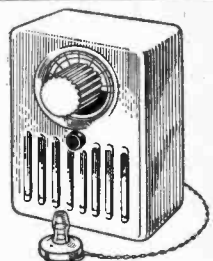


PRICE 45/- P. & P. 2/-

fully complete including ear-
piece and battery.

COMMANDER IV CRYSTAL SET

Covers the full medium wave band
and is ideal for use in Bedroom, etc.
Requires NO batteries—lasts for
ever. Operates with miniature
personal earpiece. Attractive case
and dial—a Radio set in miniature.

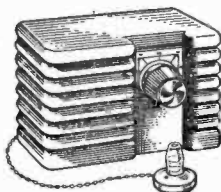PRICE 15/- P. & P. 2/-
complete with personal earpiece
and fully guaranteed.



Transradio

11, OLIVER ROAD, LONDON, E.17

TEST GEAR TECHNIQUES

—continued from page 254

dealing with the oscilloscope in a subsequent article, but a few details of the sweep generator are needed to clarify the foregoing.

The Sweep Generator

As we have seen, the input signal has to vary at a set speed and about a set frequency. The basic device to obtain this action is the reactance valve, as depicted in Fig. 6. The valve acts as a virtual capacitance and is across the tuned circuit. The r.f. in the grid circuit leads the anode voltage by almost 90°, and the grid-cathode voltage therefore leads the anode voltage by the same angle, resulting in the anode current leading the anode voltage similarly. The magnitude of the capacitance presented by this stage is thus determined by valve constants, circuit parameters, and the d.c. voltage at the grid.

An audio signal is now applied to the grid, effectively varying the d.c. and providing cyclic changes of the capacitance presented by the valve to the basic tuned circuit, thus altering the tuning in much the same way as has been done in some instruments by applying a small motor to a variable capacitor, swinging the frequency about a fixed tuned point.

As a further example, the block diagram of the Cossor f.m. receiver alignment generator, Model 1324 is shown in Fig. 7. It can be seen that the r.f. output is obtained by the mixing of two output voltages from separate oscillators. The frequency coverage at r.f. is obtained by addition of the two

outputs and the i.f. signal by their difference. The centre frequency of the f.m. oscillator is 57.5Mc/s, modulated by the reactance valve, whose swing can be determined by the application of an external voltage, such as is available from an oscilloscope, thus tying the two instruments electronically, so that a visual indication can be obtained, as will be explained later.

A deviation of $\pm 75\text{kc/s}$ from the internal 1,000c/s oscillator or from $\pm 25\text{kc/s}$ up to $\pm 400\text{kc/s}$ from an oscilloscope timebase can be obtained. R.F. output of this instrument is from $5\mu\text{V}$ to 50mV, via the attenuator. An a.f. output is available at 1,000c/s, variable up to 8V peak-to-peak, and a probe unit is provided to give a rectified output from the final anode of the i.f. stages to the Y plates of an oscilloscope, which makes it possible to carry out alignment without using the receiver's detector—often an advantage.

Many more comprehensive instruments are on the market, with expanded frequency coverage and sweep facilities suitable also for television alignment, but the above notes should make it clear that the fundamental need for a "wobbulator" when working with frequency modulated equipment makes this instrument more than a "luxury extra". As we have attempted to explain, alignment of wide passband circuits can be carried out—with sufficient patience—by the aid of a standard signal generator and a good meter, but as we shall see, the great facility of adjusting while watching a visual trace, with the aid of a wobbulator and oscilloscope, more than justifies the use of this versatile instrument.

PART 6 OF THIS SERIES APPEARS NEXT MONTH

Local Station F.M. Receiver

—continued from page 224

assume that the a.f. amplifier is switched on and running, and that the h.t. and l.t. supplies to the tuner are on. Plug in the ECF82. The valve, on warming up, should take between 15 and 25mA anode current. On rotating VC1 it will be found that the h.t. current varies over a fairly wide range.

Plug in the other valves (V2, V3—were used), the increase in h.t. current should be in the order of 15 to 20mA. A "rushing" sound will now be heard from the a.f. amplifier indicating that the oscillator is functioning. Connect a piece of wire (2ft to 3ft long) to pin of V1, when heavy morse signals, whistles etc., will probably be heard if the i.f. amplifiers are working properly. Remove the wire from pin 2 and connect a proper f.m. aerial to the aerial input socket, and rotate C7 when the local f.m. broadcasts should be heard. Decrease VR1 until the station can only just be heard and adjust the i.f. coils for maximum performance, reducing VR1 as necessary (very little adjustment will be required as the i.f.s are pre-aligned at the works).

Adjust L1 for maximum signal finally trimming RDT for maximum output. L2 should now be set so that the centre frequency station is received with C7 half closed. Set the core in place with adhesive. If the coils have been properly aligned the set will now function as designed and a reasonable quality sound output will be obtained.

Voltages on the valve electrodes of the prototype are show in Table 1.

HAVE YOUR MAGAZINE DELIVERED BY POST

Many of our readers prefer to have PRACTICAL WIRELESS sent to them every month by post. This convenient way of receiving your magazine has much to commend it, and you too may like to become a subscriber. Nothing could be simpler to arrange. Just complete the Subscription Order Form below and post it to the address shown. Send no money now—you will be invoiced in due course.


Subscription Order Form

To Subscription Manager, PRACTICAL WIRELESS(A7), Tower House, Southampton Street, London, W.C.2.

Please send me PRACTICAL WIRELESS every month for 12 months, commencing with the next issue. (One year's subscription, including postage, costs £1 9s. 0d. in the U.K. and Eire; £1 5s. 0d. in Canada and £1 7s. 6d. elsewhere overseas).

NAME

ADDRESS

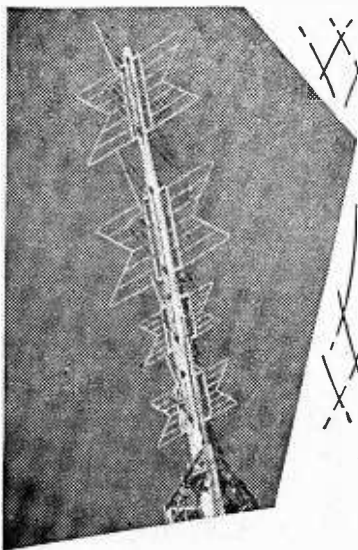

On Your Wavelength

By THERMION

lines. I must admit that up to a point, I discovered this anomaly to be true.

In my particular series of tests I also found a number of other interesting facts. Firstly, standard resistors of the same apparent value, give quite different performances on the test set-up, and on measuring it was found that some of these were over 25% out in the rating. Obviously where three or four such resistors are used, the tolerances can be all one way, and give quite a variation in performance. One hopes, of course, that the variations will be "each way," so that overall the effect will not be so noticeable, but the possibility of accumulated differences in values remains and this could make a considerable difference to the operation of a circuit, especially where the cheaper transistors are used.

I shall be hoping to give some further notes on these tests with the types of transistor, etc., at a later date, but would point out here that if you are bent on getting the best from a circuit, don't be tempted to save money on the transistors as I am certain that the above results proved the exception rather than the rule.

More Hints

The really keen amateur is always on the look out for ideas which will be of use in his hobby, and what is more important, trying to find items which can be adapted for his use and which are, in consequence, cheap or easy to obtain. No doubt most of my readers are aware of the use of the rather large tapered screw-tops from bottles, which make good looking and effective control knobs—provided you can find some method of fastening them to the appropriate spindle.

However, I have quite a number of new suggestions from readers, which indicates that this idea of looking round for articles to adapt is still with us, although I must confess I had thought it went out many years ago when components became cheaper.

As an instance I would mention a letter I recently had from a Mr. Bulbeck of Bognor Regis, who is obviously a short-wave fan. He has located the "hair curlers" at a popular department stores, and points out that these make ideal short-wave coil formers! The curlers are made of plastic, are "skeletonised," and have small spikes round the periphery, which makes them ideal for spaced or bank winding. They are available from about $\frac{1}{4}$ in. to $1\frac{1}{2}$ in. in diameter, and are about 3 in. long. They cost only a few pence each, and in the hands of the real enthusiast could, no doubt, form the basis for a really efficient set of coils, either for a receiver or transmitter, or even for items such as signal generators or wavemeters.

I FEEL that I ought to start this month's notes with a general "thank you" to all those readers who continue to write to me—either giving notes about various electronic games, or hints which they feel might be of general use. I want to take this step as I receive so much correspondence that I find it impossible to thank everyone individually, and only where the reader encloses a stamped and addressed envelope do I make a serious effort to write to him. I do, of course, have work other than the writing of these notes and whilst I am at all times anxious to drop a line to all those kind readers who go to the trouble of writing or sending me valuable information, it is impracticable to write to all of them. So I must take this opportunity of making a general acknowledgment to all of them and point out that I am deeply grateful for the many letters which I have received, and hope the above notes will explain why I have not written individually to everyone.

Transistors

I some time ago carried out a most enlightening series of experiments with transistors, after hearing of the interesting, and almost unbelievable, experiences of a reader.

Some time ago we published a design for a transistor amplifier in which some well-known proprietary transistors were recommended. A month or so after this, when the Radio Show was being held, a reader called at our stand and thanked us for the particular design, and pointed out that he had built the amplifier and that its performance had astounded him. He also pointed out that after being so impressed by the results obtained using cheap 2s. transistors, he bought and incorporated the more expensive recommended components, only to find that the performance with these was inferior! Once or twice before, I had heard of similar experiences and so I decided to carry out my own experiments along the same

POST FREE MAIL ORDER SERVICE

PORTABLE MAINS SOLDERING IRON SP.1

30 watts. Features removable handle that covers tip and barrel. Complete for 18/6.

SIGNAL INJECTION PROBE IT.1

Push button operation. Ideal for making rapid checks on radios, TV, Amps, tuners, etc. Price 42/6.



All goods
sent by
return

MICROPHONES AND STANDS

DM.16HL DYNAMIC. Dual imp. 50 ohm low, 50K ohm high. 40-15,000 cps. Price 57/6.

DM.17HL DYNAMIC. As above but cardoid pattern. Price 57/0.

100.C 3 way SLIM CRYSTAL. Response 60-10,000 cps. Price 48/-.

DM.11 DYNAMIC (illus.) with base. Response 60-12,000 cps. Price 25.5.0.

BM.36R. MAGNETIC LABEL TYPE. 1 1/2 in. dia. Price 12/6.

S.A.E. for leaflets.

FS.3. TELESCOPIC FLOOR STAND. 3 section chrome plated with heavy base. 57/6.



All goods
available as
previously
advertised

HI-FI SPEAKERS

CK.300. 12in. Two Way. Crisp clean frequency response from 30-16,000 cps. 15 watt. 16 ohms. Price 12 gns.

CR.12AE. 12in. Two Way (illus.). True Hi-Fi and superb stereo at low cost. Response 30-16,000 cps. 10 watt. 16 ohms. Price 8 gns.

CE.30AE. 12in. Three Way. Advanced triaxial design giving full 3 speaker performance. Response 30-16,000 cps. 10 watt. 16 ohms. Price 10 gns.

SA.7. 8in. Two Way. Dual cone construction ensures wide range response. 50-16,000 cps. 6 watt. 16 ohms. Price 31/-.

TP.28G. 2 1/2 in. 75 ohm speaker. Price 11/-.

S.A.E. for leaflets.



Full range
of Eagle Products
always in stock


TOOL KITS

6 Piece Screw Driver Set, Model 3360. Consisting of mechanics, electricians, Phillips, midjet and stubby types. Magnetized blades of tempered, hardened tool steel. Unbreakable, flameproof and shockproof plastic handles. Display bagged. Price 8/-.

Mult Purpose Tool Set, Model 7800. Consisting of insulated plastic handle, 6 interchangeable screw driver bits, including Phillips type, one hammer, 5 hexagon sockets (1/4-7/16") and extension bar. Complete in Vinyl roll case. Price 12/6.



No. 19. 2-8 Mc/s TRANSMITTER RECEIVER

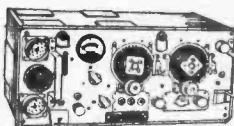

This most famous Army Transmitter Receiver covers 2-8 Mc/s. (100-37 metres in two bands). Has an intercom, amplifier. Designed for 12 and 24 volt operation but supplied with "P.W." Mains conversion details. Uses a 6 valve superhet receiver, I.F. being 485 Kcs, and a 8 valve transmitter designed for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel Controls: Frequency tuning, P.A. tuning, Gain control, MCW, CW, R/T switch. Het-tone setting. On-on Quench aerial, AVC LT-HT. Drives tests. Supplied complete with instruction book. Only 75/-.

PICK-UP ARM COMPLETE




Transcription type. Wired for stereo and complete with LP/78 Stereo/Mono turn-over cartridge. Price 23.7.0.

HI-FI AMPLIFIERS

SA.80 Integrated Stereo Amplifier (illus.). 4 x 4 watt. The perfect choice for a low cost Hi-Fi stereo system. Dual pick-up and tuner inputs. Supplied complete for only 29.10.0.

SA.150 Integrated Stereo Amplifier. 4 x 7 1/2 watt. Price 42.10.0.

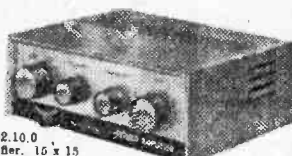SA.300 Integrated Stereo Amplifier. 15 x 15 watt. Incorporates all the latest refinements to give you professional quality Hi-Fi reproduction. Modestly priced at 232.10.0. S.A.E. for leaflets.



VISIT OUR HI-FI
SHOWROOM AT
87, TOTTENHAM CT. RD., W.I

MULTI-METERS

All complete with test leads, batteries and instructions.

Model EP.100K. 100,000 O.P.V. A handy size high sensitivity multi tester, with shockproof 9.5A meter. Ranges D.C. volts, A.C. volts, D.C. amps, Ohms, etc. Size 3 1/2 x 3 1/2 x 2 1/2 in. Originally £14.14.0.

REDA EXCLUSIVE OFFER

UNOBTAINABLE

£6.19.6


EP.50K. 50,000 O.P.V. complete £9.19.6

EP.30K. 30,000 O.P.V. complete £8.19.6

EP.10K. 10,000 O.P.V. in Kit form £3.9.6

TK20A. 1,000 O.P.V. Complete £2.9.6

S.A.E. for leaflets.

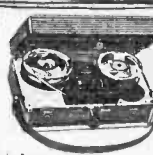

A MINIATURE TAPE RECORDER IN KIT FORM NOW ONLY £4.19.6

Exclusively offered complete with all accessories. No extras to buy. Consisting of three transistor amplifier, record-play, volume control, miniature speaker, forward-stop, coloured case, Mic. and earphone sockets, pick-up coil, mikes, operated. Simple to put together in less than one hour. Brand new and guaranteed.

rewind switch, reel of tape and spare reel, motor, attractive

Relda Radio

MAIL ORDERS TO: DEPT. 'P' 32A, COPTIC STREET, LONDON, W.C.1 Tel: MUSEUM 9606

THE NEW TRANSISTOR 6 PANDORA

Designed by

MEL ELECTRONIC

Using New, High-grade Parts

TOTAL BUILDING COST—

ONLY **£4.15.0**

P. & P. 3/6

FULL AFTER SALES SERVICE

All Components obtained direct from
MEL ELECTRONIC

Please send S.A.E. for FULL DETAILS of these and other Transistor Designs



- ★ MEDIUM WAVE AND LIGHT ON LONG WAVE
- ★ 6 TRANSISTORS + DIODE
- ★ SUPERHET CIRCUIT
- ★ AUTOMATIC WAVECHANGE
- ★ 500mW PUSH PULL OUTPUT
- ★ PRE-TINNED PRINTED BOARD
- ★ EXCELLENT RESULTS

MEL ELECTRONIC CO. LTD.,
58 OAKFIELD ROAD, PENGES, LONDON S.E.20.

COMPLETE

14 INCH
£7.10.0

100% Guaranteed.

12 months' Full
Written
Guarantee.Shown working
all channels
in Shop.

TELEVISIONS

17 INCH
£11.10.0

Legs—39/6perset

Part exchange
allowance on
ANYTHING
USEFULPersonal collection
advised, or insured
Carr. 14in. 20/-,
17in. 30/-.

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES

KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED
FOR THREE MONTHS

1C1	7/6	6BH6	5/9	12AX7	6/9	DH77	6/-	EF91	4/-	PL82	7/6
1C3	8/-	6BJ6	5/9	12BE6	8/6	DH142	8/6	EF92	5/6	PL83	7/-
1F1	8/-	6BR7	8/9	12BH7	10/6	DH150	10/-	EL41	9/6	PY81	6/9
1F3	7/6	6BW6	8/6	12K80	11/-	DK91	7/6	EL44	7/-	PY82	7/6
1FD1	8/-	6BW7	7/-	12Q7	7/6	DK96	8/-	EM44	10/-	PY83	7/6
1FD9	7/6	612	4/-	12SN7	6/-	DL92	5/9	EM85	10/-	R19	10/6
1P1	8/-	6P12	4/-	16A5	9/-	DL94	6/6	EY51	7/6	RS41	9/6
1P10	7/6	6H6GT	2/-	19A05	9/6	DL96	8/-	EY81	10/-	US2	7/6
1P11	7/6	6J7GT	7/6	25A03	7/6	EB91	4/-	EZ40	7/6	U76	7/6
1R5	6/-	6K7G	5/6	251A0T	7/6	EBC41	10/-	EZ80	6/-	U78	6/-
1S5	6/-	6K4G	6/-	25Z40	9/-	EBF80	8/6	EZ81	6/9	U142	7/6
1T4	2/9	6Q7G	5/6	30C1	7/6	ECC81	6/-	HVR2	9/6	UCB41	8/6
1U5	6/6	6L1GT	6/-	30L1	7/6	ECC82	6/9	KT33C	6/-	UCH42	9/6
3Q4	8/-	6SN7GT	8/-	351J6GT	7/6	ECC83	6/9	KT66	11/6	UF41	8/6
3S4	5/9	6V6G	7/6	35W4	8/6	ECC84	7/6	N17	5/9	U141	8/6
3V4	6/6	6X4	5/-	35Z40T	8/-	ECCF80	8/6	NY18	8/-	UY41	7/6
6Y30T	5/-	6X6G	5/9	5763	7/6	ECCF82	8/-	N19	7/6	W17	7/6
5Z4G	7/6	787	9/6	80	6/-	ECH42	7/-	N709	7/-	W76	4/6
6A5E	6/6	803	4/-	DAP91	7/6	ECH41	10/-	PC84	7/6	W142	8/6
6A5L	4/-	907	9/6	DAP96	8/-	ECL80	5/6	PC89	7/6	X17	7/6
6AM6	4/-	12A06	11/6	DC930	12/6	ECL82	8/-	PCF82	7/6	X142	8/-
6AT8	6/-	12A08	10/-	DF91	3/-	EF41	9/-	PCL82	8/-	X150	9/-
6BA6	5/-	12AT7	8/-	DF96	8/-	EF80	8/-	PCL84	9/-	Z77	4/6
6BE6	7/-	12AU7	8/9	DH76	7/6	EF86	9/-	PL81	12/6	ZD17	7/6

ASK FOR RESISTOR AND CAPACITOR COLOUR CODE. FREE WITH EVERY PURCHASE

High Stability Resistors 1W 5%, 50 Ω to 1M, 9d. Midset Ceramics 500 v. 9d. Coax. Super quality 1in., 6d. yd. Plugs 9d. Sockets 9d. Silicon H.T. Rects. 250v. 300 MA 1in. x 1in. 8/6. Contact Cooled 250v. 50 MA 6/6. 85 MA 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC26, OC66, 26/-; OC44, OC45, 9/-; OC70, OC71, 8/-; OC72, 7/6; OC72 matched in prs. 18/-; OC74, OC75, OC78, OC81, 7/6; OC82, OC170, 8/6.

VALVES MATCHED IN PAIRS

EL34 27/6, EL34 15/-, N709 15/-, 6V6G 15/-, 6BW6 14/- per pair. Push Pull O.P. Transformer for above 3 15 Ω 14/8, P. & P. 1/6. 12in. P.M. Speakers 3 Ω 24/6. Baker's 'Selhurst' 12in. 15 Ω 15W, 80/- 12in. Stereo Model £7.7.0.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94, 19/6
DK96, DF96, DAF96, DL96.....27/6
1C3, 1P1, 1FD1, 1P1.....27/6
1B5, 1T4, 1S5, 3S4, or 3V4.....19/6
Postage and packing 6d. Over £1 post free.
ECH42, EF41, EBC41, EL41: £2.40.....37/6
UCH42, UF41, UBC41, UL41, UY41.....35/-
C.O.D. 4/-.

Regun TV TUBES
21in. 99/6 17in. 79/6
15, 14 and 12in.—59/6
GUARANTEED ONE YEAR
Ins. and Carr. 10/6.
Add 10/- refundable on OLD
TUBE. 110° Tubes in Stock.

Ex Rental
15/- 36/24, 14KP4, 14I,
12I, 31/74 and others.
Set tested. Carr. 5/-.
VALVES 9d. EACH
1,000's available. Most types.
Post 1d. each. Min. 6d.
LATEST LIST AVAILABLE—Post
3d.

Condensers. 100—10/- New
Assorted electrolytics and PFs.
Resistances. 100—5/- Assorted
sizes, watts, grades.

DUKE & CO (London) Ltd
621/3 ROMFORD RD.
MANOR PARK, E.12
ILford 6001/3
Liverpool St. Stn. to Manor Park
only 10 mins.

TAPE CABINETS 20/-
To fit B.S.R. and Collaro
Studio Decks. Carriage 5/-.



SPEAKERS

7/9

EACH

P.P. 2/3.

6in. 8in. 7in. x 4in. Money back
guaranteed. Enquire for other
sizes. Ex. mfd. salvage.

EXTENSION SPEAKERS
19/9 P. & P. 3/9.

2 tone covered cabinet. PM
speaker, switch and flex. Ideal
for kitchen, sick room, etc.

TELEPHONE HANDSETS
15/6 pair P.&P. 4/6
G.P.O. standard pattern.
House to Workshop, garage,
inter-office, etc.
Works off any small battery.

Continued from page 142 of the June issue.

SETTING-UP AND ALIGNMENT

BY P. R. LEWIS

Double Conversion Communications Receiver

WITH a receiver of this complexity, it is advisable to check the completed wiring against the circuit diagram most carefully before switching on.

When satisfied that all is correct, insert a 250mA h.t. fuse and switch on the mains, with the h.t. switch S6, in the "Stand-by" position. Measure the heater voltage and check that all heaters are glowing. Measure voltage at V12 cathode, which under these conditions should be about 340V.

Leave meter probe on V12 cathode and switch on the h.t. The voltage should drop to approximately 250V as shown in voltage table (Table 1).

With a.v.c. "off", noise filter "out" and diode detector in circuit, turn up the i.f. and a.f. gain controls. The loudspeaker should show signs of life and there should be no sign of instability. If instability is present the source can usually be traced by bypassing possible "hot spots" (e.g., screen and cathode resistors, h.t. feeds) with a large capacitor (say 0.5 μ F paper) or by placing an earthed metal screen between stages. When the faulty stage has been located, rearrangement of wiring may effect a cure. If not, the remedial capacitor or screening will have to be made permanent.

Check again for instability with noise filter "in" and triode detector in circuit.

Next, with conditions as in first instance, check voltage against those shown in Table 1. After this, feed an a.f. voltage from a signal generator via 0.1 μ F capacitor to the top of the a.f. gain control to check audio amplifier.

Second I.F. Alignment

If this is satisfactory remove coil set and place shorting strap across grid winding of L6. Connect 0—100V d.c. meter across VR5. Feed a 465kc/s modulated signal on to grid 1 of V5 and adjust

both cores of IFT5 for maximum reading on meter. Now feed the signal at the same frequency to the control grid of V4 heptode (pin 2) and adjust IFT4 cores for maximum reading, reducing signal generator output as necessary.

The signal may be fed in via a 0.1 μ F capacitor if desired but a more satisfactory method is to wire a 2in. length of stiff wire to the appropriate valve pin. A rather longer length of stiff wire is erected from the output terminal of the signal generator to serve as a radiator. This system gives, by moving the generator position relative to the receiver, an easily variable input and enables the signal to be kept at the minimum strength necessary for accurate lining up.

Note.—To avoid inconsistent results the receiver chassis and generator case must be well bonded together.

TABLE 1

	Anode	Screen	Cathode
V1	170	117	2.0
V2	243	105	1.0
V3, 5	237	115	1.4
V4 heptode	241	100	1.5
V4 triode	100		
V9	85	80	2.1
V10	248	247	8.4
V11	105	—	—
V12	245 a.c.	—	255
V13	148	—	—

Table of voltages.

H.T. at C66=248V at 135mA.

Mains current=290mA at 240V a.c.

All measurements made with an Avo model 8, no signal input and i.f. gain controls fully up.

Beat Frequency Oscillator

The b.f.o. is now adjusted. Switch on by S3 and feed a 465kc/s unmodulated signal on to pin 2 of V4. Adjust core of L5 until beat note is heard in loudspeaker. If the note is weak insert a coupling capacitor (C62) of 5pF between anodes of V7b and V5. In most cases, however, the pick-up level due to stray capacitance will be adequate.

Second Oscillator

The second oscillator now requires adjusting to run at 2.065Mc/s. Remove shorting link from L6, set generator to 1.6Mc/s modulated, feeding in at same point as during previous two operations. Adjust can of L6 until signal is heard in loudspeaker and the meter reading peaks.

TABLE 2

Range	Low frequency tracking point	Centre tracking point	High frequency tracking point
3	1.84 Mc/s	2.64 Mc/s	4.5 Mc/s
4	5.5 Mc/s	7.93 Mc/s	13.5 Mc/s
5	11.55 Mc/s	16.65 Mc/s	28.36 Mc/s

Tracking points for alignment.

It is possible but unlikely that two responses will be heard. If this does occur adjust to the one for which the core is furthest out of the coil.

Finally, to check that the oscillator is in fact running at the correct frequency, use generator with unmodulated output and sweep until a beat note is heard. This should occur at 2.065Mc/s on the generator dial.

1st I.F. Alignment

The cores of IFTs 1, 2 and 3 are now lined up by feeding in 1.6Mc/s modulated at the control grids of V3 (pin 1) and V2 (pin 7) in turn, reducing coupling and/or second i.f. gain control as required.

All cores should be held in position when adjusted, preferably by dropping in a spot of melted wax. It is important to remember that when adjusting a two-cored i.f. transformer, movement of the second core may upset the alignment of the first. Therefore the cores may have to be adjusted alternately several times until correct alignment is achieved.

R.F. Circuits

Full lining-up data for the r.f. coils is supplied by Messrs. Denco, including the ideal tracking points as shown in Table 2.

Following this normal procedure insert one coil set and set the generator to the low frequency

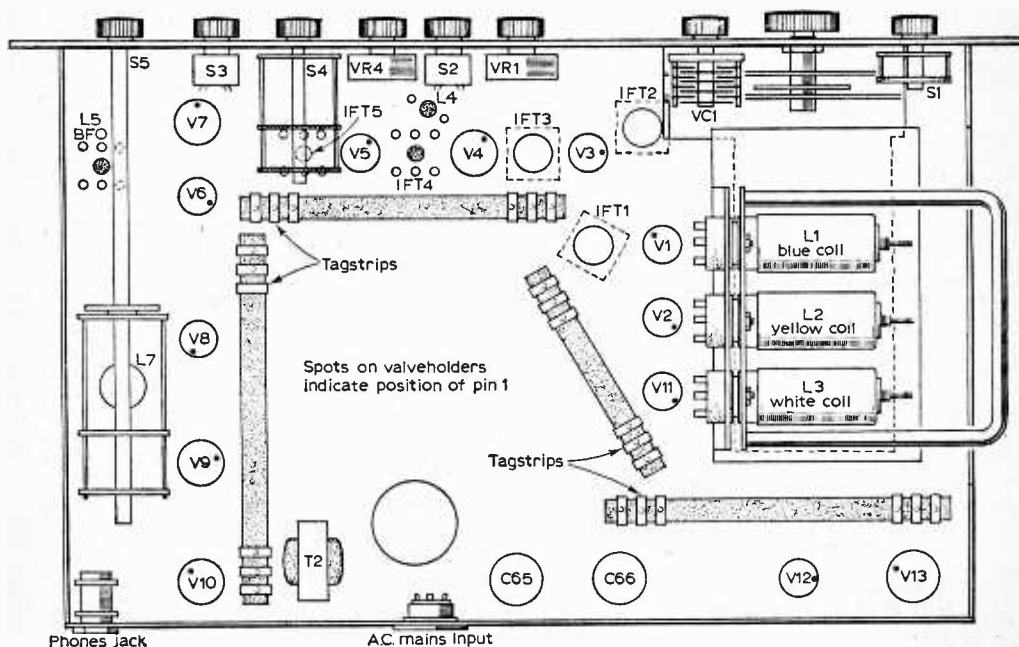


Fig. 6: Under-chassis layout of components.

SUCCESS!

The SINCLAIR SLIMLINE has proved itself. Over a thousand constructors have already built this wonderful little receiver and dozens have written to let us know how pleased they are. The reasons for this enormous success are simple:

1. The Sinclair Slimline is the smallest receiver of them all, only $2\frac{1}{2} \times 1\frac{1}{2} \times \frac{1}{2}$ in. Yet in performance and design it far surpasses sets many times as large.
2. Using only its internal ferrite rod aerial it will receive all stations on the medium wave band including Home, Light, Third, Luxembourg and dozens of continental transmissions.
3. Elegant deep royal blue case with gold lettering and calibrated dial in gold on white. Both designed by a professional artist.
4. The earpiece provided gives superb reproduction free from noise or distortion and sufficient volume even for use in a car.
5. All the components are brand new and MICRO-ALLOY TRANSISTORS are employed throughout.
6. The completely new reflex circuit developed by Sinclair Radionics engineers results in a radio with the sensitivity and selectivity of a good superhet but with no alignment problems.
7. Well illustrated, superbly clear instructions are provided.
8. A carefully designed printed circuit board, on which all the components are mounted, is supplied.
9. Assembly is perfectly straightforward and simple even for a complete beginner yet the brilliant performance will more than satisfy the expert.

A complete book on MAT's entitled "22 TESTED CIRCUITS USING MICRO-ALLOY TRANSISTORS" is available from us at 5/9 including postage.

Prices of MAT's remain

MAT 100 and MAT 120 .. 7/9	} POST FREE
MAT 120 and MAT 121 .. 8/6	



TOTAL COST

49/6 P.P.1/6

Just two of the many letters we have received. The originals may be seen at our Cambridge office.

Dear Sirs,

I have just built your Transistor Micro-Radio the "Slimline" and I'm amazed at the results. So far I've got about 10 stations including AFN, Stuttgart and Munich. I've built many sets but this one leaves them all standing."

*Thanking you,
H.S., Watford.*

Dear Sirs,

I have received delivery of the "Sinclair Slimline" and have completed assembly. The quality of reproduction for both voice and music obtained with your circuit is so delightful that I do not overstate when I say that I have lost interest in the other more conventional transistor sets that I have built. I have one good quality sound reproducer, which I described some years ago in the technical press, but have found that I can obtain an equal effect for personal listening with the "Sinclair Slimline."

I should be favoured to receive a further kit when more are available (I assume the demand will be high and shall be glad to take my turn). I enclose a cheque in payment for this further order.

*Yours faithfully,
J.F., Glasgow.*

We would like to thank all those constructors who have written us such pleasant letters and to apologise for slight delays in delivery which have occurred owing to the overwhelming demand. However we have now increased our staff to cope with this and can give a very prompt service.

SEND FOR YOUR 'SLIMLINE' TODAY TO:—

SINCLAIR radionics LTD

69 HISTON ROAD, CAMBRIDGE

"THE CONSTRUCTOR'S PARADISE"

BEAR HUDSON LTD.

63, GOLDHAWK ROAD, SHEPHERD'S BUSH, LONDON, W.12
(Next to Goldhawk Rd. Metropolitan Stn.) Phone SHE 2581/4795.
Open all day Saturday

COMPONENTS - HI-FI - BOOKS - SERVICE

24-HOUR MAIL ORDER SERVICE with all goods guaranteed.
★ FREE POSTAGE on orders over 20/-; add 1/- postage if under.
★ HI-FI INSTANT COMPARISON ARRANGEMENTS.
★ COMPREHENSIVE TECHNICAL SERVICE for Customers.
★ BULK PURCHASING DEPT. and own manufacturing facilities mean LOWEST PRICES.

THE FANTASTIC

SINCLAIR 'SLIMLINE'

VEST-POCKET RECEIVER



- ★ MAT TRANSISTORS
- ★ AMAZING RANGE AND QUALITY
- ★ 21 x 14 x 1/2 in.
- ★ SUPER SENSITIVE

All parts (except bat.) come to

49/6

POST FREE

This fantastic receiver, using latest Micro-Alloy Transistors, brings in countless stations (med. wave) with truly superb quality and sensitivity. Absolutely self-contained with printed circuit board and all parts for easy building. With free ear-piece.

WHY BE WITHOUT YOUR OWN TEST METER?

We offer an excellent range of meters for all constructor requirements. S.A.E. brings list.

VILCO POCKET RECEIVER

Special Limited Offer


Complete Loudspeaker Transistor Receiver plus battery, carrying case, extending rod aerial and earpiece. £7 value while stocks last, complete. Post Free

63/-

TRUE HI-FI FROM CRYSTAL P.U.s.

TSL CONSTANT VELOCITY EQUALISER

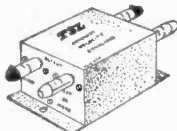This remarkable new T.S.L. development enables quality almost as good as the finest professional magnetic pick-ups to be obtained from crystal or ceramic types. With it, even cheap record players become first-class instruments. With good equipment results are astonishing. Ideal for B.B.C., Collo, Garrard and Aco. With plugs for mono or stereo. 3 years' guaranteed. Ready for use.



30/-
POST FREE

"GOLDHAWK" RADIO TUNER

Ultra-sensitive diode receiver with uniquely selective tuning system. Ideal feeder for tape, hi-fi, or use as pocket receiver. Parts with instrns. FINE QUALITY AND SENSITIVITY

21/-
POST FREE

TSL HIGH STABILITY RESISTORS AND CAPACITORS

Wide range of components always in stock, standard, miniature and min.-min. S.A.E. for lists.

SET MULLARD OF 6 TRANSISTORS

For 8/16t receivers OC44, 2 x OC45, OC81D, matched pair OC81. Save over £1. Post Free

32/6

TAPE AT THE PRICE YOU WANT
Past stocks available, all branded and money saving. S.A.E. for list.

Agents for JASON, LEAK, LORENZ, QUAD, RADFORD, TSL, WHARFEDALE, W.B., etc.

M.A.T. MICRO-ALLOY GOLD-PLATED TRANSISTORS

Phenomenal performance

A revolutionary advance in transistor technique and performance. Will operate up to 150 Mc/s with current gains of better than 250. With a single "MAT", stage gains as high as 1,000 times are possible. Absolute minimal voltage and current collector requirements, ultra low-noise, gold-plated leads. FULL DATA SHEETS FREE. Also "22 Tested Circuits using MATs" covering S.W., Hi-Fi, Personal and TV applications (size 10 1/2 x 7 1/2 in.) 5/- post free.

MAT 100	7/9
MAT 120	7/9
MAT 101	8/6
MAT 121	8/6

We stock the complete range!

BERNARD'S RADIO BOOKS

Covering almost every possible subject on radio, hi-fi, electronics for the constructor at every level of experience. Latest subjects include:

146 Hi-Fi Speaker Enclosures 5/-	173 Practical Transistor Audio Amplifiers. 3/6
151 Transistor super-het receivers 7/6	175 Transistor Test Equipment & Servicing Manual .. 3/6
163 Radio, TV and Electronics Data Book 3/6	177 Modern Transistor Circuits for Beginners .. 7/6
168/7/8 Transistor Circuits Manuals, Nos. 2, 3 & 4, ea. 2/6	179 Transistor Circuits Manual No. 5 .. 5/-

Send 6d. for FREE 1963 Comprehensive Radio Books Catalogue. Over 70 titles (24 pages).

A NEW-PRACTICAL WAY of UNDERSTANDING

Radio : Television Electronics

including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test instruments; Photo-electrics; Nucleonics, etc.

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below for full particulars.

POST NOW

TO RADIOSTRUCTOR (DEPT. G107)
READING, BERKS.

Please send brochure, without obligation to;

★ Name
Address
(We do not employ representatives)

★ BLOCK CAPS PLEASE

7/63

FREE THIS BOOK WILL INTEREST YOU!

EARNING the PRACTICAL WAY

Radiostructor EQUIPMENT-COURSES

FOR .. Your Career
.. Your Own Business
.. An Absorbing Hobby

RADIOSTRUCTOR

LEADS THE WORLD
IN ELECTRONICS TRAINING

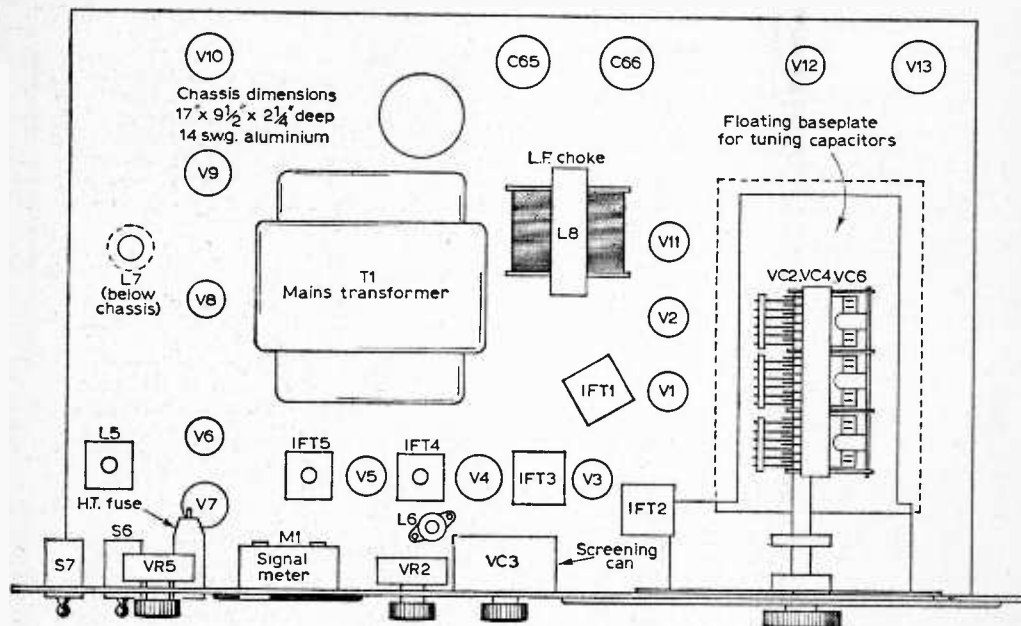


Fig. 7: Above-chassis layout diagram.

tracking point for the range chosen. Adjust the main tuning control until the pointer is at this frequency (either engraved on scale or calculated point if log scale is used) and feed in signal to signal grid of V2 (pin 7) or, to save time, to the aerial input. Adjust oscillator core L13 until a signal is heard and the meter peaks, then similarly adjust L1 and L2.

Now move signal generator frequency to the high frequency tracking point and adjust main tuning control to this frequency. Adjust the oscillator trimmer TC1 until a signal is heard and the meter reading peaks, then similarly adjust the r.f. panel mounted trimmers VC1 and VC5.

Fig. 8: A side view showing the location of the coil set.


These latter adjustments will have undoubtedly altered the tracking at the low frequency, so this must now be returned to and the cores of L1, L2 and L3 readjusted. Continue the two procedures alternately until no further improvement can be obtained at either point, after which the generator is set to the centre tracking point to check if signal level is approximately the same as at the two other tracking points.

The whole alignment procedure is now repeated for the other coil sets and the first settings of the two panel trimmers noted in each case. The trimmers must, of course, be altered to the appropriate settings whenever during operation a change of band is made.

However, if a dial with a purely arbitrary marking is used (e.g., 0—100, and therefore no oscillator trimming capacitor is used) alignment is much simplified since no dial reading need

exactly coincide with a particular frequency. In this case set the panel trimmers to the centre position, set the main tuning control to an approximately calculated setting for the centre tracking frequency and feed in a signal at this frequency. Adjust L1, L2 cores until the signal is heard and the meter peaks.

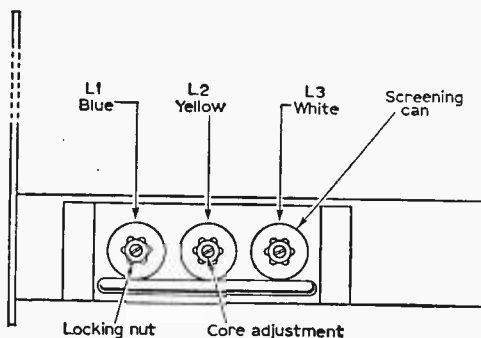If a particular coil set does not appear to cover



the specified band, experiments can be made by choosing a slightly different dial mark for the centre tracking frequency and adjusting the cores to it or by wiring a small capacitor (10—20pF) across the grid winding of the oscillator coil inside the can. Either method will result in an alteration of the band covered.

During operation, with either method of alignment, the panel trimmers will need to be adjusted to peak the signal. However, with the latter method a greater variation will be noted from one end of the band to the other, but this is no disadvantage.

One final check needs to be made to ensure maximum efficiency of conversion in the first mixer V2. Insert 0—1 d.c. meter in the earthy end of the injection grid resistor R7.

With Band 4 coil set in position and tuning control in mid-position the meter current should be 500mA, this corresponding to the correct oscillator output. The current may vary about this value, being greater when the receiver is tuned to lower frequencies and vice versa, but the use of the r.f. choke L4 to load the oscillator anode ensures that it is of the right order (without the choke it may well be below 100mA). If the mean current is low, take the oscillator feed from the anode (C55 to pin 5, V11).

Curing Instability

The possibility of instability during i.f. alignment has been mentioned earlier. With the insertion of coil sets, however, and the bringing


variable time-constants, and of the noise filter will become apparent.

The signal meter should be set to zero with the aerial input socket shorted to earth and sensitivity adjusted as required. Gain should be controlled by the first i.f. gain control wherever possible since alteration of the second i.f. gain control renders the signal meter virtually useless. Switch over to the triode detector when a very weak signal is heard, whereupon a marked increase in sensitivity will be observed.

A.G.C. Time-constants

Finally, if any further values of the a.g.c. time-constant are required the size of capacitor can be calculated quite simply as below:

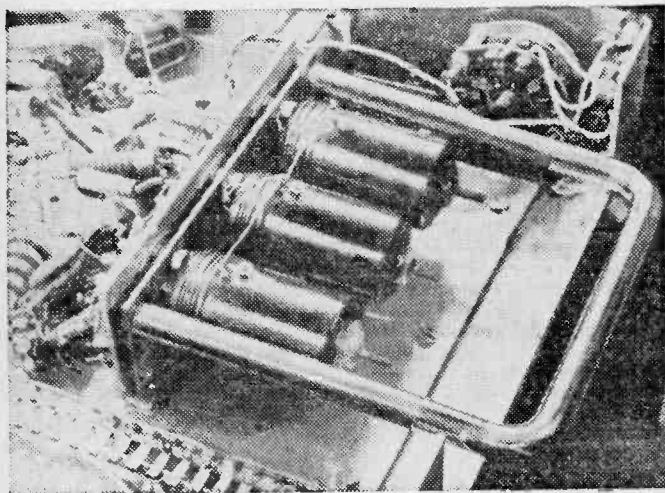Time-constant of a.g.c. circuit = sum of the products of all resistors in the a.g.c. circuit and the total capacitance following them in the circuit.



A close-up view of the coil set mounted in the receiver.

into operation of the front end further instability may become apparent. The use of stabilised h.t. lines, grid stoppers and separately decoupled h.t. feeds should have minimised the possibility, but nevertheless further screens may be necessary between the input and output circuits of V1 and V2. This should cure any instability when tuned to the higher frequencies. If trouble is apparent at low frequencies it may well be due to i.f. radiation from the detector stage getting back to the front end and screening in this direction may be useful.

Also, if in operation the bandwidth seems greater than expected it may be worth interposing a screen between the flying leads of IFT1 and IFT2 to ensure that they cannot "see" each other and that the only coupling between them is via C9.

Operating the Receiver

The receiver is now ready for air testing, when the merits of the various modes of a.g.c., with its

To simplify this with an example the time-constant in position 1 of S2=R62 (C25+C29 +C16+C12)+R16(C16)+R11(C12)

$$= 1.2 \times 10^6 (0.01 \times 10^{-6} + 0.05 \times 10^{-6} + 0.01 \times 10^{-6} + 0.01 \times 10^{-6} + 100 \times 10^3 (0.01 \times 10^{-6}) + 100 \times 10^3 (0.01 \times 10^{-6}))$$

$$= (1.2 \times .08) + 0.001 + 0.001$$

$$= 0.098 \text{ seconds } \Omega 0.1 \text{ seconds.}$$


CORRECTIONS

Two small corrections are required with respect to the first part of this article, which appeared in the May issue.

(1) In the description of the First Mixer Stage (page 49) the seventh line of the second paragraph should read: "of the grid circuit, this once again reducing any ...".

(2) In Fig. 2(c) (page 52) C44 was wrongly marked as 1,000pF. This capacitor has, in fact, a value of 0.01μF, as indicated in the Components List.

UNIVERSAL AVOMETERS

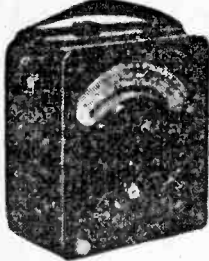

Guaranteed perfect working order. Supplied complete with leads, batteries and instructions.
Model "D" 34 range £8.19.6
Model "T" 50 range £11.0.0
Registered Post 5/- extra.

MICROAMMETERS

0-500 microamps. 2 in. circular flush panel mounting. Dials engraved. 0-15, 0-600 volts. BRAND NEW. BOXED. 15/- P.P. 1/6.

7.5 K.V.A. AUTO TRANSFORMERS

0-115-230 volts. Brand new boxed. £15. Carriage 10/-.

230/250 VOLT A.C. MOTORS
4 1/2 in. dia. 90 watts. 5,000 r.p.m. 1 in. spindle. 22/6 P.P. 1/6.

1 K.V.A. ISOLATION TRANSFORMERS

230 v. Pri.: 230 v. Sec. Boxed, £5 each. Carriage 10/-.

VARIAC TRANSFORMERS
24 amp., 230 volt primary, 185 to 250 volt output, £12.10.0. Carriage 10/-.

TELEPHONES TYPE "H"
Sound powered, generator bell ringing, 2 line connection. Fully tested, £4.19.6 pair. Carr. 5/-.

HELIPOTS
Available in the following sizes, 10kΩ, 50kΩ, 10k + 2kΩ. All new, boxed, 22/6 each. P.P. 1/3.

3000 WATT AUTO TRANSFORMERS
0-115-230 volts, step-up or step-down. Brand new, boxed ex-U.S.A. £7.10.0 each. Carr. 10/-.

PANEL METERS

100μA	2 1/2"	F.M.	D.C.	42/6
100μA	3 1/2"	F.M.	D.C.	62/6
1 mA	2 1/2"	F.M.	D.C.	25/6
300/30 mA	2 1/2"	F.M.	D.C.	9/6
350 mA	2 1/2"	F.M.	D.C.	10/6
300 v.	2 1/2"	Proj.	A.C.	19/6
300 v.	2 1/2"	F.M.	A.C.	25/-
500 v.	2 1/2"	F.M.	A.C.	25/-
120 v.	3 1/2"	F.M.	A.C.	32/6
1500 v.	2 1/2"	Electrostatic		25/-

FIELD TELEPHONES TYPE "P"

Suitable for many applications. Generator bell ringings, 2 line connection. With batteries and wooden carrying case, fully tested, £4.19.6 per pair. Carr. 5/-.

SUB-STANDARD D.C. AMMETERS
9 ranges, 150mA, 1.5A, 3A, 7.5A, 15A, 30A, 60A, 300A, and 450A. Housed in teak portable case, 8 in. mirror scale. Supplied brand new with all shunts and leather carrying case, £15 each. P.P. 10/-.

800-2,000 metres.
100-500 metres 6-22 Mc/s. output for phones or 3Ω speaker. As new £5.19.6. Carr. 10/6.
14 Mc/s. PCR2 but covers 150/550 metres. 2-7 Mc/s. 7-22 Mc/s. including top band. As new £8.8.0. Carr. 10/6.
All above models can be supplied with internal power unit to operate on 200/250 v. A.C. at 39/6 extra or alternatively plug-in external power units are 35/-.

P.C.R.2 RECEIVERS



NATIONAL H.R.O. RECEIVERS



SENIOR MODEL. Supplied complete with full set of 9 coils covering 50 kc/s. to 30 Mc/s. Each receiver thoroughly checked and available as follows:
TABLE MODEL. As new condition £25.
TABLE MODEL. Extremely good used condition £18.18.0.
RACK MODEL. Extremely good used condition £18.18.0.
Carriage £1 extra.

200/250 volt A.C. power packs for above receiver, also sold separately. 59/6. Carr. 5/-.

PRECISION COMBINATION VOLTMEETER/AMMETER FOR A.C. AND D.C.

Two separate instruments housed in polished wood case, 6 in. scales with knife edge pointers.

Ranges:
Volts A.C. and D.C. 160-300-600 v.
Amps. A.C. and D.C. 25-50-150-200 A.
Supplied complete with all current shunts, leads and leather carrying case. Manufactured by Elliott Bros. Supplied brand new. £8.18.6 each. Carriage 7/6.

HALLCRAFTER S-36 V.H.F. RECEIVERS

F.M./A.M. 27-143 Mc/s. 110 volt A.C. (transformer supplied for 230 v. A.C.) Improved version of S-27. Tested before despatch. Brand new boxed with instruction manual. £40 each. Carr. 2/-.

MINE DETECTOR No. 4A

Will detect all types of metal. Fully portable. Complete equipment supplied tested with instructions, 39/6. Carriage, 10/6. Battery 8/6 extra.

COLLARO STUDIO TAPE TRANSCRIBER

Brand new 1962 model. 3 speeds, 3 motors, digital counter, etc. With latest Bradmatic heads and interlock button. Supplied with spare spool, instructions, fixings, 10 gms. each. Carr. paid.

FABULOUS TAPE OFFER

Famous American Brand Tapes. Brand new, fully guaranteed. 5 in.—600ft., 10/6. 5 in.—800ft., 13/6. 5 in.—1200ft., 17/-, 7 in.—1200ft., 13/6. 7 in.—1800ft., 18/6. 7 in.—2400ft., 27/6. P. & P. extra. S.A.E. for full tape list.

MULTIMETERS BRAND NEW—FULLY GUARANTEED LOWEST EVER PRICES

Supplied with Leads, Batteries and Instructions.

1,000 Ω/VOLT	4,000 Ω/VOLT
0/15/150/1,000 v. A.C. and D.C.	0/10/50/250/500/1,000 v. A.C., D.C.
0/150 mA D.C.	0/250μA/0/25/500 mA D.C.
0/100 K Ω etc.	0/30K/300K/3 meg. etc.
59/6. P. & P. 1/6.	59/6. P. & P. 2/6.
20,000 Ω/VOLT	30,000 Ω/VOLT
0/10/50/250/500/1,000 v. A.C. and D.C.	0/50μA/0/25/500 mA D.C.
0/50μA/0/25/500 mA D.C.	0/50K/500K/5 meg. etc.
0/10/50/250/500/1,000 v. D.C.	0/10/10/50/250/500/1,000 v. A.C.
0/10/50/250/500 v. A.C.	0/50μA/0/10/250 mA D.C.
0/10K/1 meg./10 meg. etc.	£5.10.0. P.P. 2/6.
30,000 Ω/VOLT	0/1/1/2/10/25/100/250/500/1,000 v. D.C. and A.C.
0/50μA/5/50/500 mA/0/12 amp. D.C.	0/60K/6 meg./60 meg. etc.
£8.17.6. Post paid.	50,000 Ω/VOLT
0/10/50/250/500/1,000 v. D.C. and A.C.	0/25μA/2.5/25/250 mA D.C.
0/10K/100K/1 meg./10 meg. etc.	£7.10.0. P.P. 2/6.



Hours of Business: 3 Lisle Street, 9 a.m.—6 p.m. Half Day Saturday
34 Lisle Street, 9 a.m.—6 p.m. Half Day Thursday

MARCONI CRI00/8 RECEIVERS BRAND NEW

Packed in original transit cases and complete with handbook/manual. 60 Kc/s to 30 Mc/s. 200/250 volt A.C. operation. Tested before despatch.

£35 Carriage £2.

FIELD STRENGTH METERS

Frequency coverage 1 Mc/s to 250 Mc/s. Visual indication by 200 microamp meter or aural indication by earphone. Supplied complete with earphone, 5 section telescopic aerial and instructions, 59/6. P. & P. 2/-.

L.T. METAL RECTIFIERS

All full wave bridge connected. Brand new, guaranteed.

12/18v. 1.5A. 3/9 24/36v. 4A. 22/6
12/18v. 2.5A. 6/3 24/36v. 15A. 45/-
12/18v. 4A. 8/3 36/48v. 2A. 19/6
12/18v. 6A. 12/3 36/48v. 4A. 28/6
12/18v. 10A. 22/6 36/48v. 6A. 32/6
12/18v. 15A. 37/6 48/60v. 2A. 21/-
24/36v. 1A. 7/3 48/60v. 10A. 82/6
Please add postage.

L.T. TRANSFORMERS

All primaries tapped 200/250 volts
1 Battery Charging. 3.5, 9 or 17 volt, 1 amp., 9/9. Ditto 2 amp., 14/3. Ditto 4 amp., 16/6. 9 or 17 volt, 6 amp., 28/-.
2 Model Type 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt, 2 amp., 18/6. Ditto 4 amp., 27/6. Ditto 5 amp., 37/6. Add Postage.

MINIATURE MODEL ACCUMULATORS

Lead Acid. BRAND NEW. 2v. 1.5 A.H., 4 x 1 1/2 x 1 1/2 in., 1lb. 5/8. P.P. 1/3. 12v. 0.25 A.H., 4 x 3 x 1 1/2 in., 2lb. 15/6. P.P. 1/6.

R.C.A. PLATE TRANSFORMERS

Pri. 200/250 v. sec. 2,000-0-2,000 v. 500 mA tapped 1,500 v. New. Boxed. £6.10.0. Carriage 15/-.

DUMONT K1051P DOUBLE BEAM C.R.T.

Twin Gun. Brand new, boxed. 59/6. P.P. 3/6.

1.2 Ohm 12 Amp RHEOSTAT
Geared slider type, new boxed. 15/6 each. P.P. 3/6.

MARCONI TF-885 VIDEO OSCILLATORS

25c/s-5Mc/s. Supplied in guaranteed as new condition. £90 each.

H.R.O. DIALS

Brand new. 27/6. P.P. 2/6.

MINIATURE PANEL METERS

For 1 1/2 in. dia. panel hole.
0-50 μA 39/6 0-500 v. D.C. 27/6
0-500μA 32/6 "5" meter 35/-
0-1 mA 27/6 "VU" meter 42/6
0-5 mA 27/6

100,000 OHM PER VOLT MULTI RANGE TEST METERS.

0.5/2.5/10/50/250. 100,000 Ω/volt 0/500/1000. 35,000 Ω/volt D.C. 0.5/10/50/250/1000. 12,500 Ω/volt A.C. 10 U.A./250U.A./2.5/25/250 M.A. 10 amp D.C. 0-20 Meg. Resistance. D.B.—20 db + 62 db. With batteries, leads, and full instructions £6.18.6. P.P. 2/6.

Send S.A.E. For Bargain Lists

G.W. SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET LONDON, W.C2

T rade N ews


Transistor Power Unit

SERVICING and testing transistor equipment is much simplified if correct power supplies are available, so eliminating the need for batteries. Nombrex Ltd. have just released a new power unit for this purpose, which delivers a d.c. output voltage which is continuously variable from 1 to 15V, at mean currents up to 100mA.

The unit is designated type 61 and sells for £5 17s. A printed circuit chassis is used in the construction and the housing is a robust steel case, measuring 6½in. x 4½in. x 2½in.

Incorporated in its design is a variable overload protection arrangement which serves to protect both the circuit under test and the unit itself. This ensures that transistors cannot be damaged by overload, short-circuits or thermal run-away.

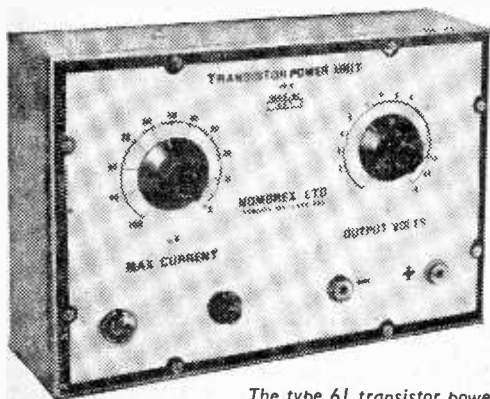The manufacturers of the type 61 power unit are Nombrex Ltd., Estuary House, Camperdown Terrace, Exmouth, Devon.



The type 61 transistor power supply from Nombrex Ltd.




The model RA-1 receiver, new from Heathkit.

Amateur Bands Receiver

A NEW kit is now available from Heathkit, which is described as a basic amateur bands receiver. This set (model RA-1) covers 160 to 10m in six bands. The circuit employs eight valves and to overcome the problem of alignment, the complete "front end" of the r.f. and mixer sections is supplied ready assembled, aligned and tested.

Several desirable features are included in the design of the RA-1, one being a signal strength tuning meter which is mounted on the front panel alongside of the illuminated slide rule scale.

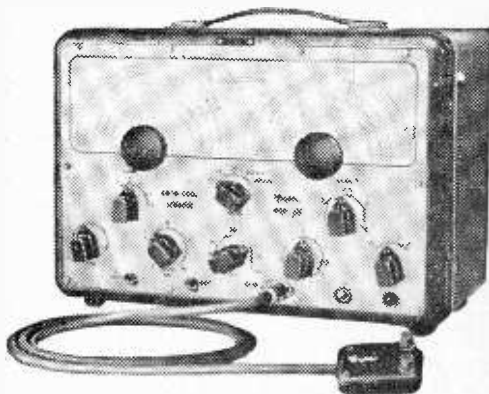Daystrom Limited, Gloucester are the makers of the kit.




Taylor's new a.m./f.m. signal generator.

A.M./F.M. Signal Generator

THE model 62A signal generator is one of the latest releases from Taylor Electrical Instruments Ltd. The a.m. section of the instrument covers 4Mc/s to 12Mc/s in five bands. The frequency coverage of the sweep generator and f.m. generator sections are the same, being 4 to 45Mc/s in four bands, and 70 to 120Mc/s.

Used in conjunction with an oscilloscope, the 62A provides complete facilities for the sweep alignment of r.f., i.f. and discriminator or ratio detectors in f.m. receivers.

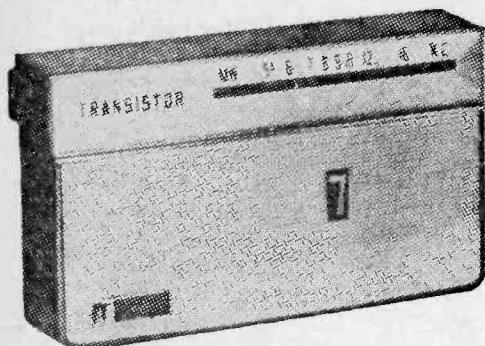The manufacturers of the 62A signal generator are Taylor Electrical Instruments Ltd., Montrose Avenue, Slough, Buckinghamshire.



This is the latest portable receiver from Denham and Morley.

Portable Receiver

THE latest addition to the Denham and Morley range of radios is the model 7 TE-2L, and is named the "Bluebell". This is a portable receiver employing a seven transistor circuit. The power is supplied by four pen-torch cells and both long and medium wave bands are tunable over the horizontal scale.

The retail price of the "Bluebell" is 10½ guineas, complete with earphone and leather case. The makers are Denham and Morley Ltd., Denmore House, 173/175 Cleveland Street, London W1.

Auditron Components

WE would like to bring the attention of our readers to the fact that certain components used by the author of the Auditron article, which appeared in recent issues of P.W., can be obtained from Neoflex Ltd., who are the British agents for Hirschmann products, the makers of the components.

Of special interest are the type AGS 10 crocodile clip (plug type, red or black) and the type BIL 20 panel socket (red or black) which can be obtained

POCKET SIGNAL INJECTOR

—continued from page 239

tip on point C (volume control slider) and turn the volume control to the full volume position. If a note is heard, then the fault lies in the r.f. or detector stages (i.e. from volume control back to aerial tuning circuit). If, however, no note is heard at point C the fault lies in the a.f. and output stages (i.e. from the volume control to the loudspeaker).

If this proves the fault to be in the r.f. stages, then methodically work back towards the aerial with the probe tip, going to points D, then E, then F, etc., right through to point K. If this is done then one point will be reached where no signal is heard and clearly the fault lies in the stage contained between this point and the one just previously tested. The stage in which the fault exists has been found very quickly and with a meter all components in it should thus be checked. The fault should then be revealed.


Similarly, if when testing at point C initially the fault appears to be in the a.f. or output stages the probe should then be placed to point A, then to

in sets of three, at 11s. per set. The address of the agents is Neoflex Ltd., 115a Cricklewood Broadway, London NW2.

Loudspeaker Pillow

AN ingenious new accessory is now on the market which will prove of interest to all users of transistor radios. This device, which is known as the "Marvel" listening pillow, allows personal listening without the inconvenience of an earpiece. The inflatable plastic pillow has a built-in "muted" loudspeaker which is connected to the receiver's earpiece socket by a cable supplied. Deflated, the pillow folds into a pocket-sized pack and the cable and plugs are then accommodated in a small pocket.

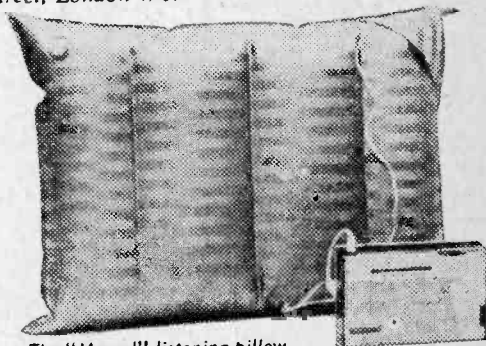The price of the "Marvel" pillow is 38s. 6d. and is available from New Lines Marketing Company, 11 Dryden Chambers, 119 Oxford Street, London W1.



The "Marvel" listening pillow.

Change of address

THE radio component retail firm of Henry's Radio Limited, have moved from their old premises in Harrow Road, to new and larger premises at 303 Edgware Road, London W2.

point B, working backwards from the loudspeaker. This should be done until no signal is heard at one of the test points, when again one can assume the trouble lies between this point and the one just previously checked and where a signal was heard. The location of the fault has thus been quickly determined in the a.f. stages and the components in the suspected area (i.e. the resistors, capacitors and transistors) should thus be checked using, where possible, a multimeter.

Once the suspect area (in either r.f., detector or a.f. stages) has been so located, the faulty component may in many cases be determined by purely using the injector. This is done by placing the probe tip on all points in the suspected area until one point is touched which doesn't produce a signal in the loudspeaker. The component or components connected to this point should then be checked to determine which one is the culprit or which is anchored to the printed circuit via a dry joint or unsoldered connection.

This should show how useful this little device can be in isolating and quickly cornering the majority of snags that can occur in modern-day equipment. ■

CLYNE RADIO LTD.




18 TOTTENHAM COURT ROAD, W.1
162 HOLLOWAY ROAD, LONDON N.7
9 CAMBERWELL CHURCH STREET, S.E.5
12 SUFFOLK HOUSE, GEORGE ST., CROYDON
10 WITTHY GROVE MANCHESTER, 4
Blackfriers 5379

All post orders, etc. to 162 HOLLOWAY ROAD, LONDON, N.7

The "AIR KING"

Our new highly successful Six transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio, with full MEDIUM wave and LONG wave coverage.

Look at these features!

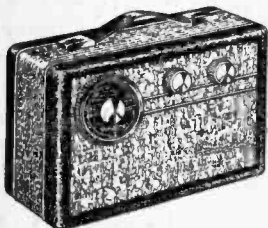

- ★ 500 milliwatt output to high flux 7 x 3in. high fidelity loudspeaker.
- ★ Six selected Mullard Transistors in latest super sensitive circuit, plus germanium diode. ★ Compact size—only 9½ x 3½ x 6in. (high).
- ★ Attractive three-tone cabinet. Black, Dark Grey, and Silver Grey, with gilt control knobs and all gilt fittings.
- ★ Coax socket for car aerial. ★ Brand new guaranteed components. ★ Push pull output. ★ Automatic volume control. ★ Long life battery. ★ Super sensitive internal ferrite rod aerial. ★ Nothing more to buy. Cabinet included.

Special inclusive price for **£7.19.6**

Plus P. & P. 4/- Alignment service available. Full assembly details and individually priced parts list, all of which are available separately. Price 1/6 post free.

The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price. Look at these features:—

- ★ Attractive styling. ★ Push-pull output. ★ 3 latest Mullard transistors plus valves type EBF83 and ECH83.
- ★ No Buzz. High Output and sensitivity. ★ Printed circuit (newest type). 7" x 4" High flux p.m. speaker.
- ★ Medium and Long Waves. ★ Push Buttons for fingertip control. ★ Extremely low Battery consumption (less than 1 amp.) ★ Easy to fit any make car (Positive earth only). ★ 12 volt operation. ★ Compact size measures only 7" x 7" x 2" deep. ★ Easy assembly. Supplied with dial and drive already mounted.



All parts available separately but if purchased at one time, the whole will be supplied at a special inclusive price of only **£10.19.6** Plus 4/- P. & P.
Parts list and comprehensive instruction booklet 2/6 post free (Deduct from cost if complete parcel purchased later.)

THE COMPONENT SPECIALISTS

MUSEum 5929/0095
NORth 6295/67
RODney 2875
Mun 3250
Blackfriers 5379

NEW BRANCH CROYDON

NOW OPEN AT
12 SUFFOLK HOUSE, GEORGE ST.

Municipal 3250
(One minute from East Croydon Station)
OPEN ALL DAY SATURDAY



MODEL TK.20A

Size 3½" x 2½" x 1½". Meter size 2½" x 1½". Sensitivity 1000 o.p.v. on both A.C. and D.C. volts, 0/5, 0/150, 0/1000 volts. D.C. Current, 0/150 mA. Resistance, 0/100K. Complete with test prods, battery and full instructions. OUTSTANDING VALUE AT

42/- Plus 1/6 P. & P.

MODEL TK.50

Size 5" x 3½" x 1½" 1000 ohms per volt AC/DC. DC Current 1-250 mA. DC and AC volts, 10, 250-500 and 1000 v. Resistance 0-10K, 0-100K. Complete with test prods, battery and full instructions. Outstanding buy at

57/6 Plus 2/6 P. & P.



The SINCLAIR SLIMLINE

A new miniature 2 TRANSISTOR printed circuit pocket radio. Completely portable and the smallest of them all—only 2½" x 1½" x 1½". Uses latest Micro Alloy Transistors and with built in ferrite aerial will receive all stations on Medium Wave—B.B.C., 208, etc. Easy to assemble—no alignment problems. All required components, including earpiece

ONLY **49/6** P. & P. 1/6.

All parts sold separately.

THE NEW "CLYMAX" !!

NEW LOW PRICE MADE POSSIBLE Through Further BULK PURCHASES !!



Nothing more to buy!

Plus 3/6 P. & P.


- ★ Completely self contained. No external aerial or earth required. ★ Full medium wave coverage, plus switched Light Programme on Long Wave. ★ Push-pull output—250 milliwatts. ★ Matched set of latest type Mullard transistors. ★ Genuine 2½in. P.M. Speaker.
- ★ New high-Q coils. ★ Ferrite rod aerial with high selectivity. ★ Size: 5½" x 3½" x 1½in. Two-tone cabinet. ★ Precision etched printed circuit with components references clearly marked. Alignment service available. All parts available separately. Full assembly instructions and individually priced parts list 2/- post free.

99/6

TAPE RECORDER CONSTRUCTORS

LATEST COLLARO STUDIO TAPE TRANSCRIBER. Latest type incorporating Record, Interlock, Lever, Button, 3 motors 3 speeds, 1½, 3½, 7½ i.p.s., takes 7in. spools. Push-button controls. NEW LOW PRICE. OF £10.10.0 ONLY! plus 7/6 P. & P. Usual H.P. facilities.

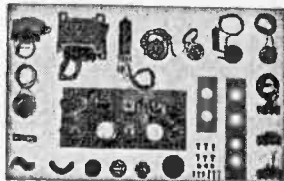NEW TAPE RECORDER AMPLIFIER TYPE 8311-V. Sub-assembled—anyone can build! Printed Circuit, all components mounted and dip soldered. Already tested. Each



lead cut to length. All that is required to complete the tape recorder is for a few components to be mounted in the cabinet and the free ends of the leads soldered to terminals which are clearly marked, everything supplied, all you need is solder, iron, pliers and screwdriver. Valve line-up: EF86, EC83, 2 x EL84, EZ81 and EM84 magic eye. Monitoring facilities, output socket for feeding to high quality amplifier, can be used as "straight" amplifier for record reproduction. EQUALISING ON TWO SPEEDS. OUTSTANDING VALUE AT £11.10.0 plus 2/6 P. & P. including all necessary instructions.

ATTRACTIVE TWO-TONE PORTABLE CARRYING CASE. Suitable for above amplifier and Collaro Studio deck. Fitted with 5in. x 5in. High Flux P.M. speaker for high quality reproduction. Inclusive price £5.5.0 plus 5/- P. & P. Full list of competitively priced mics. and stands on request. The above 3 items purchased at one time, SUPPLIED CARR. PAID.

NOW AVAILABLE! FOUR TRACK STUDIO DECK AS ABOVE, FITTED WITH HIGH-FI FOUR-TRACK HEADS. PRICE £13.19.6 plus 7/6 P. & P. Four track heads supplied separately, complete with mounting bracket for Studio Deck at 92/6 pair, plus 2/6 P. & P.

TAPE RECORDER AMPLIFIER 8311-IV. Exactly as 8311-V but four track. Suitable for the above high-fi four track heads. Price £12.12.0 plus 2/6 P. & P.

PRE-AMPLIFIER KIT TYPE 8312-CP. Complete high quality pre-amplifier kit for use with Collaro Studio Deck. Price £8.8.0 plus 2/6 P. & P.

N.B. Four-track deck and amplifier fit the above case without any modification whatsoever.

TAPE ! TAPE !

For the first time in this country Canada's Hi Fi Magnetic Recording Tape. Made by "Bel-Cleer" of Canada.

Following sizes available, others to follow. Brand New, NOT Sub-standard. High grade Acetate base, attractively boxed, fitted leaders, fully guaranteed.

5in., 600 ft. 12/6; 5in., 900 ft., 15/-; 5½in. 1,200 ft., 18/6; 7in., 1,200 ft. 18/6; 7in., 1,800 ft., 25/- P. & P. 6d. per spool. 3 or more post free. (Bona fide trade inquiries invited.)

PLASTIC SPOOL CONTAINERS for spool sizes 5in. 1/6; 5½in. 2/-; 7in. 2/3.

PLASTIC TAPE SPOOLS. Best quality. 3in., 1/3; 4in., 2/-; 5in., 2/-; 5½in., 2/3; 7in., 2/6; P. & P. 6d. per item. Orders over £1 post free.

TELEPHONE PICK-UP COIL. Designed to feed into the microphone input of either a tape recorder or any high gain amplifier. Easily attached to telephone by rubber suction attachment. The coil is electrostatically shielded to minimise hum pick-up. When positioned on telephone this model is more than adequate for a fully modulated tape recording. Brand new complete with 5 ft. shielded cable. ONLY 14/- Post free.




SENSATIONAL NEW 1963 DESIGNS — BY CONCORD

LOW PRICES ★ ★ ★ PICTORIAL STEP-BY-STEP PLANS ★ ★ ★ EASY AS A.B.C.

THE NEW "COSTA BRAVA"

42/6

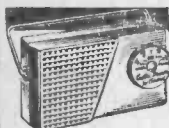

No earth or aerial required. All-transistor Radio. Revolutionary INTERNAL FERRITE AERIAL and moving coil speaker makes this

sensational pocket-size radio the best money-saving bargain of all time. Powerful, superb tone and clarity, ensures perfect reception for all your favourite programmes. Completely portable only 6½ x 3 x 1½ in. Two-tone case. Anyone can assemble with our simple PRINTED CIRCUIT PLAN. Send 42/6, plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. (All parts available separately.) FREE HIGH SENSITIVITY HIDE-AWAY EAR-PIECE GIVEN WITH EACH SET.

THE RINGO BURGLAR ALARM CLEARANCE SALE!

BIG PROFITS FOR YOU IF YOU BUY NOW!



Made to retail at 7 gns. you can now buy this famous Twin-gong Alarm for only 37/6—but only if you act now... stocks are strictly limited. Easily installed and operated. Switches on or off at any time. Fantastic FINAL reduction to clear (minimum order of 3). Car. Free. Free literature sent with each alarm. 37/6

THE NEW 4-STAGE "MINUETTE"


32/6



Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong drilled U.L.T.R.A. MODERN CASE, size only 6½ x 3½ x 1½ in. Uses three transistors and diode and SELF-CONTAINED LOUDSPEAKER. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening off 1/2 battery. Can be built FOR ONLY 32/6, including PROPER CASE, miniature speaker, etc. SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS etc., plus post and packing 1/6 (U.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

FREE HIGH SENSITIVITY HIDE-AWAY EAR-PIECE GIVEN WITH EACH SET

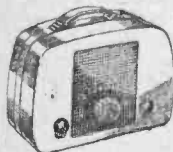THE MINUTE TRANSISTOR RADIO MIAMI ONLY 32/6



Unbelievably small—Outrageously cheap. You will be amazed at the fine quality of tone and volume of this great little radio. Only a fantastic 3½ x 2½ x 1½ in. the MIAMI will bring you great entertainment for months on a 1/2 battery. Simple assembly plan with each set. ONLY 32/6. YES 32/6!

Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

SELL SAFETY TO THE MOTORIST



Bulk purchase of bankrupt stock ensures this fabulous money-making offer. AUTOMATIC CIGARETTE LIGHTER Instantly provides ready lit cigarette without the driver taking his eyes from the road. Heavily chromium plated case holds 10. Easily and simply fitted to any car dashboard. Works off 6 or 12 volts. Retail Price 4/8. Special Clearance offer only. Carriage free. 12/6 each.

FABULOUS ST. TROPEZ Mk.6

Pocket Radio

ONLY 18/6



NO MORE TO PAY

This fantastic offer will amaze you—the compact ST. TROPEZ measuring 4½ x 3 x 1½ receives perfectly in bedroom, office or garden—over all medium waves including Luxembourg. Under 1d. per hour running cost. ANYONE can assemble it using our simple A.B.C. plan (P. & P. 2/6 extra) C.O.D. extra. Parts can be bought separately. Demonstrations daily, satisfaction guaranteed.


CONCORD ELECTRONICS (Dept. 14/16)

210, Church Road, Hove, Sussex

Extended Range to 350 Mc/s

TRANSISTORISED WIDE-RANGE SIGNAL GENERATOR 27

150 kc/s to 350 Mc/s

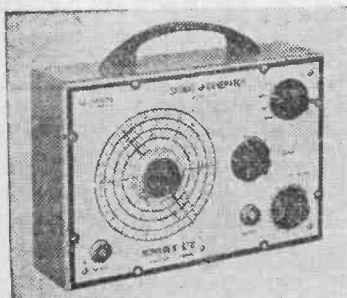

CHECK THESE FEATURES

COMPACT Only 6½" x 4½"

PORTABLE Weight 2 lbs.

ACCURACY! Under 2%

ECONOMY! 9v. Battery

DIRECT Calibration

RETAIL £7.18.6

With test lead and battery

Post and insurance 3/6 extra

CASH WITH ORDER, REGRET NO C.O.D.

EARLY DELIVERY


Trade and Export Enquiries Invited

S.A.E. for full technical leaflet.

12 Months' Guarantee.

NOMBREX LTD. (Instruments Division 57)

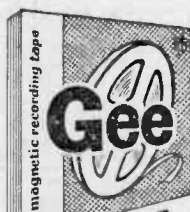Estuary House, Camperdown Terrace, Exmouth, Devon, England. Tel. 3515



LOWEST EVER PRICES

"GEE'S" SUPER QUALITY MESSAGE TAPES.

3in. Std. 150ft. 3/11
3in. L.P. 240ft. 5/-
3in. D.P. 400ft. 10/-
On brightly coloured spools in neat plastic cassettes. Ideal for gifts or messages.

"GEE'S" ACCESSORY KIT

1 "RIB" Splicer, 1 Splicing Tape, 3 Leader Tapes (3 colours), 10 Retaining Clips. Packed in plastic container. PRICE 33/8. While stocks last.

Obtainable only from:—

GEE BROS. (RADIO) LTD., Dept. P.W.7
15 LITTLE NEWPORT ST., LONDON W.C.2.
GER 6794/1453



5in. Std.	600ft.	8/6
7in. Std.	1,200ft.	12/6
5in. L.P.	900ft.	10/-
5½in. L.P.	1,200ft.	12/6
7in. L.P.	1,800ft.	15/-
4in. D.P.	600ft.	12/6
5in. D.P.	1,200ft.	15/-
5½in. D.P.	1,800ft.	22/6
7in. D.P.	2,400ft.	25/-

AMERICAN "CBS" TAPE

5in. Std.	600ft. (CIP-6)	13/-
5½in. Std.	900ft. (CIP-9)	16/-
7in. Std.	1,200ft. (CIP-12)	21/-
5in. L.P.	900ft. (LP-9)	16/-
5½in. L.P.	1,200ft. (LP-12)	19/6
7in. L.P.	1,800ft. (LP-18)	28/6
5in. D.P.	1,200ft. (CMXP-12)	32/-
5½in. D.P.	1,800ft. (CMXP-18)	37/-
7in. D.P.	2,400ft. (CMXP-24)	47/-

SPARE SPOOLS. 4in., 5in., 5½in., 2/- each; 7in. 2/6; 8in. 5/-.

P. & P. 2/- per order (over £3 post free). Other types available. S.A.E. for list.



AMATEUR RADIO SOCIETY OF CHESHAM AND DISTRICT

Hon. Sec.: Capt. C. G. Stephenson, G3CLJ/T, 21 Lynton Road, Chesham, Buckinghamshire.

As the stresses of pre-examination studying and training subside, more spare time should be available for members to concentrate on Society business, such as work on the club premises, which remains pressing.

A general discussion open to all members is held at the radio station, Bois Moor Road, on the last Sunday of each month.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

The meeting for May 8th saw the first of a series of three lectures on the subject of "Safety in the Shack and Home". At this meeting and at the meetings of 15th and 22nd May, members heard authoritative talks on first aid, electrical safety, fire prevention, etc.

The second d.f. practice run was held on May 29th, and as usual, the first meeting in the new month was a sale, held on June 5th.

FLINTSHIRE RADIO SOCIETY

Hon. Sec.: Alan Antley, Fairholme, Fairfield Avenue, Rhyl, Flintshire.

The meeting for May was held on the 27th. This meeting began with a half-hour session of slow morse practice, which was followed by GW3PCZ/T continuing his series of lectures, "Simple Hints and Kinks".

The last item on the evening's programme was a talk by W. Davies (GW3PKH/T) called "Using Relays".

LICHFIELD AMATEUR RADIO SOCIETY

Hon. Sec.: V. Hickman, G3LXR, 143 Main Street, Stonnall, near Walsall, Staffordshire.

At the meeting on May 6th, members heard the latest talk in the series on "Transistor Application", being given by John Beaman and Brian Hood.

LOTHIANS RADIO SOCIETY

Hon. Sec.: W. T. Sutherland, GM3JWS, 47 Great King Street, Edinburgh 3.

On May 9th "Railway Communications" was the subject of the lecture given by Ron McInnes. Members who attended the only other meeting in May, on the 23rd, listened to their field day briefing, in preparation for NFD.

MITCHAM AND DISTRICT RADIO SOCIETY

Hon. Sec.: A. L. Thurlay, 50 Bruce Road, Mitcham, Surrey.

May 24th proved an enjoyable meeting for all those who attended, as the evening's entertainment was supplied by the showing of the award winning film, "This is the BBC".

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

On May 22nd members enjoyed an evening's ragchew. The meeting of June 5th was "Any Questions Night" and on the following day members visited the Emley Moor television station.

READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

The first of this year's "mobile picnics", which have become so popular with members, was held on Whit Sunday, June 2nd. This picnic was held at the Childe Beale Memorial Trust, Lower Basildon.

SHEFFIELD AMATEUR RADIO CLUB

Hon. Sec.: D. A. Justice, G3PYL, 9 Leslie Road, Sheffield 6.

This Club was reconstituted last year and now holds regular meetings in its own clubroom. The second Friday of each month is devoted to a technical meeting and the fourth Friday is always a general meeting.

On May 10th, "Hints and Kinks" was the subject of a discussion. New members are always welcome and anyone interested in joining the Club should contact the secretary.

SLADE RADIO SOCIETY

Hon. Sec.: D. D. S. Williams, 117 The Boulevard, Wyde Green, Sutton Coldfield, Warwickshire.

On May 3rd, Mr. B. W. Smith gave a lecture on "Amateur Television" in collaboration with J. E. Smith. A demonstration accompanied the lecture, which was well received by all those present.

On May 17th an evening d.f. test was held, and on the 31st, Mr. T. P. Douglas gave a talk entitled "Welsh Safari with Radio".

Just in case you've forgotten—NATIONAL FIELD DAY: JUNE 8th and 9th.

R.S.G.B. Contests for June. 70Mc/s Contest (June 15th and 16th), 1250 Mc/s Tests (June 23rd) and D/F Qualifying Event (July 30th).

AMATEUR AMBASSADOR

CRITICS of amateur radio often care to observe that the hobby as a whole, and in particular licensed amateurs communicating over the air, serves no useful purpose for the community whose administrative bodies in the first place, sanction their use of the ether. This is an accusation that any enthusiast would, quite rightly, hotly deny the moment it was made, but it might be as well to have prepared retaliatory proof of the hobby's usefulness to hand, as the rantings of an enraged amateur might not, perhaps, be the best way of establishing the truth.

To begin with, it must be conceded that the days of the amateur experimenter treading undiscovered ground in the realms of electronics, ended many years ago, and now industry alone is capable of accumulating new data. Therefore anyone defending the position of the radio enthusiast should not pursue the subject of the advancement of science so much as the spread of radio knowledge, which the Clubs achieve so effectively by the contact between inexperienced beginners and their more learned elders. But all members of radio societies are already fully aware of this educational value of a club.

There is, however, one aspect of the hobby which is never given publicity and one which, quite probably, has never occurred to some. It concerns specifically the licensed operator who may at any time be in contact with amateurs in any country of the world. Every contact made outside these islands must leave an impression on the person contacted. However, this impression will not be confined to forming a mental picture of the British ham he may never meet, but will, in fact, contribute to impressing upon the mind of that foreign amateur, an image of the UK. Thus the manner in which the operator conducts his communications will, in a small way, help to make or mar the image of Great Britain abroad. Every amateur is, therefore, an ambassador for the nation. This is an important responsibility.

It is a responsibility which, if left to just anyone, would no doubt be taken very lightly, to the detriment of the people of the UK. After studying for many months to pass the R.A.E. and morse examinations, a person acquires this sense of responsibility, which is so necessary before communicating freely with other countries.

Yet another good reason why licences should not be there for the asking!

CONTINUED ON PAGE 274

BOOKS REVIEWED

MORE ABOUT LOUDSPEAKERS

By G. A. Briggs; published by Wharfedale Wireless Works Ltd., Idle, Bradford, Yorks.
136 pages, 5½ in. x 8½ in. Price 8s. 6d.

THOSE who are already familiar with the works of Mr. Briggs will know what to expect from this volume, which is a follow-up to his already well-known *Loudspeakers*. It is, in fact, a gathering together of facts and figures (and comment) relating to developments since the 5th edition of *Loudspeakers* (1958).

To the uninitiated it should be explained that Mr. Briggs has a unique style of writing which is completely unconventional. He gives as his excuse for writing the fact that he is a music lover, but his lighthearted prose is backed by numerous laboratory experiments.

His approach is essentially one of comment and the presentation of tests in an easy-to-read manner. Although at times the text is more or less "thinking aloud", there is a host of information of value to all audiophiles—technical or non-technical.

As the author says, this is not a text book and indeed contains much practical information of the type seldom found in the more ponderous volumes.

A must for all interested in sound reproduction.—*W.N.S.*

R.S.G.B. AMATEUR RADIO CALL BOOK

Published by the Radio Society of Great Britain, New Ruskin House, Little Russell Street, London, W.C.1.
80 pages, 7½ in. x 9½ in. Price 4s. 6d.

READERS active either as transmitting amateurs or short wave listeners will know that the R.S.G.B. Call Book lists, in call sign sequence, the names and addresses of all amateur stations in England, Scotland, Wales, Northern Ireland, Channel Islands, Isle of Man, and Eire.

The 1963 edition records 560 new call signs and incorporates nearly 1,000 changes of address. It also includes, for the first time, a list of stations to whom an Amateur (Sound Mobile) Licence has been issued.

Also included is a list of societies and clubs affiliated to the R.S.G.B., a list of amateur radio call sign prefixes (by prefix and by country order) and a list of amateur abbreviations.

Anyone actively interested in amateur radio transmitting or receiving will find this publication of great value.—*D.C.*

MAGNETIC PICKUP

—continued from page 235—

some pre-amplification is necessary. Fig. 3 shows a suitable transistor pre-amplifier which can be easily and cheaply constructed.

The input stage employs the grounded base configuration, giving low input impedance, eliminating the necessity for a matching trans-

ample for loading a gram amplifier. For many such amplifiers the first two stages alone should provide enough gain.

The performance of the pick-up compares favourably with many commercial models. If desired it may be encased in wood or coloured Perspex to give a neater appearance. ■

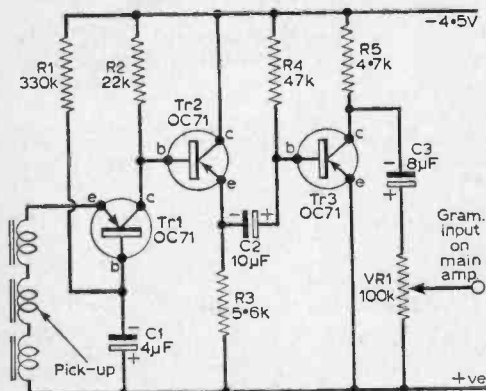


Fig. 3: Circuit of the pre-amplifier.

former. This is followed by an emitter follower and an earthed emitter stage giving a reasonably high output impedance, suitable for feeding a valve amplifier.

The output of the pre-amplifier exceeds 600mV.

CLUB NEWS—continued

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: L. A. Metcalfe, 1a Moorlands Road, Birkenshaw, Bradford, Yorkshire.

The problems of conversion to a 625-line television standard was the subject of a talk given to members on May 2nd, and on May 16th "Guided Missiles" was the title of M. A. Browne's lecture.

STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. A. G. MacIntosh, 50 Field Lane, Oldswinford, Stourbridge, Worcestershire.

Members who attended the meeting for May 7th heard a recorded lecture on "Semiconductors." Later in the month, on May 28th, details and plans of the Society's NFD effort were discussed.

WIRRAL AMATEUR RADIO SOCIETY

Hon. Sec.: A. Seed, G3FOO, 31 Wither Avenue, Bebington, Wirral, Cheshire.

May proved a busy month for this Society, starting with a junk sale on the 1st. On May 15th, Mr. Roberts (G3EGX) gave a lecture entitled "Radio Masts Follow-up", and on the 22nd NFD organisation was discussed. A d.f. contest on May 26th rounded off the month's events.

R.S.G.B. GOLDEN JUBILEE MOBILE RALLY

United States Air Force Base, Wethersfield, near Braintree, Essex.

A very full programme provided a wide variety of entertainment for visitors to this rally which was held on June 2nd. Apart from the usual exhibitions and competitions, displays of fire fighting and aircraft, film shows, go-kart racing and much more was included. One of the highlights of the day was the performance of the resident U.S.A.F. band.


PRC COMMUNICATION RECEIVERS

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of I.F., using 6 British I.O. type valves. Large 180 degrees illuminated and calibrated Dial. Flywheel Tuning with locking device. Aerial Trimmer, Tone and Vol. Controls. Band Switch from panel jacks for speaker or phones. In black metal case, size 17 in. L x 8 in. H x 10 in. D. Model PCR covers 6-18 Mc/a. 200-530 metres and 850-2,000 metres and has internal 5-in. speaker. £8.19.6. Model PCE2 has similar L & M waveband coverage. Short wave 6-22 Mc/a, but no speaker, £5.19.6. Model PCR3, as PCR2 but has 2 short wave bands 2-7 and 7-23 Mc/a, and medium wave band 190-350 metres. ONLY 8 gas. Add 10/4 carr. all models. Designed to operate from bulky EXTERNAL power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200-250 v. A.C. at extra cost of £2.

All receivers used but excellent condition and aerial tested before dispatch.


S.A.E. FOR ILLUSTRATED LEAFLET

TEST METERS FOR EVERY PURPOSE & POCKET

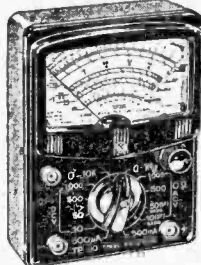


2,000 O.P.V. MODEL TP-10. Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 in. x 5 1/2 in.

£3.19.6.

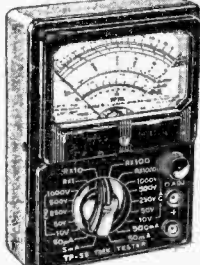

20,000 O.P.V. MODEL TP-55. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in.

£5.19.6.

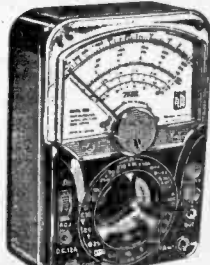

30,000 O.P.V. MODEL 500. Volts to 1,000; D.C. at 30,000 O.P.V. A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +56 Dbs; Internal buzzer short circuit warning. Size 3 1/2 in. x 5 1/2 in. x 2 1/2 in.

£8.19.6.

All New Stock, with leads, prods and internal batteries. 6 months' guarantee backed by full service facilities. Details S.A.E. Leather Case for Models TP-10 & TP-55 25/- each, for Model 500 30/-.

DOUBLE BEAM OSCILLOSCOPE TUBES, TYPE CV-1596. Equivalent to COSSOR 09D (as used in Oscilloscopes by Cossor 339 series) and Hartley & Erskine (13 series). Listed £12. BRAND NEW IN MAKER'S CRATES. ONLY 25/- (carriage 5/-).

LAVOIE UHF WAVEMETER MODEL 105. Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable. size 11 x 8 x 7 1/2 in. ONLY £3.19.6 (carriage 7/6).

HRO SENIOR TABLE MODEL RECEIVERS. Complete with 9 coil sets covering 50 Kc/s to 30 Mc/s. Used, very good condition. aerial tested. **LATE Model 5T** with I.O. valves. £22.10.0. plus carriage 30/-.

RC221 FREQUENCY METERS. The famous American crystal controlled frequency measuring standard. Coverage 125 Kc/s - 20 Mc/s. With original Calibration Book. Perfect order. Only £16. **COSSOR TYPE 1035 OSCILLOSCOPES.** A few only of these modern Double Beam scopes, thoroughly overhauled and in perfect order. ONLY £45. Further details on request.

AMERICAN DESK TELEPHONES, complete with handset. Non dial type, but has internal bell. Ideal for extension or intercom. BRAND NEW. ONLY 30/- (Postage 4/-).

ACOS 39/1 STICK MIKE with screened lead and table stand. ONLY 39/6. (Postage 1/6).

CRYSTAL DESK MIKE with screened lead and built-in stand. ONLY 10/6. (Postage 1/6).


MINIATURE MOTORS. Ideal for models. Operates on 3-6 volts D.C. Size 1 1/2 x 1 x 1 1/8 in. plus 1/4 in. spindle. BRAND NEW 5/- or 6 for 25/-.

20/- CONSTRUCTOR'S PARCEL. Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. ALL NEW (Post 2/6).

RESISTORS. 100 assorted values our choice. NEW 10/-.

CONDENSERS. 100 assorted mica and silvermica. NEW 12/6.

"P.W." 6 TRANSISTOR PERSONAL RECEIVER

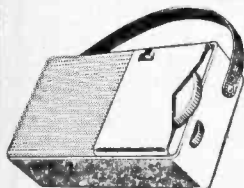

Designed by the technical staff of Practical Wireless, easy to build, using printed circuit and 1st Grade Matched Transistors and Diode. Full Medium and Long Wave coverage to internal speakers. All parts sold separately (new components only) enabling you to buy as required and full detailed price list will be sent on request. Constructional details 1/6.

Newly designed OSMOR Cabinet and reduced price. **TOTAL COST INCLUDING BATTERY AND CABINET NOW £7.19.6.** "P.W. CELESTE" Parts List. S.A.E.

THE "GOOD COMPANION" Mk. II

USING TRANSFILTERS, THE LATEST MANUFACTURING TECHNIQUE TO SAVE ALIGNMENT DIFFICULTY

THE FINEST COMBINED PORTABLE AND CAR RADIO YET DESIGNED FOR THE HOME CONSTRUCTOR

★ 750 mW output.

★ 6 transistors and diode.

★ Full Medium and Long Wave coverage.

★ Quality speaker.

★ Brilliantly styled 2-tone cabinet, size 11 x 8 x 3 in.

★ Very fine tuning with calibrated dial.

★ Latest printed circuit. ★ Internal high gain aerial with car aerial socket. Easy to follow construction data (available separately 3/6). All parts sold separately and fully illustrated details will be sent on request.

£9.19.6


Total Cost

With alternative luxury cabinet using 7 x 4 in. speaker, £10.19.6. Either type, plus 5/- post and ins. (Battery 3/6 extra).

"POCKET 4"

TRANSISTOR RECEIVER

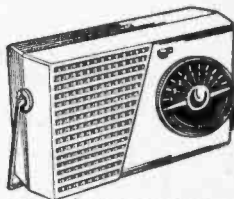Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (p. & p. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.



HARRIS ELECTRONICS
(LONDON) LTD

138 Gray's Inn Road, London W.C.1
Phone TERminus 7937

Please include carriage costs on all items.
(Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn
(Chancery Lane Station) and 5 mins. by Bus from King's Cross.

TRANSFORMERS

Auto types—60 watt 15/6 ea., 150 watt 21/9 ea., 500 watt 52/6 ea. 3 way mounting type, primary 200/250 volts, secondary 30 volts at 2 amps, with cappings in steps of three up to the maximum 30, 21/9 ea. Mains Standard Primary, 250-0-250 volts, 80mA., 6.3 at 4 amps, 5 volts at 2 amps., both tapped 4 volts, 21/9 ea. As above with 350-0-350 volts, 21/9 each.



PRACTICAL WIRELESS POCKET TRANSISTOR 6 SUPERHET on printed circuit board, all components available from stock, £7.19.6

P.W. MERCURY SIX, M. & L.W. 6 TRANSISTOR SUPERHET, 500 mw output in the new elegantly designed cabinet, printed circuit has a High Q internal ferrite aerial. All parts available from stock, £10.7.6.

GRAMOPHONE UNITS

BSR TU12 unit, with Mono TC8H cartridge, £3.19.6. BSR GU7 unit, with TC8M or TC8H cartridge, Mono, £4.15.0. BSR GU7 unit, with TC8S cartridge, stereo, £5.5.0. Garrard Autolism, automatic, with GC8 Mono cartridge, £7.15.0. Garrard Autolism, automatic, with EV26 Stereo cartridge, £8.10.0. Garrard Autolism, de luxe, with GC8 Mono cartridge, £11.5.0. Garrard Autolism, de luxe, with EV26 Stereo cartridge, £12.0.0. BSR Monarch UA14, with TC8 Mono cartridge, £6.6.0. BSR Monarch UA14, with TC8S Stereo cartridge, £7.7.0. BSR Monarch UA16, with TC8 Mono cartridge, £6.19.6. BSR Monarch UA16, with TC8S Stereo cartridge, £7.19.6.

WB STENTORIAN HI-FIDELITY LOUDSPEAKERS with Universal Speech Coil, for 3, 7.5 and 15 ohms. Model HF812 £3.12.9. HF816 £6.0.0. HF912 £3.17.0. HF1012 £4.7.6. HF1016 £7.0.0. All have die-cast chassis.

CHASSIS

Aluminium Undrilled with Reinforced Corner, available in the following sizes:

6in. x 4in. x 2 1/2in.	...	4/6 each
8in. x 6in. x 2 1/2in.	...	6/3 each
10in. x 7in. x 2 1/2in.	...	7/3 each
12in. x 3in. x 2 1/2in.	...	5/9 each
12in. x 5in. x 2 1/2in.	...	6/9 each
12in. x 8in. x 2 1/2in.	...	8/6 each
14in. x 3in. x 2 1/2in.	...	8/6 each
14in. x 9in. x 2 1/2in.	...	12/- each
16in. x 6in. x 2 1/2in.	...	9/3 each
16in. x 10in. x 2 1/2in.	...	14/- each

All are four-sided—ideal for radio receivers amplifiers—power packs, etc.

TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fee and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

TRANSISTOR AMPLIFIER

1/2 watt, 3 transistor amplifier ready built, output to 3 ohms speaker, push-pull output stage, 9 volt operation, ideal for intercom. or as record player amplifier, 39/6, plus 1/6 P.P.

1963 COMPONENTS CATALOGUE AVAILABLE. 48 pages of valves and accessories. Send 1/- in stamps for your copy.

TRANSISTORS AND DIODES

Transistors	2-OC72 16/-	18/-perpair
AC107 14/6	OC74 8/-	Matched Pns.
AD140 25/-	OC78 8/-	2xOC72 16/-
AF102 27/6	OC81 6/-	2xOC78 16/-
AF114 11/-	OC8M 8/-	Germanium
AF115 10/6	OC82 10/-	Diodes
AF116 10/-	OC83 6/-	BY100 13/-
AF117 9/6	OC170 9/6	OA70 3/-
AF118 20/-	OC171 10/6	OA79 3/-
AF124 10/-	OC91 25/-	2-OA79 6/-
AF125 10/6	TK1000C	OA81 2/6
AF126 10/-	Mixer 9/3	OA90 3/-
AF127 9/6	TK1000C	OA91 3/-
OC16 W35/-	IF & IF2	OA95 3/6
OC19 25/-	18/-perpair	OA210 9/6
OC26 25/-	TK1001C	GEX34 4/-
OC44 6/-	DR 8/-	GEX35 4/-
OC44M 9/3	TK1001C	GEX36 10/-
OC45 6/-	OP	Sundry Types
OC45M 9/-	16/-perpair	PXA102 4/-
OC70 6/6	TK1002C	Red Spot 3/6
OC71 5/-	DR 9/3	White
OC72 8/-	TK1002COP	Spot 5/-

A set of Transistors comprising 1 OC44, 2 OC45, 1 OC81D, 2 OC81, 37/6 set
SET OF AUDIO TRANSISTORS
1 x OC81 Driver; 2 x OC81 Matched pair, 15/6.

ALPHA RADIO SUPPLY CO., 103 Leeds Terrace, Wintoun Street, LEEDS 7

RADIO BOOKS

BASIC ELECTRICITY ELECTRONICS

In Simple straight-forward words and Clear Explanatory Pictures. The Reader is taken Step by Step from picture to picture.

LEARN WHILE YOU PAY FOR ONLY 2/8 PER WEEK
Officially used by the ARMY, NAVY and AIR FORCE, used by Trainees in the Radio and Electronic Industry.

Write for **FREE Illustrated Prospectus** giving details of instalment plans!
HOW TO RECEIVE Foreign T.V. programmes on your T.V. set by simple modifications 5/6

22 TESTED Circuits using Mono Alloy Transistors 5/6
BRITISH Transistor Directory (Bradley) 9/-

OSCILSCOPE Book 7/6
USING an Oscilloscope 5/6

OSCILSCOPE Equipment 5/6
MULLARD Transistor Radios 5/6

MULLARD Ref. Transistor Circuits 13/6
EXTRA Equipment Tape Recorder 6/6

COIL Design and Construction 5/6
TRANSISTOR Superhet 8/-

TRANSISTOR Audio Amplifiers 6/6
TRANSISTOR Circuits for Radio Control of Models 8/-

RADIO Servicing Instruments 5/6
HIGH Fidelity Speaker Enclosures 5/6

BOY'S Book of Crystal Sets 3/-
SERVICING Transistor Receivers 8/-

ELECTRONIC Novelties 5/6
ELECTRONIC Gadgets 5/-

RADIO Valve Det. "Wireless World" 8/6
BEGINNERS' Guide to Radio 8/6

MODERN Transistor Circuits for Beginners 8/-
TRANSISTOR Test Equipment 4/-

MAGNETIC Recording 5/6
Wire and Tape 5/6

RADIO Engineers' Pocket Book 11/6
TRANSISTOR Circuits for the Constructor (Bradley) Nos. 1, 2, 3 and 4 4/- each

All above books include postage. SEND STAMP FOR LISTS

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY KENT. Tel. HURSTWAY 1818

FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

--- FREE GUIDE ---

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the Radio industry. N.I.E. provides first-rate postal courses for **Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C & G. Telecoms., Grad. Brit. I.R.E.** Guide also gives details of range of diploma courses in **Radio/TV Servicing, Electronics** and other branches of engineering, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148 HOLBORN LONDON, E.C.1

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 25/6.	
DAF96, DF96, DK96, DL96, SET of 4, 25/6.	
OA2 5/-	DL33 7/3
1D5 6/6	DL35 7/3
1R5 5/3	DL92 4/9
1S5 4/3	DL94 6/3
1T4 2/11	DL96 6/9
3S4 4/9	EB81 3/-
3V4 6/3	EB84 7/6
5Y3GT 5/6	EBF80 7/3
5Z4G 8/-	EBL21 9/-
6K7G 1/9	ECC40 4/6
6K8G 4/6	ECC81 4/6
6Q4G 5/6	ECC82 4/6
6V6G 4/-	ECC83 5/9
6X5GT 5/6	ECC84 6/9
12K7GT 4/3	ECC85 7/3
12K8GT 9/-	ECC86 6/9
12K7GT 4/6	ECH42 7/9
128N7GT 5/6	ECL80 6/3
1457 14/-	EF41 7/6
35L5GT 7/9	EF80 4/3
55Z4GT 5/-	EF81 4/3
5847 6/6	EF86 6/9
AC/TP 21/-	EF89 5/9
CL33 8/6	EF91 2/9
DAC32 8/9	EL41 7/6
DAF91 4/3	EL94 6/6
DAF96 6/9	EY51 6/9
DF33 8/6	EY86 6/3
DF91 2/11	EZ40 5/9
DF96 6/9	EZ80 5/9
DH7 5/-	EZ81 5/-
DK32 9/-	KTW81 5/3
DK91 5/3	MU14 5/6
DK92 6/11	PC84 6/3
DK96 6/9	PC89 7/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. — Any C.O.D. Parcel 4/3 extra.

Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD, STOKES NEWINGTON, LONDON N.16



LETTERS TO THE EDITOR

INSTANT AMATEURS

SIR,—Your notes on the Club News page of the May issue, "Instant Amateurs" was enlightening in that it reported an apparently constant request from those wishing to get things the easy way—which seems to be the trend these days.

There would indeed be a muddle if licences were freely granted, and surely any worthwhile hobby warrants a little study? I simply cannot understand how anybody would wish to indulge in a hobby without knowing something about the why's and wherefore's of it.—**THOMAS C. DANDS** (Northwich, Cheshire).

MORE ON THE LANGUAGE BARRIER

SIR,—I must agree with Mr. A. Jameson (March Letters to the Editor). Mr. Collister (May issue) admits that foreign amateurs speak English "almost fluently"; "almost" being the operative word. I know from personal experience that it is much easier to understand and to be understood by foreigners using Esperanto than using broken English. Moreover, Esperanto is a neutral language, involving no question of national prestige.

I am sure that in the sphere of wireless communication, Esperanto would be an untold boon.—**R. M. DHENAU** (Sheringham, Norfolk).

SIR,—With reference to recent letters concerning the use of Esperanto, it might be interesting to consider what these two instruments of international communication (radio and Esperanto) have in common. Both, it may be said, are artificial, neutral and international, being scientific adaptations of more "natural" methods of communication, and both are potentially important factors in abolishing insularity and paving the way to international understanding.

The apt motto of the BBC could well become a reality if language were to function as a vehicle, not as an obstacle, of comprehension: it would certainly come nearer being realised if the merits of Esperanto were given more serious consideration.—**E. R. HOLT** (Billericay, Essex).

SIR,—In reply to Mr. Jameson's letter in your March issue, I have always thought part of the enjoyment of making a contact, is the language barrier. I personally have had very interesting Q.S.O.'s with foreign radio amateurs, sometimes taking up to half-an-hour to get his Q.T.H. and name, and I have always felt highly satisfied having done so.

I would suggest that Mr. Jameson finds some other more rewarding hobby: radio amateurs are governed by enough rules and regulations as it is.—**PHILIP G. JUPP** (Nairobi, Kenya).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

CALCULATOR APPRECIATION

SIR,—Thank you so much for the "Parallel Resistor and Series Capacitor Calculator" (April issue of P.W.).

It is appreciated very much, and will be a very handy tool on our work bench.—**HENRY WAGNER** (East Chicago, Indiana, U.S.A.).

A SATISFIED CUSTOMER

SIR,—As a reader of P.W. for a number of years, I have built many of the circuits that have been printed. A few months ago, I built Mr. J. Haskell's Main Amplifier which was published in the September 1962 issue. Being very much an amateur, I ran into a few snags when constructing the amplifier. I wrote to Mr. Haskell for advice, and he very kindly gave me all the help I needed.

I hope you will publish this letter, as I would like Mr. Haskell to know how greatly I appreciated his assistance.—**DEL GILLAM** (Johannesburg, South Africa).

PUBLICATIONS WANTED

SIR,—I would be pleased if some reader would be kind enough to lend or sell me the May and June 1955 editions of P.W., which deal with the construction of a radio telescope.—**G. W. JONES**, Ael-y-Bryn, Bontddu, Dolgellau, Merionethshire.

SIR,—I should like to know of any reader who would sell me a copy of June 1961 P.W. I need this issue for the article on the pre-amplifier.—**P. LEADER**, 117 Roundmoor Drive, Cheshunt, Hertfordshire.

SIR,—I would be most grateful if any P.W. readers, who might be able to lend or sell me the following issues, would contact me: January, February and March, 1962; April, May, November, 1961.—**I. GREEN**, 182 St. John's Road, Woking, Surrey.

SIR,—I wonder if any of your readers would sell or loan me the circuit and wiring details of an ex-U.S. Army BC 348-K receiver?—**J. S. MCARRAGLER**, 199 Evington Lane, Evington, Leicestershire.

PRACTICAL WIRELESS CIRCUITS

By F. J. CAMM
17th Edition
from 17/6 by post 18/7
GEORGE NEWNES, LTD.,
Tower House, Southampton Street, London W.C.2.

RECEIVERS & COMPONENTS

EXCEPTIONAL VALUE: Picture Tubes, brand new, Mazda 1912, CME1901, Mullard 191n, AW47-90/91, £4/10/-; Mullard 231n, AW59/90, £6/10/-; carriage (insured) paid, 12 months' guarantee. Note: All brand new. We also supply most other sizes completely regunned at £17/16, guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross SE14. TID 3857.

Glasgow Electronic Services

21 OLD DUMBARTON ROAD, GLASGOW, G3
Telephone WEST 2642

"FOR THE COMMUNICATIONS RECEIVER MAN"

GANG TUNING CAPACITORS: 2, 3 or 4 gang, max. capacity 310 or 487pF ceramic insulated condensers, 14/9, 19/3 and 28/3 respectively, either capacity. **BANDSPREAD TUNING CAPACITORS:** 2, 3 or 4 gang; 2 gang available 10 or 27pF max. at 11/3, 3 gang 15pF max. at 19/3, 4 gang 15pF at 27/6. **"WAVEMASTER"** S.W. VARIABLES: A range of single, ceramic insulated, brass vane, tuning capacitors. Can be ganged to form a low loss tuning or bandspread condenser. Available 15pF at 4/3, 25pF at 4/6, 40pF at 4/9, 50pF at 5/-, 60pF at 5/3, 75pF at 5/6, 100pF at 5/9, 100pF at 8/-, 200pF at 7/6. **B.F.O. TRANSFORMERS:** 85 kc/s, 465 kc/s 1.6 Mc/s nominal frequencies. Miniature size at 5/- each. **DENCO IF TRANSFORMERS:** 465 kc/s, 1.6 Mc/s or 10.7 Mc/s nominal frequency, litz wound, permeability tuned, highly efficient transformers, min. size 6/6 each. **DOUBLE SUPERHET TRANSFORMERS:** Narrow band 85 kc/s or 100 kc/s transformers. Iron dust tuning, 16/- each. **TUNING COILS:** Full range of Denco Maxi-Q coils covering from 150 kc/s to 78 Mc/s. Mixer IF, Osc., plug-in or chassis mounting from 4/- each. Full technical information, circuits, etc., in Bulletin DTR4, 2/- post paid. **SCREENED VALVE-HOLDERS:** Low loss B7G or B9A screened valveholders, ideal for SW construction, 1/10 each.

Plus, of course, our large range of accessories for receiver construction—R.F. Chokes, Chassis, tagboards, group panels, S.W. Transistor coils, capacitors of all types, etc., etc. Send for our latest list, 6d. post free.

Terms of business: Cash with Order: C.O.D. 3/- extra. Postage extra under £3 total value.

DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone TIDeway 6666, 138 Lewisham Way, SE14.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. P.W.7/9, 136 Lewisham Way, SE14. TIDeway 6666.


ALL TYPES LINE OUTPUT TRANSFORMERS SUPPLIED (RETAIL AND TRADE). Finest service in the country. Send S.A.E. for return of post service. Terms C.W.O. or C.O.D. Trade enquiries invited. **D. AND B. TELEVISION (WIMBLEDON) LTD.**, 131 Kingston Road, Wimbeldon, SW19. CHerrywood 3955.

SPEAKER REPAIRS. Cones/Fields fitted. Clock coils wound. L.S. REPAIRS, Pluckley, Ashford, Kent.

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to: Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS (continued)

ULTRA LINEAR AMPLIFIERS

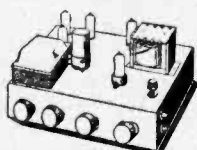

High Fidelity. 15 watts. Valves ECC83, EL84, EL84, E281. Two inputs. Sensitivity 10 millivolts. Treble controls, 3 & 15 ohms output. Kit, £6.10.0, plus 5/-.

Similar 30 watt with 7 valves. Kit £9.10.0, plus 7/6 carr. Factory built, £12, plus 7/6 carr. Leaflet free.

COMPONENT BARGAINS. Transistors. genuine Mullard OC45, OC71, OC77, 3/9. S/H Speakers, 7 x 4in. 6in., 4/-, post 2/- or post up to 8 for 4/- Turret tuners, for 16 Mc/s I.F. with plugs to convert BBC sets to I.T.A. any two coil strips fitted from channels 2, 3, 5, 9, 10, 11, 12, 7/8, post 2/-. **Electrolytics.** 25/25v. 9d., 50+50+32/350v. 2/6, 40+80+20/450v. 3/-. **Resistors** 3/- doz. Bargain lists free.

STROUD AUDIO

Bath Road, Stroud, Glos.
Tel. Stroud 783.

A.1. POST FREE BARGAINS. Guaranteed set tested Valves: EB91, EF80, 10F1. 9d. each. three for 1/6; L63 2/3; ECL80 2/6, three for 1/6; PZ30 3/6; EL38, PL33, PY81 3/6; PL2, PL3, PY30, PY82, PCF80 4/-; N37, 275U, 20P1, PY3, KT36, U91, U281, U282 4/6; ECC81, ECC82 4/9; PL81, U31, 10C2, 10P13, 20L1 5/-, EL33, PL36, U07, 30P4, 53KU 7/6; 20P3 14/6. Transistors: brand new. B.V.A. types: OC70, OC71 5/-; OC72 6/-; OC44 1/6; OC45 7/-; OC170 9/-; OC171 10/-; AP14 11/-; AP115 10/6; AP116 10/-; AP117 9/6. Tuning cond., 0001 3/-; 0003 3/9; 0005 4/-; Midset type same price. All single gang dielectric. 1in. brown knobs, three for 1/-, 2.000 ohm phones 13/6 pair. Stereo phones 27/6 pair. Loudspeakers 6in. 5/-; 8in. 7/3; 7in. x 4in. 7/6; 6in. x 4in. 6/-, A.1. **RADIO COMPONENTS.** 14 The Borough, Canterbury, Kent.

RECTIFIERS

SELENIUM HALF-WAVE

RIM3 125V rms 120mA	6/6
RIM4 250V rms 250mA	12/6
RIM5 250V rms 300mA	14/6

SILICON DIODES 500mA

100 PIV	3/-	400 PIV	4/9
200 PIV	3/8	800 PIV	7/9

SILICON ZENER DIODES

Volts:	3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27.
1 Watt rating	9/- any volts
1/2 Watt rating	15/- any volts
10 Watt rating	37/6 any volts

ALL DEVICES GUARANTEED BRAND NEW — OTHER TYPES AVAILABLE.

Cash with Order—P. & P. 1/-.


ELECTROMECH

18 LUGANO CLOSE, WATERLOOVILLE HANTS.

RECEIVERS & COMPONENTS

(continued)

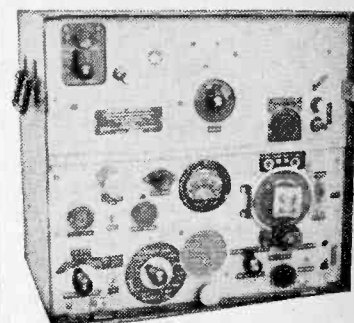MARCONI CANADIAN RECEIVER No. 52 (Brand New)



AMATEUR SHIPPING BROADCAST Magnificent 10 valve receiver in 3 wavebands covering 1.75-16Mc/s (19-170 metres), plus 3 valve crystal calibrator employing dual 100/1000kc crystal to provide marker check at 10-100-1000kc/s. 1 RF and 2 IF stages. Other refinements include valve check meter, internal 3in. speaker, RF-AM gain, Noise Limiter, BFO, Heterodyne Pitch, Wide/Narrow Bandwidth, Speaker or Phones, Man or AVC on CW and RT. Fast/Slow tuning with additional Osc. for fine adjustment. Power required: HT 160v 60mA, LT 12v. 1 1/2. Circuit supplied. **RECEIVER** (less case used) £6.19.6, carr. 15/6. Complete with Power Pack for 115/230 AC. **BRAND NEW.** Mains and 12v d.c., £12.19.6, carr. 20/-. SIZE 15" x 12" x 15". Many other surplus bargains with **PERSONAL SERVICE.** Lists 6d. S.A.E. inquiries.

A. J. THOMPSON

"EILING LODGE"
CODICOTE, HITCHIN, HERTS.
Phone: Codicote 242.

CONDENSERS. Fantastic Bargain! 500,000 Miniature Condensers. 1in. long, 1/2in. diameter. Tested 750V. Capacity .0001 to .04uf. 7/6 per 100, post free. Ideal for transistor sets. **MILWARD, 17 Peel Close, Drayton Bassett, Staffordshire.**

BARGAIN IN V.H.F. RECEIVERS

Ex-police, crystal controlled in approx. range 80 to 90 Mc/s. Built in 230v. A.C. Power Pack and 6in. Speaker. On 19in. rack panel 8 1/2in. high, dust cover. Valves 4 of KTW63, 3 of Z90 (EF50), D63, DH63, KT63, 5U4G. Suitable for modification for 4 metres, etc. Supplied in good used condition, less crystal, **ONLY £3**, carriage paid. **NO FURTHER DETAILS AVAILABLE.**

CANADIAN MARCONI 52 RECEIVERS

1.75 to 16 Mc/s, £5.10.0, or complete with 230v. A.C. power unit, two pairs headphones and spare valves, etc., £9.10.0, carriage 1/-.

Send S.A.E. for leaflet.

G.W.M. RADIO LIMITED

40/42 Portland Road, Worthing, Sussex.

HALF PRICE Transistors. Mullard OC44, OC45, OC81, OC81D, OC70, OC71. al. 4 6 each, min. 4 doz. lots: OC26, OC36 12/6 each. Post 9d. **C.W.O. RADIOMEX, 184 Kingston Road, Portsmouth.**

RECEIVERS & COMPONENTS (continued)

NEW from REPANCO Build Yourself Instructions 1/3 HIGH GAIN AMPLIFIER

for
Portable Record Player
Baby Alarm
Intercom. Unit
REPANCO Transformers used
TT52 Moving Coil Input matching.
TT53 Crystal Input matching.
TT49 Interstage. TT45 Driver.
TT46 Output.

Trade and Manufacturers'
Enquiries Invited.

REPANCO LTD. Foleshill Road, COVENTRY

CR100 60kc/s — 30Mc/s. re-aligned, guaranteed. £18/10/-. Hallicrafters SX86, as new. £15. Bendix RA1B. 150kc/s — 15Mc/s. £15. R1155N includes 1.5—3Mc/s modified o/p 250/6.3 required. £10. Command RX24V with Dyno. £4. Booster Motors, 12in. 240.v.t., 10/-. L/R Meters, new, boxed. 17/6. Transistors, OC35 15/-, Matched XC131 12/-, XA102 (OC44) 5/-. Transistor Diodes 1/-. Silicon Kees, 400V 350mA, 4/6. Twin Gang Variables, 500+150pF. 3/6. Standard O/P XFMRs 5/-. RF273 Units 30/-. Ex-TV's. Z77. EF80 1/-. ECL80, EF50 2/-. G. H. ADDISON. G3BAY. 33 Hinckley Road, Leicester.

FOR SALE

Corvair 6-Transistor Pocket Radios with all accessories, only 95/- each. Sp 1 Mains Soldering Irons, 15/- ea. T.V./F.M. Telescopic Aerials, 7/- ea. **BUMPER BARGAIN PARCELS** All Brand New. Not Ex-Gov. Contents plus many more items: 100 mixed resistors, 100 mixed condensers, volume controls, pre-set pots, tag strips, etc. This is a must, only 20/- post free.

100% Tested and Fully Guaranteed Transistors by Mullard and Mazda. All Brand New and these are not seconds.

OC44, OC45, OC81, OC81D, 3/6 each; OC170, OC171, 4/- each; ORP60, 7/- each; OC26, 12/- each; Red Spots, 1/3 each; XB103, XA102, 2/3 each; XC141, 6/6 each; XD210 Sub. Min. Diodes, 9d. each, 6/- doz.

S.A.E. FOR FREE BARGAIN LISTS

B. W. CURSONS
78 BROAD STREET
CANTERBURY, KENT

FOR SALE (continued)

HEATHKIT MOHICAN. GCIU receiver, working £30 o.n.o. Tel.: MOU 1862.

ETCHING PRINTED CIRCUIT KIT

Consists of Plastic Bath and Case. Size 9 x 5 x 2 in. Contents: Solvent, Etchant, Resist, 100 sq. in. Copper Laminate Board. Comprehensive book gives examples and circuit layouts. 18/6 inc. post.

RADIOCENTRE
94 Hurst Street, Birmingham. Dept. P

EXCEPTIONAL Transistor Portable Tape Recorder, value £26/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes 100ft 4/6). Ideal gift. £26/19/6. Satisfaction guaranteed. Postage, packing 2/6. TOMLINS, 156 Lewisham Way, New Cross, SE14.

A GENUINE RADIO BARGAIN!
"AIMOR" FAIR EASTERN DESIGN Brand New 6-valve Superhet Mains Portable Radio, MW/broadcast band. A.C. Mains. 100/250 volts. Valve line-up: 12BE6, 12BA6, 12AW6, 50C5, 35W4. Size 8 1/4 x 4 1/4 in. Weight 3 lbs. Colours Blue, Black, White. £5. postage paid.

MAZEL RADIO
122/138 London Rd., Manchester 1, Lancs. Cash with order and/or send S.A.E. for for latest list of goods for disposal.

AMATEUR LICENCE Morse Course. The new Rhythm Method of teaching takes the drudgery out of learning Morse and is the quickest known! For full explanatory booklet, 6d. stamp G3CHS, 45 Green Lane, Purley, Surrey.

E. R. NICHOLLS No. 1 BUMPER PARCEL

- 100 Assorted Resistors.
- 50 Assorted Condensers.
- 1 5in. 3 ohm Elac Speaker.
- 1 Isolating Transformer.
- 4 Terminal Blocks.
- 2 Rotary Toggle Switches.
- 1 Small Chassis containing 60 components.
- 2 Westectors.
- 2 Thermistors.
- 100 Cartridge Fuses.

No. 2 BUMPER PARCEL

- 1 Pair Test Prods, retractable with leads and spades.
- 17 x 4in. 8 ohm Speaker.
- 6 Assorted Valves.
- 6 Assorted Potentiometers.
- 6 Assorted Valve Bases.
- 25-way Plugs and Sockets with leads.
- 4 Mixed Plugs or Sockets.
- 100 Cartridge Fuses.
- 1 Inductance Variometer.

All for 20/- Post Free.
Both Parcels or 2 of each, 35/-, Post Free.

20ft. Steel Telescopic Mast. 50/-.
High Stab Resistors 6d. each.
List now ready for Paper Block Condensers, Valves, Oscillators, Test Sets. S.A.E. Please.

Mail Order and Retail Shop:
46 Loughfield Road, off Shaw Heath,
Stockport, Cheshire.

FOR SALE (continued)

HOLIDAY NEWS. Electric Razor, 12V d.c./230V a.c. inverter. "The Hiker" Portable. See your dealer. REPANCO, Coventry.

WANTED

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

WANTED VALVES ONLY

Must be new and boxed
Payment by return.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

ABSOLUTE TOP PRICES paid for Valves, Transistors, Components, etc., in quantity. Try us first. Cash by return. **WOLVERHAMPTON RADIO AND TV SUPPLIES.** 42 Darlington Street, Wolverhampton. Tel: 20315.

NEW VALVES WANTED

Any type, any quantity

CASH PAID

R.S.T. Valve Mail Order Co.,
211A Streatham Road
Mitcham, Surrey
Telephone: MITCHAM 6202

WANTED: TEST GEAR. Meters, Valves, Components, Communication Sets, Amplifiers, Letters only. **HUGGETTS LTD.,** 24 Pawson's Road, West Croydon, Surrey.

WANTED: NEW Valves and Transistors, any quantity. **S. N. WILLETS,** 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1930-1962. Prices from 1/- with free fault-finding guide. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering many popular models 20/-. S.A.E. inquiries: **HAMILTON RADIO,** Western Road, St. Leonards, Sussex.

WHY TOLERATE DELAY when we can supply your Radio or TV Service Sheet by return of post at 4/- each plus postage. List 1/-. Also Manuals for sale and hire. List 1/-. S.A.E. with inquiries, please. Mail orders only to **S.P. DISTRIBUTORS,** 44 Old Bond Street, London, W1.

TRADE SERVICE SHEETS offered by retired engineer. If I haven't got it you won't get it. All 4/- each by return. Please include large S.A.E. Mail orders only. **ETIZIONI,** 80 Merlion Avenue, Stanmore, Middx.

SERVICE SHEETS

(continued)

FAULT-FINDING FILES showing common faults that each receiver is prone to and other useful servicing information 2/- each. List 9d. plus postage. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London, W1.

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries: TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London, W2. Phone: SHE 8441.

SERVICE SHEETS, Radio and TV, 4/- each. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E. please: SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

SERVICE SHEETS Radio and TV, 4/- each post free. All types. Send S.A.E. for inquiries. D. AND B. TELEVISION (WIMBLEDON) LTD., 131 Kingston Road, Wimbeldon, SW19. CHE 3955.

MISCELLANEOUS

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & N., 20 Maude Street, Darlington, Durham. Send 2d. stamp.

YOUR KIT—Amplifier, Radio, etc., professionally assembled, wired, tested. Moderate charges. Prompt attention. Write to M. JOHNSON, Ivy Cottage, Astwood Bk, Redditch.

PWPWPW Printed Wiring. Prof work. Prac Wless ccts—any design, assembly or advice. Full details 6d. Box 46.

Cases, Chassis, Frames, etc., anything in metal. Send your drawing for quotation. 'One off's' with pleasure.

Stove enamelled with professional finish. Steel Shelving, Drawer Units, etc.

Moss Watson

40 MOUNT PLEASANT STREET
OLDHAM, LANCs. MAIN 9400

SOUND RECORDINGS

TAPE BARGAINS in all sizes. Example: Top band 5min. 1.200ft 19/6. P. and P. 1/3. S.A.E. for list. Large choice of New and Used Recorders. E. C. KINGSLEY AND CO., 132 Tottenham Court Road, London, W1. EUS 6500.

SITUATIONS VACANT



**LONDON
ELECTRICITY
BOARD**

Skilled Operators

are required by the London Electricity Board at the workshops in West Ham, Hackney, Fulham and Bexleyheath. If you are skilled in small mechanism manufacture or assembly and require permanent employment under N.J.I.C. conditions, please write or telephone for details to the Meter and Test Superintendent at:

84 Romford Rd., E.15 (Tel: Maryland 6677) (West Ham & Hackney)
Argon Mews, Effie Road, S.W.6 (Tel: Fulham 0041) (Fulham)
Rear of 257 Broadway, Bexleyheath (Tel: Bexleyheath 7711)

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London W8.

PUBLIC SCHOOL leaver required as an electronic and/or electro-mechanical trainee to assist in the design and construction of industrial controls for use in the manufacture of glass fibre products. Starting salary £728. Write giving details of education and interests to Fibrelite Industries, Trafford Hall, Chester.

A.M.I. Mech. E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc. brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), 29 Wright's Lane, London W8.

TV AND RADIO. A.M.Brit. I.R.E., City and Guilds, R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London W8.

EDUCATIONAL

LEARN RADIO AND ELECTRONICS the new and practical way. Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11, P.W., RADIO-STRUCTUR, Reading.

THE Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

EDUCATIONAL

(continued)

Radio Television & Electronics

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; P.M.G.'s certs., etc. Also Practical Courses with equipment.

All books supplied.

Write for FREE prospectus stating subjects to

I.C.S.

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11.

THE MORSE CODE can be memorised in less than one hour by the Coros System, 3/9 post free. COROS, 20 St. Mary Street, Bridgwater.

£

'S MADE

By repairing Radio and TV Sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required.

**SEND FOR
FREE BOOK
TODAY!**

RADIOSTRUCTOR

Dept. G77 READING, BERKS

NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO and ELECTRONICS

EVEN QUALIFY FOR A
CERTIFICATE

It's the most exciting news of the year! Just imagine. You can get 35 large, fact-packed lessons for little more than 1/- per lesson! The lessons are crystal clear, practical easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert.

Compares favourably with some courses costing ten times as much. You save because you receive all the lessons at one time and are not required to purchase equipment you do not need.

This is a real home-study course that has been bound into one giant 8 x 11 in. 216 page manual. Each page is divided into two columns. A wide column features the text, while a narrow column at the side has the instructor's comments, helpful suggestions and additional pictures to simplify the difficult parts.

Everyone can benefit from this practical course. No old fashioned (or pseudo modern) methods used here, just straight forward, easy to understand explanations to help you make more money in electronics.

As an optional extra, you may pay a further fee if you wish to take the Sim-Tech radio and electronics examination. Students who attain a minimum of 80% correct answers can qualify for a certificate of proficiency in basic radio and electronics. Details sent with each course ordered.

You must be convinced that this is the best value you have ever seen in electronic training, otherwise you can return the manual (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven days.

The price? Only 38/-, plus postage.

FREE TRIAL OFFER!

To SIM-TECH TECHNICAL BOOKS, Dept. WA13, Gater's Mill, West End, Southampton.

RUSH Radio and Electronics Course for seven days examination. If I keep the course I can either pay 37/8d. cash or 12/6d. deposit after seven days and two payments of 12/6d. monthly. Otherwise I will return the course post-paid and owe nothing.

SAVE! Send only 38/- if paying cash with order. (We pay postage.) Same 7-day money-back guarantee.

Name _____
Address _____
City _____ County _____

COMMUNICATION RECEIVERS

CH100/SMOD. Covers 60 kc/s-30 Mc/s in 8 bands. 11 valves. 2 R.F. and 3 I.F. stages. Crystal gate, B.F.O., etc. Ready for 200/250 volt a.c. mains. 21 watts output for 30 speaker. BRAND NEW. In original packing. £35, carr. £2. S.A.E. for illustrated details.

HRO SENIOR RECEIVERS. Complete with 9 coils. £17.10.0. S.A.E. for full details.

PCR-3 RECEIVERS. 3-wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition. Tested 8 gns. Carr. 10/-. A.C. mains internal power supply £2 extra.

SILICON RECTIFIERS. Type 1EA2 (1 x 1 in.) will handle 250 volts at up to 500mA. Replaces any TV metal rectifier. 7/6.

MOVING COIL PHONES. Finest quality Canadian with Chamolux ear muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable. BRAND NEW. 22/6, post 1/6.

AVO L.C. & R. BRIDGE. Capacity 5 pfd to 50 mfd. Resistance 5Ω to 50Ω. Inductance can be measured against external standard. Balance is indicated on a meter which can be used as a valve voltmeter from 0.1 to 15 v. Leakage test and Power Factor scale. A.C. mains operation. Tested and guaranteed and in superlative condition. £9.10.0, plus 5/- P.P.

AVO WIDE RANGE SIGNAL GENERATORS. Six turret operated ranges covering 50 kc/s to 80 Mc/s. For use on standard A.C. mains. Packed in original transit cases with accessories. Post-war type in new condition. £15. Carr. 10/-. Real Bargain.

WAVEMETER W-191A. A crystal checked, self-contained heterodyne frequency meter similar to the BC-221. Covers 100 kc/s to 20 Mc/s (harmonics to 40 Mc/s). Requires 60V HT and 2V LT acc. Output signal has optional modulation for use as SSB Gen. Accuracy 0.1%. Complete with instructions, individual calibration charts, valves and 1 Mc/s crystal. In BRAND NEW condition. 79/6, carr. 5/6. Complete set of 4 spare valves. 10/- extra.

AERIAL KITS. Comprising seven 4 ft aerial rods making a 16 ft. and a 12 ft. aerial. There is also an aerial base with a ground spike. All in a steel carrying tube with web strap. 22/7, carr. 4/-.

MULTIMETER SPECIAL MODEL CT-500. 20,000Ω/V. DC volts: 0 to 2.5-10-50-250-500-5,000 (20KΩ/V). AC volts: 0 to 10-50-250-500-1,000 (10KΩ/V). DC Current: 0 to 50 μA 5mA, 50mA, 500mA. RESISTANCE: 0 to 12KΩ, 120KΩ, 1.2MΩ, 12MΩ. Mid scale 50, 600, 6K, 60K ohms. Decibels: 20 to +22. In neat moulded case 5 1/2 x 3 1/2 x 1 1/2 in. With leather carrying handle, complete with batteries, leads and instructions. BRAND NEW. Fully guaranteed. 95/- P. & P. 2/6.

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martins Lane
London, W.C.2. Temple Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday) Open all day Saturday.

4 - TRANSISTOR AMPLIFIER

- ★ 200 mW push/pull output.
- ★ Matches 32 ohm speaker.
- ★ Printed circuit construction.
- ★ Fully wired and tested.
- ★ Separate inputs for mike and pick-up or radio etc.

42/6

COMPLETE

- Extra components if required
- ★ 5 K Volume Control with switch 5/-
- ★ 2 in. Hi-flux speaker 20/-

OAKFIELD RADIO

121 Macleodfield Road, Hazel Grove,
Stockport, Cheshire
MAIL ORDER ONLY

R E P A N C O

TRANSFORMERS FOR 10 WATT TRANSISTOR AMPLIFIERS

Type TT23 Interstage Transformer

Ratio 4:1+1

Secondary Resistance 2+2 ohms

Primary Resistance

3.5 ohms

Secondary Bifilar Wound

22/6

(P.P. 1/6)

Type TT24 Output Transformer

Ratio 1.3+1.3:1+1

Secondary Resistance

0.2+0.2 ohms

Primary Resistance

0.6+0.6 ohms

22/6

(P.P. 1/6)

Primary Bifilar Wound. 15 ohm or

3.5 ohm output

Stack Size of Both Types 2 1/2" x 2 1/2" x 1/2"

Boxed Complete with 10 watt Amplifier

Circuit

RADIO EXPERIMENTAL PRODUCTS LIMITED

33 Much Park Street, Coventry
Telephone 27141

PADGETTS RADIO STORES

OLD TOWN HALL,
KNOWLER HILL,
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

COMPLETE TV SETS UNTESTED

Bush 12in. 13 channels. TV24C .. 30/-

Bush 14in. 13 channels. TV43 .. 70/-

Bush 14in. 13 channels. TV53 .. 75/-

Pye 14in. 13 channels. V14C console .. 50/-

Pye 14in. 13 channels. V14 .. 50/-

Philips 14in. 2 and 10 channels. 1446 .. 35/-

We have 17in. TV Sets with rough cabinets,

coils fitted 2 and 10, at 50/- Carriage on any

TV Set 10/- per B.R.S. Well packed but

sent at owner's risk.

Valves Removed from TV Sets. Tested

on Mullard Valve Tester and are 100% O.K.

New. Three months unconditional guar-

antee. POST FREE.

ECL80 2/- 10C2 5/- PY80 5/-

BCC82 5/- 10F1 1/- PY81 4/-

EY51 2/6 10P13 5/- PY82 5/-

EBF80 4/6 10P14 5/- PZ30 4/-

EB91 9d. 20D1 3/- PZ80 4/6

EP91 9d. 20P1 5/- PCC84 4/6

GSN7 2/9 20L1 5/- PCL85 6/-

6F1 1/- 185BT 8/6 PL83 5/-

6F13 2/- U281 5/- PL83 4/-

6F14 5/- U282 5/- R38 4/-

6F15 5/- KT36 5/- N37 5/-

6LD20 5/- PL81 5/- ZTSU 5/-

PL82 6/- PL82 5/- U12 4/-

EF80 1/6 or 10/- per doz. Grade 2 EF80 for

test purposes. 4/- doz.

New Valves 12x Units. POST FREE.

AR12 1/6, 6 for 5/6. box of 50 20/-, IT4 2/-

AR8 2/-, ARTP2 2/-, AP74 2/-, APP37 2/-

6K7 2/-, 6K8 4/-, 5U4 3/-, 6SN7 3/-, 6V6 3/-

6V6GT 4/6, VR150/30 2/6, 6C4 2/-, EL91 1/6,

EF91 1/6, EF50 1/-, 6/- doz., 6F6 2/6, 5Z4 5/6,

6X5 4/6.

P.M. Speakers. Removed from TV Sets.

All perfect condition. Rola and Plessey,

6 x 4in., 5/-; Goodman and R. and A. 7 x 4in.

8/-; Rola and R. and A. 8in. round, 3/6;

8in. Dish. round, 5/-; 8in. round, 6/-; Post

on any speaker, 2/-.

TV Tuning Picture Tested. Reclaimed

from TV Sets. 12in. 17/-; 14in. 30/-; Carr.

7/6. 6 months unconditional guarantee.

TYPE 46 SET complete with valves, less

coils, crystals, and send-receive switch, but

otherwise complete in new condition. 8/6.

Grade two 4/6. Post 3/6.

WAVE METER 10x complete with

Mullard slow motion drive. 6/6. Post 3/6.

NEW BOXED UNITS. Type 230. Complete

with 5Z4, Y63, magic eye, four EF50 and

complete A.C. 230 volt Power Pack, 25/-

Carriage 7/6.

11 P. 230 VOLT MOTORS. Removed from

washing machines. Tested. 25/- Carr. 2/6.

RADIO CLEARANCE LIMITED

27 TOTTENHAM COURT ROAD, LONDON W.1

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE

TRADE ENQUIRIES INVITED

Telephone: MUSEUM 9188

EST. 35 YRS.

AGAIN CRASHING THE SOUND BARRIER!

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE!

SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2 1/2	7000	80	8/-	4	6000	25	10/8	5	7000	3	9/-	6	10000	35	12/-
2 1/2	7000	35	8/6	4	7000	25	11/8	5	8500	3	9/8	6 1/2	6000	3	10/8
2 1/2	7000	30	8/8	4	6000	35	10/8	5	8500	5	9/8	6 1/2	7000	3	11/-
2 1/2	7000	80	8/-	4	7000	35	11/-	5	8500	3	10/8	6 1/2	7000	5	11/-
3	8500 (E.M.I.)	3	9/8	4	9300	35	11/8	5	9500	5	10/6	6 1/2	8500	3	11/8
3	8500	5	8/8	4	9500	35	11/8	5	10000	3	11/8	6 1/2	8500	3	12/-
3 1/2	7000	35	8/8	4 twteter	6000	3	7/8	5	6000	25	10/8	8	6000	3	11/8
3 1/2	9500	50	10/8	4	7000	3	8/-	5	6000	30	10/8	8	7000	3	12/-
4	5000	3	7/8	4	7000	5	8/-	5	6000	40	10/8	8	7000	3	12/-
4	6000	3	8/-	4	7000	5	8/-	5	9500	25	11/8	8	8500	3	12/8
4	7000	3	8/8	5	6000	3	8/-	5	9500	30	11/8	8	8500	5	12/8
4	9500	3	9/8	5	7000	3	8/8	5	9500	35	11/8				
4	9500	5	9/8	5	7000	5	8/8	5	10000	25	12/-				

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	6000	3	7/6	6 x 4	9500	3	10/-	7 x 4	9500	50	11/8	8 x 2 1/2	9500	30	10/8
5 x 3	7000	3	8/-	6 x 4	9500	5	10/-	7 x 4	10000	3	12/-	8 x 2 1/2	9500	50	10/8
5 x 3	7000	5	8/-	7 x 3 1/2	9500	3	10/8	7 x 4	10000	5	12/-	8 x 2 1/2	10000	3	10/8
5 x 3	9000	3	8/8	7 x 4	6000	3	9/8	7 x 4	10000	15	12/8	8 x 2 1/2	10000	5	10/8
5 x 3	9000	4	8/8	7 x 4	7000	3	10/-	7 x 4	9500	4*	13/8	8 x 5	6000	3	9/8
5 x 3	9000	5	8/8	7 x 4	7000	4	10/-	8 x 2 1/2	6000	3	8/8	8 x 5	7000	3	9/-
5 x 3	6000	25	9/8	7 x 4	7000	5	10/-	8 x 2 1/2	7000	3	9/-	8 x 5	8500	3	9/8
5 x 3	7000	25	10/-	7 x 4	8800	3	10/8	8 x 2 1/2	7000	5	9/-	8 x 5	8500	5	9/8
5 x 3	7000	35	10/-	7 x 4	9500	3	11/-	8 x 2 1/2	9500	5	9/8	8 x 5	9500	3	10/8
5 x 3	9000	25	11/-	7 x 4	9500	4	11/-	8 x 2 1/2	9500	20	9/8	8 x 5	9500	15	13/8
5 x 3	9000	35	11/-	7 x 4	9500	5	11/-	8 x 2 1/2	8500	5	9/8	8 x 5	10000	3	10/8
6 x 4	6000	3	8/8	7 x 4	9500	5	11/8	8 x 2 1/2	9500	3	10/-	8 x 5	12000	3	11/-
6 x 4	7000	3	9/-	7 x 4	9500	30	11/8	8 x 2 1/2	9500	4	10/-	8 x 5	12000	15	14/8
6 x 4	8500	3	9/8	7 x 4	9500	35	11/8	8 x 2 1/2	9500	5	10/-				

ALLOW 2/- each Speaker for postage and packing and please specify the exact requirements—the nearest available will be sent.

OVER 50,000 SOLD & STILL THE DEMAND CONTINUES FOR OUR 'HEAVENLY TWINS'

Ask for a demonstration in the shop.

"CAPRI"

Sensitive!
Super-selective!
Superb Speaker!
NOW ONLY
79/6



(2/- p. pkg.)
Pocket Super-het MW and Droitwich.

Size 4 1/2 x 2 1/2 x 1 1/2 in.

The best and easiest transistor build-yourself sets available.

Send S.A.E. for FREE PARTS LIST

6 First Grade MULLARD Transistors, Diode(s) and all components BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight . . .


"CONTESSA Mk III"
'QUEEN OF THEM ALL'

ONLY

£9.19.6

(3/6 p. pkg.)

PORTABLE CAR RADIO
2 WAVEBAND SUPER-HET

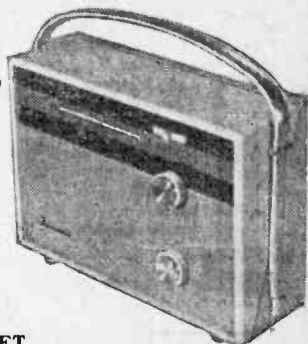

Inclusive price for all associated components, case, battery and instruction Book complete in every detail.
ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

CONTESSA III £9.19.6 (plus 3/6)

CAPRI 79/6 (plus 2/-)


SELECTED GUARANTEED BARGAINS—BRAND NEW

Beautifully geared AM/FM 2 Gang Condensers, 4/6; AM/FM IFT's 465kc/s and 10.7 Mc/s, 4/6 pair; Magnevox Crystal Tape Recorder Mikes, 12/6; Double-tuned Transistor ferrox IFT's Q120, 470 kc/s, 5/8 pr; 3 matched IFT's and oscillator coil for Mullard transistor circuits, 10/8 the set; Plessey-Brayhead turret tuners 34/38 Mc/s, valued 8/6 each; 3 watt Stereo Amplifiers, complete, ready to switch on 70/6; Sencorell rectifiers 13/2D-13-2-12, 2/6 each. **GERMANIUM DIODES**—OAT7, OAT8, OAB1, OAB2, OC45H, 2/- each. **TRANSISTORS**: Set of 6 (RP and LF) including 1 watt matched pair, heat sink and diode, 13/6 the set; OC44 (or equiv.), 8/8, OC46 4/8, OC81 5/7; matched pair 12/-, PXC 101A 4/8, matched pair 9/6, PXA 101 3/8, AF 115 4/8, SB 305 2/-, Submin. Germanium diode 1/3. Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay.

TERMS: CASH WITH ORDER or C.O.D. ON ORDERS OVER 10/-.

A NEW BOOK MORE ABOUT LOUDSPEAKERS by G. A. BRIGGS

136 pages 112 illustrations

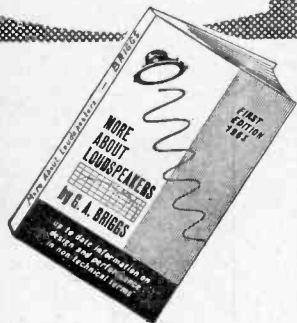Published
March 1963Price only
(9/6 post free)**8/6**

Since the 5th edition of *Loudspeakers* was published in 1958 there have been many new developments, particularly in relation to cones, diaphragms, magnets, cross-over networks, enclosures and absorbers. This book deals with these trends in non-technical terms.

CONTENTS

- Chapter 1 The General Situation
- 1 Magnets
 - 2 Response and Impedance Curves
 - 3 Transient Response
 - 4 Distortion
 - 5 Load Matching
 - 6 Adding a Speaker
 - 7 Crossover Networks
 - 8 Listening Tests
 - 9 Stereo
 - 10 Cabinets
 - 11 Mesh
 - 12 Various Models

Sold by bookshops and radio dealers or in case of difficulty may be ordered direct from the publishers

Wharfedale

WHARFEDALE WIRELESS WORKS LTD.
IDLE, BRADFORD, YORKSHIRE

Tel. Idle 1235/6

Grams 'Wharfedale' Idle, Bradford.

Lyons Radio Ltd.

3 Goldhawk Road, London W.12

MAINS TRANSFORMERS. Pri. 200/250v. Sec. tapped 3-15-6-8-9-10-12-15-18-20-21-30v. 2 amp size PRICE 22/6. 4 amp PRICE 37/6. 5 amp PRICE 48/6. Post 3/-, all sizes.

TYPE T/R. Pri. 220/240v. Sec. 230v. at 45mA and 6.3v. at 1A. Size 21 plus fixing feet x 21 x 2ins. PRICE ONLY 12/9, post 2/9.

AUTO-WOUND TYPE. Input 200v. Output 230v. 275 watts. Using two connected in series (wiring details supplied), can be used for either 200 v. or 230v. Input to give 100v. or 115v. output. Fully shrouded with fixing feet. Overall size 4 x 3 1/2 x 3 1/2 in. Brand new manufacturer's surplus. "SNIP PRICE" only 7/6 each. Post 3/- for 1, 4/- for 2.

TYPE K. Pri. 230v. Sec. 10-0-10v. at 1A. New ex-Govt. PRICE ONLY 10/-, post 2/9.

CONTACT COOLED RECTIFIERS. Full wave bridge type. Max. input 250v. A.C. Max. output 270v. at 120mA. Size 2 1/2 x 1 1/2 x 1 1/2 in. PRICE ONLY 9/-, post paid.

AERIAL RODS. Set consists of 3 copper-plated tapering steel sections each 4ft. making up a 12ft. Aerial or the ever-popular Fishing Rod. PRICE ONLY 7/6 or with mounting base PRICE ONLY 10/6. Carriage 3/6.

BATTERY CHARGERS. For charging 6 or 12 volt batteries at 3 to 4 amps. Housed in neat metal case, fitted with ammeter, mains lead, battery lead with bull-dog clips and voltage selector socket. Fully guaranteed. Special end of season bargain PRICE ONLY 55/-, post 4/6.

1/4 H.P. ELECTRIC MOTORS. 200/250v. A.C. mains split phase induction type by Crompton Parkinson. Spindle 2 x 1/2 in. dia. 1440r.p.m. reversible with mounting plate and bosses for vertical or horizontal mounting. As new and unused. BARGAIN PRICE ONLY 75/-, carriage 9/-.

POSTAL BARGAIN SALE. Send for free catalogue. S.A.E. appreciated.

H.A.C. SHORT-WAVE EQUIPMENT

WHY is it that for 3 decades

H.A.C. SHORT-WAVE KITS

have been consistently demanded by so many constructors, amateurs, professionals and schoolboys? Because H.A.C. is undoubtedly the best. The circuits are simple, yet the results are fantastic. So easy to construct (or we do it for you). The secret is, of course, our vast experience, and also we use only the very highest grade of Short Wave components. (Not surplus.) We have been famous all over the world for 30 years, as suppliers of quality

SHORT-WAVE RECEIVERS AND KITS

H.A.C. were the original suppliers of Short-Wave receiver kits for the amateur constructor. Over 10,000 satisfied customers—including technical Colleges, Hospitals, Public Schools, Hams, etc.—in fact we receive many testimonials by every post, from purchasers of H.A.C. Kits, who tell us that they regularly listen to stations from all over the world.

AUSTRALIA & AMERICA

the North Pole, and other expeditions and all at full strength. Your success like our products is

GUARANTEED

Improved designs with Denco coils: One-valve kit, model "C". Price 32/6. Two-valve kit, model "E". Price 50/- Super sensitive all-dry receiver. Special Inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering—call and inspect a demonstration receiver, or send for descriptive catalogue and order form to—

"H.A.C." Short Wave Products (Dept. TH)
44 Old Bond Street, London W.1.

Lewis have the Cabinet for you


We can supply any cabinet to your own specification

This is only one example of—
THE LARGEST RANGE OF CABINETS IN THE COUNTRY

Equipment is also our specialty.



The Grosvenor
Price 15 gns.

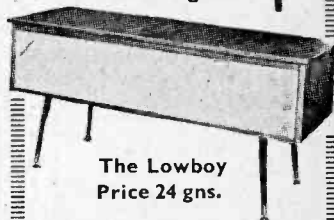

The Lowboy
Price 24 gns.

LEWIS radio

100 (PJL3) Chase Side, Southgate, London, N.14. Tel 3733/9666

Send today for the two new Lewis Catalogues

Designed to assist your choice of cabinet and equipment.

THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 64 page equipment catalogues.

Please send your two new catalogues enclosed is P.O. for 3/6 which will be credited against any purchase I make.

Name

Address

BLOCK CAPITALS PLEASE

R.S.T. VALVE MAIL ORDER CO.

Tel: MITcham 6202
Open Daily to Callers

211a STREATHAM ROAD, MITCHAM, SURREY.

All Valves Brand New and Fully Guaranteed — Obsolete valves a speciality.
Quotations given on any type not listed. Send S.A.E.

Special 24 Hour Express Mail Order Service

AC2/PEN DD AC/TP AC/VP1-5-7	ECC85 7/6 ECC88 12/6 ECC91 3/- ECF80 7/6 ECF82 8/6 ECH3 21/6 ECH21 21/- ECH35 10/- ECH42 9/6 ECH81 7/6 ECH83 8/6 ECL80 7/6 ECL81 10/- ECL82 9/6 ECL83 10/6 ECL86 9/6 EF6 21/- EF9 21/- EF22 14/- EF36 4/- EF37 8/- EF39 4/- EF40 15/- EF41 8/- EF42 10/- EF50A 3/6 EF50E 3/- EF80 5/- EF85 5/- EF86 8/- EF89 9/- EF91 4/- EF92 4/- EF95 5/- EF98 10/- EF183 10/6 EF184 10/6 EK32 8/6 EL3 21/6 EL32 4/6 EL33 10/- EL34 14/- EL35 10/- EL37 17/6 EL38 17/6 EL41 9/6 EL42 9/6 EL81 12/6 EL84 6/9 EL85 10/- EL90 8/6 EL91 4/- EL95 10/6 EM80 8/6 EM81 8/6 EM84 9/6 EM85 10/- EY1 7/6 EY81 8/6	EY83 12/6 EY86 7/- EY91 3/- EZ35 6/- EZ40 7/- EZ41 7/- EZ80 6/- EZ81 6/- EZ90 5/- E1148 2/- FC2 15/- FC2A 17/6 FC4 15/- FW4/500 9/- FW4/800 9/- G230 10/6 G232 10/6 G233 19/3 G234 13/6 G237 19/3 HABCB010/- HL41 8/- HL41DD 8/- HL92 8/6 HL133DD 9/6 HN309 26/6 IW4/350 10/- IW4/500 10/- KT33C 8/- KT36 17/6 KT61 9/6 KT66 15/- KT76 10/- KT81 15/- KTW61 8/- L63 5/- LN152 8/- LN309 11/6 LZ319 12/6 MKT4 17/6 MS4B 17/6 MVS/PEN 17/6 MVS/PENB 17/6 MU14 9/- MX40 15/- N18 8/- N37 14/- N78 22/6 N108 15/- N308 18/- N369 10/6 OD3 5/- OZ4 5/6 P2 10/- PABC80 13/- PCC84 8/-	PCC85 9/6 PCC88 12/6 PCC89 8/6 PCF80 9/- PCF82 7/- PCF84 12/6 PCF86 12/6 PCL82 9/- PCL83 10/- PCL84 7/- PCL85 9/- PCL86 12/6 PENA4 17/6 PENB4 17/6 PEN4DD 24/- PEN4VA 17/6 PEN36C 20/- PEN45 10/- PEN45DD 25/- PEN46 5/- PEN453DD 20/- PENDD4020 20/- PL33 15/- PL36 12/6 PL38 21/- PL81 9/- PL82 8/- PL83 7/6 PL84 8/- PL820 18/- PM24M 13/6 PX4 15/- PX25 25/- PY31 15/- PY32 12/6 PY33 10/6 PY80 7/6 PY81 7/6 PY82 6/9 PY83 8/- PY88 10/- PY800 10/- PZ30 15/- QS95/10 10/- QS150/15 10/- R2 10/- R16 17/6 R19 16/- R20 16/- SP41 3/6 SP61 3/6 T41 15/-	TDD4 12/6 TDD13C 17/6 TH41 27/6 TY86F 12/6 U10 9/- U12 9/- U14 9/- U22 8/- U24 21/- U25 11/- U26 10/- U31 9/- U35 17/6 U37 17/6 U47 11/- U50 7/- U52 4/- U76 7/6 U78 4/6 U145 10/6 U191 13/6 U251 15/- U281 15/- U282 19/6 U301 17/- U329 15/- U403 10/- U404 10/- U801 19/6 UABCB0 7/6 UAF42 8/6 UB41 7/6 UBC41 8/6 UBCB81 10/- UBF80 8/- UBF89 7/6 UBL21 20/- UCC84 11/6 UCC85 7/6 UCF80 12/6 UCH21 20/- UCH42 8/6 UCH81 8/- UCL82 9/6 UCL83 13/6 UF41 7/6 UF42 7/6 UF80 7/- UF85 7/6 UF86 12/6 UF89 6/- UL41 8/- UL44 20/- UL46 14/6 UL94 6/6 ULB5 7/6 UM80 10/6 URIC 15/-	UU6 17/6 UU8 15/- UU9 7/6 UYIN 12/6 UY21 15/6 UY41 7/6 UY85 6/6 VMS4B 12/6 VP4 15/- VP4A 15/- VP4B 15/- VR105/30 7/- VR150/30 7/- W61 11/- W76 5/- W77 4/- W81 6/- W81M 6/- X41 15/- X61M 10/- X65 12/6 X76 12/6 X76M 12/6 X78 26/- X79 40/9 X81 10/- Y61 10/- Y63 10/- Z63 7/6 Z66 10/- Z77 4/- Z152 5/- OZ4 5/- IA7 11/- IC5 10/- ID5 8/6 ID6 10/- IH5 9/6 IL4 5/- IN5 9/6 IR5 6/- IS4 8/- IS5 5/6 IT4 4/- IU5 5/9 2P 24/9 3A4 5/- 3A5 10/6 3Q4 8/- 3Q5 9/- 3S4 6/- 3V4 7/- SU4 4/- SV4G 7/9 SY3G 5/6 SY3GT 6/6 SZ4G 9/6 SZ4GT 12/6 6A7 9/- 6A8G 8/6	6A8GT 13/6 6AC7 6/- 6AK5 5/- 6AL5 4/- 6AM5 5/- 6AM6 4/- 6AQ5 6/6 6AT6 6/- 6AU6 9/- 6B8G 3/- 6BA6 6/- 6BE6 6/- 6BG6 15/- 6B86 6/- 6BQ7A 12/6 6BR7 10/6 6BS7 12/6 6BV6 8/- 6BW7 8/- 6C4 3/6 6C5GT 8/- 6C6 6/6 6C9 12/6 6CD6G 27/6 6CH6 10/- 6CW4 16/- 6D2 4/- 6D6 5/6 6E5 10/- 6F1 10/6 6F6 6/9 6F12 4/- 6F13 10/- 6F14 10/- 6F15 12/6 6F19 12/6 6F23 10/6 6F25 16/6 6F26 13/6 6F33 5/6 6F46 2/- 6J5 5/6 6J5G 4/6 6J7G 7/6 6K7 7/6 6K7G 2/- 6K7GT 7/6 6K8 9/6 6K8G 5/- 6K8GT 9/6 6K25 17/6 6L1 10/- 6L6 7/6 6L7 10/- 6L8 10/- 6L19 15/- 6N7GT 9/6	6P25 10/6 6P28 12/6 6Q7 9/6 6Q7G 6/6 6Q7GT 8/6 6SA7 7/- 6SC7 8/6 6SF5 10/- 6SG7 7/- 6SH7 6/- 6S17 6/6 6SK7 5/6 6SL7GT 6/- 6SN7GT 5/6 6SQ7 8/6 6U4GT 10/- 6USG 7/6 6V6G 4/6 6V6GT 8/- 6X4 4/6 6X5G 6/- 6X5GT 8/6 6Y30L2 10/- 7B5 12/6 7B6 10/- 7B7 8/6 7C5 8/- 7C6 8/6 7D5 15/- 7D6 15/- 7D8 15/- 7H7 6/- 7R7 10/- 7S7 10/- 7Y4 6/6 8D3 4/- 9B8W6 12/6 10C1 12/6 10C2 17/6 10F1 10/- 10F9 12/6 10LD11 15/- 10P13 15/- 10P14 19/- 11D5 23/6 12A6 6/6 12A8H 9/- 12AT6 7/6 12AT7 5/- 12AU6 17/6 12AU7 5/- 12AX7 5/- 12BA6 7/6 12BE6 7/6 12BH7 10/- 12C8 8/6 12J5GT 4/- 12J7GT 8/- 12K7GT 5/- 12K8GT 10/-	12Q7GT 6/6 12SA7 8/6 12SJ7 8/- 12SK7 6/- 12SL7 8/- 12SN7 10/- 12SQ7 16/- 14H7 10/- 14R7 10/- 14S7 16/- 19AQ5 8/- 19BG6G 15/- 20D1 10/- 20D2 21/- 20F2 17/6 20L1 22/6 20P1 15/- 20P3 24/- 20P4 20/- 20P5 20/- 25A6 8/- 25L6 8/- 25Y5 8/- 25Y5G 8/- 25Z4 7/6 25Z5 8/- 25Z6 8/6 27S5 19/6 30C1 9/- 30C15 12/6 30F5 10/- 30FL1 10/6 30L1 8/6 30L15 11/- 30P4 18/- 30P12 10/- 30P16 9/- 30P19 17/6 30PL1 11/6 30PL13 11/6 30PL14 16/6 35A5 15/- 35L6GT 8/6 35W4 7/6 35Z3 15/- 35Z4 7/6 35Z5 8/6 41STH 21/- 42 12/6 50C5 10/- 50CD6G 30/- 50L6 8/6 75 8/- 80 7/6 85A2 12/6 18SBT 30/- 807A 5/- 807B 5/-
--------------------------------------	---	--	---	--	---	---	---	--

COMPLETE VALVE LIST FREE WITH ORDER

METAL RECTIFIERS

RM1 7/6	14A86	23/-	16RD 2-2-8-1	12/- (FC142)
RM2 8/-	14A97	26/-	16RE 2-1-8-1	10/-
RM3 10/-	14A100	28/-	18RA 1-1-8-1	5/-
RM4 17/6	14RA 1-2-8-2	21/- (FC301)	18RA 1-1-16-1	7/- (FC116)
RM5 19/6	14RA 1-2-8-3	25/- (FC31)	18RA 2-1-8-1	12/-
	16RC 1-1-16-1	10/-	18RD 2-2-8-1	16/- (FC124)

BRAND NEW TRANSISTORS

OC44 6/-	OC74 8/-	OC81D 6/-
OC45 7/-	OC75 6/-	OC82 6/-
OC71 5/-	OC77 6/-	OC82D 6/-
OC72 8/-	OC81 6/-	

SILICON RECTIFIERS

400 volts 350 mA ... 8/- each

TERMS OF BUSINESS C.W.O. or C.O.D.

4/2 PACKING CHARGE ON ALL C.O.D.

ORDERS. POSTAGE 6d. per VALVE

SETS OF VALVES

IR5, IS5, IT4, 3S4, 3V4	...	Set of 4, 19/-
DAF91, DF91, DK91, DL92, DL94	...	Set of 4, 19/-
DAF96, DF96, DK96, DL96	...	Set of 4, 26/6

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.
12 volt 30 watt AC/DC SBC 8/8. P. & P. 1/-.
12 volt 60 watt AC/DC SBC 8/8. P. & P. 1/-.
Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt. 10/6.
P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt. 22/6. P. & P. 3/6.

Set of 4 colours **FLUORESCENT Paint**. Red, Yellow, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/6.

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts of stationery. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.

NSP2 CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/- P. & P. 1/-.

MAGNETIC COUNTERS 10 IMPULSES PER SECOND

Very latest High Speed type ex P.O. guaranteed perfect.
Type No. 100B, coil 2,300 ohms. for 48 volt D.C. operation (will work on 36 volt). overall size 4 x 1 x 1 in. Also available, type 101A which can be used as an interesting accessory with our Strobe unit. Either type price 15/- P. & P. 1/6.



Variable Voltage Transformer

Input 230 v. A.C. Output 0-260 v. at 2.5 amp. Fully shrouded. New. £5.19.8. Inc. carriage. Also available from stock, 5, 10 and 20 amp. Write for details.

4,000 Ohm Headphones, brand new (imported). 12/6 each pair. P. & P. 1/6.

SIEMENS H.S. RELAY. Very latest type, sealed. H96E. 1,700 ohms plus 1,700 ohms, single C/O contacts. Price 16/6 each, plus 1/- P. & P.

6 VOLT 40 A.H. ACCUMULATOR, in metal case with leather carrying handle. New. Price 27/6, carriage 8/-.

500 MICROAMP SUB-MINIATURE M/C METER, 1 1/2 in. diameter, flush mounting, variable hole angle. Sealed 0-1 mA. Supplied with Resistor for use as IMA if required. 29/6 plus 1/- P. & P.

230 VOLT A.C. GEARED MOTORS
Type B16G 80 r.p.m., 26 lb. inch. £11.98. P. & P. 2/-.
Type D16G 5 r.p.m., 1.7 lb. inch. £22.9.8. P. & P. 2/6.
Type D18G 13 r.p.m., 1.35 lb. inch. £22.12.6. P. & P. 2/6.

12 v. D.C. Reversible Motor with tremendous power weight ratio. 3 position switch. Weight 2.1 ounces. Size 1 1/2 x 1 1/2 in. dia. Speed 7,000 r.p.m. Self lubricating. 15/- plus 1/- P. & P.

AVO METER MODEL 7. Individually tested on all ranges and guaranteed. Inclusive of Test Leads. £11.0.0 each. P. & P. 5/-. Case 20/-.

MINIATURE LEAD ACID ACCUMULATORS. (Brand New) 2V, 1.5 A.H. Size 4 x 1 1/2 x 1 1/2 in. Wt. approx. 1 lb. 16/6 for 3. P. & P. 1/6. 12V, 0.75 A.H. Size 4 x 3 x 1 1/2 in. Wt. approx. 2 lb. (can be used as double 6V). 15/6 each. P. & P. 1/6.

TRANSISTORS

OC30	10/-	OC76	6/-	Get 114	5/6
OC41	7/-	OC77	9/-	Get 573	12/6
OC45	5/-	OC139	12/-	Get 573	25/-
OC45	9/-	OC79	9/6	Get 573	25/-
M/Pair		OC171	10/6	1N135A	4/-
OC71	5/-	OC200	10/6	2N458	20/-
OC72	7/-	OC201	21/-	25005	30/-
OC72	14/-	Get 104	6/-	25013	100/-
OC73	6/-	Get 105	10/-	SP345	7/6
OC75	7/-			TK20B	4/-

SERVICE TRADING CO.

All Mail Orders also callers.
47-49 High Street, Kingston on Thames
Tel.: KINgston 9450

Personal callers only
9 Little Newport Street, London W.C.2
(off Leicester Square)
Tel.: GERRard 0676

TRANSISTORS FROM 1/3

GREEN SPOT A.F. 3 volt. ONLY 1/3.
YELLOW SPOT A.F. 6 volt 1/6.
RED SPOTS. Now ONLY 1/9 each.
WHITE SPOTS. ONLY 2/6 each.

MICRO-ALLOY TRANSISTORS

MAT100 7/9, MAT101 8/6, MAT120 7/9,
MAT121 8/6. 22 Tested Circuits using
Micro-Alloy Transistors 5/-.

MULLARD TRANSISTORS

OC70 6/6, OC71 6/6, OC72 8/-, Matched
Pr. 16/-, OC81 8/-, Matched Pr. 16/-, OC78
8/-, OC44 9/3, OC45 9/-, OC170 9/6,
OC171 10/6, AF102 27/6, AF114 11/-, AF115
10/6, AF116 10/-, AF117 9/6, AF124 11/-,
AF125 10/6, AF126 10/-, AF127 9/6.

DIODES OA70, OA79, OA81, OA90,
OA91 all 3/- each. BY100 13/-.

SURPLUS DIODES CG12E 1/6.

Miniature Type 3 for 2/-, 7/- Doz.

TRANSISTOR HOLDERS 3 or 5 pin 1/-.

REPANCO COMPONENTS

TRANSISTOR TRANSFORMERS

TT49 Interstage, TT45 Driver, TT46 Output,
TT47 Driver. All 5/- each.
FR2 Ferrite Road Aerial 12/6.
DRX1 Crystal Set Coil M. & L. 3/-.
DRR2 Dual Range Coils 4/6.
CHI Miniature R.F. Chokes 2/6.

THE HIKER, 4 Transistor Portable.

Step-by-Step Instructions 1/6.

ALL SENT POST FREE IN U.K. by

PETHERICK'S RADIO SUPPLIES

22 High Street, Bideford, N. Devon

Tel.: Bideford 1217

S.A.E. with ALL enquiries please.

A.R.R.L. RADIO AMATEURS

HANDBOOK 1963

New edition 38/-. Postage 2/3.

The Transistor, an introduction to its Applications by Wolfendale. 40/-, post. 1/6.
Transistor Circuits for Radio Controlled Models by Boys. 7/6, postage 8d.
British Transistor Directory, new ed., by Bradley. 8/6, postage 9d.
Design and operation of Regulated Power Supplies by Gottlieb. 22/-, post 8d.
22 Tested Circuits using Micro Alloy Transistors, by Sinclair. 5/-, postage 6d.
Transistor Circuits Manual No. 5, by Sinclair. 5/-, postage 6d.
More about Loudspeakers, new edition, by Briggs. 8/6, postage 1/-.
Radio Valve and T.V. Tube Equivalents, new edition by Babani. 3/6, postage 6d.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2
(adjoining Lisle Street)

BBC · ITV · F.M. AERIALS



B.B.C. (BAND 1). Telescopic loft. 21/-. External S/D 30/-.
ITV. (BAND 3). 3 Element. Loft array. 25/-, 5 Element. 35/-.
Wall mounting. 3 Element. 35/-, 5 Element. 45/-.
COMBINED B.B.C./ITV. Loft 1+3. 41/3; 1+5. 48/9.
Wall mounting 1+3. 56/3; 1+5. 63/9. Chimney 1+3. 63/9; 1+5. 71/3.

F.M. (BAND 2). Loft S/D. 12/6; "H". 30/-; 3 Element. 58/8. External units available. Coax. cable 8d. yd. Coax. plugs 2/3. C.W.O. or C.O.D. P. 3/-.
Send 6d. stamps for illustrated lists.
Band IV 625 line Aerials also available.

K.V.A. ELECTRONICS (Dept. P.W.)
38, Godstone Road, Kenley, Surrey.

D. & B. TELEVISION (Wimbledon) LIMITED

131 & 131a, Kingston Road,
South Wimbledon, London, S.W.19
Phone: CHerrywood 3955

OPEN

Monday to Saturday, 10 a.m. to 7 p.m.
(Except Wednesday, 1 p.m.)

Nearest Tube:

South Wimbledon (Northern Line)

COMPARE OUR PRICES

For the Finest in the Country
YOUR PROBLEMS ARE OUR BUSINESS
MOST LINE-OUTPUT TRANSFORMERS
IN STOCK

Surplus or Ex-Equipment Valves
Guaranteed 3 Months. New Low Prices

EB91	2/6	PCL82	5/-	U801	17/6
EBF80	5/6	PCL83	5/6	UAF42	5/6
ECC81	4/-	PCL84	7/6	UBC41	5/6
ECC82	4/-	PL33	7/6	UCC84	8/6
ECC83	4/6	PL36	7/6	UCF80	8/6
ECL80	4/6	PL38	12/-	UF42	3/-
ECL82	6/6	PL81	6/6	6F1	3/6
EF80	2/6	PL82	5/-	6F12	2/-
EF85	5/-	PL83	5/6	6F13	5/6
EF91	2/-	PL84	5/-	6F15	6/6
EL33	5/6	PY31	7/-	6L1	7/6
EL84	5/-	PY32	8/-	6L18	6/6
EY51	3/6	PY80	4/-	6P25	5/6
EY86	5/-	PY81	4/-	6P28	8/6
EZ80	4/6	PY82	4/-	10F1	3/6
EZ81	5/-	PY83	6/6	10P13	7/-
GZ32	5/6	PZ30	7/6	10P14	6/9
GZ34	8/-			20D1	5/6
KT33c	4/-	U24	8/-	20F2	6/6
KT36	8/-	U25	7/6	20L1	9/9
KT61	6/9	U26	6/6	20P1	7/6
KT63	5/-	U31	7/-	20P3	8/-
PCB84	5/-	U32	4/6	20P4	12/6
PCF80	5/-	U191	7/9	20P5	8/-
PCF86	7/-	U301	10/-	30P4	7/6

We pride ourselves that we can obtain and supply any TV spare. Please ask us for ANY components you may require we are almost certain to have them.

TERMS: S.A.E. all inquiries. C.W.O. C.O.D. 5/- extra. Postage on Valves 6d. each. C.R.T.s 12/6 inc. Insurance.

Satisfaction assured. Return Post Service

RES/CAP. BRIDGE 39/6

p. & p. 2/6

Checks all types of resistors, condensers
6 RANGES

Built in 1 hour. Direct reading.

READY CALIBRATED

Stamp for details of this and other kits.

Please write to:

RADIO MAIL (Dept. PM)


Raleigh Mews, Raleigh Street, Nottingham

2 METRES!

The thrills of 144 Mc/s can now be yours for only 39/6, complete kit! Tunable range 150-100 Mc/s, simplified construction, etc., write today for descriptive literature, also if a newcomer-beginner to Amateur Radio ask for free copy of the world-famous "Globe-King" kits and receivers—stamp to cover postage costs appreciated. Write now to makers:

JOHNSONS (Radio)

St. Martins Gate, Worcester

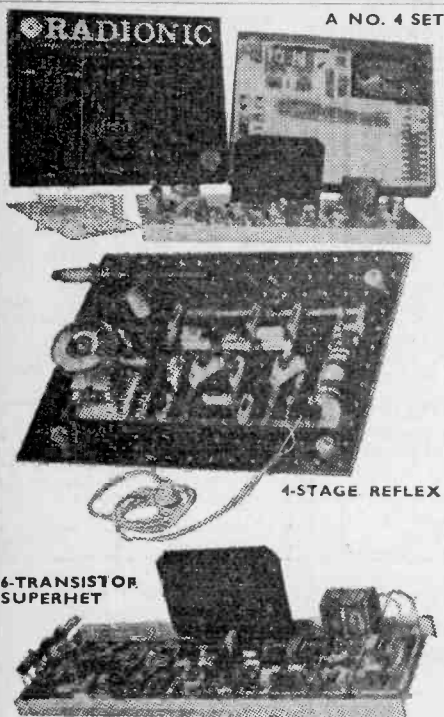

RADIONIC CONSTRUCTIONAL AND EXPERIMENTAL SYSTEM

SENSATIONAL! NEW! SIMPLE!

The Radio and Electronic construction system you have been waiting for. With top quality components mounting on colour-coded plastic bases, perforated transparent panel, perforated brass connecting strip and screw connection for positive contact you can quickly build any circuit and check it at a glance. Peak performances achieved.

NO SOLDERING—NO SPECIAL SKILL—NO MAINS—FULLY ENGINEERED—COLOUR-CODED MOUNTINGS—FIRST CLASS COMPONENTS—MULLARD TRANSISTORS—PROGRESSIVE — FLEXIBLE — EXPERIMENTAL — INSTRUCTIONAL—IDEAL RESEARCH FACILITY—RADIONIC NEWS LETTER.

Set No. 1. £5.18.6.

14 Circuit Sheets.
Diode Detector and two Amplifier stages;
Transistor Detector and Amplifier; Multi-vibrator.
Regenerative Receivers;
Earphone operation.

Set No. 2. £6.19.6.

20 Circuit Sheets.
Circuits of Set No. 1 plus capacity reaction;
T.R.F. and Reflex Receivers;
Earphone operation.

Set No. 3. £10.19.6.

22 Circuit Sheets.
High quality Push-Pull Amplifier and 11,000 lines 7×4 inch 3Ω loudspeaker convert circuits 1-20 to loudspeaker operation.
Amplifier can be operated from microphone or gramophone pick-up.

Set No. 4. £14.19.6.

26 Circuit Sheets.
Builds high quality six transistor superheterodyne receivers, as well as circuits of sets 1-3.

Postage and Packing extra on each of the above.

Sets or Separate Components available direct from Radionic Products Limited; Sets also available from authorised Retailers.

TRADE ENQUIRIES ARE INVITED.

Full Details and price lists from:

RADIONIC PRODUCTS LIMITED

ADASTRAL HOUSE, NUTFIELD, NR. REDHILL, SURREY
Telephone: Redhill (RL6) 5050 Telex: 21433

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES —

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS—NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draftsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
A.M.I.C.E.
A.M.I. Prod. E.
A.M.I.N.I.
A.I.O.B.
A.F.R.A.E.S.
B.Sc.
A.M. Brit. I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc.,
A.M. Brit. I.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page
"ENGINEERING OPPORTUNITIES"
(Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM
THAT INTERESTS ME


SE/21

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

★ TRANSISTORS ★ ZENERS ★ VALVES ★ QUARTZ CRYSTALS ★ THESE ARE OUR SPECIALITIES
DIODES RECTIFIERS TUBES COMPONENTS

EQUIVALENTS, DIAGRAMS, DETAILS AND INFORMATION IN OUR LATEST 54-page CATALOGUE. 1/6 Post Free

TRANSISTOR PORTABLE SIGNAL GENERATOR

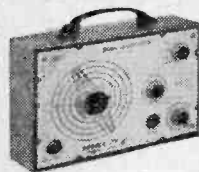

PRICE
£7.10.0
P.P. 2/6

A 1st class Signal Generator covering 220 Kc/s to 200 Mc/s in 8 ranges. Radio broadcasts and I.F., Amateur, VHF, Shipping, TV, etc. R.F., I.F., A.F., modulated R.F. outputs. Easy to read and use with full details. Within 2% accuracy. Size $6\frac{1}{2} \times 4\frac{1}{2} \times 2\frac{1}{2}$ in.
12 MONTHS' GUARANTEE
Leaflet on Request.

FIELD STRENGTH METER

Five channels cover 1 Mc/s to 200 Mc/s. Fitted 200 microamp meter for CW or RF. Indication and Earphone for AF monitoring. Designed for checking all types of transmitters. Size $4 \times 2\frac{1}{2} \times 2\frac{1}{2}$ in. Complete. Ready to Use, with instructions. 6/96 Post Free. Ideal for 27 Mc/s.

A SELECTION FROM OUR STOCKS

Please allow adequate postage or packing
Full Details in our Latest Illustrated Catalogue. 1/6 Post Free.

- | | |
|--|-------------------|
| 1. 2,000 ohm Head Phones | ... 12/6 |
| 4,000 ohm Head Phones | ... 14/- |
| Stereo Phones 2 x 8 ohm | ... 27/6 |
| 2. Make your own printed circuits. Full details with 3 boards 6 x 3 in. etc. | 19/6 |
| 3. Crystal Microphones (P.P. 1/6 any type) | |
| Acos 39-1 Stick Microphone | ... 32/6 |
| Acos 40 Desk Microphone | ... 15/- |
| Acos 45 Hand Microphone | ... 25/- |
| Lapel/Hand Microphone | ... 15/- |
| MC 24 Stick Microphone | ... 25/- |
| 100C Stick with Stand | ... 39/6 |
| BM3 Stick with Stand | ... 52/6 |
| 4. Transistor Megaphone | £12.10.0. |
| 5. 250 mV 4-Transistor Amplifier, built ready to use | ... 47/6 P.P. 1/6 |
| 6. Complete Test Lead Kits | ... 8/6 |
| 7. Miniature Vernier Dial 8 : 1 reduction marked 0/100 for 1/2 in. spindles, 1/2 in. diam. 12/6; 2 in. diam. 14/-; 3 in. diam. 16/-. | |
| 8. 931A Photomultiplier. Brand new with base | ... 30/- |

DEAC RECHARGEABLE BATTERIES

- (a) 18 volt 100mA/H 4 x 1 in. diameter. Brand new sleeved, 30/-.
(b) As above but 150mA/H, 35/-.
Both types easily split into any multiple of 1.2 volt. Brand new.

9. CV2886 (M2H) Liquid Sampling Geiger Tube, 370 volts. 22/6. P.P. 1/-.
10. Antex Miniature Mains Soldering Iron, 3/2 in. bit, 29/6. P.P. 1/-.
Pocket Iron with Pouch, 30 watt, 220/250 volt. 18/6.
Solon 15 watt 3/2 in. bit, 22/6 P.P. 1/-.
11. Pocket Radio Booster Unit, for any Radio. Improves output and quality. Size $9\frac{1}{2} \times 3\frac{1}{2}$ in. dia., 27/6. P.P. 1/-.
Size $8 \times 2\frac{1}{2}$ in. dia., 25/-, P.P. 1/-.
Ideal for using pocket radios in car.
12. 125 mV 9 volt Sub-min. 3-Transistor Amplifier. 2 x 1 x 1 in. 45/-.

RUN YOUR RADIO OR AMPLIFIER FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6. P.P. 1/-.
2. For PP4, PP7, PP9, PP10, 9 volt Portable Radio and Equipment Supplies up to 300 mA. 49/6. P.P. 2/-.
3. De Luxe version of No. 1 also charges PP3 type batteries. 24/-, P.P. 1/-.
4. Rechargeable PP3 battery. Runs as long as 100 batteries. Complete with charger unit, 25/-, P.P. 1/-.

SILICON RECTIFIERS 500mA

100 PIV	3/-	1000 PIV	... 10/-
200 PIV	3/6	100 PIV 1 amp	... 4/6
300 PIV	4/6	200 PIV 6 amp	... 12/6
400 PIV	5/-		

REMEMBER—All our transistors and devices are 100% 1st Grade and Fully Guaranteed. We can advise as to the correct type to use.

NEW TRANSISTOR, VALVE, CRYSTAL AND RECTIFIER CATALOGUE NOW READY 9d. POST FREE

13. Telephone Coil for any amplifier or Recorder, 12/6, or fitted Miniature Jack Plug, 14/-.
14. Crystal Contact Microphone for guitars, etc., 12/6.
15. Personal Earphones: 600 ohm 10/6, 1,000 ohm 12/6, Crystal 8/6, 8/10 ohm 9/6. Fitted leads, jack plugs and sockets.
16. 2-pole 2-way Miniature Honeywell Micro Switches, 7/6.
17. Transistor Baby Alarm, as previously advertised, £5.10.0. P.P. 2/-, Also Telephone Amplifier £5.10.0. P.P. 2/-.
18. 4-Transistor 2-way Intercom., £7.10.0.
19. 2-Transistor 2-way Intercom., 89/6.
19. Miniature Multi-section Telescopic Aerials: 14 in. 3/6; 38 in. 6/6; 42 in. 10/6; 64 in. 17/6.
20. Miniature 3-Press Button Switches, 6 pole 2-way and on/off 5/-, P.P. 9d.
21. Transistor Signal Injector 42/6. For circuit testing and checking.
22. Bin. 15 ohm double cone Hi-Fi Speaker, 84/-.
- Complete range of Speakers stocked.
23. 12-way Selector Tube GS12C (CV1740) 25/- each.
24. Quartz Fibre Pocket Dosimeters 0/150R and 0/500R, 12/6 each.
25. 6-Transistor speaker superhet pocket radio ready to use. Complete with leather case, phone, etc., etc. 99/6 P.P. 2/-, Fully guaranteed.
- De Luxe version 5 gns. P.P. 2/-.
26. 4+4 watts Stereo Amplifier. Size $7\frac{1}{2} \times 3 \times 6$ in. 4-valves. Inputs for MONO or STEREO. Tuner and Pickups. Finished in styled gold hammer cabinets. £9.10.0, P.P. 2/6.
27. Sub-Miniature Jack Plug and Socket, 2/6. Sub-Miniature Screened Plug, 2/-.
28. Standard Jack Plug, 2/6. Standard Screened Jack Plug, 3/6.
29. New Telephone Amplifier in moulded cabinets, 79/6.
30. Tuning Indicator and Battery Level Meter. Miniature Meter (400 μ A) for Recorders, Transmitters, etc., etc., 24/6.

ALL PARTS IN STOCK FOR WEYMOUTH (WEYRAD) MED/LONG AND MED/SHORT RECEIVERS.

METER BARGAINS

- | | |
|--|----------|
| 50 Microamp 2 in. square MC | ... 35/- |
| 1 mA 2 in. square MC | ... 25/- |
| 1 mA 2 1/2 in. Flush Round | ... 30/- |
| 2 1/2 in. Moving Coil double range Voltmeter centre zero. 30-0-30 and 3-0-3 volts. Ideal for transistor tester or voltage measurements, 12/6. Post Free. | |
| 0/500 Microamp, 2 1/2 in., flush-mounting. D.C. | ... 20/- |
| 2 1/2-0-2 1/2 mA, 2 1/2 in. flush D.C. | ... 12/6 |
| 0/40/120 mA 2 in. D.C. | ... 10/- |
| 0/15 volt M.I. 2 1/2 in. FR. A.C. | ... 8/6 |

Miniature Panel Meters

- | | |
|--|----------------------|
| *0/50 μ A (D.C.) 39/6 | *0/5 mA (D.C.) 27/6 |
| *0/500 μ A (D.C.) 32/6 | *0/300 V (D.C.) 27/6 |
| *0/1 mA (D.C.) 27/6 | *0/10 V (D.C.) 27/6 |
| *15" Meter 35/- | All Brand New Boxed. |
| * Available Clear Plastic Front or Black Moulded. State which. | |

SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working, 29/6.
- Resistor Box. Provides 24 standard values at 1 watt. 15 ohms to 10 meg., 37/6.

Each box fully calibrated with insulated leads. Invaluable for service and design.

31. Crystal Microphone Inserts: 2 in. 10/6; 1 1/2 in. 7/6; 2 in. 3/6; Acos 39-1 15/-.

32. Stereo Amplifier, 2 watts each channel. Brand new, 79/6. P.P. 2/-.

33. Precision Geared Preset Controls. 46 turns from end to end of track. 10K ohm and 30K ohm types, 12/6 each.

34. Type 38 Transmitter/Receiver. 5-valve, 7.4-9 Mc/s, 22/6. P.P. 2/6 (sold without guarantee).

35. Valve Voltmeter, AC/DC/Resistance, etc. £9.19.6. P.P. 5/-.

MINIATURE LEDEX SWITCHES

24 volt D.C. rotating switches, fitted actuator at each end of bank of contacts. Uses standard switch wafers. 5 Banks or 8 Banks of Contacts 45/-.

36. STC FIS Thermistors, 6/-, RS3 15/-.

37. ORP12 L DR Cell, 12/6; ORP60 Cell, 9/6; CPC71 Photo Trans., 27/6.

38. 1/2 Track Record/Playback Tape Heads. 2K ohms impedance, 15/-.

39. Personal Earphones with Jack Plug and Socket, 8/10 ohm 6/6; 600 ohm 9/6; 1000 ohm 10/6; Crystal 6/6.

40. 7 x 7 in. Printed Circuit Panels for etching, 5/-, post free.

41. Recording Tape. 5 in. 600ft., 12/6; 5 in. 900ft., 15/-; 7 in. 1200ft., 18/6; 7 in. 1800ft., 25/-, Excellent quality.

42. Garrard Mains Single Player, 4-speed GCB head £5.9.6. P.P. 3/6.

43. D.C. to A.C. Converter. 12 volts D.C. i.e. Car Battery up to 230 volts A.C. 15 watts. Uses 2 power transistors in special circuit. Kit 57/6. P.P. 1/6.

Henry's Radio Ltd

PADDINGTON 1008/9

303 EDGWARE RD., LONDON W.2

Open Monday to Sat. 9-6. Thurs. 1 o'clock

PLEASE TURN TO BACK PAGE

Practical Wireless

BLUEPRINT SERVICE

ALL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier ...	...	...	...	...	...
The PW Signal Generator ...	...	...	...	...	...
}					
* 5/-					
The Savoy VHF Tuner ...	...	...	...	...	...
The Mayfair Pre-amplifier ...	...	...	...	...	...
}					
* 5/-					
The Berkeley Loudspeaker Enclosure ...	...	...	...	...	...
The Luxembourg Tuner ...	...	...	...	...	...
}					
7/-					
The PW Troubadour ...	...	...	...	...	...
The PW Everest Tuner ...	...	...	...	...	...
}					
6/-					
The PW Britannic Two ...	...	...	...	...	...
The PW Mercury Six ...	...	...	...	...	...
}					
5/-					
The PW Regency ...	...	...	...	...	...
The PW International Short Wave Two ...	...	...	...	...	...
}					
5/-					

RECEIVERS

The Tutor * ...	...	...	...	...	3/-
The Citizen * ...	...	...	...	...	5/-
Junior Crystal Set ...	...	...	...	PW94	2/-
Dual-wave Crystal Diode ...	...	...	...	PW95	2/6
Modern One-valver ...	...	...	...	PW96	2/6
All-dry Three ...	...	...	...	PW97	3/6
Modern Two-valver ...	...	...	...	PW98	3/6
A.C. Band-pass Three ...	...	...	...	PW99	4/-
A.C. Coronet-4 ...	...	...	...	PW100	4/-
A.C./D.C. Coronet ...	...	...	...	PW101	4/-
The PW Pocket Superhet ...	...	...	...	...	5/-

MISCELLANEOUS

The PW 3-speed Autogram ...	...	...	...	8/-
The PW Monophonic Electric Organ ...	...	...	...	8/-
The PW Roadfarer * ...	...	...	...	5/-
The PT Band III TV converter ...	...	...	...	1/6
The Mini-amp * ...	...	...	...	5/-
The PT Olympic * ...	...	...	...	7/6
The PT Multimeter * ...	...	...	...	5/-

SOME EARLIER DESIGNS

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave ...	...	PW30a	2/6
Midget Short Wave Two ...	...	PW38a	2/6
Simple S.W. One-valver ...	...	PW88	2/6
Pyramid One-valver ...	...	PW93	2/6
BBC Special One-valver ...	...	AW387	2/6
A One-valver for America ...	...	AW429	2/6
Short-Wave World Beater ...	...	AW436	3/6
Standard Four Valve S.W. ...	...	WM383	3/6
Enthusiast's Power Amplifier ...	...	WM387	3/6
Standard Four Valve ...	...	WM391	3/6
Listener's 5-Watt Amplifier ...	...	WM392	3/6

QUERY COUPON

This coupon is available until 5th July, 1963, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, JULY, 1963.

PLEASE NOTE OUR NEW ADDRESS

Just 200 yds. from our old address

Henry's Radio Ltd.

303 EDGWARE ROAD, LONDON W.2

PAddington 1008/9

Open Monday to Sat. 9-6. Thurs. 1 o'clock

NEW SUMMER CATALOGUE

54 PAGES 10½ x 7½ in.

Fully detailed and illustrated 1/6 post free

"CAPRI" POCKET-6

6-TRANSISTOR SUPERHET



Size only
4½ x 2½ x 1½ in.

**REALLY
POCKET
SIZE!**

The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red/white or blue/white with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with fully illustrated building instructions. Push-pull output coupled with sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record Socket. Full tuning on medium waves with long wave Light.

Illustrated leaflet on request.
TOTAL COST £5.19.6 P.P. 2/-.

Slip it Into your Pocket

4 WATT PEAK OUTPUT TRANSISTOR AMPLIFIER

Order Now! New design 7-transistor amplifier and pre-amplifier. Separate treble, volume and bass controls. Small size 5½ x 2½ x 2 in. Excellent quality. £5. 10. 0. P.P. 2/-. Mains Unit 50/- extra.

½ WATT 4 TRANSISTOR AMPLIFIER



Improved Version

1½ watt peak output.

± 3dB 70c/s to 12 kc/s.

Output to 3 ohm speaker
9 volt operated.

Details on request.

Built and Tested
59/6 OR 52/6
P.P. 1/6 P.P. 1/6

MULTI-METERS



PLEASE TURN PAGE

THL33. 20,000Ω/V

(Illustrated)

0/10/50/250/500/1000 v. A.C.
and D.C.
0/500μA/10/250 mA. D.C.
0/10k/1000k/1 meg. etc., etc.
Size 5 x 3½ x 1½ in.

75/-

P.P. 1/6.

ITI-2. 20,000Ω/V.

0/5/25/250/500/2,500 v. A.C./D.C.
0/50μA. 0/2½/250 mA. D.C.
0/6k/6 meg. etc.
Size 4½ x 3½ x 1½ in.

5 gns.

P.P. 1/6.

CABY MI. 2000Ω/V.

54/-

PT34. 10,000Ω/V.

0/10/50/250/500/1000 volts A.C. D.C.
0/1/100/500 mA. D.C.
0/100k etc.
Size 3½ x 2½ x 1½ in.

45/-

P.P. 1/6.

500. 30,000Ω/V.

0/½/1/2½/10/25/100/250/500/1,000 v. A.C. and D.C.
0/50μA/5/50/500 mA. 0/12 amps.
0/60k/6 meg./60 meg. etc.
Size 6½ x 4 x 2½ in.

£8.19.6

P.P. 2/-.

TP55. 20,000Ω/V.

0/10/50/250/500/1,000v. A.C./D.C.
0/50μA/0/5/50/500 mA. D.C.
0/10k/100k/1 meg./10 meg. etc.
Size 5½ x 3½ x 1½ in.

£5.19.6

P.P. 1/6.

EP50K. 50,000Ω/V.

0/10/50/250/500/1000 V. A.C. and D.C.
0/25μA/2.5/25/250mA. 0/10k/100k/1 meg./10 meg. etc. etc.
£9.19.6 Size 6½ x 4½ x 2½ in.
P.P. 2/-.

All meters supplied complete with batteries, test leads and instructions.

Brand New—Fully Guaranteed

THE "CONTESSA"

★ COMBINED PORTABLE AND CAR RADIO ★

AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS

★ The easiest Superhet Radio to build on the market. Features clearly - marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mW push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two colour Blue or Beige cabinets with Gold handles, grilles and fittings. Size 10½ x 7½ x 3½ in. includes car aerial socket, recording sockets.

★ 6 Mullard Transistors and 2 Diodes. Guaranteed the Best Obtainable

● Attractive Appearance—Reliable Design—Quality Performance ●

UNBEATABLE FOR QUALITY AND VALUE

Fully Detailed and Illustrated Leaflet on request.



TOTAL COST OF ALL PARTS

£9.19.6

P.P. 3/6

"MINIRANGER"

3-Transistor Plus 2 Diodes. Small-size radio to build yourself. Printed circuit; full tuning. ONLY 3 x 2 x 2 in. Over 20 stations. Diagrams Free.

TOTAL COST 49/6 P.P. 1/6

"QUINETT" POCKET RADIO

Diagrams Free. Size 5½ x 3 x 1½ in. 5-Transistor, plus Diode MW/LW to build.

79/6 P.P. 2/-.



BOTH MODELS AS PREVIOUSLY ADVERTISED

● ALL PARTS SOLD SEPARATELY BOOKLETS FREE ON REQUEST ●

BATTERY RECORD PLAYERS



● 6-7½ volt Garrard turntable with crystal pick-up. Plays 45 r.p.m. Ideal for amplifier on left. 55/-. P.P. 1/6

● Suitable cabinet for amplifier and player, 17/6. P.P. 2/-.

● G.C. 9 volt 45 r.p.m. and 33 r.p.m. Player, 99/6. P.P. 2/-.

● B.S.R. 9 volt 4-Speed "Hi-Grade" Turntable with turn-over Crystal Pick-up. £5.15.0. P.P. 2/6.

ORDER NOW!

10 WATT TRANSISTOR HI-FI AMPLIFIER

(As per W/W Nov. 1961)

CALL FOR DEMONSTRATION
6 Transistors and Rectifier built on to printed circuit 4 x 2½ inches. Power transistors bolted to heat plate. Sensitivity 100mV into 33 Kohm. Output 10 watts for 3 ohm speaker or 4 watts for 15 ohm. Operates from 20 to 30 volts D.C. Can be used with any pre-amp. Ideal for hi-fi unit.

£5.19.6

Mains unit 95/- extra.

Detailed book with Preamplifier Circuits 1/6 ● Use 2 for Stereo!

TRANSISTOR AND TRANSISTOR COMPONENTS SPECIALISTS