

PRACTICAL WIRELESS

OCTOBER 1964

2¹/₂

FREE inside

**TRIMMER and
ALIGNMENT SET**

**6 Tools·Bench Stand
Extension Handle**



10-TRANSISTOR DOUBLE CONVERSION RECEIVER
S-Meter B.F.O. Mains Power Unit



SOLDERING INSTRUMENTS AND EQUIPMENT



**DESIGNED FOR
THE AMATEUR'S
RADIO STATION**

ILLUSTRATED
List No. 70 $\frac{1}{8}$ " BIT
IN
PROTECTIVE
SHIELD
List No. 68

for catalogue apply direct to:—

Sales and Service Dept.,

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD, LONDON, S.W.4**

Telephones MACaulay 4272 & 3101 Telegrams SOLJOINT LONDON SW4

'SUPER SIX' TRANSISTOR RADIO KIT

NOW ONLY £4.17.6

(post 5/-)

Owing to a fortunate bulk component contract the price of this model is now reduced to £4.17.6. Purchasers who have already paid the previous higher price will have the difference refunded on application.

- All new parts.
- 6 transistors and diode.
- 350mW output.
- Superhet circuit, Ferrite rod aerial.
- Weymouth Radio printed circuit board.
- Component positions and references printed on back of board.
- Nicely styled wooden cabinet, 11 x 7½ x 3½ in.
- Vinyl covered in various colours.
- 6 x 4 in. speaker giving good bass and treble response.



- Full instruction booklet 2/-. Free with kit.
- I.F. frequency 470 kc/s.
- Lining up service if required.
- All parts supplied separately. Write for list, S.A.E. please.
- Set can be supplied fully built for £6.17.6 tax paid and carriage paid.
- 9v. battery required. VT9 or P.P.9 (3/9 with kit).

TRANSISTORS

Packet of 3 coded RF transistors (equivalent of OC44/5) 7/6 post paid. Trade supplied.
Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation. 15/- post pd.


**ELECTRONICS (Camberley) Ltd.,
15, Victoria Avenue, Camberley, Surrey.
(Closed Saturday)**

JACKSON



the big name in **PRECISION** components

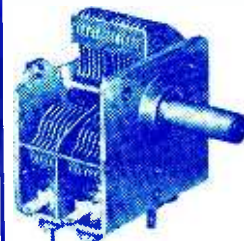Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.



"00" Twin Capacitor

The JB type "00" is designed for use in transistor portables. Aerial section 208 pF, oscillator section 176 pF. Air-spaced, robust, light and compact: 1½ x 1½ x 1½ in. deep. Also available with slow-motion drive, trimmers and oscillator section tracked for 465 kc/s I.F. in M.W. band.

JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON,
CROYDON, SURREY

Phone: Croydon 2754-5. Grams: Walfilco, Souphone, London

- all these and hundreds more

Mon.—Sat. 9 a.m.
—5.45 p.m.
Wednesday 1 p.m.
Lunch 1.30—2.30

Special 24 Hour
Express Mail
Order Service

ACS/PEN	19/6	ECC85	7/6	EY81	8/6	PABC80	13/-	T41	15/-	UM80	10/6	6A8GT	13/6	6L19	15/-	12Q7GT	6/-
AC2/PEN	19/6	ECC88	12/6	EY83	12/6	PCC84	7/-	TDD4	12/6	URIC	15/-	6AC7	6/-	6N7GT	9/6	12SA7	8/6
DD	19/6	ECC91	3/-	EY86	7/-	PCC85	9/6	TDD13C	17/6	UU6	17/6	6AK5	5/-	6P25	10/6	12SJ7	8/-
AC/TP	29/-	ECC80	7/6	EY91	3/-	PCC88	12/6			UU3	15/-	6AL5	4/-	6P28	12/6	12SK7	6/-
AC/VP1-5-7	15/-	ECC82	8/6	EZ35	6/-	PCC89	8/6	TH41	20/-	UU9	7/6	6AM5	5/-	6Q7	9/6	12SL7	8/-
	15/-	ECH3	21/6	EZ40	7/-	PCF80	7/6	TY86F	12/6	UYIN	12/6	6AM6	4/-	6Q7G	6/-	12SN7	10/-
AZ1	15/-	ECH21	21/6	EZ41	7/-	PCF82	7/6	U10	9/-	UY21	15/6	6AQ5	6/6	6Q7GT	8/6	12SQ7	12/-
AZ31	13/6	ECH35	12/6	EZ80	5/6	PCF84	12/6	U12	9/-	UY41	7/6	6AT6	6/-	6SA7	7/-	14H7	10/-
B36	9/-	ECH81	7/-	EZ91	4/6	PCF86	12/6	U14	9/-	UY85	6/-	6AU6	9/-	6SC7	8/6	14R7	21/-
CIC	10/-	ECH83	8/6	EL148	2/-	PCL82	7/6	U22	8/-	VP4	15/-	6BBG	2/6	6SF5	10/-	19AQ5	8/-
CCH35	20/-	ECL80	6/6	FC2	15/-	PCL83	9/-	U24	21/-	VP4A	15/-	6BA6	6/-	6SG7	7/-	19BG6G	15/-
CL33	12/6	ECL81	10/-	FC2A	17/6	PCL84	7/-	U25	11/-	VP4B	15/-	6BE6	6/-	6SH7	6/-	20D1	10/-
CY1	15/-	ECL82	9/6	FC4	15/-	PCL86	12/6	U26	11/-	VR105/30	7/-	6BG6G	15/6	6SK7	5/6	20D2	21/-
CY31	12/6	ECL83	10/6	FW4/500	9/-	PENA4	19/6	U31	9/-	VR150/30	7/-	6BJ6	7/-	6SK7	5/6	20F2	17/6
D77	4/-	ECL86	9/6	FW4/800	9/-	PEN4DD	22/6	U35	17/6	W61	11/-	6BQ7A	12/6	6SL7GT	5/6	20L1	22/6
DAC32	9/6	EF6	21/-	GZ30	10/6	PEN4V4	17/6	U37	17/6	W76	5/-	6BR7	10/6	6SN7GT	5/-	20P1	15/-
DAF91	5/-	EF9	21/-	GZ32	10/6			U47	11/-	W77	4/-	6BS7	12/6	6SQT	8/6	20P3	24/-
DACF6	6/6	EF22	14/-	GZ33	19/3	PEN36C	20/-	U50	7/-	W81	6/-	6BW6	9/-	6AUGT	10/-	20P4	20/-
DCC90	12/6	EF36	4/-	GZ34	13/6			U52	4/-	W81M	6/-	6BW7	9/-	6G5G	7/6	20P5	20/-
DF33	9/6	EF37	8/-	GZ37	19/3	PEN45	10/-	U73	4/6	X61M	12/6	6C4	3/6	6VG6	4/-	25A6	8/-
DF91	3/6	EF37A	8/-	HABC80	10/-	PEN45DD	25/-	U145	10/6	X65	12/6	6CSGT	8/-	6V6GT	8/-	25L6	8/-
DF92	7/6	EF39	4/-	HL41	8/-			U191	13/6	X76	12/6	6C6	6/6	6X4	4/6	25Y5	8/-
DF96	6/6	EF40	15/-	HL41DD	8/6	PEN46	5/-	U251	15/-	X76M	12/6	6C9	12/6	6X5G	5/-	25Y5G	8/-
DH63	6/-	EF41	8/-	HL92	8/6	PEN46DD	20/-	U281	15/-	X78	26/-	6CD6G	25/-	6X5GT	8/6	25Z4	7/6
DH77	7/-	EF42	10/-	HL133DD	9/6			U282	19/6	X79	40/-	6CH6	10/6	6X30L2	12/6	25Z5	8/6
DK32	11/-	EF50A	3/6			PENDD4020	20/-	U301	18/6	Y61	10/-	6C4W4	16/-	7B5	12/6	25Z6	8/6
DK91	5/6	EF50E	3/6	HN309	25/-			U329	15/-	Y63	10/-	6D2	4/-	7B7	8/-	27SL1	9/6
DK92	7/6	EF80	5/-	IW4/350	10/-	PL33	15/-	U339	13/6	Z63	7/6	6D6	5/6	7C5	8/-	30C1	12/6
DK96	7/6	EF85	5/-	IW4/500	10/-	PL33	15/-	U403	10/-	Z66	10/-	6E5	10/-	7C6	8/-	30C15	12/6
DL33	8/6	EF86	7/-	KT33C	8/-	PL36	12/6	U404	10/-	Z77	4/-	6F1	10/6	7D5	15/-	30F5	10/-
DL35	10/-	EF89	8/-	KT36	17/6	PL33	18/-	U801	19/6	Z152	5/-	6F6	5/9	7D6	15/-	30F11	12/6
DL91	7/-	EF91	4/-	KT61	12/6	PL81	7/6	UABC80	5/6	1A7	11/-	6F12	4/-	7D8	15/-	30L1	8/6
DL92	5/-	EF92	4/-	KT66	17/6	PL82	7/6	UAF42	8/6	1C5	10/-	6FL1	10/6	7H7	6/-	30L15	11/-
DL93	7/-	EF95	5/-	KT76	10/-	PL83	7/6	UB41	7/6	1D5	8/6	6FL14	10/-	7S7	17/6	30P4	18/-
DL94	7/-	EF93	10/-	KT81	8/6	PL84	8/-	UBC41	8/6	1D6	10/-	6FL15	12/6	7Y4	6/6	30P12	10/-
DL96	6/6	EF183	8/-	KTWV61	8/-	PL820	18/-	UBC81	10/-	1H5	9/6	6FL19	12/6	8D3	4/-	30P16	9/6
EA50	2/-	EF184	8/-	L63	5/-	PM24M	13/6	UBF80	7/6	1L4	5/-	6F23	10/6	8W6W	12/6	30P19	17/6
EABC80	5/6	EK32	8/6	LN152	6/6	PX4	15/-	UBF89	7/-	1N5	9/6	6F25	16/6	10C1	12/6	30PL1	15/-
EAC91	4/-	EL3	21/6	LN309	9/-	PX25	25/-	UBL21	20/-	1R5	5/-	6F26	13/6	10C2	17/6	30PL13	12/6
EAF42	9/6	EL32	4/6	LZ319	12/6	PY31	15/-	UCCB4	11/6	1S4	7/-	6F33	5/6	10F1	10/6	30PL14	12/6
EB34	2/6	EL33	12/6	MKT4	17/6	PY32	10/6	UCC85	7/-	1S5	5/-	6H6	2/-	10F9	12/6	35A5	15/-
EB41	6/-	EL34	14/-	MS4B	17/6	PY33	10/6	UCF80	12/6	1T4	3/6	6J5	5/6	10LD11	15/-	35LGT	8/6
EB91	4/-	EL35	10/-	MYS/PEN	17/6	PY80	7/6	UCH21	20/-	1U5	5/9	6J5GT	4/6	10P13	15/-	35W4	6/6
EB93	21/-	EL37	17/6			PY81	6/6	UCH42	8/6	2P	22/6	6J7	7/6	10P14	19/-	35Z3	15/-
EB33	5/6	EL38	17/6	MYS/PENB	15/-	PY82	5/6	UCH81	7/-	3A4	5/-	6J7G	5/-	10P15	23/6	35Z4	6/6
EB41	8/6	EL41	9/6			PY83	8/-	UCL82	9/-	3A5	10/6	6J7GT	7/6	12A6	6/6	35Z5	8/6
EB801	10/-	EL42	9/6	MU14	9/-	PY88	10/-	UCL83	11/6	3Q4	8/-	6K7	7/6	12AH8	11/-	41STH	22/6
EBF80	7/6	EL81	12/6	MX40	15/-	PY89	10/-	UF41	7/6	3Q5	9/-	6K7G	7/6	12AT6	7/6	42	12/6
EBF83	8/-	EL84	6/-	N18	8/-	PZ33	15/-	UF42	7/6	3S4	5/6	6K7GT	9/6	12AT7	5/-	50C5	10/-
EBF89	7/6	EL85	10/-	N37	14/-	QS95	10/10	UF80	7/6	3V4	7/-	6K8	7/6	12AU6	17/6	50CD6G	30/-
EBL1	21/-	EL90	8/6	N78	22/6	QS150	15	UF85	7/6	3U4	4/-	6K8G	4/-	12AX7	5/-	50L6	8/6
EBL21	21/-	EL91	4/-	N108	26/-			UF86	12/6	3V4G	7/9	6K8GT	9/6	12BA6	7/6	78	7/6
ECC35	8/-	EL95	10/6	N308	18/-	R2	10/-	UF89	6/-	3Y3GT	5/6	6K25	17/6	12BE6	7/6	80	7/6
ECC40	15/-	EM80	8/6	N339	30/-	R16	17/6	UL41	8/-	3Y3GT	5/6	6L1	10/-	12B7H	10/-	85A2	12/6
ECC81	4/-	EM81	8/6	N369	10/6	R19	16/-	UL44	20/-	3Z4G	7/6	6L6	7/6	12J7GT	8/6	185BT	30/-
ECC82	5/-	EM84	8/6	OD3	5/-	R20	16/-	UL46	14/6	3Z4GT	8/6	6L7	10/-	12K7GT	5/-	807A	9/6
ECC83	5/-	EM85	10/6	OZ4	5/-	SP41	3/6	UL84	6/-	6A4G	7/6	6L8	10/-	12K8GT	10/-	807B	9/6
ECC84	6/6	EY51	7/6	P2	10/-	SP61	3/6	UL85	7/6	6A8G	8/6						

COMPLETE VALVE LIST FREE WITH ORDER

METAL RECTIFIERS

RM1	7/6	14A86	23/-	16RD	2-2-8-1	12/-	(FC142)
RM2	8/-	14A97	26/-	16RE	2-1-8-1	10/-	(FC150)
RM3	10/-	14A100	28/-	13RA	1-1-8-1	5/-	(FC118)
RM4	17/6	14RA 1-2-3-221/-	(FC301)	18RA	1-1-16-1	7/-	(FC116)
RM5	19/6	14RA 1-2-8-3 25/-	(FC31)	13RD	2-2-8-1	16/-	(FC124)

TERMS OF BUSINESS C.W.O. or C.O.D.
4/2 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 6d. per VALVE

BRAND NEW TRANSISTORS

OC35	10/-	OC72	8/-	OC81D	5/-
OC42	6/-	OC74	8/-	OC81M/pr	12/6
OC44	5/-	OC75	8/-	OC82	6/-
OC45	5/-	OC77	8/-	OC82D	6/-
OC71	5/-	OC81	5/-	OC170	6/-

SILICON RECTIFIERS

400 volts 350 mA ... 7/6 each

SETS OF VALVES

IR5, IS5, IT4, 354, 3V4	Set of 4, 17/-
DAF91, DF91, DK91, DL92, DL94	Set of 4, 17/-
DAF96, DF96, DK96, DL96	Set of 4, 25/-

R.S.T. VALVE MAIL ORDER CO.

Tel: MITCHAM 6202
Open Daily to Callers

211A STREATHAM ROAD MITCHAM SURREY

LASKY'S RADIO

Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.

★ THE SKYROVER & SKYROVER De Luxe

★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THESE WELL-KNOWN SETS



The SKYROVER

Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Control. In plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle.

Can now be built for **£8.19.6 P. & P.**

H.P. Terms: 20/- deposit and 11 months, at 16/6.

The SKYROVER DE LUXE

Tone Control Circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet size 11 1/2 x 6 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Also car aerial socket fitted.

Can now be built for **£10.19.6 P. & P. 5/-**

H.P. Terms: 25/- deposit and 11 months, at 20/-. Data for each receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra.

All Components Available Separately.

A simple additional circuit provides coverage of the 1100/1350 M. band (including 1500 M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data. **Only 10/- extra Post Free**

This conversion is suitable for both models that have already been constructed.

GENERAL SPECIFICATION:

1 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 Mc. and also 4 separate switched band-spread ranges. 13M, 13M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

SPECIFICATION:

Superhet 470 Kc/s. All Mullard Transistors and Diode. Uses 4-U2 batteries, 5in. Ceramic Magnet P.M. Speaker Easy to read Dial Scale. Band Spread Tuning. 500 MW Output. Telescopic Aerial & Ferrite Rod Aerial. WAVEBAND COVERAGE: 130-576Mc. 31-94Mc and Band Spread on 13, 16, 19 and 25 metre Bands.



The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker.

★ All components mounted on a single printed circuit board, size 5 1/2 x 5 1/2 in. in one complete assembly.

★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey.

★ Easy to read dial.

★ External socket for car aerial.

★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. ★ All coils and I.F.'s etc. fully wound ready for immediate assembly.

★ An Outstanding Receiver. **LASKY'S PRICE for the complete parcel including Transistors, Cabinet, Speaker, etc. and Full Construction Data. Can be built for £5.19.6 P. & P. 4/6**

PP9 Batt. 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.

REALISTIC Seven DE LUXE

With the same specification as standard model PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial.

FOR ONLY £1 EXTRA P. & P. as std. model

RECORD PLAYERS



45 r.p.m. 6 volt Batt. operated. Complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 1/2 in. Fitted auto. stop and start. New and perfect.

45 r.p.m. Model **49/6 P. & P. 2/6**

2 speed model for 33 and 69/6 P. & P. 45 r.p.m. (as illustrated). **2/6**

DEAC RECHARGEABLE NICKEL CADMIUM CELLS



Rating 1.22 v. 3.5 AH at 10 hour rate. 1001 uses for model makers, miniature electronic equipment, portable radios and tape recs., trans receivers, photo flash etc. Hermetically sealed. Size 3 1/4 x 1 1/2 in. Listed at 35/- each.

LASKY'S PRICE 15/- Post Free Bank of 9 79/6

TRANSISTORISED TELEPHONE AMPLIFIER

Powerfully amplifies the incoming call. The pick-up is suction fixed to 'phone. Battery-operated at negligible cost. Fitted with on/off switch and vol. control. Size: 4 1/2 x 3 x 1 1/2 in. Complete with PP3 battery. **LASKY'S PRICE 69/6 P. & P. 2/6.**

GUITAR PICK-UPS

CGM5 Crystal-high imp. Size only 1 1/2 x 1 1/2 in. Clips to finger board—no screws. Complete with cable.

LASKY'S PRICE 15/11 P. & P. 1/- CGM35. Fully adjustable pick-up position carrier. Simply fixed. Separate tone and volume control. Heavy chrome finish. Pick-up size 3 1/2 x 1 1/2 in., control size 2 1/2 x 1 1/2 in. Complete with long lead and jack plug. **LASKY'S PRICE 59/6 P. & P. 1/6**

The "Sixteen" Multirange METER KIT

This outstanding meter was featured by Practical Wireless in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer.

RANGE SPECIFICATION: D.C. volts: 0-2.5-25-50-250-500 at 20,000 Ω/V . A.C. volts: 0-25-50-250-500 at 1,000 Ω/V . D.C. current: 0-50 μA , 0-2.5-50-250 mA. Resistance: 0-2,000 Ω , 0-200k Ω , 0-20M Ω . Basic movement: 40 μA f.s.d. moving coil. With universal shunt full scale deflection current is 50 μA . Size/finish: Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot, meter; meter zero. External connections: Two 5mm. sockets for test lead plugs. Power requirements: One 15V. and one 1.5V. batteries. Complete with all parts and full construction details.

Data and circuit available separately 2/6 refunded if all parts bought. Pair of Batteries, 2/5 extra.

LASKY'S PRICE £5.19.6

P. & P. 5/-

H.P. Terms: 21/- deposit and 5 months at 21/-

NEW SUPER MINIATURE POCKET RADIOS



THE SINCLAIR MICRO-6

A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. Can be built for only **59/6**

THE SINCLAIR SLIMLINE

Micro alloy transistorised and printed circuit. All components available separately

Self-contained pocket radio Size only 1 1/2 x 1 1/2 x 1 1/2 in. Truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. Can be built for only **59/6**


The new 2-transistor pocket radio size only 2 1/2 in. x 1 1/2 x 1 1/2 in.

Easy to assemble. **CAN BE BUILT FOR 49/6**

E.M.I. 4-SPEED RECORD PLAYER

New, unused and individually boxed fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13 1/2 x 12 1/2 x 4 1/2 in. A 9in. metal turntable is fitted. For use on 200/250 volt A.C. Mains, with Auto-stop. The stereo cartridge will play all types of Mono Records, 78's, L.P.s etc., but if desired a G.P. 67 LP/78 Mono cartridge will be supplied in lieu of the G.P. 73 at no difference in cost.

LASKY'S PRICE 79/6 P. & P. 3/6 extra.

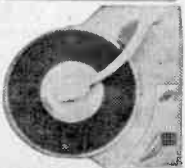

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS • RECORD PLAYERS • AMPLIFIERS ETC.
COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.

TRANSISTORISED



MICROPHONE MIXER

The Harrow will mix 4 high impedance channels: mikes, tape rec's, tuners, gram, etc. 9 v. battery operated. Neatly styled, size only 6 x 2 1/2 x 2 1/2 in. Standard Jack sockets. Complete with PP3 batt., full circuit diagram and operating instructions.

Model TM4 Mono 59/6 P. & P. 2/6

Model SM5 Stereo 72/6 P. & P. 2/6

SPEAKERS SPECIAL OFFER 12in. FANE HEAVY DUTY DUAL CORE HI-FI SPEAKER

Type 122/17A—listed at 12 gns.
Power handling 25 watts—15 ohms imp. Flux density 17,000 gauss. Special Anisotropic magnet. Limited stock.



LASKY'S PRICE £6.19.6
P. & P. 5/-

TYPE 8CX1 8in. HI-FI SPEAKER.
Power handling 10 watts—15 ohms impedance.
LASKY'S PRICE 6 Gns. P. & P. 5/-

THE HARROW CV1 VARIABLE CROSSOVER

Gives variable volume control of Woofer and Tweeter. Strong metal construction. Size 4 x 2 1/2 x 1 1/2 in. Screw tag connections.
LASKY'S PRICE 22/6 P. & P. 1/6

THE NEW STUDIO RANGE OF CELESTION HI-FI SPEAKERS NOW IN STOCK

"HARROW" POWER PACK
Battery eliminator—converts your battery portable to A.C. mains. Replaces 6 v., 4 1/2 v. or 9 v. batteries. State voltage required when ordering. Size only 3 x 2 x 2 1/2 in.
LASKY'S PRICE 29/6 P. & P. 1/6


LAFAYETTE TAPE

Famous American Brand—Fully Guaranteed

5in. Double play, 1,200ft., Mylar base....	15 0
5in. Long play, 900ft., Acetate base.....	10 0
5in. Standard play, 600ft., P.V.C. base....	8 6
5 1/2in. Long play, 1,200ft., Mylar base.....	15 0
5 1/2in. Double play, 1,200ft., Mylar base....	22 6
5 1/2in. Long play, 1,200ft., Acetate base....	12 6
5 1/2in. Standard play, 850ft., P.V.C. base....	11 6
7in. Standard play, 1,200ft., Mylar base....	12 6
7in. Long play, 1,800ft., Mylar base.....	19 6
7in. Double play, 1,800ft., Mylar base.....	25 0
7in. Long play, 1,800ft., Acetate base.....	15 0
8in. Message tape, 150ft.....	3 6
8in. Message tape, 225ft.....	4 11
8in. Message tape, 300ft.....	7 6
8in. Triple play, 450ft., Mylar base.....	12 6
8in. Triple play, 900ft., Mylar base.....	22 6
8in. Triple play, 1,800ft., Mylar base.....	42 6
8 1/2in. Triple play, 2,400ft., Mylar base.....	55 0
7in. Triple play, 3,600ft., Mylar base.....	75 0

P. & P. 1/- extra per reel; 4 reels and over Post Free

THE NEW "KUBA" CONTINENTAL AM/FM

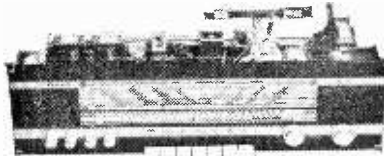


STEREO RADIOGRAM CHASSIS

Long, medium and short waveband coverage plus VHF/FM. Piano key wave-change. Separate flywheel tuning on AM and FM. Bass, treble and balance controls. Magic-eye tuning indicator. Ferrite rod aerial. The very latest printed circuitry. Provision for multiplex adaptor. 5 valves—line-up: ECC85, ECH801, ECC83, ELL80, 6AF601. Full vision tuning scale size 2 1/2 x 6 1/2 in. Overall dimensions: 21 x 6 1/2 x 8 1/2 in. Made to the very highest standards.

LASKY'S PRICE 29 1/2 GNS.

Carriage & Insurance 12/6 extra.

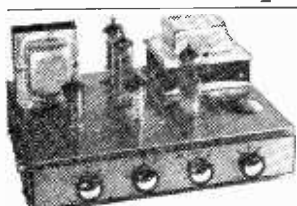

THE BH-14 HI-FI MONO 14 WATT AMPLIFIER KIT

High quality 14 watt output power amplifier with bass, treble and separate volume controls on each input. Inputs: 1—5 mV; 2—40 mV. Output impedance 8 or 15 ohms. 5 valves—line-up: 2 x EL84, 1 x ECH83 and EZ81. Frequency response 15 c/s—20 Kc/s. Ideal for the discerning hi-fi enthusiast or for guitar amplifier. Gold hammer finish with distinctive Perspex front panel. Complete kit of parts with detailed construction data.

LASKY'S 9 GNS. 7/6. avail. acc. 1/6.
AVAILABLE READY BUILT AND TESTED.
LASKY'S PRICE 11 GNS. P. & P. 7/6.

AUTOCHANGER SCOOP!!!

**LASKY'S CAN NOW OFFER B.S.M.
AUTOCHANGERS AT LOWEST EVER PRICES**



All brand new and fully guaranteed—complete with cartridge and stylus.

UA14.....	£3.19.6
UA16 4 speed, mains.....	£4.19.6
UA14 4 speed, 9 v. battery operated.....	£5.19.6
UA20 4 speed.....	£5.19.6

Add 5/- P. & P. on each.

IT'S FABULOUS!! THE TRANSISTOGRAM

A portable battery operated fully transistorised Record Player for the music of your choice—any time and place! Made by famous British manufacturer, fully guaranteed. Size only 6 1/2 x 12 x 10 1/2 in., weight 10 lbs. Operates on 6 U2 torch batteries. 4 speeds—16 2/3, 33 1/3, 45 and 78 r.p.m. Goldring Nymet record player unit with lightweight pick-up fitted with CM-80 turnover ceramic cartridge. Output 500 mW to 5in. ceramic magnet loudspeaker, fitted into lid for maximum sound distribution. Cabinet constructed of wood, covered in two tone (pale blue-grey) leathercloth. Fitted carrying handle and strong lid catches. High quality amplifier with tone and volume controls gives excellent reproduction at all speeds. Plays 7, 10 and 12in. records. Today's value 12 Gns.

LASKY'S PRICE £6.19.6

Carriage & Insurance 7/6
New, boxed and guaranteed—exc. batts

CRYSTAL PICK-UP CARTRIDGES LOWEST EVER PRICES!

All Complete with Stylus L.P. and Standard (and Stereo where shown) fully guaranteed. Standard Fitting will fit most P.U. Arms and Heads. Postage 1/- each extra.

Acostereo 73/2, Diamond LP/Stereo and		MONO	
Ronette Stereo 80 v. Turnover, 2 sapphires, 25 0		Garrard Magnetic T.O.M.2.....	15 0
Ronette Stereo type 105 and 106, 2 sapphires 25 0		Acos GP.59.....	14 0
Ronette Stereo type 105 and 106 Diamond		Acos GP.65/3.....	15 0
LP/Stereo and sapphire Std.	35 0	Acos GP.65/1.....	17 0
STEREO		AND EVEN LOWER PRICES!	
Acostereo 73/1, 2 sapphires.....	25 0	Acos GP.67/1.....	14 0
Mono C.T.1.....	4 11	Sonotone ST, stereo.....	19 11
Collaro Type C, 2 sapphires, stereo.....	15 0	Sonotone 2FA, mono.....	15 0
Collis S.C.1, Diamond LP/Stereo.....	17 6	Postage 1/- each extra.	

207 EDGWARE ROAD, LONDON, W.2.

Near Praed St. PADDINGTON 3271/2

BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd.

33 TOTTENHAM COURT ROAD, W.1.

Nearest Stn., Goodge St. MUSEUM 2605

152/3 FLEET STREET, LONDON, E.C.4.

Telephone: Fleet Street 2838

Open all day Thursday. Early closing Sat

LASKY'S FOR SPEEDY MAIL ORDER SERVICE



CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters, available ex-stock S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows. Type MR. 38P 21/2in. square fronts.

50μA	32/6	1A. DC	22/6
100μA	29/6	5A. DC	22/6
200μA	27/6	3V. DC	22/6
600μA	25/-	10V. DC	22/6
50-0-500μA	29/6	20V. DC	22/6
100-0-100μA	27/6	50V. DC	22/6
500-0-500μA	22/6	100V. DC	22/6
1-0-1mA	28/6	150V. DC	22/6
5mA	22/6	500V. DC	22/6
1mA	22/6	300V. DC	22/6
10mA	22/6	750V. DC	22/6
50mA	22/6	15V. AC	22/6
100mA	22/6	50V. AC	22/6
150mA	22/6	150V. AC	22/6
200mA	22/6	300V. AC	22/6
300mA	22/6	500V. AC	22/6
500mA	22/6	8's Meter	
750mA	22/6	1mA	29/6

Type MR. 38P	31 x 3 1/2 in. fronts.
50μA	57/6
100μA	47/6
500μA	37/6
50-0-50μA	57/6
100-0-100μA	47/6
300V. AC	38/6
1mA	39/6
Type MR. 65P	3 1/2 x 3 1/2 in. fronts.
50μA	59/6
100μA	49/6
500μA	39/6
50-0-50μA	59/6
100-0-100μA	49/6
300V. AC	35/-
VU Meter	59/6
300V. AC	35/-
Type MR. 65P	4 x 4 in. fronts.
50μA	69/6
100μA	59/6
200μA	55/6
500μA	49/6
50-0-50μA	69/6
100-0-100μA	59/6
500-0-500μA	49/6
300V. AC	45/-
1-0-1mA	45/-

Post extra



BAKELITE PANEL METERS

First grade quality. 3 1/2 in. square fronts.

25μA	65/-	100mA	29/6
50μA	42/6	1A. DC	29/6
100μA	39/6	5A. DC	29/6
500μA	35/-	10A. AC	29/6
50-0-50μA	65/-	50A. AC	29/6
100-0-100μA	39/6	100A. AC	29/6
50mV	39/6	30A. AC	29/6
100mV	39/6	60A. AC	29/6
1mA	29/6	300V. DC	29/6
5mA	29/6	300V. AC	29/6
10mA	29/6	300V. AC	35/-
50mA	29/6	VU Mtr.	49/6


*Moving iron. All others moving coil.

ILLUMINATED 1/2" METERS
Cal. in '8' units. 1mA Basic. 1/2" sq. frnt 29/6 P. & 1/2". 1/2" sq. frnt 38/6 P. & 1/2".

MORE METER BARGAINS
100μA 6in. Flush sq. 92/6
100μA 2 1/2 in. Flush rd. 42/6
500μA 2 1/2 in. Flush rd. 22/6
1mA 2 1/2 in. Flush rd. 22/6
30-0-30mA 2 1/2 in. Flush rd. 9/6
300mA R.F. 2 1/2 in. Flush rd. 25/-
300V. AC 2 1/2 in. Flush rd. 25/-
500V. AC 2 1/2 in. Flush rd. 25/-
1mA Meter Rectifiers 8/6

Please add postage

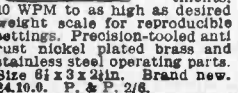SEMI AUTOMATIC BUG KEY
Super speed key. 7 speed adjustments. 10 WPM to as high as desired weight scale for reproducible settings. Precision-tooled anti rust nickel plated brass and stainless steel operating parts. Size 8 1/2 x 3 x 2 1/2 in. Brand new. £4.10. P. & P. 2/6.



NEW FROM LAFAYETTE

HA-63 COMMUNICATION RECEIVERS



S.A.E. for leaflet. Part exchanges.

De luxe 7 valve plus metal rectifier communication receiver covering 550 Kc/s-30 Mc/s on 4 bands. All usual facilities including 'B' meter, bandspread tuning, B.F.O., noise limiter, etc. Output for speaker or phones. Operation 220/240 volt A.C. Supplied brand new and guaranteed with manual. Carr. £27.10.0



LAFAYETTE "PRECON" AMATEUR PRESELECTOR CONVERTER

★Crystal Controlled ★For 30-40-20-15-10 Metre Bands ★As a converter—converts your receiver to dual conversion ★Improves selectivity ★Widens bandspread ★High signal to noise ratio ★Improved image rejection ★Self powered ★Modern styling
★80, 40 Metres preselector only. 20, 15 and 10 metres preselector and converter. GAIN: Preselector 35dB at 3.5-3.85 Mc/s on 20M. Band. 3.5-3.95 Mc/s on 15M band. 3.5-5.2 Mc/s on 10M band. VALVES: 2-48A6, 1-6BL6. CONTROLS: Aerial trimmer, function, bandswitch, gain. Two stages of R.F. AMP. Sensitivity and stability excellent. 3 crystals are included for 20, 15 and 10M Bands. SIZE: 10" x 6" x 8". Operation 220/240V A.C. 19 gns. Carr. 7/6. S.A.E. for full details.



LAFAYETTE PRECISION TEST EQUIPMENT

Modern range of precision test equipment for the service man. Supplied brand new and guaranteed with manual. For operation on 220/240 volts A.C.

TS-20 Signal Generator. 120Kc/s-200Mc/s on 8 Bands. Directly calibrated. Variable R.F. Attenuator. Variable audio output. £12. Carr. 5/-.

TS-46 Capacity Resistance Analyser. Ranges 2pF-2,000mF; 2 ohms-200 Megs. Also checks impedance, turns ratio, insulation. £15. Carr. 5/-.

30,000 O.P.V. TEST METER MODEL 500

Reads volt-ages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 o.p.v.; D.C. current to 12 amps. Resistance to 60 Megs; Decibels from -20 to +68. Incorporates internal buzzer for audible warning of direct shorts and blocking condensers for A.F. output measurements. Size 3 1/2 x 5 1/2 x 8 1/2 in. PRICE £28.17.6.



ERSKINE TYPE 13 DOUBLE-BEAM OSCILLOSCOPE

Time base 20/s-750Kc/s. Calibrations at 100Kc/s and 1Mc/s. Separate Y1 and Y2 amplifiers up to 5.5Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £27.10.0. Carr. 20/-.

TRIPLITT SIGNAL GENERATOR 1632

10 RANGES: 100Kc/s-120Mc/s on fundamentals. Six valves, stabilised H.T. FULLY ATTENUATED OUTPUT. 100 uamp carrier level meter. 1Mc/s xtal check. Operation 115V. A.C. Supplied in perfect working order. £12. Carr. 10/- (230/115V. Transformer 12/6 extra.)

OSCILLOSCOPE OS-57 USM-38

Brand new high quality American oscilloscopes incorporating 3in. tube, printed circuit and miniature valves. Time base 1, 10, 100 1K and 10Kμs/in. Calibration markers 1, 10 and 100μs. Calibrated Y input volts. X expansion, sweep stability. Operation 115 V.A.C. Supplied brand new, fully tested with test leads, probe and circuit diagram. £29.10.0 each. Carr. 10/- (230/115V. Transformer 18/6 extra.)

MODEL PV-58 VACUUM TUBE VOLTMETERS

Latest design with special circuit for stable and accurate measurements. Resistors used are all within 1% tolerance. Specially designed sin. 200μA meter. 11 meg inputs. Ranges:

-D.C. V.	0-1.5-5-15-50-150-500-1500V
+D.C. V.	0-1.5-5-15-50-150-500-1500V
A.C. V.	0-1.5-5-15-50-150-500-1500V RMS
	0-1.4-4-14-40-140-400-1400-4000 P.

Resistance: 2 ohm to 1,000 megohm.

Decibels: -10dB to +65dB. Operation 220/240 volt A.C. Size 7 x 4 1/2 in. Supplied brand new and guaranteed complete with probe and instructions. £13.19.6 P.P. 3/6.

CHASSIS PUNCH SET

Set of 5 popular size hole cutters 1", 1 1/8", 1 1/4", 1 1/2", 1 3/4". Complete with punches, dies, T drive handle, tapered reamer. Nitrid leather case and instructions 49/6. P. & P. 2/-.

PLUGS AND SOCKETS

Fainton 15 pin in-line printed circuit connectors. 7/8 pair. Large quantities available. Ditto 32-pin. 12/6 pair. Unites: 4-pin. 2/6 pr; 8-pin 3/6 pr; 12-pin. 4/6 pr; 18-pin. 4/6 pr. Push-on Miniature Joints: 4-pin. 3/6 pr; 8-pin. 4/6 pr; 8-pin. 4/6 pr; 18-pin. 7/6 pr; 24-pin. 10/6 pr; 33-pin. 12/6 pr. Post extra.

L.T. METAL RECTIFIERS

FULL wave bridge connected. 12/18V 1A 3/8 23/36V 1A 7/8 12/18V 2A 6/8 24/36V 2A 13/8 12/18V 4A 1/8 24/36V 15A 55/8 12/18V 10A 22/8 Post extra

L.T. TRANSFORMERS

For chargers, models etc. All primaries tapped 200/250V. (1) 3.5, 9 or 17V., 1 amp. 9/8; (2) ditto 2A., 14/3; (3) ditto 4A., 18/6; (4) ditto 6A., 22/8; (5) 3A., 6, 9, 10, 12, 15, 18, 24 or 30V., 2 amp. 18/6; (6) ditto 4A., 30/-; (7) ditto 5A., 37/8; (8) 50V. 1 amp. 13/8; (9) 50V. 1 amp. 15/6. Post extra.

AUTO TRANSFORMERS

step up or step down. Tapped 0/115/200/230/250V. 20W. 9/-; 16W. 12/6; 75W. 15/6; 150W. 19/6; 200W. 27/6; 300W. 42/6; 500W. 67/8; 1,000W. 90/-; 1,500W. £6.19.6 3,000W. £7.10.0. 7,500. * £15 (* only tapped 0/110/230V). Post extra.

PETTIMAX 9 VOLT

BATTERY ELIMINATOR
220/240V A.C. Same size as PP3. 15/6. P.P. 1/3.

SUBSTITUTION BOXES

Resistance—24 ranges .. 27/6
Capacitance—9 ranges .. 19/6
Post 1/6 extra.

LAFAYETTE HI-FI STEREO HEADPHONES

Air Cushioned headband, 4 in. rubber foam pads, freq. response 25-15,000 cycles. High sensitivity, impedance 8 ohms per phone. Supplied complete with all cables, wires, overload junction box and 3-conductor plug. 89/6. P. & P. 2/6.



Type "L". Two line connection. Generator bell ringing. Complete telephone intercom. Supplied in excellent condition, fully tested and complete with batteries. Only 99/6 per pair. Carr. 5/-.

Type "H". As above but moulded in bakelite case (as illustrated). Supplied complete with wooden transit case for field use. £4.19.6 per pair. Carr. 5/-.


TELEPHONES TYPE H

Sound powered, generator bell ringing 2 line connection. Fully tested. £4.18.6 pair. Carr. 5/-.

G. W. SMITH & CO. (RADIO) LTD.
3 & 34 LISLE STREET, LONDON, W.C.2.

SEE OPPOSITE PAGE

TM-59 'er 'S' METER

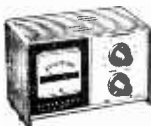

Signal strength meter using VTVM principles. Calibrated in S units. Sensitivity and zero adjustments. For any superhet receiver with AVC. Requires 150/200V. and 6 or 12V. Complete with valve and full instructions. 82/6. P.P. 2/6.

MAINS ISOLATION TRANS.

230V. to 230V. 50W. 16/6. P.P. 3/-; 100W. 29/6. P.P. 3/6; 1,000W. 25. Carr. 10/-.

MINIATURE LEAD ACID ACCUMULATORS

Brand new. 2V. 1.5A. 4x1x1 1/4in. 5/6. P.P. 1/3. 12V. 0/75. A 4x3x1 1/4in. 15/6. P.P. 1/3.

MARCONI TF146/4 STANDARD SIGNAL GENERATORS

First release of this latest mark. 85Kc/s to 2Mc/s +1%. Output variable from 1uV to 1 volt. Internal sine wave modulation 400c/s up to 75% depth. Operation 200/250 volt A.C. Offered in really excellent condition, like new, fully tested and guaranteed. £25. Carr. 30/-.

HEAVY DUTY POWER SUPPLIES
Input 200/250 volt A.C. Three H.T. outputs 2 x 400V. 175mA and 350V. 220mA. All fully smoothed. 2 x 6.3V. 5 amp. 6.3V. 4 amp. 12V. 0.5 amp. Supplied in perfect condition. £5.10.0. Carr. 20/-.

PRECISION PORTABLE VOLTMEETERS

Polished wood case. 8in. scale with knife edge pointer. A.C. and D.C. volts; 0-100 volts. 59/6; 0-100-320 volts. £5.18.6. P.P. 3/6.

TWIN MOTOR BARGAIN
200/250V. A.C. Twin concentric spindles. Either motor reversible. 14000 r.p.m. Brand new. 12/6. P.P. 2/6.

VARIAC TRANSFORMER
240V. P.P. 230V. Sec. 185/250V. £12.10.0. Carr. 10/-.

MAINS MOTORS 220/240V
90 watts. 5,000 r.p.m. 4 1/2 x 3 1/4in. spindle 22/6. P.P. 2/-.

GEARED SLIDER RHEOSTAT
12 ohms 12 amp. 15/6. P.P. 3/6.

R.C.A. HEADSETS
Low imp. Fitted with std. jack plug. 15/6. P.P. 1/6.

DESK TELEPHONES
Std. type with handset and bell. No dial. Unused. 25/- P.P. 3/6.

ROTARY TRANSFORMERS
12V. D.C. input. Output 310/360V. D.C. 30mA. New boxed. 10/- P.P. 2/-.

COLLARO MAGNAVOX. STUDIO TAPE TRANSCRIPTOR


Brand new. 3 speeds. 1 1/2, 3 1/2, 7 1/2 p.s. 3 motors, digital counter. Complete with instructions. 4 Track. £10.10.0; 4 Track. £13.10.0. Carr. Paid.

HEADSET & BOOM MICROPHONE
American type, low impedance. padded. 49/6. P.P. 2/6.

BEST BUY!
Send 1/- P.O. for full catalogue and lists.
Open 9 a.m. to 8 p.m. Every day. Monday to Saturday. Trade supplied.

PRICE SLASHED!

LAFAYETTE COMMUNICATION RECEIVERS

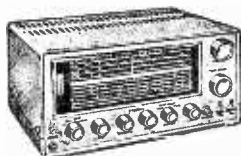

Superlative range of Modern Communication Receivers incorporating many special features at prices to suit every pocket

MODEL HE-40 4 Bands, £19.19.0 Carr. 15/-

550Kc/s to 30Mc/s. MODEL HE-30 9 Valves £35. 0.0 Carr. 15/-

4 Bands. 550Kc/s to 30Mc/s. MODEL HE-80 15 Valves, £52.10.0 Carr. 15/-

5 Bands. 550Kc/s-30Mc/s and 142-148Mc/s.

Each receiver supplied brand new and fully guaranteed complete with manual. All models for operation on 220/240 Volt A.C. S.A.E. for illustrated leaflet. Generous part exchange allowances.

TE-20A R.F. SIGNAL GENERATOR



A precision signal generator of extremely high accuracy and quality. Six ranges from 120Kc/s to 130Mc/s on fundamentals with calibrated harmonics from 120-380 Mc/s. 400 cps. INT. MOD. OR EXT. MOD. OUTPUTS MOD. RF. UNMOD RF. or 400 c/s audio. RF. output in excess of 100 mv. Large clear 5 inch dial. Handsome grey metal case with handle. Size 7 1/4 x 10 1/4 x 4 1/4in. Complete with leads. Operation 220/240 volts A.C. Supplied brand new and guaranteed £12.19.6. Carr. 5/-.

MAINS RECORD PLAYERS & AUTOCHANGERS

HALL GUARANTEED WITH ARM AND CARTRIDGE
GARRARD SRP-10 PLAYER £4.17.6
GARRARD AUTOSLIM CHANGER £6. 9.6
GARRARD AT6 CHANGER MONO £10. 8.6
GARRARD AT6 CHANGER STEREO £10.19.6
GARRARD 4 H/F MONO £14.19.6
GARRARD 4 H/F STEREO £15.15.0
GARRARD TYPE A CHANGER £17.15.0
GARRARD 301 STROBO. NO ARM £19.10.0
B.S.R. GU7 SINGLE PLAYER £4. 7.6
B.S.R. UA16 CHANGER £6.12.6
B.S.R. UA15 NEW SLIMLINE CHANGER £6.19.6
POSTAGE EXTRA

LONDON AGENTS FOR CODAR EQUIPMENT

MULTI-METERS



Brand New—Fully Guaranteed. Lowest ever prices. Supplied with leads, batteries and instructions.

MODEL PT-34. 1,000 o.p.v.
0/10/50/250/1,000V. A.C. and D.C.
0/100/500 mA D.C.
0/100KΩ
39/6. P.P. 1/6.

0/2K/200K/2 MegΩ

100pF—2mF

79/6. P.P. 2/6.

MODEL AR-620

20,000 o.p.v.

0/10/50/250/500/1,000V.

AC and DC

0/500μA/10/250mA

0/10K/100K/1 MegΩ

250pF—0.2mF

0-500 Henrys

92/6. P.P. 2/6.

MODEL NH-201

30,000 o.p.v.

0/25/110/50/250/500/

1,000V. DC

0/10/50/250/500V. AC

0/5μA/10/250mA

0/5K/500K/5 MegΩ

99/6. P.P. 2/6.

MODEL ITI-2

20,000 o.p.v.

0/5/25/250/500/2,500V.

DC

0/10/50/500/1,000V. AC

0/50μA/25/250mA DC

0/50K/5 MegΩ

0.1—3mF

82/6. P.P. 2/6.

MODEL 250J

2,000 o.p.v.

0/10/50/500/2,500V. DC

0/10/50/500/2,500V. AC

0.2 MegΩ

0/250mA

—20 to +36db

49/6. P.P. 2/6.

TWO-WAY RADIOS

New improved "LAFAYETTE" Models.

Type 1. 3 transistor. Range up to 1 mile. £8.17.6 per pair.

Type 2. 9 transistor. Range up to 5 miles. £21 per pair.

Postage extra. S.A.E. for full details.



LAFAYETTE BRAND RECORDING TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

3in. 200ft. L.P. mylar 4/-
3 1/2in. 600ft. T.P. mylar 10/-
5in. 600ft. std. plastic 8/6
5in. 900ft. L.P. acetate 10/-
5in. 1200ft. D.P. mylar 15/-
5 1/2in. 1200ft. L.P. acetate 12/6
5 1/2in. 1800ft. D.P. mylar 22/6
7in. 1200ft. std. mylar 12/6
7in. 1800ft. L.P. acetate 15/-
7in. 1200ft. L.P. mylar 20/-
7in. 2400ft. D.P. mylar 25/-
Postage 2/- Over £3 post paid.

BRAND NEW R.C.A. AR88B RECEIVERS

Unboxed £85; Boxed with spare valves, copper aerial, headset, and manual. £85. Carr. 30/-.

VARIABLE VOLTAGE TRANSFORMERS

Pri. 230V. Sec. 0-250V. 1 amp. £4.10.0; 2 amp. £5.17.6; 5 amp. £9. 8 amp. £14.10.0; 10 amp. £16.10.0; 12 amp. £18.15.0; 20 amp. £32.10.0. All fully shrouded.

CHAMOUX PADDED MOVING COIL HEADPHONES

Canadian noise excluding type. Complete with M/C microphone. New boxed, 25/- P. & P. 2/6.

Brand New Double Beam CRT's
Cossor 88D. 59/6.
Dumont K1051P1. 59/6. P.P. 4/6.

SILICON RECTIFIERS

400 P.I.V. (SCR) 4 1/2 amp 7/6
200 P.I.V. 6 amp 5/6
1,000 P.I.V. 650mA 7/6
800 P.I.V. 500mA 5/6
200 P.I.V. 200mA 3/6
400 P.I.V. 600mA 3/6
150 P.I.V. 165mA 1/-
70 P.I.V. 1 amp 3/6
95 P.I.V. 3 amp 5/6

Post extra.

MINIATURE HIGH SPEED COUNTERS

4 Digit available. 6V. 24V. or 50V. ALL 7/6 ea. P. & P. 9d.

NEW LOW IMPEDANCE HEADSET

Latest Ministry Type. Rubber moulded. Fitted with Std. Jack Plug. Brand New. boxed. 17/6. P. & P. 1/6.

4-CHANNEL TRANSISTORISED MICROPHONE MIXER

Add musical high-lights and additional sound effects to your recordings.

The MM-4 permits mixing of four signals such as microphone, records, tuner, etc. into single output. Input and output take standard plugs. Fully transistorised and self contained in handsome case.

PRICE 55/-. P. & P. 2/6.



G.W. SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C2

SURBITON PARK RADIO LTD.

ALL ORDERS DESPATCHED SAME DAY • WE PAY POSTAGE and INSURANCE
MONEY REFUND GUARANTEE

LEADING STOCKISTS OF MARTIN RECORDAKITS AND AUDIOKITS

MARTIN RECORDAKITS

HALF TRACK
TAPE AMPLIFIER FOR STUDIO DECK with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plans, screws etc. EF86, EOC83, EZ80, EM86 and 2 EL84. 3 watts output. Magic eye. Radio and Mic. inputs, ext. speaker socket, tone and monitor controls. Can be used as an amplifier. **£11.10**
COLLABO STUDIO DECK. Very latest model. 3 speeds, 3 motors, 7-inch spools. **£10.19.6**
CASE for above with 8 x 5in. speaker, two tone grey **25. 5.0**
COMPLETE KIT with tape and microphone **£29.19.6**

QUARTER TRACK

TAPE AMPLIFIER FOR STUDIO DECK as described above but Quarter track **£12.12.0**
COLLABO STUDIO DECK fitted with Marriot "X" heads **£13.19.6**
CASE with speaker, two tone grey **25. 5.0**
COMPLETE KIT with tape and microphone **£23.19.6**
TAPE PRE-AMPLIFIERS **£11. 8.0**
HALF TRACK FOR STUDIO deck, 400mV/Volts output **28. 8.0**
QUARTER TRACK as above **£9. 9.0**

MARTIN AUDIOKITS

The new Martin All Transistor TEN WATT AMPLIFIER kits represent excellent value for money. Each unit is complete, requiring only to be connected to the next. We show only the popular units here. Others are available. Please leaflet upon request.

UNIT 1—FIVE INPUT SELECTOR. Size 3 1/2 x 5in. Mag. P.U., Crystal P.U. Radio, Mic. Tape head 18 volts. Must be used with Unit 4. **£2. 7.6**
UNIT 4—PRE-AMPLIFIER AND CONTROL. 6 1/2 x 2 1/2in. Volume on/off. Bass and Treble controls. 18 Volts. Must be used with Unit 1. **£3. 2.6**
UNIT 7—MAIN AMPLIFIER. 10 watts, 6 Transistor transformerless PUSH PULL output. Mounted on heat sink, 15 ohm output 40 volts. **£6.12.6**
UNIT 8—POWER SUPPLY. 18 and 40 volts. Heavy duty transformer, rectifier and smoothing. **£2.15.0**
CONTROL PANEL for Units 1 and 4. **10.8**
ALL FOUR ABOVE UNITS WITH PANEL. 15 ohms output. **£15. 8.0**
UNIT 5—MAIN AMPLIFIER as Unit 7, 3 ohms output. 24 volts. **£5.12.6**
UNIT 6—POWER SUPPLY as Unit 8, for use with Unit 5. **£2.12.6**
ALL FOUR UNITS 1, 4, 5 and 6 WITH PANEL **£14. 5.0**

STEREO VERSIONS NOW AVAILABLE
LEAFLET ON REQUEST

GRAMOPHONE UNITS, MOTORS, PICK-UPS

Decca DREAM Arm and Plug-in Shell **25. 5.0**
Decca DREAM Transcription Cartridge **24.14.6**
Decca DREAM Auto cartridge **23.13.6**
GARRARD SRP10 with Mono cartridge. Single player **25.9.11**
B.S.R. UA14 with TCS mono cartridge, 4 speed Auto-changer **£6.19.6**
GARRARD AUTOSLIM, Mono cartridge, 4 speed changer **£7.17.0**
GARRARD AT6 Autoslim de Luxe. Mono cartridge **£11. 8.0**
GARRARD 4H/F with Mono cartridge **£17. 0.0**
GARRARD LAB. "A" Transcription Auto changer, Mono cartridge **£19.14.9**
GARRARD 801 STEREO **£22. 0.0**
PHILIPS AG 1018 Stereo Cartridge, will change 7 in. records, with adaptor 10/- extra **£12.12.0**
GOLDRING GL58, with arm but less cartridge **£17. 1.0**
GOLDRING GL70, with arm, less cartridge **£27. 9.4**
GOLDRING "88" Transcription. No arm **£18.15.6**

ARMSTRONG - NEW TUNER AMPLIFIERS

MONO

224 P.M. only Self powered tuner **£22.10.6** 90/- 12 38/-
223 A.M./P.M. Self powered tuner **£28.15.0** 115/- 12 42/-
227E A.M./P.M. RADIO CHASSIS 10 watts **£36.15.0** 147/- 12 53/10

STEREO

227 A.M./P.M. RADIO CHASSIS. Stereo Gram. 10 watts each channel **£32.15.0** 211/- 12 77/4
228 A.M./P.M. RADIO CHASSIS Stereo Gram. 10 watts each channel. Filter. Mag. P.U. etc. **£61. 0.0** 280/- 12 88/-
SHELF MOUNTING TEAK CASE AVAILABLE FOR ALL THESE UNITS **£15.15.0**

SEND FOR NEW LEAFLET GIVING FULL DETAILS

OTHER TUNERS

TRIPLETONE F.M. TUNER less power **£13.19.6** 56/- 12 20/6
TRIPLETONE F.M. TUNER with power **£16.14.6** 63/- 12 23/1

STEREO AMPLIFIERS—VARIOUS

ARMSTRONG 222 Integrated 10W per channel **£27.10.0** 110/- 12 40/4
DULCI GA605, Integrated 5W per channel **£18.18.0** 76/- 12 27/8
ROGERS CADET MK2 with P.A. 4 ELCS6 valves **£26.15.0** 107/- 12 39/2
LEAK STEREO 20 P.A. and MAIN amplifier. Complete. **£54. 0.0** 229/- 12 80/8
QUAD 22 Control Unit. Pre-amp only **£25. 0.0** 100/- 12 36/8

MONO AMPLIFIERS

LINEAR L45/A. 3 Valve 3 watts **26. 6.0**
LINEAR DILATONIC. 12 watts, suitable Mic. or Guitar **213. 8.8** 52/8 12 19/8
LINEAR CONCORD. 30 watts, ideal Guitar amp, with cover **213. 8.8** 78/- 12 27/10
DULCI GA5. Integrated amp. 5 watts. ECLC6 valve **213. 2.6** 52/8 12 19/8
DULCI DPA15. 15 watt with 2 valve pre-amp **226. 5.0** 105/- 12 38/6
TRIPLETONE. Hi Fi Major with pre-amp, suitable Microphone or Guitar **£18.15.9** 84/9 12 23/3
LEAK TL12 10 watt Main amp. only **£18.18.0** 76/- 12 27/8
LEAK VARISOPE MONO pre-amplifier **£18.15.0** 63/- 12 23/1
QUAD 15 watt MAIN amplifier only **£22.10.0** 80/- 12 33/-
QUAD Pre-amplifier MONO **£19.10.0** 78/- 12 25/7

JASON F.M. AND TV SOUND TUNER KITS

FMT1, complete with 4 EF81 valves **£7. 4.6** 29/- 6 22/8
FMT2, less power, complete with 4 EF80 valves **£9. 4.6** 37/- 6 28/-
FMT2, with power, complete with 4 EF80 valves and 1 EL84 **£11. 4.6** 46/- 8 25/-
EZ80 **£11. 4.6** 46/- 8 25/-
FMT3, less power FRINGE, complete with all valves **£10.19.0** 45/- 8 24/8
FMT3 FRINGE with power, all valves **£12.19.0** 53/- 12 18/10
JTV/2 Switched F.M. and T.V. sound. Self powered all valves **£15.12.6** 62/8 12 22/11
MERCURY II, as JTV/2, but less power. **£11. 0.0** 44/- 8 24/8

Instruction book included in all kits. Available separately.
2/8 switched 3/6.
JTV/2 READY BUILT STATE CHANNELS **£22. 6.0** 89/- 12 38/8
MONITOR READY BUILT as Mercury II **£16.15.6** 87/8 12 34/8

LOUDSPEAKERS

GOODMANS AXIET 8 inch **£5. 5.7**
GOODMANS AXIOM 10 inch **£6.5.11**
GOODMANS 15/20/XL Tweeter and X/over **£7. 7.0**
GOODMANS X050 Cross-over **£2. 11.0**
X0950 **£5.10.11**
FANE 12 inch unit 20 watts **£5. 5.0**
W.B. HF 1012. 10in. unit 3.75. 7.5 and 15 ohms **£4.12.0**
WHARFEDALE SUPER 3 Tweeter **£5.16.8**
WHARFEDALE SUPER 3 Tweeter **£5.19.7**
WHARFEDALE SUPER 3 RS DD **£8.14.2**
WHARFEDALE SUPER 10 RS/DD. Full range **£10.18.0** 44/- 8 24/8
GOODMANS AUDIOM 41. 15 watt Bass unit **£9. 2.8** 38/8 8 27/8
WHARFEDALE W12/EG. 12in. 15 watt Lead Guitar **£12.10.0** 42/- 8 29/8
GOODMANS 201. Full range 12in. unit. 15 watt **£10.17.8** 43/8 8 24/8
WHARFEDALE RS12/DD. Full range unit **£11.10.0** 46/- 8 25/6
GOODMANS 301. Full range. 12in. 20 watts **£15. 4.8** 61/- 12 24/6
WHARFEDALE W15/EG. 15in. 15 watt. Bass Guitar **£12.10.0** 70/- 12 25/8
GOODMANS AUDIOM 91. 18in. 50 watt. Bass Guitar **£29.15.0** 119/- 12 43/7

EASILY REACHED BY FREQUENT FAST TRAINS
FROM WATERLOO TO SURBITON

SURBITON PARK RADIO LTD. Phone: KIN 5549

48, SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

- Order for Cash, C.O.D. or Terms.
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open Lunch Time and all day Sat.

INCREASE YOUR KNOWLEDGE



CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING, INDUSTRIAL TELEVISION, RADIO AND TELEVISION SERVICING, ELECTRONICS, COMPUTERS AND PROGRAMMING, ELECTRONIC TECHNICIANS, SERVOMECHANISMS, TELEMETRY, COLOUR TV, INSTRUMENTATION, AND PRINCIPLES OF AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns' Cert.
C. & E. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor, Portable Signal Generator and High Quality Multimeter. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.

RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examinations and ICS technical course in radio, television and electronics. PLUS details of over 150 specialised subjects.

**YOUR
CAREER
IN**

ELECTRONIC ENGINEERING
RADIO AND TELEVISION
ENGINEERING
ELECTRICAL ENGINEERING

INTERNATIONAL CORRESPONDENCE SCHOOLS - LONDON

PLEASE SEND FREE BOOK ON.....

NAME


ADDRESS

OCCUPATION..... AGE

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11

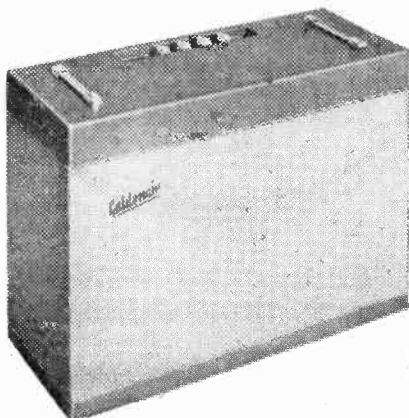10.64

The **Coldenair** GROUP-MASTER 30 WATT GUITAR AMPLIFIER



A VERSATILE UNIT FOR INSTRUMENTALISTS AND VOCAL GROUPS

being suitable for clubs and public address

- ★ Ideal for bass, lead or rhythm guitar, and all other musical instruments.
- ★ The two 12 inch 25 watt heavy duty loudspeakers are specially designed for this type of amplifier, and give outstanding reproduction.
- ★ Robust attractive two-tone finished cabinet of compact size, 28" x 20" x 10 1/2" fitted with carrying handles.
- ★ For standard AC mains 50c/s operation.
- ★ Four inputs provided can be used simultaneously with instrument pickups or mikes.
- ★ Separate Bass and Treble controls are incorporated.

Go **Coldenair**

TWICE THE QUALITY AT HALF THE PRICE

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade. Send S.A.E. for leaflet

42 GNS

or deposit of £4.12.0 and twelve monthly payments of £3.12.5.
Carriage 17/6 to be sent with deposit.

The **Coldenair** "THIRTY" HI-FI AMPLIFIER

A high quality 30 watt amplifier developed for use in large halls and clubs etc. Ideal for bass, lead or rhythm guitars, schools, dance halls, theatres and public address. Suitable for any type of mike or pickup.

Valve line-up: two EF86; one ECC83; one GZ34; two EL34.

Four separate inputs are provided with two volume controls. Bass and Treble controls are incorporated. Amplifier operates on standard 50 c/s mains. 3 ohm and 15 ohm speakers may be used.

Perforated cover with carrying handles can be provided if required, price

18/6

Go **Coldenair**

**TWICE THE QUALITY
HALF THE PRICE**

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade.
Send S.A.E. for leaflet.



16 GNS

or deposit of £1.16.0 and twelve monthly payments of £1.9.2.
Carriage 15/- to be sent with deposit.

NORTHCO BATTERY CHARGER

For all A.C. mains 200/250v., 50 c/s, 6 and 12 volts at 4 amps. Fitted with a meter. Robust ion-vented steel case. Ready for use complete with leads and battery clips. 12 months guarantee.
Price 69/11. P. & P. 4/6.



CRYSTAL SET

A wonderful educational kit for all children. Provides hours of amusement while following the easy step by step instructions. It is powered entirely by wireless waves, eliminating the expense of batteries. No soldering required. Receives all main stations. All items sold separately. Price 29/11. P. & P. 2/6.



TRANS. RADIO TUBULAR SPEAKER



Booster Speaker. Plugs into ear-piece socket of most radios and tape recorders. Gives double the volume and a hi-fi stereo effect.
that will amaze you, size Approx. 9 x 2 1/2 in. PRICE **25/-** P. & P. 1/9.

SONA STREAMLINE MICROPHONE



Omni-directional response 60-10,000 c/s. Output level 32 dB. Built in on/off switch. Provision for conversion to hand-held, cord suspended or stand mike. Attractive satin chrome finish.

Microphone **37/6** P. & P. 1/9.
Desk Stand **10/-** P. & P. 1/9.
Floor Stands Available.

BATTERY CHARGE ADJUSTERS

● Charge Rate Adjuster. ● Government manufacture. ● Easily fitted to charging circuit.
8/6 each; 2 for 6/6. P. & P. 2/8.

OPERATOR'S UNIT

Huge Purchase enables us to offer at give-away price Operator's Unit, containing standard jack socket, 250 mfd. electrolytic condenser, 4-way telephone socket, midge selenum rectifier, etc.
Price 2/6. P. & P. 9d.

SONA


MORE BARGAINS OPPOSITE

Mains Powered No. 19 Short Wave Receiver



This well known "A" set receiver covers 2 to 5 Mc/s in two overlapping bands, with optional CW/MCW/RT reception, and incorporates a built-in power-pack for A.C. mains operation. Valve line-up: 6K7 (RF amp), 6K8 (frequency changer), two 6K7 (I.F. amps), 6B8 (detector, AVC, and phone output), 6K8 (B.F.O.). This set features slow-motion tuning with two alternative tuning locks. All receivers tested before despatch. Price £5.19.8. P. & P. 10/-, Suitable phones 15/-, P. & P. 2/6.

No. 19 TRANSMITTER RECEIVER

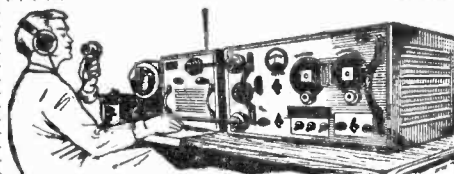

New stocks just arrived. Equipment comprises 3 separate units built into one chassis and separate power pack. Specification: "A" Set Transmitter/Receiver frequency coverage 2-4.5 Mc/s and 4.5-8 Mc/s. (150-37 metres). For R.T., C.W., or M.C.W. Range on R.T. 15 miles. C.W. 50 miles. Suitable R.X. I.F. 465 kc/s. B.F.O. etc.

R.X. valve line-up: 6K7, R.F.: 6K8 mixer. 2 6K7 I.F., 6B8 det. A.F. phone output. T.X.: 6K8, mixer, B.F.O., EF50 buffer, EB34 ADC, and output stage, which has to be de-commissioned to conform with C.P.O. requirements. Transmitter/Receiver 220-241 Mc/s. Local use up to 1 mile. Valve line-up C.V.s, 6K7 and 6V6. Intercom set 2 valve A.F. amplifier for vehicle crew inter-communication. Valve line-up 6K7 and 6V6. A 2 1/2 in. meter is built in reading I.T. and H.T. voltages, drive etc.

POWER UNIT, 12 volt DC input. Output 275 volts 110 m/a and 500 volts 50 m/a. Equipment is of American or Canadian manufacture and is supplied in good condition.

PRICE complete with Power Pack £4.10.0

Carriage 17/6.

19 set only £3.10.0

Power Unit only £1

Two 19 sets complete with Power Pack £8.10.0

Carriage 30/-.

Accessories

Handbook 3/6 P. & P. 6d.

Connectors 6 pin 7/6 P. & P. 2/6

Control Boxes, Single, new 7/6 P. & P. 2/6

Whip Aerials 8ft. 6in. 7/6 P. & P. 2/6

5ft. 4/6 P. & P. 2/6

Headphones less mike insert 5/- P. & P. 2/6

Variometers for 19 sets, less front panel but electrically sound, 7/6 each. P. & P. 3/6

TRANSISTOR SALE

Mullard OC71 (P. & P. 3d.) 2/11

Mullard OA90 (P. & P. 3d.) 1/11

Ediswan XD202 Germanium diodes (P. & P. 3d.) 1/11

Mullard OA79 (P. & P. 3d.) 1/11

Transistor holder 3-pin (P. & P. 3d.) 1/11

Transistor holder 3-pin (P. & P. 3d.) 1/11

Transistor holder 3-pin (P. & P. 3d.) 1/11

Transistor holder 3-pin (P. & P. 3d.) 1/11

CRYSTAL CALIBRATOR TEST SET No. 7 Mk. 1

New in Paxon cabinet with circuit and instructions on rear panel. Calibrates transmitters and receivers.



3 choices of calibration points: 10, 100, 1,000 kc/s apart, harmonics up to 20 Mc/s. Operates from 2v. accumulator and 130v. a.c. battery.

Price £2.15.0. P. & P. 7/6.

Price £2.15.0. P. & P. 7/6.

Price £2.15.0. P. & P. 7/6.

Price £2.15.0. P. & P. 7/6.

TRANSMITTER RECEIVER No. 46

Compactly built to be carried by one man. This has a range of app. 10 miles and being crystal controlled tuning is avoided and operation is as accurate as a telephone Frequency 3.6-9 Mc/s. Complete station comprising receiver-transmitter, rod aerial, 1 set of headphones and microphone in canvas carrying bag, but less the plug-in crystal coil units (these are easily obtainable).

Price per station £4.10.0 P. & P. 10/- each.

Two stations for Post £9.10.0 free.

Price per station £4.10.0 P. & P. 10/- each.

Two stations for Post £9.10.0 free.

Price per station £4.10.0 P. & P. 10/- each.

Two stations for Post £9.10.0 free.

Price per station £4.10.0 P. & P. 10/- each.

Two stations for Post £9.10.0 free.

Brand new individually checked and guaranteed VALVES

AC/HL 4/6	DL819 15/-	EF85 5/-
AC/P4 6/-	EF85 23/-	EF183 8/-
AC/PEN 6/-	EF148 2/6	EF184 8/-
AL90 5/-	EL106 5/6	EL171 300/-
ARS 5/-	EL145 30/-	EL182 3/6
ARP 3/6	EL124 12/6	EL184 8/-
ARP3 3/6	EA50 1/-	EL35 6/-
ARP12 2/6	EA73 7/-	EL38 17/6
ARP21 7/-	EA8C80 5/6	EL41 7/-
ARP24 3/6	EAC91 3/6	EL42 3/6
ARP34 4/6	EAF42 8/-	EL50 8/-
ARTP1 6/-	EB34 1/6	EL81 8/-
ATP4 2/3	EB91 3/6	EL83 6/3
ATP7 5/6	EB93 6/-	EL84 8/-
BL7 5/6	EB41 6/-	EL85 8/-
BL13 10/-	EB91 5/-	EL81 4/6
B84 8/-	EBF80 5/-	EL95 5/-
B85 20/-	EBF83 7/6	EM80 6/-
B894 47/6	EBF89 6/6	EM81 7/6
BE154 15/-	EC352 4/6	EM84 6/3
BT19 25/-	EC83 12/6	EM85 9/-
BT35 25/-	EC70 4/-	EN31 10/-
BT45 150/-	E690 20/-	ENU208 6/-
BT83 35/-	EC91 3/-	KY61 5/6
CW1 2/-	EC91 4/-	EY66 5/6
CL33 9/-	EC92 8/-	EL41 3/-
CW71 3/-	EC93 6/-	EZ40 5/-
CW77 6/-	EC94 5/6	EZ41 6/6
CV102 1/-	EC95 6/6	EZ80 5/6
CV103 4/-	EC99 4/-	EZ81 3/6
CV4014 7/-	EC99 6/6	EZ82 5/6
CV4015 6/-	EC99 6/6	F6081 6/-
CV4028 10/-	EC99 6/6	F6083 6/-
CV4046 40/-	EC99 6/6	FW4500 6/6
CV31 5/6	EC99 7/6	GI1371K 6/-
D1 1/6	EC99 7/6	GI1371K 6/-
D81 2/6	EC99 7/6	GI1371K 6/-
D81 2/6	EC99 7/6	GI1371K 6/-
D77 3/6	EC99 7/6	GI1371K 6/-
DA30 12/6	EF34 2/6	G232 10/-
DA60 75/-	EF36 3/6	G234 10/-
DAF98 6/-	EF37 7/-	H63 7/-
DE1 4/6	EF38 2/6	HL12200 22/6
DE75 8/-	EF40 8/-	HL12200 22/6
DET20 2/-	EF52 6/-	HL12200 22/6
DET25 15/-	EF53 4/6	HL2K 2/6
DF73 6/-	EF56 8/-	HL2K 2/6
DF91 9/-	EF71 7/6	HL23DD 6/-
DF92 6/-	EF80 6/-	K244 5/6
DF96 6/-	EF74 4/-	HVR2 9/-
DK92 6/6	EF80 5/-	K3A 30/-
DK96 6/6	EF81 6/-	KT32 8/-
DL93 6/-	EF85 4/6	KT330 6/-
DL98 6/-	EF86 4/6	KT44 5/6
DL94 6/-	EF89 3/6	KT63 4/-
DL96 5/6	EF91 2/6	KT68 12/6
DL810 8/-	EF92 2/6	KT67 15/-

8/6	QV047	8/-	W21	5/-	5B257/M	19/-
KT22/-	R3	8/-	W118	8/-	634WA	10/-
KT88	RU4/1250		W119	8/-	5R4QY	9/-
KTW61	60 -	X118	8/-	5T4	7/-	
KTW63	60 -	X145	8/-	5U4G	4/6	
KT72	60 -	X65	7/6	5V4G	8/-	
KT263	60 -	X65	7/6	5V4G	8/-	
60 -	60 -	X65	7/6	5V4G	8/-	
60 -	60 -	X65	7/6	5V4G	8/-	
60 -	60 -	X65	7/6	5V4G	8/-	
60 -	60 -	X65	7/6	5V4G	8/-	

R.S.C.BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL,
LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELDPAGE 500 FOR
ADDRESSES**BASS-MAJOR 30 WATT GUITAR AMPLIFIER**A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT
FOR VOCAL AND INSTRUMENTALIST GROUPS*Eminently suitable for bass, lead or rhythm guitar and all other musical instruments*

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

39½ Gns.Send S.A.E. for leaflet
OR DEPOSIT of £4.3.0 and 12 monthly
payments of £3.9.11. Carr. 17/6.**R.S.C. G5 GUITAR AMPLIFIER**

5-watt high quality putput. Incorporating high flux 12in. 10 watt 12,000 line loudspeaker. Sensitivity 50 m.v. High impedance jack input. Handsome strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains.

£9.19.6 Or DEPOSIT 22/3 and 9 monthly payments of £2/4. Carr. 7/6.

LINEAR TREMOLO/PREAMP. UNIT
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 8.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point, and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **4 Gns.** ONLY

HE-40 De-Luxe 4 Band. 220/240 v.
50/60 c.p.s. A.C. mains operation. Frequencies covered 550 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial. 'S' meter. Internal ferrite aerial for medium wave. Telescopic whip aerial 59in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphone. external speaker socket. Other features are electrical bandspread tuning, 0-100 logging scale. Noise limiter. A.V.C. B.F.O. stand by switch. Size approx. 14 x 8 x 6in. Handsome grey crackle finished metal cabinet with chromium fittings. Brand new with full instructions manual. Usual guarantee.

TERMS: Deposit £3.15.0, and nine monthly payments of £6/3.
Cash price if cleared **Only £24.15.0** Carr. in 3 months. Free.

spread tuning. Output for H/Phones or standard speaker. Provides 1.5 watts output. Size 15 x 10 x 7in. For 220/240v. 50/60 c.p.s. A.C. mains. A highly efficient receiver representing exceptional value at only

40 Gns.
Post Free.TERMS: Deposit £5.4.0, and nine monthly payments of 91/2.
Cash price if settled in 3 months.

SELENIUM RECTIFIERS			
F.W. BRIDGE	24 v. 2 amp.	..	14/9
6/12 v. 1a. ..	3/11	24 v. 20 amp.	89/9
6/12 v. 2a. ..	6/11	H.T. TYPES H.W.	
6/12 v. 3a. ..	9/9	150 v. 40 mA	3/9
6/12 v. 4a. ..	12/3	250 v. 50 mA	3/11
6/12 v. 6a. ..	15/3	250 v. 60 mA	4/11
6/12 v. 10a. ..	26/9	250 v. 80 mA	5/11
6/12 v. 15a. ..	35/9	250 v. 250 mA	11/9

CONTACT COOLED. 250 v. 75 mA. F.W. (Bridge). 10/11 250 v. 50 mA. F.W. (Bridge) 8/11. H.W. 250 v. 60 mA. 5/11.

HI-FI 10-WATT AMPLIFIERS.
Brand New Complete **£7.19.6** Carr. 5/6

Manufacturers' discontinued Model. Push-Pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike", Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

LARGE REXINE COVERED SPEAKER CABINETS Full range for 12", 15" and 18" Speakers. Cash or H.P.
Send S.A.E. for leaflet.

R.S.C. SENIOR 15 WATT LEAD OR RHYTHM GUITAR AMPLIFIER

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is well made and finished as Junior Model Size approx. 18 x 18 x 8in.

Only **19 Gns.** Carr. 10/-

Send S.A.E. for leaflet. Or DEPOSIT 39/11 and twelve monthly payments of 33/4.

**R.S.C. B20 BASS GUITAR AMPLIFIER**

A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.

Send S.A.E. for leaflet.
29½ Gns. Or Deposit £3.2.0 and 12 monthly payments of 51/8. Carr. 17/6.

TRANSCEIVERS. Two-way Transmitter Receivers. 9 transistor S/H circuit. Crystal controlled range up to 5 miles according to conditions. Size of each unit 8 1/2 x 3 x 1 1/2in. Complete with batteries, telescopic aerials and leather cases. Brand new guaranteed. **£25.0.0** Per Pair.

COMPLETE POWER KIT 19/11
Consisting of Mains Trans. Metal Rectifier. Double electrolytic smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v. 60 mA. 2 a. 2 a. **R.S.C. POWER KIT. 3/9.** Louvered metal case only 8 x 3 1/2 x 2 1/2in. Stove enamelled. For 220-240 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA. fully smoothed at 8.3 v. 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

R.S.C. BABY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20.0.0. Only 89/6, carr. 5/- or assembled ready for use 6 gns.



TRANSISTOR SALE. Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC22 4/9, OC81 4/9, OC171 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

EX. GOVT. SMOOTHING CHOKES.
200 mA. 3-5 H. 50 ohms. Farmeko 8/9;
150 mA. 10 H. 50 ohms 8/9; 80 mA. 20 H. 900 ohms 5/9; 120 mA. 12 H. 100 ohms 3/9;
50 mA. 50 H. 1,000 ohms 6/9; 100 mA. 10 H. 100 ohms 6/9; 60 mA. 6-10 H. 250 ohms 9/11

EX GOVT SILENIUM RECTIFIERS 12v 15v AMP (BRIDGE) F.W. ONLY **19/9**

R.S.C. (Manchester) Ltd.

MAIL ORDERS TO:

54 WELLINGTON STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied.

S.A.E. with all enquiries, please. Personal shoppers welcomed at any of the branches below. Open all day Saturday.

BRADFORD 54 Morley Street.
Nr. Alhambra Theatre
(Half-day Wednesday)

BRISTOL 14 Lower Castle Street
Open 5th October

BIRMINGHAM 6 Gt. Western
Arcade, opp.
(No half day) Snow Hill Station

DERBY 26 Osmaston Rd., The Spot
(Half-day Wednesday)

DARLINGTON 13 Post House
Wynd (Half-day
Wednesday)

EDINBURGH 133 Leith Street
(Half-day Wed.)

GLASGOW 326 Argyle Street
(Half-day Tuesday)

HULL 51 Savile Street
(Half-day Thursday)

LEICESTER 32 High Street
(Half-day Thursday)

LEEDS 5-7 County (Mecca) Arcade
(No half-day closing)

LIVERPOOL 73 Dale Street
(No half-day closing)

LONDON 238 Edgware Road
(Half-day Thursday)

MANCHESTER 8-10 Brown St.
(Market Street)
(No half-day)

MIDDLESBROUGH 106 New-
port Rd.
(Half-day Wednesday)

SHEFFIELD 13 Exchange Street.
Castle Market Bldgs.
(Half-day Thursday)

EX. GOV. 2V. ACCUMULATORS
16 A.H. Size 7 x 4 x 2 ins. Brand new, 4/9
each. Three for 12/6, carr. 5/-.

JASON FMTI
V.H.F./F.M. Radio Tuner design. Total
cost of parts including valves, Tuning
dial, Escutcheon, etc., £8.19.8.

**LINEAR L45 MINIATURE 4.5 WATT
QUALITY AMPLIFIER.** Suitable for
any record playing unit and most micro-
phones. Negative feedback 12 dB. Separate
Bass and Treble Controls. For mains
200-250 v. 50 c/s. Output for 2-3 ohm speaker.
Mullard valves E280, ECC83, EL84.
Size only 7 x 5 x 5 1/2 in. high. Guaranteed
12 months. Only 6 gns. Send S.A.E. for
leaflet. Terms: Deposit 24/9 and 5 monthly
payments of 24/9.

**R.S.C. BATTERY TO MAINS
CONVERSION UNIT**
Type BM1. An all-dry battery
eliminator. Size 5 1/2 x 4 1/2 x 2 in.
approx. Completely replaces
battery supplying 1.4 v. and
90 v. where A.C. mains 200-250
v. 50 c/s is available. Suitable
for all battery portable
receivers requiring 1.4 and
90 v. This includes low con-
sumption types. Complete
kit with diagrams. 39/9, or
ready to use, 46/6.



R.S.C. 30-WATT ULTRA LINEAR

HIGH FIDELITY AMPLIFIER A10
A highly sensitive Push-Pull high output
unit with self-contained Pre-amp. Tone
Control Stages. Certified performance
figures compare equally with most ex-
pensive amplifiers available. Hum level
70 dB down. Frequency response +3 dB
30-20,000 c/s. A specially designed sec-
tionally wound ultra linear output transformer
is used with 807 output valves. All com-
ponents are chosen for reliability. Six
valves are used EF86, EF86, ECC83, 807,
807, GZ34. Separate Bass and Treble Con-
trols are provided. Minimum input required
for full output is only 12 millivolts so that
**ANY KIND OF MICROPHONE OR
PICK-UP IS SUITABLE.** The unit is
designed for **CLUBS, SCHOOLS,
THEATRES, DANCE HALLS or OUT-
DOOR FUNCTIONS**, etc. For use with
Electronic ORGAN, GUITAR, STRING
BASS, etc. For standard or long-playing
records. **OUTPUT SOCKET PROVIDES
L.T. and H.T. for RADIO FEEDER UNIT.**
An extra input with associated vol. control
is provided so that two separate inputs such
as Gram and "Mike" can be mixed.
Amplifier operates on 200-250 v. 50 c/s. A.C.
Mains and has output for 3 and 15 ohm
speakers. Complete kit of parts with point-
to-point wiring diagrams and instructions.
If required perforated cover with carrying
handles can be supplied.

11 Gns.

Carr. 10/-

for 19/9. The amplifier can be supplied fac-
tory built with EL34 output valves and
12 months' guarantee, for 14 gns. Send
S.A.E. for leaflet.

**TERMS: DEPOSIT 33/9 and 9 monthly
payments of 33/9.** Suitable microphones and speakers available
at competitive prices.

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally
robust 2in. diam. Voice Coil Assemblies.
122/10 20watt, 5 gns. 122/10A 20watt, 6 gns.
122/12 20watt, 7 gns. 122/12A 20watt, 8 gns.
122/14 22watt, 9 gns. 122/14A 22watt, 10 gns.
122/17 25watt, £11.17.6 122/17A 25watt, £12.17.6
15in. 15 ohms. Cast chassis. Exceptionally
robust 2in. diam. Voice Coil Assemblies.
152/12 20watt, 12 gns. 152/12A 20watt, 13 gns.
152/14 27watt, 14 gns. 152/14A 27watt, 15 gns.
152/17 35watt, 16 gns. 152/17A 35watt, 17 gns.
"A" indicates dual cone type. 30-17,000
c.p.s. Send S.A.E. for leaflets. Terms
as above.

R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home,
small club, etc. Only 50 millivolts input is required
for full output so that it is suitable for use with the latest
high-fidelity pick-up heads, in addition to all other
types of pick-ups and practically all "mikes". Separate
Bass and Treble Controls are provided. These give full
long-playing record equalisation. Hum level is negligible
being 71 dB down. 15 dB of Negative feedback is used.
H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1 A. is available for
the supply of Radio Feeder Unit or Tape-Deck pre-
amplifier. For A.C. mains input of 200-230-250 v. 50 c/s.
Output for 2-3 ohms speaker. Chassis is not alive. Kit is complete in every detail
and includes fully punched chassis (with baseplate) with Blue Hammer finish and
Point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0,
or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly
payments of 22/6 for assembled unit.


THE SKYFOUR T.R.F. RECEIVER.
A design for a 3 valve long and medium
wave 200-250 v. A.C. Mains receiver with
selenium rectifier. High gain H.F. stage
and low distortion detector. Valve line-up
6K7, SP61, 6V6G. Selectivity and quality
excellent. Simple to construct. Point-to-
point wiring diagrams and instructions and
parts list 1/9. maximum building costs
£4.19.6, inc. attractive walnut veneered
wood cabinet 12 x 6 1/2 x 5 1/2 in.

TWEETERS. R.A. 3 ohm. 25/9; 15 ohm. 25/9
R.A. 12in. DUAL CONE 3 ohm 8 watt
Speakers. Ideal for Stereo. Only 39/9 ea.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM2. Size 8 x 5 1/2 x 2 1/2 in.
Supplies 120 v. 90 v. and 60 v.
40 mA and 2 v. 0.4 A. to 1 amp.
fully smoothed. Thereby
completely replacing both
H.T. batteries and L.T. 2 v.
accumulators when con-
nected to A.C. mains supply
200/50 v. 50 c/s. **SUITABLE
FOR ALL BATTERY RE-
CEIVERS** normally using
2 v. accumulators. Complete
kit of parts with diagrams and instructions.
49/9, or ready for use, 59/6.

12in. 10 WATT HIGH QUALITY LOUDSPEAKER.

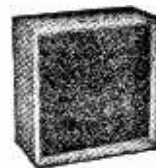

In walnut veneered
cabinet. Gauss 12,000
lines. Speech coil 3
ohms or 15 ohms.
Only £4.19.6, Carr.
5/- Terms: Deposit
11/3 and 9 monthly
payments of 11/3.
12in. 20 WATT HI-
FI LOUDSPEAK-
ERS IN CABINETS.
Size 18 x 18 x 10in.
Finish as above.

Terms: Deposit 17/9 and 9 monthly pay-
ments of 17/9. Only £7.19.6, Carr. 8/6.
For larger types see page 499.


R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer
finish. Pleasing design.

JUNIOR MODEL.
Size 20 x 11 x 8in. for
8 x 5in. or 10 x 6in.
speakers. £22.9.9.

STANDARD MODEL.
Size 27 x 18 x 12in. for
8 or 10in. speakers.
£41.19.8.

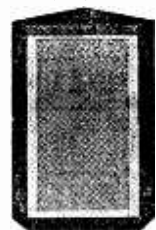SENIOR MODEL.
Size 30 x 20 x 15in. for
12in. Speaker. Suitable
speaker systems be-
low. Only 7 gns.



**AUDIOTRINE HI-FI SPEAKER SYS-
TEMS.** Consisting of matched 12in. 12,000
line, 15 ohm high quality speaker; cross-
over unit (consisting of choke, condenser,
etc.) and Tweeter. The smooth response and
extended frequency range ensure surpris-
ingly realistic reproduction. Standard 10 watt
rating £4.19.9. Carr. 5/- Or Senior 15 watt.
£6.19.9. Carr. 7/6.

R.S.C. BASS REFLEX CABINETS.
JUNIOR MODEL. Specially designed
for W.B. HP1012 Speaker, but suitable for
any good quality 10in. speaker. Acousti-
cally lined and ported. Polished walnut
veneer finish. Size 18 x 12 x 10in. Handsome
appearance. Ensure superb reproduction
for only £3.19.6.


STANDARD MODEL. As above but for
12in. speakers. Size 20 x 15 x 13in. For
vertical or horizontal use. £5.19.6. Set
of less with brass ferrules, 19/6.

A highly-sensitive 4-valve quality amplifier for the home,
small club, etc. Only 50 millivolts input is required
for full output so that it is suitable for use with the latest
high-fidelity pick-up heads, in addition to all other
types of pick-ups and practically all "mikes". Separate
Bass and Treble Controls are provided. These give full
long-playing record equalisation. Hum level is negligible
being 71 dB down. 15 dB of Negative feedback is used.
H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1 A. is available for
the supply of Radio Feeder Unit or Tape-Deck pre-
amplifier. For A.C. mains input of 200-230-250 v. 50 c/s.
Output for 2-3 ohms speaker. Chassis is not alive. Kit is complete in every detail
and includes fully punched chassis (with baseplate) with Blue Hammer finish and
Point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0,
or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly
payments of 22/6 for assembled unit.







**ARMSTRONG, DULCI, LINEAR,
ROGERS, LEAK and JASON EQUIP-
MENT, GOODMAN'S, W.B. and
FANE SPEAKERS, GARRARD and
GOLDRING T/Tables CASH or H.P.**

SUPERHET FEEDER UNIT. Design of
a high quality Radio Tuner (specially
suitable for use with our Amplifiers).
Delayed A.V.C. Controls are Tuning,
Wave and Vol. Only 250 v. 15 mA H.T. and
L.T. of 6.3 v. 1 amp. required from amplifier.
Size approx. 9 x 6 x 7 1/2 in. high. Simple align-
ment procedure. Point-to-point wiring
diagrams, instructions and priced parts list
with illustrations, 2/6. Total building cost
£5.5.0. S.A.E. for leaflet.

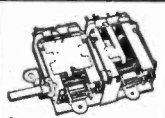MULTI-METER, CARY MI. Sensitivity
2,000 ohms per volt. A.C. and D.C. 54/-
A.10. Basic Meter sensitivity 158 micro-
amps A.C. and D.C. ranges £4.11.6. B.40.
Sensitivity up to 10,000 ohms per volt A.C.
and D.C. £8.2.6. TMK500 30,000 ohms per
volt, with overload buzzer, £8.19.6.



Just a few of our BARGAINS

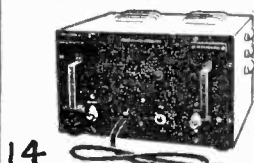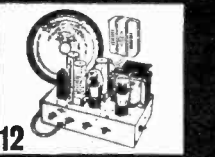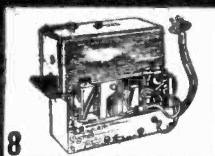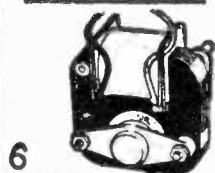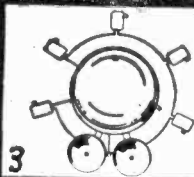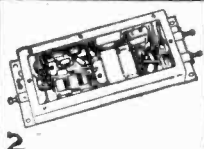

FREE OFFER
ELECTRIC
SOLDERING IRON
with the
POCKET
MULTI-METER
See item No. 7
for further details

1. CYLON A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION. Size $2\frac{1}{2} \times 2\frac{1}{2}$ in. approx. By famous manufacturer. A.M. I.F. 470 Kc/s. F.M. I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. F.M. coverage 108 Mc/s-89 Mc/s. Circuit diagrams 2/8. FREE with Tuner, 1st, 2nd, 3rd A.M. I.F.'s. 1st, 2nd, 3rd and 4th F.M. I.F.'s. V.H.F. Osc. choke, A.M. I.F. trap, A.F. 114 and A.F. 115. All the above are the R.R. end of an A.M./F.M. receiver car radio, etc. The above six items, £2.10.0.

2. TRANSISTOR INVERTOR. 50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 16c573. In solid 16 gauge aluminium case size $1\frac{1}{2} \times 6 \times 2\frac{1}{2}$ in., by famous manufacturer, 19/6, plus 6/- P. & P.

3. RINGO BURGLAR ALARM SYSTEM. A.C. mains, 200/240 volt. Fire salvage slightly tarnished. List price 7 gns. Our price, complete with double gong bell five micro switches and full instructions. 49/6. P. & P. 4/-.

4. SIGNAL GENERATORS. Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case $10 \times 6\frac{1}{2} \times 5\frac{1}{2}$ in. Three miniature valves and Metal Rectifier. A.C. mains 200-250 v. Internal modulation of 400 cps. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 multivolts, C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.

5. FLUORESCENT LIGHT FITTING. Twin 40 watt 200/250 v. less tubes 59/6. P. & P. 6/-.

6. A.C. MAINS MOTOR. Can be used for a variety of purposes, silent running, satisfactory in every way. 230/250 v. A.C., 9/6. P. & P. 2/-.

7. POCKET MULTI-METER. Size $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. Meter size $2\frac{1}{2} \times 1\frac{1}{2}$ in. Sensitivity 1,000 O.P.T. on both A.C. and D.C. A.C. and D.C. volts 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω . Complete with test prods, battery and full instructions. 35/- P. & P. 2/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

8. CHANNEL TUNER I.F. 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCF80 and PCF84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/- P. & P. 3/-.

9. The MOTORISTS' REV. COUNTER. Kit of parts comprising 270 degree 3in. moving coil movement. Manufacturer's present price of this movement would be at least £7. Complete with full instructions and circuit diagram. Scale calibrated up to 8,000 r.p.m. Can be used with any 4 or 6 cylinder car. 29/6, plus 3/6 P. & P.

10. B.S.R. MONARCH UA14 WITH FULL-FI HEAD. 4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: $12\frac{1}{2} \times 10\frac{1}{2}$ in. Space required above baseboard 4 $\frac{1}{2}$ in., below baseboard 2 $\frac{1}{2}$ in. Fitted with Full-Fi turnover crystal head, £5.19.6. P. & P. 6/6.

11. 50 MICRO-AMP METER movement by world famous manufacturer. Size $3 \times 2\frac{1}{2}$ in., 50/- post free.

12. 8-watt PUSH-PULL 5 VALVE AMPLIFIER with METAL RECTIFIER. A.C. mains 200-250v. Size $10\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$ in. 5 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kc/s. 2 dB down to 20 Kc/s. Output 8 watts at 5 per cent total distortion. Note level 40 dB down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls. £3.19.6. P. & P. 7/6. Crystal mike to suit, 15/-. P. & P. 2/6. 8in. P.M. Speaker to suit, 12/6. P. & P. 2/6.

13. FLUORESCENT LIGHT KIT. 40 watt fluorescent lighting kit comprising Siemens choke, 2 bi-pin holders, starter holder and starter, 11/6. P. & P. 3/6. Twin 20 choke instant start, complete with 4 bi-pin 200/250 v. holders, 11/6. P. & P. 4/6. Twin 40 choke instant start with 4 bi-pin 200/250 v. holders, 17/6. P. & P. 4/6.

14. FIXED FREQUENCY SIGNAL GENERATOR. Crystal control in metal case, size $10 \times 6 \times 6$ in. Incorporating two 6C13 valves, mains transformer, metal rectifier, choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new, 39/6, plus 6/- P. & P. A.C. mains 200-250 volts.

RADIO & T.V. COMPONENTS (ACTON) LTD.

21b High Street, Acton, London, W.3.

All enquiries S.A.E. Goods not despatched outside U.K.

Shop Hours 9 a.m.—6 p.m. Early closing Wednesday.

SPECIAL OFFER! FROM R. & T.V. LTD.

Elegant Seven

COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features
4½" SPEAKER


- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11½ x 2½ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 Kc/s.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY
£4.19.6

Plus 5/6 P. & P. Parts
list & circuit diagram
2/6. FREE with parts.


SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer etc. A.C. mains 200-250v. Output 9v, 50mA, 7/6.

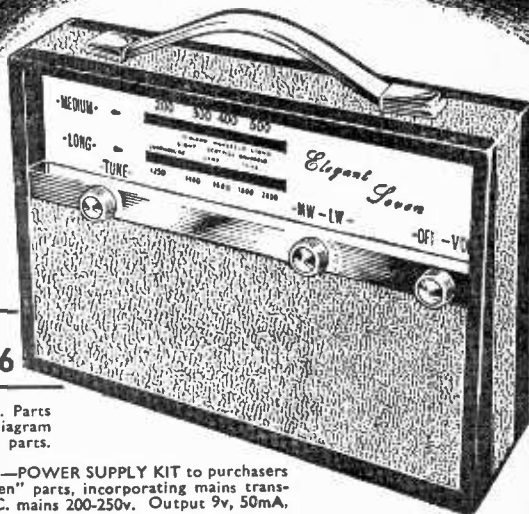Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.



RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3
Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

GUITAR AMPLIFIERS WITH TREMOLO

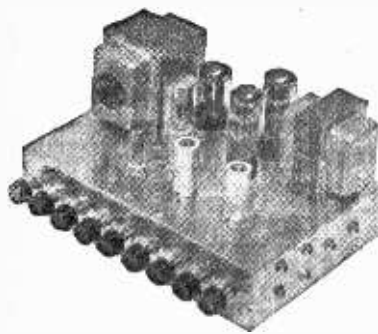

Five jack socket inputs, four with separate mixing volume controls, and one input "straight through". All inputs are of very high sensitivity, only 10 millivolts input is required for full output, making them suitable for all types of guitars and microphones. Separate Bass and Treble

controls, giving a wide range of lift and cut. Separate master gain control. Tremolo speed and depth controls. Jack socket for remote tremolo switching. Outputs for 3 and 15 ohms speakers. Valves used in the 30 watt and 50 watt amplifier ECC83, ECC83, EL34, EL34, GZ34. In the 15 watt amplifier ECC83, ECC83, EL84, EL84, E281. An extra valve ECC83 is used in the tremolo circuit. The chassis is complete with baseplate and is solidly made of 18 gauge steel, finished silver grey hammer. Size 12 x 8 x 6½ inches high.

PRICES—
50 watt with tremolo £21.10.0
50 watt less tremolo £20.10.0
30 watt with tremolo £15.10.0
30 watt less tremolo £14.10.0
15 watt with tremolo £12.10.0
15 watt less tremolo £11.10.0
Add carriage 10/- any amplifier. Send for free descriptive leaflet.

STROUD AUDIO

PAGANHILL LANE, STROUD, GLOS.

Stroud 783

BARGAINS FROM BROADWAY ELECTRONICS

12in. ALTHAM SPEAKER with built-in tweeter, 3 ohm or 15 ohm 7,000 Gauss Magnet. Only 29/6, postage 3/6.

L.S.11.75 ELECTROSTATIC TWEETER—2/6 with diagram. HAYDON CABINET (17 x 15 x 8in.) designed to take a 12in. Heavy Duty Speaker, 50/-, postage 7/6.

ATTRACTIVE TWO-TONED CABINET, 11 x 8 x 5in., room for small amplifier, fitted with ex T.V. 5in. speaker. Only 19/6, post 2/6. The Famous L.M.3 XTAL MICROPHONE with neck lanyard, 32/6 table stand for above, 9/6 extra. Xtal Insert, 7/3.

GUITAR PICK-UP, complete with clip and screened lead, 15/-, 3-WAY PUSH-BUTTON UNITS. Each button operates a 4-pole, 2-way switch, 4/6.

BARGAINS IN TRANSISTORS. Mullard RF Packs, OC44, two OC45, 12/6; AF Packs, OC81D, two OC81, 12/6; OC44, 3/6; OC45, 3/6; OC71, 2/6; OC72, 3/6; OA81 diode, 2/3; AF115, 8/6; AF117, 6/6; ORP12 Light Cell, 7/6; OC29, 12/6; OC35, 12/6.

TRANSISTOR ELECTROLYTICS, 1, 2, 4, 5, 6, 10, 15, 32, 50 100mFd—all at 15 volts, 1/3 each.

McMICHAEL TELESCOPIC TV AERIAL, 23in., extends to 45in. Fitted with co-ax plug will suit any set. Only 7/6. CARTRIDGES. Acos 67-1G Low Output, 67-2G Medium Output GP59-5 High Output, Garrard GC2 or GC8, all with mounting brackets, 15/-, Ronette Stereo with mounting bracket, 25/-.

EARPIECES with cord and 3.5 mm. plug, 8 ohm magnetic, 3/-; 250 ohm, 4/-; 180 ohm magnetic with clip, 6/6; Xtal, 4/-; 3.5 mm. plugs with nice long shank, complete with jack, 3/-; 3.5 mm. plugs with nice long shank, complete with jack, screened 4/-.

TOGGLE SWITCHES. Single pole with on-off plate, 2/6.

NEON PANEL LIGHTS, 2400 A.C. Arcolcetric, 2/6.

TERMS: C.W.O. OR C.O.D.

BROADWAY ELECTRONICS
92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984

(four minutes from Tooting Broadway Underground Station)

BOOKS

ELECTRONICS FOR THE BEGINNER

by J. A. Stanley 25s. net
**MODERN DICTIONARY OF
 ELECTRONICS** 45s. net
**ELECTRONICS MATH SIMPLIFIED
 VOL I**

by Alan Andrews 35s. net
**ELECTRONICS MATH SIMPLIFIED
 VOL II**

by Alan Andrews 35s. net
**ELECTRONICS EXPERIMENTS
 AND PROJECTS**

by Len Buckwalter 25s. net
**INTRODUCTION TO LASERS AND
 MASERS**

by Allan Lytel 16s. net
ABC'S OF ELECTRONICS

by Farl Waters 16s. net
ABC'S OF COMPUTERS

by Allan Lytel 16s. net
ABC'S OF ELECTRICITY

by the Howard W. Sams Editorial Staff
 16s. net
**ABC'S OF SHORT-WAVE
 LISTENING**

by Len Buckwalter 16s. net
**COMPUTER CIRCUIT PROJECTS
 You Can Build**

by Lee Boschen 21s. net
**HOW TO READ SCHEMATIC
 DIAGRAMS**

by Donald E. Herrington 18s. net
TRANSISTOR CIRCUIT MANUAL

by Allan Lytel 35s. net
**INTRODUCTION TO
 ELECTRONICS SERVICING FOR
 THE BEGINNER**

by J. A. Stanley 24s. net
KNOW YOUR OSCILLOSCOPE

by Paul C. Smith 20s. net
**TAPE RECORDERS: HOW THEY
 WORK**

by Charles G. Westcott and
 Richard F. Dubble 24s. net
**HANDBOOK OF ELECTRONIC
 CHARTS AND NOMOGRAPHS**

by Allan Lytel 35s. net
DIODE CIRCUITS HANDBOOK

by Rufus P. Turner 18s. net
**ELECTRONIC ENGINEERS AND
 TECHNICIANS REFERENCE
 HANDBOOK** 30s. net

**ELECTRONIC COMPONENT TESTS
 AND MEASUREMENTS**

by Robert G. Middleton 24s. net
**101 WAYS TO USE YOUR VOM AND
 VTVM**

by Robert G. Middleton 16s. net
**ABC'S OF COMPUTER
 PROGRAMMING**

by Allan Lytel 16s. net
**ABC'S OF ELECTRIC MOTORS
 AND GENERATORS**

by Allan Lytel 16s. net
**PRACTICE PROBLEMS IN
 ELECTRONICS CALCULATIONS**

by Alan Andrews 30s. net
BASIC ELECTRONIC SERIES

by Thomas M. Adams
1. TRANSISTOR CIRCUITS 24s. net
2. OSCILLATOR CIRCUITS 24s. net
**3. DETECTOR AND RECTIFIER
 CIRCUITS** 24s. net
4. AMPLIFIER CIRCUITS 24s. net

ALL TITLES CASE BOUND
 From Booksellers or, plus 8d. Postage, from

**FOULSHAM — SAMS
 TECHNICAL BOOKS**

837 YEOVIL ROAD
 SLOUGH, BUCKS,
 ENGLAND

Lewis have the Cabinet for you

We can supply any cabinet
 to your own specification

This is only one example of—
**THE LARGEST RANGE
 OF CABINETS IN THE
 COUNTRY**

Equipment is also our
 speciality.



The Grosvenor
 Price 18 gns.



The Lowboy
 Price 27 gns.



100(P104) Chase Side, Southgate
 London, N.14. Tel 3733/9666

FREE CATALOGUE

Send today for the new
 Lewis Catalogue

Designed to assist your choice of
 cabinet.


Sent absolutely free. The new Lewis
 Radio Cabinet Catalogue—the most
 comprehensive ever prepared. Choose
 from 49 different Models.

Please send your new free 24 page
 colour cabinet catalogue.

Name

Address

BLOCK CAPITALS PLEASE

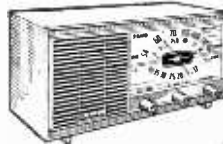

BRAND
 NEW
 A.C. MAINS
 5 VALVE
 SUPERHET
 RADIO
 RECEIVERS

Housed in beautifully styled cabinets offering
 terrific performance and very high quality
 reproduction. Built-in ferrite rod aerial for
 reception of all your favourite programmes. Fully
 guaranteed.

MODEL 55 (as illus.). Covers Medium, Long and
 Short Waves. Size 8 1/2 in. w. x 4 1/2 in. d. x 4 1/2 in. h.
PRICE ONLY £7.17.6. P. & P. 3/6.

MODEL 36. Similar circuitry to above but covers
 Medium wave only. Size 7 1/2 in. w. x 3 1/2 in. d. x 4 1/2 in.
 h. **PRICE ONLY £4.15.6.** P. & P. 5/6.

SPECIAL OFFER HIGH GRADE TWO-STAGE GRAM

Made by very well-known manufacturer.
 Using a double-wound mains transformer (fully
 isolated chassis) with tapped primary, full wave
 contact cooled rectifier, and Mullard ECL82
 triode-pentode valve. 3 watt output. Separate
 tone and volume controls. Overall size 8 1/2 in. wide
 x 3 in. deep x 4 1/2 in. high. Each amplifier Brand
 New and tested and supplied complete with
 valve. 3 ohm output transformer and knobs.
PRICE 49/6 P. & P. 4/-.

Suitable 8 in x 3 in. Speaker 10/6, plus 2/6 P. & P.
 our MK1 or MK3 FM Tuner)

BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in. 12/6; 5 in. 12/6; 6 1/2 in. 15/-; 8 in. 21/-;
 10 in. 25/-; 12 in. 27/6; 12 in. 15 ohm, 30/-;
 10 in. x 6 in. E.M.I. 131 x 8 in. with high flux
 ceramic magnet, 11,000 gauss. Aluminium centre
 cone. 10 watts. 50 c/s to 10 Kc/s. 42/-.
 P. & P. up to 6 in. 1/6; over 6 in. 2/6 per speaker.

SPECIAL OFFER !!

BRAND NEW HEAVY DUTY 12 in. SPEAKERS
 Response 45 c/s-13 Kc/s. 1 1/2 in. voice coil. Avail-
 able in 3 or 15 ohm. Guaranteed full 15 watts
 British rating. Heavy cast aluminium frame.
 These are current production by world famous
 maker and as they are offered well below list price
 we are not permitted to disclose the name.
**LIMITED NUMBER ONLY. UNREPEAT-
 ABLE AT 59/6, P. & P. 5/-.**

SPEAKER AND CABINET FABRIC
 Oatmeal or Red and Gold Vynair for speaker
 and cabinet covering, also Red Rexine for cabinet
 covering only. All 5 1/2 in. wide and usually sold at
 35/- yard.

OUR PRICE 13/6 per yard length.

plus P. & P. 1/9 (Minimum order 1 yard). Send
 S A E for samples

BARGAIN OFFER CORNER

ROLA CELESTION. Approx 9 in x 6 in 3 ohm
 Middle register speaker. 10/6. P. & P. 2/6.

MAINS TRANSFORMER

Drop thru type. Tapped primary 110v., 200v.,
 220v., 240v., 320-0-320v. at 80mA and 6.3v.
 at 3 amps. Generous core. Stack size 3 1/2 x 2 1/2
 x 1 1/2 in. Weight 4 lbs. **ONLY 15/6.** P. & P. 3/6.
ACOS CRYSTAL MIKES. High imp. For desk
 or hand use. 1/2 in. sensitive. 15/6. P. & P. 1/6.
TSB CRYSTAL STICK MIKE. Listed at 45/-.
 Our price 18/6. P. & P. 1/6.

T.C.C. SUPPRESSOR CONDENSERS. 250v. A.C.
 .005 + .005 x 1.1 in tubular can 1 1/2 in. long x
 1/2 in. dia. 2 for 3/- Post free.

**TRANSISTOR DRIVER AND O/P TRANSFORM-
 ERS.** (Tapped 3 ohms and 15 ohms output).
 plus 4 suitable Transformers giving approx 1 watt.
 output. 30/- P. & P. 2/-.

CONDENSERS. 5,000 mF. 12 v. wkg. Size
 3 x 1 1/2 in. dia. 2/- each. P. & P. 6d. each.


**BRAND NEW PLESSEY 12v. 4 pin non-synch.
 vibrators.** Type 12 1.48D. **ONLY 8/6.** P. & P.
 1/6 each.

9-PUSH BUTTON SWITCH UNIT. 4 single pole
 changeover on each push-button. Approx.
 3 x 1 1/2 x 1/2 in. An absolute Bargain at 4/6 each.
 P. & P. 1/- each.

**MATCHED PAIR OF 24 WATT TRANSISTOR
 DRIVER AND OUTPUT TRANSFORMERS.**
 Stack size 1 1/2 x 1 1/2 x 1/2 in. Output trans. tapped for
 3 ohm and 15 ohm output. 10/- pair plus 2/-.
 P. & P. Worth double.

Harverson Surplus Co. Ltd. ▶

3-VALVE AUDIO AMPLIFIER MODEL HA34

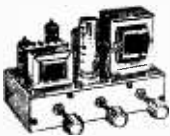

Designed for Hi-Fi reproduction of records A.C. mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. x 4 in. d. x 4 1/2 in. h. Incorporates EOC83, EL84, E280 valves. Heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, P. & P. etc., wired and tested for only **£4.50 P. & P.**


TAPE DECKS

COLLARO STUDIO DECK. £10.10.0 plus 5/6 carr and ins.
B.S.R. MORADECK. Single speed, 3 1/2 in. per sec., simple control using 5 1/2 in. spools. £8.15.0 plus 5/6 carr. and ins. (Tapes extra on both.)

STEREO AMPLIFIERS

Incorporating 2 ECL84s and 1 E280 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete

FEW
ONLY

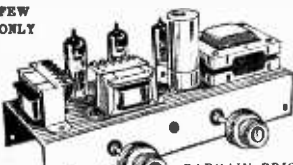

BARGAIN PRICE
89/6 P & P 5/-

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet
● Printed circuit panel (size 8 1/2 x 2 1/2 in.). ● 3 pre-aligned I.F. transformers. ● High-grain Ferrite rod aerial. x All First-grade transistors. ● Car aerial winding. ● push-pull output. ● All parts supplied with simple instructions.

All parts sold separately. Set of parts if purchased at one time.

ONLY £4.50 P. & P.

35 OHM SPEAKERS

Suitable for use with above. 2 in. Goodmans. Ideal replacement for most pocket portables. 8/8 1/2 in. 12/8; 5 in., 17/8; 7 x 4 in., 21/-.

P. & P. 1/6 per speaker.

PORTABLE CABINET

Size approx. 8 1/2 x 9 1/2 in. Suitable for above using 3 1/2 in. speaker. 25/-.

P. & P. 2/-.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (coil, loop and aerial coupling). 35/8 complete, post 1/-.

5 transistor printed circuit board to match. 8/6.

Post 8d. Circuit diagram 1/6 extra.

SPECIAL TRANSISTOR BARGAINS

ALL BRAND NEW

GET 15 (Matched Pair) 15/-
OC71 5/- OC72 6/- OC78 2/6
FXA101 6/6 XA103 6/6 V1510p 12/8
Set of Mullard 6 transistors. OC44 2-OC45.
OC81D matched pair. OC81. 25/-.

EDISMAN MAZDA

R.F.1 Pack: 1-FXA102 Mixer: 2-FXA101 L.F. Amp. (Equiv. OC44 and OC45)
R.F. 2 Pack: 2-FXA101 L.F. -FXA102 Osc.: 1-FXA102 Mixer: 12/6
L.F.6 Pack: Consisting of PXB118 Driver. Matched pair PXC171, mounted complete with heat sinks (Requ. OC81D and OC81) 12/6
ALL TRANSISTORS POST FREE

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. Size 7 1/2 in. x 2 1/2 in. d. x 5 1/2 in. h. This amplifier (which is used in a 29 gn. record player) employs EOC83 EL84, E280 valves. Bass treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested.

PRICE 49/6 P. & P. 3/6
ALSO AVAILABLE. Mounted on board with output transformer and 6 in. speaker, ready to fit into cabinet below. **PRICE 110/6 P. & P. 4/6.**

QUALITY PORTABLE RECORD PLAYER CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. Size 18 x 14 x 8 1/2 in.

PRICE £3.9.6 Carr. 5/-.

EMBASSY PORTABLE RECORD PLAYER CABINET. Will accommodate amplifier, up to 7 x 4 in. speaker and B.S.R. or GARRARD auto-changer or single player unit. Attractive rexine covered finish. Overall size 17 x 15 x 8 1/2 in. Supplied with uncut motor board. **PRICE 69/6 Carr. 5/-.**

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Makers' Original Packaging

SINGLE PLAYERS

B.S.R. TU12 £9.10.0 Carr. 3/6.

B.S.R. GU7 with unit mounted pick-up arm £4.18.8 Carr. 4/-.

AUTO CHANGERS

B.S.R. UA14 £5.19.6

Latest B.S.R. UA16 £10.18.6

Garrard AT6 Mono £10.10.0

LATEST GARRARD AUTO-SLIM. With heavy duty, 4-pole motor. FEW ONLY £7.7.0. (Standard Auto-Slim £8.10.0). Carr. 5/- on each.

NEW CARTRIDGE BARGAINS!

B.S.R. T088. High output compatible Stereo Cartridge. Brand new. Complete with Stereo LP/78 sapphire stylus and universal mounting bracket. Original price 44/11. OUR PRICE 22/6. P. & P. 1/-.

RONETTE STEREO 105 CARTRIDGE. Stereo/LP/78. Complete with two sapphires. Original list price 67/8. OUR PRICE 24/-.

P. & P. 1/-.

COLLARO HI-FI STEREO 710 CARTRIDGE. Type "C". Complete with universal bracket and stylus for Stereo, L.P. and 78. Original list price 69/8. OUR PRICE 25/-.

P. & P. 1/-.

E.M.I. 4-speed Player and P.U.

FURTHER HUGE PURCHASES enables us to offer these at

67/6 P. & P. 4/6.

Heavy 8 1/2 in. metal

turntable. Low flutter

performance 200/250

v. shaded motor with

tap at 45v. for

amplifier valve filament

if required.

Turnover LP/78 head.

THE NEW HARVERSON KIT FOR THE HOME

CONSTRUCTOR

A really excellent

all purpose A.C.

phone or record

AMPLIFIER KIT

TYPE HSL 'FOUR'

3 VALVE, 4 WATT

USING EOC83.

EL84, E280

VALVES

Special features include:

● Heavy duty double-wound mains transformer

with electrostatic screen. ● Separate Bass, Treble

and Volume controls, giving fully variable boost

and cut with minimum insertion loss. ● Heavy

negative feedback loop over 2 stages ensures high

output at excellent quality with very low distortion

factor. ● Suitable for use with guinea micro

instructions enable even the inexperienced amateur

to construct with 100% success. ● Supplied

complete with valves, output transformer (3 ohms

only), screened lead, wire, nuts, bolts, solder etc.


(No extras to buy)

PRICE 79/6 P. & P. 6/-

Comprehensive circuit diagram, practical layout

and parts list 2/6. (Free with Kit).

10/14 WATT HI-FI AMPLIFIER KIT

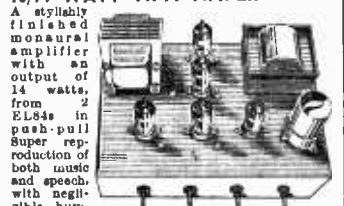

A stylishly finished monaural amplifier with an output of 14 watts, from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15 ohm speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, EF86 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).

All parts sold separately. **ONLY £6.19.6 P. & P. 6/6.**

Also available ready built and tested complete with standard input jack sockets. £8.15.0. P. & P. 6/6.

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI

● Peak output in excess of 1 1/2 watts. ● All standard

British components. ● Built on printed circuit

panel size 6 x 3 in. ● Generous size Driver and Output

Transformers. ● Output transformer tapped for 3

ohm and 15 ohm speakers. ● Transistors (GEX114

or 81 Mullard OC81D and matched pair of OC81 6p) or

99 volt operation. ● Everything supplied, wire

battery clips, solder etc. ● Comprehensive, easy to

follow instructions and circuit diagram 1/6 (Free with

Kit). All parts sold separately.

SPECIAL PRICE 45/- P. & P. 2/6

Also ready built and tested, 68/6. P. & P. 2/6.

A pair of TAI's are ideal for stereo

HARVERSON'S F.M. TUNER MK.

● F.M. tuning head by famous maker.

● Guaranteed no-drift

● Permeability tuning.

● Frequency coverage 88

100 Mc/s. ● 0.8 x 1

balanced diode output. ● Two L.F. stages and

discriminator. ● Attractive maroon and gold

dial (7 x 3 in. glass). ● Self powered, using a

good quality mains transformer and valve rectifier.

● Valves used EOC83, two EF86's, and E280

(rectifier). ● Fully drilled chassis. ● Size of

completed tuner 8 x 6 x 5 1/2 in. ● All parts sold

separately. Set of parts if purchased at one time

£6.19.6, plus 8/6 P.P. and ins. Circuit diagram and

instructions 1/6 post free. Mark II Version as above

but complete with magic eye, front panel and

brackets. £6.18.6. P. & P. 8/6.

Mark III Version as Mark I but with output stage

(ECL82) and tone control. £7.7.0. P. & P. 8/6.

Handsome Metal Cabinets. Choice of Grey, Black

or Green. To fit Mark I, 25/-.

To fit Mark II, 17/6. P. & P. 2/6.

To fit Mark III, 17/6. P. & P. 2/6.

SPECIAL PURCHASE!

TURRET TUNERS

By famous maker. Brand new and unused. Complete

with POC84 and PCF80 valves, 34-38 Mc/s I.F.

Biscuits for Channels 1 to 5 and 8 to 9. Circuit

diagram supplied. **ONLY 25/- each. P.P. 2/6**

BRAND NEW GYLDFON F.M. TUNER HEAD

Permeability tuned. 88-100 Mc/s Printed circuit.

A completely screened unit ready for direct mounting

in chassis. 10.7 Mc/s I.F. 0/P. Supplied complete

with EOC83 valve and full circuit diagram. Aerial

input circuit suitable for either 7 ohm unbalanced

or 300 ohm balanced. Size only 5 in. w. x 2 1/2 in. d.

x 1 1/2 in. h. (2 1/2 in. high with valve). Limited number

only at 87/6. P. & P. 1/6.

Also available 10.7 Mc/s I.F. trans. and disc. trans.

11/8 pair. P. & P. 1/6.

GÖRLER F.M. TUNER HEAD

88-100 Mc/s. 10.7 Mc/s I.F. 15/-, plus 1/9 P. & P.

(EOC83 valve, 8/6 extra).

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985

Open all day Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGED QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS

ORDERS CHARGED EXTRA.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE
LEFT
HAND
PAGE
FOR
MORE
ITEMS

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to success.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

Take the right course now . . .

ADVERTISING & ART

Copywriting
Layout & Typography
Commercial Illustrating
Oil & Water Colour

BUILDING & CIVIL ENG'NG

Architecture, Bricklaying
Building Construction
Builders' Draughtsman
Builders' Quantities
Interior Decoration
Quantity Surveying
Heating & Ventilation
Carpentry & Joinery

COMMERCE

Book-keeping
Accountancy & Costing
Business Training
Office Training
Purchasing, Storekeeping
Secretaryship
Short-hand & Typing
Computer Programming
Small Business Owners

DRAUGHTSMANSHIP

Architectural, Mechanical
Drawing Office Practice

ELECTRONICS

Computer
Electronic Technicians
Industrial Electronics

FARMING

Arable & Livestock
Fig & Poultry Keeping
Rabbits & Chickens

GENERAL EDUCATION

G.C.E. subjects at Ordinary & Advanced Level
Good English
Foreign Languages

HORTICULTURE

Home Gardening
Park Gardening
Market Gardening

MANAGEMENT

Business Management
Hotel Management
Industrial Management
Office Management
Personnel Management
Works Management
Work Study
Foremanship

MECHANICAL & MOTOR ENG'NG

Engineering Maths.
Diesel Engines, Welding
Industrial Instrumentation
Workshop Practice
Refrigeration
Motor Mechanics, etc.

POLICE

Entrance Examination
Police Promotion (Educ. Subj.)

PHOTOGRAPHY

Practical Photography

RADIO, TV & ELECTRICAL

Servicing & Engineering
Radio Construction (with Kits)
P.M.G. Certificates
Telecommunications
Electricians'
Electrical Contractors

SELLING

Company Reps.
Sales Management
Marketing

WRITING FOR PROFIT

Short-story Writing
Free-lance Journalism

INTENSIVE COACHING for all principal examinations —G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS (Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on

Name

Address

Occupation

10.64

INTERNATIONAL CORRESPONDENCE SCHOOLS

Designed for the electronics age . . .
PRIMAX and PRIMAXA solder guns

S
P
O
T
L
I
G
H
T

S
O
L
D
E
R

G
U
N
S



Distributed by **S. KEMPNER LTD.**

29 PADDINGTON ST., LONDON, W.1.

Tel: HUNter 0755

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94: Set of 4 for 15/-, DAF96, DF96, DK96, DL96: 4 for 22/6.

1A7GT	7/6	6X5GT	5/6	DF83	8/-	EF42	4/6	PCF84	5/-	U282	11/9
1D5	6/6	7B7	8/-	DF91	2/6	EF80	4/3	PCF86	8/-	U291	9/-
1H5GT	8/3	7C5	7/8	DF96	8/-	EF85	5/-	PCF86	14/-	U801	15/9
1N5GT	8/-	7C6	7/6	DH78	8/6	EF86	6/3	PCL82	6/6	U4020	5/9
1R5	4/9	7H7	5/9	DH77	8/6	EF89	4/3	PCL83	9/-	UABC80	5/9
1B5	3/9	7S7	14/3	DK32	8/-	FP91	2/9	PCL84	7/6	UAF42	8/-
1T4	2/6	7Y4	5/-	DK91	4/9	FP92	2/6	PCL85	8/6	UB41	6/3
3A5	6/9	10C2	12/3	DK92	6/9	EL33	7/6	PEN4DD	UBC81	7/3	
3A4	4/10	12AT6	4/3	DK96	6/6	EL38	11/9	18/6	UBF80	6/-	
3B4	4/9	12AT7	3/9	DL33	7/3	EL41	7/3	PEN44	6/6	UBF89	6/9
3V4	6/6	12AU6	5/-	DL35	6/9	EL84	7/6	PEN34	17/6	UC92	5/6
514G	4/6	12AU7	4/9	DL92	4/9	EM34	7/11	PEN383	9/6	UCC84	8/-
5Y3GT	5/-	12AX7	4/9	DL94	5/6	EM80	6/9	PL36	8/9	UCF85	6/9
5Z4G	7/-	12K7GT	4/3	DL96	6/-	EM81	7/9	PL81	7/-	UCF80	8/6
6AL5	2/-	12K8GT	6/9	EABCR80	6/3	EM84	6/3	PL82	6/6	UCH42	7/6
6A95	6/-	12Q7GT	4/3	EAF42	8/-	EM87	7/-	PL83	5/-	UCH81	6/6
6AT6	3/6	19B6G6	6/9	EB41	4/-	EY51	6/-	PL84	5/9	UCH82	7/6
6BA6	8/-	20P4	12/6	EB91	2/-	EY84	7/-	PK4	9/-	UCF83	8/3
6B66	5/3	20R5	14/9	EB93	5/-	EY86	5/3	PCX25	7/9	UP41	7/3
6B66G	12/6	25L6GT	4/9	EB41	7/3	EZ40	5/6	PY32	8/-	UF42	4/9
6BH6	5/6	25U4GT10/6	6/9	EBF80	6/-	EZ41	7/6	PY33	8/-	UF89	6/3
6J86	5/6	30L15	9/6	EBF89	6/-	EZ80	4/-	PY80	5/3	UL41	7/-
6P6G	3/9	30PL1	8/-	ECC40	7/6	EZ81	4/6	PY81	5/9	UL44	15/-
6F13	4/-	30PL13	9/-	ECC81	4/9	FW4500	6/3	PY82	5/-	UL46	8/6
6P14	9/-	30PL14	12/3	ECC82	4/9	KT32	5/-	PY83	8/9	UL84	6/3
6J5G	3/6	35A5	14/-	ECC83	7/-	KT61	7/6	PY88	7/9	UV7	6/6
6K74	1/6	35L6GT	6/3	ECC84	6/3	KT63	3/9	R17	15/-	U8	10/6
6K7GT	4/-	35Z4GT	4/11	ECC85	6/3	KT66	12/3	TID4	7/9	UY21	7/9
6K8G	4/3	35K11	13/6	EAP90	8/9	PCW4500	6/3	TH91C	8/6	UY41	4/9
8K84T	7/9	93KU	8/6	ECP82	6/3	NU14	5/-	TH233	6/9	UY85	5/-
6P28	9/6	AZ31	6/6	ECP86	10/9	N18	4/10	V22	4/9	VP41	4/9
6Q7G	4/9	B36	4/6	ECH35	6/-	PC95	9/-	V25	8/6	W76	3/6
6Q7GT	7/9	CUH35	12/3	ECH42	8/3	PC97	7/6	V26	8/6	W77	2/6
6L7GT	8/6	CL33	9/6	ECC81	6/-	PCV84	5/6	V47	8/6	W729	16/6
6S1GT	5/6	CV1	12/6	ECL80	6/3	PCV85	6/9	U50	8/-	X81M	19/6
6S1GTGT	3/9	DAC32	8/3	ECL82	7/-	PC88	8/9	U52	4/6	X109	17/6
6V6G	3/9	DAF96	6/9	EP39	3/9	PCF80	8/9	U91	8/6	Z66	7/-
6V6GT	6/6	DAF96	6/9	EP39	3/9	PCF80	8/9	U91	8/6	Z66	7/-
6X4	3/9	DOC90	6/9	EF41	6/6	PCF82	6/9	U281	8/6		

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON N.16
STA. 4587

Post 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d extra
Any C.O.D. Parcel 4/3 extra.

STERN-CLYNE

Electronics Centres throughout Great Britain

CHASSIS BARGAIN



A 6 valve Superhet Radiogram Chassis of outstanding quality covering MW 200/550 Metres. LW 1200-2000 Metres. VHF 87-100 Mc/s.

Incorporating internal Ferrite Rod Aerial and the famous Gorier Tuning Heart for VHF

Pick-up input suitable for most modern Record Players. Power output 4 watts, valve line up EZ80, EABC90, EF88, ECH71, EL84, ECC85. Volume On/Off and Tone Control, attractive black Tuning Dial size 15 x 6in. with gold lettering and contrasting cream and gold knobs. A.C. 200/250 v. Size 15 x 7 1/2 x 6 1/2 in.

PRICE 16 Gns. P. & P. 5/-
Or £3.9.0 deposit (plus P. & P.) and monthly payments of 32/8.

THE HE-30 4-BAND COMMUNICATION RECEIVER



One of the finest general coverage bandspread Receivers available at this price. Covering 550Kc/s—1800Kc/s. 4.8Mc/s—14.5Mc/s. 1.6Mc/s—4.8Mc/s. 10.5Mc/s—30Mc/s. Illuminated slide rule dial, calibrated every 5Kc/s on 80 and 40 metres. Edgewise S-meter. 0-100 logging scale, coverage from 9.55—30Mc/s. 8 valve plus Rectifier superhet circuit. RF stage with E.P.O. control Q-multiplier.

an Aerial Trimmer. 2 IF Stages. Controls: Function Switch, Audio Gain, Selectivity (Q-multiplier) Frequency (BFO), Band Selector, IF Gain Trimmer, AVC-MVC Switch, Ant Switch, Main Tuning, Bandspread Tuning and Head phone Jack. Selectivity—80dB at 10Kc/s. 0.8Kc/s at 6dB (with Q-multiplier) IF-455Kc/s. External FM Speaker reqd., 4 or 8 ohms impedance. Output 1.5 watts, 8 modern Miniature B7G Base Valves and 5Y3 Rectifier. Size 15 x 10 x 7 1/2 in. Grey crackle finish. 220/240 volt A.C. mains. 50/60 cycle operation. Full instructions and circuit diagram supplied. Send S.A.E. for leaflet.

PRICE 40 Gns. Carriage Paid

THE HE-30 COMMUNICATION RECEIVER (KT320). now available in sub-assembled form. All I.F. Transformers and coils are factory aligned and therefore only require peaking when receiver is assembled. Full easy-to-follow instructions supplied.

32 Gns. Post Paid

THE NEW HE-80 COMMUNICATION RECEIVER



The HE-80 has outstanding sensitivity 0-100 logging scale for instant re-set, built-in "S" meter special recording Jack, remote Control Socket allowing simultaneous control with transmitter. 100Kc crystal oscillator circuit providing accurate harmonic signals of either 4 or 8 ohms impedance. Two headphone sockets one high, one low.


TECHNICAL SPECIFICATIONS.

Frequency Coverage: Band 1 540—1635Kc/s; Band 2 1.6—4.9Kc/s; Band 3 4.8—14.5Mc/s; Band 4 10.5—30Mc/s; Band 5 144—146Mc/s. Band Spread (Ham Band directly read): 80 Metre Band; 40 Metre Band; 20 Metre Band; 15 Metre Band; 10 Metre Band. Sensitivity: 1 micro-volt for 10dB signal to noise ratio. Selectivity: Normal 10Kc at —75dB, 1.25 at —6dB. With Q-Multi: variable to 700 c.p.s. at 6dB. Operation: AM, SSB, CW and FM. AM diode detector. SSB/CW product detector (BFO). FM gated beam detector. Power Source: 240 volts 50/60 Cycles A.C. Power Consumption: 60 watts. Audio Output: 1.5 watts, 8 or 500 ohms impedance. Auxiliary Circuit: Electrical Bandspread, Q-Multiplier, ANL, AVC-MVC, BFO, 100Kc crystal calibrator. Valve Line-up: 4—6AQ8, 6BL8, 3—BA6, 2—6BE6, 6AL5, 5AQ5, OA2, 6CA4. Dimensions: 17 1/2 in. wide, 6 1/2 in. high, 10 1/2 in. deep.

PRICE 59 Gns. Carriage Paid

OUTSTANDING PRICE REDUCTION

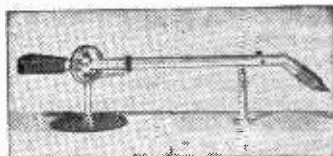THE B. & O.
ST/M PICKUP
COMPLETE
WITH SP 11
STEREODYNE
MAGNETIC
CARTRIDGE



A Transcription

Pickup of outstanding quality employing a specially designed counter balanced and unique weight adjustment. Specifications: Length 10 1/2 in. from tip of Cartridge. Height 2 1/2 in. Stereo/Mono Cartridge. Frequency Response: +2.5dB from 30 c.p.s. to 15 Kc/s. Output Voltage: 7mV per channel at 5 cm/sec. at 1000 c.p.s. Separation: 20dB minimum. DC Resistance: 1250 ohms. Inductance: 200mHs. Recommended Tracking Force: 2 to 4 grams. Compliance: 5 x 10⁻⁶ cm/dyn in all directions. Stylus: Diamond, radius of curvature: 7th. Recommended Load: 47000 ohms.

PRICE 9 1/2 Gns. Plus 3/6 P. & P.

THE HE-40 4-BAND COMMUNICATION RECEIVER

Completely built and ready to go. High sensitivity

Superhet receiver covering 550Kc/s—1.600 Kc/s, 1.6 Mc/s—4.4 Mc/s, 4.4 Mc/s—11 Mc/s, 11 Mc/s—30 Mc/s. Electrical Bandspread tuning. Slide rule type tuning dial. Internal ferrite rod aerial for medium waveband reception and 1 5/8 in. 10 section chromium plated telescopic whip aerial for the short wavebands. Sockets for optional outdoor aerial. Internal high flux monitor loudspeaker. Latest modern miniature ETC base valves. Headphone socket (may also be used for external loudspeaker). ANL, BFO, built-in "S" meter, 220/240 volt A.C. mains, 50/60 cycle operation. Handsomely styled cabinet with grey crackle finish and handsome front panel, with chrome and satin chrome fittings. Measures 13 1/2 in. x 8 1/2 in. x 5 1/2 in. (high) and weighs only 11 1/2 lb. A comprehensive instruction manual is supplied. An ideal receiver for the radio amateur and short wave listeners of all ages. Send S.A.E. for leaflet.

PRICE £24.15.0 Carriage Paid

"STARFLITE" TRANSMITTER



Designed to meet the needs of most amateurs the Starflite has single-knob band-switching, front panel switch to select any of five crystal positions with provision for an external VFO. Controlled carrier modulator permits almost 100% of the CW input to be used on AM peaks. Grid-block keying provides chirp-free operation. A full wave silicon diode power supply effects extremely low output ripple for cleaner CW transmission, electron-coupled Pierce Oscillator, capacitance bridge neutralisation of the final and a three-stage lowpass filter. An illuminated edgewise D'Arsonval panel meter. Pi-network output provides the correct impedance match between the plate circuit and any 50-72 ohm co-axial feeder. Easy to follow point-to-point instructions supplied with each set of components. When constructed the Unit is housed in a heavy gauge steel Cabinet finished in grey crackle.

SPECIFICATIONS: Power input—20 watts peak; Operation: C.W., AM Phone—crystals or VFO Control; Band coverage: 80-10 metres; Coupling: Pi-network; Valve Line-up: 6146, (2) 6CL6, 12AX7, 6DE7, Low Pass Filter. Size 13 1/2 in. wide x 12 1/2 in. deep (inc. knobs) x 6 1/2 in. high (inc. rubber feet). Weight 28 1/2 lb. Power requirements, 200/240 v, 50/60 c.p.s. 225 watts.

MAY BE BUILT FOR 35 Gns. Carriage & Insurance 15/-

SEE FOLLOWING PAGES FOR ADDRESSES AND OTHER ITEMS

STERN-CLYNE

Electronics Centres throughout Great Britain

MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV.

★ Equalisation for the latest R.I.A.A. characteristics. ★ Inputs for Crystal Pickups and variable reluctance magnetic types. ★ Input (a) Direct from High Imp. Tape Head, (b) From a Tape Amplifier or Pre-Amplifier. ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls.

KIT OF PARTS £6.60 (Carr. & Ins. 5/-)
ASSEMBLED AND TESTED £9.10.0 (Carr. & Ins. 5/-)
Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. incorporates 5 Input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 150 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case Size 111 x 41 x 41.


KIT OF PARTS £10.0.0 (Carr. & Ins. 5/-)
ASSEMBLED AND TESTED £13.13.0 (Carr. & Ins. 5/-)
Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



MULLARD "5-10" MAIN AMPLIFIER

For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS and MULLARD VALVES including PARTRIDGE MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer. **COMPLETE KIT £10.0.0** (Carr. & Ins. 6/6). **ASSEMBLED AND TESTED £13.13.0** (Carr. & Ins. 6/6).

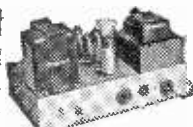ABOVE incorporating PARTRIDGE OUTPUT TRANS. £1.6.0 extra. Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



COMBINED PRICE REDUCTION


MULLARD 5-10 Main amplifier and 2 valve Pre-Amp. Kit £15.15.0. C. & I. 8/6. Built and tested. £21.10.0. C. & I. 8/6.
MULLARD 5-10 Main Amplifier and 3 valve Pre-Amp. Kit £19.10.0. C. & I. 8/6. Built and tested. £25.10.0. C. & I. 8/6. With Partridge Transformer £1.6.0 extra.

THE MULLARD 5-10RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 500mV. Specified components and new MULLARD VALVES. Includes PARTRIDGE MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus power available for Tuner.

COMPLETE KIT £12.0.0 (Carr. & Ins. 7/6).
ASSEMBLED AND TESTED £16.0.0 (Carr. & Ins. 7/6).

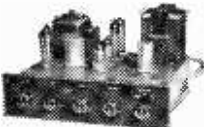Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



THE MULLARD 3-3RC

A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

KIT OF PARTS £8.8.0 (Carr. & Ins. 6/6).

ASSEMBLED AND TESTED £11.10.0 (Carr. & Ins. 6/6).

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and

L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. Please state L.S. impedance. Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1 track, Mono Tape Decks. Incorporates Ferroxcube Push-Pull Oscillator. Treble Inductor and 3-sp. Equalisation. Includes separate Power Unit.

KIT OF PARTS £14.0.0 (Carr. & Ins. 7/6). **ASSEMBLED £19.10.0** (Carr. & Ins. 7/6).

Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve separate BASS and TREBLE controls. PARTRIDGE output Transformer producing up to 3 watts undistorted output.



KIT OF PARTS £4.10.0 (Carr. & Ins. 3/6). **ASSEMBLED £6.0.0** (Carr. & Ins. 3/6).
Instruction book and detailed price list (free with kit) available separately at 2/6 Post Free.

Perfectly suited for Portable Installations for which purposes we offer PORTABLE CASE (£3.10.0), the **AMPLIFIER (Kit £4.10.0)** and **8" x 5" SPEAKER (£1.0.0)**. All for **£9.0.0** (Carr. & Ins. 3/-).

Alternatively with **ASSEMBLED AMPLIFIER £10.0.0** (Carr. & Ins. 3/-).

The Case quoted above will accommodate some 4-speed Single Record Units. A larger model is available for extra 10/-.

With this Equipment a **COMPLETE PORTABLE RECORD PLAYER** can be built for **£14.0.0** (Carr. & Ins. 3/-).



MODEL CR3/S TAPE RECORDER

MODEL CR3/S incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin-Track 3-speed Deck operating at 1in., 3in. and 7in. speeds. Complete with microphones and 1,200ft. tape.

KIT OF PARTS £33.0.0 (Carr. & Ins. 15/- extra).
ASSEMBLED AND TESTED £43.0.0 (Carr. & Ins. 15/- extra).

STEREO TAPE PRE-AMPLIFIER

MODEL STP-1. For use with current TRUVOX, BRENNEL or COLLARO "STUDIO" 1 and 1 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4-speed Equalisation Signal Lever Meter and separate Gain Control. Includes separate Power Unit. **KIT OF PARTS £22.0.0** (Carr. & Ins. 8/6). **ASSEMBLED £28.0.0** (Carr. & Ins. 8/6).

Instruction book and detailed price list (free with kit) available separately at 5/- Post Free.



MULLARD TAPE AMPLIFIER

MODEL HF/TR3 MK. II Based on Mullard's Type "A" design and suitable for most 1 track Mono Tape Decks. Incorporates Ferroxcube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit, using PARTRIDGE Mains Transformer.

KIT OF PARTS £13.13.0 (Carr. & Ins. 7/6). **ASSEMBLED £19.0.0** (Carr. & Ins. 7/6).
Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.



COMBINATION TAPE UNITS

All our Tape Units can be supplied specially matched to any Tape Deck such as Collaro, Brenell Mk.5 Series II, also the Wearite. Specimen prices as below.

	Kit	Assembled
STP-1 Pre-amp with Collaro Studio Tape Deck.....	£36. 0.0	£42. 0.0
Assembled with track switch fitted, £44.2.0		
STP-1 with Brenell Mk. 5 Series II with Track Switch fitted.....	£68. 4.0	
STP-1 with Brenell Mk. 5 Series II, 1 Track Deck.....		£74.15.0
Type "C" Pre-amp with Collaro Studio Tape Deck.....	£24.10.0	£30. 0.0
Assembled with deck wired and matched, £32.2.0		
Type "C" Pre-amp with Brenell Mk. 5 Series II Deck.....	£46.11.0	£53. 1.0
Assembled with deck wired and matched, £55.3.0		
HF/TR3 with Collaro Studio Tape Deck.....	£24. 3.0	£29.10.0
Assembled with deck wired and matched, £31.12.0		
HF/TR3 with Brenell Mk. 5 Series II Deck.....	£46. 4.0	£51.11.0
Assembled with deck wired and matched, £55.13.0		

Carr. & Ins. 15/- on above units. Send S.A.E. for comprehensive price list.

SEE PRECEDING PAGE FOR
OTHER STERN-CLYNE PRODUCTS

SEND FOR CURRENT PRICE LIST OF ALL LEADING RECORDING TAPES AND ACCESSORIES

STERN-CLYNE

Electronics Centres throughout Great Britain

THE TUDOR STEREO HI-FI SYSTEM




Comprising a Self Powered AM/FM Tuner, Stereo Pre-amplifier, 12 watt per channel Stereo Power Amplifier. The Tuner and Pre-amplifier are housed in matching black crackle finish metal cabinets (or shelf mounting, with silver metal dials and matching knobs. Specifications: **Tuner:** Outstanding quality providing full VHF/FM long and medium waveband coverage, frequency range FM 87.5-108.3 Mc/s, AM/MW 522-1650 Kc/s, LW 117-270 Kc/s, 100 mV output mains supply 105/240 A.C. Valve line-up: ECC83, ECH81, 6BF9, 6B9, EM84, ECC83. Multiplex outlet provided. **Pre-amplifier:** Designed for use with Tudor Stereo Power Amplifier with inputs for most types of pickups, direct play from Tape Heads and ample sensitivity for either Crystal or Moving Coil Microphone. Distortion 0.1%, tape outputs 100 mV from 90 K ohm source. Inputs—Microphone 5 mV, Tape 5.9 mV, R.I.A.A. 4.5 mV flat 250 mV. Tuner: 100 mV. Valve line-up: 2—ECC83, 1—ECC83, 1—6B9, 1—6B9.

AM/FM TUNER AVAILABLE AT 24 GNS. P. & P. 7/6.
STEREO PRE-AMPLIFIER AND POWER AMPLIFIER TOGETHER AT 24 GNS. P. & P. 10/-.

DUE TO PRODUCTION STREAMLINING WE ARE PLEASED TO ANNOUNCE REDUCTIONS IN PRICE!

★ J.L.10 POWER AMPLIFIER

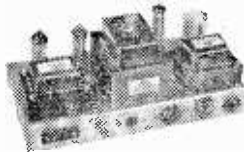

Incorporates the latest triode-pentode ECL86 valves in push-pull, PARTRIDGE ultra linear output transformer. PARTRIDGE mains transformer and smoothing choke, 10 watts power output, surplus power available for tuner, output impedance 3—7.5—15 ohms.

KIT OF PARTS £10.0.0 C. & I. 7/6
READY BUILT £13.13.0

★ DOUBLE FEATURE PRE-AMPLIFIER



Inputs for microphone, crystal or magnetic pickups, tuner unit, and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape unit deck. Push-button switching for 3 tape speeds equalised. Tape erase Bias Oscillator circuit incorporating ferro-cube transformer. Function switch, separate base, treble and volume controls, level control and latest EM87 music eye level indicator. The pre-amplifier is totally enclosed in a silver hammer finish steel case, and an attractive perspex front panel completes the presentation.

KIT OF PARTS £13.13.0 READY BUILT £19.19.0c. & I. 5/-
PRICES: If both above units are purchased together:
KIT OF PARTS £23.13.0 READY BUILT £32.0.0 C. & I. 10/-


SEND STAMP FOR COPY OF OUR INTERESTING LITTLE BOOKLET "What is High Fidelity?"

STEREO TAPE-DECK WITH BUILT-IN PRE-AMPLIFIER

A professional addition to your Hi-Fi Stereo System consisting of two basic units, the Tape Deck and Pre-amplifier, which employs 4 Transistors and 4 Valves. The Unit with record and playback 1 track stereo or 1 track mono at either 7 1/2 i.p.s. or 3 1/2 i.p.s. both speeds being fully equalised.

Features: Track System: 1 track 2 channel stereo or monaural record and playback. Independent single channel recording on either channel while playback on other channel. **Head Type:** 1 track 2 channel line stereo and a-associated erase heads. Low loss laminated pole pieces. Level indicators: 2 Meters, 1 per channel. Digital Counter: 3 digit tape position indicator. **Automatic Stop:** When tape runs out or breaks. **Inputs:** Microphone 1mV (50K ohms impedance) Gram/Tuner 50mV (high impedance). Output: (cathode follower). Monitor Sockets: 2 x 5 K ohms impedance. Audio Output: 500mV. Oscillator: Push-pull 80 Kc/s. S/N Ratio: —45dB or better at 7 1/2 i.p.s. tape speed. Separation: 45dB or more between stereo channels. Frequency Response: 40 to 15,000 cycles per sec. at 7 1/2 i.p.s., 40 to 9,000 cycles per sec. at 3 1/2 i.p.s. **Single Motor:** 4 pole heavy duty induction type. Power Supply: 240V A.C. 50 cycles. Size 6 1/2 x 10 1/2 x 15 1/2. Tape Size: Up to 7 1/2 in. Line up: 4—2SB173 Transistors, 2—12AT7, 1—1AU7, 1—12BH7 Valves.

THE 'HIGHWAYMAN'

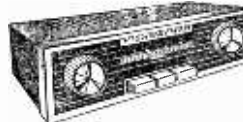

OUR QUALITY CAR RADIO TO BUILD YOURSELF AT A NEW LOW PRICE

Look at these features:

★ Attractively styled. ★ Push-pull output. ★ Three latest Mullard transistors plus valves types EBF83 and ECH83. ★ No Buzz, high output and sensitivity. ★ Printed circuit (latest type), 7 x 4 1/2 in. high flux p.m. speaker and baffle. ★ Medium and Long Waves. ★ Push button for fingertip control. ★ Extremely low battery consumption (less than 1 amp.). ★ Easy to fit any make car (Positive earth only). ★ 12-volt operation. ★ Compact size, measures only 7 x 7 x 2 1/2 in. deep. ★ Easy assembly, supplied with dial and drive already mounted.

Special inclusive price of ONLY £7.19.6 Plus 5/- P. & P. All parts available separately. Individually priced parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later). **Optional extras, 3 section chromium plated weatherproof telescopic aerials type 1 17/41, 19/6; type 2, 27/43, 29/6, both plus P. & P. 2/6 if purchased separately.**

AGOS MONAURAL STETHOSCOPE HEADSETS Suitable for Tape Recorders, or monitoring tape recorders (100 ohm impedance magnetic. Complete with lead. 12/6 P. & P. (Originally 21/-). **OUR PRICE £12/6 P. 1/6**

NEWS FLASH !!


YET ANOTHER NEW ELECTRONICS CENTRE OPENING SHORTLY AT 125, THE MOOR, SHEFFIELD

WEST END:	18 Tottenham Court Road, W.1.	MUSEum 5929/0095	Half-day Sat
(Premier Radio)	23 Tottenham Court Road, W.1.	MUSEum 3451/2	Half-day Thurs
(Premier Radio)	309 Edgware Road, W.2.	PADddington 6963	Half-day Thurs
CITY:	109 Fleet Street, E.C.4.	FLEEt St. 5812/3	Half-day Sat
NORTH LONDON:	162 Holloway Road, N.7.	NORth 7941	Half-day Thurs
SOUTH LONDON:	9 Camberwell Church Street, S.E.5.	RODney 2875	Half-day Thurs
CROYDON:	12 Suffolk House, George Street.	MUNicipal 3250	Half-day Wed
BRISTOL:	26 Merchant Street, Bristol 1.	Bristol 20261	Half-day Wed
LIVERPOOL:	52 Lord Street, Liverpool.	Royal 7450	
MANCHESTER:	20/22 Withy Grove, Manchester 4.	BLAckfriars 5379	Open 6 days a week

Mail Orders and enquiries to Dept. P.W. 3/5 Eden Grove, Holloway, London, N.7.

THE TRIPLETONE HI-FI MAJOR

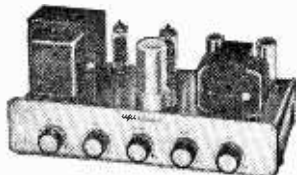PRICE ONLY **£15.18.9** COMPLETE
Guaranteed 12 Months



A 12 watt quality amplifier incorporating negative feedback, with a pre-amp for mic. and provision for mic./gram mixing. Frequency response ± 1 dB 15-20,000 c/s. Distortion only 0.15%, with noise and hum ~ 50 dB. Separate Bass, Middle and Treble lift controls. Valve line-up, 12AX7, 12AX7, EL84, EL84 and E281. Push-pull output with matching to 3 or 15 Ω . Fully isolated power supply from 200/250 v. A.C. input, with take-off for tuner etc. Size 12 x 5 1/2 x 6 1/2 in.

De Luxe Case: 14in. x 9in. x 7 1/2in. 30/- extra

New R.C.S. VALVES 90-day Guarantee

1R5	6/-	6QTG	6/-	EB4C1	8/-	PCL84	6/-
1S5	6/-	68N7	6/-	EB5C1	5/-	FL81	10/-
1R4	6/-	6V6G	5/-	EBF80	5/-	FL82	8/-
354	7/-	6X4	5/-	ECH42	9/-	PY80	8/-
3V4	7/-	6X5	6/-	ECH81	9/-	PY81	8/-
5U4	6/-	12AT7	6/-	ECH180	9/-	PY82	7/-
5Y3	6/-	12AU7	6/-	ECL32	10/-	SP61	3/-
5Z4	9/-	12AX7	7/-	EF183	7/-	U22	7/-
6AM6	6/-	12K8	14/-	EF86	10/-	UBC41	8/-
6AT6	6/-	12Q7	7/-	EF89	9/-	UBC81	6/-
6BA6	6/-	25Y6G	9/-	EL84	7/-	UBF80	6/-
6BE6	6/-	35L6	9/-	EY31	9/-	UCL82	10/-
6BE6	6/-	35Z4	8/-	EZ40	9/-	UF89	5/-
6J5	5/-	954	2/-	EZ80	7/-	UL41	9/-
6J6	5/-	DAF96	8/-	EZ81	7/-	UY41	6/-
6J7G	6/-	DF96	8/-	EC281	7/-	UY45	7/-
6K6	5/-	DK96	8/-	MU14	7/-	VR15	7/-
6K7G	6/-	DL96	8/-	PC97	7/-	VR15	7/-
6K8G	5/-	EAB080	5/-	PC84	8/-	VR150	7/-
6N7M	5/-	EB91	4/-	PCF80	5/-	W81	6/-

L.F. TRANSFORMERS 7/6 pair
465 Kc Sing Tuning Miniature Can. 2 x 1 x 1 in.
High Q and good bandwidth. Data Sheets.

NEW ELECTROLYTICS

TUBULAR	TUBULAR	CAN TYPES
1/350V 2/-	50/350V	5/6/8/1000V 9/-
2/350V 2/3	100/25V	2/- 16/450V 5/-
4/450V 2/3	250/25V	2/- 16/600V 12/-
8/450V 2/3	100/12V	3/- 16 + 16/500V 7/8
16/450V 3/1	1,000/12V	3/- 32 + 32/350V 6/6
32/450V 3/1	5,000/6V	5/- 32 + 32/450V 6/-
55/25V 1/8	8 + 8/450V	3/6 32 + 32 + 16/350V 7/-
25/50V 2/1	8 + 16/450V	3/6 50 + 50/350V 7/-
50/25V 2/1	16 + 16/450V	4/3 64 + 120/350V 11/6
50/50V 2/1	32 + 32/350V	4/6 100 + 200/275V 12/6

TELESCOPIC CHROME AERIALS. 12 to 33in. 8/6.
TRIPLETS Bands I, II, III. 12/6. COAX PLUGS 1/1.
LEAD SOCKET, 2/-; PANEL SOCKETS, 1/1.
OUTLET BOXES (Surface or flush), 4/- ea.
BALANCED TWIN FEEDER yd. 6d. 30 or 300 ohms.
TWIN SCREENED per yd. 1/- 80 ohms only.
Wirewound Int. Speaker Control, 10 x 3 1/2, 25 Ω 6/6.
WIRE-WOUND POTS. 3 WATT. Preset Min. Taper Types. All values to 10 ohms to 25 K, 3/- ea. 30 K, 4/- (Carbon 30 K to 2 meg, 3/-).
WIRE-WOUND 4 WATTS Pots. Long spindle. Value, 50 ohms to 50 K, 6/6; 100 K, 7/8.
PHILIPS TRIMMERS. 0-10 pF, 3-30 pF, 1/-.
TRIMMERS. Ceramic, 30, 50, 70 pF, 9/-; 100 pF, 150 pF, 1/3; 250 pF, 1/8; 500 pF, 750 pF, 1/8. T/T etc. TRIMMER, 1000 pF, with knob, 2/-.
RESISTORS. Preferred values. 10 ohms to 10 meg. 1 w., 1/4 w., 1/2 w., 3/4 w., 1 w., 1 1/2 w., 2 w., 3 w., 5 w., 10 w., 15 w., 25 w., 50 w., 100 w. High stability. 1 w., 1/4 w., 1/2 w., 3/4 w., 1 w., 1 1/2 w., 2 w., 3 w., 5 w., 10 w., 15 w., 25 w., 50 w., 100 w. 10 Ω to 10 meg. Ditto 5% 10 Ω to 22 meg. 9d. BRIMSTONS C21, 3/8; C22, 2/8; C23, 1/6.
5 watt WIRE-WOUND RESISTORS 1/3
10 watt 10 ohms-10,000 ohms 2/-
18 watt 10 ohms-10,000 ohms 2/-
12.5 K to 25 K 10 w. 3/-
Toggle Switches, s.p., 2/-; d.p., 3/6.
d.p.d.c., 4/-; Min. Slide d.p.d.c., 3/6.

Volume Controls 80 ohm COAX CABLE
Linear or Log Tracks
Long spindles, Midget
5 K ohms to 2 Meg.
L.S., 8/-; D.P., 4/6.
Ideal 625 lines.
Stereo L810/8; D.P. 14/6
1m. log + 1m. A/Log, 7/6

MAINS TRANSFORMER 200/250 v. A.C.

Postage 2/- each transformer
STANDARD. 250-0-250, 80mA, 6.3 v. 3.5 a. tapped 4 v. 4.4. Replier, 3.3 v. 1 a., 3 v. 2 a. or 4 v. 2 a., 22/8, ditto, 350-0-350 29/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 10/8
MIDGET, 220 v. 45 mA, 6.3 v. 2 a. 15/8
SMALL, 250-0-250, 45 mA, 6.3 v. 2 a. 17/8
STD. 250-0-250, 65 mA, 6.3 v. 3.5 a. 17/8
HEATER TRANS. 6.3 v. 11 a. 7/8
Ditto, tapped 1.4, 2, 3, 4, 5, 8.3 v. 8/8
Ditto, sec. 6.3 v. 4 amp. 10/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/8
AUTO TRANSFORMERS, 150 w. 22/8
0, 110, 220, 230, 250 v. 500 w. 28/8
MULLARD "510" Mains Transformer 33/8
MAINS POWER PACKS. Ready built with Transformers, Rectifiers, Condensers, providing H.T. and L.T. outputs.
200 v. 20 ma. D.C. 6.3 v. 1 a. A.C. 25/8
220 v. 50 ma. D.C. 6.3 v. 2 a. A.C. 45/8
250 v. 80 ma. D.C. 6.3 v. 3.5 a. tapped 4v. 45/8
and 6.3 v. 1 a. tapped 5v. 4v. 2a.

INTERVAL TRANSFORMERS. 3:1 or 5:1. 9/-
O.P. TRANSFORMERS. Heavy Duty, 5/6. Multi-ratio, 7/8. Multiratio heavy duty push-pull, 10 w. 15/8. Battery, 4/8. Sub. min. D106, 3V4, etc. 5/8. 10w. O.T. matching trans. 3, 7, 15 Ω , 12/6.
L.F. CHOKES. 15/104, 90/65 mA. 5/-; 10H. 85 mA. 10/8, 10H. 150 mA. 14/-.

C.R.T. BOOSTER TRANSFORMERS for heater cathode short circuit or with failing emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost 2v. or 4v. or 6.3v. or 10v. or 12v. State Voltage required. PRICE 10/8.

TINNED COPPER WIRE 16 to 22 swg., 1lb. 3/8. ENAMEL COPPER WIRE 16-22. 2/8; 24-30. 3/8; 32-40. 4/8; D.C.C. 28, 34, 38 swg. 2oz. 3/8.
FULL WAVE BRIDGE SELENIUM RECTIFIER. 2, 6 or 12 v. 1 1/2 amp. 8/8; 2 a. 11/8; 4 a. 17/8.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps. 15/6; 2 amps. 17/8; 4 amps. 22/8. Circuit included.
4 AMP CAR BATTERY CHARGER with ammeter, Leads, Fuse Case, etc. for 6 v. or 12 v. 59/8.

BOOKS list S.A.E.


Boys' Book of Crystal Sets. 2/6
"W.W." Radio Valve Data. 7/8
High Fidelity Speaker Enclosure 5/-
Valve and TV Tube Equivalents. 4/6
TV Fault Finding. 5/-
Mullard Amplifier Manual. 8/8
Radio Valve Guide, Books 1, 2, 3, 4 or 5 5/- each
Practical Radio Inside Out. 3/6
Master Colour Code Chart. 1/8
Transistor Controlled Models. 7/8
International Radio Stations. 2/6

4 TRANSISTOR PUSH-PULL

Size 3 1/2 x 1 1/2 in. AUDIO AMPLIFIER
A ready built miniature push-pull amplifier with Driver and output transformers, 4 transistors. Ideal for use with record players, intercoms, BABY ALARMS, etc. Complete with full instructions and circuit.

Price 47/6. 9v. Batt. 2/3. 2 1/2 in. Speaker 15/-

1964 RADIOGRAM CHASSIS

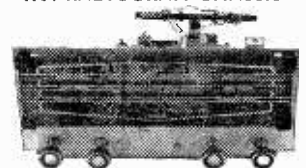

THREE WAVEBANDS FIVE VALVES
S.W. 16 m.—50 m. LATEST MULLARD
M.W. 200 m.—550 m. ECH81, EF89, EBC81,
L.W. 800 m.—2,000 m. EL84, EZ80
12-month Guarantee
A.C. 200/250 v. Short-Medium Long/Gran.
Ferrite Aerial A.C.V. 3 ohm output, 5 watts.
Tape Sockets. Glass dial, horizontal wording
size 13in. x 7in. Aligned and calibrated, isolated
Chassis size 14 1/2 in. x 7in. high x 5 1/2 in. deep.
£9.15.6 Carr. & Ins. 4/6.

Post 1/- (unless otherwise stated)
C.O.D. 2/- extra.

Our written guarantee with every purchase
NEW COMPONENTS LIST 1/-

BAKERS
'Selhurst'
—RADIO—

THE
CONNOISSEUR'S
CHOICE

"none genuine
without this seal"



8in. JUNIOR SPECIAL Sw.
Foam Suspension 40-20,000 c.p.s.

5 gns.

12in. STALWART HEAVY DUTY 15w. 5 gns.
45-15,000 cps. 3 or 15 ohm valve coils. Unlimited
Applications. Response 45 to 15,000 cps.
magnet 12,000 lines. Usability unbeatable.

12in. STANDARD HEAVY DUTY 20w. 7 gns.
More powerful magnet 14,000 lines special suspen-
sion. 40-14,500 cps. Recommended where-
ever a high standard of reproduction is desired.

12in. BASS HEAVY DUTY 25w. 12 gns.
New 1964 high power model. Aluminium coil
former with magnetic damping 25-15,000 cps.
Ideal for all electric circuits.

15in. AUDITORIUM MODEL 35w. 18 gns.
Improved magnet alcomax with heavy plated
steel plates, weight 18lbs. 17,000 lines, 20-
12,000 cps. Solid heat proofed Parolin Coil
Former. Ideal for all Electric Circuits.

LOUDSPEAKERS P.M. 3 OHM. 2 1/2, 3, 4, 5in.
7 x 4in. 15/6; 4in. Kola, 16/8; 8in. Plessey, 17/8;
9 x 6in. 5 x 5in. 21/-; 8 x 6in. 22/8; 10in. Kola
300/-; 12in. R.A. 30/-; EMI Double Cone Ceramic
magnet 10 x 13 x 5in. 45/-; Horn Tweeter, 28/8;
STENTORIAN HF1012. 10in. 3 to 15 ohms 10w.
82/-; 8in. HF124. 7 1/2; Crossover CX3000. 23/-.
EXTENSION SPEAKER CABINET. 8in. 15/6;
6in. 18/8; 8in. 19/8; 10in. 29/8; 12in. 30/-.
TWIN GANG TUNING CONDENSERS. 365 pF.
miniature 1in. x 1 1/2 in. x 1 1/2 in. 500 pF standard
with trimmers. 9/-; midget, 7/8; with trimmers. 9/-.
500 pF slow motion tuning standard. 9/-; Transistor
gang 208 + 175 pF with trimmers. 10/8. SMALL.
3 gang 500 pF. 17/-; SINGLE 365 pF. 7/8. SINGLE
10 pF. 25 pF. 50 pF. 100 pF. 150 pF. 5/8.
Solid dielectric 100, 300, 500 pF. 3/6.
CONDENSERS. New stock. 0.001 mfd. 7 v. 8/8;
T.C. 5/8; Ditto, 20 kV. 9/8; 0.1 mfd. 7 kV. 9/8;
Tubular 500 v. 0.001 to 0.05 mfd., 9d.; 0.1, 1/-;
0.25, 1/6; 0.5/350v., 1/8; 0.5/500v., 9d.; 0.01/2,000v.
0.1/1,000v., 1/8; 0.1 mfd., 2,000 volts, 3/6.
CERAMIC CONDS. 500 v. 1 pF to 0.01 mfd., 9d.
SILVER MICA CONDENSERS. 10% 5 pF to 500 pF.
9d.; 600 pF to 3,000 pF. 1/-; Close tolerance
(-10 pF) 2.2 pF to 47 pF. x. Ditto 1% to 50 pF
to 815 pF, 1/-; 1,000 pF to 5,000 pF, 1/8.

FERGUSON QUALITY AMPLIFIER 4 watts
Size 6 1/2 x 5 x 1 in. Mains Transformer, 200/
250V. Volume and tone controls. Sensitivity
200 m.v. Response 25 to 20,000 cps. Price 49/6,
or 2 units matched for Stereo, 89/6.


WAVECHANGE SWITCHES

8 p. 4-way 2 wafer long spindle 6/6
2 p. 2-way or 2 p. 6-way long spindle 3/6
4 p. 4-way or 4 p. 6-way long spindle 3/6
3 p. 2-way or 1 p. 12-way long spindle 3/8
Wavechange "MAKITS" 12 v. wafers available
in 1 p. 12 way, 2 p. 6 way, 3 p. 4 way,
4 p. 3 way, 6 p. 2 way, 1 wafer switch, 8/6;
2 wafer switch, 12/8; 3 wafers switch, 16/-;
additional wafers up to 12. 3/6 each extra.
Valveholders. EA50, 6d. B12A, CRT, 1/3
EMI and Amer. 4, 5 and 7 pin. 1/-.
Moulded Mazda and int. octal, 6d.; BTG.
B8A, B8G, B9A, 9d.; Ceramic EF50, BTG, B9A.
int. oct. 1/-; BTG. B9A cans 1/- each. Valve
plugs BTG. B9A int. octal, 2/3.

HIGH GAIN TV PRE-AMPLIFIERS

B.B.C. Channel 1 to 5. Gain 18dB.
ECC84 valve. Kit price 29/8 or 49/8
with power pack. Details 6d. (PC84
valve if preferred). Coils only 9/6.
BAND III I.T.A.—Same prices.
Tunable channels 7 to 13. Gain 17dB.
Circuit and coils only. 9/6. Chassis 4/9.

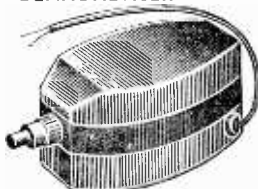THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 200/250 V. A.C.



35/-

Leaflet S.A.E.

PLASTIC RECORDING TAPE

Double Play	7in. reel, 2,400ft. 42/-	Spare Plastic Reels
	5in. reel, 1,200ft. 25/-	
Long Play	7in. reel, 1,800ft. 22/6	3in. 1/6
	5in. reel, 1,200ft. 17/6	4in. 2/6
	5in. reel, 900ft. 15/6	5in. 2/-
Standard	7in. reel, 1,200ft. 17/6	5in. 2/6
	5in. reel, 900ft. 11/6	7in. 2/6

"EASISPEL" Tape Splicer 5/-
Leader tape 4/6; Splicing tape 3/-

CRYSTAL DIODE G.E.C. 2/-, 6EX34 3/-, OA81 3/-, HIGH RES. PHONES, 3,000 ohms, 15/-, 2,000 ohms, 12/6. MOVING COIL PHONES, 100 ohms, 10/-, SWITCH CLEANER. Fluid squirt about, 4/6 tin.

"6+1" TRANSISTOR RADIO
First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, with car aerial coil, printed circuit, 8 1/2 in. x 2 1/2 in., but EXCLUDING Speaker and cabinet. **£4.5.0**
Speakers, 35 ohms, 6 x 4 in., 21/-, 15 in., 17/6; 3 1/2 in., 15/6.

BULGIN PLUGS AND SOCKETS. Non-reversible P74, 2-pin, 4/3; P73, 3-pin, 4/6; P194, 6-pin, 8/6; JACKS. English open circuits, 2/6. closed circuit, 4/3. Grounding type, 3-pin, 1/2. Grounding lead jack, 3/6. JACK PLUGS. English, 3/-; Screwed, 4/-; Grounding 3-pin, 3/6. Plug Plugs, 1/-; Sockets, 6d. ALADDIN FORMERS and cores, 1/2 in., 8d.; 3/4 in., 10d. 6-pin, 5097 or 8 pins TV1 or 2, 2 in. sq. x 2 1/2 in., or 3 in., 2/- with cores. SLOW MOTION DRIVERS, 6-1, 4/3, 36/-, 10/6. ANTEX SUB-MIN IRON, 15w, 200 or 250v., 32/6. BENCH STAND for above, 12/6. Spares in stock. PAXIPHON Panels, 10 x 8 x 1 1/2 in., 2/-; Miniature Contact Coiled Rectifiers, 250V, 60mA, 7/6; 250V, 85mA, 9/6. Selenium Rect., 300V, 85mA, 5/-, K3/25, 600V, 5mA, 5/-, RM4, RM5, 14A100, 14A116, 10/- each. FC31, 20/-, TV etc. Silicon Sub-Min. Rectifiers, 250V 450mA, 10/- 250V 150mA, 5/6.

465 kc/s. SIGNAL GENERATORS. Price 10/6, ready made with valve IS5. POCKET SIZE: 2 1/2 x 4 1/2 in. One resistor to change, full instructions supplied. Battery 8/6 extra. Details Free.

Coils Wearite "P" Type, 4/- each. Osamor Midget "Q" type, ad. dust core, from 4/- each. All ranges. List S.A.E. Repairo DRR-2 L and Med. T.R.F. with reaction, 4/6. Med. wave D.R.-3/6. Ferrite Aerials, M, 8/9; M and L, 12/6. Osamor Ferrite Rod Aerials, L and M, for transistor circuits, 10/- each. Ferrite Rods, 3 x 1/2 in., 6 x 1/2 in., 3 x 1 1/2 in., 3/-; I.F. Cores, 2/6. Osamor QCT, 6/9. T.R.F. Coils, A/HF, 7/- pair; HAX 3/6. Screwdriver, 5in., 6d. Test Prods, 2/9 ea. Neoside Trimming Tool, 1/8. Union Mains Tester Screwdriver, 5/-. Multicore Solder, 4d. yd. Dispenser, 2/6.

Blank Aluminium Chassis, 18 s.w.g. 4 sides, riveted corners, lattice fixing holes, 2 1/2 in. sides, 7 x 4 in., 4/9; 9 x 7 in., 5/9; 11 x 7 in., 6/9; 13 x 9 in., 8/6; 14 x 11 in., 10/6; 15 x 14 in., 12/6. Aluminium Panels, 18 s.w.g., 12 x 12 in., 4/6; 14 x 9 in., 4/-; 12 x 6 in., 3/-; 10 x 7 in., 2/3; 8 x 6 in., 2/-; 6 x 4 in., 1/6.

MARTIN TAPE PRE-AMPLIFIERS (PLAY-BACK THROUGH YOUR OWN AMPLIFIER)

For Collaro 2 Track Decks 8 gns.

COMPLETE RECORDING & PLAY-BACK AMPLIFIERS

For 2 Track Collaro £11.10

Tape Decks

Collaro Studio 2 Track £10.15.0

BSR TD2 2 Track Tape Deck £7.5.0

Collaro Record/Erase Heads, 1 track

35/- pair

MAINS DROPPERS. Midget adjustable sliders 0.2A, 1,000 ohms, 6/-, 0.2A, 1,200 ohms, 6/-, 0.15A, 1,500 ohms, 6/-; 0.1A, 2,000 ohms, 6/-.

LINE CORD. 3-way 100 ohm (t.), 1/- ft.

MIKE TRANSFORMERS. 50-1, 3/9.

P.V.C. Covered Wire, single or stranded, 2d. yd. Sizing, 1 or 2 mm., 2d.; 4 mm., 3d.; 6 mm., 5d. yd.

B.T.H. Tape Motors, 115 v. A.C., 12/6 ea. or pair for £30 v. (in series) 12/6.

SPEAKER-FRET. Gold Maroon or Green Cloth 17 x 25in., 5/-; 25 x 35in., 10/-. Tytan, various colours 12 in., wide from 10/-; 26in., wide from 5/- ft. Samples 1/-. Expanded Metal, Gold, 12 x 12in., 6/-.

Panel mounting fuse holder, 2/-. Fuses 1 1/2 in., 60mA, 5A, 8d. Insulated side cutters, 3/6. B.B. Strippers, 3/6.

RADIO AND TELEVISION SPARES

All leading makes, volume controls, etc., line output transformers, etc., B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

WEYRAD P50

COILS AND TRANSFORMERS FOR

3-WAVE TRANSISTOR SUPERHET

Long and Medium aerial—RA2W 6in. rod

208 pF tuning, with car aerial coil 12/6

Osc. Coil P50/LA4 175 pF tuning 5/4

1st and 2nd I.F. P50/2CC 470 k/c/s 5/2 each

3rd I.F. P50/3CC 6/-, Spare Cores 6d.

Driver Transformer—LFD4 7/6

Wavechange Slide Switch d.p.d.t. 3/6

Printed Circuit—PCAL, Size 21 x 8 1/2 in.

Ready drilled and printed 4/6

Volume Control, 5K-D1 9/6

35 ohm Speakers, 3 1/2 in., 15/6; 5 in., 17/6;

6 x 4 in., 21/-.

J.B. Tuning Gang with trimmers 10/6

Constructor's Booklet 2/-

3 ohm O.P. Trans. O.P.T.1 10/6

NEW MULLARD TRANSISTORS

OC71 6/-, OC72 7/6, OC8D 7/6, OC81 7/6,

OC44 8/-, OC45 8/-, OC171 10/6, AF117,

9/6.

Sub Miniature Condensers, 0.1 mFd, 50v, 1/3; 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mFd,

15 volt, 2/6 ea. Transistor Holders, 1/3-

SINGULAR "SLIMLINE" RADIO

Med. wave kit, 2 Transistors, 2 diodes,

carphone, ferrite aerial, Cabinet

3 x 1 1/2 x 1 in., 49/6. No aerial required!

Transistor 4 Channel Mixer with 4

separate input/output controls 59/6.

"THE POWER MITE" 45/-

PM9 Mains Unit 9 volt for Transistor

Radios. Same size as P.P.9 (200/250V.)

Miniature P.P.9 model 19/6

ADASTRA 3-3 AMPLIFIER 3 WATTS



A.C. 200-250V. Valves ECL86 and E280, 3 ohms output. Controls: bass, treble and volume. Separate front panel with de-luxe finish. Quality mains transformer. Enamelled chassis 6 in. x 5 in. x 3 in. Price £4.19.6. Details S.A.E.

"Performs agreeably well" (The Gramophone)

BUILD YOUR OWN RECORD PLAYER

FROM £9.19.6

AND SAVE POUNDS!!



4 Speed Autochanger or Single Player units with Brand New 3-tone de-luxe Cabinets 17 x 15 x 8 1/2 in. Strong, durable, gilt finish clips and hinges. Used by Famous Make for 20gns. models. Ready cutout motor board 14 x 13 in. Front baffle with 7 x 4 in. high flux loud-speaker and 3 watt 2 valve UY85, UCL82 amplifier built on metal chassis 12 x 3 x 2 1/2 in. Quality 3 ohm output transformer, low hum level circuit. Volume and Tone controls, 3-core safety mains lead. All items fit together perfectly. Special instruction, enable assembly in 30 minutes, only 5 wires to joint! 12-month written guarantee. Available separately or package deals as below.

AUTOCHANGE KITS COMPLETE (as above)

B.S.R. Monarch .. £11.10.0 P.P. 5/6

Garrard Autolism .. £12.18.0 P.P. 4/6

SINGLE PLAYER KITS. Complete (as above)

E.M.I. Junior .. £9.19.6 P.P. 5/6

Garrard SRP10 .. £11.15.0 P.P. 5/6

OR SEPARATELY

Cabinet with board 14 x 13 in.

cut out to your choice £3.9.6 P.P. 3/6

Amplifier with 7 x 4 in. speaker £3.17.8 P.P. 2/6

AUTOCHANGERS

B.S.R. UA14 .. £5.19.6 P.P. 4/6

B.S.R. UA15 Slimline .. £6.17.8 P.P. 4/6

Garrard Autolism .. £6.17.8 P.P. 4/6

SINGLE PLAYERS

Garrard SRP10 .. £5.5.0 P.P. 4/6

E.M.I. auto stop/start .. £5.5.0 P.P. 4/6

E.M.I. Junior .. £3.7.8 P.P. 3/6

TRANSCRIPTION UNITS

Garrard 4HF .. £15.15.0 P.P. 5/-

Phillips AG1016 .. £12.5.0 P.P. 5/-

Garrard AT6 .. £10.10.0 P.P. 5/-

BARGAIN XTAL PICK-UP ARM

Complete with ACOS LP-78 Turnover Head, 20/-

Replacement supple style 5/-, diamond 15/-

Mono GP59 Xials 15/-; Stereo Ronette 30/-

BARGAIN SINGLE PLAYER KIT 200/250 v. A.C.

£5.15.0 (less cabinet)

With 2-state Amplifier; 3 watt; 2 valves. UCL82,

UY85, High-flux 5in speaker; 4-speed E.M.I.

Turntable, 16, 33, 45, 78 r.p.m.; Crystal Pick-up

for LP/STD. Records, 7in., 10in., 12in.; Cut out

Mounting Boards 12 x 9 in.

ARDENTE TRANSISTOR TRANSFORMERS

D3035, 7.3 CT; 1 Push-pull to 3 ohms output 11/-

D3034, 1.7A; 1, C.T. Push-pull Driver 11/-

D3058, 11.5:1 Output to 3 ohms, etc. 11/-

D239, 4.5:1 Driver, 1in. x 1in. x 1in. 11/6

D240, 3.5:1 Driver, 1in. x 1in. x 1in. 11/6

ARDENTE TRANSISTOR VOLUME CONTROLS

VC1545, 5K with switch dia. .9in. 5/3

SUB-MIN. EARPIECE Xial or magnet 7/6

SUB-MIN. JACK AND PLUG 2.5 or 3.5 mm. 3/6 ea

MINIATURE PANEL METERS

Size 1 1/2 in. sq. Precision jewelled bearings,

2% accuracy, silvered dials, black

numerals and fine pointers, zero

adjustment screw on front of meter.

1 mA .. 27/6 50µA .. 39/6

5 mA .. 27/6 500µA .. 32/6

300V .. 27/6 "S" Meter 35/-

MOVING COIL MULTIMETER TK 20a

0-1000 v. A.C./D.C. ohms 0-100k, etc., 49/6.

0-150 ma. pocket size with 2 in. scale.

CRYSTAL MIKE INSERTS, 6/6

High output Size 1 1/2 in. dia. x 1 in.

ACOS MIC. insert 1 1/2 in. dia. x 1 in., 8/6

ACOS 39-1 DELUXE STICK MIKE 35/-

TEL. QUALITY STICK MIKE .. 25/-

TELEPHONE TAPE MIKE .. 10/6

GUITAR CONTACT MIKE .. 15/6

MOVING COIL MIKE, high or low

impedance, with ELDOX STAMP 147/-

TANNAY Carbon Hand Mike .. 7/6

COMPONENT SHOP 337 WHITEHORSE ROAD
SPECIALISTS WEST CROYDON

Telephone: THO 1665
Export welcome. Send remittance,
and extra postage, no C.O.D.

Buses 133 or 68 pass door, S.R. Station, Selhurst

**RADIO-AMATEUR GEAR
EDUCATIONAL KITS**

**TEST INSTRUMENTS
HI-FI EQUIPMENT**

World-famous kit-sets anyone can build

The clearly written instruction manuals, issued with each kit, show you how
A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, LABORATORIES

HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. output (£215.0 inc. P.T.) I.F. Amp. (FMA-4U) complete with cabinet and valves. (£133.0). Total kit £1518.0. Assembly can be arranged.



AMATEUR BANDS RECEIVER. Model RA-1. Covers all Amateur Bands from 160 to 10m. Special features incl. half lattice crystal filter, 8 valves, signal strength "S" tuning meter, tuned R.F. amplifier stage. Kit £39.6.6. Assembled £52.10.0

5W HI-FI MONO AMPLIFIER. Model MA-5. A low-priced well designed amplifier. Printed circuit construction makes it easy to build. Kit £10.19.6. Assembled £15.10.0

"COTSWOLD" HI-FI SPEAKER SYSTEMS. MFS or Standard. Range 30-20,000 c/s. Kit £23.4.0. Assembled £30.15.0

MONO CONTROL UNIT. Model UMC-1. Ideal for use with MA-12 or similar amplifier. Kit £8.12.6. Assembled £13.12.6

HI-FI EQUIPMENT CABINETS. Large range, in kit form or assembled and finished, incl. record housing range, available to meet various needs. Details on request. from £7.7.0 to £37.16.0



5in. OSCILLOSCOPE. Model 10-12U. Wide band amplifiers essential for T.V. servicing, F.M. alignment etc. T/B covers 10 c/s-500 kc/s in 5 ranges. Kit £32.12.6. Assembled £41.10.0. The ideal low-priced 'scope.

6W DE LUXE AMPLIFIER. Model S-33H. An inexpensive Stereo-Mono amplifier, with high sensitivity. Suitable for Decca Derram Cartridge. Kit £15.17.6. Assembled £21.7.6

6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7 x 4in. high flux speaker. Real high case. Very easy to build. Kit £12.11.0

SHORTWAVE TRANSISTOR PORTABLE. Model RS-W-1. Two short bands, trawler and medium wave. Kit £19.17.6

HI-FI A.M./F.M. TUNER. Covers F.M. 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000m. Tuning heart (£413.6 inc. P.T.) and I.F. Amp. £21.16.6. Printed circuit board. Total ... Kit £26.10.0

"OXFORD" DE-LUXE TWO WAVEBAND TRANSISTOR PORTABLE. Model UXR-2. The ideal domestic, car, or personal portable receiver. 10 Semi-conductors. Send for full details. £14.18.0 Kit (inc. P.T.). Assembly can be arranged.



Assembled models also available: prices on request—Deferred terms available over £10. Free delivery U.K.

SEND FOR FREE BRITISH HEATHKIT CATALOGUE—MANY MODELS TO CHOOSE FROM

PA AMPLIFIER. Model PA-1. 50W output. For vocal and instrumental groups, guitars, etc. 4 inputs, 2 speakers, Tremolo. Send for full details. Kit £54.15.0. Legs optional extra 17/6 set. Assembled £74.0.0.

50W POWER AMPLIFIER. Model MA-50. Ideal for PA work etc. Kit £19.18.0. Assembled £27.18.0.



RG-1

2 1/2in. PORTABLE SERVICE OSCILLOSCOPE. Model OS-1. An ideal light, compact 'scope for servicing and general work. Printed circuit construction. Kit £21.18.0. Assembled £29.8.0

"MOHICAN" TRANSISTOR GEN-COVERAGE RECEIVER. Model GC-1U. An excellent portable for the short wave listener. Kit £37.17.6. Assembled £45.17.6

VALVE VOLTMETER. Model V-7A. Measures up to 1,500 v. (D.C. and r.m.s.) and 4,000 pk-to-pk. Res. 0.1Ω to 1,000 MΩ. Kit £13.18.6. Assembled £19.18.6

COMMUNICATIONS TYPE RECEIVER

Model RG-1. An excellent low cost receiver. Freq cov.: 600 kc/s-1.5 Mc/s. 1.7 Mc/s-32 Mc/s.

A two speed tuning drive. R.F. "front end" supplied assembled, aligned and tested. Send for details. Kit £39.16.0. Assembled £53.0.0.

6W STEREO AMPLIFIER. Model S-33 3 w/chl. Inputs for radio-tape-gram. Stereo/Mono, ganged controls. Sensitivity 200 mV. Kit £13.7.6. Assembled £18.18.0

MULTIMETER. Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C. 0-150μA—15A D.C. 0.2Ω to 20MΩ 4 1/2 in. 50μA meter. Kit £12.18.0. Assembled £18.11.6

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s on harmonics. Up to 100 mV output all bands. Kit £13.8.0. Assembled £19.18.0



NEW MODEL! TELEVISION ALIGNMENT GENERATOR. Model HFW-1. Accurate alignment of TV receivers achieved in minimum time at low cost. Covers 3.5 to 220 Mc/s fundamentals. ONLY £30.15.0. Kit. £44.10.0 Assembled

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. CW. 60 w. peak C.C. phone. Output. Kit £33.19.0. Assembled £45.8.0.

40 w. to aerial. Prov. for VFO

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands, 160-10 m. 150 w. D.C. input, self contained with power supply. Modulator, VFO Kit £79.10.0. Assembled £104.15.0



DX-100U

DAYSTROM LTD.

Dept. P.W.10, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s) _____

NAME _____

ADDRESS _____

PW10

Practical Wireless

Vol. XL No. 692 OCTOBER, 1964

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House
Southampton Street, W.C.2.

© George Newnes Ltd., 1964

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

To any part of the world £1.9.0

Contents

Editorial	513
Round the World of Wireless ...	514
The "Ten-Five"	516
Inexpensive Intercom System ...	522
Trimmer and Alignment Set ...	524
Understanding Semi conduc- tors	527
Books Reviewed	530
On the Short Waves	531
Utility Power Pack	532
The "Spectreuphon"	536
A Simple Transistor Tester... ..	540
Miniature Power Amplifier	543
Practically Wireless	545
An Inductance/Capacitance Tester	546
Trade News	558
The "Multiphonic"	562
The Buccaneer	569
Club News	574
Letters to the Editor	577

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed; The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Good Response

TO trim, or not to trim? That is the question that must have been asked a million times in radio shack or workshop, or the corner of the kitchen table.

A lot of nonsense has been talked about the unforgivable sin of "tiddling the trimmers". The imputation is that the average radio enthusiast is quite incapable of making tuning adjustments. Such critics need an answer.

It would be foolish to ignore the fact that in the course of every year, many receivers find their way to the professional's service bench, hopelessly out of alignment due to inexpert and haphazard trimmer and core twiddling. Or that many gloomy hours are spent annually by home constructors in futile attempts to peak and calibrate newly constructed sets.

However, those that suffer in this way are usually raw novices, those with no contact with other amateurs, or those who with iron resolve refuse to put themselves out to learn a few elementary facts.

The majority of amateurs are unquestionably more competent and intelligent, and even if they do not have access to the proper test instruments they are able, under certain circumstances, to make adjustments to tune circuits without dire consequences.

When a receiver is known to be aligned—when it has been working, but a fault has developed—there is no objection to an exploratory movement of iron-dust cores and trimmers, provided a few obvious basic rules are observed.

First, cores or trimmers should be moved *one at a time*. If no improvement is noted, they should be returned to the original position before proceeding to the next. Second, a visual indication of output is very much better than trusting to the ear; more delicate adjustment is possible.

Third, where a set is completely out of alignment, the correct sequence of adjustments should be followed—and the possibility of an alternative fault should be investigated before re-tuning. A receiver that is known to be out of alignment, such as a newly-built model, should be aligned "according to the book".


Now the critics must be well aware that most readers of magazines such as PRACTICAL WIRELESS are quite conversant with the above homespun rules. Why, then, their spleen?

It seems to be based on one main bad fault—the chewed-up slug or the trimmer with the cracked insulating washer. This is generally the result of using makeshift tools. Very seldom is it caused by the true enthusiast.

The only real restriction on trimming should be the necessity for test equipment when aligning those circuits that *must* be tuned to an exact response curve. A small movement of any one core of a TV or an f.m. receiver i.f. strip may seem to make little difference, but its effect on the overall response could be deceptively damaging.

We are sure that regular readers will know not only how but *when* to adjust a tuned circuit. And we hope that the trimming tools presented with this issue may prevent a few more slugs becoming chewed up or cracked!

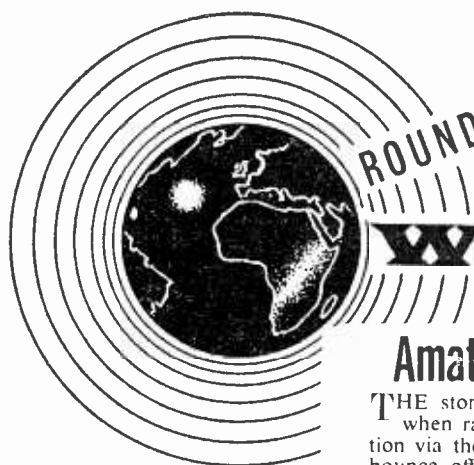Our next issue dated November will be published on October 7th



**NEWS AT HOME
AND ABROAD**

ROUND THE WORLD of WIRELESS

Amateur Radio Contacts via the Moon

THE story of amateur radio reached another milestone recently, when radio amateurs in different countries achieved communication via the moon. Pairs of amateur stations have been using signal bounce off the moon to relay radio transmissions in the 2m and 70cm ham bands.

These experiments were undertaken with the new giant 300m radio telescope in Puerto Rico, soon after its completion. (This installation is from time to time being made available for such amateur experiments.) Several contacts have already been logged using this somewhat spectacular amateur set-up, the first being on 13th June, 1964, when KP4BPZ (Puerto Rico), using the giant telescope aimed at the moon as receiver antenna, received signals from a group of Swiss and German amateurs in Hedingen, near Zurich, and, some time later, signals beamed at the moon by the British station G3LTF (Peter Blair) running 80W into a parabolic aerial.

A further successful contact with Puerto Rico via the moon was established by the German station DJ3EN (Hintergarten/Black Forest) on June 14th. On this occasion, DJ3EN ran 500W on the 2m band into a conventional ten-element Yagi aimed directly at the moon. By the time his signals had been received in Puerto Rico, they had travelled a distance of roughly half a million miles.

ELECTRONIC COMPONENTS CONFERENCE

A ONE-WEEK conference on components and materials used in electronic engineering will be held at the Institution of Electrical Engineers in London from 17th to 21st May next year, concurrent with the 1965 Radio and Electronic Component Show at Olympia.

Subjects to be discussed are recent developments in active and passive components, including integrated circuits, and in the materials of which they are made.

"Resistors", "dielectrics", "capacitors", "microwave ferrites", "electro-mechanical devices", "semi-conductor devices" are a few of the categories for which contributions have been invited for inclusion in the programme.

The conference is being organised jointly by the I.E.E. Electronics Division, the Institution of Electronics and Radio Engineers and the United Kingdom and Eire Section of the Institute of Electrical and Electronics Engineers.

450 Motorcycle Transceivers Ordered

FOLLOWING their successful introduction last year, an order for 450 Ultra 4A5 motorcycle transceiver sets for use by British Police Forces has been received by the Telecommunications Division of Ultra Electronics Limited from the Home Office.

The 4A5 set provides two-way communication on four channels with a standard spacing of 25kc/s. The single superhet receiver design is fully transistorised and uses a 10.7Mc/s i.f. crystal filter. The transmitter, now further transistorised, incorporates quick-heating valves to eliminate standby battery drain. It operates on 6 or 12V supplies.

Ultra have also received an initial order for 26 of their f.m. 4B6 Packsets for use by the Metropolitan Police.

Computer for Scottish University

A LARGE general purpose analogue computer, type 247, costing approximately £19,000, has been ordered by the University of Strathclyde, Glasgow, from the Solartron Electronic Group Ltd., of Farnborough, Hampshire.

This is the fourth 247 computer to be ordered this year, the others having already been installed at the University of Sheffield and two technical colleges. The Glasgow computer will be installed in the Electrical Engineering Department and will be used for the investigation of automatic control systems and general research.

A RECENT innovation from Mullard Ltd., which could have the probable effect of standardising more than ever before the design of transistor receivers, is a range of transistor circuit modules for a.m. radios being made available to manufacturers, having the obvious advantages of faster, easier production and greater freedom in cabinet styling.

With these devices a manufacturer will be able to build a receiver around two modules—one constituting the r.f./i.f. section, the other the complete audio amplifier—instead of assembling individual components.

The r.f./i.f. module, type LP1156, is a fully-screened i.f. amplifier and mixer stage (see photograph on this page) covering the short, medium and long wavebands using external oscillator coils. (Other versions are available for medium and long wavebands only, using internal oscillator coils, but all versions measure the same: 2.44in. x 1.19in. x 0.64in.) The mixer stage uses an AF115 transistor and the two stages of i.f. amplification use AF117's, followed by a diode detector (OA90).

The whole module is designed to operate from a 7.6V supply line derived from the audio module.


MULLARD INTRODUCE CIRCUIT MODULES FOR TRANSISTOR SETS

This latter, type LP1153, is an a.f. amplifier giving an output of 500mW into a 10 Ω loudspeaker. It is designed to operate from a 9V supply and it measures 2.01in. x 1.27in. x 1.08in.

The circuit uses an LFK4 transistor package and comprises a d.c.-coupled preamplifier stage and a complementary output stage. Overall d.c. feedback of 10dB is applied to stabilize the working condition and approximately 10dB of a.c. feedback

reduces distortion and gain spreads.

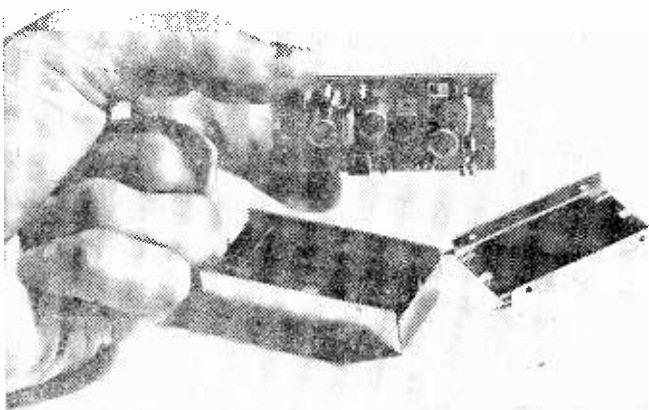To simplify manufacture further, the r.f./i.f. module comes pre-aligned, so reducing the alignment procedure of the complete receiver. In addition fault-finding by the set maker is virtually eliminated since both types of module are given stringent quality control tests during manufacture. Servicing is also simplified, the replacement of a module taking a few minutes only.



Mullard's new r.f./i.f. circuit module.

V.H.F. RELAY STATION IN FORFAR

THE BBC's new television and v.h.f. sound relay station for Forfar, which was brought into service earlier this year, is situated at Harecairn, near Monikie, Dundee. From here it serves an area including southern Angus, northern Fifeshire and small areas of eastern Perthshire and southern Kincardineshire, with transmissions of BBC-1 television and the three v.h.f. sound programmes.

The television transmissions are on channel 5 (vision 66.75Mc/s, sound 63.25Mc/s with vertical polarisation, with the Scottish Home Service on 92.7Mc/s, the Light Programme on 88.3Mc/s and the Third Programme/Network Three on 90.5Mc/s, all with horizontal polarisation).

New Radio Station in British Honduras

A NEW h.f. radio station is to be built in British Honduras for Cable and Wireless Ltd., near the city of Belize. It will cost in the region of £100,000 to build and take about 18 months to complete.

The station will be built on a site at Pine Ridge and when finished will comprise two separate buildings, about 800 yards apart, for housing transmitters and receivers, the transmitters being remotely controlled from the receiver building.


Belize is one of the youngest branches in the world-wide telecommunications network of Cable and Wireless Ltd., and its associated companies. Opened in April, 1962, it faced many difficulties as a result of the devastation caused by hurricane "Hattie", which struck Belize on October 31st, 1961.

A temporary wireless station set up in 1958 was destroyed and much of the equipment lost. An emergency station was set up while negotiations for the company to take over the external telecommunications of British Honduras continued with the Government.

The damage caused by flooding during hurricane "Hattie" emphasised the vulnerability of sites in the city of Belize and it was decided that the new station would be erected further inland on higher ground.

Four transmitters of 1kW each, and five receivers will be installed in the station. A link between the new station and the Central Telegraph Office in Cattouse Building, Belize, will be established by a multi-channel v.h.f. link.

THE "TEN-FIVE"

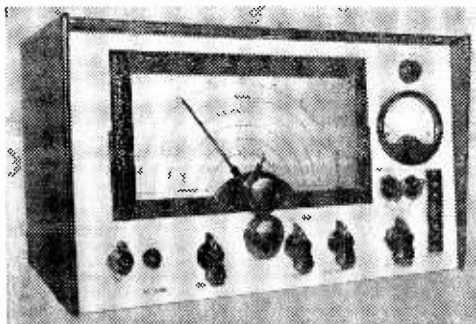

**A 10-transistor
double-conversion
communications receiver**

- s-meter •
- b.f.o. •
- mains powered •

BY A. S. CARPENTER G8ABG

NOW that suitable ready-made coils are available it is possible to construct an excellent Short Wave transistorised receiver possessing a high degree of sensitivity.

The receiver to be described was built primarily to provide signals in the various Amateur bands; it requires no valves and may be run either from a standard 9V dry battery or from the domestic mains supply at 220-240V a.c.. The semi-conductor complement comprises ten transistors and five diodes, two of which are used for a.c. rectification purposes in the mains power supply section.

The receiver is not inexpensive to construct and a fair amount of work is also involved since the design is moderately complicated. Other requirements in the workshop are: A suitable signal generator, a soldering iron fitted with a pencil bit, time, patience—and a pair of strong tweezers!

Sections of the Receiver

The block diagram of Fig. 1 shows the various sections and it will be observed that the "double

conversion" principle is employed, for as is well known this technique proves most beneficial on the higher frequency bands. A tuned r.f. stage is also included and this ensures high gain whilst also acting as a buffer stage against oscillator radiation, via the aerial system.

The primary coverage afforded by the tuned section is 1.67—31.5Mc/s (9.5—180 metres) with additional optional coverage of 0.175—1.545Mc/s (194—1700 metres.) These additional ranges are rarely likely to be needed here, however, since they are more easily and conveniently covered using a conventional portable domestic medium/long waveband transistor receiver.

Mechanical bandspreading is provided for the tuned sections via the familiar Jackson "Caliband" drive, this providing by means of its two pointers reduction ratios of 6 and 48:1. Although adequate bandspreading is achieved even on the highest frequency ranges a small panel fitted device—to be described later—is also included, this being most useful for minimising interference caused by an adjacent station.

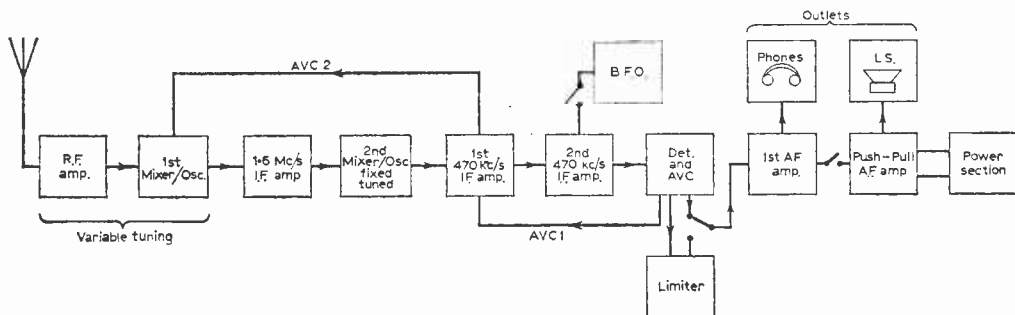


Fig. 1: Block diagram representation of the "Ten-Five" circuit.

It may be noted too that a beat frequency oscillator (b.f.o.) is also fitted together with a "pitch" control to vary the beat note. In addition, the b.f.o. may also usefully be employed in conjunction with the "Pitch" control to make single sideband (s.s.b.) transmissions intelligible.

A signal/tuning meter is fitted and operated by the receiver a.v.c system and because the a.v.c is made inoperative when the b.f.o. is in use the meter pointer reads full scale. In a permanent battery-powered construction it might then be beneficial to arrange for the meter to monitor the applied battery potential but this service was not needed in the prototype due to use of an a.c. mains power unit.

Outlets

Both phone and speaker outlets are provided on the front panel and may be selected as required by means of a switch. The phone outlet is high impedance whilst the "LS" outlet is low impedance and assumes use of an externally connected 32 unit. Some 500mW of audio is available under normal circumstances via the loudspeaker. The

as is usual in push/pull systems of the type employed. The consumption can easily rise to 45mA or more on peaks so the mains transformer supply is obviously preferable on both regulation and replacement counts. The output stage could then be advantageously allowed a larger quiescent current drain. For general phone use, however, a battery is quite satisfactory and a reasonable life can be expected.

Bandchanging

The simple "plug-in" method is employed and because the converter section is fitted with an r.f. stage three coils have to be changed for each band. A total of three sets (nine coils) covers the ranges envisaged so the problem is not very serious.

Each coil is clearly colour coded and fits a standard noval 9-pin valve holder. "Padder" connections present no problem either, for on each coil this connection is brought out to a different pin so that if the holder is appropriately wired the correct padding capacitance is automatically connected for each oscillator coil. Details relating to this and to ranges covered, etc., are given below.

TABLE I

Blue and Yellow Coils		T1—T2		White coils T3					
Maker's range No.	Ls μ H	Coverage		"Q"	Lo	C9	pin	Cto	Copi
		Mc/s	Metres						
1	2350	0.175-0.525	570-1700	60	156	50	6	35	20
2	271	0.515-1.545	194-580	100	66	110	2	20	10
3	27.2	1.67-5.30	57-180	60	13.6	340	3	11	10
4	2.9	5-15.0	20-60	90	2.22	960	4	4.5	—
5	0.65	10.5-31.5	9.5-28	110	2.35	2000	6	1.5	—*

Aerial Coils—Blue, T1. Interstage Coils—Yellow, T2. Oscillator Coils—White, T3.

Ls —Nominal inductive value of tuned winding. (Approximately 15% variation obtainable via dust core).

'Q' —Approximate 'Q' value of tuned winding—mid scale tuning point.

Lo —Nominal inductive value of oscillator tuned winding.

Cq —Padder capacitance value required.

Cto —Oscillator pF trimmer capacitance extra to 39pF assumed circuit capacitance.

Copi —Additional fixed capacitance recommended across tuned winding as appropriate using plug-in band changing method. Note: panel fitted TC4 accomplishes this.

*Harmonic mixing used on this range, the second harmonic being automatically present at alignment.

Note that Table I shows all coils available although only ranges 3-5 are likely to be required here.

phones may be left connected or may be removed as required without in any way affecting the receiver.

Consumption

The total quiescent current drain from a 9V supply is 12mA when the speaker outlet is in use but falls to 5mA on phone because the output stages are switched out. Bringing in the b.f.o. adds 0.6mA (600 μ A) and may be considered negligible. Current consumption changes very little at any time when on phone but if the speaker is in use the demand varies with the signal strength and volume

CIRCUIT DESCRIPTION

Converter and 1st 1.6 Mc/s I.F. Amplifier

The converter, intermediate frequency stages, a.v.c., demodulating and limiting sections are shown in Fig. 2. (a) and (b).

The first two transistors, Tr1, Tr2 (AF115) are the active elements of the converter. Tr1 being the r.f. amplifier feeding Tr2 as mixer oscillator. Signals from the aerial are here converted to the 1st intermediate frequency, viz., 1.6Mc/s and since no direct pick-up at this frequency is required a simple wavetrap is inserted in series with the aerial.

already referred to, each being tuned by a section of the 3-gang capacitor VC1/2/3 fitted with trimmers. The tuned sections of each transformer are coupled to the appropriate circuit by mutual inductance.

Signals at 1.6Mc/s appearing at Tr2 collector are next applied via a transformer to the base of Tr3 (OC171) for further amplification at this frequency, so increasing the need for the aerial trap.

Converter Trimming

Although variable r.f. trimmers, panel mounted, are feasible to compensate for errors due to band-changing, the first oscillator is controlled by means of TC4, labelled (Osc. Trim). In use it is assumed that the first stage is damped by the aerial so that it remains either to trim the interstage circuit to fit the oscillator or vice versa, the oscillator adjustment being preferred here since it helps compensate for C₀ and C_{opt}, Table I.

In practice TC4 is initially set to about half capacity and the tuning mechanism operated in the usual way to resolve a signal. Should this seem

"pruned" away, C10 may also be made to limit maximum circuit capacitance as required.

Second Converter and 470kc/s I.F. Amplifier

When the 1.6Mc/s signals from Tr3 are applied to Tr4 a second frequency conversion takes place. The second i.f. amplifier operates at 470kc/s and because T4 can be fixed tuned the oscillator may operate at a frequency lower than that of the signal, i.e., at 1.13kc/s. The coil (code red—range 2) must be screened, using the can provided; it has a tuned winding, quoted inductance value of 129μH and so requires a capacitor of approximately 170pF across it, although in practice accurate setting is accomplished with its core. This second converter could be operated at 2.07Mc/s if preferred, but use of a different coil would be advisable to allow adequate shunt capacitance to be added whilst Tr4 would need to be an OC44.

The 470kc/s i.f. amplifier is conventional except that transistors from the Mullard "AF" range are used instead of the more usual OC45 types which would necessitate additional items in the form of neutralising components. All the i.f. transformers

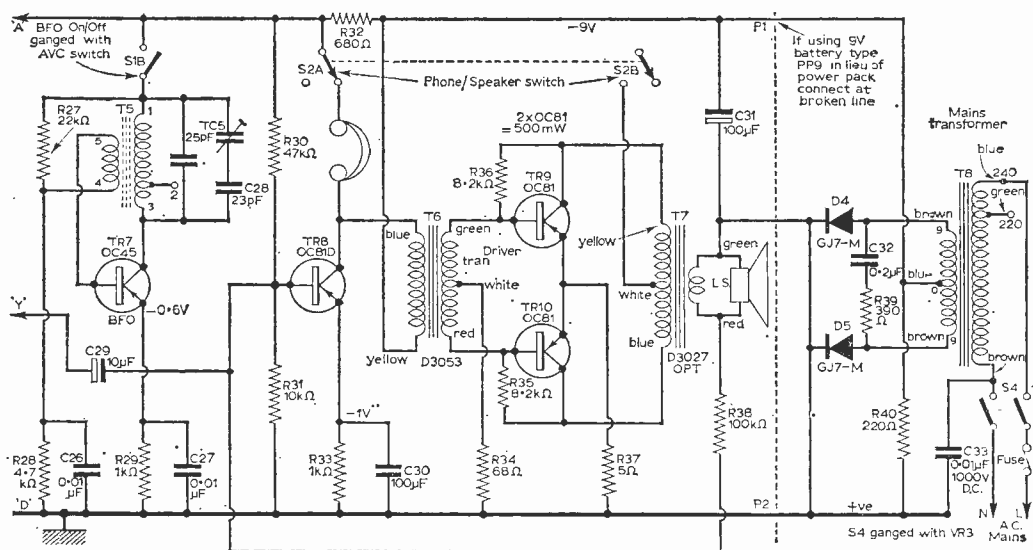


Fig. 2 (c): The b.f.o. and audio sections, plus the power supplies.

weak, the pointer mechanism is moved a fraction to one side of the transmission and TC4 experimentally adjusted. It is quickly evident which way the main pointer must go by watching the signal meter. TC4 is also useful for picking out a single transmission from a clutter, for losing adjacent c.w., etc., quality being unimportant. Sometimes a "returning" station is very slightly off frequency and TC4 is then particularly useful, for the main dial needs no alteration, both stations being heard in turn merely by moving TC4 to and fro. A large value capacitor must not be used for TC4 and the total number of vanes should be four, others being

are single tuned and selectivity is quite good. The circled figures associated with all coils and i.f. transformers refer to their basing connections for which a key is provided (Fig. 2).

The signal meter in the collector circuit of Tr5 reads in reverse but this is not important. (It could, however, be mounted upside down to give a left to right needle movement but would require a new scale.)

As the bias varies at the base of Tr5 due to demodulator action, a large rectified signal tends to cut off the collector current thereby causing the meter pointer to full back. The meter records

COMPONENTS LIST

Resistors:

R1	15k Ω	R21	680 Ω
R2	1k Ω	R22	4.7k Ω
R3	1k Ω	R23	1.2k Ω
R4	3.9k Ω	R24	22k Ω
R5	15k Ω	R25	47k Ω
R6	1.2k Ω	R26	100k Ω
R7	56k Ω	R27	22k Ω
R8	10k Ω	R28	4.7k Ω
R9	1k Ω	R29	1k Ω
R10	3.9k Ω	R30	47k Ω
R11	15k Ω	R31	10k Ω
R12	100 Ω	R32	680 Ω
R13	2.2k Ω	R33	1k Ω
R14	1k Ω	R34	68 Ω
R15	33k Ω	R35	8.2k Ω 5%
R16	6.8k Ω	R36	8.2k Ω 5%
R17	1k Ω	R37	5 Ω
R18	720 Ω	R38	100k Ω
R19	4.7k Ω	R39	390 Ω
R20	22k Ω	R40	220 Ω

All $\pm 10\%$ $\frac{1}{2}W$ miniature carbon, unless otherwise stated.

Potentiometers:

VR1	5k Ω
VR2	150 Ω
VR3	5k Ω with double-pole on/off switch (S4).

Coils and Transformers:

IFT1	I.F. transformer. Denco IFT16
IFT2	I.F. transformer. Denco IFT16
IFT3	I.F. transformer. Denco IFT13
IFT4	I.F. transformer. Denco IFT13
IFT5	I.F. transformer. Denco IFT14
T1	See Table I; plug-in transistor coil. Denco (blue)
T2	See Table I; plug-in transistor coil. Denco (yellow)
T3	See Table I; plug-in transistor coil. Denco (white)
T4	Miniature valve-type coil. Denco range 2 (red)
T5	B.F.O. transformer. Denco IFT14
T6	Driver transformer. Ardente D3053 (with clamps)
T7	Output transformer. Ardente D3027 (with clamps)
T8	Mains isolating transformer. Norcol or Osmor MT9
L1	Miniature valve-type coil. Denco range 2 (red)

Variable Capacitors:

VCI, 2, 3	310pF (nominal) 3-gang tuning capacitor with feet and trimmers (TC1, 2, 3). Jackson "F".
TC1, 2, 3	Trimmers on VCI, 2 and 3.
TC4	See text. Jackson "Air Tune".
TC5	25pF. Jackson "Air Tune".

Capacitors:

C1	75pF mica
C2	100 μ F electrolytic 12V
C3	0.01 μ F ceramic or paper
C4	0.01 μ F ceramic or paper
C5	0.05 μ F paper
C6	0.01 μ F ceramic or paper
C7	2,000pF mica
C8	0.01 μ F ceramic or paper
C9	see Table I
C10	6pF see text
C11	0.01 μ F ceramic or paper
C12	0.01 μ F ceramic or paper
C13	0.01 μ F ceramic or paper
C14	2,000 pF mica
C15	0.01 μ F ceramic or paper
C16	175pF mica
C17	10 μ F electrolytic 6V
C18	5 μ F electrolytic 12V
C19	0.01 μ F ceramic or paper
C20	0.01 μ F ceramic or paper
C21	0.01 μ F ceramic or paper
C22	100 μ F electrolytic 12V
C23	0.01 μ F ceramic or paper
C24	0.1 μ F paper
C25	0.01 μ F ceramic or paper
C26	0.01 μ F ceramic or paper
C27	0.01 μ F ceramic or paper
C28	23pF see text
C29	10 μ F electrolytic 6V
C30	100 μ F electrolytic 6V
C31	100 μ F electrolytic 12V
C32	0.2 μ F paper
C33	0.01 μ F paper 1,000V

Semiconductors:

Tr1	AF115	Tr5	AF117
Tr2	AF115	Tr6	AF117
Tr3	OC171	Tr7	OC45
Tr4	OC45	Tr8	OC81D
Tr9	OC81	Matched pair	
Tr10	OC81		
D1	OA79	D4	GJ7-M
D2	OA70	D5	GJ7-M
D3	OA70		

Switches:

S1a, b	2-pole, 2-way
S2a, b	2-pole, 2-way
S3	Single-pole change-over toggle
S4	Double-pole on/off switch on VR3

Miscellaneous:

Meter 500 μ A f.s.d. movement. $9\frac{1}{2}$ in. x 6in. x $\frac{1}{16}$ in. piece of paxolin. Nine tag strips. Lektrokit LK-2231. Aerial socket. 16 s.w.g. aluminium for flanges and screen. Two transistor mounting clips. Battery connectors. Phones/speaker outlet sockets. Jackson "Caliband" dial and drive assembly. 3 Noval low-loss valve-holders. Tags, wire, etc.

all changes of signal strength and can thus be used usefully as a tuning indicator and alignment aid. A 500 μ A meter movement shunted by a preset variable resistor enables accurate f.s.d. setting as required, at the same time temporarily removing the a.v.c. bias, i.e., by rotating S1A to "Out". Small panel type meters are easily obtainable.

The A.V.C. System

Diode D1 in connection with Tr5 collector circuit is arranged to be non-conductive on small or moderately strong signals, the reverse bias applied being in fact 0.6V. When a very strong signal is tuned in, however, a proportionately

greater bias is applied to Tr5 due to D2 which provides bias at all times, whereupon the potential at C18 changes sufficiently for D1 to conduct and thereby damp the first i.f. transformer to reduce gain still further. Simple undelayed a.v.c. thus initiates a delayed a.v.c. characteristic.

The B.F.O. and Audio Sections

The audio content of the demodulated signal appears across VR3 and is available as required via the slider, S3 determining whether the signals are extracted direct or via the simple series limiter circuit associated with D3. Carrier level maintains D3 in a conducting state but a sudden burst of noise results in cut-off so that the signal path is broken when the switch is set to "In". Distortion occurs particularly at high volume settings and there is heavy attenuation although the circuit proves useful when listening on 'phones.

The audio stages proper plus the b.f.o. are shown in Fig. 2(c). The b.f.o. calls for little comment since it is a conventional feedback-type


driver transformer secondary winding centre tap to a fixed potentiometer connected across the supply battery, etc. Here the lower member of such a potentiometer is R34 but the upper section (normally approximately 4-7k Ω) is not connected to the -9V line. Instead two resistors are used (R35/36) and connected between base and collector on each of the output pair. This arrangement not only simplifies phone/l.s. switching (Tr9/10 are completely disconnected at phone) but also introduces some degeneration due to a.c. feedback and this materially assists the overall performance in several ways, at the expense of a small amount of gain. A small portion of the output at T7 is also fed back degeneratively across the amplifier via R38 but apparent increased sensitivity results if the resistor is omitted. It may be noted that the driver and output transformers used in the prototype are Ardenite, but there is no reason why equivalent types by other manufacturers should not be used.

Powering the Receiver

Power requirements were detailed earlier and although the prototype uses an internal mains unit this is by no means essential for the construction is such that a PP9 battery will stand neatly in the area here occupied by the mains components, rectifiers, etc. Expense may be minimised initially by using the battery and adding the mains items required later. In the main, however, battery powering is uneconomical for in common with all transistor receivers batteries have to be discarded when their potential has fallen by some 30% and many volts are thrown away.

As may be seen from the illustration the mains transformer, T8, is quite small physically and is only about one quarter the size of a conventional heater transformer! The primary winding is appropriately tapped and a single secondary supplies 9.0-9V which is rectified by a pair of sub-miniature GJ7M diodes. These require no heat sinks due to low current demands. The resultant d.c. potentials are fed to the positive and negative receiver rails, R40 being included to assist in some degree, voltage stabilisation in association with C31. An automatic "earth" results from fitting C33. No heating has occurred in the prototype even after allowing the receiver to run continuously for several hours. Constructors who do not wish to include this section should omit all items to the right of the broken line in Fig. 2(c) yet retaining "On/Off" facilities via the switches integral with the volume control. Care must be taken to check that polarity is correct.

continued next month

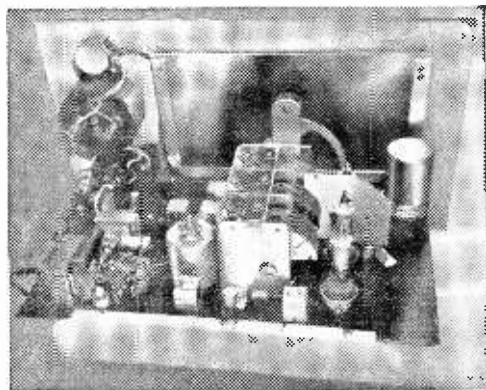

A rear view of the finished receiver.

oscillator operated close to the intermediate frequency, the precise value being controlled by panel-fitted TC5, labelled "Pitch". CW signals may then be conveniently heterodyned and in addition s.s.b. transmissions may be read. Sufficient b.f.o. injection results due to stray couplings; it may be noted that C28 is not required if a 15pF maximum capacity air-spaced variable trimmer is available for use at TC5.

The audio signal is fed via C29 to Tr8, this being a conventional audio driver transistor stage (OC81D) feeding the push/pull output pair, Tr9/10. Fitment of the phone outlet in the collector circuit of Tr8 has no adverse effect on performance for R32 is in series with the phones across the driver transformer when this function is in use. Signals of moderate phone strength are actually available at points "D" and "Y" but the amplification afforded by Tr8 is worth while using.

The output transistors bias arrangement calls for some comment. As is well known forward bias for a pair of output transistors worked in push/pull is frequently achieved by connecting the

Don't forget your

PTV

Practical Television
every month 2s.

INEXPENSIVE INTERCOM

SYSTEM by P. D. de Lacey and
A. T. Chattaway

THE intercom described here was designed to be built at low cost and to use, as far as possible, existing equipment. It provides a means of speech communication between house and workshop, and may also be used as a private telephone link between adjacent houses. It has the advantage that the sound is reproduced at sufficient volume to be heard throughout an average-sized room, leaving the user at the "slave station" free to continue his work while holding a conversation with his counterpart at the "master station".

Construction of the Master Station

The use of a loudspeaker as the microphone,

"gram-input" sockets. The switch should then look like Fig. 2.

Construction of the Slave Station

The slave station consists of a loudspeaker, as nearly as possible identical with that at the master station; a battery suitable for operating the bell (or buzzer) at the master station; and a push-button switch.

The circuit diagram is given in Fig. 3. No constructional details are given since these will vary according to the cabinet used. The push-button S2 is to ring the bell at the master station, which should then call up the slave station.

Completion of the Intercom

The wires marked A, B and C in Fig. 1 are joined to the sockets marked A, B and C in Fig. 3 respectively. Suitable wire may be purchased for about 10s. per half-mile. A valuable saving can be made by using the earth connection of the mains power supply for the connection marked C. This cannot, of course, be done where the "two-pin" fixtures are in use. **DO NOT USE THE MAINS EARTH FOR A OR B AS IT WILL INTRODUCE A LOUD HUM.**

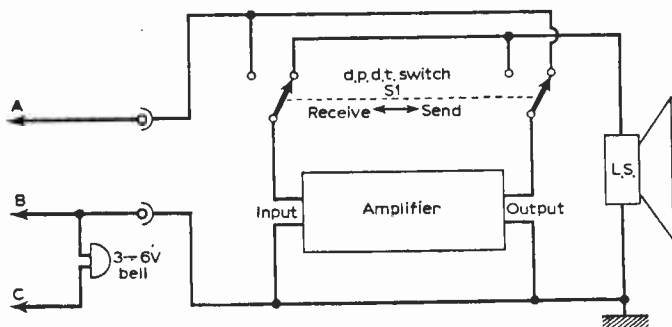


Fig. 1: Circuit of the master station.

whilst not giving an ideal frequency response, simplifies the construction to a great extent. Most enthusiasts will have at least one amplifier suitable for this purpose, the only features required being that (a) it will give a loud output using, as a microphone, a loudspeaker similar to that for which its output is matched, and (b) it has one terminal (earth or chassis) common to the input and output circuits (this avoids unnecessary complications in the switching arrangements). Most radiograms come into this category. The circuit of the master station is shown in Fig. 1.

Two sockets and a double-pole double-throw switch are screwed to the case of the amplifier. One of the sockets is connected to the earth or "common" lead of the amplifier, and the other to two diagonally opposed end terminals of the switch. The remaining two end terminals are connected to the side of the loudspeaker which is not earthed. The connection which formerly went to this terminal of the loudspeaker is now joined to one of the centre terminals of the switch, and the other centre terminal to the non-earthed side of the

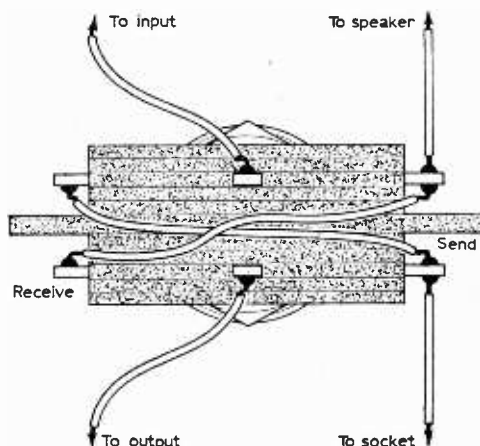


Fig. 2: Wiring of S1.

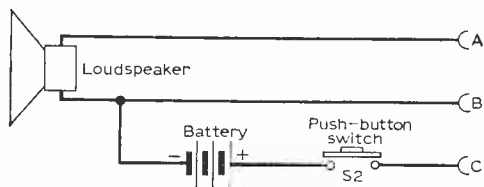


Fig. 3: Slave station circuit.

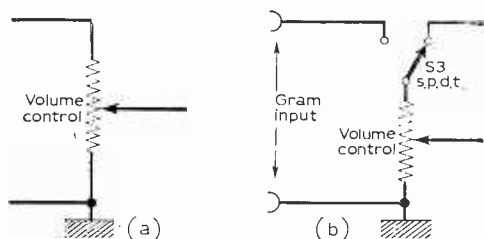


Fig. 4 (a) and (b): These show, respectively, the receiver volume control before and after the incorporation of a gram input socket and S3.

Transistorisation of the Unit

A valve amplifier needs to warm up before use and hurried calls may be delayed because of this. A transistor amplifier is therefore recommended. If a transistor radio is owned the chances are that it is not fitted with sockets for "gram input".

COMPONENTS LIST

R1 100k Ω R2 1M Ω R3 3k Ω

All $\pm 20\%$ $\frac{1}{4}$ W miniature

C1 2 μ F electrolytic 12V

C2 2 μ F electrolytic 12V

Tr1 OC71

S1 D.P.D.T. switch

S2 Bell-push switch

S3 S.P.D.T. switch

S4 D.P.D.T. switch

Using the Intercom

After everything has been correctly connected up, the master station should be switched on, the "gram-radio" switch should be put in the "gram" position, the "send-receive" switch in the "send" position, and the volume control adjusted to about half its maximum value. The user should then make some suitable announcement and switch the "send-receive" switch to the "receive" position, when he should hear suitable comments from his

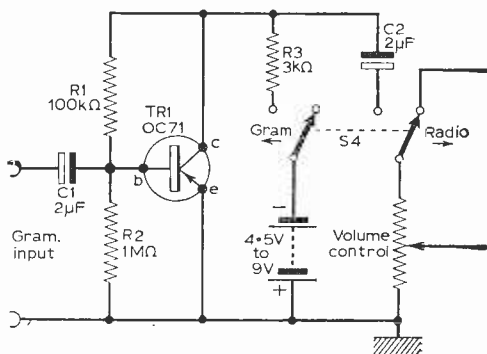


Fig. 5: Circuit of the preamplifier.

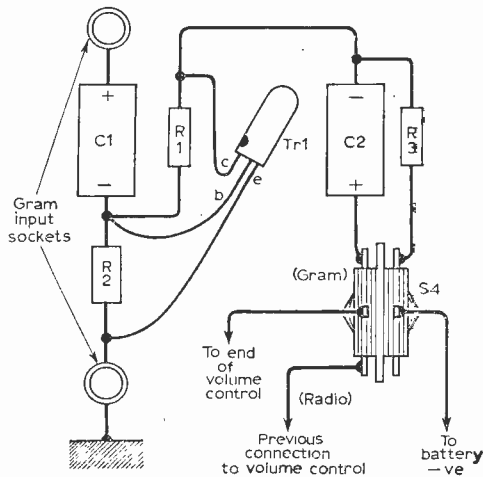


Fig. 6: Construction details of the preamplifier.


These can be fitted very simply by connecting the sockets across the volume control (in most radios). A switch should be fitted to disconnect the radio while using the amplifier. Fig. 4 (a) shows the volume control before alteration and Fig. 4 (b) shows it afterwards.

If this gives insufficient volume, a pre-amplifier is needed. This will follow the circuit of Fig. 5. The transistor is a "red spot" or OC71.

The resistors in Fig. 5 may be $\frac{1}{4}$ W, 20% tolerance types. The capacitors should have a voltage rating of at least 12V. The simplest method of construction is to solder the transistor, 100k Ω and 1M Ω resistors, and the capacitor direct to the sockets and the 3k Ω resistor and other capacitor direct to the switch.

colleague at the slave station. The best position to mount the "send-receive" switch is on the left-hand side of the cabinet, as it can then be operated with the left hand, leaving the right hand free to take notes if necessary. The volume control, if it incorporates the "on-off" switch, should be marked to enable the most convenient position to be selected each time it is switched on. The user soon acquires the knack of switching over the "send-receive" switch to listen or speak.

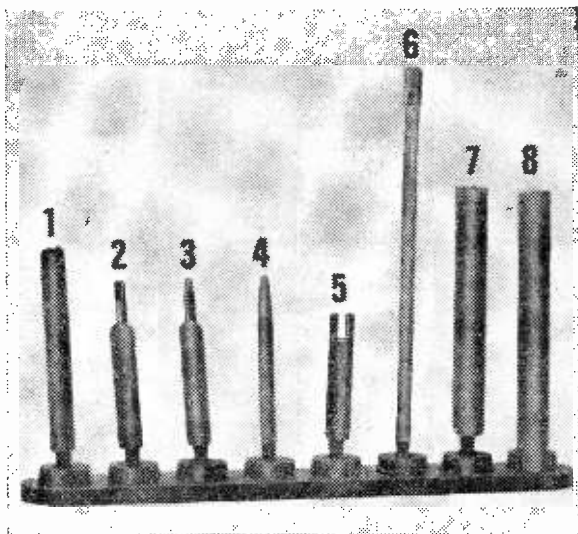The PRACTICAL WIRELESS TRIMMER and ALIGNMENT SET



TRIMMING tools are not only essential to anyone undertaking serious constructional work on receivers, but they are expendable. This is not to say they necessarily get broken, but like the canteen spoon they are liable to become elusive at the critical moment—usually because someone else has borrowed them.

Many readers, no doubt, already have a set of trimming tools, in particular those who obtained the set we presented with the April issue this year. Others make do with improvised trimming tools fashioned from plastic knitting needles or other suitable materials. We are certain, however, that all readers will welcome the new set of tools being presented with this issue—whether they already have trimming tools or not.

The new set is based on the first set but is designed in a different way. Thus the two sets may be, in some ways, complementary. One great improvement is the material from which the new tools are made: this is a new very tough plastic, admirably suited for such applications.

The photograph in the heading shows the tools assembled, and a description of their uses follows:

No. 1 has a wide "screwdriver" blade (though it should not be used as such!) and is used to adjust mica and ceramic trimmers, ferrite pot cores, and slotted hex-nut compression trimmers.

No. 2 has a fine, narrow blade for the adjustment

of slotted cores widely used in transistor radio receivers. The slots are often carried right through the core and the correct method of adjustment is to insert the trimming tool as far as possible before turning, to reduce torsion. Since this is a very popular size, two of these are provided in this kit, No. 3 being a duplicate.

No. 4 has a blade suitable for the majority of iron dust cores employed in radio and television receivers (except transistor radios).

No. 5 has a slotted end which may be used for turning the flattened shank (usually brass) which is used to move a ferrite core in the coil of many radio sets and television turret tuners.


No. 6 is for adjusting tuning slugs with hexagon-shaped holes. This has a long shank so that it may be used with transformers fitted with two such slugs one above the other. The trimming tool is inserted through the upper slug without disturbing its setting, then inserted into the lower slug which can then be adjusted independently, the diameter of the shank is small enough for it to rotate in the hexagon bore of the upper slug.

Nos 7 and 8 are extension shanks. Each has a hole in the top for receiving the spigot of any of the other trimming tools. No. 7, in addition to the hole, also has a spigot, so that it may be inserted into the end of No. 8, thus extending even further the length of the composite tool.

DOES YOUR BBC-2 PICTURE SUFFER FROM NOISE?


If so, you should get the September issue of *Practical Television* (on sale now, 2s.) in which C. H. Banthorpe describes a u.h.f. amplifier designed to overcome this problem. There's much more beside in every issue, to interest, inform and instruct.

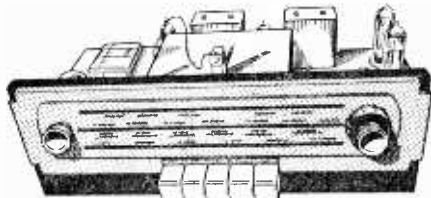BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.10.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 14 1/2 x 4 in. in 2 colours, predominantly gold, 200-250v. A.C. only. Pick-up, EXT. Speaker, A.C. In. and Dipole Sockets. Five push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.; 200-550 M.; 88-95 Mc/s. Valves E280 rect.; EC151, EP89, RABCO, EL84, EC95, Speaker 8 x 3 in. and Cabinet to fit chassis (table model), 47/6 (post 2/-).

10 x 6 in. ELIPTICAL SPEAKER 25/- to purchasers of this chassis. **TERMS:** (4) chassis £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. Circuit diagram 2/6 **ALTERNATIVE DESIGN.** L.W. 1000-1900 M.; 8 W. 69-15 Mc/s; M.W. 190-475 M. A.H.F. 57-100 Mc/s. Gram position. Otherwise similar to above chassis. Price £18.15.0 (car. paid). **TERMS:** £3.10.0 down and 6 monthly payments of £2.4.0.

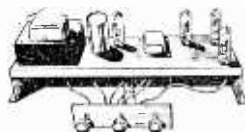

PUSH-PULL O.P. AMPLIFIER £5.5.0

(6/- Car.)

Brand new 200-240 A.C. mains Bass, treble and vol. controls, with valves E280, EC95 and 2-EL84 giving full 8 W. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trace for 2-3 ohm speaker. Front panel

normally screwed to chassis) may be removed and used as "flying panel".


LAFAYETTE BRAND TAPE

FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE	P.V.C. BASE	
5in. Double play, 1,200 ft. ...	5in. Standard play 500ft. ...	8/6
7in. Double play, 1,800ft. ...	5in. Standard play, 850ft. ...	11/6
7in. Stand play, 1,200ft. ...		
7in. Long play, 1,800ft. ...		
7in. Double play, 2,400ft. ...		
TRIPLE PLAY		
3in. 450ft. ...		12/6
4in. 900ft. ...		22/6
5in. 1,800ft. ...		42/6
5 1/2 in. 2,400ft. ...		55/-
7in. 3,600ft. ...		75/-

P. & P. 1/- extra per reel; 4 reels and over Post Free

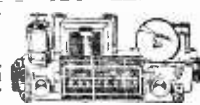
SELF-POWERED VHF TUNER CHASSIS. Covering 88-95 Mc/s. Millard permeability tuner. Dims. 10 1/2 x 4 1/2 x 5 in. high. Valves EC95 and 2-EP89 plus 2 diodes with E280 rectifier. Mains transformer. Fully wired and tested. ONLY £3.17.6 (car. paid). Room dipole 12/6. Feeder 6d. per yard.



6-TRANSISTOR

PORTABLE — Fully Built

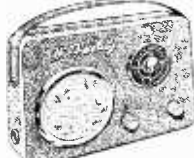The "SCALA" for only £7.10.6 car. paid. 2 1/2 x 2 x 5 1/2 in. high. Choice of colours. Revving. M.W. and L.W. Ferrite aerial Battery 2 x 9 extra. Printed circuit. Nicely styled. A professional job. 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superhet circuit.



BATTERY ELIMINATOR

For 4 Low Consumption Valves (96 range) 90v. 15 mA and 1.4v. 125mA 42/6 (4. post). 200-250v. A.C. Also for 250mA, 1.4 v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Terms available on items over £5. Sent 6d. (stamps will do) for 20 page illustrated catalogue. Delivery by return. C.O.D. 2/- extra.


ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS. Regret overseas orders cannot be executed.

GLADSTONE RADIO

NOTE: NEW ADDRESS:—
66 ELMS ROAD, ALDERSHOT, Hants. (CLOSED MON.)
(2 mins. from Station and Buses). Aldershot 22240

"REALISTIC" 'SEVEN'

7 Transistor Superhet. 350 Milliwatt output. 4 inch speaker. All components mounted on a single printed circuit board size 5 1/2 x 5 1/2 in. in one complete assembly. Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. External Socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc. and full Construction Data: **£5.19.6** P. & P. 4/6.

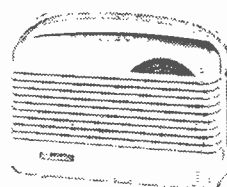

P99 Battery 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel. Any parts supplied separately.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE

PRINTED CIRCUIT. 4 in. x 2 1/2 in. 1 1/2 in. over transformers. Output for 3 ohm speaker. Suitable for microphone, record player, guitar and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types. 200 mV. 29/6; 1 watt. 41/-, P. & P. 2/6.

SINGLE RECORD PLAYER USING EMI DECK AND PICK UP

4 speed. 200-240 v A.C. Valves, rectifier and EL82. Cab. size 12 x 11 1/2 x 5 1/2 in. attractive coloured imitation leather finish. Takes 12 in. records. £7.19.6 car. paid.

ALTERNATIVE TYPE OF SINGLE RECORD PLAYER available. Using BSR G17 motor and pick up on one plate. Valves EY85 and EY82. Cab. size 13 1/2 x 13 x 5 1/2 in. red or blue rexine. Takes 12 in. records. Price £8.0.6 car. paid.



PROTECT AGAINST FIRE. AUTOMATIC FIRE ALARM



Sounds siren when air temperatures reaches 125°F. Measures 6 x 2 1/2 x 1 1/2 in. Only 27/6. (Post 2/-). Or in Kit Form with calibrated Bi-metal contacts 22/6. (Post 2/-).

5 WATT AMPLIFIER

Our price ONLY 58/- (post 5/-); a few hundred only; valves EF91 and EL84 with metal rectifier; 6 x 4 x 1 1/2 in. high (5in. over EL84). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax. input.

GRAMOPHONE AMPLIFIERS AND PLAYERS

1 1/2 watt type. With 6in. x 4in. speaker. Baffle 13 1/2 x 7 1/2 in. 200-240v. A.C. EL82 and Rectifier. Tone and Volume. On-off switch. Two knobs. Ready to play. 49/6, post 3/-.

4 watt type. Valves EY85, EY80 and EL84. 200-240v. A.C. Covered baffle 13 1/2 x 7 1/2 in. (6in. speaker), 3 front controls; bass, treble, on-off vol. 60/-, post 5/- Double wound mains transformer. Cabinet to fit either type with plain motor board £3 car. pd. Complete record player in beautifully styled cabinet, fully built (NOT A KIT) £10.17.6 with TA 14 speed autochanger, or with Garrard Autoalm 4-speed autochanger, £11.6.0.

Single player in Cab. 13 1/2 x 13 x 5 1/2 in. B.S.R. Monarch 4-speed deck, £8.17.6.

QUALITY PUSH-PULL OUTPUT AMPLIFIER

Chassis 10 x 7 1/2 in. high over trans. Used, guaranteed and in excellent order. New valve E240, EC95 and 2 x EL41; 8 watts. Mains trans. tapped 200-250 volts. O.p. Trans for 3, 8 and 15 ohms. Choke smoothing On off vol. and tone controls. For tuners, Record Players, etc. £3.15.0. P. & P. 6/- We can modify for guitar input for 15/- extra.

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12 1/2 x 3 in. Chassis size 10 1/2 x 5 x 4 in. Valves EF86, EY82 and EY84. Controls (1) MIC, Vol. (2) Tuner P.C. Vol. (3) Play back or monitor, (4) Tone, 2 Jack sockets for Tuner/P.C. and MIC-switch or superimpose. Separate power pack containing transformer and rectifier. For Carllaro studio deck only. Price £8.14.0 (6/- P. & P.).

4-SPEED AUTOCHANGERS

BSR-U14	£5.19.6
GARRARD AT108LM	£6.10.0
STEREO	£7.5.0
AT108LM DE LA FAYETTE	£10.19.6
STEREO	£11.10.0

Car. 5/- each

13 x 8 in. LOUDSPEAKER 49.6 (post 3 6).


Three ohm. Ceramic magnet of latest type. BRAND NEW.

HEATER TRANSFORMER

Mains input giving 6.3v. 2 amp Size 2 1/2 x 20 x 1 in. (2 in. over windings). 5/6 ea. Less 10% for 12, or 20% for 30. P. & P. 2/- for 1 to 6, post free more than six.

FOR THE FIRST TIME

Plug-in ELECTROLYTIC CAPACITORS

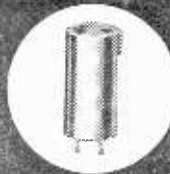

SMALL • FULLY ENCAPSULATED • PLASTIC CASED

These new T.C.C. small plastic-cased electrolytic capacitors have been specially developed for vertical mounting on printed circuit boards, and are designed for operation at temperatures from -20°C to $+60^{\circ}\text{C}$. Three case sizes are available in rated voltages up to 50V. The standard

tolerance of the range is $-20\% +100\%$ of rated capacitance. The anodes are of super-purity aluminium, with all-welded internal connections. A special electrolyte ensures low impedance at all frequencies in the audio range.

LOW LEAKAGE CURRENT & LONG LIFE—assured by fully automatic winding of elements, avoiding handling of electrodes by operatives.

TERMINATIONS OF STEEL CORE

COPPER WIRE—

specially solder coated for fast, ripple soldering technique.

QUICKER ASSEMBLY

Steel cored wire gives precision acceptance of capacitors when inserting into punched printed boards.

QUICKER IDENTIFICATION

Colour coding and embossed values enable instant selection of the right capacitance and voltage.

HIGHLY COMPETITIVE PRICES

Full full details please write for Technical Bulletin No. 102

THE TELEGRAPH CONDENSER CO. LTD.

NORTHACTON, LONDON W.1 Telephone: ACO 01 0661 (16 lines) Telegrams: Telcand, Wapphone, London. Telex: 261383
 (also at) CHESSINGTON, SURREY — BATHGATE, SCOTLAND

SUMMER BARGAINS

Air Spaced Trimmers good length 1 in. spindle 0-30pf but easily converted down to 0-5 pf 2/6 each, post 1/-, 10 to 20 pf 2 gang for P.M. Tuners etc. 4/6 each, Post 1/-.

High Voltage Condensers 2 mfd. 1.2kv 4/6, 4 mfd. 1.5kv 6/6, 2.5mfd. 4kv 6/6, .01mfd. 5kv 3/6.

Transmitting Aerial Condensers 20kv 10012mfd. 12/6, 6kv 20002mfd. 6/6.

Rectifier Valves 4 pin 4v 120ma full waves replace M12 etc. 4/6. P. & P. 1/-, 40/- per doz. Post free.

Double Trimmers. Ideal for making pre set station receiver 100pf plus 100pf 6/- per doz. Post 1/-.

Trimmer Assortment. 3 doz. various sizes and types including double and ceramic air spaced. Retail list value over £4. all new and unused 10/- for 36. Post 2/-.

Mica Condenser. 100pf, 200pf, 300pf, 500pf, 1000pf 3 doz. assorted list value £2. 3/- for 5/-, Post 2/-.

Litz Wire for coil winding. Normally over 40/- per lb. from makers, 1 lb. recs 20/- each Post and Packing 2/-.

Motor Generator. 6v input gives 12v output suitable to run 12v car battery Radio on 6v battery 17/6. Post and insurance 3/6.

Post Office Type Key Switch. 3 position 10 change over contacts 7/6. Post 1/-.

23in. T.V. Cabinet. Complete with mask. These are very fine cabinets made for Philips. We recommend you collect, but will send at your own risk. 25/- Carriage and packing 10/-

Volume Control Bargains. All fitted with switch and good length spindle following values available: 5k, 10k, 25k, 50k, 100k, 200k, 500k each. 1/- post. Orders over seven, post free.

Hours Elapsed Meter. Fine American make unused but ex equipment. 35/- each, Post 2/-, 12v 10amp Rectifier. 8 pin. sq. plates 19/6. Post 2/-.

Transistor ferrite rod aerial with medium and long wave coils with circuit. 7/6.

Oscillator Coil and set of 3 I.F. transformers for transistor set with circuit. 12/6.

Midret 3in. P.M. Loudspeaker 5 ohm, 12/6, 5 ohm, 13/6. Midret 200 pf + 150 pf two gang Tuning Condenser with trimmers for transistor set. Price 9/-.

Zener diodes for voltage control and stabilisation. Complete with circuit diagram, 3/6, each.

UNIQUE OPPORTUNITY FOR CONSTRUCTORS

Good Companion

6 Transistor superhet with remarkable performance over medium and long wave. Opportunity occurs to make this very fine receiver, which uses mainly standard parts at a very low price. Constructors parcel comprising: 2 tone cabinet as illustrated printed circuit board, wave change switch, volume control with on/off switch, self adhesive scale pointer, 2 small knobs, 1 gold embossed tuner. Full constructional data, retail value of this parcel 69/6. This month offered for 39/6 post and packing 5/6.




THIS MONTHS BARGAIN

MAINS POWER PACK designed to operate transistor sets and amplifiers. Adjustable output 6v—9 to 12 volts for up to 300ma (class B working). Takes the place of any of the following batteries. PP1-PP4, PP6-PP7, PP9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor 3000 and 500 ohm condensers, zener diode and instructions. Retail snip at only 14/6 plus 2/6 post.



Amplifier for Portable Player —

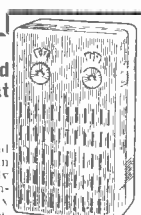uses three valves, has push pull output for quality and power and mains transformer for safety. Real bargain at 29/6 plus 2/6 post (less valves).



OUR BARGAIN OF THE YEAR

Complete kit of parts to build transistor 2 wave receiver at only 39/6.

"CORONET" Mk. III

It fully covers the medium wave-band and that part of the long wave-band to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and Plessey tuning condenser. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2. Supplied complete with carrying case.

Speaker Bargain

12in. High-fidelity loudspeaker. High flux permanent magnet type with stand and 3 ohm speech coil. Will handle up to 12 watts. Brand new, by famous maker. Price 27/6 plus 3/6 post and insurance.



This fine cabinet as illustrated but less control knobs is available this month at special snip price of 12/6, plus 3/6 post and insurance. Size is 13 1/2 in. x 9 in. x 4 in. and it is nicely covered in two-tone t.c.l. fabric.

Cabinet Snip



Siemens High Speed Relay

Two 250 ohm coils adjustable tension change over contacts—plate points 7/6. Post 1/-.

Five Core Cable

Ideal for switching circuits, intercoms, P.A. runs etc. each core flex copper with rubber insulation, cores covered overall in tough rubber or P.V.C. 3d. per yd. or 30 yds. length 15/- plus 5/- post.

ELECTRONICS (CROYDON) LTD

266 LONDON ROAD, WEST CROYDON, SURREY
 Post orders to: 43 Silverdale Road, Eastbourne, Sussex

PART I

Understanding SEMICONDUCTORS

BY LESLIE MOORE

THE series aims to give the reader a basic knowledge in the use of semiconductors and the principle of operation of several different types of circuit. It also aims to give the amateur ability to design these basic circuits with a minimum knowledge of mathematics. A knowledge of Ohm's law and the basic operation of components such as inductors, capacitors, etc., will be taken for granted.

CONTENTS OF SERIES

The principle of operation of the crystal diode with a brief explanation of their atomic structure, the circuit symbol of the diode and an illustrated explanation of the junction diode as a half-wave rectifier.

Reasons for full-wave rectification, introduction to power supplies, rectification, smoothing, stabilisation. An explanation of the smoothing circuit will be given. The zener diode and its use as a stabiliser and the conversion of thermionic rectifiers to semiconductor rectifier circuits.

An explanation of the principle of operation of the transistor, its use as an amplifier and an explanation of the derivation of a formula for current gain. The grounded emitter amplifier, input impedance, output impedance, impedance matching between stages. Frequency response of the amplifiers, negative feedback, the emitter follower. Summary of amplifier.

Oscillators—comparing the oscillator to an amplifier with feedback; the Wein bridge, phase-shift oscillators; an L.C. oscillator.

The free-running multivibrator with a brief explanation of the other multivibrators that exist (± 2 cts, etc.).

No circuits will be given as typical examples of working models. It will not be possible to include the whole of one subject in one article except that of the explanation of the principles of operations of single articles, e.g. introductory passage.

THE OPERATION OF THE CRYSTAL DIODE

Since the introduction of crystal diodes as an electronic device an amazing revolution has taken place. The semiconductor has now become a part of the modern way of life; to enable a greater understanding of their uses and applications this series of articles has been written.

A basic knowledge of atomic structure is necessary to enable the understanding of the operation of semi-conductors.

An atom, the smallest obtainable particle of an element, consists basically of a nucleus encom-

passed by orbiting particles known as electrons.

The nucleus contains several different sized particles the largest of which are the neutron, an electrically neutral particles, and the proton, which is of equal mass to the neutron but holds a positive electrical charge. The number of protons in the nucleus is equal to the number of orbiting electrons. Electrons orbit the nucleus in a set manner as can be seen in Fig. 1.

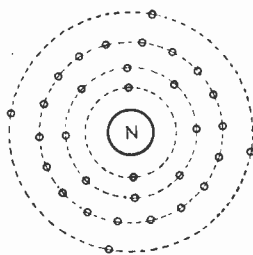


Fig. 1: The germanium atom.

The germanium atom has 32 orbiting electrons set in fixed paths known as shells. The first shell contains two electrons, the second eight, the third 18, the fourth four, but in other atoms is capable of holding as much as eight electrons.

Copper has only 29 orbiting electrons, hence it has only one electron in its outer shell. The nucleus has little influence over the single electron because of the comparatively large distance between the two; on the application of an external electrical force the single electron can be easily attracted away from the atom. This enables copper to be a good conductor of electricity, electricity being the flow of electrons.

Germanium, however, has four electrons in the outer shell, so that a greater attraction between the outer shell and the nucleus is established, making the attraction of electrons from the atom difficult. Because of this characteristic germanium is known as a semiconductor.

The atoms in a germanium crystal form themselves in such a manner so that each atom shares each one of the electrons in its outer shell, with another atom making it appear that each atom has a full outer shell of electrons. The formation is known as the crystal "lattice".

If small quantities of (a) arsenic and (b) gallium are added to germanium crystals the following will occur:

(a) Arsenic has five electrons in its outer

shell and an arsenic atom will take place in the lattice as a germanium atom; this will leave a single atom to orbit the arsenic atom. As electrons hold a negative charge this material is known as "n" type.

(b) Gallium has three electrons in the outer shell and if a similar occurrence happens as before, neighbouring atoms in the lattice will share their electrons with the gallium atom but

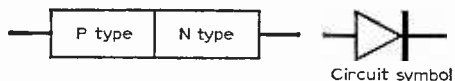


Fig. 2: Make-up of the semiconductor. The bar of the circuit symbol is equivalent to the cathode of the thermionic diode.

in return can only share three atoms with the germanium. Between two atoms, therefore, there will be a space, one electron missing, which is called a "hole". Because the electrons have a negative charge and the holes indicate a lack of negative charge the holes are said to have a positive charge; this material is called "p" type.

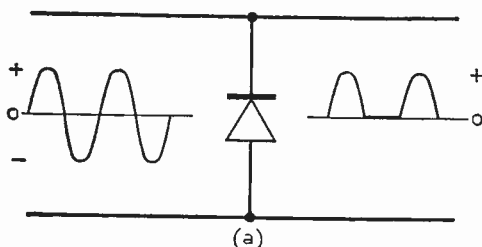


Fig. 3: The action of half-wave rectification: (a) obtaining a positive pulsating direct current; (b) a negative pulsating direct current.

When a junction is made by joining a "p" type crystal to an "n" type crystal the additional electrons in the "n" type begin to flow into the "p" type for a short period and form a barrier at the junction, preventing any further flow of electrons.

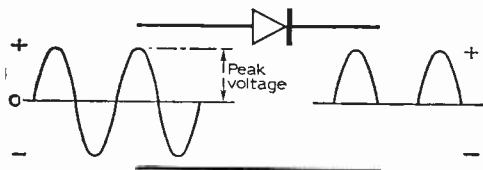


Fig. 4: Arrangement for drawing no current from the supply.

The junction barrier so formed is of such a manner to allow electron flow to take place when an external voltage source is applied to the junction, making the "p" type of positive potential with respect to the "n" type. When the voltage or "bias" is reversed the junction will not conduct.

If an alternating voltage were to be applied to the diode the action previously described and as shown in Fig. 3 would occur.


It has been explained how a semiconductor diode could be used as a half-wave rectifier. The problem with this method is one of power consumption; the half-wave not seen in the output is returned back to the supply, so that half the current drawn from the supply is wasted. If the diode were to be connected as shown in Fig. 4, on the half-cycle which is not seen at the output, no current would be drawn from the supply.

The application of rectifying circuits in electronic circuitry is most prominent in power supply units.

For reasons of economy the vast majority of mains supplies in this country are alternating current (a.c.) rather than direct current (d.c.).

The majority of electronic equipment requires a direct current supply and to produce this an a.c. to d.c. power supply unit is used as shown in Fig. 5.

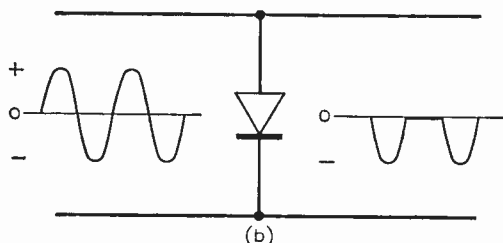The rectifying circuit produces a pulsating direct voltage from an alternating voltage. A half-wave rectifier may be used for this purpose but the average output voltage is low compared with the



peak voltage of the input. A more efficient but more expensive arrangement is the full-wave rectifier which is a combination of a number of semiconductor diodes. This is shown in Fig. 6.

(1) On the application of a positive half-cycle of alternating voltage it is seen that diode (a) will

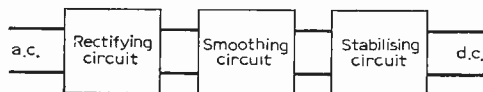


Fig. 5: Block diagram of a power supply.

conduct current but diode (b) will not, so that the positive half-cycle will appear at point A.

(2) On the negative half-cycle the signals will be seen by diodes (c) and (d). Diode (d) will not conduct current under this condition but diode (c) is biased to enable it to conduct current. The negative half-cycle will therefore appear at point B.

If the output terminal B is held at a steady voltage, usually zero voltage or "earth", the second half-cycle will appear as a positive voltage at A with respect to B.

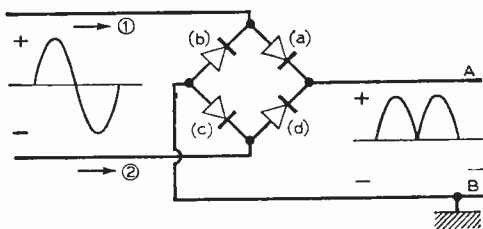


Fig. 6: The full-wave rectifier.



Fig. 7: The waveform obtained when terminal A is held at steady voltage instead of B.

If a "negative voltage" is required it is in order to hold terminal A at a steady voltage, instead of B, and the voltage at B will appear to be a pulsating negative direct voltage (see Fig. 7).

It is obvious that the full-wave rectifier produces an average voltage greater than that produced by the half-wave rectifier for the same input voltage.

Another advantage of the full-wave rectifier will become apparent when smoothing circuits are dealt with.

The basic component of a smoothing circuit is a capacitor as depicted in Fig. 8.

As the first input pulse is applied the capacitor draws current from the rectifier circuit and charges to the peak voltage. If a normal load (or a current drawing circuit) is placed across the capacitor, after the first pulse is applied, the capacitor will then supply current to the load.

Because current is being drawn from the capacitor the voltage across it will drop; the rate at which the voltage across the capacitor falls is much less than the rate at which the voltage from the rectifier falls. The voltage supplied to the load will begin to rise after the rising voltage of the second pulse from the rectifier coincides with the falling voltage across the capacitor.

The waveform due to the changing voltage difference across the capacitor is known as voltage ripple.

There are numerous types of smoothing circuits used, all of them employing the charging of one or several capacitors.

For very good smoothing a filter network, as shown in Fig. 9, is used.

The inductance or choke, L, opposes alternating voltages without dissipating excess power. The capacitor C' functions in a similar manner to

capacitor C, reducing even more the voltage ripple. A less expensive method is to replace the inductance by a resistor. The resistor opposes direct and alternating voltages equally. The effectiveness of smoothing in this case is less than the first.

The type of smoothing used for a circuit is entirely dependent on the degree of d.c. the circuit is required to produce.

The stabilising circuit involves more complex components and will be dealt with later in the series.

In many commercial radio receivers, etc., it would be uneconomical to stabilise the output from the smoothing circuit, so the stabilising circuit is omitted.

The resistor R is placed in the circuit (Fig. 10) to limit the peak rectifier current. If the peak current became excessive the semiconductor diodes

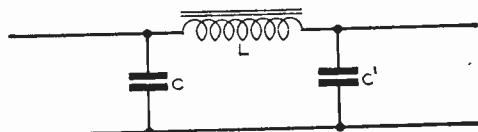


Fig. 9: A filter network.

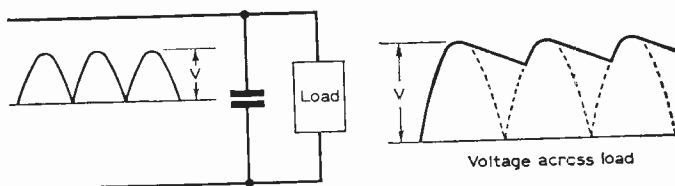


Fig. 8: The basic smoothing circuit and its action.

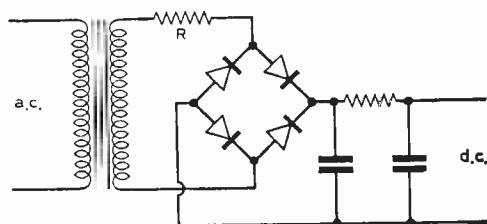


Fig. 10: A typical unstabilised power supply.

would overheat and eventually break down.

This resistor is also used to limit the effect of mains "surges" in the circuit. The mains voltage is by no means "stable" and can vary within values as much as 30V apart.

The voltage and current ratings on semiconductor diodes must be strictly adhered to; it is imperative that mains variations be taken into account when utilising this type of rectifier for a power supply unit.

Part 2 follows next month

BOOKS REVIEWED

EXPERIMENTAL RADIO ENGINEERING

By E. T. A. Rapson. Published by Sir Isaac Pitman & Sons Ltd.
214 pages, 8½ x 5½ in., boards. Price 14s.

THIS is a fifth edition of an old favourite which dates back to the war years. It will be remembered by many old hands and in its up-to-date edition will, no doubt, be welcomed by newer students of radio.

A new chapter has been added which is devoted entirely to transistors, measurement of parameters, etc.

This book is not intended for the general reader and has, obviously, been written with the technical student in mind.

The entire volume consists of a series of experiments in radio engineering which range from the characteristics of attenuators and filters to electro-acoustic tests.

This volume would, as the preface rightly points out, be suitable for a student attending a three year course in radio engineering at a technical college. Would-be students and prospective radio engineers are referred to Mr. Rapson for further details.

At the price, this is extremely good value.
—D.L.G.

COMPUTER CIRCUIT PROJECTS

By Lee Boschen. 144 pages. Price 21s.

THERE are many men in the realms of electronics, be they professional or amateur, who are bonded by one common tie—they are practical people. While they no doubt enjoy the odd spate of technical literature they are never more happy than when there is a trusty soldering iron in one hand and a reel of "resin cored" in the other.

This group should find **Computer Circuit Projects** of great interest, since it caters for just such tastes. It takes the terrifying and grand name of "computer" and transforms it into 143 pages of practical and interesting circuitry. There are 14 such projects ranging from a single stroboscope to a Rally Computer. Some of these circuits are very similar to others already published. The "Logic Lock" and the "Automatic Signal Flasher" for instance. However, there are numerous ideas to suit all tastes.

It should not be thought that this book is merely a collection of circuit diagrams printed on a few pages. Each project has photographs of it together with other illustrations, and with each there is a discussion of circuit action. The circuitry as a whole is right up to date, some using transistors, some diodes or valves, and in some cases an alternative circuit transistor and/or valve is offered.

For those who are tired of t.r.f.'s and audio amplifiers and would like to build something different but not too difficult, then you are advised to visit your local bookshop with 21s.—D.L.G.

ABCs OF COMPUTERS

By Allan Lytel. 128 pages. Price 16s.

THE word computer conjures up many things in the mind. Huge grey steel monsters with staring, winking eyes, rows of meters pulsing, and memory mechanisms buzzing. To the average man and to many electronic enthusiasts the word often means huge consoles and thousands of diodes, transistors and/or valves, and quite unconventional and frightening circuitry. Rumour even has it that the grids are taken direct to h.t.+ and that transistors are connected the wrong way round—on purpose.

For those who profess to be impartial, and prefer to think for themselves, together with those readers who would like to know some basic facts about computers, it is suggested that an outlay of 16s. of the realm be made. This modest sum will enable the "enquiring" to obtain a tome of knowledge aptly titled **ABCs of Computers**, and as this title implies it is a book which supplies the basic facts on this fascinating subject. Its 128 pages are generously sprinkled with illustrations and the text is well written and concise.

In a book of this size it is obviously not possible to enter deeply into the subject and the would-be reader, therefore, need not fear that he will be dragged into heavy technical discussions. The chapters 4 and 5 on "Numbers for computers" and "Arithmetic Operations" are a pleasure to read. The binary system seems easy enough, once it is understood, but understanding it in the first place can prove very tricky. Some writers never seem to present this binary business very clearly and often gloss over it in a few words.

However, it would not be true to say this of Allan Lytel. It would have been even more useful had values been given to all circuit diagrams, even more so in this case since the novice would not have any idea of values in these types of circuits shown.

Also, perhaps, having educated the reader to a certain standard it would have been helpful to have provided a list of suggested books for further reading. However, for the person wishing to scratch the surface of this fascinating field—**ABCs of Computers**—is recommended.—J.D.G.

ABCs OF ELECTRICITY

Howard W. Sams Editorial Staff. 96 pages. Price 16s.
These three books, originally published in the USA by Howard W. Sams & Co. Inc., and now published and distributed in this country by W. Foulsham & Co. Ltd. Each book has a preface for British readers written by W. Oliver, G3XT. The common format is 8½ x 5½ in., stiff covers.

IN any technical field there is one segment of learning more vitally important than any other—the ground work. It is essential that the basic theory be fully understood, and although this may prove a long "slogging" effort it is well worth while in the long run.

ABCs of Electricity is obviously written for the raw beginner and offers five chapters—Electricity (batteries), Magnetism, A.C. Theory and
—continued on page 535

on the Short Waves

A MONTHLY COMMENTARY BY J. GUTTRIDGE

HAVING gleaned and logged all the information we can about a station's signal we come to the business of sending off a reception report, and if possible getting it confirmed by a QSL card.

An ordinary piece of notepaper can be used for the actual report but a much neater report can be made on quarto lined paper. Neatness and simplicity are important because (except at the bigger stations) it will probably be in a language of which the evaluating engineers only have a limited knowledge.

As a general rule all stations except those in South America will accept a report in English. With South America, unless you are dealing with a station which you know to have an English section, the report should be in the local language—Spanish or Portuguese. A suitable translation is contained in "How to listen to the World".

The first thing a report should contain is your name and address. Great care (block capitals) should be taken to see that this is legible. If the station can't even read your address it is unlikely to persevere with the rest of the report!

To start off you should say something to the effect that recently you were very pleased to hear the station concerned and are enclosing a report on its signal, mentioning the reporting code you are using e.g. SINPO, SINFO, RSI. After this you should ask the station to verify the report, if it finds it to be correct, with its QSL card.

The final part of your letter should deal with your receiving equipment. Details stations are interested in are the type of your receiver (domestic or communications) and the sort of aerial you are using—dipole or end fed, indoor or outdoor.

You should then set out your report. It should take a similar form to your log with columns for date, time (stating the zone you are using, Greenwich Mean Time being the most common), frequency (stating whether kilocycles or megacycles), the report (SINPO) and remarks.

Two items go in the last column. The first of these is interference details. These should include the type (jammer, broadcast, c.w.) of the interfering station and its frequency. The second item consists of details of the programme heard. The purpose of giving these details is to prove absolutely to the station that you really heard it. Unfortunately there are some unscrupulous QSL collectors who invent reception reports in the hope of gaining QSL cards. Some stations will waive the programme details after you have proved yourself if you report regularly to them.

Ideally your report should cover at least half an hour's listening time though this need not all be at the same time. Stations that use more than one frequency for a transmission especially appreciate

comparative reports on the frequencies used. You can end your report with such things as a programme schedule request. Record requests or questions for special programmes are best sent in a special letter.

Finally there comes the question of return postage. With large and government stations this is normally unnecessary. Smaller stations, however, often appreciate it. A full list of stations requiring return postage is given in the "World Radio and Television Handbook". Postage if sent should be in the form of an International Reply Coupon which you can obtain at your Post Office. Don't forget, incidentally, that your report will usually require more than a threepenny stamp.

DX NEWS

News has just arrived from Radio Japan of its plans for broadcasting the Olympic Games to the world. An unenviable task this, as the games are taking place at about the worst time possible as far as reception conditions go. Because of this two new 100kW transmitters are being linked together to give an output of 200kW.

From October 10th to 24th when the games are in progress there will be special programmes during Radio Japan's normal transmissions and the general service will be especially extended. Normal transmissions to Europe in English will be at 0800-0820 GMT on 11.780/15.135kc/s. English broadcasts in the General Service consisting of both live and recorded items are as follows: On 9.505/15.195/15.310kc/s — 0645-0700, 0745-0800, 0845-0900, 0945-1000 and 1045-1100; on 9.505/9.740/11.815kc/s—1245-1300, 1345-1400, 1445-1500, 1545-1600, 1645-1700, 1745-1800 and 1845-1900; on 11.815/11.940/15.195—2145-2200; on 11.940/15.105/15.425kc/s—2345-0000; on 15.105/15.195/15.310kc/s—0245-0300, 0345-0400.

On October 10th the opening ceremony will be broadcast live from 0450/0700 and on October 24 the closing ceremony will be broadcast live from 0800-0900. Programme schedules giving full details are available free of charge from Radio Japan, Tokyo, Japan.

Radio Australia has been coming through well in the late evening recently. Two transmissions recently logged around 2245 in London were an Indonesian programme on 11.760kc/s and an English programme to Southern Asia. This station's U.K. transmission in English is from 0630-0730 on 9.570/11.710kc/s but is not coming through too well at present.

A Middle Eastern station presenting quite a challenge is the Kuwait Broadcasting and Television service. It is sometimes audible after 1930 through heavy CW on 4967kc/s.

For more DX news see page 573

87 Experts guide you to advancement and higher rewards



Use it Free
for 7 days

ABSOLUTELY COMPREHENSIVE!

This is what you receive without cost or obligation—

4 Volumes strongly bound in Grey Morocquette 9½ in. x 6½ in. 2,352 Pages of instructive information on latest practice. Over 2,000 Photos, Diagrams, Perspective and Working Drawings, Electrical Circuits, and Data on test procedure, etc.

24 Data Sheets in colour and 12 Quick-reference Blueprint Charts complete in strong Chart Case.

Nuclear Power Stations Booklet Contains fascinating cut-away sections in full colour with explanatory text.

Free! Newnes Electrical Pocket Book (Value 10/6) Nearly 400 pages with 258 illustrations, diagrams, tables.

Plus 2 Years' Free Postal Technical Advisory Service

YOUR FUTURE, if it is in electrical engineering, depends on your ability and the services you can render. The more experienced you are the better your prospects, the better your income... it's as simple as that! This New Edition of Newnes comprehensive and authoritative publication is invaluable to you if you mean to progress. Produced with the full technical resources of NEWNES it covers every facet of the vast field of modern electrical engineering.

INSTALLATION WORK OF ALL KINDS

Commercial Buildings, Small Houses and Flats, Hospitals, Schools, Theatres, Cinemas, Electric Appliances, Alarm Systems.

INSTRUMENTS, MACHINES, EQUIPMENT

Electric Motors, Control Gear, Transformers, Rectifiers, Electronic Control in Industry, Measuring and Recording Instruments and Electricity Supply Meters.

OPERATION, MAINTENANCE, REPAIR

Welding Plant, Electric Traction, Cranes, Lifts, X-Ray Equipment, Testing Domestic Equipment, Batteries.

GENERATION, TRANSMISSION, DISTRIBUTION

Power Stations, Power Cables, Public Supply, Underground Distribution Systems, Town and Rural Supplies, Cable-laying and Faults.

Over 2,000 Instructive Action Photographs, Diagrams, Working Drawings, Circuits. Many Concise Data Tables.

SEND TO-DAY—FREE EXAMINATION will enable you to check it for your day-to-day problems—it will surprise you!

IF KEPT SAME PRICE CASH OR TERMS—NOTHING EXTRA IF YOU PAY MONTHLY

To: GEORGE NEWNES LTD., 15-17 Long Acre, London, W.C.2
Please send Newnes PRACTICAL ELECTRICAL ENGINEERING without obligation to buy. In 8 days I will return it or post only 16/- deposit, then 16/- monthly for 20 months, paying £16. 16s. in all Cash in 8 days £16. 16s.


If under 21 your father must fill up coupon.
If married woman your husband must fill it up.

Full Name (BLOCK LETTERS) _____ (Mr., Mrs., Miss)
Address _____

Occupation _____
Signature (Mr., Mrs., Miss) _____
(PEE)72/850

Tick ✓ where applicable
The address on left is—
My Property ☐
Rented unfurnished ☐
Parents' Home ☐
Furnished Accom. ☐
Temporary Address ☐

TAKE FIVE!

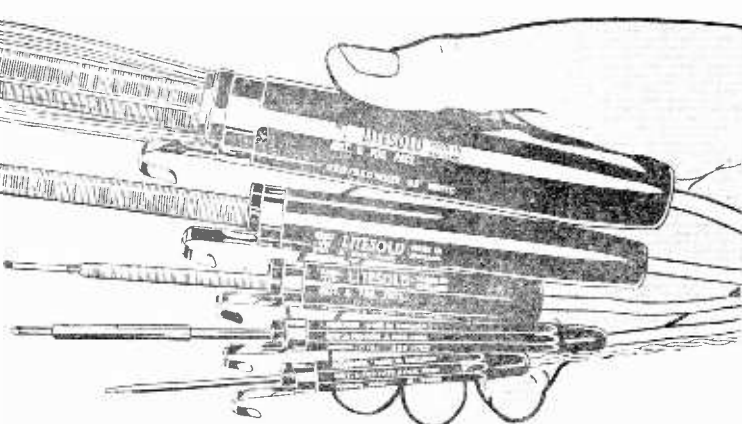


There are 30 other models, too. There ARE several other makes of soldering instruments. Big ones. Small ones. Good ones. We've seen them. We don't make the biggest ones. Or the most expensive ones. Or the most elaborate ones. We DO make the smallest ones. And the widest range. We make the best. Always have. May we send you details?

Brochure P.W.10 post free on request

LIGHT SOLDERING DEVELOPMENTS LTD., 28, Sydenham Road, Croydon, Surrey,

Telephone: CROydon 8589

TEST METERS

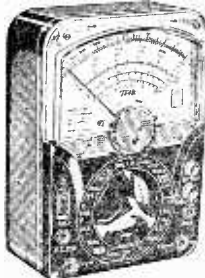

30,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 V.C. at 30,000 ohms per volt and A.C. at 15,000 ohms per volt. D.C. current to 12 amps. Resistance to 10 Megs. Headed from -20 to +50. Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.C. output measurements. Size 3 1/2 x 6 3/4 x 2 1/2 in. **£8.19.6**

2,000 OHMS PER VOLT MODEL TP-10. Reads A.C. and D.C. volts up to 1,000. D.C. current to 500mA. Resistance to 1 Meg. Capacitance to 10 pF. De-bell-front -20 to +30. Output lock for Audio measurements. Size: 3 1/2 x 5 x 1 1/2 in. **£3.19.6**

DOUBLE BEAM OSCILLOSCOPE TUBES
Another purchase in Type CV 15961 equiv. lent to Cosmo 49D as used in Os-40 scopes by Cosmo (330 series) and Bartley & Easline (13 series). Listed £12.
Brand new in Maker's **25/-** rates. Carriage 2/-.

HIGH FREQUENCY A.C. VOLTMETER. A First Grade Moving Iron Instrument with 60 in. Mirror Scale, reading up to 150V A.C. at 100 and 1,200-2,400 cycles. In substantial Oak case with removable lid overall size 8 x 8 1/2 x 3 1/2 in. Made in the Air Ministry by Expert Edgemund and in perfect order. Brand New and Unused. ONLY **£5.** Can also be supplied for 50 cycles, or either 0-150 or 0-100 volts.

20,000 OHMS PER VOLT MODEL TP-5S. Reads voltages up to 1,000 V.C. at 20,000 ohms per volt and A.C. at 10,000 ohms per volt. D.C. current to 500mA. Resistance to 10 Megs. Capacitance to 0.001 pF. De-bell-front -20 to +30. Size: 3 1/2 x 5 x 1 1/2 in. **£5.19.6**

TRANSISTORISED INST. LA'OLA TESTER. One hand operation, no cranking of generator. 3 testing voltages 100, 250 and 500 to measure up to 500 Megohms. Complete with leather carrying case and test leads. ONLY **£17.10.0**. Illustrated details on request.

SUPER CRYSTAL SICK MIKE. Complete with heavy desk stand neck cord, and screened lead. ONLY **49/6** (post 2/6).

SPRAGUE CONDENSERS. Metal case, wire end. New 0.1 mfd. 1,000 volt and 0.1 mfd. 500 volt 7/3 per dozen. Special quotes for quantities.

TEST.ORS. 100 assorted values on choice. New 7/6.

PANEL METERS

25 microamps D.C. 2 1/2 in. Prot. circular 59/6. 50 microamps D.C. 2 1/2 in. Finish circular 59/8. 100 microamps D.C. 2 1/2 in. Finish circular 59/8. 10 amps D.C. 2 in. Prot. circular 7/6. 500 volts A.C. 2 1/2 in. Finish circular 25/6.

MOVING COIL STICK MIKE complete with heavy desk stand, and screened lead. ONLY 59/6 (post 2/6).

ACOS 30/1 STICK MIKE with screened lead and table stand ONLY 32/6 (post 1/6).

CRYSTAL DESK MIKE with screened lead and built-in stand. ONLY 15/- (post 1/6).

15 OHMS P.M. SPEAKERS. Special Heavy Duty 12 in. 55.0.

Wharfedale W12EG 12 in. or Lead Guitars. **£10.10.0**. Wharfedale W15EG 15 in. Bass Guitars. **£17.10.0**. 12 in. wedge type speaker cabinet 29.12.6. (Phone add 5/- with all items).

CONDENSERS. 100 assorted sizes and silver mica. NEW 10/-.



VARIABLE VOLTAGE TRANSFORMERS. Fully shrouded. Input 230 v. A.C. 50/60 cycles. Output 0-250 v. 2.5 amps. type 55.17.5. 5 amps. type 29 10 amps. type 115.10.0. Brand new import fully guaranteed. Immediate delivery and service. Illustrated details on request.

30/- CONSTRUCTOR'S PARCEL Assorted colour wiring wire solder, resistors, condensers, volume controls, tag panel. ALL NEW (post 2/6).

LINEAR AMPLIFIERS. LC34, 4 watts, size 8 1/2 x 4 1/2 x 2 1/2 in. high. **£5.5.0**. 1.45 A 5 watts, size 7 x 7 x 5 in. high. **£5.19.6**. Protective cover 12 9. 1.55 5.5 watts stereophonic, size 10 1/2 x 8 x 5 in. high **£12.12.0**. Cover with carrying handles 25/6. "Hi-Fi" 10 watts Hi-Fi Ultra Linear Push-Pull, size 9 x 7 x 6 in. high. **£12.12.0**. Cover with carrying handles 19/6. 1.1 10 10 watts Hi-Fi Ultra Linear size 9 x 7 x 5 in. high **£13.18.0**. Cover with carrying handles 19/6. "Oneohm" 20 watts Hi-Fi Ultra Linear size 12 1/2 x 7 1/2 x 5 in. high. **£13.16.0**. Cover with carrying handles 25/6. 1.50 50 watts Hi-Fi Ultra Linear, size 14 x 10 x 5 in. high. **£23.2.0**. Cover with carrying handles 32/6. All amplifiers for normal A.C. mains, and ex stock. Details on request.

"Tripletone" Convertible Amplifier. size 10 x 3 x 4 1/2 in. high. 4 watts output matched for 2-3 ohms. Or 2 amplifiers can be coupled together for STEREO **£6.19.6** each.

"Tripletone" F.M. Tuner, size 11 x 6 x 5 in. high. Coverage 80-104 Mc/s. **£13.19.6** (unpowered), or **£15.14.6** (self powered). Details on request.

HETERODYNE FREQUENCY METERS TYPE LM14. Frequency range 125-20,000 kc/s in 2 bands. This is the United States Navy Model of the well-known R-221 Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation circuits and Crystal control ensure extreme accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a signal generator. Size only 8 1/2 x 8 x 3 1/2 in. Full information on request.

HARRIS ELECTRONICS (London) LTD.
138 GRAY'S INN ROAD, LONDON, W.C.1

Telephone: 41 RUMORS 7357.

Please include carriage cost on ALL items

Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross

easily measured but with the values of R, C1 and C2 shown, 150mA fuses are satisfactory.

It is important that the rectifiers should have adequate peak inverse voltage rating. Referring again to Fig. 1, when the right hand side of SR1 is 250V rms above earth, the peak voltage at this point will be 1.414 times as great, i.e., approximately 350V.

Capacitor C2 and the left hand side of SR2 will also be at this potential; but the right hand side of SR2 will at the same instant be 350V peak negative to earth so that the peak voltage across it in the non-conducting direction will be 700V. In practice, this theoretical figure may be increased somewhat by the effect of line surges, wave form distortion and such-like disturbances, so the rectifier peak inverse rating should not be less than 800V.

Construction

Fig. 2 shows the positions of the components and the connections to be made. The wiring should be no longer than necessary and if 20 s.w.g. tinned copper is used, it can be laid neatly in position and will stay there. The tag strip holding the smoothing resistor etc., must be soldered to the transformer frame, using a large iron, and the rectifiers tucked neatly beneath it as shown in the illustration.

Take care not to use the earthed tags for any of the connections. The outer metal bodies of the rectifiers are "live" so they must be firmly positioned clear of the transformer frame. The indicator lamp is considerably under-run and so is not likely to need replacement; it can therefore be soldered permanently into circuit without a lamp holder. The fuse holders are secured with impact adhesive.

Safety Precautions

In view of the exposed h.t. connections it is advisable, if the unit is for bench use, to fit some sort of cover over both sides of the transformer. This was done in the case of the prototype by bending two pieces of 1/16in. perspex to the required rectangular shape and securing them to the sides of the transformer frame with self-tapping screws.

The bending can be accomplished quite easily after clamping the perspex between two pieces of plywood along the line of bend and dipping the assembly in very hot water.

The cover should be about half an inch shorter than the height of the transformer so that an opening can be left at the bottom for through ventilation which the smoothing resistor at the top will promote by convection. The double pole on-off switch, S1, S2, is fitted to the cover on the

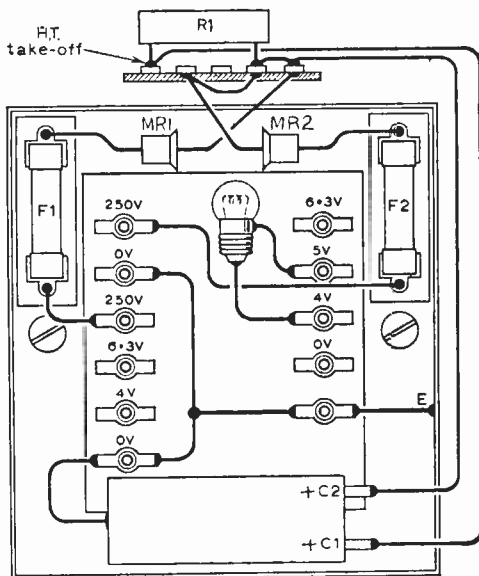


Fig. 2: Construction details of the unit.

mains input side of the transformer. If desired, an additional fuse can also be fitted here in the a.c. supply line as a protection against heater line short circuits etc.

A suitable rating, allowing for surge is 250 to 500mA.

BOOKS REVIEWED

—continued from page 530

Generators and Alternators. Although there is no question that this book offers a great number of basic facts there are one or two puzzling aspects of it.

In Figs. 1—13 and 1—14 the battery mysteriously reverses polarity and the voltages in Fig. 13 are given with respect to reference point D. The voltage then would be minus 6V and minus 5V and not just 6V or 5V as stated. In Fig. 1—17, page 24, we are told to note that 4 amps of current flow toward point A, but there is, in fact, no such reference point marked A in the Fig. 1—17 at all. In the photographs, Figs 2—4 and 2—6, the same battery is shown twice, and perhaps a different

photograph would have been more educational. It would certainly prove more interesting.

A graph appears on page 62 and the vertical axis is marked in gauss, yet the word gauss does not appear to be included in the text at all. These points may appear small, but since the book is intended for beginners it is felt they should be mentioned.

Vector diagrams start to appear on page 73 and it is regrettable that no clear explanation of them appears, particularly as their importance is very great, as anyone who has studied a.c. theory will know.

The book is priced at 16s. and it is suggested that any reader contemplating purchasing it should be in a position to examine it first rather than send money "blindly" through the post. —D.L.G.

The "Spectreuphon"

SOME IDEAS FOR EXPERIMENTS WITH CHROMASONIC DISPLAYS

BY I. J. KAMPEL

DESCRIBING a unique device, which from an existing audio source, improves mono or stereo reproduction, and provides a visual conception of the music, by means of changing colours, to match the mood of the music.

There are many examples of how sound and colour can be subtly merged to produce an unparalleled emotional effect—producing not only extreme pleasure, but a pleasing relaxation of mind. This is offered as a supplement to all hi-fi and audio fans—so much more than the 'flat' sound from a single-speaker mono system, and much more pleasing than the simpler two-speaker stereophonic system.

The *Spectreuphon* provides a visual conception of the music to be provided from an existing audio source.

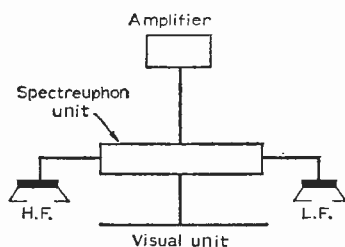


Fig. 1a (above): The basic layout of a mono system using the "Spectreuphon".

Fig. 1b (right): The arrangement for stereo.

Direct coupling to most modern radios, tape-recorders, record-players, is simply made through extension speaker sockets. It will be necessary, however, to fit a switch on the audio unit, if one does not exist, to cut out the internal speaker.

Before describing the unit in detail, a brief description of the effect would be in order.


Effect of Mono Spectreuphon

The author has previously described a unit for feeding two loudspeakers from an existing audio source (mono), giving an effect not unlike stereophonic sound to the unexperienced, average listener. No owner of a stereo set-up would mistake it for stereo, but if suitable speakers are used, he would be forced to admit there was a fair comparison. Some listeners to the system were in fact convinced that it was stereo, and found it

just as satisfactory! (The original unit—the *Euphon*—appeared in the October, 1963, P.W.) The mono version of the *Spectreuphon* contains the original *Euphon* circuit. (Section 2, Fig. 2.)

The *Spectreuphon* should be listened to—and viewed—in a darkened room.

Let us suppose that the unit is connected to a record-player, and a record has just been put on. Until the record begins there will be complete darkness—then comes the music—and light. The coloured light thereafter faithfully follows the pitch, volume, beat, and general mood of the music. As the volume increases so the light becomes more intense; it follows visually if there is a distinct beat; if there is a predominance of treble, mid-range, or bass, so there is a predominance of one particular colour, and as the ranges merge together so do the colours, mixing, diffusing together, giving subtle intermediate shades and hues. If the record ends in a fade-out, so the light dies down to darkness with the sound.

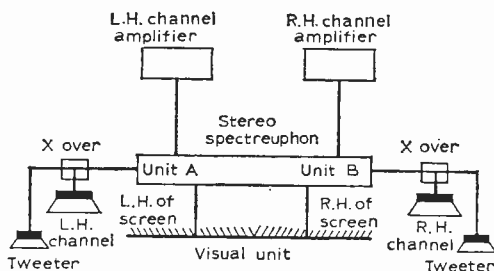

Effect of Stereophonic Spectreuphon

Two inputs are required for this unit, these being taken from the sockets to which left-hand and right-hand channel speakers are usually connected. The audio to these speakers is then fed via the *Spectreuphon* unit. This is necessary, as the unit must have a volume level on it.

The left-hand audio channel then controls the left-hand side of the display unit—consider it as a screen for now—whilst the right-hand audio channel covers the other half. This means that beside the visual effects described in the mono version, the stereo version provides left and right emphasis according to speakers, and also a colour shift if there should be an audio movement shift.

The stereo *Spectreuphon* does not improve sound reproduction in itself. If, as later diagrams

indicate, two crossover networks are employed, and a four-speaker system set up, then there will be a great improvement. Many stereo systems have, however, these networks built in, with twin woofer and tweeter.

Single Speaker Spectreuphon

If for one reason or another, only a single speaker may be employed, or a single speaker

view, it consists simply of a number of lights.

There are three groups of lights, each group controlled by a different filter network and channel of the *Spectreuphon*. One set of bulbs responds to bass, one to treble, and the third to mid-range.

Fig. 2 is the complete mono *Spectreuphon*, which includes a two-channel audio network to feed two loudspeakers, to give an effect similar to stereophonic sound. This circuit diagram is divided

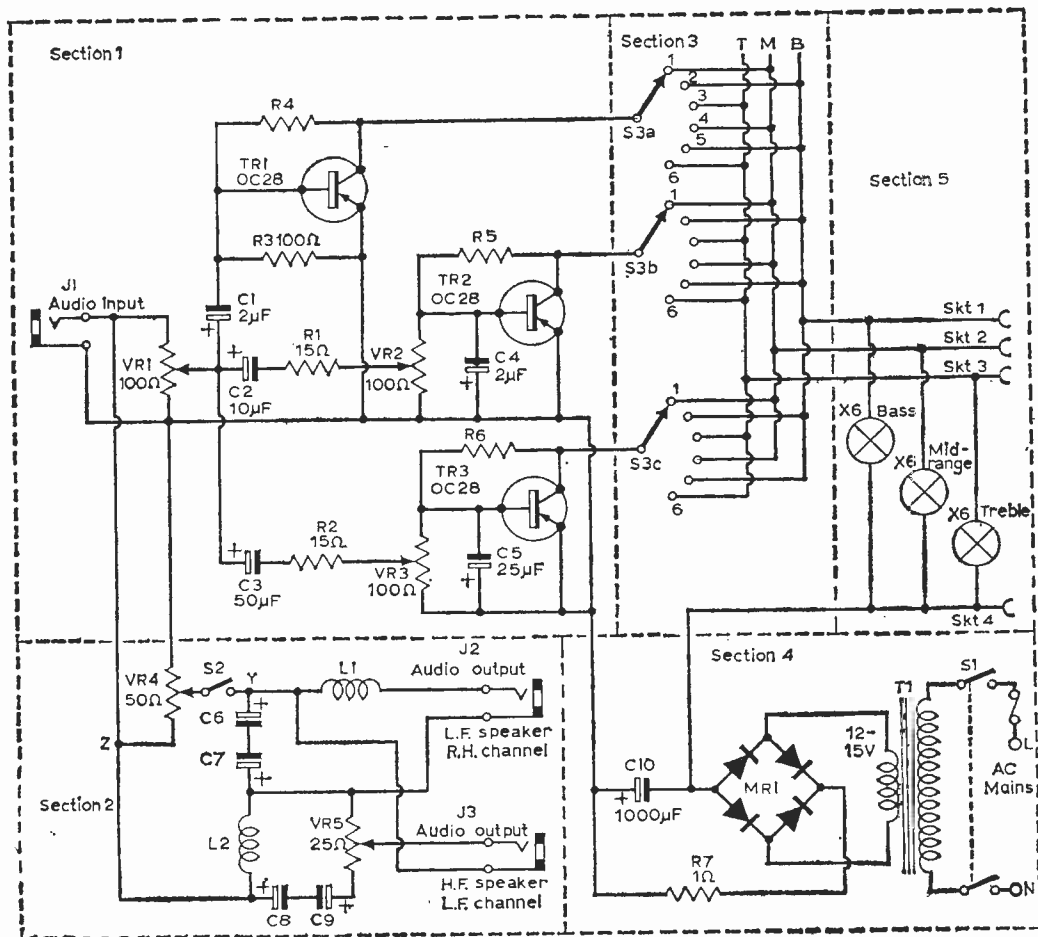


Fig. 2: The complete circuit of the mono "Spectreuphon".

unit, slight adaptations will have to be made to the circuit of the mono unit. Details of this will be given later. It is possible to use only the one existing speaker.

The Spectreuphon Circuit (Mono)

Fig. 1a is a block diagram of the basic principle and lay-out of the mono system. Actual visual units will be described later, but whatever type is used, basically, and from the electronic point of

view, it consists simply of a number of lights into five sections so that reference to this circuit is simpler.

Section 1 is the three-channel filter network which separates treble, mid-range, and base, and so controls a group of lights on each of these channels. An increase in one range, and the consequent additional transistor bias, increases the collector current, and consequently the lights brilliance, being connected directly in the collector line.

Section 2 is the two-channel audio network, which feeds J2 a low frequency output, and J3 a high frequency output, so the speaker connected to J2 produces mainly bass, and the speaker to J3 mainly treble. Coil and cap. details are to be found in **Table 1**.

Section 3 is simply a switching unit on the three outputs of Section 1. Each of these outputs feeds a different set of lights, of a different colour. Hence, the six-way, three-pole switch, allows any combination of colours and channels to be obtained, so giving a greater variety.

Section 4 is simply the smoothed power supply. There is little to say about this, as any suitable

TABLE 1

C	L	Speaker Impedance	C	L
6-9	1-2	3Ω	30—32 μF electrolytic	3Ω 0.135 mH
		15Ω	5—8 μF electrolytic	15Ω 0.675 mH
X	Y	3Ω	30 μF paper	3Ω 0.135 mH
		15Ω	6 μF paper	15Ω 0.675 mH

Suitable makes	L1—L2	as below
X & Y	Hunts W54/1—WP44 (30 μF) W49/1—B551 (6 μF)	Denco divider network coils

full-wave bridge rectifier and transformer are satisfactory.

Section 5 indicates the form the lights will take. Only one of six bulbs on each channel is indicated. It will be seen that they all have a common negative—the only contact with the negative side of the rectifier—except the smoothing capacitor.

Controls

VR1, VR2, VR3, are sensitivity controls, and require some patience to set for best performance from the visual unit.

VR4, is an audio volume control. The volume control on the existing audio unit is turned up until a suitable level is obtained in the lights unit. VR4 is then used to turn down audio to a comfortable level.

VR5, is a balance control, and with this it is possible to shift the treble-base emphasis, according to individual requirements.

Details of Construction

It will be seen from the circuit diagram (Fig. 2) that resistors R4, R5, and R6, have no value indicated on them. The reason for this is that they tend to vary according to particular transistors. To find the right value resistor, the method indicated in Fig. 3 should be employed. Here a variable resistor and a set resistor are connected, in series, collector to base. The six bulbs should be in circuit for this test, on each channel. Set this system up on each of the three transistors. For this test, the audio part of the circuit need not be operational, but it will probably be found that the level required to operate the unit will be too high for listening to, and hence the speaker on the audio unit will have to be cut out.

Firstly, in daylight, adjust each of the three 3K potentiometers until the filaments of the bulbs on each of these channels have just gone out. When this has been carried out on all channels, start the audio unit up. The lights should then light up and

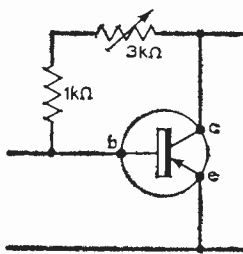


Fig. 3: Determining the values for R4, R5 and R6, see text.


fluctuate in brilliance. Adjustment of VR1, VR2 and VR3 may be necessary, but if the lights are working as described, it is pointless at this stage, to try and adjust them for optimum treble—mid-range—bass performance.

In Fig. 3 the 1k resistor is in series with the potentiometer as a safety measure, and should not be omitted. If it is, a collector-base short could occur, causing permanent damage to the transistor. When the correct level has been found, the resistance then across the collector-base of each transistor should be measured, and replaced by a resistor of the same value. If space will permit, leave the potentiometers in circuit. These potentiometers should be mounted inside the unit,

COMPONENTS LIST

Number required			
Mono	Stereo		
2	—	L1, L2	Euphon Circuit (Sect. 2 Fig. 2)
4	—	C6-C9	See Table 1
1	—	VR5	See Table 1
			25 Ω wirewound pot.
			LIGHTS FILTER
			NETWORK Etc. (Sect. 1)
3	4	J1-J3, Jx	Jack plugs and sockets
3	6	VR1-VR3 (x2)	100 Ω wirewound pots
1	—	VR4	50 Ω wirewound pot
—	1		Twin-ganged 50 ohm wirewound pot
2	4	R1, R2 (x2)	15 Ω ½ watt res.
1	2	R3 (x2)	100 Ω 1 watt res.
2	4	C1, C4 (x2)	2 μF elec. 25V
1	2	C2 (x2)	10 μF elec. 25V
1	2	C3 (x2)	50 μF elec. 25V
1	2	C5 (x2)	25 μF elec. 25V
4	7		Wander plugs and sockets
18	24		6.3V 150 mA bulbs
2	2	S1, S2	D.P. S.T. toggle switches
1	—	S3	6W. 3P. rotary switch (mono)
			6W. 6P. rotary switch (stereo)
			or as required
3	6	Tr1-Tr3 (x2)	OC20
			Test Requirements
3	6		1kΩ res.
3	6		3kΩ wirewound pots
			POWER SUPPLY
			(Sect. 4 Fig. 2)
One 3A	One 4A	T1	Transformer: primary to suit; secondary 15V
1	1	C10	1000 μF elec. cap. 25V
1	1	R7	1 Ω 1 watt res.
1	1		Full-wave rectifier 3A/4A
1	1		3A/4A Fuse

Fig. 4: Connections to an OC28 transistor.

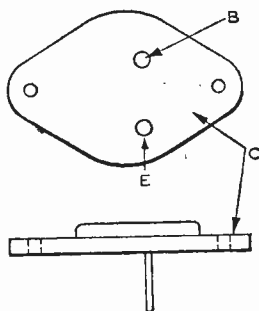

so that they are only disturbed when required. The response of the lights is far more sensitive if adjusted as described.

Fig. 5 indicates the mounting of the power transistor.

Oversize holes are drilled in the chassis to ensure that the connections do not short to chassis. The transistor rests on a lead heat-sink, and underneath this is a mica washer to insulate the collector from the chassis.

Should it be found that the lights will not dim, then a higher value potentiometer or resistor should be fitted in place of the original.

Sk1, Sk2, Sk3, are the positive contacts of the three sets of bulbs. Six bulbs, in parallel, are connected to each of these sockets, their common negative on all sets, going to Sk4.

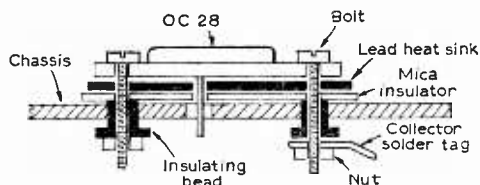


Fig. 5: Mounting details of the power transistor.

When ready for the final test of audio and visual unit, each of these sets of bulbs will be a different colour.

The Spectreuphon Without Additional Speaker Cabinet

If it is required to have the visual unit with original sound (mono), and it is found on test that the volume is not too high when turned up high enough to operate the *Spectreuphon* light-control unit, then you have no problem. Forget Section 2 and just plug in to extension speaker sockets for light control. If, however, as expected, it is too high, then the audio level has to be brought down by another control.

In Fig. 6, a two-way, two-pole switch is inserted between the speaker and output transformer. In one position there is a straight path through and in the other position, the path is through to socket, JA.

A lead is then taken from this, preferably

screened, to JB or JI on Fig. 2.

The 50Ω potentiometer is then used to turn the volume down to a suitable level, and the signal is fed back to the original unit, and speaker, via JC on the *Spectreuphon* unit, and JD on the audio source.

If this is the method that is to be employed, because of reasons of expense or space, sound could be improved by the addition of a small tweeter in the record-player or what-have-you, in which the speaker is contained.

The circuit of Fig. 7, the usual crossover network, should then be employed. The coil and capacitor values given in this table are also suitable for the *Euphon* circuit.

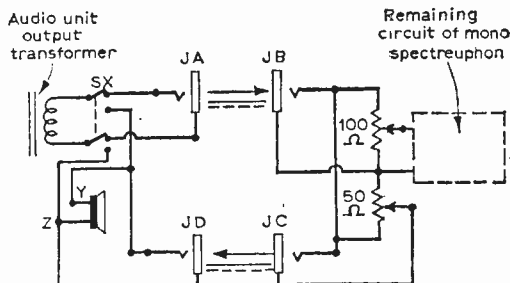


Fig. 6: Incorporating a two-way, two-pole switch between the speaker and output transformer.


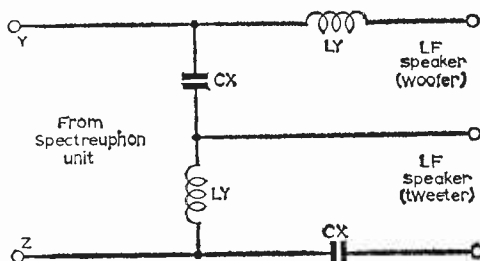


Fig. 7: A crossover network for the "Spectreuphon".

Unless the audio source is of the standard known to-day as hi-fi, the addition of this network is pointless. This also applies to some extent in the audio circuit of the *Spectreuphon*. If there is not any response below say 10kc/s, or a cut-off before it reaches the higher frequencies, little will be gained by the use of this unit.

If there is room for a single cabinet, a large woofer and small tweeter mounted together in the same cabinet, if large enough, will produce far superior audio to that previously experienced with a single—perhaps small—speaker, in a cabinet which did not allow the required resonance. The cross-over network of Fig. 7 should be used for this, connected across YZ on the original circuit (Fig. 2).

TO BE CONTINUED

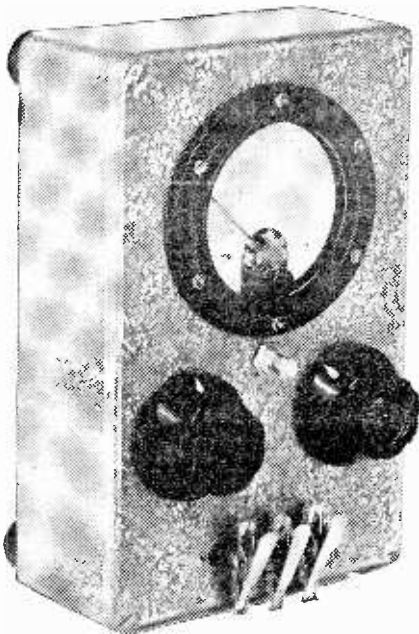

A SIMPLE transistor

for either npn or pnp transistors with a central "off" position, whilst switch S2 is used to measure either I_{co} or "Beta." When switched to I_{co} the base circuit of the transistor is left open circuit and a $4.5k\Omega$ resistor is connected in series with the meter to prevent it being damaged if a transistor having a short circuit between collector and emitter is tested. When the tester is switched to read I_{co} a check on battery voltage may be made by shorting the collector and emitter terminals, the meter should then read full scale or thereabouts, since the meter is connected as a voltmeter reading 4.5V full scale. It may, incidentally also be used as a continuity tester or ohmmeter! There are two positions of S2 for measuring "Beta," the first giving a full scale

THIS transistor tester was developed to facilitate rapid transistor testing in the workshop. The main purpose of this tester is to make what are primarily "go"—"no-go" tests, by measuring the transistor collector leakage current and current amplification factor in the common emitter configuration, i.e. I_{co} and β . Experience has shown that a tester of this type is all that is required to tell whether a transistor is working or not or to measure or compare "Beta" for matching transistors etc. Furthermore testers of this type are generally used in preference to the more accurate and comprehensive transistor parameter test sets.

The basic tester is suitable for testing only low power receiving type transistors.

COMPONENTS LIST

Resistors:

- R1 $45k\Omega$ ($33k\Omega + 12k\Omega$) $\frac{1}{4}W$ h.s.
- R2 $112k\Omega$ ($100k\Omega + 12k\Omega$) $\frac{1}{4}W$ h.s.
- R3 $4.5k\Omega$ ($3.3k\Omega + 1.2k\Omega$) $\frac{1}{4}W$
- R4 390Ω

Switches:

- S1 2-pole 3-way rotary (or 4-pole 3-way, see text).
- S2 3-pole 3-way rotary
- S3 Bell-push type: push to make

Miscellaneous:

- M1 1mA moving coil meter
- $4\frac{1}{2}V$ battery. Case. Knobs, terminals, crocodile clips, etc.


SPECIFICATION

- Collector Leakage Current (I_{co}) 0-1mA
- Current Amplification Factor (β) 0-100 } two
0-250 } ranges
- Transistor Type pnp or npn


CIRCUIT AND THEORY

The circuit of the tester is shown in Fig. 1. A $4\frac{1}{2}V$ dry battery is used as the power source, one of quite small capacity being suitable since the maximum drain is 10mA and that only for the few seconds required to take a reading.

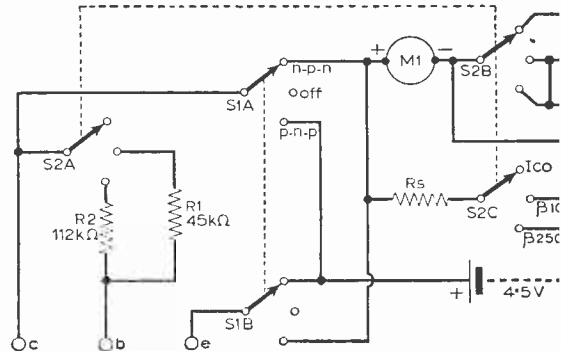Switch S1 selects the supply polarity required



tor tester

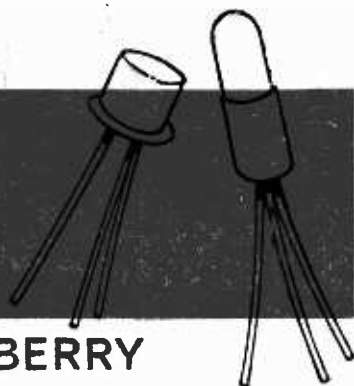

By K. BERRY

reading of 100 and the second of 250. The measurement of "Beta" is effected by injecting a known current into the base of the transistor and measuring the resultant collector current. Thus when the meter is switched to the "Beta" range giving a full scale reading of 100, a current of

$$4.5 \times 1,000\text{mA} = 0.1\text{mA}$$

is injected into the base of the transistor. Now

$$\text{"Beta"} = \frac{\Delta I_c}{\Delta I_b}$$

hence, assuming a linear characteristic,

$$\text{"Beta"} = \frac{I_c}{I_b} \text{ (approx.)}$$

If I_{co} is small compared with the collector current, I_c , this is a reasonable approximation. So if the meter reads 3mA "Beta" = $\frac{3}{0.1} = 30$.

With the meter having a full-scale deflection of 10mA the reading of 3mA so obtained will correspond to a "Beta" of 30, which is the correct result.

When S2 is switched to read "Beta" a 390Ω

resistor is connected in series with the meter to protect it from damage should a transistor having an internal short circuit be connected to the tester. This resistor may be removed by pressing a push button, S3, which then shorts the 390Ω resistor, though in practice the value of "Beta" indicated varies very little whether the resistor is in or out of circuit.

In the circuit shown, the meter reads the collector current plus the base current, but since the latter is so small it makes very little difference to the indicated value of "Beta." This slight error can be overcome by moving the meter circuit from its present position to one where it is in the collector circuit. The only drawback is that S1 then becomes a four pole switch since the meter must be reversed as well as the battery when changing from pnp to npn transistors. The modified circuit is given in Fig. 2.

CONSTRUCTION AND COMPONENTS

The prototype tester made by the author is illustrated in Fig. 3 and was made as small as



Fig. 1 (left): The basic circuit of the transistor tester.


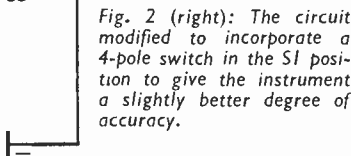


Fig. 2 (right): The circuit modified to incorporate a 4-pole switch in the S1 position to give the instrument a slightly better degree of accuracy.

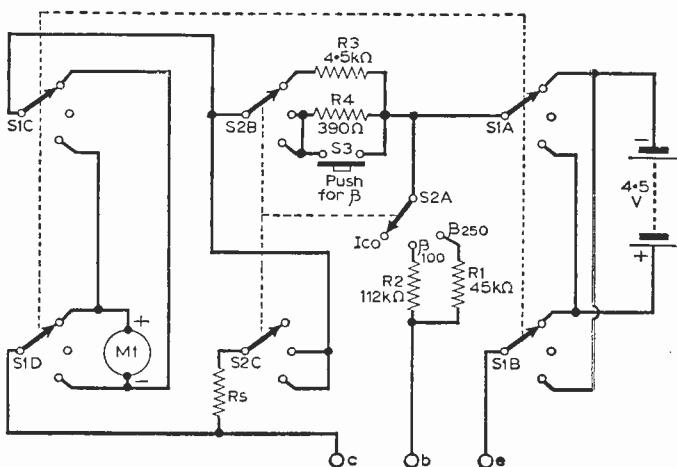

possible. It is housed in a small proprietary die-cast box measuring 7½ in. x 2½ in. x 4½ in. (Eddy-stone Cat. No. 845). Small rubber feet are fitted to the underside of the instrument to prevent it scratching polished surfaces.

The meter used originally was a 2½ in. diameter moving coil meter with a resistance of 180Ω, but any 1mA meter will suffice. It will be seen that in the components list the value of R_s , the meter shunt, is not given. This is because the value of this resistor will depend on the resistance of the meter used. Its value may be calculated from the

$$\text{expression: } R_s = \text{meter resistance} \times \frac{10}{90} \Omega.$$

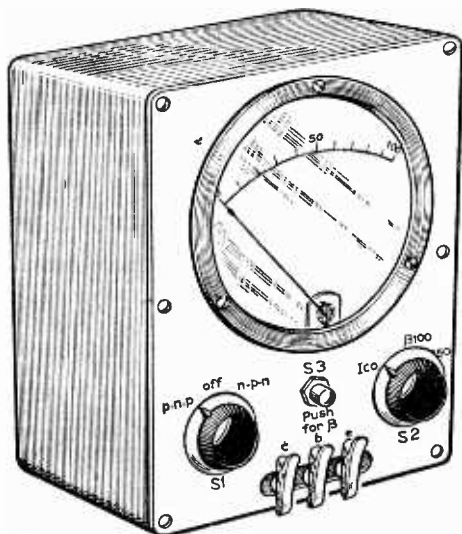


Fig. 3: A view of the finished instrument showing the front panel layout of controls, etc.

Hence in the original transistor tester, which used a meter with a resistance of 180Ω, the shunt

$$R_s \text{ has a value of } 180 \times \frac{10}{90} = 20\Omega.$$

The type of components used is unimportant, though it is suggested that the resistors controlling the base current 100kΩ + 12kΩ and 33kΩ + 12kΩ should be 1/4W high stability types. Fig. 4 shows the internal layout of components and the wiring.

TEST CONNECTORS

The connections to the transistor under test are brought out to the front panel via sockets which take "wander" plugs such as are used for the older type of h.t. battery. To facilitate connecting a transistor to the tester, the standard "wander" plugs have been modified by cutting off their heads and soldering "crocodile" clips to them as shown

in Fig. 5. The plug portion of the plug/crocodile clip assembly is then inserted in the tester socket.

USING THE TESTER

Having assembled and wired the tester it may now be given an initial test before being used. This may be done by switching to npn and Ico when once again the meter should read full scale. When this has been done a "known good" transistor should be tested as follows: First connect the transistor to the tester. Next select npn or pnp as required by S1. Then set S2 to Ico and note meter reading. Finally switch S2 to "Beta" 100 range and note reading. If reading is greater than 100 switch to "Beta" 250.

It should be appreciated that when testing a transistor on this tester there is no thermal stabilisation and in consequence measurements of "Beta" should be made quickly, otherwise the junction will rise in temperature, with the result that Ico will increase and thermal runaway might occur.

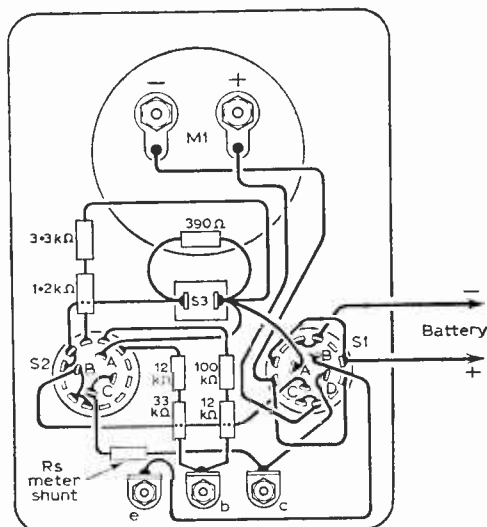


Fig. 4: The wiring inside the case. This diagram shows the wiring for the circuit of Fig. 2, i.e. with 4-pole switch.


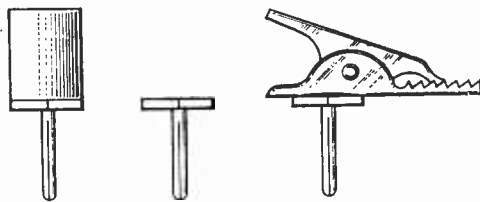


Fig. 5: The modified wander plug/crocodile clip transistor connector.

Miniature POWER Amplifier

by J. Harrison

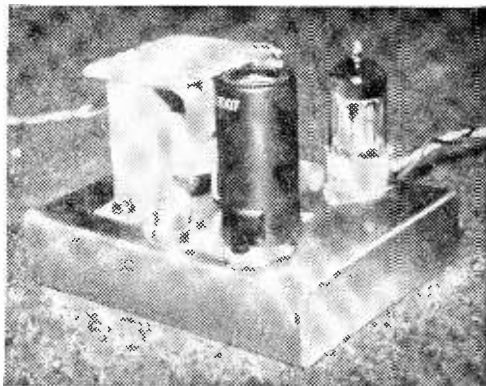

THIS small power amplifier was developed while converting a mono radiogram to stereo, but since making the unit many other uses have been found, among them as a centre channel amplifier for experiments in 3 channel stereo, as the output stage of a domestic radio and as a monitor during tests on equipment when using an oscilloscope. No doubt the constructor will find plenty of other uses for this compact cool-running amplifier.

For constructors who are tired of the usual single-ended small amplifier designs (usually employing a valve of the ECL80, ECL82, ECL86 variety), this circuit makes an interesting and rewarding project, easily assembled in a few hours.

The two valves used are almost sure to be found in the spares-box and are 12AX7 (amplifier and phase-splitter) and 12AU7 (push-pull output). These can be bought for around 6s. 0d. each.

The advantages of push-pull operation are well known and 90% of all amplifiers with a hi-fi tag to them have push-pull output. The main advantage for an inexpensive amplifier is the fact that there is no d.c. flux in the output transformer and no signal currents flow around the power supply, which contributes greatly towards amplifier stability.

In a practical amplifier, due to slight unbalance of valve currents and signals, perfect cancellation is not achieved but even so there is a great improvement compared to single-ended working. The only disadvantage is, more signal drive is required because the signal is halved between the two output valves.

The Circuit

One half of the first valve is used as a voltage amplifier directly coupled to the other half used as a phase-splitter. The

anode load of the first stage is large (470k Ω) and working into the high-impedance of the phase-splitter produces a greater than usual stage-gain.

Provision has been made in the circuit for a negative feed-back loop (if required) from the output transformer secondary to the cathode of V1A.

The amplifier should be tried out at first without any feedback, tested and if satisfactory then it should be incorporated. The amount of n.f.b. will depend upon how much gain the constructor can afford to lose, however, even without any n.f.b. sound is clean and well-damped.

Construction

Construction is quite simple and there is plenty of room on a 4 $\frac{1}{2}$ in. x 4in. x 1in. chassis. The layout shown in the diagrams is definitely the best for

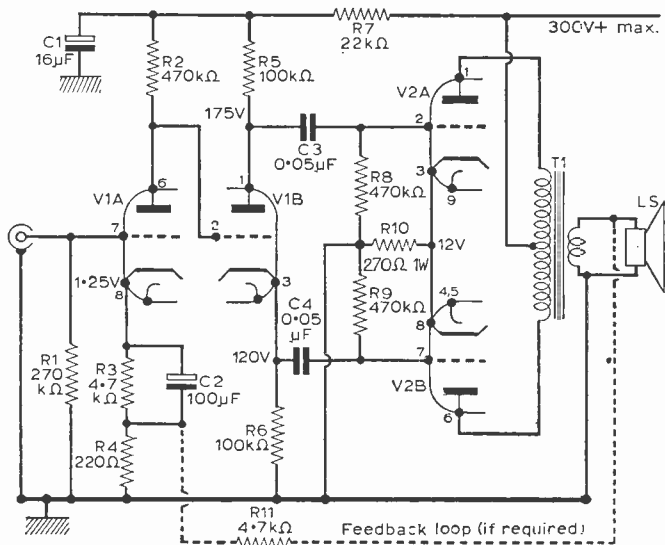


Fig. 1: The simple two-valve circuit.

short leads and constructors are recommended to follow it.

Most of the components are mounted on a small tag-board which has ten pairs of tags. These have been numbered for reference 1 to 20 in the wiring diagram. Some of the tags are linked together and wiring these first before mounting any components will make the job much easier.

There are three components not on the tag board:

- (1) Input grid resistor R1 between pin 7 on V1A and earth solder tag.
- (2) Output valves bias resistor R10 from the commoned cathodes of V2 to the centre

—continued on page 566

COMPONENTS LIST

Resistors:

R1 270k Ω	R7 22k Ω
R2 470k Ω	R8 470k Ω
R3 4.7k Ω	R9 470k Ω
R4 220 Ω	R10 270 Ω 1W
R5 100k Ω 1% h.s.	R11 4.7k Ω
R6 100k Ω 1% h.s.	

All $\pm 5\%$ $\frac{1}{2}$ W, unless otherwise stated.

Capacitors:

C1 16 μ F electrolytic 350V
C2 100 μ F electrolytic 6V
C3 0.05 μ F 350V
C4 0.05 μ F 300V

Valves:

V1 12AX7 (ECC83, CV4004)
V2 12AU7 (ECC82, CV4003)

Miscellaneous:

- T1 Output transformer, to match 10k Ω anode load (see text).
Two B9A valveholders. 10-way tag strip.
Coaxial socket.

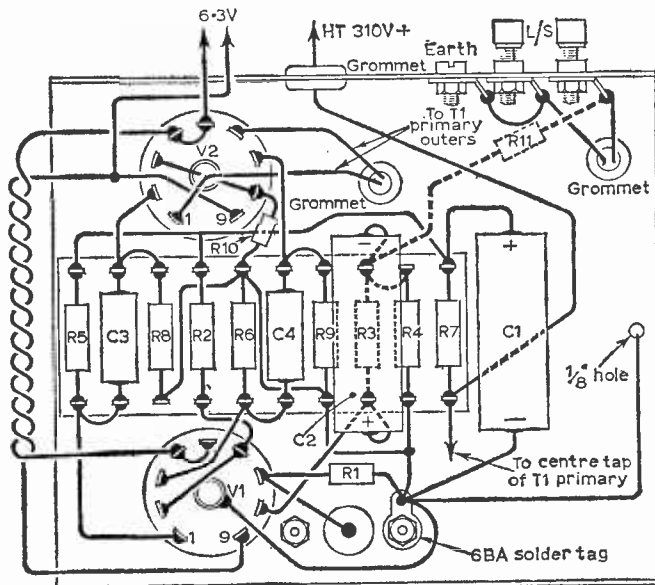


Fig. 2: The main wiring diagram; below is an underchassis view of the finished amplifier.

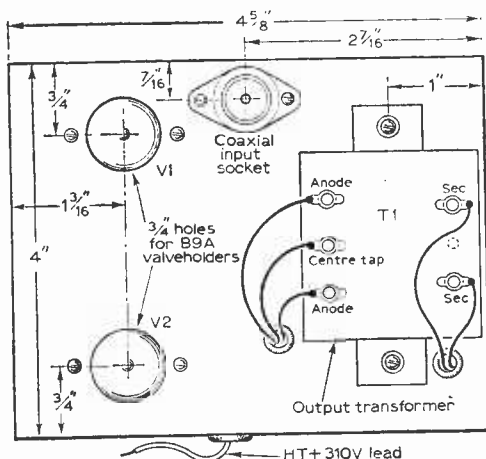
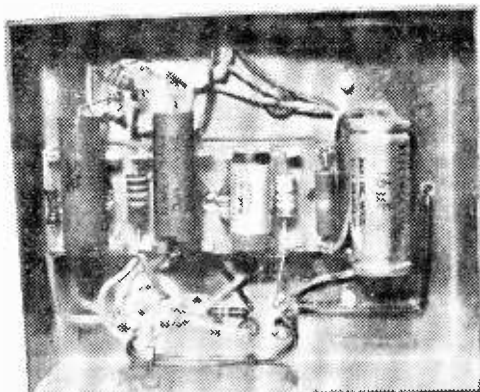


Fig. 3: Above-chassis layout and dimensions.

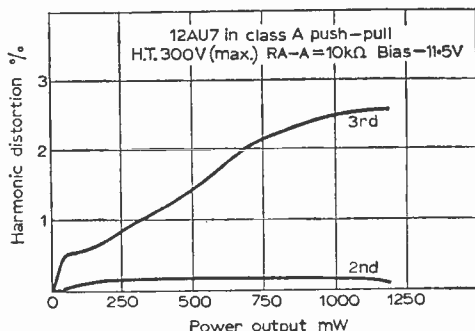


Fig. 4: Harmonic distortion plotted against output for the 12AU7 operated in Class A push-pull.

A COMMENTARY BY HENRY

PRACTICALLY
WIRELESSNo. 2
Show-Biz

SOME like circuses, others prefer bread. The organisers of the Radio Show contrive to offer us both.

Some of the other exhibitions around town look with envy on the Earls Court Dichotomy. But radio and television are a natural gift to the show-biz-minded organiser. After all free samples of synthetic butter, or a static, unreal room, or even a bevy of this year's winners of the nursemaid stakes can hardly compete with the Fair of the Air.

Behind it all there is a pretty formidable feat of dovetailed planning. And not a little skull-duggery.

It is the aim of many exhibitors to unveil a last-minute surprise. "You want a better set—we have it . . . at last", they seem to say. This leads to a frenzied rushing around on preview and opening days of the gentlemen of the Press. Dashing the free gin from their lips, they converge on the suspected harbour of secrets and attempt to lift the veils—or at least those ugly dust covers that so many exhibitions affect. (Haven't they heard of polythene?)

Hard on their heels come the rival representatives. They try to look unconcerned as they teeter on tiptoe, wondering whether that box behind the stand is going to turn out a trend-setter TV or merely contains the managing director's packaged chicken and champagne lunch.



Frenzied rushing around

Up in the Organiser's Office the headache grows yet more intense. Piles of statistics have to be sorted, analysed and sent to the corners of the world. The bloke with the late-entry surprise may find he has defeated himself by missing the Press boys' deadline. Or he may lose his impact entirely with the kind of oracle who sits in the Press Office and writes his report to the readers of Little Midmarsh from the wealth of exhibition handouts.

On the stands all is glitter and smiles. Bright new models look better than they ever will again. Silver and gold plated dissections revolve on their stands. Art-crafty scenes vie with the blatantly humorous displays, while here and there, as if in defiance, some bold maker stacks his exhibits like a row of cheeses. One expects the immaculately dressed vendor to bark: "Roll up, roll up. Every one a winner".

The annoying thing to some hardened visitors is the lack of information available on their favourite hobby-horse subjects. The deferential gent at the front of the stand is not quite sure. He will have to ask Mr. Mumblegum. This elusive character is hidden behind a phalanx of broad backs, within the drapes and hardboard, like a Rugby forward changing his tattered shorts.

In the meantime there is much else to see. The special attraction, for example, of the XYZ demonstration. We consult the guide, the official map, which even a child could understand. We are stupidly adult. We end up wandering in widening circles between towering walls of brick. When we finally reach the Dem. Room a forbidding clockface, its hands leering toward some impossible, future appointment, confronts us.

For the moment we must be satisfied with the information in the leaflets so lavishly displayed



Changing his shorts.

on every other stand save where we forage. Little boys with capacious satchels have long since skimmed the cream.

But there is still plenty to see. The designers of both the technical innards and the fashion-conscious cabinets and cases (for some modern sets can hardly be described as having cabinets) are at pains to cry their originality. Which makes it all the more surprising when we see the same styling on so many stands. Are we to believe that design has reached a saturation point of near-perfection? (Stand up that man who gave a hollow laugh!)

In our bemused wandering around this Aladdin's Cave of wonders we are likely to lose sight of the great amount of background work. The miles of specially laid cable, the carpentry, the decoration, the problem of assembling people and products under one roof at any given period.

Think of that next time you curse the unexpected hump on the floor of the main aisle, the confusing layout of stands that always seems to lead you past the same eye-catching display, the queues for lukewarm tea, the foot-wearying iron stairs, the heat, the draughts, the impassable crowd around the rostrum.

Whether your taste is for bread or circuses, remember we must have both.

AN INDUCTANCE/CAPACITANCE TESTER

by H. Webster

A simple but versatile two terminal oscillator which enables inductance and capacitance measurements to be carried out with good accuracy is described. In addition, gang capacitor sections and inductances, whether screened or unscreened, can be matched to a high degree of accuracy. Further suggestions are given for the construction of a signal generator which is a novel departure from the usual type of instrument.

A problem which is frequently encountered by the constructor is the measurement of inductance. In particular, one is often faced with the task of matching inductances to fairly close tolerances. Even when two coils are wound as physically similar as possible, the inductances of the respective coils may well vary by as much as 2%. In most cases the error will generally exceed this figure.

As a simple example consider an inductance of $100\mu\text{H}$ in parallel with a capacitance of 200pF . The resonance frequency of the combination is 1125 Kc/s . Replacement of the $100\mu\text{H}$ inductance with one of $99\mu\text{H}$ results in the new resonance frequency of 1131 Kc/s . Since the miss match between the two inductances is a mere 1%, the 6Kc/s error is somewhat astonishing. Nevertheless, a simple calculation will convince the experimenter of the truth of this statement.

Two such coils used in the radio frequency stages of a receiver would give extremely bad alignment. Since hand wound coils are less reproducible than machine wound coils, these errors are frequently much greater than in the foregoing example.

For some time past the author has employed a simple unit which can be used to match inductances to a high degree of accuracy. In addition, the inductances of coils can be measured, capacitances determined and tuning capacitor sections equalised. Slight modification of the oscillator is necessary if inductance and capacitance measurements are contemplated. The modified circuit diagram is given in Fig. 1.

Principle of operation

Inductance measurement.

A simplified block diagram of the basic circuit for the measurement of inductance is given in Fig. 2.

The mode of operation is as follows. L, the unknown inductance, is placed in parallel with a standard capacitance C. The resonance frequency of the combination LC is determined by means of a calibrated receiver. A knowledge of this frequency enables one to determine the inductance utilising the formula

$$L = \frac{25,330}{C f^2}$$

where L is expressed in microhenries, C in microfarads and f in kilocycles/second. Since several

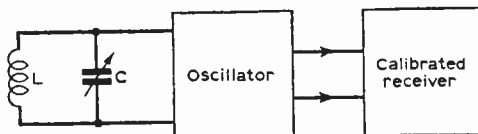


Fig. 2: The basic arrangement for making inductance measurements.

factors have been excluded, this method is only suitable for approximate measurements.

In the block diagram, the tacit assumption has been made that the capacitance C is the only capacitance in circuit. Since circuit wiring and valve electrode capacitances are present these so called stray capacitances must be taken into account.

Consider the following argument:

- Let L = inductance μH .
- C_s = stray capacitance μF .
- C_1 = maximum capacitance of C μF .
- C_2 = minimum capacitance of C μF .
- F_1 = resonance frequency of combination L, C_1 C_s kc/s.
- F_2 = resonance frequency of combination L, C_2 C_s kc/s.

When C_1 is in circuit, total capacitance = $C_1 + C_s$.


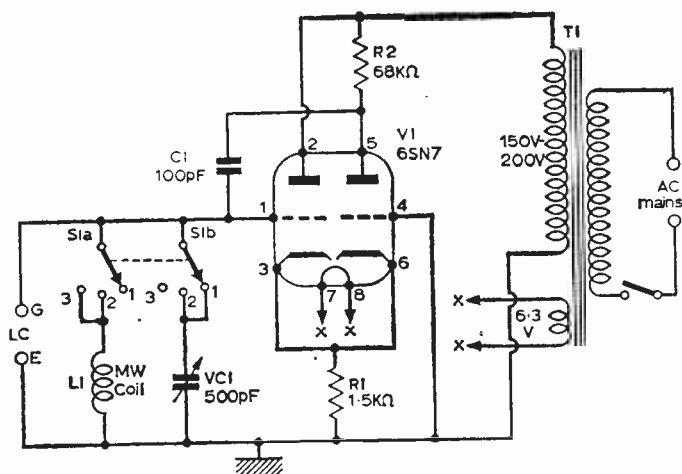


Fig. 1: The basic circuit of the instrument.

Easy-to-make cabinets to house your hi-fi

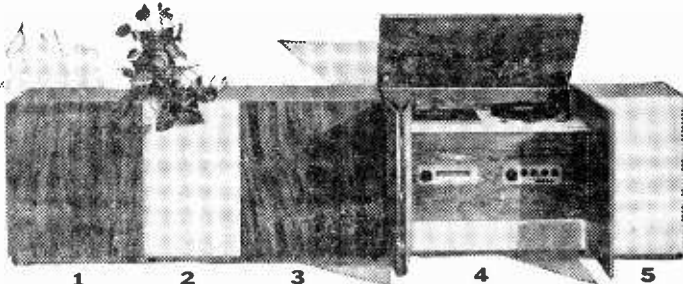- 1 Tape deck/record storage
- 2 & 5 Loudspeaker
- 3 Record storage
- 4 Radio/record player



These easy-to-make sectional units are part of an outstanding new range of designer-styled cabinets for high fidelity sound equipment. They are the direct result of a close collaboration between well-known industrial designer Frank Guille Des RCA FSIA and Percy Wilson MA, technical editor of "The Gramophone" and prominent authority on acoustical engineering. The cabinets which will house almost any combination of Hi-Fi equipment have been especially designed for making in Vipboard. Vipboard


is a fine quality board with superior screw-holding qualities; specifically made for easy and economical furniture-making within the home. It comes in 20 standard sizes, fully veneered on all surfaces and ready

to polish. No special skills are required, and you need only basic household tools. Total cost of Vipboard for the cabinets shown above is £27.0.4. The individual cabinets cost from £3.8.11 (units 2 and 5).

Vipboard fully veneered chipboard with the natural wood finish

Find out how you can choose and build the units best suited to your Hi-Fi requirements—at a fraction of their "shop price". Ask for Free Instruction Leaflets and the Vipboard Furniture Brochure at your local Vipboard stockist, or write to: Vipboard Division, G.W.E. Boards Limited, 6 John Street, London WC1, Holborn 8421

BUY AND BUILD STAGE BY STAGE

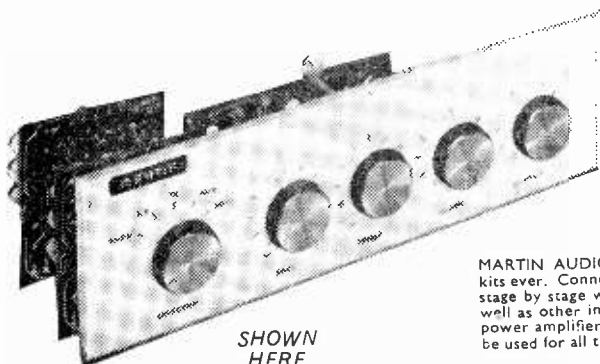

SHOWN
HERE

5-stage selector. Tone Control and Pre-amp Stage. in Stereo complete with attractive escutcheon. This, with two amplifiers and power supply comes to well under £30.



MARTIN ELECTRONICS LTD.
154/5 High St., Brentford, Middlesex. Phone 15Leworth 1161 2

FROM A MONO AMPLIFIER TO
A 20 WATT INTEGRATED HI-FI
STEREO ASSEMBLY

- ★ FULLY TRANSISTORISED PRE-FABRICATED ADD-ON UNITS.
- ★ PROFESSIONAL STANDARDS OF PERFORMANCE AND APPEARANCE.

MARTIN AUDIOKITS are the most efficient and imaginatively designed kits ever. Connections are arranged to enable you to expand your assembly stage by stage with ease. The range includes a unique 3-channel mixer as well as other important pre-amplifier stages, and you can choose 10 watt power amplifiers with either 3 or 15 ohms output. Martin equipment can be used for all true hi-fi requirements. Power pack Units are also available.

IMPORTANT NEW LEAFLET

The new MARTIN AUDIOKIT Leaflet details in full the entire range of units. No one wishing to build all-transistor hi-fi should be without this information.

MARTIN ELECTRONICS, 154 HIGH ST., BRENTFORD, MD'SEX.
Details of all MARTIN AUDIOKITS please

NAME

ADDRESS

BLOCK LETTERS P.W.10

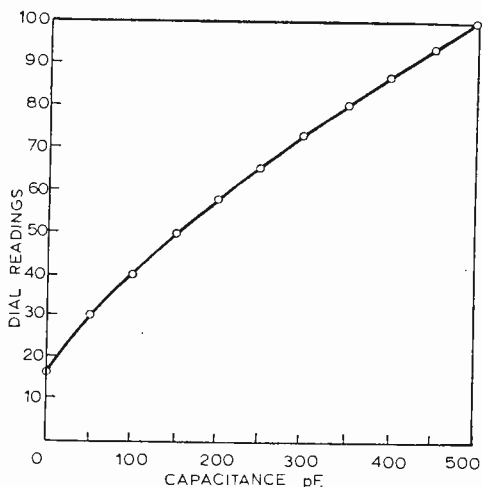


Fig. 3: Specimen graph of dial readings plotted against capacitance. The apparent zero capacitance at a dial reading of 16 occurs because of the arbitrary choice of 500pF as maximum capacity.

When C_2 is in circuit, total capacitance $= C_2 + C_s$.

$$\therefore \text{since } LC = \frac{K}{f^2} \text{ where } K = 25,330$$

$$\text{then } L(C_1 + C_s) = \frac{K}{f_1^2}$$

$$\text{and } L(C_2 + C_s) = \frac{K}{f_2^2}$$

Subtracting

$$L(C_1 + C_s) - L(C_2 + C_s) = \frac{K}{f_1^2} - \frac{K}{f_2^2}$$

$$\text{or } LC_1 + LC_s - LC_2 - LC_s = \frac{K(f_2^2 - f_1^2)}{f_1^2 f_2^2}$$

$$\text{or } L(C_1 - C_2) = \frac{K(f_2 + f_1)(f_2 - f_1)}{f_1^2 f_2^2}$$

transposing

$$L = \frac{K(f_2 + f_1)(f_2 - f_1)}{f_1^2 f_2^2 (C_1 - C_2)}$$

Hence, if the resonance frequencies, f_1 and f_2 , are found and $C_1 - C_2$ is known, then L can be calculated. Two points arising from this expression are worthy of note. First, the stray capacitance term C_s is automatically cancelled out in the derivation. Secondly, the expression contains in the denominator the factor $C_1 - C_2$. Since this is merely the difference, ΔC , between two quantities, the absolute value of C , the variable capacitor, is not required. What is required, however, is an accurate knowledge of ΔC .

Practical considerations

An accurate calibration of the variable capacitor

is absolutely essential if reliable results are to be obtained. A method for the determination of ΔC will now be given.

With the switch in position 2 the standard medium wave coil is brought into circuit. The variable capacitor is turned to maximum capacity. In the author's instrument this capacitor had a nominal value of 500pF and was fitted with a dial calibrated from 0-100.

A table, divided into two columns, is drawn up. One column represents capacitance, the other column dial readings. The capacitance column is divided in 50pF intervals, starting with 500pF, corresponding to a dial reading of 100.

The modulated r.f. signal emitted by the oscillator is picked up on the calibrated receiver which is tuned to the medium wave band and placed a suitable distance from the oscillator. A knowledge of the frequency of the emitted signal is not necessary for calibration of the capacitor.

The receiver setting is left undisturbed and a close tolerance ($\pm 1\%$) capacitor of 50pF capacitance placed across the LC terminals. The variable capacitor is retuned until the signal is again picked up on the receiver. Since the inductance is constant, the reading of the variable capacitor must have decreased by 50pF. The dial reading must therefore correspond to 450pF. With the dial setting of the variable condenser unchanged the 50pF standard is removed and the signal again picked up on the receiver. The 50pF standard is replaced across LC and the variable capacitor retuned as before. In this way a series of capacitance points, each differing by 50pF can be obtained. The variable capacitor dial readings are then plotted against the appropriate capacitance readings on a sheet of graph paper as shown in Fig. 3. Reference to the graph will then enable the constructor to determine the capacitance difference between any two points on the dial.

The factors affecting the accuracy of the foregoing calibration will be apparent: First, the calibration is based on the accuracy of the fixed standard capacitor, and secondly, it is necessary to decide whether two signals are of equal magnitude. For all practical purposes a $\pm 1\%$ silver mica capacitor is adequate for calibration purposes. The second source of error can be largely eliminated by fitting the receiver with an output meter. Alternatively, if a.v.c. is fitted, a 0-10 v. d.c. meter may be connected across the bias resistor of one of the controlled valves.

Applications of instrument Inductance measurements

The experimenter is often required to wind a coil to a given inductance value. In general the required number of turns can be obtained either by calculation, using some type of empirical formula, or by graphical methods. After winding the coil with the appropriate number of turns it is frequently found that inductance is quite different from the nominal value.

Now let us suppose that a coil of inductance 170 μ H is required for medium wave band coverage. Reference to tables or formulae will indicate that approximately 98 turns of 34 s.w.g. enamelled wire close wound on a 1 in. diameter former will give this value of inductance. Starting at the grid end of the coil, wind on 5 turns and space this section from the remaining 93 turns by approximately $\frac{1}{8}$ in. Switch the oscillator to position 1 and connect the coil across the LC terminals. Set the variable capacitor

to 400pF and tune in the resulting signal on the receiver. Note the frequency f_1 . Reset the capacitor to 300pF and again note the new frequency f_2 . The values obtained in this way are substituted in the formula and the inductance calculated. Adjustment of the inductance can be made either by spacing of the 5 turn section or by removal of turns.

As an example of an experiment by the author, a coil of nominal inductance $170\mu\text{H}$, was required. It was found that with 400pF in circuit the resonance frequency was 600kc/s. With 300pF in circuit the resonance frequency was 680kc/s. Substitution in the formula gives

$$L = \frac{25330 \times (680 + 600) \times (680 - 600)}{680^2 \times 600^2 \times .0001} = 156\mu\text{H}$$

Although the arithmetic is simple, the working out is a little heavy and the use of logarithms is recommended. In the above case the inductance was increased by bringing the 5 turn section into closer proximity with the main coil.

A serious source of error in the preceding experiment can arise in reading the frequency on the receiver dial. Unless the receiver calibration can be relied upon a better procedure is as follows. Tune the receiver to a station of known frequency at the l.f. end of the medium wave band. Adjust the oscillator variable capacitor until zero beat is obtained. With the aid of the graph note the capacitance corresponding to the dial reading. Retune the receiver to a station of known frequency near the h.f. end of the band. Adjust the variable capacitor for zero beat, again noting the capacitance reading. The inductance is calculated as in the preceding example.

When other inductance values are required a rough calculation will give the approximate frequency coverage and the receiver can be switched to the appropriate band.

Inductance matching

Although the foregoing experiments are of interest, particularly where an exact knowledge of the inductance of a coil is required, in practice, the constructor is more interested in the matching of coils rather than in the determination of absolute values. It will now be shown how exact matching of two or more coils is possible.

Let us assume that two coils L_1 and L_2 , require matching. Insert L_1 across the LC terminals and place the switch in position 1. Adjust the variable capacitor to any convenient value and note the frequency f_2 of the resulting signal on the calibrated receiver. Remove L_1 and insert L_2 and again note the frequency f_1 of the signal. If f_1 and f_2 coincide the coils are perfectly matched. However, the author

assures readers that this is extremely unlikely! In the more likely event of f_1 and f_2 being different, note whether f_2 is greater or less than f_1 . If f_2 is greater than f_1 then L_2 is less than L_1 and conversely, if f_2 is less than f_1 then L_2 is greater than L_1 . Since it is more practicable to remove turns from a coil, inductance matching is carried out on the higher of the two inductances. The following procedure is adopted.

With the lower of the two inductances determine the frequency with the calibrated receiver. Without disturbance of the generator or receiver settings, remove the inductance and insert the inductance of higher value. The coil is then adjusted, either by placing or removal of turns until the emitted signal coincides with the receiver setting. The coils are then matched.

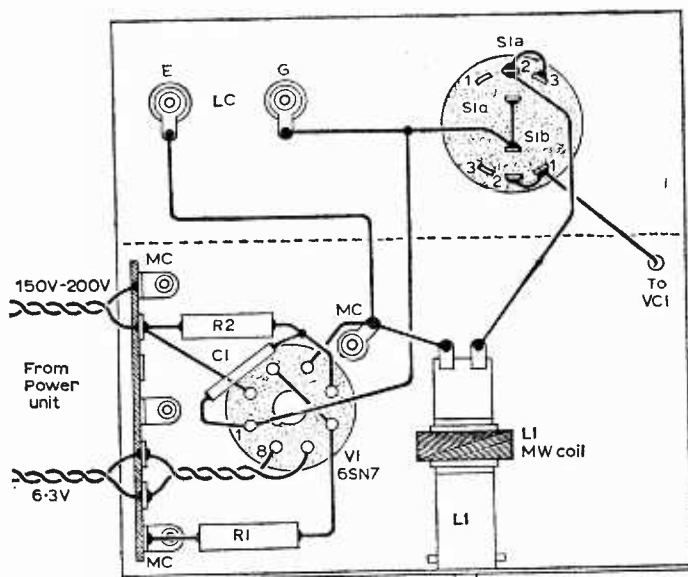


Fig. 4: The underchassis wiring diagram.

If greater accuracy is required the coils can be matched by zero beating against a station of known frequency. With practice, a high degree of accuracy can be achieved.

It is important to note that after each adjustment of the coil, the hand or any other earthed object should not be in close proximity with the coil. Since it is inevitable that the panel is near to the coil, each determination is carried out at exactly the same distance from the panel.

Gang capacitor matching

It is not generally realised that gang capacitor sections are rarely equal. In many cases the errors involved may be as great as 2%. For exact ganging of circuits not only must the inductances be matched and stray capacitances balanced out but also the gang capacitor should have equal capacitance in each section at every setting of the gang capacitor. Too often this source of error is overlooked when poor receiver alignment is obtained. Provision is generally

NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO, TV, AND ELECTRONICS

Anyone can afford these amazing courses—anyone can understand this practical training—No complicated mathematics to hold you back—No old-fashioned, obscure explanations to frustrate you! The lessons are **CRYSTAL CLEAR, PRACTICAL, EASY TO MASTER AND USE**—Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert! Compare favourably with some courses costing very much more! By creating a mass market for these savings directed to you! Each course is printed on extra large quarto size sheets and bound into one manual to simplify handling and distribution. Please select the course most suitable for your requirements from the following:

No. 1. RADIO COURSE. Fundamental facts—Electrons—Conductors and Insulators—Radio Batteries—Circuits—Magnetism—Ohm's Law—Resistor Colour Code—Chart—What resistor to use—Electro-Magnetism—Electromagnetic Induction—Self Induction—Radio Frequency Inductances—Capacity Coupling—I.F. Transformers—Radio Cols—Radio Capacitors—The Farad—Dielectric—Capacitor Colour Code—Alternating Current Theory—Frequency and Reactance and Resistance—Charts to calculate Capacity—Radio Servicing—Inductance—Handy Radio Formulae—Practical Aspects of Radio Servicing—Diode Action—Transistor Action—D.C. Stabilization—Transistor Bias Adjustment—R.F. Amplification—Superheterodyne Principles—A.V.C. Power Supplies—Meters—Multimeters and Valve Testers—Unit to Point Servicing—Signal Generators and Signal Tracers—Unit to Point Servicing—Alignment—Amplifiers and P.A. Equipment—High Fidelity—Advantages of Inverse Feedback—Speakers—Frequency Modulation—How to Obtain Radio Jobs. Price for the complete course. **ONLY 36/-**. Plus postage 1/6.

No. 2. ELECTRONICS COURSE. Includes most of the above lessons plus L.C. and R. Combined Circuits—Resonance Phenomenon—Behaviour at Resonance—How Meters Work—Making a Voltmeter—Ohm meter Connections—Valves—Electron Behaviour—Triode—Characteristic Curves—Power Supplies—Audio Amplifiers—Push Pull and Parallel—Class Inverter Circuit—Radio Frequency Voltage Amplifiers—I.F. and Multiband Cols—Detection—Receiver Circuits—Results of Frequency Mixing—A.V.C.—Electronic Oscillators—Quartz Crystals—Radio Transmitter Circuits—Modulation and Tuning—Lines, Antennas and Radiation—Test Equipment Using Meters—Electronic Test Equipment—Syntrons—Photo-Cell Equipment—Radio Compass—H.F. Heating—Electronic Shaping Circuits—Electron Microscope—Electric Strain Gauges—Inter-Communicators—Radio Servicing Techniques—Servicing Printed Circuits. Price for the complete course. **ONLY 39/6**. Plus postage 1/6. Graduates of the Electronics Course can qualify for a certificate—details sent with each order.

No. 3. TELEVISION COURSE. Effect of Mis-adjusted controls—Pictures of various faults—Service adjustments—Circuit Faults Indicated by a Poor Pattern—Flinding Bad Valves by observing Picture Faults—Separate Channel I.F. System—Inter-carrier I.F. System—Negative Picture—Interference—Antenna Principles and Practices—U.H.F. Transmission Lines—Facts About the T.V. Signal to Help you in Service Work—Synchronizing Separators—T.V. Interference Aids—All about Cathode Ray Tubes—Explanation of T.V. Circuits—Video Detector—Video Amplifier—D.C. Restorer Circuit—Automatic Gain Control—Oscillators—Deflection Cols—Automatic Frequency Control Circuits—Analysis of Stagger—Tuned I.F. Receiver—Analysis of Three Inter-carrier Type Receivers—The Vertical Deflection Circuit—The Horizontal Deflection Circuit—Waveforms—Schematics of various sections of a T.V.—U.H.F. Converters and Tuners—T.V. Test Equipment and Alignment—Analysis of Various Problems. Price for the complete course. **ONLY 36/-**. Plus postage 1/6.

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION You must be convinced that this is the best value you have ever seen in Electronic, Radio or T.V. Training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE 70-PAGE BOOK. Tick on the coupon one book for each course ordered with full cash. **RADIO SERVICING FAULT FINDING BOOK. TELEVISION FAULT BOOK. OSCILLOSCOPE BOOK.** These free books are authoritative, and loaded with information. Would cost at least 5/- each if bought separately—by sending cash you reduce book-keeping and other costs, which savings we pass back to you!

FREE TRIAL OFFER

Pay only 5/- per week if you wish. Clip coupon right now for this special offer To: **Sim-Tech Book Company, Dept. CW5, Gater's Mill, West End, Southampton, Hants.**

Please send the following courses for a full seven days' trial.

- ☐ No. 1. RADIO COURSE. 37/6, incl. postage.
☐ No. 2. ELECTRONICS COURSE. 41/-, incl. postage.
☐ No. 3. TELEVISION COURSE. 37/6, incl. postage.

(Free trial customers tick one only please.)

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price OR 5/- weekly until purchase price plus 2/6 service charge has been paid.

- ☐ Tick here if enclosing full purchase price.
☐ Please send me ☐ FREE. RADIO FAULT FINDING BOOK.
☐ FREE. T.V. FAULT FINDING BOOK. ☐ FREE. OSCILLOSCOPE BOOK.
 Amount enclosed £.....

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

NAME
 ADDRESS

City County

DE-LUXE RECORD PLAYER KIT

Incorporating a 4 Sp. Garrard Auto-Spin unit and Mullard latest 3 w. amplifier (5C12L85 and E280), vol., bass and treble controls, with 8 x 5in. 10,000 ohm speaker. Superb quality reproduction. Contemporary styled two-tone cabinet, charcoal grey and off-white with matching blue relief. Complete Kit

Size 17 1/4 in. x 16 in. x 5 in.

Cat. and Const. details 2/6. (Free with kit) **FRONT SECTION**, which houses amp. and speaker is detachable from cabinet. Price, as separate unit for stereo £57.5/6. Carr. 5/-.

£13.19.6



STANDARD RECORD PLAYER KIT USING BSR UA14 UNIT. Complete Kit

£11.16.0 plus 7/6 carr. Ready-wired amplifier and 7in. x 4in. quality speaker and O.P. Trans. £2.19.6. Carr. 2/6. BSR UA14 Unit £2.10.0. Carr. and Ins. 5/-.

Recline covered cabinet in 2-tone maroon and cream size 15 1/2 in. x 14 1/2 in. x 8 1/2 in. with all accessories plus uncut record player supporting board, 14in. record player, Carr. and Ins. 5/-.

BARGAINS GARRARD PLAYER UNITS

SINGLE PLAYERS: Carr. 4/6

Model SRP10 5 gns.

Model 4HP £12.10.0. Carr. 7/6

AUTOCHANGERS: 4 speed, Carr. 2/6.

"Autolink" Model £6.17.6.

Latest Model AT.5 with transcription arm plug-in head, mono 10 gns. Stereo 11 gns.

EXPANDED ANODIZED METAL.

Attractive gilt finish. 4in. x 4in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4ft. x 3ft. 47/6 plus carr. Ditto, smaller mesh 4/6 sq. ft. Multiples of 12in. only. Max. size 3ft. x 2ft. 27/6 plus carr.

TYGON FRET (Various patts.) from 2/- sq. ft. Any size to 6in. cut. Vynair ditto 2/- sq. ft.

RECORDING TAPE

Famous American Columbia (CBS)

Prizes a quality tape at BARGAIN

PRICES A genuine recommended

Quality Tape—TRY IT. Brand

new, boxed and fully guaranteed.

Fitted with leader and stop folk.

Standard Double Play

5in. 600ft. 13/- 1.200ft. 31/8

5 1/2in. 900ft. 16/- 1.800ft. 37/6

7in. 1.200ft. 21/- 2.400ft. 47/6

Post & Pack.

per reel. 1/- plus 6d. ea.

5 1/2in. 1.200ft. 17/6 for additional

7in. 1.800ft. 28/6 reels.

SPECIAL OFFER. 3in. Message

tape, 1500ft. 3/9; 3in. L.P. 225ft.

4/9; 3in. D.P. 300ft. 6/6. P. & P.

per reel 6d.

TAPE REELS. Mfrs. surplus

7in. 2/3; 5 1/2in. 2/-; 5in. 2/-; 4in.

2/-; 3in. 1/3. Plastic spool

containers. 3in. 1/3; 5in. 1/6; 7in.

2/-; 7in. 2/6. **TAPE ACCESSORIES STOCKED.**

ENAMELLED COPPER WIRE—1lb.

reels 14/-20s. 2/6; 22s-28s. 3/-;

30s-34s. 3/9; 36s-38s. 4/3; 39s-40s.

4/6, etc.

VALVE HOLDERS—Int. Oct. 6d.

BONDACAST Speaker Cabinet Acoustic Wadding (1in. thick approx.) 12in.

wide any length cut, 1/6 (1in. 3/-; 2/-).

TINNED COPPER WIRE, 16-22s.

2/6 1lb. **ERSIN MULTICOORE SOLDER**, 60/40, 4d. per yard. Carbons 8/6 etc.

Nylon or Ceramic, B7G, B9A unskirted 9d. B7G, B9A skirted 1/- each; B7G with Can 1/8; B9A with Can. 1/8 each.

STYLUS REPLACEMENTS. Diamond stylus for L.P. or Stereo, for all pop. types, BSR, Collaro, Garrard, etc. 11/8 ea. 12 mths. SAPPHIRE ditto. 5/8 ea. (Comp. range in stock).

TAPE DECK BARGAINS

BSR MONARDECK Type T.D.

Two-track £7.7.0

Four-track £9.10.0

Carr. 5/-

COLLARO STUDIO 3-SPEED

DECK

Two-track £10.10.0

Four-track £14.10.0

Carr. 7/6

We manufacture all types Radio Mains Trans., Chars., Quality O.P. Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain lists 2d. stamp.

Only a few items are listed from our comprehensive stock. Write now for full bargain lists. 3d.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m. - 6 p.m. 1 p.m. Wed. THO2188. Terms C.W.O. or C.O.D. Post and packing up to 4d. 9d.; 11s. 1/3; 2/3; 5s. 2d.; 8s. 5/6.

made for the adjustment of gang capacitor inequalities by the provision of split end vanes in each section. Using the oscillator, excellent matching of gang capacitor sections can be achieved in the following manner.

For the purpose of illustration the matching of a twin gang capacitor will be described. With the oscillator switch in position 3 the medium wave coil is brought into circuit and the variable capacitor switched out of circuit. Connect one section of the gang capacitor across the LC terminals of the oscillator. Turn the gang capacitor from maximum capacity to minimum capacity until the first segment of the split end vane is completely in mesh with the stator plates. Tune the receiver to the h.f. end of the medium wave band until the oscillator signal is heard. Remove the clip from the stator tag of the first section and replace on the second section tag. The end segment is then gently bent out from the vertical and away from the other rotor vanes until the radiated signal coincides with the receiver setting.

Naturally the choice of section for adjustment depends on which section has the higher capacitance value. The higher the capacitance, the lower the frequency, conversely the lower the capacitance, the

capacity (500pF) the resultant frequency is observed on the receiver. The unknown condenser is placed across the LC terminals and the variable capacitor tuned until the signal is again heard. The capacitance reading of the oscillator dial is noted. For example, if the setting of C without the unknown capacitance is 500pF and 450pF with the unknown capacitance in circuit, then the value of the unknown capacitance is $500 - 450 = 50\text{pF}$. This method is unsuitable for capacitances greater than 500 pF since the greatest measurable capacitance can never be greater than the capacitance swing of the variable capacitor.

Constructional details

The oscillator is constructed on a $5\text{in.} \times 3\text{in.} \times 2\text{in.}$ chassis, the relevant dimensions being given in Fig. 5. Wiring of the instrument is not critical and most of the components will probably be to hand. The variable capacitor is the most critical item and it is strongly recommended that a good specimen manufactured by a reputable firm is used. Since the current consumed by the oscillator is negligible a small midjet transformer will suffice for the power requirements. In the author's instrument the transformer is separate from the oscillator but there is no reason why other constructors should not make the transformer an integral part of the unit. A slightly larger chassis will of course be necessary if this is envisaged.

Fig. 5 (left): Principal chassis dimensions.

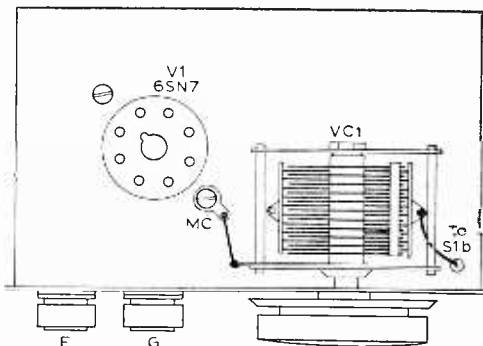
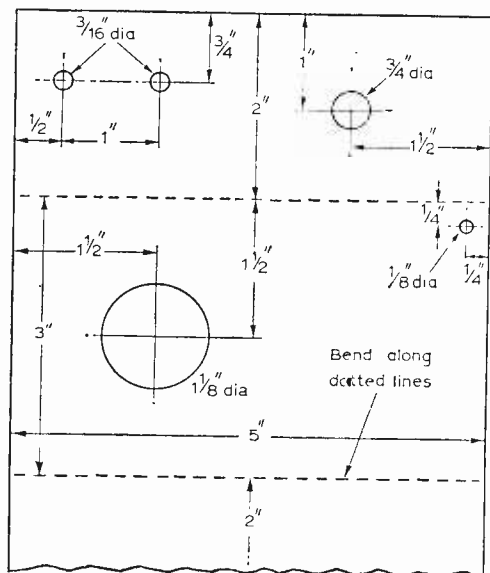


Fig. 6: An above-chassis view.

higher the frequency. The adjustment is always carried out on the section with the higher capacitance.

When equality has been obtained the process is repeated with the remaining segments until a perfect match is obtained at all settings of the gang capacitor.

Capacitance measurement

Capacitors in the range 10-500pF can be measured with reasonable accuracy by means of the oscillator. The accuracy of measurement is limited only by the errors involved in the calibration of the oscillator variable capacitor. The principle of the method is similar to that employed in the calibration method.

With the variable capacitor set to maximum

The connections of the unknown inductance or capacitance to the LC terminals are of considerable importance. These connections should be constructed from thick copper wire so that the leads are self supporting. The two leads terminate in crocodile clips which can be firmly attached to the component under test. When testing gang capacitor sections it is important that the frame of the capacitor is connected to the terminal marked E. Similarly, if screened coils are being tested the screen and earthy end of the coil should be firmly earthed to the same terminal.

The oscillator switch performs three functions. Position 1 is used for inductance testing and matching, position 2 for capacitance testing and matching, gang capacitor matching.

When testing or matching inductances it is essential to ensure that the two coils are tested in the same

position relative to the instrument panel. To avoid undesirable screening effects it is recommended that the test leads are not less than 3 in. in length.

The author has found that the instrument is greatly superior to the grid dip oscillator for the measurement of inductance and capacitance. If desired, the basic circuit could be embodied in a complete signal generator with the additional facilities of inductance and capacitance testing being incorporated. A suggested circuit for the experimenter who desires to elaborate on the test unit is given in Fig. 9.

Appendix

For the sake of completeness and as a convenient reference for constructors the following data is included.

Several expressions are available for the calculation of the number of turns required for a given inductance. The author has used two well known formulae which have proved satisfactory in practice. The first formula is applicable to single layer coils.

$$N = LR \left[1 + \sqrt{\frac{9}{aLR^2}} \right]$$

Where N is the required number of turns
 L is the inductance in microhenries
 a is the radius in inches

and $R = \frac{20}{nd^2}$ where

n is the number of turns per inch
 d is the diameter in inches

The second formula is applicable to pile wound coils.
 See Fig. 8.

$$L = \frac{0.2 \times a^2 \times N^2}{3a + 9b + 10c}$$

where a is the mean diameter
 b is the winding length
 c is the depth of winding
 N is the number of turns
 all dimensions being expressed in inches

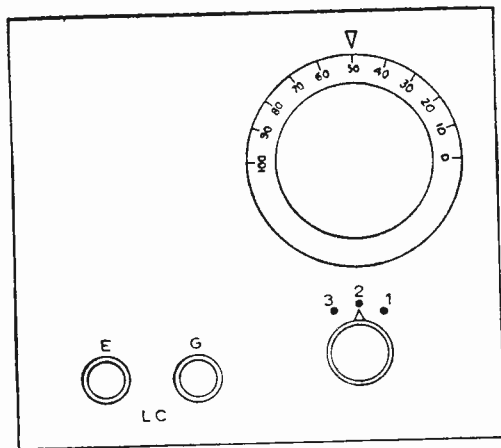


Fig. 7: Front panel layout of controls.

Applications to coil winding

The frequency coverage of a given coil and variable capacitor is given by the expression

$$\frac{f_2}{f_1} = \sqrt{\frac{C_1}{C_2}} \text{ where } C_1 \text{ is the maximum capacity of}$$

the variable capacitor and C_2 the minimum capacity. In practice, stray capacitances have to be taken into account. These extraneous capacitances have a bearing on the frequency coverage of the given combination of C and L . Now let us suppose that it is desired to cover the medium wave band with a given coil and a variable capacitor of 500pF nominal capacity. Average values for the maximum and minimum capacitances of such a capacitor are 500 and 15pF respectively. To these values must be added stray capacitances, which in general may be as high as 15pF. The capacitance coverage is now 515—30pF. The total minimum capacitance is now brought up to some predetermined value by the use of a trimmer capacitor. Let this excess capacitance be 20pF. The capacitance coverage is now 535—50pF. We can now calculate the frequency coverage using the previous expression. If we assume the lowest frequency we wish to cover is say 560kc/s then

$$\text{Since } \frac{f_2}{f_1} = \sqrt{\frac{535}{50}} = 3.27$$

then $f_2 = 560 \times 3.27 = 1753 \text{kc/s}$.

The inductance of the required coil may be calculated utilising the expression

$$L = \frac{25,330}{Cf^2}$$

Substitution of the previous values of C and F gives

$$L = \frac{25,330}{0.000535 \times 560^2} = 165 \mu\text{H}$$

The required coil may now be wound to this inductance value using the first inductance formula. Let the diameter of the former be 1 in. and assume that the given enamelled wire occupies a winding length of 100 turns per inch. e.g. 34 s.w.g.

$$\text{Since } R = \frac{20}{nd^2} \text{ then } R = \frac{20}{100 \times 1^2} = 0.2$$

$$\therefore N = 165 \times 0.2 \left[1 + \sqrt{1 + \frac{9}{0.5 \times 165 \times 0.4}} \right] = 97$$

Hence the coil can be wound with 97 turns of 34 s.w.g. wire, close spaced and occupying a length of approximately 1 in.

An example of inductance calculation utilising the second formula will now be given. Assume that a coil of 2000μH inductance is required to be wound on a 1 inch former and using 34 s.w.g. wire. Any arbitrary value of b may be chosen. Let this value be $\frac{1}{4}$ inch. The number of turns of wire occupying this length is approximately 12. It is now necessary to try several trial solutions. Assume that 100 turns are required. The number of layers is therefore

$$\frac{100}{12} = 8 \text{ ca.}$$

Why NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk III


5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 m.c. Push-pull output for room filling volume from rich toned heavy duty 3in. speaker. Air spaced ranged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather look case with tilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP4 battery available anywhere).

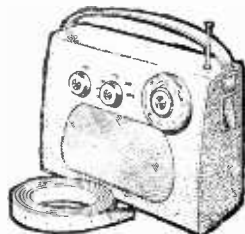Total cost of parts now only **£5.19.6** P. & P. 5/6
Parts Price List and easy build plans 3/-




Tested at volume and found it really came up to expectations. S. G. Staddon-Peas

TRANSONA FIVE

Volume, Tone, A.F.C., Lux. all at one Volume Control. G. P. Darham.


● 7 stages—5 transistors and 2 diodes

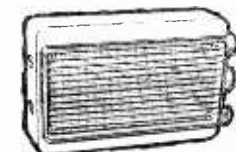Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. 12BR battery available anywhere. Parts Price List and easy build plans 2/-



with red-speaker grille. (Uses 12BR battery available anywhere.)
Total cost of all parts now only **42/6** P. & P. 3/6

MELODY SIX

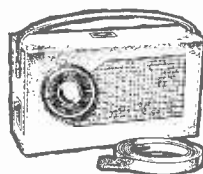

● 8 stages—6 transistors and 2 diodes


Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive ferrite rod aerial. Push-pull output. Wonderful reception of B.P.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket grille and supplied with hand and shoulder straps. Parts Price List and Total cost of all parts now only **£3.9.6** P. & P. 3/-

easy build plans 2/-

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

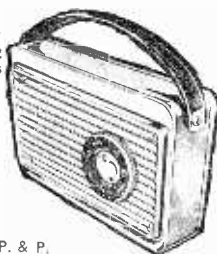This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear, attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere)



Total cost of all parts now only **59/6** P. & P. 3/6
Parts Price List and easy build plans 2/-

POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round super sensitive Ferrite Rod Aerial and fine tone 2in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3/4 in. (Uses 12BR battery available anywhere). Parts Price List and easy build plans 1/6



Total cost of all parts now only **42/6** P. & P. 3/-

SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 RF Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7 x 5 1/2 x 1 1/2 in. (Uses 9V battery, available anywhere).



Total cost of all parts now only **£3.19.6** P. & P. 3/6
Parts Price List and easy build plans 2/-


All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at fixed prices stated.

ROAMER SIX NEW!!

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND!!

● 8 stages—6 transistors and 2 diodes

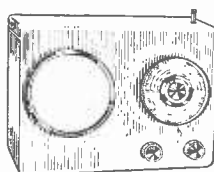

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long waves. Trawler Band and two short waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with tilt trim. Size 7 1/2 x 5 1/2 x 1 1/2 in.

● Extra band for easier tuning of LUX. etc. Parts Price List and Total cost of all parts now only **£3.19.6** P. & P. 2/-

RADIO EXCHANGE CO.

61, HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance
Barratts Shoe Shop
Open 9—5 p.m.
Sats. 10—12.30 p.m.

LINEAR

For

**HIGH SENSITIVITY
MAXIMUM RELIABILITY**

**HIGHEST FIDELITY
REASONABLE COST**

We regret to announce that after maintaining our prices for seven years (with the exception of one unit) we are reluctantly announcing a revised price list.

L.50. 50 watt Amplifier approximately 14x10x8in. Sensitivity 25 m.v. output for 3 and 15 ohm Speakers. Retail price **22 guineas**.

CONCHORD. 30 watt Hi-Fi Amplifier with two separately controlled inputs. Retail price **17 guineas**.

L.10. 10 watt Hi-Fi Amplifier with separate pre-amp. Retail Price **16 guineas**.

L.1/10. 10 watt Hi-Fi Amplifier with integral pre-amp. Retail price **13½ guineas**.

DIATONIC. 10/14 watt Hi-Fi Amplifier with integral pre-amp. Retail price **12½ guineas**.

L.5/5. Stereophonic Amplifier. Output 5 watts each channel. Retail price **12½ guineas**.

Trade and Export Enquiries invited—

LINEAR PRODUCTS LTD. ELECTRON WORKS Tel. Leeds 63-0126 (3 lines)
ARMLEY, LEEDS. S.A.E. for catalogue.

LT.45X. Tape Amplifier with equalisation adjustment for 1½, 3½ and 7½ in. per second. Suitable for Collaro Studio Tape Transcriptor. Complete with integral power pack. Retail price **12½ guineas**.

LP.1 Tape Pre-Amplifier. As above but less power pack facilities.

L.45A. 4/5 watt Amplifier. Retail price **6 guineas**.

LG.34. 3/4 watt Amplifier. Shelf mounting type for gram use. Retail price **£5.10.0**

TREMOLO UNIT. For Guitar purposes to plug into mains Amplifier. Retail price **4 guineas**.

HOME RADIO CATALOGUE

New Edition! New Policy!

With the arrival of the 10th Edition of the famous Home Radio Catalogue we announce a fresh policy. The new price of 5/- will just cover the cost of the paper and printing, but on the first page of the catalogue you will find 5 coupons, each worth 1/- if used as directed. Briefly the system will operate thus: for each complete £1 of your order you enclose one of the coupons and deduct 1/- from the money you send. **There is no time limit** so if you purchase £5 worth of components from us—even though spread over several years—your catalogue will have cost you nothing!

We need only add that our new Catalogue is bigger and better than ever . . . so fill in the Coupon, enclose 6/- [5/- plus 1/- postage], and pop it in a letter box right away!

PLEASE WRITE YOUR NAME & ADDRESS IN BLOCK CAPITALS

NAME _____

ADDRESS _____

HOME RADIO LTD., DEPT. P.W., 187 LONDON RD.,
MITCHAM, SURREY

The depth therefore is $\frac{8}{100}$ in. = C.

Substituting these values in the formula gives

$$L = \frac{0.2 \times 1.08^2 \times 100^2}{3.24 + 1.11 + 0.8} = 454 \mu\text{H}$$

thus giving one trial solution. The process is repeated for other values of N. A rough plot of N against


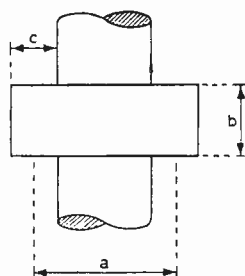


Fig. 8: Critical coil dimensions in inductance calculations.

Fig. 9: Input circuit for combined signal generator and inductance/capacitance tester. S1: pos. 1 inductance match and test; 2 capacitance test and 560-1600 kc/s; 3 gang capacitor match; 4 180-600 kc/s; 5 1.6-5 Mc/s; 6 5-15 Mc/s; 7 10-30 Mc/s.

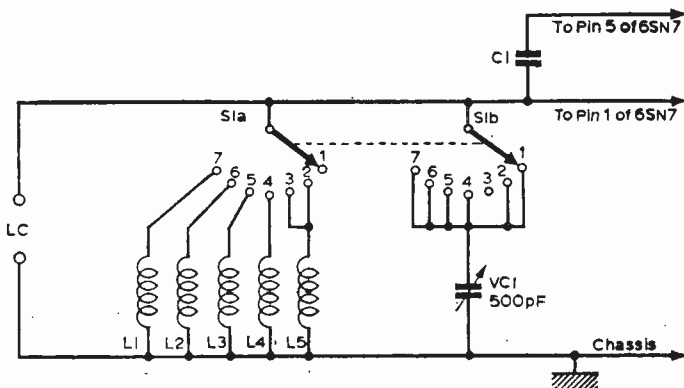

inductance is made, when the required number of turns for the given inductance may be read off from the curve.

Another and possibly less tedious method of computation may be carried out with this formula

$$\text{Since } L = \frac{0.2 a^2 N^2}{3a + 9b + 10c}$$

Transposition gives

$$N^2 = \frac{L(3a + 9b + 10c)}{0.2a^2}$$

The preceding 2000 μH inductance may now be calculated as follows.

Two arbitrary values are assigned to b and c. For the purpose of calculation let $b = \frac{1}{8}$ inch and $c = \frac{1}{8}$ inch, then since $L = 2000$ and $a = 1\frac{1}{8}$

$$\text{Then } N^2 = \frac{2000(3 \times 1\frac{1}{8} + 1\frac{1}{8} + 1\frac{1}{8})}{0.2 \times 1\frac{1}{8} \times 1\frac{1}{8}} = 49,400$$

$$\therefore N = 222$$

The required gauge of wire is now calculated. Let

COMPONENTS LIST

R1	1.5k Ω 1W	R2	68k Ω 1W
C1	100pF silver mica		
VC1	500pF variable		
L1	Medium wave coil		
S1a, b	2-pole 3-way switch		
V1	6SN7		
T1	Mains transformer: miniature type		
	Octal valveholder, terminals, aluminium chassis, panel, etc.		

COMPONENTS LIST

S1a, b	Altered to two-bank switch: single-pole 7-way each bank
L1	0.45 μH
L2	2 μH
L3	19 μH
L4	1,500 μH
L5	165 μH

n be the number of turns per inch. Then the number of turns in length $b = bn$, and the number of turns in depth $c = cn$

\therefore Total number of turns = $bn \times cn = bc$ and this value is equal to N

\therefore Since $N = 222$ then $bcn^2 = 222$ and since $b = c = \frac{1}{8}$ in.

$$\text{then } n = \sqrt{\frac{222}{\frac{1}{8} \times \frac{1}{8}}} = 120$$

From wire tables it is found that the nearest gauge which has a winding length of 120 turns per inch is 38 s.w.g. enamelled wire.

The required data is therefore 222 turns of 38 s.w.g. enamelled wire, pile wound to a length of $\frac{1}{8}$ in. and a depth of $\frac{1}{8}$ in.

The required number of turns for the inductances given in the suggested circuit of Fig. 9 can be calculated by means of these formulae. These calculations are left as an exercise for the experimenter.

TRADE NEWS • TRADE NEWS • TRADE NEWS • TRADE NEWS • TRADE NEWS

Wide Range Sine-Square Generator and a New Valve Voltmeter

THE Paco G.34 is a combined sine-square wave generator covering a frequency range of from 7c/s to 750kc/s for sine and 7c/s to 300kc/s for square waves. Distortion is claimed to be less than 0.3% from 20c/s and frequency response is flat within $\frac{1}{2}$ db from 120c/s to 120kc/s and 1db to 750kc/s. Sine wave output is 0-10V across 600 Ω . Square wave output 20V p.p. no load, with a rise time of less than 0.15 μ s.

The output level is controlled by an attenuator, with three 20db steps, also a control for fine adjustment. The Paco G.34 is priced at £40 7s. complete, or may be purchased in kit form at £38 5s.

Also from Paco comes a new valve voltmeter, the V.70. This instrument has 7 d.c. ranges from 0-1500V, 7 a.c. ranges from 0-1500V r.m.s. and 0-4000V peak-to-peak, an ohmmeter range of 0-1000M Ω and a decibel range of -6db to +66db.

The V.70 comes complete with a detachable 3-way probe, but the AV.1 high frequency crystal probe and the AV.2 high voltage probe are also available for use with the valve voltmeter permitting direct readings of voltages up to 60kV.

The Paco V.70 is priced at £22 12s. and may be purchased in kit form for £20 8s. *K.L.B. Electric Limited, 335 Whitehorse Road, Croydon, Surrey.*



This is the Paco G.34 sine-square wave generator.

Sony Agreement

THE Radio and Electrical Division of St Aldate Warehouse Ltd. (a Debenham Import & Distribution Company) have signed an agreement with the Sony Corporation of Japan, for exclusive distribution rights in the U.K. of Sony Products. The products included in the agency agreement are radios, tape recorders, and all future Sony products to be introduced into the United Kingdom markets.



The Sabafon TK230-S tape recorder.

New Equipment from SABA

NEW from SABA Electronics Ltd., is a range of audio equipment. Featured among this is a stereo/mono four track, two speed tape recorder, the Sabafon TK 230-S. This machine incorporates two amplifiers with matched transistor input stages, a built-in mixer unit with inputs for two sound stages, two push-pull output stages providing 5W per channel for stereo and 10W for mono, and a built-in tape cleaner. There are input sockets provided for gram, radio, pedal switch, slide synchroniser, time switch, stereo microphone, external loudspeakers and high impedance headphones. Weight is approximately 30lbs, and the price is 95 guineas. *SABA Electronics Ltd., Eden Grove, Holloway, London, N.7.*

Lighting Control Switch

A NEW lighting control switch has been introduced by Regentone, which enables room lighting to be adjusted easily to any level.

Called the "Varilite", the new control replaces the conventional wall switch and uses a new kind of rectifier which enables it to control up to 300W of lighting without generating wasteful heat and without taking up too much space.

The "Varilite" uses no power itself, therefore reducing electricity bills—since payment is only made for the light selected—and prolonging the life of the bulb.

The "Varilite" costs 6 $\frac{1}{2}$ guineas, fits any standard wall switch box and can be installed in a few minutes with the aid of a screwdriver. *Regentone Radio and Television Ltd., Footscray, Kent.*

New Portable from Ever-Ready

NEW from Ever-Ready is the "Sky Queen". It is one of a new range of Ever Ready transistor radio receivers. The Sky Queen is a 7 transistor superhet covering medium and long wavebands, and having an output power of 500mW. There is provision for car aerial and ear-

CRYSTALS & COMPONENTS LTD

TEL: TEM 1189 Dept. P.W.18 2, 4 EARLHAM STREET W.C.2.

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations
HOURS OF BUSINESS: 9 to 6. Saturdays 9 to 1. OPEN ALL DAY THURSDAY

CRYSTALS!!!

CRYSTALS!!!

CRYSTALS!!!

WE ARE NOW UNDER NEW MANAGEMENT AND WISH TO ASSURE READERS THAT THEIR ORDERS AND ENQUIRIES WILL BE DEALT WITH PROMPTLY AND RELIABLY

Below are just a few of the many useful crystal frequencies in stock. We have a large and varied range of 10X, 10X1, FT241 and FT243 types and will be pleased to send you our current list on request (S.A.E. preferred).

5840	5842	5850	5865	5870	5875	5880	6000	6010	6015	6020
6021	6040	6050	6070	6076	7730	7840	7850	7788	8001.43	8007.69
8021	8036	8090	8091	8092	8103	8104	8110	8790	—	—

most of our stock frequencies including the above are offered at 5/- each. A special discount of 20% (4/- in the £) on all orders for crystals in these ranges amounting to 25/- and over. Allow 6d. per xtal, P. & P.

Also in stock at 10/- each: 2 Mc/s, 3 Mc/s, 4 Mc/s, 5 Mc/s. 15/- each, 1 Mc/s, 100 kc/s, 500 kc/s.

Sockets for all above types 1/3 each, universal (1/4 in. or 3/8 in.) 2/-.

Miniature twin crystals in glass envelope wire ended, 5/- each.

10xac1 19887.5 and 19937.5 kc/s

10xac2 19987.5 and 20037.5 kc/s

10xac3 20087.5 and 20137.5 kc/s

10xac4 20187.5 and 20237.5 kc/s

10xac5 20287.5 and 20337.5 kc/s

10xac6 20387.5 and 20437.5 kc/s

10cac10 (single) 31.5 kc/s.

HIGH SPEED IMPULSE COUNTERS

By DAVIS, WYNN and ANDREWS

4in. dial and pointer registers up to 100 and 4-digit counter, both manually re-settable. The drive to the counter is by an inverse escapement so that there is no loading of the pointer mechanism when digits are changed, and adjustable pawls are unnecessary.

Coil resistance 100 ohms for nominal 50 volt operation, but the device works reliably from 20 volts at rates up to 10 impulses/sec. In circuit with a thyratron or neontron counting rates up to 100 impulses/sec are possible provided pulse width is restricted to keep mean current to 100 mA.

Highly suitable as readout element for Geiger counters and similar devices where the pointer movement would give a clear impression of change in rate of count.

Brand new in individually sealed boxes

£4.7.6



WIRELESS TRANS-RECEIVER

TYPE 19

with power pack for 12V. Input covers 2-3Mc/s and 240 Mc/s. V.H.F.I.F. used 465 kc/s. C.W. or speech. Untested, in good condition, fully valved.

£4.17.6 plus £1 p. & p.
Combined Mike-headset 17/6, p. & p. 2/6.
Aerial variometer 17/6, plus 2/6 p. & p.
6-pin Power Connector 5/- each. P. & P. 1/-.

Control box 10/- plus 2/- p. & p. 12-way connector lead 12/6 plus 2/- p. & p.



SELENIUM F.W. BRIDGE RECTIFIERS

BRAND NEW WITH MAKER'S GUARANTEE

Plate size 7 1/2 x 7 1/2 x 7 1/2 in.

12 V.D.C.	12 amps	£ s d	curr
12	..	18	1 12 6	3/6
12	..	18	1 19 6	3/6
12	..	36	3 19 6	7/6
12	..	54	5 17 6	7/6
24	..	18	3 19 6	7/6
24	..	36	5 19 6	7/6
24	..	54	11 15 0	7/6
36	..	18	5 17 6	7/6
36	..	36	11 15 0	7/6

Plate size 4 1/2 x 4 1/2 in.

12 V.D.C.	8 amps	£ s d	curr
12	..	8	1 19 6	2/6
24	..	8	1 19 6	3/6
36	..	8	2 19 6	3/6

D.C. out	1 amp	£ s d	curr
..	..	2 1/2	8/6	plus 1/6
..	..	4	12/6	plus 1/6
..	..	8	19/6	plus 2/-

New and guaranteed transformers suitable for use in conjunction with the above, tapped at following voltages: 3.4.5.6.8.9.10.12 15.18.20.24.30.

2 amps D.C.	£ s d	curr
4	1 19 6	.. 4/-
5	2 5 0	.. 4/6
10	4 15 0	.. 8/-

FOSTER VARIABLE Voltage TRANSFORMER

Input 120-250V. output 0-250 at 3 amps or 250 at 2 amps. Brand new in cylindrical pot size 6 1/2 in. high plus 1 1/2 in. control knob, diam. 6 1/2 in., weight 11 lb.

Few Only **£7.5.0** p. & p. 4/-.

DUBILIER "PULSPAK" CAPACITORS

Latest type, 1,000 mF.d. 250 V.D.C. size 4 1/2 in. 2 1/2 in. diam.

12/6 p. & p. 1/-.

FIELD STRENGTH METERS

100-150 Mc/s incorporates 0-1 mA meter I.S.S., telescopic aerial battery operation 90 and 1.5 V. in black crackle case, 7 x 7 x 7 1/2 in.

35/- p. & p. 2/9.

SILICON RECTIFIERS

800 P.I.V. 550 mA out. **7/6** each. 1000 P.I.V. **9/-** each. P. & p. 1/- each.

0-50 MICRO AMMETERS


Fan shaped, surface mounting, linear scale calibrated 0-500 Rontgens/hour. Will fit in panel space 2 1/2 x 2 1/2 in. Two fixing holes 1 1/2 in. centres.

25/- plus p. & p. 2/-.



FOR CALLERS ONLY

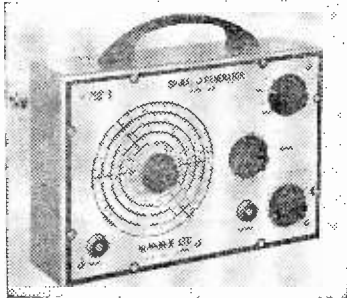We have a large and varied quantity of odd types of valves, many brand new all at 1/- each, callers only. Come in and sort 'em out! Many other interesting items for personal callers.



Wide-range Transistorised
SIGNAL GENERATOR—Model 27
Range 150 Kc/s to 350 Mc/s

- ★ Accuracy better than 2%
- ★ Directly calibrated
- ★ Battery operated
- ★ Compact and light

£9.12.3

with test lead and battery.

Post and Packing 3/6 extra.

H.P. 48/- deposit and 27/- monthly.

Trade and Export Enquiries Invited


NOMBREX INSTRUMENTATION

Wide range Transistorised
AUDIO GENERATOR—Model 63
Range 10—100,000 c/s

- ★ Laboratory Standard Specification
- ★ Sine and Square Wave
- ★ Direct Frequency Calibration
- ★ Accuracy and Low Distortion
- ★ Calibrated Output Voltage
- ★ Battery Operated and Compact

£16.15.0 complete with test lead

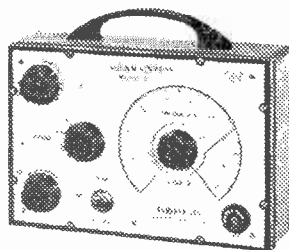Battery 2/3. Post and Packing 3/6.
H.P. 4 gns. deposit and 41/- monthly.



Wide-range Transistorised
C.R. BRIDGE—Model 62
6 Ranges: 1 Ω to 100M
1pF to 100μF

- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated

£8.7.3

including battery.

Post and Packing 3/6 extra.

H.P. 40/- deposit and 24/- monthly.

S.A.E. for full technical leaflets

NOMBREX LTD. Instruments

ESTUARY HOUSE, CAMPERDOWN TERRACE
EXMOUTH, DEVON. Phone: 3515

CONSTRUCTORS BARGAINS

THE 'REALISTIC' 7

Transistorised Portable Receiver made to the highest professional standard. Comprises 7 Mullard Trans. plus Crystal Diode, 350 milliwatt output to 4in. speaker—1 F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3in. fitted socket for car aerial. Complete with full instructions.

MAY BE BUILT FOR £5.19.6. All parts sold separately
P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)
Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial.
ONLY £1 EXTRA All parts sold separately
Battery 3/9 extra. P. & P. 4/6.



"THE SPRITE"

6 transistor mini pocket receiver. Full L. and M. waveband coverage. Size only 4 1/2 x 2 1/2 x 1 1/2 in. In sub assemblies. 3in. speaker.
CAN BE BUILT FOR 79/6 Leather case, ear- 12/6 extra
BUILT FOR phone and battery. All parts sold separately. P. & P. 3/6.

SUPER AMERICAN TAPE

LAFAYETTE BRAND, FULLY GUARANTEED

MYLAR BASE		ACETATE BASE	
5in. Double play, 1,200ft.	15/-	5in. Long play, 900ft.	10/-
5in. Long play, 1,200ft.	15/-	5in. Long play, 1,200ft.	12/6
5in. Double play, 1,800ft.	22/6	7in. Long play, 1,800ft.	15/-
7in. Stand. play, 1,200ft.	12/6		
7in. Long play, 1,800ft.	19/6	MESSAGE TAPES	
7in. Double play, 2,400ft.	25/-	3in.—150ft.	3/6
3in. Triple play, 450ft.	12/6	3in.—225ft.	4/11
4in. Triple play, 900ft.	22/6	3in.—300ft.	7/6
5in. Triple play, 1,800ft.	42/6	P.V.C. BASE	
5in. Triple play, 2,400ft.	55/-	5in. Standard play, 600ft.	8/6
7in. Triple play, 3,600ft.	75/-	5in. Stand. play, 840ft.	11/6

P. & P. 1/- extra per reel. 4 reels and over Post Free.

WIRECOMP ELECTRONICS
378 HARROW ROAD, LONDON W9

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day
Saturday. Opposite Paddington General Hospital.
Buses 18B and 38 pass the door.

NEW SUPER MINIATURE POCKET RADIOS

THE SINCLAIR MICRO-6. Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1 1/2 in. A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data.

Can be built for only **59/6**

Mercury cell 1/11 extra (2 required).

THE SINCLAIR SLIMLINE. The new 2-transistor pocket radio size only 2 1/2 in. x 1 1/2 in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. Can be built for **49/6**



IT'S FABULOUS!! THE TRANSISTOGRAM

A portable battery operated fully transistorised Record Player—for the music of your choice—any time any place! Made by famous British manufacturer, fully guaranteed. Size only 6 1/2 x 12 x 10 1/2 in. weight 10 lbs. Operates on 6 U2 torch batteries. 4 speeds—16", 33", 45 and 78 r.p.m. Goldring Sygnet record player unit with light weight pick-up fitted with CM-60 turn over ceramic cartridge. Output 500 mw to 5 in. ceramic magnet loudspeaker fitted into lid for maximum sound distribution. Cabinet constructed of wood, covered in two tone (pale blue/grey) leather cloth. Fitted carrying handle and strong lid catches. High quality amplifier with tone and vol. controls gives excellent reproduction at all speeds. Plays 7, 10 and 12 in. records. Today's value 12 Gns. **WIRECOMP'S £6.19.6**
Carr. 18s. 7/6.
New, boxed and guaranteed—exc. batts.




Transistor TELEPHONE AMPLIFIER


A must for business or pleasure. This neat little transistorised amplifier powerfully amplifies the incoming call and at last leaves you with both hands free while continuing your conversation normally. The pick-up is suction fixed to 'phone. Battery-operated at negligible cost. Fitted off switch for private conversation. Size 4 1/2 x 3 x 1 1/2 in. Complete with battery. **WIRECOMP'S PRICE 69/6** P. & P. 2/6.

piece or tape recorder connection.

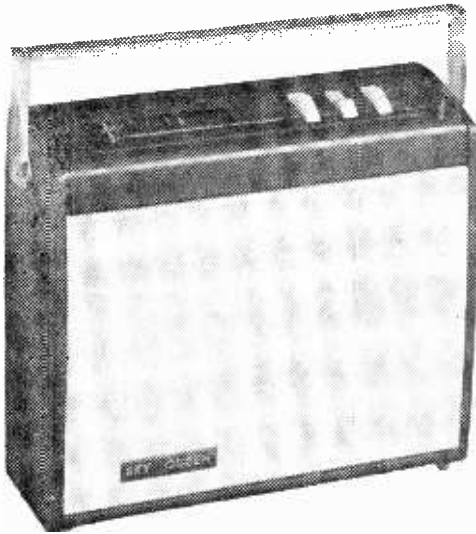The set is powered by an Ever Ready PP9 battery giving some 190-200 hours playing time, and the price, including purchase tax, is fixed at 15 guineas. *Ever Ready Co., (Great Britain) Ltd., Hercules Place, Holloway, London, N.7.*



Ever Ready's new "Sky Queen" portable.

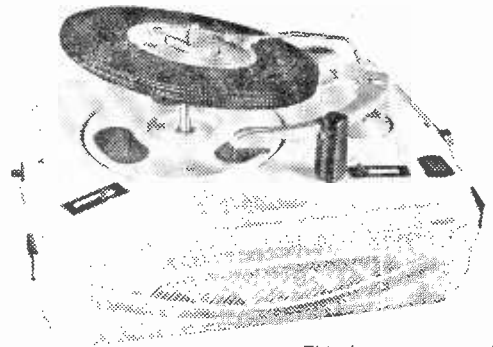

This battery-operated record player is made by W. H. Sanders (Electronics) Ltd.

Battery Autochange Player


BULK production has begun of a transistorised battery-powered record player, for 7in. 45 r.p.m. records, designed and manufactured by W. H. Sanders (Electronics) Ltd.

This automatic portable record player has been designed as a "take-anywhere" gramophone, its construction being exceptionally robust and featuring built-in transit protection for the pick-up and needle. Retail selling price is expected to be less than £15. *W. H. Sanders (Electronics) Ltd., Gunnels Wood Road, Stevenage, Hertfordshire.*

FREE INSIDE **PRACTICAL** **NEXT MONTH'S WIRELESS**


BLUEPRINT **P.W. AUTOCRAT** *to build LOW COST* **CAR RADIO**

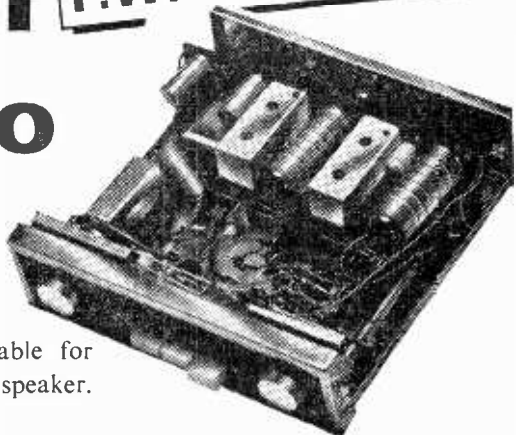3 Transistors 2 Valves. Push-pull transistor output, 1.5 watts. Medium and long waves. All parts easily obtainable including ready drilled chassis if required. Compact 7in. x 2in. x 7in. deep, suitable for fascia's of most British vehicles. Elliptical speaker.



ORDER FROM YOUR NEWSAGENT TODAY!

THE "MULTIPHONIC"

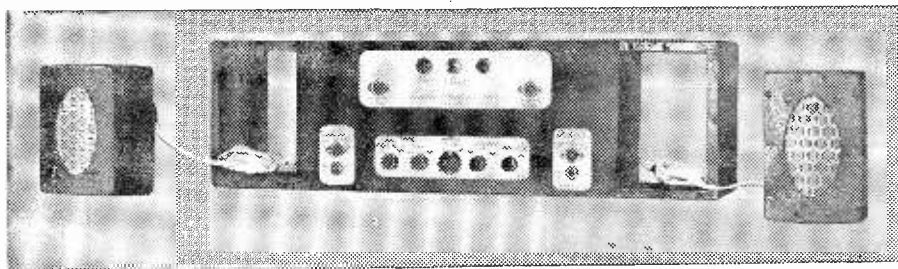

A 13-STAGE STEREO AMPLIFIER

BY MARTIN L. MICHAELIS

CONTINUED FROM PAGE 421 OF THE SEPTEMBER ISSUE

PROVIDED that the points outlined last month regarding h.t. voltage for the output stages are observed, almost any reasonable arrangement with available components may be used as h.t. supply if the exact specified items are not to hand.

If a transformer with a centre-tapped full-wave h.t. winding 250-0-250V (do not use a higher voltage one) is used operate one rectifier MR1, MR2 off each 250V end. The value of R20 will almost certainly need to be raised somewhat under such circumstances. If valves type ECC88 are available in place of PCC88 all heaters may be run in parallel off a single 6.3V winding, so that only one such winding (rating about 3A) is then needed. However, such valves are rarer than PCC88s. If a single heater winding used in this way has no tap earth one side and operate D1 and D2 off the other end.

The resulting increased bias voltage may be applied to V4 without further modification but C11 on each amplifier must now be shunted with a 5V Zener diode (cathode to chassis). If a 4V tap is present earth the "0" end and operate D1, D2 off the 4V tap. Naturally, when using ECC88s R41-R44 are not required.

Circuit Details of Input/Output Matrix

V4 and V5, on the one hand, and V3 on the other hand constitute two separate units, either or both of which may be omitted if not required. V3, with its function of splitting a monaural input into two channels, is the more important. It is hardly sensible to omit it if one is likely to operate with monaural signals in addition to pure stereo.

The output matrix section V4, V5 may be

omitted if one never contemplates using outputs other than the two main speakers, and when the latter are substantial enough to give good bass reproduction themselves, not requiring the use of a common middle position bass amplifier and speaker operated off P4 when feeding a large audience in a large room with large baseline stereo signals.

The circuit arrangement of V3 is known as "anode-splitter". Both grids of the double triode are fed in parallel from the monaural input via separate grid-stoppers to prevent parasitic oscillation. The anode circuits are separate, giving two identical but electrically separate outputs.

The unbypassed cathode resistors both reduce gain (largely unwanted in this stage) and neutralise any would-be cross-talk between stereo signal channels due to this stage. R22/VR1/VR2 form an output voltage divider, coupling into the respective main amplifier channels; C14 is the normal h.t. voltage blocking capacitor.

This very high impedance voltage divider serves the purposes of further removal of unwanted gain of V3, thus not unnecessarily raising the hum and noise level, and it also prevents loading of the stereo input through the anode circuits of V3. R21 serves no electrical purpose, being merely a convenient anchorage point in the layout specified.

This sort of measure is a useful trick to remember: if a string of required components in series requires anchorage at a junction a very high value resistor or very low value capacitor can be used as a dummy tie-point to chassis or some other convenient anchorage. One must merely be certain that the electrical side effects are in all cases truly negligible.

ELECTRONICS

**LEARN - THE
PRACTICAL
WAY . . .**

your career . . .

hobby . . .

own business . . . ?

The demand for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities, then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises **ONLY** in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.


A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS' CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION
- RADIO AMATEURS' LICENCE EXAMINATION
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

OTHER COURSES

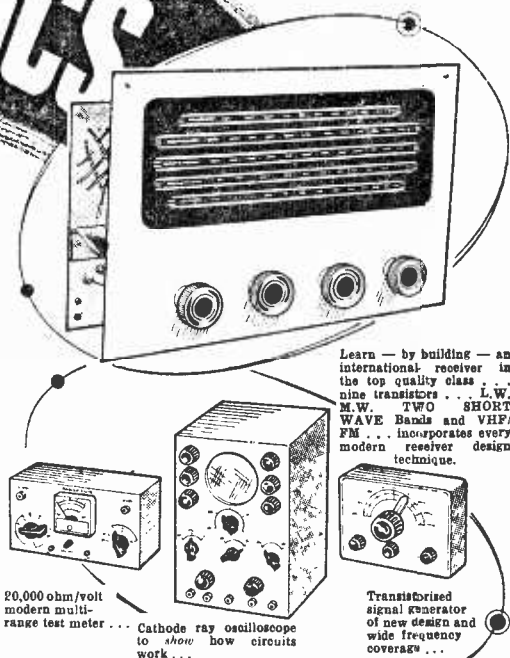- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS



Complete picture way library of theory books and practical manuals
NO MATHEMATICS!

BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVE BANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 9v. battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

FREE



POST NOW TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.

Please send me your free Brochure, giving details of your Courses, without any obligation, to:—

NAME _____

ADDRESS _____

I am interested in _____

(We do not employ representatives)

} Block Caps
Please

course above
PW 10/64

British National Radio School

Fringevision Ltd

ELCOT LANE
MARLBOROUGH · WILTS
 TELEPHONE: 657 and 658



**WIDE BAND
 UHF AERIALS**
 for BBC2 now
 and ITV 2

FIVE STAR QUALITY AERIALS

★ Anodised elements for protection. ★ Modern plastic moulding techniques used for convected reflector and parasitic elements giving longer life. ★ Staggered spaced elements for maximum performance with all channel band width. ★ Multi-element reflector giving high back to front ratio. ★ Maximum efficiency of matching by using laboratory developed collector plate—without any other matching device.

Model	Description	Gain DB	B/F Ratio DB	Retail Price
UF/H3	3-ELEMENT, HEAD ONLY with CLAMP	7.0	18.0	31/6
UF/H5	5-ELEMENT, HEAD ONLY with CLAMP	8.25	19.5	36/6
UF/H7	7-ELEMENT, HEAD ONLY with CLAMP	10.5	24.5	41/-
UF/H10	10-ELEMENT, HEAD ONLY with CLAMP	12.5	26.0	47/-
UF/H12	12-ELEMENT, HEAD ONLY with CLAMP	13.5	28.0	51/-
UF/H14	14-ELEMENT, HEAD ONLY with CLAMP	15.0	29.0	55/-
UF/H18	18-ELEMENT, HEAD ONLY with CLAMP	16.25	30.0	70/-
UF/H22	22-ELEMENT, HEAD ONLY with CLAMP	17.0	31.0	85/-

PLEASE STATE LARGE OR SMALL CLAMP REQUIRED



The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. ERSIN Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

THE HANDY DISPENSER



Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 14 feet 5 core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser.
2/6 each

SAVBIT ALLOY
saves wear on soldering iron bits

SAVBIT SIZE 1 CARTON

Contains approximately 37 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex.
3/6 each



MULTICORE SOLDERS LTD.

MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)

CHMS 24

R.C.S. PERSONAL SET

Designed for personal listening without disturbing others. Supplied complete with battery and earpiece—no extras to buy! Sensitive one transistor diode circuit gives quality reproduction over medium wave band. Attractive case with large tuning dial. Ideal for use as tape tuner. Size only **22/6 P. & P.**
 3 1/2 x 2 1/2 x 1 in. ONLY **2/-**




BATTERY ELIMINATORS

The ideal economical and safe way of running any TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. requiring voltages shown.

Types Available: 9 volt. 6 volt. 4 1/2 volt (single output). Size 3 1/2 x 3 x 2 in. PRICE 35/- each. P. & P. 2/9.
 9 v. + 9 v., 6 v. + 6 v., 4 1/2 v. + 4 1/2 v. (Two separate outputs). Size 3 x 3 x 2 in. PRICE 42/6 each. P. & P. 2/9.
 All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

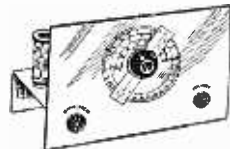LISTEN TO THE WORLD ON TELSTAR our I-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs **35/-** P. & P. 2/-.

R.C.S. CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components including case. **8/6** P. & P. (Suitable headphones 9/6). Easily converted to 1-transistor or 2-stage transistor receiver



All parts available separately

R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)
 Export Trade Enquiries Invited

V4 operates simultaneously as a pair of independent cathode-followers for the stereo output at P3 and as an additive anode amplifier developing a combined monaural signal across R34 from the stereo input to the two grids.

The monaural anode signal is passed on to V5 as output cathode-follower. R35 and R37 as voltage divider set an operating point of sufficient standing anode current for V5 as the d.c. voltage across R37 is repeated by d.c. cathode-follower action across R38. Such a method of positive grid bias on an h.t. bleeder is not usable for V4 because it would pass d.c. into the track of VR3, making operation of that control scratchy.

The use of extra blocking capacitors would produce unnecessary bass loss and phase shift, detrimental to stereo reproduction with a central common bass speaker. Thus cathode bias is used here as an alternative.

Speakers

The cabinet design used in the prototype for the complete unit aims at giving a complete self-contained installation for "personal" stereo listening in a small room. Two small oval speakers of about 3 x 5 in. are specified and housed in niches at each end of the amplifier cabinet, giving a baseline of about 2ft. This gives a reasonable stereo impression when the unit is standing on the table in front of the listener about a yard from his head.

A more intense effect is obtained when the speaker units are removed from the niches and placed as far apart as the listener recedes from them. The room area in which stereo effect obtains is thereby also greatly increased, enabling larger audiences to be served.

However, with the small speakers specified the tone is likely to be very shrill and thin when they are moved apart, with a rather empty "middle". This defect may be combated either by using in addition, placed centrally, a third amplifier and large bass speaker, operated off P4, or simply by using an identical pair of much larger speakers in good cabinets.


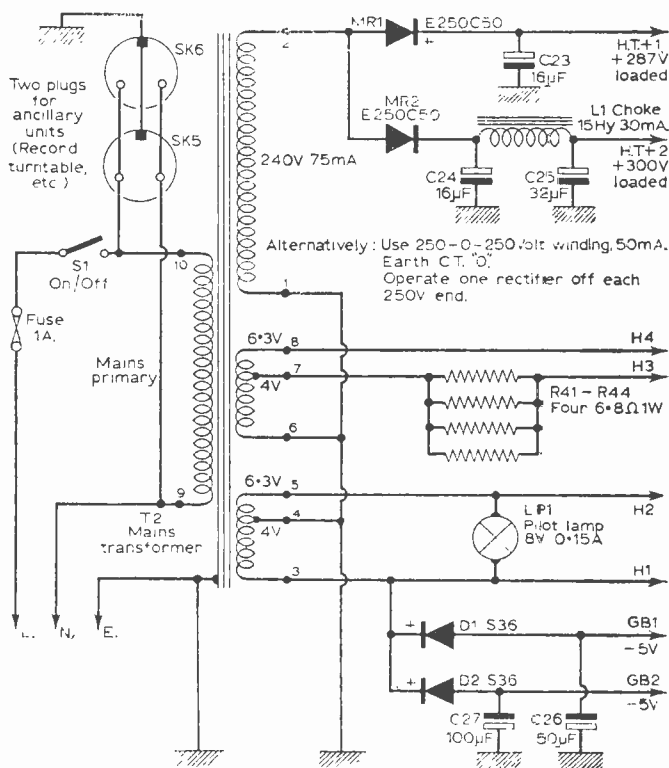


Fig. 4: The amplifier power supply

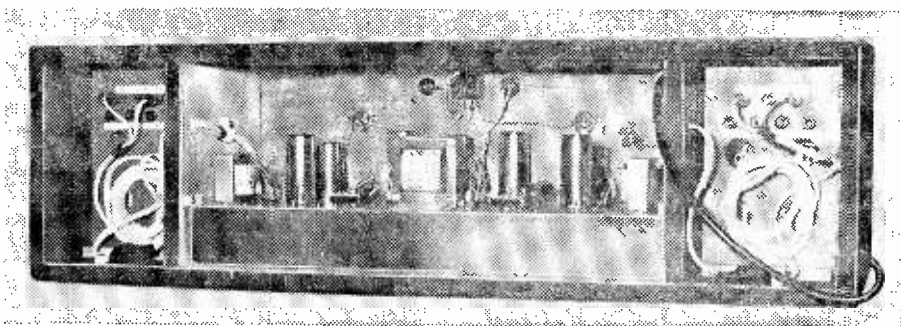

The "Multiphonic" viewed from the rear.

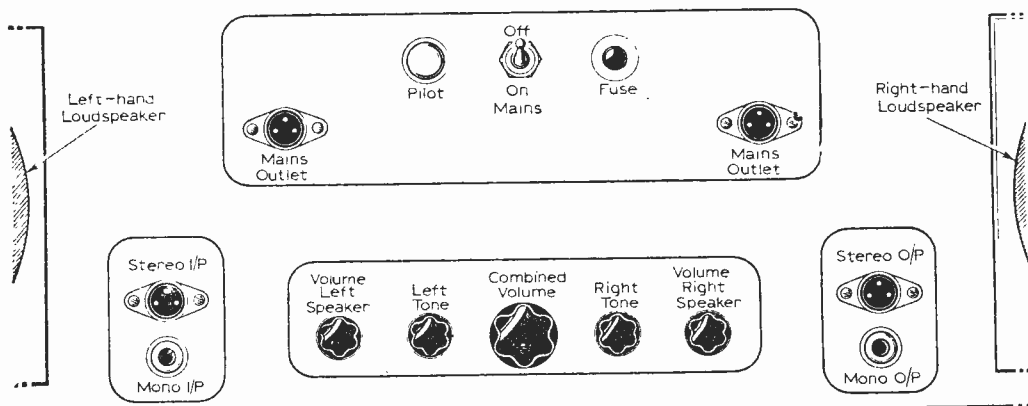


Fig. 5: Control layout on the front panel of the completed "Multiphonic".

Performance is very good indeed if a pair of 10in. speakers with 15Ω speech coils are mounted in bass reflex corner cabinets, stood in adjacent corners of the room and operated directly off the two amplifier channels.

A general rule for stereo listening is that the lines from the ideally positioned listener to the respective speakers should be approximately at right-angles. Frequencies below about 200c/s do not contribute greatly to the stereo effect as the human ear is not able to distinguish direction of origin very clearly at low frequencies.

Thus a common central speaker, obtaining bass from both channels, may be used. It is even

possible to use passive cross-over networks for three speakers from the two amplifier outputs for this type of arrangement.

However, the use of two-channel speakers alone, both having adequate bass response, is generally preferable because—even though bass stereo contribution is negligible—the phasing is always purer in such an arrangement, thus definitely improving performance.

If a central bass speaker is used it is essential that a top-cut filter is used, preventing frequencies above at the most 500c/s reaching this speaker in audible amount. Otherwise the stereo effect is greatly weakened. ■

Miniature Power Amplifier

—continued from page 544

spigot on valve-holder No. 2.

- (3) Decoupling capacitor C1 from tag No. 20 to earth.

Use rubber grommets in the holes in the chassis where wires pass through to prevent the plastic insulation being cut by sharp edges. Wiring should follow normal audio practice, twisted leads for heaters and single earth connection to chassis. When wiring-up do not forget the centre spigot on the valve-holders, which must be earthed, plus one side of the output transformer secondary.

Power Supplies

Almost any power unit will be able to supply the modest power necessary, smoothed h.t. of approximately 280/290V, at 20mA and 6.3V a.c. at 0.6A. An h.t. supply of 300V must not be exceeded.

Components

Resistors of 1/2 watt rating are adequate. Only two close-tolerance resistors are needed and these are the phase-splitter anode and cathode loads,

where signal balance depends upon equality of the resistors. 1% tolerance must be used here.

Resistors for the rest of the circuit are preferably high stability of 5% tolerance, these are only slightly more costly than normal 10% carbon types and are well worth the slight extra cost.

Do not use a midget-sized o.p. transformer, otherwise low-frequency power output will be severely limited. A 3/4in. stack of laminations is the minimum for reasonable fidelity. The correct anode to anode load is $10k\Omega$ and the turns ratio of the transformer for different loud speaker impedances is as follows:

Speaker Z	Ratio
3Ω	60 to 1
8Ω	35 : 1
15Ω	25 : 1

Testing

When connected to a suitable power supply and correctly matched to the loudspeaker, feed in a signal from tape-recorder or radio tuner and if satisfactory a test of voltages in the circuit can be made.

Voltages indicated are for no-signal conditions and should be within 5% of the indicated values. If voltages across the cathode bias resistors are low this indicates low emission of the valve(s). ■

DO IT YOURSELF

Build a Record Player and Save Pounds

The Cheapest Way The L.K. Way

● **SCOOP! Transistor Tape Recorder.** The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed. Reduced from 12 gns. **OUR price £7.10.0 P.P. 3/6.** Complete with microphone, tape, batteries and operational booklet. Features push-pull amplifier, two motors, single switch operation, pause, speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.

Famous Autochanger or Single Player Units supplied with brand new, two-tone, de-luxe portable cabinets, 17 x 15 x 8 1/2 in. Strong carrying handle, gilt finish clips and hinges are used by famous make for 22 gn. model. Ready cut out motor board, 14 x 13 in. Front baffle 7 x 4 in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee. Available separately or package deals as below.

Our NEW MKII Superb Kits are now being dispatched.

L. K. PRICES FOR COMPLETE KITS:

Autochanger Kits as above
B.S.R. U.A. 14, T.C.8 Mono £10.17.6 P.P. 5/6
Garrard Autoslim, Mono £11.7.6 P.P. 5/6

Single Player Kits as above
Garrard S.R.P.10, Mono £10.12.6 P.P. 5/6
E.M.I. Autostop, Mono £10.17.6 P.P. 5/6

Individual Prices for those who wish to purchase separately.
Record Player Cabinet with Cut-out Board £2.15.0 P.P. 3/6
Amplifier with 7 x 4 in. speaker £3.10.0 P.P. 2/6

Autochangers
B.S.R. U.A.14, T.C.8 Mono £5.7.6 P.P. 5/6
Garrard Autoslim, Mono £6.0.0 P.P. 4/6

Single Players
E.M.I. Autostop, Mono £5.7.6 P.P. 4/6
Garrard S.R.P.10, Mono £5.5.0 P.P. 4/6
E.M.I. Separate Pick-up £3.0.0 P.P. 3/6

Transcription Units—Stereo Head—Mono
Garrard 4 H.F. Stereo £14.10.0 P.P. 5/-
Philips A.G.10/16, Stereo £12.0.0 P.P. 5/-
Garrard A.T.6, Stereo £9.19.6 P.P. 5/-

● **SCOOP! B.S.R. U.A.14 Autochangers.** T.C.8 Mono P.U. Brand new and boxed. Wired for stereo. Note **OUR price £5.7.6 P.P. 5/-**. Latest model.

● **SCOOP! Garrard Autoslim.** Mono P.U. Brand new and boxed. Wired for stereo. Latest model. Note **OUR price £6.0.0 only P.P. 5/-**.

● **SCOOP! Diodes—over 1,000,000 in stock—ideal substitute** O.A.81 vision detector. Note **OUR price £1.0.0 per 500 P.P. 2/-**. (In 500 lots only).

● **SCOOP! 3-watt Gramophone Amplifier.** Complete with Sin. Speaker, 49/6 P.P. 5/-.

The amplifier is complete, on a fabric-covered baffle board. Output transformer included. Tone and volume controls and on/off switch. Ready to switch on and play. Terrific volume. Size 12 1/2 in. x 6 in. x 3 1/2 in. back to front. For 200-250 v. A.C. Output 3 watts.

● **SCOOP! Miniature 4 valve superhet chassis.** Size only 6 x 4 x 1 1/2 in. Gives full medium wave coverage from ferrite rod aerial. Designed to operate from miniature batteries. Complete with case, speaker, etc. Only 50/- plus 2/3 post & packing.

Please send for our Amplifier and Hi-Fi lists, they are FREE. Our prices the most competitive in the trade.

● **SCOOP! Microphones.** Complete Lead Coax. Plug. Brand New. Our price 5/- only P.P. 1/6.

● **IF NOT ADVERTISED IT IS STILL IN STOCK**

● **MAIL ORDER ONLY TO THIS ADDRESS PLEASE**

TRANSISTOR SECTION

● **SCOOP! A first-class 2 wave-band 6 transistor superhet** chassis by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves. Note **OUR price £4.4.0 only.** Suitable speaker 10/6. A few cabinets can be supplied at 22/6 each. **OUR price for the package deal £5.5.0 only.**

● **SCOOP! As above, 8 transistor.** **OUR price £5.4.0 only.** Suitable speaker 10/6. Cabinet (very attractive two-tone). 22/6.

OUR price for the package deal £6.10.0 only.

● **SCOOP! A limited Number Only. Tape Decks** by B.S.R. Latest model. A.C./200/240 v. Brand new and boxed **OUR price £6.0.0 only P.P. 4/6.**

● **SCOOP! Tape Recorder Amplifiers.** Suitable for B.S.R. or Collaro Decks. Price: £6.10.0 for B.S.R. Deck: £6.12.0 for Collaro Deck. P.P. 6/-.

Mk.III. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1 1/2 in. Overall height 5 1/2 in. Front to back measurement 5 1/2 in. The amplifier is supplied complete with the switch waffer fully wired for B.S.R. deck. For Collaro deck, a completely wired separate switch with spindle is supplied. Magic Eye DM70 fitted.

● **SCOOP! Superb 1964 F.M.-M.W.-L.W. 3-Band Radiogram Chassis** with F.C.C. certification. Frequency: F.M. 88-108 Mc/s; B.C. 535-1605 kc/s; S.W. 3.5-9 Mc/s. Output, 5 watts. A.C. only. Ferrite rod aerials. Product of very famous manufacturer. Brand new with full maker's guarantees.

List price 22 gns. **OUR price 15 gns. only P.P. 5/6.**

FREE! with this superb chassis for one month only, two 5 x 6 in. P/M Dynamic Speakers and beautiful cabinet with matt chrome trim. Knobs are included to suit the chassis.

Please send for our Chassis Lists they are FREE. We are Main Agents for Brittamer "Empress" Chassis.

● **SCOOP! Complete 14in. TV Sets—Untested.** Choice of Pye, Philips, Ecko and Sobell, well packed—but at owners' risk. £2 each. Also few 17in. TV sets £4.10.0 each. Plus carriage and packing inner London 10/-, elsewhere 15/-.

VALVES—Ex-equipment Tested and Guaranteed

EB91	2/-	EZ80	4/-	PY80	3/6	6F1	2/6	6BW6	5/-
EBF80	4/-	KT33C	4/-	PY81	3/6	6F12	2/6	6BW7	4/-
EBF89	4/6	KT86	7/-	PY82	3/6	6F13	5/-	1A57	10/-
ECC81	3/6	PCC84	4/-	PY83	6/-	6F14	5/-	30F5	5/-
ECC82	4/-	PCF80	4/-	PZ30	7/-	6F15	6/-	35Z3	5/-
ECC85	5/-	PCF82	4/6	U25	6/-	6F19	6/-	35Z4	5/-
ECH35	6/-	PCL82	5/-	U26	6/-	6L1	7/-	30PL1	7/-
ECH42	6/-	PCL83	5/6	U191	7/-	6L18	7/-	PL12	5/6
ECH81	6/-	PCL84	6/6	U301	9/-	6P25	5/-	30PL13	6/-
ECL82	6/-	PL33	7/-	UAF42	5/-	6P28	8/-	30FL1	7/-
EF85	4/6	PL36	6/6	UBC41	5/-	6P28	8/-	6J0L2	7/-
EF91	2/3	PL81	5/6	UCC84716	7/6	6P28	8/-	R19	6/6
EL33	5/-	PL82	4/-	ECC80	7/6	7C5	6/-	50CD6	16/-
EL84	5/6	PL83	5/-	UFA42	2/6	757	10/-	6CD6G	12/-
EY51	3/-	PY32	7/6	6C9	10/-	787	6/-		
EY86	4/6	PY33	7/6	6X5	4/6	7V4	5/-		

EF80 in a batch of 12 for 16/-, plus 2/6 P.P. ECL80 in a batch of 6 for 14/-, P.P. 2/6. P.P. is 6d. on each valve.

Mullard 14in. tubes of all types. AW and MW. All 17/6 each. P.P. 10/-.

Speakers ex Equipment. 5in. 5/-, 7in. x 4in. 6/-, 6in. 6/6, 8in. 7/-, P.P. 1/6 each.

S.A.E. enquiries please. Our Complete Lists 1/- only—credited against your order.

● **THE CHEAPEST, THE BEST, THE QUICKEST SERVICE.**

L.K. ELECTRONICS (Victoria) LTD.



17 GILLINGHAM ROW, WILTON ROAD, LONDON, S.W.1.



TRANSISTORS

AC115	4/-	OA79	3/-	OC75	5/6
AC155	4/-	OA81	2/-	OC76	8/8
AC156	5/6	OA85	3/-	OC78	8/-
AC157	5/6	OA86	4/-	OC79	8/-
AC113	5/6	OA90	3/-	OC81	5/6
AC157	7/-	OA91	3/-	OC82	10/-
AD140	25/-	OA95	3/6	OC83	4/-
AF102	27/6	OC16W	35/-	OC84	8/-
AF111	11/-	OC19	25/-	OC139	8/-
AF115	10/6	OC32	25/-	OC140	19/-
AF116	5/-	OC35	12/-	OC141	31/-
AF117	9/6	OC36	21/6	OC189	10/-
AF118	20/-	OC41	8/-	OC170	5/6
AF121	11/-	OC42	8/-	OC182	8/-
AF125	10/6	OC43	12/6	OC200	10/6
AF126	10/-	OC44	5/-	OC201	29/-
AF127	9/6	OC45	5/-	OC202	24/6
BY100	7/6	OC70	6/6	OC203	13/6
BY114	6/-	OC71	4/6	OC204	19/-
GET114	6/6	OC72	5/6	OC212	8/-
GET115	9/6	OC72	5/6	MAT100	7/9
GET116	17/-	pair	16/-	MAT101	8/6
OA70	3/-	OC73	16/-	MAT120	7/9
OA73	3/-	OC74	8/-	MAT121	8/6
				ADT140	15/-

SETS OF TRANSISTORS

Set No. 1: comprising OC44, 2 x OC45, OC81, matched pair OC81 20/-.

Set No. 2: comprising OC81, matched pair OC81 10/-.

CATALOGUE

Our latest 1964/65 Catalogue is now available. Copies have been sent to many of our regular customers. If you have not received your copy please drop us a card. Please send 1/- in stamps.

TERMS: Cash with Order or C.O.D. Postage and Packing Charges Extra. Single values 9d. Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA

RADIO SUPPLY CO.

103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7



PUBLICATIONS

"Loudspeakers" by G. A. Briggs. The why and how of good reproduction. (5th edition)...	19/6
Mullard "Maintenance Manual" (2nd edition)	18/-
"Sound Reproduction" by G. A. Briggs. (3rd edition)	17/6
"How to get the best out of your Tape Recorder"	5/6
"Transistor and Crystal Diodes" B. R. Beltridg	3/-
"British Transistor Manual"	12/6
"Points on Pickups" F. Wilson. (4th edition)	10/6
"Stereo Handbook" G. A. Briggs	15/6
"A-Z in Audio" G. A. Briggs	19/6
"Audio Biographies" G. A. Briggs	7/6
"Servicing Transistor Radios"	2/6
"Emplate Guide to Better Recording"	2/6

MULTI-RANGE TESTMETERS

Earle TK20A	£2.9-6
Earle EP10K	£4.9-6
Earle EP20K	£4.19-6
Earle EP30K	£6.19-6
Leather Case for above	19/6
Earle EP50K	£9.19-6
Leather Case for above	29/6
Coby M1	£2.14-0
Coby A10	£4.17-6
Coby B40	£6.2-6
Altham 200H	£5.5-0
Taylor 127A	£10.10-0
Leather Case for above	£2.5-0

TRANSISTOR AMPLIFIER T615 DKE

15WT—Two mixing and separately controlled inputs. Description: P/Pull Class B.P.A. set with inputs for microphone and gram. Operated from 12v. battery. Output 15 watts Peak into 15 ohm load. Fully mixing inputs. Pre-amplifier stage being of such sensitivity that practically any make or type of microphone can be used. Specification: Mic Sensitivity 2 m.v. (600 ohm). Gram sensitivity 200 m.v. (100K), for full output. Frequency response ± 3 d.b. 60 c.p.s. to 7 Kc/s. Harmonic distortion 1% at 10 watts. Current Consumption: Quiescence 270 m.a. Average Speech Music 1.3/1.5 Amps. Size: 9" x 5 1/2" p 6 1/2". Weight 6 lbs. Special Features: Sensible size permits generous heat sink which is 1/8 swg. aluminium and occupies whole of roof area. Accent is upon reliability, even to extent of hand-made wire-wound resistors. Useful output even when worked from car battery down to 10v.. £16.10.0.

EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY

TEL. CRO 9186

VALVES

NEW TESTED AND GUARANTEED FOR THREE MONTHS

JCI	5/6	6BA6	5/-	12KSGT11/-	DL94	6/-	EL84	7/-	PY81	8/9	
1C1	7/6	6BE6	7/-	12QGT	7/6	DL96	7/6	EM85	10/-	PY82	7/6
1C3	7/6	6BR7	8/9	12SN7	4/6	EB91	4/-	EV51	7/6	PY83	7/6
1F1	7/6	6BW7	7/-	16A5	9/-	EB41	4/-	EV81	10/-	R19	5/6
1F3	2/-	6D2	4/-	19A5	9/6	EBF80	8/6	EV86	8/6	RS8A1	9/6
1F81	7/6	6F12	4/-	25L6GT	5/-	EC8A1	4/-	EZ40	5/6	TT15	27/6
1F89	5/6	6H6CT	2/-	30C1	7/6	EC82	6/6	EZ80	6/-	V2	7/6
1P1	7/6	6K76	5/6	30L1	7/6	EC83	6/6	EZ82	6/6	V7	5/-
1P10	5/6	6K84	6/-	35L6GT	7/6	EC84	6/6	EV12	8/6	V142	7/6
1P11	6/-	6K76	5/6	35C5	7/6	EC85	7/6	N17	5/6	V1841	8/6
1P5	5/6	6SL7GT	6/-	80	6/-	ECF80	6/6	N18	5/6	V1142	8/6
1P5	5/6	6SN7GT	7/6	DAF91	5/6	ECF82	7/6	N19	6/-	V141	8/6
1P4	2/-	6V6G	7/6	DAF96	7/6	ECF42	4/-	N709	7/-	V141	8/6
1P5	5/6	6X4	5/-	DP91	2/-	ECF41	10/-	PCF80	7/6	V141	7/6
3Q4	5/6	6X5G	5/6	DP96	7/6	ECF50	8/6	PCF80	7/6	V17	2/-
3B4	5/6	6Y4	4/-	DT76	7/6	ECF82	7/6	PCF82	7/6	V76	4/6
3V4	6/-	6Y7	9/6	DT77	5/-	EF41	4/-	PCF82	6/9	V142	8/6
5Z40	6/6	12AD6	7/6	DL142	6/6	EF80	8/-	PCF84	5/6	V147	5/6
6AK6	5/6	12AT7	4/-	DL150	10/-	EF86	8/-	PCF84	11/6	V149	9/-
6AL5	4/-	12AT7	6/6	DL81	5/6	EF91	4/-	PL82	7/-	V150	9/-
6AM6	4/-	12AX7	5/6	DL96	7/6	EF92	5/6	PL83	7/-	Z77	4/-
6AT6	5/-	12BB6	4/6	EL4	5/6	EL41	9/6	PCY33	12/6	ZD17	5/6

ASK FOR RESISTOR AND CAPACITOR COLOUR CODE FREE WITH EVERY PURCHASE

Latest model Radiokram Chassis. L.M.S.G. ext. LS and Tape sockets. complete with 10 or 12in. Speaker. £11.19.6.

High Stability Resistors (W 5%, 50Ω to 1MΩ. Midset Ceramics 500 v., 9d. Coax. Super Quality 1/2in. 6d. yd. Plugs 8d. Sockets 8d. Silicon H.T. Rects. 250 v. 300 mA 1/2in. x 1in. 8/6. Contact Cooled 250 v. 50 mA 6/8. 85 mA. 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC26, OC36, 25/-; OC44, OC45, 8/-; OC70, 8/-; OC71, 5/-; OC72, 8/-; OC72 Matched pair, 12/-; OC74, OC75, OC78, 7/6; OC81, 6/-; OC81 Matched pair, 12/-; OC170, OC171, 7/6.

VALVES MATCHED IN PAIRS

EL34, 27/6; EL84, 15/-; N709, 15/-; 6V6G, 15/-; Push-Pull O.P. Transformer, 21/-; 12in. 3Ω (or 15Ω) Speaker, 30/-; P. & P. 1/6; 12in. P.M. Speakers 22/-; 24/6. Baker's "Selhurst" 12in. 15Ω 15W Stalwart, £55.0. 15in. Auditorium 15Ω 50w, 18 gns.

SETS OF VALVES

DK91, DP91, DAF91, DL92 or DL94 17/6
DK90, DP90, DAF90, DL96 29/6
6K8, 6K7, 847, 6V6, 5Z4 or 6X5G 19/6
1R3, 1T4, 1R5, 3B4 or 3V4 17/6

Postages and packing 4d. Over £1 post free

C.O.D. 4/-

RECORD PLAYER AND TAPE DECK UNITS

BSR Monarch UA14. £6.6.0.
Stereo Version. £6.17.6.
BSR Monarch UA15. £6.19.6.
Stereo Version. £7.15.0.
BSR Monarch TU12. £3.10.0.
Battery version of above. £3.17.6.
BSR Monarch UG7. £3.17.6.
Battery version of above. £4.4.0.
BSR Monarch TD2 Tape Deck, 2 track, £6.8.0.
4 track version of above. £9.9.0.
Garrard Autolism. £6.19.6.
BSR Monarch TD10 Tape Deck, 2 track, £9.9.0.
4 track version of above. £10.10.0.
Garrard Autolism De Luxe Model AT6. £11.5.0.

GOODMAN HIGH FIDELITY LOUDSPEAKERS

8" Axielte 8, 6 watts, £5.5.7; 10" Axiom 10, 10 watts, £6.5.11;
12" Axiom 20, 15 watts, £10.17.4; 12" Axiom 30, 20 watts, £15.4.6;
9 1/2" Axiom 80, 6 watts, £20.6.3; 12" Triaxiom 1220c, 20 watts, £18.10.0.

AMATEUR RADIO

CHAS. H. YOUNG LTD.

AERIAL EQUIPMENT

TWIN FEEDER 300 ohm twin ribbon feeder, similar K25 6d. per yard K35B Telecon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

COPPER WIRE, 14 G. H D 140ft. 17/-; 70ft. 8/6, P. & P. 2/6. Other lengths pro rata.

AERIAL INSULATORS, Shell type, 2in. 9d. Plus Postage. **CERAMIC FEEDER SPREADERS**, 6in. type F.S. 10d. each. P. & P. 2/-.

CERAMIC "T" PIECES, Type A.T. for centre of dipoles 1/6 each. P. & P. 1/-.

2 METER BEAM ELEMENT W.S. YAGI. Complete in box with 1-23in. mast head bracket. PRICE 49/-, P. & P. 3/6. **SUPER AERIAL CABLE**, 75 ohms 300 watts very low loss 1/8 per yard, P. & P. 2/-; 50 ohm, 300 watt coax very low loss 1/9 yard, P. & P. 2/-.

ABSORPTION WAVEMETERS 300 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. 22/6 post free.

VARIABLE CONDENSERS All brass with ceramic end plates and ballrace bearings. 50 pF, 5/9, 100 pF, 6/6, 160 pF, 7/6, 240 pF, 8/6 and 300 pF, 9/6. All fitted with rear extension for ganging, P. & P. 1/-; Also Flexible Couplers, 1/- each. **SETS OF VALVES** for AR88 (14) £3.10.0 post free.


METERS, 3 1/2in. with 2 1/2in. scale, 0-10 mA, 15/-; 0-100 mA, 15/-; P. & P. 1/6.

THERMO, 2 1/2in. round 0-2.5 amp, 7/6 each. P. & P. 1/6.

170-172 CORPORATION ST.

BIRMINGHAM 4

Telephone CEN 1635

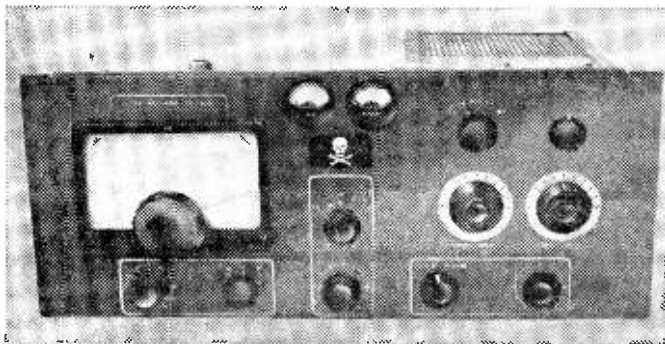

The BUCCANEER

MULTI-BAND TRANSMITTER

By J. E. Alban G3JEA

CONTINUED FROM PAGE 438 OF THE SEPTEMBER ISSUE

THE transmitter is assembled on a standard 16in. x 9in. x 2½in. deep chassis, and the valve base holes cut as shown in Fig. 4. If the Labgear unit is used, a drilling template is supplied by the makers and this should be positioned as indicated. The v.f.o. box is approximately 3in. high, 2½in. wide and 4in. deep, but should this not be readily available a small chassis could be used and a side cover fitted, access being made through the left hand side should repair be necessary. Alternatively, an Eddystone die-cast box can be used. The p.a. compartment is made rather on the

large side to allow for ample ventilation.

All wiring should be carried out in 20s.w.g. tinned copper, covered with suitable insulated sleeving. Heater leads, h.t. leads other than those carrying r.f. must be screened. In each case the metal screening must be exposed and wherever leads cross one another or run parallel for more than 3 or 4in., they should be bound together with a few turns of tinned copper wire and soldered and bonded to the chassis. The modulator section clumper wiring, and bias supplies should also be screened and decoupled with disc ceramic conden-

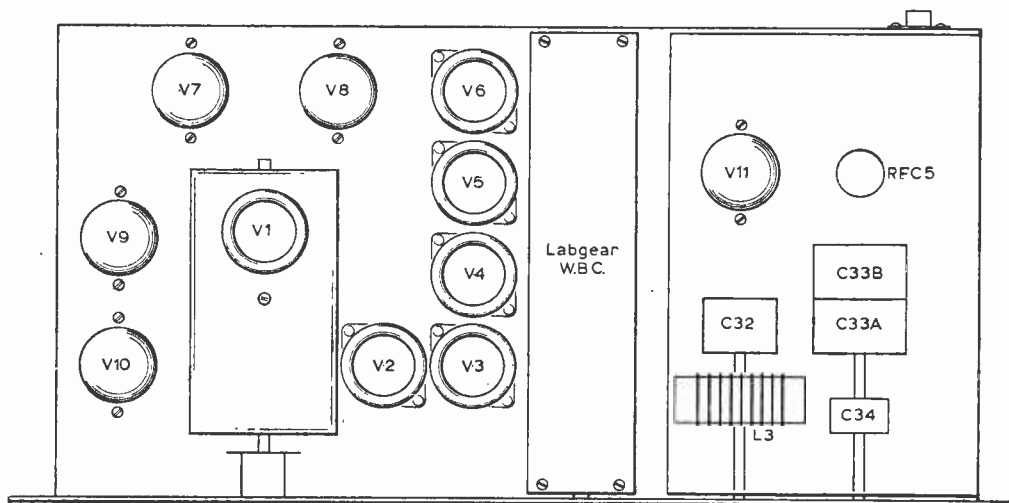


Fig. 4: Above-chassis layout of the major components.

MATERIALS FOR CHASSIS, PANEL, ETC.

Rack panel, 19 x 10in., black crackle finish
Chassis, 16 x 9 x 2½in.

Chassis bottom cover, 16 x 9in.

Box for v.f.o., 4 x 3 x 2½in.

V.F.O. box side cover, 4 x 3in.

All the above materials may be obtained from H. L. Smith & Co. Ltd. as standard ready-made items.

Two p.a. box side covers, 8½ x 5½in. with ½in. flange.

P.A. box rear and front panels, 6½ x 5½in.

P.A. box top cover, 8½ x 6½in. expanded aluminium.

32 x ½in. angle aluminium for top cover.

sers where indicated

When mounting the v.f.o. box on the chassis, care should be taken to see that the feed-through capacitors should be well clear of the holes drilled through the chassis, avoiding any possibility of short circuits or ineffectiveness of the condensers. Before any wiring is attempted, all holes indicated should be drilled in the front, rear, and top of the chassis. To avoid confusion, a Belling type of coaxial socket is used for the microphone, an Igranite socket for the key and ordinary banana-plug type of sockets for the station change-over relay connections. A Bulgin 5-way socket is used for the h.t. and l.t. connection to the power supply, there being ample spacing across the pins to wire in the r.f. decoupling chokes and condensers.


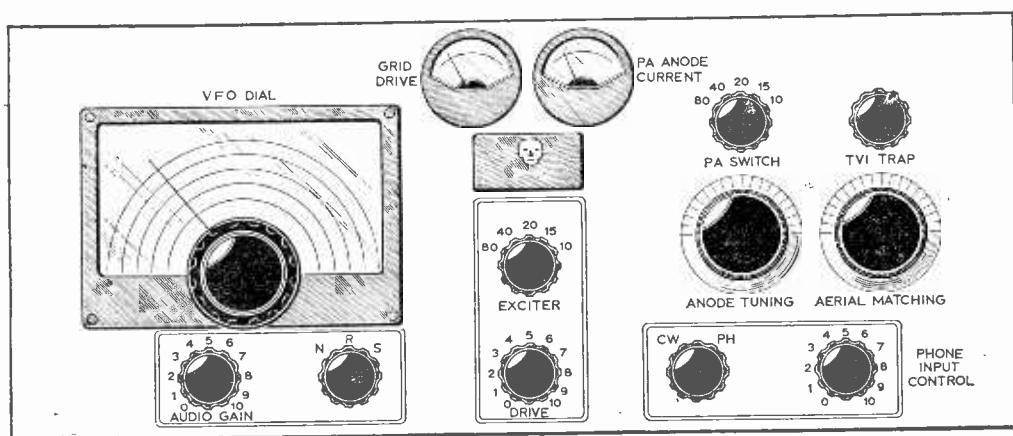


Fig. 5: Design for the front panel of the "Buccaneer".

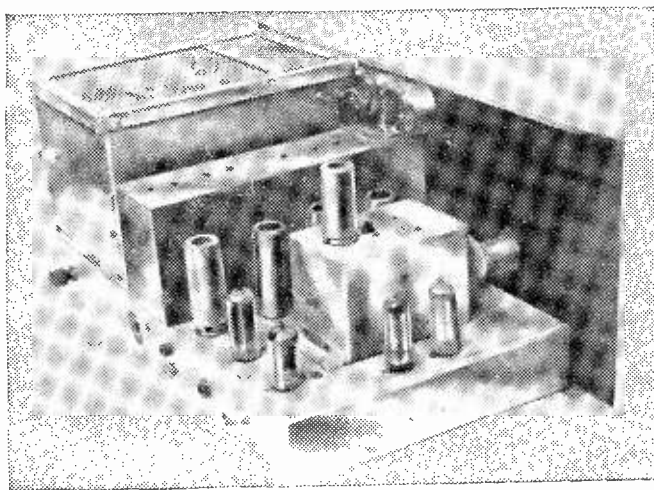

The completed chassis of the "Buccaneer".

When assembling the p.a. stage, a small circular screen 3in. high and 2½in. diameter should be affixed to the chassis with the valve-holder screws. In the writer's case, this is a small aluminium can, obtained for the asking from the local chemist's shop, and used for the bulk packaging of tablets. The metal frames of the variable capacitors in the pi-network and that of the harmonic trap should be bonded together with copper braid or 16s.w.g. copper wire, and earthed to the chassis, as close to the cathode connection of the 807 as possible. Likewise, the 807 heater choke and decoupling capacitors should be soldered directly to the valve socket by the shortest lead possible.

Tuning Up Procedure

The v.f.o. should first be set to cover the bands as required. By using the bandset condenser and

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW AVAILABLE ACTUALLY IN STOCK
NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	4/8	6BW6	6/9	6X5	4/8	20P5	12/3	ACHLD08/	EAB080	5/6	EL37	12/3	KTZ41	5/6	Q8150/10/8	U50	4/6	AF125	10/6		
0B2	4/8	6BW7	5/8	6Y9G	4/8	20A6	7/6	AC/PEN	EAC91	3/8	EL41	7/3	L63	3/8	R12	5/6	U52	4/6	AF126	10/6	
0Z4GT	4/8	6BX6	3/8	6Z4	5/8	25A6	4/8	(5) 7/8	EAC92	7/8	EL42	7/8	LN152	6/8	R16	28/6	U76	4/6	AF127	9/8	
1A3	2/6	6C4	2/3	7A7	12/6	25UGT16/2	AC/PEN		EB34	1/8	EL81	8/3	LN309	7/9	U17	17/8	U78	3/8	BZ13	11/6	
1A5	5/8	6C5	4/8	7B6	12/6	25Y5	7/9	(7) 17/8	EB41	4/8	EL83	6/9	LN319	8/8	U19	18/8	U84	10/8	G13	6/8	
1A7GT	7/8	6C6	3/8	7B7	7/8	25Y6G	7/9	AC/SG/22/6	EB91	2/3	EL84	4/6	LP2	9/6	R16	6/8	U101	12/8	G16	6/8	
1C1	4/8	6C8	3/8	7C3	7/3	25Z4	6/8	AC/SG/VM	EB93	20/8	EL85	7/8	L2319	5/6	R52	9/8	U107	12/8	G14	10/8	
1C3	6/3	6C9	10/8	7C6	6/8	25Z5	7/3	EBH33	9/8	EL86	7/3	L2329	5/6	RGL1240A	U191	9/8	GET103	7/8			
1C5	5/8	6C10	7/8	7D3	13/6	25Z6GT	8/8	ACTH115/	EB94	6/8	EL91	2/8	ME41	13/8	64/2	U251	9/8	GET104	10/8		
1C5	5/8	6C12	6/8	7D5	20/8	25Z8	23/3	AC/TP/18/	EB95	5/8	EL95	5/6	ME91	12/6	U281	8/8	GET106/17/8				
1C6	10/6	6C17	12/6	7D6	14/8	25Z17	6/8	AC/VP/12/	EB96	3/8	EL360	27/8	MH4	3/6	U282	12/8	GET111/12/8				
1D5	6/8	6C19G	12/6	7D8	15/8	30C1	5/6	AC/VP/2	EB97	5/8	EL820	16/8	MH14	8/8	U283	11/3	GET112/12/8				
1D9	9/8	6C19	5/8	7E1	5/8	30C2	5/8	ATP4	2/3	EB98	5/8	EL822	18/8	MH16D16/2	8/8	U289	9/8	GET114	6/8		
1F1	5/8	6C14	24/8	7E2	12/6	30C18	10/6	AZ1	5/8	EB98	7/3	ML6	15/8	U290	9/8	U339	9/8	GET172	10/8		
1F2	2/3	6D1	1/6	7E7	14/8	30F5	5/8	EB99	6/8	EB99	6/8	EM4	17/8	M84	20/5	U292	4/8	GET173	9/3		
1F3	2/3	6D3	9/8	7Y4	5/8	30FL1	9/3	AZ31	6/8	EB121	8/8	MS14	12/8	U301	4/8	U305	27/2	U301	16/3	GET174	9/8
1FBI	5/8	6D6	3/8	7Z4	4/8	30L1	5/6	B36	4/8	EC52	4/3	MS35	12/8	U305	27/2	U301	16/3	GET175	6/3		
1F9	3/6	6E5	9/6	7Z5	2/6	30L15	9/3	B319	5/6	EC53	12/6	MX18	8/8	U306	5/8	U4020	6/8	GET176	10/8		
1G6	6/8	6F1	9/8	9B8W6	9/6	30P4	12/3	BL33	6/8	EC54	6/8	EM80	6/3	N37	23/3	T41	9/8	VMP44	11/8	GET177	6/3
1H5GT	7/8	6F5	6/3	9D2	3/8	30P12	7/6	C1C	12/6	EC61	4/8	EM81	7/8	N78	26/2	TD02	12/6	VMS48	12/8	GET178	6/3
1L4	2/3	6F6G	9/8	9D7	7/6	30P16	6/8	C1C	12/6	EC81	39/6	N108	26/2	U314	8/8	U315	4/8	GET179	6/3		
1L6	16/10	6FGGT	7/6	10C1	8/8	30P19	12/3	CH33	12/6	EC90	2/3	EM85	8/8	N39	15/8	TH16	10/8	U316	15/8	GET180	6/3
1L15	4/8	6F8	5/8	10C2	12/3	30P11	8/8	CK306	6/8	EC91	3/8	EM87	7/6	P41	3/8	TH21C	10/8	U317	14/8	GET181	6/3
1L25	4/8	6F9	5/8	10C3	11/3	30P13	9/6	C14	19/6	EC92	6/8	EN31	10/8	P61	2/6	TH30C	14/6	U318	14/8	GET182	6/3
1N5GT	8/6	6F12	3/8	10D2	11/3	30P14	12/6	CL33	11/6	EC93	11/3	EN01	10/8	PAC80	6/8	TH23	6/8	U319	14/8	GET183	6/3
1P1	5/8	6F13	4/8	10F1	10/8	30A5	14/6	CV6	2/6	EC94	2/6	EN31	6/8	PC86	10/3	TH22	5/8	U320	14/8	GET184	6/3
1P10	4/8	6F14	23/3	10F9	9/8	35L6GT	6/8	CV6	10/6	EC95	21/7	EN31	6/8	PC86	10/3	TH22	5/8	U321	14/8	GET185	6/3
1P11	5/3	6F15	6/8	10F10	9/8	35W4	4/8	CV85	14/6	EC96	5/3	EN31	6/8	PC86	10/3	TH22	5/8	U322	14/8	GET186	6/3
1R5	4/8	6F16	6/8	10L13	6/3	35Z23	14/6	CV21	12/6	EC97	5/3	EN31	6/8	PC86	10/3	TH22	5/8	U323	14/8	GET187	6/3
1R4	5/8	6F17	12/6	10D11	9/8	35Z24GT	6/8	CV1	16/4	EC98	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U324	14/8	GET188	6/3
1R6	3/6	6F18	13/6	10P13	8/3	35Z25GT	6/8	CV1C	6/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U325	14/8	GET189	6/3
1T2	29/8	6F19	4/6	10P14	11/6	39	2/6	CV1	5/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U326	14/8	GET190	6/3
1T4	2/3	6F23	6/3	11D3	17/6	40S4	6/8	D1	1/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U327	14/8	GET191	6/3
1U4	5/8	6F24	9/8	11D5	17/6	41TH	15/8	D15	13/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U328	14/8	GET192	6/3
2A7	12/6	6F32	3/8	11E1	4/8	42	5/8	D15	13/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U329	14/8	GET193	6/3
2C26	2/6	6F33	3/6	12A5	2/3	45Z5	15/8	D77	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U330	14/8	GET194	6/3
2D13C	7/8	6G6	2/6	12A8	19/6	50A5	21/10	DAC32	7/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U331	14/8	GET195	6/3
2D21	5/8	6H16	1/8	12A06	8/8	50B5	6/8	DAF91	3/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U332	14/8	GET196	6/3
2P	23/3	6G53	3/8	12A06	8/8	50B5	6/8	DAF91	3/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U333	14/8	GET197	6/3
2X3	3/8	6G5GT	4/8	12A06	8/8	50B5	6/8	DAF91	3/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U334	14/8	GET198	6/3
3A4	3/8	6G6	3/8	12A17	5/8	50C6D44/8	6/8	D14	12/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U335	14/8	GET199	6/3
3A5	6/8	6G7	4/8	12A18	10/8	52K4	14/6	D14	12/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U336	14/8	GET200	6/3
3B7	5/8	6G7GT	4/8	12A18	10/8	52K4	14/6	D14	12/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U337	14/8	GET201	6/3
3D6	8/8	6G8	12/6	12A17	3/8	72	6/8	EDT25	7/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U338	14/8	GET202	6/3
3Q4	5/8	6G8GT	4/8	12A18	10/8	52K4	14/6	D14	12/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U339	14/8	GET203	6/3
35GT	7/8	6K70	1/3	12A17	4/8	78	4/8	DF65	15/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U340	14/8	GET204	6/3
384	4/8	6K7GT	4/8	12A18	10/8	52K4	14/6	D14	12/6	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U341	14/8	GET205	6/3
3V4	5/8	6K8GT	3/3	12A17	4/8	80	3/3	DF72	30/8	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U342	14/8	GET206	6/3
4D1	3/8	6K8GT	7/8	12A17	4/8	83	22/6	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U343	14/8	GET207	6/3
4B4GY	8/8	6K9	5/8	12A17	4/8	85	22/6	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U344	14/8	GET208	6/3
571	7/8	6L1	10/8	12B88	4/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U345	14/8	GET209	6/3
5V4G	4/8	6L5G	6/8	12B17	6/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U346	14/8	GET210	6/3
5V4G	4/8	6L5G	6/8	12B17	6/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U347	14/8	GET211	6/3
5V3GT	4/8	6L7GT	4/8	12B17	6/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U348	14/8	GET212	6/3
6F4	9/8	6L7	12/6	12B17	6/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U349	14/8	GET213	6/3
6Z3	7/8	6L18	10/8	12B17	6/8	90AG	6/8	DF91	2/3	EC99	5/8	EN31	6/8	PC86	10/3	TH22	5/8	U350	14/8	GET214	6/3
6Z4	7/8	6L19	9/8	12K5	10/8	150C2	4/8	HA10718/11	EF22	6/8	EL41	8/3	PNB4	7/8	U351	14/8	GET215	6/3			
6Z0L2	8/3	6L10	6/8	12KGT	9/8	161	13/8	DK32	7/9	EF36	3/8	HL1DD8/6	23/11	U352	14/8	GET216	6/3				
6A8G	5/8	6L13	7/8	12KGT	9/8	18B2B/34/11	6/8	DK91	4/8	EF39	8/8	HL1DD8/6	23/11	U353	14/8	GET217	6/3				
6A8GT	4/8	6L20	5/8	12KGT	9/8	2158G	6/8	DK91	4/8	EF39	8/8	HL1DD8/6	23/11	U354	14/8	GET218	6/3				
6AC7	8/8	6L21	5/8	12KGT	9/8	2158G	6/8	DK91	4/8	EF39	8/8	HL1DD8/6	23/11	U355	14/8	GET219	6/3				
6AG5	2/6	6P1																			

UNUSUAL SINGLE SPEAKER SYSTEM

A CONCRETE COLUMN

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in. or 10in. unit has attracted much interest and admiration because of its clean open sound. Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.



Price **£3.15.0** for 8" model. Recommended 8" unit—Super 8/RS/DD **£6.14.2** including purchase tax.

Price **£4.18.0** for 10" model. Recommended 10" units—Super 10/RS/DD **£10.18.8**; Golden 10/RS/DD **£7.17.5**; 10" Bronze/RS/DD **£4.12.9** Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet free on request from:



WHARFEDALE WIRELESS WORKS LTD.
IDLE BRADFORD YORKSHIRE
Grams: Wharfedale Bradford
Phone: Idle 1235/6

OSMOR

CHANGE OF ADDRESS To

540 PURLEY WAY CROYDON (NEAR AIRPORT)

SURREY

(Send 3d. stamp for lists)

Telephone
CROYdon 5148-9

Phone
ILford
6001/2/3

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12
Liverpool St.—Manor Pk.—10 mins.


Stamp
For Free
List

EX-RENTAL T.V. SETS

Coloured FREE LIST. Demonstrations daily from our large selection.

12 months written guarantee.

Channels for all areas.

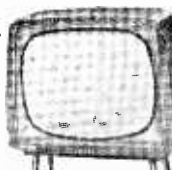

17in. **£11.10.0**
14in. **£7.10.0**

Carr. 14in. 20/-
17in. 30/-
Personal Collection Advised

AERIALS. BBC/ITA combined Loft and room aerials—From 25/-, BBC2/UHF and colour aerials—From 37/6. **SEND FOR FREE LIST.**

VALVES 9d. each. Thousands available. Send for list.

CONDENSERS. 100—10/-. New. Assorted electrolytics and p.f.s. P. & P. 2/6.

V/CONTROLS. 20—10/-. A selection of types and sizes. P. & P. 2/6.

SPEAKERS. 7/9, 6in., 8in., 7 x 4in. and 8 x 3in. Ex. incl. Salvage. P. & P. 2/3.

NEONS. 25 box 2/-, (S.B.A.D.P. fittings). Mains tester and visual reminders. P. & P. 1/-.

Telephone
Handset
15/6 pair

G.P.O. pattern House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

EX-MAINTENANCE TESTED TUBES


17in. — 35/-, 14in. — 15/-.

Carriage 5/- Satisfaction Guaranteed.

REGUNNED TUBES

Guaranteed one year

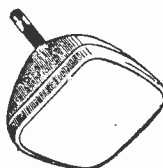Carr. 10/6. Add 10/- refundable on OLD TUBE (110° Tubes in stock).



21 in. **99/6**
17 in. **79/6**
15, 14 **59/6**
12 in.

the dust core of the inductance, some degree of variation is obtained in the bandspread coverage of the 15pF capacitor, TC1.

When satisfied with the coverage, the exciter bandswitch should be set to 3.5Mc/s and the main h.t. rail switched off. The drive control should be set at two-thirds open and key depressed. Some drive may be immediately apparent on the p.a.

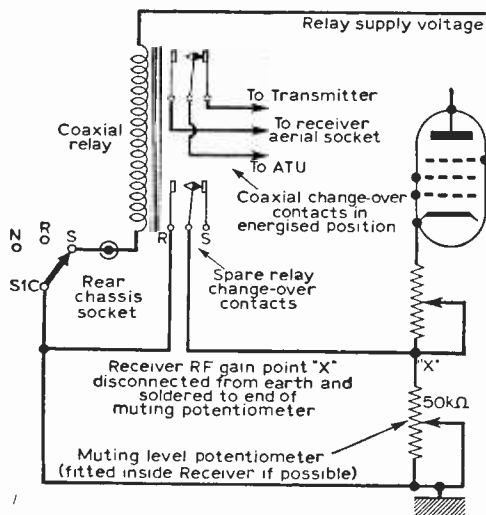


Fig. 6: The receiver muting and antenna change-over switching circuit.

grid current meter, but whether or not current is indicated, the first trimmer on the multiplier, that is, the one immediately behind the panel, should be peaked up for maximum drive. These adjustments to the wide band multiplier unit should only be made with reference to the manufacturers'

details supplied with the unit. Reduce the level of the drive control by stages should the meter be overloaded. The v.f.o. should be set at 3.5Mc/s for this adjustment. When satisfied that the first trimmer is peaked at maximum, the v.f.o. should be tuned to the h.f. end of the band and the trimming procedure repeated, this time using the other trimmer. Now, should the drive fall off badly to one end or the other, further trimming should be carried out. The final adjustment should be carried out on the v.f.o. output capacitor TC2, situated at the rear of the v.f.o. box. As the latter is brought into resonance, it will be observed that the strength of the v.f.o. signal in the station receiver will decrease, allowing the oscillator to be left running all the time without hampering reception.

The other bands are then set up in turn, using the trimmers for 7Mc/s and 14Mc/s, etc., until all bands have been adjusted and drive is fairly linear across them. Final peaking adjustments can be carried out on these bands with the Philips trimmers underneath the chassis. It is only necessary to obtain around 4mA with the drive control at maximum, to get more than sufficient power to drive the 807 to full input. In practice it is found that 1.5mA is ample when running at 90W input on phone and c.w. For phone operation the t.x. is adjusted in the c.w. position first, then the switch turned to the other mode, also, the input level control should be adjusted to give approximately 12mA standing anode current in the p.a. Using the mike gain control and speaking normally it should be adjusted until the anode current peaks reach the same level as when the key is pressed in the c.w. mode. The key is bypassed with a switch, so that it can be left in circuit if so desired.

The relay-control switching, shown in Fig. 6, is self-explanatory. Care should be taken to obtain a relay with reasonably wide spacing for the antenna change-over. Send-receive switching is a joy to use with just the one control to change over the antenna, mute the receiver, allow monitoring, and keep a snappy QSO going without the use of too many hands.

Amateur Band DX by G3JDG

Top Band has been particularly disappointing. At one session only two stations were audible: G3SCP (RST599) and G3SVV (459) both calling CQ.



Eighty Metres has been rather "quiet" although some DX has appeared. Mostly Europeans in evidence, SM, DJ, OK, etc., and, of course, the usual G sideband net up the h.f. end discussing everything from rhombics to rhinoceros.

Forty Metres proves by far the noisiest band of the bunch and at times almost bedlam. The l.f. segment has been a hive (literally) of activity, but phone stations seem to be harder to find these days. For those who can stick at it the stations are there in amongst the noise, the commercials, and the many strange squeaks and whistles peculiar to the 7-7.1Mc/s portion of the short-wave bands.

Twenty Metres is by far the best DX band at the moment in spite of its annoying habit of fading out for a time. On July 28th 13 countries were heard in 14 minutes from 21.27 to 21.41 hrs. All Europe was in full swing: UT5, YO, F2, I1, OE, DJ, LZ, OH, UB5, UA1, DM, average report was 579. In the h.f. sector the "W"s were roaring in averaging 5 and 7 to 8 and easily readable in spite of the QRM and slight QSB. All these on an odd piece of wire for an aerial and no matching ATU.

Fifteen Metres rather dead and neglected. Rumours of exotic DX breaking through may well be true but they were not audible to your scribe. Anyone else hear anything on this band??

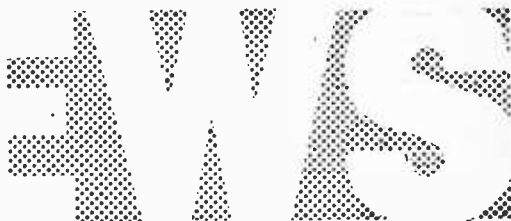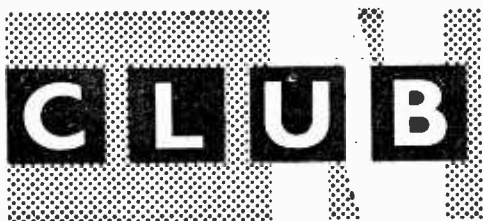Ten Metres—Reputed to be dead as the proverbial Dodo—sunspot cycle at its lowest—waste of time—"Lucky if you hear a 'G'". Friends you have been misled! Sunday morning 26.7.64 from 1030 to 1400hrs—OK, UA3, OK1, SP8, DJ8, DL7, G3, LA8, DM3/P, OZ5, EI, HB9 and GM. ALL ON AM PHONE. Clearly there's life in the band and no doubt SWL reports would be appreciated.



ACTON, BRENTFORD AND CHISWICK RADIO CLUB Hon. Sec.: W. G. Dyer, 3GEH, 188 Gunnersbury Avenue, London, W.3.

At the September meeting of this society, to be held on the 22nd, G3IGM will be giving a talk entitled "Application of Theory to Practice".

BRADFORD RADIO SOCIETY Hon. Sec.: E. G. Barker, G3OTO, 63 Woodcot Avenue, Baildon, Nr. Shipley, Yorkshire.

Members of this society who attended the August meeting on the 18th, heard a lecture on "Civil Defence".

The first meeting in September was on the 1st and was an informal evening.

CHESHUNT AND DISTRICT RADIO CLUB J. V. Beavan, G3GBL, 41 Albury Ride, Cheshunt, Hertfordshire.

This society meets on the first Friday of each month at the Civil Defence Centre, Turners Hill, Cheshunt. The meetings begin at 7.30 p.m. when visitors and prospective members will be welcomed.

On August 7th the Club met to hear a tape recorded lecture on test gear and other subjects.

This Saturday—5th September—Club members will be operating a demonstration station in the playing field at Goffs Lane, Cheshunt, under the call-sign GB3CRC. Visitors to the site will be welcomed by the members and all communications will be by telephony to create more interest for the less technical amongst them. The station will be on the air from 11.30 a.m. to dusk on 160 and 80 m.

CHESTER AND DISTRICT AMATEUR RADIO SOCIETY Hon. Sec.: P. J. Holland, Field House, 19 Kingsley Road, Gt. Boughton, Chester, Cheshire.

After the activity of Net Night held at the beginning of August, members settled down to open discussion on the 11th. An open night on the 18th once again provided the opportunity for quite a ragchew amongst members.

CLIFTON AMATEUR RADIO SOCIETY Hon. Sec.: J. Rose, G3OGE, 63 Broomfield Road, Beckenham, Kent.

Recent additions and alterations to the Club's aerial array have made it possible to increase activity on 144 Mc/s. and 70 cm.

On August 16th, members took part in the second 3.5 Mc/s. d.f. contest.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

This Society's mobile rally which is held annually at Rykneld School, went off successfully on August 16th after preparations had been finalised a few days before at a meeting on the 12th.

GUILDFORD AND DISTRICT RADIO SOCIETY Hon. Sec.: D. H. Mead, G3OXI, 41 Egley Road, Woking, Surrey.

Chobham Common was the venue for a group of members of this Society working portable gear on August 21st. At the meeting on the 28th, members discussed plans for the demonstration station they are manning at this year's Guildford Town Show, being held the following weekend.

NORFOLK AMATEUR RADIO CLUB Hon. Sec.: A. W. Pease, G3TCO, School of Biological Sciences, Wilberforce Road, Norwich, NOR 7TH.

Since its inception in January this year, membership of this society has risen to nearly 40 with Club activities likewise increasing. Recently a regular series of lectures has begun, to be followed by R.A.E. classes and Morse practice sessions.

New members will of course be welcomed at any of the meetings held each Monday, beginning at 8 p.m.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

Members of this Society provided two demonstration stations during August, one being at the Halifax Agricultural Show held

on the 8th, and the other at Crossleys Carpets Gala held on the 15th. On the 16th of the month, a group of members paid a visit to the radio telescope station at Jodrell Bank, Cheshire.

August ended with a ragchew night on the 19th, with no more club activities until September 2nd, when Northern Heights A.R.S. played host to members of the Manchester Radio Society at a Pea and Pie Supper.

READING AMATEUR RADIO CLUB Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven," 9 Holybrook Road, Reading, Berkshire.

The Club met on August 29th to hear several members describe various pieces of ancillary equipment made by them for use with typical transmitter rigs.

WEST KENT AMATEUR RADIO SOCIETY Hon. Sec.: H. F. Richards, 17 Reynolds Lane, Tunbridge Wells, Kent.

The main event of this Society during August proved to be a very enjoyable one for all who attended. It was held on August 30th and was in fact, a picnic at Sussex's Sheffield Park.

COURSES OF INSTRUCTION

BIRKENHEAD TECHNICAL COLLEGE

It is expected that an R.A.E. course will be run at this college on Thursday evenings. Enquiries for membership can be made either to the college or to A. Seed, 31 Withert Avenue, Bebington, Wirral, Cheshire.

BRENTFORD EVENING INSTITUTE

Several courses of interest to the radio enthusiast are being run by this Institute this autumn, including R.A.E. and Morse. Enrolment for any of the classes may be made between 14th to 17th September at the Brentford Evening Institute, Clifden Road, Brentford, Middlesex.

CENTRAL EVENING INSTITUTE

R.A.E. classes are being held at the Lea Mason Centre of the Central Evening Institute in Birmingham, starting on 14th September. Enrolment week commences 7th September.

EAST HAM TECHNICAL COLLEGE

An R.A.E. course will begin at the East Ham Technical College, High Street South, London, E.6, on 21st September. Candidates should enroll on the 14th, 15th or 16th September.

NORTHSIDE SCHOOL

On 21st September, an R.A.E. course begins at Northside School, Percy Road, Finchley, London, N.12. Morse instruction will also be given later in the course. Enrolment for the course can be made between 14th and 17th September.

WEMBLEY EVENING INSTITUTE

At the Copland School of this Institute in Wembley High Road, R.A.E. classes will be held from 21st September. Enrolments will be accepted between 14th and 17th September.

WESLEY EVENING INSTITUTE

A radio and television course will begin at this Institute on 21st September. Enrolment can be made at the Institute in Wesley Road, London, N.W.10, between 14th and 18th September.

AUDIO OSCILLATOR DESIGN

We wish to point out that the article "Audio Oscillator Design", which appeared in the August 1964 issue of PRACTICAL WIRELESS, was based on a chapter of the Mullard Reference Manual of Transistor Circuits, published by Mullard Limited.

TOP QUALITY—LOW COST



AMATEUR RADIO EQUIPMENT

BUILD YOUR SHORT WAVE STATION WITH CODAR-KITS.

CR 66 COMMUNICATIONS RECEIVER

THE FINEST SUPERHET KIT EVER OFFERED

Hundreds of testimonials (can be seen at our offices) prove this highly sensitive top quality receiver to be the finest value ever offered. No technical knowledge or equipment is required. Assembled Coil Unit and I.F. Transformers are factory aligned. Frequency range 540 Kc/s to 30 Mc/s in 4 bandswitched ranges. Separate Electrical Bandspread. Regenerative I.F. stage for maximum gain and B.F.O. Panel aerial trimmer, AVC, Standby, Speaker switches. 3 watts output for 2-3 ohm external speaker. Valve line-up: ECH81, EBF89, ECC81, EL84, EZ80, EM84. Tuning Indicator. Modern styling in Silver Grey Cabinet 16 x 6½ x 8½ in.



Complete Kit, 17-page Instruction Manual..... £19. 2/6
Ready Built £21. 12/6

"S" Meter Model Kit £21. 2/6
Ready Built £23. 15/0

Carriage on all models 6/-.

H.P. Terms available on request.

★ P.R. 30 R.F. PRESELECTOR ★

Frequency range 1.5-30 Mc/s. Substantially improves the performance of any superhet receiver.


G4HZ writes "... I am delighted with it, it improves my Eddystone 640 in all respects. The difference with the Pre-selector is fantastic, a weak signal on 15 metres about S2 changed to S8. On the L.F. Bands, unwanted noise and mush is cut out.

G3RIA writes "... The results in conjunction with my Eddystone 888 are amazing. Signals are twice as strong with much higher signal/noise ratio. A first-class product well worth the money. The P.R.30 uses EF183 Frame Grid R.F. Amplifier and provides up to 20 dB gain. Features include vernier tuning, gain control, selector switch for either dipole or end fed antenna. External power supplies (obtainable from Rx). Smart styling in grey and black. Complete, READY BUILT, with all plugs, cable.

Now available in two models.


P.R. 30 for external power supplies 180-250 volts H.T., 6.3 volts 3 amp. L.T. (obtainable from receiver). £4.17.6

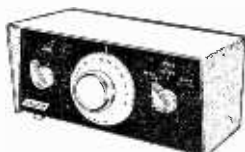P.R.30X self powered with internal power supply for 200-250 volt A.C. Will provide 200 volts up to 25 mA and 6.3 volts 1 amp. for other accessories. £7.2.0



CR 45 MAINS T.R.F. SHORT WAVE RECEIVER

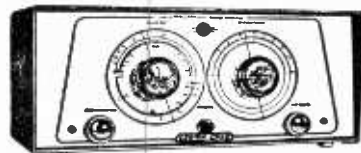World-wide short wave reception, North-South America, India, Russia, Far East, Australia, amateurs, shipping, etc.



- ★ Separate electrical bandspread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb modern styling and Top quality components throughout. Complete CODAR-KIT, with valves and 3 Coils, 10-28, 25-75, 60-176 metres. Instruction Manual 11 pages, less Cabinet £7.5.0, Carr. 4/6.

CR 45 Cabinet Silver Grey 12 x 5½ x 7in. with sliding door for easy coil changing and detachable louvered rear panel 28/6. Instruction Manual only 4/- post free. Extra coils 4/9 each.

★ CAN BE SUPPLIED READY BUILT PRICE ON REQUEST.

STILL AVAILABLE! THE FANTASTIC MINI-CLIPPER

Miniature 1 valve s.w. receiver Can be built in one evening, ready to switch on, to bring the fascination of Short Wave listening at very low cost. Complete MINI-CLIPPER CODAR-KIT, valve, and one coil 25-75 metres. Instruction Manual 4 pages, carriage 2/6. 36/6

Extra Coils 4/9 each. Provision to add two-transistor amplifier. Electrical Bandspread available. Instruction Manual only 2/-, post free.

★ IT'S HERE! CODAR A.T.5 12 WATT 2 BAND MINIATURE TRANSMITTER "THE tiny TX with the BIG voice"

The CODAR A.T.5 is the newest, most compact Tx for fixed or mobile use on 160/180 metres. 12 watts phone 15 watts C.W.

CHECK THESE OUTSTANDING FEATURES★

High stability new type calibrated V.F.O. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export).

Low loss air-spaced CODAR-Coil Pi-net output.

P.A. Plate current meter, plus neon indicator.

Plate/screen modulation. AM/CW switch and panel key Jack.

Plug changeover for 6 or 12 volt heater supply.

Small and smart for XYL appeal. Grey cabinet only 8½in. wide, 5in. deep, 4in. high.

Base area is less than this page? Front panel Black and Satin silver, grey and chrome control knobs.

Complete, Ready Built..... £16.10.0

Matching power supply unit for 200-250 volts A.C. with Standby/Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby/transmit indicator.

12 volt mobile power supply available shortly. Transmitter or P.S.U. available separately. £8.0.0



£16.10.0 Carr. 4/-
£8.0.0 Carr. 5/-

CODAR-KITS are famous for PEAK PERFORMANCE, EASY TO FOLLOW INSTRUCTIONS, CLEAR PICTORIAL DIAGRAMS. Some of the Top Quality names who supply material for CODAR-KITS ... MULLARD, BRIMAR, JACKSON, DENCOR, ELECTRONIQUES, THORN, A.E.I. etc. ... only the best is good enough for the high CODAR standards which make complete success certain. 6d. in stamps brings illustrated leaflets.

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX

G3IRE

CANADA: CODAR RADIO OF CANADA, TWEED, ONT.

G3HGQ

WEYRAD

TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistor Superhets:—

P50/1AC Oscillator Coil for 176 pF tuning	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers	5/7 ea.
P50/3CC 3rd I.F. Transformers	6/- ea.
All mounted in individual cans $\frac{1}{2}$ in. diam x $\frac{3}{4}$ in. high.			
RA2W Ferrite Rod Aerial 208 pF Tuning	12/6 ea.
LFDT4 Driver Transformers	9/6 ea.
OPT1A Output Transformers	10/6 ea.
PCA1 Printed Circuit Panel	9/6 ea.
Constructor's Booklet	2/- ea.

VALVE RECEIVER COILS

Our individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.


H Coils 3/9 each.

WEYMOUTH RADIO MANUFACTURING CO., LTD.

REGENT FACTORY, SCHOOL STREET,

WEYMOUTH, DORSET

THE COMMON

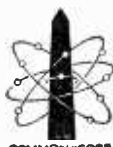

COMMON-CORE

CORE SERIES

BASIC ELECTRICITY (5 parts)

BASIC ELECTRONICS (6 parts)

BASIC SYNCHROS & SERVOMECHANISMS (2 parts)

BASIC ELECTRONIC CIRCUITS (2 parts)

WHAT READERS HAVE SAID ABOUT THEM—

"... Thank you for sending **BASIC ELECTRONICS**. I read the first part last night and was more amazed as I read further. After reading the section on Filter Circuits once, I understood more about them than I have been able to find out in a whole year from the obscurities of other text books and manuals. Thank you for a really first class work ..."

"... I think the **Basic Books** are the best I have ever read, and I've read a hell of a lot ..."

"... A truly excellent publication, not in the least complicated by endless mathematics ..."

"... The books are excellent and contain the information I have been seeking for years ..."

"... Your books seem to explain things much more easily. I wish they were on sale when I had to learn radio ..."

COUPON - SEND NOW!

OR ASK YOUR BOOKSELLER

TO THE TECHNICAL PRESS LTD.
112 Westbourne Grove, London, W.2.

Please send me your **FREE** prospectus describing **THE COMMON-CORE SERIES**

Name
Address



LETTERS TO THE EDITOR

AMERICAN LITERATURE

SIR.—Recent issues of your journal have, more often than not, included a page of book reviews, and this, in my opinion, well reflects the state of the book market which is currently being flooded by technical publications both from home and abroad.

Many of the imported books come from the U.S.A. and while any additions to the amount of technical literature available is to be welcomed, much of the value of these books might be lost by an unwary reader in this country who does not allow for the very real language differences to be encountered in works of American origin. When reading books from the U.S.A. dealing with radio and electronics, I find it necessary to accustom myself to substitute automatically "earth" for "ground", "anode" for "plate", etc., for to stop, think and translate every unfamiliar term as it occurred in the text would be disastrous for any reader trying to absorb the contents.

There is then, I suggest, a strong case for making available information to explain and clarify these differences, a sort of English/American dictionary. It is probably true that English versions of technical works originally written in French, German or Russian suffer less from these difficulties than American books, as translators of foreign language books are aware of English expressions and take this into account, whereas books which come from the United States are left "raw" because officially both countries use the same language.

If it were just a matter of substituting one word for another, there would be little to worry about; however, very often the whole approach to a piece of theory differs in the U.S.A. and even circuit diagrams and symbols have a peculiar and confusing appearance to the British reader.—**JAMES GOODWIN** (Scarborough, Yorkshire).

PAST ISSUES OF P. W.

SIR.—With reference to your "Sell or Loan" column, I have available every copy of *PRACTICAL WIRELESS* from 1950 to 1962, also every copy of *Practical Television* from No. 1 to 1962, and I am willing to give any of these issues, free of charge, to anyone who cares to write, enclosing postage sufficient to cover any issues they require. This is a genuine offer now that I find I am forced to dispose of these magazines as they take up more space than I can afford.—**J. F. HITCHCOCK** (86 Reigate Avenue, Sutton, Surrey).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents.

TRANSISTOR PREAMP

SIR.—Regarding the Transistor Preamp on page 358 of the August issue of *PRACTICAL WIRELESS*. When used with the power supply unit for a valve amplifier (Fig. 3) the output should be taken from C4 and the negative line. This will avoid having a potential difference between the preamp output and valve amplifier input circuits. The input circuits should be isolated by a 25 μ F 25V electrolytic in series with the +ve lead to the volume control and input sockets (negative to VRI and sockets). This will prevent d.c. from reaching the tuners and gram p.u. if they are earthed to the amplifier chassis.

I would also like to correspond with any radio enthusiasts of my own age (13).—**ALAN CAMPBELL** (30 Barnsdale Road, St. Ninians, Stirling, Scotland).

POCKET SIGNAL INJECTOR

SIR.—It would be interesting to know the variety of containers used by your readers to make the Pocket Signal Injector and also the Signal Tracer when they found that the specified pencil torches were in short supply. I see that in your August issue Mr. Raymond Cruise used a film cassette tin. Myself I turned to the little clear plastic boxes in which "Desogen" throat tablets are packed. They measure 3in. x 1½in. x ½in., will contain a U16 1.5V battery, but with difficulty, or Mallory cells very easily, and have the advantage that they do not need insulating for a.c./d.c. work. They enabled me to make neat jobs of both the Injector and the Tracer with which I am very satisfied. The printing on the boxes can be removed with metal polish and elbow grease!

Making the probe from 2B.A. threaded rod with a hand drill is by no means child's play. Unless the rod is supported very little filing effect is obtained from a file held on the rod and the file cannot be controlled and prevented from slipping all over the place. I found that I had to nail a thick block of soft wood to my bench and fix the hand drill in the vice so that the 2B.A. rod in the chuck lay flat on this block. Then I drove a good-sized staple into the block so that I could put the point of my file into it and utilise it to get pressure on the rod. Even then I found the file tended to be dragged into the staple so that it jammed and lateral movement of it was impossible. This meant another nail in the block for a file stop to prevent the jamming. Another nail near where the rod entered the chuck jaws

acted as a lateral stop and completed this Heath Robinson rig. After all this I had no difficulty in finishing two nicely tapered probes. I hope other readers will find this tip helpful for both of these neat and extremely useful instruments.—R. S. WELFORD (Sunbury-on-Thames, Surrey).

SHAKE-PROOF WASHERS

SIR,—No one these days seems to know what the shake-proof washers on such things as potentiometers and air-spaced condensers are for.

They are supplied to prevent the whole component from turning when heavy-handed people twist the knob; *not* to prevent the screw from turning. Therefore the washer should be fitted to the spindle of the component *before* it is fitted to its chassis.

It is true that some of these types of components are fitted with positioning lugs, in which case the washer should be placed on the *same* side of the chassis as the locknut.—A. MARTIN (London, S.W.19).

THE IMPORTANCE OF THE RAE

SIR,—While I am in favour of commercial broadcasting and think the BBC monopoly ought to be broken, I think the comments of W. Jenkins and A. Sidi, on Thermion's *Caroline* views should be put into proportion.

I would like to say that *Caroline's* operation outside Territorial Waters is merely a protest to the Postmaster General for his refusal to issue commercial broadcasting licences, and is not an advocate for the issue of licences to unqualified operators such as we would have in a "Citizen Band". The RAE is not an electronic wizard's examination. It merely tests one's knowledge of basic radio theory, and most important, the necessary knowledge to deal with any interference which may result from the operation of one's station.

If Mr. Jenkins or Mr. Sidi cannot be bothered to learn these few basic facts, then I suggest they try some other hobby. I can just imagine the answer they would give to their irate TVI-prone neighbours, to say nothing of the model enthusiast from down the street who has just lost a beautiful radio controlled plane. I should imagine it would be something to this effect, "Sorry mate, I don't know a thing about radio, I just operate it for fun".—A. MAYNARD, B.R.S. 26128 (Bognor Regis, Sussex).

(We endorse Mr. Maynard's remarks concerning the R.A.E.. The amateur transmitting licence is not a barrier to the real enthusiast. Readers interested in obtaining their "ticket" will find something of interest in the next issue—EDITOR.)

Sir—I would be grateful if any reader could sell or loan me . . .

. . . following issues of P.W.: Dec. 1961, Jan., Feb., Mar., Apl., May 1962, and Jan. 1963. I will pay full price for all copies in good condition.—J. J. BOWYER, 2 Chichester Street, Chester.

. . . the circuit and booklet of Marconi Communications Receiver CR100.—WAH KHAI LIANG, Department of Radio, Radio Malasia, Penang, Malasia.

. . . the March 1964 issue of P.W.—J. G. TANGNEY, 18 Green Park, Wilton Lawn, Cork, Irish Republic.

. . . the circuit and servicing data for the Defiant AF7.—R. W. SHEPPARD, 97 Hermitage Woods Crescent, St. John's, Woking, Surrey.

. . . circuit diagram and any other information regarding the PCR3 receiver.—B. GIBSON (ZS2PG), 69 First Avenue, Newton Park, Port Elizabeth, S. Africa.

. . . details or handbook on the Lavoie Laboratory Micro Wave Frequency Meter Model 105SM Serial 2876, covering 375 to 725Mc/s.—F. B. BLAKE, 2 Fair View, School Lane, Seer Green, Beaconsfield, Buckinghamshire.

. . . circuit or manual on the Super Skyriider Halli-crafter SX 16, also the data for the D.B.20 Preselector.—R. MCLACHLAN, 66 Haigh St., Halifax, Yorkshire.

. . . circuit diagram and manual for Halli-crafter receiver SX 28, and a circuit of about 60W c.w./phone v.f.o. transmitter with a suitable s.s.b. adaptor for the same. I shall arrange payment through a friend in U.K.—S. L. ANAND, 3066/5A Street No. 10, Ranjit Nagar, New Delhi -12, India.

. . . test instructions for Hansen Multimeter, Model T.S.—J. DUNNETT, 7 Lorne House, Kinlochleven, Argyll.

. . . the handbook, circuit or any other data on the R1132A communications receiver.—F. H. LADD, 4 Wellington Close, Melbourne Park, Chelmsford, Essex.

. . . the manual of the R.107 set ZA 3050.—B. CATCHPOLE, 45 Balmoral Drive, Borehamwood, Hertfordshire.

. . . circuit and any information on the receiver of Ex-Government Rx/Tx Model 3/11 (also known as B11).—A. PARKIN, 9 Dawsons Rough, Shawbury, Shropshire.

. . . circuit or any information as to the connections of the 12 pole outlet socket of the 38 a.f.v. transceiver.—D. K. COOPER, c/o R.E.C. & Co., Lefkara, Cyprus.

. . . list of valves or the circuit diagram for Philips Receiver, Type BX 516 A/10.—C. K. OCRAN, P.O. Box 205 Takoradi, Ghana.

. . . the February 1963 issue of PRACTICAL WIRELESS —S. SAETHERN, Roberg, Tonsberg, Norway.

. . . any aerial details or the circuit for Communications Receiver P.C.R.3.—A. GARGETT, 30 Dryden Road, West Cliff Est., Scunthorpe.

. . . any information on the Roding Transportable Tape Recorder.—H. WILSON, 59 Gatehope Drive, South Ockendon, Essex.

. . . circuit and any other details of a Crosley Prestotune set.—J. SMART-OKUOKA, 7 St. George's Road, Coventry.

. . . the August 1962 issue of PRACTICAL WIRELESS. —J. B. WHITE, 1 Lansdown Place West, Bath, Somerset.

. . . issues of PRACTICAL WIRELESS dealing with modifications to the R109 A receiver.—T. R. SMITH, 50b Aldershot Road, Guildford, Surrey.

. . . circuit diagram and component values for the Ekco Car Radio CR61/A.—P. HEARNE, 1 Derwent Close, Gossops Green, Crawley, Sussex.

CATALOGUE RECEIVED

MESSRS. Henry's Radio have recently published a new 1964 edition of their comprehensive catalogue. It comprises 86 pages and is fully illustrated, covering a very wide range of electronic components.

Cadmium sun-cells, crystal owens, dosimeters, deccatrons, printed circuit etching kits, ferrite pot cores, geiger tubes, gamma probes and mercury cells, are but a few of the items listed.

A wide range of transistors and associated components are included, plus a transistor equivalent chart and connection details.

It is a well-produced book and much thought obviously has been given to its preparation. The price is 2s. 6d. post free and copies may be obtained from Messrs. Henry's Radio Ltd., 303 Edgware Road, London, W.2.



that is, if you can see it from there!

What is it? It's a radio—a real honest-to-goodness station-getting six stage British set so small that not even the Japanese, Americans or Germans have got anywhere near it. A gimmick, did you say? Indeed not! If you're technical, you'll see on the pages which follow how this cute little Micro-6 works.

All I know is that it's loud, it's clear and there seems no end to the stations you can tune in. You have to build it yourself of course, but they say that's half the fun. This one was given to me . . . makes a lovely present for someone, doesn't it?

**A BRITISH
PRODUCT**

SINCLAIR MICRO-6

the smallest set on earth!



ACTUAL SIZE

- MEASURES $1\frac{4}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- WEIGHS LESS THAN 1 oz.
- BUILD IT IN AN EVENING

Technical details and more Sinclair designs
on next pages.

Now on to next pages

All parts including
transistors, case, ear-
piece and instruc-
tions come to


59'6

SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE Phone 582

WORLD-BEATING


6 STAGES FROM ONLY 3 TRANSISTORS

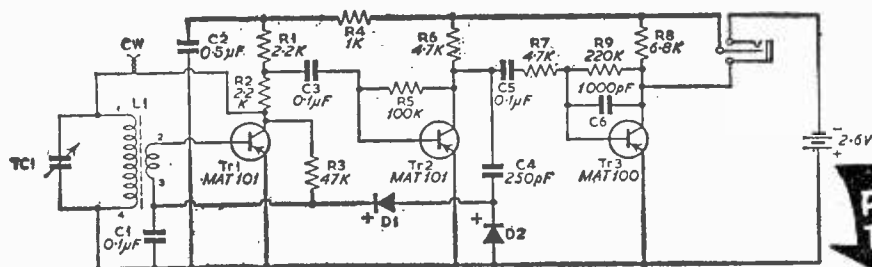IN A CIRCUIT THAT ONLY UNIQUE MATS AND APPLIED RESEARCH MAKE POSSIBLE



The most advanced radio circuit ever made available to constructors

The Micro-6 uses three Micro-Alloy Transistors (MATs) in a unique double reflex circuit. The signal selected by L1 and TC1 is amplified at R.F. by Tr1 and Tr2. The output from Tr2 is rectified by the detector stage D1 and D2, and the resultant A.F. signal passed back to Tr1. Tr1 and Tr2 then amplify the signal again—this time at A.F. Thus both Tr1 and Tr2 have been used twice and give a gain normally only obtainable with four transistors. The output from Tr2 drives Tr3, the output stage, which feeds into the featherweight earpiece (or the TR 750 power amplifier.) Tuning is over the medium waveband with bandspread for easy reception of Luxembourg and A.G.C. eliminates fading. It is important to realise that the Micro-Alloy Transistors which the Micro-6 uses not only give extremely high gains and low noise levels, but they consume only a fraction of a mA from the two minute batteries used to power the set. Battery working life is over 70 hours!

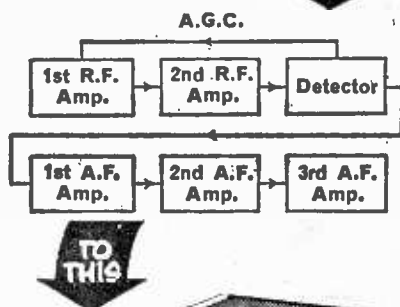

**YOU CAN BUILD THIS SET
IN AN EVENING!**

The Micro-6 is simplicity itself to build when you follow the meticulously detailed instructions. No special tools are required to build it. All parts including three MAT transistors, two diodes, elegant white and gold case, lightweight earpiece and 8 page instructions manual come to

59/6

"TRANSRISTA" STRAP for wearing your Micro-6 on the wrist. Black or grey nylon

7/6

Mallory Mercury Cell type ZM312 (two required) each
Pack of six — 10/6

1/11

sinclair

MICRO-6

SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE Telephone COMBERTON 682

**USE
THIS
ORDER
FORM**




SINCLAIR DESIGNS

THE MICRO-6 uses the smallest components ever

We show here some of the components. We didn't have room for case, dial, earpiece and some of the capacitors, drawn to actual size. They include the smallest ever to be made available to domestic set constructors, being of the kind used in space and computer electronics, so they have to be reliable. The tuning system has ingenious vernier control for easy station separation. 8 page fully illustrated instruction manual and all parts including case, vernier dial and ear-piece, come to

59/6

CAPACITORS

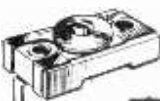


TRANSISTORS

RESISTORS






DIODES

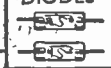

BATTERIES



AERIAL

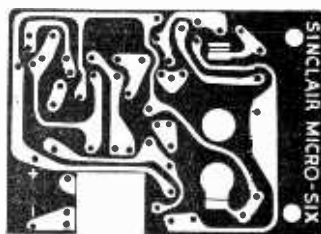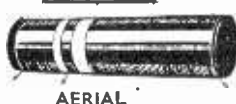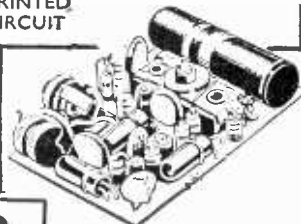PRINTED
CIRCUIT

COMPLETE WITH
BUILT-IN VOLUME
CONTROL AND ON/
OFF SWITCH



SINCLAIR TR750 POWER AMPLIFIER

PERFECT FOR USE WITH THE
MICRO-6 AND SLIMLINE

Measuring only 2 x 2in. and having its own built-in volume control and on-off switch, the TR750 has a full 750 milliwatt transformer less output for 10mV into 10K ohms. Frequency response is from 30 to 20,000 c/s within ± 1 dB. This amplifier makes a powerful car, domestic or portable radio used with the Micro-6 or Slimline receivers, or a hi-fi record reproducer used singly or paired for stereo. There are many other uses for the TR750, which is available for building or ready built. All parts with instructions come to

39/6

Ready built
and tested **45/-**

UNIQUE
SINCLAIR
GUARANTEE

If you are not completely satisfied with your purchase (we are confident that you will be delighted) your full purchase price will be refunded instantly and without question.

FULL SERVICE FACILITIES ALWAYS AVAILABLE TO SINCLAIR CUSTOMERS

SINCLAIR INJECTOR

Using 2 MAT's it generates and injects a test signal into any part of equipment at 1 kc/s to 30 Mc/s to locate faults rapidly.

1 1/8 x 1 3/16 x 3/4 in. excluding probe. With full instructions. Invaluable to all constructors. Parts and instructions come to



27/6

Ready built

32/6

Build an F.M. Transmitter with the Sinclair Micro-amplifier

Smaller than a 3d. piece! Frequency response 30 to 50,000 c/s ± 1 dB. Power gain 60dB (1,000,000 times)

Instructions show you how to make a broadband R.F. amplifier, F.M. transmitter or a sub-miniature hi-fi amplifier with an output suitable for any earpiece or even loudspeaker.



Smaller
than a 3d. piece
Parts and
instructions
come to

28/6

SINCLAIR SLIMLINE

EXTRA EASY TO BUILD

Ideal for newcomers. Has self-contained ferrite rod aerial and takes standard PPS battery, yet measures only 2 1/2 x 1 1/4 x 3/4 in. This four stage receiver tunes over the medium waveband. Great power and quality. All parts including royal blue and gold case, earpiece and instructions come to



49/6

TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE

Please send items detailed below

£ s. d.

Phone: COMBERTON 682

NAME

ADDRESS

TOTAL £

For which I enclose cash/cheque/money order

BLOCK LETTERS

P.W.10

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV. 1925-1964. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models, 1/6. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists, HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television, 3/6 post paid. VEST AND EMERY, 17 Hollgarth St., Durham.

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

S.E.S. SERVICE SHEETS for all TV Radio and Tape Recorders, etc. List 1/6 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St. George's Road, Hastings, Sussex.

SERVICE SHEETS, also current and obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London, W12. Phone: SHE 8441.

SERVICE SHEETS

4/- ea., plus postage.

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country, and can supply by return of post.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name: _____

Address: _____

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1
Please supply Service Sheets for the following:

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV

I also require list of Service Sheets at 1/6.

I also require list of Manuals at 1/-. (please delete items not applicable)

I enclose remittance of _____
MAIL ORDERS ONLY

RECEIVERS & COMPONENTS

TRANSISTORS now half price. unmarked but tested packets of 16; unmarked, untested packets of 40; duds suitable as diodes, packets of 80. All packets 10/- each, postage 1/-. Four packets post free C.W.O. K. R. WHISTON (Dept. PWT), New Mills, Stockport.

RATES: 7/6 per line or part thereof average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS

(continued)

SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

A.1. POST FREE BARGAINS. Guaranteed reclaimed valves. Send for full list to Dept. MO/W., A.1. Radio Components, 14 The Borough, Canterbury, Kent.

VALVES, RADIO & TV. New cheap, modern, obsolete. S.A.E. C. MASON, Pagemoss House, Pagemoss Lane, Liverpool, 14.

DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the UK. Line Output Transformers, Frame Output Transformers, Defector Coils for most makes. Official sole suppliers for many set makers. Same day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. For quotes, Day and Night Telephone GIPSY Hill 6166, 126 Hamilton Road, West Norwood, S.E.27.

VHF COMMUNICATION
RECEIVER 1392

15 valve Superhet. Covering 85-155 Mc/s (2-3 metres) Police, Aircraft and Amateur Broadcasts. Power required 240-250 volts at 80mA, 6.3v at 4 amps. Size 19 x 10 x 10in. £6.15.0. Carr. 15/-.

4 VALVE 4 WATT AMPLIFIER

"C" Core transformers. A.C. Mains 110/230 volts 600 ohms or high impedance input. Output 600 ohms. Controls: ON/OFF switch. Gain control. Indicator light. Valve inspection panel. 19 x 7 x 7in. Brand New in makers cartons. £4.5.0. Carr. 12/6.

TRANSMITTER. 1.75-16 Mc/s 3 waveband tuneable, grid modulation using 813. Used complete with all valves, circuit £7.10.0. Carriage 10/-.

MOVING COIL HEADPHONES. BRAND NEW. Chamois padded, complete with jack plug 15/6. Post 2/-.

ROTARY TRANSFORMERS. 12V DC input. 300V DC, 120mA output. note size only 4 1/2 x 2 1/2in. 15/- Post 2/6.

R.C.A. AR88D RECEIVERS. Brand New. £7.5. Carriage 30/-.

POWER UNIT. Type ZE12. Designed for Canadian No. 52 receiver. 52/6. Carr. 5/- All No. 19 set parts available.

Many other bargains. S.A.E. all enquiries.

A. J. THOMPSON

"ELLING LODGE"

CODICOTE, HITCHIN, HERTS.

Phone: CODICOTE 244.

RECEIVERS & COMPONENTS

(continued)

NEW VALVE TESTERS £12. Molineux, Lowfield Heath, Sussex.

TRANSISTORS! Give-away price. NKT124/5 Power Type. 6 for 10/- 2SO17 4W, up to 60mc/s, 5/- each. Post free. G. F. MILWARD 17 Peel Close, Drayton Bassett, Staffs.

R & R RADIO & T V SERVICE

Dept. P.W.
44 MARKET STREET, BACUP, LANCs.
Telephone 405

SALVAGE VALVES Tested before dispatch

6F13	4/6	10P14	5/-	PLS2	3/6	20P4	6/6
6L18	4/6	20P5	6/6	U801	7/6	30P16	5/-
EF80	1/6	30P4	7/-	10P1	1/6	PCL34	5/-
ECX82	3/-	6F15	5/-	20P2	5/6	PCL33	5/-
EC180	3/6	EB91	1/-	30FL1	5/-	PY81	3/6
30F5	5/-	EF85	5/-	PY32	6/-	U301	6/-
PL38	6/-	6/30L4	4/-	6U4GT	5/-	10P13	5/6
PCL40	4/-	20P3	6/-	RF1	2/6	20D1	2/-
PL81	5/-	30PL1	4/-	ECX81	3/-	30P12	5/-
PZ30	5/-	PL36	6/-	EX86	4/-	PY82	5/-
U329	5/-	PCL82	5/-				

Speakers, Ex-TV. 5in. round, 6 x 4in. 3/6; 8in. round, 6/-; post 2/-.

Line Output Transformers available. State set model No.

Turret Tuners, 8/-, post 2/-.

Scan Coils etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

RESISTORS! You can't resist this! 1W, 1W, 2W Polythene wrapped on cards of 10. Mixed values and wattages. £2/10/- per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD. Dept. PW7/9, 126 Hamilton Road, West Norwood, S.E.27. GIPSY Hill 6166.



Receivers, Marconi CR100. 60 kc/s to 30 Mc/s. Crystal filter. B.F.O. two r.f. stages, etc. Good condition and working order. £18/10/- carriage £1. Control Units No. 1 for 52 Set. These contain pair of good quality chamois padded headphones, low impedance, and microphone. Morse key, hand generator, bell, etc. 27/6 carriage 7/6. Siltcon Rectifiers. 1 amp. 70 p.l.v. Only 6d. each, post 3d. any number. American Morse Keys with lead and jack. 4/6, post 1/-. Power Units 230V. A.C. for R1332, P104, or R1392. £2.5.0, carriage 10/-.

(Carriage charges apply to England and Wales only).



FOR SALE

HAMMER FINISH PAINT. The modern finish for all electronic equipment. (Not crackle finish). Just brush it on, no stoving, the effect appears at once and dries in 20 minutes. Blue or pewter 24oz. tins 3/6, 1 pint 7/6, 1 pint 15/-. From radio & model shops or post free from us. Trade Supplied. FINNIGAN SPECIALITY PAINTS (pw). Mickley Sq. Stockfield, Northumberland.

SUPER BREAKDOWN UNIT

Remote Control Unit Type F. New in sealed cartons, containing P.O. Relay 2,000 ohms Resistance, 100 volt Plessey Hand Generator, Telephone Ringing Bell A.C. 8 amp Morse Key on base, 2 D.P. D.T. Key Switches, Double Phone Jack, moulded 5 position 6 pole Yaxley Switch, Induction Coil tapped 1-17-33 ohms, 7 Brass Screw Terminals on panels, plus Resistors, Condensers, Pointer Knobs. All in a handy metal box with hinged lid and side fasteners. Also web carry strap. Size 10 1/2 in. x 10 in. x 7 in., 25/- post free. Or items may be purchased separately. Relay 5/-, Hand Generator 7/6, Bell 5/-, Morse Key 4/6, Key Switches 5/- pair, Double Phone Jack 2/6, Yaxley Switch 2/-, Ind Coil 2/-, Terminals 7 for 2/-, all post free.

Also available Key Switches, 4 pole 2 throw 3/6 each or 3 position D.P. plus D.P. centre off 5/- or rotary switch 6 pole 3 way 3/-.

Bank of 4 Pye Sockets with plugs and leads 5/- set. Ever Ready Batteries, 90 volts plus 4 1/2 volts 4/6 each.

Plessey 2-4-12-25 way plugs and sockets, all 5/- pair.

Jones Plugs and Sockets 4-12-18-24-32 way all 5/- pair.

Special Lightweight 7 in. x 4 in., 3 ohm P.M. Speaker, 6/-.

Metal Frames, suitable for stock, Job Cards. Bins, Crates, 2 1/2 in. x 5 in., 12/6 per 100—£4 per 1,000.

19 in. RACK FITTING CABINET. 34" high by 21" deep with telescopic drawer slides. Louvred sides, back and top. Brand new Swedish make, £4.4.0 only, plus B.R.S. delivery.

ECR Tube with Screen and Base, with ECR 35 data, 25/-.

5U7P Tube with Screen and Base, with data, 30/-.

20ft. Steel Telescopic Mast, 50/-.

COLLARO AUTO CHANGE

3 speed Gramophone Decks
Tested and guaranteed
Post free 50/- each
Brown or Cream

Copper Laminate Board, single or double sided, 5/- per square foot panels, either type 3 1/2, by 4 1/2, 33/-.

High Stab Resistors. 5% 6d., 2% 9d., 1% 1/-, Every six packed in 7-compartment linen finish component box. Unmarked.

Speakers. 3 ohm P.M. 5 in. 5/-, 6 in. 8/-, 7 x 4 in. 7/-, 8 in. 8/-, 10 in. 12/6.

U.K. ONLY

E. R. NICHOLLS

Mail Order and Retail Shop:
46 LOWFIELD ROAD
58 SHAW HEATH, STOCKPORT
CHESHIRE

FOR SALE (continued)

TESTED TRANSISTORS

All new, few equivalent.
OA202

1/- each, Red or White Spots.

2/- each, XA101, XA102, XB103,
OA90, OC430, XA112, XA111.

3/- each, OC44, OC45, OC70,
OC71, OC81, OC81D, OC200,
GET16.

4/- each, AF114, AF115, AF117,
OC170, OC171, SX658, XU611.

5/- each, OC72, OC139, OC140,
OC204, ORP60, BY100, GET8.

10/- each, OC35, OC26, OC28,
GET57, 2SO13. All new, few
equivalent.

ZENER DIODES 4.7 v. to 33
volt 1/4 watt, 3/6 each. 1.5 watt,
5/- each, 7 watt, 6/- each.

Send 3d. stamp for Full
Price List, and Free Equiva-
lent Chart.

B. W. CURSONS

78 BROAD STREET
CANTERBURY, KENT

SURPLUS SWITCHES. Capacitors.
Valves. Transistors. Transformers.
etc. New, very cheap. S.A.E. list.
Rosedene, Eversholt, Bletchley.

MORSE MADE EASY!

The famous RHYTHM RECORDED
COURSE cuts the practice time down
to an absolute minimum!

One student, aged 20, took only 13
DAYS and another, aged 71, took 6
WEEKS to obtain a G.P.O. pass
certificate. If you wish to read Morse
easily and naturally enclose 6d. in
stamps please for full explanatory
booklet.

To GCHS. 45 GREEN LANE,
PURLEY, SURREY

CONDENSER BARGAIN! Miniature
paper condensers, 1 in. x 1 in. Ideal
for transistor sets. .0001, .001, .002,
.005, .02, .04 uF. Your choice 7/8. per
100 or £3 per 1,000. G. F. MILWARD,
17 Peel Close, Drayton Bassett, Staffs.

240 WATT ELECTRIC POWER ANYWHERE

ANYTIME from 12 with CAR BATTERY

with AMERICAN DYNAMOTOR UNIT

Input 12v. output 240/250v. at 150 in 220 watts.
Perfect for television, power tools and all
external AC/DC electrical equipment, gives
wonderful results. Price only £8.95 no cartage.
Send stamped envelope for full illustrated details
to "SCIENTIFIC PRODUCTS, CLEVELY, LANCS."

FOR SALE continued

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN OFFER

Lightweight Pistol Grip handle
40 watt, 240/250v. A.C. Solid
copper bit. Detachable handle
forms cover for iron when not in
use. With 4 1/2 ft. Safety 3-core
flex. Indispensable for
every home handym-
an. A boon to model
makers and a necessity
for every wireless en-
thusiast. Offered to P. & P. 1/-
you at this new amaz-
ing price.

ONLY
9/6

G. H. SERVICE, (Dept. P.W.3)
Lusted Hall Lane, Tatsfield, Kent

SOUND RECORDINGS

A UNIQUE BUY! Recording Tape,
top brand, 5 1/2 in. 1,200ft. 19/6; 7 in.,
2,400ft., D.P. 28/6. P and P. 1/6 per
spool. Bargains in all sizes. S.A.E.
for list. E. C. KINGSLEY AND CO.,
132 Tottenham Court Road, London,
W.1. EUSTON 6500.

RECORDING TAPES

ANOTHER SPECIAL

PURCHASE OF

III-FI RECORDING TAPES

Standard

3 in. x 150 ft.	...	3/-
5 in. x 600 ft.	...	10/-
5 1/2 in. x 900 ft.	...	13/-
7 in. x 1200 ft.	...	15/6

Long Play

5 in. x 900 ft.	...	13/-
5 1/2 in. x 1200 ft.	...	15/6
7 in. x 1800 ft.	...	23/-

Double Play

5 in. x 1200 ft.	...	26/-
5 1/2 in. x 1800 ft.	...	29/6
7 in. x 2400 ft.	...	35/-

Send for Lists, stocks limited

C.W.O. or C.O.D. extra
Please add 1/- for Post

DIAMOND (Mail Order) PRODUCTS

(Dept. PT) MBC/DIA
LONDON, W.C.1

WANTED

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

WANTED VALVES ONLY

Must be new and boxed

Payment by return.

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

WE BUY new valves for cash, large or small quantities, old types or the latest. Send details, quotations by return. **WALTONS WIRELESS STORES**, 15, Church Street, Wolverhampton.

WE BUY new Valves and transistors. Amplifiers, Short-wave Receivers and Components, etc. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

NEW VALVES WANTED

Any type, or quantity

CASH PAID

R.S.T. Valve Mail Order Co.

211A Streatham Road

Mitcham, Surrey

Telephone: MITCHAM 6202

MISCELLANEOUS

ALUMINIUM

Sheet for Radio Chassis and general use. Out to size. Also Brass, Copper, steel, etc. in Sheets, Tubes, Rods, Foils, Sections, etc. Write for **FREE ILLUSTRATED PRICE LIST**. Callers welcome.

SENMOB METALS, Dept. R/6
35 St. Johns Road, Isleworth, Middx.
ISL: 6017

CONVERT ANY TV SET into an oscilloscope. Instructions and diagrams 12/6. **REDMOND**, 26 St John's Road, Hove, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write **NOW** for free leaflet and further details to **C. & S.**, 20 Maude Street, Darlington, Durham. Send 24d. stamp.

EDUCATIONAL

CITY AND COUNTY OF BRISTOL EDUCATION COMMITTEE

BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc. (Eng.), M.I.Mech.E., M.I.Prod.E.

CAREERS IN RADIO AND RADAR

Marine Radio Officers

2-year full-time course for young men aged 16 upwards, leading to 1st and 2nd class P.M.G. Certificates and M.O.T. Radar Maintenance Certificate.

Conversion Course (2nd class to 1st class). R.T. Courses (for Full or Restricted Licence).

Training given on the latest types of Marine and Aircraft Equipment in newly equipped Laboratories at

Aircraft Radio Maintenance Engineers

2-year full-time course for A.R.M.E. Licences, categories A & B.

Courses for Radar Rating in association with the above.

THE SCHOOL OF RADIO AND RADAR

Senior Lecturer: F. E. Barltrop

For details write to

The Registrar, Bristol Technical College, Ashley Down, Bristol 7

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1964/65. Day and Boarding Students. Grants and scholarships available. Stamp for Prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE

with Formulae. Master Mathematics quickly and easily the Understandable Way.

1st lesson
and details
FREE

The Dryden School of
UNDERSTANDABLE MATHEMATICS
11 J. Dryden Chambers, Oxford
St., London W.1.

Name _____

Address _____

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam Home-study Courses in Radio, TV Servicing and Maintenance. R.T.E.B., City and Guilds, etc. Highly informative 120 page Guide—**FREE**. **CHAMBERS COLLEGE** (Dept. 363), 148, Holborn, London, E.C.1.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from the great book, The Principles of TV Receiver Servicing. 10/6 all book houses and radio wholesalers. If not in stock from Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

SITUATIONS VACANT

A.M.I.Mech.E., A.M.I.E.R.E., City & Guilds, G.C.E., etc., brings high pay and security. "No pass—no fee" terms. Over 95% successes. For details of Exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook **FREE**. **B.I.E.T.** (Dept. 242B), London, W.8.

RADIO TECHNICIAN

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician - Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19 £722, at 25 £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997—£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Apply:

RECRUITMENT OFFICER (RT 37)
Government Communication
Headquarters, Oakley, Priors Road,
Cheltenham.

STUDY AT HOME FOR A PROGRESSIVE POST IN RADIO, TV AND ELECTRONICS.

Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs'), R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor. Write for **FREE prospectus** and find out how ICS can help you in your career.

**ICS DEPT. 541, PARKGATE ROAD
LONDON. S.W.11.**

(continued)

PUBLIC APPOINTMENTS

RADIO AND TELEVISION SERVICING

METAL WORK

**CABINETS • CASES
CHASSIS**

MOSS. WATSON

40 Mount Pleasant Street, Oldham,
Lancs. MAIN 9400

METAL WORK. All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.,** Chapman St., Loughborough.

BLIXT



**THE NEW
SOLDERING IRON
FROM SWEDEN**

No fumbling with BLIXT, the one-hand operated soldering iron. The trigger mechanism feeds solder direct to the point where it is required. Your other hand is, therefore, free to hold wires or components in position.

Tel. HIL 0291

COMMISSION AGENTS WANTED

TRADE ENQUIRIES INVITED.

NEW VALVES!


Guaranteed Set Tested

24-HOUR SERVICE

LONDON, N.16

TRANSISTORISED MORSE OSCILLATOR

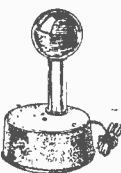Little Newport Street, London, WC2
(off Leicester Square) Tel: 01-673 6578



FLIGHT SENSITIVE SWITCH

KIT of parts, including ORP .12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP .12 including circuit, 10/6 each plus 1/- P. & P.

TRANSISTORS

OC41	7/-	OC44	10/-	GET573	12/8
OC45*	5/-	OC139	12/-	2G110	17/8
OC71	5/-	OC140	19/-	2N458	20/-
OC72*	7/-	OC171	10/8	SB345	7/8
OC73	6/-	OC300	10/8	AC107	14/8
OC75	7/-	OC301	51/-	AF114	11/-
OC76	6/-	OC303	14/-	AF115	10/6
OC77	9/-	GL1114	-	AF116	10/-

*Available in matched pairs.

SERVICE TRADING CO.

47-49 High Street, Kingston on Thames
Tel: KIngston 9450
Personal callers only

9 Little Newport Street, London, WC2
(off Leicester Square) Tel: GERard 0576

TRIPLET 1632 SIGNAL GENERATOR. Handsome well designed instrument, ex U.S.A. Forces. 100 Mc/s. to 120 Mc/s. on fundamentals. 10 directly calibrated ranges. 6 valves, buffer amplifier, well screened ladder, attenuator, variable carrier level, (100µA monitor meter), stabilised H.T. Int. mod., 1Mc/s crystal mixing facilities for crystal check and for use as heterodyne wavemeter. In first-class condition, tested with circuit attenuator, etc. In special portable case, operates from 115v. A.C. 50 c/s (suitable auto transformer for 240v. A.C. operation, 17/6 extra). PRICE ONLY £12. Carr. 10/-.

SILICON RECTIFIERS. Type BY100 (Hn. x Hn.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier. BRAND NEW—not seconds. 7/6.

AR-88 VIBRATOR PACKS. For 6V. operation. Complete with vibrator and OZ4 rectifier. NEW in original cartons. 17/6. P. & P. 2/6.

AR-88 SPARE VALVES. Complete Set of BRAND NEW individually boxed original valves (1-4), 50/-, Plus 2/6 P. & P.

MOVING COIL PHONES. Finest quality Canadian with Chamols ear muffs, lead and jack plug. Noise excluding, supremely comfortable. 22/6, post 1/6. Similar to above but complete with moving coil microphone. 25/-, post 2/6. **LOW IMPEDANCE (D.I.R.-5)** h'phones with attached throat m'phone, 12/6, post 1/6. All these items BRAND NEW.

MAGNETIC COUNTERS (ex-G.P.O.). 4 figures to 9,999. Coils 500µ for 24 V. operation. Tested. (No reset), 5/- each. P. & P. 1/6. SPECIAL OFFER! 10 for 30/-, P. & P. 6/-.

MICRO-AMMETER. 0-500µA. Made by R.C.A., Weston Westinghouse and other famous American manufacturers. Circular 2 1/2 in. flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-, 0-1mA 2 1/2 in. circular flush panel mounting. Resistance 75Ω. 25/-, 0-300V A.C. (moving iron) 2 1/2 in. circular flush panel mounting. 22/6. Post and packing 1/- per meter.

HEAVY DUTY TRANSFORMER. Input 220 to 250 volts A.C. mains (tapped every 5 volts). Output 50V. at 15 amps. A really rugged job, very conservatively rated. Size 7 1/2 x 5 1/2 x 7 in. Weight 28 lbs. ONLY £5.19.6. Carr. 7/6.

CHARLES BRITAIN RADIO LTD., 11 UPPER SAINT MARTINS LANE, LONDON, W.C.2. Temple Bar 0545 Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday.

PADGETTS RADIO STORES
OLD TOWN HALL, KNOWLER HILL,
LIVERSEDGE, YORKS.
Telephone: Cleckheaton 2888

Motors removed from Washing Machines
Fully guaranteed, 230 volt, 1/4 hp., 25/-.
Carriage 8/- B.R.S. Rail quicker 10/6.
Hoover Motors, 1/6 hp. Complete with Drive Pulley, 15/- Carriage 6/-.
Hoover Pump, 7/6. Post 2/6.
Transistor Clearancer, Top Grade. OC71, OC72, OC45, OC200, OC77, all at 3/6 each. Post paid. Diodes, 4/- dozen.
New 12in. Speaker with Built-in Tweeter, 25/6. 3 or 15 ohms. Post free.
New Valves Ex Units. POST FREE.
6X7 1/6 each, doz. 12/-, 6K8 2/6 each, doz. 22/-, 6V6 2/6 each, doz. 22/-, 807 U.S.A. 6/-, PP250 (PX4) 5/-, ACAPEN (PEN4A) 2/6, 6U4 3/-, 6V6GT 4/6, EF81 1/6, EL31 1/6, 6X3 2/-, 5Z4 5/6, 5Y3 4/6, 6X5 4/6, EF50 1/6, 6/- doz. ARP12 1/6, 6 for 5/6, box of 50 15/-, KT68 8/-, ART22 2/-, ART4 2/-, APP37 2/-, AR8 2/-, IT4 2/-.
13 Channel TV Sets, 14in. untested 30/-, carr. 10/-, 17in. untested 50/-, carr. 10/-, Well packed, sent at owner's risk.
TV Tubes, Complete rebuilt and refaced. 12 months guarantee. Sizes up to 17in. Special trade price of 75/-, Carr. and ins. 7/6 B.R.S. Rail 12/6.

RECLAIMED TUBES

Mullard 12 and 14, Mazda CRM141-2 at 17/-, carr. 7/6. Mullard and Mazda 17in., 30/-, 6 months' guarantee.
P.M. Speakers, Guaranteed ex TV Sets, 6in. round, 5x 4in. Rola and Plessey, Philips 6in. round, all at 3/- each. Post 2/-, 6 for 20/-, post paid. Goodmans 7 x 4in., 5/-, post 2/-, 6in. round, 6/-, post 2/-.
Valves Removed from TV Sets. Tested on a Mullard valve Tester and are 100% as new. Three months' unconditional guarantee. POST FREE.
Spares for your 19 Set. 500 micro-amp meter, 5/-, post 1/6.
Complete Set of Tester Valves, 15/-, post free.
Relays type 3000, 1/8, post 1/9, doz. lots 20/-, post paid.
ECL80 2/-, 10P14 5/-, PL33 4/-, ECC82 3/-, 20D1 5/-, PL38 8/-, EY51 2/6, 20L1 5/-, PY80 5/-, EBF90 4/6, 20P3 5/-, PY81 4/-, EB91 9/-, 20P4 5/6, PY82 5/-, EF91 9/-, 20P1 5/-, PCF80 4/6, EL38 6/-, U25 5/-, PCC84 4/6, 6SM7 2/6, U801 8/6, B36 4/-, 6F1 1/-, U281 5/-, N37 5/-, 6F14 5/-, U282 5/-, 6U4 4/-, 6F15 5/-, U329 5/-, 6P25 3/6, 6LD20 5/-, KT36 5/-, 6K25 5/-, 10C2 5/-, PL81 5/-, 6P28 3/-, 10P13 1/-, PL83 5/-, PZ230 5/-, 10P13 5/-, PL83 5/-, 18SBT 8/-.
EP80 1/6, or 10/- per doz. Grade II EP80 for test purposes 4/- per doz.

2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 39/6 complete kit (by post, carriage and packing, 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-King" kits and receivers. Home and Overseas Sales.

JOHNSONS (Radio)
81, Martins Gate, Worcester

COMPONENTS

NEW, TOP QUALITY, GUARANTEED

Moulded valveholders B7G, B9A, Octal	8d.
Air spaced variables, small, 17 pFd, 50 pFd.	
150 pFd, 365 pFd	6/8
Slider switches S/P	1/8
Slow motion drive with dial flange	3/8
3in. dial 0-100 to fit above	2/6
Mains transformers, fully shrouded, 250-0-250	
60 mA, 6.3 v, 3 amp	P. & P. 2/9 15/-
Midget 230 v, 40 mA, 6.3 v, 1 amp P. & P. 2/3 14/6	
Miniature silicon rectifiers 250 v, 500 Ma.	5/6
465 kv/s I.P. Trans. high gain ferrite cores, pre-aligned pair	9/8
4 meg Volume controls D.P. switch	4/-
less switch	2/6
16+16 mFd, 450 v.w. electrolytics	3/9
8 mFd, 350 v.w. small	1/9
Midget smoothing chokes 10h. 60 mA	5/6
4 Pole 3 way switches	3/-
0.01 mFd 400 v.w. tubular	8d.
0.1 mFd 125 v.w.	8d.
0.1 mFd 400 v.w.	10d.
100 pFd, ceramics	3d.
OAST diodes	2/9
8K ohm elite type volume controls with switch, white	3/6
Resin-cored solder	4d. yd.
Co-ax sockets	9d.
Co-ax plugs	1/-
High sensitivity Headphones, 4000 ohms	15/-

B. ELLIS

7 RECTORY FARM ROAD, SOMPTING, SUSSEX

P. & P. charge 1/-. Cash with order, no C.O.D. please. Cash refunded if not completely satisfied.



The PUNCH you need!

HOLE PUNCHES

Instant Type	diameter	6/10. ea.
Screw-up Type	diameter	Toggle switch	8/6 "
"	"	B7G	9/- "
"	"	B8A, B9A	9/6 "
"	"	"	10/2 "
"	"	"	10/8 "
"	"	"	11/8 "
"	"	diameter Int. Octal	13/4 "
"	"	"	16/2 "
"	"	"	18/10 "
"	"	B9G	21/8 "
"	"	"	24/4 "
2 1/2"	"	Meter	33/2 "

Complete Set £9.3.6.

No extra charge for postage and packing in the U.K.

Oliver & Randall Ltd

Dept. 7
7 KELSEY PARK ROAD
BECKENHAM, KENT
Tel.: Beckenham 8262

NEW EDITION

AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR

by A. Douglas

15/- Postage 1/-

SHORT WAVE AMATEUR RADIO, by J. Schaap, 21/-, Postage 1/-.

RADIO & LINE TRANSMISSION, by G. L. Danielson and R. S. Walker. Vol. 1, 21/-, Vol. 2, 22/6. Postage 1/- each.

RADIO, TELEVISION & ELECTRICAL REPAIRS, by R. C. Norris. 50/-, Postage 2/-.

RADIO SERVICING, by A. Marcus. 50/-, Postage 1/6.

CABINET HANDBOOK, by G. A. Briggs. 7/6, Postage 6d.

RADIO VALVE DATA, 7th Ed. Compiled by "WV". 7/6, Postage 10d.

COMPLETE CATALOGUE 1/-

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

★ ★ MANY BARGAINS ★ ★

DUE TO MOVING TO LARGER PREMISES

MAKE 5 DIFFERENT TRANSISTOR RADIOS FOR



35/-

NO EXPERIENCE NECESSARY. NO


Soldering. Only 11 connections for first radio to work. Just look, you get

Giant 4 colour box, 1ft. 2in. x 10 1/2in. x 2 1/2in. containing Radio Book, A.B.C. Plans, Cabinet, Carrying Case, Loudspeaker (alone 17/6) Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud, clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS:** GLORE. Mr. R. O'D. of Londonderry, writes:—“I received your components and I must say that I am very satisfied with them. I have it already set up.” **COMPLETE HOME RADIO COURSE.** Originally 26. **SEND ONLY 35/- plus 2/6 post etc. (C.O.D. 3/- ex.)**

NEW RADIO

ANYONE
CAN BUILD
IN 2-3 HOURS

19/6

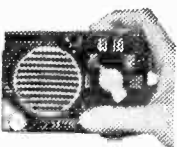

EVEN THE OLDER CHILDREN BUILD THEM!... no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2in. Many Testimonials: M.H. of Bradford, writes:—“I have just completed one of your sets successfully. It is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them.” **Direct from Manufacturers to You. SEND 19/6 plus 1/6 post etc. (C.O.D. 2/6 ex.).**
PARTS AVAILABLE SEPARATELY

AMAZING CIGARETTE

RADIO!

ONLY

18/6



Yes, a perfectly ordinary packet of cigarettes!—but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly-sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file. Mr. D.H. of Huddersfield writes:—“I have fitted the parts in and it is working wonderfully.” **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6 plus 1/6 post, etc. (C.O.D. 2/6 ex.).** (Parts available separately).

READ WHAT SATISFIED CUSTOMERS SAY

R.C. of HARRINGAY writes
Received with thanks Skyrama
... Very pleased. Working
well.

L.S. of LONDON W.8 writes
... given it a good try out
and I am very pleased with
the results.

D.R. of GLASGOW writes
... it is a lovely little thing
and as clear as a bell.

J.W. of BRIGHTON writes
... I have recommended your
radio to many of my friends.


B.M. of HARROGATE writes
... I would like to thank
you ... It is a real bargain.

S.B. of SOMERSET writes
... delighted with this radio
... glad if you could send
one more.

T.F. of STEVENAGE writes
I would just like to say how
pleased my son is with this
radio.

W.H. of MIDDLESEX writes
Thank you for my dear
little radio. It is a real
treasure to me.

MINIATURE SPY CAMERA

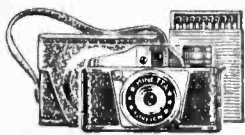

ONLY 19/6 NO MORE

World shattering Purchase by our FOREIGN AGENTS makes this exclusive scoop yours for **ONLY 19/6**. This exciting little 2 speed camera is not a toy but a precision-made photographic instrument in chromed steel and leather with minute multi-Magnifying Lens—each 14mm. film takes 10 pictures—size 1 1/2 x 1 1/2 in.—Only 19/6. P. & P. 1/6 ex. **FREE** Leather Carry-case. Six Rolls of Film.

TRANSISTOR POCKET RADIOS



ONLY 28/6

No More To Pay

**BULK PURCHASE
ENABLES US TO
MAKE THIS FANTASTIC OFFER
—AND WITH
MONEY BACK
GUARANTEE**

The “BAN REMO”... so tuned that it brings the voices of star entertainers and vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months off 1/2 battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6. 2/6 P. & P. C.O.D. 2/6 extra. (Parts can be bought separately.) Limited period—so rush your order before it's too late. **DEMONSTRATIONS DAILY**



THE MINUTE TRANSISTOR RADIO


MIAMI

ONLY 17/6

Unbelievably small—outrageously cheap. You will be amazed at the fine quality of tone and volume of this Great little radio. Only a fantastic 3 1/2 x 2 1/2 x 1 1/2 in., the **MIAMI** will bring you great entertainment for months on an 8d. battery. Simple assembly plan with each set. **ONLY 17/6.** YES 17/6. Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

READY TO PLAY

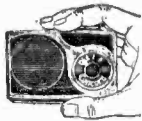**TRANSISTOR RADIO
FULLY TRANSISTORISED
SKYROMA MK. 7.** This latest 1964 model is cheered by experts for its fantastically low price. Built in two-tone case, size 4 1/2 x 2 1/2 x 1 1/2 in. Receives M.W. stations loud and clear. Every radio is fully tested before despatch. Price ready built 25/-, P. & P. 1/6 extra. Free earpiece with set. No more to pay



FOR ONLY 25/-

Fabulous ST. TROPEZ MK. 6

The Sensational Pocket Radio



This fantastic offer will amaze you—the beautifully compact ST. TROPEZ, measuring 4 1/2 x 3 x 1 1/2 in. receives perfectly in bedroom, office or garden—over all medium waves including Luxembourg. Under 1d. per hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan, 25/- (P. & P. 2/6 extra). (Case extra). Parts can be bought separately



AMAZING NEW INVENTION AUTOMATIC CAR LIGHTER

ONLY 10/-

We have been lucky enough to purchase 1,500 only of these fully automatic Car Cigarette Dispenser/Lighters made to sell at about 45/- Retail and ingeniously designed in heavy chromium. Holds packet of cigarettes (any make and size) you reach out with one hand, press a button and a lighted cigarette is in your hand! Can be fitted by anyone in 2-3 minutes. For 6 or 12 volts, full connecting details—only one wire to connect! Each one in own coloured box, brand new and untouched. Only 10/-, add 2/- P. & P. (C.O.D. 2/6 extra).

CONCORD ELECTRONICS

LTD. (Dept. P.W.12) 9 Western Road, Hove, Sussex

RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt
 ● Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● MARTIN AUDIO KITS

High quality Transistor Amplifying Equipment. Following units now available: Input Selector Unit £2.78; Pre-Amplifier with Volume Control £1.17.8; Mixer Unit £3.18.8; Pre-Amplifier with Tone Control £2.23.6; 10 watt Main Amplifier £5.12.8; Power Supply Unit £2.12.0. Fully detailed literature available. H.P. Terms on any combination of units—ask for quotation.

● SPECIAL LOUDSPEAKER BARGAINS

E.M.I. 13 x 8in. Elliptical. 10 watts. 3 ohms. 39/8. P. & P. 2/6. RICHARD ALLAN 12in. 5 watts. 3 ohms. 27/6. P. & P. 2/6.

● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log. 500k. 1 meg. 2 meg. ★ Log/Log. 50k. 250k. 1 meg. 2 meg. ★ Lin/Lin 250k. 500k. 1 meg. 2 meg. All 10/6 each. Postage extra.

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS ALL POST FREE Cash Price Deposit Hire Purchase Mthly/Pmts.

RECORD CHANGERS				
GARRARD AUTOSLIM (Mono PU)	£6.17.6	£1.12.8	6 of	£1
GARRARD AUTOSLIM De-luxe AT6 (Mono PU)	£11. 8.0	£2. 6.0	12 of	16/11
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	£12. 5.4	£2. 9.4	12 of	18/-
B.S.R. UA14 (TCS Mono PU)	£6.15.0	£1.10.0	6 of	£1
B.S.R. UA14 Monarch (TCS Stereo/LP78)	£7.15.0	£1.18.0	6 of	£1.2.0
B.S.R. UA15 (TCS Mono PU)	£7.15.0	£1.18.0	6 of	£1.2.0
B.S.R. UA15 (TCS Stereo/LP78)	£8.15.0	£2. 6.0	6 of	£1.4.0

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

FMT1. £6.12.6; FMT2 (less power), £7.15.0.
 FMT2 (with power), £9.12.6; FMT3 (less power), £9.8.6.
 FMT3 (with power), £11.7.6. Mercury 2, £10.14.6.

Hire Purchase Terms available. Ask for list.

● OUTPUT TRANSFORMERS

GILSON: W0896A, W0896B, 60/6, post 2/6. W0892, 75/-, post 2/9. W0767, 32/8, post 1/6. W0796, 66/-, post 2/6. W1796A, 66/-, post 2/6. W01932, 32/8, post 3/-.
 PARTBRIDGE: P3667, 75/-, post 2/9. P4131, 75/-, post 2/9.
 PARMEKO: P2629, 49/8; P2642 47/3; P2643, 49/8. All plus post 2/9.
 P2641, 30/8, post 2/-; P2623, 16/8, post 2/-; P2632, 43/-, post 4/6.

● MAINS TRANSFORMERS

GILSON: W0741A, 75/-, post 4/-; W0839, 58/8, post 2/9; W0132B, 69/8, post 3/6; W0129B, 69/8, post 3/6; W0156B, 96/-, post 4/6; W01341, Choke, 43/-, post 2/-.
 PARMEKO: P2631, 37/-, post 2/9; P2630, 57/3, post 3/3; P2644, 60/-, post 4/-; P2630, 43/-, post 3/-; P2631, 59/6, post 3/3.

★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £5 minimum of 4/2. Over £5 and under £10, 2/8. Over £10, no charge. Postage extra on CASH order under £5 except where stated. Postage extra on overseas orders irrespective of price.

WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address

Callers welcome by appointment

● SPECIAL OFFER STEREO CARTRIDGES

RONETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and stylus. List 59/4. OUR PRICE 23/6. Post Free.

● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510. Mullard 2-3, Mullard 2 and 3 Valve Pre-amp. Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits or Audio Amplifiers", 9/5. Post free.

● LATEST TEST METERS

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
AVO Model 8 Mark III	£24. 0.0	£4.16.0	12 of £1.15.2
AVO Model 7 Mark II	£21. 0.0	£4. 4.0	12 of £1.10.10
AVO Multimeter Mark 4	£9.10.0	£1.18.0	12 of 14/4
T.M.K. TP10	£23.18.6	£1. 3.6	3 of £1.2.0
T.M.K. TP58	£5.19.6	£1.15.6	3 of £1.11.4
T.M.K. Model 500	£5.19.8	£1.15.6	12 of 13/8
TAYLOR MODEL 127A	£10.10.0	£2. 2.0	12 of 15/8

Full details of any of the above supplied free on request.

The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

● TAPE RECORDING EQUIPMENT

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
COLLARO STUDIO, latest Model, Two track, Bradmatic Heads	£10.19.6	£2. 3.6	12 of 16/4
Four Track, Marriott Heads	£17.17.0	£3.12.0	12 of 26/2

● MARTIN TAPE AMPLIFIER KITS

Tape Amplifiers For Collaro 8311-V 2-Track £11.11.0. 8311-4 V 4-Track £12.12.0.

Tape Pre-Amplifiers For Collaro 8319-CP 2-Track £8.8.0. 8319-4-CP 4-Track £8.8.0.

Drop through assembly for mounting 8319 Pre-amp under Collaro Deck, £1.11.6.

Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier, £5.5.0.

H.P. TERMS available on decks, amp. and cases. Ask for quote

● MULLARD TAPE PRE-AMPLIFIER KIT

We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

● HI-FI LOUDSPEAKERS

GOODMANS: Axlette 8in., £5.5.7; Axlom 10in., £6.5.11; 12in. Axlom 201, £10.17.4; 12in. Axlom 301, £15.4.6; 12in. Axlom 51 Bass, £9.2.8; 12in. Axlom 61 Bass, £14.7.8; Trebas Tweeter, £6.10.2; Cx3000 Crossover unit, £2.0.11.
 WHITELEY: HF1016 10in., £7.7.0; HF1017 10in., £4.12.0; HF816 8in., £8.6.0; TS16 8in., £5.19.6; T10 Tweeter, £4.12.0; T359 Tweeter £1.12.3; Cx3000 Crossover unit, £1.1.3; Cx1500 Crossover unit, £2.2.0. H.P. Terms available on all speakers.

★ HIRE PURCHASE TERMS

Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 6/- in the £. Service charge 5%. minimum charge 10/-. Six months: Deposit 5/- in the £. Service charge 7 1/2%, minimum charge 15/-. Twelve months: Deposit 4/- in the £. Service charge 10%, minimum charge 20/-.

The up-to-the minute data book for all enthusiasts—

PRACTICAL WIRELESS RADIO AND TELEVISION REFERENCE DATA

compiled by J. P. Hawker

Contains full details of colour codes; a comprehensive collection of everyday formulae, e.g., for calculating the values of biasing components, potential dividers, resonance, gain, etc.; aerial dimensions; a quick frequency-wavelength conversion table; radio and television broadcasting stations and frequencies; common symbols and abbreviations; notes on amateur radio and a list of call-sign prefixes; communication receiver I.F.s; mathematical data including logarithm tables; wire and cable data; battery equivalents; and a full and up-to-date listing of valve, transistor and picture tube pin connections, bases, ratings and equivalents, including selected CV types.

96 pages, illustrated, over 62 pages of tables. 10s.6d.

FROM ALL BOOKSELLERS

...or, in case of difficulty, 11s. 6d. by post from George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

NEWNES

FAMOUS FOR THIRTY YEARS for
SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS



H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1964 RANGE

1-Valve model "CX", complete kit, Price 34/6
Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model K, price 77/-

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. T.E.), 44 Old Bond St., London W.1

BBC2 (625 LINE) TV AERIALS



EXTERNAL MAST MOUNTING ARRAYS

9 element 45/-; 11 element 55/-;
14 element 62/6

WALL MOUNTING: with CRANKED ARM. 9 element 60/-; 11 element 67/6; 14 element 75/-. CHIMNEY ARRAYS with LASHINGS. 9 element 72/-; 11 element 80/-; 14 element 87/6. LOFT ARRAYS. 9 element 32/6; 11 element with TILTING ARM & 4 ELEMENT GRID REFLECTOR 62/6; 14 element ditto. 70/-. Co-ax. Plugs, 1/3. Low Loss Co-axial Cable, 1/6 yd.

BBC • ITV • F.M. AERIALS



B.B.C. (BAND D). Telescopic loft 21/-. External S/D 30/-.

I.T.V. (BAND 3). 3 Element loft array 25/-. 5 Element 35/-. Wall mounting. 3 Element 35/-. 5 Element 45/-.

COMBINED B.B.C./I.T.V. Loft 1+3. 41/3; 1+5. 48/9. Wall mounting 1+3. 56/3; 1+5. 63/9. Chimney 1+3. 63/9; 1+5. 71/3.

F.M. (BAND 2). Loft S/D. 12/6. "H". 30/-. 3 Element. 52/6. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes 12/6. C.W.O. or C.O.D. P.P. 3/-. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
3b, Godstone Road, Kenley, Surrey
CRO 2527

LONDON CENTRAL RADIO STORES

INTER-COM TELEPHONES
20-WAY PRESS-BUTTON INTER-COM. TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. 27/15/-.
10-WAY PRESS-BUTTON INTER-COM. TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. 26/15/-.
P.M. MOVING COIL SPEAKERS
5in. 9/6. Min. 3 ohm 10/6. Elliptical 7x4in. 3 ohm 10/6
SUPERIOR TYPE DESK PHONES, black Bakelite cases. Complete with Hand Set. Dial 0-9 and internal bell. 43/7/6.
2-P.O. TELEPHONE TYPE CARBON HAND-SETS 10/6.
8-BANK UNISELECTOR SWITCHES. 25 contacts, alternate wiring 22/15/-, 8 bank half wipe 22/15/-, 6 bank, half wipe, 25 contacts 47/6.

EX-EQUIPMENT: COLLARO

3 speed auto changers, with arm and p.n. Hi-Fidelity Model SC54, also Model R031 A.C. mains. Approx. size 13in. x 14in. Height 7in. 23.

ELECTRICITY SLOT METERS (1/- in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250 v. 10 A. 84/-; 15 A. 94/-; 20 A. 104/-; other amperages available. Reconditioned as new. 2 years' guarantee.

QUARTERLY ELECTRIC CHECK METERS. Reconditioned as new. 200/250 v. 10 A. 42/6; 15 A. 52/6; 20 A. 57/6. Other amperages available. 2 years' guarantee.

23 LISLE ST. LONDON W.C.2

Prices include U.K. carr. GER. 2969
Closed Thursday 1 p.m. Open all day Saturday

FOOTBALL POOL COMPUTER

Novel low-cost circuit for forecasting
Analogue Computer. Multiplication and division by electrical analogue. Simple demonstration of computer principles. Both above circuits for 3/6 post free.
Noughts and Crosses Machine. Full circuit and instructions for our fabulous design 3/6. Cannot be beaten!

Multimeter Kit. 18,000 o.p.v. 25 range kit with Weston 50µA meter, only 65/- (2.5A range 4/- extra). Stamp for details.

Multimeters. Illus. leaflet on request. 7K20A, 1,000 o.p.v., 33/-, post 1/6; EP10K, 10,000 o.p.v., 69/6, post 1/6; EP30K, 30,000 o.p.v., 95/6, post 2/-; EP50K, 50,000 o.p.v., 130/-, post 2/6.

Audio — I.F. — R.F. Oscillator. Simple square wave circuit giving output at audio frequency, and over the whole radio spectrum up to 1.5 Mc/s. Use for rapid "dead" set testing, use for Morse practice etc. Variable amplitude. Basic kit comprises transistors, condensers, resistors, tag strips, pot, switch, knob. Price 10/-, post 1/-, with circuit and instructions.

Precision Wirewound Resistors 1W. 1 ohm to 5K 1% 3/-; to 20K 4/3; 1% add 3d. Your value would to order.

High Stab Resistors. 1W 1% 2/-. Full standard range 10 ohms to 10M plus many special multimeter values.

Annual Hol., Aug. 29th to Sept. 12th

PLANET INSTRUMENT CO.,
25 DOMINION AVENUE, LEEDS 7

A.R.R.L. AMATEURS RADIO HANDBOOK 1964

New Edition 36/-. Postage 2/6.
ABC's of Computers by Lytel. 16/-, postage 1/-.
Know your Oscilloscope by Smith. 20/-, postage 1/-.
Beginners Guide to Electronics by Squires. 15/-, postage 1/-.
Amateur Radio Call Book by R.S.G.B. 4/6, postage 6d.
Radio Valve Data by Wireless World. 7/6, postage 6d.
Guide to Broadcasting Stations by W.W. new edition. 5/-, postage 6d.
Teach Yourself Radio Servicing by Butterworth. 10/6, postage 1/-.
Basic Electronics by Van Valkenburgh in 6 parts. 15/- each or 78/- set of 6, postage 1/- each of 3/- set.

UNIVERSAL BOOK CO.

12 Little Newport Street, London W.C.2
(adjoining Lisle Street)

RADIO BOOKS

TELEVISION & RADAR ENCYC.

Published Price 30/- Book Bargain 9/6
INDUSTRIAL TELEVISION

Published Price 15/- Book Bargain 4/6

STEREO FOR BEGINNERS 8/6

HI-FI FOR BEGINNERS 8/6

SOUND & CINE FOR BEGINNERS 8/6

AUDIO & ACOUSTICS by Briggs 11/6

MORE about Loudspeakers by Briggs 9/6

CABINET Handbook by Briggs 8/6

AT A GLANCE Valve and T.V. Tube equivalents 4/-

OSCILLOSCOPE Book 5/6

USING an Oscilloscope 7/-

OSCILLOSCOPE Equipment 5/6

MULLARD Circuits for Audio Amp. 7/6

MULLARD Ref. Transistor Circuits. 13/6

EXTRA Equipment Tape Recorder 6/6

TRANSISTOR Circuits for Radio 8/-

Control of Models 8/-

SERVICING Transistor Receivers 8/-

ELECTRONIC Novelties 5/6

ELECTRONIC Gadgets 5/6

RADIO Valve Data "Wireless World" 8/6

BEGINNER'S Guide to Radio 8/6

MODERN Transistor Circuits for Beginners 8/-

ABC of Transistors 5/6

ABC of Ultra Sonics 5/6

ABC of Magnetism 5/6

ARC of Missile Guidance 5/6

All books include postage. List S.A.E.

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY

KENT. Tel. HURSTWAY 1818

RES/CAP. BRIDGE 39/6

p. & p. 2/6

Checks all types of resistors, condensers

6 RANGES

Built in 1 hour. Direct reading

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept E)

Raleigh Mews, Raleigh Street, Nottingham

FIRST-CLASS RADIO AND T/V COURSES...

GET A CERTIFICATE!

After brief, intensely interesting study — undertaken at home in your spare time — YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSSES

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
(Dept. 461), 148 HOLBORN
LONDON, E.C.1

Tubes

Carr. & Ins. 12/-

HIGHEST QUALITY—
COMPARE OUR PRICES

	GUARANTEED		NEW TYPES
	6 months	12 Months	
MOST MULLARD			
MAZDA, COSSOR,	12.	£2. 0.0	£3. 0.0
EMITRON, EMI-			
SCOPE, BRIMAR,	14in.	£2.10.0	£3.10.0
FERRANTI TYPES,			
PROCESSED IN	15-17in.	£3. 5.0	£4. 5.0
OUR OWN	21in.	£3.15.0	£5.15.0
FACTORY			
			£6.0.0

★ GUARANTEED VALVES ★

by return of post
THE MOST ATTRACTIVE COMPETITIVE VALUE
LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised

POST	3 MONTHS	FREE TRANSIT IN-
1 Valve 6d., 2-11. 1/-	GUARANTEE	SURANCE. Satisfaction
FREE for 12 or more valves.	In writing with every valve.	or Money back Guarantee on Goods if returned within 14 days.

SATISFACTION GUARANTEED

EKCO L.O.P.T. Unused replacements for Perceps based 1954/77 models, complete with E.H.T. rect. unrepeatable. **39/-**

CO-AX, low loss, 6d. yd., 25 yards, 11/8, 50 yds., 22/-, 100 yds., 42/6. Co-ax Plugs 1/3. Wall outlet boxes 3/6

SPECIAL C.R.T. OFFER
Due to huge Bulk Special Purchase we are offering MW 31/74 Tubes at the unrepeatable price of 29/-, MW 30/74 ditto, 30/-, F.P. 12/6. The above are guaranteed for 6 months.

LOUDSPEAKERS. 3 Ohm Top Makes 84in. **7/6** 7 x 4in. **8/6**

CONNECTING WIRE
P.V.C. Bright colours. Five 25ft. coils only. **4/-**

3 VALVE AMPLIFIERS
Kit of new parts, consisting chassis, mains and output transformers, valves (P61, 6GG6, 6X50) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feedback, back, etc. Truly unusual value at **29/-**

MAINS TRANSFORMERS
Excellent Quality Guaranteed. Upright mounting 250-0-250 V 60 ma., 5d V 3 A (60/2 12/6) **9/6**
Ditto semi-enclosed 9/6.

13 CHANNEL T.V.s
Table Models. Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchase direct from source. They are untested and not guaranteed to be in working order. Carr. etc., 15/-.
12in. **£2.19.0** 14in. **£4.19.0**

LEAK AMPLIFIER SNIPS
Due to a fortunate purchase we are able to make the following unrepeatable offers. All amplifiers have line matching Output Transformers (Transformers to match these Amplifiers to 15Ω Speakers can be supplied at 22/6 each).
TLE/25 WATT (new)..... £15
Note—These Leak Amplifiers all have the added facility of volume and tone controls so that they can be used without a pre-amp. if very high gain is not required.

★ **BULK BARGAINS** ★
12 POTS. Popular values. 5K 4/6
2 Meg. Unused, mixed, pre-set, long sp., switch, etc. **4/6**
CONDENSERS, 25 Micro. Electrolytic. Many popular sizes. List Value £5. Our price **10/-**

100 RESISTORS 6/6
Excellent. Sizes 1/3 watt.

100 CONDENSERS 9/6
Miniature Ceramic Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER £5.

25 TAG STRIPS 4/-
2, 4, 6, 8 way etc. Unused.

100 HI STABS 9/6
1% to 5% 100Ω to 5MΩ.

TRANSISTORS

GUARANTEED TOP QUALITY

Huge reduction. Red Spot standard L.F. type now only **1/6**
White Spot R.F. type..... **2/-**

Mullard Matched Output Kits OC81D and 2-OC81 **12/6**
R.F. Kits (OC44, OC45 (2), 3 transistors. **12/6**

AF 114	8/-	OC44	5/8
AF 115	7/6	OC45	5/8
AF 116	7/6	OC78	5/8
AF 117	7/-	OC81	5/8
AF 127	9/6	OC81D	5/8
OC26	12/6	OC82	8/-
OC38	14/-	OC170	8/6
		OC171	8/6

GERMANIUM DIODES
General Purpose miniature detector. A.V.C., etc. or 6/8 doz. **8d.**

Gold Bonded highest quality. Individually tested. **1/-**
9,6 doz.

SILICON RECTIFIERS
Guaranteed performance. Top Make. Tested 300V working.
100mA **3/9** 250mA **7/6**
(3 for 9/6) (3 for 18/6)

VALVE HOLDERS. B70, 6d. ea., with Screen 8d. ea. BSA 6d. ea., with Screen 8d. ea. Int. Octa. 6d., Mazda Octa. 4d. BSA 6d. (less 15% in dozens).

TURRET TUNERS

Most makes, your choice if available, with valve 16/-, less valves 10/- S.A.E. enquiries.

COSSOR D.B. SCOPE TUNES. Type 09/1 split beam. Ideal for building your own quality oscilloscope whilst stocks last. **55/-**

LINE TRANS.

Huge quantity, most makes at only S.A.E. enquiries. **29/-**

RECTIFIERS. 250 v., 80 mA, 5/-, RM2, 6/8; RM3, 7/6; RM4, 10/6; RM5, 10/6; 14A86, 17/-; 14A97, 19/6; 14A100, 19/6; 16RC1-1-16-1, 7/6; 18RA1-1-16, 6/-; 18RD2-2-8-1, 10/-; 14A1-2-5-2, 17/-; 14RA1-2-5, 20/-.
ELECTRIC MOTORS. AC/DC 3-8 volts. Totally enclosed standard mounting, powerful V pulley, spare brushes, 2in. x 2in. **7/6**

AM/FM RADIOS

Fantastic offer. 7 valves plus 2 diodes. Contemporary Cabinet. Top quality and finish. A.F.C. A.V.C. Absolutely complete. Guaranteed 3 months. **11 gns**

ENQUIRIES WELCOMED

Quantity Prices or Quotes for items not listed. Particularly rare values. **TELEPHONE C.O.D. ORDERS DISPATCHED THE SAME DAY.**

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. 2/- extra). ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

TECHNICAL TRADING CO.

SHOPS RETAIL ONLY
350-352 Fratton Road, Portsmouth (Tel: 22034)
72 East Street, Southampton (Tel: 25851)
ALL MAIL ORDER, RETAIL SHOP AND HLT ROOM
11-12 NORTH ROAD, BRIGHTON. Tel: 67999

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

● OUR STOCKS ARE FAR TO VAST TO ADVERTISE—A CATALOGUE IS, THEREFORE, A MUST ●



MAINS AND BATTERY RECORD AND TAPE DECKS

- All Decks Complete with Cartridges**
- ★ BSR UA14 4-speed Auto ... £5 16 6
 - ★ BSR UA15 4-speed Auto ... £6 19 0
 - ★ Garrard Autoslim Auto. ... £6 10 0
 - ★ Unpluggable Hd. Versn. Auto ... £6 19 6
 - ★ Battery Autoslim ... £8 19 6
 - ★ Stereo Version Auto. ... £7 19 6
 - ★ SRP10 4-speed Single Player ... £5 0 0
 - ★ SRP10 Battery Version ... £5 19 6
 - ★ BSR GU7 4-speed Single Player ... £5 0 0
 - ★ Garrard AT6 with Stereo Cartridge Autochanger ... £10 19 6
 - ★ AT6 Mono ... £10 10 0
 - ★ Collaro 2-track Studio Deck ... £10 10 0
 - ★ Collaro Studio 4-track Deck ... £13 19 6
 - ★ BSR TD2 2-track ... £7 19 6
- P. & P. 3/6 any type above.
- ★ 9 volt Starr, 45 r.p.m. ... 39/6
 - ★ 45 or 33 r.p.m. Starr 9V. ... 92/6
 - ★ 45 r.p.m. Garrard, 6V. ... 35/-
 - ★ 4-speed B.S.R. 9V. ... 5 gns
 - ★ Garrard 9V. 2-speed, 2-track Tape Deck with cassette ... £11 15 0
- P. & P. 2/6 any of above.



MULTI-METERS

Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateurs designers, repair shops, all domestic uses. Full details and specification in our catalogue.

PT34	1 Kohm/volt	39/6
MI	2	£2 9 6
THL33	2	(illus.) £3 15 0
EP10K	10	79/6
ITI-2	20	82/6
TP55	20	£5 19 6
EP30K	30	£5 10 0
500	30	£8 19 6
EP50K	50	£8 10 6
EP100K	100	£9 19 6

★ Leather Cases available.

RECORD/REPLAY/ERASE TAPE HEADS



Marriot Type R/RP3 1/2 track record/replay head and Mullard type TS erase head with mounting post. Bargain offer 15/- pair. P.P. 9d.

★ TRANSISTOR POCKET RADIOS

Ready to use, complete with Battery. Leather Case. Earphone. P.P. 2/- any type. Fully Guaranteed.

6-Transistor De Luxe ...	£9/6
7-Transistor Zephyr ...	79/6
6-Transistor MW/LW	£5.19.6

All Parts in Stock for the following PW Designs.

- PW-6 Superhet.
- PW S.W. Converter.
- PW Beginners SW2.
- PW Transistor Inverter.
- PW Mains Power Pack.
- PW Build and Learn Series.

Send S.A.E. with list of parts required for quotation.

CATALOGUE

Now 86 pages fully detailed and illustrated with hundreds of new items and bargains. PRICE 2/6. Post Paid.

TRANSISTOR PORTABLE TRANSCEIVERS

9-transistor Portable Trans-receivers. Supplied complete with leather cases, batteries, aerials, etc. in presentation case. Range up to 5 miles in favourable conditions. Sizes 6 1/2 x 3 x 1 1/2 inches. Superhet crystal controlled on transmit and receive. Price £25 Per Pair. P.P. 3/6.

TRANSISTOR TRANSCEIVER

3-transistor crystal controlled version of above. Range up to 1/2 mile. Price £8.19.6 Per Pair. P.P. 2/6.

A SELECTION FROM OUR STOCKS

- See Catalogue for full details.
- Sinclair Micro-6 (to build) ... 59/6
 - Sinclair TR 750 amp. (to build) ... 39/6
 - Sinclair Micro Injector (to build) ... 27/6
 - PP3 9 volt Battery Eliminator ... 18/6
 - Tape Jack Tuner ... 29/6
 - 10-Watt Horn Tweeter ... 29/6
 - 20-Watt Super Tweeter ... 69/6
 - Two-channel Mixer ... 15/-
 - 1 to 200 Mc/s. F/str. Meter ... 69/6
 - 2-Watt 4-transistor 9 v. 3 ohm ... 49/6
 - 5-hole Chassis Punch Kit ... 49/6
 - Headphones 2K ohm 12/6; 4K ohm Stereo Headphones 8 + 8 ohm 3 gns.
 - Stereo Stethoscope Headset 8 + 8 ohm ... 25/-
 - Resistor Substitution Box ... 37/6
 - Crystal Mono Stethoscope Headset ... 10/6
 - Magnetic Mono Stethoscope Headset ... 12/6
 - Transistor Signal Injector ... 39/6
 - Fully Disappearing Car Aerial ... 35/-
 - Test Lead Kit with Pouch ... 8/6
 - Capacitor Substitution Box ... 29/6
 - De Luxe Stereo Headsets with junction box ... £6
 - 4-channel transistor mixer ... 55/-
 - ★ 3-Transistor MW Superhet tuner ... 67/6
 - ★ 4-Transistor Superhet MW/SW Tuner ... £7.9.6
 - Transistor Telephone Amplifier ... 65/-

FM VHF TUNING HEART

Printed circuit construction. RF stage and osc./mixer stage, fully tunable 85 to 105 Mc/s. Completely screened. Requires UCC85 (8/6). Brand new in maker's cartons 15/- P.P. 1/-.

Supplied with circuit.

MULLARD POT CORES

LA1	12/6	LA5	17/6	LA45	15/-
LA2	15/-	LA6	22/6	LA2503	15/-
LA3	19/6	LA9	17/6	LA2504	15/-
LA4	12/6	LA10	17/6	LA2505	17/6

30 watt Soldering Iron 14/6. P.P. 1/-.

- 2-Track Demagnetiser ... 29/6
- 2K ohm lin. diam. mag mic. ... 15/-
- Antex 15 watt min. soldering Iron 29/6
- Earphones mag. or crystal ... 5/-
- Telephone Recording attachment... 12/6
- Crystal Guitar contact mic. ... 12/6
- ★ 7-Transistor Record Player or tuner amplifier with treble/bass and vol. controls, £5.19.6.
- ★ 4-Transistor 2 watt amplifiers. Kit, 39/6. P.P. 1/6. Built 49/6. P.P. 1/6.

RECORDING TAPE

5in. 600ft., 12/6; 5in. 900ft., 15/-; 7in. 1,200ft., 18/6; 7in. 1,800ft., 25/-; 7in. 2,400ft., 27/6. Excellent quality.

● SCOTCH BOY TAPE. 3 1/2 in., 300ft. L.P. complete with spare spool. 5/6. P.P. 9d.

BUILD A QUALITY TAPE RECORDER




- ★ 6 Valve Printed Circuit designs. 2-track or 4-track units. 11 gns.
- 2-track, 12 gns. 4-track, 12 gns.
- ★ Collaro Studio Decks. 2-track 10 gns. P.P. 3/6. 4-track £14. P.P. 3/6.
- ★ Portable cabinets with Speakers. 5 gns. P.P. 3/6.

Complete Systems

2-track £26, P.P. 8/6. 4-track £30, P.P. 8/6.

● Complete in Every Detail ● Leaflet on request also on amplifiers to use decks with existing hi-fi equipment.

NOMBREX TEST EQUIPMENT

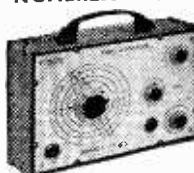

All transistor portable units supplied with full instructions.

Leaflets on Request.

- ★ 150 Kc/s to 350 Mc/s generator. RF Mod., AF. 8 ranges. Leads batteries, instructions, £9.10.0.
 - ★ Resistance/Capacitance Bridge, £8.5.0.
 - ★ Transistorised Power Supply, £6.10.0.
 - ★ Audio Generator, £16.15.0.
 - ★ Inductance Bridge, £18.
- Fully Guaranteed.



CRYSTAL MICROPHONES

- Acos 39-1 Stick Microphone 32/6
- Acos 60-1 Stick Microphone 27/6
- Acos 40 Deck Microphone... 15/-
- Acos 45 Hand Microphone 19/6
- Lapel/Hand Microphone... 12/6
- 100C Stick with Stand... 39/6
- BM3 Stick with Stand... 49/6
- Lapel/Hand Magnetic... 8/6

QUALITY MICROPHONES

Large range of Dynamic and crystal microphones in stock. (See new Catalogue for full range.)

QUARTZ CRYSTALS

100 kc/s 15/-; 500 kc/s 15/-; 455 kc/s 12/6; 456 kc/s 15/-; 27.255 Mc/s 15/-; Twin Crystal, 1 Mc/s, and 100 kc/s 22/6. Over 800 frequencies in stock.

Henry's Radio Ltd.

PADddington 1008/9
303 EDGWARE RD., LONDON W.2
Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

Practical Wireless

BLUEPRINT SERVICE

ALL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier	}	*	5/-
The PW Signal Generator			
The Savoy VHF Tuner	}	*	5/-
The Mayfair Pre-amplifier			
The Berkeley Loudspeaker Enclosure	}	*	5/-
The Luxembourg Tuner			
The PW Troubadour	}	*	7/6
The PW Everest Tuner			
The PW Britannic Two	}	*	6/-
The PW Mercury Six			
The PW Regency	}	*	5/-
The PW International Short Wave Two			

RECEIVERS

The Tutor *	3/-
The Citizen *	5/-
Junior Crystal Set	PW94	2/-
Dual-wave Crystal Diode	PW95	2/6
Modern One-valver	PW96	2/6
All-dry Three	PW97	3/6
Modern Two-valver	PW98	3/6
A.C. Band-pass Three	PW99	4/-
A.C. Coronet-4	PW100	4/-
A.C./D.C. Coronet	PW101	4/-
The PW Pocket Superhet	5/-

MISCELLANEOUS

The PW 3-speed Autogram	8/-
The PW Monophonic Electric Organ	8/-
The PW Roadfarer *	5/-
The PT Band III TV converter	1/6
The Mini-amp *	5/-
The PT Olympic *	7/6
The PT Multimeter *	5/-

SOME EARLIER DESIGNS

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave	PW30a	2/6
Midget Short Wave Two	PW38a	2/6
Simple S.W. One-valver	PW88	2/6
Pyramid One-valver	PW93	2/6
BBC Special One-valver	AW387	2/6
A One-valver for America	AW429	2/6
Short-Wave World Beater	AW436	3/6
Standard Four Valve S.W.	WM383	3/6
Enthusiast's Power Amplifier	WM387	3/6
Standard Four Valve	WM391	3/6
Listener's 5-Watt Amplifier	WM392	3/6

QUERY COUPON

This coupon is available until 7th October, 1964, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, OCTOBER, 1964.

WE ARE THE SPECIALISTS *Transistor Equipment & Components*


86 PAGE CATALOGUE
PRICE 2/6. Post Paid.

TRANSISTOR HIGH FIDELITY EQUIPMENT FOR MAINS OR BATTERY OPERATION 10 WATTS MONO OR 20 WATTS STEREO

● MONO FULL FUNCTION PREAMPLIFIER/ CONTROL UNIT


PRICE **£5.10.0** P.P. 2/-.

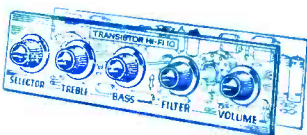- ★ Fully detailed. Dark brown and gold front panel plate 8/6.



For use with transistor power amplifiers as below or valve amplifiers—hum free—high sensitivity—8 inputs between 1.5 mV. and 300 mV., with full equalisation. For all pick-ups—microphones, tuners—tape replay. Separate treble and bass with cut and boost—4 position low pass filter. Volume, 40 c/s. and 20 kc/s., etc. Output 250 mV. Overall size 9 x 2½ x 2in. Battery operated (2½ mA.) or from power supply. Signal to noise ratio 70 dB at 10 watts with power amplifier. Supplied built and ready to use.

● INTEGRATED STEREO PREAMPLIFIER

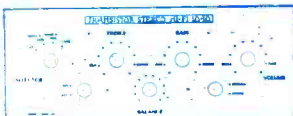

PRICE **£10.19.6** P.P. 3/6.

Two channel version of above with addition of balance and mono/stereo controls. Overall size 9 x 3½ x 1½in. deep. Designed to feed two 10 watt power amplifiers as below. Supplied built and ready to use.

- ★ Dark brown and gold front panel plate 12/6.

● MULTI-INPUT PREAMPLIFIER


For use with the transistor power amplifier. A simplified version of the full function preamp. 8 inputs from 1.5 mV. to 300 mV. Input selector, tone and volume controls. Size 5 x 2½ x 2in.

PRICE **65/-** P.P. 1/6.



- ★ Dark brown and gold front panel plate, 6/6.

● 10 WATT POWER AMPLIFIERS

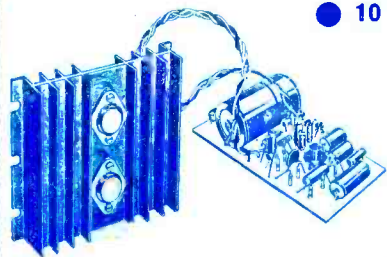

★ 15 ohm 10 watt
40 volt supply.
£5.19.6
p.p. 2/6.

★ 3 ohm 10 watt
24 volt supply.
£5.10.0
p.p. 2/6.

Direct coupled transformerless design. Sensitivity 100 mV. from 10 K ohm source for 10 watts output. Response 1 dB, 40 c/s. to 20 c/s. 0.25% total distortion at 10 watts. Push-pull class B output. 60 dB feedback. Two versions available for 3/4 ohm and 15 16 ohm output. Battery or mains supply operation. For use with mono or stereo pre-amplifiers as above. Supplied built and ready to use. 3 ohm version suitable for use on 12 volts and also 5, 8 and 15 ohm speakers.

● MAINS POWER PACKS

- PS245 For single amplifier, 24 volt **59/6**
PS402 For single amplifier, 40 volt **59/6**
PS24 For two amplifiers, 24 volt **69/6**
PS40 For two amplifiers, 40 volt **69/6**

DETAILS WITH
CIRCUITS OF
ABOVE UNITS
ON REQUEST
(TRADE SUPPLIED)

● VHF FM TRANSISTOR TUNER

- 5-Transistor.
- High Sensitivity.
- 4 Diodes.
- Full coverage 87 to 105 Mc/s.
- AFC and AVC.
- Up to 1 volt output.

Printed circuit design of high sensitivity and quality.

Output for valve or transistor amplifiers.

Size 3½ x 2½ x 4in. Simplified building instructions. All parts sold separately.

Detailed Circuit Book on Request.



TOTAL COST **£7.19.6** P.P. 2/6.

(Gold sprayed cabinet assembly 20/- extra).

"CONVAIR"



PUSH-BUTTON
MW/LW
PORTABLE/
CAR RADIO

Total Cost of
ALL Parts
£7.19.6

P.P. 3/6.

Batteries 6/- extra.

Size 10 x 7 x 3½in.

ALL PARTS SOLD
SEPARATELY

Leaflet on Request.

★ The easiest to
build—the best
performance—
realistic price.

- New printed circuit 6-Transistor superhet design. Over 700mW push-pull output.

- Push-button selection of MW and LW with full tuning on both wavebands.

- A new design with amazing performance at a realistic price.

- New attractively designed portable cabinet with horizontal tuning and all stations marked. Colours Red or Blue with White.

MINIGRAM TRANSISTOR PORTABLE RECORD PLAYER



- Made by well-known British manufacturer. Features ready built 4-transistor printed circuit 1 watt amplifier, elliptical speaker and volume control. Low current. Starr, constant speed 45 r.p.m. turntable with crystal pick-up. Strong moulded two colour cabinet with handle. Plays anywhere on long life 9 volt battery. Requires less than

half an hour's work to connect up using ready built units and easy instructions.

TOTAL COST **79/6** P.P. 5/- (Battery 3/9).

Or amplifier with volume control and 5 x 3-inch Speaker, 4-Transistor, 35/-, P.P. 2/-.
9 volt Starr Player with Pick-up **39/6**, P.P. 2/6. And Two-Tone Case 5/-, P.P. 2/-.

HENRY'S RADIO LTD.

PADDINGTON 1008/9.
303 EDGWARE ROAD, LONDON W.2.
(Open Monday to Saturday all day 9 a.m. to 6 p.m. Half-day Thursday 1 p.m.)

PLEASE TURN TO INSIDE PAGE

● ANYTHING TO DO WITH TRANSISTORS CONTACT US WITHOUT DELAY ●