

PRACTICAL WIRELESS

JULY
1969

310

AC/DC METER



ALSO INSIDE
integrated circuit
AF SIGNAL INJECTOR

ADCOLA

PRODUCTS LIMITED
(Registered Trade Mark)

THE RELIABLE SOLDERING INSTRUMENT!



SEND COUPON FOR LATEST LEAFLET

ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD
LONDON SW4

NAME

ADDRESS

PW171

17in.—£11.10.0
19in. SLIMLINE
SOBELL—24 Gns.

TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS

**FREE ILLUSTRATED
LIST OF TELEVISIONS**


17"–19"–21"–23"
WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

**TWO-YEAR GUARANTEED
REGUNNED TUBES**

70° and 90° 14in.—£9/6, 17in.—£9/6, 21in.—
£9/6, 110° 17in., 19in. and 21in.—£9/6,
23° (not bonded)—£19/6. Exchanged bowls.
Carr. 10/6.



COCKTAIL/STEREOGRAM CABINET 19 gns.

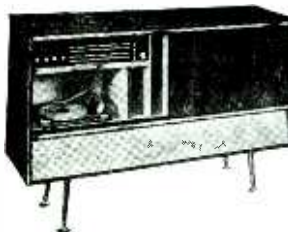

Polished walnut veneer with elegant
glass fronted cocktail compartment,
padded. Position for two 10in. ellipti-
cal speakers. Record storage
space. Height 35½in., width 52½in.,
depth 14½in. Legs 1 gn. extra.

Speakers 6/6: 2"–75Ω. 2½"–35Ω.
P. & P. 2/6. **Acos Mics.** 35/- Stand-
ard: Stick Mic. 2 gns. P. & P. 3/6.
Asstd. Condensers: 10/- for 50.
P. & P. 7/6. **Asstd. Resistors:** 10/-
for 50. P. & P. 4/6. **Asstd. Controls:**
10/- for 25. P. & P. 7/6. **Transistors:**
Mullard matched output kit 9/-
OC81D–2 OC81's. P. & P. FREE.

Ferrite Rods 3/6: 6", 8" x ¾" complete with LW/MW Coils. P. & P. FREE.
TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9½" x 6½" x 3½"
P. & P. 4/6. Similar cases in plastic 7/6.

RECORD PLAYER CABINETS 49/6. Cloth covered, size 16½" x 14½" x 8". Takes
any modern autochanger. P. & P. 7/6.

SINGLE PLAYER CABINETS 19/6. P. & P. 7/6.

STRIP LIGHT TUBES 3/9 each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal
for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1.
P. & P. free.

DUKE & CO. (LONDON) LTD.


621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

PRINTED CIRCUIT KIT

**BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with
PARTS and TRANSISTORS from your SPARES BOX**

CONTENTS: (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Match-
box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist. Solvent.
(6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*.
(9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential
Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS.
A very comprehensive selection of circuits to suit everyone's requirements and
constructional ability. Many recently developed very efficient designs published
for the first time, including 10 new circuits.

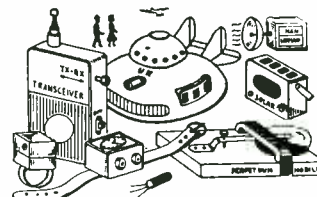

**EXPERIMENTER'S
PRINTED CIRCUIT KIT**

8/6

Postage & Pack. 1/6 (UK)

Commonwealth:

SURFACE MAIL 2/-

AIR MAIL 8/-

Australia, New Zealand
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler
detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio
Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double
Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with
self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio.
The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
(10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12)
Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or
bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Inter-
com. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal.
Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor
Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator.
(25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant
Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop
Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less
Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo
Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone
"Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39)
Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all
52 Radio, Electronic and Photoelectric Projects Assembled.

Lasky's Radio

LASKY'S RADIO ESTABLISHED OVER
36
YEARS

TMK Model PL-436

20,000 O.P.V. Multimeter for the amateur or professional. Features mirror scale and wood grain finish front panel. SPEC.: DC/V ranges: 0-6, 3, 12, 30, 120, 600V at 20K/O.P.V. AC/V ranges: 3, 30, 120, 600V at 5K/O.P.V. DC current: 50µA, 0-6, 60, 600mA. Resistance: 10K, 100K, 1M and 10M ohms end scale (65, 650, 6.5K and 65K ohms centre scale). Decibels: -20 to +57dB in four ranges. Operates on 2x1.5V U7 type batteries. Size: 5½ x 4½ x 2½in.



LASKY'S PRICE £7.19.6 Post 5/-

TTC Model C-1000


A really tiny 1,000 O.P.V. pocket multi-tester with "big" meter performance. Precision 2 jewel meter movement. Hand calibrated to ±3% accuracy on full scale of DC ranges, 4% on AC ranges. 2½in. square meter. SPECIFICATIONS: AC/V ranges: 0-10, 50, 250, 1,000V at 1K/O.P.V. AC/V ranges: 0-10, 50, 250, 100V at 1K/O.P.V. DC current: 0-1-100mA. Resistance: 0-150K/ohms (3,000 ohms centre scale). Decibels: -10 to +22dB. Operated on one penlight cell. Two colour buff/green case—size only 3½ x 2½ x 1½in. Click stop range selection switch. Ohms zero adjustment. Complete with test leads, battery and instructions with circuit data.



LASKY'S PRICE 39/6 Post 2/6

TTC Model C-1051

A completely new design 20,000 O.P.V. pocket multimeter with mirror scale and built in thermal protection circuit. Exceptionally large easy to read meter with D'Arsonval movement. Colour coded scales. Single positive click-in, recessed selection switch for all ranges. Ohms zero adjustment. Range spec. AC volts: 0-6-30-300-1200V at 10K/ohms/V. DC volts: 0-3-15-150-300-1.2KV at 20K/ohms/V. Resistance: 0-60K-6megs DC current: 0-60µA-300mA. Decibels: -20dB to +17dB. Hand calibration gives extremely high standard of accuracy on all ranges. Uses one 1½V penlight battery. Strong impact resistant plastic cabinet—size only 4½ x 3½ x 1½in. Two colour buff/green finish. Complete with test leads and battery. Original list price 52s.

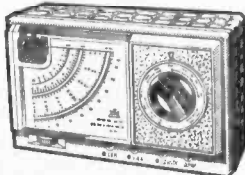

LASKY'S PRICE 75/- Post 2/6 **JUST ARRIVED** Model C-1052 3000 O.P.V. meter. Similar appearance to 10051. **PRICE £5.19.6.** Free.

LASKY'S CLEAR PLASTIC PANEL METERS

Precision made in Japan by HIOKI. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 Post on each. Quotes for quantities.

Type KR-52 3 x 2½in. (illustrated)

1mA	38/6	50µA	56/-
5mA	38/6	1mA 8 meter	38/6
100mA	38/6	100µA	52/6
300 V	35/-	500µA	45/-

Type MK-38A 1½in. square

1mA	28/6
5mA	27/6
100mA	27/6
300V	27/6
50µA	37/6
1mA 8 meter	28/6
100µA	37/6
500µA	28/6

Type MK-65A 3in. square


1mA	38/6	50µA	59/6
5mA	38/-	1mA 8 meter	38/6
100mA	38/-	100µA	52/6
300 V	38/-	500µA	42/-

Type MK-45A 2in. square

1mA	28/6
5mA	28/6
100mA	28/6
300 V	28/6
50 μ A	49/6
1mA 8 meter	32/6
100 μ A	42/6
500 μ A	35/-
Type KR-65 3½ x 3in.	
1mA	38/6
5mA	37/6
100mA	38/6
300 V	38/-
50 μ A	59/6
1 mA 8 meter	42/-
100 μ A	56/-
500 μ A	48/-



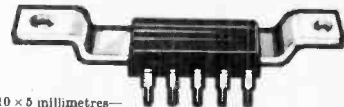ANOTHER EXCLUSIVE FIRST PRESENTING THE IC-403 INTEGRATED CIRCUIT AMPLIFIER MODULE AVAILABLE NOW!



These tiny modules—size only 26 x 10 x 5 millimetres—represent the most amazing breakthrough in circuit design since the introduction of the transistor. The actual circuit—no bigger than a pin-head—is encapsulated in solid plastic fused with the heatsink and connecting pins to make an almost indestructible unit. The IC-403 is an integrated power and pre-amplifier requiring only the addition of tone and volume controls, power source and speaker to form a complete audio amplifier of 3W output. Originally developed for computer and space projects—there are many applications for this unique device, wherever high efficiency and ultra compact size is required, i.e. miniature P.A. and audio amplifiers, intercoms, electronic organs, tape recorders etc. etc.

SPECIFICATION (ratings at 20°C): Output power typically 3W from 250mV input. Frequency response 20Hz to 80KHz ±3dB. Power amp. distortion 0.3% (at 1W, 400Hz). Pre-amp. gain 24dB. Power amp. gain 26dB. Max. operating voltage 21V. Min. operating load 7.5 ohms. Noise level -75dB. Pre-amp. input imp. 2m/ohms. 50w Pre-amp. and power amp. D.C. input current 50µA.


THE IC-403 IS AVAILABLE FROM STOCK EXCLUSIVELY FROM LASKY'S—COMPLETE WITH INSTRUCTION DATA AND SUGGESTED CIRCUIT APPLICATIONS.

LASKY'S PRICE ONLY 52/6 Post 2/6

NEW FANTAVOX TRC-2

SOLID STATE COMPACT CASSETTE RECORDER

A new Lasky's STAR BARGAIN this beautifully made compact cassette recorder and play back machine offers tremendous performance and value. **BRIEF SPEC:** 6 transistor and 1 thermister circuit Constant speed capstan drive system. AC bias recording. PM magnet erase. 2½in. PM Dynamic speaker. Economical operation on 4 x 1.5V (U-2 type) batteries. **SPECIAL FEATURES:** Absolutely foolproof operation. Piano key controls. Powerful volume with recessed control. Handsome impact resistant cabinet finished in black with satin aluminium and ivory trim. Size 9½ x 5½ x 2½in. Jack sockets for remote control microphone, earpiece and external 6V battery pack (or AC adaptor). **COMPLETE WITH** Remote control Dynamic microphone, earpiece, removable carrying strap, batteries, full instructions and three C-60BX cassettes.

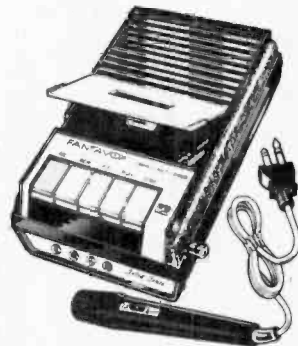

LASKY'S PRICE £17.10.0 POST 5/-

'OVERTURE' BUDGET PRICED CASSETTES

High quality cassettes from the U.S.A.
C.60-10/6 C.90-15/- C.120-20/- Special 6-C.60-59/6 Post Free
Post 1/- each. 4 and over Post Free. Special quotes for quantities.

GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL FREE
16 colour pages in large 16 x 11½in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test Equipment.
Send 1/- for post only and inclusion on our regular mailing list.

Branches

207 EDGWARE ROAD, LONDON, W.2

Open all day, 9 a.m.—6 p.m. Monday to Saturday

33 TOTTENHAM CT. RD., LONDON, W.1

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4

Open all day Thursday, early closing 1 p.m. Saturday

Tel.: 01-723 3271

Tel.: 01-636 2605

Tel.: 01-353 2833

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1

Open all day, 9 a.m.—6 p.m. Monday to Saturday

Tel.: 01-580 2573

118 EDGWARE ROAD, LONDON, W.2

Open all day Saturday, early closing 1 p.m. Thursday

Tel.: 01-723 9789

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

STEP UP YOUR EARNINGS

IT TELLS YOU ALL ABOUT
—Installing domestic
wiring, regulations,
equipment, testing, cables
and faults, meters and
switchgear, lighting,
water heating, space
heating, cookers,
refrigeration, public
address equipment
— in fact everything
you need to add to your
income, to really advance
in your work.

WITH PRACTICAL ELECTRICAL ENGINEERING

You can have this handsomely-bound library of facts, vital theory and day-to-day practices sent to your home to examine free of charge. It will help you understand the many branches of the vast electrical industry from installation work, Equipment, Instruments, Motors and Machines, Repair work, Maintenance and Operation right through to the Generation and Distribution of electricity. And, to make the 2,350 pages of absorbing text crystal clear there are over 2,000 "action" photos and explanatory drawings.

LEADING EXPERTS EXPLAIN IN DETAIL
Written by 87 experts, this PRACTICAL library is planned to give you the knowledge which would normally take a lifetime to acquire.

YOU RECEIVE 4 VOLUMES strongly bound in Grey Morocco, containing 2,352 pages of instructive information on latest practice; 2,100 Photographs, Diagrams, Working Drawings, 24 Data Sheets in colour, 12 Quick-reference Blueprint Charts, each in the large size of 16½ in. x 11½ in. **NUCLEAR POWER STATIONS BOOKLET.**

FREE GIFT. Newnes Electrical Pocket Book. Nearly 400 pages with 258 illustrations, diagrams, tables. (Value 10/6d)

Sent to you by post on 7 days

FREE TRIAL



To: Buckingham Press Ltd., 18-19 Warren Street, London, W.1
Please send PRACTICAL ELECTRICAL ENGINEERING without obligation to buy if you accept my application. I will return the books in 8 days or post—
Tick (✓) here ☐ Full cash price of £16, or
☐ 16/- deposit and 16 monthly payments of 20/-.
If you are under 21 your father must fill up the coupon.

Full Name.....
(Block letters)
Address.....
County.....
Occupation.....
Signature.....
Subscription Price £16.16.0. PEE/4001

Please tick (✓) here
The address on left is
My/our property ☐
Rented ☐
unfurnished ☐
Furnished accom ☐
Temporary ☐
address ☐
If none of the above
please answer here

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!


SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6. DAF96, DF96, DK96, DL96, 4 for 26/-.

OZ4 4/6	20F2 13/6	DK96 7/-	EL41 10/6	PEN44 12/6	UCC84 7/9
1A7GT 7/6	20P3 11/9	DL35 5/-	EL84 4/9	PEN38C15/-	UCC85 8/9
1H5GT 7/6	20P4 18/6	DL92 5/9	EL90 5/-	PFL20012/6	UCF80 8/3
1N6GT 7/6	25L6GT 5/-	DL94 6/-	EM80 5/9	PL36 9/9	UCH42 9/9
185 4/6	25U4GT11/6	DL96 7/-	EM81 6/9	PL31 7/9	UCH81 6/9
1T4 2/9	30C15 18/-	DY86 5/9	EM84 6/9	PL82 7/-	UCL82 7/3
384 5/9	30C17 16/-	EABCO8 6/6	EM87 7/6	PL83 7/-	UCL83 11/6
3V4 6/-	30C18 8/6	EAF42 8/9	EY81 7/8	PL84 6/6	UF41 9/9
5U4G 4/6	30F5 16/-	EB91 2/3	EZ40 7/6	PL500 13/-	UF80 7/-
5Y3GT 5/9	30FL1 13/9	EB93 8/6	EZ41 7/6	PL504 13/6	UF85 6/9
5Z4G 7/6	30FL12 14/6	EB41 8/8	EZ50 4/6	PL506 23/6	UF89 6/9
6/30L2 12/6	30FL14 12/6	EBF80 6/9	EZ81 4/9	PL89 14/6	UL41 10/6
6AL5 2/3	30L1 6/6	EBF89 6/3	GZ32 8/9	PM84 7/9	UL44 20/-
6AM6 3/6	30L15 14/-	ECC81 3/9	KT32 5/-	PX25 10/6	UL84 7/-
6AQ5 4/9	30L17 15/6	ECC82 4/9	KT61 8/9	PY31 5/6	UM84 7/6
6AT6 4/-	30P4 12/-	ECC83 7/-	KT66 16/-	PY32 10/-	UY41 7/-
6BA6 4/6	30P12 13/9	ECC84 5/6	ME140015/-	PY33 10/-	UY85 5/9
6BE6 4/9	30P19 12/9	ECC85 5/9	N78 14/9	PY82 6/3	VP43 10/-
6BJ6 7/-	30PL1 13/9	ECC804 12/6	PABCO 7/-	PY83 5/9	VP182121/-
6BW6 13/-	30PL13 15/6	ECC80 7/-	PABCO 7/-	PY88 6/3	Z77 3/6
6F13 3/6	30PL14 15/6	ECC82 6/9	PC88 10/3	PY800 7/6	Transistors
6F14 9/-	35L6GT 8/-	ECH35 6/-	PC86 8/6	PY801 6/9	AC107 3/6
6F23 14/3	35V4 4/6	ECH42 10/6	PC97 8/6	R19 6/6	AC127 2/6
6K7G 8/6	88ZAGT 5/-	ECH81 5/9	PC900 8/6	R20 12/6	AD140 7/6
6K8G 4/3	6083 12/6	ECH84 7/6	PCC84 6/6	TH21C 9/9	AF102 13/-
6L18 6/-	AC/VP210/-	ECL80 6/9	PCC85 6/6	U25 12/-	AF116 3/6
6V6GT 9/6	AZ31 9/-	ECL82 6/9	PCC88 9/9	U26 12/-	AF17 3/3
6X4 4/3	B729 12/6	ECL83 9/-	PCC89 10/6	U47 13/6	AF124 7/6
6X5GT 5/6	CCH35 10/-	ECL85 8/8	PCC189 11/6	U49 13/6	AF125 8/6
7B6 10/9	CL38 13/6	EF37A 6/6	PCF80 6/9	U52 4/6	AF128 7/-
7B7 7/-	CY31 6/9	EF39 4/9	PCF82 6/6	U75 4/3	AF127 3/6
7C6 6/9	DAC32 7/3	EF41 9/6	PCF86 9/6	U91 12/6	OC26 5/9
7X4 6/6	DAF91 4/3	EF80 4/9	PCF800 13/6	U301 13/6	OC44 2/3
10F1 15/-	DAF96 6/6	EF85 6/-	PCF801 6/9	U301 13/6	OC45 2/3
10F13 16/6	DF33 7/9	EF86 6/3	PCF802 6/6	UABC80 6/6	OC71 2/3
12A18 2/9	DF91 2/9	EF89 5/3	PCF805 8/6	UAF42 9/6	OC72 2/3
12AT7 3/9	DF96 6/-	EF91 3/6	PCF808 12/-	UB41 6/6	OC75 2/6
12AUG 4/9	DH77 4/-	EF183 6/-	PCL82 7/-	UBC41 7/6	OC81 2/3
12AU7 4/9	DH81 10/9	EF184 5/6	PCL83 9/-	UBC81 7/6	OC81D 2/3
12AX7 4/9	DK32 7/9	EH90 6/6	PCL84 7/6	UBF80 6/-	OC82 2/3
12CKGT 7/-	DK91 8/9	EL33 8/9	PCL85 9/9	UBF89 6/9	OC82D 2/3
19BG6G17/6	DK92 9/3	EL34 9/6	PCL86 8/6	UC92 5/-	OC170 2/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

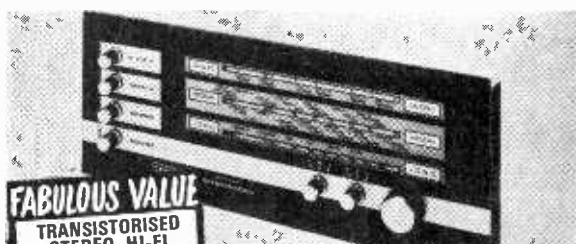Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Sereade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer. Advanced solid state amplifier only 4½" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.


EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED
Only 28 Gns. + P&P 17/6
H.P. terms available. Dep. £9.16.0 & 12 monthly payments of 36/9 (Total H.P. £31.17.0).
Send £10.13.6 today.
Amplifier available separately at only 17 Gns.

FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL" FULLY TRANSISTORISED STEREOGRAPHIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price ONLY 10 Watts Total output 34½ GNS.17/6
17 Transistors & 10 diodes
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
H.P. available £12.1.6 dep. plus 18 monthly payments of 32/- (Total H.P. £40.17.0).

Send £12.19.0 today.

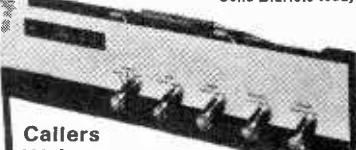

Callers Welcome

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name.....
Address.....
LEWIS radio
100 CHASE SIDE, SOUTHGATE, DEP. P789
LONDON, N.14. TELEPHONE PAL 3733/9666

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1

Tel: 01-636 3451




COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-

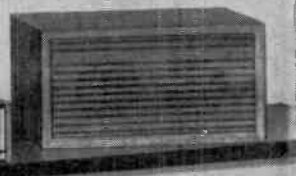

The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor Amplifier has an output of 5 watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12" x 5 1/2" x 3 1/2" high (Amplifier available separately if required £14.19.6. Carr. 7/6).

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dale, Wharfedale, Goodmans, Goldring, Shure, etc. etc.

GARRARD RECORD UNITS

1025 Stereo/Mono cart.	£7.19.6	Teak Plinth with perspex cover as above £5.10.0. Carr. 6/6 extra.
2025 Stereo/Mono cart.	£8.19.6	
3000 with 9TAHCD Carriage 7/6 extra	£9.19.6	
AT60 MKII less cart.	£13.19.6	
SP25 MKII less cart.	£11.19.6	

AP75 less cart.	£19.0.0	Teak Plinth with perspex cover £7.10.0. Carr. 7/6 ex. SL95 less cart. £38.10.0. Carriage 10/- extra.
SL75 less cart.	£29.0.0	
SL95 less cart.	£38.10.0.	

GOLDRING RECORD UNITS

GL68 less cart.	£22.7.0.
GL75 less cart.	£35.15.5.

Carriage 10/- extra.

PICK-UP CARTRIDGES AT MONEY SAVING PRICES!

GOLDRING G800 (Stereo)	£9.19.6
B & O SP1 (Stereo)	£5. 0.0
PICKERING V16/AC2 (Stereo)	£25.10.0
SONOTONE 97AHC/Diamond (Stereo)	£25.10.0
AC08 GP91/18C (Mono compatible)	£1.13.5
AC08 GP93-1 (Stereo)	£2. 8.7
AC08 GP94 (Stereo)	£2.14.8
B & R X3M (Mono compatible)	£1.16.5
B & R X3H (Mono compatible)	£1.16.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 101 (Stereo)	£1.16.0

All complete with mounting brackets and instructions
Post and Packing 1/6 each

SPECIAL OFFER OF SHURE STEREO CARTRIDGES Look at our special prices!

M3D	List £8.10.6.	Premier Price £6.19.6
M44-6	List £14.9.1.	Premier Price £11.11.0
M44C	List £12.19.5.	Premier Price £10.10.0
M48E	List £17.9.4.	Premier Price £13.19.6
M55E	List £20.15.1.	Premier Price £16.19.6
M75-6	List £17.8.4.	Premier Price £13.19.6
M75E	List £25.18.10.	Premier Price £21.0.0

Post and Packing 1/6 each

"PREMIER" TAPE CASSETTES



C60 (60 min.)	10/6
C90 (90 min.)	15/-
C120 (120 min.)	20/-

P. & P. 1/-



CASSETTE HEAD CLEANER
Removes unwanted deposits from delicate tape heads. Fits all cassette recorders.
P. & P. 1/-
15/-




HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8ohm impedance. Complete with 6ft. lead and stereo jack plug.
59/6 P. & P. 5/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low Imp. 25/- P. & P. 2/-.
MONO STETHOSCOPE SET Low Imp. 10/6 P. & P. 2/-.

"PREMIER" SPEAKER SYSTEM

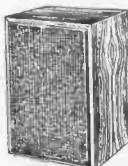Specially designed oiled teak cabinet with vynair front. Size 12 1/2" high, 7 1/2" wide, 6 1/2" deep. Fitted 6 1/2" EM1 Sohn Bass speaker with rolled surround and matching 3" E.M.I. tweeter. Fully lagged.
£7.19.6 Carr. 7/6



MULTI TESTERS

MODEL D14. A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltage in three ranges of 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. Size only: 3 1/2" x 2 1/4" x 1 1/4". Complete with battery, test leads and instructions.
49/6 P. & P. 2/6.



POCKET SIZE MODEL. With wide-angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 18 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50 uA-5 mA-250 mA D.C. 0-6000 ohms-6 megohms, 10u uf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions.
£4.19.6 P. & P. 3/6.

WELLER SOLDERING TOOLS



"Expert" Solder Gun. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant shut heat. 100/140 watt. 240 volt A.C. 67/6 P. & P. 2/-.
"Markman" Soldering Iron. Lightweight, conventional 3/16" pencil bit. Ideal for regular bench use and all those jobs around the home. 25 watts. 240 volt A.C. 31/6 P. & P. 2/-.

MONO GRAM AMPLIFIER

2 1/2 watts output. Uses EL84 valve, double wound mains transformer. Ideal for use with any record deck. Volume/ on/off and tone controls on flying leads. Output impedance 3 ohms. Size overall 5 1/2" w. x 5 1/2" d. x 3" h. A.C. 200/240V. ONLY 49/6. P. & P. 5/-.


JULIETTE NA.5018 5 BAND 18 TRANSISTOR MAINS/BATTERY RADIO

Covers AM 540-1600Kcs. Marine 1.6-4Mc/s. FM 88-108Mc/s. VHF 108-134Mc/s. PB 148-174Mc/s. Ferrite bar aerial for AM/MB. Telescopic aerial for FM/VHF/PB. 4" P.M. Speaker. Operates on AC 250v. or D.C. by four 1.5v. batteries. Size: 9 1/2" x 5 1/2" x 3 1/2".
PREMIER 33 GNS. P. & P. 10/-.



TWO STATION TRANSISTOR INTERCOMS.

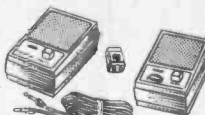Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc.
49/6 P. & P. 4/-.



FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire 27.19.6 P. & P. 3/6.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/6	DT6 5 1/2" 1800' POLYESTER	23/6
TT3 3" 450' POLYESTER	7/6	TT6 5 1/2" 2400' POLYESTER	37/6
DT3 3 1/2" 600' POLYESTER	11/6	SP7 7" 1200' POLYESTER	12/6
SP5 5" 600' P.V.C.	8/6	LP7 7" 1800' P.V.C.	15/-
LP5 5" 900' P.V.C.	10/-	DT7 7" 2400' POLYESTER	25/-
DT5 5 1/2" 1200' POLYESTER	15/-	TT7 7" 3800' POLYESTER	50/-
LP6 5 1/2" 1200' P.V.C.	12/6		

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/6. TAPE CASES 5", 5 1/2", 7" 2/6.
Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/- (3 reels and over Post Free).



RACAL RA-17

First ministry release of these world famous communication receivers. Frequency range 500 kc/s-30 Mc/s. Available in excellent condition, fully tested and guaranteed. £150. Carr. 40/-.

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. \$5.19.8. Carr. 7/6. Or brand new with accessories. \$7.19.8. Carr. 7/6.

CLASS D WAVEMETERS No. 2

Crystal controlled, 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. \$12.10.0. Carr. 30/-.



MARCONI CT/44/TF956

AF Absorption Wattmeter
1 μ Watt to 6 watts.
\$20. Carr. 10/-.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω . Operation 200/250V. A.C. Supplied in perfect order. \$12.10.0. Carr. 10/-.



AVOMETERS

Supplied in excellent condition, fully tested and checked. Complete with prods, leads and instructions. Model 47A \$9.10.0. P. & P. 7/6.

SOLARTRON CD-1016 OSCILLOSCOPE

Double beam. D.C. To 5 Mc/s. Excellent condition. \$55 each. Carr. 20/-.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airme. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporated precision dial, level meter, precision attenuator 1 μ V-10mV. Operation from 12 volt D.C. or 0/110/250/250 volt A.C. Size 12 x 8 1/2 x 9 in. Supplied in brand new condition complete with all connectors fully tested. \$45. Carr. 20/-.

GEARED MAINS MOTORS

Paralux type SD19 230/250V. A.C. Reversible. 30 r.p.m. 40 lb./ins. Complete with capacitor. Excellent condition. 99/6. Carr. 10/-.

SINCLAIR EQUIPMENT



Z12 12 watt amplifier, 89/6 P24 Power Supply Unit 89/6 Stereo 25 Preamp. \$9.19.8 Q14 Speakers \$7.19.8 Micromatic Radio Kit 49/6. Built 59/6.

SPECIAL OFFER

Two Z12 Amps., P24 Power Supply, Stereo 25 Preamplifier, \$29, or with two Q14 speakers, \$37.

NEW SINCLAIR 2000 SYSTEM

35 watt Integrated Amplifier, \$29. Carr. 5/- Self-powered FM Tuner, \$25. Carr. 5/-.

ECHO HS-606 STEREO HEADPHONES




Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6

13 gns.

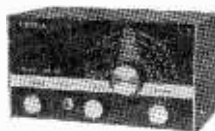

TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 8SB-CW $\bullet$ ANL $\bullet$ Variable BFO $\bullet$ 8 meter $\bullet$ Sep. bandspread dial $\bullet$ IF 455 Kc/s $\bullet$ Audio output 1.5 W. $\bullet$ Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10 in. With instruction manual and service data. \$42.10.0. carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally \$5.19.6. OUR PRICE \$3.15.0 if purchased with above receiver.

TRIO JR-500SE 10-80 METRE AMATEUR COMMUNICATION RECEIVER IN STOCK £69

HAMMARLUND SP600JX COMMUNICATION RECEIVER

High quality professional dual conversion communication receivers available for the first time in this country at a reasonable price. Frequency range 840 Kc/s-54 Mc/s. in 6 bands variable tuning or 6 channel crystal controlled. 2.5 watt output into 600 ohms. Input 110/230V. A.C. 20 valve circuit incorporating: Xtal filter B.F.O. A.N.L. Xtal calibrator, 8 meter etc. Size 19 x 12 x 22 in. (List \$220). Offered in excellent condition, fully tested and checked. \$100 each.




LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



10 transistors, 8 diodes, 1HF music power, 30W at 8 Ω . Response 30-20,000 $\pm$ 2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16 Ω . Separate L and R. volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 x 3 9/16 x 7 13/16 in. Operation 115/230V. A.C. \$28. Carriage 7/6.


MARCONI TEST EQUIPMENT

EX-MILITARY RECONDITIONED. TF.144G STANDARD SIGNAL GENERATORS, 85 Kc/s-25 Mc/s, \$25. Carr. 30/- TF.885 VIDEO OSCILLATOR 0-5 Mc/s \$45 Carr. 30/- TF.195M BEAT FREQUENCY OSCILLATOR 0-40 Kc/s. 200/250V. A.C. \$20 Carr. 30/- TF.142E Distortion Factor Meter, \$50 Carr. 20/- All above offered in excellent condition, fully tested and checked. TF.1100 VALVE VOLTMETER, Brand New, \$50. TF.1267 TRANSMISSION TEST SET, Brand New, \$75. TF.1371 Wide Band Millivolt Meter, Brand New, \$50.

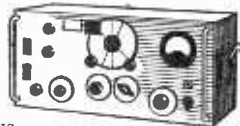


MULTIMETERS for EVERY purpose!

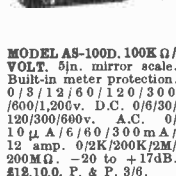LAFAYETTE DE-LUXE 100K Ω /VOLT "LAB TESTER" Giant 8 1/2 in. scale. Built-in meter protection 0/5/10/20/50/100/250/500V A.C. 0/1000V D.C. 0/3/10/50/250/500 μ A/10/100/500mA/2.5/10A. 1K/10K/100K/10M/10M Ω . -10 to 49.4dB. \$18.10.0. P. & P. 5/-.




MODEL AS-100D. 100K Ω /VOLT. 5 1/2 in. mirror scale. Built-in meter protection. 0/1.2/3/6/12/30/300/600/1200V. D.C. 0/6/30/120/300/600V. A.C. 0/10 μ A/6/60/300mA/12 amp. 0/2K/200K/2M/200M Ω . -20 to +17dB. \$12.10.0. P. & P. 3/6.

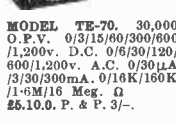MODEL TE-90 50,000 O.P.V. mirror scale overload protection 0/3/12/60/300/600/1200V. D.C. 0/6/30/120/300/600mA. D.C. 0/3/6/60/600mA. D.C. 16K/160K/1.6/16Meg Ω . -20 to +63dB. \$7.10.0. P. & P. 3/-.



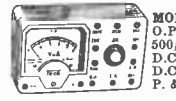MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1200V. D.C. 0/6/30/120/300/600mA. A.C. 0/30 μ A/3/30/300mA. 0/16K/160K/1.6/16 Meg Ω . \$5.10.0. P. & P. 3/-.



MODEL PT-34. 1,000 O.P.V. 0/10/50/250/500/1000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K Ω . 39/6. P. & P. 1/6.




TE-900 20,000 Ω /VOLT GIANT MULTIMETER mirror scale and overload protection. 6 1/2 in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V. A.C. 0/25/125/5/10/50/250/1,000/5,000V. D.C. 0/50 μ A/10/100/500mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. \$15. P. & P. 5/-.




LAFAYETTE 57 Range Super 50k Ω /volt Multimeter. D.C. volts 12 mV -1000V. D.C. volts 1.5V -1000V. A.C. current 25 μ A-10 amp Ohms 0-10meg Ω D.C. -20 to +81dB. Overload protection. \$12.10.0. Carr. 3/6.



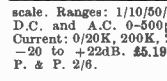PROFESSIONAL LAB. TYPE MULTIMETER. Automatic overload protection. mirror scale. Ranges: 1/10/50/250/500/1,000 volts. D.C. and A.C. 0-500 μ A, 10mA, 250mA. Current: 0/20K, 200K, 2 megohm. Decibels: -20 to +22dB. \$5.19.6. P. & P. 2/6.



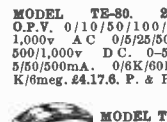MODEL TE-80. 20,000 O.P.V. 0/10/50/100/500/1,000V. A.C. 0/5/25/50/250/500/1,000V. D.C. 0-50 μ A, 5/50/500mA. 0/6K/60K/600K/6Meg Ω . \$4.17.0. P. & P. 3/-.



MODEL TE-12 20,000 O.P.V. 0/10/50/100/500/1,000/5,000/10,000V. D.C. 0/5/30/120/600/1,200V. A.C. 0/60 μ A/6/60/600mA. 0/6K/600K/6Meg/60 Meg Ω . 50pF. 0-2mPd. \$5.19.6. P. & P. 3/6.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth. 2 CFS-1 mHz. Input imp 2 meg Ω 25 pF. Illuminated scale. 2 in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240V. a.c. Supplied brand new with handbook. \$22.10.0. Carr. 10/-.



FIELD TELEPHONES TYPE 1

Generator ringing, metal cases. Operates from two 1.5V batteries (not supplied). Excellent condition. \$4.10.0 per pair. Carr. 10/-.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0.1/0.03/1/3/13/130/100/300V. 12 N.B. 400-1.2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17.10.0. Carr. 5/-.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150 W. \$12.6. P. & P. 3/6.
300 W. \$2.7.6. P. & P. 3/6.
500 W. \$3.10.0. P. & P. 6/6.
1,000 W. \$5.10.0. P. & P. 7/6.
1,500 W. \$8.10.0. P. & P. 8/6.
7,500 W. \$16.10.0. P. & P. 20/-.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine 20cps to 200 Kc/s on 4 bands. Square: 20cps to 30Kc/s. Output impedance 5,000 ohms. 200/240V. A.C. Supplied brand new and guaranteed with instruction manual and leads, \$16.10.0. Carr. 7/6.



TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ω range (0-1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0-05dB. Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new \$27.10.0. P. & P. 5/-.



TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. 7/6. Size 140 x 215 x 170 mm.



TY75 AUDIO SIGNAL GENERATOR

Sine Wave 20 CFS-200 Kc/s. Square Wave 20 CFS-30 Kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Brand new with instructions. \$18. Carr. 7/6. Size 210 x 150 x 120 mm.



Full range of all components - valves semiconductor - test equipment receivers - hi-fi equipment - all at discount prices.

G. W. SMITH & CO (RADIO) LTD.
Also see oppo. page

NEW CATALOGUE

Nearly 200 pages giving full details of a comprehensive range of COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT. Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices.

Free Discount Coupons Value 10/-

SEND NOW—ONLY 7/6 P&P

GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS

SRP22 Mono	£6.10.0	*8P25 MK II	£11.19.6
SRP22 Stereo	£6.19.6	*8L25	£11.18.6
*1025 Mono	£7.10.0	A70 MK II	£12.10.0
*1025 Stereo	£7.15.0	*A70 MK II	£13.10.0
*2025 Stereo	£7.19.6	*8L65	£14.14.0
*2025 T/C		AP75	£19.0.0
Mono/Stereo	£8.17.6	401	£28.7.6
*3000 Stereo	£9.19.6	8L75	£29.0.0
		8L95	£25.0.0

Carriage/insurance 7/6 extra any model. WB4 Bases £3.19.6. Perspex covers £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carr. 5/-. Full range of Garrard accessories available.



TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5-5 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.

ADMIRALTY B.40 RECEIVERS


Released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 500 Kc/s. Incorporates 2 R.F. and 3 I.F. stages, band-pass filter, noise limiter, crystal controlled B.F.O., callibrator. O/F output, output for phones. Operation 150/230 volt A.C. Size 18 1/2 x 13 1/2 x 16in. Weight 14 lbs. Offered in good working condition. £22.10.0. Carr. 30/-. With circuit diagrams. Also available B.41 L.F. version of above. 15 Kc/s-700 Kc/s. £17.10.0. Carr. 30/-.



Offered in good working condition. £22.10.0. Carr. 30/-. With circuit diagrams. Also available B.41 L.F. version of above. 15 Kc/s-700 Kc/s. £17.10.0. Carr. 30/-.

R209 MK II COMMUNICATION RECEIVER

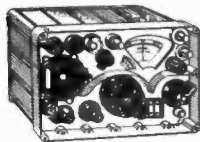11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £16.0.0. Carr. 20/-.




ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. VM.76 VALVE VOLTMETER. R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 100V with accuracy of +2% D.C. range 300 MV to 1 KV. A.C. range 300 MV to 30 V RMS. Resistance 0-2-500 MΩ. Price £72. VM.78 A.C. MILLIVOLT METER. Transistorised 1 MV-300 V. Frequency 1 c/s to 1 Mc/s. Price £55. VM.79 UHF MILLIVOLT METER. Transistorised. A.C. range 10 MV-3 V. D.C. current range 0.1μA-3 MA. Resistance 1 ohm-10 megohms. Price £125. H1B AUDIO SIGNAL GENERATOR. 15 c/s-50 Kc/s. sine or square wave. Price £30. J1B AUDIO SIGNAL GENERATOR. 15 c/s-50 Kc/s. Price £20. J2B AUDIO SIGNAL GENERATOR. As per J1B except fitted with output meter. Price £35. TT15 TRANSISTOR TESTER. £37.10.0. Carriage 10/- per item.

Brand new and boxed in original sealed cartons. VM.76 VALVE VOLTMETER. R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 100V with accuracy of +2% D.C. range 300 MV to 1 KV. A.C. range 300 MV to 30 V RMS. Resistance 0-2-500 MΩ. Price £72. VM.78 A.C. MILLIVOLT METER. Transistorised 1 MV-300 V. Frequency 1 c/s to 1 Mc/s. Price £55. VM.79 UHF MILLIVOLT METER. Transistorised. A.C. range 10 MV-3 V. D.C. current range 0.1μA-3 MA. Resistance 1 ohm-10 megohms. Price £125. H1B AUDIO SIGNAL GENERATOR. 15 c/s-50 Kc/s. sine or square wave. Price £30. J1B AUDIO SIGNAL GENERATOR. 15 c/s-50 Kc/s. Price £20. J2B AUDIO SIGNAL GENERATOR. As per J1B except fitted with output meter. Price £35. TT15 TRANSISTOR TESTER. £37.10.0. Carriage 10/- per item.

SOLARTRON MONITOR OSCILLOSCOPE TYPE 101

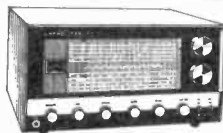An extremely high quality oscilloscope with time base of 10μs/sec to 20m/sec. Internal Y amplifier. Separate mains power supply 200/250V. Supplied in excellent condition with cables, probe, etc., as received from Ministry. £8.19.6, carriage 30/-.



LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-.



Variable Voltage TRANSFORMERS

Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-250 volts. Bulk quantities available. 1 amp. - £5.10.0; 2.5 amp. - £6.15.0; 5 amp. - £9.15.0; 8 amp. - £14.10.0; 10 amp. - £18.10.0; 12 amp. - £21.0.0; 20 amp. - £37.0.0.



CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Type MR 38P. 1 1/2 in. square fronts.

500-0-500μA	25/-	50mA	25/-	150V. D.C.	25/-
1mA	25/-	100mA	25/-	300V. D.C.	25/-
1-0-1mA	25/-	150mA	25/-	500V. D.C.	25/-
2mA	25/-	200mA	25/-	750V. D.C.	25/-
5mA	25/-	300mA	25/-	15V. A.C.	25/-
10mA	25/-	500mA	25/-	50V. A.C.	25/-
750mA	25/-	50V. D.C.	25/-	100V. A.C.	25/-
1 amp	25/-	10V. D.C.	25/-	500V. A.C.	25/-
2 amp	25/-	20V. D.C.	25/-	8 meter ImA	25/-
5 amp	25/-	100V. D.C.	25/-	VU meter	38/8
20mA	25/-				

Postage Extra. Larger sizes available—send for lists.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11 MΩ. L. 1μH-111 HENRY. C. 8 ranges ±1%. 1.11 MΩ. 1.11 HENRY. 8 ranges -2%. C. 10pF ±1110 MFD. 6 ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 1/2 in. £20. P. & P. 6/-.

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-. Additional probes available: R.F. 35/-, H.V. 42/8.



AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.

3in. 225ft. L.P. acetate	3/6
3 1/2in. 600ft. T.P. mylar	10/-
5in. 600ft. std. plastic	8/8
5in. 900ft. L.P. acetate	10/-
5in. 1,200ft. D.P. mylar	15/-
5 1/2in. 1,200ft. L.P. acetate	12/6
5 1/2in. 1,200ft. L.P. mylar	16/-
5 1/2in. 1,800ft. D.P. mylar	32/8
5 1/2in. 2,400ft. T.P. mylar	39/8
7in. 1,200ft. std. acetate	12/6
7in. 1,800ft. L.P. acetate	15/-
7in. 1,800ft. L.P. mylar	20/-
7in. 2,400ft. D.P. mylar	25/-
7in. 3,600ft. T.P. mylar	45/-

Postage 2/- Over £3 post paid.

RECORDING HEADS

Reuter j-track. As fitted to Collaro Mk. IV and Studio Decks. High imp. record playback low imp. erase. Brand new 19/6 pair. CORMOCORD j-track heads. High imp. record/playback 65/- Low imp. erase 20/- MARRIOTT j-track heads. High imp. record/playback 65/- Low imp. erase 20/- Post extra.

★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 1/4 x 9 1/4 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.



TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 51 x 51 x 3 1/2 in. Complete with instructions and leads. £7.19.6. P. & P. 4/-.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec: A: 0-7-0-9867. B: 5-200. Ico: 0-50 microamps 0-5mA. Resistance for diode 200Ω-1MΩ. Supplied complete with instructions, battery and lead. £6.19.6. P. & P. 2/6.



TE-23RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-250 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instructions. £15.0.0. P. & P. 7/6. S.A.E. for details.



ARF-100 COMBINED AF-RD SIGNAL GENERATOR

A.F. SINE WAVE 20-200,000 c/s. Square wave 20-30,000 c/s. O/P. HIGH IMP. 21V. P/P 600Ω 3-8V. P/P. TF 100 Kc/s-300 Mc/s. Variable R.F. attenuation Int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £30.0.0. Carr. 7/6.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF 2000 mFd 2 ohms 200 megohms. Also checks impedance, turns ratio, insulation, 200/260V. A.C. Brand New £17.16.0 Carr. 7/6.



NOW OPEN IN EDGWARE ROAD

Our new walk around shop is now open at 311 Edgware Road fully stocked with all Hi-Fi, Communication and Test Equipment. Call into your nearest shop—Edgware Road for all Equipment—Lisle Street for all Equipment and Components.

G.W. SMITH & CO (RADIO) LIMITED

3 and 34, LISLE STREET, LEICESTER SQ., LONDON, W.C.2 01-437 8204
311, EDGWARE RD., LONDON, W.2 01-262 0387
(ALL MAIL ORDERS TO:- 3, LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2)

OPEN 9 a.m. to 6 p.m. every day Monday to Saturday (Edgware Road 1 day Thurs.) Trade supplied.

MARTIN

IS HIGH FIDELITY

plus

ADD-ON-ABILITY
THRILLING POWER
DEPENDABILITY
GENUINE ECONOMY

How would you like to start with a simple amplifier, say, and add to it until it became a fully stereo twenty watt amplifier with FM tuner and facilities to take the most sensitive low output pickups ever made? With Martin Audiokits it's easy, for with these superbly engineered all-transistor prefabricated units, success is built in from the start and you build to your own preferred plan. IT'S A MONEY SAVING SCHEME, TOO.

Details from: **MARTIN ELECTRONICS LTD.**, 155 High St., Brentford, Middlesex. ISLeworth 1161

● Trade enquiries invited.

To MARTIN ELECTRONICS, 155, High Street, Brentford, Middlesex.

I have not had your leaflets before. Please send them on
AMPLIFIERS ☐ FM TUNER ☐ RECORDAKITS ☐
(Tick as required)

NAME
ADDRESS
PW7

F.A.L.

Phase 32

*You must
hear this
superb
unit*



**15 + 15
WATT
HIGH
FIDELITY
OUTPUT**

SOLID STATE STEREO AMPLIFIER

Recommended
Retail Price **ONLY 35 Gns.**

- ★ *Excellent performance*
- ★ *High grade components and transistors*
- ★ *Impressive technical specification*
- ★ *Attractive appearance*
- ★ *Modest cost*


Housed in Teak veneered Cabinet,
Switched selection of Mic., Mag-
netic P.U., Ceramic P.U., Radio
Tuner, Tape Rec.

Available from your local Hi-Fi Dealer

Wholesale and Retail enquiries to Manufacturers

FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13

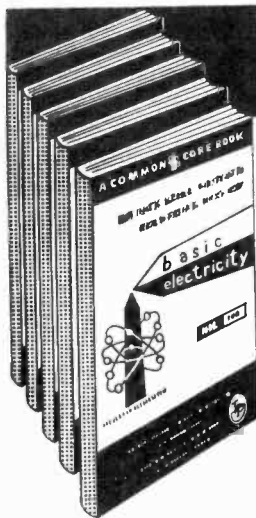**SEND S.A.E.
FOR FULLY
DESCRIPTIVE
LEAFLET**



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning

BASIC ELECTRICITY (5 VOLS.)

BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful **NEW PICTORIAL METHOD**—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the **PICTORIAL APPROACH** to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"They certainly confirm everything your readers say about them and I am more than delighted with them. They will be of great value to me in my job as Hospital maintenance electrician." A. B., Birmingham.

"I am entirely satisfied with the books, they are everything you claim them to be." S.S., Cardiff.

"An extremely marvellous set of books." C.B., London.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

■ ■ ■ ■ ■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me **WITHOUT OBLIGATION TO PURCHASE**, one of the above sets on **7 DAYS FREE TRIAL**, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY** 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. **BASIC ELECTRONICS** 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to **UNITED KINGDOM ONLY**. Overseas customers cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ **BASIC ELECTRICITY** ☐ **BASIC ELECTRONICS** ☐
Prices include Postage and Packing.

■ **Signature** (If under 21 signature required of parent or guardian)

■ **NAME**
BLOCK LETTERS

■ **FULL POSTAL**
ADDRESS

TECHNICAL TRAINING in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

7/69

INTERNATIONAL CORRESPONDENCE SCHOOLS

SPEAKER SYSTEMS

All cabinets are new and speakers are mounted on 1/4 in. chipboard baffles. All speakers ex TV reconditioned hi flux magnet. All carefully tested before despatch.



THE CAXTON COLUMN
This is a column cabinet. 23 1/2 x 8 1/2 x 5 1/2 in. wide, fitted with 3 speakers. This will handle 8 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at 59/6. P. & P. 10/6.


THE MILTON A. HI-FI Bookcase Cabinet. Size 9 x 5 x 6 in., with 5 in. speaker. Finished in Teak cloth with bold silk front 30/-. P. & P. 4/6.




The Tennyson. Wedge shaped for table or wall mounting 13 1/2 x 16 x 8 1/2 in. Fitted EMI 13 1/2 x 8 in. Speaker. Finished in Grey cloth with matching Vynair. 24.7.8 P. & P. 7/6.



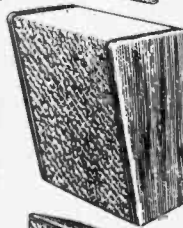DUO. Wedge shaped Speaker Cabinet. Size 7 1/2 x 7 1/2 in. fitted 7 x 4 in. speaker. Covered in attractive two tone Vynair. Price 32/6. P. & P. 4/6.




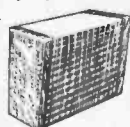THE IMP. Extension Speaker Cabinet. Wedge shaped, size 7 1/2 x 6 1/2 in. fitted 7 x 4 in. speaker.



The Cowdry. Corner Cabinet in natural teak finish. Fitted 8 x 3 in., 7 x 4 in. and three 5 in. round speakers wired in series to match 15 ohm impedance. 26.8.0. P. & P. 8/6.

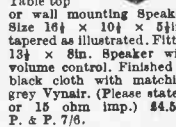THE 800T. Table top or wall mounting Speaker. Size 16 1/2 x 10 1/2 x 5 1/2 in., tapered as illustrated. Fitted 13 1/2 x 8 in. Speaker with volume control. Finished in black cloth with matching grey Vynair. (Please state 3 or 15 ohm imp.) 24.5.0. P. & P. 7/6.



SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line, 10 in. round, 10 x 6 in. 3 ohm, or 15 ohm, 48/6. P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13 1/2 x 8 in. 3 ohm 45/-. 15 ohm 48/6. P. & P. 3/6. E.M.I. 3 in. tweeter, 17/8. P. & P. 1/6. E.M.I. 13 1/2 x 8 in. fitted two 2 1/2 in. tweeters, 15 ohms, 77/8. P. & P. 4/6. E.M.I. 13 1/2 x 8 in. (15 ohm) Hi Fi Quality, 26.10.6. P. & P. 4/6. E.M.I. Woofers, 8 1/2 x 6 1/2 in. square, 8 ohm, 59/8. P. & P. 4/6. E.M.I. Crossover, 16/8. P. & P. 1/-. EAGLE Crossover units, 3 or 16 ohms, 16/-. P. & P. 1/-. Bakers 12 in., 25 watt, 15 ohm, 26.8.0. P. & P. 3/6.

TEAK PLINTH AND PERSPEX DUST COVER for 8P25 etc. 25.5.0. P. & P. 5/-. **VYNAIR** Widths from 40 to 54 in., 17/6 yd. off roll. P. & P. 1/9. 1/2 yard, 9/- P. & P. 1/9. Send 1/- stamps for samples. **SPEAKER MATCHING TRANSFORMERS**, 3, 7, 15 ohms, 8 watt, 11/6 P. & P. 1/6.

MICROPHONES: Xtal Hand Mikes. B1201 with stand, 54/8. P. & P. 3/6. ACOS Mike 45, 21/-. ACOS Mike 40, 15/6. Dyn. Mike DM-391, 30/-. CM21 Xtal, 12/8. Telephone Pick-up, 10/6. P. & P. 1/-. Xtal lapel Mike, 7/6. Guitar Mike, 12/8. P. & P. 1/-. **FERROX RODS:** 8 x 1/2 in., 2/6; 4 x 1/2 in., 2/-; 6 x 1/2 in., 2/6; 8 x 1/2 in., 3/-. P. & P. 1/- each.

FERROX RODS WITH COILS: 4 x 1/2 in., 3/8; 6 x 1/2 in., 5/8; P. & P. 1/- each. **ROTARY SWITCHES:** 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-. **TRANSISTOR SPEAKERS:** 8 ohm 2 in., 6/6. 3 in., 10/8. 3 1/2 in., 12/8. P. & P. 1/-. **CARTRIDGES**

Stereo: Sonotone 9TA H/C Diamond 47/8. 9TA Sapphire, 37/8. 8TA Sapphire, 30/-. Ronette S105 Medium Output, 28/8. S108 High Output 28/8. DC284 Stereo Compatible 28/8. Aco GPF31 Sapphire, 37/8. GPF41 Sapphire, 39/8. GPF1 Diamond 42/-. GPF1 Stereo Compatible (High, Medium or Low Output), 25/-. TA800 converts Philips AG3001, A3306 to B.S.R. SX1H. Plug-in head complete with cartridge 50/-. TA700 equivalent to B.S.R. SX1M, 35/-. Japanese equivalent to B.S.R. TC8, 35/-. Mono: Aco GPF72 will replace Collaro and Garrard Mono cartridges, 15/8. T.T.C. Crystal High Gain, 15/-. B.S.R. TC8H Jap. equivalent, 26/-. Sonotone 2T88, 16/-. Post and Packing 1/6. **EARPIECES WITH CORD** and 3-5 mm. plug, 8 ohm magnetic, 3/-, 280 ohm, 4/-, 180 ohm with clip, 6/8. Xtal, P. & P. 6d. **PIANO KEY PUSH BUTTON SWITCHES,** 7 button inc. mains on off, 6 banks of 6 P.C.O., 8/8. P. & P. 1/-.

BROADWAY Electronics

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday) (Few minutes from Tooting Broadway Underground Station)

Burgess instant heat solder gun

Only the tip heats—but fast! About 7 seconds! Pre-focused lamp lights the job up. Exclusive full-length trigger on pistol grip eases finger fatigue. Finger-tight is right for screw-in tips — no pliers needed. Kit complete with conical tip, chisel tip, 6" extension barrel, double-ended probe, gun and solder. £4 12 6.

Full details and nearest stockist from:

Burgess Products Co Ltd, Sapcote, Leicester LE9 6JW



a complete stereo system for only 28 gns!



THE DUETTO 9 GNS.

Integrated Transistor Stereo Amplifier P & P 7/6

The Duetto is a good looking quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.


Specification: R.M.S. power output: 3 watts per channel into 10 ohms speakers.

Input Sensitivity: Suitable for medium or high output crystal cartridges and tuners. Crosstalk better than 30dB at 1 Kc/s.

Controls: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

Tone Control: Treble lift and cut. Separate on/off switch.

A preset balance control.

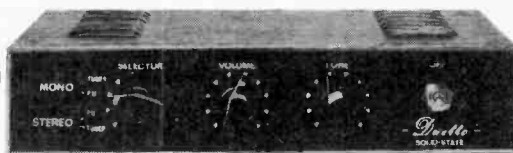


THE DUO 4 GNS.

The new Duo general purpose 2-way system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Specification: Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" and 2 1/2" tweeter. Teak finish. 12" x 6 1/2" x 5 1/2", 4 gns each, p & p 7/6

Garrard Changers from £7.19.6 p & p 7/6

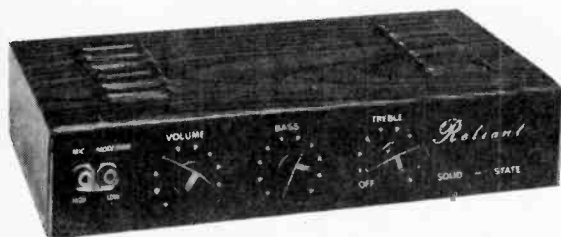Cover and Teak finish Plinth £4.15.0 p & p 7/6



THE RELIANT

Solid State General Purpose Amplifier

6 1/2 GNS.

P & P 7/6

Specification—Output: 10 watts into a 3 ohm speaker. Inputs: (1) for mike (10mV). Input (2) from gram, radio (250mV) individual base and treble control. Transistors: four silicone and three germanium. Mains Input: 220/250 volts. Size: 10 1/2" x 4 3/4" x 2 1/2". Price: 6 1/2 guineas in teak finished case. Less teak case 5 1/2 gns, p & p 7/6. Mike to suit (Crystal): 12/6 plus 1/6 p & p.

8" x 5" speaker 14/6 plus 3/- p & p.



THE VISCOUNT

13 1/2 GNS.

P & P 17/6

Integrated High Fidelity Transistor Stereo Amplifier

Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner, Tape and Tape Rec. Out. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency Response: 40Hz-20KHz+ 2dB. Tone Controls: Separate bass and treble controls; treble, 13dB lift and cut at 15KHz; Bass, 15dB lift and 25dB cut at 60Hz. Volume Controls: Separate for each channel. AC Mains Input: 200-240v. 50-60Hz. Size, 12 1/2" x 6" x 2 1/2" in teak finished case. Built and tested.

RADIO & TV COMPONENTS (ACTON) LIMITED

All orders by post to our Acton address

21c High Street, Acton, London, W.3. and also at 323 Edgware Road, London, W.2.



RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only
high grade components and transistors.



LT55 6 WATT AMPLIFIER

A HIGH FIDELITY UNIT PROVIDING EXCELLENT RESULTS AT MODEST OUTPUT LEVELS.

Sensitivity 5 mv (max).
Frequency Response 80-20,000 cps—2dB
Harmonic Distortion 0.5% at 1,000 cps
Output for 8-815 ohm Loudspeakers.
Input Sockets for "Mike," Gram and
Radio Tuner/Tape Recorder.

Recommended **9 gns**
Retail price
Size $9\frac{1}{2} \times 2\frac{1}{2} \times 5\frac{1}{2}$ in.
Controls (5) Volume, Bass,
Treble, Mains Switch, Input
Selector Switch.


LT66 12 WATT STEREO AMPLIFIER

A TWIN CHANNEL VERSION OF
THE LT55 PROVIDING UP TO
6 WATTS HIGH FIDELITY OUT-
PUT ON EACH CHANNEL.

Switched Input Facilities
Socket (1) Tape or crystal PU
(2) Radio Tuner (3) Ceramic PU
Microphone.

Controls (6) Volume, Bass, Treble, Balance, Mains Switch, Input Selector
Switch. Stereo/Mono Switch.

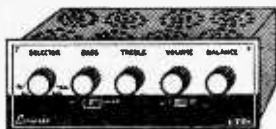Facia Plate Rigid Perspex with black/silver background and matching
black edged knobs with spun silver centres.



Recommended **16 gns**
Retail price
Size $12 \times 3\frac{1}{2} \times 6$ in.

If required an attractive
wood cabinet with
stain. Teak veneer
finish can be supplied
for any model.
Prices from **70s.**

Please send a stamped addressed envelope for full details of
above units, also TUNER/AMPLIFIERS STEREO and MONO
AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Wholesale and Retail enquiries to:

LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds

Announcing...

The VHF/UHF Manual

by George Jessop, G6JP

If you have any interest in the frequencies
above 30 MHz then you need this book. It is
the first complete manual for the metre and
decimetre bands ever published outside of
North America. It is probably the most com-
prehensive work of its kind ever produced,
ranging from advanced material to simple
circuits for the rank beginner to VHF.
Illustrated with over 600 drawings.

Like all of RSGB's technical books, it is
British produced and thus all parts are avail-
able in this country. An attractive layout and
clear style make the VHF/UHF Manual
equally suitable for construction or just
reading.

Obtainable at 21/- over the counter
or 22/6 by post from:-

R S G B Publications

35 DOUGHTY STREET, LONDON, W.C.1.

Aerial Wire: Coils of 25 yds. solid core, 2/3 plus 1/- P. & P.

Battery Eliminators for Transistor Supplies.
9v., 7½v., 6v., 29/6 plus 2/6 P. & P.

Condensers: Large range available from 6d. each.

Coax Sockets: Flush, 6d. plus 6d. P. & P.

Cartridges: Acos GP67/2G, 14/9; BSR TC8H,
30/-; TC8M, 28/6; X1M inserts, 22/6, etc.

Ear Pieces: 2.5µ/m or 3.5µ/m Mag., 2/6 plus 1/-
P. & P. 2.5µ/m or 3.5µ/m Crystal, 5/6 plus 1/-
P. & P.

High Impedance Horns: 1½ to 4½ volt, ideal for
alarms, 3/6 plus 1/- P. & P.

Loudspeakers: Large range. 2in. 8 ohm, 7/6;
4in. 8 ohm, 12/6; 5in. 8 ohm, 16/6 plus 2/- P. & P.

Transistors: Full range, i.e. OC44, OC45, OC71,
OC82, 2/6; OC35, 9/-; Fet.MPF103, 9/6.

Transformers: 12 volt battery charger, £1.2.6.
250-0-250 volt 60mA, 18/9; 0-250 with 6-3 volt, 19/6
plus 3/6 P. & P.

Relays: 12 volt suitable for car alarm, 21/-;
6 volt A.C. 28/6; 240 volt A.C. 27/6 plus 3/- P. & P.

Ex. Govt. Panel Meters: 0-5M/A, 17/6; 0-300V
A.C./D.C. 25/6 plus 2/7 P. & P.

Many other items, please send S.A.E. for free
price list.



**BOTHWELL ELECTRIC
SUPPLIES (Glasgow) LTD.**
64 EGLINTON STREET,
GLASGOW, C.6. Tel. 041 80UTH 2904

Member of the Lander Group

4-STATION INTERCOM



£7/15/0

Solve your communica-
tion problems with this
4-Station Transistor Intercom system (1 master and
3 Subs), in de-luxe plastic cabinets for desk or wall
mounting. Call/talk/listen from Master to Subs and
Subs to Master. Ideally suitable for Business, Surgery,
Schools, Hospital, Office and Home. Operates
on one 9V battery. On/off switch. Volume control.
Complete with 3 connecting wires each 66ft. and
other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for
instant two-way, loud and clear communication.
On/off switch and volume control. Price 18 gns.
P. & P. 8/6 extra.

INTERCOM/BABY ALARM



65/-

Same as 4-Station Intercom for two-way instant
communication. Ideal as Baby Alarm and Door
Phone. Complete with 66ft. connecting wire.
Battery 2/6. P. & P. 4/6.

TRANSISTOR TELEPHONE AMPLIFIER



59/6

Why not boost
business effi-
ciency with this incredible De-luxe Telephone Ampli-
fier. Take down long telephone messages or converse
without holding the handset. A useful office aid. On/
off switch. Volume Control. Battery 2/6 extra. P. & P.
8/6. Full price refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (P/W)
169 KENSINGTON HIGH STREET, LONDON, W.8.

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting
bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/6.
11 element, 45/-; 14 element, 52/6. 18
element, 60/-; Wall Mounting with
Cranked Arm, 7 element, 30/-; 11 element,
67/-; 14 element, 75/-; 18 element, 82/6.
Mast Mounting with 2in. clamp, 7 element,
42/6. 11 element, 55/-; 14 element, 62/6. 18
element, 70/-; Chimney Mounting Arrays,
Complete, 7 element, 72/6. 11 element, 80/-.
14 element, 87/6. 18 element, 95/-; Complete
assembly instructions with every unit. Low
Loss Cable, 1/6 yd. U.H.F. Preamps from
75/-; State clearly channel number required
on all orders.

BBC - ITV AERIALS



BBC (Band 1). Tele-
scopic loft, 25/-; External
S/D, 30/-; "H", £215.0.
ITV (Band 2). 3
element loft array, 30/-; 5
element, 40/-; 7 element
50/-; Wall mounting, 3 ele-
ment, 47/6. 5 element
52/6. Combined BBC/
ITV. Loft 1+3, 40/-; 1+5,
50/-; 1+7, 60/-; Wall
mounting 1+3, 57/6; 1+5,
67/6; Chimney 1+3, 67/6;
1+5, 75/-.
VHF transistor pre-
amps, 75/-.

COMBINED BBC1 - ITV - BBC2
AERIALS 1+3+9, 70/-; 1+5+9, 80/-;
1+5+14, 90/-; 1+7+14, 100/-; Loft mounting
only. Special leaflet available.
F.M. (Band 2). Loft S/D, 15/-; "H", 32/6.
3 element, 55/-; External units available.
Co-ax. cable 8d. yd. Co-ax. plugs, 1/4.
Outlet boxes, 5/-; Diplexer Cross-over Boxes,
13/6. C.W.O. or C.O.D. P. & P. 6/-; Send 6d.
stamps for illustrated lists.

Callers welcomed - open all day Saturday


K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

Build yourself a quality transistor radio

backed by our
after sales service!

roamer seven mk IV SEVEN WAVEBAND PORTABLE

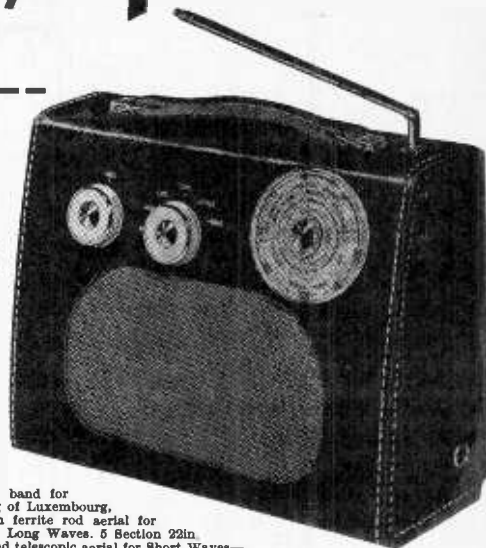SEVEN TUNABLE WAVEBANDS—
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.



pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
44'6 P. & P.
3/6

Extra M.W. band for easier tuning of Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push pull output. 7 transistors and 2 diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Volume on/off control wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build.

Total building costs
£5.19.6 P. & P.
7/6 Personal Earpiece with switched socket for private listening 5/- extra.

Parts price list and easy build plans 3/- (Free with parts).

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½in. x 1½in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
47'6 P. & P.
3/9

super seven

THREE WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
69'6 P. & P.
4/6

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/-.



Total building costs
79'6 P. & P.
4/6

NEW LOOK melody six

TWO WAVEBAND PORTABLE

8 stages—5 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3½in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. stages for extra boost. High "Q". Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2½in. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
69'6 P. & P.
4/3

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER SEVEN	☐	ROAMER SIX	☐
TRANSONA FIVE	☐	SUPER SEVEN	☐
POCKET FIVE	☐	MELODY SIX	☐

Parts price list and plans for

Name

Address

PW7

* Callers side entrance Stylo Shoe Shop

* Open 10-1, 2.30-4.30 Mon-Fri. 9-12.30 Sat

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit **191 1/2 Gns.**
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms. Carr. 12/6
 ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet, (2) 3-way quarter section series cross-over system, (3) 8 x 5in. high flux middle range speaker, (4) High efficiency tweeter, (5) Measured weight of woollen acoustic damping material, (6) Teak veneered cabinet, (7) Circuit and full instructions. Terms: Dep. 25.10.6 and monthly payments 39/- (Total £23.1.0) DEMONSTRATIONS AT ALL BRANCHES.

R.S.C. STEREO/20 HI-FI AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PEAK PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE. (7) valves ECC83 (2) ECL86, (4) E281. Frequency Response: +2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 30 millivolts max. Harmonic Distortion: 0.2% ★ Four-position tone compensation and Input Selector Switch. ★ Stereo/Mono switch. ★ Neon panel indicator. ★ Handsome Perspex Frontplate. ★ Separate Bass and Treble controls. Output transformers are high quality sectionally wound. Outputs for 3 and 15 ohm speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 mths' gntee 19gns. Or Dep. £4.10.0 and Carr. 12/6 9 monthly payments 22/- (Total £22.10.0). Send S.A.E. for leaflet.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Performance figures of factory built units: Hum level—70dB. Frequency response +3dB 30-20,000 c.p.s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble controls. Sensitivity: 30 millivolts max. For use with high impedance microphones, Crystal or Ceramic P.U.s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V, 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. Carr. 12/6 14 Gns. Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 17 gns. TERMS: Deposit 26 and 9 monthly payments of 22/- (Total £20.9.0) Send S.A.E. for leaflet.

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram etc. High sensitivity. 5 valves—ECC83 (2), EL84 (2), E281. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response +3dB 30-20,000 c.p.s. Hum level—60dB. SENSITIVITY 40 millivolts. For use with Gram, Crystal or Ceramic P.U.s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V, 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built 12 Gns.) Twin handled metal cover 27/6. TERMS ON ASSEMBLED UNITS. Deposit 9/6 and 9 monthly payments of 22/- (Total £14.15.0).

R.S.C. A11 TRANSFORMER VERSION OF above complete kit 9 Gns (Assembled 13 Gns)

R.S.C. BASS-REAGENT 50 WATT AMPLIFIER

An exceptionally high quality all-purpose unit for lead, rhythm, bass guitar, vocal, gram, radio, tape. Peak O/P rating. ★ Two extra heavy duty 12in. Loudspeakers. ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. 52 Gns. Carr. 30/- or dep. £10.1.9 and 9 monthly payments of 25.11.9. (Total 571 gns.). Send S.A.E. for leaflet. G100 100 watt peak output with Pr. speaker columns and a Bass Unit. 12 in. and Two 15" speakers. 800 gns.

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250V, 50c/s is available. Complete kit with diagram 49/11 or assembled 69/11.

SELENIUM RECTIFIERS (F.W.D. Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 4/3. 1 1/2a. 5/6. 2a. 6/11. 3a. 9/9. 4a. 12/9. 5a. 15/9.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250V. 50c/s. Screened.
 MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.
 250V, 60mA, 6-3v. 2a. 15/11
 250-0-250V, 60mA 6-3v. 2a. 16/11
 FULLY SHROUDED UPRIGHT MOUNTING
 250-0-250V, 60mA, 6-3v. 2a., 0-5-6-3v. 2a. 21/9
 250-0-250V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 300-0-300V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 300-0-300V, 130mA, 6-3v. 4a., c.t., 6-3v. 1a. 37/9
 For Mullard 510 Amplifier
 350-0-350V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 350-0-350V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 350-0-350V, 150mA, 6-3v. 4a., c.t., 5v. 3a. 47/9
 425-0-425V, 200mA, 6-3v. 4a., c.t., 5v. 3a. 75/-
 425-0-425V, 250mA, 6-3v. 4a., c.t., 5v. 3a. 75/-
 450-0-450V, 250mA, 6-3v. 4a., c.t., 5v. 3a. 75/-
 TOP SHROUDED DROP-THROUGH TYPE
 250-0-250V, 70mA, 6-3v. 2a., 0-5-6-3v. 2a. 21/9
 250-0-250V, 100mA, 6-3v. 3-5a. 25/9
 250-0-250V, 100mA, 6-3v. 2a., 6-3v. 1a. 26/9
 350-0-350V, 80mA, 6-3v. 2a., 0-5-6-3v. 2a. 27/9
 250-0-250V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 300-0-300V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 300-0-300V, 130mA, 6-3v. 4a., 0-5-6-3v. 1a. 37/9
 Suitable for Mullard 510 Amplifier
 350-0-350V, 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 37/9
 350-0-350V, 150mA, 6-3v. 4a., 0-5-6-3v. 3a. 45/11
 FILAMENT or TRANSISTOR POWER PACK Types
 6-3v. 1.5A. 7/9; 6-3v. 2A. 8/9; 6-3v. 3A. 10/9; 6-3v. 6A. 19/9; 12v. 1A. 8/9; 12v. 3A. or 24v. 1.5A. 21/9; 0-5-18v. 1 1/2A. 17/9; 0-12-250-42v. 2A. 29/9.
 CHARGE TRANSFORMERS 0-15v. 1 1/2A. 14/11; 2 1/2A. 17/9; 3A. 19/11; 5A. 23/9; 6A. 27/9; 8A. 33/9. 10A. 55/11.
 AUTO (Step Up/Step Down) TRANSFORMERS
 0-110/120V. 200-230-250V. 50-80 watts 15/9
 150 watts, 29/11; 250 watts 49/9; 500 watts 99/9
 OUTPUT TRANSFORMERS
 Standard Pentode 5,000 Ω, or 7,000 Ω to 3 Ω. 8/9
 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω. 25/9
 Push-Pull 10 watts 6V6 BC100 to 3 Ω, 5 Ω or 15 Ω. 25/9
 Push-Pull EL84 to 3 Ω or 15 Ω 12-12 watts. 21/9
 Push-Pull Ultra Linear for Mullard 510, etc. 39/9
 Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω. 35/9
 Rectifier 20 watt, high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω. 59/9
 SMOOTHING CHOKES
 150mA, 7-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11.

BLACKPOOL

AGENT APPOINTED
 O. & C. ELECTRONICS
 227 CHURCH ST.

R.S.C.
 HI-FI CENTRES LTD.

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynal, ideal for vocalists and Public Address, 15 ohm matching. C57 15 watt inc. five 7 x 4in. speakers £7.19.11.
 TYPE C483 30WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 67/- and 9 mthly pmts 34/9 (Total £18.19.9) Carr. 10/-
 TYPE C412S 50WATTS. Fitted four 12in. 11,000 line 15 watt 24 Gns. speakers. Overall size 56 x 14 x 8in. approx. Carr. 15/-
 Or Deposit £4.13.6 and 9 monthly payments of 52/9 (Total £28.5.0).

30 WATT HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold perspex facia. Neon indicator. For 200-250V. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 4 gns. and 9 mthly payments of 59/8 (Total 21 gns.). 18 Gns. Carr. 12/6

12in. HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinets 15 Watt 11,000 line 20 Watt 10,000 lines 30r 15ohms. Carr. 7/6 15 ohms. Carr. 8/9 £8.19.9

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 year guarantee. High Flux 14,000 line ceramic magnets. Heavy cast chassis.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt	15" 60 Watt	12" 50 Watt
19 GNS. Carr. 15/-	12 GNS. Carr. free	10 GNS. Carr. free

POWER PACK KIT Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250V, A.C. mains. Output 250V, 60mA 6-3v. 2a. Supplied with case in lieu of chassis 29/11. Or assembled 39/11. 25/11

CLEARANCE LINES

HIGH QUALITY 8" x 3" LOUDSPEAKERS 1000 Gauss 11/9 3 ohm only Post 2/-

15" 40 WATT LOUDSPEAKERS IN CABINET 14 Gns

Heavy construction. Covering Rexine and Vynal

14 WATT HI-FI AMPLIFIERS

High sensitivity. Two separate inputs. Two vol. controls for mixing purposes. Separate Bass and Treble controls. Valves ECC83, ECL86, E281. Output for 15 ohm Loudspeaker. 200-250V 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 6in. Factory built and fully guaranteed. Limited number to clear at £7-19-11 Carr. 10/-

E.M.I. HIGH FIDELITY LOUDSPEAKERS 13" x 8" 15 ohms 5 1/2 Gauss 13,000 lines. Formed flexible P.B.C. cone surround for very low fundamental resonance. Range 30-15,000 c.p.s. Rating 10 watts. Gns

CABINET 'SPEAKERS' 29/9

Emi PLAYER TURNTABLES with P.U. 4 speed. Turnover cart-ridge. Limited number. Mono 59/9 Stereo 69/9

PHONE AMPLIFIERS

free. Standard dry battery operated. Attractive black moulded case. 59/9

1 WATT TRANSISTOR AMPLIFIERS

louspeakers. Miniature size. Brand new boxed. Post free 37/9

PRINTED CIRCUIT KITS

Complete with 72 square ins. laminated board and necessary fluids. Post 2/9 12/9

J.B. VHF/FM DIAL & DRIVE ASSEMBLIES

ONLY 9/9 Complete with escutcheon. Size 7" x 4 1/2". Escutcheon 7 1/2" x 2 1/2". Post 2/9

TAPE RECORD/PLAYBACK AMPLIFIERS

Eye Recording level indicator. For 3 ohm L/S. All normal facilities. Less Facia plate. For 200/250 A.C. mains. Carr. 8/6. 4 watts out. Magic £8.15.0

ARMSTRONG UNITS CLEARANCE

Our Price Stereo Amplifier 222 £25 Carr. 10/6 AM/FM Tuner Amplifier 227M £35 Carr. 10/6

MINI-8 HI-FI LOUDSPEAKER UNITS

Teak or Afrormosia veneered cabinet, size approx. 10 1/2 x 6 1/2 x 7 1/2 in. Peak power handling 8 watts 3 ohms. Carr. 5/- Clearance Price 59/11

JASON VHF/FM TUNER DESIGNS

Total cost of parts FMT1 5 Gns. FMT2 £6.19.11. JTV2 9 1/2 Gns. Please state channel

STEREO/TEN HIGH QUALITY AMPLIFIER

5 watts high quality peak output on each channel Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo cartridges. Ganged Bass and Treble Controls. Valves ECC83 (2), EL84 (2), E281. For 2-3 ohm speakers. Assembled with 12 months' guarantee Carr. 7/9 £11.19.6

6/12V CAR BATTERY CHARGERS

Complete kit of parts with Ammeter and Circuit. Both models with variable charge rate selector. 4 amp 49/9 6 amp 69/9

All types 200-250V. A.C. Mains. Built 10/- extra.

R.S.C. SENSATIONAL HIGH FIDELITY STEREO PACKAGE OFFERS

"PACKAGE 3" 30 WATT OUTPUT
 ★ Goldring Transcription Turntable on Plinth
 ★ Super 30 Amplifier in veneered housing
 ★ Pair of Stanton Loudspeaker Units
 Special total price. Four fully wired units ready to "plug-in". Carr. 25/-
TERMS AVAILABLE ALL PACKAGE OFFERS

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range 40-15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.
 Prices include carriage. HF100D 10" 15W 25.15.0
 HF510L 5" 10W 57/9 HF120 12" 15W 89/9
 HF810D 8" 8W 58/9 HF120D 12" 15W 79/9
 HF810L 8" 10W 4 gns. HF126 12" 15W 89/9
 HF120D 10" 8W 58/9 HF126D 12" 15W 5 gns.

HIGH FIDELITY LOUDSPEAKER UNITS
 Cabinets latest style Satin Teak or Afformosia veneer. Acoustically lined or filled with woolen damping. Ported where appropriate. Credit terms available



DORCHESTER Size 16 x 11 x 9 in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 12 x 8 in. Dual £8.19.9
 Cone spkr. Imp. 3 or 15 ohms. Carr. 7/6

STANTON IIIS Size 18x11x10 in. Rating 10 watts. Incorporating Fane 803B speaker with roll rubber cone surround and 15,000 line magn. High flux tweeter. Handsome Scandinavian design cabinet. Range 30-20,000 c.p.s. Impedance 15 ohms. Gives smooth realistic sound output. 16 Gns. Carr. 7/6

GLOUCESTER Size 25 x 16 x 10 in. 12 in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 40-20,000 c.p.s. Impedance 15 ohms. 12 1/2 Gns.

E2 EQUIPMENT CABINET
 Size 17" wide 14" deep 11" high. Cut for TA12. Super 15. Super 30 and other amplifiers. 'Roll over' perspex cover. Satin Teak or Afformosia veneer finish. Price inc. carr. 8 Gns.

MOTOR BOARDS cut for Garrard Turntables and many other units. Price 12/9

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER
 200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio/Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating 1.5W. Fully enclosed enamelled case, 9 1/2 x 5 1/2 in. Attractive brushed silver finish face plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. £6.19.9
 Carr. 7/6
 Or factory built with 12 months guarantee. £8.19.9

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER
 ★ High-sensitivity ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Rejection. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Simple alignment instructions. ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. ★ Any MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts. point to point wiring diagrams and detailed instructions. Carr. 15/-
 Unit/factory built 28 Gns. or deposit £7.5.0 and 9 monthly payments 58/3. (Total £32.13.3). Or in veneered housing 31 Gns. Carr. 15/- or deposit £7.3.6 and 9 monthly payments 64/- (Total £35.19.6). Send S.A.E. for leaflet.

R.S.C. SUPER 15 HI-FI AMPLIFIER
 FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 3-4 ohms. TRANISTORS: 9 current types of high quality by leading manufacturers. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10Kc/s. NEG FEEDBACK: 52dB. BASS CONTROL: +17dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.2%. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6
 Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9). Or in Teak or Afformosia veneer housing as illustrated. 19 Gns.
 ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING MANUFACTURERS.

R.S.C. SUPER 30 STEREO AMPLIFIER
 FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 30 WATTS R.M.S. cont. into 15 ohms. 30 WATTS R.M.S. cont. into 3-4 ohms. TRANISTORS: 9 current types of high quality by leading manufacturers. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10Kc/s. NEG FEEDBACK: 52dB. BASS CONTROL: +17dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.2%. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6
 Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9). Or in Teak or Afformosia veneer housing as illustrated. 19 Gns.
 ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING MANUFACTURERS.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
BIRMINGHAM 30/31 Gt. Western Arcade opp. Snow Hill Station 021-236-1278 (Half-day Wed.)
DERBY 26 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 328 Argyle St. (Half-day Tues.) Tel. City 4158
 403 Sauchiehall St. (Opp. Locarno) (Half-day Tues.) Tel. 332-1572
HULL 91 Paragon Street. (Half-day Thursday) Tel. 20505

Matching as recommended for optimum performance. Send for coloured brochure showing other money saving offers.



Illustrated with TFM1 Mk II Tuner fitted
EXTREMELY ATTRACTIVE AND VERSATILE PLINTHS
 finished in Teak or Afformosia veneer. Tinted Perspex "roll over" cover with satin chrome handle.

RECORD PLAYING UNITS
 Money saving units. Ready to plug into amplifier or RP2 Tape Recorder. Consisting of Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on Plinth, Inc. Perspex cover. Carr. 22 Gns. 15/-

RP3 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear 10 Gns.

10 W HIGH FIDELITY AMPLIFIERS
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder. 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating 1.5W. ★ Handsome brushed silver finish. ★ Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee 16 Gns or Deposit £5.2.6 and 9 mthly pymts 31/6 (Total £19.6.0) Or in Teak or Afformosia veneer housing 19 1/2 Gns. Dep. £5.10.6 and 9 mthly pymts 39/- (Total £23.1.6)

RP2 As above but with Goldring Lenco CL58 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. £28 Carr. 21/-

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 59/9 1000. 2000. 3000. AT6, AT60, SP25 etc. etc. Available with clear Perspex cover. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/8

"PACKAGE 2" 30 WATT OUTPUT
 ★ Garrard SP25 Mk II Turntable on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ Super 30 Amplifier in veneered housing
 ★ Pair Stanton Speaker Units 76 Gns. Carr. 25/-
 Special total price. Four fully wired units ready to "plug-in"

"PACKAGE 1" 13 WATT OUTPUT
 ★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester L'speaker Units. Special total price. 51 Gns.
 Or Dep. £10.0 and 9 monthly payments 25.11.0. (Total £58.19.0.) Perspex cover 3gns. extra.

"PACKAGE 1" 13 WATT OUTPUT
 ★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester L'speaker Units. Special total price. 51 Gns.
 Or Dep. £10.0 and 9 monthly payments 25.11.0. (Total £58.19.0.) Perspex cover 3gns. extra.

"PACKAGE 1" 13 WATT OUTPUT
 ★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester L'speaker Units. Special total price. 51 Gns.
 Or Dep. £10.0 and 9 monthly payments 25.11.0. (Total £58.19.0.) Perspex cover 3gns. extra.

"PACKAGE 1" 13 WATT OUTPUT
 ★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester L'speaker Units. Special total price. 51 Gns.
 Or Dep. £10.0 and 9 monthly payments 25.11.0. (Total £58.19.0.) Perspex cover 3gns. extra.

"PACKAGE 1" 13 WATT OUTPUT
 ★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester L'speaker Units. Special total price. 51 Gns.
 Or Dep.

LOOK!


PRACTICAL!
VISUAL!
EXCITING!

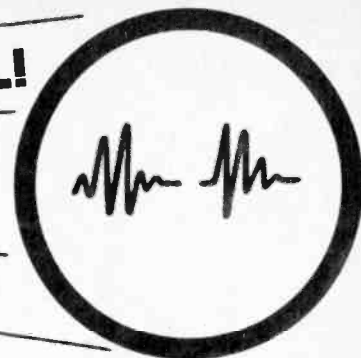

a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

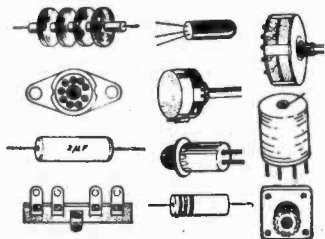complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

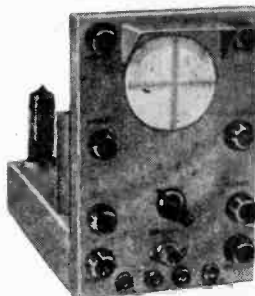a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND
CIRCUIT DIAGRAMS

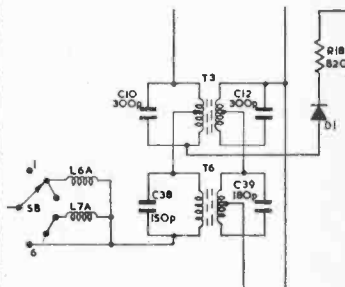

4 ▶

CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW 7

PRACTICAL WIRELESS

VOL 45 No 3

Issue 749

JULY 1969

TOPIC OF THE MONTH

Self-satisfaction

WHY do we do it? Now, there's a leading question if ever there was one. With the keenly competitive market of today, and the resultant multiplicity of receivers, units, test equipment, and the like, often at prices impossible to match by the lone enthusiast, it would seem to the outsider to be difficult to account for the continued popularity of our hobby.

Yet, despite all logical attempts to understand the reasons why the home constructor should still spend his leisure hours making something he could probably buy cheaper, the ranks increase in number. Certain projects, of course, *are* much cheaper to build oneself, especially if the proverbial spares box has any pretensions. But it is necessary to dig a little deeper to discover why more and more people are actively engaged in connecting R1 to C4. For it is obvious that the mere saving of money is not the primary motive.

Man is a curious animal (in at least two definitions of the phrase!). In the first place he is blessed with an intuitive inquisitiveness which may manifest itself in anything from wanting to go to the moon to wondering if it is possible to build a portable radio that not only looks good but sounds good. Perhaps this is the main driving force.

Another well-established characteristic of many specimens of *homo sapiens* (though not in all, by a long way!) is an inherent seeking for the pride that comes from a sense of achievement. In the past, very many people could attain this mental condition at their workbenches but the days of individual craftsmen are fast disappearing. With mass production and modern manufacturing techniques, many erstwhile craft jobs have given way to those offering little in the way of personal satisfaction. This seems to have created a void and is no doubt a strong reason for the astonishing boom in all kinds of do-it-yourself activities.

Many of these frustrated artisans take up radio and electronics. And it is paradoxical that one of the reasons for the de-humanising of industry is the increasingly widespread use of electronics!

W. N. STEVENS—*Editor*.

NEWS AND COMMENT

Leader	167
News and Comment	168
Electronics at the Norway Trade Centre	169
Practically Wireless <i>by Henry</i>	181
MW Column <i>by C. Molloy</i>	195
Letters to the Editor	200
On the Short Waves <i>by Christopher Danpure and David Gibson, G3JDG</i>	211

CONSTRUCTIONAL

AC/DC Meter <i>by H. T. Kitchen</i>	170
Ready Calibrated Signal Generator <i>by F. G. Rayer</i>	175
A.F./I.C. Signal Injector <i>by S. Elliott</i>	188
Directional Microphone <i>by C. R. Bradley</i>	193
Take 20, Mini Metronome <i>by Julian Anderson</i>	203

OTHER FEATURES

Pulse Circuits in Operation, Part 2, <i>by I. J. Kampel</i>	182
Aerials, Part 4, Transmission Lines <i>by A. J. Whittaker</i>	190
Transistor Output Stages, Part 2 <i>by I. R. Sinclair</i>	196
P.W. Guide to Components, Part 7 <i>by M. K. Titman, B.Sc.</i>	204

AUGUST ISSUE WILL BE PUBLISHED
ON JULY 4th

QUERY COUPON

This coupon is available until 4th July, 1969 and must accompany all queries in accordance with the rules of our Query Service. An s.a.e. must be included.

PRACTICAL WIRELESS, JULY 1969

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Phone: 01 836 4363. Advertisement Department: Fleetway House, Farringdon Street, London, E.C.4. Subscription rates, including postage: 42s. per year to any part of the world. ©IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

NEWS AND COMMENT...

RADIO AND TV SERVICING FOR THE YOUNG

The Department of Employment and Productivity has produced a *Choice of Careers* booklet (No. 66) on careers in radio and television servicing. The booklet states that most homes now contain at least a radio and television and in many cases a record player and tape recorder as well. It says that it is therefore essential that adequate repair facilities are available and that there are excellent prospects for the "keen young man who has the aptitude for the job, applies himself wholeheartedly to learning it thoroughly and is prepared to keep abreast of current developments".

The book says that prospects are not limited solely to servicing and those with the ability to extend their knowledge through further study and training may qualify for executive and administrative posts.

Radio mechanics and technicians are responsible for the maintenance of radio receivers and transmitters, weather radar sets, direction and position finding equipment and a wide range of electronic safety and navigational aids. There are also jobs with independent and multiple retailers, with the service organisations, with manufacturers' servicing departments, rental and relay companies, the radio and television organisations and government departments.

There are openings for girls—on production, sometimes with servicing, and some jobs doing semi-skilled work.

The booklet is amply illustrated with photographs showing the branches of the work.

The price of the booklet is 1s. 6d. and is obtainable from H.M. Stationery Office.

THE "WATERCHECK"



Automents Ltd., New Street, Oadby, Leicester, LE2 4LB, specialise in designing, developing and manufacturing car instruments and accessories and their latest design is called the "Watercheck". It consists basically of a Darlington pair and is a water-level indicator. Whenever the water level falls to the level of the probe, fitted into the header tank at a predetermined level, a signal is passed to the Watercheck instrument on the dashboard flashing an amber light, so warning the driver to take action before engine damage occurs. The makers claim the unit can be fitted by the average driver in 20 minutes and there are only three electrical connections to make. Two models are available—12V positive and 12V negative earth. The cost is £3. 15s including postage.

Automents Ltd. state that they will be launching, within the next few months, a windscreen wiper control and a unit called the "Speedset"—an audible speed computer which sounds an alarm as soon as a predetermined speed has been exceeded.

15 + 15W STEREO AMPLIFIER



Futuristic Aids Ltd., 106 Henconner Lane, Leeds, announce their "Phase Thirty-Two" solid state stereo amplifier. Sensitivities are: Magnetic p.u., 3.5mV, Ceramic, 30mV, Radio, 100mV, Tape, 500mV, Microphone, 5mV and Tape Head, 2mV. Frequency response is 10–40,000 c.p.s. —3dB; hum level, —80dB and signal-to-noise, —60dB. Harmonic distortion is 0.1% at 10W r.m.s. 1,000 c.p.s.

The unit is housed in a satin teak veneered cabinet and the fascia plate is Perspex with black background and silver lettering. There is a 5-position input selector—disc, radio, tape, mic., tape head. The price is 35 guineas.

CODAR MOVE

Codar Radio Co. (Inc. Codar Electronics Co.), Bank House, Southwick Square, Southwick, Sussex, have moved into their new factory.

Now all correspondence and goods must be addressed to: *Codar Radio Company, *Codar Electronics (*as applicable) Thesiger Close, Meadow Road Industrial Estate, East Worthing, Sussex. Telephone: Worthing 37315.

NEW MULLARD PUBLICATION

Consumer Electronics is the title of a new Mullard quarterly which concentrates entirely on the existing and future applications of electronics in consumer goods.

Among topics dealt with in the 18-page March issue are: the control of domestic appliances by thyristors, an electronic controller for electric blankets, rental for domestic appliances, colour TV picture tubes, micro-miniaturisation and hearing aids, and a quartz-controlled wristwatch.

Consumer Electronics is free to all interested in the design and manufacture of consumer goods in which electronic devices are or could be used. It is not, however, intended for retailers or consumers. Requests for issues should be addressed, on company headed notepaper, to C.I.H./C.M.S. Dept., Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.

CABLE & WIRELESS APPOINTMENT

Mr. Robert F. Forrest, is the new secretary of Cable and Wireless Ltd.

During the Second World War he saw service on one of the famous Blue Trains—mobile radio stations which provided frontline communications for Allied troops.

Mr. Forrest, in fact, travelled with his Blue Train from Algiers to Vienna, visiting Naples, Rome, Frankfurt and other war-torn cities on the way.

NEWS AND COMMENT...

NEW MULLARD PHOTO-CELL

A new cadmium sulphide cell announced by Mullard has a larger photo-sensitive element than the well-established ORP60, but is the same size externally (6mm in diameter and 16.5mm long excluding leads). Hence, the new cell, type ORP69, is more sensitive and has a higher dark resistance.

The ORP69 will dissipate 100mW and withstand voltages up to 350V d.c. Its initial dark resistance is greater than 100M Ω ; in an illumination of 50 lux from a lamp with a colour temperature of 2700°K, the cell resistance is typically 30k Ω . It has a sensitivity of approximately 17 μ A/lux.

PERIOD STYLE SEPARATES

In Queen Anne style, the Dynatron Hambledon Model HFC13, illustrated on the right, incorporates the SRX25 tuner-amplifier with the Garrard 3500 auto-changer with stereo cartridge and diamond stylus.

Recommended retail price including purchase tax £139 15s.


Matching Queen Anne style loudspeaker enclosures—Model LS250—are available for this model at the recommended retail price including purchase tax of £30.



ELECTRONICS at the Norway Trade Centre

Mr. S. Walter Rostoft, the Norwegian Minister of Industry, recently opened the first exhibition at the new Norway Trade Centre at 20 Pall Mall, London, S.W.1.

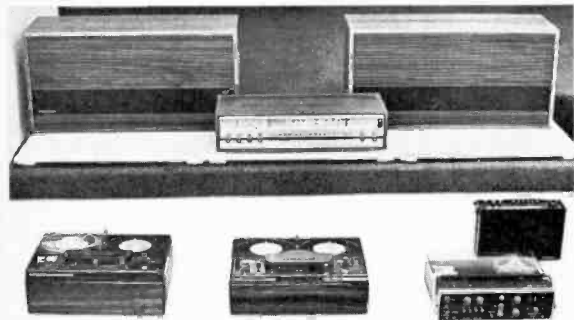Called "Design for Export", the exhibition showed a wide range of Norwegian export products. Many of the exhibits were design articles for the home, including glass, china, cutlery, furniture etc. but another section of the exhibition featured a number




From Tandbergs Radiofabrikk A/S, radio "Huldra" in palisander with two loudspeakers also in palisander. On the left, tape recorder 1200X, the series 15 and the tape recorder 11 which is battery driven. The TP 3-3 portable radio is on the right.

of electronic articles including tape recorders, radio receivers and television.

Tandbergs Radiofabrikk A/S Oslo, represented in the United Kingdom by Elstone Electronics Ltd., Leeds, were the major exhibitor at the exhibition. Tandbergs export 50% of production to the UK, Sweden and the USA.


Norway's oldest radio manufacturer, A/S Radionette, established in 1927, was showing its Multi-recorder f.m. tape recorder, its Kurer u.h.f./v.h.f. portable TV working from mains or battery and housed in a wooden cabinet, and its new Soundmaster HiFi stereo radio which employs pressure chamber speakers. This set cover 6 wavebands: Long, Medium, Short 1 (60-24m), Short 2 (24-10m), f.m. and Marine Band. In the UK Radionette is represented by Denham & Morley Ltd., London, W.1.

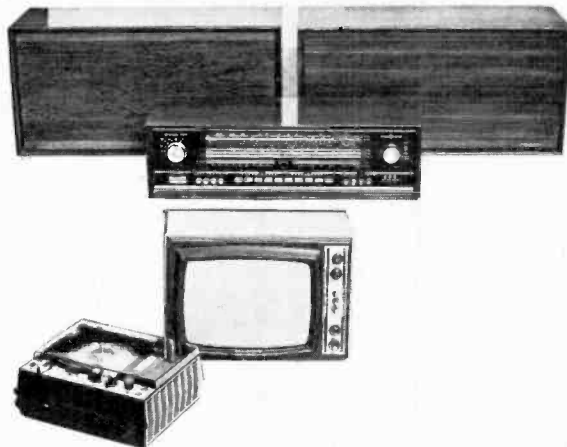

From A/S Radionette, the Soundmaster Hi-Fi Stereo with pressure-chamber speakers, the "Kurer" 11in. TV and the Multi-recorder—FM—a one-spool portable tape recorder with built-in f.m. radio.

AC-DC METER

H. I. KITCHEN

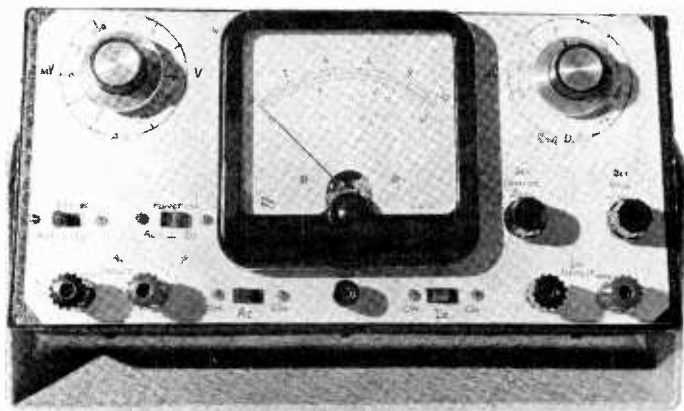

THE further the enthusiast ventures along the electronics path, the more he realises the limitations of the ubiquitous test meter. For many applications the test meter is adequate, often indispensable, and it is only when he begins to delve into the regions of millivolts, or begins to soar into the kilohertz region that the limitations of the ordinary test meter become obvious. In order to explore these regions successfully, more sophisticated equipment is necessary. It was to fulfil such a requirement that the test set to be described was evolved.

The cost of such an instrument, even if home made, is relatively high when one considers the multitude of cheap and usually good test meters available to the enthusiast.

In the "good old days" of vacuum state equipment, test meters having input resistances of one or two $k\Omega/V$ were quite adequate. A $10k\Omega/V$ meter was occasionally necessary; a $20k\Omega/V$ meter was really something. Nowadays, silicon transistors drawing only a few hundred micro-amps collector current are not uncommon, with base currents in the nA ($nA = \text{nanoamp} = 0.001 \mu A$) or a few μA region. In such an instance, even a $20k\Omega/V$ meter can impose an intolerable drain on the circuit, giving readings well below the true value, or even no reading at all. Quite clearly, a much higher input resistance meter is required, and since the major requirements, such as sensitivity, and robustness and resistance against damage due to mechanical shock, conflict, there is a limit to the degree of sensitivity attainable in the meter movement itself. Recourse has to be made to "active" voltmeters containing amplifiers that can increase the minute voltages to the extent that relatively insensitive, and therefore mechanically robust, meter movements can be used. These amplifiers constitute what are in effect, impedance transformers that allow the low resistance high current consumption meter movement to be connected into a high resistance low current consumption circuit without affecting it adversely.

One other limitation of the ordinary test meter is its restricted measuring range. Few test meters are intended for measuring voltages below a few volts a.c. and d.c., so that the very limited a.c. output voltages from tape leads, moving coil pickups and microphones are virtually undetectable, let alone measureable. As far as d.c. in concerned, voltage differences of a few hundred mV are not uncommon—and are difficult to measure accurately on the average test meter.

A further limitation is that of frequency response, or rather the lack of it. Most of the older test meters employed selenium rectifier for the a.c. ranges, and the response of these rarely exceeded several kHz. The response of the germanium or silicon rectifiers, however, in current use, is much better.

Having proved, I hope, the necessity of parting with more hard earned (?) cash, we can now get to grips with the article itself.

The design to be described consists of two entirely separate amplifiers, one for a.c. and one for d.c., the outputs of which may be selected, to feed a moving coil meter. Two separate meter amplifiers are used for maximum efficiency; one meter movement for maximum economy. In practice, where it matters most, the compromise works well, since the inputs of the amplifiers can be connected into the parts of the circuit under examination, and the meter switched into the output of either meter amplifier as required. This method therefore resulting in the minimum of circuit disturbance.

DC Amplifier

The d.c. amplifier is the simpler of the two, and will accordingly be described first. The circuit shown in Fig. 1 contains five transistors of which the first four Tr1-Tr4 function as a long tailed quartet, and form the amplifier proper. The fifth transistor operates as a constant current source serving two different, and very useful functions.

Without the amplifier, the d.c. meter would have an input resistance of only $20k\Omega/V$ at a f.s.d. (full scale deflection) current consumption of $50\mu A$. With the amplifier added, the meter has an effective input resistance of $3M\Omega/V$ and an f.s.d. current consumption of $333nA$. The amplifier therefore, has a current gain of $\times 150$. Even higher gains are possible, but as will be explained later, are not a practical proposition.

An explanation of the action of the d.c. amplifier is perhaps best effected by temporarily ignoring Tr5 and its associated components R19 and D1 and by connecting the slider of VR2 to the negative line. Tr1 to Tr4 will then be seen to comprise a very high gain push-pull amplifier, with input voltage applied between the bases of Tr1 and Tr4 with the output voltage developed by Tr2 Tr3 across R13 R16 applied to the meter. The amplifier is therefore a differential amplifier.

Assuming component equality "either side" of the meter movement, the bases of Tr1 and Tr4 will be at the same potential as each other, as will the collectors of Tr2 and Tr3. There will therefore be no current flow through the meter. If a d.c. voltage is now applied between the bases of Tr1 and Tr4, the balance will be disturbed and the current flowing through one pair of transistors, (Tr1 Tr2) will increase, the current through the other pair will decrease, and a current will therefore flow through the meter. Due to the amplification afforded by the transistors, a minute current into the bases, in this instance 330nA, will cause the meter to pass 50 μ A and so read full scale.

Due to manufacturing tolerances, component equality cannot be assured, and so other means have to be sought to bring the meter pointer initially to zero. This is achieved by VR1 and VR2, the former equalising the base voltages, the latter the emitter. Base bias is by R11 R12 VR1 for Tr1 Tr2, and by R17 R18 and VR1 for Tr3 Tr4.

The reason for requiring two equalising controls is quite simple. It is quite possible to effect meter zero by equalising the emitter voltages only by means of VR2, even if the base voltages are dissimilar. However, the transistors will amplify the *difference in the base voltage as well as the wanted voltage*. Considerable errors are therefore possible, the error being a function of the difference in polarity and magnitude of the "difference" and "wanted" voltages.

An unfortunate aspect of high gain d.c. amplifiers is that the zero once set, tends to drift, the tendency to drifting increasing with increased amplifier gain. Unless this drift can be curtailed, meter readings will be subject to error.

SPECIFICATION

D.C. METER

Ranges:

100mV, 300mV, 1V, 3V, 10V, 30V, 100V, 300V.

Input Resistance:

3M Ω /V–10V constant at 30M Ω thereafter.

Input Current:

330nA for f.s.d. to 10V thereafter 1 μ A for 30V, 3.3 μ A for 100V, 10 μ A for 300V.

Accuracy: 3% or better.

A.C. METER

Ranges:

3mV, 10mV, 30mV, 100mV, 300mV, 1V, 3V, 10V, 30V, 100V, 300V.

Input Resistance:

3M Ω +35pF 3mV–1V.

10M Ω +15pF 3V–300V.

Frequency Response:

± 0.5 dB 20Hz–200kHz

± 3 dB 10Hz–400kHz.

Noise:

10 μ V on 3mV range, input short circuited.

Accuracy: 3% or better.

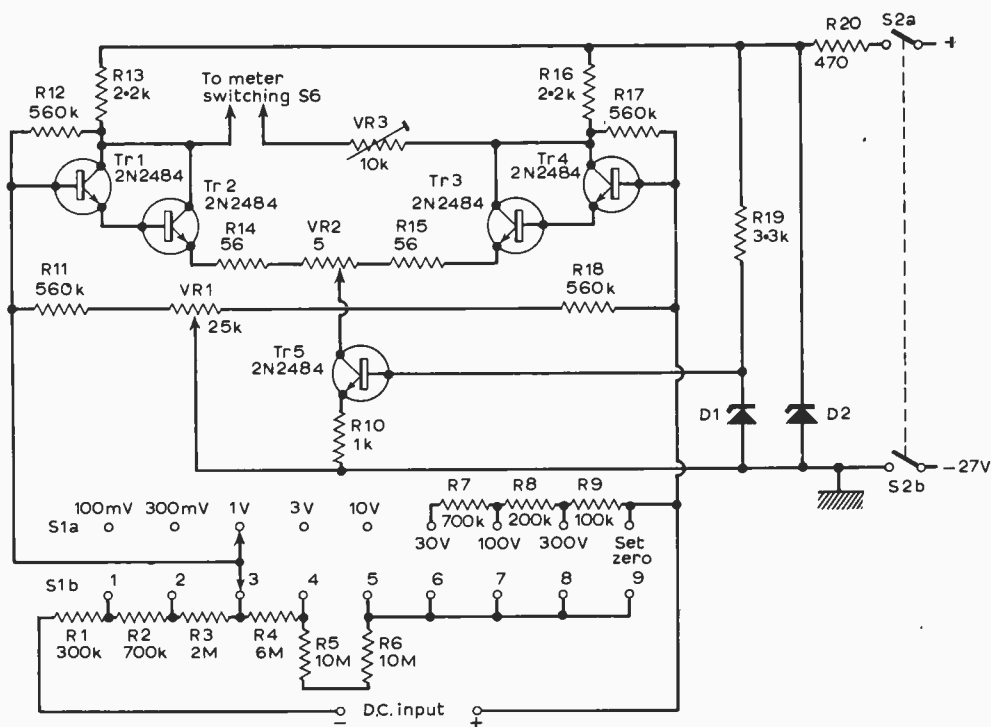


Fig. 1: Complete circuit of the d.c. differential amplifier.

Assuming the zero is initially correct, drift is caused by a component altering its characteristics. The adoption of high stability close tolerance resistors assists in the maintenance of good zero stability, and also by the use of silicon transistors. The biggest enemy of good zero stability is a temperature differential existing between components, principally the transistors on "opposite" sides of the meter. This can be easily demonstrated on the completed instrument by lightly resting a finger—nothing warmer is required—on one of the input transistors, when the zero will be seen to rapidly drift. Even the output transistors will cause a change in the zero setting, though this is usually less severe than the drift due to the input transistors. On removing the finger, or by placing another finger on the "opposite" transistor, the zero setting will be restored, assuming equality of finger temperature of course! The temperature differential can be minimised by placing the opposite pairs of transistors in close proximity or by enclosing them in a common heatsink, though normally a heatsink is quite unnecessary due to the minute power dissipation in each transistor.

Heavy negative feedback is developed in the circuit in two ways. Firstly, by means of R12 and R17 which are returned to the collectors, and thus passes back any variation in collector voltage to the base. Secondly, by means of R14 VR2 and R15, as variations in emitter voltage take place through the common load Tr5, and are therefore once again in opposition. The effect of this feedback is threefold. It stabilises amplifier gain, reduces zero drift, and improves linearity.

Equalisation of the emitter and base voltages is effected, as already explained, by VR1 and VR2. As both affect the collector voltages, it is necessary to adjust VR2 first by temporarily short-circuiting the bases of Tr1 and Tr4 together. The s-c is then removed and the bases are equalised by VR1. As there is a degree of mutual interdependence, several attempts are necessary before correct zero is obtained.

We come at last to the purpose of Tr5, which serves two purposes. Firstly, it improves the common mode rejection ratio, which is the ability of the amplifier to amplify the wanted signal applied to the bases of Tr1 and Tr2 differentially, and to reject any unwanted signal that may reach both bases simultaneously. This purpose is fulfilled by Tr5 in a most acceptable manner. The other purpose of Tr5 is almost incidental. It improves the stability of the amplifier gain most markedly, so that whilst the zero shifts with changing supply voltage (temporarily disregarding D2) the gain remains constant.

When the amplifier was first built, a sensitivity exceeding 20M Ω /V was obtained. Zero stability was however unacceptably poor, drifting (in time) to the extent of $\pm 10\mu\text{A}$, and it was necessary to improve matters. As feedback was at a maximum, it was decided to reduce the sensitivity of the meter movement. This was done by means of VR3 and the zero drift dropped to about $\pm 1\mu\text{A}$, the input resistance dropping to 3M Ω /V.

Another reason for reducing the sensitivity was the virtually impossible task of obtaining economically the very high value resistors necessary. Assuming one would tolerate a slow drift of $\pm 10\mu\text{A}$, where would one obtain a resistor of 6,000M Ω in order to provide a 300V range? Even with the sensitivity

reduced to the level of 3M Ω /V, a series of shunt resistors (R7 R8 R9) are required to keep within the range of easily obtained resistor values.

Range switching is effected by S1a and S1b. S1b switches in the series resistors R1-R6. After R6, the contacts are connected together and S1b is used to bring the series of shunt resistors into circuit, so reducing the sensitivity and allowing a maximum voltage of 300V to be measured. In the final position, position 9, S1a and S1b are arranged to s-c the bases of Tr1 Tr4 together, so allowing emitter zero to be set. This end of the scale was deliberately chosen so that, having set zero, one started at 300V and worked way down the scale, so obviating the possibility of setting zero and then absentmindedly (it has been done) trying to measure 300V on the 300mV switch position.

The power supply of 27V is provided by three 9V batteries in series. This is dropped to, and stabilised at 20V by R20 and D2. The current consumption is very modest and the batteries should have a long and useful life. On/off switching is effected by S2a-b, a miniature slide two-pole two-way switch.

AC Amplifier

As far as the a.c. amplifier is concerned, at least two bipolar transistors, in the Darlington configuration, would be required to provide the requisite high input resistance and the use of an f.e.t. in this position was considered to be a viable proposition. The a.c. amplifier, Fig. 2, is basically quite simple. The a.c. input is applied to a coarse attenuator comprising S3a-b, R21 TC1 and R22 C1. The output from the slider of S3a is applied via C2 to the gate of the f.e.t Tr6. Bias to this stage is by means of the gate resistors R26-R32 in the source circuit, the source current being 450 μA . Bootstrapping of Tr1 is by means of C3 which feeds back the a.c. signal at the source to the junction of the gate resistors R23 R24 and R25. The input resistance of Tr6 stage is in the region of 5M Ω in parallel with 3.5pF.

From the wiper of S3b, the a.c. signal is passed via C6 to the base of Tr7, which is the input transistor of the amplifier proper comprising Tr7 Tr8 and Tr9. These three transistors are d.c. coupled throughout. The coupling, from Tr9 collector to Tr7 base forms a d.c. feedback loop that very effectively stabilises the collector currents of all three transistors. Since only d.c. feedback is wanted along this route, a.c. decoupling is necessary and is effected by C7. Originally, R37 and R38 were used for feedback purposes, being 270k Ω each. However, due most probably to the variation in the d.c. leakage resistance of C7, the d.c. conditions tended to be somewhat unstable. No sooner were R37 and R38 selected for the requisite collector current in Tr9, than they had to be changed again. Reducing R37 and R38 and introducing R41, small in comparison to the leakage resistance of C7, has improved matters and the d.c. characteristics are now stable.

Negative feedback with all its advantages is via meter rectifier diodes D3-D6 and C10 to the emitter circuit of Tr8. Variation of feedback and hence of the amplifier gain, is effected by VR4 and C9. When the slider of VR4 is at the earthy end of its travel,

feedback is at minimum, the emitter is short-circuited (to a.c.) by VR4 and the amplifier gain is at a maximum. With VR4 slider at the emitter end of its travel, C9 is uncoupled, feedback is at a maximum and the amplifier gain is at minimum. Variation of VR4 allows the gain to be set at any intermediate figure. The meter deflection for any given input can therefore be set within quite wide limits, thereby allowing for the variation in hfe between individual transistors.

So much for the "active" side of the circuit. We come now to the "passive" side, the attenuator

Briefly then, the primary attenuator passes all voltages below 1,000mV or 1V to the gate of Tr6, the secondary attenuator which is of course coupled to the primary attenuator, tapping off the sequence 1-3-10-30 etc., so that the input to Tr7 never exceeds 3mV. The "attenuation" factor of the primary attenuator is, at this stage, zero, i.e. the a.c. input is fed directly to the gate of Tr6 via the d.c. blocking capacitor C2.

Voltages exceeding 1V are still fed to the gate of Tr6 via C2, but have now to pass through the primary attenuator which now offers an attenua-

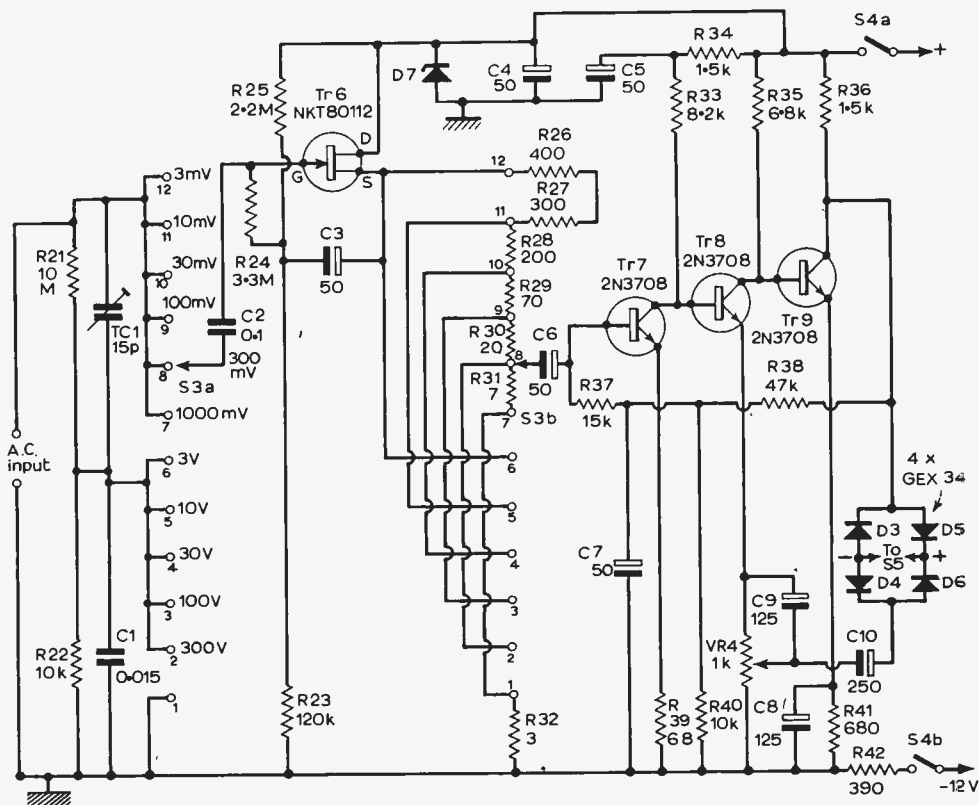


Fig. 2: The a.c. amplifier—note the use of an f.e.t. in the input.

comprising S3a-b together with other sundry components. The "split" attenuator used is a time-honoured design intended to overcome a number of problems involving input resistances and voltage, and frequency compensation. The sensitivity of the main amplifier Tr7-Tr9 is 3mV for f.s.d. on the meter. Inputs exceeding 3mV will cause the meter to exceed f.s.d and if excessively high, could damage the transistors and/or the meter. In the source circuit of Tr6 is a six position (essentially) attenuator that limits the input to Tr7 to 3mV on each of its ranges. The total resistance of this chain of resistors comprising R26 to R32 is 1,000Ω, low enough not to require frequency compensation at the frequencies involved.

The input stage Tr6 will accept voltages up to 1,000mV without undue stress. Since we will wish to measure voltages greatly exceeding this figure, the primary of the split attenuator is arranged to feed the gate of Tr6 limiting the input to 1,000mV or less.

tion of $\times 1,000$. The inputs to the base of Tr7 are still only millivolts, i.e. 3V is reduced to 3mV, 10V to 10mV and so on. The last five positions of the secondary attenuator are connected to the first six, i.e. 1 to 7, 2 to 8, and so on, so that the 1-3-10 sequence established for millivolts is still retained for volts, and the main amplifier still receives its requisite 3mV for meter f.s.d.

Frequency compensation of the primary attenuator is eased by having only two attenuation factors, of $\times 0$ and $\times 1,000$. Since the $\times 0$ is straight through, only the $\times 1,000$ requires compensation, and this is effected by TC1, which is set so that the time constant of $TC1 \times R21$ is equal to the time constant of $C1 \times R22$, the frequency response then being, in theory anyway, to infinity.

The primary and secondary attenuators are built on two separate single-pole twelve-way wafers mounted on a common spindle, thus transference of the primary attenuator from volts to millivolts, and

★ components list

Resistors:

R1 300kΩ 1% 1W	R23 120kΩ
R2 700kΩ 1% 1W	R24 3.3MΩ
R3 2MΩ 1% 1W	R25 2.2MΩ
R4 6MΩ 1% 1W	R26 400Ω 1% 1W
R5 10MΩ 1% 1W	R27 300Ω 1% 1W
R6 10MΩ 1% 1W	R28 200Ω 1% 1W
R7 700kΩ 1% 1W	R29 70Ω 1% 1W
R8 200kΩ 1% 1W	R30 20Ω 1% 1W
R9 100kΩ 1% 1W	R31 7Ω†
R10 1KΩ	R32 3Ω†
R11 560kΩ	R33 8.2kΩ
R12 560kΩ	R34 1.5kΩ
R13 2.2kΩ	R35 6.8kΩ
R14 56Ω	R36 1.5kΩ
R15 56Ω	R37 15kΩ
R16 2.2kΩ	R38 47kΩ
R17 560kΩ	R39 68Ω
R18 560kΩ	R40 10kΩ
R19 3.3kΩ	R41 680Ω
R20 470Ω	R42 390Ω
R21 10MΩ 1% 1W	R43 2.2kΩ
R22 10kΩ 1% 1W	R44 2.2kΩ

All resistors 5% $\frac{1}{2}$ W hi-stabs except where shown as 1% 1W. * R5 R6 may be replaced by single 20MΩ 1% if available. † R31 R32 may be selected from 10% range or wound from 36 s.w.g. Eureka wire. 42.5cm and 18.5cm for 7Ω and 3Ω respectively.

Switches:

- S1a, b, S3a, b R.S. "Maka-switch" shafting (2 off)
Four single pole twelve-way wafers.
- S2 Two-pole two-way slide switch
- S4 Two-pole two-way slide switch
- S5 Two-pole two-way slide switch
- S6 Two-pole two-way slide switch

Meter:

50μA f.s.d. Sifam type M404, 4½in. square. Scaled 0-3 and 0-10 (internal resistance 1250Ω) or similar.

Capacitors:

C1 0.015μF silver mica or paper
C2 0.1μF paper 250V wkg. p.c. mounting (see note below)
C3 50μF 15V wkg. p.c. mounting
C4 50μF 15V wkg. p.c. mounting
C5 50μF 15V wkg. p.c. mounting
C6 50μF 15V wkg. p.c. mounting
C7 50μF 15V wkg. p.c. mounting
C8 125μF 6V wkg. p.c. mounting
C9 125μF 6V wkg. p.c. mounting
C10 250μF 6V wkg. p.c. mounting
C11 1000μF 6V wkg. p.c. mounting
TC1 15pF trimmer

Note: D.C. working voltage of C2 depends on magnitude of d.c. it is likely to be connected across. For example, when measuring a.c. ripple on a high potential d.c. supply, the difference could easily be 300V d.c. to 100mV a.c. or even greater.

Semiconductors:

- Tr1 to Tr4 2N2484
- Tr5 BC109
- Tr6 NKT80112
- Tr7 to Tr9 2N3708
- D1 3.9V 5% 400mW zener
- D2 20V 5% 400mW zener
- D3 to D6 GEX34
- D7 7.5V 5% 400mW zener
- D8 and D9 1S940

Potentiometers:

- VR1 25kΩ w.w. or carbon linear
- VR2 5Ω w.w. linear or up to 25Ω w.w.
- VR3 10kΩ linear, skeleton p.c. mounting
- VR4 1kΩ linear, skeleton p.c. mounting

Miscellaneous:

Knobs; ½in. r.h. chromed 6BA screws with nuts; ½in. self-tapping screws; insulated wire assorted colours; terminals, two red, two black, one black earthing type.

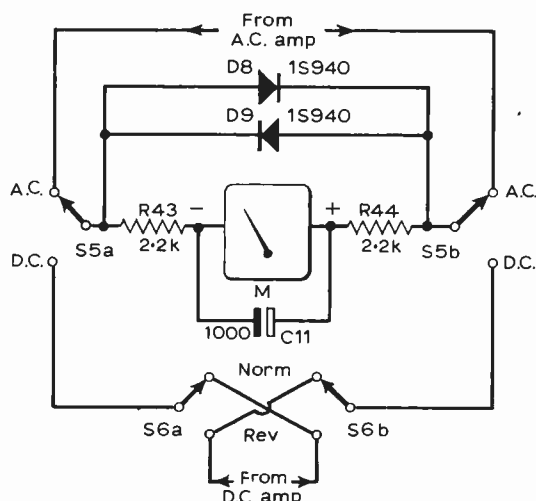


Fig 3: Switching circuitry, relevant to the moving coil meter and amplifiers.

of the two "separate" sections of the secondary attenuator, are completely automatic. The synchronisation of the primary and secondary attenuators on to a common switch means only one switch has to be manipulated in order to measure any voltage from 3mV to 300V.

The power supply is again by means of batteries, two of 6V each being employed to give a 12V supply. This is then dropped to, and held at the required 7.5V by R42 and the zener diode D7. The current consumption is quite modest and the batteries should have a usefully long life. On/off switching is effected by a miniature two-pole two-way slide switch, S4.

In the interests of economy, which is of more interest to the average amateur than the slight increase in operating time, a single meter is used, switched into the output of either amplifier as required by S5. On a.c. the meter connects straight into the output of the a.c. amplifier; but for d.c. a polarity reversing switch S6 is interposed between the meter movement and the d.c. amplifier.

TO BE CONTINUED

READY CALIBRATED

SIGNAL GENERATOR

F. G. RAYER

A SIGNAL generator giving an audio output, c.w. or modulated output in the range about 150kc/s to 35Mc/s is extremely useful for stage-by-stage checks of audio and intermediate frequency stages, the alignment of i.f. and aerial circuits, and similar purposes. When such an instrument is constructed, its calibration can be something of a problem unless other accurately calibrated equipment or means of calibration are available.

To overcome this difficulty the signal generator described here has ready-made fixed-inductance coils L1, L2, L3, L4 and L5, see Fig. 1, tuned by a particular specified variable capacitor VC1. As these coils are manufactured to high accuracy and other items have very little influence on frequency, it is possible to adopt ready-made scales.

Five bands are covered, as follows:

- (1) 35-10Mc/s (2) 10-3.2Mc/s (3) 4-1.2Mc/s
- (4) 1500-425kc/s (5) 450-150kc/s

This covers all bands from about 9-2000 metres and includes those frequencies generally needed for i.f. circuit alignment. Tuning is by means of a reduction drive which has a 0-100 logging scale so frequencies can be written directly on the dial.

In Fig. 1, V1a is the r.f. oscillator, each coil L1 to L5 having its own feedback winding selected by SW1b. R.F. is taken through R3 and C3 to VR1, which allows adjustment of output; C5 isolates external circuits. Space was left for a buffer/amplifier between V1a and the output circuit, but with r.f. taken from the feedback windings in the way shown, such a stage was found unnecessary.

V1b is the audio oscillator, with transformer T1; the audio tone can be provided as output through C4 or used to modulate V1a. With SW2 at "c.w." an unmodulated radio frequency signal is obtained, with this switch at "Mod." the r.f. signal is modulated and thus audible on an ordinary receiver. When the switch is at "a.f." an audio frequency output is obtained for a.f. circuit tests.


Cabinet and chassis

A strong and inexpensive case is made from "Universal Chassis" members, the case top, chassis, and case bottom are 8 x 3in. and flanged. Cut away $\frac{1}{2}$ in. from the ends of the long flanges on one 8 x 3in. member so that it will fit inside the side members which are 7 x 3in. This 8 x 3in. item forms the chassis and it is bolted to the 8 x 7in. plate (panel) $2\frac{1}{2}$ in. from the bottom, see Fig. 2.

L3, L5 and T2 are fixed to the panel before fitting the dial using countersunk bolts. Wiring is completed and the signal generator is tested before adding the bottom and right-hand side (viewed from the rear). The box is closed with perforated zinc, or with a second 8 x 7in. plate in which holes have been punched. Self-tapping screws have to be used here.

Layout from behind

Figure 2 shows the positions of most components; the drive listed has a paper template as a guide to

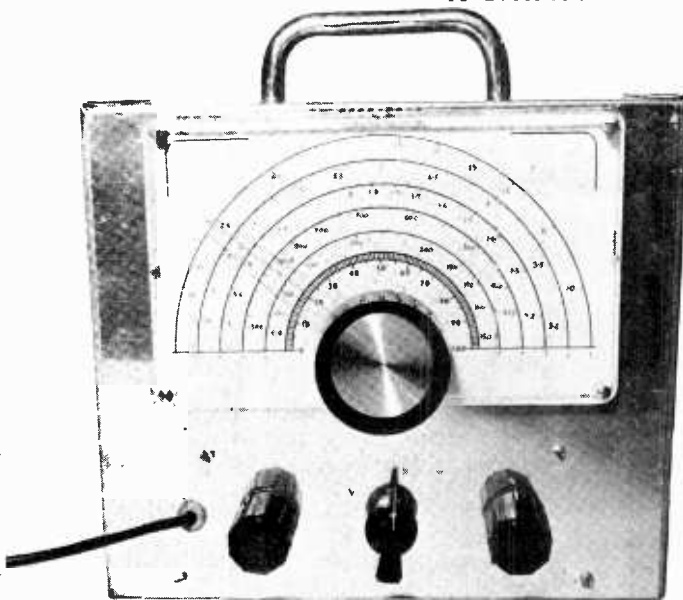

drilling. An insulated lead is soldered to the lower fixed tag of VC1, before mounting this item and passes down through a hole to SW1a.

C6/C7 is a dual capacitor and its common negative tag is connected to the chassis. The contact-cooled rectifier D1 is held by means of bolts.

The positions for other items can be seen from Fig. 3. T1 should have a ratio of about 3:1, and a primary suitable for the combined anode currents of both sections of the ECC81; transformers intended for use with transistors are not suitable. Connections in Fig. 3 are for the specified transformer. If another transformer is used and no audio tone is obtained, reverse the connections to one winding.

A three core flexible cord is required for the mains lead, and the earth conductor is secured to the case by a bolt holding the chassis and side together. Output was arranged with a co-axial lead, the inner conductor going to C5 and the outer brading to chassis. A co-axial socket may be preferred as shown in Figs. 2 and 3.

Coils and switching

The coils are placed to allow short connections for the h.f. ranges, and to prevent absorption by windings not in circuit. Red tags go to SW1a. For ranges 2, 3, 4 and 5 the next tag clockwise goes to SW1b. The next tag on all coils is wired to chassis, and the remaining tag of coils for ranges 2, 3, 4 and 5 go to the h.t. circuit at C2. For range 1, tag 2 goes to R2, and tag 4 to SW1b (anode), Fig. 3. The following details should be helpful.

Range 1. Solder a $\frac{3}{4}$ in. wire from red tag to adjacent tag of SW1a. Take a wire $1\frac{1}{2}$ in. long from

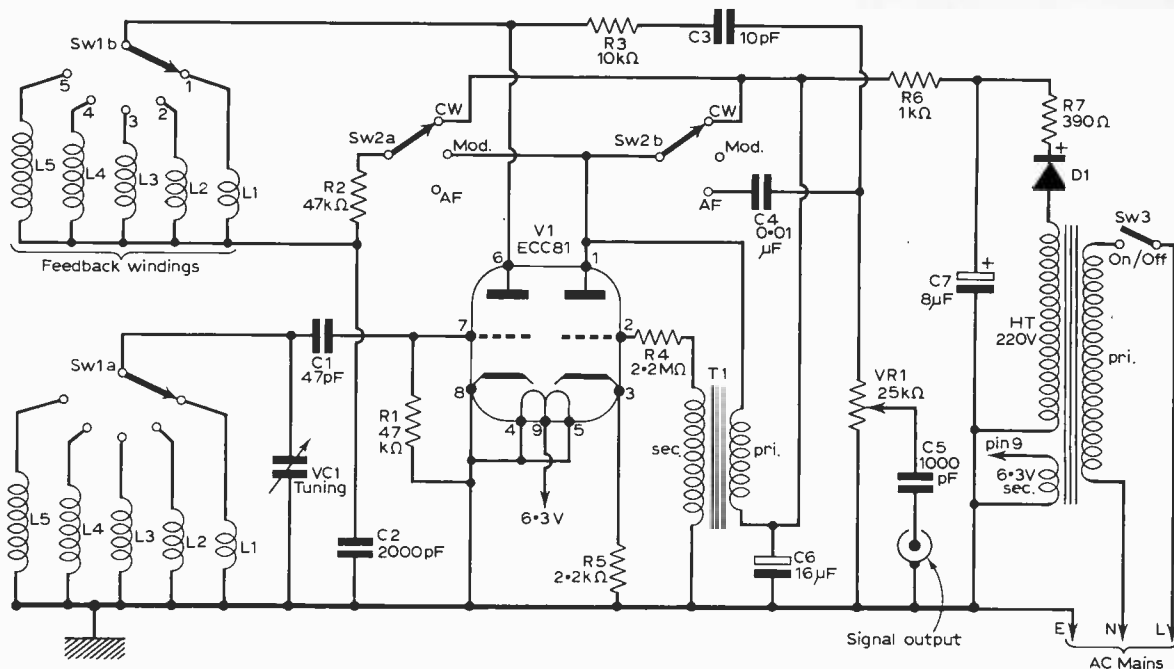


Fig. 1. The circuit of the ready calibrated signal generator.

★ components list

tag 3, directly to chassis near the valve, Fig. 3. Join C2 immediately between this chassis tag and tag 2 of L1. Connect tag 4 to SW1b.

Range 2. This coil mounts on the case side, Figs. 2 and 3. The wire from SW1a to tag 1 is $\frac{1}{2}$ in. long, and the chassis return from tag 3 is $1\frac{1}{2}$ in. long. Tag 4 is wired directly to C2 and tag 2 on L1.

Range 3. This is mounted on the panel in the position shown in Fig. 2. Leads pass down through the chassis, and their exact length has no significant effect on frequency coverage.

Range 4. This is secured to the chassis, Fig. 2. As with other coils, it is a little over the coil-diameter away from metal parts.

Range 5. This is mounted above L3, leads passing down to the switch.

Coil connections are shown in Fig. 3. Referring to Fig. 1 and Fig. 3, switching must be so arranged that each tuned winding L1 to L5 is selected by SW1a and the appropriate anode winding is in circuit (via SW1b) at the same time. Feedback windings must also be in correct phase or no r.f. output will be obtained.

Function switch

In the "c.w." position, SW2a applies h.t. to the r.f. oscillator, and SW2b shorts the primary of T1. With this switch in the "Mod." position, SW2a obtains h.t. for V1a from the anode of V1b, for a modulated output. In the "a.f." position, no h.t. reaches V1a, and a.f. from V1b is via C4 to the output circuit.

Scales

The drive listed has a half-cursor, used temporarily for calibration. Marks made along the straight edge of this cursor will afterwards be under the hair-line of the normal cursor. One scale provided with the

Resistors:

R1 47kΩ $\frac{1}{2}$ -watt	R5 2.2kΩ $\frac{1}{2}$ -watt
R2 47kΩ 1-watt	R6 1kΩ $\frac{1}{2}$ -watt
R3 10kΩ $\frac{1}{2}$ -watt	R7 390Ω $\frac{1}{2}$ -watt
R4 2.2MΩ $\frac{1}{2}$ -watt	VR1 25kΩ carbon linear pot

Capacitors:

C1 47pF silver mica	C5 1000pF mica
C2 2000pF 500V disc ceramic	C6 16μ 350V
C3 10pF silver mica	C7 8μF 350V
C4 0.01μF 400V	
VC1 500pF Jackson E1, Home Radio (Mitscham) Cat. No. VC5.	

Fixed Inductance Coils:

L1 0.5μH Home Radio (Mitscham) Cat. No C084D
L2 5.5μH " " " " " C084E
L3 37.5μH " " " " " C084F
L4 310μH " " " " " C084G
L5 2200μH " " " " " C084A

Miscellaneous:

T1 3 : 1 12mA Home Radio (Mitscham) Cat. No T1V1
T2 Half-Wave 200/230V 25mA, 6.3V 0.5A or similar
D1 250v contact-cooled rectifier.
Drive and Dial, Electronics, SMD2
8 x 7 x 3in. Universal Chassis box and extra 8 x 3in. runner
8 x 7in. perforated zinc
Type A, H2, 4in. handle (Home Radio)
Mains toggle switch
2-pole 3-way rotary switch
2-pole 6-way ditto
Three knobs
3-tag strip (2 insulated)
Co-axial socket or cable, 3-core mains cord, etc.
ECC81 valve
B9A valve holder

drive is numbered 0—100 and has five spare ranges. The innermost is used for range 5 and the outermost for range 1. This agrees with the positioning of the bandswitch knob.

Readings should be taken from the calibration table and written on the spare scales. Set VC1 fully closed and the cursor at 100 before beginning. When markings are finished, fit the usual cursor and dial cover.

If the generator is assembled as shown, with the specified coils and VC1 as listed, accuracy should be similar to that of popular, ready-made signal generators. The coils are doped, and so calibration should not change.

If the necessary equipment is available, there is no reason why the generator should not be individually calibrated from this source. The calibration table will then provide a close guide. The use of an all-wave communications type receiver and 1Mc/s and 100kc/s crystal oscillators will allow most satisfactory and easy calibration. The required 1Mc/s or 100kc/s harmonics are tuned in on the receiver and the signal generator is then tuned to the same frequency and its scale marked. The 500kc/s and 50kc/s markings can be obtained by beating the generator 2nd harmonic against the 1Mc/s or 100kc/s crystal harmonics.

Generator uses

It is only proposed to give brief notes on these.

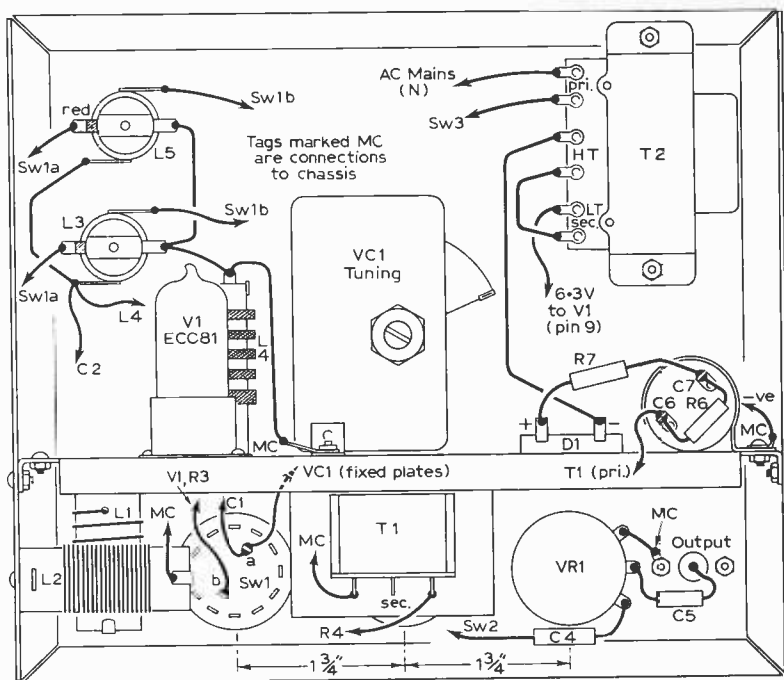


Fig 2: The component layout viewed from the rear. The added chassis plate is fixed 2 3/4 in. from the bottom.

as more comprehensive details have appeared from time to time.

AF CIRCUIT CHECKS. If a receiver or audio amplifier gives no results an audio signal can be injected, working back point by point from the output stage. When the source of the fault has been passed, the audio tone is no longer heard in the speaker. Investigation is then confined to one stage or a few components or connections.

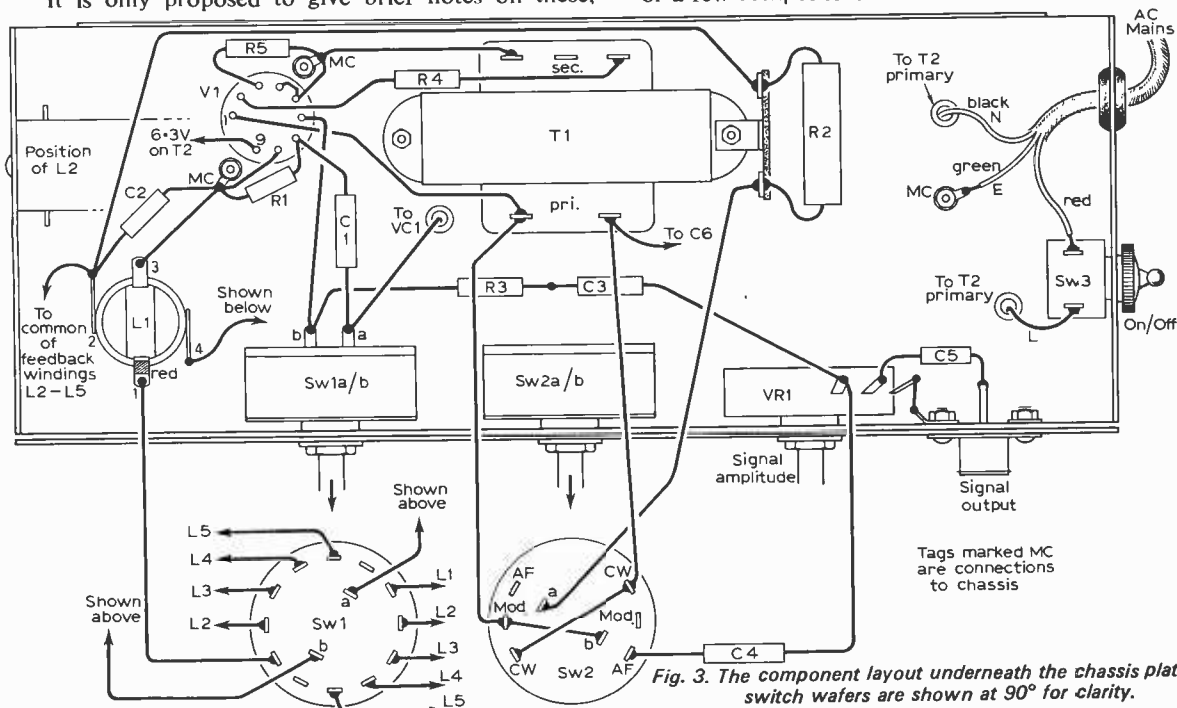


Fig. 3. The component layout underneath the chassis plate; the switch wafers are shown at 90° for clarity.

IF CIRCUIT CHECKS. A fault in the intermediate frequency section of a receiver, causing lack of reception, can be quickly found by injecting a modulated r.f. signal in at the final i.f. transformer, working backwards from here, stage by stage. Signals stop when the fault has been passed. Thus a single i.f.t., transistor, or valve, and its associated wiring etc., only need be checked in detail. If the intermediate frequency is not known, tune the signal generator until the receiver provides an audible output (probably around 455-470kc/s, for most receivers; or around 1.6Mc/s for s.w. receivers or the first i.f. section of dual-conversion receivers).

IF CIRCUIT ALIGNMENT. A signal of the appropriate frequency is injected at various points in the i.f. amplifier and the i.f.t.'s are adjusted for best results.


RF CIRCUITS. Wavebands of a receiver can be trimmed and aligned to secure best results or agreement with a calibrated dial on the receiver. A direct connection is usually not needed, the generator output lead inner conductor being placed near the receiver aerial circuit.

CALIBRATION TABLE

Range 1		Range 4	
Mc/s.	Dial	Kc/s.	Dial
35	9	1500	5½
30	15	1300	11
28	17	1100	18½
25	22	1000	23
20	33½	900	28
17	44	800	36
15	53	700	46½
14	59	600	57½
13	65	550	65
12	71½	500	74
11	80½	450	85½
10	91	425	92

Range 2		Range 5	
Mc/s.	Dial	Kc/s.	Dial
10	5	450	5
9.5	8	400	11
9	11	350	17½
8	17½	300	29
7	25½	250	43½
6	36½	220	55
5	50½	200	64
4.5	60	180	74½
4	71	170	81
3.8	76	160	88½
3.5	85	150	97
3.2	96½		

Range 3		The positions for intermediate markings can be estimated.
Mc/s.	Dial	
4	5½	
3.5	11½	
3	18	
2.5	29	
2	45	
1.8	53	
1.7	57½	
1.6	63	
1.5	69	
1.4	76	
1.3	84	
1.2	94	

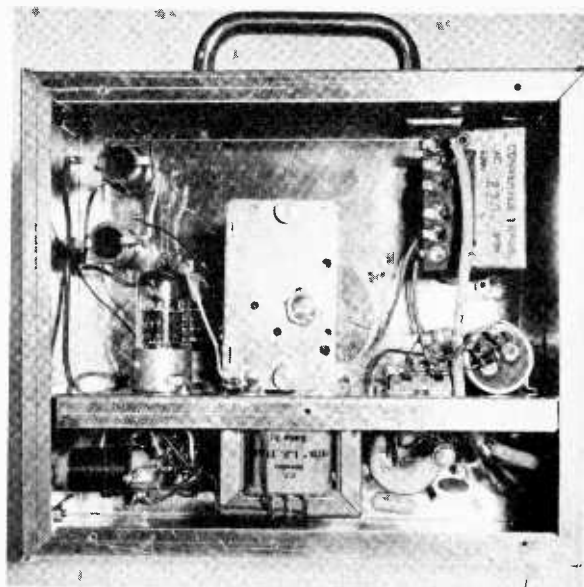

An interior view of the finished signal generator.

In all tests signal strength is kept down to avoid overloading stages in the receiver. The c.w. signal will operate a tuning meter or indicator, and is most suitable for some adjustments. For an audible signal with r.f. tests, the switch is placed at "Mod." ■

PRACTICAL TELEVISION

IN THE JULY ISSUE

WAVEFORMS IN COLOUR RECEIVERS

There are many more waveforms in a colour receiver than in a monochrome one—the colour-difference signals, the ident, reference oscillator and burst signals, various pulse trains, convergence waveforms and so on—and a knowledge of these is an essential aid to colour receiver servicing. A comprehensive guide is provided by Gordon J. King in this new illustrated series.

AERIALS FOR ALL!

A corner reflector u.h.f. loft aerial with bow-tie dipole which has a gain equal to a 9-12 element Yagi array and, for DX enthusiasts, a Band I omnidirectional X array.

FIELD LINEARITY FAULTS

Field linearity faults are a common cause of picture distortion. A detailed guide to fault-finding in this part of the receiver is provided.

ON SALE JUNE 20

CODAR CR.70A

Communications Receiver 540-10 metres



The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £21 the CR.70A is outstanding value for money. In four stable ranges the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres, where the rapidly improving conditions that now prevail allow the regular reception of world-wide call-signs!

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5 1/2" x 7 1/4" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months!

New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.

20 gns.

Carriage 7/6 extra

*Ideal for SWLs *5 valves (inc. two twin triodes) giving 7 valve line-up *Excellent on amateur and shipping frequencies *Calibrated signal strength meter (illuminated) *Automatic volume control *Separate B.F. oscillator for morse and S.S.B. signals *Two speed vernier tuning *Separate output for recording etc.



T21 RECEIVER FOR 160 & 30 METRES AMATEUR BANDS
Provides 18-24Mc/s and 3-5-9 Mc/s. bandspread 18-24Mc/s and 3-5-9 Mc/s. 12 volts, only 8" x 4" x 3 1/4". Ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £15.17.6. Carr. 4/6.



CR45 MAINS T.R.F. SHORT-WAVE RECEIVER

World wide reception. *Separate electrical band-spread. *33 slow motion drives. *Output 3 watts for 2/3 ohm speaker. *Valves ECC81, EL84, E280. Size 12" x 5 1/2" x 7". CODAR-KIT CR.45K with 3 coils (10-28, 25-75, 60-176 metres). £9.15.0. Carr. 6/-, or ready built CR.45 £11.19.6. Carr. 6/-. Extra coils 5/4 each.



R.F. PRE-SELECTOR MODEL P.R.30

Provides up to 20dB gain plus substantial image rejection. Improved signal/noise ratio and selectivity. Power requirements 180-250 volts 12mA H.T. 8.3 volts, 3 amp L.T. Size 8 1/2" x 5" x 4". Ready built complete with cables, plugs and instructions. £5.19.6. Carr. 4/6. Self-powered P.R.30X £7.19.6. Carr. 4/6.



MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER

*Can be built in one evening. *Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price £2.4.6. Carr. 3/-. Extra coils 5/4.

CRC **CODAR RADIO COMPANY**
UNIT 7, MEADOW ROAD, INDUSTRIAL ESTATE,
EAST WORTHING, SUSSEX. WORTHING 37315
World-wide Mail Order Service


Please supply—
(tick as required)
☐ I enclose cheque/
M.O./P.O. value of
£.....

NAME
ADDRESS

☐ No stamp enclosed
for leaflets

POST ORDER FORM TODAY

DE LUXE STEREO AMPLIFIER

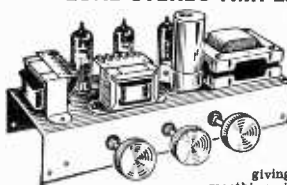

A.C. mains 200-240 volts. Using heavy duty fully isolated main transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: —2 × ECL86 Triode Pentodes, 1 × EZ80 as full wave rectifier. Two Dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A Dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV. for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs. Chassis size 11" x 4 1/2" x 4 1/2". Overall height including valves 5". Ready built and tested to a high standard. PRICE 8 gns. P. & P. 8/-.

hum. Valve line up: —2 × ECL86 Triode Pentodes, 1 × EZ80 as full wave rectifier. Two Dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A Dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV. for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs. Chassis size 11" x 4 1/2" x 4 1/2". Overall height including valves 5". Ready built and tested to a high standard. PRICE 8 gns. P. & P. 8/-.

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response +3dB. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 4 amp. PRICES: AMPLIFIER KIT \$10.10.0; POWER PACK KIT \$3.0.0; CABINET \$3.0.0. All Post Free. Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).



SPECIAL PURCHASE!
E.M.I. 4-SPEED PLAYER
Heavy 8 1/2 in. metal turntable. Low futter performance 200/250 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with 1/2 stylus for LP/78. ONLY 68/- P. & P. 6/6.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
E.M.I. Model 999 Single Player with unit mounted pick-up arm and mono cartridge . . . \$55.0
B.S.R. UA25 with latest mono compatible cart. \$61.98
All plus Carriage and Packing 6/6
LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest prices! PLINTH UNITS cut out for Garrard Models, 1025, 2025, 3000, 3000, AT60, SP25. With rigid perspex cover. OUR PRICE 6 gns. complete. P. & P. 6/6

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/78. Only 32/6. P. & P. 2/-.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono stereo records on mono equipment. Only 30/- P. & P. 2/-.
SONOTONE 9TAHC compatible Stereo Cartridge with diamond stylus 50/- P. & P. 2/-.
FEW ONLY! ACOS High-G Mono Cartridge for EP and LP. Only 10/- P. & P. 2/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI

● Peak output in excess of 1 1/2 watts.
● All standard British components.
● Built on printed circuit panel size 6 x 3 in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET114 or 81 Mullard AC128D) and matched pair of AC128 o/p.
● 9 volt operation.
● Everything supplied, wire, battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/- P. & P. 3/- Also ready built and tested, 52/6. P. & P. 3/-.



8-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates EOC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 45.5.0. P. & P. 6/-.


10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2EL84s, EOC83, EF86 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0. P. & P. 8/6.

BRAND NEW 8 OHM LOUDSPEAKERS
5in. 14/-; 6in. 18/6; 8in. 27/-; 7 x 4in. 18/6; 10 x 6in. 27/6
E.M.I. 8 x 5in. with high flux magnet 21/- E.M.I. 13 x 5in. with high flux ceramic magnet 42/- (15 ohm 45/-)
E.M.I. 13 x 8in. with two built-in tweeters and crossover network, 3 or 15 ohms 4 gns. P. & P. 5in. 2/-; 6 1/2 x 8in. 2/6
10 x 12in. 3/6 per speaker.
BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiDux ceramic ferrobar magnet assembly 26.10.0. P. & P. 6/-.
Guitar models: 25w. 26.0.0. 35w. 28.0.0.
E.M.I. 8in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

VYNAR AND REKINE SPEAKER AND CABINET FABRICS. Approx. 54in. wide. Usually 35/- yard. Our PRICE 18/6 per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

NEW! HSL.700 MONO TRANSISTOR AMPLIFIER

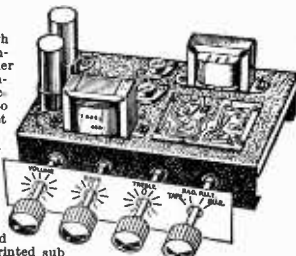

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240V. Controls: Bass, Treble, Volume/on/off. Function selector for PU1, PU2, Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 x 4 1/2 in. high.

Performance figures:
Sensitivity: PU1-50mV/v. 56K input impedance.
PU2-110mV/v. 1 meg input impedance.
Tape-110mV/v. 1 meg input impedance.
Radio-110mV/v. 1 meg input impedance.
Output power measured at 1Kc-6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohms. Overall frequency response 30 c/s-18 Kc/s. Continuously variable tone controls; Bass, +8 db to -12 db at 100 c/s. Treble, +10 db to -10 db at 10 Kc/s.
The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder pre-amp but is also capable of being used in conjunction with a guitar by connecting to PU1 socket and the peak output power will then be in the region of 15 watts. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, front spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.
Our Special Price £7.19.6 P. & P. 7/6.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6.
CARBON MIKE INSERTS. Brand new 2 1/2 in. dia. 5/- P. & P. 1/6.

QUALITY RECORD PLAYER AMPLIFIER MKII
A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7" w. x 5" d. x 6" h. Ready built and tested. PRICE 75/- P. & P. 6/-.
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.
DELUXE QUALITY PORTABLE R/P CABINET MKII
Uncut motor board size 14 1/2 x 12in. Clearance 2in. below. 4 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6. P. & P. 9/6

MAINS TRANSFORMER. Primary 200-240V two separate wave secondaries giving approx 16V at 1 amp and 20V at 1 1/2 amp; secs. can be connected in series for 36V at 1 1/2 amp. Ideal for transistor power supplies. Drop through mounting. Stack size 2 1/2 x 3 1/2 x 1 1/2 in. 18/- P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. 11/- P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6.

Open all day Saturday
Early closing Wed. 1 p.m.

A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Please write clearly
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

MOBILE S.W. LISTENERS

The Halson Mobile Antenna for
AMATEUR RECEIVING and
TRANSMITTING

The most efficient mobile All-Band
Whip on the market. COILS FOR ALL
BANDS. Complete with one coil
£6.17.6, plus 3/6. Extra coils £3.17.6,
plus 3/-.

From leading amateur radio stores or
direct from the manufacturers:

HALSON ELECTRICAL SERVICES
Dover Road, off Ansdell Road,
Blackpool.

Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the
Amateur enthusiast and constructor.
For 2 and 4 metres, the unique two
transistor model SR2/P, 70-150Mc/s,
75/6, p.p. 4s. New super 5V all-
wave, all-band kit, also "Mini-Amp"
self-contained, cabinet, size a mere
4 1/2 x 3 1/2 x 2 1/2. Write today, enclosing a
stamped addressed envelope for
interesting free literature, and details,
direct to

JOHNSON'S (RADIO)
St. Martin's Gate, Worcester

PLEASE MENTION

"PRACTICAL WIRELESS"

WHEN REPLYING TO

ADVERTISEMENTS

practically wireless

commentary by HENRY

No. 58

Hard
on
Hardware

YOU are always going on about computers, Henry: have you seen the latest news?

About the Edinburgh University computer that taught itself to balance a pole on a moving cart for 90 minutes, you mean? That must have been fun for Professor Donald Michie. The best one of his students could do was five seconds flat. I wonder if it was a caber that the Department of Machine Intelligence experimented with. That would have been worth watching at next year's Highland Games.

No, I was not being frivolous. I was referring to the chess matches.

Oh, that's old hat. Computers have been whacking men at chess and noughts and crosses since the abacus was invented by Confucius' nephew.

That is just the point. This was a Russian...

Confucius' red nephew then. What's the difference? Moscow has been crowing ever since their M-20 beat an American version some time last year.

You are getting warmer. It was actually the M-20 that was involved in this incident, in a contest sponsored by the *Uralsky Rabochy* and the Soviet Academy of Sciences' Institute of

Theoretical and Experimental Physics.

Sounds as if you are making this up!

Do not be sceptical, Henry. I am indebted for my information to *Janus of Electronics Weekly*, and the Soviet chess champion, Lev Polugayevsky.

Apparently the contest went on for four months. Playing against the computer were chess fans from 80 towns in the Urals, and this was the first mass competition to involve an electronic computer.

Evidently, you haven't heard about Operation Match.

Frivolity again, I am not concerned with computer selection of dating couples, and, anyway, that was in London. The point I am trying to impress upon you is that the USSR competition was arranged by feeding moves suggested by the majority of fans, via letters to the aforesaid newspaper, to the M-20 computer, which worked under the same programme it had used to beat the Americans in the straight computer match last year. So what! First prize a trip to Siberia; second prize a longer trip. The computer always comes out on top. What's the point of all this?

If you will stop interrupting, I'll tell you. During the play, the computer exhibited some "human" weaknesses. It began by taking an opposing pawn without due caution—and after 19 moves, the computer resigned.

SAY THAT AGAIN!

After nineteen moves the computer resigned. It could foresee an inevitable mate in three further moves. This would seem to indicate a triumph for the human mind, and some hope for the future of mankind in a world rapidly becoming more and more dominated by—

Shut him up, Mr. Editor. Who let that man in? Surely it is obvious that the computer was com-



After 19 moves the computer resigned

pletely bemused by the variation in approach, in style of play, by the 80 groups of fans, many of them probably mere enthusiastic amateurs, even in Soviet Russia. We must be careful how we treat our electronic brains. Look at what happened at St. Louis, and again at Harvard, for example. In the first case, an engineer fed a computer with the listed numbers in four local exchanges and the machine gave him back all the non-listed numbers. He then used these to get access to private-leased trunk lines. The *Wall Street Journal* doesn't tell us whether the computer was arrested as an accessory.

In the second case, students at Harvard used a computer, a recorder (the type you blow through), and their native ingenuity to imitate signalling tones and bypass the telephone company's billing computer, getting free calls anywhere. They even obtained access to Defence Department trunk lines—when they were finally caught. There is a thousand dollar fine for this Federal offence, but apparently these lads got away with it, after they had told the Trunks and Telegraphs Company exactly how they performed their anti-social swindle.



Computer that balanced a pole

pulse circuits in operation

I. J. KAMPEL

SATURATION switching was dealt with in last month's article. We shall now turn to various switching circuits, a large number of which employ saturation switching. Others avoid this in order to minimise the stored base charge.

The multivibrator is surely the simplest and the most familiar pulse circuit there is, yet the transistors seen in multivibrator designs are all too frequently required to operate in conditions which exceed their maximum ratings. Since most such ratings include a safety factor, operation under such conditions is usually satisfactory, but the practice can hardly be recommended. The multivibrator has an inherently slow rising edge, and it is not always appreciated that with a slight circuit modification, such a fallibility may be overcome.

The term "multivibrator" is frequently used erroneously to describe any two-transistor circuit which has regenerative action and switches between stable or quasi-stable states. The true "multivibrator" has two quasi-stable states, that is to say there are two basic states which the circuit may be in at any moment in time, but without any external stimuli, the circuit oscillates between these two states. The multivibrator may be used to generate an approximately square wave in its most basic form, or, with unequal quasi-stable states, act as a pulse generator. As such, the multivibrator may be the heart of a section of pulse circuitry.

Figure 2.1a shows the simplest form a multivibrator may take, with the two quasi-stable states as follows: Tr1 bottomed, Tr2 cut off; Tr2 bottomed, Tr1 cut off. Operation is as follows. When the circuit is initially switched on random current flows in the circuit, and even though basically a symmetrical circuit, the slightest unbalance, which must exist, will cause one or other of the transistors to take more current than its partner. In consequence, this transistor now turns fully on, the regenerative action to be described switching the other transistor into the OFF state.

Figure 2.1b shows the voltage waveforms at various points in the circuit for a short duration. We shall assume that initially Tr1 switches on. Base current flows through R2 and collector current through R1. The base-emitter voltage (V_{BE}) may be regarded as substantially constant at 0.7V for a silicon transistor, and for the rest of this article only silicon transistors will be considered. Since $V_{B1}=0.7V$, a current $I_{B1}=\frac{V_{cc}-V_{BE1}}{R2}$ is

set. This programmes the current which will flow in the

collector of Tr1 with no saturation since this will be the d.c. gain times the base current, i.e., $I_{C1}=h_{FE}I_{B1}$. The collector load is chosen such that Tr1 is driven into saturation with the programmed base current.

Section (a) of Fig. 2.1b shows the collector voltage during the first part of the cycle at V_{CEsat} , and part (b) shows the base voltage at V_{BE1} . During the initial period before Tr1 switched on, both capacitors have charged through the collector loads. As Tr1 switches on, the charge on capacitor C1 thus takes the base of Tr2

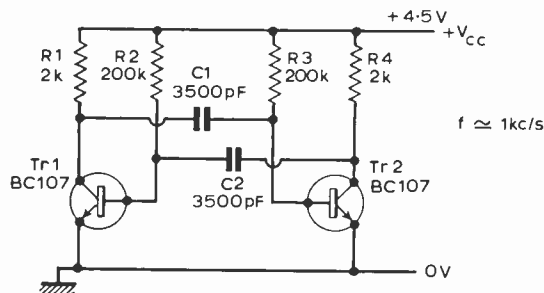


Fig. 2.1(a): The basic form of multivibrator (n-p-n).

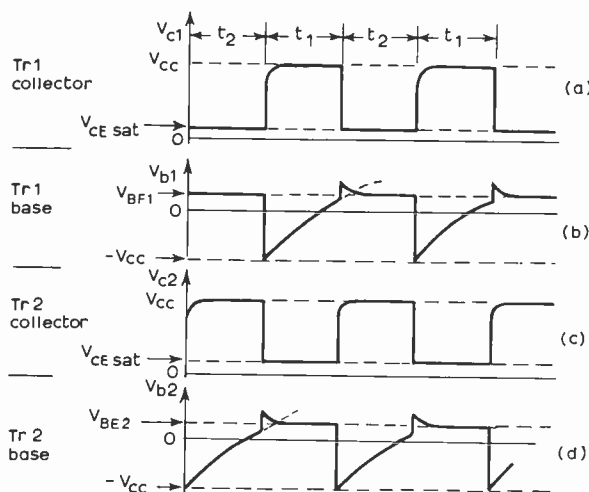


Fig. 2.1(b): Voltage waveforms of the multivibrator.

part two multivibrators

LIND-AIR OPTRONICS LTD

See our vast range of
Electronic Components
at our new
Component Centre
25 Tottenham Court Road



Battery Eliminator. Enables transistor equipment to be operated from AC mains. 6/9. 12v. output selector switch and on/off switch. Case size 4" x 2 1/2" x 2 1/2". Complete with mains lead, connecting leads and instructions. 59/8. P. & P. 3/6.

GARRARD DECKS



NR122 less cartridge £5. 9.6
1025 Stereo/Mono with cart. £8.19.8
2025 Stereo/Mono with cart. £7.19.8
3000S Stereo/Mono with cart. £9.19.8
30001 Stereo/Mono with cart. £10.19.8
8P25 less cartridge £11.19.8
8P25 with Decca Deram cart. £17. 4.6
SL55 less cartridge £11.19.8
SL55 with Decca Deram cart. £17. 4.6
SL55 less cartridge £14.9.6
Covers for above £2.19.8
Bases for above £2.10.0
AP75 less cartridge £18.19.8
SL75 less cartridge £28.7.0
SL85 less cartridge £28.19.8
Bases for above £4.19.8

SPECIAL OFFER!
8P25 less cart., with base £13. 2.6
P. & P. Decks 12/6. Cover 4/6. Base 4/6.
P. & P. Deck/Cover/Base 17/-.

"HI-TONE" LOUDSPEAKER
British made full range 10in. unit handles up to 10 watts. Ceramic magnet. Freq. response: 40-10,000 cps. Imp: 15Ω. Flux density: 10,000 lines. 49/6. P. & P. 4/6.

TTC C1001 MULTITESTER in leather case. 20,000 ohm. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. DC Current 0-50μA, 0-250mA. Resistance 0-60K, 0-6 Megohms. Decibels -20 to +22dB. Size of meter 4 1/2" x 3 1/2". 55/- P. & P. 3/6.



SOLDERING GUN
Comfortable grip with trigger control. "U" shaped 3in. bit to minimise wear. Light beam automatically directed on to end of bit when ON/OFF trigger is in use. 230-250 volts. 85 watt element. 49/8. P. & P. 3/6.

"ADASTRA" SOLDERING IRON. 30 watt. Employs its protective cover as a handle. AC 250/250v. With 4ft. lead 12/6. P. & P. 2/6.

NEW-VHF AIRCRAFT BAND CONVERTER. When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 108-135Mc/s. can be obtained. All transistor, 9v. battery operation. Fully tunable 18in. x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2in. 79/8. P. & P. 3/6.



STEREO AMPLIFIERS

DULCI STEREO AMPLIFIER MODEL 207



1Mohm. Phono 100mV into 1Mohm. 3 position selector on front panel. Frequency response: 40c/s to 10Kc/s ±2dB. Separate bass and treble controls with boost and cut. balance control. Mono/Stereo Function switch (both channels work in parallel). Normally £23.2.0. LIND-AIR PRICE 18/- Gns. Plus P. & P. 9/-.

8 watts per channel. Integrated high fidelity transistor Stereo amplifier. An attractive free standing unit with provision for mounting in equipment cabinet. Finish Dark Grey vinyl simulated leather grain. Front panel satin alloy. Specification: Sensitivity, Radio/Tape 100mV into 1Mohm. Phono 100mV into 1Mohm. 3 position selector on front panel. Frequency response: 40c/s to 10Kc/s ±2dB. Separate bass and treble controls with boost and cut. balance control. Mono/Stereo Function switch (both channels work in parallel). Normally £23.2.0. LIND-AIR PRICE 18/- Gns. Plus P. & P. 9/-.



NEW—SINCLAIR IC-10 INTEGRATED

CIRCUIT 10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/8. P. & P. 1/6

SPECIAL PURCHASE!

DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. Only 59/8. P. & P. 3/6.



NEW STEREO/MONO HEADPHONES

SDH-7. Soft rubber earpieces with slide switch for mono/stereo listening and 1/4" vol. controls. Impedance 8-16 ohm. Freq. response 25-15,000 cps. With lead and stereo plug. £6.0.0. P. & P. 3/6.

HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY
J1001 3" Long Play PVC 600ft. 225/- P. & P. 1/2.
J1002 3" Triple Play PVC 600ft. 10/6 P. & P. 1/2.
J1003 5" Long Play PVC 900ft. 10/- P. & P. 1/8.
J1004 5" Double Play Poly 1200ft. 15/- P. & P. 1/8.
J1005 5" Long Play PVC 1200ft. 12/6 P. & P. 1/8.
J1006 5" Double Play Poly 1800ft. 22/6 P. & P. 2/-.
J1007 7" Standard Play PVC 1200ft. 12/6 P. & P. 2/-.
J1008 7" Long Play PVC 1800ft. 17/6 P. & P. 2/-.
J1009 7" Double Play Poly 2400ft. 25/- P. & P. 2/-.
J1010 7" Triple Play Poly 3600ft. 50/- P. & P. 2/-.



NEW TRANSISTOR MODULES

E.1311. PHONO PRE-AMPLIFIER. Size 2 x 1 x 1 1/2in. Built-in R.I.A.A. characteristics enabling low output magnetic pick-up cartridges to be amplified up to 1 volt. Input 100Kohm. Gain 28dB. Max. output 3v. Max. input 50mV. Distortion 0.15% (at 1v level). Power supply 9-12v. 29/6. P. & P. 2/-.

E.1313. MICROPHONE PRE-AMPLIFIER. Enables a low output microphone to be used with an amplifier or radio. Input imp. 100Kohms. Gain 28dB. Max. output 3v. Max. input 50mV. Distortion 0.15% (at 1v level). Freq. response 10Hz-50KHz. Power supply 9-12v. 29/6. P. & P. 2/-.

E.1318. DUAL LAMP FLASHER. A switch module for electronically alternating two miniature bulbs, 6V, 100-200mA. Ideal for models, toy boats and planes, displays, warning and security devices, communication signals, etc. Flasher time 1 sec. Power supply 6v DC. Current 150mA. Lamp 6v 150mA. 25/- P. & P. 2/-.

E.1315. ELECTRONIC ORGAN TONE OSCILLATOR. Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz. Output 80mW. Current 15mA. 25/- P. & P. 2/-.

E.1314. POWER AMPLIFIER. When used in conjunction with E.1311, E.1312 and E.1313 units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input imp. 1,000 ohms. Gain 20dB. Output 300mW. Distortion 3% (at 300mW output level). Freq. res. 50Hz-10KHz. Power supply 9v. Current 20mA at no signal, 80mA at max. output. 29/6. P. & P. 2/-.


E.1317. MINIATURE MORSE TRANSMITTER. Will transmit to any adjacent AM Receiver, also makes a useful oscillator for trouble shooting. Audio tone 400c/s. Radio frequency range 400c/s to 30Mc/s. Power supply 9v DC. Current 35mA. 25/- P. & P. 2/-.

E.1312. TAPE PRE-AMPLIFIER. Incorporating N.A.R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input imp. 100Kohm. Gain 25dB. Max. output 2v. Max. input 50mV. Distortion 0.15% (at 1v level). Power supply 9-12 volts. 29/6. P. & P. 2/-.

E.1316. MORSE CODE OSCILLATOR. A transistorised Morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone freq. 400Hz. Power output 80mW. Power supply 3-9v. Current 45mA. 25/- P. & P. 2/-.

Visit our Brand New
Hi-Fi Demonstration Room,
Tape Bar, Scientific Show of
Microscopes, Binoculars,
Telescopes also Watches at
18 Tottenham Court Road

COMPACT 2-WAY INTERCOMS

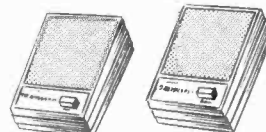


For table or wall mounting. Smart two tone grey cases size 3 1/2 x 1 1/2 in. Complete with lead, staples and 9v battery. 55/- P. & P. 3/6.

MOTOR BARGAINS




Ideal for model makers, record players, tape decks, etc.
6.3 D.C. Motor. 10,900 r.p.m. at 230 mA. 1 1/2in. x 1in. diameter. Shaft 1/16in. long x 3/64in. diameter. 9/6. P. & P. 2/8.

MAINS KEYNECTOR SAVES TIME—SAFELY!

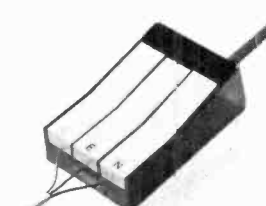


One mains "Keyconnector" instantly and safely connects electrical appliances to mains supply without the use of a plug. A number of appliances may be used simultaneously up to the full 13 amp rating of this device. A red light glows when "live". The "Keyconnector" is fused and has its own robust switch which is interlocked to prevent connections when "live". Invaluable to handymen, servicemen, demonstrators etc.

39/6 P. & P. 3/-.

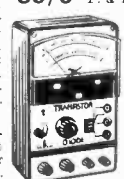

NEW TRANSISTOR CHECKER.
For measuring alpha, beta and Ico. factors of transistors also for checking germanium and silicon diodes. Internal 9v. battery. Wide reading scale. Moulded case size 7 x 4 1/2 x 3 1/2in. Ranges: Alpha 0.7-0.9967; Beta 0.300; Ico 0.50-5,000A. Diode test: forward and reverse internal resistance. Resistances: 200 ohm-1 megohm. Complete with connectors and instruction booklet. £7.19.8. P. & P. 3/6.

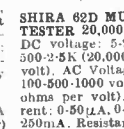

SHIRA 62D MULTI-TESTER. 20,000 o.p.v. DC voltage: 5-25-50-250-500-2.5K (20,000 ohms per volt). AC voltage: 10-50-100-500-1,000 volts (10,000 ohms per volt). DC Current: 0.50μA, 0.2-5mA, 0-250mA. Resistance: 0-6K, 0-6M (300 ohm and 30K at centre scale). Capacitance: 10pt. to .001 mfd., .001μf to 1μf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 1/2in. Complete with case 77/- P. & P. 3/6.



LIND-AIR OPTRONICS LTD

18, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

ALL
MAIL ORDERS
To Dept. PW769,
54a Tottenham
Court Road,
London, W1.

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.
—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Customers

Tel. 769-0199/1649

1A7	7/9	6BQ7A	7/-	6K7G	2/-	9BW6	7/-	20P5	20/-	80	7/8	DF96	7/8	ECF80	6/8	EM80	7/8	PC97	8/9	RG5/50080/-	UF89	7/8	
1D6	7/8	6BR7	17/-	6K7GT	4/8	10C1	12/6	25A6	5/9	85A2	7/3	DH77	4/9	ECF82	6/8	EM81	8/3	PC84	6/8	8130	40/-	UL41	12/-
1H5	7/-	6BR8	12/6	6K8M	11/8	10C2	12/6	25L6GT	7/-	100B2	11/6	DK32	7/9	ECH21	12/6	EM84	7/6	PC89	10/8	8P4	8/-	UL84	7/-
1LD5	6/-	6B87	25/-	6K8G	3/-	10F1	14/9	25Y5	6/-	150C4	9/8	DK91	6/-	ECB35	11/8	ESU15020/-		PC189	10/8	8F41	3/8	UM80	5/8
1N5GT	8/-	6BW6	14/8	6K8GT	7/-	10F3	18/-	25Z4	6/3	801	9/8	9K92	9/-	ECB42	11/-	EY51	7/6	PCF80	6/9	8P61	3/8	U06	21/-
1R5	6/-	6BW7	13/-	6K25	15/-	10F9	10/6	25Z5	8/-	807	9/-	DK96	9/9	ECH81	5/8	EY86	7/-	PCF82	6/8	8TV280/80		U07	21/-
184	5/8	6C4	5/-	6L1	12/-	10F18	8/-	25Z6	8/8	813USA		DL66	25/-	ECB83	3/8	EZ36	6/-	PCF84	8/-			U08	21/-
186	4/8	6C5G	5/-	6L6G	7/9	10L1	8/-	28D7	9/3	813	75/-	DL92	6/3	ECB86	9/-	EZ40	8/3	PCF86	9/-	8U25	19/8	U09	8/3
1T4	4/-	6C8	3/9	6L18	6/-	10LD11	10/6	30C1	6/9	813	75/-	DL93	4/-	ECL82	7/-	EZ41	9/8	PCF81	9/9	8U2150	12/8	U02	9/8
3A4	4/-	6C8G	6/-	6Q7G	8/8	10P13	13/8	30C15	15/-	866A	15/-	DL94	6/9	ECL83	10/3	EZ80	5/8	PCF82	9/9	T41	17/8	U04	8/8
3Q4	7/9	6CD6G	24/-	6Q7GT	8/8	11E3	70/-	30C17	16/-	964	5/3	DL95	7/9	ECL86	9/-	EZ81	5/8	PCF85	15/-	TDD4	8/8	U05	6/8
3Q5	7/-	6CH6	7/6	6SA7M	7/-	12AT6	4/9	30C18	15/-	1625	6/8	DL96	7/6	ECL800		GZ30	10/-	PCF86	13/8	U10	7/6	VMP4G	15/-
384	8/3	6CW4	12/-	68C7	7/-	12AT7	6/-	30F5	17/-	4022AR67/-		DM70	6/-			GZ32	10/-	PCF88	15/8	U14	7/8	VR4B	25/-
3V4	8/9	6D6	3/9	68G7	6/-	12AU6	5/9	30FL1	16/-	5763	12/-	DY86	6/-	EF9	20/-	GZ34	11/-	PCB2	7/9	U19	35/-	VR105/30	
5R4GY	10/8	6E5	7/8	68H7	3/3	12AU7	5/9	30FL12	19/-	7193	2/-	DY87	6/8	EF37A	7/-	K736	18/-	PCB3	10/3	U25	15/8		
5U4G	5/8	6F1	12/6	68J7	6/-	12AX7	5/3	30FL14	16/8	7475	14/-	B88CC	12/-	EF39	8/-	K761	17/8	PCB4	10/3	U36	16/8	VR150/30	
5V4GT	6/-	6F5G	8/-	68K7GT	4/9	12BA6	6/-	30L15	17/-	A61	9/8	EASO	3/8	EF41	10/-	K766	21/-	PCB5	9/3	U78	4/6		
5Y3GT	6/-	6F6G	5/-	68L7GT	4/9	12BE6	6/8	30L17	17/-	ATP4	2/3	EAB380	6/8	EF50	5/-	K781	35/-	PEN44	20/-	U191	13/9	VT25	15/-
5Z4G	7/-	6F8G	5/8	68N7GT	5/6	12C8GT	5/-	30P12	16/-	ATP5	12/-	EAF42	10/-	EF80	5/-	K781	(7C5)	PEN44	20/-	U251	16/3	VT31	80/-
6/30L2	15/-	6F11	6/8	68Q7	7/8	12E1	20/-	30P19	15/-	ATP7	8/8	EB41	10/-	EF86	7/-			PEN44	20/-	U301	12/6	VT31	80/-
6A7	15/-	6F13	6/8	6U4GT	12/-	12J5GT	2/8	30P11	18/-	AU2	80/-	EB91	3/-	EF86	6/8	K788	30/-	PEN45	7/-	U403	6/8	VT120	12/8
6A8G	12/6	6F14	12/6	6U5G	7/6	12J7GT	6/8	30P13	18/8	AU5	8/9	EB93	3/8	EF89	5/8	K7W61	8/8	PEN46	4/-	U404	7/8	VT308	35/-
6AC7	4/-	6P23	16/-	6V8M	12/-	12K7GT	7/-	30P14	15/-	AZ1	8/-	EB41	9/8	EF91	3/8	K7Z41	8/8	PL36	10/9	U801	23/8	WB1M	12/8
6AK5	5/-	6P24	14/-	6V6G	4/8	12K8GT	8/-	35A5	11/8	AZ31	10/-	EB93	3/8	EF92	2/8	M14	17/8	PL81	8/-	UAB380	6/8	XB1-5	5/-
6AL3	3/-	6P25	15/-	6V6GT	6/-	12K9GT	8/-	35L6	9/-	CB1.31	16/-	EBF90	7/8	EF98	15/-	ML6	7/8	PL82	8/8	UAF42	10/8	XB1-5	5/-
6AM5	4/8	6P28	14/-	6X4	4/8	12M4	8/-	35W4	4/8	CCB35	15/-	EBF83	9/-	EF183	6/8	MP4	10/-	PL83	7/8	UBC41	9/3	Y63	7/8
6AM6	3/6	6P28	14/-	6X5G	4/8	12M7	6/-	35Z3	10/-	CL33	20/-	EBF89	6/8	EF184	7/-	MP4	10/-	PL84	7/8	UBC41	9/3	Tabs	
6AQ5	6/3	6H6	3/-	6X5GT	6/-	12M7	3/-	35Z4GT	8/8	CY30	18/8	EBL1	14/-	EL32	3/8	MX40	12/8	PL500	14/8	UBF80	7/8	3EG1	65/-
6AS7G	16/-	6J5M	9/-	7B6	11/6	12M7	3/9	35Z5	8/-	CY31	8/8	EBL21	12/-	EL33	12/8	N78	19/-	PL4	14/-	UBF89	7/8	3FP7	28/-
6AT6	4/9	6J5G	4/-	7B7	7/8	12M7	4/9	37	6/8	DAC32	7/-	EBL31	27/8	EL34	10/8	N108	28/-	PY33	10/8	UCB84	8/8	5CP1	55/-
6AU6	6/-	6J5GT	5/8	7C5	15/-	12M7	5/-	42	6/-	DAF91	4/8	EC80	5/-	EL41	10/8	NGT1	3/8	PY81	5/8	UCB85	7/8	CV1526	40/-
6B4G	20/-	6J6	3/6	7C6	15/-	14H7	9/8	50B5	6/8	DAP96	7/8	EC81	6/-	EL42	10/8	NGT7	55/-	PZ2	5/3	UCB86	8/8	VCB37	35/-
6B8G	2/-	6J7M	8/8	7D5	8/-	19AQ5	5/-	50C5	6/3	DC90	10/8	EC82	5/3	EL44	9/8	OA2	6/-	PY83	7/8	UCB87	7/8	VCB37	35/-
6BA6	5/-	6J7G	8/-	7H7	6/8	20D1	10/-	50C6G31/-		DF33	8/-	EC83	6/3	EL49	6/3	OC3	5/-	PY80	6/8	UCB88	7/8	VCB37	35/-
6BE6	5/-	6J7GT	7/8	7R7	13/-	20F2	14/-	50L6GT	8/-	DF70	9/-	EC84	5/8	EL95	6/8	OC4	4/8	PY81	9/8	UCB89	7/8	VCB37	35/-
6BH6	9/-	6K6GT	7/-	787	45/-	20L1	20/-	75	9/8	DF91	4/-	EC85	5/-	EL96	6/8	OC4	4/8	PL8	11/8	UCB90	7/8	VCB37	35/-
6BJ6	9/-	6K7M	6/8	7Y4	8/8	20P4	20/-	78	5/-	DF92	3/8	EC88	7/8	EM34	21/-	PC88	11/8	R2	7/9	UFA1	10/8	VCB37	35/-

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Express postage 9d. per valve.
Ordinary postage 6d. per valve. C.W.O. No C.O.D.
Complete range of T.V. Tubes available from £4.5.0.
Manufacturers and Export Inquiries Welcome

**Special 24 Hour
Express Mail
Order Service**

DAF91, DF91, DK91, DL92 or DL94	19/-	plus postage
DAF96, DF96, DK96, DL96	27/8	plus postage
TRANSISTORS		
AC127 7/8	OC25 11/-	OC71 4/8
AF114 7/-	OC28 18/-	OC72 6/-
AF116 7/-	OC35 11/8	OC75 8/-
AF118 7/-	OC44 6/8	OC76 8/-
AF117 7/-	OC45 4/-	OC77 3/-
OC81 4/-	OC82 6/-	OC82D 6/-
OC81D 4/-	OC81D 4/-	OC83 6/-
OC170 7/-	OC82 6/-	OC200 7/8

SEND S.A.E. FOR LIST OF 2,000 TYPES

HOME RADIO (Components) LTD., Dept. PW, 234-240 London Road, Mitcham, Surrey, CR4 3HD Phone: 01-648 8422



HOME RADIO
HOME RADIO (COMPONENTS) LTD

**THE ELECTRONIC COMPONENTS CATALOGUE
THAT SETS THE STANDARD**

**Used and
acclaimed by:-**

**SCIENTISTS
ENGINEERS
TECHNICIANS
TEACHERS &
STUDENTS**

This edition of the Home Radio Catalogue is the result of eleven years of careful selecting, compiling and indexing. It is the most comprehensive we have ever produced—it has 330 pages, over 8,000 items and over 1,500 illustrations. With each catalogue we supply a 30-page Price Supplement, a Book Mark giving Electronic Abbreviations, an Order Form, and 6 Vouchers each worth 1/- when used as directed. All this for only 8/6 plus 3/6 post, packing and insurance. Send the coupon today, with your cheque or P.O. for 12/-.

Please write Name & Address in block capitals

NAME _____

ADDRESS _____

Home Radio (Components) Ltd., Dept PW, 234-240 London Road, Mitcham, Surrey, CR4 3HD

Of course no catalogue is ever really finalised. As soon as we have one edition off the press, our researchers get busy finding out what is the latest in the world of Radio and Electronics—ready for the next printing.

The price of 12/- applies only to catalogues purchased by customers residing in the U.K.

hard negative. Initially the capacitor will have a voltage at its terminals equal to the line voltage, V_{cc} , the collector end of C1 just before switching being $+V_{cc}$. Since the collector goes to near the ground potential and the voltage still remains across the capacitor, V_{B2} goes to $-V_{cc}$, or more exactly, $V_{CE2sat} - V_{cc}$. Thus if the line voltage was 5V, the capacitor has 5V across its terminals initially. Upon switching, V_{C1} drops to 0.1V and V_{B2} is taken to $-4.9V$.

Tr2 is driven into reverse bias and is thus cut hard off, ensuring that only I_{CBO2} flows through R4 and that V_{C2} is approximately at $+V_{cc}$. In normal operation C2 would not be charged, but at the initial cycle it may well be. If it is not fully charged, it now becomes so, charging from $V_{B1}=0.7V$ to $+V_{cc}$. Section (c) of Fig. 2.1b shows the collector of Tr2 at line potential and the positive-going voltage at Tr2 base is seen in section (d).

This latter waveform shows how the voltage at the negative side of C1 is changing. Directly after switching it is at $-V_{cc}$, but it then begins to discharge through the Tr2 base resistance, R3, in an effort to charge its negative end to $+V_{cc}$ through this resistor. The voltage thus reduces across the capacitor until, with the capacitor totally discharged, Tr2 base is taken to $+0.1V$. The capacitor now begins to charge in the opposite potential as the negative side of the capacitor aims for $+V_{cc}$. It is not allowed to charge to this potential, however, for when it reaches the V_{BE} of Tr2, Tr2 is switched on, and the emitter base holds the negative end of the capacitor from rising any further. By this time capacitor C2 will be fully charged at line potential.

Tr2 switches on, its collector dropping to V_{CE2sat} , as shown in Fig. 2.1b. Just as Tr1 caused Tr2 base to drive negative on switch-on, now Tr1 base is driven negative to $-V_{cc}$, and Tr1 is cut off. Now C2 begins to gradually discharge through R2, and C1 begins to charge through R1 since $V_{C1}=V_{cc}$.

It will be appreciated that due to the difference between magnitudes of base and collector currents, the base resistances are very much larger than the collector resistances. It is thus ensured that the time constant for the capacitors to charge through the collector loads is shorter than for the discharge through the base resistances, and thus it is certain that upon switching, the new timing capacitor to come into action will start fully charged. This action is repeated and regenerative switching continues as long as the supply is connected.

Examining the waveforms more closely, at first glance their shapes might seem a little unusual, but when considering the full cycle in detail the shapes are explained. Considering the base waveforms, they are seen to cut off sharply when reverse bias is applied, as might be expected. We then see a normal capacitor discharge into the positive region, followed by the rather unusual "pip". At this point the capacitor is aiming to charge to the line potential through the base resistor, and as the emitter-base diode comes into conduction there is for a short period an interaction as the base current settles down to a steady state value, whilst the voltage at the base attempts to increase above V_{BE} . The emitter-base is finally in full conduction and holds constant at 0.7V.

Considering the collector waveforms, a fast falling edge is observed. When a transistor goes into the ON state it is switched on sharply and wastes little time in dropping to V_{CEsat} . When the transistor switches off however, the situation is a little different. The capacitor attached to the collector is charged a little in the opposite polarity, and it now has to recharge in its normal polarity through the collector resistance. With a small

voltage across the terminals in the reverse polarity, it tends to pull down on the collector as it tries to rise to line potential, and hence we see the slow rising edge of the basic multivibrator.

The switching periods of the multivibrator may be determined as follows. Taking the situation where Tr2 has just switched on, and Tr1 base has just been driven to $-V_{cc}$, the base end of C2 begins to charge to an aiming potential of $+V_{cc}$, i.e. an effective $2.V_{cc}$ volts. It does not reach this potential since when it reaches an effective V_{cc} volts (i.e., really approximate potential of the earth line), switching occurs.

The basic expression for the instantaneous voltage of a capacitor C, charging through a resistor R, to a potential V, is given by:

$$\text{instantaneous voltage, } v = (V/R) e^{-t/CR}$$

Applying this to the case in question,

$$V_{B1} = 2.V_{cc} (1 - e^{-t_1/R_2.C_2}) - V_{cc}$$

This simplifies to

$$V_{B1} = 2.V_{cc} - 2.V_{cc}.e^{-t_1/R_2.C_2} - V_{cc} \\ = V_{cc} (1 - 2.e^{-t_1/R_2.C_2})$$

To simplify the expression, assume the emitter-base voltage is negligible, i.e. assume $V_{B1}=0$.

Then,

$$0 = V_{cc} (1 - 2.e^{-t_1/R_2.C_2})$$

Therefore,

$$1 - 2.e^{-t_1/R_2.C_2} = 0 \text{ since } V_{cc} \text{ is not zero.}$$

Simplifying,

$$2.e^{-t_1/R_2.C_2} = 1$$

Taking logarithms to base e,

$$\log_e 2 + (-t_1/R_2.C_2) \log_e e = \log_e 1$$

Therefore,

$$\log_e 2 - t_1/R_2.C_2 = 0$$

Rearranging,

$$t_1/R_2.C_2 = \log_e 2$$

Therefore,

$$t_1 = \log_e 2.R_2.C_2 = 0.693.R_2.C_2$$

This thus explains the approximation frequently used for such circuits of $t=0.7C.R$.

If the capacitors and base resistors are identical, and with the usual circuit only the capacitors might differ, the ON and OFF states for both transistors will be equal. If one capacitor is larger than another, it will take longer to discharge, and will hold the transistor in the OFF state for a longer period of time. Unequal quasi-stable states will result, and one collector will provide short positive-going pulses, the other collector long positive-going pulses. Output may be taken from either collector, most simply by capacitive coupling. It is possible to d.c. couple, however, if this is desired.

The frequency is given approximately by:

$$f = \frac{1}{t_1 + t_2}$$

In these articles n-p-n transistors will be dealt with for consistency, and since they are the more common types with modern silicon planar transistors. A p-n-p version of any of the n-p-n circuits would simply have a reversed rail polarity, and reversed capacitor and diode polarities.

Figure 2.2 has been included to illustrate this point, being the p-n-p version of Fig. 2.1a.

To now consider the practicalities of calculating component values, some very simple mathematics show the requirements.

Assuming $V_{CEsat} \approx V_{EB} \approx 0$

Then, where R_B is the base bias resistor and R_C the collector load,

$$R_B \approx \frac{V_{cc}}{I_B} \text{ and similarly, } R_C \approx \frac{V_{cc}}{I_C}$$

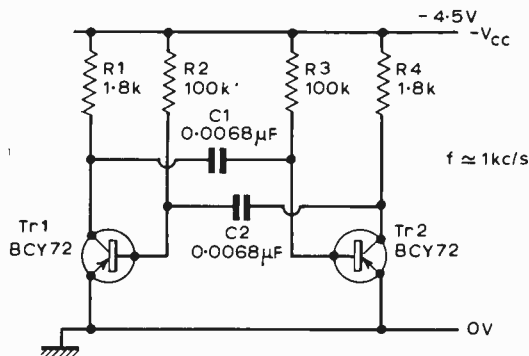


Fig. 2.2: A p-n-p multivibrator of similar design to Fig. 2.1(a).

Now, $I_C \approx h_{FE} \cdot I_B$. Therefore,

$$\frac{V_{CC}}{R_C} \approx h_{FE} \cdot \frac{V_{CC}}{R_B}$$

Simplifying,

$$\frac{1}{R_C} \approx \frac{h_{FE}}{R_B}$$

Therefore,

$$R_B = h_{FE} \cdot R_C$$

i.e., the base resistance will be approximately larger than the collector load by the factor of the d.c. gain for saturation switching. Thus if the required collector current is 1mA into a collector load of 4.7kΩ, the base resistance should be 4.7kΩ × h_{FE} . For a high gain silicon transistor h_{FE} might be 200, giving a base resistance of 940kΩ, say 820kΩ as the nearest lower preferred value. We see that V_{CC} is set at $I_C \cdot R_C = 4.7V$, and have only to substitute R_B into the 0.7CR formula to design for a particular frequency.

Out of interest, and to conclude the mathematics, let us calculate the minimum value of h_{FE} for reasonable operation. To simplify the maths, let us select a suitable voltage for V_C to reach. If we allow V_C to reach 0.99 V_{CC} we are assured of the collector voltage making its full excursion.

We may express the requirement in terms of an unknown, X for the moment.

Let $t_1 = 0.7 \cdot C_2 \cdot R_2$ be greater than $x \cdot C_1 \cdot R_1$

and thus $(1 - e^{-x}) = 0.99$

Therefore, $e^{-x} = 0.01$.

Thus, $x = 4.6$.

Now if $C_1 = C_2$

$$0.7 \cdot R_2 (\text{min}) = 4.6 \cdot R_1$$

Therefore,

$$R_2 \text{min} = 6.6 \cdot R_1$$

Or in more general terms,

$$R_B = 6.6 \cdot R_C$$

Therefore,

$$h_{FE \text{min}} = 6.6$$

With the gains of modern silicon transistors it is seen that we should do far better than $V_C = 0.99V_{CC}$. Higher gain, that is, of the order of one or two hundred, allows smaller capacitors to be used and consequent saving in space, and possibly cost.

It was stated at the beginning of this article that transistors in multivibrator circuits are sometimes seen in circuits where the maximum ratings are exceeded. The rating referred to is the maximum emitter-base reverse bias. With typical silicon transistors, this is usually of the order of 5V. A 5V line will thus take the transistors to this limit when the capacitor takes the base to 5V below the earth rail. It is not always appreciated that this is in fact what happens, and if the supply voltage for the multivibrator exceeds the maximum reverse bias of the emitter-base junctions of the transistors, special pre-

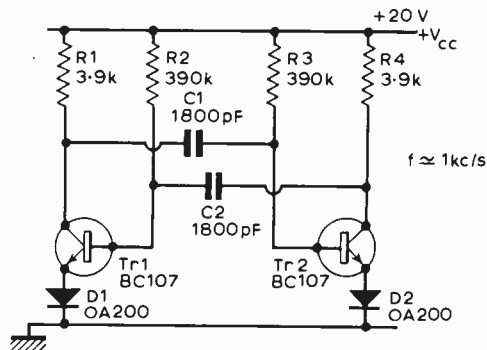


Fig. 2.3: Emitter diodes protect the transistors against excess reverse emitter-base voltage.

cautions should be taken in a correctly designed circuit.

Figure 2.3 shows one method of overcoming this problem. Here diodes have been placed in the emitter lines of the two transistors, and if the bases of the transistors are now taken more negative than the maximum rating for the transistor's reverse V_{EB} , even a modest diode will not break down at normal line voltages, and the reverse-biased diode will protect the transistor.

Speeding-up the Rising Edge

For some applications it may be desirable to improve the rather slow rising edge which is a characteristic of the basic multivibrator. This may be achieved by the addition of two further resistors, and two diodes, as shown in Fig. 2.4. Operation of the multivibrator is now as follows.

Assuming Tr1 is initially on, and Tr2 cut off, C1 is discharging from $-V_{CC}$ at the base of Tr2, and C2 is now charging chiefly through R5. With $V_{C2} = V_{CC}$, diode D2 is reverse biased as far as the charging capacitor is concerned, and it charges through the resistor indicated. C2 will be fully charged by the time that the potential at Tr2 base rises to +0.7V. When Tr2 switches on its collector goes negative, taking with it Tr1 base. Tr1 collector now suddenly rises toward the + V_{CC} rail, and it is here that the capacitor C1 would normally exert its influence in slowing down the collector's rise towards the rail.

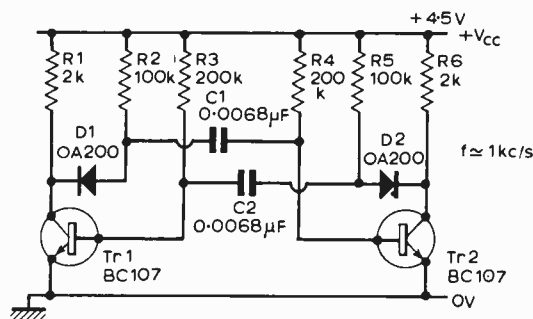


Fig. 2.4: A low voltage multivibrator with fast switching times

Initially, with about 0.7V reverse bias on it, the anode of D1 is at about earth potential, and when Tr1 cuts-off and the collector rises, the diode is cut off into reverse bias. This acts as a gate, a block between C1 and Tr1 collector, and the collector is free to rise sharply up to the positive rail. Capacitor C1 may now recharge in normal polarity through resistor R2.

It should now be possible to obtain fast rise and fall times from either collector, provided that the value of R2 is suitably chosen. When a transistor is in saturation,

the diode connected to its collector will be forward biased and conducting, and if the diode coupled resistor is small, it will shunt the true collector load resistance, and may cause the transistor to come out of saturation. It was pointed out before that since the collector load is usually much smaller than base bias resistors, this ensured that the capacitors could recharge fully before switching took place due to the discharging capacitor. It is therefore necessary to make the diode coupled resistor significantly smaller than the base bias resistor.

For normal silicon transistors, a useful rule of thumb is to make the diode coupled resistor about one-half the value of base bias resistor. It will be seen that for a transistor with a gain of say 100, with a $1\text{k}\Omega$ collector load, and a $100\text{k}\Omega$ base resistance, this would give a diode coupled resistance value of about $50\text{k}\Omega$. Such a value will not appreciably shunt $1\text{k}\Omega$, and will provide a much shorter time constant for the charging capacitor than it will see on discharge.

Low gain transistors should be avoided in this type of circuit. Rise and fall times of the order of 100ns are possible to achieve with this type of circuitry and high frequency transistors. For high speed operation, the diodes should also be fast types.

The method of placing emitter diodes in circuit to protect transistors against excessive reverse V_{BE} 's may not be desirable in certain circumstances. One disadvantage of this is that when the transistor is driven into saturation, its collector voltage will be $V_{CE\text{sat}} + V_F$ where V_F is the forward voltage of the diode, which will be of the same order as a V_{BE} . With silicon components, the collector voltage in saturation might therefore be slightly larger than 0.8V . A voltage dropping right to the earth rail (effectively) might be desired, and if so, a diode cannot be placed in the emitter.

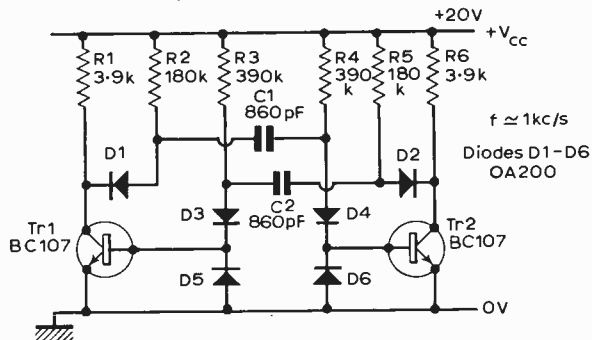


Fig. 2.5: A high voltage multivibrator with fast attack and decay.

A method of protecting the emitter-base for higher line voltages without using emitter diodes is shown in Fig. 2.5. If we assume Tr1 has just switched on, the negative-going collector will have just taken the anode of D4 negative to $-V_{CC}$. Diode D1 comes into conduction when Tr1 drives into saturation, so the potential at the anode of D1 will be $V_{CE\text{sat}} + V_F$. Now with the anode of D4 taken below the earth rail, it is reversed biased, cutting off the base current supply to Tr2, and hence cutting off Tr2. The base of Tr2 cannot be taken more negative than the forward voltage of diode D6 since this comes into forward conduction when V_{B2} is taken down to approximately -0.7V .

If we consider D4 short-circuited for the moment, Tr2 emitter-base would still be protected, and would still cut off, but the restraining voltage of the diode D6 would prevent the capacitor from going as far negative as it wishes to, and reflects back to the collector of Tr1.

With D4 in circuit, since reverse-voltages may be anything under the break down, the capacitor is free to go to full $-V_{CC}$.

As in normal operation, C1 will rise towards the positive rail through R4 eventually, Tr2 will come back into conduction, at a slightly later point, when D4 anode voltage is $V_F + V_{EB}$, and regenerative switching takes place.

Without diodes D3 and D4 the circuit will operate in that it will oscillate, but, another point to bear in mind, apart from the resulting degraded waveform, is that diodes D5 and D6 will then present a low impedance discharge path, and the frequency of operation will also be affected.

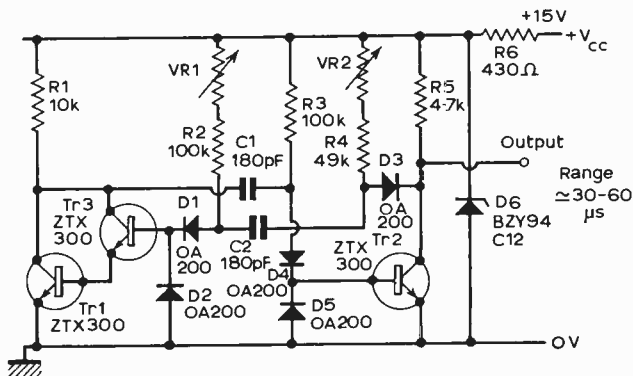


Fig. 2.6: Basic form of a variable pulse generator.

Figure 2.6 shows the basic form a pulse generator might take, the heart of which is a high speed multivibrator. Since an output will only be required from one side, it is not necessary to achieve a fast rising edge at the collector side which will not be used. A diode coupled resistor is thus only used on the output side, D3. Now in a pulse generator, we shall wish to vary the repetition rate and pulse length, and have a constant amplitude output with good fast edges. For low repetition rates, excessively large capacitors might be required, leading to stability problems. In the figure, the left-hand components will determine the repetition rate, whilst the transistor Tr2 will determine pulse length with its associated components.

A Darlington Pair, Tr1 and Tr3 give the repetition rate transistors a high gain, which enables us to use very high resistances in the base bias, and consequently reduced capacitance values to still obtain a long repetition rate. VR1 in series with a fixed resistor to ensure that the base bias resistance can never be zero, enables the repetition rate to be adjusted over a given range, related to C2, and Tr2 similarly allows an adjustment of pulse length. For a wide range instrument since the resistance range is limited for reasonable bias conditions and assurance of transistor saturation, capacitors C1 and C2 will simply be selected capacitors in switched ranges, the variable resistors allowing variation between the limits set by these ranges.

In this circuit, a zener diode D4 sets a fixed and stable V_{CC} and hence pulse height, and Tr2 should drive into saturation for a stable bottom level of the pulse. Diode protection has been afforded to allow a large voltage output in a similar manner to that described in Fig. 2.5.

There is thus more to the simple multivibrator than might at first be thought. A single article on it alone proves this point.

In next month's article, the family of monostable circuits will be discussed.

integrated circuit audio signal injector

This pocket signal injector takes full advantage of the size and cheapness of the more available I.C.s and will provide an excellent introduction for the beginner to these new components.



S. ELLIOTT

MOST cigar tube type a.f. signal injectors tend to be rather large and cumbersome to use and a small but reliable injector was needed. The outside diameter should not exceed $\frac{3}{8}$ in. for easy handling, for over this size it cannot be held like a pen, which is the natural way to hold the instrument. Four inches (excluding the probe) is about the maximum length, but if it were light in weight a much longer casing could be used; the length of the probe is up to the user. The injector described here falls well within these limits, with an outside diameter of $\frac{3}{8}$ in. and an overall length (excluding probe) of only 3 in.

It was decided to use an integrated circuit to save space and the one chosen was the Fairchild μ L914, a digital I.C. which is readily available. This I.C. contains ten components six of which are used in the injector. There are five discrete components. It is not recommended that beginners and those that have no previous experience of semiconductors build this project as it requires that some of the soldering takes place almost

on the component bodies themselves and prolonged heating could ruin them.

The circuit

The circuit of the injector shown in Fig. 1 is a straightforward multivibrator (astable) with no frills. Suppose Tr1 is off and Tr4 is on; therefore as the collector of Tr4 is more or less at earth C1 charges through Tr4 and R1. This causes the base of Tr1 to become more positive and so it begins to conduct. A regenerative action occurs and Tr1 switches on quickly. The negative-going pulse at Tr1 collector is transferred via C2 to Tr4 base and causes it to turn off, which in turn sends a positive-going pulse via C1 to Tr1 base which makes Tr1 conduct even more. Now Tr4 is off and Tr1 is on. C2 charges through R2 and Tr1, and so the cycle repeats.

The output is taken from Tr4 collector via C3 to the injector probe.

The period of oscillation is determined by:

$T = 0.69 (R1, C1 + R2, C2)$
but $R1 = R2 = R$
and $C1 = C2 = C$
where T is the time constant.
 $\therefore T = 1.38RC$

$$f = \frac{1}{T}$$

$$f = \frac{1}{1.38RC}$$

In this particular case:

$$f = \frac{1}{1.38 \times 10^4 \times 10^{-7}}$$

$$= \frac{10^3}{1.38}$$

$$= 725 \text{ c/s.}$$

This is slightly modified by transistor impedances in the final circuit.

Construction

To start, leads 1 and 5 are cut off as near to the I.C. as possible, lead 4 is cut off about $\frac{1}{8}$ in. from the I.C. and a lead soldered on, this is the negative supply to the oscillator. Next R2 is connected up by positioning it inside the lead configuration, the lower end being taken

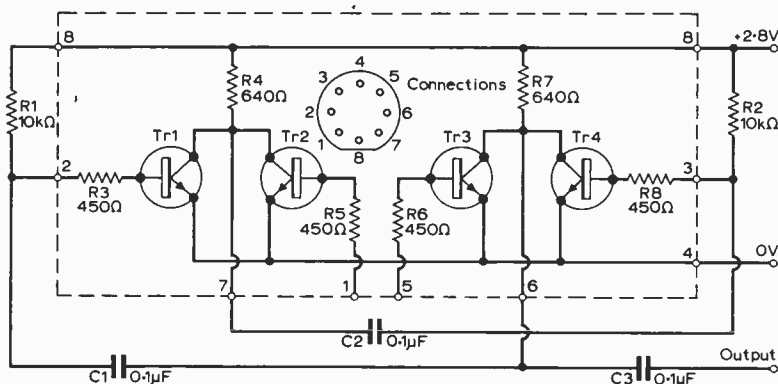


Fig. 1: The circuit of the I.C. audio signal injector.

★ components list

R1 and R2 10kΩ, 0.1 watt subminiature type.
C1, C2 and C3 0.1μF 3V subminiature type.
Integrated circuit: Fairchild μ L914 (Henry's Radio).
Miniature press button switch (G. W. Smith).
2in. $\times$ $\frac{1}{2}$ in. diameter copper tube. Coax plug.
Crocodile clip. Araldite. Batteries: two RM675H (Ever Ready).

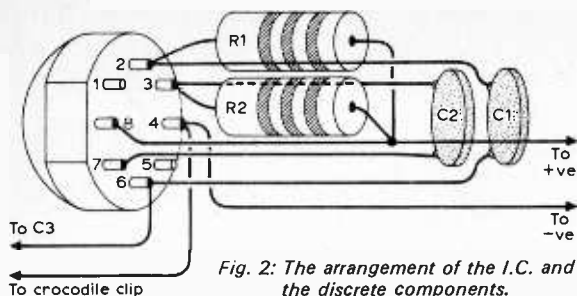


Fig. 2: The arrangement of the I.C. and the discrete components.

to lead 3 and the upper to lead 8, the positive supply line. R1 is positioned beside this, the top of it connected to the top of R2 and the bottom to lead 2. Lead 8 is cut off above the join of R1 and R2 and is soldered to a length of wire, this is the positive supply line. The two capacitors C1 and C2 are miniature disc ceramic types and are roughly the same diameter as the I.C. They are positioned above R1 and R2 and directly over the I.C. The leads are bent and soldered as in Fig. 2. A lead is soldered to lead 6, this will eventually go to C3 and the output probe.

Testing

The oscillator should be checked at this stage to see if it is functioning correctly. The two power leads are

This piece of the plug has striations down its side. A plug should be chosen that has not got these striations down its whole length; if the unstriated part is filed down it should be a tight fit into the end of the copper tube. It may be found that the end of the tube has to be expanded by pushing a pair of long nosed pliers down it and twisting them round so forcing the sides of the tube outwards slightly.

The probe end of the injector is formed by the other pieces of the coax plug. The pin is removed from the nylon insulator by heating with a soldering iron and withdrawing it when the nylon is just melting around the pin. The shoulder is then cut off the nylon with a razor blade so that it will go right to the end of the remaining part of the plug as shown in Fig. 3. This remaining part of the plug is then cut in half just below where the threads finish. This should now fit into the end of the copper tube loosely.

The probe is then heated and fitted into the nylon so that it barely comes out the other side. C3 is then soldered to this end. The nylon is glued with Araldite or a similar resin glue to the piece of coax plug. The hollow in which C3 is fitted is completely filled with Araldite, care being taken that the leads do not touch the case. A piece of wire is soldered to the other side of C3 and the whole assembly is glued to the copper tube. It will probably be found that the assembly will have to be clamped in place while the glue is setting so that it is

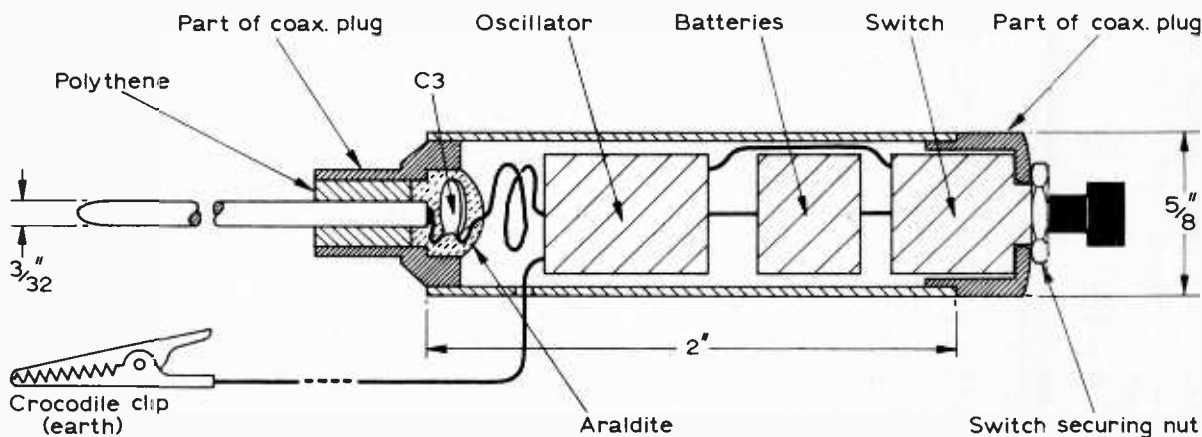


Fig. 3: The assembly of the completed signal injector.

connected to a 3V battery or the two mercury cells that will be used in the final injector. The output is taken via a 0.1μF capacitor to an amplifier and loudspeaker; upon connecting the battery a note should be heard. If it is not, disconnect immediately and check the wiring against the circuit diagram. If all is well the whole circuit is wrapped in p.v.c. tape to insulate it from the case, care being taken that none of the leads are likely to come into contact with each other. Now the next stage of construction, the case, can be started.

The case

The main body of the case is a piece of half-inch inside diameter copper tubing (the type used in small bore central heating). A piece is cut 2in. long and its ends are filed smooth. A coax plug is used for the ends. The end through which the cable should go is of sufficient size to incorporate a push-button switch sold by G. W. Smith Ltd., at 1s. 6d.

The switch is put into place and the nut tightened up.

not glued in at an angle to the copper tube. A hole is drilled in the copper tube near the prod end for the earth wire (—ve). This wire is soldered to pin 4 of the I.C.

The mercury batteries are soldered together—care being taken so that they are not overheated. It doesn't matter whether the positive or negative lead is switched; in the prototype the negative was switched. One side of the switch goes to pin 4 of the I.C. and the other is more or less soldered directly to the negative button of the battery. The other side of the battery is taken to pin 8 of the I.C. The batteries are wrapped in p.v.c. tape and the whole electronics assembly is slid into the tube. The injector is now ready for use.

The output waveform is not good enough for measurements and assessing the frequency response of an amplifier but it provides a portable audio source that can be used in many ways for tracing circuit faults. In conjunction with an audio amplifier it could be used as morse oscillator but in this case it need not be built into such a small housing.

AERIALS

A. J. WHITTAKER

PART 4—TRANSMISSION LINES

THE fourth part of this series on aerials will primarily concern transmission lines, or feeders, but to introduce the subject we will describe an amateur bands transmitting aerial which uses transmission lines in rather a special way to enable it to function over a wide band of frequencies. The aerial is the G5RV dipole, 102ft. long, designed to cover the 1·8, 3·5, 7, 14, 21 and 28MHz amateur bands.

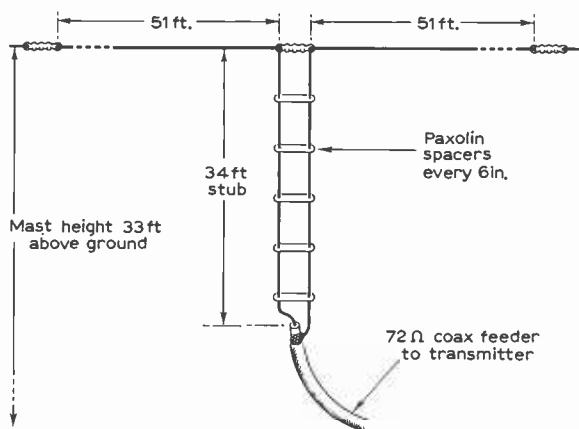


Fig. 4.1: The G5RV multiband dipole aerial.

The aerial is shown in Fig. 4.1. It is made from two lengths of covered wire, each 51ft. long, and coupled in the centre by a suitable strong insulator. From this centre point is taken a 34ft. open wire feeder, which acts as a matching stub, and to this is connected any convenient length of 75Ω coaxial cable. The whole aerial should be suspended above ground $\frac{1}{2}\lambda$ at 14MHz, i.e., 33ft., which will ensure a good match to the 75Ω feeder. On 1·8MHz, the two feeder wires at the transmitter end should be joined and fed via a series tuned coupling network. On 3·5MHz, the electrical centre of the aerial appears to be some 15ft. down the feeder, meaning that 30ft. of the aerial are folded into the open wire line. At 7MHz, the aerial is two half-waves in phase, also with a section "folded" in the line in the centre. On 14MHz, the aerial is three half-wavelengths long, and the stub acts simply as a 1 : 1 transformer. On 21MHz, it is a slightly lengthened two-wavelength aerial, and on 28MHz, it consists of two $1\frac{1}{2}\lambda$ aerials fed in phase.

The important part of this aerial which enables it to function over such a wide frequency range is the matching stub. The theory behind this stub comes under the general category of transmission lines, which is a very complicated and lengthy subject to explain. In the rest of this article, however, we will attempt to provide a simple explanation of the fundamentals, and if you find

that after reading it you are sufficiently interested in studying the subject, some suitable references will be provided for further reading.

Transmission Lines

Generally speaking, there are two types of aerial feeder: (i) the parallel or open wire feeder, and (ii) the concentric feeder, i.e., coaxial cable.

Dealing with (i) first, this consists of two wires running parallel and supported at least 6ft. above the ground. Spacers are provided at regular intervals to support and keep the wires an equal distance apart. Twin feeders are essentially balanced devices and are suitable only for feeding balanced aerial systems such as dipoles or an array of dipoles.

At any point along the twin-wire feeders the currents in the two wires are equal in magnitude and opposite in sign, so as the wires are close together the possible radiation is cancelled. The characteristic impedance for a twin wire feeder is given by

$$276 \log \frac{2D}{d}$$

where D is the distance from the centre to centre of feeder wires and d is the diameter of the feed wires (Fig. 4.2a). This formula gives a typical impedance of between 400 and 800Ω.



Fig. 4.2: Conductor identification for open wire and coaxial feeders.

Concentric feeder has one conductor completely enclosed by the other, as in the construction of coaxial cable. The characteristic impedance for a concentric feeder is given by

$$138 \log \frac{b}{a}$$

where a is the diameter of the inner conductor and b is the inside diameter of the outer conductor or screen. Fig. 4.2b. The usual characteristic impedance for this type of feeder is 75Ω, although 50Ω is quite common for transmitters. Losses are higher than with twin-wire feeder, for a low loss coaxial cable described as having an impedance of 75Ω and a shunt capacitance of 18pF per foot, exhibits losses of 0·68dB at 10MHz and 2·7dB at 200MHz.

Transmission line theory

A transmission line made up of two parallel wires has distributed inductance (L) and capacitance (C) per unit length. Fig. 4.3.

If the end of the line is short-circuited, standing waves are set up along the wires, i.e., the current waves which

have travelled along in one direction will return along the other wire and produce a standing wave pattern on the feeder. Fig. 4.4.

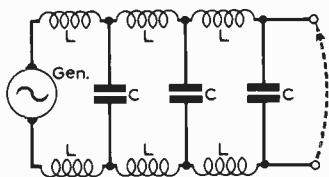


Fig. 4.3: The equivalent circuit of a transmission line without resistive loss.

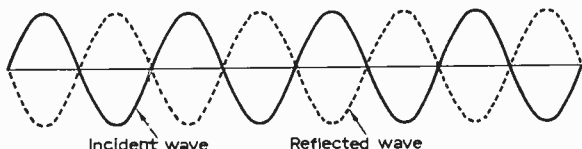


Fig. 4.4: How standing waves are represented. In this case 100% reflection occurs.

In this condition the receiving end becomes a point of low impedance (volts low, current high). Similar conditions occur if the receiving end is open-circuited. In either case the relative impedance will vary along the wires with the distance from the generator or source. If no energy is reflected no standing waves will be present on the feeder wires and these will only carry travelling waves and behave as if the lines were of infinite length. It can be shown that such a line possessing distributed inductance (L) and capacitance (C) has the property of a resistance given by

$$R = \sqrt{L/C} \text{ called characteristic impedance.}$$

If a resistance of this value be fixed across the ends of a feeder it will behave as if it were infinitely long and waves will travel along it without reflection (i.e. travelling waves). The only losses are due to the high frequency resistance of the wires which is higher than the ohmic resistance due to the phenomenon of skin effect. (i.e. h.f. currents induce a voltage into the current carrying conductors in opposite direction to the currents producing them, so forcing the initial currents to travel along the surface, or skin, and so effectively increasing the resistance.)

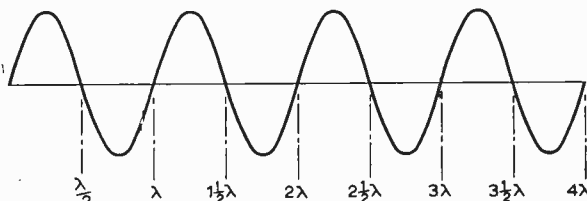


Fig. 4.5: The theoretical appearance of waves travelling along a feeder (Fig. 4.3).

Figure 4.5 is a sketch of travelling waves along a feeder, where each successive $\frac{1}{2}\lambda$ may be considered as a tuned circuit (series or acceptor circuit). The peak value of the current is given by,

$$I = \frac{V}{\omega L} \quad (\omega = 2\pi \times \text{Frequency})$$

As the circuit is tuned

$$\omega = \frac{I}{\sqrt{L/C}}$$

By substitution

$$I = V \sqrt{\frac{L}{C}}$$

As the wave travels along the feeder towards the receiving end it will carry its stored energy with it. If the receiving end is terminated with an impedance Z_r the peak value of current flowing through it will be

$$I = \frac{V}{Z_r}$$

and if there is no reflection

$$I = \frac{V}{Z_r} = V \sqrt{\frac{L}{C}}$$

That is $Z_r = \sqrt{L/C}$

The $\frac{1}{4}$ Wave Matching Line

If a transmission line is $\frac{1}{4}\lambda$ the impedance at each end will be the same: $Z_s = Z_r$ (1)

It therefore follows that the $\frac{1}{4}\lambda$ line behaves as a 1/1 transformer. The ratio of the impedances at each end depends upon $\sqrt{L/C}$ and from transmission line theory we have $Z_s Z_r = Z_0^2$ (2).

This relationship is true when there is no reflection and $Z_s = Z_r = Z_0 = \sqrt{L/C}$. Equation 2 means that a $\frac{1}{4}\lambda$ line acts like a step up or down transformer, and this led to the $\frac{1}{4}\lambda$ matching line. For example, if a 600 ohm line is to be matched to an 80 ohm dipole the matching line would have a characteristic impedance of $\sqrt{600 \times 80} = 220$ ohms approx.

The process of matching consists of adjustment of the $\frac{1}{4}\lambda$ matching line spacing " Z_0 " until no reflection occurs in the transmission lines. A $\frac{1}{4}\lambda$ matching line is also known as a "Q" bar (Fig. 4.6).

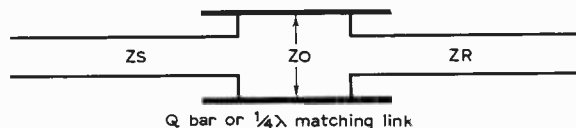


Fig. 4.6: An impedance matching device known as a Q-bar.

The Balun Transformer

The name balun is derived from BALanced to UNbalanced and this device is used when an aerial requires a balanced feed with respect to ground. The balun converts the unbalanced co-ax feeder to the balanced output required by the aerial system, an example being matching an unbalanced feeder to a dipole.

Figure 4.7 below is a sketch of $\frac{1}{4}\lambda$ OPEN Balun or "Pawsey Stub".

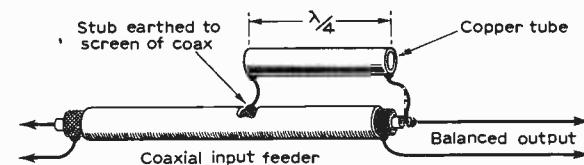


Fig. 4.7: An open Balun made from coaxial cable.

Point A presents a high impedance preventing the wave from travelling over the surface and spilling over the end and tending to travel back along the braiding of the co-ax. If this occurs the re-radiated wave on the surface

of the braiding modifies the aerial polar diagram and the outer surface of the feeder is found to have a r.f. voltage on it. This may be detected by placing your hand around the co-ax. If r.f. is present it will affect a received signal.

A Balun may be made using a $\lambda/4$ piece of coaxial cable and connected as above.

To complete these notes on feeders a word or two about audio-frequency lines would not be out of place. Here then are a few empirical rules.

Short high impedance A.F. lines

Main factors affecting short line (about 100ft. long) working are,

- 1 Series inductance;
- 2 Series resistance;
- 3 Shunt capacitance.

Series inductance offers a variable impedance to the line current which varies with frequency. Typical values for series $L=20\mu\text{H}$ per 100ft.

Series resistance provides a uniform resistance at all frequencies, typical values for single and double core cables ranging from 1 ohm to 1.5 ohms per 100ft.

Shunt capacitance provides a by-pass to the line current which varies inversely with frequency (i.e., falls in value with increasing frequency). Typical values for single core cable are 6,000 pF and for double core cable 4,000 pF per 100ft. The maximum effect of these impedances will depend on the relative value of the generator and load impedances. The series R and L will have little effect if the generator or load impedances

are high in comparison (i.e. so that the line current will be low). In general, the generator or load impedances should be at least twice the value of the impedance of L and R at the highest frequency it is desired to transmit down the lines.

Shunt capacitance—here the impedances offered by the generator or load should be less than half the impedance offered by the shunt capacity at the highest frequency it is desired to transmit down the line. Typical examples of shunt capacities are, 26k Ω at 8kHz for 30ft, $\frac{1}{4}$ mile, shunt capacitance 500 Ω at 8kHz.

References:

- 1 *Short Wave Radio Communication* (Ladner & Stoner).
- 2 *Admiralty Handbook Wireless Telegraphy*.
- 3 *Amateur Radio Handbook*.

TO BE CONTINUED

CQ! CQ! CQ! CQ! CQ! CQ!

ISSUES FOR DISPOSAL

... all the issues of *Practical Electronics* from the No. 1 issue. What offers?—E. Salter, c/o *Practical Wireless* Editorial.

... many issues of *Practical Wireless*, *Practical Television*, *Practical Electronics*, *Radio Constructor*, *RSGB Bulletins* etc. All at cover price. Send s.a.e. for details.—R. Collins, 39 Cadogan Gardens, South Woodford, E.18.


... August 1966, October 1966 and June 1966 issues of *Practical Wireless*. Will swap for any interesting electronic bits and pieces.—L. Cook, 7 Plum Tree Close, Eccleston Park, Prescott, Lancashire, L35 7JT.

... exchange about 50 or more issues of P.W. (with blueprints) from 1962 to date, for the *Sintech Elementary Radio Book*.—P. P. Skivington, 16 Bowood Road, Enfield, Middlesex.

NEXT MONTH IN

THE TRANSET

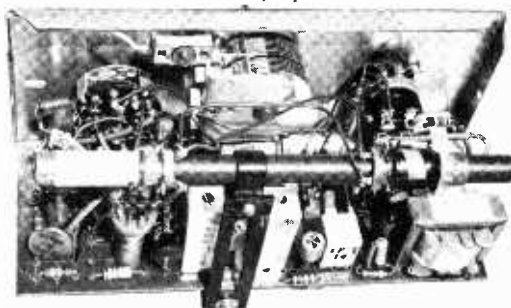Assembly details of a seven transistor, three wave-band portable receiver. It includes, in addition to long and medium wavebands, coverage of the 21–50 metre short waveband. Easy to follow constructional details make this an ideal project for the enthusiast.




The August issue also contains details of an inexpensive miniature pocket organ (costs less than 20/- to build), a further constructional project in the popular "Take 20" series by Julian Anderson.

PRACTICAL WIRELESS

VERSATILE INTERCOM SYSTEM

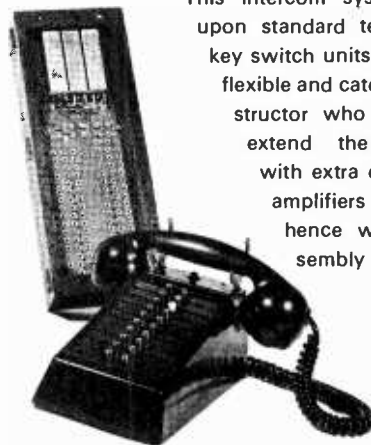This intercom system is based upon standard telephones and key switch units. The design is flexible and caters for the constructor who may wish to extend the arrangement with extra extensions. No amplifiers are required, hence wiring and assembly are simplified.



Do not miss your copy of the August issue of *Practical Wireless*—on sale 4th July price 3/-

DIRECTIONAL MICROPHONE

C.R. BRADLEY

THE directional microphone to be described was built for outdoor tape recording in connection with amateur movie sound-tracks. It effectively reduced offstage noises e.g. wind noise, traffic roar, camera sounds.

A directional microphone has many other applications. Public address systems can be operated at higher levels before feedback howl is produced. The acoustic characteristics of a "noisy" (reflective walled) room, such as a tiled bathroom, can be reduced or exaggerated for recording purposes. If the microphone is pointed at a speaker in such a room his voice will sound "flat" and echoless. If the microphone is directed away from the speaker it will pick-up his voice by reflection from the walls, giving the voice an echo-chamber effect. Another advantage of a directional microphone is that distant sound sources which cannot be approached easily (birds, animal, trains, aeroplanes) can be recorded with less background noise.

The heart of the microphone is a magnetic microphone cartridge. This is mounted at one end of a cylindrical case made of plaster of Paris. The heavy case shields the cartridge from sound sources behind and to the side. Ordinary carpet felt is used to deaden reflections inside the case (Fig. 2a). The cartridge "sees" only a small angle of the outside world and the microphone is sensitive in this direction. It is very directional but rather insensitive. This is remedied by a low-noise self-powered preamplifier.

The directional microphone can be built quite cheaply.

The microphone casing is cast in plaster of Paris in a simple mould made of card or heavy paper.

There should be no difficulty in doing this if the mould is waxed (by rubbing with a candle) before the plaster is poured in. This should be mixed with plenty of water and poured in immediately. The cast will get quite warm as the plaster hardens. Small air-bubbles in the cast do not matter. The outer surface can be left plain, painted, or covered with material as desired. A coat of glossy paint will help protect it against chipping.

The microphone cartridge chosen has a metal case and a tiny gauze-covered round "window". It is not very directional as the case is very thin. The first step is to encapsulate the cartridge in Araldite epoxy cement leaving only the "window" exposed. Successive layers of cement are applied until the cartridge is deeply embedded. Use plenty of cement (about half a 6s. two-tube pack) to give the encapsulation plenty of weight. Three cotton threads are

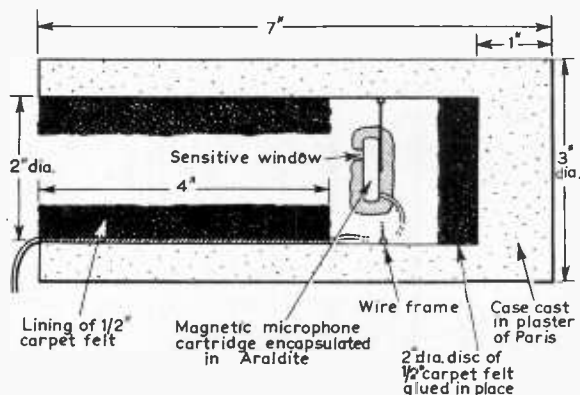


Fig. 2 (a): Cross-section of the microphone.

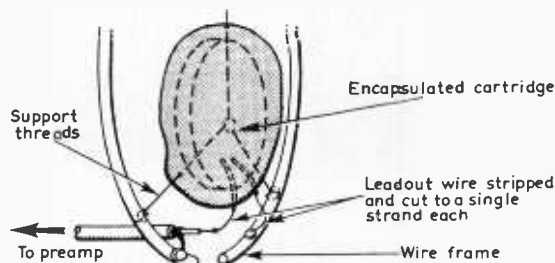


Fig. 2 (b): Cartridge connections. Leave sufficient slack in the leadout wires to allow for cartridge movement.

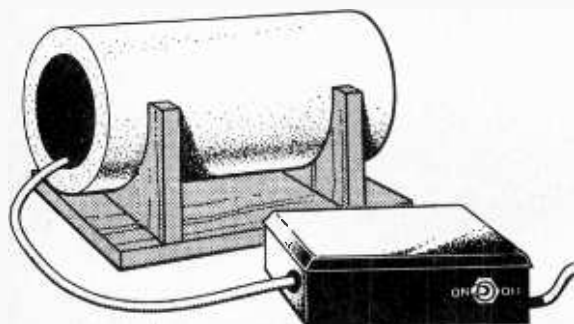


Fig. 1: Directional microphone and preamplifier, with microphone table stand.

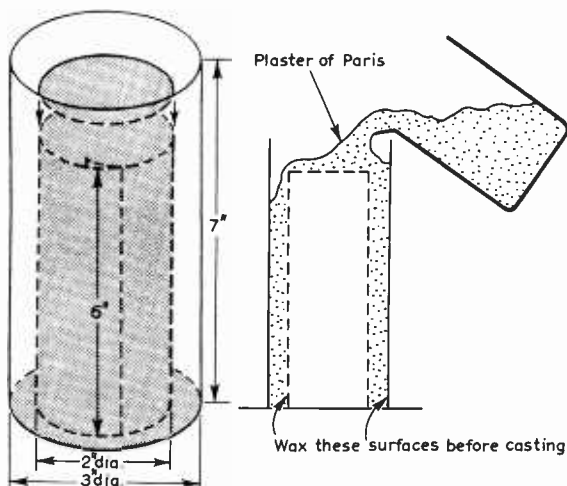


Fig. 3: Paper mould for casting the microphone case.

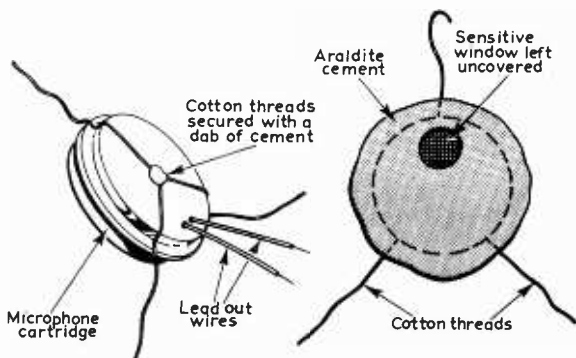


Fig. 4: Microphone cartridge encapsulation.

embedded with the cartridge as shown in Fig. 4 and the lead-out wires are brought out at the back. The cartridge will now be found to be less sensitive but much more directional. The weight of Araldite used also makes it less sensitive to handling noises, i.e. sounds picked up by mechanical contact.

About six inches of stiff wire is bent into a round frame about two inches in diameter. This should be a tight push fit into the plaster case. The encapsulated cartridge is now mounted in the frame by tying and cementing the support threads to it. In this way the cartridge is mechanically isolated as far as possible. It is mounted eccentrically with the sensitive "window" at the centre of the frame. It must not touch the frame and some Araldite should be filed away if this occurs.

The stranded lead-out wires are stripped and cut down to a single strand each. They are soldered to a screened cable as shown in Fig. 2b. Note that the strands are left slack to allow for movement of the cartridge. The cable screen is connected to the wire frame.

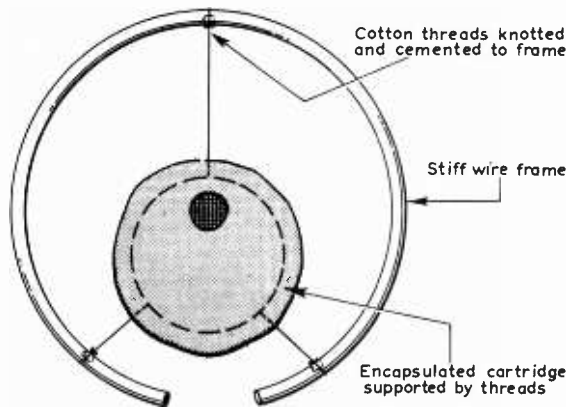


Fig. 5: Cartridge mounting. Sensitive window must be in centre of frame, and the frame a push fit in the plaster microphone case.

Two pieces of ordinary carpet felt are used. Felt about $\frac{1}{2}$ in. thick is suitable. A 2 in. diameter disc of felt is cut and glued inside the plaster case. The frame carrying the cartridge is now pushed into the case until the cartridge almost touches the felt. Another piece of felt is now rolled into a 4 in. long cylinder and pushed into the case, not far enough to touch the cartridge. The microphone cable is brought out under the felt to the front (or through a small hole drilled in the plaster) and the microphone is complete. The cartridge "window" should just be visible at the back of the case and the encapsulated cartridge should not touch the wire frame, the felt or the case.

To compensate for the low sensitivity of the microphone a two-transistor preamp is used. This is wired inside a small (tobacco) tin and is self-powered. The input cable from the microphone should be as short as possible.

Two silicon n-p-n transistors are used. The microphone signal is coupled by C1 to the base of Tr1 which is operated at low collector current for low noise. The divider R1/R2 furnishes base bias. Part of the emitter resistance (R4) is not decoupled by C2 and therefore provides negative feedback, reducing noise further. The amplified signal is taken from Tr1 collector to the base of Tr2 by C3. Tr2 is connected as an emitter follower with the output

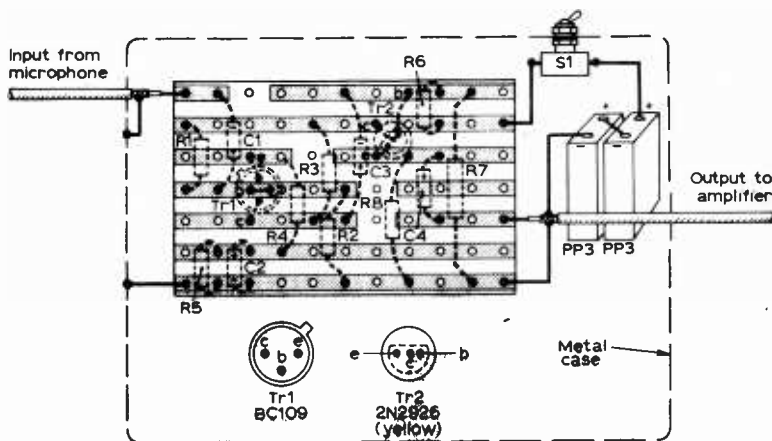


Fig. 6: The preamplifier can be conveniently wired on Veroboard.

★ components list

Resistors:

R1	39kΩ	R5	4.7kΩ
R2	6.8kΩ	R6	22kΩ
R3	22kΩ	R7	22kΩ
R4	470Ω	R8	1.8kΩ
All ¼W 10%			

Capacitors:

C1	50μF 6V electrolytic
C2	50μF 6V electrolytic
C3	50μF 6V electrolytic
C4	100μF 10V electrolytic

Semiconductors:

Tr1	BC109 (Mullard)
Tr2	2N2926 (yellow)

Miscellaneous:

'Norman' magnetic microphone cartridge; 1 pack Araldite epoxy cement; cotton thread; 6in. heavy gauge wire; plaster of Paris; ½in. carpet felt; S1 SPST on/off switch; B1 2 x PP3 batteries; battery clips; Veroboard; metal box; screened cable, etc.

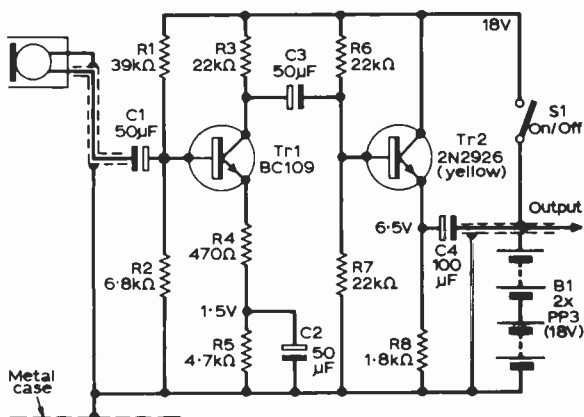


Fig. 7: Low-noise preamplifier circuit.

signal appearing across R8. The output here is of low impedance and may therefore be run through several yards of screened cable without hum pickup problems. It can be fed to an amplifier or tape recorder.

The circuit can be wired on a small piece of Veroboard as shown in Fig. 6. The components are closely packed, so check that they will fit on the board before wiring. After cutting the copper strips as shown in Fig. 6 the components are wired, leaving the transistors until last. No excessive precautions need be taken with these but *do not* shorten their leads and *do* solder as quickly as possible. Note the different wire arrangements of the two transistors.

The circuit is connected via S1 to two PP3 9-volt batteries in series and mounted inside the tin. The tin is connected to the input and output cable screens. The output lead is fitted with a suitable plug and the microphone is ready for use. The way in which it is mounted will depend on the application; a suitable table stand is shown in Fig. 1. ■

THE MW COLUMN

It is unlikely that the MW DXer will be content merely to log a distant station. Much of the pleasure of DXing in this band comes from writing to stations, telling them they have been heard and hoping they will reply with a "verification" which can be preserved as a memento and shown to other DXers.

Obtaining a QSL from medium wave stations requires a rather different approach than when writing to those on the short waves. The latter operate international services aimed at listeners abroad and these stations are usually very pleased to make contact with their audience and to provide them with QSL cards, programme schedules etc. The MW DXer however is located well outside the service area of the stations he listens to and he should remember that they are doing him a favour when they reply as he is really an eavesdropper. Many MW stations are genuinely surprised and pleased to have been heard at a great distance and will verify a correct report with pleasure, sometimes publicising it over the air or in the local press.

A reception report to a MW station should contain sufficient evidence in the form of programme details to enable the station to check that they were really heard by the DXer. It should be sent off as soon as possible after the logging and must always be accompanied by return postage. Unused foreign postage stamps can be obtained from stamp dealers but an International Reply Coupon is more convenient and can be purchased at main post offices.

North American stations are good verifiers. Many issue QSL cards and nearly all will reply to an accurate reception report. These should be sent to the Chief Engineer while the address should include the station call letters (e.g. Radio Station WINS) followed by the name of the city or town and the state (or province if in Canada). Mention the frequency, call letters, date and time of reception (preferably in the local time of the station) and details of the programmes heard must always be given. A common error made by beginners is to compile a list of records or the titles of tunes played over the air. Unfortunately, stations seldom retain this information. In the United States a station log is kept of all announcements made. Station identification comes on the hour and generally on the half-hour too. Commercials, names of announcers, weather reports, public service announcements, station slogans, provide the "meat" from which the DXer can compile a report which the station staff can check against the station log. Reporting codes such as SINPO or RST should be avoided, so should the use of International Q Code abbreviations such as "QRM" as it is unlikely these will be understood. Just give a simple verbal description such as "the signal was strong (or weak)". Conclude the report with a brief description of the receiver and aerial in use and then *request* a verification. Finally, do not forget to thank the Chief Engineer for taking the time and trouble to reply—he is probably a busy man.

CHARLES MOLLOY

TRANSISTOR OUTPUT STAGES

PART 2

I. R. SINCLAIR

Continued from June

Transformer Input

This type of input is shown in Fig. 7. The input transformer has three windings, the two primaries usually being wound bifilar, meaning that two wires are wound as one so that the windings are as near as possible identical. The ratio is not very important and is usually about 3 : 1+1, meaning three primary turns to one turn on each secondary.

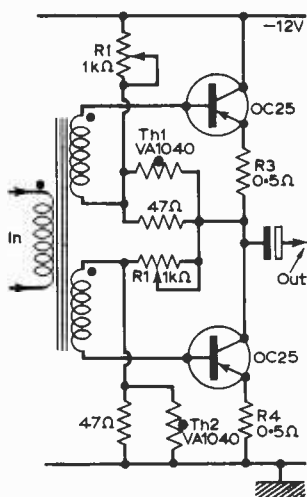


Fig. 7: A transformerless-output amplifier with a driver transformer enables the amplifier to be driven by a single-ended stage.

The use of a transformer means that single-ended stage can be used for driving, and that the driving transistor need not supply the full current required for the bases of the output transistors. This is important in a high power stage where the bases may take peak currents of 0.5A, requiring a lower power output stage to drive them. For amplifiers with outputs of 10W or more, this is an economical and reliable circuit, and the transformer imposes very little restriction on the band-width. A suitable transformer design is shown in Table 2.

Paraphase Transistor Input

A long-tailed pair circuit driving through CR coupling can be used just as in valve practice, provided that the bias is suitable for each transistor of the totem pair, but the most common transistor driving circuit is the complementary pair shown in Fig. 8, which is directly coupled to the output pair.

The bias on the output pair now depends on the current in the complementary pair, which in turn is regulated by the voltage between their bases; the voltage at the output (which should be midway between — and + lines) is regulated by the voltage level at the collector of the driver. In most circuits the driver bias is used to adjust the voltage level of the output and the small load resistor between base connections to the complementary pair is used to adjust output current. This small load resistor usually consists of a resistor in parallel with a thermistor so that there is some compensation for temperature effects. Note that each transistor of the complementary pair must be able to supply the maximum base current demanded by each output transistor, so that load resistors must be small and bias current fairly high.

Complementary Pair Output


If, in the previous circuit, the complementary pair can provide sufficient power, we can remove the final pair and use the complementary pair as the output. This is an admirably simple arrangement provided suitable pairs of transistors can be found. Such pairs are now available in the lower powers (for example AC128/AC176 for about 2½W, AD161/AD162 for about 6W) although not so easily found in the higher power range among transistors manufactured in this country. A typical circuit is shown in Fig. 9.

Load Coupling and Drive Impedance

A totem-pole output pair can be coupled directly to a load, provided that the other terminal of the load can be biased to the same voltage as the no-signal voltage at the output. This normally requires a tapped power supply, which is no difficulty if the amplifier is designed to operate from two 12V batteries, as are many public address amplifiers, but there is always a difficulty in ensuring that no direct current flows through the load; particularly important when this load is a loudspeaker, as a steady current causes the cone to be displaced from rest position.

In a mains operated circuit it is more normal to


Table II

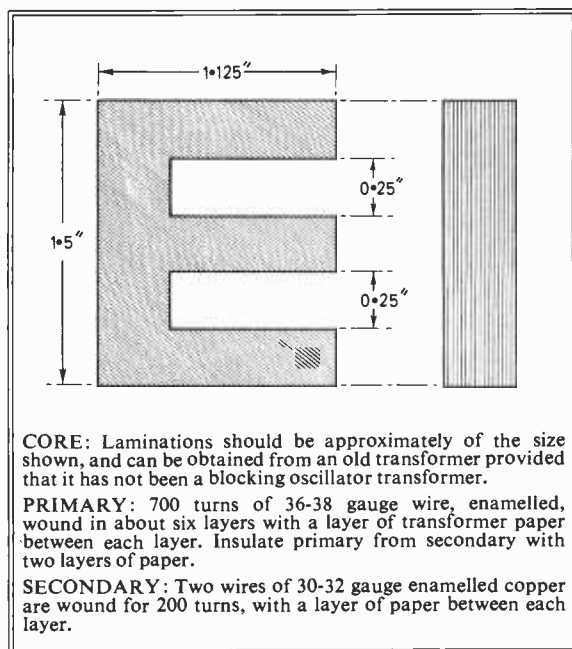

*The design that's
based on
Peak Sound
Cir-Kit*

P.W. DOUBLE 12

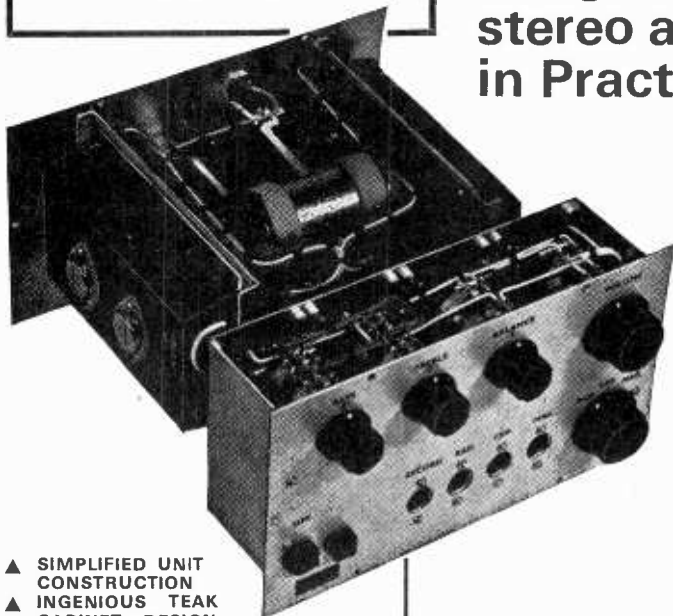**Integrated high-fidelity
stereo amplifier as described
in Practical Wireless**



Peak Sound are justifiably proud to be associated with this outstandingly successful P.W. design and that so much of it has been made possible because of Peak Sound products and design techniques. Basically, the design of the "P.W. Double 12" demonstrates the value of using "Cir-Kit" in modern circuit board units whether for single or prototype examples. In this instance, however, Peak Sound have contributed more besides to the success of this project. This includes the remarkable power amplifiers, the power pack and the ingeniously styled cabinet which almost assembles itself, it is so simple to build. The "P.W. Double 12" has already been fully described in Practical Wireless for April, May and June, so that you can go right ahead now and build this exciting new design with authentic, exact-to-specification Peak Sound kits as described. With this unit you will be able to enjoy standards of reproduction of the highest order for very modest outlay.

- ▲ SIMPLIFIED UNIT CONSTRUCTION
- ▲ INGENIOUS TEAK CABINET DESIGN
- ▲ PROFESSIONAL IN EVERY WAY AND MONEY SAVING TOO!

This is your "P. W. Double 12" shopping list

These are the Peak Sound units with which you can build this excellent design. They are exact to specification. Transistors included.

2 Spools of "Cir-Kit" at 2/- each	4	0
2 Pre-amp and tone control kits	4	13 0
4 Pre-amp matrix boards	7	0
2 PA.12-15 Power Amplifier Kits	7	19 0
2 Heat Sink assemblies	12	0
2 P.A. matrix boards	8	0
1 PS.45K 45 volt power supply kit	4	10 0
1 Pack-flat afroomsia teak finished Cabinet kit	2	12 6
5 Controls as specified	2	0 0

TOTAL COST £23 5 6

Metal work (make or buy), knobs, plugs and sockets, fuses etc. allow £3.0.0. From your local dealer.

Go to your Dealer NOW

for your authentic Peak Sound Kits. In case of difficulty, please send direct, giving the name and address of your usual supplier where possible and add 11/- postage for complete assembly, or 5/6 if without power pack.

TRADE ENQUIRIES INVITED

PEAK SOUND (HARROW) LTD., 32 ST JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, Phone EGHAM 5316

"CIR-KIT" makes it possible!



"Cir-Kit" is at the heart of building this fine design. Made from almost 100% pure copper with unique adhesive backing, it is the superb circuit builder for all requirements. In 5' spools, $\frac{1}{16}$ " wide, 2/- each.

▲ P.W. Double 12 abridged specification

Formation—Two pre-amp panels, two tone control panels, two power amplifier modules, power supply unit on chassis, housed within teak finished cabinet.
Controls—Bass and treble cut and lift based on Baxandall circuitry/Volume/Balance/Rotary selector.
Input Sensitivity—Magnetic P.U. (per channel) 2-5mV into 68k Ω . Ceramic P.U.—25mV into 27K Ω , equalised for flat response. Radio/Aux. 60mV.
HIGH OVERLOAD FACTOR ON ALL INPUTS.
Frequency Response—20Hz to 30KHz $\pm$ 1dB overall.
Output—12 watts per channel into 15 Ω (8 Ω) speakers

may be used).

Negative Feedback—43dB over each section.
Power required—45V D.C. (supplied by built-in power unit).

Cabinet—Afroomsia teak finish, pack-flat, easy to build kit. Size 9 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in. high x 9 $\frac{1}{2}$ in. deep.

Transistors—Ultra low noise in pre-amp and tone control stages.

PERFORMANCE CHARACTERISTICS. PARTS REQUIRED, ETC., SEE P.W. FOR APRIL, MAY AND JUNE.

THESE PEAK SOUND PRODUCTS WILL HELP



PA.12-15 POWER AMPLIFIER

As specified for "P.W. Double 12" and available ready built complete with heat sink for mounting directly into position as described, but can also be used in other applications. Also available as a kit less heat sink and board.

Built **£5.19.6**

Kit (less heat sink, board and "Cir-Kit") **79/6**

Heat sink and baseboard assembly **10/-**

Please add 2/6 p/p either model if ordered direct, or 5/- for two.

ES. 10-15 BAXANDALL SPEAKER

This easy to build loudspeaker provides genuine hi-fi standards by the use of unique equalising principles. Frequency response 60-14,000Hz (100-10KHz $\pm$ 3dB). Easy-to-build kit including 18 x 12 x 10 in cabinet.



£10.2.3

(Carr. 12/6). Leaflet available. + £1.2.0 P/Tax

BENTLEY ACoustic CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone Primrose 9090

EXPRESS POSTAL SERVICE. SAME DAY DESPATCH BY FIRST CLASS MAIL.

All goods are offered subject to the standard three month guarantee.

0A2 5/9	6D6 3/-	12A77 3/9	90AV 87/6	DW4/350	BH90 8/8	N78 38/4	R20 11/9	VP4B 10/8	AFZ12 5/-	M3 2/10
0B2 6/-	6E5 7/6	12A06 4/9	90CG 34/6	DW4/500	BL32 3/8	N108 27/4	RP34 7/8	VP32 2/8	ASV27 8/8	0A5 5/8
0Z4 4/3	6F1 8/9	12A07 4/8	90CV 33/6		EL33 12/-	N152 7/3	SP4 7/8	VP32 2/8	ASV28 8/8	0A9 2/8
1A3 4/4	6F6 4/-	12A08 4/8	90C1 16/-		EL34 10/-	N308 17/6	SP13C 12/6	VP32 2/8	ASV29 10/-	0A7 2/-
1A7GT 7/-	6F8 3/3	12A09 4/8	90C2 15/-		EL35 10/-	N339 25/-	SP12 12/6	VP32 2/8	BA102 9/-	0A70 3/8
1C1 5/6	6F13 3/8	12A17 8/9	150C2 5/9		EL37 17/3	N359 7/3	SP11 3/3	VP32 2/8	BA105 2/8	0A73 3/8
1C2 7/9	6F15 9/6	12B0A 6/-	302 16/-		EL38 24/-	N379 6/3	TH44 3/3	VP32 2/8	BA116 9/-	0A79 1/9
1C3 7/9	6F18 7/6	12B0B 5/9	303 15/-		EL39 24/-	N389 12/-	TH45 10/-	VP32 2/8	BA129 2/8	0A81 1/9
1C5 4/9	6F23 13/3	12B0T 6/-	305 16/-		EL40 24/-	N399 4/8	TH46 10/-	VP32 2/8	BA130 2/8	0A85 1/8
1D5 6/9	6F24 11/9	12E1 17/-	306 13/-		EL41 9/8	N709 4/8	TH47 10/-	VP32 2/8	BC101 3/8	0A86 1/8
1D6 9/8	6F25 11/9	12J5GT 2/6	807 11/9		EL42 9/8	N709 4/8	TH48 10/-	VP32 2/8	BC102 3/8	0A87 1/8
1FD1 6/-	6F28 10/6	12J7GT 6/8	956 2/-		EL43 9/8	N709 4/8	TH49 10/-	VP32 2/8	BC103 3/8	0A88 1/8
1FD9 3/9	6F32 3/-	12K5 10/-	1821 10/9		EL44 9/8	N709 4/8	TH50 10/-	VP32 2/8	BC104 3/8	0A89 1/8
1G6 6/-	6G06 2/6	12K7GT 5/9	5763 10/8		EL45 9/8	N709 4/8	TH51 10/-	VP32 2/8	BC105 3/8	0A90 1/8
1H5GT 7/-	6H6GT 1/9	12K8GT 7/8	6060 5/8		EL46 9/8	N709 4/8	TH52 10/-	VP32 2/8	BC106 3/8	0A91 1/8
1L4 2/6	6J5G 3/8	12Q7GT 4/8	7193 10/8		EL47 9/8	N709 4/8	TH53 10/-	VP32 2/8	BC107 3/8	0A92 1/8
1LD5 6/-	6J5GT 4/8	12S7GT 2/6	7475 4/-		EL48 9/8	N709 4/8	TH54 10/-	VP32 2/8	BC108 3/8	0A93 1/8
1LN5 8/-	6J6 3/-	12S8GT 2/6	8184 20/-		EL49 9/8	N709 4/8	TH55 10/-	VP32 2/8	BC109 3/8	0A94 1/8
1NSGT 7/9	6J7GT 4/9	12S9GT 3/-	AC2PEN 19/6		EL50 9/8	N709 4/8	TH56 10/-	VP32 2/8	BC110 3/8	0A95 1/8
1P1 7/-	6J7GT 6/8	12S9GT 3/-	AC2PEN 19/6		EL51 9/8	N709 4/8	TH57 10/-	VP32 2/8	BC111 3/8	0A96 1/8
1P10 4/9	6K6GT 5/-	12S9GT 3/-	AC2PEN 19/6		EL52 9/8	N709 4/8	TH58 10/-	VP32 2/8	BC112 3/8	0A97 1/8
1P11 5/6	6K7GT 5/-	12S9GT 3/-	AC2PEN 19/6		EL53 9/8	N709 4/8	TH59 10/-	VP32 2/8	BC113 3/8	0A98 1/8
1R5 5/6	6K8GT 5/-	12S9GT 3/-	AC2PEN 19/6		EL54 9/8	N709 4/8	TH60 10/-	VP32 2/8	BC114 3/8	0A99 1/8
1R5 3/9	6K8GT 3/-	12Y4 2/-	AC2PEN 19/6		EL55 9/8	N709 4/8	TH61 10/-	VP32 2/8	BC115 3/8	0A99 1/8
1T4 2/9	6L1 19/6	13D3 9/-	AC2PEN 19/6		EL56 9/8	N709 4/8	TH62 10/-	VP32 2/8	BC116 3/8	0A99 1/8
1U4 5/9	6L6GT 7/9	14H7 9/8	AC2PEN 19/6		EL57 9/8	N709 4/8	TH63 10/-	VP32 2/8	BC117 3/8	0A99 1/8
2A7 12/8	6L8 18/8	14S7 9/8	AC2PEN 19/6		EL58 9/8	N709 4/8	TH64 10/-	VP32 2/8	BC118 3/8	0A99 1/8
2D13C 7/-	6L19 19/-	19 10/8	AC2PEN 19/6		EL59 9/8	N709 4/8	TH65 10/-	VP32 2/8	BC119 3/8	0A99 1/8
2D21 5/8	6L19GT 8/6	19A05 4/9	AC2PEN 19/6		EL60 9/8	N709 4/8	TH66 10/-	VP32 2/8	BC120 3/8	0A99 1/8
2X2 4/9	6N7GT 6/6	19H1 40/-	AC2PEN 19/6		EL61 9/8	N709 4/8	TH67 10/-	VP32 2/8	BC121 3/8	0A99 1/8
3A4 3/6	6P1 12/-	20D1 13/-	AC2PEN 19/6		EL62 9/8	N709 4/8	TH68 10/-	VP32 2/8	BC122 3/8	0A99 1/8
3A5 10/-	6P2 12/-	20D4 20/5	AC2PEN 19/6		EL63 9/8	N709 4/8	TH69 10/-	VP32 2/8	BC123 3/8	0A99 1/8
3B7 5/-	6P26 12/-	20F2 14/-	AC2PEN 19/6		EL64 9/8	N709 4/8	TH70 10/-	VP32 2/8	BC124 3/8	0A99 1/8
3D6 3/9	6P28 25/-	20L1 13/-	AC2PEN 19/6		EL65 9/8	N709 4/8	TH71 10/-	VP32 2/8	BC125 3/8	0A99 1/8
3Q4 6/6	6Q7G 6/-	20P1 17/6	AC2PEN 19/6		EL66 9/8	N709 4/8	TH72 10/-	VP32 2/8	BC126 3/8	0A99 1/8
3Q5GT 8/-	6Q7GT 8/6	20P3 18/6	AC2PEN 19/6		EL67 9/8	N709 4/8	TH73 10/-	VP32 2/8	BC127 3/8	0A99 1/8
3S4 4/9	6R7G 7/9	20P4 18/6	AC2PEN 19/6		EL68 9/8	N709 4/8	TH74 10/-	VP32 2/8	BC128 3/8	0A99 1/8
3V4 5/6	6R7M 1/9	20P5 18/6	AC2PEN 19/6		EL69 9/8	N709 4/8	TH75 10/-	VP32 2/8	BC129 3/8	0A99 1/8
4D1 3/9	6S4GT 7/7	25A6G 7/8	AC2PEN 19/6		EL70 9/8	N709 4/8	TH76 10/-	VP32 2/8	BC130 3/8	0A99 1/8
5R4GY 9/9	6A7 7/-	25L6G 5/8	AC2PEN 19/6		EL71 9/8	N709 4/8	TH77 10/-	VP32 2/8	BC131 3/8	0A99 1/8
5U4G 4/9	6C7GT 6/6	25Y5 6/-	AC2PEN 19/6		EL72 9/8	N709 4/8	TH78 10/-	VP32 2/8	BC132 3/8	0A99 1/8
5V4G 7/6	6S0GT 6/-	25Y5G 8/6	AC2PEN 19/6		EL73 9/8	N709 4/8	TH79 10/-	VP32 2/8	BC133 3/8	0A99 1/8
5Y3GT 5/6	6B7 3/-	25Z4G 6/-	AC2PEN 19/6		EL74 9/8	N709 4/8	TH80 10/-	VP32 2/8	BC134 3/8	0A99 1/8
5Z3 8/-	6B7 6/6	25Z5 6/-	AC2PEN 19/6		EL75 9/8	N709 4/8	TH81 10/-	VP32 2/8	BC135 3/8	0A99 1/8
5Z4G 6/9	6B7GT 4/6	25Z6G 8/6	AC2PEN 19/6		EL76 9/8	N709 4/8	TH82 10/-	VP32 2/8	BC136 3/8	0A99 1/8
6J30L2 12/6	6B7GT 4/6	30C1 6/6	AC2PEN 19/6		EL77 9/8	N709 4/8	TH83 10/-	VP32 2/8	BC137 3/8	0A99 1/8
6A8G 5/6	6B7GT 4/6	30C15 13/6	AC2PEN 19/6		EL78 9/8	N709 4/8	TH84 10/-	VP32 2/8	BC138 3/8	0A99 1/8
6A7 3/6	6B87 3/-	30C17 12/6	AC2PEN 19/6		EL79 9/8	N709 4/8	TH85 10/-	VP32 2/8	BC139 3/8	0A99 1/8
6A5G 3/6	6U4GT 12/-	30C18 8/6	AC2PEN 19/6		EL80 9/8	N709 4/8	TH86 10/-	VP32 2/8	BC140 3/8	0A99 1/8
6A76 8/6	6U7 8/-	30F1 13/6	AC2PEN 19/6		EL81 9/8	N709 4/8	TH87 10/-	VP32 2/8	BC141 3/8	0A99 1/8
6AK5 4/6	6V6G 3/6	30FL1 15/-	AC2PEN 19/6		EL82 9/8	N709 4/8	TH88 10/-	VP32 2/8	BC142 3/8	0A99 1/8
6AK6 6/-	6V6GT 6/-	30FL12 18/-	AC2PEN 19/6		EL83 9/8	N709 4/8	TH89 10/-	VP32 2/8	BC143 3/8	0A99 1/8
6AK8 6/-	6X4 3/6	30FL13 8/-	AC2PEN 19/6		EL84 9/8	N709 4/8	TH90 10/-	VP32 2/8	BC144 3/8	0A99 1/8
6AL5 2/3	6X5GT 5/-	30FL14 12/6	AC2PEN 19/6		EL85 9/8	N709 4/8	TH91 10/-	VP32 2/8	BC145 3/8	0A99 1/8
6AM5 2/6	6V6G 8/-	30L1 6/-	AC2PEN 19/6		EL86 9/8	N709 4/8	TH92 10/-	VP32 2/8	BC146 3/8	0A99 1/8
6AM6 3/3	6V7G 12/6	30L15 13/6	AC2PEN 19/6		EL87 9/8	N709 4/8	TH93 10/-	VP32 2/8	BC147 3/8	0A99 1/8
6AQ5 4/9	7A7 12/6	30L17 13/-	AC2PEN 19/6		EL88 9/8	N709 4/8	TH94 10/-	VP32 2/8	BC148 3/8	0A99 1/8
6AR6 20/-	7AN7 6/-	30P4 12/6	AC2PEN 19/6		EL89 9/8	N709 4/8	TH95 10/-	VP32 2/8	BC149 3/8	0A99 1/8
6AT6 4/-	7B6 10/9	30P4MR 17/-	AC2PEN 19/6		EL90 9/8	N709 4/8	TH96 10/-	VP32 2/8	BC150 3/8	0A99 1/8
6AU8 5/-	7B7 7/-		AC2PEN 19/6		EL91 9/8	N709 4/8	TH97 10/-	VP32 2/8	BC151 3/8	0A99 1/8
6AV6 5/-	7C6 6/-	30P12 13/-	AC2PEN 19/6		EL92 9/8	N709 4/8	TH98 10/-	VP32 2/8	BC152 3/8	0A99 1/8
6B8G 2/6	7D6 15/-	30P19 12/-	AC2PEN 19/6		EL93 9/8	N709 4/8	TH99 10/-	VP32 2/8	BC153 3/8	0A99 1/8
6BA6 4/6	7H7 5/6	30P11 15/-	AC2PEN 19/6		EL94 9/8	N709 4/8	TH100 10/-	VP32 2/8	BC154 3/8	0A99 1/8
6BE6 4/3	7R7 12/-	30P13 15/-	AC2PEN 19/6		EL95 9/8	N709 4/8	TH101 10/-	VP32 2/8	BC155 3/8	0A99 1/8
6BG6G 20/5	7B7 20/-	30P14 15/-	AC2PEN 19/6		EL96 9/8	N709 4/8	TH102 10/-	VP32 2/8	BC156 3/8	0A99 1/8
6BH6 7/6	7V7 5/-	30P15 15/-	AC2PEN 19/6		EL97 9/8	N709 4/8	TH103 10/-	VP32 2/8	BC157 3/8	0A99 1/8
6BQ6 6/9	7Y4 6/6	35A5 15/-	AC2PEN 19/6		EL98 9/8	N709 4/8	TH104 10/-	VP32 2/8	BC158 3/8	0A99 1/8
6BQ5 4/6	7Z4 4/6	35D5 11/9	AC2PEN 19/6		EL99 9/8	N709 4/8	TH105 10/-	VP32 2/8	BC159 3/8	0A99 1/8
6BQ7A 7/-	8BW6 7/-	35L6GT 8/-	AC2PEN 19/6		EL100 9/8	N709 4/8	TH106 10/-	VP32 2/8	BC160 3/8	0A99 1/8
6BR7 8/6	9D7 9/-	35W4 4/6	AC2PEN 19/6		EL101 9/8	N709 4/8	TH107 10/-	VP32 2/8	BC161 3/8	0A99 1/8
6BR8 8/-	10C1 12/6	35Z3 10/-	AC2PEN 19/6		EL102 9/8	N709 4/8	TH108 10/-	VP32 2/8	BC162 3/8	0A99 1/8
6BR7 11/6	10C2 10/-	35Z4GT 4/9	AC2PEN 19/6		EL103 9/8	N709 4/8	TH109 10/-	VP32 2/8	BC163 3/8	0A99 1/8
6BW6 12/9	10D1 8/-	35Z5GT 6/-	AC2PEN 19/6		EL104 9/8	N709 4/8	TH110 10/-	VP32 2/8	BC164 3/8	0A99 1/8
6BW7 11/6	10D2 14/7	42 5/-	AC2PEN 19/6		EL105 9/8	N709 4/8	TH111 10/-	VP32 2/8	BC165 3/8	0A99 1/8
6BX8 4/8	10F1 15/-	43 10/-	AC2PEN 19/6		EL106 9/8	N709 4/8	TH112 10/-	VP32 2/8	BC166 3/8	0A99 1/8
6BZ6 6/-	10F9 9/-	50B5 8/6	AC2PEN 19/6		EL107 9/8	N709 4/8	TH113 10/-	VP32 2/8	BC167 3/8	0A99 1/8
6C4 2/9	10F18 7/6	50C6 6/3	AC2PEN 19/6		EL108 9/8	N709 4/8	TH114 10/-	VP32 2/8	BC168 3/8	0A99 1/8
6CGT 6/-	10LDS 7/6	50C6GT 6/3	AC2PEN 19/6		EL109 9/8	N709 4/8	TH115 10/-	VP32 2/8	BC169 3/8	0A99 1/8
6C5 3/9	10LD11 10/-	50C6GT 6/3	AC2PEN 19/6		EL110 9/8	N709 4/8	TH116 10/-	VP32 2/8	BC170 3/8	0A99 1/8
6C9 11/-	10P13 13/-	59KU 14/6	AC2PEN 19/6		EL111 9/8	N709 4/8	TH117 10/-	VP32 2/8	BC171 3/8	0A99 1/8
6CD6G 19/6	10P14 12/6	59KU 14/6	AC2PEN 19/6		EL112 9/8	N709 4/8	TH118 10/-	VP32 2/8	BC172 3/8	0A99 1/8
6CD7 9/6	12A6 3/6	72 8/6	AC2PEN 19/6		EL113 9/8	N709 4/8	TH119 10/-	VP32 2/8	BC173 3/8	0A99 1/8
6CH6 6/-	12A6G 6/-	73 6/6	AC2PEN 19/6		EL114 9/8	N709 4/8	TH120 10/-	VP32 2/8	BC174 3/8	0A99 1/8
6CL6 8/6	12A6G 6/-	75 8/6	AC2PEN 19/6		EL115 9/8	N709 4/8	TH121 10/-	VP32 2/8	BC175 3/8	0A99 1/8
6D3 7/6	12A76 4/6	90AG 67/6	AC2PEN 19/6		EL116 9/8	N709 4/8	TH122 10/-	VP32 2/8	BC176 3/8	0A99 1/8

MATCHED TRANSISTOR SETS 1—OC44 and 2—OC45 8/8; 1—OC81D and 2—OC81 7/8; 1—OC82D and 2—OC82 8/8; Set of three—OC83 (GET118/119) 8/8; LP15 package (AC113, AC154, AC157, AA120) 10/6; Postage 6d. per set. S.T.C. 1 watt Zener diodes. 2.4v: 2.7v: 3.0v: 3.6v: 4.3v: 13v: 16v: 18v: 30v. All 3/6d. each.

WE REQUIRE FOR PROMPT CASH SETTLEMENT ALL TYPES OF ABOVE GOODS LOOSE OR BOXED, BUT MUST BE NEW

ELECTROLYTICS. Can types: 8x8mfd/500v 7/9; 8x16mfd/500v 7/9; 16mfd/500v 6/-; 16x16mfd/500v 8/9; 16x32mfd/500v 9/9; 32mfd/500v 5/9; 50x50mfd/350v 5/6; 60x250mfd/275v 9/9; 50x50mfd/275v 8/6; 64x100mfd/450v 21/-; 64x120mfd/350v 8/6; 100x200mfd/275v 8/6; 100x200m

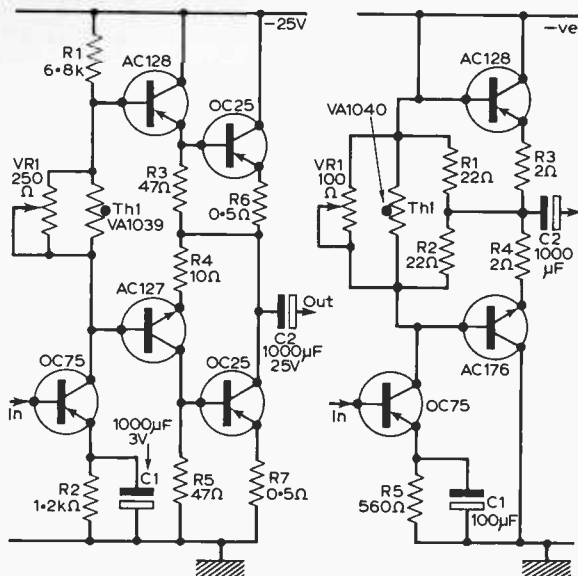


Fig. 8: A transformerless-output amplifier driven by a complementary pair.

Fig. 9: A simplification of Fig. 8 which can be adopted if the complementary pair can be made to provide sufficient power.

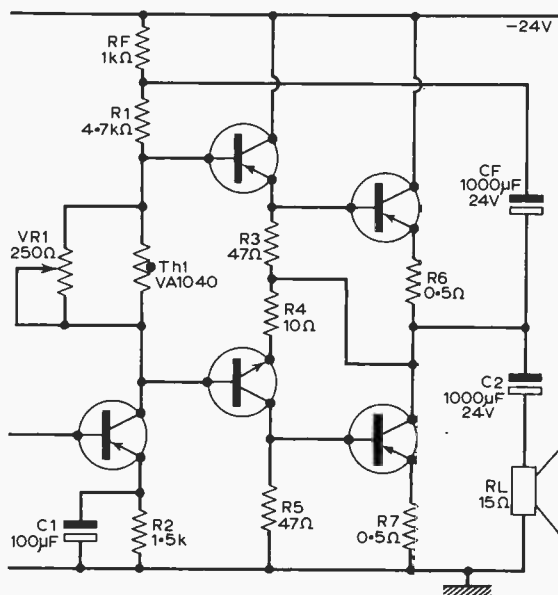


Fig. 10: If a loudspeaker coupling capacitor is used, positive feedback can be used to compensate for a lack of bass response.

couple the loudspeaker through a large capacitor (typically 1,000µF, 6V), and earth. This inevitably causes attenuation at low frequencies, but this can be compensated for by positive feedback (bootstrapping) back to the driver stage. An example of this is shown in Fig. 10. For this to be effective the feedback time constant ($C_F \times R_F$) should be considerably greater than the load time constant ($C_L \times R_L$), and fortunately this is usually easy to arrange.

In class B stages where the driver is CR coupled to the output transistors, the low input impedance is made worse by the low resistance of the bias network; necessarily low to prevent thermal runaway. This causes a restriction on low frequency amplification which can be dealt with by isolating the base from the bias network during the "on" time of the transistor. This is most easily arranged by connecting the bias through a diode which is back-biased during drive (Fig. 5).

Thermal Calculations

The power which can be dissipated in an output stage depends much more on the efficiency with which heat can be removed from the collector junction than on the type of transistor used. Several American manufacturers publish dissipations calculated for the case where all the heat generated in the case of the transistor could be removed with 100% efficiency (infinite heatsink); the practically obtainable dissipations are much less. British manufacturers usually quote more realistic ratings; for example, the dissipation of the OC28 is given as 30W provided the case temperature is less than 45°C. The actual dissipation which can be used depends on (1) the maximum collector junction temperature which can be tolerated (usually 90°C for germanium transistors and 200°C for silicon types) and (2) the resistance to the removal of heat caused by the connection to the case, heatsink etc.

For every transistor, the *thermal resistance* (which is

the heat equivalent of electrical resistance) of the collector junction is quoted. But before heat can be totally removed, it has to flow through mica washers, if used, to a heatsink and from there to the air around whose temperature must also be taken into account. Since all these resistances are in series, they have to be added together, and the power dissipation permissible is given by $P = \frac{T}{\theta}$ where T is the difference between the maximum junction temperature and the maximum air temperature and θ is the total thermal resistance in °C per watt.

For example, if the maximum junction temperature is 90°C, the maximum air temperature is 30°C and the thermal resistance is 4.5°C/W, the maximum dissipated power is $\frac{90-30}{4.5} = \frac{60}{4.5} = 13.3\text{W}$.

As a guide, the maximum air temperature for use in industrial atmosphere and in car radios is taken as 45°C; for indoor use in living rooms (for example, hi-fi equipment) 25°C is more realistic as the maximum provided the transistors are not in the path of heat from a radiator, fire or TV set. A thermal resistance of 4.0-4.5°C/W is also reasonable for most power transistors well bolted down to a *blackened* heatsink of aluminium at least 7in. square. If extruded alloy heatsinks are used, the thermal resistance should be known and should be added to that for the transistor (usually 1-2°C/W) plus an allowance of 0.5°C/W extra if a mica washer is used or 0.2°C/W if the transistor is bolted directly to the heatsink. In every case silicone grease should be used between transistor, mica and heatsink to ensure good thermal conductivity.

For most applications, it is preferable to mount transistors on separate heatsinks which are insulated from the chassis; this avoids the use of mica washers. The heatsink should be blackened before use by using matt black paint (obtainable from photographic suppliers) or printer's ink. The difference in thermal resistance between a polished metal surface and a matt black one is enough to mean the loss or use of two good transistors!

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents.

All a question of holes

Mr. Green is perfectly correct when he says that we have no difficulty in discussing a hole in our bank balance as an overdraft but this does not make it a tangible reality. You cannot withdraw an overdraft in the bank and pay it into another bank. You must first get an overdraft in another bank by withdrawing money from it and then you can satisfy the overdraft at the first bank.

In the same way a "hole" in a semiconductor cannot move without an equal and opposite movement of electrons. It is impossible to move a "hole" without moving electrons because it is not a tangible reality—it has no mass, no existence in its own right. The fact that we have to use the idea of holes in explaining transistor action would seem to point to an error in physical theory. In reality we have not explained transistor action but have "explained it away". Surely this is unscientific. D. H. Ross (Edinburgh).

A little therapy

I have to thank Mr. Green (Letters P.W. May 1969) both for taking the trouble to write and also for supplying a splendid example of incomprehensible thought—the characteristic symptom found in those of our unfortunate friends afflicted with Hiatitis Pungens.—A little therapy might help.

I have always understood, and the massive Oxford Dictionary convinces me, that the English language is the richest in the world fully capable of supplying the needs of anyone for any purpose. Certainly I have seldom been at a loss for words.

It would also give me much pleasure to be present at any time when Mr. Green found it necessary to explain to a man that the severe electric shock he had just received was an abstract idea quite incapable of description in the English language. No, Sir, it just will not do.

It is not the English language which is inadequate, it is the ideas which are wrong. For too long have the "blindlers with Science" had it all their own way and the time has come to call their bluff. I maintain that there is nothing at all complicated or diffi-

cult about transistor operation and, when I wrote my (March 1969 P.W.) letter I was under the impression that I was alone in denouncing "hole theory" in print. Since then one of my students has lent me a book which gives me powerful support. It is written by Dr. M. G. Suffern who, among other achievements before and since, ended the war—1945—as Deputy Director of Electronics, Ordnance Dept., US Forces.

Referring to n-p-n he writes:

"... Note the arrow on the emitter points away from the base, because of the same unfortunate compromise found in other devices in which the supposed current flows in an opposite direction to that of electrons. Conservative thinking cannot break away from old ideas and tend to complicate rather than simplify.

For our purposes, rather than to surrender to outmoded ideas, we shall continue to observe the (—ve) direction of current flow as is proper."

Again, later, referring to p-n-p, he writes:

"... In fact, some individuals call such positive charges 'holes', (atoms lacking an electron and bearing a positive charge). For our purposes, however, the actual electron flow comprises the electric current and the direction of such current is that of electron flow."

I like that "some individuals" bit. It puts the "holier than thou" theorist firmly in his place.

English is inadequate indeed! I am having to forcibly restrain myself to avoid writing sufficient to fill an issue of P.W.

A mathematician myself, I cannot see that directed numbers have any bearing on our discussion and Mr. Green has himself answered the only point he made, i.e., if the accident of history had been reversed and electrons were called positive instead of negative, he (not I) would have been talking about —ve "holes" so what difference does that make?

Even so, I still seem to be the only person with an alternative electron theory of p-n-p. The textbooks now appearing are adopting the crafty habit of describing n-p-n in detail and giving only a casual unexplained reference to p-n-p.

I do not know if my ideas are

100% correct but I do know that I am happy to go on record as stating categorically that "hole" theory is 100% nonsense.

I am in no predicament. I am simply heartily sick of teaching nonsense at the insistence of authors and examiners who should be setting an example of clear thought and not simply redrafting the same ideas in this uncritical manner. I am very grateful for the opportunity which P.W. has given me of making this firm protest. As I had already said in another place before this opportunity arose, I believe that "hole theory" is a great mistake and sooner or later it will have to be discarded. When that happens, all the "hole theorists" will jump on the wagon and will happily talk about things as they really are and hope that nobody will remember that they previously said something quite different. If anything I have said hastens this day, I shall be more satisfied. I repeat—there is nothing unimaginable about transistor theory as long as the imagination stays firmly with electrons. It is the incorrectness of the whole idea of "holes" which makes THAT theory unimaginable.—B. R. Meredith, G2CYV (London).

A fair swap

Which British reader of PRACTICAL WIRELESS would like to exchange his already-read monthly edition with the Dutch radio-magazine *Radio-Bulletin*.

Radio-Bulletin is a monthly with a contents identical to that of P.W., but in the Dutch language. This, however, will not give many difficulties, because schemes, sketches and symbols are international.


You will also find lots of advertisements in it, just as in P.W.

Please write to me.—B.W.C. van Albeslo (Bumerweg 8 Winterswijk—Holland).

We should like to thank readers for correspondence received on the subject of Commercial Radio. We shall shortly be publishing a selection of these letters.

"Listen in" on the World with HEATHKIT shortwave receivers

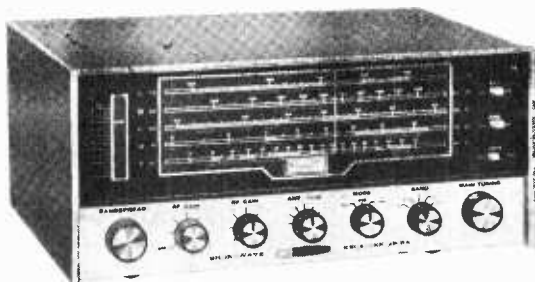TREAT YOURSELF TO A WORLD TOUR... *WITHOUT LEAVING HOME!*



GR-54

DELUXE 5 BAND SHORTWAVE RECEIVER GR-54


This receiver offers exceptional performance and many special features at such a low price. It covers 2MHz to 30MHz plus 550KHz to 1550KHz AM broadcast band and 150KHz to 420KHz aeronautical and radio navigation band. Receives AM/CW/SSB, 6 x 4in. PM speaker and sleek, "low-boy" styling. Operates on 115-230V 50Hz AC.

Kit K/GR-54 £44.16.0. Carr. 9/-

LOW COST 4 BAND SHORTWAVE RECEIVER GR-64

Makes an ideal present for the youngster. It has high performance features plus world-wide reception, shipping, aircraft, radio amateurs plus the popular medium broadcast band. It covers 1MHz to 30MHz plus 550KHz to 1620KHz AM, with sleek "low-boy" styling, operates on 115-250V 50Hz AC.

Kit K/GR-64 £22.8.0. Carr. 9/-

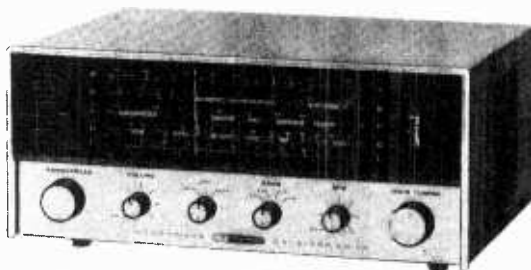

GR-64

GENERAL COVER- AGE RECEIVER GC-1U

A welcome traveller wherever you go! Covers 580 to 1550 KHz and 1.69 to 30MHz in 5 bands with calibrated bandspread scales for 80, 40, 20, 15 and 10 metre amateur bands. Completely solid state and self contained for portability. Operates on two internal PP6 batteries (not supplied) or 230V AC with a suitable power supply.

Kit K/GC-1U £39.16.0. Carr. 11/-



AMATEUR BANDS RECEIVER RA-1

Unequalled value for the radio amateur. Covers 160 to 10 metres. High quality lattice crystal filter for optimum communications selectivity. Optional 100KHz crystal calibrator plugs in inside receiver. 8 valve and 2 diode circuit. Operates on 115, 200-250V AC, 50Hz.

Kit K/RA-1 £39.16.0. Carr. 9/-



Free Catalogue !



See these models and many more in our 1969 catalogue. Models for Stereo/Hi-Fi, Industry, Education and the Home Workshop. Heathkit —the world's largest selling selection of electronic kits and equipment.

To
DAYSTROM LTD., Dept. PW-7, GLOUCESTER, GL2-6EE.

Please send me FREE CATALOGUE ☐

NAME

ADDRESS

Prices and specifications may be subject to change without prior notice

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.

THIS month we have a really simple project—a unit that simulates beautifully the sound of a time bomb ticking away! For those more attracted to gentler pastimes it may also serve as a metronome, that is it gives a loud click at regular intervals, the actual interval being varied by a potentiometer in the circuit. It's very simplicity also makes it highly suitable for use as an audio warning device, inserting the alarm switch in the supply line.

THE CIRCUIT

The actual working of the circuit is fairly simple; on applying a voltage across R1, VR1, C1 and the loudspeaker, the capacitor C1 charges up till a point is reached when Tr1 switches on, this in turn switches Tr2 to a conducting state meaning that a voltage is applied across the loudspeaker causing it to "plop". As these little electrons charge up the emitter lead and out through the collector a few get diverted and pass out through the base and neutralise the charge on C1 and soon the voltage on the base will reach the stage where the transistor is turned off; thus the cycle starts all over again. The rate at which C1 charges depends upon VR1 and thus by altering this the interval between each cycle can be varied.

SURPLUS TRANSISTORS

The actual transistors used are unimportant, I have tried a large variety and all have worked successfully. One of the transistors is a p-n-p, the other n-p-n and several advertisers are offering 60 or more germanium transistors and 30 or more silicon types at 10s. for each pack. The germanium ones are similar to the OC71, OC44 etc. and the silicon ones are like the BC108, BC109, 2N2926 etc; not all the transistors in these packs work, you will probably get about 10% duds (even many of these can be used as diodes) but those you have left work out at only pennies each and are ideal for projects such as this. In the near future I will be describing many projects using these unmarked transistors and for those who are following *Take 20* a pack of each will be an investment.

CONSTRUCTION

The components are mounted on a small piece of Veroboard, one end is drilled to take the potentiometer (¼ in. spindles are virtually standard) and the other components are mounted and soldered at the other end. The project is so simple that very little can go wrong and immediately you switch on regular "plops" will be heard. By altering VR1 a wide range

No. 3 A MINI METRONOME

of intervals should be covered but if you want slower ones—that is with several seconds' interval, increase the value of C1, if you want faster ones lower its value.

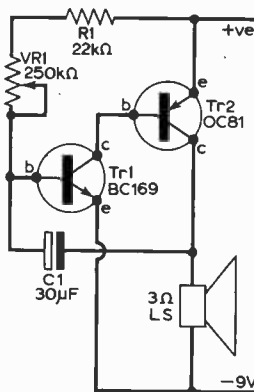


Fig. 1: The circuit

USES

The circuit described is certainly the cheapest method of getting a sound from a loudspeaker and thus it makes an ideal warning device, the plops themselves are loud and the unit could be used as a burglar alarm arranging the supply voltage to be switched on when a window is opened etc; even if the plopping isn't heard by anyone you can bet it'll get your unwelcome visitor worried. The

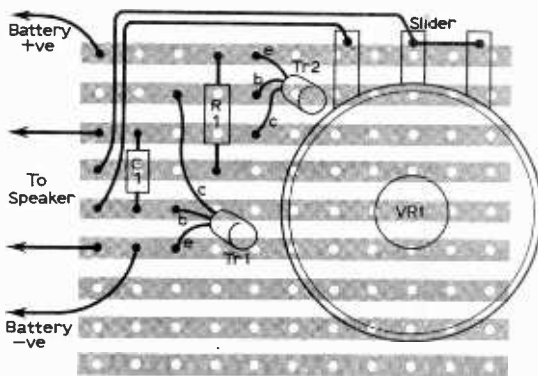


Fig. 2: The component layout on the Veroboard

★ components list

R1 22kΩ, 10%, ½W
C1 30μF 12V
VR1 250kΩ lin pot
Tr1 BC169, see text
Tr2 OC81, see text
Loudspeaker any 3Ω or 8Ω type
Veroboard 1½ × 1½ in. 0.15 in. matrix
9V battery

time intervals are regular and the unit will serve well for its intended use as a metronome providing the beat for music lessons etc.

Next month our project will be an electronic organ using a unijunction transistor. For those wanting to build it a 2N2646 or equivalent is needed; this should cost between 7/6 and 10/-.

P.W. GUIDE TO COMPONENTS

PART 7

M. K. TITMAN, B.Sc. (Eng)

ELECTROMAGNETIC devices are components which use the magnetic field derived from an energised coil to provide a force to actuate a mechanical movement. The most important components in this group are: relays, solenoids, loudspeakers, microphones and meters. As the principle of electromagnetic force has been understood for a considerable time all the devices in this group have been available in some form for many years. Therefore little discussion will be spent on operating principles but attention given to constructional features, design restrictions, availability, price and reliability.

Relays

Relays have been used since the days of the earliest "electric telegraph". Since then improved materials and methods of construction have increased their reliability and decreased their size. Figure 1 shows the essential

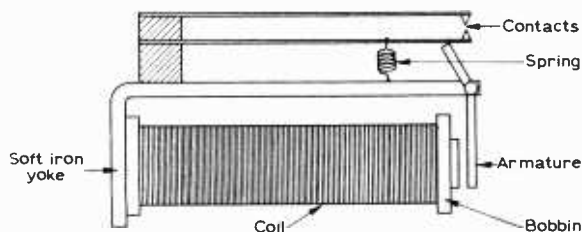


Fig. 1: Basic construction of a relay.

construction of a relay. It consists of a coil wound on a bobbin and soft iron core. The armature piece is fixed by means of a pivot and spring loaded away from the core pole. In this position the contacts are open. When the coil is energised the armature is attracted to the pole against the spring force and closes the contacts. The spring returns the armature to the contact open position when the coil is de-energised.

The action of a relay is that of a switch controlled by an electrical circuit. As the coil power is low a considerable power gain is inherent. Ideally therefore a relay should have a control coil which uses a minimum of power whilst the contacts should be capable of switching a maximum power. Also the mechanical construction should be such as to give the fastest speed of switching and greatest reliability.

The coil is constructed as a solenoid wound on a plastic bobbin with a soft iron or similar magnetic material core. The coil is designed for a specific operating voltage and the resistance determined by the magnetic force (ampere-turns (AT)) necessary to close the contacts. The coil power also has to overcome frictional forces and usually a power of 1-5W is used to

give the required characteristics, such as speed of switching, reliability etc. By semiconductor standards this power requirement is high and as a result usually necessitates a driver transistor in order to operate the relay. Because the relay coil is inductive, several limitations result in surge voltages due to the inductance which would break down the transistor. As a result a protection diode as shown in Fig. 2 is incorporated in

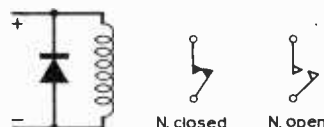


Fig. 2: Relay symbols.

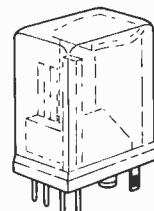


Fig. 3: Plug-in relay.

the circuit and allows a circulation path for the inductively maintained current. However this has the effect of maintaining the ampere-turns and consequently delays the contact release by 10-20msecs. The inductance and inertia also reduce the switch-on time which is also of the order of 10-20msecs.

The other essential component of a relay is the contacts. Usually the armature operates a bank of changeover contacts and from one to four such contacts are usual. The actual contact face is welded to a link and often the link is of spring steel and itself provides the return force for the armature. Contacts are made of palladium, silver-gold-plated silver, or gold, in order to have a low surface resistivity. The contact resistance determines the maximum current which the contacts can pass. However this is usually considerably greater than the maximum current which can be switched.

The relay contacts are perhaps the most unreliable component in the relay, especially in relays working near the maximum contact rating. The faults associated with contacts are: dirt on the contact surface which increases contact resistance; pitting and corrosion of the surface due to arcing; and welding of the contacts. For these reasons the contacts are manufactured from pure, inert metals and for greatest reliability should be operated well below the rated power levels. Modern relays are also often enclosed in a plastic casing in order to minimise the effect of dust and other surface corrosive elements. Plug-in relays are also commonly employed in modern circuits and Fig. 3 shows a typical plug-in, plastic enclosed relay. It is worth noting that for reliable operation it is essential to use a retaining clip to prevent movement of the relay.

Relays are commonly specified in terms of coil

COMET Hi-Fi DISCOUNT WAREHOUSE

- ALL ITEMS OFFERED ARE FULLY GUARANTEED AND BACKED BY COMET.
- OPENING HOURS OPEN DAILY UNTIL 5.30 p.m. (8.0 p.m. THURS. AND FRI. EVENINGS) AND 5.0 p.m. SATURDAY.
- COMPLETE FREE PRICE LIST CONTAINING OVER 500 ITEMS ON REQUEST.

	Rec. Retail Price	Comet Price
AMPLIFIERS		
DULCI 207 Stereo Amplifier	£23 2 0	£18 0 0
DULCI 207M Stereo/Amplifier takes magnetic P/U	£27 6 0	£21 19 0
DULCI 220 Princess	£44 2 0	£34 19 6
GOODMANS Maxamp	£54 0 0	£45 18 0
New LEAK Stereo 30 Plus	£52 0 0	£44 0 0
New LEAK Stereo 30 Plus In teak case	£58 10 0	£48 14 0
New LEAK Stereo 70	£63 0 0	£55 0 0
LINEAR LT.66 Stereo Amplifier	£15 15 0	£13 10 0
QUAD 33 Preamp/Amplifier	£43 0 0	£38 11 9
QUAD 303 Stereo Main Amplifier	£55 0 0	£49 15 0
ROGERS Ravensbourne 50 watt Stereo	£59 10 0	£50 12 0
ROGERS Ravensbourne In teak case	£64 0 0	£54 8 0
TRUVOX TSA.200	£51 9 0	£42 9 0
WHARFEDALE GP 50 Mark II P.A. Amplifier	Special Price	£50 0 0

TUNERS

ARENA 211 Stereo with decoder	£39 18 0	£34 18 0
DULCI FMT.7 FM Tuner	£22 1 0	£19 0 0
DULCI FMT.7S FM Stereo Tuner	£29 8 0	£23 0 0
GOODMANS Stereomax AM/FM Stereo Tuner	£80 19 0	£70 19 9
LEAK FM Troughline	£35 15 4	£30 10 4
LEAK Troughline Tuner with multiplex	£50 11 4	£42 19 6
QUAD Stereo FM Tuner	£50 0 0	£45 15 0
ROGERS Cadet Mark III Tuner	£20 12 6	£17 13 0
ROGERS Ravensbourne Tuner with Decoder	£60 15 3	£52 2 0
TRUVOX FM 200/IC Tuner	£52 0 0	£42 0 0

TUNER-AMPLIFIERS

ARENA 2400 with Decoder	£90 6 0	£75 0 0
ARENA 2500 complete with Decoder	£97 0 0	£79 0 0
TELETON MX.990 Stereo Tuner/Amplifier with AM/FM Multiplex Stereo	£64 13 2	£54 16 0
Radio c/w two Speakers each speaker containing 8in. bass, 2in. tweeter	£72 7 0	£59 19 6
TELETON 302X AM/FM Stereo Tuner/Amplifier 20 Watts RMS	£107 8 3	£84 0 0
TELETON 502X AM/FM Stereo Tuner/Amplifier 40 Watts RMS	£92 11 9	£75 0 0
TELETON 602X FM Multiplex Stereo Tuner/Amplifier 70 watts RMS	£43 0 0	£37 0 0
TELETON F.2000 AM/FM Stereo Tuner/Amplifier 2 x 5 watts RMS with silicon transistors	£60 19 6	£49 19 6
TELETON R.8000 AM/FM Stereo Tuner/Amplifier 2 x 6 watts RMS, complete with 2 speaker boxes	£126 0 0	£99 0 0
TELETON CMS.400 AM/FM Multiplex Tuner/Amplifier with 2 speaker boxes and turntable		

BUDGET HI-FI STEREO SYSTEMS

Garrard 3500 Turntable. Amplifier 8 watts per channel. VHF Tuner and pair of matched speakers beautifully finished in teak, at a low price of only

£85 0 0	£54 0 0
---------	---------

Van der Molen stereo system with Garrard SP25 mounted in teak case and perspex cover. Fitted with Sonotone Cartridge and Integrated stereo amplifier (12 watts R.M.S.). Complete with 2 speakers in teak cabinets

LL Nova with VHF Radio, Garrard 2025TC Auto-changer with cueing device. 10 watts RMS amplifier and 2 matched bookshelf speakers

Windsor 1500S Solid Teak plinth with Garrard 2025TC unit solid state amplifier 10 watts RMS and 2 speaker units with 9 x 5 ellipticals, complete with tweeter domes housed in solid teak cabinets of pleasing design

Also available with Garrard SP25 turntable
Phillips Stella ST 8008 with Philips Autochange turntable. Integrated transistorised stereo amplifier and 2 separate speakers. All in attractive teak cabinets

	Rec. Retail Price	Comet Price
Special Price	£52 0 0	

£72 9 6

£57 15 0

£61 19 0

£51 19 0

£44 0 0

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

SPEAKERS

CELESTION Ditton 10	£20 15 6	£17 16 0
CELESTION Ditton 15	£30 12 4	£26 5 0
DULCI AS3 Speaker	£8 8 0	£6 19 6
GOODMANS Maxim	£20 0 5	£16 19 6
GOODMANS Mezzo II	£30 18 0	£25 13 0
GOODMANS Magnum-K.	£40 2 0	£32 19 6
GOODMANS Mirimba	£26 0 0	£21 0 0
GOODMANS Mambo	£19 19 0	£15 0 0
LEAK Sandwich	£43 10 0	£35 19 6
LEAK Mini-Sandwich	£29 15 0	£24 10 0
TELETON SB.1002 8 watts RMS 8 Ohms. 2 Speaker System 5 1/2" x 10 1/2" x 7 1/2"	£9 11 0	£8 0 0
TELETON SA.1003 Speakers 5 watts RMS 8 Ohms. 1 Speaker System 6" x 9" x 5" (Rec. for use with F.2000)	£5 0 0	£4 8 3
WHARFEDALE Denton	£16 6 0	£13 18 0
WHARFEDALE Super Linton	£20 13 0	£17 10 0
WHARFEDALE Melton	£29 10 0	£25 0 0
WHARFEDALE New Dovedale 3	£39 10 0	£32 19 6

B & O Speakers also available at discount prices

TURNTABLES

GARRARD SP.25, Mark II	£15 6 4	£11 10 0
GARRARD AP.75	£23 8 1	£18 19 6
GARRARD SL.55	£13 10 11	£11 12 6
GARRARD SL.65	£17 19 4	£15 5 0
GARRARD SL.75	£34 4 11	£29 10 0
GARRARD 3000	£11 4 1	£9 10 0
GARRARD 3500	£11 18 10	£10 1 10
GOLDRING Lenco GL.68	£22 7 2	£17 19 11
GOLDRING Lenco GL.75	£35 15 5	£28 15 5
GOLDRING 75P	£46 18 8	£38 0 0

THORENS TD.150	£25 16 11	£25 7 0
THORENS TD.150B	£32 17 6	£28 18 0
THORENS TD.150AB	£39 1 7	£33 19 6
THORENS TD.124/11	£45 18 1	£40 7 0

Bases, plinths and covers stocked to suit all the above turntables.

HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

AKAI X-150D deck 4 track	£130 2 4	£109 0 0
AKAI X-300 2 track	£263 0 0	£220 0 0
AKAI X-300 4 track	£263 0 0	£220 0 0
AKAI X-360 4 track	£339 0 0	£284 0 0
AKAI X-360D deck 4 track	£290 0 0	£243 0 0
AKAI 1710 4 track w/o acc.	£109 0 0	£91 0 0
AKAI 1800 4 track	£158 0 0	£133 0 0
AKAI 1800SD 4 track	£199 0 0	£167 0 0
AKAI 3000D deck 4 track	£99 10 0	£83 6 0
AKAI X-V 4 track	£180 0 0	£151 0 0
AKAI M-9 4 track w/o acc.	£195 0 0	£156 0 0
FIDELITY HF Playmaster 2 track	£26 15 6	£19 19 6
FIDELITY Braemar 2 track	£30 9 0	£24 17 5
FIDELITY Braemar 4 track	£33 12 0	£27 8 11
MARCONI 4214 twin-track Tape Recorder	£35 16 0	£31 0 0
MARCONI 4216 4-track Tape Recorder	£41 5 0	£35 19 6
MARCONI 4218 Stereo Tape Recorder	£88 0 0	£77 19 6
MARCONI 4238 4 track Tape Recorder	£58 11 0	£49 19 6
PHILIPS battery operated tape recorder Model 4200	£35 6 0	£21 19 6
SHARP 504 battery/mains tape recorder, complete with all accessories	£35 5 3	£24 19 6
SHARP RD.707 Stereo Tape Recorder	£96 12 0	£81 0 0

RECORD PLAYERS, 'GRAMS, RADIO AND TV

Bush VTR 133 VHF Radio	£31 9 0	£24 19 6
Fidelity RG33 Radiogram	£64 11 6	£54 11 6
Fidelity HF 35 Record Player with auto change and tone control	£17 6 6	£12 19 6
Fidelity HF 36 Record Player (Stereo)	£55 11 0	£44 2 6
Fidelity HF 37 Record Player	£30 9 0	£25 19 6
Hitachi Transistor Radio, long, medium and short bands, with extra marine band and RDF	£30 9 0	£18 19 6
Hitachi VHF Transistor Radio	£21 0 0	£12 19 6
Philips 265 Radio	£10 13 1	£7 19 6

CAR RADIOS

Philips Car Radio, Model 240T	£13 9 9	£11 19 6
Philips Car Radio, Model 268 (push-button)	£18 10 0	£15 19 6
Philips Car Radio, Model RM 368, push-button deluxe	£22 15 0	£20 19 6
Philips Car Radio and Cassette Tape Player, Model RN 582	£43 0 0	£38 19 6

TV AT DISCOUNT PRICES

Ferguson 19" TV (latest model)	£75 2 0	£59 19 6
G.E.C. 2039 23" TV (latest model)	£83 8 1	£69 8 0
G.E.C. 19" Colour TV	£276 18 9	£219 10 0
Philips 25" Colour TV	£347 19 7	£265 14 6

Most Makes of HF Stereo Tape Decks and Tape Recorders at Discount Prices.

Comet Discount Warehouse
Reservoir Road, Clough Road, Hull. Tel. 42363

DELIVERY. Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.
Add 9/- for post and packing on all orders.

FANTASTIC SCHAUB-LORENZ MUSIC CENTRE

**MODEL
5001**

**VALUE
£200!**



COMBINED 4 WAVEBAND RADIO & 126 TRACK TAPE RECORDER

GIVING 46 HOURS OF RECORDING TIME

**OUR
PRICE 89 GNS. CARR. &
PKG. 50%**

An amazing piece of equipment combining a 4-band radio and a 126 track tape recorder in one modern compact unit 31 x 13 x 11in. The recorder section gives 46 hours of continuous unrepeatable playing time—fantastic but true—46 hours of music can be yours at the touch of a switch. Brief specification: Incorporates 27 transistors and 15 diodes. Four wavebands VHF/MW/LW/SW, with exclusive "Auton Control" to give precise station tuning. Separate Bass and Treble controls. A wide magnetic tape records 126 tracks of 22 minutes each. Every track is able to record/replay so that you need not touch the machine for the total 46 hours record/replay time. Rewind time for each 22 minutes track only 25 seconds. Tape speed 10.5cm/sec. Inputs for direct recording from microphone and record player. Pause control fitted. 10 watts quality output. Built-in 10in. speaker and tweeter. Sockets for extension speakers. Beautifully housed in wooden cabinet. Complete with switched audio input adaptor for mike and gram. Brand New in Maker's Carton.

OBTAINABLE
ONLY FROM

LODGE TRADING CO.
21 Lodge Lane, North Finchley, London, N.12.

TEL: 01-445 0749 (AFTER HOURS DEMONSTRATIONS AND SALES 01-445 2825).
PERSONAL CALLERS WELCOME—9 a.m. to 6 p.m. (Sats. 9 a.m. to 4 p.m.)

BI-PRE-PAK LTD

442-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0702) 46344

RETURN OF THE UNBEATABLE P.1. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P.1 PLEASE ASK FOR PAK P.1. ONLY 10/-
2/- P & P on this Pak.

Pak No.	NEW, UNMARKED, UNTESTED PAKS	
B78	12 Integrated circuits, Mixed types, data supplied with orders.	10/-
B80	8 Dual Transistors, Sil NPN Matched output pairs.	10/-
B82	10 OC45-OC81D-OC81 Transistors, Mullard glass types.	10/-
B83	200 Trans. Newmarket reject and other types NPN and PNP.	10/-
B84	100 Silicon diodes DO-7 Case, OA200 -OA202 Polarity marked.	10/-

	NEW, TESTED AND MARKED PAKS	
B79	4 1N4007 Silicon Diodes, 1000 P.I.V. 1 Amp Min. Type.	10/-
B81	10 Reed switches Min. type with Coils and Magnets.	10/-
B85	24 Integrated circuits on panels, data of types sup. with orders.	10/-

Transistors	Price
AC126	2/6
AC127	2/6
AC176	5/-
AD149	10/-
ASY29	5/-
BC107-8-9	4/6
BC171	3/-
BC172	3/-
BC173	3/-
OC22	6/-
OC23	6/-
OC25	7/6
OC26	5/-
OC28	10/-
OC35	5/-
OC44	2/6
OC45	2/6
OC71	2/6
OC83	4/-
OC139	2/6
OC140	3/6
OC201	8/-
OCPT1	10/-
SC108	3/6
SC109	3/6
2N4284	3/6
2N4285	3/6
2N4286	3/6
2N4287	3/6
2N4288	3/6
2N4289	3/6
2N4290	3/6
2N4292	3/6
2N3055	15/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE lists and catalogue of all our products. Check your own equivalent with our free substitution chart.

Matched Set. NPN/ PNP AD161-AD162 Comp. pair Pak B.77.	10/- PR.	Complementary Set. NPN/PNP Germ. trans. Pak F.3	2/6 PR.
--	-----------------	---	----------------

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/-.
CASH WITH ORDER PLEASE, add 1/- post and packing.
OVERSEAS ADD EXTRA FOR AIRMAIL

Fabulous Value

STEREOPHONIC KUBA "ROYAL" RADIOGRAM
This radiogram chassis is offered complete with carefully matched loudspeaker system, two 10in. speakers, two 4in. Cone Tweeters and latest BSR UA70 Mono/Stereo record changer—a complete quality stereophonic radiogram at half normal price.
4 wavebands—AM/FM—8 piano keys control. 8 watt push-pull output per channel—frequency response 30-20,000 cycles. EASY TO INSTALL. NO TECHNICAL KNOWLEDGE REQUIRED
ONLY £79.19.6.
H.P. terms available.
Deposit £26.13.2 and 24 monthly payments of 55/7 (total H.P. £93.7.2). Send £27.10.8 today or write for free leaflet.

Fantastic Bargain Offer

KUBA "IMPERIAL 666" STEREOHONIC HI-FI RADIOGRAM CHASSIS—complete with two 10in. x 6in. speakers and the latest BSR Mono/Stereo record changer—a complete AM/FM chassis with the very latest printed circuitry—7 push button control, 12 watts total output. Provision for stereo decoder. Only 493 Gns. plus P. & P. 17/6. EASILY FITTED. NO TECHNICAL KNOWLEDGE NECESSARY. H.P. available £17.6.6 deposit plus 24 monthly payments 36/2 (total H.P. £60.14.0). Send £18.4.0 today.

CALLERS WELCOME

**POST
THIS
COUPON
NOW!**

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name
Address

LEWIS radio

100 CHASE SIDE, SOUTHEGATE,
Dept. P769A, LONDON, N.14
TELEPHONE 01-886 3738/9666

voltage ratings and contact current and voltage ratings. The coil resistance is also included especially for low voltage coils intended for transistor circuits. Standard coil voltages are 6, 12, and 24V d.c. with coil resistances of 100 Ω –1000 Ω . A.C. operated coils are usually for 115, 240, and 440V r.m.s. circuits. Coil power is generally 1W–5W for most electronic relays but is considerably more for power relays and contactors.

Coils are normally rated for continuous operation and for this reason a maximum coil voltage is stated together with a minimum coil voltage for the just-operate condition. It is preferable to operate relays at their rated voltages since the mechanical characteristics are designed for these conditions. Working at low voltages gives low speed switching and increases the danger of arcing or welding of the contacts. High voltage working decreases the reliability of the coil whilst the mechanical shock of the contacts through faster switching causes switch bounce and vibration and a consequent reduction in mechanical life.

Contact ratings are often ambiguous since commonly they are rated for maximum voltage and current. Whilst these are true for the steady state closed or open conditions, they do not apply to the transient opening and closing periods during which arcing may occur. The transient condition is usually limited by the power rating of the contacts which is considerably lower than the value indicated by the maximum voltage and current ratings. Thus contacts with maximum ratings of 250V a.c. and 3A a.c. steady state ratings usually have a power rating of 200VA or 80W.

Relays are inherently unreliable components since they have a definite mechanical life. However due to the use of modern materials the reliability has increased and a life of 10^6 – 10^8 operations is often quoted. Reliability is very high for relays employed in low power switching applications but falls with high power levels.

Relays are common circuit elements particularly in control circuits and they are consequently readily available. Average prices for the smaller devices used in electronic circuits vary from 15s. to £5 depending on quality and standardisation. It should be remembered that the cheaper relays unless bulk produced are of poorer quality and as a result tend to be less reliable. With relays the familiar quotation "You get what you pay for" is particularly true.

Reed relays

Reed relays are essentially a development of the relay to increase the reliability and speed of operation. The reed consists of two leads of sprung magnetic material encapsulated in a glass envelope as shown in Fig. 4. The leads have contact faces, usually of diffused gold, which are brought together by the action of an external magnetic field. The reed therefore is simply an encapsulated contact, and the contact operation is illustrated in Fig. 5.

Reed switches can be purchased as contacts for use with permanent or electromagnet systems. For example reeds are commonly employed for proximity applica-



Fig. 4: Reed relay contacts.

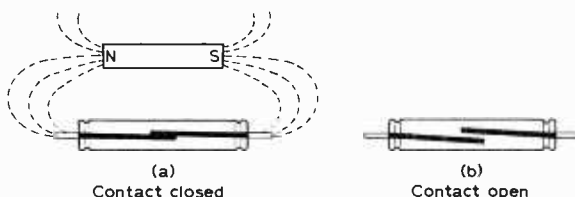


Fig. 5: Reed relay operation.

tions in conjunction with permanent magnets. Generally however they are used in conjunction with separate coils which are for printed circuit mounting or in complete encapsulations. One or more coils are employed to switch the relay and by changing the coil polarities logic functions can be achieved. One or more reeds are employed and changeover configurations are available. Thus a complex system of reeds and coils can be built up.

The design of reed relay assemblies is easily achieved since reed parameters always quote the minimum or just-operate ampere-turns (AT) required to switch the contacts. Average values of AT are from 20–50 for small reeds 1.5in. long to 70–150AT for 3in. power reeds. Thus a 100AT reed requires a coil of 100mA current and 1,000 turns to just operate the switch. Wound coils on printed circuit bobbins are also available suitable for 12V circuits and have resistance values from 500 Ω to 2k Ω .

Reed contacts are rated for maximum current and voltage but the maximum power for reliable operation is considerably lower than conventional relays. Typical maximum power ratings are 3–10W for small reeds and 10–20W for the larger types. Again, operation well below the rated power level gives a considerable increase in life expectancy. Generally breakdown voltages are in excess of 400V and the maximum current ratings are 0.25–1A.

The principal advantages of reed relays are their long switching life of 10^8 operations and the speed of switching. Typical turn-on time is from 1–2msecs with turn-off times of the same order. Reed switches can therefore be used for switching at up to 2kHz rates. Another important advantage, particularly in logic circuits, is the lack of switch bounce.

Reeds and relay assemblies are now readily available. Individual reeds vary in price from 4s. to £1 whilst coil assemblies vary in price from 6s. to £1. Complete encapsulations including a magnetic shield range from £1 to £4.

Mercury wetted relays

Mercury wetted relays are designed for extremely reliable systems where the characteristics of high speed switching and lack of switch bounce are required. Lifetimes in excess of 10^9 – 10^{10} operations can be achieved and this is due to the construction which continually "wets" the contact surfaces with mercury by capillary action. These devices are available for operation between 6V and 50V supply voltages and cost from £3 to £5. A disadvantage results from the limitations in mounting, since for the capillary action to operate they must be mounted vertically.

Meters

Meters are devices which convert electrical power into a mechanical force which is counterbalanced by a

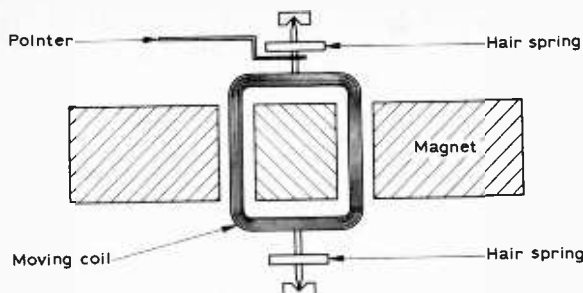


Fig. 6: Basic moving-coil meter construction.

spring movement. The physical movement of the coil is used to give an indication on a dial. As moving-coil meters are by far the most widely used type only these will be considered here.

Figure 6 illustrates the essential components of a moving-coil meter. A coil is suspended in a strong magnetic field produced by a permanent magnet. The bearings are often jewelled and movement of the coil is prevented by a coil spring. When the coil is energised by a direct current flowing through it, a rotational force is exerted on the coil due to the interaction of the permanent and electromagnetic fields. This force is opposed by the torque characteristics of the spring and in consequence the accuracy of reading depends upon the linearity of the force-displacement characteristics of the spring. As springs generally have a linear relationship between force and displacement moving-coil meters have a linear scale reading. It can be seen therefore that moving-coil meters are direct current meters since it is direct current which is linearly related to the mechanical force exerted upon the spring.

The ideal moving-coil meter should have an absolute linearity between coil current and scale reading and the range of current measured should be as large as possible. Also the time taken for the meter to arrive at a stable reading should be a minimum. In order to achieve the ideal meter the suspension system of the coil would have to be frictionless and the permanent magnetic field should be uniform and radial. The reading accuracy and range of an instrument are largely determined by the physical size of the scale over which the pointer moves. This is physically limited by the size of the meter and the pivot and suspension system. But in any event as the scale is linear, accuracy at the low end of the scale is essentially less than at the top end.

The speed in which a reading is obtained is also important especially since a force instantly applied to a coil inherently results in an oscillation of the spring

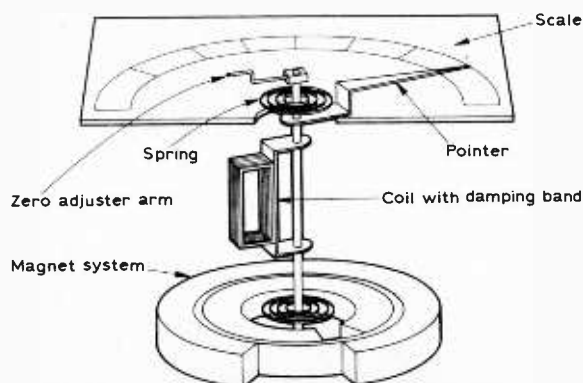


Fig. 7: Exploded view of moving-coil meter.

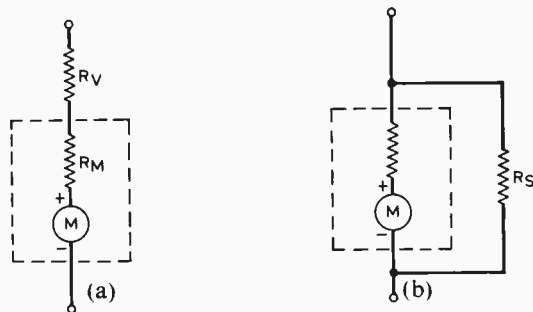


Fig. 8: Meter modifications to measure (a) d.c. voltage and (b) direct current.

system. Thus practical meters have damping systems which are designed to give critical damping. This is an oscillatory condition in which stability is achieved in a minimum time. If the movement is overdamped then the pointer moves slowly and creeps up to the final reading, whilst underdamping results in the pointer swinging about the final reading.

Most of these limitations have been reduced to minute proportions by the practical meter design shown in the exploded view of Fig. 7. The magnet has a strong radial field and is generally of Al Ni Co, whilst the spring and coil system is light with little inertia or friction. Damping is by air vanes, magnet systems or oil dash-pots. Scales are physically limited in size and 2 to 5in. is general but 10 to 20in. can be achieved. To improve reading accuracy mirrored scales are used. However the basic limitation due to linearity remains, and a reading accuracy of 1% of the full scale value is only possible with high quality meters.

All moving-coil meters are basically direct current operated and the current required by the coil to give full-scale deflection varies, from 10μA to 10mA for average meters. Most however are within the range 50μA to 1mA. This basic current determines the quality of the meter since moving-coil meters can be used for the measurement of most electrical quantities providing a direct current in the above range is present. By using resistors as shown in Fig. 8 the meter can be used to measure d.c. voltage and current, whilst the addition of a rectifier enables the meter to read a.c. voltage and with a transformer alternating current.

The resistors R_v and R_s for d.c. measurements can be calculated from the following formulae:

$$R_v = \frac{V_{d.c.}}{I_m} - R_m$$

where $V_{d.c.}$ is the full scale voltage reading in volts,
 I_m the basic meter current in amps and
 R_m the meter coil resistance.

$$R_s = \frac{I_m R_m}{(I_{d.c.} - I_m)}$$

where $I_{d.c.}$ is the full-scale current reading in amperes.

The quality of a meter is dependent upon the current for full-scale deflection and the figure of merit quoted on most universal meters is derived from the series resistance required to measure d.c. volts; and is stated in ohms/volt. Thus from the formula a 50μA meter requires $1/50 \times 10^{-6}$ or 20,000Ω/V total series resistance, whilst a 1mA meter requires $1/1 \times 10^{-3}$ or 1,000Ω/V series resistance. Inherent meter resistance (R_m) reduces with figure of merit and is of the order of 100Ω for 1mA meters to 1kΩ for 50μA meters.

TO BE CONTINUED

POWERITE UNIVERSAL BATTERY ELIMINATORS AND STABILISED POWER PACKS

The most economical method of running transistorised equipment from A.C. mains. Power radios, record players, etc. Mark 1 model: replaces all 9 volt batteries. Price only 35/-, p. & p. 5/- Mark 2 model: output 6, 7, and 9 V. STABILISED, making it ideal for running Hi-Fi and test gear and cassette tape recorders. Price only 55/-, p. & p. 5/-

SURPLUS BARGAINS HEAVY DUTY ACCUMULATORS

Type 1 (6 volt) 40AH. In metal cabinet. Size approx. 10 x 8 x 6 in. Complete with output socket, carrying strap. Brand new and unused. Worth £10 each. Our Price 55/-, carriage and insurance 15/-
Type 2 (6 volt) 16AH. In sturdy wooden cabinet with carrying strap. Worth £7 each. Brand new and boxed, only 32/6 each, p. & p. 12/6
FIELD TELEPHONES
Type F. Housed in a portable wooden case. Ideal for indoor/outdoor communication up to 10 miles. Absolutely brand new. Price only £5.19.6 per pair carriage and insurance 15/-
19 Set Headphones and Mike. Not new but in working order. Only 7/6 per set, p. & p. 4/6
Tannoy Mikes. As new, 9/6 each, p. & p. 3/6 (heavy duty, ideal for F.A. work).
High Quality moving coil headphones and mike. Brand new, only 17/6, p. & p. 5/6. Suitable for most applications (cost approx. £3 per pair).

WE BUY ALL TYPES OF SCIENTIFIC & ELECTRONIC EQUIPMENT AND TEST GEAR

Please let us know what you have in single items or large quantities. Send S.A.E. We will send you an offer by return. Also required are all types of electric motors, Dynamotors, rotary converters. All optical equipment, lenses and prisms etc.

TRANSISTOR SALE


OC44 1/6 each, p.p. 4d. Three for 5/- post free.
OC72 1/6 each, p.p. 4d. Three for 5/- post free.
OC71 1/3 each, p.p. 4d. Three for 4/6 post free.
OC45 1/3 each, p.p. 4d. Three for 3/8 post free.
OC81 2/- each, p.p. 4d. Three for 5/- post free.
AC128 2/- each, p.p. 4d. Three for 5/- post free.
BBY 38a 3/6 each, p.p. 4d. Three for 10/- post free.
BC108/107 4/6 each, p.p. 4d. Three for 12/6 post free.
2N708 2/6 each, p.p. 4d. Three for 8/6 post free.
2N2926 2/- each, p.p. 4d. Three for 8/6 post free.
BBY27 300 m/c/s silicon 7/6 each, p.p. 4d. Three for £1 post free.

AIRCRAFT PLUS GENERAL V.H.F. TELECOMMUNICATIONS BAND REC.

Listen to the thrills of Aircraft Pilots and Airports at work. Also Civil Depts, Fire and Ambulance services. Gas and electricity depts. Ideal for receiving 2 meter amateurs. Gives super reception within the range of all transmissions. A fully transistorised receiver covering 97-147mc/s VHF broadcasts. Robust attractive 2-tone finish metal cabinet size approx. 7 x 4 x 4 in. Operates from a 9 volt internal battery. Speaker or earphone output plus chrome telescopic aerial. Only £8.19.6 carr. and insurance 10/6 C.W.O. or C.O.D.

HEAT LIGHT SPEED CONTROL Unit

An electronic unit capable of controlling electrical equipment up to 3000 WATTS. Full fingertip control of all AC & Universal apparatus. Gives full wave control from zero to full power. Suitable for the control of electric motors of up to 2 hp. Suitable for controlling all types of lighting. Makes an ideal dimmer unit with no loss of power. Will control up to 3 K.W. Heaters. Ideal for fine control of Lathes, Power Tools, Conveyor Belts, pumps etc. Contained in a robust metal cabinet, attractively designed, with matching control panel. Size approx. 6 x 5 x 2 in. New design makes possible full wave control. Not to be confused with earlier half wave thyristor unit. Now employs the latest electronic techniques. Ideal for all industrial applications. Price £9.19.6. Carriage and Insurance 10/-.

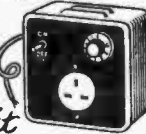

STANDARD DESK TELEPHONE

Fresh stocks have arrived at last. In a far superior condition to telephones advertised previously. Complete with Dial, Magneto, Cradle Bell etc. Also details on how to connect the telephones. Thousands already sold. Price 37/6 each. P.p. 7/6. Two phones £4 post free.



RUN YOUR 19 SET TX/RX FROM AC MAINS

We manufacture a brand new unit ready to operate all 19 set Trans/Rec. direct from the mains. Complete ready to plug in with full connecting instructions. Contained in an attractive steel cabinet. Price £8.10.0, carr. & insur. 10/- Receiver version only. £4.10.0, carr. & insur. 5/-

NEW SHOP NOW OPEN at

38 Bridge End, Meadow Lane, Leeds 1
Open 9 a.m. to 6 p.m. weekdays and Saturdays. All goods advertised available for inspection and demonstration. The North's newest walk-round Scientific and Electronic Store.

PRECISION PANEL METERS

Brand new, boxed and fully guaranteed. With fixing nuts and bolts. Size approx. 3 1/2 in. square. 0-500 volts FSD. As used by leading laboratories. Ex-stock, only 30/-, p. & p. 5/- Two for 55/- post free.

HEAVY DUTY POWER SUPPLY UNITS

Bulk Purchase. Famous manufacturer. Must have cost nearly £40 each. Input 200/250 volts 50c/s a.c. Output 250 volts d.c. at approx. 175 m.a. 6.3/12 volts at approx. 4 amps a.c. Robust metal rack mounting cabinet, size approx. 19 x 15 x 5 in. Price only 85/- carriage and insurance 15/- All units are fully fused and metered.

TANK AERIALS

Full interlocking copper plated rods. One foot sections. Ideal for car or scooter aerials. Will make excellent dipoles, 81x sections for only 4/6, p. & p. 1/6. 12 sections for 10/- post free.

TOP PRICE PAID FOR COMMUNICATION EQUIPMENT RECEIVERS TRANSMITTERS WALKIE-TALKIES EX-GOVT AND COMMERCIAL

What have you for sale in this line. Anything considered. Send S.A.E. with details. We will send you an offer by return.

COMMUNICATION RECEIVER TYPE T.R.G.D.X.20.C.

Brand new fully transistorised and fully portable Communications Receiver. Specifications: 4 complete ranges 550 K/c/s. to 30 M/c/s, covering all amateur bands, shipping and trawler bands, and broadcast band. A highly efficient double tuned superhet, comprising R/F aerial tuning section. A.V.C. and built in B.F.O. Ideal for fixed or mobile reception. With speaker and headphone output. 2-tone crackle finished robust steel case of pleasing modern design. Size approx. 9 x 7 x 6 in. British manufacture. Due to bulk purchasing we can offer these excellent receivers at less than half their normal worth. Complete with handbook, £16.10.0, carriage and insurance 15/- Headphones if required 17/6 extra, 2/6 p. & p.

MORSE PRACTICE OSCILLATOR SET

Complete with "Hints on Learning Morse" manual. Fully Transistorised, 19/6, p. & p. 3/6.

TRANSFORMER BARGAINS

Absolutely Fully Guaranteed. Interleaved and impregnated. Input 200-250 volts 50 c/s.

UPRIGHT MOUNTING (fully shrouded)
Type 1. 250-0-250 60 m.a. 6.3 v at 2 amps. 0-5-6.3 volts 2A. 21/-

Type 2. 250-0-250 v 100 m.a. 6.3v 4a 0-5-6.3v at 4a. 35/-

Type 3. 300-0-300v at 140 m.a. 6.3v 4a. c.t. 6.3v 1a. 45/-

Type 4. 350-0-350 at 150 m.a. 6.3v 4a. 0-5-6.3v at 4a. 48/6

Type 5. 420-0-425 at 220 m.a. 6.3v 4a. 0-5-6.3v at 4amps. 72/6

Type 6. 450-0-450v at 250ma. 6.3v at 4a c.t. 5v at 4a. 85/-

Postage, packing and insurance 5/- on each.

Filement and Transistor Power Pack types. 6.3v 1.5a 7/6. 6.3v 2a 8/6. 6.3v at 3 amp 10/6. 6.3v at 6a 19/11. 12v 1a 8/6. 12v 3 amp 19/11. Postage and Packing and insurance 2/6 on each.

CHARGER TRANSFORMERS
0-9-15 volts 1 1/2 amps, 12/6; 3 amps, 17/6; 5 amps, 24/-; 6 amps, 28/-; 8 amps, 32/6. Postage and packing 3/6 on each.

AUTO TRANSFORMERS (STEP UP/DOWN TYPES)
0/110/250v. 200-230 250v 50-100 watts 15/- 150 watts 27/6. 250 watts 47/6. 500 watts 95/-. Postage and packing 5/- on each.

Khord Hi-Fi Solid State Amplifier

10 watts continuous output. 15 watts Music. Output to 3-16 ohms impedance. Freq. Response +2dB 20-20000 c.p.s. Distortion at full power < 0.15% Complete with pre-amp main amp and power unit all self contained. 5 position selector switch for all types of input. Mains input 200/250 volts 50 c/s. Attractively housed in a compact metal cabinet size approx. 9in. x 6in. x 5in. Distinguished control panel. Full tape monitoring facilities. Supplied factory built with full 12 months guarantee. Only 12 1/2 gns. Carr. 7/6

TOP BAND SPECIAL

These well made superbet Radios were made for the Govt. by a well known manufacturer. Valve line up: 6K8, 6K7, 6Q7, and 6V6. Freq. coverage brings in Top Band Amateurs, Marine, Aircraft, etc. Slow motion tuning. Built Power pack for 6 volt operation but easily converted for mains use. Contained in a robust cabinet with a built-in high quality loudspeaker. Few only as new. Price £4.19.6, carr. & insurance 10/6.

MATCHING P.S.U. For R1132 and 1392 Receivers. Only £3.10.0 each, carriage 10/- Absolutely brand new in maker's cartons.

AIR/SEA TRANS/REC. RESCUE

Compact VHF Trans/Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over £50 each. Regulations state must not be operated in UK so please mention "For Dismantling purposes only" when ordering. Price £2.10.0 each, p. & p. 10/- Two sets for £3.5.0, post free. Four sets £8. carriage free. Bulk sale of 10 sets £15, carriage £1. Export enquiries invited.



HT/LT BATTERY ELIMINATOR. All dry battery eliminator size 6 x 4 x 2 in. Replaces all batteries at 1.5v. and 90v. Price 65/-, p. & p. 5/-
SPECIAL HT/LT for running Surplus Radio equipment. Output 150v. and 3v. Will run the 38 set, 48 set and lots of others. Price 69/6, p. & p. 5/-

FANTASTIC MINI-KHORD INTEGRATED AMPLIFIER. A general purpose 6 watt transistorised amplifier. Freq. response 30-20,000 c/s. Independent bass and treble controls. Input for Mic., Gram. and Tape. 3-15 ohms output. Size 10 x 3 x 5 in. Attractive fascia. Price built up and tested with 12 months guarantee £7.19.6, carr. & insa. 10/6.

MINIATURE TRANSLATORISED B.F.O. UNIT. This is a miniature transistorised B.F.O. unit (tunable) that will enable your set to receive C.W. or S.S.B. reception. Compact. Single hole anywhere. Ideal for all Ex-Govt. Communication Receivers and most Commercial Types. Complete with fitting instructions. 49/6, post free.

MINIATURE MOVING COIL SPEAKERS. 1 1/2 in. dia. Only 3/6 each, p. & p. 1/6. Two for 8/6 post free. 4 for 15/- post free.

19 SET CONTROL BOXES Brand new and boxed 10/-, p. & p. 5/- Two for 27/6 post free. If purchased with 19 set phones and mike, deduct 5/- from total.

12 VOLT HEAVY DUTY DPDT RELAYS. High current double pole contacts plus auxiliary low current contacts 12 or 24 volt operation. Up to 20 amp handling capacity. Worth nearly £3. Make ideal aerial changeover units, car, or house burglar alarms, switching relays. Size only 3 x 2 x 2 in. Price 17/6 each, p. & p. 2/6. 2 for 30/- post free.

RECTIFIER SALE 6 1/2 volt full wave bridge. 4 amps. Brand new manufacturers surplus only 4/6 each, p. & p. 1/6. 2 for 10/- post free.

GLOBE SCIENTIFIC LTD Mail orders only to DEPT. P.W. 24 CAWOODS YARD, MARSH LANE, LEEDS 9

M. & B. RADIO

15a HUNSLET ROAD, LEEDS LS10 1JQ
Telephone: 0532-35649

R210 RECEIVER. Modern 14 miniature valve receiver. 2-16Mc/s in 7 bands each 50in. film strip scale. 10/100Kc/s xtal calibrator. BFO. CW filter. Internal 24V psu. Supplied c/w handbook and home-made mains psu. £30, carr. 25/-.

VHF MOBILE TX/RX. Miniature valve trans-receiver with 12V transistor power unit. Double conversion receiver. Xtal controlled but easily converted to tuneable. High or low band models (2 or 4 metres). Please state which when ordering. Positive or negative earth. Supplied c/w circuit and notes. TESTED £9.10.0, carr. 27/6.

TRANSISTORISED 2-METRE CONVERTERS. 2 RF stages. Various IF frequencies. Please state preference when ordering. £7.15.8, plus 5/- pp.

12 VOLT TRANSISTOR INVERTERS. Gives 240V DC at 40 watts. Ideal for caravan fluorescent lighting. £6, plus 7/6 pp.

Various other transistor inverters. Please send SAE for details.

Radiotelephone press to talk microphones. Used. 5/-, plus 2/- pp.

Spring loaded mobile whip base sections. Chrome finish. Brand new. 6/6, plus 1/6 pp.

GRANADA 4. Transistor amps in cabinet with speaker. Tested. 62/6, plus 7/6 pp.

GPO Telephones with dial. 17/6, plus 6/- pp. Modern style telephone 42/6, plus 6/- pp.

QQV03/10 6/- tested. **QQV06/40A** 37/6 tested. 800piv 16 amps silicon diodes on heat sink, 6/-.


BY128 2/6. 2 x OC35s on heat sink, 10/-.

STETHOSCOPE HEADSETS. Brand new. Ideal for stereo or mono. Low imp. 27/6, plus 3/6 pp.

2-METRE TRANSISTOR P.A. £7.10.0. Transistor amplifiers, modulators, mic pre-amps. VHF transmitters. Scopes. Aerials. Valves. Etc.

LISTS 6d, plus SAE.

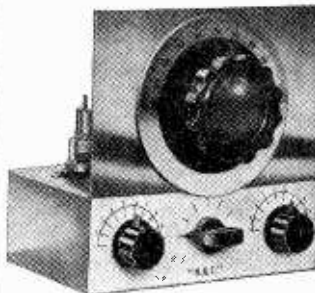H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1969 RANGE

One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1969 List now
available at 2/-
plus postage

If list is required
indicate with X

From
Address

enclose remittance of.....
(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (July PW)

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For DC45)	P50/1AC (For AF117)	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	5/7
2nd I.F. Transformer	P50/2CC (For DC45)	P51/2 (For AF117)	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	6/-

Rod Aerial	RA2W	12/6
Driver Transformer	LFDT4/1	9/6
Output Transformer	OPT1	10/6
Printed Circuit	PCA1	9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

THE days seem to fly by and we are now in the summer season here in the Northern Hemisphere. With summer conditions the best DX is found during night hours and early morning. So set your alarm clocks for 0400 and you may get some good DX on 11, 9, 7, 6, 5, 4 and 3MHz. But during the day you'll find 25, 21, 17, 15 and 11MHz swamped by *R. Liberty*, *R. Free Europe* plus the whole Russian and Iron Curtain jamming network working overtime, together with *R. Moscow*, *The Voice of America* and all the high power stations. So sleep at day and DX at night. Now on to the propagation predictions for the summer months.

West Africa: 0800-1600 21, 17 and 15MHz; 1600-1800 21, 17, 15 and 11MHz; 1800-2000 21, 17, 15, 11, 9, 7 and 6MHz; 2000-2200 17, 15, 11, 9, 7, 6, 5, 4 and 3MHz; 2200-0200 15, 11, 9, 7, 6, 5 and 4MHz; 0200-0400 11, 9, 7, 6, 5, 4 and 3MHz; 0400-0600 15, 11, 9, 7, 6, 5 and 4MHz; 0600-0800 17, 15, 11 and 9MHz.

South Africa: 0800-1600 21 and 17MHz; 1600-1800 21, 17 and 15MHz; 1800-2000 21, 17, 15, 11, 9 and 7MHz; 2000-2200 17, 15, 11, 9, 7, 6, 5 and 4MHz; 2200-2400 15, 11, 9, 7, 6 and 5MHz; 2400-0200 11, 9, 7, 6 and 5MHz; 0200-0400 9, 7, 6 and 5MHz; 0400-0600 11, 9 and 7MHz; 0600-0800 21, 17 and 15 MHz.

East Africa: 0600-1600 21, 17 and 15MHz; 1600-1800 21, 17, 15, 11 and 9MHz; 1800-2000 17, 15, 11, 9, 7 and 6MHz; 2000-2200 15, 11, 9, 7, 6, 5 and 4MHz; 2200-2400 11, 9, 7, 6 and 5MHz; 2400-0200 11, 9, 7 and 6MHz; 0200-0400 11, 9 and 7MHz; 0400-0600 17, 15, 11 and 9MHz.

South Asia: 0600-1400 17 and 15MHz; 1400-1600 17, 15 and 11MHz; 1600-1800 17, 15, 11, 9 and 7MHz; 1800-2000 15, 11, 9, 7, 6, 5 and 4MHz; 2000-2200 15, 11, 9, 7, 6, 5, 4, and 3MHz; 2200-2400 11, 9, 7, 6, 5 and 4MHz; 2400-0200 11, 9, 7 and 6MHz; 0200-0400 11 and 9MHz; 0400-0600 15 and 11MHz.

South East Asia: 0600-1200 17MHz only; 1200-1400 15MHz only; 1400-1600 17, 15 and 11MHz; 1600-1800 17, 15, 11 and 9MHz; 1800-2000 15, 11, 9, 7, 6 and 5MHz; 2000-2200 11, 9, 7, 6 and 5MHz; 2200-2400 11 and 9MHz; 2400-0400 11MHz only; 0400-0600 15MHz only.

East Australia via Asia: This circuit is rather unpredictable in results, the official forecast reads as follows: 1600-1800 on 11MHz only; 1800-2000 9MHz only; 2000-2200 11 and 9MHz; 2200-2400 15 and 11 MHz. But signals have been logged via this route round about 0700 on 21MHz and 0900 on 15MHz.

West Coast South America (South of Peru): 1200-1800 17MHz only; 1800-2000 21, 17 and 15MHz; 2000-2200 21, 17, 15 and 11 MHz; 2200-2400 17, 15, 11 and 9MHz; 2400-0200 15, 11, 9, 6, 5 and 4MHz; 0200-0400 11, 9, 6, 5, 4 and 3MHz; 0400-0600 11, 9, 6 and 5MHz; 0600-0800 9MHz only.

Those were the propagation predictions as supplied by Cable and Wireless, London.

Times • Frequencies
in GMT • in kHz

THE BROADCAST BANDS

Christopher Danpure

The other day I received a very nice letter from Mr. P. J. McNamara concerning a new Shortwave Listeners' Club which has just opened. The name of the club is the "Limerick City Short Wave Radio Club". They publish a very well produced monthly bulletin which as well as giving DX tips also has tips on such things as how to report correctly to a station for a QSL card. The cost to receive the club bulletin for 1 year is 7s. 6d. and membership is open to all SWL's anywhere in the world. The address to write to for further information is Limerick City Short Wave Radio Club, 7 Colbert Park, Janesboro, Limerick City, Ireland.

Now on to this month's DX and SWL's tips.

ASIA

North Vietnam: *R. Hanoi* has been heard closing at 1700 on 15,018 in Vietnamese irregularly. This station does QSL and sends out schedules and information about N. Vietnam, I believe, and according to loggings this station is not using directional aerials for this frequency.

AFRICA

Ghana: External Services, *R. Ghana*, Accra is now beaming its English service to Europe from 2045-2215 on 15,285 according to Limerick City S.W. Club Bulletin.

Liberia: *R. Station ELWA* has been heard closing at 2200 in English on new frequency of 9,760 according to Limerick City S.W. Club Bulletin.

NORTH AMERICA

USA: *R. Station WNYW* is now on the following schedule. To Europe from 1600-1830 on 21,525; 1600-1820 on 15,440; 1830-2130 on 17,760; 1900-2140 on 15,440. To Africa from 1600-1850 on 21,580; 1850-2140 on 21,525. To Caribbean and the Americas 1600-2145 on 17,845; 2140-2145 on 21,525, 15,215 and 15,130; 2145-2150 21,525, 17,760, 15,215 and 15,130; 2150-0020 on 21,525, 17,835, 17,760, 15,215 and 15,130. Many thanks for this tip to Mr. C. M. Pearson in Epsom, Surrey. A good fresh item.

EUROPE

Switzerland: The Swiss Shortwave Service, Berne is now on the following schedule until September 7 for its English programmes. 0700-0800 (daily) on 11,775 and 9,590; 0700-0800 (weekdays only) on 9,535 and 6,165; 1000-1100 on 21,520, 17,795 and 15,305; 1130-1230 on 11,865 and 9,665; 1315-1415 on 21,520, 17,845 and 15,135; 1500-1600 on 17,830 and 15,305; 1815-1915 on 17,795 and 15,180; 1930-2030 on 11,865 and 9,665; 0130-0230 on 15,305, 11,715 and 9,535; finally 0445-0545 on 11,715 and 9,720. Well that's about it for this time. Deadline for all those DX-logs is May 20th. So until next time good listening and 73s.

EVEN those with a piece of wet string and a cat's whisker must have heard DX this month on the amateur bands. It was uncle David's month for draping the ageing eardrums around 10 metres, and cor, wasn't it lively up there? Must have been purgatory for the owners of beams, wondering which way to point the darned things for fear of missing something good in the other direction. Using just one vertical in the loft raised all five continents at the same time. The citizens band, too, was really humming with a collection of the most amazing call-signs and conversations you could think of. Incidentally, if "Big fat mumma" somewhere in Brooklyn reads this, you owe me thirty bob for a new front end and I strongly disagree with your remarks concerning women in the summer.

The other end of the spectrum didn't fare too well with me, but logs received indicate that the DX was there, so it must be me. Certainly one could log quite a large number of W stations in the 3-8 to 4MHz segment, but apart from this there didn't seem much about, discounting EUs.

Nigel Thornley (Northamptonshire), tells tales of a strange noise which blanketed 20 metres but no remarks from any other sleuths. (It's like that most evenings on 160 anyway). Only a very small number of logs for the l.f. bands but a large number cashed in on the 10 metre openings.

LOGS LOW

Successful ingredients for an r.f. topband cake coming up. Take one B40 receiver, 175ft. of wire and poke in the terminal marked "antenna". Oh yes, put the head of one **R. Moore** (Dorset) between the headphones and you get—GC3ULZ/P, GD3VMQ, GM3FXM, GW3WBU/P, OE3KIW, OK1TH, OK1VC, OK1KVW, OK2BFI, OK2PCN, OK3CJV, OK3YBE, OLIAGK, OL2AIO, OL5ALY, PAØCC, TA2E, ZB2AY. Most of these on c.w.

Rumours that a GM station has been known to "drop in" for a chat on the Verulam 160-metre club net. Cynics should QRX Saturday nights around 2230 BST on 1980 or thereabouts.

Christopher Lamb (Dorset) sends me hieroglyphics which turn out to be the best of his "heard on 80 metres" log—KP4S, K2ISM, K2VOE, VE1AFY, W1ABC, W2BGG, ZL2GJ, ZL4II, ZL4JW. Wish I could hieroglyph like that.

Bill Wright (Staffs) has an RG-1 and a 180ft. long wire. A fantastic log for 3.5MHz (that's the posh way to write 80 metres) all s.s.b.—CN8AW, CO2DC, CO2FA, CR4BB, EA8EX, EP2BQ, FG7XX, FG7TI/FS7 (French St. Martin), HI8OSA, K1THQ, K2BZT, K4JN, KP4AST, KZ5WH, MP4TAF, MP4TCU, OD5BA, PJ7JC, PY7ASQ, PY7GV, TF3BV, TI2ES, VE1OW, VE2AYA, VE3AGW, VO1FG, VP2AA, VP9L, W1AP, W2AC, W5LHO, W8GZ, W9BV, WA3LFN, XE1CE, XE3AF, YV1SA, YV3RP, YV4DN, YV5BPG, ZB2BS, ZC4GM, ZL4LM, 3AØCU, 4X4AS, 5A1TN, 5R8AO (Malagasy), 6Y5CC, 9E3USA, 9H1BL, 9Y4LP, 9Y4MM.

LOGS HIGH

Congrats to **Jim Baker** who now wears a shiny new badge engraved G3YHB. Jim is now working

them instead of just listening, although he confesses to a spot of TVI teething troubles. On 20, he managed—CR6TP, CT2AK, 4X4AS, 7X2AL, 9K2BV; while 15 brought—OD5CX, TJ1AI. All with a PCR3 and a Panda Explorer tx.

O. Shaw (Yorks.), AR88D, 180ft. end fed went s.s.b.-ing on 20 for—EA8RCS, HC1SJ, HS1HS, HKØPKS, HK7UL, HZ1AB, IS1LIO, KG6AKR, TF3AP.

D. Isaac (S. Wales) is 13 and has a homebrew (good lad) 4-valve (what are they?) superhet. Sixty feet of wire and 20 metres produced—CR61V, EL2E, FR7ZG, HI5PW, HK3VO, KH6AFN, KP4CL, VK2AO, VK3TG, VK5MQ, VK7AZ, VK3RX, VK2AO, VK3TG, VK5MQ, VK7AZ, VK7RX, VO1CX, ZL1AGO, ZL2RC, ZL3QN, ZP5JB, ZS5JY, 3AØCU, 4X4IX, 5Z4KO.

Robert Dinning (Ayrshire) sends a 15-metre log plus a photograph of himself and his station (he's got more hair than me!). The line-up is HA350 plus PR3OX plus RQ1OX and a 380ft. long long wire with a Z-match on the end. All s.s.b.—CR6GA, CR7BO, HR1WSG, JX1OM, KZ5BU, MP4TCE, OHØNI, PX1JQ, VK2FU, VK2FA, VQ9GA, ZC4HS, ZD5R, ZE5JU, 9J2GJ, 9M2DQ, W1—WØ, VE1—8.

TEN METRES

J. Moore (Leicestershire) reports great happenings on 10. The log to prove it reads—CR6CA, CR6IS, CR7IC, EP2JP, ET3REL, FG7XX, HK3VA, HK4AZX, HS3DR, JA1NVF, JA1OYT, JA2BVZ, JA3GFO, JA6BEE, K5CNZ/P/YV5, KR6EL, KR6JT, PY2EOQ, TL8GL, VK6KM, VK6NM, KR9BB (New Guinea territory), VS6AA, WA6GZZ/AM, ZS1JC, ZS4AA, 4X4CY, 5A1TA, 5N2AAF, 5N2ABG, 7Z3AB (Saudi Arabia), 9X5AA.

G. Lawlor (Ireland) R1155 plus RF24B, 10-metre dipole logged—CR6CA, EP2CF, ET3USA, FG7XT, HS3AL, MP4BHL, OA4OS, PY6WG, SVØWJJ, UH8UU, ZD8JW, ZS5KS, 5A3TX, 5Z4DW, 6W8DY, 7Q7WW, 9H1BN.

P. Cavill (Gloucestershire), CR45 plus 65ft. end fed eavesdropped on—CE7DW, CP5ED, CR6CA, EL2BE, HS3DR, KV4AD, OD5AP, PY7EC, SV1AL, VE5CK, W4NMK/MM, YV5CPA, ZD3D, 5A1TK, 5A3TX, 6W8DY, 9H1BG, 9J2DT which is pretty good for a t.r.f.

R. Pusey (London, N.2), KW201 and 20ft. whip at 30ft logged this bunch on s.s.b.—CE3RR, CR6CA, HK3VA, HS3DR, JA3JAZ, JA6DCE, KH6GRW/P, KV4AD, KZ5JW, TU2BC, VK4HR, VK6KN, VP2BQ, VP8KD, VQ8CG, VS6AD, VU2DK, VU2OLK, YBØAAC, 8P6AH, 9G1BS, 9J2RV.

NEWS

Happenings for the month of June include: June 5th—7th, special station from Edinburgh, call sign unknown; 7th—8th, National Field Day (start brushing up on your c.w. now); 22nd, 4-metre portable contest; 29th, Mobile rally at Longleat, near Warminster in Wilts; July 5th—6th, topband contest; 5th—6th, 2-metre contest; 6th, South Shields mobile rally.

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/8—twin stethoscope instead of earpiece 11/- extra—post and ins. 2/6.

MINIATURE

WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 8/6 each. 30/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

BATTERY CHARGER FOR NICADS

This is in plastic case, size 5 x 4 x 3in. approx. All wired up with 3 core output lead and 3 core mains input lead. Contains mains transformer with 40v. 250mA secondary and standard 200/240 primary. Also contains full wave bridge rectifier, neon indicator, wired up with resistors to charge 3 Nicad batteries simultaneously. Charge rates of 50mA and 25mA respectively. Batteries up to 30 volts may be charged. Price 39/8 each, plus 3/6 postage and insurance.

MAINS TRANSFORMER SNIP

Making a power pack for amplifier or other equipment? These transformers have normal mains primaries (230/40v.) and isolated secondaries two types (1) 12v. 500mA at 8/6; (2) 15v. 500mA at 8/6.



PP3 ELIMINATOR. Play your pocket radio from the mains! Save 6s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions, only 6/6 plus 1/- post.

WIDE ANGLE LENS FOR CLOSED CIRCUIT TV


16mm. Made by the Swiss company, Kern Paillard. Year 1:2.8 f=75mm. Brand new in leather case 33/6, which is less than half current list price.

TIMED SWITCH OR MEMORY JOGGER

If you are the forgetful type this can save you embarrassment. Pre-settable up to 13 hours, operated by clockwork motor so can be used in car or anywhere independently of the mains. Switch rated at 15A, 250V can control any type of alarm, 29/6d less than the current list price. Brand new and unused.

KETTLE ELEMENT

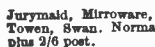350/240V 1500 watt. Made by Best for kettles with 1 1/2 in. dia. hole including: Best, Beco, Chalfont, Davidson, Dimble, Griffin, Hawkins, Jaymaid, Mirroware, Monogram, Plico, Revo, Town, Swan. Normally 32/6. Our price 15/- plus 2/6 post.



QUICK CUPPA

Mini Immersion Heater, 350w. 300/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 19/6, post and insurance 1/6. 12v. car model also available.



MAINS TRANSISTOR POWER PACK


Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP8, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

16 RPM GEARED MOTOR

Made by Smith's Electric, these are almost silent running, but are very powerful. They operate from normal 240V mains and the final shaft speed is 16 r.p.m. 16/- Post & ins. 2/6.

REED SWITCH

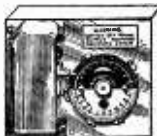Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass encased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 8/6 each, or 24/- a dozen. Suitable magnets are 1/- each.



ELECTRIC TIME SWITCH

Made by Smiths these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 6 amp changeover contacts will switch circuit on or off during these periods. 59/8, post and ins. 4/6. Additional time contacts 10/- pair.




NICAD RECHARGEABLE CELLS

3-6V 500mA size 1 1/2 x 1 1/4 in. dia. type ref. DKZ500 really powerful will deliver 1 amp for 1 hour. Regular price 32/6 our price 17/8 each. New and guaranteed. Other voltages available, single cell 1-2V 6/8. 5 cell 6V 29/8. 9 cell 10-8V 47/8.



DRILL CONTROLLER

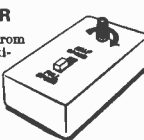Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 3/6 post and insurance. Or available made up 29/8, plus 2/6 post.



THIS MONTH'S SNIP

DEAC RECHARGEABLE BATTERY

1-2V-2000 mA/hr. type (3000DKZ). Size 2 1/2 in. dia. x 1 in. thick approx. Tremendously powerful, will deliver 4 amp for 1 hour. Regular price over £2 each. Snip price 25/- each. NEW AND UNUSED.

REPAIRABLE RADIOS

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/4 in.—complete with soft leather zippered bag. Specification:—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kcs. Sensitivity: 5 mV/m. Intermediate frequency: 465 Kcs. or 455 Kcs. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. These radios require attention. Circuit diagram is not available. Price only 17/8 each plus 2/6 post and insurance. 4 radios 33 post free.



LAST CHANCE FOR THIS BARGAIN

CASSETTE LOADED DICTATING MACHINE for only 99/6

Battery operated and with all accessories. Really fantastic offer a British made £31 outfit for only 99/6, brilliantly designed for speed and efficiency—cassette takes normal spools, drops in and out for easy loading—all normal functions—accessories include: stethoscopic earpiece—crystal




microphone has on/off switch—telephone pick-up—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY 34.19.6 plus 7/6 post and insurance. Foot switch 18/6 extra. Spare Cassettes at 4/6 each, three for 10/-.

THERMOSTAT WITH PROBE

This has a sensor attached to a 15A switch by a 14in. length of flexible capillary tubing—control range is 30°F to 160°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heat pump to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch.

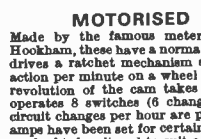Made by the famous Teddington Co., we offer these at 12/6 each. Postage and insurance 2/6.



MOTORISED CAM SWITCH

Made by the famous motor company Chamberlain and Hookham, these have a normal mains 200-240V motor which drives a ratchet mechanism so geared to give one ratchet action per minute on a wheel with 60 teeth thus a complete revolution of the cam takes place in one hour. The cam operates 8 switches (6 changeover and 2 on/off thus 480 circuit changes per hour are possible). Contacts, rated at 15 amps have been set for certain switch combinations but can, no doubt, be altered to suit a special job. Also other switch wafers or devices can be attached to the shaft which extends approximately one inch. 47/8, p. & ins. 4/6.



HI FI BARGAIN

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for HI-FI and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 2 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—2in. diam. on pitch circle 1 1/4 in. diam.—Overall height 5 1/4 in. A 26 speaker offered for only 23.9.6 plus 7/6 p. & p. Don't miss this offer. 15in. 30 watt 27.19.6.



Where postage is not stated then orders over 23 are post free. Below 23 add 2/6. Semi-conductors add 1/- post. Over 21 post free. S.A.E. with enquiries please.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.



SNIPSCOPE

Famous war-time "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the

infra-red strike it. A golden opportunity for some interesting experiments. 7/6 each, post 2/6. Data will be supplied with cells, if requested.

AC FAN

Small but very powerful mains motor with 6 1/4 in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are superior, mostly resin filled. Kit A—15-30 w. 19/8. Kit B—30-40 w. 19/8. Kit C—40-60 w. 19/8. Kit D—60-75 w. 19/8. Kit E—75-100 w. 19/8. Kit F—100-150 w. 19/8. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kits F 5/6 on first kit then 3/6 on each two kits ordered.

TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6.

MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly costly when you have to buy them in a hurry—so you should take advantage of this offer: 3in. moving coil flush mounting meters only 9/6. These are actually B.F. meters and cost about £3 each but if you don't want them for B.F. then all you have to do is to remove the thermocouple and you will have a 2-3 mA meter which you can make into almost anything by adding shunts or series resistor. New and unused.

MINIATURE RELAY

American make—530 ohm coil 30-30 volt operation—2 pole change over 4/6 each 48/- doz.


THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 9/6 plus 1/- post. Suitable box for wall mounting, 5/-, P. & P. 1/-
Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-60°F. Internal screw alters the setting so this could be adjustable over 80° to 1000°F. Suitable for controlling furnaces, ovens etc.
Type "C" 15 amp. This is a 17in. long rod type heater or to make flame-stat or fire alarm 8/6 plus 2/6 post and insurance.
Type "D". We call this the Ice-stat as it cuts in and out at around freezing point, 3/3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blackest wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/-
Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.
Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 160°F. Price 18/-, plus 2/- post and insurance.

ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH
Also 102/3 Tamworth Road, Croydon

sinclair

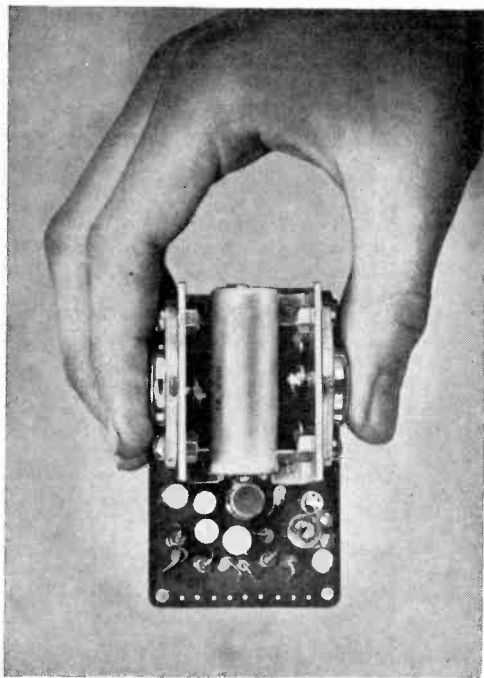

Z.12 - for all you want from any amplifier

The Z.12 is a most versatile integrated amplifier and pre-amp in which power, compactness and true high-fidelity standards are combined within a unit of very modest price. The most widely used unit of its kind in the world, the Z.12 has an output of 12W R.M.S. continuous sine wave (24W peak) or 15W music power (30W peak). It has Class B ultralinear output which can be fed into any loudspeaker from 3 to 15 ohms. (Two 3 ohm speakers can be used in parallel.) Frequency response—15 to 50,000Hz $\pm$ 1dB; input sensitivity—2mV into 2 kilohms. The Z.12 will operate from any power source between 6 and 20V d.c. As such,

a car battery or the PZ.4 are eminently suitable, giving much wider than usual scope in the applications to which the Z.12 may be put. As well as hi-fi, these include systems for P.A. electronic guitars, organs, intercom systems, laboratory, education or industry. You will find the Z.12 in use in such instances again and again. The Sinclair Z.12 is supplied ready built, tested and guaranteed, complete with manual of circuits and instructions for matching it to your precise requirements. Two may be used in stereo when, with the Stereo 25 and PZ.4 together with two Q.14s, you will have an ideal high fidelity assembly.

89/6

Q.14 - the unique loudspeaker




New materials and original design techniques have been used to produce a speaker of fantastic quality at a most attractive price. Experts and reviewers have enthusiastically endorsed its performance. The shape and size of the Q.14 make it far more adaptable to its environment than is the case with conventionally styled speakers so that it is much easier to position this speaker in the room in which it is to be heard. The Sinclair Q.14 has a substantially flat frequency response

from 60 to 16,000Hz and outstandingly good transient response. It will comfortably handle up to 14W loading and is positively brilliant in stereo. Measuring 9 $\frac{1}{2}$ in. square by 4 $\frac{1}{2}$ in. deep, this loudspeaker is finished in matt black with solid aluminium bar trim. Try the Q.14 in your own home without delay. If you are not delighted with it, your money, including cost of return postage to Sinclair, will be refunded immediately.

£7.19.6

+ 2/11d P.T. Surchage

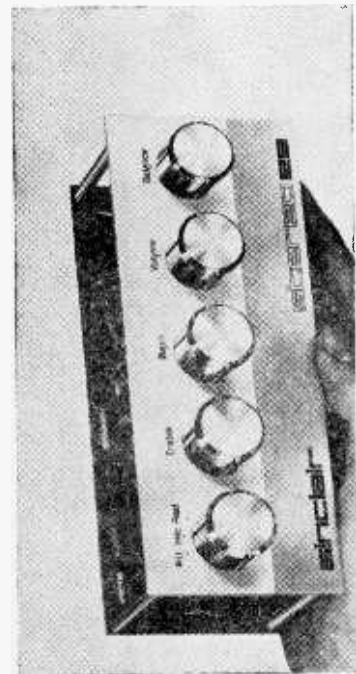


Stereo 25 de-luxe pre-amp/control unit

This is a very elegantly styled unit, which, although designed basically for use with the Z.12, is readily adaptable for use with any high quality power amplifier system. The switched input selector allows for Pick-up, Radio and Auxiliary and there are controls for bass cut and lift, treble cut and lift, volume and stereo balance. P.U. input is equalised to R.I.A.A. curve

from 50 to 20,000Hz $\pm$ 1dB and the instructions manual provided gives matching details for pick-ups, shows how to connect up, etc. The front panel of the Stereo 25 is finished in brushed and polished aluminium enbellished in black. The control knobs are in solid aluminium to match. Size 6 $\frac{1}{2}$ x 2 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in. plus knobs. Supplied built, tested and guaranteed.

£9.19.6

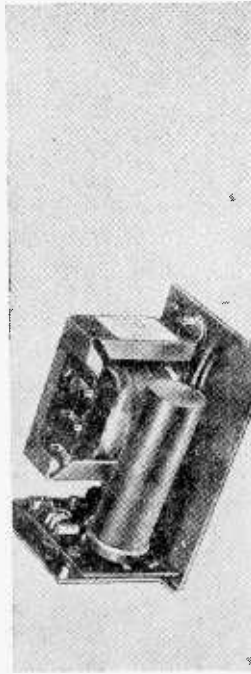

PZ.4 - stabilised power supply unit

Designed specially to meet the power requirements for an assembly of two Z.12s and the Stereo 25, this heavy duty transistorized power supply unit has stabilised output of 18V d.c. at up to 1.5A. It is for a.c. mains operation 200/250V.

Supplied built, tested and guaranteed.

99/6



SINCLAIR MICROMATIC

Whether you buy your Micromatic in kit form or built ready for use, you must not deny yourself the thrill of owning this fantastically small British receiver. Smaller than a matchbox, it has power range and selectivity that must be experienced to be believed. The high quality magnetic earpiece supplied with the set ensures excellent reproduction indoors and out. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact you will find this set performing in some cases where other sets cannot be heard at all. The Micromatic is housed in a neat black case given an elegantly modern appearance by the attractive aluminium front panel and matching tuning control.

Kit in fitted pack with magnetic earpiece, instructions and free solder.

49/6 + 11d P.T. Surcharge

Built, tested and guaranteed, inc. magnetic earpiece.

59/6 + 11d P.T. Surcharge

Mallory Mercury Cell type RM.675 (2 required) 2/9 each

YOUR SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. Full service facilities available to all purchasers.

Goods sent post free in U.K. and Overseas by surface mail. Air-freight charged at cost.

Please send

NAME

ADDRESS

For which I enclose cash/cheque/
money order

PW.769

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE OCA-3 52731

WIRECOMP ELECTRONICS SALE MART

BRAND NEW EMI Emitape

Famous British made tape—brand new and perfect in makers sealed cartons.

Type 88/4	300ft 4" Standard	SALE PRICE 7/6
	List price 11/-	
Type 88/6	600ft 5" Standard	SALE PRICE 13/6
	List price 21/10	
Type 881/9	900ft 5 1/2" Standard	SALE PRICE 15/-
	List price 28/10	
Type 88/12	1,200ft 7" Standard	SALE PRICE 19/6
	List price 36/2	

Post 1/- per reel. Orders of 6 reels and over POST FREE.

NEW	Emitape 5" 900ft LP on 5 1/2" spool. List Price 28/9	SALE PRICE 19/11
NEW	Scotch Tape 5 1/2" 1,200ft LP on 7" self-thread spool. List Price 36/-	SALE PRICE 27/11
NEW	Scotch 7" self-threading spools. List price 8/11	SALE PRICE 6/6

WHARFEDALE BARGAINS Reflex Baffle Extension Speaker

6in. L/speaker unit in polished walnut veneered wood cabinet, size 10 x 8 x 4in. Volume control fitted. 1 1/2-5 ohms imp. Complete in maker's carton with 5ft. flex.

List price 76/11 SALE PRICE 45/- P. & P. 3/6

Wharfedale "Truqual"

Constant impedance volume control. Provides attenuation from 0 to -24dB in 5 steps plus OFF. For 1 1/2 to 5 ohm speaker systems. Flush mounting.

List price 20/- SALE PRICE 7/6 P. & P. 2/6

Hi-Sky HS-30 Cassette Recorder

High quality transistorised cassette recorder. Features include: Push button operation • Record level meter • Safety record button • Operates on 4 x U11 type batteries • Complete with Real Leather case with carrying handle and accessory compartment. Dynamic remote control microphone and C-60 cassette. Brand new and boxed.

List Price £21.0.0 SALE PRICE £17.10.0 P. & P. 6/6

WIRECOMP SPECIALITIES FOR THE ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps., meters, speakers, etc., etc. ALL faulty or damaged needing repair—

AT GIVE AWAY PRICES!

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — 2/- each

ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

SPOT CASH PART EXCHANGES WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone

COME AND LOOK TODAY (Open 6 days a week!)

ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1

Tel. 01-636 0647

MAIL ORDERS TO:

378 HARROW ROAD, PADDINGTON, LONDON, W.9

PLEASE NOTE: Owing to increased handling charges — MINIMUM Mail Order value £1 (including postage).

NEWMARKET TRANSISTORS

NKT11 9/3	NKT452 12/6	BCY71 9/3	2N930 8/-
NKT12 7/3	NKT453 8/-	BCY72 4/6	2N1131 8/6
NKT72 5/-	NKT603F 6/6	BDY20 22/3	2N1132 10/-
NKT73 5/-	NKT613F 7/3	BFX29 11/6	2N1302 4/6
NKT124 8/6	NKT674F 5/-	BFY30 13/9	2N1303 4/6
NKT125 5/9	NKT677F 4/6	BFX84 8/6	2N1304 5/6
NKT126 5/-	NKT713 5/-	BFX85 8/6	2N1305 5/-
NKT135 5/-	NKT717 8/-	BFX86 8/6	2N1306 6/6
NKT137 6/6	NKT734 5/-	BFX87 8/-	2N1307 6/6
NKT210 5/9	NKT736 6/6	BFX88 7/3	2N1308 8/6
NKT211 5/-	NKT773 4/6	BFY50 5/-	2N1309 8/6
NKT212 5/-	NKT781 5/-	BFY51 4/6	2N1613 5/9
NKT213 6/6	NKT10419 5/-	BFY52 5/-	2N1711 6/6
NKT214 4/6	NKT10519 5/9	BFY53 4/6	2N1893 12/6
NKT215 5/-			2N2217 7/3
NKT216 10/-			2N2217A 15/6
NKT217 10/9			2N2218 8/6
NKT219 5/-			2N2218A 10/-
NKT223 5/9			2N2219 10/9
NKT224 4/6			2N2219A 12/6
NKT225 4/6			2N2220 7/3
NKT229 5/-			2N2221 8/6
NKT237 7/3			2N2221A 10/-
NKT238 4/6			2N2222 10/9
NKT239 5/-			2N2222A 12/6
NKT240 4/6			2N2297 9/3
NKT241 5/-			2N2368 4/6
NKT242 3/-			2N2369 4/6
NKT243 14/-			2N2369A 5/-
NKT244 3/-			2N2483 8/6
NKT245 3/9			2N2484 10/9
NKT261 3/9			2N2220A 10/9
NKT262 3/9			2N2904 10/9
NKT264 3/9			2N2904A 12/-
NKT271 3/9			2N2905 15/6
NKT272 3/9			2N2905A 12/6
NKT274 3/9			2N2906 12/6
NKT275 3/9			2N2906A 13/3
NKT281 5/-			2N2907 14/-
NKT302 16/6			2N2907A 20/9
NKT304 13/3			2N3053 5/9
NKT331 11/6			2N3055 20/9
NKT401 18/-			2G345 4/-
NKT402 19/3			2G371 4/-
NKT403 16/-			2G378 4/-
NKT404 13/3			2G382 10/-
NKT405 14/9			2G384 8/6
NKT406 13/3			2G385 8/6
NKT420 40/-			2G386 8/6
NKT451 13/3			2G387 8/6

FERRANTI TRANSISTORS

ZTX300	1/11
ZTX302	3/-
ZTX44	12/9
ZTX1613	7/9
ZTX1700	17/9
ZTX1701	22/6
ZTX3055	20/6
KR54	27/6
KR56	27/6
ZR12	16/9
ZS170	1/11

NKT10339	6/6	BFY90	29/6
NKT10439	7/3	BSX19	4/6
NKT12329	11/6	BSX20	4/6
NKT12429	14/-	BSX60	16/6
NKT13329	5/-	BSX61	10/-
NKT13429	5/-	BSY35A	9/9
NKT35219	22/3	2N696	5/-
NKT16229	11/6	2N697	5/-
NKT20329	12/6	2N706	3/-
NKT20339	8/6	2N706A	3/-
BC107	4/6	2N708	4/6
BC108	3/-	2N709	11/9
BC109	4/6	2N914	11/6
BCY55	70/-	2N918	11/6
BCY70	5/-	2N929	7/3

Quantity	25/49	5%
Discount:	50/99	10%
	100/299	15%
	300/999	20%
	1,000	25%

all one type

ORGAN BUILDERS!

SILICON N.P.N. TRANSISTORS SUITABLE FOR USE IN DIVIDER CIRCUITS—1/8 each or 25 per 100.

UNMARKED TRANSISTORS (tested) similar to:

2N753 1/8, BSY28 1/8, BSY65 1/8, OC44 1/8, OC71 1/-, OC72 1/-, ORP12 CADMIUM SULPHIDE LIGHT-SENSITIVE RESISTORS 9/- each.

GIANT-SIZE SELENIUM SOLAR CELLS—PRODUCE UP TO 6mA AT 6 VOLTS FROM DAYLIGHT! 67mm. diameter 10/- each. 50mm. x 37mm.. 2 for 10/-.

MULLARD POLYESTER CAPACITORS FAR BELOW COST
PULLEY 0.001µF 400V 3d., 0.0015µF 400V 3d., 0.0018µF 400V 3d., 0.0022µF 400V 3d., 0.01µF 400V 3d., 0.15µF 160V 6d., 0.22µF 160V 6d., 0.27µF 160V 6d., 1µF 125V 1/-.

RECORD PLAYER CARTRIDGES, COMPLETE WITH NEEDLES
GP87/2 Mono 15/-, GP91/3 Compatible 21, GP93/1 Crystal Stereo 25/-, GP94/1 Ceramic 30/-.

TRANSISTORISED SIGNAL INJECTOR KIT 10/-.

SIGNAL TRACER KIT 10/-, CAR REV. COUNTER KIT 10/-.

VEROBOARD

2x 1' 0.15 matrix 1/3 5 x 3 1/2' 0.15 matrix 5/6 3 1/2 x 3 1/2' 0.1 matrix 4/9
3 1/2 x 2 1/2' 0.15 matrix 3/3 17 x 2 1/2' 0.15 matrix 11/- 5 x 2 1/2' 0.1 matrix 4/7
3 1/2 x 3 1/2' 0.15 matrix 3/11 17 x 3 1/2' 0.15 matrix 14/8 5 x 3 1/2' 0.1 matrix 5/6
5 x 2 1/2' 0.15 matrix 3/11 3 1/2 x 2 1/2' 0.1 matrix 4/2
Spot Face Cutter 7/6, Pin Insert Tool 9/6, Terminal Pins 3/6 for 36, Special Offer! Spot Face Cutter and 5 2 1/2 x 1" boards 9/9 only

PAPER CONDENSERS, Mixed bags 0.001µF to 5µF, 12/6 per 100. SILVER-MICA, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values, 10/- per 100.

RESISTORS. Mixed types and values, 1/2 to 1 watt, 6/6 per 100. 55/- per 1,000. Wire-wound resistors, 1 watt to 10 watts. Mixed values, 20 for 10/-.

TRANSISTORS. Mixed, unmarked, mainly O.K. 7/6 for 50.

12 VOLT TRANSISTORISED FLUORESCENT LIGHTS. HALF NORMAL PRICE.

8 Watt 12" tube. Reflector type 22.19.8. 15 watt 18" Batten type 23.19.8. IDEAL FOR CAMPING OR CARAVAN HOLIDAYS! A BRIGHT LIGHT FOR VERY LITTLE CURRENT!

ELECTROLYTIC CONDENSERS

0.25µF	3 volt	4µF	4 volt	10µF	25 volt	64µF	9 volt
1µF	6 volt	12µF	12 volt	20µF	6 volt	100µF	9 volt
1µF	20 volt	4µF	25 volt	25µF	8 volt	320µF	4 volt
1.25µF	16 volt	5µF	6 volt	25µF	12 volt	320µF	10 volt
2µF	3 volt	6µF	6 volt	25µF	25 volt	400µF	6.4 volt
2µF	350 volt	8µF	3 volt	30µF	8 volt	All at 1/- each.	
2.5µF	16 volt	8µF	12 volt	30µF	10 volt	20 assorted	
3µF	25 volt	8µF	50 volt	50µF	6 volt	(our selection)	
3.2µF	64 volt	10µF	6 volt	64µF	2.5 volt	10/-	

Orders by post to:

G. F. MILLWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum order 10/-. Stamped addressed envelope must accompany any enquiries.

For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

NEW PRICES ON NEW COMPONENTS

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: $\frac{1}{4}$ W; 8×2.8
 $\frac{1}{2}$ W; 10×4.3

Leads: 35

10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series).

5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

	each	10 off	25 off	100 off
$\frac{1}{4}$ W 10%	2d.	1/6	3/3	10/4
$\frac{1}{4}$ W 5%	2½d.	1/9	3/8	11/8
$\frac{1}{2}$ W 10%	2½d.	1/9	3/8	11/7
$\frac{1}{2}$ W 5%	3d.	2/-	4/-	12/10

CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads.

±10% tolerance. 100 Volt Working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
0.001, 0.002, 0.005	6d.	4/3	8/4	30/-
0.01, 0.02	8d.	6/-	12/6	41/8
0.05	10d.	7/1	15/6	51/-
0.1	1/2	10/-	20/10	68/6
0.2	2/-	17/6	37/6	125/-

Polystyrene film, Tubular, Axial leads. Unencapsulated. ±5% or ±1pf tolerance. 160 Volt Working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
10, 12, 15, 18, 22, 27, 33	5d.	3/7	7/9	24/-
39, 47, 56, 68, 82, 100, 120, 180, 220, 270, 330, 390	6d.	4/-	8/8	26/8
470, 560, 680, 820, 1,000, 1,500	7d.	5/-	10/10	33/4
2,200, 3,300, 4,700, 5,600	8d.	6/-	13/-	40/-
6,800, 8,200, 10,000, 15,000	9d.	6/9	18/-	45/4

Polystyrene film, Tubular, Axial leads. Professional Grade. Hard Epoxy Resin encapsulation.

±1% tolerance. 100 Volt Working.

Prices—per Capacitance value (µF)—except where stated).

	each	10 off	25 off	100 off
100, 120, 150, 180	1/3	10/2	21/2	64/6
220, 270, 330, 390, 470	1/3	10/8	23/1	71/-
560, 680, 820	1/6	13/10	29/11	92/-
1,000, 1,200, 1,500	1/9	14/1	31/-	96/-
2,200, 2,700	1/9	15/2	32/10	101/-
3,300, 3,900, 4,700, 5,600	2/-	15/11	34/9	107/4
6,800, 8,200, 10,000, 12,000	2/3	17/3	37/10	115/-
15,000, 18,000	2/6	20/1	43/6	133/9
22,000, 27,000	2/9	22/1	47/10	147/4
33,000, 39,000	3/3	24/9	53/8	165/4
47,000, 56,000	3/6	26/1	56/6	173/9
68,000	3/9	27/3	59/4	182/8
82,000	3/9	30/3	65/10	202/-
0.1 µF	4/3	34/2	73/7	228/-
0.12 µF	5/-	37/10	81/11	252/3
0.15 µF	5/-	37/10	81/11	252/3
0.18 µF	6/-	47/-	101/10	313/4
0.22 µF	6/9	53/9	116/8	358/4
0.27 µF	7/3	58/10	126/11	390/-
0.33 µF	7/9	65/-	140/10	433/4
0.39 µF	9/9	75/2	137/7	500/-

POTENTIOMETERS (Carbon)

Superior grade enclosed controls. Low rotational noise. Body Dia. 1 in., Spindle 2 in. x 1/4 in. Tolerance 20%. Linear: 1K to 2M. (1/4W at 40°C.). Logarithmic: 5K to 2M. (1/4W at 40°C.).

Prices—per ohmic value

	each	10 off	25 off	100 off
2/-	16/8	37/6	133/4	

GANGED STEREO POTENTIOMETERS (Carbon)

1/4W at 70°C. Long Spindle.

Logarithmic and Linear: 5k to 1M + 1M.

Prices per ohmic value

	each	10 off	25 off	100 off
8/-	70/-	162/6	575/-	

SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1 in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at 70°C. ±20% below 1M, ±30% above 1M. Horizontal (0.7 in. x 0.4 in. P.C.M.) or Vertical (0.4 in. x 0.2 in. P.C.M.). Subminiature: 0.1W at 70°C. ±20% below 2.5M, ±30% above.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

JACK PLUGS

1 in. Type P1. Standard. Screened. Heavily chromed.

1 in. Type SE/P1. Side-entry version of Type P1.

1 in. Type P2. Standard. Unscreened. Unbreakable moulded cover.

1 in. Type P3. Tip-Ring-Sleeve Stereo version of Type P1.

1 in. Type P4. Tip-Ring-Sleeve Stereo version of Type P2.

3.5mm. Type P5. Standard. Screened. Aluminium cover.

3.5mm. Type P6. Standard. Unscreened. Unbreakable moulded cover.

Prices	each	10 off	25 off	100 off
P1	3/-	26/8	62/5	233/4
SE/P1	3/6	30/10	68/8	280/-
P2	2/6	23/4	54/2	200/-
P3	6/6	60/-	137/6	500/-
P4	6/2	59/6	127/6	455/-
P5	2/2	19/2	43/9	158/4
P6	1/8	15/-	33/4	116/8

JACK SOCKETS

1 in. Type S3. Stereo version for use with P3 or P4 plugs.

1 in. Type S5. Standard. Moulded body. Chrome insert.

3.5 mm. Type S6. Standard. Moulded body. Chrome insert.

Available with make or break contacts on Tip, Ring and Sleeve.

Prices	each	10 off	25 off	100 off
S3	3/3	30/-	68/9	250/-
S5	2/9	25/-	56/8	216/8
S6	1/6	13/4	33/4	100/-

ELECTROLYTIC CAPACITORS (Mullard). -10% to +50%.

Subminiature (all values in µF)

	each	10 off	25 off	100 off
4V	32	64	125	250
6.4V	8	16	32	64
10V	4	8	16	32
16V	2.5	5	10	20
25V	1.6	3.2	6.4	12.5
40V	1	2	4	8
64V	0.64	1.28	2.56	5.12
Price	1/4	1/3	1/2	1

Small (all values in µF)

	each	10 off	25 off	100 off
4V	800	1,250	2,000	3,200
6.4V	640	1,000	1,600	2,500
10V	400	640	1,000	1,600
16V	250	400	640	1,000
25V	160	250	400	640
40V	100	160	250	400
64V	64	100	160	250
Price	1/6	2/-	2/6	3/-

POLYESTER CAPACITORS (Mullard)

Tubular 10%, 160V: 0.01, 0.015, 0.022 µF, 7d. 0.033, 0.047 µF, 8d. 0.068, 0.1 µF, 9d. 0.15 µF, 11d. 0.22 µF, 1/- 0.33 µF, 1/3 0.47 µF, 1/6 0.68 µF, 2/3 1 µF, 2/8. 400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0.01, 0.015, 0.022 µF, 7d. 0.033 µF, 8d. 0.047 µF, 9d. 0.068, 0.1 µF, 11d. 0.15 µF, 1/2 0.22 µF, 1/6 0.33 µF, 2/3 0.47 µF, 2/8.

Modular, metalised, P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022 µF, 7d. 0.033, 0.047 µF, 8d. 0.068, 0.1 µF, 9d. 0.15 µF, 11d. 0.22 µF, 1/- 0.33 µF, 1/3 0.47 µF, 1/8 0.68 µF, 2/3 1 µF, 2/9.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/- OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/- OC139, 5/3. OC25, 7/- OC35, 8/- OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/- 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/- (0.75A): 200 P.I.V., 1/6. 400 P.I.V., 2/- 800 P.I.V., 3/3. (6A): 200 P.I.V., 3/- 400 P.I.V., 4/- 600 P.I.V., 5/- 800 P.I.V., 6/-.

THYRISTORS (5A): 100 P.I.V., 8/- 200 P.I.V., 10/- 400 P.I.V., 15/- SWITCHES (Chrome finish. Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off 5/- Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/- DP/ST, 4/6. DP/DT, 5/-.

ROTARY SWITCHES (Wafer)

High quality. Rear tags. Long spindle, 1/4 in. dia.

1p/12w. 2p/6w. 3p/4w. 4p/3w. 2p/3w.

Prices	each	10 off	25 off	100 off
All Types	4/6	38/4	83/4	283/4

PRINTED CIRCUIT BOARD (Vero).

0.15 in. Matrix: 3 1/2 in. x 2 1/2 in., 3/3. 5 1/2 in. x 2 1/2 in., 3/1 1/2. 3 1/2 in. x 3 1/2 in., 3/11. 5 in. x 3 1/2 in., 5/6. 0.1 Matrix: 3 1/2 in. x 2 1/2 in., 4/- 5 in. x 2 1/2 in., 4/6. 3 1/2 in. x 3 1/2 in., 4/6. 5 in. x 3 1/2 in., 5/3.

SEND S.A.E. FOR 1969 CATALOGUE

DUXFORD ELECTRONICS (PW)

97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/-.

C.W.O. Post and Packing 1/6

BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,
150 REGENT ST., LONDON, W.1.

KING OF THE PAKS SUPER PAKS

Unequalled Value & Quality
BI-PAK NEW—UNTESTED
SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

PAK NO.		
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 Watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-Amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-Amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 Amp SCR's TO-5 can up to 600 PIV CRS1/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise 2N3707	10/-
U32	25 Zener diodes 400mW DO-7 case mixed Vits. 3-18	10/-
U33	15 Plastic case 1 Amp silicon rectifiers W4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

FULLY TESTED

AC107	3/6
AC126-78	2/6
AF116-117	2/6
AF139	1/6
AI102	1/6
BC107-8-9	5/-
BFY60-51-52	7/6
BSY26-7	3/6
BSY28-9	4/6
BSY35-35A	4/6
OC22-25	2/6
OC26-35	5/-
OC28-29	7/6
OC44-45	1/6
OC71-81	1/6
OC72-75	2/6
OC81D-82D	2/6
OC82	2/6
OC140	5/-
OC170	2/6
OC171	7/6
OC201	3/6
ORP12-60	8/6
OC71	8/6
OA5-10	1/6
OA47	2/6
OA70	1/6
OA79	1/6
OA81-85	1/6
OA91	1/6
OA95	1/6
OA300	3/6
OA202	3/6
2N697-7	5/-
2N706	3/6
2N708	5/-
2N2160	15/-
2N2646	15/-
2N2712	5/6
2N2926	2/6
MAT100-101	3/6
MAT120-121	3/6
ST140	3/6
ST141	4/-

SIL. RECTS TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/6	4/6	8/6
100	1/3	3/3	4/6	15/-
200	1/3	4/-	4/6	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/3	6/6	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-. Plus 2/- P. & P.

UNIUNCTION

UT46	Eqvt. 2N2646, 7/6
Eqvt. TS43	
FET's	
2N3819	10/-
2N3820	25/-
MPF105	8/-
AD161-162	NPN-PNP
Comp. Pair	12/6 pr.
28034	15/- ea.

TRANSISTOR EQUIVALENT BOOK

52 pages of Cross References for transistors and diodes, types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

PLEASE NOTE.—To Avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal Service" which is second to none, we have re-organized and streamlined our Dispatch Order Department and we now request you to send all your orders together with your remittance, Direct to our Warehouse and Dispatch Department, postal address:—BI-PAK SEMICONDUCTORS, Dispatch Dept., P.O. BOX 6, WARE, HERTS. Postage and Packing Still 1/- per order. Minimum Order 10/-.

TESTED SCR's

PIV	1 AMP	7A	16A	30A
25	5/6	7/6	8/6	30/-
50	7/6	8/6	10/6	35/-
100	8/6	10/6	15/-	55/-
200	12/6	15/-	20/-	55/-
300	15/-	20/-	25/-	55/-
400	17/6	25/-	35/-	80/-
500	30/-	40/-	45/-	85/-
600	40/-	50/-		

INTEGRATED CIRCUITS

I.C. Operational Amplifier with zener output.	
Type 701C. Ideal for P.E. projects. 8 Lead TO-5 case. Full Data. Our Price 12/6 each. 5 off 11/- each. Large qty prices quoted for.	
Fairchild Epoxy TO-5 8 Lead. I.C.	
uL900 Buffer	10/6
uL914 Dual Gate	10/6
uL923 J.K. Flip-Flop	14/-
I.C. Data Circuits etc.	1/8
Mullard I.C. Amplifiers	70/-
TAA293 ORP.AMP.	70/-
TAA263 Min AF Amp	18/6
TAA293 G.P. Amp	26/-
RCA CA3020	30/-
Audio Amp	30/-

ELECTROVALUE


EVERYTHING BRAND NEW AND TO SPEC. NO SURPLUS

SPECIALIST SUPPLIERS OF TRANSISTORS IN TYPES TO SUIT ALMOST ALL APPLICATIONS

- COMPETITIVE PRICES
- HIGH QUALITY COMPONENTS FOR TRANSISTOR CIRCUITS
- PEAK SOUND AS ADVERTISED
- CATALOGUE PACKED WITH UP TO THE MINUTE ITEMS AND INVALUABLE INFORMATION. Send 1/6 for your copy now.
- DISCOUNTS—10% on orders for components for £3 or more. 15% on orders for components for £10 or more.
- POSTAGE on order for £1, add 1/-. FREE on orders for £1 or over. Overseas orders welcome—Carriage charged at cost.

ELECTROVALUE

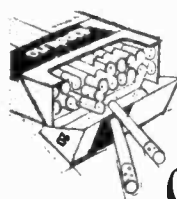(Dept. PW), 32a ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY. Tel: Egham 5533 (STD 0784-3)



We put
23,340
cigarettes

in our Budget
combination storage
unit!

Think what you could
put in it!

Storage. Lots of it, for a thousand things you stock; replacement parts; light bulbs; cameras; anything up to 7 x 8 x 10 1/2 in. Safety drawer-stops as 'standard'. Smooth guide runners thro'out. All in a compact 3ft. 6in. high, 2ft. 11in. wide, 1ft. deep area. Ready assembled, in stove enamelled green or grey. With 18 handy, 6 large, 8 king-sized drawers. At £17 5s. worth every penny! See the rest of the N. C. Brown range!



£17 5s.

Carriage free
on mainland



N.C. BROWN LTD.

pacesetters in storage equipment

Send your FREE BROCH.
URE ☐ or Send ☐ (how
many) Budget Storage Units
at £17. 5s. in green or
grey.

NAME _____
ADDRESS _____
Dept. PW Eagle Steelworks, Heywood, Lancs. Tel: 69018
London: 25-27 Newton St., W.C.2. Tel: 01-405 7931

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK




Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Front panel aluminum and black—12 1/2 x 4 1/2 in. 200-250 A.C. Mains Trans. Off/On-Tone; Vol./Mic.; Vol./Gram.; Mic. Input; Gram. Input; Monitor; Valves 6BR7, 6EC83, 6EM84, EL84 and Rect. 2 Track \$10.10; 4 Track \$12 (12/6 p. & p.). Ready for bolting direct to Magnavox deck.

FULLY BUILT STEREO AMPLIFIER. 2 x 3 watts, mains trans., metal rect., 2 x UCL82, 2 o.p. trans. for 3 ohm, vol/on-off, tone, balance, chassis type with 3 controls on front. 11 x 3 1/2 x 4 in. high. \$6 (8/- p. & p.).

8W. PEAK PUSH-PULL OUTPUT AMPLIFIER. 200-250V A.C. E280, 6EC83, 2 EL84, Bass, treble, vol/on-off, \$7.17.6 (post paid). Size 12 x 3 1/2 x 4 in. high. For Record Player, Radio Tuner, etc. Mains Trans. o.p. trans. for 3 ohm.



6 PUSH-BUTTON STEREOGRAM CHASSIS

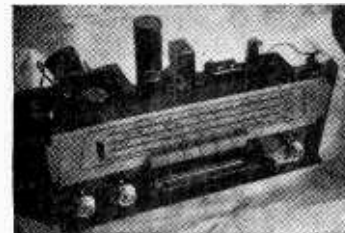

M.W.: 8.W.1: 8.W.2: V.H.F.: Gram; Stereo Gram; Vol; Tone; Mains Trans; 200-250 Volts; 2 o.p. for 3 ohm. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial silver and black 15 x 3 in. 190-550M; 16-51M; 60-187M. VHF 86-100 Mc/a. Valves: 6EC85, ECH81, EF89, 2x ECL86, EM84 and Rect. Price \$19.18.0, carr. paid. With Stereo Decoder fitted \$7.10.0 extra.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

..... Please

7/69

BRITISH NATIONAL RADIO SCHOOL

TRANSISTORS etc.

AC107	3/-	OC35	7/6
AC126	3/-	OC44	2/0
AF115	3/-	OC45	2/0
AF116	3/-	OC70	2/3
AF117	2/6	OC71	2/-
BFY18	4/6	OC72	2/3
BFY51	4/6	OC73	2/3
GET113	2/6	OC75	2/2
OA5	1/8	OC81	2/-
OA9	1/8	OC81D	2/-
OA81	1/8	OC82D	2/3
OA85	1/8	OC140	5/-
OA91	1/8	OC169	3/8
OC23	6/8	OC170	2/2
OC25	5/-	OC171	2/2
OC26	5/-	OC202	4/6
OC28	6/8	TK22C	1/6

Crystal Diodes—6 for 2/6. (7d.).

Also 8µF 350V 1/2, 25µF 25V 1/3 and 50µF 50V 1/9.

Postage, Packing and Insurance all above 7d. up to 3/- from 4-11; 12 and over paid.

2 GANG VAR. CONDENSER: Mod., air-spaced, .0005 ea. sec. 5/- (1/-).

SUB-MIN. TRANSFORMERS: Output (30 for OC72 etc.) 2/6. Driver 2/6 (either 7d.).

MULTIMETER: 20,000 Ω/V D.C. 10,000 Ω/V A.C. 0-5/25/50/250/500/1K volts D.C.

● 0-10/50/100/500/1K volts A.C. ● 0-50µA/2-5mA/250mA D.C. ● 0-6K Ω/6 meg Ω

● 10µF/100µF/1000µF/10mF. ● —20 to +22dB. ● Complete with test leads and instructions.

● Over-load protected 1969 model with every refinement. \$4.75 (2/6). JUNIOR MODEL

at 4/7 (2/6) 1000 Ω/V described in free list.

SOLDERING IRON. Slim Mod. British. High speed, 8 1/2 in., all parts replaceable, fully

guaranteed for professional, radio and general D.T.Y. use. 19/6 (1/-).

DIAMOND STYLII. Replacements for BBR TC8LP, TCS and TC8LP/STEREO:

COLLARO "O": RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67;

all at 7/6 each (6d.). ACOS GP91 ST/PL; BBR ST4 and ST9; SONOTONE 9TA and

STAHC, PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304) state whether long or

short type, all at 13/6 (6d.).

SAPPHIRE all the above 7/8 types only, also ACOS GP87 at 3/3 each (6d.). ACOS

at 6/9 (6d.). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES, all fitted Styl and Standard fittings. Mono GP67/8, 13/6. ●

Mono de Luxe GP91/3, 17/-. ● Stereo Compatible—Mono which also plays Stereo records

monaurally with min. wear. GP91/50, 19/6. ● Latest Stereo GP95, 23/-. ● Ceramic

Stereo, top quality for expensive outfits, GP94, 23/6 (all 1/-).

FFS ELIMINATOR (A.C.) 17/6 (1/6). ● **7W. STATION TRANS. INTER-COM.** Excellent

Baby alarm, instant, easy fitting with leads, plugs and battery. All you require 22/6 (3/-).

TRANSISTORISED AMPLIFIERS, 3 watt, 5V operation, 45/6 (1/9); 7 1/2 watt, 6 trans.

24V operation, 67/6 (2/6).

Extra High Torque MINI-MOTOR, 4 1/2 to 12V, 1 1/2 x 1/2 in. 5/- (5d.). 9,000 r.p.m.

Mech. REV. COUNTER to 999, reset wheel, for T/records etc. 5/6 (1/-).

SUBSTITUTION BOXES, Capacitance 24/6 (1/6). Resistance 32/6 (1/6). Both full range and

complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24" Red and Black leads, thin 4 1/2" prods, 1 1/2" plugs

4/8 (9d.).

RECORDING TAPE: Finest quality British Mylar. STANDARD: 5in. 600ft. 7/8, 5 1/2 in.

500ft. 8/9, 7 1/2 in. 1200ft. 11/3, LONG PLAY 5in. 800ft. 10/-, 5 1/2 in. 1200ft. 11/3, 1800ft.

13/- (13 real). Still the finest quality and value obtainable.

MICROPHONES—CRYSTAL. MIC91, Desk, 16/3; MIC45, curved hand grip 17/3; Stick

"60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut"

stand, switch and 2 leads with 2-5 and 3-5 plugs 11/-. Lapel (or hand) with clip 6/6 (1/-).

Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands,

25/- (1/6). DYNAMIC: Cream hand/table 14/- (1/-). MS10 50K Ω, 3 1/2 x 1 1/2 in. with Base,

Adaptor and Neck Cord 27/6 (2/6). Miniature, but fixed on flexible swan neck to switch

fitted base 42/6 (2/6). DM128 Uni-directional, 50K/800 ohms imp, stand adaptor, very

high quality 6 1/2 x 2 x 1 1/2, \$5.9.6 (5/-).

CARDIOM DYNAMIC OMNI-DIRECTIONAL: Two recently introduced highly successful

mikes "SQUARE" 208, \$5.10.0. "BALL" type, 209, with built-in vol. control, switch

50K/800 ohms imp, \$5.17.6 (either type 5/-). Full details in list.

MICROPHONE HEADSETS: Diameter 1-7/8 in. or 0-9 in. either size 5/6 (6d.).

SPEAKERS: 12in round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 35/6 (5/6); 9 1/2 in. 3 Ω

6/6 (1/-); 6 x 4 heavy duty 3 Ω 13/6 (3/6) or for Stereo 32/6 pair, post etc. paid; 8 x 3 in.,

3 Ω, 8/6 (1/-). Limited quantity powerful 2 1/2" PM transistor replacement speaker, high

ohms, excellent, 5/6 (1/-). **HEADPHONES** High Res. 2000 Ω ea. Earpiece 18/6 (1/6);

Stereo Dyn 3-16 Ω, 65/- (3/-); **EARPIECES** with lead etc., Min. Plug Magnetic 1/6;

Crystal 4/9 (either 7d.).

AERIALS, Car Types: Telescopic, vandol proof, locks retracted, 2 keys and all fittings,

22/6 (2/6) Motor driven, 12V, 5 section, complete \$7.10.0 (5/-).

FOR ALL PORTABLES and F.M. SETS. Telescopic 5 section 5 1/2 in. with swivel, 5/-.

● 7 section 5 1/2 in., no swivel, screw hole in base, 5/6. ● 10-section 6 1/2 in., no swivel,

each hole in base 12/6. **DISAPPEARING 8 section,** swivel, fixing assembly, 6 1/2 in. 10/-.

New 6 section 5 1/2 in., screw hole in base, no swivel 4/-, (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 3/3, SPDT 8/3.

DPST 3/-, DPDT 2/3. Slide types: Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre

"off" 1/9. Reed magnetic on/off 1/9 (7d. each, all types). Rotary switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch 2/6, 13 volt 7 pin synch 10/-.

6 volt 7 pin synch 10/- (1/- each, all types).

MAINS REON TESTER: Fly leads 3/- (7d.). Pocket screwdriver type 3/6 (6d.). **PLUGS:** 8td.

Jack, plastic body 2/3. Screened 3/- (7d.). **SOCKETS** 1/6 (all 7d.). **VALVE HOLDERS:** B7G or

B9A, Moulded 6d. (7d. up to 4, 1/- over 4). **CONNECTING WIRE:** 5 coils asstd. coils each

5 yds. Solid Core 2/6. Flexible 3/-, Super thin for transistor wiring etc. 3/- (6d. all types,

per 6 coils). **PICK-UP WIRE:** Twin Super thin Flex, Screened, 1/8 yd. (6d. up to

6 yds. over 6 yds. post free). **TWIN MIKE CABLE:** 1/3 yd. **SINGLE MIKE CABLE:**

7d. yd. Both flexible, screened and sheathed. ● **FEEDER CABLE:** Twin r.f. bal. "fig. 8",

80 Ω, or flat 300 Ω transparent polythene insulated, either 6d. per yd. (all cables up to

three yards 8d., each additional yard, 1d. extra).

R.F. INDICATOR, 5-Band, with meter antenna, monitoring crystal earpiece etc. 45/6

(1/6). Details in list.

IRRETRACTABLE FLEXIBLE LEADS. Space saving "Curly", many uses in car and home;

with phono plug each end, 6 ft., 4/6; 12 ft., 7/9. With phono plug one end, phono socket

at other, 6 ft., 5/-, 12 ft., 8/6 (9d. on any).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors

and circuit. M. and L. wave. Separate speaker and baffle. Absolutely complete, for + or

— chassis. \$11.11.0 (6/6).

CURRENT LIST: Sent with all orders or free for s.a.e. details of cable, croc, clips and leads,

Continental din plugs for Grundig, Telefunken equipment, etc., dials, plugs and sockets,

panel meters, record player and tape recording accessories. **BATTERY CHARGERS,**

test equipment, test prods, tape recorder, special transistors, portable sets, car radio,

more switches and other components, tools, Veroboard etc., etc. This advertisement

cancels all previous ones and lists supplied prior to April 30th.

ELSTEAD ELECTRONICS

(PW20)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost, plus 3/2 registration or insurance fee. S.A.E. please for all enquiries, otherwise regret cannot be replied to.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. for insertion in the next available issue.

SITUATIONS VACANT

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts, Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

SERVICE ENGINEERS—we are an old established electronics company, but headed by a young management team and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead phone Michael Adler at 01-636 9606.

RADIO TECHNICIANS

VACANCIES TO BE FILLED BY
OCTOBER 1969

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment (in Cheltenham and other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to such candidates who can also offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications. A knowledge of Electro-mechanical equipment will be an advantage.

Pay according to age, e.g. at 19—£869 at 25—£1,130 (highest age pay on entry) rising by four annual increments to £1,304.

Prospects of promotion to grades in salary range £1,217-£2,038. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

RECRUITMENT OFFICER (RT 37/54)
GOVERNMENT COMMUNICATIONS
HEADQUARTERS,
OAKLEY, PRIORS ROAD,
CHELTENHAM, GLOS. GL52 5AJ

MISCELLANEOUS

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions 19/6 C.W.O. 'Circuit-tetch', 12 Cambridge Road, St. Albans, Herts.

BUILD IT in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

YOUR CALL SIGN ENGRAVED. White Letters Black Plate 6 x 1 1/2in. 5/6. 2 x 1/2in. Badge Pin, 4/-. Post Free. C.W.O. Workshops for Disabled, Northern Road, Cosham, Portsmouth. PO6 3EP.

ELECTRONIC SOUND and musical devices required for exploitation. Adequate finance available. Projects developed to pre-production stage required. Royalty payments guaranteed. Box 87

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

MUSICAL MIRACLES. Send S.A.E. for details of Rhythm Modules, versatile bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50µA meters, 25/- post paid. HURRY. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

ELECTRICAL

240 VOLT
ELECTRICITY
ANYWHERE



BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY

Exclusive World Scoop Purchase. The fabulous Mk. 2D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only \$419.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. FW STANFORD ELECTRONICS, Rear Derby Road, North Promenade, Blackpool, Lancashire.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman Street, Loughborough.

EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies in September and January. Grants available. Day and Boarding students. Stamp for prospectus Wireless College, Colwyn Bay.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms and Radio Amateurs) R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541, INTERTECH HOUSE,
STEWARTS ROAD, LONDON, SW8

WANTED

DAMAGED AVO METERS, Models 7 & 8, any quantity. Send for packing instructions. HUGGETT'S LTD., 2/4 Pawsons Road, West Croydon.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED NEW VALVES, televisions, radios, transistors, etc. **STAN WILLETT'S**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WANTED: New valves, transistors etc.; state prices. E.A.V. Factors, 202 Mansfield Road, Nottingham.

WANTED (continued)

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

BOOKS & PUBLICATIONS



This useful Handbook gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment etc; also contained are some suggested modification details and improvements for the equipment. Incorporated in this revised edition is a surplus/commercial cross referenced valve and transistor guide. This book is invaluable to radio enthusiasts, radio clubs, universities and laboratories. The latest edition priced at 45/-, per volume plus 5/- p & p is obtainable only from us at

GILTEXT (LEEDS) LTD
Dept. P.W., 24 Stanfield Chambers, Gt. George Street, Leeds 1.
s.a.e. with all enquiries, please. Extra postage for foreign orders. Circuits now available individually for most surplus equipment on request.

AUDIO. America's foremost journal. Year's subscription 50/-. Specimen copy 4/6. All American radio journals supplied—list free. **Willen** (Dept. 40), 61a Broadway, London E.15.

SURPLUS HANDBOOKS

- 19 set Circuit and Notes .. 8/6 p/p 6d.
- 1195 set Circuit and Notes .. 8/6 p/p 6d.
- H.R.O. Technical Instructions .. 5/6 p/p 6d.
- 36 set Technical Instructions .. 5/6 p/p 6d.
- 46 set Working Instructions .. 5/6 p/p 6d.
- 66 set Technical Instructions .. 7/- p/p 6d.
- BC.221 Circuit and Notes .. 5/6 p/p 6d.
- Wavemeter Class D Tech. Instr. .. 5/6 p/p 6d.
- 16 set Circuit and Notes .. 5/6 p/p 6d.
- BC.1000 (31 set) Circuit and Notes .. 5/6 p/p 6d.
- CR.100/B.28 Circuit and Notes .. 10/- p/p 6d.
- R.107 Circuit and Notes .. 7/- p/p 6d.
- A.R.88D Instruction Manual .. 18/- p/p 6d.
- 62 set Circuit and Notes .. 6/6 p/p 6d.
- Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348, BC.348 (E.M.P.), BC.624, 22 set.
- 52 set Sender and Receiver circuits 7/6 post free

Resistor colour code Indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

AERIALS

BAKER & BAINES

FOR TELEVISION AND F.M. AERIALS

Examples of prices: F.M. dipole 21/-, H 38/-, BBC dipole 30/-, X 38/-, H 42/-, 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/6, 11 ele 57/6, double 8 112/-, combined BBC/ITA 1 + 5 45/-, H + 5 69/-, X + 5 75/-, BBC 2 ele 29/-, 14 ele 37/-, 18 ele 54/-, 22 ele 63/-.

All types generally available including accessories—prices include mounting clamps and postage. CWO please. Please state channels when ordering.

11 DALE CRESCENT, NEW TUPTON
CHESTERFIELD.

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV, 5,000 Models, List 1/6. S.A.E. Enquiries. **TELRAY**, 11 Mauldland Bank, Preston, Lancs.

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/- Over 8,000 models available. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS)

Only 5/- each, plus large S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of
Service Sheets (strictly by return of post).
Please state make and model number
alternative.

Free TV fault tracing chart or TV list on request.

Mail order only.

RECEIVERS & COMPONENTS

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 4-20 watt, 12/6 Post Free. **WHITSAM ELECTRICAL**, 33 Drayton Green Road, West Ealing, W.13.

SIGNAL INJECTOR. Transistorised square wave generator probe, British Made, only 19/6, P & P 1/6 S A E for details and lists **WILSIC ELECTRONICS LTD.**, 6 Copley Road, Doncaster, Yorks.

COMPLETE RANGE of Amateur, Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. **Stephens-James Ltd.**, 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

BRAND NEW ELECTROLYTICS, 15 volt 0.5, 1, 2, 5, 6, 8, 10, 15, 20, 30, 40, 50, 100, 200 mFds, 7/6d. per dozen, postage 1/- The C.R. Supply Co., 127 Chesterfield Road, Sheffield 8.

COMPONENTS

Samples from our catalogue: Geared motors 300 rpm-1r/24H from 7/6; 15v. 300mW Zeners 3/-, 10K + 10K 2% 3in ganged pots, 20/-, 220 ohm 200 watt resistors 7/6; 6d stamp for catalogue.

F. HOLFORD & CO.

6 Imperial Square, Cheltenham.

RECEIVERS & COMPONENTS

(continued)

COSSOR TWIN BEAM OSCILLOGRAPH SCOPE. Model 1049, Mk IIIa. Complete with Stand, in perfect working order. £55 or near offer. **WADKINS**, 177 Maesglas, Cardigan, West Wales.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2inX4in packed with semiconductors and top quality resistors, capacitors, diodes, etc.

Our price, 10 boards 10/-, P & P 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK. 25 boards for £1. P & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 85/-, P & P. 6/6. With a guaranteed minimum of 350 transistors.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4X OC28) 10/-, P & P. 2/-.

TRIM POTS. on 2inX4in boards + other components. 100Ω, 500Ω, 15K, 20K. State requirements. 5 boards 10/-, P & P. 2/-.

NPN GERMANIUM TO 51 WATT POWER TRANSISTORS on small heat sink, on 2inX4in panel. 5 for 10/-, P & P. 2/-.

POWER TRANSISTORS 5m. to 2N174 ex eqpt., 4 for 10/-, P & P. 2/-.

Above on Finned Heat Sink (10D). 4 for £1. P & P. 5/-.

LONG ARM TOGGLE SWITCHES ex eqpt. SPST 13/6 doz., DPST 15/- doz. P & P. all types 2/- doz.

ORGAN BUILDERS' SPECIAL 300 TO 1 TRANSISTORS + 200 SI DIODE GATES on panels. £4. P & P. 6/-.

OVERLOAD CUT OUTS. Panel mounting in the following values... 5/- each. 2, 3, 4, 7, 10 amp. P & P. 1/-.

MINIATURE GLASS NEONS, 12/6 doz. P & P. 1/-.

150 PIV. 10 amp. DIODE BRIDGE RECTIFIERS on HEAT SINK, 12/- + 2/- P & P. ea.

Above at 150 PIV. 20 amps. £1. + 3/6 P & P. each.

LARGE CAPACITY ELECTROLYTICS 4 1/2in, 2in diam. Screw terminals. All at 6/- each + 1/6 each P & P.

4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
6,000mF 45V d.c. wkg.
16,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

KEYTRONICS, 52 Earls Court Road
London, W.8. Mail order only

BRAND NEW SEMICONDUCTORS

IN914 1/6	2N2219 6/-	2N4059 5/-	BCY31 4/6
IN916 1/6	2N2220 5/-	2N4060 5/-	BCY32 7/6
IN4007 4/6	2N2221 5/-	2N4061 5/-	BCY33 5/6
18021 4/-	2N2222 5/-	2N4062 5/6	BCY34 4/6
18025 5/-	2N2369A 5/6	40250 17/6	BCY35 5/6
18120 5/6	2N2848 11/6	40361 13/6	BCY39 5/6
18130 2/6	2N2904 3/-	40362 14/6	BCY70 5/6
18131 2/6	2N2904A 3/-	4C107 6/6	BCY71 9/6
18132 2/6	2N2905 3/-	4C126 4/6	BCY72 5/6
AA119 2/-	2N2905A 3/-	4C127 3/6	BD124 12/-
BZ210 6/-	2N2906 3/-	4C176 5/6	BF115 4/6
BZ211 7/6	2N2906A 3/-	4C167 12/-	BF167 5/6
BZ213 5/-	2N2926	4C188 12/-	BF180 3/6
OA5 2/6	Green 3/6	ACY17 5/6	BF184 7/6
OA79 1/6	Yellow 3/6	ACY18 5/6	BF194 6/6
OA81 1/6	Orange 3/6	ACY19 5/6	BF192 6/6
OA85 1/6	Red 2/6	ACY20 5/6	BFX13 5/6
OA91 1/6	Brown 2/6	ACY21 5/6	BFY60 4/6
OA200 2/-	2N3053 6/6	ACY22 4/6	BFY51 4/6
OA212 2/-	2N3054 12/6	AD140 8/-	BFY52 4/6
2N696 5/-	2N3055 15/-	AD149 8/-	B8X16 5/6
2N697 5/-	2N3391 7/6	AD161 7/6	B8X30 5/6
2N704 5/6	2N3391A 6/-	AF114 5/6	BBY26 4/-
2N706A 3/-	2N3393 6/6	AF116 5/6	BBY27 4/-
2N1131 9/6	2N3402 8/6	AF117 5/6	BBY28 4/-
2N1132 9/6	2N3403 9/-	AF124 5/6	BBY29 4/-
2N1302 4/6	2N3404 12/6	AF126 5/6	BBY28A 3/6
2N1303 4/6	2N3405 12/6	AF127 5/6	OC25 6/6
2N1304 5/6	2N3702 4/-	AF131 8/6	OC28 8/-
2N1305 5/6	2N3703 4/6	AF186 11/-	OC35 6/6
2N1306 6/6	2N3704 5/6	AF239 12/6	OC36 6/6
2N1307 6/6	2N3705 5/6	AF212 5/6	OC44 4/-
2N1308 8/-	2N3706 4/6	ASV26 6/6	OC45 2/6
2N1309 5/6	2N3707 4/6	ASV28 5/6	OC71 2/6
2N1633 6/6	2N3708 4/6	ASZ21 7/6	OC72 4/6
2N1711 6/6	2N3709 4/6	BC107 3/6	OC75 4/6
2N1893 8/-	2N3710 4/6	BC108 3/6	OC81 4/-
2N2147 17/6	2N3711 4/6	BC109 3/6	OC83 4/6
2N2148 12/6	2N3819 9/6	BC113 6/6	OC139 6/6
2N2160 16/6	2N3820 20/-	BC147 5/6	OC140 6/6
2N2217 6/-	2N3823 21/6	BC148 4/6	OC202 8/6
2N2218 6/-	2N4058 6/6	BC149 5/6	ORP12 8/6

Send 6d. stamp for complete list. Over 1,000 types Semiconductors in stock. Capacitors, Resistors and Pots also available.

**A. MARSHALL & SON
(London) LTD.**

28 Cricklewood Broadway, London, N.W.2
01-452 0161/3

FOR SALE

TELEVISION TUBES

Large stocks of television tubes, London's leading wholesale suppliers, all tubes complete with guarantee card. By return despatch. Terms: Cash with order, s.a.e. all enquiries.

14in. types. AW36/20, AW36/21, AW36/80, MW36/24, CRM141, CRM144, CME1402 etc.	£4 17 6
17in. types. MW43/80, AW43/80, CRM173, CME1702 MW43/69 CRM172, AW43/88, AW43/89, CME1703, CME1705 etc.	£4 17 6
19in. types. AW47/90, AW47/91, CME1901, CME1903, CME1902, C19AH	£4 19 6
21in. types. AW53/88, AW53/89, CME2101, CME2303	£6 12 0
MW53/80, AW53/80, MW53/20, CRM211/2	£8 18 10
23in. types. AW59/90, AW59/91, CME2301, CME2303	£6 12 0
23in. Twin Panel. CME2306, A59-16W	£13 1 0
23in. Panorama. A59/11W etc.	£12 0 0
19in. Twin Panel. A47-13W, CME1906 etc.	£10 1 0
19in. Panorama. A47/11W etc.	£9 0 0

We stock all types of tubes.

Carriage and Packing 12/6d. per British Road Services.

Large stocks of valves, transistors components. L.O.P.T.'s, Electrolube, Servisol switch cleaner, Multicore solder. Service Tools.

WILLOW VALE ELECTRONICS LTD.

The Service Dept. Wholesalers, 4 The Broadway, Hanwell, London, W.7. Tel: 01-567 2971/5400

CATALOGUE TRADE ONLY. S.A.E. Please

RECEIVERS & COMPONENTS

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard Alloy Chassis

Width	Depth	4" Height £ s. d.	6" Height £ s. d.	7 1/2" Height £ s. d.
6 1/2"	3 1/2"	12 6	15 0	18 0
6 1/2"	4 1/2"	13 6	16 0	1 0 0
8 1/2"	3 1/2"	15 0	1 0 0	1 1 0
8 1/2"	4 1/2"	1 1 0	1 6 6	1 11 3
10 1/2"	7 1/2"	1 8 6	1 15 6	1 18 9
12 1/2"	3 1/2"	1 1 0	1 6 6	1 11 0
12 1/2"	4 1/2"	1 8 0	1 14 0	1 17 6
12 1/2"	6 1/2"	1 16 0	2 3 0	2 7 3
14 1/2"	3 1/2"	1 5 0	1 11 6	1 14 0
14 1/2"	4 1/2"	2 3 0	2 15 9	2 18 6
16 1/2"	6 1/2"	1 18 6	2 6 3	2 11 6
16 1/2"	10 1/2"	2 10 0	3 5 0	3 11 9

Cases—Post 4s. 6d. per order.

Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases			All 2½" Walls					
	s.	d.		s.	d.		s.	d.
6" x 3"	5	6	10" x 7"	8	6	14" x 3"	7	3
6" x 4"	5	9	12" x 3"	6	9	14" x 9"	14	6
8" x 3"	6	6	12" x 6"	7	6	16" x 6"	10	9
8" x 6"	7	9	12" x 8"	10	9	16" x 10"	16	0

Chassis—Post 3s. 0d. per order.

Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD
STOCKPORT - CHESHIRE
Tel: 061-480 2179

FET HI-FI PRE-AMP MODULE

Latest low-noise FET in special circuit. Matches ANY ceramic/Xtal PU, Xtal mike, valve pre-amp, FM tuner, etc. DIRECTLY into ANY transistor power amp. Input impedance 2 Meg. Dist. <0.2%. 25 Hz—200 kHz $\pm$ 1 dB. Power 6-15 volts.

With full instructions ONLY 25/-, post free (Stereo pair 45/-). Mail order only, c.w.o.

MORRIS

1 Birch Drive, Shawbury, Shrewsbury.

FOR SALE

£6,000 IN VOUCHERS GIVEN AWAY. See free Catalogue for details. Tools, materials, mechanical, electrical, thousands of interesting items. WHISTON, Dept. VW, New Mills, Stockport SK12 4HL.

TOP TRADE DISCOUNTS FOR ALL

COMPONENTS VALVES TUBES

TRANSISTORS

Free Trade Catalogue

Engineers & Service Dealers Only

WILLOW VALE

THE SERVICE DEPT.

WHOLESALE, 4 The Broadway, Hanwell,

London, W.7

01-567 5400/2971

YUKAN SELF-SPRAY

30 PROFESSIONAL THE YUKAN AEROSOL WAY

Get these NOW! air drying **GREY HAMMER** OR **BLACK WRINKLE** (CRACKLE) finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional translatable snap-on trigger handle (value 5/-) for 18/11 carriage paid. Choice of 13 self-spray paint colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

YUKAN, 307A, EDGWARE ROAD, Dept. M/6 LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday, Closed Thursday afternoons.

MORSE MADE !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, a.s.d. 01-660 2896 send 8d. stamp for explanatory booklet to: 68CH8 (BOX 11), 45 GREEN LANE, PURLEY, SURREY

NUT DRIVERS in 22 sizes. B.A., A/F. & M.M.

Send S.A.E. for lists to

Bargain Spot, 268 London Road, Croydon.

FOR SALE (continued)

THE IDEAL Panel Mounting Meter Movement for any Sensitive Test Meter etc.

200 Micro Amp F.S.D. 4 1/2in. x 4 1/2in. In clear plastic case. Our special price only 39/6d. P. & P. free. Limited number only. WALTON'S WIRELESS STORES, 55A Worcester Street, Wolverhampton, Staffs.

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE, YORKS.

Tel. Cleckheaton 2886

Indicator Unit type 26

Size 12 x 9 x 9in. with outer case. Fitted with 2 1/2" tube C.R.T. type CV1528. Nine B7G valves. Clean condition, but not tested. 32/6, p. & p. 10/-.

New 12" Speakers with built in tweeter 3 ohm or 15 ohm 6 watts max 28/6, post pd. Ex. Washing Machine Motors. Single phase 230 volt 1/2 H.P. 1425 R.P.M. All perfect. 26/- p. & p. 10/-.

Silicon Rectifier 500mA, 800 P.I.V. No duds. 2/6, post paid. 24/- per dozen, post pd. Jap Ear Piece. Magnetic 8 ohm. Small and large plug. 1/11, post paid.

Reclaimed TV tubes with six months guarantee. 17in. type AW43/88, AW43/80, 40/-; MW43/69, 30/-; 14in. types, 17/-; All tubes, 12/- carriage.

Speakers removed from TV sets. All PM and 3 ohms.

6in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

8 x 4in., 3/-, p. & p. 3/-; 6 for 24/-, post paid.

7 x 4in., 5/-, p. & p. 3/-; 6 for 34/-, post paid.

5in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

Slot Speakers, 8 x 2 1/2in., 5/-, p. & p. 3/-; 6 for 30/-, post paid.

Indicator Unit type 116a VCR97 tube. Mu metal screen and EF50 valves. Good condition, but not tested. 22/6 carriage 10/-.

Untested Pye, KB, RDG, Ekco 17in. TV sets. Bush 17in. TV sets, 50/- each, carriage 15/-.

Passenger train, double rate.

VALVE LIST

Ex Equipment, 3 months' guarantee Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12	1/6	PCL83	5/-	6BW7	2/6
EP91	3d.	PL36	5/-	6K7	1/9
EP86	3/-	PL38	6/-	6U4	5/-
EPF80	3/-	PL81	4/-	6V6	1/9
ECC81	3/-	PY33	5/-	6P28	5/-
ECC82	3/-	PY81	1/6	10P13	2/6
ECC83	4/-	PY82	1/6	185BT	8/8
ECL80	1/6	PZ30	5/-	20D1	3/-
EP60	1/-	U191	5/-	20P1	5/-
EP80	1/6	U281	5/-	20P3	2/6
EP91	8d.	U282	5/-	30PL1	8/-
EY86	5/-	U301	5/-	30P12	5/-
PC84	2/-	U329	5/-	30P3	2/6
PCF80	2/-	U251	5/-	30PL1	5/-
PCL82	4/-	6B8	1/8	630L2	5/-

Interested in cutting your motoring costs?

You can save a considerable amount of money by tackling some of the car maintenance jobs yourself and the PRACTICAL MOTORIST ANNUAL is designed specially to help you.

Authoritative articles and step-by-step instructions show you how to maintain the engine, ignition, cooling, carburation, transmission, suspension and steering, brakes, tyres, bodywork, electrics, etc., and give advice on simple tuning.

With holidays in mind there is a most helpful section on camping and caravanning.

Every motorist needs

Practical Motorist Annual

now on sale 3/6

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

IR5 5/6	DY86 5/3	EY86 5/9	PL500 12/9
IS5 4/8	DY87 5/3	EZ80 8/9	PL504 12/3
IT4 2/9	EAB80 5/9	EZ81 4/6	PY32 10/-
384 5/9	EBC41 8/-	KT61 8/3	PY33 10/-
3V4 5/9	EBF80 6/-	KT66 15/9	PY81 5/-
6AQ5 4/6	EBF89 5/9	N78 14/8	PY82 5/-
6L18 6/-	ECC81 8/9	PAB80 6/9	PY83 5/3
30C18 8/6	ECC82 4/-	PC86 10/3	PY88 6/-
30FL1 13/6	ECC83 4/9	PC88 10/3	PY800 7/3
30FL12 14/3	ECC85 5/6	PC97 7/9	PY801 6/6
30FL14 11/9	ECH35 5/6	PC900 7/6	R19 6/3
30P4 11/6	ECH42 10/6	PCC84 6/3	U25 12/9
30P19 11/6	ECH81 5/9	PCC89 9/9	U26 11/6
30PL1 13/6	ECL80 6/3	PCC89 9/9	U191 12/3
CCH35 9/9	ECL82 6/3	PCF80 6/3	UAB80 8/9
CL33 17/6	ECL86 7/6	PCF801 8/6	UBC41 8/3
DAC32 6/9	EF37A 6/-	PCF805 8/6	UBF89 6/3
DAF91 4/3	EF39 4/6	PCF808 11/9	UCC84 7/9
DAF96 6/3	EF80 4/9	PCL82 6/9	UCC85 6/6
DF33 7/6	EF85 5/9	PCL83 8/9	UCF80 8/-
DF91 2/9	EF86 6/3	PCL84 7/-	UCH42 10/6
DF96 5/11	EF89 4/9	PCL85 8/9	UCH81 7/-
DK32 6/9	EF183 5/9	PCL86 8/3	UCL82 6/9
DK91 5/6	EF184 5/3	PCL20011/9	UF41 9/6
DK96 6/9	EH90 6/3	PL36 9/3	UF89 6/6
DL35 4/9	EL33 8/3	PL81 7/-	UL41 10/3
DL92 5/9	EL41 10/3	PL82 6/9	UL84 6/9
DL94 5/9	EL84 4/9	PL83 6/9	UY41 6/6
DL96 6/9	EY51 7/3	PL84 6/3	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16



ELECTRAMA

FANTASTIC SPEAKER BARGAIN

Famous English, 12" high flux, heavy cone, 10 watts speaker with built-in tweeter, 3 or 15 ohms. P. & I. 4/9
Two for 88/-, post 6/9 **35/6**

HI-FI HORN 10 watts

Add this 16 ohms unit to your existing speaker system and create real live sound! ONLY **25/6**
P. & I. 3/6
Variable cross-over unit 22/6 P. & I. 2/6



DIAMOND Cartridge makes an

assures quality reproduction of sound. Mono

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

HI-FI PICK-UP

Your reproduction is only as good as your pick-up. Our diamond turnover unit assures quality reproduction of sound. Mono

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

16/- or Stereo 28/- P. & I. 1/9

Send for catalogue price 6d.
Dept. PW87, 1 George St., Hailsham, Sussex

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS



FANTASTICALLY POPULAR ★ TAPE ★

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more pence than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
6in. 900ft.	10/6	6in. 1,200ft.	13/6
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/6
4in. 600ft.	8/-	5in. 1,800ft.	25/6
5in. 1,200ft.	15/6	6in. 2,400ft.	34/6
6in. 1,800ft.	19/6	7in. 3,600ft.	44/6
7in. 2,400ft.	27/6	8in. 4,800ft.	54/6

Postages 1/- each.
Post Free less 5% on three reels.
Quantity and Trade enquiries invited.
NOTE: Large tape stocks at all branches.

TUBES

Highest Quality— Compare Our Prices	
GUARANTEED	
Carr. & Ins.	12 Months
12/6	6 Months
14in.	\$2.10.0
17in. & 19in.	\$3.5.0
21in. & 23in.	\$3.15.0

SATISFACTION GUARANTEED
Most Mullard, Mazda, Cossor, Emitron, Emiscope, Brimar, Ferranti types processed in our own factory.
NOTE: ALL tube orders only to Portsmouth branch please.

NEW and SPECIAL Lines at the keenest prices

AM/FM STEREO MULTIPLEX RECEIVERS
18 transistors, 9 diodes, 1 variable diode, 2 Silicon Rectifiers. Push-pull Stereo Amplifiers. FM Stereo Reproduction 15dB. AM Medium Wave 180-550 Metres. Power output 10W R.M.S., 220V/240V A/C Mains. Beautiful wooden plinth case—approximately 15"(w) x 6"(h) x 9"(d). Controls: Function Switch, Balance, Base/Treble Control, Volume, Tuning. Fine finish. Special purchase enables us to offer these superb machines of famous make at a ridiculously low price. Unrepeatable offer at a fraction of list price . . . only 26 GNS. POST FREE.

SHARP RD504 Mains Battery Tape Recorder, List 26 gns	28 gns
HITACHI Marine D/P Receivers SW/MAR/RW/LW	27 gns
GARRARD 1025 Changers with Stereo Cartridge	£8 10s
JASON 12in. Diecast full range twin cone Speakers	£4 10s
AJAX Mains/Battery, AM/FM larger Radio	12 gns
WELESMERE AM/FM High Sensitivity Black Leather	7 gns
HITACHI WB37E All-Wave, full size. Excellent Short Wave	13 gns
HI-FI By Leak, Wharfedale, Goodmans, WB, Dulci, Arona, Teleton, etc., etc.	

All items previously advertised available. Huge Hi-Fi and Component stocks at all branches. Please call and view without obligation.



RETAIL BRANCHES:
LONDON, 10 Tottenham Court Rd. (MUS 2639)
PORTSMOUTH, 350-352 Fratton Road (Tel. 22034)
SOUTHAMPTON, 72 East Street (Tel. 25851)
BRIGHTON, 6 Queen's Road (Tel. 23975)

MAIL ORDER WAREHOUSE:
Devonian Court, Park Crescent Place, Brighton. (Tel. 680722)

BARGAIN PARCELS
Including variable condensers, i.f. coils, loudspeaker plug/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we now pack them in several sizes—be amazed—try one now.
3 lbs. (post 3/-) 9/-
7 lbs. (post 5/-) 17/6
14 lbs. (post 6/-) 29/-

www.americanradiohistory.com

VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications— Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elem.
Electrical Science — Electri-
cal Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng.—
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work—Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

**WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.
OF EDUCATION, ETC.

British Institute of Engineering Technology

453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT
CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theore-
tic Course for beginners in
Radio, T.V., Electronics, Etc
A.M.I.E.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS

The specialist Elec-
tronics Division of
B.I.E.T.
NOW offers you a
real laboratory train-
ing at home with
practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading
"ENGINEERING OPPORTUNI-
TIES", and if you are earning less than
£30 a week you should send for your
copy *now*—FREE and without
obligation.

POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING
OPPORTUNITIES." I am interested in (state subject,
exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE



THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE—HIGH FIDELITY AUDIO EQUIPMENT


Mono or Stereo Audio. Equipment developed from Dinsdale MkII—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM £15.5.0

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately

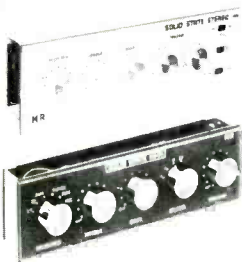SEND FOR FREE BROCHURE (No. 21) TODAY! DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



for complete listening satisfaction choose either the—

INTEGRATED TRANSISTOR AMPLIFIERS

6 WATTS MONO OR 12 WATTS STEREO

We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways—with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.

MAY MONO OR STEREO Mains £8.10.0 POST PACKING EITHER MODEL £16.10.0 OPTIONAL MAINS UNIT PS20 £2.60 pp 4.

Illustrated leaflets 12 and 14 FREE on request



DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tuneable

on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.

TOTAL COST £6.19.6. P.P. 4/6 TO BUILD Send for Brochure 1



NEW MODELS NOMBREX TRANSISTORISED

Test Equipment PRICE Leaflet

MODEL	£ s. d.	No.
29s R.F. Generator	21 0 0	35
29s Aial R.F. Generator	29 10 0	35
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	26
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	29

ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS

The MAYFAIR Acclaimed by everyone


A completely new development in portable electronic musical instruments and a new field for the home constructor. The MAYFAIR produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. It includes 155 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle.

THE MAYFAIR 99 GNS BROCHURE 9



The GROSVENOR

The Grosvenor is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises two four-octave (49 note) keyboards and a thirteen-note pedal board. It has four pitches (i.e. 8, 4, 2, 1) on the upper or solo keyboard, three pitches (i.e. 16, 8, 4) on the lower or accompaniment keyboard, two pitches (i.e. 16, 8) on the pedal board. Variable sustain on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and kit sections are available separately including the Oak Console at £66.18.0

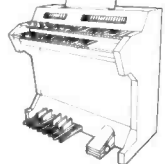

THE GROSVENOR KITS FROM £220 terms available BROCHURE 9B

A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service and advice freely available. Once built the 'MAYFAIR' or 'GROSVENOR' will then provide years of enjoyable entertainment. Call in—See them for yourself.

PRACTICAL ELECTRONICS—ELECTRONIC ORGAN KIT

We are able to supply Parts as described in this series. Details on request

ORGAN COMPONENTS: COMPLETE RANGE IN STOCK • 49 AND 61 NOTE KEYBOARDS • 2 TO 5 PAIR GOLD CONTACTS • COILS AND CHOKES • REVERBERATION SPRINGS AND UNITS • STOP TABS AND ASSEMBLIES • PEDAL BOARDS • RHODIUM AND GOLD CLAD WIRE. ALSO PRINTED CIRCUITS ETC. COMPLETE RANGES FOR TRANSISTORISED ORGANS. ASK FOR NEW PRICE LISTS WITH DETAILS LEAFLET 9B ALL ENQUIRIES TO: ORGAN DEPT.—MR. ELVINS

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses. Intercoms, Baby Alarms, Guitar Practice, Telephone or Record Player Amplifier. Optional Resin covered Wood cabinet 12 x 8 x 4, £16. 1 x 4 in. speaker, £7/4 Uses PP9 battery.




QUALITY CAR RADIOS

A precision engineered car radio that's perfect company for long hours on the road. Quick push-button operation for immediate station selection and choice of Medium or Long wave frequency. Output of 35 watts ensures crisp, top quality sound even at high motorway speeds. Includes full accessories and instructions.

POSITIVE/NEGATIVE EARTH PRICE £12.12.0 pp 4/6 MANUAL as above £18.6.0 but with single MW/LW Push Button.

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNADOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.

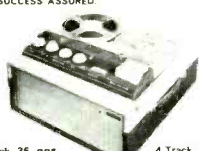

2 Track 36 gns. P.P. 2/6 silver model. Kit comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1 200 ft. tape, spare spool. ALL UNITS AVAILABLE SEPARATELY. ASK FOR BROCHURE 6. Today's Value £46.

VHF FM SUPERHET TUNER MKII

5 MULLARD TRANSISTORS 4 x DIODES 300 KVA BANDWIDTH PRINTED CIRCUIT CONSTRUCTION HIGH FIDELITY REPRODUCTION MONO AND STEREO

A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and, with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability, economically priced. PARTS TOTAL COST £6.19.6. DECODER £3.9.6. (CABINET 20/-) ASK FOR LEAFLET 3



NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES

RM12 1.35 with 3000 mAH output size 2 1/2 dia. • RM25 1.35 with 350 mAH output size 1 1/2 dia. Pack of 8, Size 2 1/2 x 1 1/2. OUR PRICE 10/- each. Easily split into eight 1.25v. cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITIES AVAILABLE.



GARRARD RECORD DECKS

ALL BRAND NEW at huge savings

	£ s. d.
2025 Mono/Stereo GKS 25	8 8 0
3000 LM Mono/Stereo 9 TAHC	9 19 6
SP25 Mk II	11 19 6
AT60 Mk II	13 0 0
AP75	19 0 0
SL55	11 19 6
SL65	14 14 0
SL75	29 0 0
SL95	36 0 0
A70 Mk II	12 12 0
B.S.R. UA25 Mono	6 19 6
B.S.R. MA65	9 19 6
B.S.R. MA70	12 12 0
B.S.R. MA75	16 10 0
401 Garrard	28 10 0

Carriage/Packing 7/6d. all models. Complete range of accessories available. Send for New 8 page brochures 16/17

TRANSISTORS—SEMICONDUCTORS

MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY, SEMI-CONDUCTOR BULLETIN listing over 300 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY, WRITE TO US (on Company Headed Newspaper please) requesting our SEMI-CONDUCTOR BULLETIN. FOR TELEPHONE QUOTATIONS, PHONE (01) 723 1008/9 Extn. 4 (01) 723 0401 Extn. 4.

We purchase medium to large quantities of Transistors and Devices excess to Manufacturers' and Distributors' requirements. Write or Phone Extn. 4.

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY. (list 36)

S.C.R.'s from 5/- Field Effect Transistors from 7/6 Power Transistors from 5/- Diodes and Rectifiers from 1/-


HI-FI equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE ROAD AND SAVE UP TO £25 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE for all leading makes

AMPLIFIERS
TUNERS
DECKS
SPEAKERS
MICROPHONES
TEST EQUIPMENT
HEADPHONES
CARTRIDGES, etc.

All with Terrific Savings

It will PAY YOU to pay us a VISIT!

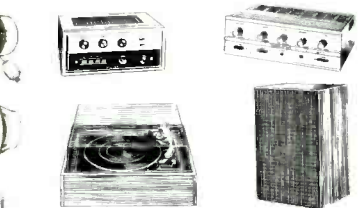

COMPLETE SYSTEMS from £46—Saves £12.10.0! SEND FOR NEW 8-PAGE ILLUSTRATED HI-FI LIST 16/17

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10 - worth discount vouchers FREE WITH EVERY COPY
• 32 pages of transistors and semi-conductor devices, valves and crystals.
• 210 pages of components and equipment.
• 70 pages of microphones, decks and Hi-Fi equipment.



6,500 ITEMS

320 BIG PAGES

Send today 7/6 Post etc 2/-

HENRY'S RADIO LTD HR

OPEN MON.-SAT. 9 a.m.-6 p.m. THURS. 9 a.m.-1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9 309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963