

PRACTICAL WIRELESS

OCTOBER
1969

310

AUDIO SIGNAL GENERATOR



also inside: **PRINTED CIRCUIT DESIGN**

ADCOLA
PRODUCTS LIMITED
 (Regd Trade Mark)

THE RELIABLE SOLDERING INSTRUMENT!



SEND COUPON FOR LATEST LEAFLET

ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD
LONDON SW4

NAME

ADDRESS


PW174

JACKSON

the big name in PRECISION components
MINIATURE TUNING CAPACITORS

The Jackson 'O' range contains six basic types of different air-dielectric tuning capacitors with a wide variation of capacities available in each type. In addition, there are optional extras such as concentric-spindle slow-motion drives, built-in trimmers and plastic covers. The maximum capacitance per section ranges from 12, 18 or 24 pF for FM types to 420 pF for AM types.

TYPE "OO"

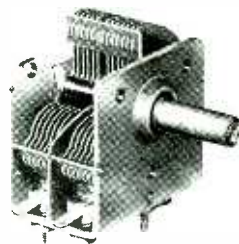


- ★ Type OO miniature twin capacitor at 12/6 each
- ★ Type OFM two-gang for FM at 12/9 each
- ★ Type O two-gang for AM at 12/9 each

Write for literature

JACKSON BROS. (LONDON) LTD. (Dept. P.W.)
 KINGSWAY-WADDON, CROYDON, CR9 4DG
 Phone Croydon 2754-5 (01-688) Grams: Walfilco, Croydon
 U.S. Office:—M. SWEDGAL
 258 Broadway, New York. N.Y. 10007

PHOTOELECTRIC KIT

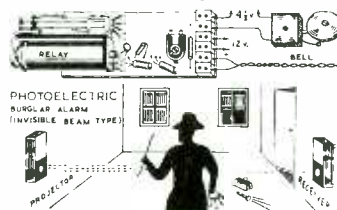CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage and Pack. 2/6 (UK)
 Commonwealth:
 SURFACE MAIL 3/6
 AIR MAIL £1.0.0
 Australia, New Zealand
 S. Africa, Canada and U.S.A.
 Also Essential Data Circuits
 and Plans for Building
 10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.


Lasky's

AMAZING VALUE AD-309K PICK-UP ARM

FITTED WITH
AD-76K CARTRIDGE

This new AUDIO DEVELOPMENT precision counterbalanced pick-up arm—ready fitted with the outstanding AD-76K magnetic cartridge—offers a truly remarkable breakthrough in quality and value for the Hi-Fi enthusiast. The arm is constructed of brass throughout, heavily chrome plated; uses needle and miniature ball race bearings; both coarse and fine balance adjustment is provided. The fixed head has standard 1/4 in. mounting centres and is finished in black enamel with chrome lifting handle. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 1/4 in. dia. mounting hole. Completely wired, with all fixing nuts and washers. Arm rest also supplied.

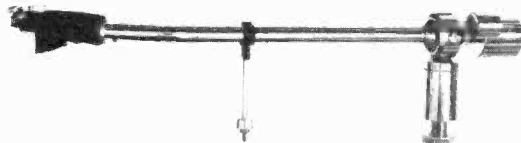BRIEF DETAILS OF AD-76K. Magnetic cartridges: High compliance with stereo diamond LP stylus/Output 5mV, frequency response: 20-20KHz, tracking weight 2 grammes.



LASKY'S PRICE £9.19.6 Post 5/-

TMK METER KITS ANOTHER LASKY'S EXCLUSIVE

These two meter kits by TMK offer both the professional, electronics hobbyist and student the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The impact resistant bakelite cabinets are supplied with the meter scale and movement mounted in position; the model 200 also has the rotary range selector in position.



MODEL 200 20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3 x 2 1/2 in. meter. Full scale accuracy: DCV and current: ±2%, ACV: ±3%, resistance ±3%. Special 0-6V DC range for transistor circuit measurements.

LASKY'S PRICE 85/- Post 3/6

MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES



A highly reliable instrument using an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is clearly indicated on the actual meter face facilitating instant identification without taking your eyes from the meter. High speed rotary range selection knob; also features polarity reversal switch, shielded meter movement with overload protection circuit; Special uA and mA measurement ranges.

SPECIFICATION ● DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0.25-125-500V at 50K/OPV. ● ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. ● DCuA: 0-25uA at 125mV. 0-50uA at 250mV. ● DCmA: 0-2-5-25-250mA at 125mV. 0-5-50-500mA at 250mV. ● DC Amps: 0-5A at 125mV. 0-10A at 250mV. ● Resistance: 0-10M/ohms (13, 65, 650, 6.5K and 65K/ohms at centre scale). ● Output: Capacitor (0-1uF, 400VW) in series with ACV ranges. ● Decibels: -20 to +81.5dB in 10 ranges. ● Operates on two 1.5V (U7 type) batteries. Black bakelite cabinet, size 5 1/2 x 6 1/2 x 2 1/2 in. Strong, resilient plastic handle. Complete with test leads.


LASKY'S PRICE £10.10.0 Post 5/-

ALSO AVAILABLE READY BUILT AND TESTED £18.10.0. Post 5/-.

Garrard

SP25 MkII

**LASKY'S
PRICE £11.19.6**

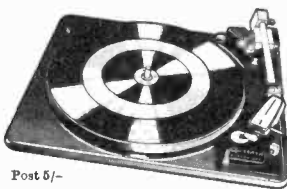

AUTOCHANGERS
1025 less cartridge .. £8.98
1025 with GCM21 mono cartridge. Stereo compat. .. £8.19.6
2025TC with GCM21 mono cartridge. Stereo compat. .. £7.19.6
SL55 with J2006 stereo cartridge .. £11.19.6
SL65 less cartridge .. £14.15.0
SL75 less cartridge .. £28.10.0
SL85 less cartridge .. £35.0.0
A70 Mk II less cartridge .. £13.19.6
AT 60 Mk II .. £13.5.0
BBR UA47 less cartridge .. £5.98
SINGLE PLAYERS
AP75 with AD.88K magnetic .. £21.10.0

cartridge .. £21.10.0
AP75 less cartridge .. £18.10.0
SRP22 Mains model less cartridge .. £18.12.10
SRP22 Battery model less cartridge .. £7.15.3
TRANSCRIPTION DECKS
401 .. £28.10.0
GARRARD BASES
WB1 £3.6.11; WB4 Mk II £5.8.11; WB5 £5.8.11
CLEARVIEW PERSEPEX COVERS:
SPC1 £3.5.0; SPC4 Mk II £4.6.6
Postage on all above 5/-


tion. The highest quality components and 1% tolerance resistors are used throughout. Both offer professional standards of accuracy. Supplied complete in every detail with full constructional, circuit and operating instructions.

SPECIFICATION

● DCV: 0-0.6-6-30-120-600-1200V at 20K/OPV.
● ACV: 0-6-30-120-600 1200V at 10K/OPV. ● DC Current: 0-0.06-6-60-600mA. ● Resistance: 0-10K-100K-1M-10M ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0-002-0.2uF (AC 6V range). ● Decibels: -20 to +83dB. ● Output: 0.05uF blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet—Size: 5 1/2 x 3 1/2 x 1 1/2 in. Complete with test leads.

DENSHI BOARD KITS NEW EXPERIMENTAL AND EDUCATIONAL CIRCUIT SYSTEM

The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study. In addition each DENSHI BOARD KIT comes complete with an 80 page manual of circuits and data.

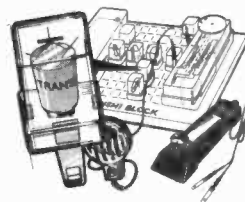

THESE ARE JUST A FEW OF THE CIRCUITS YOU CAN BUILD IN MINUTES:
VARIOUS RADIO RECEIVERS, AMPLIFIERS, MORSE CODE PRACTICE DEVICE, CONTINUITY TESTER, SIGNAL INJECTOR, SIGNAL TRACER, WIRELESS MICROPHONE ETC., ETC.

DENSHI BOARD KIT SR-1A comprises:

Base board; tuner block; 4 resistors; choke coil; transformer; 28A transistor for RF; 2 diodes; 3 capacitors; battery block; morse key; antenna lead; crystal earphone; various bridge and connecting pieces and 80 page manual. This kit permits the building of 16 basic circuits.

Post 3/6

LASKY'S PRICE £4.19.6 Post 3/6

DENSHI BOARD KIT SR-2A as SR-1A but with the following additional parts; 28B transistor for AF; 2 resistors; 1 capacitor; crystal microphone; test probes; electrode additional connecting pieces; 9V battery. This kit permits the building of 30 basic circuits.

LASKY'S PRICE £7.2.6 Post 2/6

GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL

16 colour page catalogue in large 16 x 11 in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test Equipment, Components etc., etc.

Send 1/- for post only and inclusion on our regular mailing list (5/- overseas)

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2

Tel. 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1

Tel. 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4

Tel. 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1

Tel. 01-580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2

Tel. 01-723 9789


Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1

Tel.: 01-790 4821



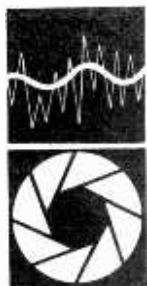the
1969
INTERNATIONAL
audio
festival
&
Photo-Cine
FAIRS
OCTOBER
16-22



Hear and compare the world's finest sound producing equipment for the home. The top loudspeakers, amplifiers, tape-recorders, pick-ups, tapes and accessories have been brought together under one roof to give you a superb Festival of Sound and Sight. Both newcomer and expert . . . everyone who takes pleasure in using and listening to Hi-Fi equipment of the Highest Standard must visit this International Audio Fair.

Lovers of music of all types, if they are true to their enthusiasm, can hear for themselves, how exactly and faithfully their favourite passage can be played back to them.

Admission 4/-

OLYMPIA

10 a.m.—9 p.m.

Not Sunday

London W14


17in.—£11.10.0
19in. SLIMLINE
SOBELL—24 Gns.

TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS


FREE ILLUSTRATED
LIST OF TELEVISIONS
17"—19"—21"—23"
WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

TWO-YEAR GUARANTEED
REGUNNED TUBES

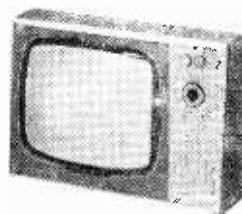70° and 90° 14in.—£9/6, 17in.—£9/6, 21in.—
£9/6, 110° 17in., 19in. and 21in.—£9/6.
23° (not bonded)—£11/6. Exchanged bowls.
Carr. 10/6.



COCKTAIL/STEREOGRAM CABINET 19 gns.

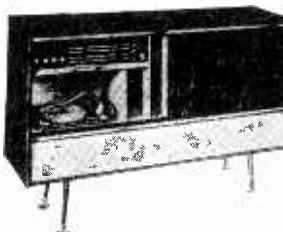

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35½in., width 52½in., depth 14½in. Legs 1 gn. extra.

Speakers 6/6: 2"—75Ω. 2½"—35Ω. P. & P. 2/6. Acos Mics. 35/- Standard: Stick Mic. 2 gns. P. & P. 3/6. Asstd. Condensers: 10/- for 50. P. & P. 7/6. Asstd. Resistors: 10/- for 50. P. & P. 4/6. Asstd. Controls: 10/- for 25. P. & P. 7/6. Transistors: Mullard matched output klt 9/- OC81D—2 OC81's. P. & P. FREE.

Ferrite Rods 3/6: 6", 8" x ¾" complete with LW/MW Coils. P. & P. FREE.

TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9½"x6½"x3¼" P. & P. 4/6. Similar cases in plastic 7/6.

RECORD PLAYER CABINETS 49/6. Cloth covered, size 16½"x14½"x8". Takes any modern autochanger. P. & P. 7/6.

SINGLE PLAYER CABINETS 19/6. P. & P. 7/6.

STRIP LIGHT TUBES 3/9 each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

Lasky's

NEW SCOOP

THE
ASTRAD ORION
THE WORLD'S
SMALLEST
6 TRANSISTOR
TWO WAVEBAND
RADIO RECEIVER
FROM RUSSIA



Made to the highest Russian space-age standard—this remarkable micro-size set measures only 1 11/16 x 1 3/10 x 5 5/16in. yet it contains 6 transistors and other components combined in a photo etched circuit, only ½ x ½in.; tuning capacitor, ferrite rod (or core) aerial, battery, wave band selection, switch etc. Output to a high impedance, crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec. Waveband coverage—Medium wave 525 to 1605kc/s. Long wave 150kc/s to 408kc/s. Sensitivity: 35mV max. Selectivity—10dB (at 30kc/s de-tuning). Power consumption 4mA max. Power source: 1 x 1.4V Mercury battery (Mallory type RM625 or equivalent).

The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic presentation/carrying case (matching the Orion). Never miss your favourite music, sport, news—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others. Lasky's price 39/6 Post 2/- Extra battery (rechargeable type) available.

*NOTE: The battery we supply with the Orion is a rechargeable type. Charger units will shortly be available enabling you to recharge the battery from AC Mains 220/240V supply. Price 19/6—post free if ordered now with radio—otherwise 2/-. If you purchase your charger now we will forward as soon as stocks arrive.

LASKY'S RADIO LTD., 3-15 Cavell St., London E.1
See our other advert for list of London branches

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1

Tel: 01-636 3451



SPECIAL OFFER OF SHURE STEREO CARTRIDGES

Look at our special prices!

M3D	List £8.10.8.	Premier Price £6.19.6
M44-5	List £14.9.1.	Premier Price £11.11.0
M44C	List £12.19.5.	Premier Price £10.10.0
M44E	List £17.8.4.	Premier Price £13.18.6
M55E	List £20.15.1.	Premier Price £16.19.6
M75-6	List £17.8.4.	Premier Price £13.19.6
M75E	List £25.18.10.	Premier Price £21.0.0

Post and Packing 1/6 each

"NOVA" TRANSISTOR STEREO AMPLIFIER

A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 10 watts per channel. Frequency response 40-20,000 Hz $\pm$ 3dB. Inputs for radio, P.U. Ceramic, P.T. Magnetic Tape. Separate bass and treble controls. Volume and Balance controls Mono/Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14 1/2" x 8 1/2" x 3 1/2". A.C. 200/250V.



WONDERFUL VALUE AT ONLY 25 Gns. Carr. 10/-

PICK-UP CARTRIDGES AT MONEY SAVING PRICES!

GOLDRING G800 (Stereo)	£8.19.6
SONOTONE 9TAHC/D (Stereo)	£2.15.0
ACOS GP91/18C (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94 (Stereo)	£2.14.8
B 8 R X3M (Mono compatible)	£1.16.5
B 8 R X3H (Mono compatible)	£1.16.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

COMPLETE STEREO SYSTEM

FOR ONLY **39 GNS**
CARRIAGE 35/-



The Premier Stereo System consists of an all transistor stereo amplifier. Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dukel, Wharfedale, Goodmans, Goldring, Shure, etc. etc.



E.M.I. 13 x 8 in. HI-FI SPEAKERS

Fitted two 2 1/2 in. tweeters and crossover network. Impedance 3 and 15 ohms. Handling capacity 10 watts. Brand new. 99/6, p. & p. 7/6.

Also available without tweeters 49/6, p. & p. 7/6.

TEAK FINISHED CABINET
Size 17 1/2 x 10 x 7 1/2 in. Ideal for above speakers £5.10.0, p. & p. 10/-



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

59/6

P. & P. 5/-
MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-.
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-.

VERITAS V149 MIXER


Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplug output. Attractive teak wood grain finish case.



MONO 59/6 STEREO 69/6 P. & P. 2/6.

VERITAS V313 TAPE HEAD DEFLUXER

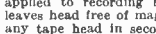A must for all tape users! Tape heads become permanently magnetized with constant use: this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



34/6 P. & P. 1/6.

SPECIAL PURCHASE

EKCO "EXPLORER" CAR RADIO

Frustrated Export Order! A truly dependable and selective car radio giving world-wide reception. 8 transistor. 12v. P. or Neg earth operation. 9 wavebands—MW 135-570 metres and 88.5-108.0 Mc/s—17.9 Mc/s (90, 60, 49, 41, 31, 25, 19, 16 Metre Bands). Size 2 in. high x 7 in. wide x 5 1/2 in. deep. Original price £35. OUR PRICE 21 GNS. P. & P. 7/6. (Suitable Philips Speaker, baffle and brackets £2.13.0. P. & P. 5/-)

MULTI TESTERS




MODEL D14. A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltage in three ranges of 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. Size only: 3 1/2" x 2 1/2" x 1 1/2". Complete with battery, test leads and instructions. 49/6 P. & P. 2/6.



POCKET SIZE MODEL. With wide-angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts DC. 0-10-60-100-600-1000 volts AC. 0-50 μ A-2.5 mA-250 mA DC. 0-6000 ohms-6 megohms, 10 μ A-0-001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. £4.19.6 P. & P. 3/6.

TWO STATION TRANSISTOR INTERCOMS.

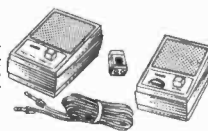Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. 65/- P. & P. 4/-.



FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6. P. & P. 5/6.

"PREMIER" TAPE CASSETTES



C60 (60 min.)	7/6
C90 (90 min.)	12/6
C120 (120 min.)	17/6

P. & P. 1/-.



CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 11/6 P. & P. 1/-

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed

LP3 3" 250'	P.V.C.	5/8	LP6 5 1/2" 1200'	P.V.C.	12/6
TT3 3" 450'	POLYESTER	7/8	DT6 5 1/2" 1800'	POLYESTER	22/6
DT3 3 1/2" 600'	POLYESTER	11/6	TT6 5 1/2" 2400'	POLYESTER	37/6
SP5 5" 600'	P.V.C.	8/8	SP7 7" 1200'	P.V.C.	12/6
LP5 5" 900'	P.V.C.	10/-	DT7 7" 2400'	POLYESTER	25/-
DT5 5" 1200'	POLYESTER	15/-	TT7 7" 3600'	POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5" 5/-, 7" 1/9. TAPE CASES 5" 7" 2/6.

Post and Packing 3" 1/-, 5" 5/-, 7" 1/9. (3 reels and over Post Free).



a complete stereo system for only 28 gns!



The Duetto

Integrated Transistor Stereo Amplifier

9 Gns.
+ 7/6 p & p

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

Specification: R.M.S. power output: 3 watts per channel into 10 ohms speakers. **Input Sensitivity:** Suitable for medium or high output crystal cartridges and tuners. Crosstalk better than 30dB at 1Kc/s. **Controls:** 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control. **Tone Control:** Treble lift and cut. Separate on/off switch. A preset balance control.



The Duo

4 Gns.
+ 7/6 p & p

The new Duo general purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 Specification: Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2 1/2" tweeter. Teak finish. 12" x 6 1/2" x 5 1/2", 4 gns each, p & p 7/6. Type 2 as Type 1. Size 17 1/2" x 10 1/2" x 6 1/2". Incorporating Elac 10 1/2" x 6 1/2", 10,000 lines & 2 1/2" tweeter. 3 ohms impedance.

5 1/2 gns p & p 7/6

Garrard Changers from £7.19.6 p & p 7/6
Cover & Teak finish Plinth £4.15.0 p & p 7/6




The Classic

8 1/2 Gns. + 7/6 p & p

Controls: Selector switch Tape speed equalisation switch (3 1/2 and 7 1/2 l.p.s.). Volume. Treble, Bass, 2 position scratch filter and 2 position rumble filter.

Specification: Sensitivities for 10 watt output at 1KHz. **Tape head:** 3mV (at 3 1/2 l.p.s.). **Mag. P.U.:** 2mV. **Cer. P.U.:** 80mV. **Radio:** 100mV. **Aux.:** 100mV. **Tape/Rec. output:** 100mV. Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. **Tone control range:** Bass ± 13dB at 60 Hz. Treble ± 14dB at 15KHz. **Total distortion:** (for 10 watt output) < 1.5%. **Signal noise:** < -60dB. A.C. mains 200-250v. Built and Tested. Size 12 1/2 in. long, 4 1/2 in. deep, 2 1/2 in. high. Teak finished case.

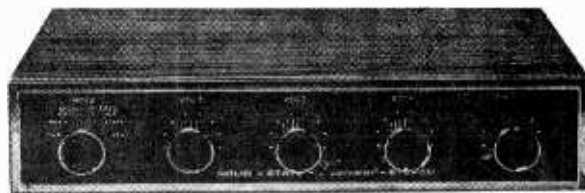

The Viscount

13 1/2 Gns. + 7/6 p & p

Integrated High Fidelity Transistor Stereo Amplifier

Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). **Input:** 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U., Tuner, Tape and Tape Rec. Out. **Sensitivities:** All inputs 100mV into 1.8M ohm. **Frequency Response:** 40Hz-20KHz ± 2dB. **Tone Controls:** Separate bass and treble controls; treble, 13dB lift and cut (at 15KHz); Bass, 15dB lift and 25dB cut (at 60Hz). **Volume Controls:** Separate for each channel. **AC Mains Input:** 200-240v. 50-60Hz. **Size:** 12 1/2" x 6" x 2 1/2" in teak finished case. Built and tested.

SPECIAL OFFER!

Complete stereo system comprising BALFOUR 4-speed autoplayer with stereo head, 2 duo speaker systems, size 12 in. x 6 1/2 in. x 5 1/2 in. Plinth (less cover) and the DUETTO stereo amplifier. All above items

19 gns. plus 20/- p & p

RADIO & TV COMPONENTS (Acton) LTD
Also see opposite page



THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Size: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 EXTRA.

PRICE 5 GNS. + 7/6 p. & p. CIRCUIT 2/6 FREE WITH PARTS.

THE ELEGANT SEVEN MK III (350mW Output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.



EXTRACTOR FAN 27/6

plus 7/6 p.p.

AC mains 230/250v. complete with pull switch. Size 6 x 6 x 4in.

X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0-33 microamp). Total Distortion at 1KHz. at 5 watts 0-35%, at rated output 1-5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V d.c. at 800mA (6-24V may be used).

Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.

2. Treble: PRICE 5/-.

3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:

P101 M (for mono) 35/- plus 4/6 p. & p.

P101 S (for stereo) 42/6 plus 4/6 p. & p.



Price 69/6

plus 2/6 p. & p.

CAR TRANSISTOR IGNITION SYSTEM (by famous manufacturer)

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.). PRICE £4.19.6. (post and packing 5/- extra).

50 WATT AMPLIFIER A.C. MAINS 200-250V




Price 27 gns.

Plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS

3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITIES AND INPUT IMPEDANCES. Channels 1 & 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 & 4 300 mV at 1m. Suitable for most high output instruments (gram, tuner, organ etc.). Input sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60 Hz/s. Bass Cut -13dB at 60 Hz/s. Treble Boost +11dB at 15 KHz/s. Treble Cut -12dB at 15 KHz/s. With bass and treble controls central -3dB points are 30 Hz/s and 20 KHz/s. POWER OUTPUT. For speech and music 50 watts rms. 100 watts peak. For sustained music 40 watts rms. 90 watts peak. For sine wave 38-5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3-2% at 1KHz/s. Total distortion at 20 watts 0-15% at 1KHz/s. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEED BACK 20dB at 1KHz/s. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES. Adjustable from 200-250v. A.C. 50-60 Hz/s. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.

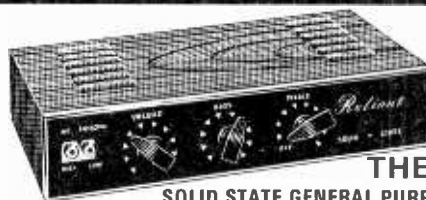

THE RELIANT SOLID STATE GENERAL PURPOSE AMPLIFIER

SPECIFICATIONS

Output—10 watts

Inputs—1. xtm mic 10mV

2. gram/radio 250mV

Output Impedance—3 to 4 ohms

Tone Controls—Treble control range ± 12 dB at 10KHz

Bass control range ± 13 dB at 100Hz

Frequency Response—(with tone controls central) Minus 3dB points are 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220-260V. A.C. Size of chassis—10 1/2" x 4 1/2" x 2 1/2". A.C. Mains, 200-250V. For use with St4, or L.P. records, musical instruments, all makes of pick-ups and makes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested, 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.

Reliant Mark I. 5 1/2 gns. plus 7/6 p. & p.

As above less teak case.

Reliant Mark II. 6 1/2 gns. plus 7/6 p. & p.

In teak finished case.

CYLDON

2 TRANSISTOR U.H.F. TUNER

Brand new. Complete with circuit diagram.

£2.10.0 plus 1/- p. & p.

THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20Kc/s. Size 13 1/4 x 8 1/4 x 4 1/4 inches. By famous manufacturer. List Price £7. Our price 74/6 plus 5/- P. & P. Similar speaker to the above without tweeters in 3 and 15 ohms 44/6 plus 5/- P. & P.

RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and insurance 7/6 extra.



POCKET MULTI-METER

Size 3 1/4 x 2 1/4 x 1 1/4 in. Meter size 2 1/4 x 1 1/4 in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current. 0-150mA. Resistance 0-100K. Complete with test leads, battery and full instructions. 42/6. P. & P. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

B.S.R. TD-2 TAPE DECK

takes 5 1/2 in. spools, fitted with B.S.R.

1/2 Track Heads. Size 13 1/2 in. long by 8 1/2 in.

wide. £6 19s. 6d. plus 7/6 p.p.




MOTEK

3 Speed 2 track Tape Deck complete with heads, takes 7 in. spool.

Incorporating 3 motors.

A.C. mains, 240 volts, listed at £21.0.0.

Our Price £9.19.6, plus 10/- P. & P.

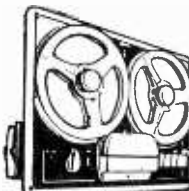

Goods not despatched outside U.K. Terms C.W.O. All enquiries S.A.E.

RADIO & TV COMPONENTS (ACTON) LIMITED

All orders by post to our Acton address

21c High Street, Acton, London, W.3. and also at 323 Edgware Road, London, W.2.

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCA1		9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

AUDIO EFFECTS

5 SHAW LANE, HALIFAX

Buy with confidence and get results. Refund if not delighted.

RHYTHM GENERATOR. 29 silicon transistors and 119 diodes. Finger tip selection of seven instruments in nine basic rhythms in any sequence. Self contained in an attractive case 14 x 13 x 7½ in. Retail at over £74. Our Price Only £66.9.6 plus 10/6 p.p. & ins. S.A.E. for illustrated leaflet.

REVERBERATION AMPLIFIER. Self contained transistorised battery operated. An entirely different approach to sound reproduction. Normally sound reproduction from a single source has a flat one dimensional effect. With this, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar etc., in and the output into your amplifier. Supplied in a beautiful walnut cabinet 7½ x 3 x 4½ in. £10.4.0, p.p. & ins. 6/-.

POWER CONTROLLER. Power at your finger tips. Not just half wave control but full wave. One variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Complete with box, power socket etc. Ideal for flood-lights, fires, motors, etc. In kit form £8.9.6. Ready built £9.4.6 plus 5/6 p.p.

VOX SWITCH KIT. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc., etc. You speak, it switches. High & med imp. inputs. AF take off point. Drives your 12 volt relay. 42/6, p.p. 2/6.

METRONOME KIT. Variable beat. Listen whilst you play and keep in the groove. Easy to build, pocket size with personal mini earphone. 25/-, p.p. 2/6.

MORSE OSCILLATOR KIT. PC board, transistors, (high stab. components, battery carrier, ear piece Adj. tone. Just attach your key. Drives phones or speaker. 15/6, p.p. 2/-.

Free lists with every order. For lists only send 1/- P.O. deductible from first order).

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

The ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v., 7½v. and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½ in. (Extra lead with DIN plug for Cassette Recorders 7/6)



57/6 P. & P. 2/6



45/- P. & P. 2/6

Also available—Unit to run your Cassette Recorder from 12v. Car Battery 32/6. P. & P. 2/6.

MAINS UNIT for FI-CORD 202A TAPE RECORDER P. & P. 5/-

£4.15.0

MAJOR POWER PLUS MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 30/6. For two separate outputs, 4½v + 4½v, 6v + 6v, 9v + 9v, 42/6. P. & P. 2/6 per unit. (Please state outputs reqd.)



R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.). 31 Oliver Road, London, E.17

Learn at home... First Class Radio and TV Courses

get a certificate

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of certificate courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of "Satisfaction or Refund of Fee"

Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.


Founded 1885—Over 150,000 successes

CHAMBERS COLLEGE
(Incorp. National Inst. of Engineering)
(Dept. 885F) 148 Holborn, London, E.C.1.

LIND-AIR OPTRONICS LTD

See our vast range of
Electronic Components
and Accessories at our en-
larged Component Centre
25 Tottenham Court Road

MAINS KEYNECTOR SAVES TIME—SAFELY!

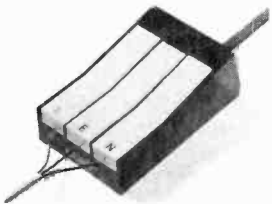

One mains "Keyconnector" instantly and safely connects electrical appliances to mains supply without the use of a plug. A number of appliances may be used simultaneously up to the full 13 amp rating of this device. A red light glows when "live". The "Keyconnector" is fused and has its own robust switch which is interlocked to prevent connections when "live". *Invaluable to handymen, servicemen, demonstrators etc.*

39/6 P. & P. 3/-.

VHF AIRCRAFT BAND CONVERTOR.

When placed within lin. of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistors, 9v battery operation. Fully tunable 15 $\frac{1}{2}$ in. x 7 section telescopic aerial. Size 4 x 2 1/2 in. 79/6. P. & P. 3/6.



MODEL MAKER'S MOTOR
No. 15RM. Voltage 11.5v.
Current 400mA. Torque.
12g.-cm. Body size
1 1/2" long x 1/2" dia.
Shaft 3/16" long x
1/16" dia. Ideal for
small models and
toys. 5/6 each.

P. & P. 1/3. 3 for 15/- P. & P. 2/6.



DE-LUXE STEREO HEADPHONES

With soft rubber
earpieces. Impedance
8-16 ohms. Frequency
response 23-13,000cps.
With lead and stereo
plug.
Only 59/6. P. & P. 3/6.

NEW STEREO/MONO HEADPHONES

SDH-7. Soft rubber
earpieces with slide
switch for mono/
stereo listening and
ind. vol. controls.
Impedance 8-16 ohm
Freq. response 25-
15,000 cps. With lead
and stereo plug.
£6.6.0. P. & P. 3/6.



SINCLAIR IC-10 INTEGRATED CIRCUIT



10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6. P. & P. 1/6.

HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY				
J1001	3"	Long Play PVC	225ft.	5/6 P. & P. 1/3.
J1002	3"	Triple Play Poly	600ft.	10/6 P. & P. 1/3.
J1003	3"	Long Play PVC	900ft.	15/- P. & P. 1/8.
J1004	5"	Double Play Poly	1200ft.	15/- P. & P. 1/8.
J1005	5 1/2"	Long Play PVC	1200ft.	12/6 P. & P. 2/-.
J1006	5 1/2"	Double Play Poly	1800ft.	22/6 P. & P. 2/-.
J1007	7"	Standard Play PVC	1200ft.	12/6 P. & P. 2/6.
J1008	7"	Long Play PVC	1800ft.	17/6 P. & P. 2/6.
J1009	7"	Double Play Poly	2400ft.	25/- P. & P. 2/6.
J1010	7"	Triple Play Poly	3600ft.	50/- P. & P. 2/6.



Visit our Brand New Hi-Fi
Demonstration Room, Tape,
Record Bar and Scientific Show of
Microscopes, Binoculars,
Telescopes and Watches at
18 Tottenham Court Road

TRANSFORMERS

AUTO WOUND TRANSFORMERS

All Winding Voltage Ratings and Tapping 0-115-200-220-240v except MT113-0-115-210-240v.

MT113	20W	Size 2 1/2 x 1 1/2 x 1 1/2 in.	Wgt 11oz	Price 12/6	P & P 2/6
MT154	75W	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb 14oz	Price 21/9	P & P 4/6
MT174	150W	Size 3 1/2 x 2 1/2 x 3 1/2 in.	Wgt 4 1/2 lb	Price 33/-	P & P 6/-
MT65	200W	Size 3 1/2 x 4 1/2 x 4 in.	Wgt 4 1/2 lb	Price 38/6	P & P 6/-
MT66	300W	Size 4 x 4 x 3 1/2 in.	Wgt 6 1/2 lb 7oz	Price 59/4	P & P 9/-
MT110	400W	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 11 1/2 lb	Price 85/-	P & P 10/-
MT67	500W	Size 5 1/2 x 4 1/2 x 4 in.	Wgt 12 1/2 lb 8oz	Price 89/-	P & P 10/6
MT68	750W	Size 6 1/2 x 5 1/2 x 4 1/2 in.	Wgt 13 1/2 lb 4oz	Price 95/7	P & P 10/6
MT64	1000W	Size 6 1/2 x 5 1/2 x 4 1/2 in.	Wgt 16 1/2 lb	Price 142/2	Carr. ex.
MT63	1500W	Size 6 1/2 x 5 1/2 x 4 1/2 in.	Wgt 25 1/2 lb 9oz	Price 170/6	Carr. ex.
MT94	1750W	Size 5 1/2 x 6 1/2 x 6 1/2 in.	Wgt 31 1/2 lb	Price 185/-	Carr. ex.
MT95	2000W	Size 7 x 6 1/2 x 8 1/2 in.	Wgt 40 1/2 lb	Price 211/2	Carr. ex.
MT73	3000W	Size 6 1/2 x 7 1/2 x 8 1/2 in.	Wgt 45 1/2 lb 8oz	Price 300/-	Carr. ex.

LOW VOLTAGE 12 VOLT RANGE

Primary 200-250v. Secondary 12v				
MT111	0.5 Amp	Size 3 x 2 1/2 x 1 1/2 in.	Wgt 1 1/2 lb	Price 15/8 P & P 2/6
MT71	2 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb	Price 19/- P & P 3/6
MT69	4 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 2 1/2 lb 4oz	Price 28/- P & P 6/-
MT70	6 Amp	Size 4 x 3 x 3 1/2 in.	Wgt 3 1/2 lb 12oz	Price 39/- P & P 6/-
MT72	10 Amp	Size 3 1/2 x 4 1/2 x 4 in.	Wgt 6 1/2 lb 3oz	Price 51/- P & P 9/-
MT105	20 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 11 1/2 lb 13oz	Price 95/- P & P 9/-
MT187	30 Amp	Size 6 1/2 x 4 1/2 x 4 in.	Wgt 16 1/2 lb 12oz	Price 180/- P & P 13/6

LOW VOLTAGE 24 VOLT RANGE

Primary 200/250v. Secondary 24v				
MT68	1 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb 7oz	Price 23/9 P & P 4/6
MT114	3 Amp	Size 2 1/2 x 3 x 3 in.	Wgt 3 1/2 lb 8oz	Price 38/- P & P 6/-
MT72	5 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 5 1/2 lb 12oz	Price 58/10 P & P 6/-
MT17	8 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 7 1/2 lb 8oz	Price 72/7 P & P 9/-
MT115	10 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 11 1/2 lb 13oz	Price 95/- P & P 11/-

LOW VOLTAGE 30 VOLT RANGE

Primary 200/250v. Secondary Tapped 12-15-20-24-30				
MT112	0.5 Amp	Size 3 1/2 x 2 1/2 x 1 1/2 in.	Wgt 1 1/2 lb 4oz	Price 17/4 P & P 3/9
MT79	1 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 2 1/2 lb	Price 23/- P & P 6/-
MT20	3 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 4 1/2 lb 6oz	Price 48/2 P & P 6/-
MT61	6 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 6 1/2 lb 8oz	Price 60/9 P & P 9/-
MT62	8 Amp	Size 5 1/2 x 3 1/2 x 4 in.	Wgt 9 1/2 lb 6oz	Price 81/6 P & P 9/-
MT89	10 Amp	Size 6 1/2 x 4 1/2 x 4 in.	Wgt 12 1/2 lb 2oz	Price 103/6 P & P 11/-

LOW VOLTAGE 50 VOLT RANGE

Primary 200-250v. SECONDARY TAPPED 12-25-30-40-50v				
MT102	0.5 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb 11oz	Price 21/8 P & P 6/-
MT104	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 6 1/2 lb	Price 45/8 P & P 6/-
MT106	4 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 9 1/2 lb 4oz	Price 77/- P & P 9/-
MT118	8 Amp	Size 5 1/2 x 5 1/2 x 4 1/2 in.	Wgt 18 1/2 lb 9oz	Price 132/- P & P 13/6
MT119	10 Amp	Size 6 1/2 x 4 1/2 x 6 1/2 in.	Wgt 19 1/2 lb 12oz	Price 165/- P & P 15/6

LOW VOLTAGE 60 VOLT RANGE

Primary 200/250v. Secondary Tapped 24-30-40-48-60				
MT124	0.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 2 1/2 lb 4oz	Price 24/- P & P 6/-
MT127	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 5 1/2 lb 6oz	Price 52/10 P & P 6/-
MT123	4 Amp	Size 4 1/2 x 3 1/2 x 4 1/2 in.	Wgt 10 1/2 lb 6oz	Price 99/- P & P 11/-
MT122	10 Amp	Size 6 1/2 x 5 x 6 1/2 in.	Wgt 23 1/2 lb	Price 152/- Carr. ex.

MAINS H.T. RANGE


Size				
MT1AT	250-0-250v	80MA	6-3v 3-5A 5/6-3v 1A	3 1/2 x 3 x 3in. 33/- 6/-
MT6AT	250-0-250v	100MA	6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in. 38/3 6/-
MT110	250-0-250v	120MA	6-3v 3-5A 5/6-3v 1A	4 x 4 x 3 1/2 in. 44/9 6/-
MT11AT	300-0-300v	100MA	6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in. 37/9 6/-
MT12AT	300-0-300v	120MA	6-3v 4A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in. 46/2 9/-
MT33AT	300-0-300v	150MA	6-3v 4A 5/6-3v 1A	4 x 4 x 3 1/2 in. 59/4 9/-
MT2AT	350-0-350v	80MA	6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in. 38/6 6/-
MT7	350-0-350v	100MA	6-3v 3-5A 5/6-3v 1A	4 x 3 x 3 1/2 in. 42/4 6/-
MT8	350-0-350	120MA	6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in. 50/- 6/-

BATTERY CHARGER TYPES

Primary Voltage 200-250v. Secondary 6-12v.				
MT7	1 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb 6oz	Price 15/- P & P 4/6
MT46	1.5 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 1 1/2 lb 9oz	Price 21/9 P & P 4/6
MT48	2 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 2 1/2 lb 4oz	Price 25/4 P & P 6/-
MT47	3 Amp	Size 4 x 3 x 3 1/2 in.	Wgt 3 1/2 lb 8oz	Price 28/4 P & P 6/-
MT5	4 Amp	Size 4 x 2 1/2 x 3 1/2 in.	Wgt 3 1/2 lb 11oz	Price 33/- P & P 6/-
MT78	5 Amp	Size 4 x 3 x 3 1/2 in.	Wgt 5 1/2 lb 4oz	Price 42/- P & P 6/-
MT86	6 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 5 1/2 lb 12oz	Price 48/- P & P 6/-
MT48	7 Amp	Size 4 x 4 x 3 1/2 in.	Wgt 6 1/2 lb	Price 56/7 P & P 9/-
MT146	8 Amp	Size 3 1/2 x 4 x 4 in.	Wgt 6 1/2 lb 4oz	Price 75/- P & P 9/-
MT49	9 Amp	Size 4 x 3 1/2 x 4 in.	Wgt 7 1/2 lb 8oz	Price 99/- P & P 9/-
MT147	10 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 9 1/2 lb 3oz	Price 105/- P & P 9/-
MT50	12.5 Amp	Size 5 1/2 x 4 1/2 x 4 in.	Wgt 11 1/2 lb 14oz	Price 125/- P & P 11/-


Amperages are D.C. with nominal selenium bridge rectifiers
MAINS ISOLATING RANGE ALSO AVAILABLE

TTG.01001 MULTITESTER in leather case.

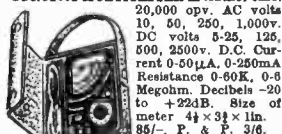

20,000 opv. AC volts
10, 50, 250, 1,000v.
DC volts 5-25, 125,
500, 2500v. D.C. Cur-
rent 5-500 μ A, 0-250mA
Resistance 0-60K, 0-5
Megohm. Decibels -20
to +22dB. Size of
meter 4 1/2 x 3 1/2 x 1 1/2 in.
85/- P. & P. 3/6.

SHIRA 62D MULTI-TESTER 20,000 o.p.v.

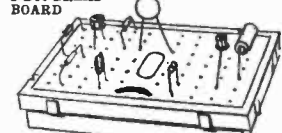

DC voltage: 5-25-50-250-
500-2.5K (20,000 ohms per
volt). AC Voltage: 10-50-
100-500-1000 volts (10,000
ohms per volt). DC Current:
0-500 μ A, 0-2-5mA, 0-
250mA. Resistance: 0-6K,
0-6Mg (300 ohm and 30K
at centre scale). Capacitance: 10pt. to -0.01
mfd, -0.01 μ f to -1 μ f. Decibels: -20 to
+22dB. Size 4 1/2 x 3 1/2 x 1 1/2 in. Complete with
case 77/- P. & P. 3/6.

S-DeC BREAD BOARD

British Made
Solderless breadboard panels, for fast re-
liable component connections.
Single DeCa. One S-DeC with Control
Panel, Jig and Accessories for solderless
connections to controls, etc., with booklet
"Projects on S-DeC" giving construction
details for a variety of circuits. 29/6.
P. & P. 2/6.

GARRARD DECKS



SRP22 less cartridge	£5. 9/6
1025 Stereo/Mono with cart.	£8.19.6
2025 Stereo/Mono with cart.	£7.18.6
3000S Stereo/Mono with cart.	£9.19.6
3000D Stereo/Mono with cart.	£10.19.6
SP25 less cartridge	£11.19.6
SP25 with Decca Derram cart.	£17. 4/6
SL65 less cartridge	£11.19.6
SL65 with Decca Derram cart.	£17.4.6
SL65 less cartridge	£14.9.6
Covers for above	£2.19.6
Bases for above	£2.10.0
AP75 less cartridge	£18.18.0
SL75 less cartridge	£28.7.0
SL95 less cartridge	£38.19.6
Bases for above	£4.19.6

SPECIAL OFFER!

SP25 less cart., with base £18. 2.6
P. & P. Decca 12/6, Cover 4/6, Base 4/6.
P. & P. Deck/Cover/Base 17/-.

MINIATURE SOLDERING IRON

British made and designed for use with
transistor circuitry but ideal for many
other uses. AC 240v. 18 watt. Length
7 1/2 in., 1/4 in. slide on bit. Price 32/6
P. & P. 2/-.



LIND-AIR OPTRONICS LTD
18, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679


Shops open 9-6pm. Monday to Saturday. Thursday until 7pm.

ALL
MAIL ORDERS
To Dept. PW1069,
54a Tottenham
Court Road,
London, W1.

R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

30 WATT OUTPUT
 ★ Goldring Transcription Turntable on Plinth
 ★ Shure or Goldring Magnetic Pick-up Cartridge
 ★ Super 30 Amplifier in veneered housing
 ★ Pair of Stanton Loudspeaker Units
 Special total price. Four fully wired units ready to "plug-in". Carr. 30/-
TERMS AVAILABLE ALL PACKAGE OFFERS

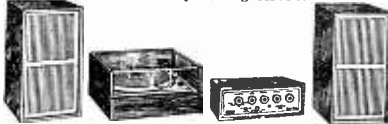Matching as recommended for optimum performance. Send for coloured brochure showing other money saving offers.



30 WATT OUTPUT
 ★ Garrard SP25 Mk II Turntable on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ Super 30 amplifier in veneered housing
 ★ Pair Stanton Speaker Units
 Four fully wired units ready to "plug-in" Special total price **76 Gns.** Carr. 30/-

AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range 40-15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

Prices include carriage.
 HF510L 5" 10W 5/9 HF120L 12" 15W 7/9
 HF801D 8" 10W 5/9 HF120D 12" 15W 8/9
 HF811D 8" 10W 4 gns. HF126 12" 15W 25. 5.0
 HF121D 10" 10W 65/- HF126D 12" 15W 25. 5.0

HIGH FIDELITY LOUSPEAKER UNITS
 Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled woollen damping. Ported where appropriate, credit terms available

DORCHESTER Size 16 x 11 x 9in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. Dual **£8.19.9** Cone spkr. Imp. 3 or 15 ohms Carr. 7/6

STANWAY II Size 20x10x9in. Rating 10 watts. Incorporating Fane 13x8in. speaker with rubber cone surround and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Ported where appropriate, credit terms available

net. Range 35-20,000 c.p.s. Impedance 16 Gns. 15 ohms. Gives smooth realistic sound output. Inc. Carr.

GLOUCESTER Size 25 x 16 x 10in. 12in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 12 1/2 Gns. 40-20,000 c.p.s. Impedance 15 ohms. 2

E2 EQUIPMENT CABINET
 Size 17" wide 14" deep 11" high. Cut for TA12. Super 15. Super 30 and other amplifiers. Roll over transp. plastic cover. Satin Teak or Afrormosia veneer finish. Inc. carr. **8 Gns.**

MOTOR BOARDS cut for Garrard Turntables and many other units. Price **12/9**

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. A.C. mains operated Frequency Response 30-20,000 c.p.s. 2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble Inc. Carr. Or factory built 16i gns. Or in Teak finished cabinet as illustrated 19i gns. Terms: Deposit £5 and 9 monthly payments £2. Total £23.

Or factory built with 12 months guarantee. £8.19.9

EXTREMELY ATTRACTIVE PLINTHS
 finished in Teak or Afrormosia veneer. Transparent plastic "roll over" cover.

RECORD PLAYING UNITS

Money saving units. Ready to plug into Amplifier or Tape Recorder. Consisting of Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on Plinth. Inc. transp. plastic cover. **22 Gns.** Inc. Carr.

RP3 As above but with Goldring Lenco GL68 Transcription unit and CS90 Cartridge. Supplied with transp. plastic cover. **28 Gns.** Inc. Carr.

R.S.C. PLINTHS

for Record Playing units. Teak finish cut for Garrard 2000. **59/9**

3000. AT6. AT60. SP25 etc. Available with transp. plastic cover. Inc. **6 Gns.** Carr. Cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. **39/9**

INTEREST CHARGES REFUNDED on Credit Sales settled in 3 months.

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

Total cost of parts with detailed wiring diagrams & instructions. **14 Gns.** Or factory built 16i gns. Or in Teak finished cabinet as illustrated 19i gns. Terms: Deposit £5 and 9 monthly payments £2. Total £23.

13 WATT OUTPUT

★ Garrard SP25 Mk II 4 sp player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in veneered housing
 ★ Pair of Dorchester Loudspeaker Units. Special total price. Carr. 25/-

Or Dep. £10 and 9 monthly payments £5.11.0. (Total £59.19.0.) Transparent plastic cover 3 gns. extra.

R-S-C TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating I.H.F.M. ★ Handsome brushed silver finish Facia and knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mth gntee **16 Gns** or Deposit **£5.2.6** and 9 mthly pymts **31/6** (Total **£19.6.0**) Or in Teak or Afrormosia veneer housing **19i Gns.** Dep. **£5.10.6** and 9 mthly pymts **39/-**. (Total **£23.1.6**)

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 15,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**

15,000 line Speaker **£6.15.0** Carr. 6/6

HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. Prices Inc. carr.
 JPS Size 16 x 11 x 9in. Pressurised. Gives **£4.10.0**
 pleasing results with any 8in. Hi-Fi speaker.
 SE8 For optimum performance with any 8in. **£5.10.0**
 Hi-Fi speaker. Size 22 x 15 x 9in. Ported.
 SE10 For outstanding results SE12 For exelnt prfmrnce with 12in Hi-Fi speaker. Size 25 x 16 x 10in. **£6.15.0**

R.S.C. SUPER 15 HI-FI AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 10 Watts R.M.S. per chan. cont. into 15 ohms. 15 Watts R.M.S. per chan. cont. into 3-4 ohms. TRANSISTORS, 9 current types of high quality by leading manufacturers. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10 Kc/s. NEG FEEDBACK: 52dB. BASS CONTROL: +17dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.2%. Complete kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6. Supplied factory built 15i Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9). Or in Teak or Afrormosia veneer housing as illustrated. 19 Gns. ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING MANUFACTURERS.

R.S.C. SUPER 30 STEREO AMPLIFIER

SOLID STATE CONSTRUCTION SPECIFICATIONS COMPARABLE WITH UNITS COSTING CONSIDERABLY MORE
 MARK II DUAL CHANNEL VERSION OF THE SUPER 15 Employing Twin Printed Circuits. High quality Gangs. P.M.T. Matched Components. CROSS TALK: -32dB at 1,000 c.p.s. CONTROL: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch, INPUT SOCKETS (Matched Pairs). (1) P.U. (2) Tape Amp. (3) Radio/Aux. (4) Mic. or R.F. Head. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. wide, 3in. high and 8in. deep. Neon Panel Indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15. THESE UNITS ARE ESPECIALLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE SUPER SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/- Unit factory built 28 Gns. or Deposit £7.5.0 and 9 monthly payments 56/8. (Total £32.13.3). Or in veneered housing 31 Gns. Carr. 15/- or Deposit £7.3.6 and 9 monthly payments 64/- (Total £35.19.6). Send S.A.E. for leaflet.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
BIRMINGHAM 30/31 Gt. Western Arcade opp. Snow Hill Station 021-236-1279 (Half-day Wed.)
DERBY 26 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 326 Argyle St. (Half-day Tues.) Tel. City 4158
HULL 91 Paragon Street. (Half-day Thursday) Tel. 20505

R.S.C. HI-FI CENTRES LTD.
MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries please. Open all day Sats.
 32 High Street. (Half-day Thurs.) Tel. 56420 **LEICESTER**
 5-7 County (Mecca) Arcade, Briggate (Half-day Wed) Tel 28252 **LEEDS**
 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**
 106 Newport Rd (Half-day Wed) Tel. 47096 **MIDDLESBROUGH**
 41 Blackett Street (Opp. Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
 13 Exchange Street (Castle Market Bldgs.) (Half day Thursday) Tel. 20716 **SHEFFIELD**

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit
★ Response 30-20,000 c.p.s. Impedance 15 ohms.
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 8-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Woolen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 39/- (Total £23.1.0).

20 Gns.
Carr. 12/6



DEMONSTRATIONS AT ALL BRANCHES

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level - 70dB. Frequency response +3dB 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 38 mV. Suitable for high Impedance microphone or Crystal or Ceramic P.U.s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. Carr. 12/6

Twin-handled perforated cover 27/8. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 gns. TERMS: Deposit £6.3.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram, etc. etc. High sensitivity. 5 valves - ECC83 (2), EL84 (2), E281. High quality sectionally wound output transformer. Bass and TREBLE CONTROLS. Frequency response +3dB 30-20,000 c/s. Hum level - 80dB. SENSITIVITY 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance

For Musical Instruments such as String Bass, Electronic Guitars etc. Size approx. 12 x 8 x 7in. For A.C. mains 200-250V. 50 c/s Output for 3 and 15 ohm speakers. S.A.E. for leaflet. Complete kit. 9/6 Gns. Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built 12/6 gns.). Twin handled metal cover 27/8. TERMS: ON ASSEMBLED UNITS. Deposit 99/6 and 9 monthly payments of 23/- (Total £15.6.0)

RSC A11 TRANSFORMER VERSION OF above complete kit 9 Gns (Assembled 13 Gns)

R.S.C. BASS-REAGENT

50 WATT AMPLIFIER

An exceptionally powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak O/P rating.

★ Two extra heavy duty 12in. Loudspeakers.
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

55 Gns. Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60/1 gns.). Send S.A.E. for leaflet. 6100 100 watt peak output with P.r. speaker columns and a Bass Unit (Six 12" and Two 15" Spkrs). 100 gns

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 in. approx.

Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250V. 50c/s is available. Complete kit with diagram 49/11 or assembled 59/11

SELENIUM RECTIFIERS (Bridged) All 8/12V. D.C. output. Max. A.C. input 18v. Ia. 4/3. 2a. 0/11. 3a. 9/9. Ia. 12/8. 6a. 15/9.

6/12V CAR BATTERY CHARGERS Complete kit of parts with Ammeter and Circuit. Both models with variable charge rate selector. 4 amp 49/9 6 amp 69/9 All types 200-250V. A.C. Mains. Built 10/- extra.

14 WATT HI-FI AMPLIFIERS High sensitivity. Two separate inputs. Two controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, E280. Output for 15 ohm Loudspeaker. 200-250V 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 8in. Factory built and fully guaranteed. Limited number to clear at £7-19-11 10/-

BLACKPOOL

AGENT APPOINTED
O. & C. ELECTRONICS
227 CHURCH ST.

R.S.C.
HI-FI CENTRES LTD.

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair, ideal for vocalists and Public Address. 15 ohm matching. C57 15 watts inc. five 7 x 4in. speakers £7.19.11 TYPE C48S 30W ATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 87/- and 9 mthly pmts 34/9 (Total £18.19.9) Carr. 10/- TYPE C412S 50W ATTS. Fitted four 12in 11,000 line 15 watt 26 Gns. speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- Or Deposit £17.6 and 9 monthly payments of 54/6 (Total £30.7.0).

30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group A 2 or 4 input. 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold perspex facia. Neon indicator. For 200-250V. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 5 gns. and Carr. 15/- 9 mthly payments of 58/8 (Total £25.8.8) 19 Gns. Carr. 12/6



F.A.I. 'Phase Fifty' PUBLIC ADDRESS AMPLIFIER

Solid State Circuitry. 50 Watts Peak Output. 3 separately controlled inputs for mixing purposes. Separate Bass and Treble Controls. Output for loudspeakers 3-30 ohms. Suitable for Dynamic, Ribbon or Crystal Mikes. For Clubs, Theatres, Restaurants, Hotels, Schools, etc. For Vocal or Instrumental Groups. Send S.A.E. for leaflet. only 29 Gns.

HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinets
L13 13" x 8" 10 Watt L12 12" 20 Watt 10,000 lines £8.19.9
10,000 lines £4.19.9 15 ohms Carr. 8/9
3or15ohms Carr. 7/6



FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 year guarantee. High Flux 14,000 line ceramic magnets. Heavy cast chassis.


'POP' 100	'POP' 60	'POP' 50
18" 100 Watt	15" 60 Watt	12" 50 Watt
21 GNS. Carr. free	12 GNS. Carr. free	10 GNS. Carr. free

POWER PACK KIT

Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250V. A.C. mains. Output 250V. 60mA 6.3v. 2a. Supplied with case in lieu of chassis 29/11. Or assembled 39/11. 25/11

MINI-8 HI-FI Loudspeaker Units Special Offer

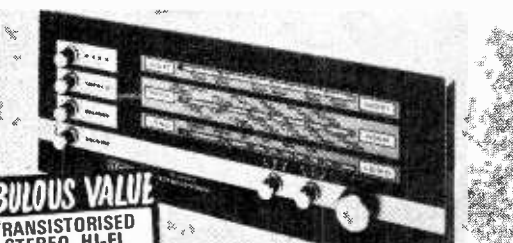Teak or Afrormosia veneered cabinet, size approx. 10 1/2 x 6 1/2 x 7 1/2 in. Peak power handling 8 watts 3 ohms. Inc. Carr. 69/11



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL

NO TECHNICAL KNOWLEDGE REQUIRED

Only 28 Gns. + 1/6 P

H. P. terms available. Dep. £9.18.0 & 12 monthly payments of 38/9 (Total H.P. £31.17.0). Send £10.13.6 today. Amplifier available separately at only 17 Gns.


FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL"

FULLY TRANSISTORISED STEREO PHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer - a complete radiogram at half normal price ONLY

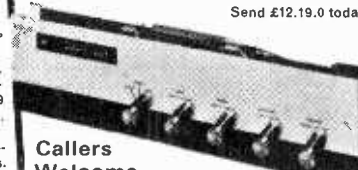10 Watts Total output 17 Transistors & 10 diodes 34 1/2 GNS. 17/6 EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY H.P. available £12.1.6 dep. plus 18 monthly payments of 32/- (Total H.P. £40.17.6)



Callers Welcome

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name _____ Address _____

LEWIS radio 100 CHASE SIDE, SOUTHGATE, DEP. P1069 LONDON, N.14. TELEPHONE PAL 3733/9666

POST THIS COUPON NOW!

BOOKS BY G. A. BRIGGS

OVER A QUARTER OF A MILLION COPIES SOLD
SINCE 1948

AERIAL HANDBOOK (second edition)

176 pages, 144 illustrations.
Price (semi-stiff cover) 15/- (16/6 post free).
Cloth bound 22/6 (24/- post free).



CABINET HANDBOOK

112 pages, 90 illustrations.
Price 7/6 (8/6 post free). Semi-stiff cover.
Cloth bound 15/- (16/6 post free).



AUDIO BIOGRAPHIES

344 pages, 64 contributions from pioneers
and leaders in Audio. Cloth bound.
Price 25/- (27/- post free).



MUSICAL INSTRUMENTS AND AUDIO

240 pages, 212 illustrations. Cloth bound.
Price 32/6 (34/6 post free).



LOUDSPEAKERS

Fifth edition—336 pages, 230 illustrations.
Cloth bound.
Price 30/- (32/6 post free).



A to Z in AUDIO

224 pages, 160 illustrations. Cloth bound.
Price 15/6 (17/- post free).



PIANOS, PIANISTS AND SONICS

190 pages, 102 illustrations. Cloth bound.
Price 18/6 (20/- post free).



AUDIO AND ACOUSTICS

168 pages, 140 illustrations.
Price 12/6 (13/6 post free). Semi-stiff cover.



ABOUT YOUR HEARING

132 pages, 112 illustrations.
Price (semi-stiff cover) 15/6 (16/6 post free).
Cloth bound 22/6 (24/- post free).



LETTERS FROM ABROAD

Feb., 1969

Extract of letter from Mr. Wendell C. Ward of Texas, U.S.A.
September 1968.

I have recently read through Mr. Briggs' book "A to Z in Audio" and found it most interesting. It's refreshing to find a man who can write about what could be a dry subject with enthusiasm and humor.

Extract of letter from Mr. R. G. Bernaldez of Madrid, Spain.

Many thanks for the copy of "About Your Hearing" that you were so kind to send to me. I have found your book to be really interesting. As always, it is puzzling the way you manage to make any subject easy to read, in that delightful style of your own.

Please send orders and enquiries to:

RANK WHARFEDALE BOOK DEPT. B.W.S
13 WELLS ROAD, ILKLEY, YORKSHIRE

Telephone: ILKLEY 4246

Published by
RANK WHARFEDALE LTD., IDLE, BRADFORD, YORKSHIRE

MAINLINE ELECTRONICS LIMITED

Service with the personal touch

Mainline Electronics is a new Service for users of electronic equipment and components in the field of experimental work.

Backed by one of Europe's leading Distributors and enjoying the support of the Industry, Mainline Electronics specialises in quality components from leading manufacturers. These products are characterised by excellent materials and workmanship, proved reliability and known performance. Service is the watchword of Mainline Electronics' activities. The company not only supplies the right components at the right price but, also supplies the necessary data through the data service published in the component guide.

Your Complete Professional Guide to Components and Prices



Send today for Europe's finest, most up-to-date and most comprehensive Price List of Semi-conductors and associated components, with details of manufacturers full application data.

4/-
Post Free

Get this invaluable reference now — to
RCA — IR — SGS —
Emihus — Semitron —
CCL — Plessey —
Morganite — Litesold
to name but a few.

A DOZEN OF THE BEST



70 Watts of Audio

Mainline introduce a trio of amplifiers the Mainline '12', Mainline '25', Mainline '70'. The design of these audio amplifiers was the result of SGS and RCA combining their tremendous resources to produce these quasi circuits.

Each Kit complete with circuit diagram contains all semiconductor — resistors — capacitors and printed circuit board.

Mainline 12A — £7.0.0.
Prices: Mainline 25A — £8.5.0.
Mainline 70A — £10.10.0.

Mainline Electronics Limited,
Thames Avenue, WINDSOR, Berkshire.
(A member of the ECS Group of Companies)

Quality Transistor Radios to build yourself backed by our after sales service

NEW! roamer eight mkl WITH VARIABLE TONE CONTROL


6 Tunable Wavebands: Medium Wave, Long Wave, Trawler Band, SW1, SW2, SW3. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output utilises 600 Mw transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

£6.19.6

Parts Price List and Easy Build Plans 5/- (Free with parts).

P & P 7/6.

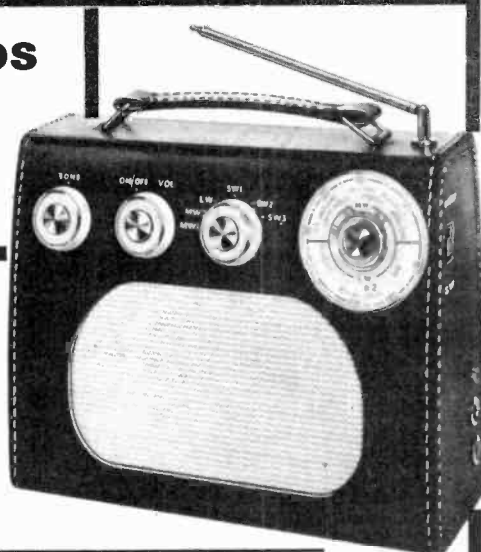

roamer seven mklv

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

£5.19.6

P. & P. 7/6



NEW! trans eight

SIX WAVEBAND
PORTABLE WITH
3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. All top grade components. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts) Earpiece with switched socket for private listening 5/- extra.

Total building costs
P & P 5/6


89'6



pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

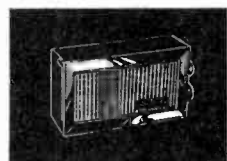

Total building costs

44'6

P. & P.
3/6

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

47'6

P. & P.
3/9

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/-.



Total building costs

79'6

P. & P.
4/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	☐	ROAMER SEVEN	☐
TRANSONA FIVE	☐	TRANS EIGHT	☐
POCKET FIVE	☐	ROAMER SIX	☐

Parts price list and plans for

Name


Address

PW10

* Callers side entrance Stylo Shoe Shop

* Open 10-1. 2.30-4.30 Mon-Fri. 9-12 Sat

CAR LIGHT FLASHERS

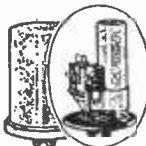

Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/6 each P. 2/6. (3 for 17/6 P. 4/6).

R209 MK II

COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12V D.C. internal power supply. Supplied in excellent condition, fully tested and checked **£16.0.0.** Carr. 20/-

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D.B. oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5-5 Mc/s. Sensitivity 33mV/Cm. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. **£22.10.0.** Or complete with all accessories, probe, leads, lid, etc. **£25.** Carriage 30/-



MARCONI T/44/TF956 AF Absorption Wattmeter

1. μ /watt to 6 watts. **£20.** Carr. 10/-

SOLARTRON CD-1016 OSCILLOSCOPES

Double beam. D.C. To 5 Mc/s. Excellent condition. **£55** each. Carr. 20/-

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. **£5.19.6.** Carr. 7/6. Or brand new with accessories. **£7.19.6.** Carr. 7/6.

CLASS D WAVEMETERS No. 2
Crystal controlled. 1-2.19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. **£12.10.0.** Carr. 30/-

SOLARTRON CD.711S.2 OSCILLOSCOPES


Double beam. D.C. to 9Mc/s. Perfect order. **£65.** Carr. 50/-

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS-1 MHz. Input Imp 2 meg Ω 25 pF. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 250/240V. a.c. Supplied brand new with handbook. **£28.10.0.** Carr. 10/-



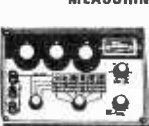TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω -11.1 meg Ω . 6 Ranges $\pm 1\%$. L.I. μ H - 111 HENRYS 6 Ranges - 2% C. 10pF $\pm 1110mF$. 6 Ranges $\pm 2\%$. TURNS RATIO 1:1/1000-1:11100. 6 Ranges $\pm 1\%$. Bridge voltage at 1,000 cps. Operated from 9 volts. 100 μ A. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2in. **£20.** P. & P. 5/-

UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6 **13 gns.**



LAFAYETTE SOLID STATE HA800 RECEIVER
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s FET front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 meter • 24in Bandspeed • 250V. A.C./18V. D.C. neg. earth operation • R.F. gain control. Size 16in. x 9 1/2in. x 8 1/2in. Weight 13 lbs. EXCEPTIONAL VALUE. **£45.** Carr. 10/- S.A.E. for full details.



TRIO COMMUNICATION RECEIVER MODEL 9R-590E

4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical bandspeed on 10, 15, 20, 40 and 80 metres. 3 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW • ANL • Variable BFO • 8 meter • Sep. bandspeed dial • IP 455 Kc/s • Audio output 1.5 W. • Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size 7 x 15 x 10in. With instruction manual and service data. **£42.10.0.** carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally **£5.19.6.** OUR PRICE **£3.16.0** if purchased with above receiver.

TRIO JR-500SE 10-80 Metre AMATEUR RECEIVER

Covers all the amateur bands in 7 separate ranges between 3.5 and 29.7 Mc/s. 7 valves, 2 transistors and 5 diodes plus 8 crystals: output 8 and 500 ohm and 9,000 ohm phone jack. Crystal controlled oscillator. Variable BFO. VFO. AVC. ANL. 8 meter, SSB-CW. Stand-by switch. Special double gear dial drive with direct reading down to 1 kHz. Remote control socket for connection to a transmitter. Audio output 1 watt. 115/250V. A.C. mains. Superb modern styling. Size 7 x 13 x 10 1/2in. with instruction manual and service data. **£69.10.0.** Carr. Paid.

TRIO TS 510 AMATEUR TRANS-CEIVER with speaker and mains P.S.U. £212. IN STOCK!



SPECIAL BONUS OFFER!

TRIO SP5D Matching Speaker Mate and TRIO HS4 Communication Headphones. Normal Value **£10.7.0.** FREE OF CHARGE with every JR-500SE purchased.

HAMMARLUND SP600JX COMMUNICATION RECEIVER

High quality professional dual conversion communication receivers available for the first time in this country at a reasonable price. Frequency range 540 Kc/s-54 Mc/s. In 6 bands variable tuning or 6 channel crystal controlled. 2.5 watt output into 600 ohms. Input 110/230V. A.C. 20 valve circuit incorporating: Xtal filter B.F.O. A.N.L. Xtal calibrator, 8 meter (List **£290.**) Offered in excellent condition, fully tested and checked. **£100** each.



RCA COMMUNICATIONS RECEIVERS AR88D

Latest release by ministry BRAND NEW in original cases. 110-250V. A.C. operation. Frequency in 6 Bands. 535 Kc/s-32 Mc/s continuous. Output impedance 2-5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price **£87.10.0.** Carr. **£2.**



LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. **£87.10.0.** Carr. 10/-



CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters. Type MR 38P. 1 1/2in. square fronts.



50 μ A.....	37/6	50mA.....	25/-	150V. D.C.....	25/-
50-0-50 μ A.....	35/-	750mA.....	25/-	300V. D.C.....	25/-
100 μ A.....	35/-	1-0-1mA.....	25/-	500V. D.C.....	25/-
100-0-100 μ A.....	32/6	2mA.....	25/-	750V. D.C.....	25/-
200 μ A.....	32/6	5mA.....	25/-	15V. A.C.....	25/-
500 μ A.....	37/6	10mA.....	25/-	50V. A.C.....	25/-
		750mA.....	25/-	150V. A.C.....	25/-
		1-0-1mA.....	25/-	300V. A.C.....	25/-
		2mA.....	25/-	500V. A.C.....	25/-
		5mA.....	25/-	8 meter 1mA 25/6	
		10mA.....	25/-	VU meter 1A 25/6	
		20mA.....	25/-		

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET


Variable Voltage TRANSFORMERS
Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 60-60 cycles. Output full variable from 0-280 volts. Bulk quantities available. 1 amp.—**£5.10.0**; 2.5 amp.—**£6.15.0**; 5 amp.—**£9.15.0**; 8 amp.—**£14.10.0**; 10 amp.—**£18.10.0**; 12 amp.—**£21.0.0**; 20 amp.—**£37.0.0**.



RACAL RA-17

First ministry release of these world famous communication receivers. Frequency range 500 Kc/s-30 Mc/s. Available in excellent condition, fully tested and guaranteed. **£150.** Carr. 40/-

AVOMETER MOVEMENTS

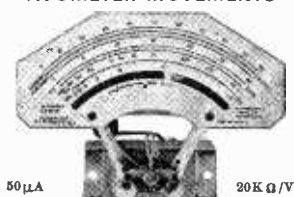

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multi-meter. Brand New & Boxed. 69/6. P. & P. 3/6.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: .01/.003/.1/.3/1/3/10/30/100/300V. R.N.S. 4cps. 1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. **£17.10.0.** Carr. 5/-



LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5 Ω . Operation 200/250V. A.C. Supplied in perfect order. **£12.10.0.** Carr. 10/-

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,000V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17.10.0.** P. & P. 6/- Additional probes available: R.F. 25/-, H.V. 42/6.



OSBORNE 1049 DOUBLE BEAM OSCILLOSCOPES. D.C. coupled. Band width 1Kc/s. Perfect order. **£25.** Carr. 30/-

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmo. Frequency coverage 20-200 Kc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1 μ V-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. **£45.** Carr. 20/-

GEARED MAINS MOTORS

Paralux type 8D19 230/250V. A.C. Reversible. 30 r.p.m. 40 lb./ins. Complete with capacitor. Excellent condition. **99/6.** Carr. 10/-

TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800Hz modulation. 5 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. **£7.19.6.** P. & P. 4/-

FIELD TELEPHONES TYPE L

Generator ringing, metal cases. Operates from two 1.5V batteries (not supplied). Excellent condition. **£4.10.0** per pair. Carr. 10/-

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded. 150 W. **£12.6.** P. & P. 3/6. 300 W. **£2.7.6.** P. & P. 4/6. 500 W. **£3.10.0.** P. & P. 6/6. 1,000 W. **£5.10.0.** P. & P. 7/6. 1,500 W. **£7.19.6.** P. & P. 8/6. 7,500 W. **£15.10.0.** P. & P. 20/-

G. W. SMITH & CO (RADIO) LTD.
Also see oppo. page

ARF-100 COMBINED AF-RD SIGNAL GENERATOR



A.F. SINE WAVE 20-200,000 c/s. Square wave 20-50,000 c/s. D.P. HIGH IMP. 21V. P/P600 3-8V. P.P. TF 100 Kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. \$30.00. Carr. 7/8.

TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-200 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instructions. \$15.00. P. & P. 7/8. S.A.E. for details.

PEAK-SOUND PRODUCTS. Full range of Amplifiers, Kits, Speakers in stock.

TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 20c/s to 200 Kc/s on 4 bands. Square: 20c/s to 30Kc/s. Output impedance 5,000 ohms. 200/250V. A.C. Supplied brand new and guaranteed with instructions. \$18.10.0. Carr. 7/8.

MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. \$20. Carr. 15/-.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd 2 ohms 200 meg. ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New \$17.10.0 Carr. 7/8.



MODEL ZQM TRANSISTOR CHECKER It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9967. B: 2-200. Ico: 0-50 microamps 0-5mA. Resistance for diode 200Ω-1MΩ. Supplied complete with instructions, battery and lead. \$5.19.6. P. & P. 2/6.

ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. **VM-76 VALVE VOLTMETER.** R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 100V with accuracy of +2% D.C. range 300 MV to 1 KV. A.C. range 300 MV to 300 V RMS. Resistance 0.2-500 MΩ. Price \$72. **VM-78 A.C. MILLIVOLT METER.** Transistorised 1 MV-300 V. Frequency 1 c/s to 1 Mc/s. Price \$55. **VM-79 UHF MILLIVOLT METER.** Transistorised. A.C. range 10 MV-3 V. D.C. current range 0.1 to 3 MA. Resistance 1 ohm-10 megohms. Price \$125. **H1B AUDIO SIGNAL GENERATOR.** 16 c/s-50 Kc/s. sine or square wave. Price \$30. **J1B AUDIO SIGNAL GENERATOR.** 15 c/s-50 Kc/s. Price \$30. **V1B AUDIO SIGNAL GENERATOR.** As per J1B except fitted with output meter. Price \$35. **TT18 TRANSISTOR TESTER.** \$37.10.0. Carriage 10/- per item.

SONOTRONIC PORTABLE OSCILLOSCOPES. Rx govt. scope, general purpose. 3in. CRT. Mains operated. Fully tested and checked. \$12.10.0. Carr. 7/6. **SOLARTRON MONITOR OSCILLOSCOPE TYPE 101** An extremely high quality oscilloscope with time base of 10μsec to 20msec. Internal Y amplifier. Separate mains power supply 200/250V. Supplied in excellent condition with cables, probe, etc., as received from Ministry. \$2.19.6. carriage 30/-.

NEW CATALOGUE

Nearly 200 pages giving full details of a comprehensive range of COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT. Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices.

Free Discount Coupons Value 10/-

SEND NOW-ONLY 7/6 PEP!

GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS

8RP22 Stereo	\$5.19.6	*SP25 MK II	\$11.19.6
*1025 Mono	\$7.10.0	*SL55	\$11.19.6
*1025 Stereo	\$7.15.0	*A70 MK II	\$12.10.0
*2025 Stereo	\$7.19.6	*AT60 MK II	\$13.5.0
*2025T/C		*SL65	\$14.14.0
Mono/Stereo	\$8.17.8	AP75	\$17.17.0
		401	\$23.7.6
*3000 Stereo	\$9.19.6	SL75	\$23.10.0
		SL95	\$25.5.0



Carriage/Insurance 7/8 extra any model. WB4 Bases \$3.19.6. Perspex covers \$3.10.0. *Special offer base and cover available for these models at \$4.15.0. Carr. 5/- Full range of Garrard accessories available.

LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



19 transistors, 8 diodes, IHF music power. 30W at 8Ω. Response 30-20,000 + 2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16Ω. Separate L and R. volume controls. Treble and bass control. Stereo phono jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/2 x 9 1/8 x 7 1/8. Operation 115/230V. A.C. \$28. Carriage 7/6.

MULTIMETERS for EVERY purpose!

TE-51. NEW 20,000Ω/VOLT MULTIMETER with overload protection and mirror scale. 0.6/60/120/1,200v. A.C. 0.3/30/60/300/600/3,000v. D.C. 0-60μA/12/300mA. D.C. 0.60K/6 meg. ohm. \$2/6. P. & P. 2/6.



TE-900 20,000Ω/VOLT GIANT MULTIMETER mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2-5/10/250/1,000/5,000 v. A.C. 0/25/12-5/10/50/250/1,000/5,000v. D.C. 0/50μA/110/100/500 mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. \$15. P. & P. 5/-.

MODEL AG-100D. 100K Ω/VOLT. 5in. mirror scale. Built-in meter protection. 0.3/12/60/120/300/600/1,200v. DC 0.6/30/120/300/600/300/600/300 v. D.C. 0/10μA/6/60/300 mA/12 amp. 0/2K/200K/2M/200M Ω. -20 to +17dB. \$12.10.0. P. & P. 3/6.

MODEL TE-10A. 20KΩ/Volt 5/25/50/250/500/2,500v. D.C. 10/50/100/500/1,000 v. A.C. 0/50μA/2-5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100mFd. 0-100-0-1mFd. 60/6. P. & P. 2/6.




MODEL TE-90 50,000 Ω/Volt mirror scale overload protection 0.3/12/60/300/600/1200 v. D.C. 0.6/30/120/300/1200v. DC. 0.6/60/60/600mA. DC. 16K/160K/1.6/16meg Ω. -20 to +63dB. \$7.10.0. P. & P. 3/-.




LAFAYETTE 67 Range Super 50KΩ/volt multimeter. D.C. volts 12 mV -1000V. A.C. volts 1-5V -1000V. D.C. current 25μA-10 amp. Ohms 0-10 meg Ω -20 to +81 dB. Overload protection. \$12.10.0. Carr. 3/6.

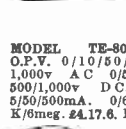MODEL TE-70. 30,000 Ω/Volt. 0.3/15/60/300/600/1200v. DC. 0.6/30/120/300/600/1200v. AC. 0.3/30/120/300/600/1200v. A.C. 0.16K/160 K/1.6M/16 Meg. Ω. \$5.10.0. P. & P. 3/-.



MODEL TE-80. 20,000 Ω/Volt. 0.1/10/50/100/500/1,000v. AC. 0.6/25/50/250/500/1,000v. D.C. 0-60μA. 5/50/500mA. 0.6K/60K/600 K/6meg. \$4.17.6. P. & P. 3/-.

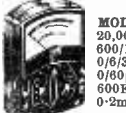MODEL PT-34. 1,000 Ω/Volt. 0.1/10/50/250/500/1,000v. AC. and DC. 0.1/100/500mA DC. 0/100K Ω. 39/6. P. & P. 1/6.



MODEL TE-12 20,000 Ω/Volt. 0.1/10/50/100/500/1,000/5,000/2,500v. D.C. 0.6/30/120/600/1,200v. A.C. 0/60μA/6/60/600mA. 0/6K/600K/6Meg. 60 Meg. Ω. 50F. 0-2mFd. \$5.19.6. P. & P. 3/6.

★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/4 in. 3 I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. \$3.7.6. P. & P. 2/8. Stereo multiplex adaptors 99/6.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. \$6.19.6. P. & P. 3/6.



SINCLAIR EQUIPMENT

Z12 12 watt amplifier. 89/6
P24 Power Supply Unit 89/6
Stereo 25 Preamp. \$9.19.6
Q14 Speakers \$7.19.6
Micromatic Radio Kit. 49/6. Built 59/6.

Now in Stock
IC10 59/6. All post paid.

SPECIAL OFFER
Two Z12 Amps., P24 Power Supply, Stereo 25 Preamp, \$22, or with two Q14 speakers, \$37.

NEW SINCLAIR 2000 SYSTEM
35 watt Integrated Amplifier, \$29. Carr. 5/-.
Self-powered FM Tuner, \$25. Carr. 5/-.

ECHO HS-606 STEREO HEADPHONES



Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

TE111. DECADE RESISTANCE ATTENUATOR



Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600Ω range (0-1dB x 10) + (1dB x 10) to +20 + 30 + 40dB. Frequency: 0 to 200KHz (-3dB). Accuracy: 0-05dB. +Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new \$27.10.0. P. & P. 5/-.

RECORDING HEADS

Reuter i-track. As fitted to Collaro Mk. IV and Studio Decks. High imp. record playback, low imp. erase. Lower track only. Brand new 10/-.
OSMOCORD i-track heads. High imp. record/playback 65/- Low imp. erase 20/-.
MARRIOTT i-track heads. High imp. record/playback 65/- Low imp. erase 20/-.
Post extra.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.
3in. 225ft. L.P. acetate 3/6
3 1/2in. 600ft. T.P. mylar 10/-
5in. 600ft. std. plastic 8/6
5in. 900ft. L.P. acetate 10/-
5in. 1,200ft. D.P. mylar 15/-
5in. 1,200ft. L.P. acetate 18/6
5in. 1,200ft. T.P. mylar 18/-
5in. 1,800ft. D.P. mylar 22/6
5in. 2,400ft. T.P. mylar 29/6
7in. 1,200ft. std. acetate 12/6
7in. 1,800ft. L.P. acetate 15/-
7in. 1,800ft. L.P. mylar 20/-
7in. 2,400ft. D.P. mylar 25/-
7in. 3,600ft. T.P. mylar 45/-
Postage 2/- Over 43 post paid.

MAXELL TAPE CASSETTES
C60, 10/8; C90, 14/3; C120, 19/6. Post extra

G. SMITH & CO (RADIO) LIMITED

3 and 34, LISLE STREET, OI-437 8204
LEICESTER SQ. LONDON, W.C.2 OI-437 9155
311, EDGWARE RD, LONDON, W.2 OI-262 0387
(ALL MAIL ORDERS TO:- 3, LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2)

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722-9090

SAVE POSTAL COSTS! CASH AND CARRY BY CALLERS WELCOME

0A2 5/9	6AU6 5/9	6BD20 8/8	12AE8 7/8	30C15 13/8	5763 10/-	DK91 5/8	EC92 6/6	EF183 8/-	HN309 27/4	PCF801 7/-	Q8150/15 9/8	UY41 6/9
0B2 6/-	6AV6 5/8	6B7GT 6/6	12AT6 4/8	30C17 12/8	6060 5/8	DK92 7/9	EC93 12/8	EF184 8/-	HVR2A 8/9	PCF802 9/-	QV40/7 8/-	UY85 5/8
0Z4 4/8	6B9G 2/6	6P1 12/8	12A77 3/8	30C18 8/9	7189 10/8	DR96 7/9	EC93 28/1	EH90 6/6	W3 6/6	PCF805 8/9	R10 18/-	U10 9/8
1A3 4/8	6BA6 4/8	6P25 12/8	12AU7 4/8	30F5 13/8	7476 4/-	DL33 6/9	EC94 29/6	EL32 3/6	W4/350 5/6	PCF806 12/8	R11 19/8	U16 15/-
1A5 5/-	6BE6 4/8	6P26 12/8	12AU7 4/8	30FL1 15/-	A1834 20/-	DL35 4/9	EC94 9/6	EL33 12/8	W4/500 8/-	PCL51 9/-	R16 34/11	U17 5/8
1A7GT 7/9	6BH6 7/8	6P28 25/-	12AV6 5/8	30FL12 16/-	A2134 10/-	DL92 4/9	EC98 8/9	EL34 9/8	KT2 5/-	PCL52 7/-	R17 17/8	U18/20 10/8
1C5 4/9	6B36 6/9	6Q7G 6/9	12AX7 4/8	30FL14 12/8	A3042 15/-	DL94 5/8	EC98 4/8	EL35 10/-	KT3 8/8	PCL53 8/-	R18 9/8	U19 24/8
1D5 6/9	6BQ5 4/8	6Q7 8/8	12AX7 9/9	30L1 9/-	AC2FEN 19/8	DL96 7/9	EC98 4/8	EL37 17/8	KT32 5/8	PCL54 7/8	R19 6/8	U22 7/9
1D6 9/9	6BQ7A 7/-	6R7G 7/-	12BA6 6/-	30L15 13/9	AC2PEN/ 19/8	DL98 7/9	EC98 5/8	EL41 9/8	KT41 19/8	PCL55 8/8	R20 11/8	U25 13/8
1FD1 6/-	6BR7 8/8	6R7 11/-	12BE6 5/9	30L17 13/-	DD 19/8	DM70 6/9	EC98 5/8	EL42 9/8	KT44 20/-	PCL56 8/8	R22 7/8	U26 11/8
1FD9 3/9	6BR8 8/-	6BA7GT 6/6	12BH7 6/-	30P4 12/-	AC6PEN/ 4/9	DM71 7/8	EC98 5/8	EL43 9/8	KT61 12/-	PCL58 15/-	RK34 7/8	U31 6/-
1G6 8/-	6BR7 16/8	6BG7 6/6	12R1 17/-	30P4MR 17/8	AC6PEN/ 4/9	DM71 7/8	EC98 5/8	EL43 9/8	KT63 4/-	PEN45 7/-	SP42 12/8	U33 29/8
1H6GT 7/-	6BW6 12/8	6BG7 6/6	12TGT 13/-	30P12 13/-	AC/PEN (5) 19/8	DW4/5008/8	EC98 5/8	EL44 4/8	KT66 17/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1LA 2/6	6BW7 11/-	6BH7 8/-	12K5 10/-	30P12 13/-	AC/PEN (7) 19/8	DW6 5/9	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1LD5 5/-	6C4 2/9	6B37 6/6	12K7GT 5/8	30P19 12/-	AC/PEN (7) 19/8	DY87 5/9	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1LN5 8/-	6C6 3/9	6BK7GT 4/8	12K8GT 7/8	30PL1 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1N5GT 7/9	6C9 11/-	6BN7GT 4/8	12QGT 4/8	30PL13 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1R5 6/8	6CD6G 19/8	6BGTGT 6/6	12A7GT 4/8	30PL14 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
184 4/9	6CH6 6/-	6U4GT 12/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
185 3/9	6CL6 8/8	6UTG 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1U4 5/9	6D3 7/8	6V6G 8/8	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
1U5 6/9	6D6 3/-	6V6GT 6/6	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
2D21 5/9	6F1 8/9	6X4 3/8	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3A4 3/8	6F6 12/8	6X5GT 5/8	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3A5 10/-	6F9G 4/-	6X7G 12/8	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3B7 6/9	6G12 8/8	6Y7G 10/8	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3D6 2/9	6F13 3/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3Q4 6/8	6F15 9/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3Q5GT 6/8	6F18 7/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
384 4/9	6F23 18/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
3V4 5/8	6F24 11/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
5R4GY 8/9	6F28 10/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
5V4G 7/8	6H6GT 9/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
5Y8GT 5/8	6J6G 8/9	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
5Z3 8/9	6J5 8/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
5Z4G 6/8	6J7G 4/9	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6/80L2 12/8	6J7GT 6/6	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6A8G 5/8	6K6GT 5/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AC7 8/-	6K7G 2/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AG5 3/8	6K7GT 4/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AK5 4/8	6K8G 3/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AK6 6/-	6K9GT 7/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AL5 2/8	6L1 19/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AM6 3/8	6L6GT 7/9	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AQ5 4/8	6L7GT 12/8	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AR6 8/9	6L8 5/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8
6AT6 4/-	6L19 19/-	6Y7 7/-	12C7 6/9	30PL15 15/-	AC/TH1 10/-	E83F 24/-	EC98 5/8	EL45 4/8	KT74 12/8	PEN45DD 12/8	SP42 12/8	U33 29/8

All goods are new and subject to the standard 90-day guarantee. We do not handle manufacturers' seconds, nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Business hours Mon.-Fri. 9-5.30 p.m. Sat. 9-1 p.m. Terms of business. Cash with order only. Post/packing 6d. per item. Orders over £5 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 6d. extra. Complete catalogue of valves, transistors and components with conditions of sale, price 10d. post free. No enquiries answered unless S.A.E. enclosed for reply.

A LONG COOL LIFE

for your valuable components with the
S.D.C. DeC range of SOLDERLESS breadboards

S-DeC Available as single packs with accessories and control panel @ 29/6d or the DeCSTOR double pack containing 2 S-DeCs, accessories, control panel, all in a plastic storage container. Only 67/6d. A 4 DeC pack is available, only 117/6d.


T-DeC Now available to the amateur. 208 connection points. 38 independent junctions. Accommodates I.C.s using standard carriers. Three times the capability for only twice the price! Unit pack with control panel 50/-d.

µ-DeC Primarily for use with integrated circuits; further details on request.

T-DeCs, S-DeCs and Accessories are all obtainable from leading suppliers throughout the U.K. In case of difficulty complete the coupon and mail without delay.

Post to:

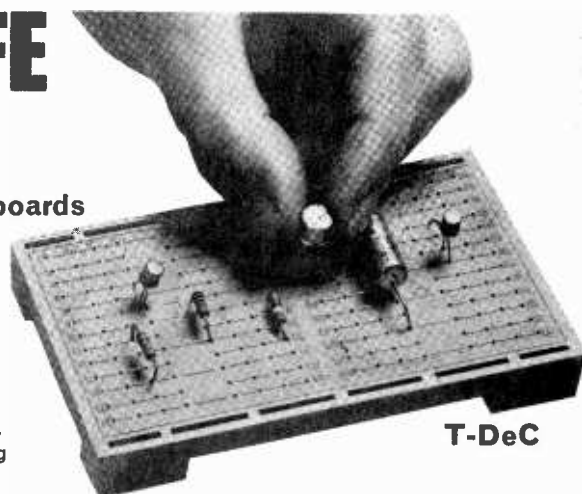S.D.C. Electronics (Sales) Ltd.,
34, Arkwright, Astmoor Industrial Estate,
Runcorn, Cheshire. Tel: Runcorn 5041



T-DeC


Please send me:

..... T-DeC Pack S-DeC Single Pack
..... DeCSTOR Pack 4-DeC Pack

Tick here if you require further details of the µ-DeC
I enclose PO/Cheque/Money Order value £ | | d.
Money refunded if not satisfied.

Name.....

Address.....

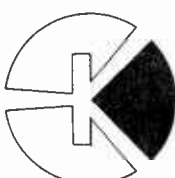

COMET Hi-Fi DISCOUNT WAREHOUSE

- ALL ITEMS OFFERED ARE FULLY GUARANTEED AND BACKED BY COMET.
- OPEN TO THE PUBLIC 9 to 5.30 p.m. daily (8 p.m. Thursday and Friday evenings) and 5 p.m. Saturdays.
- COMPLETE FREE PRICE LIST CONTAINING OVER 800 ITEMS ON REQUEST.

Rec. Retail Price Comet Price

AMPLIFIERS

DULCI 207 Stereo Amplifier	£25 0 0	£18 0 0
DULCI 207M Stereo Amplifier takes magnetic P/U	£30 0 0	£21 19 0
DULCI 220 Princess	£44 2 0	£34 19 6
GOODMANS Maxamp	£54 0 0	£42 18 0
New LEAK Stereo 30 Plus	£52 0 0	£41 10 6
New LEAK Stereo 30 Plus In teak case	£52 0 0	£41 19 6
New LEAK Stereo 70	£63 0 0	£50 19 6
LINEAR LT.66 Stereo Amplifier	£15 15 0	£13 10 0
QUAD 33 Preamplifier	£43 0 0	£34 19 6
QUAD 303 Stereo Main Amplifier	£55 0 0	£45 19 6
ROGERS Ravensbourne 50 watt Stereo	£59 10 0	£48 19 6
ROGERS Ravensbourne In teak case	£64 0 0	£54 8 0
ROGERS Ravensbrook	£41 0 0	£34 19 6
ROGERS Ravensbrook In teak case	£46 10 0	£39 19 6
TELETON 203E	£28 7 6	£23 7 6
TRUVOX TSA.200	£54 12 0	£42 9 0
WHARFEDALE GP 50 Mark II P.A. Amplifier	Special Price	£50 0 0

TUNERS

ARENA 211 Stereo with decoder	£39 18 0	£34 18 0
DULCI FMT.7FM Tuner	£22 1 0	£19 0 0
DULCI FMT.7S FM Stereo Tuner	£29 8 0	£23 0 0
GOODMANS Stereomax AM/FM Stereo Tuner	£82 10 5	£69 19 6
LEAK Troughline Tuner with multiplex	£51 10 6	£39 19 6
QUAD Stereo FM Tuner	£51 0 0	£43 19 6
ROGERS Cadet Mark III Tuner	£20 12 6	£17 13 0
ROGERS Ravensbourne Tuner with Decoder	£60 15 3	£52 2 0
TRUVOX FM 200/IC Tuner	£52 0 0	£42 0 0

TUNER-AMPLIFIERS

ARENA 2400 with Decoder	£90 6 0	£69 19 6
ARENA 2500 complete with Decoder	£97 0 0	£79 0 0
(NEW) GOODMANS Model 3000 with stereo decoder	£77 14 7	£68 0 0
TELETON MX.990 Stereo Tuner/Amplifier with AM/FM Multiplex Stereo Radio c/w two Speakers, each speaker containing 8in. bass, 2in. tweeter	£64 13 2	£49 19 6
TELETON F.2000 AM/FM Stereo Tuner/Amplifier 2 x 5 watts RMS with silicon transistors	£43 0 0	£35 19 6
TELETON R.8000 AM/FM Stereo Tuner/Amplifier 2 x 6 watts RMS, complete with 2 speaker boxes	£60 19 6	£49 19 6

Rec. Retail Price Comet Price

TELETON 7AT1 Stereo Tuner/Amplifier AM/FM 50 watts RMS Stereo Decoder with F.E.T.	£133 0 0	£95 0 0
TELETON CMS.400 AM/FM Multiplex Tuner/Amplifier with 2 speaker boxes and turntable	£126 0 0	£99 0 0
THE GOODMAN 3000 MUSIC AUDIO SUITE A complete Audio Suite with Stereo Radio, complete with Speakers, Turntable and magnetic cartridge. All wired and ready to go. Beautifully finished In Teak	£140 9 0	£115 9 4

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

SPEAKERS

CELESTION Dilton 10	£21 13 1	£17 16 0
CELESTION Dilton 15	£31 3 7	£26 5 0
DULCI AS3 Speaker	£8 8 0	£6 19 6
GOODMANS Maxim	£20 15 6	£16 19 6
GOODMANS Mezzo II	£30 18 0	£25 13 0
GOODMANS Magnum-K	£40 2 0	£29 19 6
GOODMANS Mirlimba	£26 0 0	£18 19 6
GOODMANS Mambo	£22 6 6	£18 11 9
GOODMANS Loudspeaker System. Model 3005 (per pair)	£25 0 0	£21 0 0
KEF Celeste	£29 0 0	£23 19 6
KEF Concord	£43 10 0	£36 0 0
LEAK Sandwich	£43 10 0	£32 19 6
LEAK Mini-Sandwich	£29 15 0	£21 19 6
QUAD ELECTROSTATIC	£66 0 0	£55 0 0
WHARFEDALE New "Airedale"	£69 10 0	£57 14 0
WHARFEDALE Denton	£16 6 0	£12 19 6
WHARFEDALE Super Linton	£21 0 0	£16 19 6
WHARFEDALE Melton	£29 10 0	£22 19 6
WHARFEDALE New Dovedale 3	£39 10 0	£30 19 6
WHARFEDALE Rosedale	£55 0 0	£45 0 0
WHARFEDALE UNIT 3 Speaker Kit	£10 17 6	£9 10 0

TURNTABLES

GARRARD SP.25, Mark II	£15 11 11	£11 10 0
GARRARD AP.75	£23 16 7	£17 19 6
GARRARD SL.55	£13 17 9	£11 2 6
GARRARD SL.65	£18 8 4	£14 19 6

Rec. Retail Price Comet Price

GARRARD SL.75	£35 12 5	£26 19 6
GARRARD SL.95	£45 9 1	£34 19 6
GARRARD 401	£31 14 2	£25 10 0
GARRARD 3000	£11 4 1	£9 10 0
GARRARD 3500	£12 4 0	£10 1 10
GOLDRING Lenco GL.68	£22 7 2	£16 19 11
GOLDRING Lenco GL.75	£35 15 5	£26 19 6
GOLDRING 75P	£46 18 8	£38 0 0
GOODMANS Model 3025 Complete with Magnetic Cartridge	£37 14 9	£31 19 6
THORENS TD.125	£63 4 9	£55 0 0
THORENS TD.150	£28 16 11	£25 7 0
THORENS TD.150A	£35 14 6	£28 10 0
THORENS TD.150B	£32 17 6	£28 18 0
THORENS TD.150AB	£39 16 9	£32 19 6
THORENS TD.124/11	£45 18 1	£40 7 0

Bases, plinths and covers stocked to suit all the above turntables.

HI-FI STEREO TAPE DECKS AND

TAPE RECORDERS

AKAI X-150D deck 4 track	£130 2 4	£109 0 0
AKAI X-360 4 track	£339 0 0	£284 0 0
AKAI X-360D deck 4 track	£290 0 0	£243 0 0
AKAI 1710 4 track w/o acc.	£109 0 0	£89 19 6
AKAI 1800 4 track	£158 0 0	£133 0 0
AKAI 1800SD 4 track	£199 0 0	£167 0 0
AKAI 4000D deck 4 track	£99 10 0	£79 19 6
AKAI X-V 4 track	£180 0 0	£151 0 0
AKAI M-9 4 track w/o acc.	£195 0 0	£139 19 6
MARCONI 4214 twin track Tape Recorder	£35 16 0	£31 0 0
MARCONI 4216 4-track Tape Recorder	£41 5 0	£35 19 6
MARCONI 4218 Stereo Tape Recorder	£88 0 0	£77 19 6
MARCONI 4238 4 track Tape Recorder	£58 11 0	£49 19 6
PHILIPS battery operated tape recorder Model 4200	£35 6 0	£21 19 6
SHARP 504 battery/mains tape recorder, complete with all accessories guaranteed 5 years	£35 5 3	£24 19 6
TELETON 7D 70 Stereo Tape Deck	£85 10 3	£62 0 0
TELETON FXB501D Stereo Tape Deck and preamplifier	£65 0 8	£49 0 0
TELETON 401X FM Multiplex Stereo tuner/amplifier 20 watts RMS	£67 2 6	£49 0 0
TRUVOX R54 3 speed 4-track	£72 2 0	£52 2 0
TRUVOX R52 3 speed 2-track	£72 2 0	£52 2 0

PICKUP ARMS

GOLDRING Lenco L75	£12 6 6	£10 10 0
GOLDRING Lenco G65	£7 13 6	£6 10 0
SME 3009 with S2 shell	£27 19 2	£23 17 6
SME 3012 with S2 shell	£29 0 0	£25 17 6

COMET DISCOUNT WAREHOUSE

Reservoir Road, Clough Road, Hull. Tel 407906
68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally.
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.
Add 9/- for post and packing on all orders. Make cheques, Money Orders payable to "COMET".

M. & B. RADIO

15a HUNSLET ROAD, LEEDS LS10 1JQ

Telephone: 0532-35649

R210 RECEIVER. Modern 14 miniature valve receiver. 2-16Mc/s in 7 bands each 50in. film strip scale. 10/100Kc/s xtal calibrator. BFO. CW filter. Internal 24V psu. Supplied c/w handbook and home-made mains psu. £30, carr. 25/-.

VHF MOBILE TX/RX. Miniature valve trans-receiver with 12V transistor power unit. Double conversion receiver. Xtal controlled but easily converted to tuneable. High or low band models (2 or 4 metres). Please state which when ordering. Positive or negative earth. Supplied c/w circuit and notes. TESTED £9.10.0, carr. 27/6.

TRANSISTORISED 2-METRE CONVERTERS. 2 RF stages. Various IF frequencies. Please state preference when ordering. £7.15.9, plus 5/- pp.

12 VOLT TRANSISTOR INVERTERS. Gives 240V DC at 40 watts. Ideal for caravan fluorescent lighting. £6, plus 7/6 pp. Various other transistor inverters. Please send SAE for details.

RADIOTELEPHONE press to talk microphones. Used. 5/-, plus 2/- pp.

SPRING LOADED mobile whip base sections. Chrome finish. Brand new. 6/6, plus 1/6 pp.

GRANADA 4. Transistor amps in cabinet with speaker. Tested. 62/6, plus 7/6 pp.

GPO Telephones with dial, 17/6, plus 6/- pp. Modern style telephone 42/6, plus 6/- pp.

QQV03/10 6/- tested. **QQV06/40A 37/6** tested. 800piv 16 amps silicon diodes on heat sink. 6/- BY 128 2/6. 2 x OC35s on heat sink. 10/- OC35 on small heat sink 5/-, 1/- pp.


STETHOSCOPE HEADSETS. Brand new. Ideal for stereo or mono. Low imp. 27/6, plus 3/6 pp.

2-METRE TRANSISTOR P.A. £7.10.0. Transistor amplifiers, modulators, mic pre-amps. VHF transmitters. Scopes. Aerials. Valves. Etc.

TELEMETER. A well finished cabinet containing lots of useful items for the constructor. Tape unit and head, 2 motors, speaker, auto and mains transformers, miniature valve I.F. unit etc. Ideal for stripping or modifying. 77/6 plus 7/6 carriage.

STEREO CABINETS. A beautifully finished polished wood cabinet supplied in original carton. NEW. 47/6 plus 6/6 carr.

LISTS 6d., plus SAE.

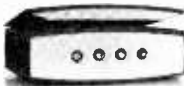

over

15,000

copies sold

Now in its
second printing

Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's British origin ensures easy availability of components. The standard work in its field.

69s post paid

R.S.G.B. INTERNATIONAL RADIO ENGINEERING & COMPONENT EXHIBITION

Royal Horticultural Society's New Hall,
Greycoat Street, Westminster, S.W.1.

Come and see everything in international radio, from a threepenny resistor to a thousand pounds worth of ssb equipment. The world's Premier Radio Show in London.

OCTOBER 1-4, 10 a.m. to 9 p.m.

Don't miss this one!

Free Publications list, plus free details of the
RADIO SOCIETY of GREAT BRITAIN
from RSGB PUBLICATIONS
35 DOUGHTY STREET, LONDON, WC1

BIGGEST BREAKTHROUGH IN RADIO KITS!

THE REVOLUTIONARY APOLLO "6" CAN BE BUILT

SPECIALLY made for the thousands of discriminating people who want the finest easy-to-build radio... at a reasonable price! *This is a different breed—it will starve you!* EIGHT MONTHS AGO our two designers were briefed to produce a radio kit that would fill these technical demands:—**DEMAND—A. IT SHOULD BE POSSIBLE TO BUILD PAINLESSLY IN ONE EVENING**... **ANSWER—the Apollo "6" has simplified, well illustrated step-by-step plans.**

CONTAINS FEATURES THAT CAN'T BE BOUGHT IN READY MADE SETS—AT ANY PRICE

- receives medium wave & trawler broadcasts.
- every component brand new—no surplus rejects or "seconds".
- uses latest Silicon Planar Epitaxial Epoxy transistors.
- six stage stable reflex—2 R.F., 1 Diode demodulation, 3 A.F.
- simplified illustrated plans.
- from parts to programmes in an evening

...PLUS MANY MORE!

No soldering iron is necessary and you don't have to have a magnifying glass and a pair of tweezers. **DEMAND—B. IT SHOULD WORK FIRST TIME**... **ANSWER—**

Apollo "6" uses latest rugged Silicon Transistor Circuitry and every single transistor, diode, capacitor, resistor, inductance etc. is brand new and fully tested—no surplus parts, no manufacturers

rejects, no manufacturers' "seconds", and uses "Ever Ready" battery. **DEMAND—C. IT MUST HAVE THE POWER TO OPERATE**... **AL LOUDSPEAKER... DEMAND**... **—D. IT MUST GIVE GOOD RECEPTION IN DIFFICULT AREAS**... **DEMAND—E. IT MUST WORK ON ITS OWN INTERNAL FERRITE ROD AERIAL**... ETC. ETC.

ANSWER—The Apollo "6" does all this—and much more!


REVOLUTIONARY SILICON PLANAR EPOXY CIRCUIT DESIGN

Apollo "6" will probably be bang up-to-date well into the seventies! It bristles with latest technical innovations. Six stage stable reflex N.P.N. and P.N.P. circuit consisting of 2 Radio Frequency stages, 1 Diode demodulation stage and 3 Audio Frequency stages. Uses latest Silicon Planar Epitaxial Epoxy transistors (similar to types used in America's Space

IRON CLAD GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full, at once and without quibble or question...

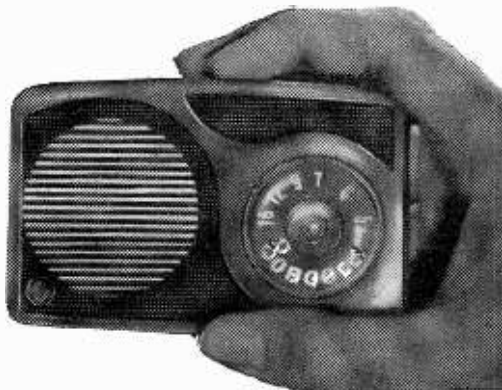(Project). The first two transistors give amplification of 100 to 400 each, (at only 100 Microamps collector current approx). Output transistor gives amplification



of 235 to 470. Stable reflexing gives the Apollo "6" staggering selectivity, uncanny sensitivity, true-to-life sound reproduction—in fact its range, power and selectivity must be experienced to be believed. Enter a new magic world of reception—station after station (home and abroad).

THRILLING SOUND OF AN SOS AT SEA

Listen to the thrilling sound of an SOS at sea—tune in to a world you've never heard before... **NOTE.** Because members of our own Staff (and their friends) are enthusiastic and have already bought Apollo "6" parts we know demand will be enormous. **DON'T DELAY—SEND FOR YOURS NOW,** send 59/6+3/6 P. & P. for all parts, illustrated plans, personal listening earpiece etc. (all parts can be bought separately) **MONEY BACK GUARANTEE** (see panel).


Orders despatched in strict rotation.



PHOENIX ELECTRONICS (Dept. PW4) 18 Little Preston St, Brighton, 1. Sussex.

NEW! HSL.700 MONO TRANSISTOR AMPLIFIER

A really high fidelity mono-amplifier with performance characteristics to suit the most discriminating listener. 8 transistor circuit with integrated pre-amplifier assembled on special printed sub-panel. AD161-AD163 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for PU1, PU2, Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis. Bronze hammer enamel finish, size 9 1/2 x 6 x 4 1/2 in.

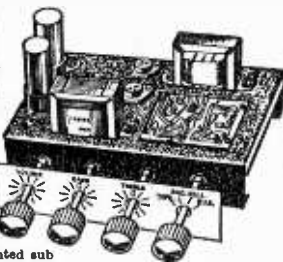

Performance figures:
Sensitivity: PU1-50mV/v. 66K input impedance.
PU2-110mV/v, 1 meg input impedance.
Tape-110mV/v, 1 meg input impedance.
Radio-110mV/v, 1 meg input impedance.
Output power measured at 1Kc-6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s: Continuously variable tone controls; Bass, +8 db to -12 db at 100 c/s. Treble, +10 db to -10 db at 10 Kc/s. The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front enclosure panel, full circuit diagram and operating instructions.

Our Special Price **£7.19.6** P. & P. 7/6.

LOUDSPEAKER BARGAINS

5in. 3 ohm 16/-, P. & P. 3/-; 7 x 4in. 3 ohm 21/-, P. & P. 4/-; 10 x 6in 8 ohm 27/6, P. & P. 6/-; R.M.I. 8 x 5 in 3 ohm with high flux magnet 21/-, P. & P. 4/-; E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-), P. & P. 6/-; E.M.I. 13 x 8in. 3 or 15 ohm with two built-in tweeters and crossover network 4 gns. P. & P. 6/-.

BRAND NEW. 12in. 15w. H/D Speakers. 3 or 15 ohms. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly 45/10.0. P. & P. 7/6. Guitar models: 25w. 50.0.0, 35w. 58.0.0.

R.M.I. 8in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

18in. "VRA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm 27/6, P. & P. 6/-.

55 OHM SPEAKERS

3 1/2in. 14/-, P. & P. 2/6; 7 x 4in. 21/-, P. & P. 4/-.

SPECIAL OFFER

HI-FI Celestion Speaker Unit. Size 6 x 4in. Powerful 11,000 line magnet with specially treated cone surround. 10-18 ohm impedance. Few only at 20/-, P. & P. 3/6.

QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6.

DUAL PURPOSE BULK TAPE ERASER AND TAPE HEAD DEMAGNETISER 35/-, P. & P. 3/-.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 18/6, P. & P. 1/6.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-, P. & P. 1/6.

S.T.C. TYPE 35 MINIATURE RELAYS-48 volt. 4 s/p. c/o contacts. 1 min. timing. Coll. resistance 5,800 ohms. Size approx. 1 x 1 1/4 x 1 1/4in. High. 8/6 each. P. & P. 1/6.

SPECIAL OFFER! FLEISSEY TYPE 29 TWIN TUNING GANG. 400pF + 145pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 Kc/s L.F. Size approx. 2 x 1 x 1 1/4in. Only 8/6, P. & P. 2/6.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 15 alternatives. Primary: 0-210-240v. Secondary combinations: 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/4in. wide x 3in. deep. Price 22/6, P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 0-9-9 at 500 mA. 11/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6, P. & P. 3/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6.


BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240v. AC Sec. 240v. at 50mA and 6-3v. at 1.5 amp. 34c each. Size 2 1/4 x 1 1/4 x 1 1/4in. 10/6, P. & P. 3/6. (Special quotations for quantities.)

HIGH GRADE COPPER LAMINATE BOARDS 8 x 6 x 1/16 in. FIVE for 10/-, P. & P. 2/-.

Open all day Saturday
Early closing Wed. 1 p.m.

A few minutes from South Wimbledon
Tube Station

TRANSISTOR STEREO 8 + 8 MK II

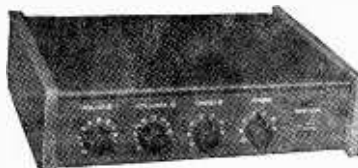

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Ch-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response +3dB. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -18dB. Negative feedback 18dB over main amp. Power requirements 25V at 5 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free.
Also available STEREO 10+10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12. POWER PACK KIT £3.10.0.**
Circuit diagram, construction details and parts list (free with kit) 1/8. (S.A.E.).

Official stockists of all
PEAK SOUND HI-FI EQUIPMENT

Including the
P.W. DOUBLE 12 STEREO AMPLIFIER as featured in Practical Wireless April, May and June issues. Component pack as specified. Total cost £23.5.6 Plus P. & P. 11/- (Excluding metalwork, knobs, plugs and sockets and fuses.)



SPECIAL PURCHASE!
E.M.I. 4-SPEED PLAYER
Heavy 8 1/2in. metal turntable.
Low flutter performance 300/200 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 68/-, P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MKII
A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, E230 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in deep x 6in. high. Ready built and tested. PRICE 75/-, P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6, P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MKII
Uncut motor board size 14 1/2 x 12in. clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.B.R. or GARRARD autotuner or Single Player Unit (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 78/6, P. & P. 6/6.



8-VALVE AUDIO AMPLIFIER HA34 MK II.
Designed for HI-FI reproduction of record. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 x 4 1/2 x 4 1/2 in. Incorporates EOC83, EL84, E230 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 48 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.15.0. P. & P. 6/-.


HBL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 78/6, P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V15/10p 10/-; OC71 8/-; OC76 6/-; AF117 8/6; 263339 (NPN) 8/-.
Set of 3 Mullard transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

VYNAIR AND REXINE SPEAKER AND CABINET FABRIC. Approx. 64in. wide. Usually 35/- yard. OUR PRICE 18/6 per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

BRAND NEW! PARMEKO MAINS TRANSFORMERS
Primary 110v-260v. Secondary 330-0-330v. 100 mA and 6-3v. at 2 amps. 6-3v. at 2 amps and 6-3 v. at 1 amp. Constructively rated. Fully impregnated Electrostatic screen. Suitable for vertical or drop through mounting. Overall size 4 1/2 x 3 1/2 x 3 1/2in. Weight 8 lb. Limited number only at 27/6, P. & P. 8/-.

DE LUXE STEREO AMPLIFIER

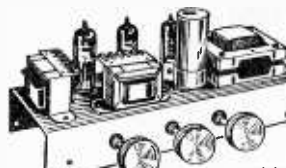

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: —2 x ECL85 Triode Pentodes. 1 x E230 as full wave rectifier. Two Dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A Dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV. for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs. Chassis size 11 1/2 x 4 1/2. Overall height including valves 5". Ready built and tested to a high standard. PRICE 3 gns. P. & P. 8/-.

4-SPEED RECORD PLAYER BARGAINS

Main models. All brand new in makers packing. B.B.R. UA25 with latest mono compatible cart. £6.19.6 All plus Carriage and Packing 6/6

LATEST GARRARD MODELS. All types available 1925, 1925S, SP25, 3000, AT60 etc. Send S.A.E. for latest Prices!
PLINTH UNITS cut out for Garrard Models, 1925, 2025, 3000, 3000, AT60, SP25. With transparent plastic cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. Only 22/6, P. & P. 2/-.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/-, P. & P. 2/-.

SONOTONE 9TAHD compatible Stereo Cartridge with diamond stylus 55/-, P. & P. 2/-.

FEW ONLY! ACOS High-G for EP and LP. Only 10/-, P. & P. 2/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI

- Peak output in excess of 1 1/2 watts.
 - All standard British components.
 - Built on printed circuit panel size 6 x 3in.
 - Generous size Driver and Output Transformers.
 - Output transformer tapped for 3 ohm and 15 ohm speakers.
 - Transistors (GEM14 or 81 Mullard AC128D and matched pair of AC128 o/p).
 - 9 volt operation.
 - Everything supplied, wire, battery clips, solder, etc.
 - Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately.
- SPECIAL PRICE 45/-, P. & P. 3/-.**
Also ready built and tested, 58/6, P. & P. 3/-.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E230 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. **FREE ONLY.**

OUR ROCK BOTTOM BARGAIN PRICE **49/6** P. & P. 6/-.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and group allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2EL84, EOC83, EF86 and E230 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. **ONLY 27.9.6, P. & P. 8/6.**
Also available ready built and tested complete with std. input sockets. 29.5.0, P. & P. 8/6.

Please write clearly
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

There are Catalogues AND Catalogues!

Ours is THIS kind...



... the kind that's

INDEXED THOROUGHLY. For instance "Aerials Telescopic" under "A" and "Telescopic Aerials" under "T".

PLANNED LOGICALLY. Having over 8,000 items it *needs* to be! Components are listed alphabetically in logical sections.

ILLUSTRATED PROFUSELY. Over 1,800 pictures. Some are photos, some are drawings, but all clearly show the features you look for.

PRINTED CLEARLY. No eyestrain here. Large easy-to-read type, on 330 sensible-size pages—9½ x 7½ in. (ignore our artist's enthusiastic exaggeration!)

BOUND SECURELY. This catalogue is bound to receive long and frequent use. Glossy laminated covers don't show fingerprints, don't tear easily.

PRICED REASONABLY. Just 8/6d plus 3/6d for post, packing and insurance. Folk tell us it's worth twice the price! We quite agree.



Yes — the Home Radio Catalogue is a pleasure to buy and to use

By the way, every Catalogue contains six Vouchers, each worth 1/- when used as directed, and we supply free a 30-page Price Supplement, a Bookmark giving electronic abbreviations and, of course, an Order Form.

POST THIS COUPON NOW
with cheque or P.O. for 12/-

The price of 12/- applies only to catalogues purchased by customers residing in the U.K.



Please write your Name and Address in block capitals

Name _____

Address _____



HOME RADIO (COMPONENTS) LTD., Dept. PW,
234-240 London Rd., Mitcham, Surrey, CR4 3HD



PRACTICAL WIRELESS

VOL 45 No 6

Issue 752

OCTOBER 1969

TOPIC OF THE MONTH

Them—and us

IMAGINE, if you can, a radio, TV and audio exhibition at which the general public (some 700,000 of them) are encouraged to enter into the spirit of the event by seeing rehearsals of favourite TV and radio shows, meet show business personalities, and even try out their own talent (or lack of it) in front of the cameras. Add to this studios for hi-fi dems., displays of telecommunications equipment and special features for the amateur radio enthusiast.

Then consider colour TV promotion which includes a 7,500 sq. ft. screen showing colour shots of the exhibition scene, and colour programmes of shows and amateur talent displayed throughout the exhibition in special viewing lounges. For good measure, let us also imagine supporting social activities such as fashion shows, promenade concerts, cable car trips, a miniature railway, and an amateur dancing contest. Not forgetting the static displays mounted by 120 manufacturers.

No, this is not an LSD-inspired fantasy. It is this year's German Radio Exhibition at Stuttgart. And while the Germans justifiably grow prosperous on expanding sales, our own dull and unimaginative industry slithers further into the doldrums, admittedly hindered by restrictive Government measures, and reduced to an uncoordinated splatter of exhibitions in hotel suites which are held together only by the vague concept of "traditional show time" yet from which, perversely, the paying customers, the general public, are strictly barred.

With colour on three channels imminent and extended v.h.f. radio in the offing, to name just two selling tags, the industry is missing an opportunity it seems foolish to ignore. From the outside it appears that they don't want the business.

There is, however, one crumb of comfort to readers of P.W. We still have the RSGB exhibition. It does not have the glamour of a Stuttgart or the glitter of our erstwhile public radio shows, but it stands unrivalled as an exhibition and social get-together combined, where everyone you meet is interested in amateur radio. Make a note in your diary—October 1-4 inc.—and support the one event still left. P.W. will be there; we hope you will be, too.

W. N. STEVENS—*Editor.*

NEWS AND COMMENT

Leader	387
News and Comment	388
On the Short Waves	
<i>by Malcolm Connah and</i>	
<i>David Gibson, G3JDG</i>	401
Practically Wireless <i>by Henry</i>	408
Letters to the Editor	424, 426
Your Questions Answered	438

CONSTRUCTIONAL

Audio Signal Generator	
<i>by C. John Courtney</i>	390
Mono-Stereo Amplifier	
<i>by James Hossack</i>	396
Adding Squelch	
<i>by C. R. Bradley</i>	409
Medium Wave DX Receiver	
<i>by D. Gibson, G3JDG</i>	412
Take 20, One transistor radio	
<i>by Julian Anderson</i>	418
Beginner's Transistor	
Capacitance Bridge	
<i>by Keith Johnson</i>	429
A Versatile Intercom System,	
Part 3	
<i>by J. E. Barrett</i>	437

OTHER FEATURES

Printed Circuit Design	
<i>by A. G. Blewett</i>	394
Pulse Circuits in Operation,	
Part 5	
<i>by I. J. Kampel</i>	405
Basic Semiconductor Technology,	
Part 5	
<i>by M. F. Docker, M.Sc.</i>	416
P.W. Guide to Components,	
Part 10	
<i>by M. K. Titman, B.Sc.</i>	419

NOVEMBER ISSUE WILL BE PUBLISHED
ON OCTOBER 3rd

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Tower House, Southampton Street, London, W.C.2. Address correspondence regarding advertisements to Advertising Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS AND COMMENT...

BROADCASTING IN THE 'SEVENTIES—BBC RESHAPING PLAN

The BBC plan for reshaping radio in a way planned to best meet the requirements of the 1970s has now been submitted to the Postmaster-General for approval. It features improved m.w. coverage, a further step towards v.h.f. expansion and a scheme for setting up a 40-station local broadcasting network.

A high priority in the plan is to improve m.w. coverage of Radio 1 and Radio 4 and this is to be achieved by making better use of m.w. channels released by discontinuing Radio 3 on m.w. and by eliminating the English Regional "opt-outs" from Radio 4 which will be no longer needed with the proposed new network arrangements.

Radio 1: This is planned as a popular music programme with news summaries on the half-hour, transmitted on m.w. only. Despite reallocation of frequencies there will continue to be night-time interference from Continental stations, but the new plan will make Radio 1 available to 4½ million more people.

Radio 2: Light music programme with news summaries on the hour, transmitted on l.w. and v.h.f. The l.w. coverage is 98% during the day and 83% at night, a situation it will be difficult to improve upon. A BBC spokesman told **PW** that a good deal of stereo is planned for the v.h.f. channel.

These two networks will be kept separate during the daytime and possibly late in the evening but will combine during the main evening periods.

Drive Against Car Radio Licence Dodgers

A huge drive against car radio licence evaders is likely in the near future. A recent estimate gives the number of car radios at over 3 million, yet only a third of that number of licences have been issued.

At present a licence is required only if the radio is a fixture in the car, that is permanently installed and powered by the car battery; ordinary portable radios,

Radio 3: This is to be shifted completely to v.h.f., but the BBC assures us that a m.w. facility will be available until such times as the m.w. outlets can be phased out. Programmes will consist of mainly classical music with some drama and speech in the evenings.

Radio 4: Mainly speech, with emphasis on news and current affairs, and with plays, discussions and light entertainment, to be transmitted on m.w. and v.h.f. Night-time reception on the m.w. band will be improved for some 11 million people; the daytime coverage being substantially total.

It is proposed that the v.h.f. transmitters should also be used part of the time for the Open University (28½ hours per week) and the schools and further education programmes (5 hours per week); the m.w. transmission of these latter would then be discontinued.

This complete overhaul of the m.w. services is estimated to cost some £400,000, phased over two years, including the construction of a new 150kW station at Stagshaw.

Audiences: Some interesting figures have been supplied by the BBC on listening habits. For Radio 1 and 2 the main audience is during daytime, between 0700 and 1500, peaking to 14 million. After 1500 the audience tails off to an average of 1 million in the evenings. Radio 4 peaks to 7 million at 0800 and 1400 and again at 3 million at 1800. Radio 3 has an average audience of only 100,000, but this is quite evenly spaced throughout the hours of

broadcasting.

Local Radio: One of the main proposals in the plan is to expand the present experimental group of 8 v.h.f. local broadcasting stations to a system of 40 stations reaching nearly 90% of the population of England. This would be basically a v.h.f. service but during the transitional period some m.w. support may be provided. The first phase would be to launch 20 stations, covering 70% of the population, within a year of approval.

Additional v.h.f. channels would be required to accommodate the complete chain of stations. These would be in the band of 95-97.6MHz in which the BBC now only have 7 frequencies, the remainder being used for non-broadcasting services. These are being cleared gradually and will be completely free within five years. The type of local stations envisaged by the plan will have an e.r.p. of 5kW and will cost around £80,000 each.

Although these local stations would broadcast local news, information and commentary programmes, it is anticipated that many would want to carry the Radio 1 broadcasts as a main evening sustaining programme. Provision has been made to arrange this facility.

Fourth V.H.F. Service: The band 97.6-100MHz is now used exclusively by non-broadcasting services. It is planned to make these eventually available for a fourth national BBC v.h.f. network at a capital cost of £4 million.

even if they use a proper car antenna, have been exempt. It is probable that this anomaly will disappear and licences will be necessary whenever a radio is used in a vehicle. The cost of a car radio licence is available for 25s. from major post offices.

£1,000,000,000


This is not the first prize for spotting all the mistakes in News and Comment but the output of the British electronics industry during 1968. The actual output

rose 19% over the previous year to reach a figure of £1,047 million.

Of this, exports and re-exports totalled £222 million while imports were worth £196 million. Consumer electronics are of course only a small part of the total industry and accounted for just under £150 million. The armed forces were the single largest customer spending £142 million. Computers and related equipment totalled £110 million of which £39 million was exported.

NEWS AND COMMENT...

Danish Speaker Kits

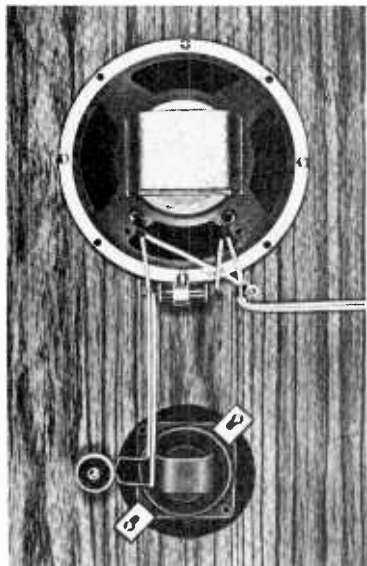

P. F. and A. R. Helme have been appointed sole UK distributors for *Peerless Fabrikkerne A/S* of Denmark. The company is the largest speaker manufacturer in Scandinavia and amongst their range are a wide variety of speakers, crossover networks and speaker kit systems.

Illustrated above is the *Peerless 2-8* which consists of a 6½in. woofer and 2½in. tweeter. Frequency response is claimed as 50-18,000Hz with a handling capacity of 8 watts. Price, less cabinet and baffle board is £6 7s. 10d. The impedance of the entire range is 8Ω.

P. F. and A. R. Helme, *Summerbridge, Harrogate, Yorks.*

IC FM TUNER KIT

The first f.m. tuner available in kit form using i.c.s. with pulse counting techniques is being marketed by *General Avionic Associates Ltd.*

The circuit was developed by *Marconi-Elliott Microelectronics* in conjunction with the distributors. The pulse counting technique eliminates the need for complex discriminator and i.f. transformers and removes the problems associated with the alignment and stability of this type of receiver.

The tuner has built-in automatic frequency control (a.f.c.) and with the inherent stability

of the i.c.s. a reliable and easily set up circuit is offered to the home constructor. The circuit in effect contains 44 transistors including those in the integrated circuits and although a fairly high number of discrete components are used, the entire tuner is built on a board measuring approx. 4 x 5½in. The price of the complete kit is £9 19s. 6d. plus 5s. postage from *General Avionic Associates Ltd., 9 Wimpole Street, London, W.1.*

HI-FI AND RADIO AMATEURS COURSES

The *Brentford Centre for Adult Education* is running two courses starting in late September which will be of interest to readers. The first deals with Hi-Fi and Tape Recording which includes both theory and construction; the series will include a section on film sound recording. The *Radio Amateurs Course* prepares students for the City and Guilds examination which qualifies successful candidates to become licensed "Hams".


Enrolment is in mid-September; further details from the *Adult Education Office, Hounslow Manor School, Holloway Street, Hounslow.*

Sony Radio TFM 8030L



New to the *Sony* range of portable radios is the TFM 8030L—a three band portable designed especially for the British market. At a recommended retail price of £29 15s. 0d., the radio covers m.w., l.w. and v.h.f. bands—in the case of the latter a.f.c. is incorporated. It will operate from three power sources, internal battery, car battery or from a.c. mains using an optional adaptor. The case is finished in a black padded leatherette.


TWO NEW TUNER-AMPLIFIERS

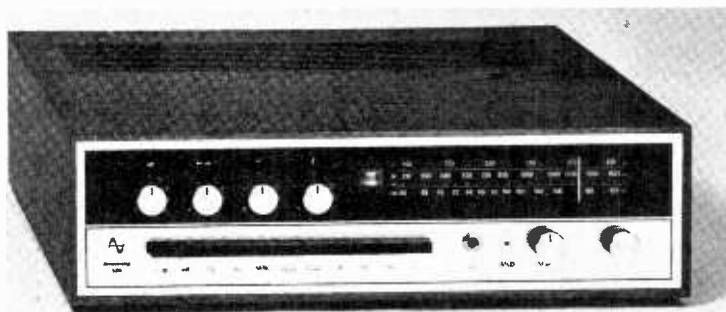

Two new stereo tuner-amplifiers (it seems wrong to call them radios) will be available from late August from *Armstrong Audio Ltd.* The 525 FM is a v.h.f. only model, while the 526 AM-FM (illustrated) includes coverage of the medium and long waves.

Both models have an excellent specification: power output of 25 watts per channel; inputs for magnetic and ceramic pickups and tape playback; tape recording and headphone outputs; bass and treble controls; bass and treble filters; a loudness control and tape monitor. There is a suppression control for f.m. inter-station noise and automatic mono-stereo switching on f.m.

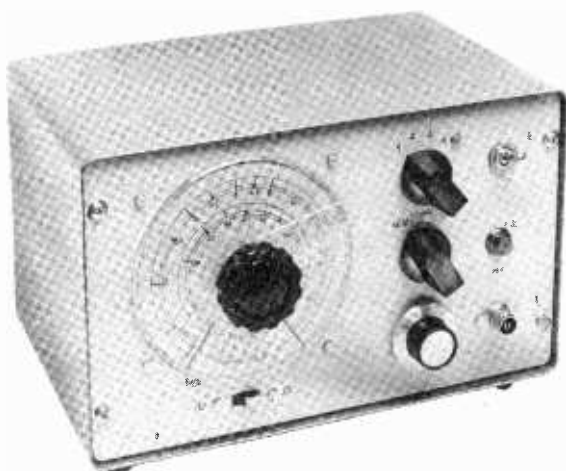The recommended prices are £87 16s. 9d. for the 525 FM and £98 15s. 6d. for the 526 AM-FM.



audio signal generator

C. JOHN COURTNEY

MANY circuits for sine-wave audio signal generators have appeared in the popular technical journals but few with both sine- and square-wave output have ever been presented particularly in simplified form and suitable for home construction from readily available components. This design (Fig. 1) is based on a transistorised Wien bridge oscillator published some time ago by Mullard Limited. The original circuit employed p-n-p transistors and delivered a sine-wave only output of approximately 1V r.m.s. The writer has retained the original Wien bridge circuitry which has been suitably modified for operation with silicon n-p-n transistors (except Tr2) and to which has been added a squaring circuit, switching for sine- or square-wave output and an attenuator network.

CIRCUIT DETAILS

The oscillator employs a Wien bridge network with fixed capacitive elements, frequency variation over the range 15 to 100,000Hz being obtained by varying the resistive elements (VR1 and VR2).

The n-p-n/p-n-p pair of transistors Tr1 and Tr2 between them form a high gain amplifier coupled to a n-p-n emitter follower. Feedback is provided by the unbypassed emitter resistors of Tr1 and Tr2 and also via the thermistor (TH) between the output and the emitter circuit of Tr1. The thermistor also ensures constant amplitude output regardless of small variations in supply voltage and temperature.

For sine-wave output the signals are taken from the emitter of Tr3 via S3 and S4 to VR3 which is the variable section of the output attenuation network formed by Tr7 (emitter follower) and the switched ladder attenuator R17, R18, R19, R20 and R21. This switched attenuator allows r.m.s. output levels of 1 volt, 100mV and 10mV, each range being continuously variable from zero to maximum. The variable attenuator VR3 is a linear control so that with a dial calibrated 0-10 the output signal levels can be determined with reasonable accuracy.

For square-wave signals, an overdriven amplifier (Tr4 and Tr5) has been employed ending with an emitter follower (Tr6). Note that the large value coupling capacitors (C12 and C13) are essential for

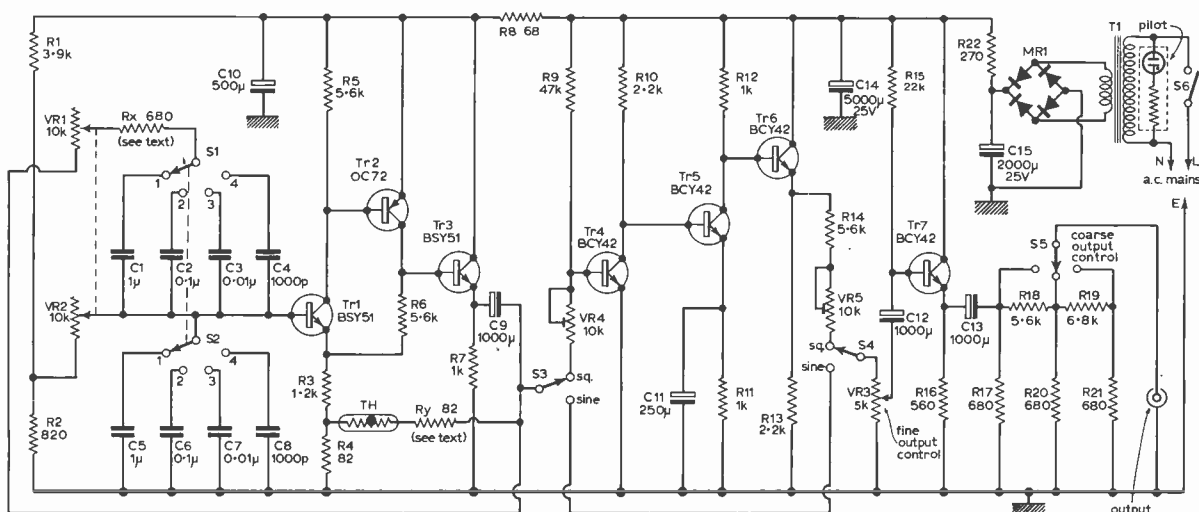


Fig. 1: Complete circuit of the sine and square wave audio signal generator.

a perfectly uniform square-wave right down to 15Hz. The square-wave signal from Tr6 is switched via S4 to the output network. The adjustment of the pre-set resistors VR4 and VR5 will be dealt with later.

The generator could be operated from batteries (12V) since the total current is only 30mA. An incorporated power supply does however ensure a constant voltage and is more economical if the generator is to be run for long periods. No stabilisation is necessary as the thermistor (TH) takes care of small fluctuations in supply voltage. However, more than adequate smoothing is essential to reduce a.c. ripple to an amount which can be considered as negligible, hence the use of the large reservoir and smoothing capacitors C15 and C14 respectively.

CONSTRUCTION

The prototype shown in the photographs was constructed to fit comfortably into an Electroniques Dinki-case type DD6106. A case of similar dimensions 10 × 6 × 6 in. could of course be constructed from aluminium or mild steel. Details for drilling the front panel are given in Fig. 2 and for the mounting of components on the panel in Fig. 3. The two transistor and components boards are also attached to the front panel as in Fig. 4 by means of aluminium angle $\frac{1}{2} \times \frac{1}{2}$ in. Plain Veroboard with a 0.15 in. matrix is used for the component boards. Component board 2 contains the transistors and components for the squaring circuit (TRs, 4, 5 and 6) and the output stage Tr7. The output attenuator network resistors, R17, R18, R19, R20 and R21 are wired directly to the switch S5. Component board 1 contains the Wien bridge oscillator Tr1, Tr2 and Tr3 and appropriate components including the thermistor TH. Board 2 measures 4 × 3½ in. and board 1, 4½ × 3½ in.

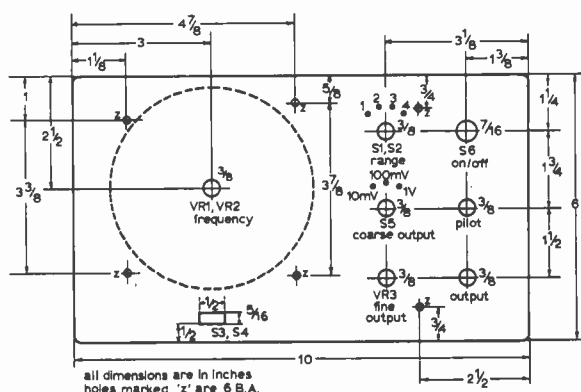


Fig. 2: Front panel dimensions and drilling details.

The power supply chassis is simply a small sheet of 16 s.w.g. aluminium mounted on pillars or threaded rod so as to clear the panel components beneath it (see Fig. 3). Some idea of the layout for components on the two boards and for the power supply can be obtained from the photographs. VR1 and VR2 however call for comment regarding the wiring. To obtain the requisite increase in frequency with clockwise rotation VR1 and VR2 must be wired as shown in Fig. 5. Note that RX which is

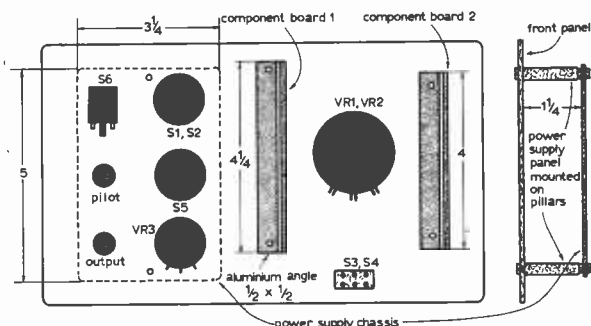


Fig. 3: Layout of panel components, viewed from rear. The power supply panel is shown on right.



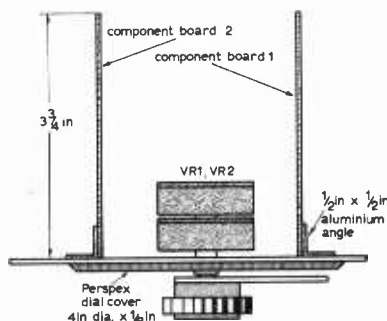


Fig. 4: The two transistor and component boards are attached to the front panel as shown on left. Details of the Perspex dial cover are also shown.

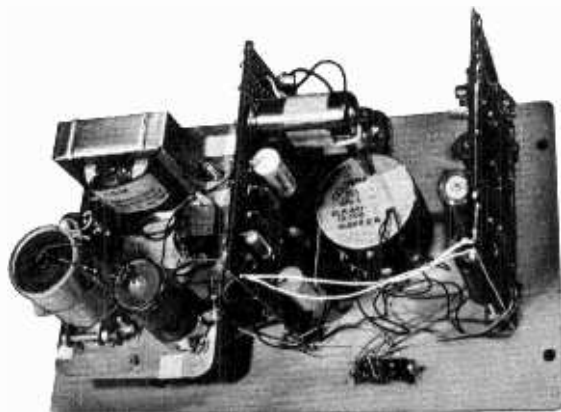

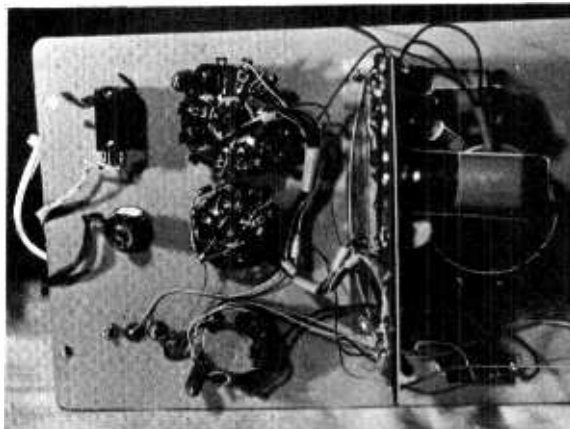The above photograph shows the internal view of the assembled instrument and below, before the power supply unit is fitted.



nominally 680 ohms is wired directly to VR1.

In order to give the finished instrument a nice appearance a circular Perspex cover was made for the frequency dial. This is optional of course and could be cut from celluloid or clear cinemoid. For the original, as shown in the photographs, $\frac{1}{8}$ in. thick Perspex was used; the 4 $\frac{1}{2}$ in. disc being first cut with a fretsaw. The disc was then mounted on an electric drill and the edge smoothed and bevelled with a Surform tool. The hair-line pointer was also fashioned from $\frac{1}{8}$ in. Perspex and fitted to a $\frac{1}{2}$ in. diameter control knob.

ADJUSTMENT AND TEST

First ensure that the Wien bridge section is operating correctly and producing a pure sine-wave. This can only be done correctly with an oscilloscope for although a small error in wiring or a faulty component might not stop the oscillator from working, one or the other could be the cause

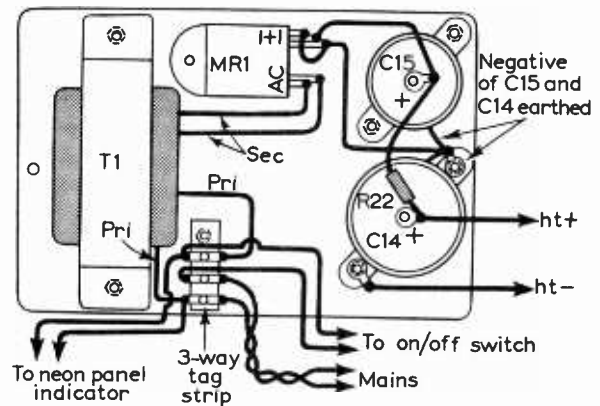


Fig. 6: Layout and wiring of the power supply.

of a poor waveform. The maximum output signal should be 1V r.m.s. plus or minus a few millivolts but can only be accurately checked with a valve voltmeter. To obtain an accurate 1V r.m.s. sine-wave output signal level some adjustment to the value of the nominally 82 ohm resistor Ry in series with the thermistor TH may be necessary. However, this should not be increased to greater than 120 ohms otherwise the waveform will become distorted.

The square-wave mark/space ratio is controlled by VR4 and again an oscilloscope is necessary to check the waveform. VR4 should be adjusted to obtain a 1 to 1 mark/space ratio. The output from the squaring circuit is pre-attenuated by VR5, which should be adjusted to obtain 1 volt

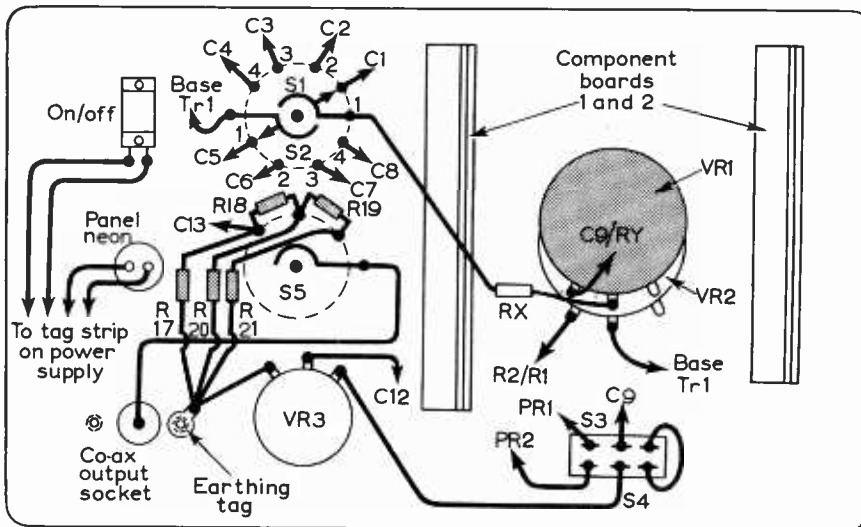


Fig. 5: Showing front panel wiring and layout.

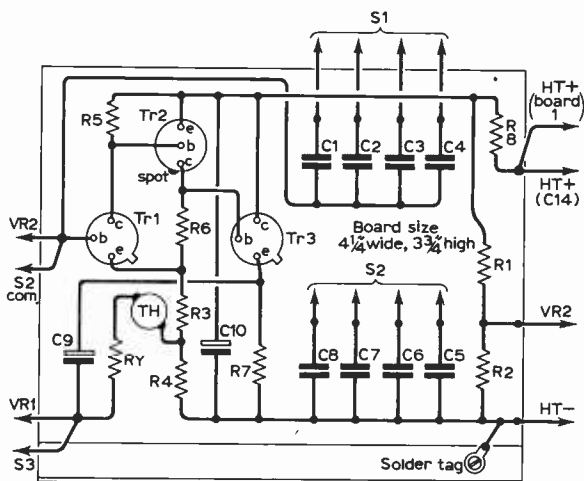


Fig. 7: Layout and wiring of component board 2 (oscillator). All transistor connections are viewed from the underside.

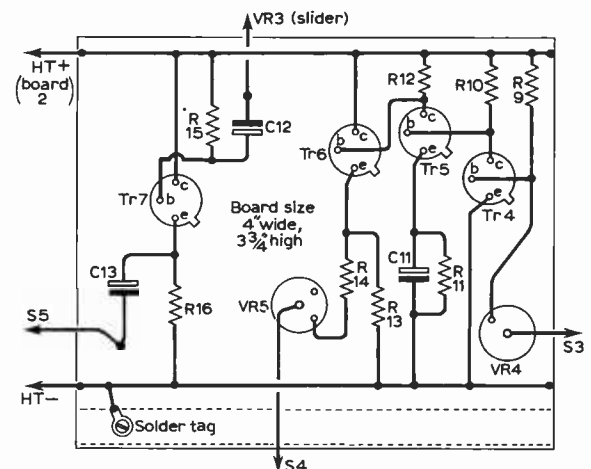


Fig. 8: Component board 1 layout and wiring (squaring circuit and emitter follower output stage).

r.m.s. at the generator output socket with the switched attenuator S5 in the 1V position and VR3 fully clockwise

The preceding tests are best made at a frequency of 1,000Hz as the settings of the controls should then hold good for the full frequency range of the generator. It is possible however, that the output attenuator network may require some adjustment, i.e., a small variation of R18 and R19 may be necessary to obtain an exact 100mV and 10mV respectively with VR3 fully clockwise. Otherwise the output voltages should be within $\pm 5\%$ of the rated output using the resistor values quoted.

★ components list

Resistors:

R1	3.9k Ω	R13	2.2k Ω
R2	820 Ω	R14	5.6k Ω
R3	1.2k Ω	R15	22k Ω
R4	82 Ω	R16	560 Ω
R5	5.6k Ω	R17	680 Ω
R6	5.6k Ω	R18	5.6k Ω
R7	1k Ω	R19	6.8k Ω
R8	68 Ω	R20	680 Ω
R9	47k Ω	R21	680 Ω
R10	2.2k Ω	R22	270 Ω
R11	1k Ω	RX	680 Ω (see text)
R12	1k Ω		

all 10% $\frac{1}{4}$ watt.

Potentiometers:

VR1/VR2	10k Ω + 10k Ω Colvern CLR5018/15F type G
VR3	5k Ω linear, wire wound
VR4, VR5	10k Ω miniature pre-set

Capacitors:

C1	1 μ F paper
C2	0.1 μ F paper
C3	0.01 μ F paper
C4	0.001 μ F paper
C5	1 μ F paper
C6	0.1 μ F paper
C7	0.01 μ F paper
C8	0.001 μ F paper
C9	1000 μ F 12V wkg. electrolytic
C10	500 μ F 12V wkg. electrolytic
C11	250 μ F 12V wkg. electrolytic
C12	1000 μ F 12V wkg. electrolytic
C13	1000 μ F 12V wkg. electrolytic
C14	5000 μ F 25V wkg. electrolytic
C15	2000 μ F 25V wkg. electrolytic

All paper capacitors, miniature, low working voltage.

Semi-conductors:

Tr1, Tr3	BSY51
Tr2	OC72
Tr4, Tr5, Tr6, Tr7	BCY42

Switches:

S1/S2	two-pole four-way rotary
S3/S4	two-pole two-way slide
S5	single-pole three-way

Miscellaneous:

Case (see text) 10 x 6 x 6in.; Thermistor TH, STC type R53; H.T. transformer T1, Henry's Radio type PS12; H.T. rectifier MR, Henry's Radio type 1H3 contact cooled; 0.15in. matrix plain Veroboard.

Frequency range	Range 1	15 to 150Hz.
Sine- or square-wave:	Range 2	150 to 1,500Hz.
	Range 3	1,500 to 15,000Hz.
	Range 4	15,000 to 100,000Hz.

Output level: Max. 1 volt r.m.s. with attenuation to 100mV and 10mV. Each range continuously variable.

Sine-wave: Distortion less than 0.75%.

Square-wave: Uniform 15 to 100,000 Hz.
Rise time better than 1 microsecond.
Mark space ratio 1 to 1.

Output level: ± 0.5 dB 15 to 100,000Hz.
Sine- or square-wave.

Output impedance: Nominal 600 ohms.

Note: Output load must not be less than 600 ohms on the 1 volt range.

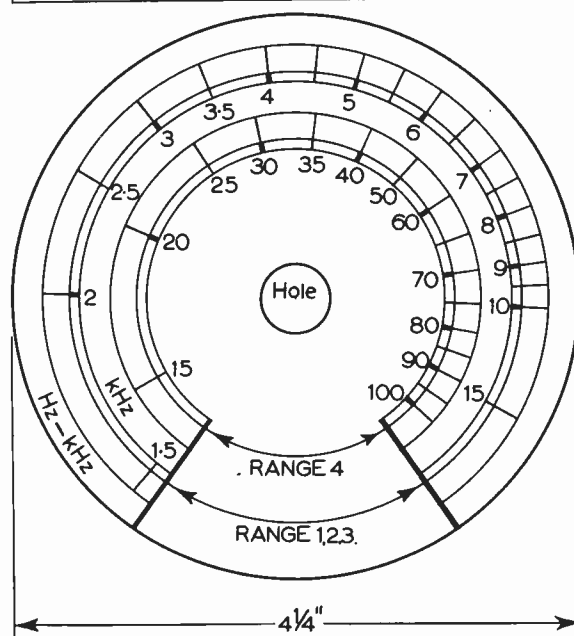


Fig. 9: The calibrated dial. This may be scaled-up to 4 1/2 in. diameter to give actual size.

CALIBRATION

The calibration of testing instruments always presents a problem unless one has another by which to check. For really accurate calibration it will be necessary to employ another generator and an oscilloscope and use the Lissajous pattern method to determine the requisite spot frequencies. This is how the prototype of the generator described here was calibrated and from which the dial given in Fig. 9 was obtained. Note that a small adjustment to frequency can be made by variation of RX (nominally 680 ohms).

continued on page 395

PRINTED CIRCUIT Design

A.G. BLEWETT

HOME-built transistor designs are invariably built on some form of printed circuit, the tendency these days being to use the readily available SRBP perforated board, or that with copper strip bonded to it.

Although this makes for rapid assembly, the result is by no means professional looking, works out comparatively expensive, and is not as compact as it might be by other means. The copper strip type of board costs about 5d. per sq. in., whereas ordinary copper laminate board can be obtained at around ½d. per sq. in.; 10 times cheaper!

Besides these considerations, a great deal of satisfaction can be gained by designing and preparing a tailor-made printed circuit, the finished job can then be said to be completely "home brewed."

PLANNING AND LAYOUT

In circuits where the capacitance of the copper is not significant, i.e., below v.h.f., such as a.f. low r.f. and switching circuits, almost any layout can be adopted, but the writer has found the best method being to follow the circuit diagram as far as is practical, with regard to the relative positions of components.

Knowing the size of the components, and the required distance between lead-out wires etc., a rough layout and connection diagram can be drawn, full size. All points to be connected together are supplied with this connection in the form of copper "blocks". Figure 2 shows the final design of a Wien bridge oscillator, which is one of the P.C. boards used in the construction of an a.f. sine/square generator, and shows the use of these copper "blocks". The circuit from which the design was evolved is given in Fig. 1. Note that those components not labelled on the theoretical diagram are external to the P.C. board. The drawing in Fig. 2 is shown full size.

The optimum position and size of these copper "blocks" is determined by trial and error, the writer having found that 3 drawings were necessary; (1) the rough layout as per the circuit diagram, (2) the layout drawn as neatly as possible taking into consideration component size and best use of space on the P.C. board, and (3) the final design, which is drawn on tracing paper, having ironed out any anomalies that may have arisen in designs 1 and 2. Difficulty may be experienced where far-reaching feedback paths or cross-connections are required, such as in bistable circuits in the latter case. Here, the best solution lies in using "link" wires, an example of which occurs between the collector of Tr3 and the emitter of Tr2 in Fig. 1.

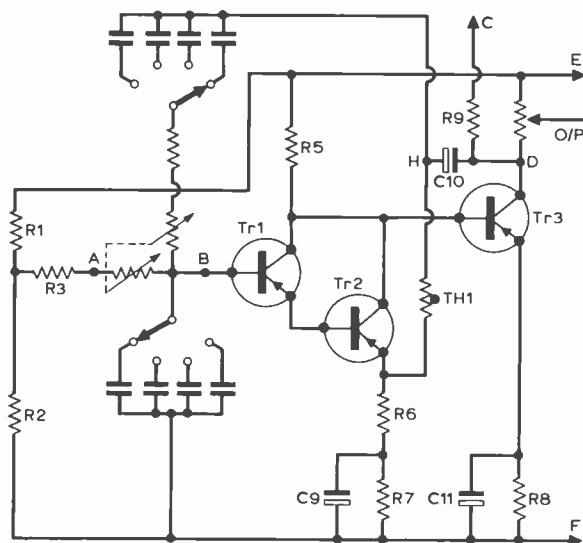


Fig. 1: Circuit of a wien bridge audio oscillator. The points marked A, C, D etc. are explained in the text.

A link wire is used to connect the thermistor and Tr2 emitter together (Fig. 2). Had this not been done, a thin copper strip would have had to be designed to wend its way through the other copper blocks. The link wires go on the side of the board away from the copper.

TRACING AND ETCHING

The laminate board is cut to the required size with a fine saw and the edges cleaned up with a file. The copper should now be scrupulously cleaned using domestic wire wool. Cleanliness at this stage is most important, as any oxide impedes the etching process.

The final design on the tracing paper is then lined up on the board, and with carbon paper interposed between paper and board, the design is traced to the copper. During this process the paper can be folded and stuck at the back with Sellotape, to hold it steady on the board. There is no need to mark the position of the holes at this stage. Transparent tape (Sellotape) is then stuck in strips over the copper, so as to cover it completely. The board can now be handled with no danger of the design being rubbed off.

Using a steel rule and a sharp modelling knife, the areas to be retained after etching (the blocks) are now cut out, and can be removed with a pair of

tweezers. Care should be taken to apply only such pressure to the knife that is required to cut the Sello-tape, and not mark the copper underneath excessively.

The copper side of the board is now painted, car touch-up enamel is ideal for this as it dries rapidly. The remaining adhesive tape will have acted as a mask, and when the paint is dry it is removed, again using tweezers, to leave the accurate design in paint on the copper surface.

The etching solution used comprises 30% ferric chloride, 1% dilute hydrochloric acid, and 69% water, per unit volume. These chemicals are readily available from the larger chemists, and may be ordered from the others. The acid can be omitted if desired, but is included to speed up the chemical etching process. A depth of about half an inch of this solution is poured into a shallow plastic or glass container, and the prepared board put in. Avoid physical contact with the etchant—rubber gloves should be worn to protect the hands.

Left alone a circuit board such as given in the example will take about 45 minutes to etch completely, but if the solution is agitated frequently, etching can be complete in around 25 minutes. Inspection will determine when it is complete, ensure there are no "spots" or "hairlines" of copper left exposed, and that the edges of the painted areas are clean cut in appearance.

The board is now washed in water to remove all

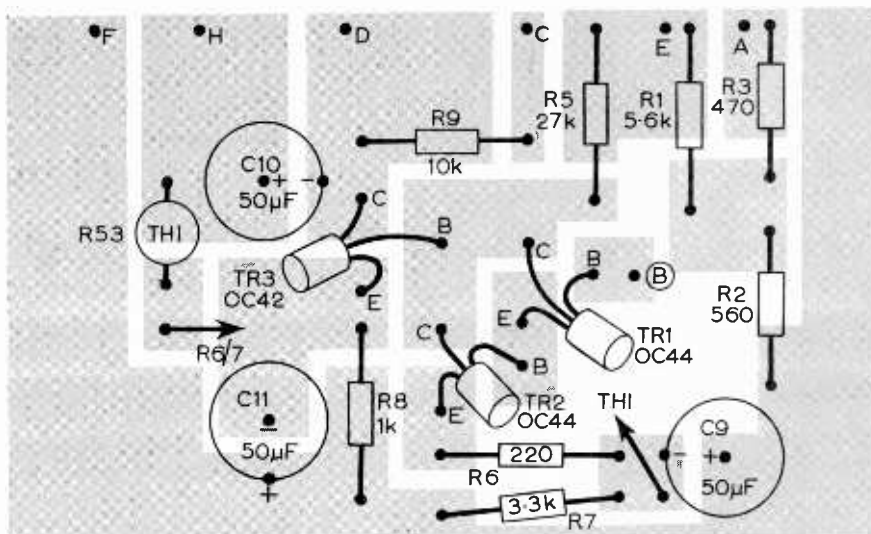


Fig. 2: Printed circuit design for the circuit given in Fig. 1.


traces of etchant, and the paint cleaned off. This can be done using a solvent for the paint (acetone in the case of cellulose enamels), or by carefully rubbing with domestic wire wool. The writer prefers the latter method as it makes far less mess, and leaves an ideal soldering surface.

The tracing paper design is now positioned over the etched circuit, and the position of the holes marked using a scribe. The writer has found a 3/64in. drill ideal to take component lead out wires, but any size may be used as required, the only precaution being necessary is that the holes should be drilled from the copper side, to avoid lifting the copper foil.

Not including the original outlay of chemicals the board shown cost the writer approximately 2d., not including labour, but we don't do it for the money anyway do we!

AUDIO SIGNAL GENERATOR

—continued from page 393

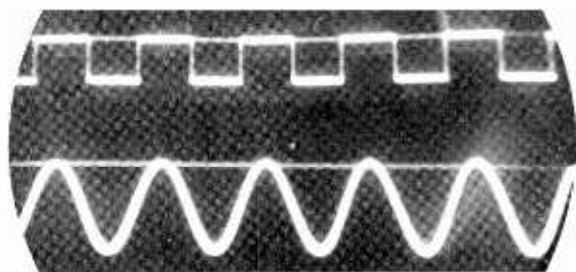

The photograph above shows oscilloscope traces of square and sine wave outputs at 1kHz, that below shows square wave output at 15kHz.



The oscillograms show actual photographs of the generator waveforms displayed on a Cossor 1049 Mk. III Oscilloscope.

One final point concerns the h.t. voltage. This must be as near 12 volts as possible at the junction of R22 and C14, with the generator operating on sine-wave output. If not, then adjust the value of R22 by a small amount as necessary. The recommended mains transformer (T1) only should be used.

R S G B EXHIBITION 1-4 October 1969

10 am—9 pm daily

Don't forget to visit the PRACTICAL WIRELESS stand at the R S G B EXHIBITION, Royal Horticultural New Hall, Greycoat Street, Westminster, London, S.W.1.

MONO-STEREO

JAMES HOSSACK AMPLIFIER

THE newcomer to stereo, unless he has previously been an enthusiast in the field of mono hi-fi and consequently knows precisely what his requirements are likely to be, is usually a little bewildered by the wide choice of equipment available. Most record players sold today, even those in the medium or lower price range, are fitted with a stereo pick-up cartridge with provision for adding an external amplifier, so that advantage may be taken of the stereo characteristics of modern recordings. It would be necessary to construct or purchase a small transistor amplifier and speaker, which, suitably positioned and wired to the player, will be capable of providing a surprisingly inexpensive introduction to the exciting dimension of "stereo sound". Unfortunately, perhaps because of its simplicity, this solution is not always the best one. In the first place, there are now two sets of batteries to be replaced (assuming the built-in amplifier were also transistorised), and, secondly, the volume and tone controls for each channel are independent, and have to be manipulated simultaneously when alterations of the settings are required, with the result that correct balance between the two channels is difficult to maintain. It is then that thoughts begin to turn to the possibility of procuring a single amplifier for both channels.

There is a further consideration. V.H.F. radio broadcasts are now transmitted in stereo over a large part of the country, and can be made available by the addition, to the average radio or tuner, of a simple decoder arrangement, *provided* a 2-channel amplifier is available to handle the resulting dual signals. Finally, and perhaps of more direct interest to the experimenter, is the possibility of feeding a stereo signal simultaneously to the amplifier from microphones, tape head, or even musical instrument pick-up coils. For this latter purpose, a fairly high-gain amplifier is necessary, and since matching transformers may have to be used before the input, special precautions will have to be taken as regards pick-up of extraneous hum and other noise by careful screening of the input to this section of the equipment.

The amplifier which is described here will be found eminently suitable for experimental applications of the type mentioned, as well as providing a useful stand-by


amplifier for a hi-fi stereo system. It was designed, originally, for use with a *mono* v.h.f. tuner, with the additional consideration that it could also be used as the "second channel" for a cheap record player of the type described above. Valves were chosen in preference to transistors, because the record player in question used a valve line-up.

Although v.h.f. stereo broadcasts had not reached the writer's area, and a mono amplifier was therefore considered at the time to be sufficient, it was decided to make provision for the future, and sufficient room was left on the chassis for the construction of a duplicate amplifier. In addition, the original intention having been to provide mixing facilities for microphone or tape input for announcements, etc, as required, a low-noise, high gain audio pentode, together with the appropriate mixing controls, was included in the amplifier circuit. Partly to preserve the symmetry of the layout, and partly with an eye to possible future applications, these mixing facilities were duplicated when the second channel was constructed. The result is a very useful and versatile amplifier with a performance in the medium to high-fidelity range and an output of about four watts per channel, which can, moreover, be built up in sections and added to as time and the available budget permit.

A chassis must be chosen of sufficient size to accommodate, eventually, both channels, together with a power supply of ample reserve capacity. The amplifier can then be constructed in one of four ways; as a simple record player/tuner amplifier for one channel only; as a dual microphone and p.u./tuner mono amplifier with mixing facilities; and finally as a stereo amplifier using one or both of the preceding arrangements. Further modifications to suit the individual experimenter's needs are also possible.

Circuit

The circuit of the complete stereo amplifier, including both microphone preamplifier sections, is shown in Fig. 1. It will be observed that, though dual-purpose valves are used, none of these is common to both channels, which can thus be constructed and operated quite independently of each other. For descriptive purposes, it is convenient to divide each channel into a main amplifier and two preamplifiers. The main amplifier comprises one-half of an ECC83 feeding into an ECL82 triode-pentode, which provides an output power of about four watts, with an overall distortion figure of under 2% when the normal negative-feedback circuit in the output stage is fully operative. The remaining half of the ECC83 forms a preamplifier for use with a record pick-up or high-output tuner. In order to bring the total harmonic distortion figure down to less than 1.5%, two further negative feedback circuits were incorporated, one over each ECC83 half-triode. Despite the resulting reduction in gain, full power output can still be obtained with 50-60mV of input signal.

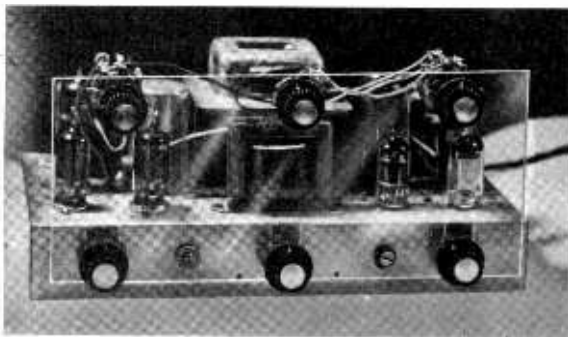

View of the assembled amplifier.

Main Amplifier

C6 is the coupling capacitor which feeds both pre-amplifier outputs to the second ECC83 half-triode, this functioning as the first stage of the main amplifier. Like the first half of the ECC83 this triode also has a proportion of its output fed back, via R8, in order to obtain a more linear characteristic. C8 is used to couple this stage to the triode section of the ECL82. The values of both capacitors C6 and C8 have been purposely kept smaller than is usual with a circuit of this type in order that some attenuation of bass will be obtained. Since bass boost is incorporated at a later stage, the overall effect is to provide a "normal" bass response at about mid-position of the boost control; but, if boost only is desired, with no attenuation, this can easily be achieved by increasing the value of these capacitors slightly. Do not go however, above about 0.05 μ F.

There are no unusual features in the triode-pentode circuit. R14 is necessary to prevent parasitic oscillation, and should not be omitted. If the amplifier is being constructed for stereo operation from the outset, the impedance and power-handling capacity of the loudspeakers, together with a pair of matched transformers, will probably already have been chosen. Even if the second channel is to be added at a later stage, it is a good plan to obtain a suitable pair of transformers, similar though not necessarily identical, since matching of components in the two output stages will ensure more satisfactory operation of the bass and balance controls, which, as explained in the next section, are incorporated in the negative feedback line to this stage.

Controls

The arrangement of the gain-controls (two single and one ganged) has already been dealt with. Potentiometer VR2, in conjunction with C10, is a conventional treble cut arrangement, and provides equalisation for records and v.h.f. radio. Treble boost was felt to be unnecessary. The arrangement of bass and balance controls, although a little unusual, has been found completely satisfactory in practice, although it does call for one or two special precautions. Examination of Fig. 1 shows that one side of the output transformer secondary is taken directly to the ECL82 triode cathode, which is earthed via R11. The feedback voltage is thus developed directly across this resistor. However, no actual feedback can result unless the other secondary lead is also at, or near, earth; any impedance present at this point being regarded by the transformer as if it were directly in series with the feedback line. The mode of operation of VR3 and VR5 will now be clear. The latter controls the degree of feedback distribution operating on each channel; the former renders this feedback frequency-selective, so that, for each channel, the setting of VR3, in conjunction with the reactance of C12, determines the extent of feedback reduction, and hence the boost, at the lower frequencies. It will be seen, therefore, that in order to obtain an equal degree of lift on both channels in the bass region of the response curve, the balance control must be in approximately the correct position at the outset, otherwise, feedback may be insufficient on one channel to permit satisfactory boost to be obtained.

The second precaution is to ensure that no external earth connection is made directly to the speaker or the output transformer secondary. This is important if the amplifier is being used, for example, in a small hall.

★ components list

Resistors:

R1	R51	100k Ω	R12	R62	100k Ω
R2	R52	1M Ω	R13	R63	1M Ω
R3	R53	2.2k Ω	R14	R64	1k Ω
R4	R54	270k Ω	R15	R65	470 Ω 2 watt
R5	R55	270k Ω	R16	R66	100k Ω
R6	R56	8.2M Ω	R17	R67	2.2M Ω
R7	R57	100k Ω	R18	R68	8.2M Ω
R8	R58	100k Ω	R19	R69	220k Ω
R9	R59	12k Ω	R20	R70	470k Ω
R10	R60	8.2M Ω	R21	R71	820k Ω
R11	R61	100 Ω	R22	R72	220k Ω

(All resistors are $\frac{1}{2}$ watt carbon, 10% tolerance unless otherwise stated)

Capacitors:

C1	C51	0.1 μ F
C2	C52	25 μ F 25V elec.
C3	C53	0.1 μ F
C4	C54	32 μ F 350V elec.
C5	C55	100pF
C6	C56	0.015 μ F
C7	C57	0.022 μ F
C8	C58	0.015 μ F
C9	C59	0.1 μ F
C10	C60	0.022 μ F
C11	C61	25 μ F 50V elec.
C12	C62	4 μ F 9V elec.
C13	C63	0.015 μ F
C14	C64	0.027 μ F
C15		32 μ F 350V elec.
C16		32 μ F 350V elec.

(All capacitors paper, 350V wkg. except where stated)

Potentiometers:

VR1	VR51	250k Ω log.
VR2	VR52	50k Ω log. ganged
VR3	VR53	25k Ω log ganged
VR4	VR54	500k Ω log ganged, with switch (S2)
VR5		1.5k Ω linear
VR6	(if used)	500k Ω linear (see text)

Transformers:

T1	T51	Output transformers, pri. matched to ECL82, sec. to 3 or 15 Ω speaker
T2		Mains transformer 250-0-250V 150-200mA; 5V 2A; 6.3V 5A

Valves:

V1	V51	EF86
V2	V52	ECC83
V3	V53	ECL82
V4		GZ34 or alternative

Miscellaneous:

S1 Single-pole rotary or toggle switch; L1 Smoothing choke, 20H 150mA; several 3, 4, and 5-way etc tag strips; Screened cable; Co-axial sockets (coloured stereo type); L/S output sockets; 6 B9A valve-holders; 1 octal-base holder; 1 clip for upright-mounting double can electrolytic; 6 pointer knobs.

Here, facilities are sometimes provided for a low-voltage extension speaker connection which dispenses with the

continued on page 411



Sign here..!

for your miniature soldering iron.

from 32/6

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts.



G18 watts. Fitted 3/32" bit for miniature work or production lines. Interchangeable spare bits. 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/3.



E20 watts. Fitted with 1/4" bit. Interchangeable spare bits 1/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 25/-.




ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Very high temperature iron. For 240, 220, 110, 24 or 12 volts. From 35/-.



F40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6. Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit

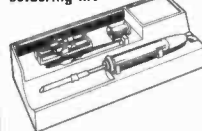

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits. 1/8", 3/16", 1/4".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

31/-



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

- ☐ Please send me the Antex colour catalogue
- ☐ Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |

I enclose cheque/P.O./cash value

NAME

ADDRESS

P.E.10

PLEASE FILL IN THE COUPON FOR

★ FREE FLOG LIST No. 4

★ A FEW
EXAMPLES !

★ QUANTITY !
DISCOUNTS !

★ GUARANTEED !
NEW GOODS !

TRANSISTOR RADIOS. Large 11 waveband AM/FM Radios many refinements, limited number. Recommended list price over £60. Many Others Listed from only 49/-!

AMPLIFIERS. 10 watt high quality. Type AC 106 Transistorised. Bass and Treble Controls. Complete with built in Mains Power Pack. Many Others Listed from only 49/-!

AM/FM STEREO TUNER AMPLIFIERS with Stereo Multiplex. Famous make. 10W output. Full length S.M. scale. "Rosewood" case. Recommended list price over £40. Absolutely complete in sealed case.

LOUDSPEAKERS. Bookshelf size In Heavy Veneered "Rosewood". Teak or Mahogany. Infinite Baffle Cases with most attractive Tygan Fronts. Size 12 x 8 x 6in. High compliance "Piston" wide frequency. 8 ohms Drive Unit (8 watts USA). Most excellent reproduction for the price. Ideally matched for the above Tuner Amplifier.

39 GNS.

9 1/2 GNS.

25 GNS.

6 GNS.

POST NOW FOR FREE "FLOG LIST"

To Technical Trading Co., Park Crescent Place, Brighton
Please send free "Flog List", without obligation, to

NAME _____
Block Capitals Please
ADDRESS _____

PW10.69

TECHNICAL TRADING

ANNUAL STOCKTAKING

SUMMER SALES

INCLUDING
"FLOG LIST" ITEMS
NOW ON AT ALL
BRANCHES

CALLERS—ENQUIRIES

WELCOMED WITHOUT OBLIGATION

★ LONDON: 10 Tottenham Court Road Tel: MUS 2639

★ PORTSMOUTH: 350-352 Fratton Road Tel: 22034

★ BRIGHTON: Devonian Court, Park Crescent Place

★ SOUTHAMPTON: 72 East Street

★ BRIGHTON: 6 Queens Road

Tel: 25851

Tel: 23975

All Mail Orders to Devonian Court (Orders Recorded 24 hours—Brighton 680722)

AND 100's MORE !!!

- ★ Power Packs
- ★ Cartridges
- ★ Record Player Decks
- ★ Tape Recorders
- ★ Stereo Headsets
- ★ Valves
- ★ Tools
- ★ Microphones
- ★ Test Equipment
- ★ Tuners
- ★ Amplifiers
- ★ Transformers
- ★ Transistors
- ★ Potentiometers
- ★ Cabinets
- ★ Aerials
- ★ Speakers
- ★ Etc., Etc.



★ TAPES ★

We offer you fully tensilised polyester/Mylar and PVC tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Standard		Long	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double		Triple	
3in. 300ft.	3/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/-	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	7in. 3,600ft.	44/-
Postage 1/- reel.		3in. 600ft.	8/6

Post free less 5% on three reels.

Quantity and Enquiries invited.
NOTE. Large tape stocks at all branches.

0.0005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/8 each. 24/- doz.

ELLIOT SEALED CONTACT REED RELAY

Three circuits closed by 3V or 100MA. 9/6 each.

SLIM TUBULAR MICROPHONE

For hand holding or frontal suspension—lever switch—high impedance with lead and plugs for cassette tape recorder but suitable for most amplifiers. 18/6.

500 MICRO AMP MOVING COIL METER

2in. flush mounting round meter, ex Government but unused and perfect. 17/6.

PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.

5000mFd 12V CONDENSER

Tubular size 3in. x 1in. dia. made by Plessey. 4/8 each, 48/- doz.

5A. 3 PIN SWITCH SOCKETS

An excellent opportunity to make that bench dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/6 post and insurance. (20 boxes post free.

5in. x 5in. Printed Circuit Board
Ideal for dozens of projects. Heavy copper on 3/32in. sheet, 1/8 each or 15/- per dozen.

MAINS MOTOR

Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters etc. New and perfect. Snp at 9/8. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

DIGITAL CLOCK

An imposing instrument ideal for modern reception centre or for Managing Director's office—definitely a showpiece to create interest and efficiency—mains frequency controlled so always keeps right time without adjustment—in black semi-matt perspex case—made up, tested and guaranteed—offered for only the cost of components £29.10.0, post and insurance 10/-.



ATLAS SLIMLINE FLUORESCENTS


THE TWENTYLITE



A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1 unit). Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. Postage and insurance 6/6 extra.


1 WATT AMPLIFIER & PREAMP

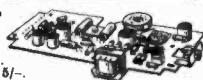5 transistors—highly efficient, made for use with tapehead G4 but equally suitable for microphone or pick up—limited quantity 39/6. Full circuit diag. also shows tape controls 8/-.



DREAMLAND CLOCK SWITCH

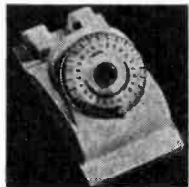The wonderful DREAMLAND mains operated clock switch will automatically switch your blanket on and off each evening and you will always have a warm bed. It's luminous; you can always see the time and it's a really beautiful unit. An ideal gift. Can also control tape recorder, radio, lamp, etc., up to 500 watts. 39/6 plus 3/6 post & ins.



FLEX CABLE BARGAIN

23/0076 triple core P.V.C. covered, circular, normally sold at 1/6 yd. Our price, 100 yd. coil £3.19.6. Post and insurance 6/6.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

OUT OF SEASON BARGAIN

Famous Norvic electric blanket claimed to be the most reliable in Britain. We offer at less than wholesale price "Corona de luxe" model, this has flame resistant super safe element and double-thick fleecy cover attached by press studs—just undo the press studs to wash cover—double bed size 60 x 48in.—with control switch giving choice of three heat—in presentation box showing regular price £9.9.0—we offer at £5.19.6, post and ins. paid.

THERMAL CUTOUT

A miniature device 1in. dia. on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron switch off, etc., etc.—15 amp contacts open with flame—radiant or conducted heat. 1/8 each, 15/- doz. £5 100.

STEREO CABINET

Size 25 x 14 x 9 1/2in. deep—speaker compartment each end—centre portion with hinged lid and removable bottom has platform for autochanger and room for amplifier—two tone (red and grey) rexine covered by loud speaker ends need metal grille—with handle and clips—22/6, carriage and packing 15/-.



2 1/2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/2 kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £8.15.0. Post and ins. 7/6.

COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. 26 doz. post paid.

500W IMMERSION HEATER

For small process tanks, etc., 200/240V 4 1/2in. into tank, 2 1/2in. outside of tank, dia. approx. 1 in., chrome plated 14/6. Post and insurance 4/6.



ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH

Also 102/3 Tamworth Road, Croydon

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

I HAVE, at short notice, taken the position of temporary editor of this column. I would like to receive many reports and letters from readers of the column so I can estimate exactly what you require from these articles. This particular column is inclined more towards the DX side of the hobby than previous articles and I would be interested to hear if this is what the readership requires.

The **Limerick City Short Wave Radio Club** now issues certificates for the verification of 15, 30 and 50 countries on the Broadcast Bands. The awards can be obtained by sending a list of the QSL's that you hold and a 1s. postal order to: *Limerick City SWRC, 7 Colbert Park, Janesboro, Limerick City, Ireland.*

Propagation forecast for the month of September is as follows: Europe 7 and 9MHz; North America 17 and 21MHz; South America 17 and 21MHz; Africa 11 and 15MHz; Asia 11 and 15MHz, and Oceania 11MHz. These figures apply to reception in Europe during the period 1700-2100, figures for the remainder of the 24 hours are easily estimated if you remember that darkness anywhere on the path lowers the frequency whilst daylight increases the frequency.

AFRICA

Biafra: *Radio Biafra* is often heard at this QTH on 6144 between 2300 and 2315.

Liberia: *ELWA*, Monrovia, Liberia has changed frequency to 15095 and can be heard in Arabic from 2130 until 2200 when they close down. Identification in English is given at close down.

Morocco: *Radio Rabat* has three new frequencies of 6045, 6170 and 6190.

Ruanda: The new 250kW relay of *Deutsche Welle* is testing from 0000 to 0300 on 17865.

ASIA

Kuwait: The most recent programme schedule available for the *Kuwait Broadcasting Service* is as follows: 0400-0600 English for India on 15150; 0900-1100 Arabic for Europe on 15430; 1300-1905 Arabic for N. Africa on 21685; 1600-1900 English for Europe on 15405.

Nepal: *Radio Nepal* is making test transmissions between 0220-0700 and 1300-1600 on 11970.

Syria: *Radio Damascus* has replaced 15165 by 15270 for the Foreign Service transmissions from 1730-2100.

UAR: *Radio Cairo* is requesting reports on its test transmissions on 9630.

Times
in GMT

Frequencies
in kHz

THE BROADCAST BANDS

Malcolm Connah

EUROPE

Andorra: *Radio Andorra* is reported to be using English from 2300 until 0400 on 5995. I would like to hear from anyone who can confirm this.

Portugal: *Radio Portugal* has a new transmission to Africa at 1715 on 15345 in parallel with 21700.

NORTH AMERICA

Hawaii: The *Billy Graham Evangelistic Association* is planning to build a 500kW Short Wave station on the island of **Maui**.

Grenada: The *Windward Islands Broadcasting Service (WIBS)* is now using the frequency of 21690 up to close down at 2245.

OCEANIA

Australia: The *ABC* has changed frequency from 15180 to 15160 for the 2000 to 0830 transmission.

SOUTH AMERICA

Guatemala: Dennis M. Evans, an ex-member of the ISWL, is now a volunteer technician at *La Voz de Nahuala*. The station operates on 3360 between 2300 and 0300 except Tuesday, Thursday and Sunday when it opens at 2000. The transmitter used by the station is a Philips 1kW. Several reports have been received from American listeners and Dennis hopes to receive the first report from a European listener in the near future.

Netherlands Antilles: The *Radio Nederland* transmitter at **Bonaire** does not use the frequency of 9715 despite several reports to the contrary.

In conclusion here is a list of special Latin American holidays (my thanks go to the Cimbler DX Club for this item). These holidays often lead to extended schedules and good DX. September 14 Nicaragua; Sept. 15 El Salvador, Guatemala, Honduras, Costa Rica and Nicaragua; Sept. 16 Mexico; Sept. 18 Chile; Sept. 24 Dominican Republic; Sept. 29 Paraguay. October 3 Honduras; Oct. 9 Ecuador; Oct. 12 Costa Rica, Ecuador, El Salvador, Guatemala, Honduras, Mexico, Nicaragua, Argentina and Chile; Oct. 20 Guatemala; Oct. 21 Honduras. November 1 Guatemala and Peru.

73s, good listening and hoping to hear from you soon.

THE AMATEUR BANDS

David Gibson, G3JDG

MUCH the same conditions as last month prevail and, alas, no real improvement in 10 metres. The short skip on 20 has been rather more noticeable. There's always something weird about hearing odd G stations at S9 on this band. One scribe informed that the sunspots were rather reluctant to decline and that the count was still high. However, at my QTH, 10 metres has been very quiet indeed. The JDG solid state tx, running a cool 30 milliwatts (v.f.o. and buffer only) has produced results on the home receiver but not on anyone else's apparently.

Almost all the logs sent in were for 20 and 15, although one or two did reckon to have heard a mumble or two on 10. Nobody even mentioned topband (shame on you all) and 40 metres was only referred to in a highly offensive fashion. Data available under plain cover!

TWENTY/FIFTEEN

Quads and beams proved useless compared to a 380ft. long wire according to **Robert Dinning** (Scotland) who made the practical comparisons. Verticals on 15 and 20 fared better though. The earth system is a car radiator buried 6ft. down below the spring line of a nearby river. (What happened to the driver?) The back-up equipment is an HA350, RQ10, PR3OX and a pair of stereo headphones. On 20 metres s.s.b. the log reads—CP5DB, HB9FC/P/VP9, HBØAG, HP9FC/MM, JX10M, KP4AMI, LZ1XA, MP4TCN, OX3MT, OY9LV, PJ2CJ, PJ6ZF, TI2TH, VK6FD, VP2KF, YA1DAN, ZA1KAA, ZP5CE, 3A1TL, 5A1TL, 5H3MA, 5Z4DW, 6Y5AK, 8R1G, 9A1K.

Fifteen s.s.b. produced—AP2MR, CEØAE, CN8HL, CR7IC, CT2AU, CX7BF, ELØC/MM, ET3USA, FL8DJ, HBØAFM, HR1KAS, HS1AF, JA2AHV, JA4WI, JA7GIV, JH1QLW, KZ5MC, MP4BGX, PZ1BX, U78AJ, VK2FU, VK9KY, VK9XI, VP8KL, VS6AA, WB6AGZ/MM (U.S. hospital ship off 3W8 coast), XE1CE, YA1AR, YA1DAN, IJM, YBØACC, YN1FR, 7P8AB.

John Moore (Leics), found topband and 80 useless, while a peep at 40 produced PY-type signals promptly blotted out by BC or EU's. John favours 15 which, he says, is open to 9M2/9V1 from around 1500 hrs onwards. In the evenings the CR6/JA contingent are a constant feature. John's best on 15 were—CN8HL, CR6CA, EL2I, ET3USA, F6ABP/FC, JA3LVT, JA3MIY, JH1FZM, KG4AA, KV4AD, MP4BHL, VE3ACD, VS6AA, VS9MB (Gan), W6FEX, YA1JK, 4X4GT, 4Z4HF, 6W8DY, 7Z3AB, 9H1R, 9M2BD, 9V1OE, 9X5AA. All these s.s.b. except the MP4 on a.m. Gear is a CR100/2 plus 60ft. end fed.

Ian Poole (Yorks), sent a picture of a very neat shack. Equipment spotted by your scribe included a KW/Geloso converter fed into a 19 set which, in turn, is fed by a 60ft. long wire. (So, it was a big picture!) The 15-metre log reads—AP2MR, CEØAE, HS3 ML, KR6VX, MP4TAF, VP2AW, VS6AL, XW8CS, YA1AR, YA1SG,

ZS3HX, 7P8AB, 9M2BD, 9N1MM, 9V1CN.

If you've been taking "A" level exams and you reside at Spalding in Lincolnshire, you stand a very good chance of being **K. Tatnall**. If you are he, then you'll know all about your modified "Clubman" receiver and 65ft. aerial not to mention you hearing—EA6AR, EA8FG, EP2BQ, EL2Y, HI8LA, HK1BQR, HP1XS/MM, JA1PNA, JA1WEK, JA3ERG, JA3MNP, JA4DGG, JA8DO, KP4DEY, KR6DI, MP4TAF, PY1TX, SVØWJJ, TF2WLJ, VP5AA, VP8KD, VS5PH, VS9MB, YV4RZ, ZF1GC, ZP5CN, 4X4RQ/AM, 5N2ABG, 5Z4LS, 7Q7RM, 9G1DY, 9M2BO. Oh yes, you heard that on 15 s.s.b. remember?

Just think, at the exact spot on the whole world map, just exactly where **Michael Pipes** is living, there's a Trio 9R—59DE as well. By the most amazing coincidence, this is also the exact location of a 66ft. end fed too. And by the very strangest of happenings, while all these other things were together, who should come along but—AP2MR, CE3AIA, DU1LP, FH8CD, HC2MM, HBØGJ, ITØARI, PY7PT, TA3AB, VU2DK, VQ9EP, VS9MB, 4S7PB, 4U1ITU, 5L2BJ, 5N2ABG, 6W8DY, 9M2BD, 9Q5GE, 9V1PA, 9Y4VT. All s.s.b. on 15.

ELSEWHERE

Not many logs for the other bands this month. **Stephen Cole** wrote while on holiday in Devon where the temperature was 80 degrees plus—and that was in the frig! Back home in Monmouthshire Stephen runs a Trio JR60 and a 25ft. vertical. He sent a fab log for 15 which I'm not putting in (write out 500 times—JDG's a baddie) but the list for 80 reads—F9RY/FC, PY7ASQ, WB2NCS/VP9, W1AW, VS9MB, YV4QG, 9H1BQ, 9Q5EP which just goes to show what's about.

Let's see now, Carisbrooke, Isle of Wight, JXX converter into a tuneable i.f. at 28-30MHz into the receiver, a GC-1U. No name at the bottom but the log for two metres looks good. Stations 80-110 miles away—F1RJ/P, F5NS, (both these in Normandy), G2JF (Ashford, Kent), G3KDG (Devon), G3OZF (Essex), G3UCC (Somerset), GC8AZZ/P (Jersey, C.I.). Further afield in the 140-160 mile range—F1APK (Brittany), F1TC (Brittany), G3OQB (Shropshire), G8BBB (Cambridgeshire), and G3GZJ at Redruth in Cornwall at 180 miles heard on c.w. The antenna is only a 6ft. length of wire in the bedroom. Just think what an 8 over 8 would pull in.

EVENTS


Happenings for September include—6-7th, v.h.f. n.f.d.; 14th, 3-5MHz field day; 21st, national finals of the d.f. hunt at Rugby; 21st, 144MHz contest. One mobile rally this month at Magdalene Laver, near Harlow in Essex. See any of you at this one? Owners of R1155 receivers will be pleased to hear of the 1296MHz contest on October 5th.

DON'T FORGET

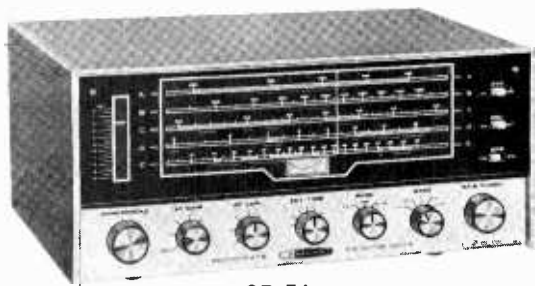1-4 October, the annual get-together of Radio Amateurs of the RSGB International Radio Engineering and Communications Exhibition, Royal Horticultural Hall, Greycoat Street, Westminster, London, S.W.1 (10 am to 9 pm).

"Listen in" on the World with HEATHKIT shortwave receivers

TREAT YOURSELF TO A WORLD TOUR... *WITHOUT LEAVING HOME!*



GR-54

DELUXE 5 BAND SHORTWAVE RECEIVER GR-54


This receiver offers exceptional performance and many special features at such a low price. It covers 2MHz to 40MHz plus 550KHz to 1550KHz AM broadcast band and 150KHz to 420KHz aeronautical and radio navigation band. Receives AM/CW/SSB, 6 x 4in. PM speaker and sleek, "low-boy" styling. Operates on 115-230V 50Hz AC.

Kit K/GR-54 £48.16.0. Carr. 9/-

LOW COST 4 BAND SHORTWAVE RECEIVER GR-64

Makes an ideal present for the youngster. It has high performance features plus world-wide reception, shipping, aircraft, radio amateurs plus the popular medium broadcast band. It covers 1MHz to 30MHz plus 550KHz to 1620KHz AM, with sleek "low-boy" styling, operates on 115-250V 50Hz AC.

Kit K/GR-64 £24.16.0. Carr. 9/-

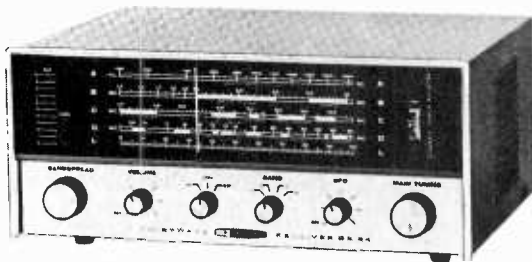

GR-64

GENERAL COVER- AGE RECEIVER GC-1U

A welcome traveller wherever you go! Covers 580 to 1550 KHz and to 40MHz in 5 bands with calibrated bandspread scales for 80, 40, 20, 15 and 10 metre amateur bands. Completely solid state and self contained for portability. Operates on two internal PP6 batteries (not supplied) or 230V AC with a suitable power supply.

Kit K/GC-1U £39.16.0. Carr. 11/-



AMATEUR BANDS RECEIVER RA-1

Unequalled value for the radio amateur. Covers 160 to 10 metres. High quality lattice crystal filter for optimum communications selectivity. Optional 100KHz crystal calibrator plugs in inside receiver. 8 valve and 2 diode circuit. Operates on 115, 200-250V AC, 50Hz.

Kit K/RA-1 £39.16.0. Carr. 9/-



Free Catalogue!



See these models and many more in our 1969 catalogue. Models for Stereo/Hi-Fi, Industry, Education and the Home Workshop. Heathkit —the world's largest selling selection of electronic kits and equipment.

To
DAYSTROM LTD., Dept. PW-10, GLOUCESTER, GL2-6EE.
Please send me FREE CATALOGUE ☐

NAME

ADDRESS

Prices and specifications may be subject to change without prior notice



Adamin

MODEL 15



MICRO SOLDERING INSTRUMENT

● EXTREME VERSATILITY

Range of 8 interchangeable bits, from 3/64" (.047") to 3/16", including new non-wearing PERMATIPS.

● ULTRA-SMALL SIZE

Length 7 1/8". Weight 1/2 oz.
Max. handle dia. 7/16".

● EXTRA-HIGH PERFORMANCE

Heating time 90 secs. Max. bit temp. 390°C. Loading 15 watts — equals normal 30/40 watt iron.

● ALL VOLTAGES

The ADAMIN range includes five other models (5, 8, 12, 18 and 24 watts), Thermal Strippers (PVC and PTFE) and a De-soldering Tool. Please ask for colour catalogue A/10.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL
Telephone 01-688 8589 and 4559



SENSATIONAL STEREO OFFERS!

SAVE
UP TO
33 1/3%
OFF OUR
STEREO
SYSTEMS

NuSound
Britain's Largest Stereo Specialists

As Britain's Largest Specialists our tremendous purchasing power enables us to offer you the famous makes—Garrard, Goldring, Rogers, Decca, Wharfedale, Arena, Philips, etc., etc.—at unbelievably low prices. We offer over 30 HI-FI Stereo Systems utilising these famous makes all showing substantial savings off our normal list prices. A NUSOUND STEREO SYSTEM represents the finest value for money available today. Every system is complete with all leads, plug etc., fully guaranteed and backed by 100% NuSound after sales service. Illustrated literature and technical data sent by return of post (Dept. PW/OT).

24 OXFORD STREET, LONDON. W.1

Tel: 01-580 4638, 4639, 5755
50 yards from Tottenham Ct. Road Tube
Open 6 days a week

WIRECOMP ELECTRONICS

LONDON'S LEADING BARGAIN SPECIALISTS FOR THE RADIO • HI-FI & ELECTRONICS ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps., meters, speakers, etc., etc. ALL faulty or damaged needing repair—

AT GIVE AWAY PRICES!

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — from 2/- each

ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

SPOT CASH PART EXCHANGES WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone

COME AND LOOK TODAY (Open 6 days a week!)

ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1

Tel. 01-636 0647

W. E. C. LTD. New Quality Components

A MUST for your DEN, GARAGE, WORKSHOP.

Mains Distribution Unit. Grey hammer finish, steel case 4 x 13A Flat Pin Sockets and 5ft. of heavy duty cable. Bench or Wall Mounting. £4.19.6.

SEMICONDUCTORS

A selection from our list of over 500 types OA70 1/6 ea. BC109 4/6 ea. BFY52 5/- ea. OC35 15/- ea. BF115 4/- ea.

BARGAIN OF THE MONTH
15A Fused Flat Pin Quality
White Plug. Box of 10 for £1
Plus p. & p. 4/6

RESISTORS

Most values in stock 1 watt 4d. ea.

TRANSFORMERS

15-0-15V 200 mA Superior Finish Shrouded. 12/6 each.

P.C.B. POTENTIOMETERS

1K shrouded 2/0 ea. 500 1K 2K 5K skeleton 1/9 ea.

HARDWARE

Nuts, Bolts, Washers, Tags, Metal, Bakelite Sheet etc.

ALSO IN STOCK

Relays, Capacitors, Knobs, Switches, Terminals, etc.

Send Stamp for latest Catalogue containing approximately 2,000 items.

Terms C.W.O. plus 2/6 p. & p.

W. E. C. LTD
74 THE STREET, ASHTEAD, SURREY

pulse circuits in operation

I. J. KAMPEL

In pulse circuitry there are various other forms of elements designed to speed up pulses in order to obtain a fast trigger pulse from a slow input trigger pulse. It is also a frequent requirement that a circuit trigger at a pre-determined level, and switch off at a predetermined level. The Schmitt Trigger will perform both of these functions.

The most basic Schmitt Trigger is shown in Fig. 5.1. In its normal state no input is provided, Tr1 is therefore in the OFF state, and since $V_{c1} = V_{cc}$, Tr2 is switched into hard saturation. If a positive voltage is gradually increased at the input terminals, a point will be reached where Tr1 will switch on. The circuit current in the OFF state of Tr1 is given by:

$$I_{e2\text{sat}} \approx \frac{V_{cc}}{R_2 + R_3}$$

since only about 0.1V are dropped by $V_{ce2\text{sat}}$. From this the triggering voltage to switch Tr1 into the ON state may be determined by:

$$V_{\text{trig (on)}} \approx V_{be1} + \frac{R_3 \cdot V_{cc}}{R_2 + R_3}$$

When Tr1 switches on, V_{c1} drops to $V_{ce1\text{sat}} + V_{r3}$. There is not sufficient voltage to support V_{be2} and

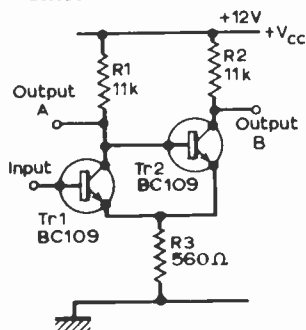


Fig. 5.1: A basic Schmitt trigger.

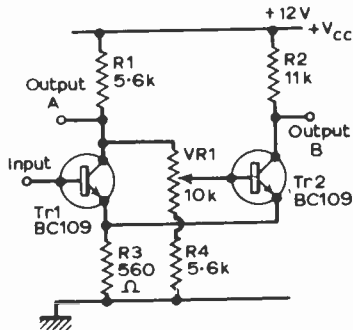


Fig. 5.2: A Schmitt trigger with variable setting.

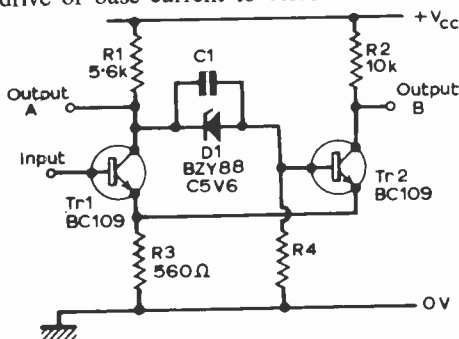


Fig. 5.3: Use of a Zener diode to set the triggering point.

thus Tr2 is cut off, causing a positive-going output at B, with a corresponding negative-going output at A. Since both transistors share the same emitter resistor, during the actual switching operation, as the input pulse causes Tr1 collector to go negative, I_{e2} starts to reduce at the same moment that I_{e1} starts to increase. The reduction of emitter current in Tr2 encourages the current to be transferred to the emitter which is now opening up, that of Tr1. A regenerative effect thus occurs, the switching off of Tr2 speeding up the switch on of Tr1. Fast outputs thus occur.

Tr1 will stay in the conducting state for as long as a positive voltage is applied at the input. If this voltage is reduced, Tr1 will switch off as soon as its V_{be} is not supported. The switching off of Tr1 speeds up the switch on of Tr2 and again fast edges are realised. In

practice there is a slight backlash in such a circuit, i.e. it takes a slightly different potential to switch Tr1 on than to switch it off. The loop gain should be greater than one for positive switching.

The Schmitt Trigger can be used in conjunction with a ramp generator to form a delay line. If a slowly rising positive-going ramp is applied to the input of the Schmitt Trigger, the circuit will only trigger when the ramp voltage will support V_{be1} . It will thus be seen that there is a delay: the initial trigger pulse triggers the ramp to start, and the output is delayed until the Schmitt circuit triggers.

Figure 5.2 is a modified Schmitt Trigger in which a potential divider is used to set the base potential of Tr2. By making the potential of the divider adjustable by means of Vr1, the point at which the circuit triggers on a rising input may be adjusted.

Figure 5.3 also uses a potential divider, but a zener diode is employed to give a positively predetermined trigger. In this circuit, the states will change when:

$$V_{ce1} \approx V_z + V_{be2}$$

A speed-up capacitor C1 is used to give Tr2 an initial overdrive of base current to drive it into hard

saturation initially, relaxing after the initial transient with the only base current through the zener diode.

Schmitt Trigger circuits can have very fast rise and fall times, and by modifying the design with lower loads or clamping diodes so that the transistors do not drive into saturation, switching times better than 10nS are possible.

It should be pointed out that the formulae given on the Schmitt Trigger have been chiefly to indicate in the explanation how the circuits work. It is very difficult to exactly predict switch-on and switch-off voltages, and these should ultimately be determined experimentally. It is quite usual for circuits such as that of Fig. 5.1 to have a backlash greater than 1.5V. The greatly simplified expressions given earlier in the text should give voltages within the backlash voltage range.

part five the trigger and ramp generator

COMPLEMENTARY SWITCH

Figure 5.4 shows a fast switch using complementary transistors, i.e. similar n-p-n and p-n-p types, although they need not be closely matched. An advantage with this circuit is that it only draws leakage current until

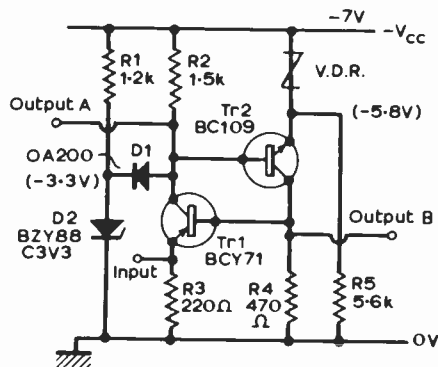


Fig. 5.4: A trigger similar to the Schmitt circuit but which draws virtually no current when off.

an input voltage is applied, if the zener current is ignored. In fact, with modern silicon planar zener diodes (such as the BZY88 C3V3 for D2) it is possible to only drive the zener diodes with a few hundred microamps, and the same applies to the v.d.r.

This circuit operates as follows. Since there is a closed loop round the emitter-base of Tr1 when no input is applied, Tr1 cannot switch on. V_{e1} is therefore at $-V_{cc}$ volts, and since the v.d.r. ensures that the emitter of Tr2 is about 1.2V away from the negative line, the emitter-base of Tr2 is under reverse bias. If a positive voltage is applied at the input terminal, it carries Tr1 emitter positive, below the earth rail, and it then enables Tr1 to switch on. As it switches on, the collector voltages go positive, bringing into conduction Tr2. As Tr2 goes on it increases the voltage at the base of Tr1 which further increases the current through Tr1. There is thus a loop encouraging the two transistors to switch sharply on. Output A goes positive and output B goes negative.

Now the zener diode clamps the cathode of D1 at $-3.3V$, thus preventing the collector of Tr1 falling below about $-2.6V$, and stopping it from being driven into saturation. This will result in minimal stored base charge, and will assist a fast turn-off time. When the positive input is removed, regenerative action similar to that in the switch-on encourages a fast switch-off, further enhanced since Tr2 tends to have its emitter-base reverse-biased.

The complementary circuit thus acts in a similar manner to the Schmitt Trigger. If the fastest switching characteristics are not required and the zener diode and the clamping diode are removed, allowing Tr1 to drive into saturation, an excellent switching circuit still exists with the virtue of practically no drain current when not in operation. For many purposes the circuit will operate rapidly enough if the emitter of Tr2 is simply taken to the $-ve$ rail through a resistor, R5 then of course not being in circuit. The emitter-base of Tr2 will not then drive into reverse bias, but with Tr1 switched off, Tr2 will still be switched off, if not quite so positively.

A GATED RAMP GENERATOR

There are a number of uses for rising or falling voltage ramps, one of which, as a delay, has already been mentioned. Ramp generators are of course, the basic elements of scanning systems.

Figure 5.5 shows a simple gated ramp generator. We shall assume initially that capacitor C3 is fully charged to $V_{cc} - V_{cesat}$ volts. Tr2 is initially non-conducting, as is Tr1. If a positive pulse is applied via C1, Tr1 switches on, driving the base of Tr2 negative. Resistor R1, being smaller than the input impedance of Tr1, gives a more specific time constant at the input.

As Tr1 collector goes negative it brings into conduction Tr2, C2 acting as a speed-up capacitor. Tr2 is driven hard on and effectively shunts C3 with its low saturation impedance. C3 discharges through the transistor provided that the input pulse is long enough to ensure this. When the trigger pulse is removed, Tr1 and Tr2 switch off and the shunt across C3 is removed. Since the voltage at the base of Tr3 is constant, held so by the potential divider of R5 and R6, and since V_{be3} may be regarded as constant, the voltage across R4 is constant, and a constant current is therefore driven into Tr3 emitter. Virtually all of this current passes out of the collector and flows into C3. C3 is thus charged with a constant current, and produces a fairly good linear ramp. The ramp will continue until Tr3 goes into saturation, or until the cycle is started again by the application of a positive trigger pulse.

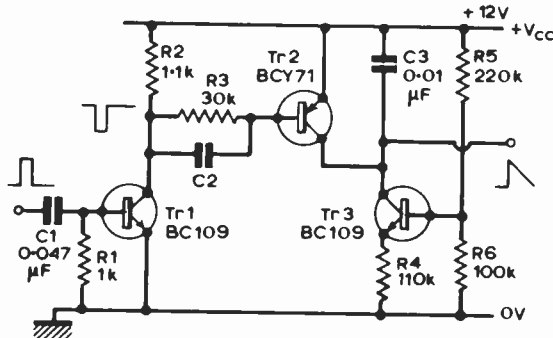


Fig. 5.5: A sawtooth or ramp generator.

If a ramp generator is required to give a continuous sawtooth output, a multivibrator might be used to supply trigger pulses, or a feedback mechanism from the ramp output itself can be used so that when the ramp reaches a certain voltage, it switches on a monostable circuit which gates on Tr2. When the monostable releases Tr2, after the C3 discharge period, the ramp will start again.

CONCLUSION


In this series saturation switching, astable, monostable, bistable circuits, Schmitt triggers, complementary triggers and ramp generators have been discussed in detail. It is hoped that the original aim of clearly describing pulse circuits in operation has been achieved, and that this treatment may have assisted the beginner in particular to appreciate some of the finer points of transistors in pulse circuits.

SOME HIGHLIGHTS OF NEXT MONTH'S P.W.

PEDAL STEEL GUITAR

The popularity of "Country and Western" style music has brought about a new kind of electrical musical instrument. It stems from the Hawaiian steel guitar and has become generally known as the "pedal steel guitar".

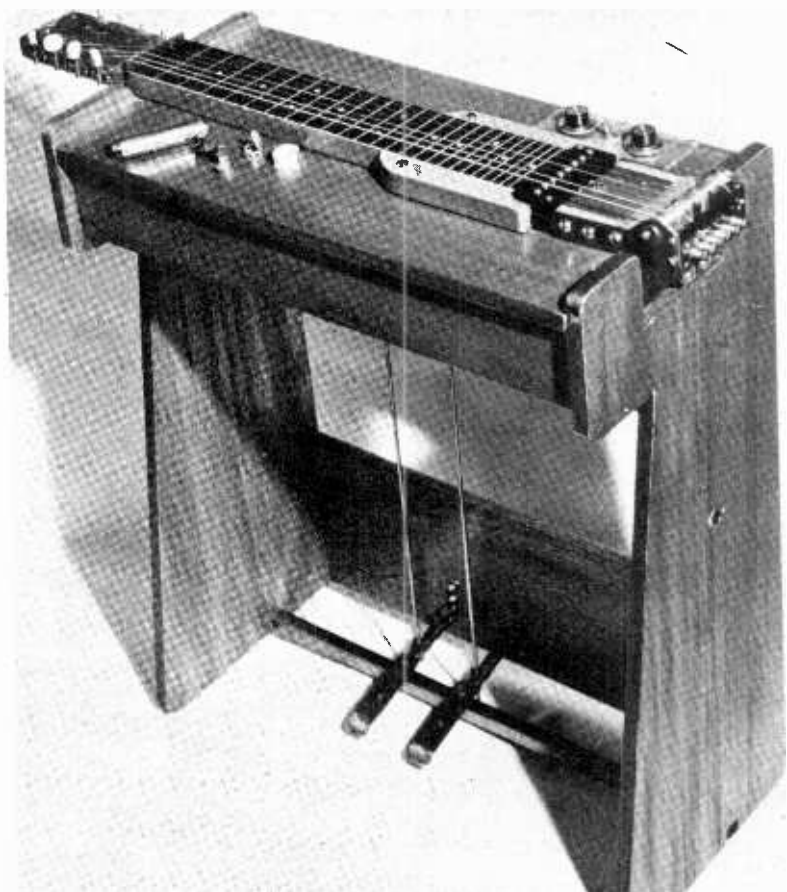The cost of commercially-made pedal steel guitars ranges from around £350, but the instrument to be described in the November and following issues should not involve a total outlay of more than about £30. Within the console body a preamplifier is incorporated, and the output may be taken to a suitable external power amplifier.



IC OF THE MONTH

Integrated circuits in ever increasing numbers are now being offered by advertisers to the home constructor. A number of designs have appeared already in PRACTICAL WIRELESS in which an IC is incorporated. Starting with the next issue we are introducing an "IC of the Month" series, each article of which will describe the practical application of a different device. Part I will feature the construction of an IC short wave converter.

AUDIO SUPPLEMENT

With the increasing interest in audio and hi-fi equipment, a special Audio Fair supplement will be published in next month's issue of PRACTICAL WIRELESS. It will include details of manufacturers' products and a preview of things to come at the 1969 Audio Fair.

PRACTICAL WIRELESS

All in the November issue on sale
Friday, October 3

ORDER YOUR COPY NOW

practically wireless

commentary by HENRY

No. 61

Power
Complex

AT the risk of riding my hobby-horse too hard, I must revert again to the sore subject of audio output power. Not all the pundits agree on power nomenclature, it seems, though all deprecate the copywriters who make a six-watt struggler appear (in the brochure) too dangerous to couple to anything less than a pair of hundred-watt speakers.

"The greater the power, the more dangerous the abuse," quotes Editor John Crabbe in *Hi-Fi News*. Edmund Burke's argument is inside-out when applying politics to audio. The less the actual power the more it is made to sound good. Just now there is another trick way of defining power output. From America (of course) comes $\text{IHF} \pm 1\text{dB}$. If a manufacturer of an amplifier can specify "so many watts, $\text{IHF} \pm 1\text{dB}$ " he is giving himself a scope for variations wide enough to admit a London 'bus. $\pm 1\text{dB}$ with a 100W amplifier is like saying "anything between 79 and 126 watts". And those "watts", remember, are music power, not your true-blue British r.m.s.

What have I said? R.M.S.? That's taboo now, according to Mr. Myall, of Wow and Flutter fame. He would like to know, what are "Watts r.m.s.". Me too!

The product of root-mean-square voltage and current is average power, or equivalent con-

stant power. If we wish to express a varying power in the form of an equivalent constant power, it must be equal to the *average* value, not root-mean-square, which is 0.707 of peak. If the phrase "continuous sine-wave power" is to be taken literally, then half the peak value (implying a sinusoidal drive voltage) is neither r.m.s. nor average.


Continuous, in the terms of the audio boys, really means over a period of many cycles. It implies that the driving force, i.e. the sinewave voltage, is continuous, *not* that the power is flat and even over a long straight graph of output. The power must vary cyclically, or we couldn't hear the dratted noise it makes.

So we are asked to interpret r.m.s. power as "power arising from the r.m.s. voltage of a continuously applied sinewave signal".

We can accept that the power waveform is $\sin^2$, and half the peak value becomes the average.

None of this helps us if the manufacturer, or his indefatigable Boswell, the copywriter, uses EIA terms. The Engineering Industries Association of America has a standard which permits the manufacturer to quote power output at mid-frequency at a distortion content of 5%. And if $\text{IHF} \pm 1\text{dB}$ admits a London 'bus, this so-called standard would leave room for a couple of hansom cabs also.

Frank Jones gives the best analogy I have seen to explain the difference between the various power specifications. Imagine, he says, you are in a car and wish to overtake a lorry. Your engine must produce power to accelerate and let you pass. With continuous power, you could just accelerate in time to avoid bashing your brains out on an oncoming bonnet. By comparison, no other type of power would be so effective.

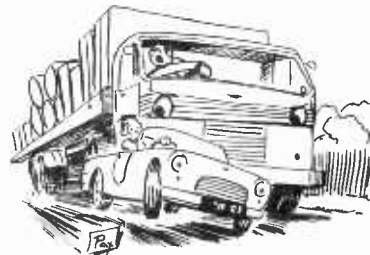

You could just accelerate in time...

Music power has excellent initial acceleration, but there is no sustaining strength, and the engine "dies away" as you are abreast of the juggernaut. EIA power would simply mean that as you put your foot down, the engine would make a horrible noise, but get you nowhere, and $\text{IHF} \pm 1\text{dB}$ would not allow you to pull out and pass; neither would any form of peak power.

He does defend one practice that has a slight whiff of embellishment. Doubling up the power because you are in stereo is legitimate because "... a stereo amplifier should be capable of handling power on both channels together, or on either channel by itself. Peaks can occur on one channel only." Too true, especially with some of the gimmicky records dealers have been unloading since r.p.m. was abolished.

So how do we specify power, when there are so many ways we can be fooled? Mr. Crabbe suggests we ask for continuous power for a set period of time, say two seconds. He does not mention distortion, nor specify the test frequency.


All this, and my hobby-horse hasn't even worked up a sweat. What about the vexed question of power handling (speakers) or the myth of transistor sound which usually means that the speakers now have to handle a wider response and cleaner transients... what about... well, your turn, Joe. How do you figure in the power game?



We couldn't hear the dratted noise

ADDING SQUELCH

C. R. BRADLEY

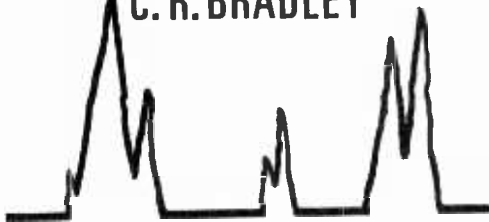

VIRTUALLY all radio receivers and tuners incorporate a.g.c. (automatic gain control), also known less accurately as a.v.c. (automatic volume control). This works by utilising an otherwise wasted by-product of detection, the d.c. level produced by the carrier signal. This voltage depends on the strength of the carrier and is not affected by any sound modulation of the carrier. It is generally prevented from reaching the radio's audio stages by a capacitor after the detector. The principle of a.g.c. is to return this voltage to one or more r.f. stages in the receiver where it will progressively reduce gain by biasing one or more stages away from the normal Class A working point towards cut-off. Thus the carrier level reaching the detector is kept fairly constant over a wide range of received signal strengths.

The effect is that the radio is more satisfactory to use, a.g.c. can counteract atmospheric fading of radio signals, and the effect of moving a portable radio. One can tune across the wavebands without being "blasted" by strong signals and missing weak ones. Stages which are a.g.c. controlled and subsequent stages are not overloaded by strong signals. Of course a.g.c. cannot produce any improvement in the radio's maximum gain or signal-to-noise ratio and in fact must be carefully designed to avoid impairing these qualities.

A.G.C. circuits often work over a very wide range and tend to be taken for granted. It is interesting to disconnect the a.g.c. line from the detector and connect it to the radio's earth temporarily. The effect on reception of, say, Radio Luxembourg (while fading) is instructive, but be prepared for sound "blasting" if trying this on a radio with a powerful audio output.

SQUELCH

There is one defect in all a.g.c. circuits which can be remedied by a squelch circuit. The a.g.c. circuit cannot "know" whether a weak signal or no signal is being received. Therefore the r.f. stages work "flat out" (full gain) when there is no signal, and the radio reproduces interference and circuit noise at unpleasant volume, this is especially noticeable when a car radio gives a burst of crackle when driving under a bridge which shields the signal, and when a loud hiss (circuit noise) is heard between stations on a v.h.f. receiver. A squelch circuit removes this annoyance by muting the audio output until a carrier of predetermined strength is received. The squelch circuit to be described is a relay

with transistor amplifier which is connected to the radio a.g.c. line. When there is no a.g.c. feedback, indicating that no signal is being detected, the relay closes and its contacts are arranged to mute the receiver audio.

Valve and transistor a.g.c. circuits must be considered separately as the voltage levels are slightly different. Figure 1 shows the essential a.g.c. components of a typical a.m. transistor radio using p-n-p transistors. The r.f. transistor is normally biased in Class A by R1 which supplies emitter-base current via i.f.t.1 secondary. A strong signal detected by D1 produces a swing in the positive direction in the r.f. transistor's bias, i.e., the emitter-base current is reduced and the transistor moves towards cut-off. Thus the voltage across the $8\mu\text{F}$ smoothing capacitor which is sensed by the squelch unit varies as follows:

No signal: -1.5 volts approx.

Strong signal: 0 volts approx.

If the a.g.c. circuit is similar but n-p-n transistors are used, the voltages are positive.

Figure 2 shows a squelch circuit suitable for both p-n-p and n-p-n transistor radios. A simple current amplifier driving a relay would not be sufficient due to the relay hysteresis or voltage lag between energised and non-energised conditions. To reduce hysteresis the relay coil RL is driven by a Schmitt trigger, Tr2/Tr3.

The a.g.c. supply is tapped off by VR1. If the a.g.c. voltage is sufficiently high (no signal), Tr1 draws current through R1 and away from Tr2. Tr2 and Tr3 share load resistor R3 and therefore the circuit resembles a long-tailed pair in that as Tr2 turns off, Tr3 is biased on by the initial reduction in voltage drop across R3. But Tr2 and Tr3 are also coupled in the same sense by R4. At a certain threshold value of input to Tr1, the loop gain of the trigger exceeds unity and Tr3 is suddenly turned full on by Tr2. When the input to Tr1 drops below the

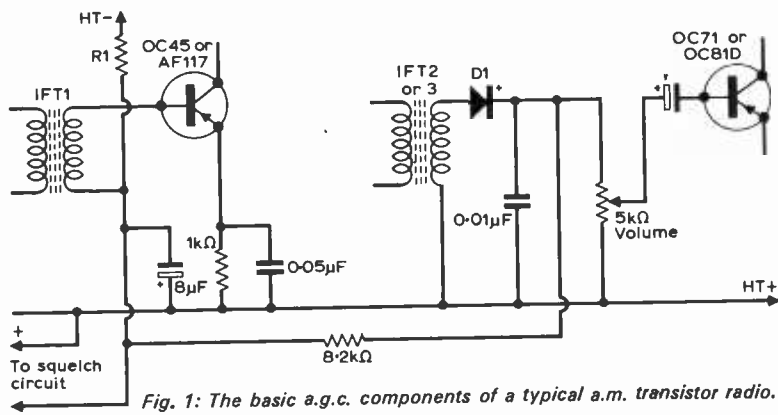


Fig. 1: The basic a.g.c. components of a typical a.m. transistor radio.

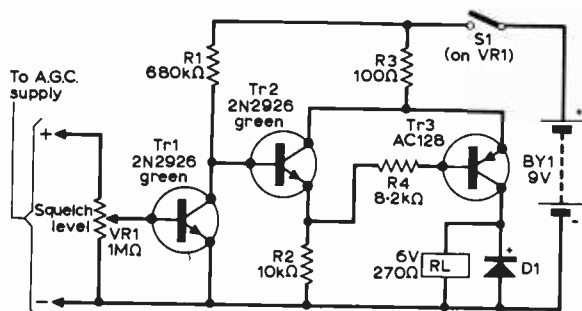


Fig. 2: Squegl circuit suitable for transistor radios.

threshold value, Tr2 suddenly turns on and turns Tr3 off. With the circuit shown, the threshold input current to Tr1 was about 1/25th of a microamp and the hysteresis was too small to measure. Since Tr3 turn off very rapidly, diode D1 is included to protect it from reverse transients induced in the relay coil.

The relay contacts are arranged to mute the audio when the relay is energised. This can be done in a variety of ways e.g., by breaking the h.t. supply to an audio stage or bypassing audio at some point to earth through a capacitor somewhat larger than the nearest audio coupling capacitor. For audio stages not working at peak level it is safe to interrupt the audio at the loudspeaker in the following manner.

Where there is an audio output transformer; wire the relay contacts to short the speaker terminals together when the relay is energised. Where there is no output transformer; wire the relay contacts to open-circuit the loudspeaker connection when the relay is energised. These rules must be observed to avoid damage to the audio output stage.

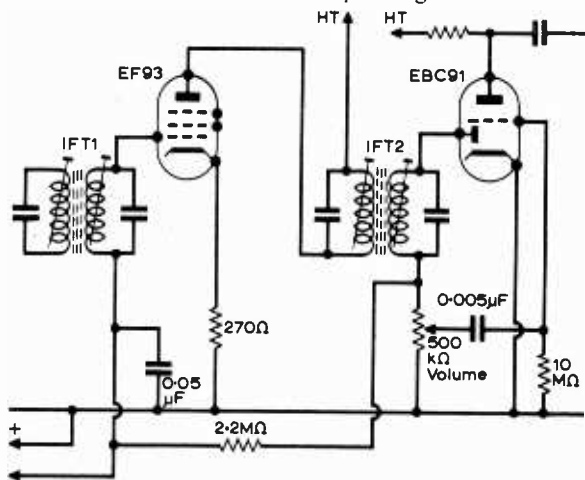


Fig. 3: The basic a.g.c. components of a typical valve radio.

The essential components of a valve receiver a.g.c. circuit are shown in Fig. 3. The EBC91 valve contains a detector diode which provides both a.g.c. and audio. There are many variations on this arrangement; sometimes separate diodes provide a.g.c. and audio. When a strong signal is received, the detected audio and a negative voltage appear at the top end of the volume control. The 0.005μF capacitor couples the audio to the grid for further amplification. The negative voltage passes through the 2.2MΩ resistor and the secondary of i.f.t.1 to the grid of r.f. valve EF93. As this is a variable-μ pentode, applica-

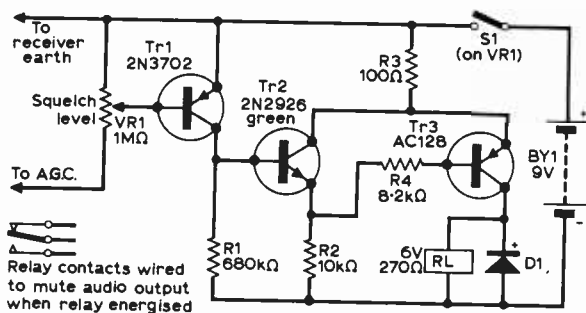


Fig. 4: The modified squegl circuit for valve radios.

★ components list

Resistors:

R1 680kΩ R3 100Ω
R2 10kΩ R4 8.2kΩ
All 10%, 1/4 watt miniature

Semiconductors:

Tr1 2N2926 green (Fig. 1) Tr3 AC128
2N3702 (Fig. 2) D1 Any germanium
Tr2 2N2926 green diode e.g. OA70

Miscellaneous:

VR1 1MΩ carbon pot. with switch; RL 6V 270Ω miniature Siemens relay, one set of contacts used. 9V battery; Aluminium chassis; tagstrip; battery clips; knob for VR1, etc.

tion of increased negative bias progressively reduces the gain of the stage. Thus the voltage across the 0.05μF decoupling capacitor varies as follows:

No signal: -3 volts approx.

Strong signal: -6 volts approx.

Actual voltages may be considerably different, depending on the circuit. The important point is that the a.g.c. voltage *increases* when a strong signal is received as opposed to the opposite action in a transistor radio. For valve circuits, the squegl circuit must be rearranged slightly as shown in Fig. 4. Tr1 is now a high gain p-n-p transistor which supplies current to Tr2 when a *high* a.g.c. voltage is sensed across VR1. The delay coil is therefore energised when there is no radio signal as before.



CONSTRUCTION

The layout of the squegl circuit is not critical and it can be built small enough to fit inside almost any radio. The author's prototype was laid out on a tagstrip bolted to a piece of aluminium without any attempt at miniaturisation as shown in Fig. 5. This layout is for the circuit in Fig. 2 and the necessary re-arrangement for the circuit in Fig. 4 can be deduced easily. A piece of the aluminium chassis is bent up to carry the squelch level control VR1. The tagstrip must be clean and dry around the base connection of Tr1 as the circuit will trigger on the slightest leakage current here. Just touching the base and collector leads of Tr1 with a fingertip causes the relay to energise.

None of the components are critical and there is no harm in trying substitutions. Tr1 and Tr2 were chosen for high gain and low leakage and similar cheap silicon types should work. Tr3 is a general-purpose

Fig. 5 (below): The component layout of the circuit shown in Fig. 2; this will have to be slightly modified for the circuit in Fig. 4.

Fig. 6: A.G.C. circuits of valve receivers using (a) a ratio detector and (b) a discriminator.

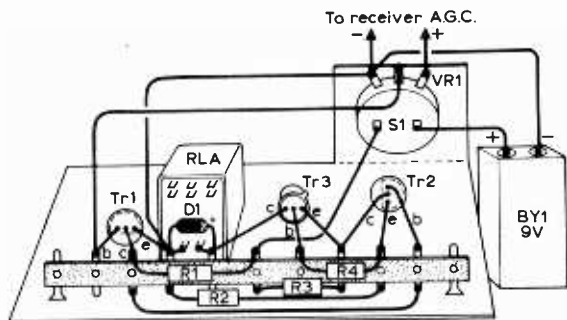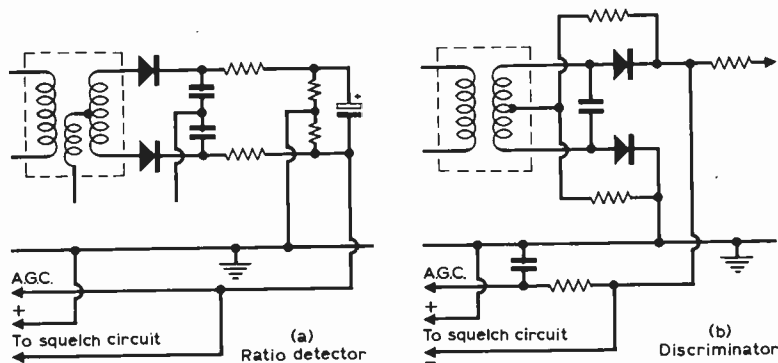

germanium type and an OC81 would be a possible substitute. A miniature Siemens 6 volt relay was used as it is available cheaply. A 24 volt 400 Ω relay was also made sufficiently sensitive to work in the circuit by stripping it of three of its four contact sets and carefully weakening the one remaining spring. Any relay coil that will pull in on about 12mA will work in the circuit if the d.c. resistance is below 1 k Ω .

If the relay does not energise, try reducing R2 to 8.2k Ω and/or increasing R1 to 820k Ω or 1M Ω . If the relay remains constantly energised with no input to Tr1 base, try increasing R2 or reducing R1 to 500k Ω . These adjustments should only be necessary with lower gain transistors and/or a less sensitive relay and result in a less sensitive circuit.

CONNECTION TO RADIO

The possible ways in which the relay contacts can be arranged to mute the receiver audio when the relay is energised have been mentioned and a suitable arrangement can easily be made. With valve receivers it is best to leave low level audio circuits alone to avoid introducing hum and muting is best achieved by interrupting the h.t. supply to the output valve. In this case a 0.1 μ F capacitor should be wired across the relay contacts to minimise sparking.

On a.m. receivers, the a.g.c. decoupling capacitor to which the squelch circuit is connected is easily located by reference to Figs. 1 and 3. It is usually just "one resistor away" from the live end of the volume control.

On f.m. receivers, the way in which the a.g.c. voltage is derived depends on the type of detector used. Figure 6 shows the a.g.c. circuits of typical valve receivers with ratio and discriminator detectors. The a.g.c. controlled stage(s) work in the same way as in the a.m. circuits Figs. 1 and 3 and the a.g.c. voltage varies as before for p-n-p transistor, n-p-n transistor and valve stages.

For normal squelch use, VR1 is set so that the relay just energises when no signal is received by the

radio. Any reasonable signal will then cause the relay to de-energise but it is often useful to set VR1 so that only strong signals can break through the squelch. In this way, the crowded medium wave band can be "weeded out" so that it is reduced to a few strong local stations separated by silence.

Although the squelch circuit is very sensitive, it is necessary to switch it off in order to receive very weak signals that do not produce any noticeable a.g.c. voltage.

The circuit draws about 15mA when the relay is energised. In normal use the relay will not be energised for long periods and several week's life can be expected from a PP3 battery; the author's circuit continued to work with a battery voltage as low as 4 volts. It is important to switch off the circuit when the radio is off or the battery will soon be drained, especially with the valve radio circuit where the relay would remain energised.

MONO-STEREO AMPLIFIER

—continued from page 398

usual twin wiring, and relies on a single wire, with earth return. The amplifier, as shown, will not operate satisfactorily under these conditions.

Power Supply

This is quite conventional. The only points to note are that the mains transformer and smoothing choke are sufficiently large to handle the current required. The rectifier specified (GZ34) is the octal-based near-equivalent of the popular EZ81, which can equally well be pressed into service if desired. A B9A holder is required in place of the octal base. If this valve, or an EZ80 is used in preference to the GZ34, a separate 6.3V heater winding will not be necessary on the mains transformer, as the heater-cathode insulation of these valves is sufficient to permit using them with the heater winding which supplies the remaining valves. The EZ80 is on the low side to handle the power necessary for stereo operation but will be sufficient, initially, for a mono version of the amplifier, and has the same base connections as the EZ81, with which it can be later interchanged. Smoothing capacitors C15 and C16 should be of the rated capacity, or slightly larger. Decoupling capacitors C4 and C54 are essential for stability, and should not be omitted, although, if space is at a premium, they may be reduced to 16 μ F at the rated working voltage.

to be continued

MEDIUM WAVE **DK** • RECEIVER •

D. GIBSON G3JDG

DESIGNS for various types of receiver have commonly appeared in the popular construction journals. However, these have fallen into two categories, those for the short wave amateur bands from 1.8 to 30MHz, and those more specialist types intended for the higher frequencies such as 144MHz.

To date, the medium wave enthusiast appears to have been sadly neglected, and the purpose of this article is to offer ideas on which a specialist receiver, intended specifically for the 0.5 to 1.5MHz segment of the r.f. spectrum, may be founded.

The circuitry provided offers a medium wave solid state receiver, but there is room for improvement both in performance and construction. It is intended, therefore, that this article should stimulate ideas for further experiment and improvement rather than offer circuitry which should be copied parrot-fashion.

DESIGN CONFLICTIONS

Any design is, of necessity, a compromise. In dealing with a medium wave receiver the same confictions arise as for any receiver. Perhaps the two most important are sensitivity and cross-modulation characteristics with second channel interference running a close third. Other problems, such as noise, selectivity and spurious responses must be considered.



An inherent weakness in superhet design is image interference. The receiver shown minimises this by the choice of a high i.f. frequency—1.6MHz instead of the more usual 465kHz. Selectivity is good because there are two tuned circuits prior to the mixer. The i.f. bandwidth at the 6dB points is approximately 2kHz, this narrow bandwidth assists in selectivity and a reduction in noise.

An a.m. signal, which is the normal type on medium waves, has two sidebands each containing identical information. Thus if we receive only one, it is possible to achieve intelligibility, a technique used in this design.

The narrow i.f. bandwidth is achieved by the use of a half-lattice crystal filter containing two crystals. The result is a filter having response characteristics with very steep sides.

In order to minimise cross-modulation problems the gain of the receiver is purposely kept low ahead of the mixer, the main gain coming after the crystal filter.

In designing the receiver it was envisaged that the average constructor would not have access to expensive test equipment and many would not possess a wobulator or oscilloscope, two items needed to align an i.f. section accurately. Thus, in the present circuit, a commercial i.f. strip is used which is pre-aligned and on setting up in the completed receiver

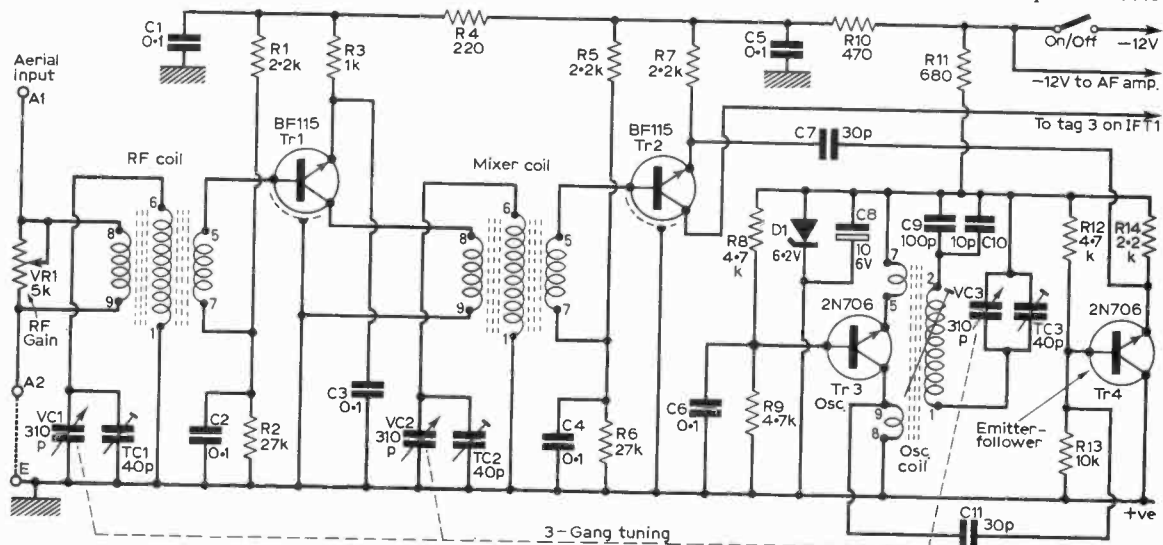


Fig. 1: The front end circuit of the prototype receiver. Alternative circuits are given elsewhere in the article.

★ components list

Resistors:

R1 2.2kΩ	R13 10kΩ	R25 1kΩ
R2 27kΩ	R14 2.2kΩ	R26 56Ω
R3 1kΩ	R15 1kΩ	R27 1Ω
R4 220Ω	R16 10kΩ	R28 1Ω
R5 2.2kΩ	R17 1kΩ	R29 18kΩ
R6 27kΩ	R18 68kΩ	VR1 5kΩ 1in.
R7 2.2kΩ	R19 10kΩ	VR2 50kΩ log.
R8 4.7kΩ	R20 33kΩ	VR3 5kΩ log.
R9 4.7kΩ	R21 2.2kΩ	VR4 5kΩ 1in.
R10 470Ω	R22 470Ω	VR5 10kΩ 1in.
R11 680Ω	R23 560Ω	
R12 4.7kΩ	R24 4.7kΩ	

All resistors 10% $\frac{1}{4}$ W miniature, all potentiometers miniature carbon

Capacitors:

C1 0.1 μ F
C2 0.1 μ F
C3 0.1 μ F
C4 0.1 μ F
C5 0.1 μ F
C6 0.1 μ F
C7 30pF
C8 10 μ F 6V electrolytic
C9 100pF
C10 10pF
C11 30pF
C12 10 μ F 6V electrolytic
C13 10 μ F 6V electrolytic
C14 100 μ F 6V electrolytic
C15 100 μ F 15V electrolytic
C16 100 μ F 15V electrolytic
C17 100 μ F 15V electrolytic
C18 200 μ F 15V electrolytic
C19 1,000 μ F 12V electrolytic
C20 1,000 μ F 12V electrolytic
VC1/VC2/VC3 310pF swing variable 3-gang capacitor

TC1/TC2/TC3 40pF trimmers (air spaced if possible)

Cx see text

Cz see text

All capacitors 125V wkg., miniature foil or polyester unless otherwise stated.

Semiconductors:

Tr1 BF115 \ (or OC170 or 2N3819,

Tr2 BF115 } (see alternative circuits)

Tr3 2N706; Tr4 2N706; Tr5 OC81; Tr6 OC81D;

Tr7 OC81; Tr8 AC127

D1 6.2V 5% zener diode, 250 mW.

Inductors:

R.F. coil Denco blue transistor coil 2T

Mixer coil Denco yellow
transistor coil 2T

Oscillator coil Denco white
transistor coil 2T

R.F. coil. Denco blue miniature dual purpose valve

coil 2T
Mixer coil Denco yellow

miniature dual purpose
valve coil 2T

I.F.T.1 S1/T11/1-6 Denco

Miscellaneous:

I.F. strip IFA/1.6/SSB Mk. II, Electroniques; S-meter, 0-1mA, Eagle; 10 Ω -35 Ω loudspeaker; two open-circuit jack sockets; tuning dial assembly, Electroniques SM2; case and chassis, Philpotts Metal Works, Chapman Street, Loughborough; panel labels, Sherrard's Training Centre Digswell, near Welwyn, Herts.; plain Veroboard, 0.1 in. matrix and matching pins, r.f. board 2 x 3 $\frac{3}{4}$ in., a.f. board 1 $\frac{3}{4}$ x 3 $\frac{3}{4}$ in.; three terminals; five knobs; two toggle on-off miniature switches; one single pole changeover switch; two PP1 batteries; battery clips.

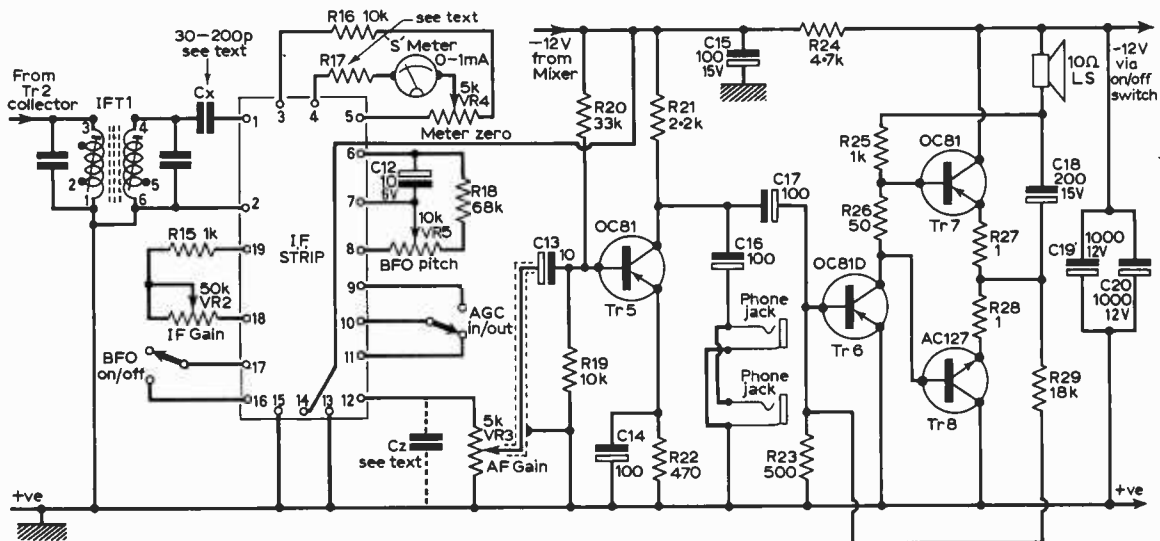


Fig. 2: The i.f., detector and audio stages. R17 is 1K in the prototype but its value will depend upon the d.c. resistance of the meter chosen.

For constructors who are unhappy about the use of n-p-n devices in upside down circuitry, a p-n-p front end was tried using the trusty Mullard OC170. This circuitry gave greater gain than that shown in the final circuit but by the same token proved more susceptible to the terrors of cross modulation. It must be admitted, however, that sensitivity with the circuit configuration gave most impressive results when using ten feet of twin lighting flex as an aerial.

For the experimentally minded, the other two front ends tried are shown in Figs. 3 and 4. Again, these were wired up on a strip of Veroboard in superb "rats nest" style and would doubtless benefit from a little thought for further improvement.

One last point regarding the f.e.t. A friend working at a university offered to check the actual gain of an f.e.t. and with an untuned load found this to be only 3dB, a result verified by his learned tutor.

LOCAL OSCILLATOR

The oscillator uses a standard Denco coil but note that this is the white one intended for an i.f. of 1.6MHz. It is coupled to an emitter follower, also a 2N706, which gives good isolation between the oscillator proper and the mixer stage. This isolation is further enhanced by the use of very low value coupling capacitors, nominally 30pF.

The use of a separate oscillator is common in communications receivers to avoid any slight variations in the load offered by the mixer from detuning the oscillator slightly or "pulling" it off frequency. The emitter follower is an admitted luxury but the circuit works very well and no pulling can be detected in the prototype.

Both oscillator and emitter follower are fed from a stabilised supply obtained with the aid of a 6.2V 250mW zener diode decoupled by a 680Ω resistor and a 10μF 6V electrolytic. This is not the most stable of supplies but the use of further transistors in either series or shunt stabilising circuitry was not considered necessary, and to date this decision has proved correct.

A transistor mixer requires very little in the way of oscillator injection voltage and thus the low voltage to the oscillator stage plus the very low coupling capacitors are entirely adequate. No advantage was evident when either or both were increased. The coupling capacitors were increased in value up to 1,000pF with no apparent increase in performance and strangely enough, no apparent pulling of the oscillator.

The i.f. strip has two crystals with the resultant response centred on 1.62MHz and not 1.6MHz which is the frequency for which the oscillator coil is intended. No deleterious results have come to light so far, the oscillator core allowing a wide adjustment of frequency. For the purist, intent on squeezing the very last ounce of performance out of the circuit, then theoretically the padder capacitor should be made variable so that the slight variation in frequency can be adjusted with due regard for the correct LC ratio. In this case, it would be in order to use an 82pF silver mica capacitor in parallel with a 30pF trimmer, preferably a beehive type so that these very slight adjustments can be catered for.

THE I.F. STRIP

Coupling to the i.f. strip is via an i.f. transformer mounted separately on the underside of the chassis. The secondary winding is capacitively coupled to the

i.f. transformer on the strip. The value here is nominally 30pF. Increasing the capacitance will result in a greater transference of signal but will load the i.f. transformer on the strip more heavily. The result is that although "better" results are obtained from the loudspeaker, the shape of the response curve is distorted and it thus becomes again a matter of compromise as to how much shape distortion can be tolerated.

In an effort to check this to the limit, the collector of the mixer transistor was taken directly to the input of the i.f. transformer on the strip itself, thus bypassing completely the separate i.f.t. The resultant distortion of the i.f. shape factor was quite marked but selectivity was still reasonable.

A very important point is the adjustment of the strip's input i.f.t. This has two cores which can be adjusted by a special plastic tool. Under no circumstances should the top core of this transformer be touched. Only the lower core, accessible from the bottom of the can, should be adjusted. This is very important since the other, the top core, is carefully pre-aligned by the manufacturers for the correct response from the crystal filter.

The strip is colour coded by little blobs of paint. These correspond to the numbers shown in the diagram. To avoid any error here, a table has been included showing which colour corresponds to which number. This information is also included in the *Hobbies Manual* which the manufacturer also markets.

The resistor shown in series with the meter, i.e., between the meter and point 4 on the strip was found superfluous with the particular meter used. Originally a 5kΩ skeleton preset was wired in directly behind the meter for adjustment. A separate front panel control permits the meter to be set to zero.

In the manufacturer's circuitry for the strip there is an error in the wiring of the a.g.c. on/off switch. This should be wired as shown in the circuit diagram and not as in the *Manual*.

The original circuitry also showed a 0.1μF capacitor wired directly across the a.f. gain potentiometer. The omission of this component will result in an increase in signal but will also be accompanied by an increase in noise. Varying the value of the capacitor will produce *pro-rata* results.

A.F. SECTION

The a.f. amplifier section was derived from an early Mullard design which was modified and ruthlessly pruned of components until the bare minimum workable circuitry remained. Considerable experiment was called for to get the circuit to function satisfactorily in both performance and current consumption. With the values as shown, the circuit draws approximately 8mA in its no-signal condition. Current on peaks is far greater than this.


Two jack sockets are wired in immediately following the preamplifier stage. This was to allow headphone reception for one or two listeners or to take a lead out to a tape recorder. The speaker remains in circuit when these jacks are in use and it might be an idea to utilise jack sockets with spare contacts which could be arranged to break the supply to the other three transistors in the interests of battery economy.

In its present form the receiver covers from 0.5MHz to 1.5MHz over a 180° dial. It has three separate

—continued on page 434

BASIC SEMICONDUCTOR TECHNOLOGY

PART FIVE

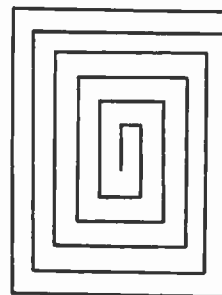

by M. F. DOCKER, M.Sc.

PREVIOUS articles in this series have shown how semiconducting materials can be made to rectify alternating current, respond to light signals by producing a varying current when the illumination is altered, and so on. These devices have all been two electrode ones, or diodes. Their electrical behaviour has been shown to be connected with the internal, atomic energy levels of the materials used, and with the distribution of impurity concentrations within the devices.

Discovering the transistor

Shockley, Bardeen and Brattain together with other research workers sought for many years to find a solid state device which would produce amplification of power; in other words a solid state version of the thermionic triode valve. They were aiming to make a device which had been theoretically predicted by Lilienfeld. In 1948 they disclosed the invention of an amplifier, different from the one that they were trying to make, but none the less an amplifier. They called it a transistor, a contraction of the term TRANSfer resISTOR. It was not until several years later, in the 1960s, that the device they were seeking, the field effect transistor, was found. This had to await the advent of higher purity materials than were at that time available.

The device which they did make was a variant of the point contact diode. They placed two metal cat's whiskers close together on the same chip of germanium. One of the diodes thus formed was forward biased and the other reverse biased. The amazing fact that came to light was that the current between the two metal contacts depended strongly on the current flowing into the forward biased junction. A large current could be made to flow across a high impedance reverse biased junction, amounting to a high power output, simply by altering the current flowing in a low impedance forward biased junction, a low power input. The solid state amplifier was here to stay!

Basic transistor operation

In order to explain the transistor action it is convenient to discuss the p-n-p junction transistor. This is a descendant of the point contact transistor and the methods used in their manufacture will be described later. At present it suffices to say that it consists of an n-type base region, corresponding to the semiconducting chip in the point contact device, and two p-type regions called the emitter and collector corresponding to the forward and reverse biased junctions respectively. The cross section of a typical device of this form is shown in Fig. 1. The two p-type regions have to be placed very close together in order to get a good transistor action.

The voltages (batteries) shown in this figure correspond to those used in the basic common emitter

transistor circuit. The emitter to base junction is forward biased by making the emitter positive with respect to the base, and the collector to base junction is reverse biased by making the collector negative with respect to the base.

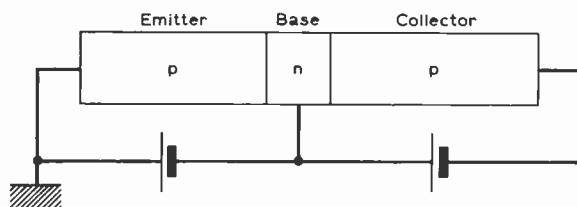


Fig. 1: Basic physical representation of a junction p-n-p transistor. The connections here correspond to the common emitter mode (emitter earthed).

At the forward biased emitter-base junction there is a flow of holes from the p-type region to the n-type region and a flow of electrons in the opposite direction. However the impurity concentration of the emitter is arranged to be much greater than that of the base so that the number of electrons flowing from the base to the emitter can be ignored in the simple treatment of the transistor. In more rigorous treatments of the device the "injection efficiency" of the emitter is involved: this is defined as the ratio of the current flowing across the emitter base junction due to the hole flow to that due to the electron flow together with that due to the holes, or more simply it is the ratio of hole current to total current.

Now consider what happens to the holes which are injected into the base region. If the base region were infinite in length all the individual holes would eventually recombine with the majority carriers, electrons, which are present in large numbers in the base region. However the holes can travel on average a certain distance through the base region before recombining. The time they exist in the base region is called their lifetime and is again an average concept. In the transistor the base region is made as narrow as possible so that a large fraction of the injected holes are able to diffuse to the collector junction.

At the collector junction they come under the influence of the electric field across the depletion layer, and because of their positive charge they are attracted to the collector which is negative with respect to the base.

Once the holes reach the collector they constitute the emitter to collector current. The holes which recombine with electrons in the base region result in the number of electrons in the base region decreasing. However the concentration has to remain constant in order to maintain equilibrium so electrons flow into the base from the external power supply, contributing to the base input current.

If by open circuiting the base no electrons are allowed to flow into the base region from the external circuit, only a very small emitter to collector current will flow. However if a small base current is permitted to flow an emitter to collector current many times this will be able to flow. In this way current amplification has been achieved. The ratio of the number of holes crossing the base junction to the number suffering recombination is called the beta of the device and given the symbol β .

Power gain

It is now possible to see how a power gain can be achieved. Considering the circuit of Fig. 2, called the common base mode of transistor operation, it is seen that the emitter current is almost the same as the collector current as just explained. The input current is the emitter current and the output current is that

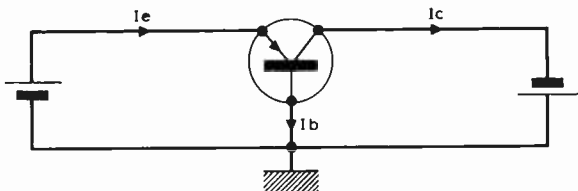


Fig. 2: Circuit showing the common base transistor arrangement (base earthed this time).

flowing from the collector. However these are nearly the same in size, the ratio of collector to emitter current being called the alpha of the device and given the symbol α . So how has a power gain been achieved?

Remember that the collector junction is reverse biased so the base to collector voltage V_{bc} is large, perhaps 10V in a small transistor or 100V in a larger device. However the base to emitter voltage V_{be} is very much smaller, typically 0.3V for a germanium device and 0.5V for a silicon device. Consequently there is a power gain between the emitter input and the collector output of several hundred times.

A simplified relationship between the α and the β of the transistor can easily be found. From the explanation so far given it is clear that the emitter current is equal to the sum of the collector and base currents. Consequently from the definitions of α and β the following equations can be written:

$$\alpha = I_c / I_e = I_c / (I_c + I_b) = I_c / (I_c + I_c / \beta) = \beta / (\beta + 1).$$

Alternatively the equation can be written in the form $\beta = \alpha / (1 - \alpha)$.

The equation for α shows that it is always less than 1 as β is always positive. A typical transistor could have a current gain, β , of 100. Consequently the value of α for this device would be 0.99. Obviously a large change in β gives rise to only a small change in α .

The manufacture of transistors

Various processes are used in the manufacture of transistors in order to produce devices of different capabilities in respect of frequency response, speed of switching, power dissipation, maximum collector voltage and so on. However many of the procedures are common to those used in the manufacture of diodes.

The starting point in the production of a transistor is once again a highly purified slice of silicon or germanium or perhaps some other semiconductor as mentioned previously such as gallium arsenide which is being increasingly used in the manufacture of devices.

Into this material the appropriate impurities are introduced in order to obtain the junctions upon which the action of the transistor depends.

The grown junction transistor

The grown type of transistor is produced by the same process used to prepare the grown diode. Either the impurity content of the melt from which the crystal is being grown is altered to obtain p- and n-type regions, or else the rate at which the crystal is pulled is altered giving the rate growth process. In either case very close control over the process has to be exercised in order to obtain a transistor which conforms to the required specifications.

A grown junction transistor might be made in the following way. Initially the collector is grown using a comparatively high purity n-type melt and a suitable seed crystal. After a short length of this material has been grown p-type impurity is added to the melt in order to over-compensate for the n-type impurity giving a net p-type behaviour to the region. A very short region of this material is produced to give a thin base. Finally the emitter is grown by adding an excess of donor impurity in order to give a region of low resistivity and a high injection efficiency. Typical resistivities of the collector, base and emitter regions might be 10, 1 and 0.02 Ω/cm . respectively. The resistivities of the regions of course vary inversely with their impurity concentration, low resistivity corresponding to a high impurity concentration. This process can be repeated several times in the growth of one crystal so that many transistors can be produced together.

The next step towards a finished transistor is to cut the crystal into slices. This means that the junctions have to be located, and this is done by etching the crystal, when the junctions are easily seen under a high power microscope. The transistor slices are then cut and divided up into small dice, perhaps one millimetre square, to give the individual transistors which are then mounted on to metal headers. Finally the leads are attached by soldering or by alloying and the complete transistor is encapsulated in its case and hermetically sealed to prevent contamination by airborne impurities.

The alloy junction transistor

One of the most popular types of transistor is the alloy junction device. This is made in the case of a germanium p-n-p device by attaching two indium "dots" to an n-type germanium dice. This is then raised to an accurately controlled temperature of around 600° C for a short time. The indium dots melt and dissolve some germanium from the dice until they are

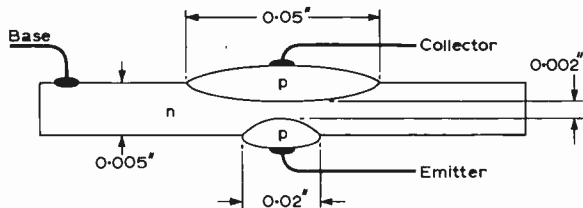


Fig. 3: The structure of a typical p-n-p alloy junction transistor.

saturated. After a short time the heating is removed and the wafer allowed to cool. The indium solidifies again but the germanium near the edge of the molten indium

—continued on page 423

P.W. GUIDE TO COMPONENTS

PART 10

M. K. TITMAN, B.Sc. (Eng)

Part 9 last month dealt with temperature-sensitive transducers. This month a number of transducers sensitive to other physical effects are described.

Proximity Detectors

Proximity detectors are used to sense mechanical changes in objects, including the measurement of length, position and movement. Among the most prominent components used for these applications are microswitches, reed relays, capacitive and inductive probes.

Microswitches

The simplest form of proximity detector is the mechanically operated microswitch and these devices are widely used for control and safety applications. Basically they are mechanical switches operated by a small movement of a plunger and a typical microswitch is illustrated in Fig. 8. Single or double contact

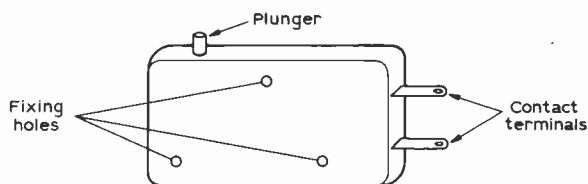


Fig. 8: Typical microswitch.

versions are available including normally open, normally closed or changeover. The contact is usually made by a wiping action rather than a contact closure as in relays and thus microswitches tend to be self cleaning and consequently more reliable. The actual movement is a sprung snap action which generally requires a small button plunger movement of less than 0.1 in.

Most microswitches are available with various add-on lever movements for depressing the button and some are also available for rotary activation. These are illustrated in Fig. 9 and can usually be modified by the designer to fit a particular require-

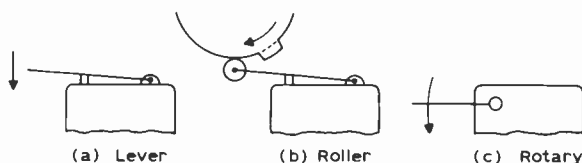


Fig. 9: Microswitch movements.

ment. As the force requirement to operate the button is usually from 2oz. to 10oz. for small microswitches, the mechanical advantage of a lever allows extremely sensitive, low force operation. Indeed low torque devices requiring torques of less than 1oz. are available.

Contacts are usually of silver or gold and in common with relays maximum current and voltage ratings are given. However it must be remembered that the actual power which can be reliably switched is considerably less than the product of these two maximum ratings. Maximum contact ratings vary from 0.2A, 250V d.c. and 2A, 250V a.c. to 1A, 250V d.c. and 10A, 250V a.c. Power levels for these contacts would generally be 20W and 100W respectively for reliable operation. Contact and mechanical life are generally 10^5 to 10^6 operations.

Since microswitches are mechanical in operation they are inherently unreliable components as they have a definite lifetime. However they are widely available at prices from 5s. to 20s. for domestic types, to 10s. to £10 for robust and special purpose industrial units. Disadvantages include the low speed of operation—usually less than 500 operations per minute—and the switch bounce associated with contact closure. Operating time including snap action and switch bounce is usually 5-15msecs.

Microswitches are used in electronic equipment for safety applications such as the disconnection of dangerous h.t. voltages when panels and casings are removed and also as the switching element of push buttons. They are particularly suitable for button arrays where their size contributes to high button density on front panels. In domestic and industrial applications they are used to sense the closure of doors and guards and as limit switches for machinery.

Reed Relays

Reed relays in conjunction with permanent magnets are being used increasingly in applications where high reliability and noncontact conditions are required. Since the construction, rating and design limitations of reed relays have been discussed in Part 7 in this series we will consider only the transducer aspects of their operation.

The reed operation when activated by a permanent magnet is shown in Fig. 10. It should be noted that the axis of the magnet should be in the same plane as the reed axis for correct operation. As the magnet approaches the reed the contact is closed (Fig. 10(a)) and the minimum distance for reliable operation for a given magnet and reed is termed the just operate distance. When the magnet moves away

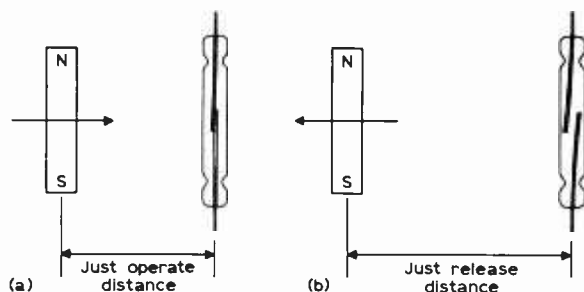


Fig. 10: Reed relay operation.

from the reed the contact opens (Fig. 10(b)) and this distance is known as the just release distance and is greater than the just operate distance. Typical spacings are 0.2-0.4in. and 0.3-0.6in., just operate and release distances respectively, for small 0.2in. diameter, 1in. long magnets and average reeds to 1-2in. for larger 0.5in. diameter 2in. long magnets.

Permanent magnet and reed combinations are used as proximity detectors for applications where high speed switching or noncontact operation is required or for high reliability. Reed switching times are an order better than microswitches at 1-5msecs and operating rates are higher with maximum greater than 100 operations per second. Lifetime is also increased to 10^7 - 10^8 operations, however the contact ratings are considerably reduced at 3-10W.

Capacitance Probes

Whilst capacitance probes are not generally available as components they are useful as proximity detectors particularly for metal detection. They consist of a plate connected to an oscillator circuit whose capacitance, with respect to the earthed object being detected, increases as the probe approaches. This alters the oscillator frequency and by feeding into a tuned circuit and detection stage a voltage variation is achieved which can operate a meter or switch a relay. The operation is illustrated in the block diagram of Fig. 11.

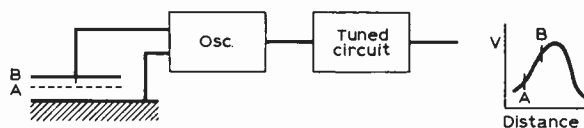


Fig. 11: Capacitance probe system.

The advantage of this form of proximity detector is that a proportional signal results and can be used for measurement and in addition the probe is very robust and easily constructed. Disadvantages are that the probe requires additional circuitry for control purposes and can be affected by atmospheric conditions such as humidity.

Inductive Probes

Inductive probes are used for precise linear measurement and a typical probe is shown in Fig. 12. The inductance of the coil is varied by the movement of the plunger which moves the coil core. The inductance variation is used to vary the frequency of an oscillator and the frequency variation is

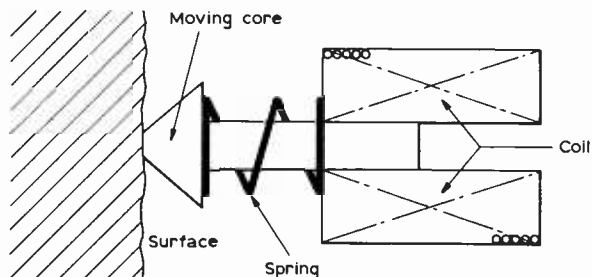


Fig. 12: Inductive proximity transducer.

monitored by a frequency to d.c. converter. Hence a proportional signal can be achieved and used for position or thickness measurement. The spring loading of the plunger allows a continuous surface or thickness variation measurement to be made.

Such transducers are generally used for fine linear measurement in the region of 0.001in. to 0.02in. Consequently they are precision made and extremely expensive. They are not robust and consequently are not generally used for control applications.

Pressure Transducers

By far the most interesting pressure transducers to the electronic engineer are those used for sensing and producing acoustical air pressure variations. However since loudspeakers and microphones have been discussed in a previous part in this series no further discussion is necessary. The remaining pressure transducers are not generally used in electronic equipment as components and have specialist applications only. Consequently they will be discussed only briefly.

Mechanical Pressure Transducers

Standard pressure gauges are used as electrical transducers when fitted with electrical contacts, mechanically operated. Two basic configurations are used as illustrated in Fig. 13. The Bourdon pressure gauge consists of an elliptical cross-section tube which tends to uncoil as the pressure increases and this results in the pointer moving: at a specific point the contacts close. Both normally-open and normally-closed versions are available as well as changeover types.

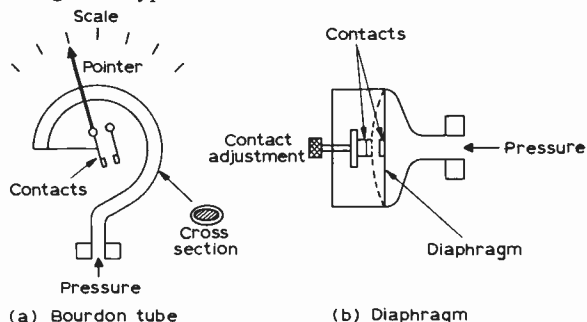


Fig. 13: Mechanical pressure gauge and transducer.

The diaphragm pressure gauge is the basis for most pressure transducers and in Fig. 13(b) the

electrical output is obtained from contacts which close when a pressure increase forces the diaphragm outward. Adjustment of the pressure at which the contacts close is achieved by screw adjustment of the contact. Since the diaphragm displacement is proportional to pressure any form of linear displacement transducer may be used. The basic methods used however are: the alteration in air gap of a transformer which gives a variation in transformer output; the resistance method in which carbon piles are used and connected in bridge form with resistors to give a balanced output; and the piezoelectric method which uses changes in the characteristic of a crystal and hence an oscillator frequency to give the required output variation.

Many miniature pressure transducers utilise a semiconductor strain gauge element connected as a bridge to give a proportional electrical output signal. Such a device is illustrated in Fig. 14. The pressure



Fig. 14: Miniature pressure transducer.

range for all these devices is dependent largely upon the mechanical properties of the diaphragm and varies from 0-10 p.s.i. to 0-1000 p.s.i. Prices vary considerably and are generally in the range £5-£50.

Load Cells

Load cells are basically diaphragm pressure gauges using piezoelectric, semiconductor strain gauge or potentiometric electrical outputs for the direct measurement of force or weight. Such devices are generally available in miniature form at prices from £5 to £25.

Light Operated Transducers

Since light operated transducers can be used in a wide range of measurement and control applications a very large number of devices is available. The applications include density measurement and control, colour matching and mixing, exposure meters, counting and pulse speed measurement and control, proximity detection, infra-red sensing and security applications. Three basic types of photoelectric cell are used and these are known as photovoltaic devices, photoemissive cells and photoconductive elements.

Photovoltaic Devices

These are essentially e.m.f. generators and are the only devices which do not require an externally applied voltage. The voltage generated across the cell terminals is proportional to the light intensity and although small can be used to drive a current meter since it is generated at low source impedance.

Selenium Cells

The selenium cell is one of the most widely used light sensing mechanisms especially since its spec-

tral response is very like that of the human eye. The response peaks in the region of yellow-green and falls off in infra-red and ultra-violet.

The construction of a selenium photovoltaic cell is illustrated in Fig. 15. The selenium is spread whilst

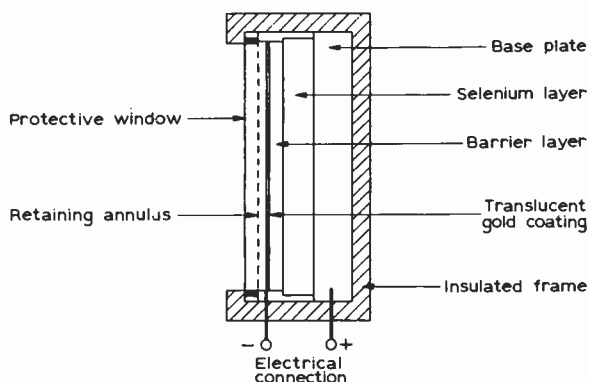


Fig. 15: Selenium photocell construction.

molten across an aluminium base plate and then annealed. The annealing produces a barrier layer on the surface on to which is deposited an extremely thin layer of gold to form a translucent surface electrode. The surface is then protected by a transparent glass or plastic window. Since the voltage is produced by light impinging on the selenium surface the cell is essentially a surface operated device and for high power output levels a large surface area is required. This can be an advantage in some applications since it can average light intensity over a large surface.

The mechanism by which the e.m.f. is generated depends upon the semiconductor characteristics of the device. The barrier layer formed on the surface of the selenium produces a barrier potential between the translucent conductor and the selenium and this is broken down by photon bombardment: the greater the light intensity the greater the breakdown and consequently the higher the e.m.f. produced. Since the impedance is low only low e.m.f. levels are generated but the current is sufficiently large to drive sensitive current galvanometers. Alternatively the e.m.f. can be amplified to give reading and control signals. However the response characteristics can vary with external influences and with time and in consequence they are generally only used for non-critical measurements and control functions. Another disadvantage is that the cells suffer from fatigue when subjected to light for long periods.

Selenium cells are widely available at prices ranging from 10s. to £5 depending on construction and size. They are also available in multifocus panel form and as simple panels. They are fairly large and commonly 1in. square or larger in panel size since they are primarily intended to give direct readings of light intensity to galvanometers.

Photovoltaic cells are also manufactured using alternative semiconductor materials in order to operate in other spectral regions. Notable amongst these materials are cuprous oxide and iron selenide. Another important device is the gallium arsenide photovoltaic detector which has an extremely high amplification factor and is considerably more sensitive than photomultipliers. These devices do not suffer from lack of sensitivity at high light levels

and can operate at temperatures in excess of 100°C. They are however very expensive.

Photoemissive Devices

Photoemissive devices are valve-like structures in which the flow of electrons is regulated by the light intensity on the cathode. The cathode is surfaced with a light sensitive material such as caesium, which when bombarded with photons releases electrons which are attracted to the anode which is maintained at a high positive potential. Figure 16 illustrates this construction and the circuit shows the load resistor. The assembly is encapsulated in a glass envelope and is either evacuated or filled with an inert gas such as argon.

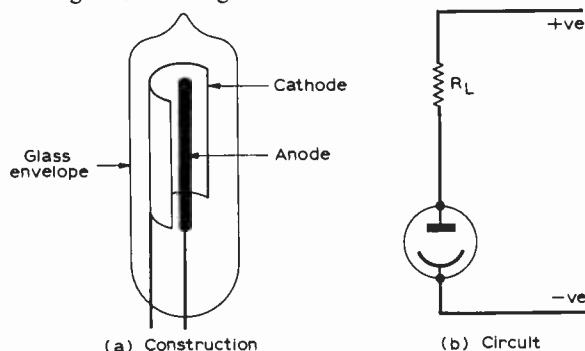


Fig. 16: The photoemissive valve.

The vacuum photocell is used for precision luminosity measurements since the current flow is independent of anode voltage provided this is maintained at a sufficiently high level to catch all the electrons emitted from the cathode. The current is also linear with light intensity which makes it particularly suitable for critical measurement and indication. A further important advantage is that the vacuum cell can operate at frequencies up to 10MHz.

The gas filled photoemissive cell operates in the same manner as the vacuum cell but providing the anode is at a sufficiently high potential electron collisions with the ionised gas particles releases further electrons. Consequently a current magnification is achieved and a magnification of 10 is possible. However these cells suffer from lack of linearity and are limited to operating frequencies below 10kHz.

The spectral response depends upon the cathode material and response peaks from the infra-red region (caesium on silver oxide) to the ultra-violet (caesium antimony) can be obtained. Disadvantages of this type of device are generally due to their large size and relative fragility. They are widely available at prices ranging from £1 to £15.

Photoconductive Elements

These are basically light dependent resistors of which cadmium sulphide and cadmium selenium cells are widely used. Most of the photovoltaic devices can also be used in conductive modes of operation such as selenium and silicon. A typical miniature cadmium sulphide cell is illustrated in Fig. 17 and the deposited CdS track can clearly be seen.

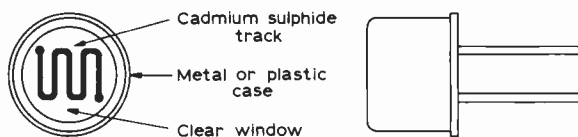


Fig. 17: The cadmium sulphide cell.

When no light reaches the conductive element the resistance is high and this is known as the dark resistance and the minimum value for a particular device is quoted. Typical values are from 100kΩ to 10MΩ. The resistance decreases rapidly with light intensity falling to values of from 50Ω to 2kΩ. Since they are capable of high power dissipation—from 200mW to 1W—they can be used at current levels which are sufficient to drive meter movements or relays. Consequently they can be used in conjunction with low voltage batteries in direct control systems, for example the automatic exposure control of cameras. They are also small and very robust which makes them particularly suitable for portable apparatus.

The spectral response is generally biased towards the red and infra-red regions but covers the visible spectrum. The peak is in the orange-red region. However since the response continues into the infra-red region precautions must be taken when this is not required. The operating temperature range is wide and -40°C to +70°C is normal. Cadmium sulphide cells are readily available at prices ranging from 5s. to 40s. and are available with either end view operation, as illustrated, or with side view. The variation in price is determined largely by method of construction and quantity requirements.

Photodiodes and Phototransistors

The photodiode is essentially a photovoltaic device since it operates by current flow due to incident light breaking down the barrier potential of the diode junction. However since the current flow is dependent upon light it can be operated in the photoconductive mode. Both germanium and silicon photodiodes are available but silicon devices have now largely superseded germanium devices due to the wider operating temperature range and increased power dissipation. In addition modern fabrication techniques have resulted in a higher frequency response of up to 150kHz compared with germanium devices having cut-off frequencies of 3-10kHz. The dark current is in the region of 50nA-10μA for silicon devices and 15-300μA for germanium.

The spectral response peaks in the red to infra-red region but covers the visible spectrum up to ultra-violet. Since the sensitivity is high in the infra-red region they can be used as infra-red detectors in such applications as fire and smoke detection.

The phototransistor is essentially a photodiode which amplifies the current generated at the base-emitter junction by incident light. Consequently the operation and spectral response are similar whilst the power output is considerably increased. The frequency response however tends to be limited and is usually less than 100kHz.

Figure 18 shows typical encapsulations for plastic encapsulated silicon diodes and transistors. Generally the lens is also of plastic, moulded to give the

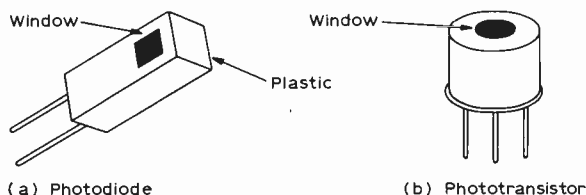


Fig. 18: Photodiode and phototransistor encapsulations.

correct focal characteristics. Glass encapsulations are used for applications where humidity is critical. The circuit symbols are shown in Fig. 19 for both p-n-p and n-p-n phototransistors.

Both photodiodes and phototransistors are readily available at prices ranging from 10s. to 60s. Multiple arrays for such purposes as computer character

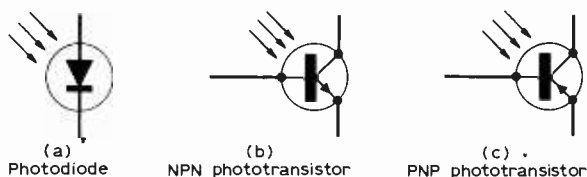


Fig. 19: Photodiode and phototransistor circuit symbols.



Fig. 20 (left): Circuit symbol for the light-activated s.c.r. (l.a.s.c.r.).

recognition and readouts are also available and the price depends largely upon the complexity. Photodiode and phototransistor arrays are now used for a large number of applications such as paper tape and card readers, interfaces and even in an extremely complicated matrix form as a television camera tube replacement.

Light Activated S.C.R.

The gate diode of an s.c.r. can be operated by incident light by the same mechanism as the phototransistor and consequently these devices are a logical extension of phototransistor applications. Since the s.c.r. or thyristor behaves essentially as a switch these devices cannot be used for light intensity measurement but are extremely useful in power control circuits. Light activated s.c.r.s (l.a.s.c.r.) can directly switch power levels up to 2kW and are therefore the most powerful light operated component. They are used in industrial applications for motor and heat controls as well as high power lamp controls. The circuit symbol is shown in Fig. 20.

Since the applications of l.a.s.c.r.s are limited they tend to be relatively expensive control elements. Prices range from £2 to £20 and only a few of the major semiconductor suppliers manufacture them. However as their application becomes more widely known it is expected that prices will fall.

The Future

Transducers are perhaps one of the least known groups of electronic components in the electronic industry. Since they largely measure and monitor physical phenomena in fields unfamiliar to the electronic engineer this is to some extent understandable.

Conversely as they are essentially electronic, engineers of other disciplines are likewise uninterested. However it is in this group of components that some of the most spectacular advances may be made, since they can be linked directly with electronic complexes such as computers. This should give increased stimulus to their development, particularly since the breakthrough of thyristors into the domestic equipment field will increasingly require direct transducer control.

Among the advances likely in the very near future are integrated circuit photodiode arrays to replace television camera tubes, especially for computer interface uses such as character recognition and drawn information. Similarly pressure sensing and temperature controlling elements will be incorporated in linear integrated circuits to give direct electronic outputs. All these advances will be stimulated by increased interest by electronic and other engineers and it is for this reason that an understanding of transducer mechanisms is essential in electronics today.

TO BE CONTINUED

BASIC SEMICONDUCTOR TECHNOLOGY

—continued from page 417

recrystallises into the main lattice. As the recrystallised germanium contains indium as an impurity it is of the p-type near to both of the indium dots. Consequently at the boundaries between each of the p-type zones and the n-type zones there are p-n junctions and the device is now a p-n-p alloy junction transistor. Fig. 3 shows the structure of such a p-n-p alloy transistor.

The two dots used for the emitter and collector regions are either punched from a very thin sheet of indium or else formed in small drops from molten indium. The collector is made several times larger than the emitter to improve the efficiency of collection of the holes injected into the base from the emitter. In this way only a small percentage of holes are lost by diffusion to the surface of the base region where they recombine with electrons on the surface.

In the alloy junction transistor difficulty is experienced in precisely controlling the width of the base region during manufacture. The slightest variation in the heating process can produce a base which is too wide or too narrow. If it is too wide the frequency characteristics of the device are poor because injected holes take a long time to cross to the collector junction, and also the alpha of the device will be reduced because the number of recombined holes increases with the transit time across the base. If the base is too thin the maximum voltage which can be applied to the base-collector junction will be reduced since if too large a voltage is applied the collector junction depletion layer will reach right through to the emitter and short out the transistor. This means that it is difficult to achieve a very close tolerance during manufacture and in many cases devices are prepared in families and selected into individual types after they have been completed. Finally, the device has leads attached and is then encapsulated in a suitable container depending on the power dissipation expected in the device.

Despite their limitations this type of transistor is used extensively in low frequency amplifiers, power control circuits and so on, although they are slowly being replaced by the newer epitaxial devices.

TO BE CONTINUED

LETTERS

■ ■ ■ The Editor does not necessarily endorse the views expressed by correspondents.

Ex-Meter

Why do radio enthusiasts place the S meter so high in the list of receiver requirements? On tuning the bands, one so often hears remarks like, "... coming in S7 here, Jack ... using AR88 plus 40m dipole." Very well, Jack knows his signal is getting out, but he knows nothing about his *field strength* at that location. No doubt he and his contact both relate it with S readings, so they continue with the ragchew quite happily.

Looking closer at this business, we find that on a receiver, when a particular level of signal is present at the aerial terminal, a particular reading is given on the S meter; but this is *only* true if the r.f., i.f., and aerial atten. circuits are in the same condition as when the S meter was calibrated, i.e. all gains unchanged and all r.f. and i.f. circuits in tune. Even with such a receiver, we find that different aerials will give different S readings for the same field strength. To give useful signal strength information to a contact, all front end controls must be set to maximum gain, and average S meter reading taken over a short period, and the result sent back with full details of the aerial type, length, height, direction along with details of its special peculiarities due to surrounding objects. From what I hear on the bands, nothing approaching this is given, which is understandable. Personally I dislike touching the controls after reaching a good balance between r.f., i.f., and a.f. gains. I am not against operators having a rough guess at the signal strength, but am merely pointing out that there is no need for a S meter. If one wants to start using instruments then use a proper field strength meter and give the figures in volts/metre—not in meaningless S units.

Someone may say "Well I use the S meter to find a peak while tuning in weak signals". Speaking for myself, I have rarely come across any DX which did not require slight offset tuning to avoid adjacent channel interference or to increase intelligibility.

Take my advice, disconnect that worthless gadget, add a switch and a shunt, and use it to measure something worthwhile—like the h.t. current in each section!—**R. Mitchell** (Glasgow).

Take 20

I have built the electronic organ by Julian Anderson (August issue) and while I am extremely pleased with the results, I feel that the claim that it can be built for twenty shillings is highly misleading as my components cost 39s., the 2N2646 alone cost 16s!

I realise one can buy components at one shop cheaper than at another, but the differences are small. Would it not be better for the author to either confine himself to the limit or to change the title of the series?—**S. King** (York).

The author replies

The business of costing projects is very difficult and this is why prices are rarely given. The object of Take 20 is to provide each month a simple constructional project which will fall within the pocket of most readers. I am sorry that Mr. King had to pay 39s. for his components but I can assure him that this project was costed out from components available from advertisers in PRACTICAL WIRELESS. In the August issue OC81 transistors were advertised for prices between 2s. and 5s. (excluding untested cheaper ones). Many shops charge 6d. for resistors yet the same ones are available for under 2d. from other advertisers.

The reasons for these price differences are not usually due to one retailer making a thumping great profit but because a lot of the components sold are surplus in one form or another.

Because of this readers are well advised to obtain as many lists and catalogues as possible, especially if component cost is a major consideration in whether to build a project or not.

Can I take this opportunity to thank all the readers who have written to me on Take 20 giving various suggestions—these are genuinely welcome especially the ones asking for particular projects.—Julian Anderson.

Availability of Integrated Circuits

We continually hear that new integrated circuits are being introduced and that soon most constructional projects will be based on them.

Your excellent magazine has given a number of circuits utilising i.c.s. yet the component stockists in my area do not have them and I am told that manufacturers are reluctant to make these generally available.

I wonder why this is so? I am sure that in the past amateurs like the readers of P.W. have contributed to the growth of the electronics industry, why should we now be deprived of the latest devices for experimenting?—**J. Pope** (London E.12).

Jack's alright

I agree in the main with your comments in the June leader, although I would prefer to see your magazine carry on using cycles. However, one point which did strike me was your comment on DIN plugs. As one who has spent many hours making special leads and soldering phono plugs I see a need for standardisation. However, I wonder why not the GPO Jack, which has been used by the BBC and others for years. The two versions, two way and three way, provide most normally needed connections, in addition to which they are very strong, easy to fit and enable switched sockets to be used. Equivalent DIN plugs and sockets are also usually at least 2s. more than their counterpart jack sockets.—**R. J. Paulton** (Birmingham, 26).

Old Name?

I wonder how many readers have thought about the name Practical Wireless? "Wireless" as a word has almost fallen from our vocabulary and "Radio" has taken its place, yet our most progressive magazine sticks to its title. I am not complaining, in fact I think it is rather a pleasant link with the early days—but it is a bit odd isn't it?—**K. Matthews** (Cambridge).

RADIO SOCIETY GREAT BRITAIN

**SEE WORLD'S FINEST
COMMUNICATION RECEIVERS
& RADIO EQUIPMENT**

AT THE
**INTERNATIONAL RADIO ENGINEERING
COMMUNICATIONS EXHIBITION**

*ROYAL HORTICULTURAL NEW HALL
Greycoat Street, Westminster, London S.W.1.*

**Wednesday to Saturday
1 to 4 OCTOBER 1969**

OPEN 10 a.m. to 9 p.m.

ADMISSION 3/6

DISPLAYS BY

- CABLE & WIRELESS
- ROYAL AIR FORCE
- ROYAL SIGNALS
- ROYAL NAVY
- POST OFFICE
- HOME CONSTRUCTION AND
DESIGN COMPETITION & DISPLAY
- COMPLETE TRANSMITTING STATIONS
WORKING THE WORLD
- EDUCATION AND TRAINING
INFORMATION

**WIN
£185**

HQ 170A & V.H.F.
HAMMARLUND
RECEIVER

by
exchanging this
advert for free
raffle entry form
at EXHIBITION

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents.

Can't stand the din!

Whilst agreeing with most of your June editorial concerning changing standards your appraisal of the DIN plug does nothing but arouse my utmost wrath.

Admittedly the "dreaded DIN plug" does have the advantage of multiple connections compared with, for example, that other horror, the cheap 'n' nasty phono plug. However just thinking about all those close packed pins waiting for the stray strand of wire or blob of solder to short them out makes me shudder, not to mention those two pieces of metal casing which will inevitably collapse between the fingers or that tenacious plastic cover which never budes an inch (sorry 25.4 mm!!) in an emergency. Even one of my friends—a most staunch supporter of the beast, was somewhat daunted when, after carefully rewiring all the DIN sockets on his tape recorder to the international convention, he found that the machine would not match anyone else's leads.

Anyone with any great respect for his equipment should stick to that good old stalwart, the *standard* jack plug. Reliable, almost indestructible and easy to connect, with switched sockets, screening and 3-way (stereo) systems all easily available this is quite simply unbeatable. And if this is a little on the expensive side another frequently neglected plug (and, incidentally, the only other species known to survive a year of university parties, dances and amateur dramatics!) is the metal TV co-ax plug, which I and several friends have *independently* concluded to be the next best thing, both on grounds of performance, availability and cheapness.

So all I have left to say to you, DIN plug is go home and never darken these shores again!—**J. Dowson** (Trinity College, Cambridge).

★ ★ ★

It is with regret that I see you are lending your support to the abominable DIN plug system. The spread of these connectors is one more example of the current trend towards choosing the

worst conceivable alternative and making it a "standard"; a trend which has already given us meaningless mains flex coding and an inconvenient unit of length (millimetres, used for dimensions of cabinets), and will doubtless introduce peak music power before long.

Quite apart from the poor construction, reliability and endurance of the DIN plugs available at present—a thing which could be remedied—the system possesses inherent faults. The plugs must be angularly aligned, which in their usual inaccessible position is difficult. The simultaneous use of different pins results in a loss of versatility. Some twelve different plugs exist, which makes separate leads necessary for each function even when functions are not required together; and within the common five-pin 180° plug, variations are still necessary to accommodate the morass of reversed connections, pin bridges and series resistors. Did somebody say *standard*?—**R. A. Lyons** (Reading, Berkshire).

[We agree that the DIN plug system is not perfect but at least it is a standard—something that UK audio manufacturers have not bothered to devise as yet.—Editor.]

No Mars bar here

Now you DX experts, having on your splendid equipment received hosts of stations, look about 11 pm towards the east! There is a splendid prize for you, the acme of man's most earnest endeavours, to contact any intelligent beings, outside his own planet. It is the red planet Mars!

I believe that Lowell's ideas are nearer the truth even today, than are all those of his opponents! I am convinced there are a few Martians left, safely ensconced within some great castle-like refuges, inside covered craters.

Go down the garden path to your quiet den. Put on your phones. At once the sweet silence is subdued by babel. Yet may there not still be some small unexplored "windows"? Through one of these a clattering, staccato, intensive message may be

received? The well informed operator will know it can be from nowhere on earth. He will be the lucky guy to receive the first "message from Mars!"

During the quite early days of wireless, during Martian oppositions, there were quite earnest and some even desperate attempts to contact Mars. "Popular Wireless" even made a 24-valve set as early as 1924. The results were rather inconclusive. Some people actually claimed to have received signals; even the great Marconi did! Nothing however could be proved absolutely. Equipment today is so much more powerful, that success may be at last attained!

With my little one to four valve sets I myself have tried. My finest results have generally ended with a sweet little voice announcing, "this is Sydney, etc, etc." That however was a well worth while achievement.—**A. Trowbridge** (Middlesex).

The secret of success

I'm in rather a desperate situation at the moment and I wonder if any of your readers could help?

Having used valves in all my constructional projects up till now I have been blessed with about 99% success, but being more and more tempted by gleaming transistors (and incidentally the almost complete absence of valve designs in P.W.) I decided to have a go with semiconductors. So far I have attempted about a dozen designs of one sort and another and the only one that worked was a crystal set!

My latest project has been a complementary push-pull amplifier—could I get anything out of it?—not a !!!! I adjusted biasing resistors, substituted transistors, checked the wiring till I was blue in the face and I still couldn't even get a mA of quiescent current. Meanwhile my friends design these contraptions, which always work perfectly, and then even sell their designs but still not a sausage out of my own designs.

Please, what is the secret?—**Richard Ross** (Warwickshire).

60 r.p.m. Geared Motor. This is a powerful unit, driven by a mains motor of similar type to, but rather larger than the average Tape Deck or Record Player motor. The gear boxes may be detached. It is, in fact, a unit measuring approximately 3 1/2 x 2 1/2 x 1 1/2 in. thick. The final drive shaft is 1/2 in. wide, 1 in. long. 35/-

A Micro Meter bargain. Limited quantity only, centre zero 50-0-50 micro amps. This is a Weston Meter enclosed in clear perspex case for flush mounting. Dial size approximately 2 1/2 in. wide. The scale is not engraved but has a red part in the centre and a green part to the left of centre. Scale could be cleaned off and re-written to suit your particular requirements. Regular price probably over £5 each, our price 29/8 each.

Battery Record Player. Made by Collaro. This is made up on a unit plate with speed selector and pick-up. The turntable is a heavy one and measures approximately 9 1/2 in. Pick-up is fitted with the famous "Studio" cartridge. Price 69/8, postage and insurance 6/6.

E.H.T. Condenser. 28 Kv. 0-0011 mfd. Suitable for transmitting test conditions 6A at 300kc. Bakelite case. 18/8 each.

85 Watt Tubular Element. Very well made unit. The element is wound on a porcelain former then encased in a brass tube terminated with beaded leads 12 in. long. Normal mains voltage. Price 5/6 each or 54/- per doz.

Fuses to Make Switch. Double pole, 5 amp contacts or can be used as single pole, 10 amp, contacts 250 volt working. Single hole fixing. 2/8 each, 24/- dozen.

Door Switch. Contacts open when plunger is depressed. Prevents lights being left on. 15 amp contacts, 230 volt working. Made by Arrow. 3/8 each, 88/- per dozen.

Rotary Appliance Switch. 16 amp, 230 volt on moulded ceramic base. Operated by pointer knob (not supplied). 2/- each, 18/- per dozen.

1/40th h.p. Motor. Made by the French (Casar) Company. This is an excellent totally enclosed motor, powerful enough to operate small lathe, drilling machine, washing machine, etc. It's speed is 1,450 r.p.m. Made for normal 50 cycle, 230/250 volts mains, totally enclosed, size 2 1/2 x 3 1/2 in. dia. with 1 in. of 1/2 in. spindle. Price 19/6 plus 4/6 postage and insurance.

Burglar Alarm Kit. Protect your home and family by frightening away the intruder. With our circuit a mains operated bell rings loudly directly the door or window is opened. Kit comprises 12 reed switches, 12 magnets, relay, mains transformer and bell with circuit. Price 49/8.

NICAD RECHARGEABLE BATTERIES

3-6V 500mA size 1 1/2 x 1 1/2 in. dia. type ref DKZ500. Really powerful, will deliver 1 amp for 4 hours. Regular price 32/6. Our price 17/6 each. New and guaranteed. Other voltages available. Single cell 1-2V 6/6, 10 cell 12V 66/-.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 89/8, less than the value of the clock alone—post and insurance 2/9.

INDICATOR LAMP

Panel mounting, consists of neon lamp in red plastic lens with resistor in leads for mains operation. 2/6 each. 24/- dozen.

BECKASTAT

This is an instant thermostat, simply plug your appliance into it and its lead into wall plug. Adjustable set point for normal air temperatures. 13A loading. Will save its cost in a season. 19/6. Post and insurance 2/9.

SOLDER GUN

A must for every busy man. Gives almost instant heat; also illuminates job. 100 watt 220/240V. 89/8 (saves you over 80/-), post & ins. 4/6. BIG JOB 250 watt model 99/8 (saves you over £8.10.0), post & ins. 6/6.

FLEX BARGAINS

Screwed 3 Core Flex. Each core 14/0076 Copper PVC insulated any coloured, the 3 cores laid together and metal braided overall. Price £3.15. per 100 yds. coil.

15 Amp 3 Core Non-kink Flex. 70/0076 insulated coloured cores, protected by tough rubber sheath, then black cotton braided with white tracer. A normal domestic flex as fitted to 3 Kw. fire. Regular price 3/6 per yd. 50 yd. coil £4.10.0, or cut to your length 2/6 per yd.

10 Amp 3 Core Non-kink Flex. As above but cores are 12/0076 Copper. Normal price 2/6 per yd. 100 yd. coil £7.10.0, or cut to your length 1/8 per yd. 6 Amp 2 Core Flex. As above, but 2 Cores each 20/0076 as used for Vacuum Cleaners, Electric Blankets, etc. 89/8 100 yd. coil.



ELECTRIC TIME SWITCH

Made by Smith's these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. 59/8, post and ins. 4/6. Additional time contacts 10/- pair.

The Full-Fi STEREO SIX

The amplifier sensation of the year



You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-up and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "Treble Lift and Cut", "Balance" and separate Mains on/off switch. Price is £29.9.0, plus 7/6 post and insurance. Speakers (with tweeters) in oiled teak finish cabinets to match amplifier, £8.8.0 per pair.

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 29/6, plus 2/6 post.



THIS MONTH'S SNIP

3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Cyclon" Company for the equally famous Radiomobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra if required) with a frequency coverage 1820 Kc/s-925 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2 x 2 x 1 1/2 in. thick) with reduction gear for fine tuning. Snip price this month 18/6, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post Free.



Horstmann 'Time and Set' Switch

(A 15 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fire, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6, p. & ins. 4/6.

DISTRIBUTION PANELS


Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs. Supplied complete with 6 feet of heavy cable and 13 amp plug. Similar advertised at 25. Our price 89/8, + 4/6 P & I.

VARYLITE

Will dim incandescent lighting up to 800 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob 88.10.6.

BUY TIME SLOT METERS

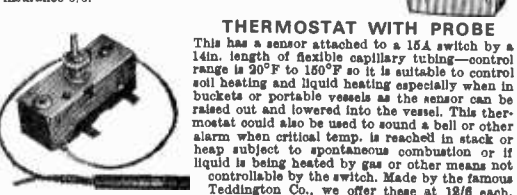If you hire out equipment such as TV sets by the hour then these slot meters are what you require. We have 3 types, 8d. an hour, 1/- an hour and 1/6 an hour. Brand new. Made by the famous Weston Company. Price £3.19.6, postage and insurance 6/6.



THERMOSTAT WITH PROBE

This has a sensor attached to a 15A switch by a 14in. length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stock or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at 12/6 each. Postage and insurance 2/9.

HI FI BARGAIN

FULL F1 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 80-10,000 c.p.s.—specify 8 or 16 ohms—Mains resistance 600 c.p.s.—Chassis Diam. 12in.—12in. over mounting lug—Baffle hole 11in. Diam.—Mounting holes 4, holes 1/4in. diam. on pitch circle 11 1/2 in. diam.—Overall 12 1/2 x 5 1/2 in. A 25 speaker offered for only £3.9.6 plus 7/6 p. & p. Don't miss this offer. 15in. 80 watt £7.10.6.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4 in. diameter. Will make and break up to 4 amp up to 300 volts. Price 2/6 each. 24/- dozen.

Standard. 2in. long x 3/16 in. diameter. This will break currents of up to 1 amp, voltages up to 250 volts. Price 8/- each. 18/- per dozen.

Flat. Flat type, 2in. long, just over 1/16 in. thick, approximately 1/2 in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating lamp, 200 volts. Price 8/- each. 24/- dozen.

Small ceramic magnets to operate these reed switches 1/8 each. 12/- dozen.



ROTISSERIE MOTOR

Very powerful 7 r.p.m., operates from standard A.C. mains. 89/8, plus 8/6 P. & I.

EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. At the pull of a cord it extracts grease, grime and cooking smells before they dirty decorations. Suitable for kitchens, bathrooms, factories, changing rooms, etc.

It's so quiet it can hardly be heard. Compact, slim, casing with 5 1/2 in. fan blades. Suitable wherever it is necessary to move air fast. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector and fixing brackets. 39/6 + 8/6 post and ins.



230 VOLT SOLENOID 1/2 in. stroke. Size 2 1/2 in. x 2in. x 1 1/2 in. 14/6, postage 2/9.

FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—50 w. 19/6. Kit D—65 w. 19/6. Kit E—80 w. 19/6. Kit F—100 w. 19/6. Kit G—120 w. 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit F 1/6 on first kit then 3/6 on each two kits ordered.

DEAC RECHARGEABLE BATTERY

1-2V-9000 mA/hr. type (3000DKZ). Size 2in. dia. x 1 1/2 in. thick approx. Tremendously powerful, will deliver 4 amp for 4 hour. Regular price over £2 each. Snip price 19/6 each. NEW AND UNUSED.

MAINS TRANSFORMER SNIP

Making a power pack for amplifier or other equipment? These transformers have normal mains primaries (280/240V) and isolated secondaries of two types (1) 12V. 500mA. at 8/6; (2) 15V. 500 mA at 8/6.



THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knob. Quickly adjustable from 30-80°F. 9/6 plus 1/- post. Suitable box for wall mounting. 5/- P. & I. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-90°F. Internal screw alters the setting so this could be adjustable over 80° to 1000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16 yd 10/-) is wound round the pipes. 7/6 P. & I. 1/-.

Type "E". This is a standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks, developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH

Also 102/3 Tamworth Road, Croydon

TECHNICAL TRAINING *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

10/69

INTERNATIONAL CORRESPONDENCE SCHOOLS



AMAZING MINI-DRILL

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6, p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money ref. g'tee.

FOR PRECISION MODEL WORK

+ 6 TOOLS

ONLY 39/6

MERLIN SUPPLY CO.

Dept. PW10D, Nailsea, Bristol BS19 2LP

BI-PRE-PAK LTD

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0702) 46844

RETURN OF THE UNBEATABLE P.1. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P.1 PLEASE ASK FOR PAK P.1. ONLY 10/-
2/- P & P on this Pak.

Pak No.	NEW, UNMARKED, UNTESTED PAKS	Price
B78	12 Integrated circuits, Mixed types, data supplied with orders.	10/-
B80	8 Dual Transistors, 811 NPN Matched output pairs.	10/-
B82	10 OC45-OC81D-OC81 Transistors, Mullard glass types.	10/-
B83	200 Trans. manufacturer's rejects all types NPN, PNP, 811 and Germ.	10/-
B84	100 Silicon diodes DO-7 Case, OA200 -OA202 Polarity marked.	10/-

Pak No.	NEW, TESTED AND MARKED PAKS	Price
B79	4 IN4007 Silicon Diodes, 1000 P.I.V. 1 Amp Min. Type.	10/-
B81	10 Reed Switches, mixed types large and small	10/-
B99	200 Capacitors, Electrolytics, paper, silver mica, etc. Post and packing, this Pak 2/6.	10/-

Transistors	Price
AC126	2/6
AC127	2/6
AC176	5/-
AD149	10/-
BC107-8-9	2/6
BC171	3/-
BC172	3/-
BC173	3/-
OC22	6/-
OC23	6/-
OC26	7/6
OC28	5/-
OC35	10/-
OC38	5/-
OC44	2/6
OC45	2/6
OC71	2/6
OC83	4/-
OC139	3/6
OC140	3/6
OC201	8/-
OC711	10/-
8C109	3/6
8C109	3/6
2N4284	3/6
2N4285	3/6
2N4286	3/6
2N4287	3/6
2N4288	3/6
2N4289	3/6
2N4290	3/6
2N4292	3/6
2N3055	15/-
28Q34	10/-
2N3819 FET	9/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE list and catalogue of all our products. Check your own equivalent with our free substitution chart.

Matched Set. NPN/ PNP AD161-AD168 Comp. pair Pak 10/- PR.	Complementary Set. NPN/PNP Germ. trans., Pak F.3 2/6 PR.
--	---

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/-.
CASH WITH ORDER PLEASE, add 1/- post and packing.
OVERSEAS ADD EXTRA FOR AIRMAIL

PRACTICAL INTEGRATED CIRCUITS

Constructional projects in
Microelectronics for the
amateur experimenter

New from Newnes-Butterworth

by A. J. McEvoy, M.Sc. and
L. McNamara, B.Sc.


1969 144 pp. many illustrations
18s by post 19s. 6d.

THE BUTTERWORTH GROUP
88 Kingsway, London, WC2

a beginner's TRANSISTOR CAPACITANCE BRIDGE

PART 1

KEITH JOHNSON

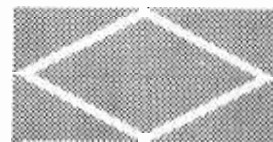

A NUMBER of useful LCR bridges suitable for the home constructor have been described in the past, some with fairly complex circuitry, and therefore suitable as accurate laboratory standards. The author, however, felt the need for a quite simple instrument which would constitute a useful addition to the average home workshop. The present bridge was built up on Cir-kit board, with used components which were immediately to hand in the spares box. All parts can, of course, be purchased new if necessary.

Of the three constants, inductance, capacitance, and resistance, commonly encountered in electronic circuits the one most likely to require test facilities which are not immediately available is capacitance. Generally, coils and resistors can be satisfactorily tested, at least for continuity and resistance, with a good ohmmeter. Even larger value electrolytic capacitors of 16 μ F and above can be roughly examined in this way, by comparing the size of the "flick" registered on the ohmmeter due to the charging current with that shown by a sound capacitor. D.c. leakage is, in this case, detected by the presence of a steady current, or a fixed value of high resistance, which is generally greater in one direction than the other. It is when dealing with small values of capacitor, in the range, say, from 10pF up to a few microfarads, that difficulties may be encountered with the usual meter tests, and it is therefore in this range that the present instrument fulfils its most useful purpose.

While the bridge principle will probably be familiar to experienced constructors, a brief summary of the basic principles involved may not be out of place for those encountering this type of circuit for the first time. Referring to Fig. 1, a typical

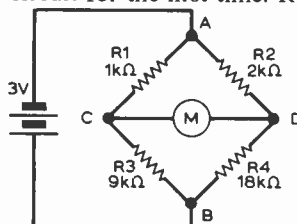


Fig. 1: A basic Wheatstone bridge.

Wheatstone bridge, the application of a voltage of, for example, 3V, between points A and B results in no voltage appearing across C and D with the values of resistance shown, so that no reading is shown on the meter, M. This is because the bridge is in what is known as the "balanced state". In actual fact, the voltages at C and D are each 0.3V with respect to A, and are therefore zero with respect to each other. The circuit would now become unbalanced if, for example, resistance R2 were replaced by either a

higher or lower value. In these cases, the voltage at D would differ from that at C, and this unbalance would be registered by a reading on the meter.

A little consideration will show that, in Fig. 1, the condition of balance is obtained when $\frac{R1}{R2} = \frac{R3}{R4}$

so that $R1 = \frac{R2 \times R3}{R4}$ when the bridge is in balance.

This basic circuit can, therefore, be used to determine the value of an unknown resistance when the other three are known.

If we now replace R3 and R4 by capacitors, and the source by an alternating voltage, the circuit becomes that of Fig. 2, where, in the unbalanced state, an a.c. signal appears between C and D, resulting in an audible note in the headphones, H.

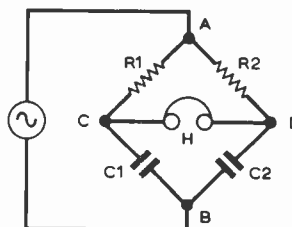


Fig. 2: A Wheatstone bridge adapted for reactance balancing, using an a.c. source and headphones for detecting balance.

Now, let us consider how to use this arrangement to determine the value of an unknown capacitor. If $R1 = R2$, by making the unknown capacitor C1 in the figure and substituting different values in turn for C2, we would eventually achieve a balanced state (as indicated by silence on the phones) when $C1 = C2$, as only then would the above ratios be equal. Note that the resistance of a capacitor to d.c. is inversely proportional to its capacitance. Obviously, this would be a rather clumsy procedure, and a much better scheme is to fix C2 at some convenient value, not greatly differing from the expected value of C1, and make one of the resistors variable. This will enable an equally satisfactory condition of balance to be obtained. Then, by measuring the value of the resistance at this balance point, and either having a calibrated scale, or calculating from the above equation, the value of C1 can be determined. In practice, since we wish to be able to carry out measurements over quite a wide range of capacities, C2 becomes a switched bank of capacitors increasing in steps of 10 from 10pF to 100 μ F. In this way, capacitors from 1pF to 100 μ F can be tested, and measurements carried out on cable and even valve inter-electrode capacitances. Some typical applications are discussed at the end of the article.

To return to the circuit of Fig. 2, this could be made the basis of a very simple bridge, merely by employing a 50 Hz mains input (obtained, for

example, from the secondary of a mains transformer), retaining the headphones for detection purposes. However, the slightly more elaborate arrangement employed in the present bridge, as shown schematically in Fig. 3, was considered well worth while. The three main sections are an audio oscillator, the bridge itself, and an audio amplifier feeding into an indicating meter. The choice of this arrangement has three advantages. First, the tester is completely portable, being operated from two 9V batteries; second, the operating frequency can be chosen to enable the most suitable resistance-reactance combination to be employed on all ranges; and third, by amplifying the signal following the bridge, the use of a meter becomes possible, enabling higher accuracy to be obtained than would be the case with a simple audio detector. A further advantage concerns the testing of a capacitor for leakage.

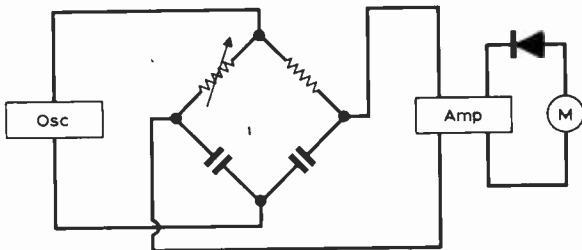


Fig. 3: A practical arrangement for a capacitance measuring bridge, with an amplifier and meter to give a more positive reading than Fig. 2.

This test is especially important in the case of the sub-miniature type of coupling capacitor (usually 4 or $8\mu\text{F}$) used in transistor audio circuits, as a partially leaky component here can easily introduce sufficient bias voltage variation to ruin a transistor. The presence of leakage in a capacitor of this type is immediately indicated with the present instrument.

Oscillator and Amplifier

Figure 4 shows the oscillator circuit. Only one transistor is used, and the transformer can be any audio type which is conveniently to hand. Separate batteries are used for the oscillator and amplifier, so as to avoid unwanted feedback, or the effect of the signal being picked up directly from the bridge instead of through the bridge. Since the instrument is a null-point detector, it can be realised that a small amount of pickup of this type would have a serious effect on accuracy. Using a separate battery also means that the oscillator portion can be checked immediately after construction, which, in any case, is advisable, for some adjustment to the values of R_1 and C_1 may have to be made if oscillation is difficult to obtain. If this is the case, try also reversing the connections to the windings of the audio transformer, or reversing the windings themselves. R_1 and C_1 will also vary the frequency, so these should be altered, if necessary, to provide a note of about 800



Hz indicated by headphones across R_2 . The current should be approximately 1mA. Headphones could be used directly to the bridge after this oscillator circuit, but some amplification enables a meter to be used, as already explained.

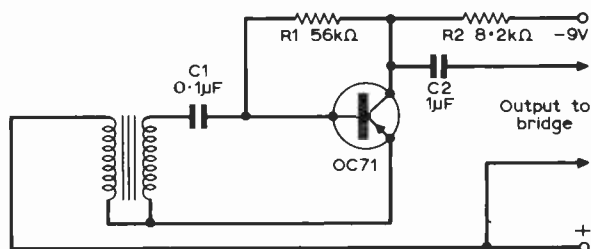


Fig. 4: A simple 800Hz audio oscillator suitable for driving a bridge.

A straightforward push-pull amplifier circuit was decided upon, as the transformers and transistors were available from an old amplifier which had just been dismantled. The circuit is shown in Fig. 5, and presents no novel features. It should be tested with a speaker first, by injecting a signal from any a.c. source. The no-signal current should be about 8mA. A diode in series with the secondary of the output transformer is used to rectify the d.c. signal and provide a d.c. voltage to operate the microammeter. In the original bridge, an army surplus moving-coil


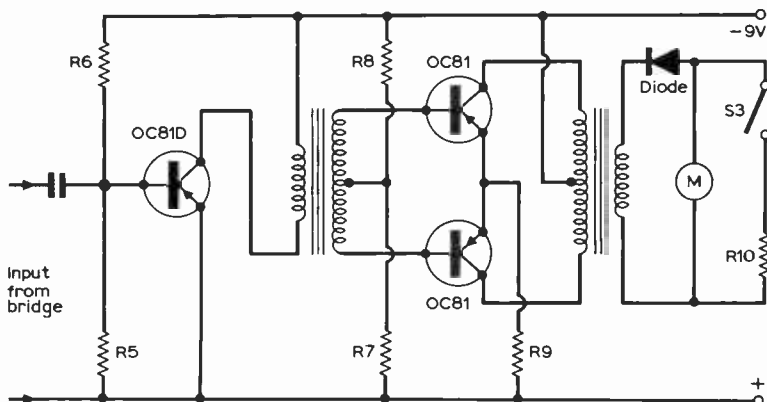


Fig. 5: A push-pull amplifier, detector and meter.

LOOK!


PRACTICAL!
VISUAL!
EXCITING!

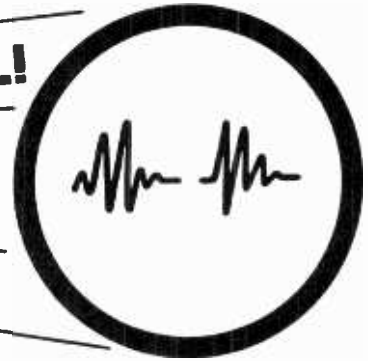

a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

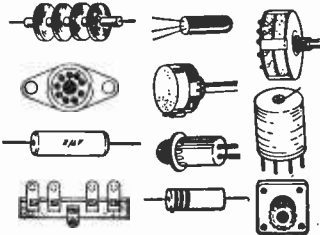complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

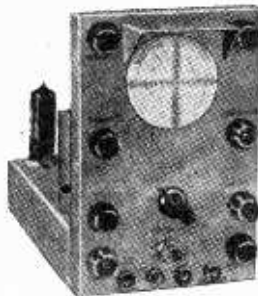a modern and professional **CATHODE RAY OSCILLOSCOPE**



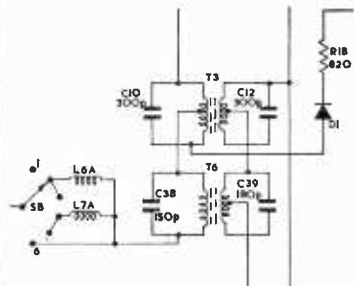3 ▶ READ and DRAW and UNDERSTAND CIRCUIT DIAGRAMS



4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESSPLEASE PW10

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



THE COWDREY FIVE. Specially designed Corner Cabinet. Fitted rubber feet. 20 1/2 x 13 x 7 1/2 in. deep. Finished in teak wood grain cloth with Vynal front. Fitted 8 x 3 in., 7 x 4 in. and three 5 in. round speakers wired in series to match. 15 ohm impedance (handles 15 watts). £6.5.0. P. & P. 8/6 each.

THE IMP. Wedge shaped extension speaker cabinet is fitted with 7 x 4 in. speaker. Covered in walnut wood grain cloth with fawn Vynal front keyhole slot in back. 7 1/2 x 6 1/2 in. Only 25/6. P. & P. 4/6 each.



SPEAKERS: Elac Heavy duty Ceramic Magnets 11 000 line 10 in. round, 10 x 6 in. 3 ohm or 15 ohm, 48/6. P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13 1/2 x 8 in. 3 ohm, 45/-. 15 ohm 48/6. P. & P. 3/6. E.M.I. 3 in. tweeter 17/6. P. & P. 1/6. E.M.I. 13 1/2 x 8 in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6. P. & P. 4/6. E.M.I. 13 1/2 x 8 in. (15 ohm) Hi-Fi quality £5.19.6. P. & P. 4/6. E.M.I. Woofers, 6 1/2 x 6 1/2 in. square, 8 ohm, 50/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/-. EAGLE Crossover units 3 or 16 ohms, 16/-. P. & P. 1/-. Bakers 12 in., 25 watt 15 ohm £6.5.0. P. & P. 3/6.

THE CAXTON COLUMN. This is a column cabinet 23 1/2 x 5 1/2 x 5 1/2 in. deep fitted with three speakers. Handles 8 watts and will improve the quality of any tape recorder or record player. Finished in wood grain cloth with sandstone Vynal front it is a real bargain at 59/6. P. & P. 10/6 each.



THE TENNYSON. Wedge shape for table or wall mounting size 16 x 13 1/2 x 8 1/2 in. deep, finished in grey cloth with matching Vynal front. 12 in. Kelson speaker is fitted with built-in tweeter. £4.7.6. P. & P. 7/6 each.



THE SCOTT. The elegant tapered cabinet, for table or wall mounting measuring 10 1/2 x 16 x 5 1/2 in. deep, is attractively finished in black cloth with a striped grey Vynal front. Fitted with 13 1/2 x 8 in. speaker with volume control. Please state impedance required—3 or 15 ohm. £4.5.0. P. & P. 7/6 each. Fitted with two E.M.I. 13 x 8 in. speakers and tweeter. 15 ohm impedance capacity 10 watts 30/- extra.



TEAK PLINTH AND PERSPEX DUST COVER for SP26 etc. £5.5.0. P. & P. 3/6. **VYNAL** Widths from 40 to 54 in. 17/6 yd. off roll. P. & P. 1/6. 1 yard, 9/- P. & P. 1/6. Send 1/- stamps for samples.

SPEAKER MATCHING TRANSFORMERS 3, 7, 15 ohms, 8 watt, 11/6 P. & P. 1/6.

MICROPHONES: Xtal Hand Mike. B1201 with stand, 54/6. P. & P. 3/6. ACOB Mike 45, 21/-, ACOB Mike 40, 18/6. Dyn. Mike DM-391, 30/-, CM21 Xtal, 12/6. Telephone Pick-up, 10/6.

P. & P. 1/-. Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-. **FERRUX RODS:** 6 x 1/2 in., 2/6; 4 1/2 x 1/2 in., 2/-; 6 x 1/2 in., 2/6; 8 x 1/2 in., 3/-. P. & P. 1/6 each.

FERRUX RODS WITH COILS: 4 1/2 x 1/2 in., 3/6; 8 x 1/2 in., 5/6. P. & P. 1/6 each. **ROTARY SWITCHES:** 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/6.

TRANSISTOR SPEAKERS 8 ohm 2 in. 8/6. 3 in., 10/6. P. & P. 1/6.

CARTRIDGES
Stereo: Sonotone 9TA H/C Diamond 47/6. 9TA Sapphire, 37/6. 9TA Sapphire 30/-, Ronette 8105 Medium Output, 28/6. 8106 High Output 28/6. DC284 Stereo Compatible 22/6. Acos GP93/1 Sapphire, 37/6. GP94/1 Sapphire, 39/6. GP91 Diamond, 42/6. GP91 Stereo Compatible (High, Medium or Low Output), 25/6. TA800 converts Philips AG3301, AG3306 to B.S.R. 8X1H. Plug-in head complete with cartridge 50/-, TA700 equivalent to B.S.R. 8X1M

35/-, Japanese equivalent to B.S.R. TC8, 35/-

Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 16/-, B.S.R. TC8H Jav. equivalent, 26/-, Sonotone 2T88, 15/-, Post and Packing 1/6.

EARPIECES WITH COIL and 3-5 mm. plug. 8 ohm magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6, Xtal. P. & P. 6d.

PIANO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/-.

BROADWAY Electronics

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday) (Few minutes from Tooting Broadway Underground Station)

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 769-0199/1649

1A7	7/9	6BQ7A	7/-	6K7M	6/6	7Y4	8/6	20P5	20/-	80	7/6	DF96	7/6	ECF80	6/6	EM80	7/6	PC97	8/9	RG5/50080/-	UF89	7/6	
1D5	7/6	6BR7	17/-	6K7G	2/-	9BW6	7/-	25A6	5/9	85A2	7/3	DH77	4/9	ECF82	6/6	EM81	8/3	PC98A	8/6	R130	40/-	UL41	12/-
1H5	7/6	6BR8	12/6	6K7GT	4/6	10C1	12/6	25L6GT	7/-	150B2	11/6	DK32	7/9	ECF83	12/6	EM84	7/6	PC98B	10/6	SP4	8/-	UL42	7/-
1LD5	6/-	6BR7	25/-	6K8	3/9	10C2	12/6	25Y5	8/-	180C4	9/6	DK91	6/-	ECH21	11/6	ESU15080/-	8/6	PC989	10/6	SP41	5/6	UM90	5/6
1N6GT	8/-	6BW6	14/6	6K8M	11/6	10F1	14/9	25Z4	6/8	801	9/6	9K92	9/-	ECH42	11/-	EY91	7/6	PCF80	6/9	SP6	5/6	U16	21/-
1R5	6/6	6CW7	12/-	6K8G	8/-	10F3	8/-	25Z5	8/-	807	9/6	DK96	7/-	ECH51	5/6	EY88	7/-	PCF82	6/6	STV280	10/6	U17	21/-
1S4	5/6	6C4	5/-	6K8GT	7/-	10F9	10/6	25Z6	8/6	813UBA	12/6	DL96	25/-	ECH52	8/6	EZ35	6/-	PCF84	8/-	8U25	19/6	U18	21/-
1S5	4/6	6C5G	6/-	6K25	15/-	10F18	8/-	25D7	9/8			DL92	6/8	ECL80	5/9	EZ40	8/3	PCF86	9/6	8U25	19/6	U19	8/3
1T4	4/-	6C6	3/9	6L1	12/-	10L1	8/-	30C1	6/9	813	75/-	DL93	4/-	ECL82	7/-	EZ41	9/6	PCF80	9/6	8U25	19/6	U21	9/6
3A4	4/-	6C8G	6/-	6L6G	7/9	10LD11	10/6	30C15	15/-	866A	15/-	DL94	6/9	ECL83	10/8	EZ80	8/6	PCF802	9/6	T41	17/6	U41	5/6
3Q4	7/9	6C8DG	24/-	6L18	6/-	10L13	18/6	30C17	16/-	954	5/8	DL95	7/9	ECL86	9/-	EZ81	8/6	PCF805	15/-	TDD4	9/6	U45	8/6
3Q5	7/-	6CH6	7/6	6Q7G	6/-	11E3	7/9	30C18	15/-	1926	6/6	DL96	7/6	ECL800	10/-	GZ30	10/-	PCF801	13/-	U10	7/6	VP4B	25/-
3B4	6/8	6C4	5/-	6Q7GT	8/6	12A7	4/9	30F5	17/-	4022A	67/-	DM70	6/-	GZ32	10/-	GZ32	10/-	PCF803	15/6	U14	7/6	VP4B	25/-
3V4	6/9	6D6	3/9	6A7M	7/-	12A7T	7/-	30FL1	16/-	5763	12/-	DY88	6/-	EF9	20/-	GZ34	11/-	PCF804	15/6	U19	85/-	VR105	30/-
5R4GT	10/6	6E5	7/9	6BC7	7/-	12A7G	5/9	30FL12	19/-	7198	8/6	DY87	5/-	EF37A	7/-	KT36	18/-	PCF83	10/8	U25	15/6		6/6
5U4G	6/6	6F1	12/6	6BG7	6/-	12A7U	5/9	30FL14	15/6	7475	14/-	R88CC	12/-	EF39	8/-	KT61	17/6	PCF84	9/6	U28	15/6	VR150	30/-
5V4G	8/-	6F6G	8/-	6BH7	3/8	12A7T	6/3	30L15	17/-	A61	9/6	EAS0	3/6	EF41	10/-	KT66	21/-	PCF85	9/6	U78	4/6		
5Y3GT	6/-	6F24	14/-	6B5G	7/6	12B7G	6/-	30L17	17/-	ATP4	2/8	EAB30	6/6	EF50	5/-	KT81	35/-	PCF86	9/6	U191	13/6	VT25	15/-
5Z4G	7/-	6F11	6/6	6BL7GT	6/-	12C8GT	5/-	30P19	15/-	ATP7	8/6	EB41	10/-	EF80	4/8	KT81	7C5	PEN44	20/-	U261	16/8	VT31	30/-
6B0L2	15/-	6F13	6/6	6BN7GT	5/6	12E1	20/-	30P11	16/-	AU2	8/6	EB91	3/-	EF86	6/6	KT88	30/-	PEN45	7/-	U403	6/6	VU111	8/9
6A7	15/-	6F14	12/6	6BQ7	7/6	12J5GT	2/6	30P13	18/6	AU5	8/9	EB93	8/6	EF89	5/6	KTW61	8/6	PEN46	4/6	U404	7/6	VU120	12/6
6A8G	12/6	6F23	16/-	6U4GT	12/-	12J7GT	6/6	30P14	16/-	AZ1	3/-	EB94	9/9	EF91	2/9	KTZ41	6/-	PL38	10/9	U801	83/6	VC120	12/6
6AC7	4/-	6F24	14/-	6V6M	12/-	12K8GT	7/-	35A5	11/6	AZ31	10/-	EB90	4/9	EF92	2/9	ML4	17/6	FL81	8/-	UAB80	6/6	VCR97	85/-
6AK5	5/-	6F25	15/-	6V6M	12/-	12K8GT	7/-	35L6	9/-	CB131	16/-	EBF90	7/6	EF98	15/-	ML5	7/6	FL82	9/6	UAB81	6/6	VCR97	85/-
6AL5	3/-	6F28	14/-	6V6G	4/6	12Q7GT	6/-	35W4	4/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML6	7/6	FL83	9/6	UAB81	6/6	VCR97	85/-
6AM5	4/6	6F32	2/9	6V8GT	6/6	12S4T	6/-	35Z2	10/-	CB33	15/-	EBF89	6/6	EF98	15/-	ML7	7/6	FL84	9/6	UAB81	6/6	VCR97	85/-
6AM6	3/6	6G6	2/6	6X4	4/6	12S4T	6/-	35Z4	10/-	CB33	15/-	EBF89	6/6	EF98	15/-	ML8	7/6	FL85	9/6	UAB81	6/6	VCR97	85/-
6A95	8/6	6H6	3/-	6X6G	4/6	12S4T	6/-	35Z5	10/-	CB33	15/-	EBF89	6/6	EF98	15/-	ML9	7/6	FL86	9/6	UAB81	6/6	VCR97	85/-
6B5GT	10/6	6J5M	9/-	6X6GT	6/-	12S4T	6/-	35Z6	10/-	CB33	15/-	EBF89	6/6	EF98	15/-	ML10	7/6	FL87	9/6	UAB81	6/6	VCR97	85/-
6AT6	4/9	6J5G	5/6	7B6	11/6	12S4T	6/-	37	6/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML11	7/6	FL88	9/6	UAB81	6/6	VCR97	85/-
6AU6	5/-	6J5GT	5/6	7B7	7/6	12S4T	6/-	42	6/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML12	7/6	FL89	9/6	UAB81	6/6	VCR97	85/-
6B4G	20/-	6J6	8/6	7C5	22/6	14H7	9/6	50B5	6/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML13	7/6	FL90	9/6	UAB81	6/6	VCR97	85/-
6B8G	20/-	6J7M	8/6	7C6	15/-	19AQ5	5/-	50C5	6/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML14	7/6	FL91	9/6	UAB81	6/6	VCR97	85/-
6BA6	5/-	6J7G	6/-	7D6	8/-	20D1	10/-	50C6G	8/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML15	7/6	FL92	9/6	UAB81	6/6	VCR97	85/-
6B26	5/-	6J7GT	7/6	7E7	12/6	20F2	14/6	50L6GT	8/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML16	7/6	FL93	9/6	UAB81	6/6	VCR97	85/-
6B86	9/-	6K6GT	6/-	7E7	12/6	20L1	20/-	75	9/6	CB33	15/-	EBF89	6/6	EF98	15/-	ML17	7/6	FL94	9/6	UAB81	6/6	VCR97	85/-
6B36	9/-	6K7	1/9	7E7	45/-	20P4	20/-	78	5/-	CB33	15/-	EBF89	6/6	EF98	15/-	ML18	7/6	FL95	9/6	UAB81	6/6	VCR97	85/-


SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Express postage 9d. per valve.
Ordinary postage 6d. per valve. C.W.O. No C.O.D.
Complete range of T.V. Tubes available from £4.5.0.
Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service

SETS OF VALVES
DAF91, DF91, DK91, DL92 or DL94 ... 19/- plus postage
DAF96, DF96, DK96, DL96 ... 27/6 plus postage

TRANSISTORS
AC127 7/6 OC28 4/6 OC71 4/6 OC81 4/6 OC82D 6/6
AF114 7/6 OC28 16/6 OC72 6/6 OC81D 4/6 OC83 7/6
AF115 7/6 OC39 11/6 OC75 6/6 OC81DM OC170 7/6
AF116 7/6 OC44 4/6 OC76 6/6 OC82 6/6 OC171 8/6
AF117 7/6 OC45 4/6 OC77 8/6 OC82 6/6 OC200 7/6

SEND S.A.E. FOR LIST OF 2,000 TYPES

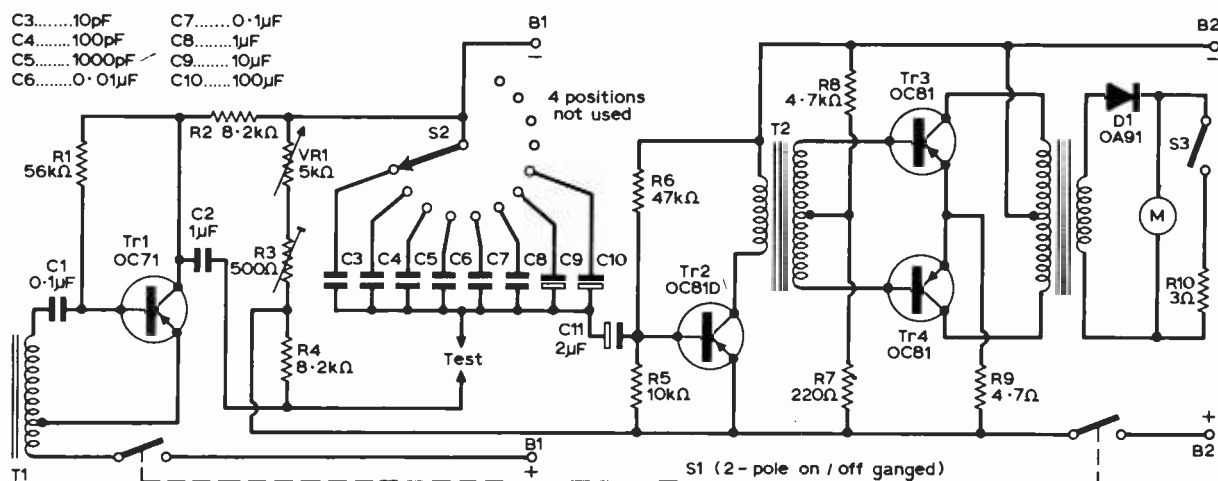

meter of 0.5mA (500mA) f.s.d. was used; constructional details are therefore given using this meter, but, if a commercial meter is preferred, the front panel cut-out can be modified accordingly (see Fig. 8).

loads imposed by the relatively large current on the higher ranges, the switch then being operated as the condition of balance is approached, to enable the dip to be detected more accurately. Since the on-off positions are not indicated, there is a natural tendency to return it to the "safe" position after use.

The bridge consists of variable resistor, VR1, which in association with the test capacitor, fixed resistors R3 and R4, and the switched bank C3-C10, constitute the balancing bridge circuit by means of which the null-point (dip) is obtained. A pointer knob and scale, graduated in capacitance from 1 to 10 are affixed to VR1. It was found originally that the readings of capacitance tended to be cramped to one end of the scale, and the pre-set resistor, R3, was therefore added in series with VR1. Although this does not completely prevent cramping, it does tend to distribute the readings more evenly over the entire scale. Once the optimum position for this pre-set has been determined, it can be waxed in position.

Consider three capacitors of the usual tolerance (5%) with a 10 times ratio in their values, e.g. 200, 2,000 and 20,000pF. On the $\times 100$ range, with the first of these connected in the test position, the bridge should of course, register a null indication at a point corresponding to 2 on the capacitance scale. Let us assume that we start with a blank scale and a reasonably accurate capacitor bank, then this point can be pencilled in as 2, which, unless we were particularly unlucky in the choice of this first capacitor ought to represent a reasonably correct marking. Now switch to the $\times 1$ range, and substitute the 2,000pF capacitor which should result in a minimum reading at the same point on the scale. If it does not,

★ components list

R1	56k Ω	R7	220 Ω
R2	8·2k Ω	R8	4·7k Ω
R3	500 Ω preset	R9	4·7 Ω
R4	8·2k Ω	R10	3 Ω
R5	10k Ω	VR1	5k Ω log. pot.
R6	47k Ω		

C1	0.1 μ F	C7	0.1 μ F
C2	1 μ F	C8	1 μ F
C3	10 pF	C9	10 μ F
C4	100 pF	C10	100 μ F
C5	1,000 pF	C11	2 μ F
C6	0.01 μ F		

TR1	OC71	TR4	OC81
TR2	OC81D	D1	OA91
TR3	OC81		

T1 Interval transformer
T2 Driver transformer
T3 Output transformer

B1, B2 PP3 or equiv.; M, Meter, 0-0.5mA; S1, two-pole on/off switch; S2, one-pole twelve-way wafer switch; S3, one-pole on/off switch.

vary C5 by substitution until the scale does register 2 at this point. Similarly, C6 on the $\times 10$ range, using the third capacitor for testing, can be adjusted to give the correct reading. This procedure is repeated for all ranges. The author was fortunate in having a fairly large stock of capacitors. For the constructor lacking this facility, the use of close tolerance capacitors in the fixed bank might prove a better, and possibly cheaper, solution.

On some of the ranges, it may not be possible to obtain a reading in both the 1 and 10 positions on the scale, but, with the large coverage of the instrument, this is unavoidable. If the reader wishes to make a more accurate bridge, and is willing to accept reduced test facilities, say, equivalent to the first six ranges from 10pF to 1 μ F, this can be achieved by using the full number of positions in the range switch (which, in the original design, is a 12-pole type, with four poles unused. See Fig. 6), and reduc-

Table I

Components	Value for full range coverage	Value for half coverage
C3-C10	10pF, 100pF etc.	10pF, 50pF, 100pF etc.
four additional capacitors	—	0.1 μ F, 0.5 μ F, 1 μ F, 5 μ F
VR1	5000 Ω pot.	2000 Ω pot.
R4	8.2k Ω	4.7k Ω

ing the capacitance coverage on each range by half. Suggested alterations to component values are given in Table 1.

TO BE CONTINUED

M.W. DX RECEIVER—continued

gain controls for r.f., i.f. and a.f. The a.g.c. may be switched in or out and a b.f.o. is also available at the

TABLE I

Connection and colour codes for the IFA/1.6/SSB Mk II i.f. strip.

Connection Number	Function	Colour code
1	Input	Brown
2	Input (Earth)	Plain
3	"S" Meter	Plain
4	"S" Meter	Red
5	"S" Meter	Black
6	B.F.O. control	Plain
7	B.F.O. control	Orange
8	B.F.O. control	Yellow
9	A.G.C. on/off	Green
10	A.G.C. on/off	Blue
11	A.G.C. on/off	Violet
12	A.F. output	Grey
13	A.F. output (earth)	Plain
14	Negative line—12V	Black
15	Positive line (earth)	Plain
16	B.F.O. on/off	White
17	B.F.O. on/off	Black
18	I.F. gain	Black
19	I.F. gain	Pink

NOTE: All numbers without colour, i.e., plain, are connected to earth. All numbers coloured black are connected to the negative line.

flick of a switch. The "s" meter may be zeroed and is useful for signal strength comparisons. The aerial circuitry is wired for a single wire feed, but by a simple modification can offer a balanced input. This will be useful for devices such as balanced loop aerials and the like.

Next month we will consider the construction of the receiver followed by the alignment procedure. A signal generator will be needed since the set must be aligned carefully because of the very narrow bandwidth of the i.f. strip.

TO BE CONTINUED

PRACTICAL TELEVISION in the OCTOBER issue

TRANSISTOR AND DIODE ANALYSER

Not just a tester—an analyser! This tester will not only carry out the normal diode and transistor tests, including a test of transition frequency to establish the frequency limitations of a device, it can also be used to determine all the information required for experimental purposes on a transistor that is unmarked and whose connections, type and purpose are unknown. You don't even have to know whether it is a pnp or npn, germanium or silicon device.

HEAT EFFECTS IN TV RECEIVERS

Heat is the cause of more trouble in a TV set than any other shortcoming. The faults attributable to excess heat are examined and the steps that can be taken to reduce heat described.

TOMORROW'S SETS

Next month we shall be looking at the effects on TV receiver design of the increased use of integrated circuits over the next few years. The problems of design, the setmakers, the retail trade and servicing will all be considered.

TRANSISTOR LINE OSCILLATORS

Basic waveform generating circuits described, including the flywheel sync techniques invariably used with modern line oscillator stages.

SERVICING TV RECEIVERS

The next chassis to be tackled is the STC VC11 chassis as used in the KB Featherlight portable and associated models.

PLUS ALL THE REGULAR FEATURES

on sale

September 19th

DE LUXE PLAYERS

PORTABLE CABINET As illustrated. To fit standard 75/- player or autochanger. **RCS AMPLIFIER 3 WATT.** Ready made and tested. This is a 2-stage unit using a triode pentode condenser coupled valve giving a 3 watt output into a 3 ohm loudspeaker. Tone and volume controls mounted on panel. Supplied with knobs, loudspeaker and valves UCL82, UY85. Frequency response 50-12,000 cps. Sensitivity 200mV. **59/6**

AUTOCHANGERS MONO
Balfour Princess £25.19.6
BSR Supralim UA25 £26.19.6
MA70 Transcrip £13.19.6
Garrard 3000 with Sonotone £12.19.6
ETA Diamond £12.19.6
All fitted LP78 stylus and pickup cartridge complete. Stereo/mono pickup 20/- extra except 3000.

GARRARD TEAKWOOD BASE WB.1. Ready cut out for mounting 1025, 3000, SP25, AT90, etc. **65/-**
GARRARD PERSECT COVER SPC.1 for WB.1 BASE. Durable tilted attractive appearance. **65/-**

E.M.I. PICK-UP ARM Complete with mono cartridge 29/6; Xial GP67 17/6; Stereo Ceramic 35/-; ACOS LP only 10/6.

CRYSTAL MIKE INSERTS

1 1/4 in. dia. 8/8; ACOS 1 1/4 in. dia. 9/8. RM3, 1 1/4 in. dia. 9/8. QUALITY RIBBON MIKE WITH GOOSENECK £11.11.0.

PORTABLE TRANSISTOR AMPLIFIER PLUS DYNAMIC MICROPHONE

A self-contained fully portable mini-p.a. system. Many uses - ideal for Parties, or as a Party Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4 in. with powerful 7 x 4 in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone. Uses PP3 battery. Brand new in makers' carton with full makers' guarantee. World famous make. **Only 90/- Post Free**



WEYRARD P50-TRANSISTOR COILS

RA2W 5in. Ferrite Aerial with ear aerial coil... 12/6
Oso. P50/LAC... 5/4
I.P. P50/200 400 k/s... 5/7
3rd I.P. P50/370... 6/-
Telescope Chrome Aerials 3in. extends to 23in. 5/-
Ferrite Rods Only 8 x 1/4 in. 4/-; 6 x 1/4 in. 5/-

VOLUME CONTROLS

80 Ohm Coax 8D yd.
BRITISH AERIALITE AERIAL AIR SPACED 40 yd. 20/-; 80 yd. 30/-
FRINGE LOSS LOSS 1/6 yd.
Ideal 625 lines

WIRE-WOUND TAPERS

Standard size pots. Values 10Ω to 30K. **4/6**
Carbon 30K to 2 meg. **4/6**

VEROBOARD 0.15 MATRIX

2 1/2 x 5in. 3/8 2 1/2 x 3 1/2 x 3 1/2 x 5in. 5/2.
EDGE CONNECTORS 16 way 5/-; 24 way 7/6.
PINS per packet 3/4. PACK CUTTERS 7/6.
S.R.B.P. Board 0.15 Matrix 2 1/2 in. wide 6d. per lin. 3 1/2 in. wide 9d. per lin. 5 1/2 in. wide 1 1/4 per lin. (up to 17 in.).
S.R.B.P. drilled 1/16 in. Board. 10 x 8in. 3/-.

BLANK ALUMINIUM CHASSIS 18 a.w.g. 2 1/2 in. sides 7 x 4 in. 6/8; 9 x 7 in. 6/8; 11 x 8 in. 6/8; 11 x 7 in. 7/8; 13 x 8 in. 9/8; 14 x 11 in. 12/8; 16 x 14 in. 15/-.

ALUMINIUM PANELS 18 a.w.g. 12 x 12 in. 6/8; 14 x 9 in. 5/6; 12 x 8 in. 4/6; 10 x 7 in. 3/6; 8 x 6 in. 2/6; 6 x 4 in. 1/6.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
1 in. 18/-; 1 1/4 in. 17/6 1 1/2 in. 19/6 1 3/4 in. 24/-; 2 1/4 in. 44/8
1 1/2 in. 19/6 1 3/4 in. 20/6 1 1/2 in. 29/-; 2 1/4 in. 57/8
1 1/2 in. 16/6 1 3/4 in. 19/6 1 1/2 in. 21/6 2 in. 29/-; 1 in. sq. 36/8

WAVE-CHANGE SWITCHES WITH LONG SPINDLES.

2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each.
1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/6 each.
Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 5 p. 2-way, 1 water 12/-, 3 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-.

TOGGLE SWITCHES.

sp. 2p; sp. dt. 3/8; dp. 3/8; dp. dt. 4/6.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive... 35/-
LOW RESISTANCE HEADPHONES 3-6 ohms... 39/6
DELUXE PADDED STEREO PHONES 8 ohms... 39/6

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

200/250 v. A.C. Leaflet S.A.E. **42/6**



BARGAIN STEREO/MONO SYSTEM

Attractive Slim PLAYER CABINET with B.S.R. STEREO Autochanger 4 + 4 AMPLIFIER and TWO matched 6in. LOUDSPEAKERS Carr. 10/6 (Only 4 pairs of wires to join). **£19.19.6.**

NEW TUBULAR ELECTROLYTICS

2 1/2	3	4	5	6	8	10	15	20	30	50	100	200	500	1000	2000	5000	10000
2/350V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3
4/350V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
8/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
16/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
32/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
64/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
128/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
256/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
512/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	
1024/450V	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	2/3	

SUB MIN. ELECTROLYTICS

1, 2, 3, 4, 5, 8, 15, 25, 30, 50, 100, 250mF 15V 10/-; 500, 1000mF 15V 3/6; 2000mF 25V 7/-.

CERAMIC. 500V 1pF to 0.01mF, 9d.

PAPER. 350V-0.1 9d; 0.5 2/8; 1mF 3/-; 2mF 150V 3/-; 500V-0.001 to 0.05 9d; 0.1 1/-; 0.25 1/8; 0.5 3/-; 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 0.2, 1/8.

SILVER MICA. Close tolerance 1%, 5-500pF 1/-; 560-2,200pF 1/-; 2.700-5,500pF 3/8; 6,800pF 1/-, mid 6/8 each.

TWIN GANG. "0-0" 20pF + 170pF 10/6; 36pF, miniature 10/-; 500pF potentiometer with trimmers 12/6; 500pF midge less trimmers 7/6; 500pF slow motion, standard 9/-; small 3-gang 500pF 19/6. Single "0" 38pF 7/6.

SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF, 150pF 200pF 10/6 each.

TUNING. Solid dielectric. 100pF, 500pF, 500pF, 7/- each.


TRIMMERS. Compression ceramic 30, 50, 70pF 1/-; 100pF, 150pF, 250pF, 1/6; 600pF, 750pF, 1000pF, 2/6.

RECTIFIERS. CONTACT COOLED 1 wave 60mA 7/8; 85mA 9/8; 2Y100 10/-; Full Wave Bridge 75mA 10/-; 150mA 19/6; TV rect. 10/-.

NEON PANEL INDICATORS. 250v. AC/DC, 3/6.

RESISTORS. Preferred values, 10 ohms to 10 meg. 1w, 1/4 w, 1/2 w, 2W, 5W, 10W, 15W, 20W, 25W, 30W, 35W, 40W, 45W, 50W, 55W, 60W, 65W, 70W, 75W, 80W, 85W, 90W, 95W, 100W, 110W, 120W, 130W, 140W, 150W, 160W, 170W, 180W, 190W, 200W, 220W, 240W, 260W, 280W, 300W, 330W, 360W, 390W, 430W, 470W, 510W, 560W, 620W, 680W, 750W, 820W, 910W, 1000W, 1100W, 1200W, 1300W, 1400W, 1500W, 1600W, 1700W, 1800W, 1900W, 2000W, 2200W, 2400W, 2600W, 2800W, 3000W, 3300W, 3600W, 3900W, 4300W, 4700W, 5100W, 5600W, 6200W, 6800W, 7500W, 8200W, 9100W, 10000W, 11000W, 12000W, 13000W, 14000W, 15000W, 16000W, 17000W, 18000W, 19000W, 20000W, 22000W, 24000W, 26000W, 28000W, 30000W, 33000W, 36000W, 39000W, 43000W, 47000W, 51000W, 56000W, 62000W, 68000W, 75000W, 82000W, 91000W, 100000W, 110000W, 120000W, 130000W, 140000W, 150000W, 160000W, 170000W, 180000W, 190000W, 200000W, 220000W, 240000W, 260000W, 280000W, 300000W, 330000W, 360000W, 390000W, 430000W, 470000W, 510000W, 560000W, 620000W, 680000W, 750000W, 820000W, 910000W, 1000000W, 1100000W, 1200000W, 1300000W, 1400000W, 1500000W, 1600000W, 1700000W, 1800000W, 1900000W, 2000000W, 2200000W, 2400000W, 2600000W, 2800000W, 3000000W, 3300000W, 3600000W, 3900000W, 4300000W, 4700000W, 5100000W, 5600000W, 6200000W, 6800000W, 7500000W, 8200000W, 9100000W, 10000000W, 11000000W, 12000000W, 13000000W, 14000000W, 15000000W, 16000000W, 17000000W, 18000000W, 19000000W, 20000000W, 22000000W, 24000000W, 26000000W, 28000000W, 30000000W, 33000000W, 36000000W, 39000000W, 43000000W, 47000000W, 51000000W, 56000000W, 62000000W, 68000000W, 75000000W, 82000000W, 91000000W, 100000000W, 110000000W, 120000000W, 130000000W, 140000000W, 150000000W, 160000000W, 170000000W, 180000000W, 190000000W, 200000000W, 220000000W, 240000000W, 260000000W, 280000000W, 300000000W, 330000000W, 360000000W, 390000000W, 430000000W, 470000000W, 510000000W, 560000000W, 620000000W, 680000000W, 750000000W, 820000000W, 910000000W, 1000000000W, 1100000000W, 1200000000W, 1300000000W, 1400000000W, 1500000000W, 1600000000W, 1700000000W, 1800000000W, 1900000000W, 2000000000W, 2200000000W, 2400000000W, 2600000000W, 2800000000W, 3000000000W, 3300000000W, 3600000000W, 3900000000W, 4300000000W, 4700000000W, 5100000000W, 5600000000W, 6200000000W, 6800000000W, 7500000000W, 8200000000W, 9100000000W, 10000000000W, 11000000000W, 12000000000W, 13000000000W, 14000000000W, 15000000000W, 16000000000W, 17000000000W, 18000000000W, 19000000000W, 20000000000W, 22000000000W, 24000000000W, 26000000000W, 28000000000W, 30000000000W, 33000000000W, 36000000000W, 39000000000W, 43000000000W, 47000000000W, 51000000000W, 56000000000W, 62000000000W, 68000000000W, 75000000000W, 82000000000W, 91000000000W, 100000000000W, 110000000000W, 120000000000W, 130000000000W, 140000000000W, 150000000000W, 160000000000W, 170000000000W, 180000000000W, 190000000000W, 200000000000W, 220000000000W, 240000000000W, 260000000000W, 280000000000W, 300000000000W, 330000000000W, 360000000000W, 390000000000W, 430000000000W, 470000000000W, 510000000000W, 560000000000W, 620000000000W, 680000000000W, 750000000000W, 820000000000W, 910000000000W, 1000000000000W, 1100000000000W, 1200000000000W, 1300000000000W, 1400000000000W, 1500000000000W, 1600000000000W, 1700000000000W, 1800000000000W, 1900000000000W, 2000000000000W, 2200000000000W, 2400000000000W, 2600000000000W, 2800000000000W, 3000000000000W, 3300000000000W, 3600000000000W, 3900000000000W, 4300000000000W, 4700000000000W, 5100000000000W, 5600000000000W, 6200000000000W, 6800000000000W, 7500000000000W, 8200000000000W, 9100000000000W, 10000000000000W, 11000000000000W, 12000000000000W, 13000000000000W, 14000000000000W, 15000000000000W, 16000000000000W, 17000000000000W, 18000000000000W, 19000000000000W, 20000000000000W, 22000000000000W, 24000000000000W, 26000000000000W, 28000000000000W, 30000000000000W, 33000000000000W, 36000000000000W, 39000000000000W, 43000000000000W, 47000000000000W, 51000000000000W, 56000000000000W, 62000000000000W, 68000000000000W, 75000000000000W, 82000000000000W, 91000000000000W, 100000000000000W, 110000000000000W, 120000000000000W, 130000000000000W, 140000000000000W, 150000000000000W, 160000000000000W, 170000000000000W, 180000000000000W, 190000000000000W, 200000000000000W, 220000000000000W, 240000000000000W, 260000000000000W, 280000000000000W, 300000000000000W, 330000000000000W, 360000000000000W, 390000000000000W, 430000000000000W, 470000000000000W, 510000000000000W, 560000000000000W, 620000000000000W, 680000000000000W, 750000000000000W, 820000000000000W, 910000000000000W, 1000000000000000W, 1100000000000000W, 1200000000000000W, 1300000000000000W, 1400000000000000W, 1500000000000000W, 1600000000000000W, 1700000000000000W, 1800000000000000W, 1900000000000000W, 2000000000000000W, 2200000000000000W, 2400000000000000W, 2600000000000000W, 2800000000000000W, 3000000000000000W, 3300000000000000W, 3600000000000000W, 3900000000000000W, 4300000000000000W, 4700000000000000W, 5100000000000000W, 5600000000000000W, 6200000000000000W, 6800000000000000W, 7500000000000000W, 8200000000000000W, 9100000000000000W, 10000000000000000W, 11000000000000000W, 12000000000000000W, 13000000000000000W, 14000000000000000W, 15000000000000000W, 16000000000000000W, 17000000000000000W, 18000000000000000W, 19000000000000000W, 20000000000000000W, 22000000000000000W, 24000000000000000W, 26000000000000000W, 28000000000000000W, 30000000000000000W, 33000000000000000W, 36000000000000000W, 39000000000000000W, 43000000000000000W, 47000000000000000W, 51000000000000000W, 56000000000000000W, 62000000000000000W, 68000000000000000W, 75000000000000000W, 82000000000000000W, 91000000000000000W, 100000000000000000W, 110000000000000000W, 120000000000000000W, 130000000000000000W, 140000000000000000W, 150000000000000000W, 160000000000000000W, 170000000000000000W, 180000000000000000W, 190000000000000000W, 200000000000000000W, 220000000000000000W, 240000000000000000W, 260000000000000000W, 280000000000000000W, 300000000000000000W, 330000000000000000W, 360000000000000000W, 390000000000000000W, 430000000000000000W, 470000000000000000W, 510000000000000000W, 560000000000000000W, 620000000000000000W, 680000000000000000W, 750000000000000000W, 820000000000000000W, 910000000000000000W, 1000000000000000000W, 1100000000000000000W, 1200000000000000000W, 1300000000000000000W, 1400000000000000000W, 1500000000000000000W, 1600000000000000000W, 1700000000000000000W, 1800000000000000000W, 1900000000000000000W, 2000000000000000000W, 2200000000000000000W, 2400000000000000000W, 2600000000000000000W, 2800000000000000000W, 3000000000000000000W, 3300000000000000000W, 3600000000000000000W, 3900000000000000000W, 4300000000000000000W, 4700000000000000000W, 5100000000000000000W, 5600000000000000000W, 6200000000000000000W, 6800000000000000000W, 7500000000000000000W, 8200000000000000000W, 9100000000000000000W, 10000000000000000000W, 11000000000000000000W, 12000000000000000000W, 13000000000000000000W, 14000000000000000000W, 15000000000000000000W, 16000000000000000000W, 17000000000000000000W, 18000000000000000000W, 19000000000000000000W, 20000000000000000000W, 22000000000000000000W, 24000000000000000000W, 26000000000000000000W, 28000000000000000000W, 30000000000000000000W, 33000000000000000000W, 36000000000000000000W, 39000000000000000000W, 43000000000

BUILD AND ENJOY THE PW DOUBLE 12

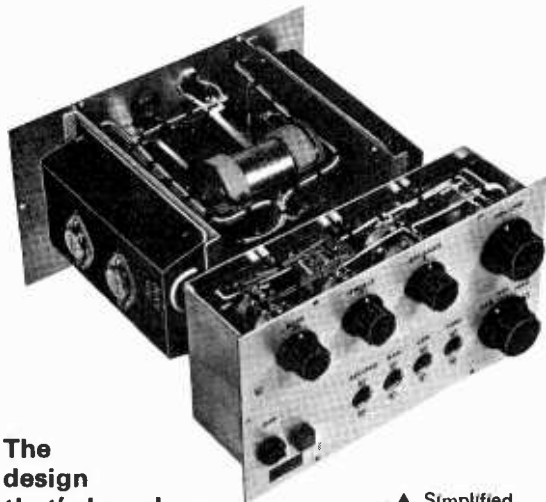

The design that's based on PEAK SOUND "Cir-Kit"

- ▲ Simplified Unit Construction
- ▲ Fantastic Performance

This 12+12 watt integrated stereo hi-fi amplifier and pre-amp is proving one of the most successful P.W. designs ever. With good ancillary equipment, you will find it one of the best you have ever heard, and it is a delight to build and handle. Basically, the design of the "P.W. Double 12" as described in P.W. April, May and June demonstrates the value of using "Cir-Kit". However, Peak Sound have contributed more besides to the success of this project. This includes the power amplifiers, the power pack and the ingenious cabinet which almost assembles itself. Go right ahead and build this exciting new design now with authentic, exact-to-specification Peak Sound kits as recommended by the designers.

This is your PW Double 12 Shopping List

These are the Peak Sound units with which you can build this excellent design. Transistors included.

- 2 Spools of "Cir-Kit" at 2/- each 4 0
- 2 Pre-amp and tone control kits 4 13 0
- 4 Pre-amp matrix boards 7 0
- 2 PA.12-15 Power Amplifier Kits 7 19 0
- 2 Heat Sink assemblies 12 0

- 2 P.A. matrix boards 8 0
- 1 PS.45K 45 volt power supply kit 4 10 0
- 1 Pack-flat afrormosia teak finished Cabinet kit 2 12 6
- 5 Controls as specified 2 0 0

TOTAL COST £23 5 6

- Hardware Kit of knobs, plugs, sockets, switches, fuses, screws, wire, etc. £2 10 0
- Metalwork cut, shaped and punched. £2 12 6

P.W. Double 12 abridged specification

Controls—Bass and treble cut and lift based on Baxandall circuitry/Volume/Balance/Rotary selector.
Input Sensitivity—Magnetic P.U. (per channel) 2.5mV into 68k Ω . Ceramic P.U.—25mV into 27k Ω , equalised for flat response. Radio/Aux. 60mV. HIGH OVERLOAD FACTOR ON ALL INPUTS.
Frequency Response—20Hz to 30kHz $\pm$ 1dB overall.
Output—12 watts per channel into 15 Ω (8 Ω speakers may be used).
Negative Feedback—43dB over each section.
Cabinet—Afrormosia teak finish, pack-flat, easy to build kit. Size 9 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in. high x 9 $\frac{1}{2}$ in. deep.
Transistors—Ultra low noise in pre-amp and tone control stages.

GO TO YOUR DEALER NOW

for your authentic Peak Sound Kits. In case of difficulty, please send direct, giving the name and address of your usual supplier where possible and add 11/- postage for complete assembly, or 5/6 if without power pack.

TRADE ENQUIRIES INVITED

PEAK SOUND (HARROW) LTD

32 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM
Egham 5316 SURREY.

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new
TECHNATRON Outfit! No mathematics.
No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the fast, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new TECHNATRON Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—**"ENGINEERING OPPORTUNITIES"**—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court,
Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B, ALDERMASTON COURT,
ALDERMASTON, BERKS.

I would like to know more about your
Practical Radio & Electronics Course. Please
send me full details and FREE 164-page book.

name.....

address.....

.....age.....

POST
THIS
COUPON
NOW!

A VERSATILE INTERCOM SYSTEM

PART 3

Two units on two-wire extension

It was found useful at a later stage to add a second extension to the two-wire extension so that incoming calls could be received by either extension and similarly outgoing calls could be made to the parent by either.

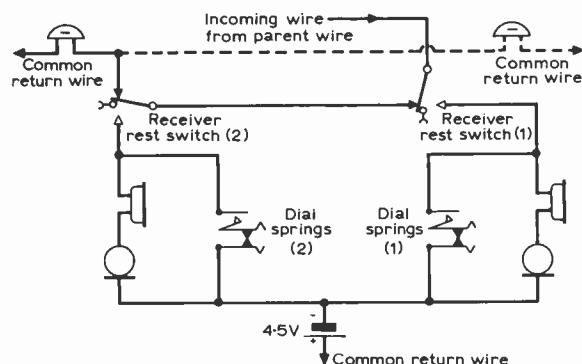


Fig 10: Two extensions having access to two-wire line to parent

Note that calls cannot be made from one extension to the other, since lifting the receiver of either extension cuts out the other. The circuitry is simple and involves the use of two GPO type dial phones. Only the dial springs and receiver rest switch are needed so the remainder of the equipment may be removed, the battery may be housed in either unit. If the units are in close proximity, only one bell will be required but an extra one may be added as shown if required.

Auto-extension

It was found convenient for an extension to call another unit without access to the parent unit. The block diagram in Fig. 11 clarifies this point.

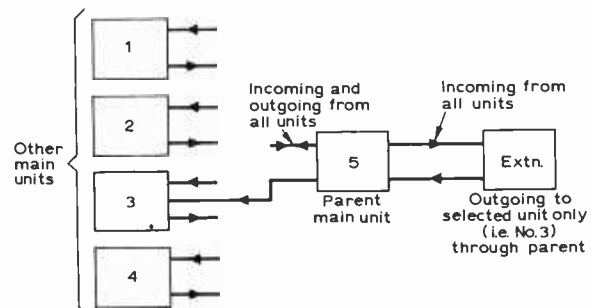


Fig. 11: Block diagram showing connection of auto-extension.

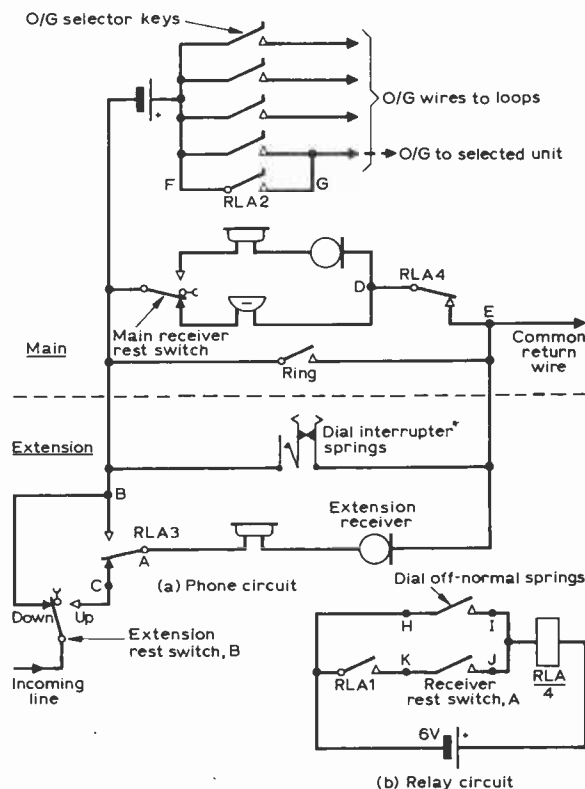


Fig. 12: Circuit diagram of auto-extension.

The extension is wired to the parent in such a way that dialling out from the extension causes the call to route to the prewired main unit. The facility is useful, for example, when the main unit is on a desk with the extension by the bed. The extension is a GPO dial phone, the circuit is shown in Fig. 12.

The relay, RLA, is operated from a 6V dry battery which, with moderate use, should last six months or more.

Lifting the receiver has no effect on the circuit at the moment. As soon as the dial is moved off normal, the contacts complete the circuit for RLA to the battery. RLA1 operates and latches the relay through the receiver rest switch A. RLA2 switches the outgoing line selector to the main unit being called (prewired) RLA4 operates to cut out the main unit

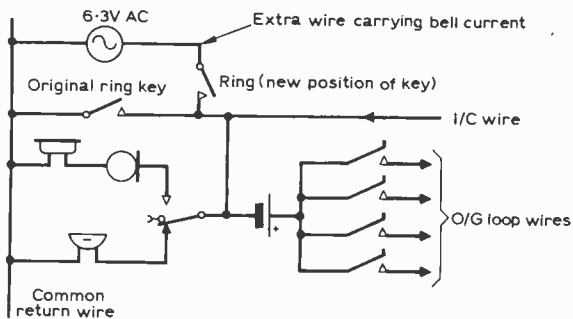


Fig. 13: Modification of circuit for a.c. ringing.

and a path is set up for the receiver through RLA3. When the dial is released, after dialling 0, ten pulses are sent along the outgoing loop wire to operate the buzzer at the distant end. Conversation may proceed on lifting the receiver of the called unit. At the termination of the call the relay, RLA, is de-operated by the receiver rest switch A when the receiver is replaced and all the contacts restore to normal.

If a large intercom is to be constructed for an office or small works, the reader may be interested in using a transformer to supply ringing current instead of relying on the 4.5V battery on which there is quite a considerable current drain during ringing. The part of the circuit to be modified is shown in Fig. 13. One side of the transformer (6.3V sec) is permanently connected to the common return wire and an extra wire carrying the ringing current is run with the loop wire.

PRACTICAL WIRELESS QUERY SERVICE

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

- (a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.
- (b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.
- (c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.
- (d) We regret we are unable to answer technical queries over the telephone.
- (e) It helps us if queries are clear and concise.
- (f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 10th October, 1969 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, OCTOBER 1969

Published approximately on the 7th of each month by IPC Magazines Limited, Tower House, Southampton Street, London, W.C.2. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia, Malawi and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 2s 0d.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

YOUR QUESTIONS ANSWERED

Altering Charging Rate

I have a battery charger that charges at 2 amps (12 volts). I also have a radio set (ex-army) that requires 12 volts plus 14V for the wobblulator network.

The battery I have six 2 volt batteries wired up together in series to give 12 volts. On the side of these batteries it has printed "...charge at 1 amp".

Is it possible to alter the charge from my battery charger from 2 amps to 1 amp?—H. Waite (Staffs).

In order to reduce the charging current of your battery charger, it will be necessary to add a resistor in series with one of the leads between the charger and the battery. The resistor will have a value of a few ohms only, but will need to be rated at a suitable wattage. The procedure is to connect an ammeter in the circuit and gradually reduce the value of the resistor until the charging current is 1 amp.

A.M., F.M. and S.S.B.

When one uses an a.m. transmitter, the books state that one transmits the r.f. carrier and also the sidebands. With an f.m. transmitter the frequency varies with the a.f. but I do not understand this with a.m.

If you could explain these things to me, I would be extremely enlightened about many radio topics, i.e., s.s.b.—H. Mason (Bolton).

It is really beyond the scope of a letter, and our query service, to examine a.m./f.m. transmission in detail, however, we hope the following will help regarding s.s.b.

Suppose the transmitter is operating on a frequency of 1,000kHz. Suppose also that the signal is modulated with an audio signal of 1kHz, say, a sine wave. It can be shown that there are now three frequencies involved apart from the 1kHz tone. These frequencies are: the 1,000kHz carrier, and two sidebands at 999kHz and 1,001kHz. The point to remember is that the carrier frequency of 1,000kHz is unaltered and this is the reason why, in single sideband (s.s.b.), it can be left out, although it must be reinserted at the receiver so that the information contained in the sidebands can be extracted. Again, since reception of either sideband will give exactly the same information, then one of the sidebands can be eliminated also which is what happens in s.s.b., both carrier and one sideband are removed.

CORRIGENDA

TAKE 20 No. 5 Transistor Tester Plus. Julian Anderson.

The author has drawn our attention to an error in the text of this article. R1 and R2 are referred to in the text as 330Ω; this should have read 330kΩ as in the circuit.

INCREASE YOUR KNOWLEDGE



MANY COURSES TO CHOOSE FROM incl.
RADIO & TV ENGINEERING & SERVICING,
TRANSISTOR & PRINTED CIRCUIT SERVICING,
CLOSED CIRCUIT TV, ELECTRONICS,
NUMERICAL CONTROL ELECTRONICS,
TELEMETRY TECHNIQUES, SERVOMECHANISMS
PRINCIPLES OF AUTOMATION,
COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

C. & G. Telecommunication Technicians' Certs
C. & G. Electronic Servicing
R.T.E.B. Radio/TV Servicing Certificate
P.M.G. Certificates in Radiotelegraphy
Radio Amateurs' Examination
General Certificate of Education, etc

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 170, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
10/69

NOW FREELY AVAILABLE

**SINCLAIR
IC-10**



the world's most advanced high-fidelity amplifier

This remarkable amplifier has been in production for some months, and now that we have caught up with the backlog of orders, we can supply the IC-10 promptly. We wish to apologise for the delay in reaching full production, which was due to circumstances beyond our control. We hope that now you can purchase the IC-10 without difficulty, you will enjoy to the full the great possibilities this unique Sinclair device offers.

The Sinclair IC-10 is the World's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, which has an output power of 10 Watts, is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick. This tiny chip contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, all of which are formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins.

Monolithic I.C.'s. were originally developed for use in computer and space applications where their extraordinary toughness and reliability were even more important than their minute size. These same advantages make them ideal for linear applications such as audio amplifiers, but hitherto they have been confined to low power applications. The IC-10 thus represents a very exciting advance. Not only is it far more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most

important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, the IC-10 is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc.

The photographic masks required for producing monolithic I.C.'s. are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. So we are able to sell the IC-10 at a price far below that of the components for a conventional amplifier of comparable power. At the same time, we give a 5 year unconditional guarantee on each IC-10 knowing that every unit will work as perfectly as the original and do so for a lifetime.

sinclair


SINCLAIR RADIONICS LIMITED, 22 NEWMARKET ROAD, CAMBRIDGE.

Telephone 0223 52996

10 WATT MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER


■ Specifications

Power Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm$ 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5 mV.
Input impedance	Adjustable externally up to 2.5 M ohms for above sensitivity.

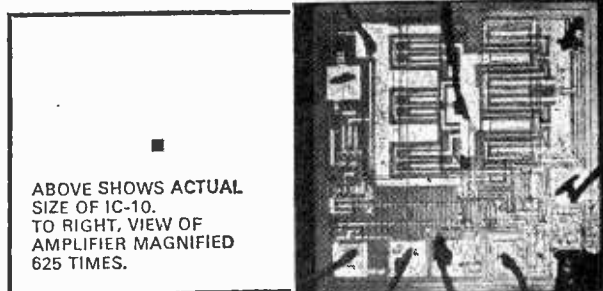

■ Circuit Description

The circuit diagram of the IC-10 is shown on the right. The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. The output stage operates in class AB with closely controlled quiescent current which is independent of temperature. A high level of overall negative feedback is used round both sections and the amplifier is completely free from cross-over distortion at all supply voltages. Thus battery operation is eminently satisfactory.

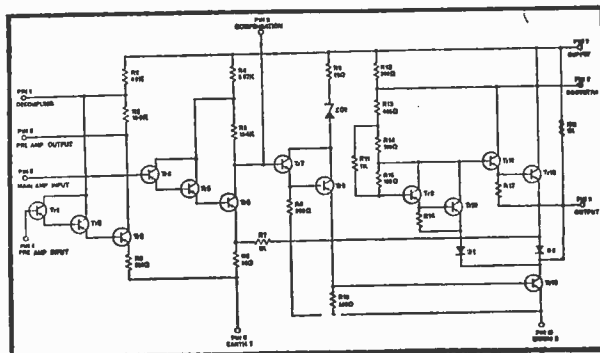

■ Construction

The monolithic I.C. chip is bonded onto a gold plated area on the heat sink bar which runs through the package. Wires are then welded between the I.C. and the tops of the pins which are also gold plated in this region. Finally the complete assembly is encapsulated in solid plastic which completely protects the circuit. The final device is so rugged that it can be dropped thirty feet on to concrete without any effect on performance. The circuit will also work perfectly at all temperatures from well below zero to above the boiling point of water.

■ Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity uses. These include public address, loud-hailers, use in cars, inter-com., stabilised power supplies, electronic organs, oscillators, volt meters, tape recorders, solar cell amplifier, radio receivers.

The transistors in the IC-10 have cut off frequencies greater than 500 MHz so the pre-amp section can be used as an R.F. or I.F. amplifier making it possible to build complete radio receivers without any additional transistors.



SINCLAIR IC-10

The complete IC-10 with the manual and 5 year guarantee costs just

59%


Post free

SINCLAIR RADIONICS LIMITED,
22 NEWMARKET ROAD, CAMBRIDGE
Telephone 0223 52996

**ORDER FORM AND MORE SINCLAIR
DESIGNS OVERLEAF**

SINCLAIR Z.12

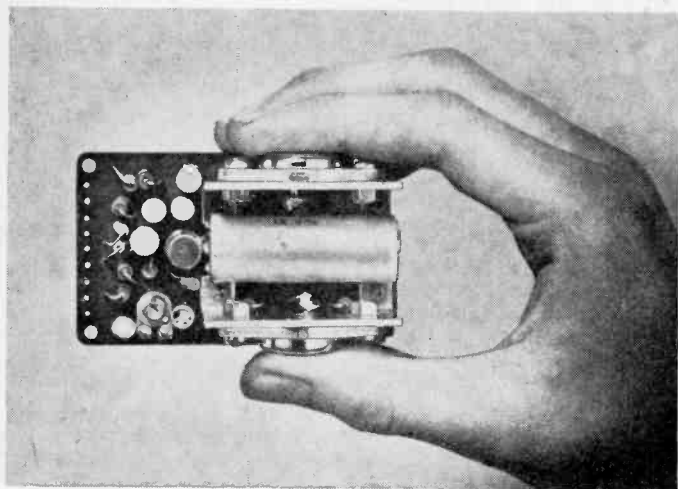12 WATT INTEGRATED HI-FI AMPLIFIER & PRE AMP



12 watts R.M.S. continuous sine wave output

This is the recommended amplifier for those requiring greater power than that provided by the IC.10. This eight transistor amplifier is the most successful of its kind ever designed. It has an excellent power to size ratio and is easily adapted to a wide variety of applications. The Z.12 performs satisfactorily from a wide range of voltages and it can easily be run from car batteries. This true 12 watt amplifier comes to you ready built, tested and guaranteed together with useful manual of circuits and instructions for matching the Z.12 to your precise requirements. Two may be used for stereo, when the Sinclair Stereo 25 will be found the ideal control unit for use with it.

Size—3in x 1½in x 1½in Class B Ultralinear Output: Frequency response from 15 to 15,000Hz ± 1 dB: Output suitable for loudspeakers from 3 to 15 ohms impedance Two 3 ohm speakers may be used in parallel: Input 2mV into 2K ohms: Output 12 watts R.M.S. continuous sine wave (24 watts peak); 15 watts music power (30 watts peak) Power requirements 6—20V d.c. from battery or PZ.4 Mains Supply Unit. Ready built, tested and guaranteed.


89/6



SINCLAIR STEREO 25

De Luxe Pre-amp and Control Unit to use with Z.12 Stereo assemblies. Switched input for PU (equalized to R.I.A.A. curve from 50 to 20,000Hz ± 1 dB), Radio and auxiliary. Supplied ready built with very attractive solid brushed and polished aluminium front panel. Control knobs for Bass/Treble/Volume/Balance/Input are solid aluminium. Size—6½ x 2½ x 2½in. plus knobs. Built, tested and guaranteed.

£9.19.6

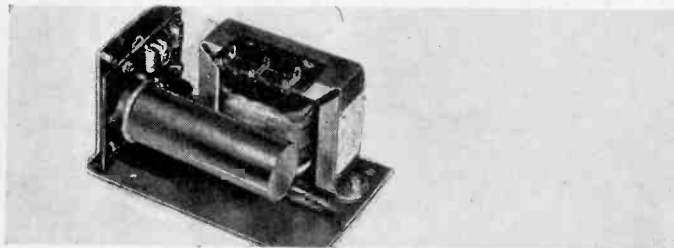

SINCLAIR PZ4

STABILISED MAINS POWER SUPPLY UNIT

Heavy duty transistorised power supply unit to deliver 18V d.c. at 1.5A. Designed specially for use with two Z.12 or IC.10 Amplifiers together with Stereo 25. Built, tested and guaranteed.

99/6

sinclair

SINCLAIR RADIONICS LIMITED, 22 NEWMARKET ROAD, CAMBRIDGE.

Telephone 0223 52996

SINCLAIR MICROMATIC

Britain's smallest radio




This fantastic little British pocket receiver is available in kit form to build for yourself or ready built, tested and guaranteed. Its range and selectivity must be experienced to be believed; its power and quality everything you could want. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact, you will find your Micromatic performing where other sets cannot be heard at all. The neat black case with aluminium front panel and tuning control give the Micromatic elegantly modern appearance.

- High quality magnetic earpiece
- Choice of many stations
- Plays anywhere

Kit with ear-piece, solder and instructions. **49/6**
+ 11d P.T. Surcharge

Built, tested and guaranteed. **59/6**
+ 11d P.T. Surcharge

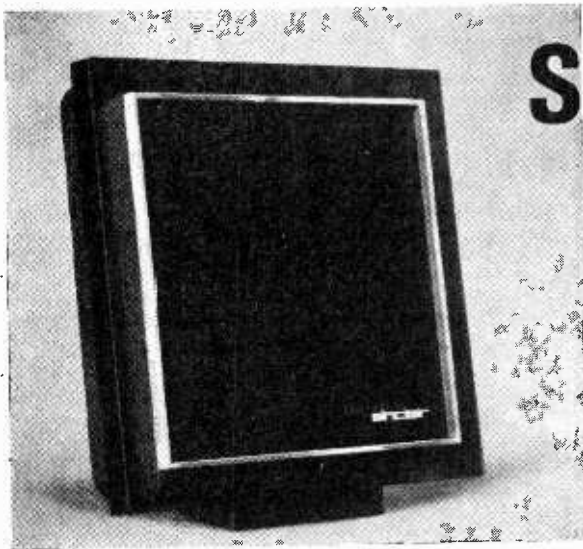Mallory Mercury Cells RM.675 (2 reqrd.) each 2/9.



SINCLAIR Q.14

the most challenging loudspeaker design in years

It is more than a matter of saving money when you choose the Q.14. This is the loudspeaker that delights experts and critics alike for its fine forward quality, its clarity and exceptional adaptability. Designed on original lines and from unusual materials, the Q.14 will easily carry up to 14 watts and has very smooth response from 60 to 16,000Hz. Size—9½in square x 4½in deep, with matt black finish and solid aluminium bar embellishment. Input impedance—8 ohms.

The Q.14 costs about a quarter of what you might expect to pay for a good stereo speaker system. A pair used with two Z.12s and the Stereo 25 will give you superb high fidelity to stand comparison with far costlier equipment.

Try the Q.14 in your own home without delay. If it does not delight you, send it back and your money including cost of postage will be refunded in full.

£7.19.6

+ 2/11 P.T. Surcharge

THE SINCLAIR Q.14 LOUDSPEAKER has a seamless sealed acoustic pressure chamber contoured to ensure forward sounding presence and wide dispersal of sound. The driver unit employs a massive ceramic magnet special cone suspension and aluminium speech coil resulting in brilliant transient response. The input impedance of 8 ohms makes the Q.14 particularly suitable for use with transistor amplifiers. It can be used as a bookshelf speaker, a corner reflect or flush mounted on any appropriate flat surface, etc.

GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. Full service facilities available to all purchasers.

ORDER FORM BRINGS PROMPT DELIVERY SENT TO YOU POST PAID

To: SINCLAIR RADIONICS LIMITED, 22 NEWMARKET ROAD, CAMBRIDGE.

Please send

NAME.....

ADDRESS.....

For which I enclose cash/cheque/money order.

PW 1069

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD,
CAMBRIDGE 0223 52996

ELECTROVALUE

**RAPID
MAIL ORDER
SERVICE**

**EVERYTHING BRAND NEW AND TO EXACT
SPECIFICATION • NO SURPLUS GOODS**

AMPLIFIER KITS

PEAK SOUND P.W. DOUBLE 12

Complete stereo kit including cabinet, but less panel and other metalwork. £23 net. Available in separate packages as follows: Main amplifier kit £3.19.6 per channel, net. Accessories 19/- mono, 36/- stereo.

Pre-amplifier kit £1.7.0 per channel, net. Accessories 13/6 mono, 27/3 stereo.

Tone control kit 19/- per channel, net. Accessories 8/9 mono, 22/6 stereo.

Power supply kit £4.10.0 mono or stereo, net.

Cabinet kit £2.12.6 net. Metalwork available separately from other sources, details on request.

30 WATT (designed by Dr. A. R. Bailey). Published May 1968 W.W., modified November 1968 W.W.

Full kit for main amplifier £9.9.6 (less power supply). Transistors only for main amplifier £7.9.6. PC board supplied free with above kit. Heat sinks for output transistors 8/6 extra.

Power supply kit, unregulated, November 1969 circuit £4.14.0. Regulated version, 60V 1.6A or 0.8A, current limiting, re-entrant characteristic: does not need re-set button £8.10.0. Transformer only: 0-25-45-50V 2A 58/-.

8 x 8 watt Stereo only. Peak Sound SA 8 x 8 kit. Sensitivity 50mV into 1MΩ, output into 5Ω. Complete with cabinet and power supply. Kit complete £16.10.0 net. Built and tested £21 net.

BARGAINS IN BRAND NEW ELECTRONIC COMPONENTS

Ultra low-noise resistors (under 0.1μV/V) Electrofil TR5: Metal oxide, 2% tolerance, range 10Ω to 1MΩ. All values in E24 series available. 1/4W rating. 1-24 10d. each; 25-99 9d. each; 100 up 8d. each. (Ohmic values may be mixed to obtain quantity price.)

Potentiometers, carbon track, long plastic spindles: Single gang linear 220Ω to 2.2MΩ 2/6 each; log 4-7KΩ to 2.2MΩ 2/6 each. Dual gang stereo-matched lin or log 10K to 1MΩ 8/6 each. Stereo balance log/anti-log 10K, 47K, 1MΩ only, 8/6 each. All types available with 1/2A D.P. switch 2/3 extra.

TRANSISTORS, etc.

2N696	5/6	2N3704	3/9	BC107	3/6	BFY51	4/3
2N697	6/-	2N3705	3/5	BC108	3/-	MC140	6/3
2N706	3/5	2N3707	4/-	BC109	3/6	MJ480	21/-
2N1302	4/-	2N3794	2/11	BC125	12/-	MJ481	27/-
2N1303	4/-	2N4286	2/11	BC126	12/-	MJ491	31/-
2N1304	4/-	2N4289	2/11	BC148	3/3	MPF103	11/6
2N1305	4/-	2N4291	2/11	BC149	4/3	MPF105	7/6
2N2147	18/9	cheapest FET:		BC169	2/3	OA47	1/9
2N2926yellow 1/9		2N5163	5/-	BC183L	2/-	OA90	1/3
2N2926green 2/3		40361	12/6	BC184L	2/3	OA91	1/3
2N3053	5/3	40362	16/9	BD124	16/-	OA202	2/-
2N3054	15/6	AD149	17/6	BFX85	8/3	P346A	5/9
2N3055	16/6	AD161	14/-	BFX88	7/9	TPMD	
2N3702	3/6	AD162	pr.	BFY50	4/9	(=ORP12)	6/-
2N3703	3/3						

Large capacitors, high ripple current types. 2000μF 25V 7/-; 2000μF 50V 9/3; 5000μF 25V 10/3; 5000μF 50V 17/6. S-DeC 30/6; 2-DeC DeCstore 69/6; 4-DeC 119/6.

● **DISCOUNTS** (on all but net items): 10% for total order value of £3 or over. 15% for total order value of £10 or over.

● **POSTAGE and packing:** on orders up to £1 add 1/-. Over £1 post free in U.K. Overseas orders welcomed: carriage charged at cost.

● **CATALOGUE** gives further details of above products and much information on semiconductor characteristics etc. 1/6 post free.


ELECTROVALUE

(Dept. P.W.10)

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.
Tel: Egham 5533

F.A.L.'PHASE 50'

Public Address Amplifier

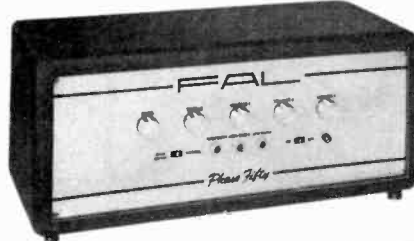

A superb solid state A.C.
Mains unit for vocal and
Instrumental groups and
General Public Address use.

29 Gns

Recommended
Retail price

- ★ 50 Watts Output (Music Rating)
- ★ Output matching for speakers from 3-30 ohms
- ★ 3 separately controlled inputs
- ★ Separate Bass and Treble Controls
- ★ Frequency Response 22c.p.s. to 30Kcs.
- ★ High Sensitivity

SEND S.A.E.
FOR FULLY
DESCRIPTIVE
LEAFLET

Available from your local Dealer

Wholesale and Retail enquiries to Manufacturers

FUTURISTIC AIDS LTD, 103 HENCONNER LANE, LEEDS 13

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6. DAF96, DF96, DK96, DL96, 4 for 28/6.

0Z4	4/6	12SN7GT	8/8	DK92	9/3	EL34	9/6	PCL84	7/8	UC92	5/-
1A7GT	7/8	19BG6G17/8	6/8	DK96	7/-	EL41	10/6	PCL85	9/-	UC94	7/9
1H5GT	7/3	20P2	13/8	DL35	5/-	EL54	4/9	PCL86	8/3	UC95	8/9
1N5GT	7/9	20P3	11/9	DL92	5/9	EL90	5/-	PEN4412/6	UC98	8/3	
1R5	5/9	20P4	18/6	DL96	7/-	EL500	12/8	PFL20012/6	UC942	11/9	
1R5	5/8	25L6GT	5/-	DY86	5/9	EM80	7/8	PL36	9/9	UC981	8/3
1T4	5/9	25U4GT11/8	6/8	EABCS0	6/6	EM81	7/8	PL81	7/3	UC982	7/6
384	5/9	30C1	6/8	DY87	5/9	EM84	6/8	PL82	7/-	UC983	11/6
3V4	6/-	30C15	13/-	EABCS8	6/6	EM87	7/8	PL83	7/-	UF41	10/6
6U4G	4/6	30C16	14/-	EAP42	8/9	EY61	7/8	PL84	6/6	UF80	7/-
6Y3GT	5/9	30C18	11/6	EB91	2/3	EZ40	6/6	PCL507	13/-	UF85	6/9
6Z4G	7/8	30F5	16/-	EB93	8/3	EZ41	7/8	PL508	6/6	UF89	8/9
6L0L2	12/-	30FL1	18/9	EB94	8/3	EZ40	4/6	PL803	14/8	UL41	10/6
6AL2	2/3	30FL12	14/6	EB94	8/3	EZ81	4/9	PM84	7/9	UL84	7/-
6AM6	3/8	30FL14	12/6	EB94	8/3	EZ82	8/9	PX25	10/9	UM84	7/-
6AQ5	4/9	30L1	8/8	ECC81	3/9	EY33	8/9	PY33	10/9	UY85	5/5
6AT6	4/-	30L15	14/-	ECC82	4/9	KT61	8/9	PY31	5/-	VP48	10/9
6AU6	4/6	30L17	16/6	ECC83	7/-	KT66	18/8	PY33	10/9	VP48	10/9
6BA6	4/8	30P4	12/-	ECC85	5/9	ME140015/-	7/8	PY81	5/3	VP132121/-	
6BE6	4/8	30P12	18/9	ECC85	5/9	N78	17/8	PY82	5/3	Z77	3/8
6B6	3/8	30P19	12/-	ECC85	5/9	PC8070	7/8	PY83	5/9		
6BW6	13/-	30P19	12/-	ECC85	5/9	PC86	10/3	PY83	5/9		
6F13	3/8	30P19	12/-	ECC85	5/9	PC88	10/3	PY83	5/9		
6F14	9/-	30P19	12/-	ECC85	5/9	PC96	8/6	PY801	6/9		
6F23	14/3	35L6GT	8/6	ECC85	5/9	PC97	8/6				
6K7G	2/6	35W4	4/8	ECC85	5/9	PC98	8/6	R19	6/6		
6K9G	4/3	35Z4GT	5/8	ECC85	5/9	PC98	8/6	R20	12/6		
6L6	8/8	6063	12/6	ECC85	5/9	PC98	8/6	TH21C	9/9		
6V6G	3/8	ACV9219/6	12/6	ECC85	5/9	PC98	8/6	U26	13/6		
6V6GT	6/8	AZ31	9/9	ECC85	5/9	PC98	8/6	U26	13/6		
6X4	4/8	B729	12/6	EF37A	6/6	PC98	8/6	U42	12/6		
6X6GT	5/9	CC835	10/-	EF39	4/9	PC98	8/6	U42	12/6		
7B7	7/-	CL33	18/6	EF41	10/9	PCF82	6/6	U45	13/6		
7C6	6/9	CY31	9/9	EF80	4/6	PCF86	9/9	U78	4/4		
7E6	9/8	DAC32	7/3	EF82	6/-	PCF90	13/8	U81	12/6		
10F1	14/-	DAF91	13/9	EF86	6/6	PCF90	13/8	U81	12/6		
10P13	15/6	DAF96	8/6	EF89	5/3	PCF801	9/9	U801	19/6		
12AH8	33/-	DF33	7/9	EF91	3/8	PCF802	9/9	UABCS80	6/6		
12AT7	3/9	DF91	2/9	EF94	4/6	PCF80511/6	9/9	UAF42	6/6		
12AU6	4/9	DF96	6/6	EF183	6/-	PCF80812/-	9/9	UB41	6/6		
12AV7	4/9	DE77	4/-	EF184	5/8	PCF81	7/8	UB41	6/6		
12AX7	4/9	DK32	7/6	EF89	5/3	PCF82	9/9	UF80	8/9		
12K8GT	7/-	DK91	5/9	EL33	8/9	PCF83	9/-	UBF89	6/6		

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.
Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

NEW PRICES ON NEW COMPONENTS

ELECTROLYTIC CAPACITORS (Mullard).—10% to + 50%.

		Working Voltage (V)—Capacitance (μF)				Price each		Pack Prices	
4V	6.4V	10V	16V	25V	40V	64V	10 off	25 off	100 off
8	6.4	4	2.5	1.6	1	0.64	1/4	12/4	26/6
32	25	16	10	6.4	4	2.5	1/2	10/6	23/-
64	50	32	20	12.5	8	5	1/2	10/4	22/6
125	100	64	40	25	16	10	1/-	8/9	18/9
250	200	125	80	50	32	20	1/1	9/6	20/9
400	320	200	125	80	50	32	1/2	10/4	22/6
800	640	400	250	160	100	64	1/6	13/4	29/6
1250	1000	640	400	250	160	100	2/-	18/10	37/9
2000	1600	1000	640	400	250	160	2/6	22/3	44/3
3200	2500	1600	1000	640	400	250	3/-	26/9	59/-
				800	500	320	5/3	46/6	101/-
				1250	800	500	6/6	57/6	125/4
				2000	1250	800	8/-	71/4	157/-
				4000	2500	1600	12/6	91/6	194/9
				6400	4000	2500	15/-	133/4	291/8

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: 1/8W: 8 × 2.8
1/4W: 10 × 4.3

Leads: 35

10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series).
5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

	each	10 off	25 off	100 off
1/8W 10%	2d.	1/6	3/3	10/4
1/4W 5%	2 1/2d.	1/9	3/8	11/8
1/4W 10%	2 1/2d.	1/9	3/8	11/7
1/2W 5%	3d.	2/-	4/-	12/10

CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads.

±10% tolerance. 100 Volt Working.

Prices—per Capacitance value (μF)

0.001, 0.002, 0.005, each	10 off	25 off	100 off
0.01, 0.02	6d.	4/3	8/4
0.05	8d.	6/-	12/6
0.1	10d.	7/1	15/6
0.2	1/2	10/-	20/10
0.5	2/-	17/6	37/6

Polystyrene film, Tubular, Axial leads. Unencapsulated. ±5% or ±1pf tolerance. 160 Volt Working.

Prices—per Capacitance value (μF)

10, 12, 15, 18, 22, 27, 33, each	10 off	25 off	100 off
39, 47, 56, 68, 82, 100, 120,			
180, 220, 270, 330, 390	5d.	3/7	7/9
470, 560, 680, 820, 1,000,			
1,500	6d.	4/-	8/8
2,200, 3,300, 4,700, 5,600	7d.	5/-	10/10
6,800, 8,200, 10,000, 15,000	8d.	6/-	13/-
22,000	9d.	6/9	18/-

POTENTIOMETERS (Carbon)

Miniature, fully enclosed, rear tags, carbon brush wiper. Long life, low noise. Body dia., 1/8 in. Spindle, 1 in. × 1/8 in. 1/4W at 70°C. ±20% below 1/4M, ±30% over 1/4M. Lin. 100 ohms to 10 Megohms. Log. 5 Kohms to 5 Megohms.

Prices—per ohmic value each 10 off 25 off 100 off

	each	10 off	25 off	100 off
Miniature (0.3W)	2/-	18/4	41/8	150/-

GANGED STEREO POTENTIOMETERS (Carbon)

1/4W at 70°C. Long Spindle.

Logarithmic and Linear: 5k + 5k to 1M + 1M.

Prices—per ohmic value each 10 off 25 off 100 off

	each	10 off	25 off	100 off
Miniature (0.1W)	8/-	70/-	162/6	575/-

SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1 in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at 70°C. ±20% below 1/4M, ±30% above 1/4M. Horizontal (0.7 in. × 0.4 in. P.C.M.) or Vertical (0.4 in. × 0.2 in. P.C.M.). Subminiature: 0.1W at 70°C. ±20% below 2.5M, ±30% above.

Prices—per ohmic value each 10 off 25 off 100 off

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

POLYESTER CAPACITORS (Mullard)

Tubular, 10%, 160V: 0.01, 0.015, 0.022μF, 7d. 0.033, 0.047μF, 8d. 0.068, 0.1μF, 9d. 0.15μF, 11d. 0.22μF, 1/- 0.33μF, 1/3. 0.47μF, 1/6. 0.68μF, 2/3. 1μF, 2/8.
400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0.01, 0.015, 0.022μF, 7d. 0.033μF, 8d. 0.047μF, 9d. 0.068, 0.1μF, 11d. 0.15μF, 1/2. 0.22μF, 1/6. 0.33μF, 2/3. 0.47μF, 2/8.
Modular, metalised, P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022μF, 7d. 0.033, 0.047μF, 8d. 0.068, 0.1μF, 9d. 0.15μF, 11d. 0.22μF, 1/- 0.33μF, 1/5. 0.47μF, 1/8. 0.68μF, 2/3. 1μF, 2/9.

JACK PLUGS

1 in. Type P1. Standard. Screened. Heavily chromed.

1 in. Type SE/P1. Side-entry version of Type P1.

1 in. Type P2. Standard. Unscreened. Unbreakable moulded cover.

1 in. Type P3. Tip-Ring-Sleeve Stereo version of Type P1.

1 in. Type P4. Tip-Ring-Sleeve Stereo version of Type P2.

3.5mm. Type P5. Standard. Screened. Aluminium cover.

3.5mm. Type P6. Standard. Unscreened. Unbreakable moulded cover.

Prices	each	10 off	25 off	100 off
P1	3/-	26/8	62/6	233/4
SE/P1	3/6	30/10	66/8	280/-
P2	2/6	23/4	54/2	200/-
P3	6/6	60/-	137/6	500/-
P4	6/2	59/6	127/6	455/-
P5	2/2	19/2	43/9	158/4
P6	1/8	15/-	33/4	116/8

JACK SOCKETS

1 in. Type S3. Stereo version for use with P3 or P4 plugs.

1 in. Type S5. Standard. Moulded body. Chrome insert.

3.5mm. Type S6. Standard. Moulded body. Chrome insert.

Available with make or break contacts on Tip, Ring and Sleeve.

Prices	each	10 off	25 off	100 off
S3	3/3	30/-	68/9	250/-
S5	2/9	25/-	56/8	216/8
S6	1/6	13/4	33/4	100/-

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/-, OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/-, OC139, 5/3. OC25, 7/-, OC35, 8/-, OC23, OC28, 8/3.

SILICON RECTIFIERS: (0.5A). 170 P.I.V., 2/9. 400 P.I.V., 3/-, 800 P.I.V., 3/3. 1250 P.I.V., 3/9. 1500 P.I.V., 4/-, (0.75A); 800 P.I.V., 3/3. (6A); 200 P.I.V., 3/-, 400 P.I.V., 4/-, 600 P.I.V., 5/-, 800 P.I.V., 6/-.

THYRISTORS (5A): 100 P.I.V., 8/-, 200 P.I.V., 10/-, 400 P.I.V., 15/-.

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off, 5/-. Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/-. DP/ST, 4/6. DP/DT, 5/-.

PRINTED CIRCUIT BOARD (Vero).

0.15 in. Matrix: 3 1/2 in. × 2 1/2 in., 3/3. 5 1/2 in. × 2 1/2 in., 3/11. 3 1/2 in. × 3 1/2 in., 3/11. 5 in. × 3 1/2 in., 5/6.
0.1 in. Matrix: 3 1/2 in. × 2 1/2 in., 4/-, 5 in. × 2 1/2 in., 4/6. 3 1/2 in. × 3 1/2 in., 4/6. 5 in. × 3 1/2 in., 5/3.

SEND S.A.E. FOR 1969 CATALOGUE

DUXFORD ELECTRONICS (PW)

97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)



MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/6

Keynector

A REVOLUTIONARY PRODUCT

cuts out plugs

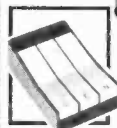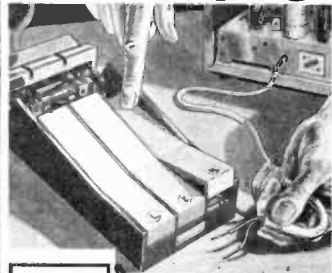

**SAFEST & QUICKEST
WAY TO CONNECT
ELECTRICAL EQUIP-
MENT TO THE MAINS**

No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. The Keynector casing is in two-tone plastic and measures 5 x 3 x 1 1/2 in. Price 39/6, plus 5/- p. & p.

E. B. INSTRUMENTS

DIVISION OF ELECTRONIC BROKERS LTD.
49-53 PANCRAS ROAD, LONDON, N.W.1.
Telephone: 01-837 7781

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/8, 11 element, 45/-, 14 element, 52/6, 18 element, 60/-, Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6, 11 element, 80/-, 14 element, 87/8, 18 element, 95/-, Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

BBC · ITV AERIALS



BBC (Band 1), Tele-
scopic loft, 25/-, External
S/D, 30/-, "H" £2.15.0.
ITV (Band 3), 3 ele-
ment loft array, 30/-, 5
element, 40/-, 7 element
50/-, Wall mounting 3 ele-
ment, 47/8, 5 element,
52/6. Combined BBC/
ITV, Loft 1+3, 40/-; 1+5,
50/-; 1+7, 60/-; Wall
mounting 1+3, 57/8; 1+5,
67/8; Chimney 1+3, 67/8;
1+5, 75/-.
VHF transistor pre-
amps, 75/-.


COMBINED BBC1 — ITV — BBC2
AERIALS 1+3+9, 70/-, 1+5+9, 80/-,
1+5+14, 90/-, 1+7+14, 100/-, Loft mounting
only. Special leaflet available.
F.M. (Band 2), Loft S/D, 15/-, "H", 32/6,
3 element, 55/-, External units available.
Co-ax. cable 8d. yd. Co-ax. plugs, 1/4.
Outlet boxes, 5/-, Diplexer Crossover Boxes,
13/6, C.W.O. or C.O.D. P. & P. 6/-, Send 6d.
stamps for illustrated lists.

Callers welcomed — open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

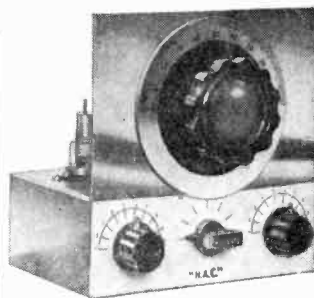


Famous for over 30 years for Short-Wave Equip-
ment of quality, "H.A.C." were the Original
suppliers of Short-Wave Receiver Kits for the
amateur constructor. Over 10,000 satisfied
customers—including Technical Colleges, Hos-
pitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1969 RANGE

One-valve model "DX", complete kit—price 56/6
(Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve
S.W. Kit available at any price. America and
Australia received clearly at good volume." This
kit contains all genuine short-wave components,
drilled chassis, valve accessories and full instruc-
tions. Ready to assemble, and of course, as all our
products—fully guaranteed. Full range of other
S.W. kits still available, including the famous
model "K" (recommended by radio clubs). All
orders despatched by return. (Mail order only.)
Send now for a descriptive catalogue, order form.

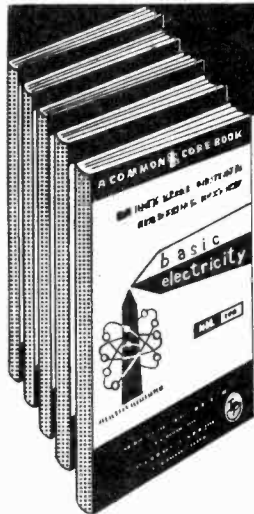"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this out-
standingly successful NEW PICTORIAL
METHOD—the essential facts are explained
in the simplest language, one at a time, and
each is illustrated by an accurate, cartoon-
type drawing. The books are based on

the latest research into simplified learning
techniques. This has proved that the
PICTORIAL APPROACH to learning is the
quickest and soundest way of gaining mastery
over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series
of manuals has proved a
valuable course in training
technicians in Electricity,
Electronics, Radio and
Telecommunications.

WHAT READERS SAY

"May I take this opportunity to thank you for such enlightening
works and may I add, in terms, easily understood by the novice."
L. W. M., Birmingham.

"I find that the new pictorial method is so easy to understand, and I
will undoubtedly enjoy reading the following five volumes: thank you
for a wonderful set of books." C. B., London.

"They certainly confirm everything your readers say about them and I
am more than delighted with them. They will be of great value to me
in my job as Hospital maintenance electrician." A. B., Birmingham

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

■ Please send me WITHOUT OBLIGATION TO PURCHASE, one of the
above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid,
in good condition within 7 days or send the following amounts. BASIC
ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3
fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price,
or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each.
This offer applies to UNITED KINGDOM ONLY. Overseas customers
cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ BASIC ELECTRICITY ☐ BASIC ELECTRONICS ☐

Prices include Postage and Packing.

■ Signature _____
(If under 21 signature required of parent or guardian)

■ NAME _____
BLOCK LETTERS

■ FULL POSTAL
ADDRESS _____

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS —2 or 4 TRACK



Chassis 12½ x 5½ x 4½ in. high. Front panel alum and black—12½ x 4½ in. 200-250 A.C. Mains Trans. OM/On-Tone; Vol./Mic.; Vol./Gram.; Mic. Input; Gram. Input; Monitor; Valves 6BR7, 6OC83, 6EM84, EL84 and Rect. 2 Track \$10.10. 4 Track \$12 (12/8 p. & p.). Ready for bolting direct to Magnavox deck.

STEREO AMPLIFIER type HV— 2 x 3 Watts

Fully built. On off, sep. vol. and tone each channel. 12 x 4½ x 6 in. high. EZ90, 2 x ECL86; for 3 ohm speakers, double wound main trans; fixing flanges and base plate; suitable for crystal cat. tuner etc. \$5.17.6 (8/- p. & p.). Available as kit with full instructions at \$4.17.6 (8/- p. & p.).



STEREO AMPLIFIER type RC— 2 x 3 Watts

Fully built. 2 x UCL82, metal rect; ganged vol. and tone cont; on-off, balance. 11 x 3½ x 4 in. high double wound mains trans. with supporting brackets. For 3-ohm speakers. \$6 (8/- p. & p.).



SUPER SIX KIT Mk. 2

MW and LW fully tunable. Wooden cabinet 9½ x 8½ x 3 in., carrying handle, two tone cabinet; 4 in. speaker; 6 transistors; full book of instructions. 2/6 (free with kit) All parts may be purchased separately. S.A.E. for price list. Price of parts \$4.5.0 (8/- p. & p.).

We can accept H.P. orders for our Stereo Radiogram Chassis previously advertised and still available at \$19.19.0. Terms £7 deposit and 6 monthly payments of 47/6 (by Banker's Order only). Total H.P. Price £21.5.0.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 28240
CLOSED WEDNESDAY. S.A.E. for enquiries please.

TRANSISTORS etc.

AC107	3/-	OC85	7/6
AC126	2/-	OC44	2/0
AF115	3/-	OC45	3/0
AF116	3/-	OC70	2/3
AF117	2/9	OC71	2/-
BFY18	4/6	OC72	2/2
BFY51	4/-	OC73	2/3
GET113	2/6	OC75	2/2
OA5	1/8	OC75	2/2
OA9	1/8	OC81	2/-
OA47	1/9	OC81D	2/-
OA81	1/6	OC82D	2/3
OA85	1/6	OC140	5/-
OA91	1/9	OC169	3/6
OC23	6/6	OC170	2/3
OC25	5/-	OC171	2/2
OC26	5/-	OC202	4/6
OC28	6/6	TK22C	1/6

Crystal Diodes—6 for 2/6 (7d.).

Additional Transistors—AF147 and AF150, 24v. Larger envelope, 4 leads, collective current 10mA, gain 70—4/- each. AF149—gain 225—4/6 each.

Also 8µF 50V 1/2, 25µF 25V 1/3 and 50µF 50V 1/8. Other electrolytics in current list. Postage, Packing and Insurance all above 7d. up to 3/-; 1/- from 4-11/-; 12/- and over paid.

2.0 µF VAR. CONDENSER: Mod., air-spaced, .0005 ea. sec. 5/- (1/-).

SUB-MIN. TRANSFORMERS Output (3 for OC72 etc.) 2/8. Driver 2/9 (either 7d.).

MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/250/500/1K volts D.C.

0-10/50/100/500/1K volts A.C. 0-50 µA/2-5mA/250mA D.C. 0-6K Ω/6 meg Ω

0-10 µA/0-100mV/1mV. —20 to +22dB. Complete with test leads and instructions.

Over-load protected 1989 model with every refinement. \$4.7.6 (8/- p. & p.). JUNIOR MODEL

at 47/6 (2/6) 100 Ω/V described in free list.

SOLDERING IRON. Slim Mod. British High speed, 8½ in., all parts replaceable, fully

guaranteed for professional, radio and general D.I.Y. use. 19/6 (1/-)

DIAMOND STYLII Replacements for BSR TC8LP, TC8/S and TC8LP/STEREO:

COLLARO "O": RONETTE BP40LP; GARRARD GC2LP and GC8LP; ACOS GP85/67;

all at 7/6 each (6d.). ACOS GP91 8T/LP; BSR 8T4 and 8T9; SONOTONE 9TA and

9TAHC, PHILIPS AC808 and 3060 (3063, 3066, 3301, 3302, 3304) state whether 4 in. or

4½ in. type, all at 18/6 (6d.).

SHAPIRE all the above 7/6 types only, also ACOS GP37 at 3/6 each (6d.). ACOS

GP91 at 6/9 (6d.). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES, all fitted 8T4 and Standard fittings. Mono GP87/2, 13/6. Mono

de Luxe GP112, 17/-. Stereo Compatible—Mono which also plays Stereo records

monaurally with min. wear, GP81/2, 19/6. Latest Stereo GP88, 22/-. Ceramic

8T4, top quality for expensive outfit, GP84, 38/6 (all 1/-).

PP3 ELIMINATOR (A.C.) 17/6. (1/6) TWO STATION TRANS. INTER-COM. Excellent

baby alarm. Instant, easy fitting with leads, plugs and battery. All you require 52/6 (3/-).

TRANSISTORISED AMPLIFIERS, 3 watt, 9V operation, 45/6 (1/6); 7½ watt, 6 trans.

24V operation, 67/6 (2/6).

Extra High Torque MINI-MOTOR, 4½ to 12V, 1½ x ½ in. 5/- (6d.). 9,000 r.p.m.

SUBSTITUTION BOXES, Capacitance 24/9 (1/6). Resistance 22/6 (1/6). Both full range and

complete. Full details in list.

TEST PROBES: Flexible, unbreakable 24" Red and Black leads, 1/6 "4" probe, 1½" plugs

4/9 (9d.).

RECORDING TAPE: Finest quality British Mylar. STANDARD: 5 in. 600ft. 7/8, 5½ in.

800ft. 8/9, 7 in. 1200ft. 11/8. LONG PLAY 5 in. 900ft. 10/-, 5½ in. 1200ft. 11/8, 7 in. 1800ft.

12/- (1/3 each). Still the finest quality and value obtainable.

MICROPHONES—CRYSTAL, MIC91, Desk, 16/8; MIC45, curved hand grip 17/8; Stick

"60" 20/8; Stick "39" 28/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut"

stand, switch and 2 leads with 2-5 and 3-5 plugs 11/-, Lapel (or hand) with clip 6/6 (1/-).

Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands,

25/- (1/6). DYNAMIC: Cream hand/table 14/- (1/-). MS10 50K Ω, 3½ x ½ in. with Base,

Adaptor and Neck Cord 37/6 (2/6). MS11, similar, but fixed on flexible 5/4 in. neck to switch-

fitted base 42/6 (2/6). DM128 Uni-directional, 50K/600 ohms imp, stand adaptor, very

high quality 6½ x 2 x 1½, \$5.9.6 (5/-).

CARDIOID DYNAMIC OMNI-DIRECTIONAL: Two highly successful mikes "SQUARE"

208, \$5.10.0. "BALL" type, 209, with built-in vol. control, switch 50K/600 ohms imp.,

\$5.17.6 (either type 5/-). Full details in list.

MICROPHONE INSERTS: Diameter 1.7 in. or 0.9 in. either size 5/6 (6d.).

SPEAKERS: 12 in. round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 55/6 (5/6); 2 in. 3Q

6/6 (1/-); 6 x 4 heavy duty 3Q 14/6 (3/6) or for Stereo 34/6 pair, post etc. paid. Limited

quantity powerful 2 in. FM transistor replacement speaker, high ohms, excellent, 5/6

(1/-). HEADPHONES High Res. 2000 Ω ea. Earpiece 18/6 (1/6); Stereo Dyn 8-16 Ω,

89/- (3/-); EARPIECES with lead etc. Min. Plug Magnetic 1/6 (state whether 2-5 or

3-5mm.). Crystal 4/9 (either 7d.). (3-5mm. only).

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings

28/6 (2/6). Motor driven, 12V, 5 section, complete 27.10.0 (5/-).

FOR ALL PORTABLES and F.M. SETS. Telescopic 5 section 54-22 in. with swivel, 5/6.

7-Section 54-32 in., no swivel, screw hole in base, 6/6. 10-section 64-47 in., no swivel,

screw hole in base, 12/6. DISAPPEARABLE 8 section, swivel fixing assembly, 64/35 in. 10/-.

New 8 section 54/25 in., screw hole in base no swivel 4/-, (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 2/9.

DPST 3/-, DPDT 3/8. Slide types. Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre

"off" 1/9. Reed magnetic on/off 1/9 (7d. each, all types). Rotary Switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch 2/6, 12 volt 7 pin synch 10/-

6 volt 7 pin synch 10/- (1/- each, all types).

MAINS NEON TESTER: Fly leads 2/- (7d.). Pocket screwdriver type 2/6 (6d.). PLUGS: Std.

Jack, plastic body 2/8. Screened 3/-, Sockets 1/11 (all 7d.). VALVE HOLDERS: B70 or

B94, Moulded 6d. (7d. up to 4, 1/- over 4). CONNECTING WIRE: 5 coils assd. cols. each

5 yds. Solid Core 2/6 (7d.). Flexible 3/- (9d.). Super thin for transistor wiring etc. 3/- (7d.).

PICK-UP WIRE: Twin Super thin Flex, Screened, Shashed, 1/3 yd. (6d. up to 6 yds.,

over 6 yds. post free). TWIN MIKE CABLE: 1/8 yd. SINGLE MIKE CABLE: 7d. yd.

Both flexible, screened and sheathed. FREDER CABLE: Twin r.f. bal. "Bg. 8", 80 Ω,

or flat 300 Ω transparent polythene insulated, either 6d. per yd. (all cables up to three

yards 8d., each additional yard, 1d. extra).

R.F. INDICATOR, 5-Band, with meter antenna, monitoring crystal earpiece etc., 48/6

(1/6). Details in list.

RETRACTABLE FLEXIBLE LEADS. Space saving "Curly", many uses in car and home:

with phono plug each end, 6 ft. 4/8; 12 ft., 7/8. With phono plug one end, phono socket

at other, 6 ft., 5/-, 12 ft., 8/6 (9d. on any).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors

and circuit. M. and L. wave. Separate speaker and baffle. Absolutely complete, for + or

— chassis. \$11.11.0 (6/8). A huge success since introduction.

CURRENT LIST: Send a free for a.s.e. details of cable, croc. clips and leads,

volume controls, Continental din plugs for Grundig, Telefunken equipment, etc., dials,

plugs and sockets, panel meters, record player and tape recording accessories. Battery

chargers, test equipment, test prods, tape recorder, special transistors, portable sets,

more switches and other components, tools, Veroboard etc. This advertisement cancels

all previous ones and lists supplied prior to August 31st.

FELSTEAD ELECTRONICS

(PW23)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost, plus 3/2 registration or insurance fee. S.A.E. please for all enquiries, otherwise regret cannot be replied to.

BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,
150 REGENT ST., LONDON, W.1.

KING OF THE PAKS SUPER PAKS

Unequaled Value & Quality

BI-PAK NEW—UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC91, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO-5 can up to 600PIV CRS1/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
U33	15 Plastic case 1-amp Silicon Rectifiers 1N-4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2N302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	10/-
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2N322	10/-
U38	20 Fast Switching Sil. trans. NPN 400Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N3060	10/-
U41	30 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

FULLY TESTED

AC107	3/6
AC126-7-8	2/6
AF116-117	1/6
AF139	10/-
AL102	15/-
BC107-8-9	5/-
BFY60-81-82	7/6
BSY26-7	3/6
BSY28-9	4/6
BSY96-95A	4/6
OC22-25	5/-
OC26-35	5/-
OC28-29	7/6
OC44-45	1/9
OC71-81	5/6
OC72-75	2/6
OC81D-82D	2/6
OC82	2/6
OC140	5/-
OC170	2/6
OC171	2/6
OC201	7/6
ORP12-80	8/6
OCPT1	8/6
OA5-10	1/9
OA47	2/-
OA79	1/9
OA79	1/9
OA81-85	1/6
OA91	1/3
OA95	1/9
OA300	3/6
OA309	3/6
2N696-7	3/6
2N706	3/6
2N708	5/-
2N2160	15/-
2N2646	15/-
2N2712	5/6
2N2926	2/6
MAT100-101	3/6
MAT120-121	3/6
8T140	3/6
8T141	4/6
2N3819	10/-
2N3820	25/-

TESTED SCR's

PIV	1 AMP	7A	16A	30A
25	7/6	8/6	10/6	25/-
50	7/6	8/6	10/6	25/-
100	8/6	10/-	15/-	45/-
200	12/6	15/-	20/-	55/-
300	15/-	20/-	25/-	—
400	17/6	25/-	35/-	80/-
500	30/-	40/-	45/-	95/-
600	—	40/-	50/-	—

SIL. RECTS. TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/8	9/6
100	1/3	3/8	4/8	15/-
200	1/8	4/-	4/9	20/-
300	2/3	4/8	9/6	25/-
400	2/6	5/6	7/6	28/-
500	3/-	6/-	8/6	30/-
600	3/3	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/8	11/6	15/-	—

PLEASE NOTE. To avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: **BI-PAK SEMI-CONDUCTORS**, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

BRAND NEW TEXAS GERM. TRANSISTORS

Code and Guaranteed	Pak No.	EQVT.
T1 8 2G3710	OC71	10/-
T2 8 2G374	OC75	10/-
T3 8 2G3744A	OC81D	10/-
T4 8 2G381A	OC81	10/-
T5 8 2G382T	OC82	10/-
T6 8 2G344A	OC44	10/-
T7 8 2G345A	OC45	10/-
T8 8 2G378	OC78	10/-
T9 8 2G399A	2N1302/10	10/-
T10 8 2G417	AF117	10/-

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-16V.
400mW 2/6 each
1.5W 8/6 each
10W 5/- each
All fully tested. State voltage required.

180 VCB NIXIE DRIVER TRANSISTOR 8lm. BSX21 & C407. 2N1893 FULLY TESTED AND CODED ND120. 1-24 3/6 each. TO-5 NPN 25 up to 8/- each.

UNIUNCTION

UT46 Eqty. 2N2646, 7/6
Eqvt. T1843 BEN3000 7/6
25-99 5/-, 100 up 4/- each

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-. Plus 2/- P. & P.

GRAND CLEARANCE SALE

everything must go

SUPER WHIP AERIALS. Brand new specially designed telescopic, chrome plated 25in. sectional aerials. Consists of 6 sections and screw base. An ideal aerial for TX/RX use. Price only 6/6 each, p.p. 1/6. Two aerials for 12/6 post free. Four aerials £1 post free.

PRECISION METERS. Brand new and boxed, size 3 1/2 in. sq. Type 1 0-500V FSD; Type 2 0-150 mA. Moving coil movement. Fully guaranteed. List £3.10.0. Sale price 30/- each. Two for 50/- post free.

RADIATION METERS. Pocket type. Brand new in makers cartons. Only 9/6 each, p.p. 1/6. Two for 17/6 post free.

TANNOY MIKES (Heavy Duty). Ideal for P.A. work. Complete with high quality moving coil headphones. Only 17/6, p.p. 5/-.

PRINTED CIRCUIT TOP BAND SUPERHET CHASSIS. Uses standard components. Complete with circuit. Only 15/- post free.

MINIATURE TRANSISTORISED B.F.O. UNIT. A compact B.F.O. unit that will enable your set to receive CW or SSB. Compact single hole fixing. The Unit will fit anywhere. Ideal for all Ex-Govt. and Commercial receivers. Complete with fitting instructions. Only 39/6, p.p. 2/6.

19 SET CONTROL BOXES. Brand new and boxed. 10/-, p.p. 5/-.

HEAVY DUTY POWER SUPPLY UNITS. Famous manufacture. Input 200/250V A.C. Output 250V D.C. at 175 mA. 6.3V/12V at 4A. Robust rack mounting cabinet. List £42. Sale price 69/6 carr. 10/-.

MATCHING MAINS P.S.U. For R1132 and 1392 receivers. Brand new and boxed only 59/6, carr. and insurance 10/-.

GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuit details and notes on most British and American wireless equipment. Only 35/-, p.p. 5/-.

R.F. AMPLIFIERS No. 2 Mk. III. Increase the output from your TX. Only 79/6, carr. 10/-.

DOUBLE 365 pF tuning capacitors with slow motion drive. Brand new. Normally 17/6 each. Our price 6/- each, p.p. 1/6. Two for 10/- post free. £1 for five post free.

RUBBER TELEPHONE HANDSETS. Moving coil type with press-to-talk switch and connecting cable. Brand new and boxed. 7/6 each, p.p. 2/6. 2 for 15/-, post free.

RHEOSTAT DIMMER UNITS. Will control up to 50V at 3A. Compact metal case. Ideal for lab. work. Only 15/-, p.p. 2/6. Two for 30/- post free.

IFT TRANSFORMER SETS. Comprising double tuned 1st and 2nd 3rd If single tuned. Only 12/6 per set of three post free.

TELEPHONE SPARES. 600 TYPE RELAYS. Only 3/6 each, p.p. 1/-.

Ten for £1 post free. **EYEBALL INDICATORS.** 6/- each. Four for £1 post free. **TELEPHONE DIALS** 4/6 each, p.p. 1/6. Four for £1 post free.

2 1/2 in. MOVING COIL SPEAKERS. 3 ohms. Brand new. Only 4/11, p.p. 1/1. Two for 10/- post free. **30 mfd 250V WIRE ENDED TUB ELECTROLYTIC CAPS.** £1 per doz. post free. 10 mfd 15V working tag ended electrolytics, 1/6 each. 10/- per doz., post free.

MEDIUM WAVE FERRITE SLAB AERIALS. Will fit most transistor radios. Only 3/6 each, p.p. 6d. Two for 6/- post free. Four for 10/- post free.

TELEPHONE EXCHANGES. PMBX Type Ex-GPO in good condition. Complete and ready to use. Cordless type only £13.10.0, carriage 50/-.

Cord type £12.10.0, carriage 30/-.

AIRCRAFT BAND CHASSIS. Printed circuit uses standard components. Full circuit details only 17/6 post free.


SMOOTHING UNITS. Cure your hum problems. Beautifully made pieces of equipment. 12V or 24V DC input gives a fully smoothed, fully regulated DC output. Worth £30 each. Robust metal cabinet with provision for stand-by battery. Brand new in makers cartons, price 55/- post free.

HANDY PLASTIC CASES. Size 2 1/2 x 1 1/2 x 3/4 ins. Ideal for building your transistorised equipment into. Only 1/- each, p.p. 4d. 12 for 10/- post free. 24 for 15/- post free. 50 for 30/- post free. 100 for 50/-, p.p. 5/-.

A very versatile little box.

ELECTRONIC CAR FAULT TRACING UNIT/BATTERY CHARGER. A wonderful piece of equipment enabling you to trace most faults on your car and a great aid to tuning your car. Meant to sell at six guineas each. Sale price £4.15.0, carriage and insurance 5/-.

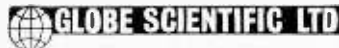Full 12 months guarantee. An ideal Christmas present.



Dept. PW, GLOBE SCIENTIFIC LTD, 38 BRIDGEND, LEEDS 1

Fully guaranteed Individually packed VALVES

PERSONAL CALLERS WELCOME

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to £1, 2/-; over £1, 2/- per £1; over £2 post free. C.O.D. 4/- extra

ColomOR
brand

ALL valves
guaranteed

TRANSISTORS, ZENER DIODES etc.

CY31	7/6	ECL80	8/6	KT66	21/-
DAF90	7/6	ECL82	6/6	KT88	29/-
DF96	7/6	ECL83	10/6	N78	15/-
DF92	9/-	ECL86	8/6	OA2	6/6
DK96	7/6	EF36	3/6	OB2	6/6
DL92	4/6	EF37A	3/6	PABCS8	7/6
DL94	6/6	EF39	6/6	PC86	10/6
DL96	8/6	EF40	9/6	PC97	9/6
DM70	6/6	EF41	10/6	PC900	7/6
DM71	7/6	EF42	13/6	PC84	6/6
DY86	6/6	EF80	4/6	PC89	9/6
DY87	6/6	EF83	9/6	PC189	10/6
DY802	9/6	EF85	6/6	PC82	17/-
EABL80	6/6	EF86	6/6	PC801	15/6
EAF42	9/6	EF89	5/6	PC82	6/6
EB91	2/6	EF91	3/6	PCP84	9/6
EB93	3/6	EF92	2/6	PCF86	9/6
EB94	9/6	EF95	5/6	PCF200	15/6
EB95	6/6	EF183	6/6	PCF201	15/6
EBF80	7/6	EF181	7/6	PCF801	3/6
EBF83	8/6	EF800	21/6	PCF802	9/6
EBF89	6/6	EF812	18/6	PCF805	14/6
EC081	6/6	EF1200	15/6	PCF806	14/6
EC082	5/6	EH90	7/6	PCF809	14/6
EC083	5/6	EL34	10/6	PCH200	12/6
EC084	5/6	EL41	10/6	PCL81	9/6
EC085	5/6	EL42	11/6	PCL82	7/6
EC086	5/6	EL44	10/6	PCL83	13/6
EC088	7/6	EL85	4/6	PCL84	8/6
EC089	9/6	EL86	5/6	PCL85	9/6
EC084	12/6	EL800	17/6	PCL86	8/6
ECF80	6/6	EL8035	17/6	PFL200	
ECF82	6/6	EM31	5/6		
ECF83	12/6	EM80	7/6	PL36	10/6
ECF80112	6/6	EM84	7/6	PL81	9/6
ECF80212	6/6	EM87	11/6	PL82	8/6
ECF80312	6/6	EY61	7/6	PL83	7/6
ECI84	7/6	EY86	8/6	PL84	6/6
ECI83	7/6	EY88	8/6	PL500	13/6
ECI42	10/6	EZ40	8/6	PX4	14/6
ECI81	5/6	EZ41	8/6	PX25	12/6
ECI83	10/6	EZ80	5/6	PY33	10/6
ECI800		EZ11	5/6	PY50	6/6
		EZ34	11/6	PY81	5/6

OA5	2/6	OC16	15/-	OC83	5/6	AC176	7/6	CR81/20	9/6	MPF102	
OA10	3/6	OC22	10/-	OC83B	4/6	AC178	4/6	CR81/30		MPF103	9/6
OA70	2/6	OC26	7/6	OC139	7/6	AD140	13/6		10/-	MPF104	
OA71	2/6	OC28	5/6	OC140	9/6	AF117	5/6	CR81/35			10/-
OA79	1/6	OC39	15/-	OC170	5/6	AF118	10/6	CR81/40	11/6		
OA81	1/6	OC35	10/6	OC171	6/6	AF124	7/6				
OA200	1/6	OC38	3/6	OC172	7/6	AF127	5/6	CR81/40	12/6		
OA202	2/6	OC44	4/6	OC200	7/6	AF139	10/6	CR83/05	6/6		
OA210	7/6	OC45	2/6	IN21	3/6	AF178	12/6	CR83/20			
OA211	8/6	OC71	2/6	IN21B	5/6	AFY19	22/6				
OA220011		OC72	4/6	IN25	12/6	AFY28	5/6	CR83/30	9/6 ca.		
OA220110		OC73	11/6	IN43	4/6	BFY19	5/6				
OA2202	6/6	OC75	6/6	IN70	4/6	BFY27	5/6	CR83/40	15/6		
OA2206	8/6	OC76	5/6	2N1306	6/6	BFY51	5/6				
OA2207	8/6	OC81	4/6	2N1307	6/6	BFY52	4/6				
OA2208	6/6	OC81D	3/6	28303	10/6	BY213	5/6				
OA2223	6/6	OC82	5/6	AC126	6/6	BY215	5/6				
OA2225	10/6	OC82	5/6	AC127	7/6	CR81/10	5/6				
		OC82DM	3/6	AC128	6/6						

6K6GT	8/6	12BE6	6/6	866A	15/-
6K7	6/6	12BH7	3/6	954	4/6
6K7G	2/6	12C8	3/6	955	2/6
6K7GT	4/6	12E1	17/6	956	2/6
6K8G	4/6	12K5	10/6	957	5/6
6K8GT	7/6	12K6GT	7/6	991	6/6
6K25G	16/6	12Q7GT	5/6	1822	17/6
6L6	14/6	12R7	4/6	2051	5/6
6L6GA	9/6	14S7	15/6	3505	13/6
6P25	13/6	19AQ5	5/6	3576	10/6
6SA7	7/6	19G3	60/6	5678	10/6
6SA7GT	6/6	19G6	20/6	5726	7/6
6SC7	7/6	19H4	70/6	5933	22/6
6SC7GT	5/6	20P4	20/6	6067	10/6
6SG7	6/6	25L6GT	7/6	6060	7/6
6SJ7	6/6	30C15	15/6	6064	7/6
6SJ7GT	6/6	30C17	18/6	6065	8/6
6SJ7Y	6/6	30C18	15/6	6080	27/6
6SK7	7/6	30F5	10/6	6146	28/6
6SL7GT	6/6	30FL1	15/6	9001	3/6
6SN7GT	6/6	30FL12	19/6	9002	4/6
6SQ7GT	7/6	30FL13	9/6	9003	8/6
6V6G	2/6	30FL14	15/6	9004	2/6
6V6GT	6/6	30L15	17/6	9006	2/6
6V6M	3/6	30L17	17/6	C.B. Tubes	
6X4	4/6	30P12	16/6	E4504/B	16/6
6X5G	5/6	30P19	14/6	OJ9	75/6
6X5GT	5/6	30PL1	14/6	VC97	32/6
6-30L2	14/6	30PL13	18/6	VC9139A	30/6
6Z4	5/6	42	5/6	VC917B	30/6
7C5	14/6	50CD6G		VC91750	30/6
7C6	6/6	50EH5	7/6	VC917B	30/6
7D4	3/6	50E15	7/6	55/6	
7Y4	9/6	75	5/6	VC917C	30/6
9D6	2/6	78	5/6	5CP1	30/6
11E2	30/6	80	7/6	5FP7	26/6
12AT6	4/6	85A2	7/6	Photo Tubes	
12AT7	4/6	31C5	25/6	816	12/6
12AU7	4/6	807	9/6	6M6Z5	45/6
12AV6	5/6	813	75/6		
12AX7	6/6	829A	45/6		
12BA6	6/6				

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
(01) 743 4946

29/41H. AERIALS each consisting of ten 3ft. 1/2 in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect. In canvas bag. £3.9.5. P. & P. 10/6.

METERS Full List of our very large stock of meters on request.

ALL OVERSEAS ENQUIRIES AND ORDERS
Please address to
ColomOR (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.
Tel.: 01-743 0899



We put
23,340
cigarettes

in our Budget
combination storage
unit!

Think what you could
put in it!

Storage. Lots of it, for a thousand things you stock; replacement parts; light bulbs; cameras; anything up to 7 x 8 x 10 1/2 in. Safety drawer-stops as 'standard'. Smooth guide runners thro'out. All in a compact 3ft. 6in. high, 2ft. 11in. wide, 1ft. deep area. Ready assembled, in stove enamelled green or grey. With 18 handy, 6 large, 8 king-sized drawers. At £17 5s. worth every penny! See the rest of the N. C. Brown range



£17 5s.

Carriage free
on mainland

N.C. BROWN LTD.
pacesetters in storage equipment

Send your FREE BROCHURE ☐ or Send ☐ (how many) Budget Storage Units at £17. 5s. in green or grey.

NAME
ADDRESS
Dept. PW Eagle Steelworks, Haywood, Lancs. Tel: 69018
London: 25-27 Newton St., W.C.2. Tel: 01-405 7931

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME Block
ADDRESS Caps.
Please
10/69

BRITISH NATIONAL RADIO SCHOOL

SEMICONDUCTORS BRAND NEW AND FULLY GUARANTEED

1N914	1/6	2N2904	8/-	ACY18	5/-	BD124	12/-	MJ491	89/6
1N916	1/6	2N2904A	8/-	ACY19	5/-	BF115	4/6	MPF102	8/6
1N918	3/-	2N2905	8/-	ACY20	4/-	BF117	10/6	MPF103	7/6
1N920	3/6	2N2905A	8/-	ACY21	5/-	BF167	6/6	MPF104	7/6
1N921	4/-	2N2906	8/-	ACY22	4/-	BF173	7/6	MPF105	8/-
1N925	5/-	2N2906A	8/-	ACY28	4/-	BF180	9/-	NKT0013	8/6
1N913	8/-	2N2907	8/-	AD140	8/-	BF181	8/6	NKT016	10/6
1N920	8/6	2N2907A	8/-	AD149	8/-	BF184	7/6	NKT017	8/6
1N921	8/6	2N2923	5/-	AD161	7/6	BF194	6/6	NKT261	4/6
1N930	2/6	2N2924	5/-	AD162	7/6	BFX12	5/6	NKT262	4/6
1N931	2/6	2N2925	5/6	AF114	5/-	BFX13	5/6	NKT264	4/6
1N932	2/6	2N2926	5/6	AF116	5/-	BFX29	12/6	NKT271	4/6
1844	2/4	Green	3/-	AF117	5/-	BFX30	8/6	NKT372	4/6
2G921	4/-	Yellow	2/6	AF118	12/6	BFX35	19/6	NKT274	4/6
2G922	4/-	Orange	2/6	AF124	5/-	BFX43	8/6	NKT275	4/6
2G923	4/-	2N3011	5/-	AF127	5/-	BFX44	8/6	NKT281	5/6
2G924	3/-	2N3053	6/6	AF139	7/6	BFX84	8/-	NKT403	15/-
2G925	3/6	2N3054	12/6	AF181	8/6	BFX85	10/-	NKT404	15/-
2G926	3/6	2N3055	10/6	AF186	11/-	BFX86	8/-	NKT405	15/-
2G927	3/6	2N3056	10/6	AF239	7/6	BFX87	10/-	NKT406	15/-
2G928	3/6	2N3057	4/6	AF212	8/6	BFX88	5/-	NKT407	15/-
2G929	3/6	2N3058	4/6	ASV26	5/6	BFY10	4/6	NKT408	15/-
2G930	3/6	2N3059	4/6	ASV27	5/6	BFY11	4/6	NKT409	15/-
2G931	3/6	2N3060	4/6	ASV28	5/6	BFY12	4/6	NKT410	15/-
2G999	3/6	2N3128	4/6	ASV96	5/6	BFY80	4/6	NKT478	15/-
2G100	3/6	2N3129	4/6	ASV97	5/6	BFY81	4/6	NKT479	15/-
2G101	3/6	2N3130	4/6	ASV98	5/6	BFY82	4/6	NKT480	15/-
2G102	3/6	2N3131	4/6	ASV99	5/6	BFY83	4/6	NKT481	15/-
2G103	3/6	2N3132	4/6	ASV100	5/6	BFY84	4/6	NKT482	15/-
2G104	3/6	2N3133	4/6	ASV101	5/6	BFY85	4/6	NKT483	15/-
2G105	3/6	2N3134	4/6	ASV102	5/6	BFY86	4/6	NKT484	15/-
2G106	3/6	2N3135	4/6	ASV103	5/6	BFY87	4/6	NKT485	15/-
2G107	3/6	2N3136	4/6	ASV104	5/6	BFY88	4/6	NKT486	15/-
2G108	3/6	2N3137	4/6	ASV105	5/6	BFY89	4/6	NKT487	15/-
2G109	3/6	2N3138	4/6	ASV106	5/6	BFY90	4/6	NKT488	15/-
2G110	3/6	2N3139	4/6	ASV107	5/6	BFY91	4/6	NKT489	15/-
2G111	3/6	2N3140	4/6	ASV108	5/6	BFY92	4/6	NKT490	15/-
2G112	3/6	2N3141	4/6	ASV109	5/6	BFY93	4/6	NKT491	15/-
2G113	3/6	2N3142	4/6	ASV110	5/6	BFY94	4/6	NKT492	15/-
2G114	3/6	2N3143	4/6	ASV111	5/6	BFY95	4/6	NKT493	15/-
2G115	3/6	2N3144	4/6	ASV112	5/6	BFY96	4/6	NKT494	15/-
2G116	3/6	2N3145	4/6	ASV113	5/6	BFY97	4/6	NKT495	15/-
2G117	3/6	2N3146	4/6	ASV114	5/6	BFY98	4/6	NKT496	15/-
2G118	3/6	2N3147	4/6	ASV115	5/6	BFY99	4/6	NKT497	15/-
2G119	3/6	2N3148	4/6	ASV116	5/6	BFY100	4/6	NKT498	15/-
2G120	3/6	2N3149	4/6	ASV117	5/6	BFY101	4/6	NKT499	15/-
2G121	3/6	2N3150	4/6	ASV118	5/6	BFY102	4/6	NKT500	15/-
2G122	3/6	2N3151	4/6	ASV119	5/6	BFY103	4/6	NKT501	15/-
2G123	3/6	2N3152	4/6	ASV120	5/6	BFY104	4/6	NKT502	15/-
2G124	3/6	2N3153	4/6	ASV121	5/6	BFY105	4/6	NKT503	15/-
2G125	3/6	2N3154	4/6	ASV122	5/6	BFY106	4/6	NKT504	15/-
2G126	3/6	2N3155	4/6	ASV123	5/6	BFY107	4/6	NKT505	15/-
2G127	3/6	2N3156	4/6	ASV124	5/6	BFY108	4/6	NKT506	15/-
2G128	3/6	2N3157	4/6	ASV125	5/6	BFY109	4/6	NKT507	15/-
2G129	3/6	2N3158	4/6	ASV126	5/6	BFY110	4/6	NKT508	15/-
2G130	3/6	2N3159	4/6	ASV127	5/6	BFY111	4/6	NKT509	15/-
2G131	3/6	2N3160	4/6	ASV128	5/6	BFY112	4/6	NKT510	15/-
2G132	3/6	2N3161	4/6	ASV129	5/6	BFY113	4/6	NKT511	15/-
2G133	3/6	2N3162	4/6	ASV130	5/6	BFY114	4/6	NKT512	15/-
2G134	3/6	2N3163	4/6	ASV131	5/6	BFY115	4/6	NKT513	15/-
2G135	3/6	2N3164	4/6	ASV132	5/6	BFY116	4/6	NKT514	15/-
2G136	3/6	2N3165	4/6	ASV133	5/6	BFY117	4/6	NKT515	15/-
2G137	3/6	2N3166	4/6	ASV134	5/6	BFY118	4/6	NKT516	15/-
2G138	3/6	2N3167	4/6	ASV135	5/6	BFY119	4/6	NKT517	15/-
2G139	3/6	2N3168	4/6	ASV136	5/6	BFY120	4/6	NKT518	15/-
2G140									



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 90 ft. 18 gauge on plastic reel. Recommended retail price 15/-



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 202 ft. 22 gauge on plastic reel. Recommended retail price 15/-



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	2/6*
Size 5 (Illustrated)	Savbit	18	2/6*
15	60/40	22	3/-*

*Recommended Price




INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



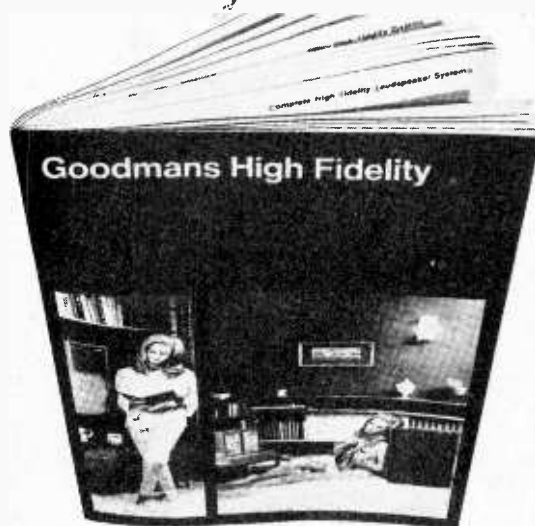From Electrical and Hardware shops. If unobtainable, write to:
Multicore Solders Ltd., Hemel Hempstead, Herts.



Thinking of High Fidelity—first read Goodman's 28 page High Fidelity Manual. It contains interesting articles on Stereo; an Introduction to High Fidelity; Stage-built systems; as well as full details of Goodman's High Fidelity audio products.

Send for your free copy

Please send me a free copy of Goodman's Manual



Name _____

Address _____

PW10

Goodmans Loudspeakers Limited
Axiom Works, Wembley, Middlesex. Tel: 01-902 1200

There is scope,
variety and
responsibility as a

RADIO TECHNICIAN

in Air Traffic Control

Join the National Air Traffic Control Service, a Department of the Board of Trade, as a Radio Technician and you have the prospect of a steadily developing career in a demanding and ever-expanding field.

Entrance qualifications: you should be 19 or over, with practical experience in at least one of the main branches of telecommunications.

Once appointed and given familiarisation training, you will be doing varied and vital work on some of the world's most advanced equipment including computers, radar and data extraction, automatic landing systems and closed-circuit television. Work is based on Civil Airports such as Heathrow, Gatwick and Stansted, Air Traffic Control Centres, Radar Stations and other specialist establishments.

Starting salary is £915 (at 19) to £1,189 (at 25 or over); scale maximum £1,372 (higher rates at Heathrow), and some posts attract shift-duty payments. *From January 1970 these rates will be increased to £985, £1,295, £1,500 respectively.* Every opportunity and assistance is given to study for higher qualifications. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Send this coupon for full details and application form:

To: **A. J. Edwards, C.Eng., M.I.E.E., M.I.E.R.E.**
Room 705, The Adelphi, John Adam Street,
London, WC2 marking your envelope 'Recruitment'.

Name.....

Address.....

PW/A2

Not applicable to residents outside the United Kingdom

NATCS National Air Traffic Control Service

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

FOR SALE

EDDYSTONE 870A Receiver used only approximately 50 hours. Completely checked by makers before being advertised. £18. o.n.o. Korn, 15 Avenue Road, Dorridge, Warks.

SEEN MY CAT? Tools, Rod, Bar and Tube, Small Screws, mechanical and electrical gear. 21-years' trading £6,000 in vouchers given away. Free Cat. of 5,000 items. S.A.E. to: K.R. WHISTON, Dept. VCW, New Mills, Stockport.

YUKAN SELF-SPRAY
Get these *air drying* **GREY HAMMER**
NOW! OR **BLACK WRINKLE**
(CRACKLE) Finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 3/-) for 18/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

307, EDGWARE ROAD, W.2
Dept. M/9 YUKAN, LONDON, W.2

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organizations—we can supply you too.

Open all day Saturday. Closed Thursday afternoons.

MORSE MADE !! EASY

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RYTEM** without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2596 send 8d. stamp for explanatory booklet to: G8CH8 (BOX 11), 45 GREEN LANE, FURLEY, SURREY

AMIOD 12 kc/s Mobile Radio telephone for sale, slightly damaged by water. £15 o.n.o. Apply: A. J. Nicol, Estate Office, Ramsey, Huntingdon.

ELECTRICAL

**240 VOLT
ELECTRICITY
ANYWHERE**

**BEST EVER 200/240 VOLT "MAINS"
SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk. 2D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvelous for Television, Drills, Power Tools Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only \$419.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW STANFORD ELECTRONICS, Rear Derby Road, North Promenade, Blackpool, Lancashire.

EDUCATIONAL



**RADIO AND TELEVISION SERVICING
RADAR THEORY AND MAINTENANCE
TELECOMMUNICATIONS**

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to:
The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5.
Tel. 01-373-8721

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV., automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies in September and January. Grants available. Day and Boarding students. Stamp for prospectus Wireless College, Colwyn Bay.

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/6 p/p 6d.
1155 set Circuit and Notes	6/6 p/p 6d.
H.R.O. Technical Instructions	5/6 p/p 6d.
38 set Technical Instructions	5/6 p/p 6d.
46 set Working Instructions	5/6 p/p 6d.
88 set Technical Instructions	7/- p/p 6d.
BC.221 Circuit and Notes	5/6 p/p 6d.
Wavemeter Class D Tech. Instr.	5/6 p/p 6d.
18 set Circuit and Notes	5/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes	5/6 p/p 6d.
CR.100/B.28 Circuit and Notes	10/- p/p 6d.
R.107 Circuit and Notes	7/- p/p 6d.
AR.88D Instruction Manual	18/- p/p 6d.
62 set Circuit and Notes	6/6 p/p 6d.
Circuit Diagram 5/- each post free, R.1118/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.	
52 set Sender and Receiver circuits 7/6 post free	

Resistor colour code Indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

BOOKS & PUBLICATIONS (continued)

SURPLUS RADIO EQUIPMENT HANDBOOK

Over 120 pages of data including circuits/operating for 40+ types; many useful mods. and valve transistor equivalents list. A must for all using ex-Government sets. Only 30/- including p. & p. from: (Mail Order Only)

SYMBOL BOOKS (Dept. 3) 210 EASTERLY ROAD, LEEDS LS8 8ER

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS CAR RADIOS)

Only 5/- each, plus large S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request.

Mail order only.

SERVICE SHEETS (continued)

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

AERIALS

BAKER and BAINES FOR TELEVISION and LOFT AERIALS

Examples of prices: FM dipole 21/-, H 38/-, BBC dipole 30/-, X 38/-, H 42/- 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/6, 11 ele 57/6, double 8 112/-, double 11 140/-, combined BBC/ITA 1 + 5 45/-, H + 5 69/-, X + 5 75/-, BBC 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, double 22 142/-, Loft special BBC/ITA 1 + 5 complete with pole and brackets 37/-, Prices include clamps and P.P. CWO, state channels please.

11 DALE CRESCENT, TUPTON, CHESTERFIELD

SITUATIONS VACANT

RADIO TECHNICIANS

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment (in Cheltenham and other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to such candidates who can also offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications. A knowledge of Electro-mechanical equipment will be an advantage.

Salary. Scale is from £915 at 19 to £1,180 at 25 (highest pay on entry) rising to £1,374. (These scales are being further increased at 1.1.70.) Posts are unestablished, but opportunities exist for establishment and also advancement to higher grades up to £2,145 with a few posts carrying still higher salaries.

Annual Leave allowance of 3 weeks 8 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

RECRUITMENT OFFICER (RT 37/54)
GOVERNMENT COMMUNICATIONS
HEADQUARTERS,
OAKLEY, PRIORS ROAD,
CHELTENHAM, GLOS. GL52 5AJ

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts, Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV SERVICE ENGINEER & Trainee for London retail business of the highest standing: estd. over 40 years: good position & prospects for suitable applicants. State age & detail of experience. Box 91.

MISCELLANEOUS

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions 19/6 C.W.O. 'Circuit-etch', 12 Cambridge Road, St. Albans, Herts.

BUILD IT in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

5% RESISTORS 3d EACH

High stability, Carbon Film, 1/4 Watt. 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91Ω . . . etc. to 1MΩ.

PRINTED CIRCUIT KITS ONLY 17/6

TRANSISTORS 2N3706A 1/6 EACH

Hfe 20-60, Vce 30, 200mW, 200 Mc/s. Brand new, fully guaranteed. P. & P. 1/-.

J. M. KING

14 Acton Street, London, W.C.1

6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at £2.19.6

post paid.

or in kit form 50/-

SALOP ELECTRONICS

23 Wyle Cop, Shrewsbury. S.A.E. for lists.

MISCELLANEOUS (continued)

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

YOUR RADIO KITS assembled for you cheaply. Professional Job. All Types Audio, Receivers, Transmitters, Radio Control etc. Box No. 92.

YOUR TRANSISTORS TESTED. 1/- each, C.W.O. To: J. A. Kinder, 6 Hooker Road, Heartsease, Norwich, Nor. 25R.

YOUR CALL SIGN ENGRAVED. White Letters Black Plate 6 x 1 1/4in. 5/6. 2 x 1/4in. Badge Pin, 4/-, Post Free. C.W.O. Workshops for Disabled, Northern Road, Cosham, Portsmouth. PO6 3EP.

MUSICAL MIRACLES, Send S.A.E. for details of Rhythm Modules, versatile bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50μA meters, 25/- post paid. HURRY. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications, PHILPOTTS METAL WORKS LTD., Chapman Street, Loughborough.

SITUATIONS VACANT (continued)

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION
- P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multimeter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL
CORRESPONDENCE
SCHOOLS

International Correspondence Schools
(Dept. 173) Intertext House, Stewarts Road,
London, S.W.8.

NAME.....
Block Capitals Please

ADDRESS

10/69

A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!

WANTED

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED NEW VALVES, televisions, radio-grams, transistors, etc. STAN WILLETT, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WANTED: New valves, transistors etc.; state prices. E.A.V. Factors, 202 Mansfield Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS-LTD
103 North Street, Leeds 7

AVO METERS, MODELS 8 & 9, ANY QUANTITY, ANY CONDITION, ALSO WEE MEGGERS. SEND FOR PACKING INSTRUCTIONS. HUGGETT'S LTD., 2/4 PAWSONS ROAD, W. CROYDON.

RECEIVERS & COMPONENTS

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 12/6 Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, W.13.

HI-FI loudspeaker systems for the home constructor, cabinet kits, the new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding, speaker fabric (samples on request) and all other necessary components. Send 5d in stamps to: AUDIOSCAN, Dept. PW, 4 Princes Square, Harrogate, Yorks.

COMPLETE RANGE of Amateur, Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

SILICON PLANAR TRANSISTORS. 100% tested and full data supplied with orders. NPN types for organ projects, 25 for £1. PNP types similar to 2N3702 and germanium similar to ACY22, 50 for £1. Post free. WESTEK, P.O. Box 7, Rickmansworth, Herts.

FET HI-FI PRE-AMP MODULE
Latest low-noise FET in special circuit. Matches ANY ceramic/Xtal PU, Xtal mike, valve pre-amp, FM tuner, etc. DIRECTLY into ANY transistor power amp. Input impedance 2 Meg. Dist. <0.2%. 25 Hz-200 kHz $\pm$ 1 dB. Power 6-15 volts.
With full instructions ONLY 25/- post free (Stereo pair 45/-). Mail order only, c.w.o.

W. T. MORRIS

1 Birch Drive, Shawbury, Shrewsbury.

NEW VHF KIT

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/-, P. & P. FREE U.K. ONLY

Postal Orders, Cheques to
Dept. P.W.2

Galleon Trading Co., 298A Lodge Lane, Romford, Essex.

RECEIVERS & COMPONENTS (continued)

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2in. x 4in. packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards, 10/-, P. & P. 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 85/-, P. & P. 7/6. With a guaranteed minimum of 350 transistors.

GIANT PANELS. 5 1/2 x 4in., min. 20 transistors, 9 x 56 μ H inductors, resistors, diodes etc. 3 for £1. P. & P. 2/-.
PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-, P. & P. 2/-.
TRIM POTS. On 2 x 4in. boards + Ta caps and other components. 100 Ω , 500 Ω , 15K Ω , 20K. State requirements. 5 boards 10/-, P. & P. 2/-.
NPN GERMANIUM TOS 1 WATT POWER TRANSISTORS. On small heat sink, on 2 x 4in. panel. 5 for 10/-, P. & P. 2/-.
POWER TRANSISTORS. Sim. to 2N174 ex eqt. On Finned Heat Sink (10D), 4 for £1. P. & P. 5/-.
ORGAN BUILDERS' SPECIAL 300 TOS TRANSISTORS + 200 SI DIODE GATES on panels. £4. P. & P. 6/-.
DIODES. Ex eqpt., Silicon, 150 PIV, 10 amp. 4 for 10/-, 150 PIV, 20 amp. 4 for £1. Post free.
OVERLOAD CUT OUTS. Panel mounting in the following values... 5/- each. 2, 3, 4, 10 amp. P. & P. 1/-.
MINIATURE GLASS NEONS, 12/6 doz. P. & P. 1/-.
PAPST FANS. Powerful Extractor/Blower fans. 230/250V. 100 c.f.m., 2,800 r.p.m. 35/-, P. & P. 5/6 ea.
MICRO SWITCHES, miniature button type. 10/- doz. P. & P. 1/6.
TOGGLE SWITCHES LONG ARM ex eqpt. SPST 13/6 doz., DPST 15/- doz., DPDT 22/6 doz. P. & P. all types 2/- doz.
NEW SPRAGUE 0-22 μ F 250V. small capacitors. 5/- doz. P. & P. 1/-.
NEW SPRAGUE ELECTROLYTICS, 4 μ F 150V. 5/- doz. P. & P. 1/-.
LARGE CAPACITY ELECTROLYTICS 4 1/2in., 2in. diam. Screw terminals. All at 7/6 Post free.
4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

KEYTRONICS 52 Earls Court Road,
London, W.8. Mail order only

QUALITY NEW VALVES

Guaranteed six months

DY86 6/8	EF80 4/9	PC97 8/-	PCL86 8/6
EABC80 6/8	EF85 5/6	PC84 9/6	PL86 10/-
EB91 8/-	EF86 6/8	PC89 9/6	PL81 9/-
EBF89 6/8	EF183 5/9	PCF80 6/8	PL804 14/6
ECC82 5/-	EF184 6/8	PCF801 7/6	PY81 5/6
ECC83 5/8	EL84 4/9	PCF802 9/6	PY800 7/-
ECC85 5/8	EY88 6/9	PCF805 9/-	PY801 7/8
ECH81 5/8	EZ80 4/6	PCL82 7/8	UCH81 7/8
ECL80 7/-	EZ81 4/9	PCL83 10/-	UCL82 7/6
ECL82 6/6	PC86 10/8	PCL84 7/6	UL84 6/9
ECL86 8/8	PC88 10/8	PCL85 8/6	UY85 6/9

SEMICONDUCTORS

AC107 4/-	AF114 4/-	BC108 3/6	OC44 2/6
AC128 3/6	AF117 3/8	BC109 3/1	OC71 3/-
AC176 5/-	AF279 9/-	BY100 3/6	2N819 8/8
AD149 7/-	BC107 8/-	OC35 6/-	2N8245 10/10

Post paid 10/- and over, under add 6d. Orders 25 and over less 5%. Full price lists valves, transistors, components on request.

J. R. HARTLEY

78B, High Street, Bridgnorth, Shropshire.

EMSAC BASIC ANTENNA SYSTEMS.
Please send SAE for comprehensive details of Antennas and Transmatchers for Receiving and Transmitting. Electronic & Mechanical Sub-Assembly Co. Ltd. Highfield House, West Kingsdown, Kent.

RECEIVERS & COMPONENTS (continued)

Video Line Amplifiers

These units contain the following useful parts. Mains trans P1a 230v Sec 250-0-250 at 80 Ma 6-3v, 3a and 6-3v 1a, smoothing choke, valves EZ80 and ECF80x2, Fuses, Toggle swt, Coax Sks complete on chassis size 8x5x2in. Good condition 32/6 plus 6/6 carr.

Leadex Switches

Coil 1k ohm, 3 pole 11 way 3 bank with motoring contact, new ex equip 7/6 plus 2/6 post.

Uni Selectors

Coil 14 ohm will work on 12v, 17 way 8 bank 4 pole alternate wipe. New ex equip. 17/6 plus 2/6 post.

High Grade Electrolytic Conds.

Made by Siemens fully isolated cases suitable for series connection, 1000 μ F 35v, 500 μ F 110v 100 μ F 250v, 50 μ F 350v, 25 μ F 350v, 16 μ F 550v all at 2/6 each plus 1/- postage, 5 or more post paid.

Coax Plug and Socket

Standard T.V. type coax plug with socket all metal plug, these are ex equip in clean condition. 6 pairs for 6/- post paid.

Silicon Diodes

Rated 800 P.I.V. at 500 mA made by Siemens these are ex equipment. 12 for 6/- post paid.

Mains Transformers

These are all 220v P1a voltages given are for 240v mains. H.T. Sec 0-420-450-480 at 250 mA and 0-375-400-425 at 250 mA C Core trans will give 900v at 250 mA 35/- plus 6/- carr.

L.T. Sec 0-1-22-23-24v at 2 amps, 20v 2a, 6-5v 5a, 6-5v 1a, 20v 250 mA open type 22/6 plus 6/- carr.

Heater Sec 6-5v at 3a, 6-5v at 1a twice 20v 250 mA 3 times open type 12/6 plus 6/- carr. Med H.T. Sec 0-70-75-80-85v at 20 mA small open type 7/6 plus 3/6 post. The above trans are all ex equip in good condition and good quality.

Blower Units

These are a twin outlet blower unit mounted in a 19in. Rack cabinet. Motor 115v 50c/s 4a 2-700 R.P.M. 2 phase type with condenser blower size each end Inlet 5in. Dia Outlet 3 1/2 x 3 1/2in. overall size 12 1/2 x 8in. Dia top class unit made for U.S.A.F. £2 10s plus 10/- carr.

A. H. SUPPLIES

57 Main Road, Darnall, Sheffield S9 5HL
S.A.E. for lists.

Open to callers Mon, Wed, Fri and Sat.

VALVE BARGAINS

Any 5-9/-, 10-14/-, 100 £5.10.0.

From the list below:-

ECC82, ECC83, ECL80, EF80, EF85, EY86, ECC84, PCF80, PCL82, PCL83, PL36, PL81, PL82, PL83, PY33, PY81, PY82, 30F5, 6-30L2, 30FL1, ALL VALVES SET TESTED. P & P 1/-

Velco Electronics, 62 Bridge Street, Ramsbottom, Bury, Lancs.

INTEGRATED CIRCUITS at lowest price GE Type PA234 1 Watt Audio Amplifier 17/6d. each incl. data. Newest GE Silicon NPN plana transistor 2N5172. Epoxy for economy Passivated for reliability. 25 volt 200 mW hfe 100 min. 1/9d. each. C.W.O. P. & P. 1/-d. per order. JEFF ELECTRONICS, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only.

PACKS of mixed 4BA and 6BA plated screws and nuts. Min. quantity of 150 items per pack. 10/- per pack incl. postage. For specific requirements send SAE. WESTEK, P.O. Box 7, Rickmansworth, Herts.

RECEIVERS & COMPONENTS (continued)

RECEIVER PANELS MW/LW. Size 8 x 3in. Six transistors, OC44, OC45 (2 off), OC81D, OC81 (2 off), 1 watt output, contains all resistors, capacitors, I.F. transformers, osc. coil and transistors but will require ferrite aerial, tuning capacitor, wavechange switch, and volume control, supplied with connecting data, as brand new, made by famous British manufacturer, ONLY 32/6 post paid.

TUNING CAPACITORS (Brand new and boxed). 345pF + 165pF with two 20pF sections for F.M. tuner, size 2 1/2 x 2 x 1 1/2in. ONLY 4/6 each or 8/- for two. 325pF + 375pF with two 20pF sections for F.M. tuner, size 2 1/2 x 1 1/2in. ONLY 4/6 each or 8/- for two.

VOLUME CONTROLS. 5k log. with S.P. switch, 1in. dia. spindle. 2/- each (new).

DISC CERAMIC CAPACITORS. 0.02mF 500v.w. wire ended, 1,800pF 1,000v.w. wire ended, 0.047 mF 30v.w. P.C. type, all 8/- doz.

Thyristors. 400 P.I.V. at 5 amp. Ideal for drill speed controls. 12/6 each.

TRANSISTORS. GT45B equiv. to OC45, OC71, etc. (BRAND NEW marked). 1/8 each, 12/- doz.

TRANSFORMERS. 250V a.c. input, 22 volts at 1 amp. output. 11/- post paid.

TAG STRIPS. 4 1/2in. long with 9 insulated tags and 2 earth tags. 4d. each, 3/- doz.

MIXED BAG. Silver mica and ceramic capacitors, approx. 150 items 10/- bag. Approx. 250 for 15/-.

5K63 SILICON DIODES. Unmarked 300 P.I.V. at 1 amp. tested 8d. each, 5/- doz.

ELECTROLYTICS. 32 + 32mF 250v.w. 2/- each.

TRANSISTOR. Single tuned 470Kc/s I.F. transformers, 1/8 each, 4 for 5/-.

VALVE. 465Kc/s I.F. transformers 1 1/2 sq. 1 1/2in. high, some 2in. high, 2/- each.

HUNTS. .25mF 350v.w. 1/2 x 1 1/2in. brand new wire, ended, 6d. each, 4/- doz.

TELEVISION mains dropper resistors—send for list. 12-7 Mc/s and 13-125 Mc/s HC6/U xtals. tested, ex-equipment, 4/6 each.

ALL ITEMS PLUS 1/6 POSTAGE UNLESS STATED. MAIL ORDER ONLY
S.A.E. FOR LISTS

A. J. H. ELECTRONICS 59 WAVERLEY ROAD, THE KENT RUGBY, WARWICKSHIRE RUGBY 71066

BRAND NEW ELECTROLYTICS, 15/16 volt, 0, 5, 1, 2, 6, 8, 10, 15, 20, 30, 40, 50, 100, 200 mfd. 8/- per dozen, postage 1/- The C.R. Supply Co., 127 Chesterfield Road, Sheffield 8.

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1969 List
available at 2/-
plus postage

If list is required
indicate with X

From
Address

enclose remittance of.....

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (October PW)

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 8/6 extra.

INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (P/W10) 169 KENSINGTON HIGH STREET, LONDON, W.8.

ELECTRAMA

FANTASTIC

SPEAKER BARGAIN
Famous English, 12" high flux, heavy cone, 10 watts speaker with built-in tweeter. 3 or 15 ohms. (P. & I. 4/9) 35/-

2 for 66/- (P. & I. 6/9)
NEW RELEASE

HI-FI COLUMN

SPEAKER CABINET

Beautifully made. Suitable for 7-12" speakers. Rose wood finish. Screwed and glued. Attractive grey cloth front measures 24" x 13" x 10" with tweeter hole above.

69/6 (Carr. 10/-)

With 12" speaker as advertised above 99/- (carr. 10/-)
1 George St., Hailsham, Sussex



Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the Amateur enthusiast and constructor. For 2 and 4 metres, the unique two transistor model SR2/P, 70-150Mc/s, 75/-, p.p. 4s. New! multi-range Pre-Amp all bands from SW to UHF (colour T/V!) No mods, fitted instantly aerial input. Write today, enclosing a stamped addressed envelope for interesting free literature, and details, direct to

JOHNSON'S (RADIO)

St. Martin's Gate, Worcester

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

IR5	5/6	DL94	5/9	EY51	7/8	PL500	12/9
IR6	4/3	DL96	6/9	EY86	5/9	PL504	13/3
IT4	2/9	DY86	5/3	EZ80	3/9	PY32	10/-
384	5/9	DY87	5/3	EZ81	4/8	PY33	10/-
3V4	5/9	EABCO80	5/9	KT61	8/3	PY81	5/-
6AC5	4/8	EB041	9/9	KT66	15/9	PY82	5/-
6L18	6/-	EBF80	6/-	N78	17/-	PY83	5/3
2516GT	4/6	EBF89	5/9	PABC80	5/9	PY88	6/6
30C18	8/6	ECC82	4/-	PC86	10/3	PY800	7/3
30FL11	13/6	ECC83	4/9	PC88	10/3	PY801	6/8
30FL12	14/3	ECC85	5/8	PC97	8/3	R19	6/3
30FL14	11/9	ECH35	5/8	PC900	7/8	U26	12/9
30F4	11/8	ECM42	10/6	PC84	6/8	U28	11/8
30F19	11/6	ECM81	5/9	PC89	9/8	U191	12/3
30PL11	13/6	ECL80	6/8	PCF80	5/11	UABC80	6/-
30PL13	14/9	ECL82	6/3	PCF801	6/8	UBC41	8/3
CCH35	9/9	ECL86	7/6	PCF805	8/6	UBF89	6/8
CL33	17/6	EF37A	6/-	PCF808	11/9	UC84	7/9
DAC32	6/9	EF39	4/6	PCL82	6/9	UC85	6/6
DAF91	4/3	EF80	4/6	PCL83	8/9	UCF80	8/-
DAF96	6/3	EF85	5/3	PCL84	7/-	UCH42	10/6
DF33	7/6	EF86	6/3	PCL86	8/9	UCH81	6/9
DF91	2/9	EF88	4/9	PCL86	8/-	UCH82	6/9
DF96	6/3	EF183	5/9	PCF20011	9	UF41	10/6
DK32	6/9	EF184	5/3	PCF8	9/3	UF89	6/6
DK91	5/6	EH90	6/-	PL81	7/-	UL41	10/3
DK96	6/6	EL33	3/3	PL82	6/9	UL84	6/9
DL35	4/9	EL41	10/3	PL83	6/9	UY41	8/3
DL92	5/9	EL84	4/9	PL84	6/9	UY85	5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS.

Indicator Unit Type 26, Size 12 x 9 x 9in. With Outer Case fitted with 2 1/2in. CRT Type CV1526 9 B7G Valves. Clean condition but not tested. 32/6, p. & p. 10/-.

Aircraft Sighting Head with Gyro Unit complete with Transit Case. Condition fair. 18/6, carriage B.R.S. 12/-.

Oscillator Type 37. Complete with AC230 Volt Power Pack, Circuit and Grid Ref. Map condition good 37/6, carriage B.R.S. 12/-.

N.S.F. Toggle Switches D.P.D.T. Ex Units 1/-, post 1/-; 12 for 10/- post paid.

Ex Washing Machine Motors. Single phase 230 volt 1425 R.P.M. All perfect 26/-, post and packing 10/-.

New 12in. Speakers with built in tweeter 3 ohm and 15 ohm 6 watts max. 28/6, post paid.

Speakers removed from T.V. Sets. All PM and 3 ohm. 6in. round 3/-, p. & p. 3/-; 6 for 24/- post paid. 6 x 4in. 3/-, p. & p. 3/-; 6 for 24/-, post paid. 5in. round 3/-, p. & p. 3/-; 6 for 24/- post paid. 7 x 4in. 5/-, p. & p. 3/-; 6 for 34/- post paid. Slot Speakers 8 x 2 1/2in. 5/-, p. & p. 3/-; 6 for 30/- post paid.

Reclaimed T.V. Tubes, with 6 months' guarantee 17in. Type AW43/80, AW43/88 40/-, MW43/69 30/-, 14in. Type 17/- All Tubes 12/- carriage. T.V. Tubes as above with slight scratch on face £1 each. Carriage 12/-.

Silicon Rectifier 500 MA 800 PIV. 2/6 post paid. 24/- per dozen post paid.

Jap Earpiece. Magnetic 8 ohm. Small and Large Plug 1/11 post paid.

G.P. Diodes 3/6 per dozen, post paid.

Top Grade Mylar Tapes. 7in. Standard 11/6. 7in. Long Play 14/-, 7in. Double Play 19/6. 5in. Standard 7/9. 5in. Long Play 10/- plus post on any tape 1/9.

VALVE LIST—Ex Equipment, 3 months guarantee
Single Valves Post 7d., over 3 Valves p. & p. paid

AR12	1/6	PCL82	4/-	6B8	1/8
EB91	9d	PCL83	5/-	6BW7	2/6
EP85	2/-	PL36	5/-	6K7	1/9
EPF80	3/-	PL38	5/-	6U4	5/-
ECC81	3/-	PL81	4/-	6P28	5/-
ECC82	3/-	PY33	5/-	10P13	2/6
ECC83	3/-	PY81	1/8	185BT	8/6
ECC85	4/-	PY82	1/8	20D1	3/-
ECL80	1/6	PZ30	5/-	20P1	5/-
EF50	1/-	U191	5/-	20P3	2/6
EF80	1/6	U281	5/-	30PL1	5/-
EF91	9d	U282	5/-	30P12	5/-
EY86	5/-	U301	5/-	30P5	2/6
PC084	2/-	U329	5/-	30P11	5/-
PCF80	2/-	U251	5/-	6/3012	5/-

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/6. No C.O.D. orders accepted.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANgham 8403
Open all day Saturday

0A3	6/8	6AT6	5/-	6DK6	8/6	9BW6	8/6
0A3	9/-	6AU4GTA		6DQ6B	12/-	10C2	10/-
0B2	6/6			6D84	15/-	10D1	8/-
0B3	10/-	6AU5GT		6E8A	11/-	10D2	8/-
0C3	7/6		22/8	6EH7	6/6	10P1	18/-
0D3	8/6	6AU6	5/-	6EJ7	7/-	10P9	10/-
1B3GT	7/6	6AV5GTA	6F1	14/-	10F18	8/-	
1L4	3/6		13/-	6F6G	5/-	10L1	8/-
1N5GT	8/6	6AV6	6/-	6F11	6/6	10LD11	11/-
1Q5GT	10/-	6AW8A11/-		6F12	4/6	10P13	11/-
1R4	6/6	6AX4GTB		6F13	7/-	10P14	20/-
1R5	7/6		9/-	6F14	12/-	12AB5	10/-
1S4	5/6	6AX5GT		6F15	11/-	12AC6	7/6
1S5	5/6		13/-	6F18	8/-	12AD6	7/6
1T4	4/6	6BA6	4/6	6F22	6/6	12AH7GT	
1U4	6/6	6BB6	5/-	6F23	15/6		
1U5	9/6	6BP5	16/-	6F24	13/6	12AL5	5/-
1V9	9/6	6BR6	9/-	6F25	15/-	12AM6	5/-
1X2B	7/6	6BGG	12/-	6F26	7/-	12AT6	5/-
2CW4	12/-	6BHG	8/6	6F28	14/-	12AT7	6/6
2D21	6/6	6BJ6	8/6	6F29	6/6	12AU6	5/-
3A3	11/-	6BK4	21/-	6F30	7/-	12AU7	6/6
3A4	4/6	6BK7A10/-	6/4	9/6		12AV6	6/6
3A5	10/-	6BL7GTA		6JGT	9/6	12AV7	9/6
3ASGT	10/-		19/-	6J7	9/6	12AX4GTB	
3Q4	8/6	6BL8	7/-	6K6	10/-		
3Q5GT	8/6	6BN4	13/-	6K7	6/6	12AX7	7/6
3B4	7/6	6BN5	8/6	6K8G	6/6	12AY7	13/6
3V4	8/6	6BN6	8/6	6K23	10/-	12BA4	10/-
5R4GY	11/-	6BQ5	9/6	6K25	15/6	12BA6	6/6
5U4G	6/6	6BQ6GT		6L6GT	9/-		
5U4GB	7/6		13/-	6L7	6/6	12BE6	6/6
5V4G	8/6	6BQ7A	7/6	6L18	6/6	12BH7	7/6
5Y3GT	6/6	6BR7	17/6	6LD20	6/6	12BY7	10/-
5Z3	9/6	6BR8	13/-	6NTGT	7/-	12C8	6/6
5Z4G	7/6	6BR7	26/-	6P1	12/-	12CU6	15/-
5Z4GT	8/6	6BW4	18/-	6P28	12/6	12F5GT	6/6
6J0L2	15/-	6BX7	13/6	6Q7	7/6	12K5	10/-
6A8G	6/6	6BX6	5/-	6R7G	7/-	12K7GT	7/-
6A3A	8/6	6B26	6/6	6R2	8/-	12K8	10/-
6AC7	4/6	6C4	6/6	6R47	7/6	12Q7G	5/-
6AF4A	9/6	6CBGT	7/6	6R67	6/6	12R67	5/-
6AG7	7/6	6C3	17/6	6R7	7/6	12RGT	7/-
6AH6	10/-	6CA4	5/6	6R87	6/6	12SH7	5/-
6AJ7	5/6	6CA7	10/6	6R17GT	6/6	12SJ7	5/-
6AK5	6/6	6CB6	5/6	6RNTGT	6/6	12SK7	8/-
6AK6	11/6	6CD6GA		6RQ7	8/-	12SL7GT	
6AL3	8/6		23/-	6R87	7/6		
6AL5	8/6	6CG7	9/6	6T8	6/6	12SN7GT	
6AM5	5/6	6CH6	11/-	6U4GT	12/6		
6AM6	4/6	6CL10	10/-	6U8	7/-	12RQ7	6/6
6AQ5	6/6	6CU6	13/6	6V6GT	6/6	12R7	6/6
6AQ6	10/-	6CW4	12/6	6X4	5/-	1487	18/-
6AR5	6/6	6CY5	8/6	6X5GT	9/6	20D1	10/-
6AR6	6/6	6CY7	12/6	6X3	11/-	20L1	20/-
6AS5	2/6	6D3	8/6	6Y6G	12/-	20P1	10/-
6AS7G	10/-	6DC6	13/6	6Z4	5/6	20P3	12/-

First Quality Fully Guaranteed



ELECTRONIC VALVES

20P4	20/-	85A2	7/8	E55L	55/-	ECL82	6/6
90AG	48/-	E130L	9/6	ECL83	12/6	EY81	8/-
28C5	9/-	90AV	48/-	E180F	19/-	EY83	11/-
251AGT	7/6	90C1	15/-	E280	5/-	EY84	11/-
252AG	6/-	90C5	25/-	EAB30	6/6	EZ80	5/6
2526GT	12/-	90CV	25/-	EAF42	10/-	EY87	8/6
30A5	8/-	807	9/6	EAF901	9/6	EY88	8/6
30A5	8/-	868A	14/-	EBC35	9/6	EZ35	5/6
6080	27/6	EBC41	10/6	EF41	12/6	EZ40	9/6
30C15	15/-	EBC81	6/6	EZ41	14/-	EZ41	9/6
30C17	16/-	EBC90	5/6	EZ50	5/6	EZ81	5/6
30C18	15/-	EBC91	6/6	EF80	5/6	EZ90	5/6
30P5	17/-	6360	25/-	EF80	5/6	FW4/500	
6939	42/-	EFP83	8/6	EF85	7/-		
30PL12	18/6	EFP85	6/6	EF86	6/6		
30PL13	10/-	EFP86	6/6	EF89	5/6		
30PL14	15/6	EFL31	25/-	EF91	4/6		
30L1	7/-	9003	10/-	EF92	7/6		
30L15	17/-	AZ31	10/-	EF93	4/6		
30L17	17/-	CB11	17/-	EF94	5/-		
30P12	16/-	CB131	17/-	EF95	6/6		
30P18	7/6	CL33	17/6	EF96	4/6		
30P19	15/6	CG31	7/-	EF97	10/-		
30PL1	15/6	DAF41	11/-	EF183	6/6		
30PL13	18/-	DAF91	5/-	EF184	7/-		
30PL14	17/6	DAF92	9/6	EF800	20/-		
35A3	10/-	DAF96	7/6	EF804	20/-		
35A5	11/-	DC90	9/-	EF811	15/-		
35B5	13/-	DP96	9/6	EF812	15/6		
35C5	7/-	DK40	10/-	EF814	13/6		
35D5	13/-	DK91	7/6	EF815	13/6		
35L6GT	9/6	DK92	9/-	EL34	10/6		
35W4	5/-	DK96	8/6	EL36	9/6		
35Z3	11/-	DL91	5/6	EL38	27/6		
35Z4G	6/6	DL92	7/-	EL41	11/-		
35Z5GT	7/6	DL93	4/6	EL42	11/6		
50A5	13/-	DL94	8/-	EL43	10/-		
50B5	7/-	DL95	8/-	EL48	8/8		
50C5	7/-	DL96	7/6	EL49	5/6		
50C6GT	8/6	DM70	8/6	EL50	9/6		
50C7	8/6	DY70	12/-	EL58	8/6		
50L6GT	8/6	DY86	6/6	EL68	8/6		
83A1	14/-	DY87	7/6	EL90	6/6		
85A1	25/-	DY87	7/6	EL91	5/6		
		DY802	10/-	ECL81	8/6		

EL360	22/-	PCC85	8/-	PL500	15/-	U801	20/-
EL803	17/-	PCC88	12/-	PL504	16/-	UABCS8	6/6
EL821	11/-	PCC89	10/6	PL509	20/6	UAF41	10/6
EL822	18/-	PCC189	11/-	PL608	17/6	UAF42	10/6
EL880	17/-	PCC808	17/-	PL601	16/6	UB41	11/-
EM34	18/-	PCC806	17/-	PL602	14/6	UBC81	9/6
EM71	12/6	PCC800	15/-	PL610	11/-	UBC81	9/6
EM80	8/6	PCF80	6/6	PM84	9/6	UBF80	7/6
EM81	8/6	PCF82	6/6	PX4	20/-	UBF89	7/6
EM84	7/6	PCF84	9/-	PX25	20/-	UBL1	10/6
EM87	11/-	PCF86	11/-	PY31	5/6	UBL21	12/6
EN91	6/6	PCF87	10/6	PY32	11/6	UC92	8/6
EY61	8/-	PCF800	15/-	PY33	12/6	UC95	8/6
EY80	9/-	PCF801	10/-	PY80	6/6	UCF80	10/6
EY81	8/-	PCF802	10/-	PY81	6/6	UCH21	11/6
EY83	11/-	PCF805	15/-	PY82	6/6	UCH42	13/6
EY84	11/-	PCF806	18/-	PY85	7/6	UCH43	13/6
EY88	8/6	PCF808	18/-	PY88	8/6	UCH81	6/6
EY87	8/6	PCH300		PY800	20/-	UCL41	11/-
EY88	8/6			PY800	10/-	UCL42	7/6
EZ35	5/6	PCL30	15/-	PY801	10/-	UCL83	12/6
EZ40	9/6	PCL81	10/6	QV02	6/6	UD143	15/6
EZ41	9/6	PCL82	7/6			UP9	11/-
EZ50	5/6	PCL83	13/6	QV03	10/6	UP9	11/-
EZ81	5/6	PCL84	8/6	QV03-30A		UF41	10/6
EZ90	5/6	PCL85	9/6	UF42	12/6	UF43	12/6
FW4/500		PCL86	9/6	UF43	11/6	UF43	11/6
GS47X	12/6	PCL87	17/6	UF80	7/6	UF80	7/6
GY501	18/-	PCL800	18/6	UF85	8/6	UF85	8/6
GZ30	7/6	PCL801	15/6	UP89	7/6	UP89	7/6
GZ31	6/6	PEN400		QV03-12		UL41	12/6
GZ32	9/6	PEN41	12/6			UL84	6/6
GZ33	18/6	PEN36C		SP41	7/6	UM4	8/6
GZ34	11/6	PEN45	12/6	SP42	12/6	UM84	4/6
HABCS8	6/6	PEN45D		SP81	7/6	UY1N	10/6
HBC91	6/6	PEN45D		SU2150A		UY1	11/6
HP93	6/6	PEN45	15/-	T721	15/6	UY21	11/6
HP94	6/6	PEN46	7/6	U71	48/6	UY41	8/6
HP90	6/6	PEN383		U18/20	13/6	UY82	10/6
HL92	7/6	U20	12/6	U20	13/6	UY85	8/6
HL94	8/6	PEN384		U25	15/6	VP23	6/6
KT66	27/6	U26	15/6	U26	15/6	VP41	7/6
KT68	33/6	U31	9/6	U31	9/6	VP133	15/6
ME140028		PEN453DD		U37	30/6	VR105/30	
MSFNT		U50	6/6	U50	6/6	VR150/30	
MY12/14		U52	6/6	U52	6/6	VR150/30	
N78	8/6	PF86	11/6	U76	5/6	VU33	10/6
PABCS8	8/6	PF818	17/6	U78	6/6	VU39A	10/6
PL81	9/6	PFL200	14/-	U81	13/6	VU111	10/6
PL82	13/6	PL36	11/6	U91	15/6	VU120	15/6
PC88	13/6	PL81	9/6	U91	15/6	VU133	10/6
PC97	9/6	PL82	8/6	U92	8/6	W729	12/6
PC900	9/6	PL83	8/6	U93	11/6	Z309	10/6
PC984	7/6	PL84	7/6	U403	10/6	Z319	55/6
		PL302	15/6	U404	7/6	Z329	17/6

INTEGRATED CIRCUIT AMPLIFIERS

- CA3005 RF Amplifier with 100mc/s bandwidth. Max. dissipation 26mW. For use as RF amplifier, balanced mixer, product detector or self-oscillating mixer 27/-
- CA3012 wide Band Amplifier (up to 20mc/s), suitable as IF Amplifier for VHF/FM receivers 22/-
- CA3020 General Purpose Audio Amplifier of 550mW output 30/-
- CA3038 Buffer amplifier consisting of two 'super-alpha' pair of transistors suitable for stereo pick-up systems 19/- The above four I.C.'s are in TO5 encapsulation.
- PA222 Audio Amplifier providing a max. output of 1.2 watts 65/-
- PA234 Audio Amplifier providing a max. output of 1 watt 27/6
- PA237 2 watts Audio Amplifier 40/-
- The above three I.C.'s are in epoxy moulded double four-in-line package.
- MC1709CG General Purpose operational amplifier in TO-99 case 40/-
- TAA283 3-stage direct coupled amplifier for use from DC to 600kc/s; 70mW dissipation. Output 10mW into 150 Q load 15/-
- TAA283 3-stage amplifier with connection brought out to the individual leads. Bandwidth 600kc/s. 160mW dissipation. Output 10mW into 150 Q load 20/-
- TAA280 MOST input stage followed by a bi-polar transistor stage. 200mW dissipation. 13/-

Data sheets are available for all the above I.C.'s.

OUR NEW CATALOGUE 1969/1970 IS NOW READY. IT INCLUDES PRICES OF SOME 4,000 TYPES OF VALVES AND TUBES AND SEMICONDUCTORS. ESSENTIAL CHARACTERISTICS OF KLYSTRONS, MAGNETRONS, CATHODE RAY TUBES AND SEMI-CONDUCTORS ARE GIVEN. THIS IS A REAL REFERENCE BOOKLET AND IS AVAILABLE FREE OF CHARGE. PLEASE ENCLOSE QUARTO S.A.E.

WESTINGHOUSE EPOXY ENCAPSULATED WIRE ENDED MINIATURE RECTIFIERS
1N5399, 1,000 p.i.v., 1.5 amps D.C.; Max. surge 50A diameter .140in. Overall length (with leads) 2.3in. 4/6.
1N5408, 1,000 p.i.v., 3 amps D.C.; Max. surge 200A. Diameter .210in.; overall length (with leads) 2.875in. 6/6.

MULTIMETERS



TYPE MF16
D.C. voltage range:
0-0.5-10-50-250-500V.
A.C. voltage range:
0-10-50-250-500V.
D.C. current

VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications—Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elem.
Electrical Science — Elec-
trical Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work—Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun E., CITY & GUILDS, GEN. CERT.
OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT
CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds (Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy now—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES


SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT

Mono or Stereo Audio, Equipment developed from Dinsdale Mk II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM


£15.5.0

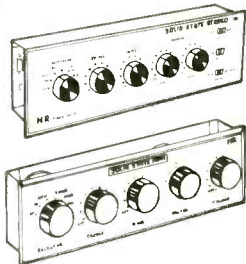THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS



All units available separately.

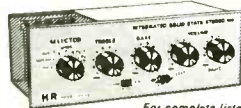SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



MA7 MONO
£8.10.0

OR THE STEREO
POST PACKING 5/-
EITHER MODEL

INTEGRATED TRANSISTOR AMPLIFIERS

MA66 12 WATTS STEREO

We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways—with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.

For complete listening satisfaction choose either these—

MA66

£16.10.0 OPTIONAL MAINS UNIT

PS20 62/6d. p.p. 4/-

Illustrated leaflets 12 and 14 FREE on request.

PORTABLE GEIGER COUNTERS



FOR MEASUREMENT OF RADIO-ACTIVITY
Supplied complete with instructions, haversack, cables and probe. List price £70. **OUR PRICE, NEW, TESTED COMPLETE WITH BATTERIES £7.10.0**
POST 10
SPARE BATTERIES 15/- PAIR POST 5




NEW MODELS NOMBREX TRANSISTORISED Test Equipment

PRICE Leaflet

MODEL	£	s	d	0	35
29s RF Gen.	21	0	0	0	35
29x Xtal RF Gen.	28	10	0	0	35
30 Audio Generator	19	10	0	0	24
31 R.F. Generator	12	10	0	0	25
32 C.R. Bridge	10	10	0	0	26
33 Inductance Bridge	20	0	0	0	29

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDART. This comprises a special, high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED

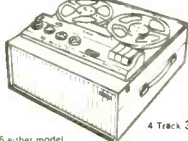

4 Track 39 gns.

P.P. 22/6 each model
Kit comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1 200 ft tape, spare spool
ALL UNITS AVAILABLE SEPARATELY.
ASK FOR BROCHURE 6

Today's Value £60.

VHF FM SUPERHET TUNER MKII

'S' MULTI-TRANSISTORS & 4 DIODES - 300 KC/S BANDWIDTH - PRINTED CIRCUIT CONSTRUCTION - HIGH FIDELITY REPRODUCTION MONO AND STEREO
A popular VHF FM Tuner now used throughout the country for quality reception of mono and stereo, with the decoder stereophonic broadcast. There is no doubt about it—VHF FM gives the true 'real sound'. Excellent stability, excellent sound, excellent value. PARTS TOTAL COST £6.19.6.
DECODER £5.19.6 (CABINET 20/- EXTRA) ASK FOR LEAFLET 3.



MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY WRITE TO US (on Company Headed Newspaper please) requesting our SEMI-CONDUCTOR BULLETIN. For TELEPHONE QUOTATIONS, PHONE (01) 723-1008 9 a.m. to 5 p.m. (01) 723-0401 1 p.m. to 4 p.m.
We purchase medium to large quantities of Transistors and Devices excess to Manufacturers and Distributors requirements.
Write or phone 723-0401 extn. 4.

ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS

Acclaimed by everyone

The MAYFAIR


A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuits panel, special fully sprung and depth of touch actuated keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service.



THE MAYFAIR 99 GNS BROCHURE 9

The GROSVENOR

is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises two four-octave (48 note) keyboards and a thirteen-note pedal board. It has four pitches (i.e. 8ft, 4ft, 2ft, 1ft) on the upper or solo keyboard three pitches (i.e. 16ft, 8ft, 4ft) on the lower or accompaniment keyboard two pitches (i.e. 16ft, 8ft) on the pedal board. Variable sustains on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and kit sections are available separately including the Oak Console at £65.18.0.

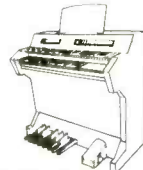

THE GROSVENOR KITS FROM £220 terms available. BROCHURE 9B

A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service and advice freely available. Once built the 'MAYFAIR' or 'GROSVENOR' will then provide hours of enjoyable entertainment. Call in—See them for yourself.

PRACTICAL ELECTRONICS—ELECTRONIC ORGAN KIT

We are able to supply Parts as described in this series. Details on request.

ORGAN COMPONENTS: COMPLETE RANGE IN STOCK - 49 AND 61 NOTE KEYBOARDS 2 10S AMP GOLD CONTACTS COILS AND CHOKES REVERBERATION SPRINGS AND UNITS STOP TABS AND ASSEMBLIES PEDAL BOARDS RHODIUM AND GOLD WIRE WELD PRINTED CIRCUITS ETC. COMPLETE RANGES FOR TRANSISTORISED ORGANS. ASK FOR NEW PRICE LISTS WITH DETAILS. LEAFLET 9B. ALL ENQUIRIES TO ORGAN DEPT. MR. ELVINS

GRAVINER FIRE DETECTOR UNIT



The Detector Unit consists of a highly sensitive 931A photo-electric cell combined with a firing circuit incorporating a single cold cathode electronic relay, capacitors and resistors designed to fail to safety if external wiring is open or short circuited. Encapsulated in a resin which fully insulates the unit electrically and provides a high degree of mechanical and thermal shockproofing. Original price £75. **OUR PRICE, BRAND NEW £5 each, with date sheet**
Limited quantity available.


SCOOP! STARR RECORD PLAYER

Deck. Plays 33, 45, 78 records, 9 volt operated. With mono cartridge. Brand new. As illustrated. 58/6 post 3/6.
MULLARD 1 WATT AMPLIFIER 9 volt, 5 transistor unit complete with volume control. Output to 3 ohms. Ideal for use with Starr record Deck. 45/- post 3/-. Send for leaflet 2.




NEW—MALLORY LONG LIFE MERCURY BATTERIES

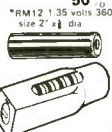50% OFF LIST PRICES
*RM12 1.35 volts 3600 m/AH size 2 1/8 dia.
*RM25 1.35 volts 350 m/AH Pack of 8 Size 2 1/8 dia.
OUR PRICE 10/- each
Easily split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required.
QUANTITIES AVAILABLE.



GARRARD RECORD DECKS

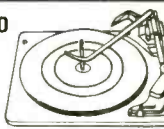BRAND NEW
All below list price £ s d
2025 Mono/Stereo GKS 25 8 8 0
3000LM Mono/Stereo 9 16 6



SP25 Mk II	9 16 6
AT60 Mk II	13 0 0
AP76	13 0 0
SL55	11 19 6
SL65	14 14 0
SL75	28 0 0
SL95	35 0 0
A70 Mk II	12 12 0
B.S.R. UA25 Mono	5 19 6
MA65	9 19 6
MA70	12 12 0
MA75	15 5 0
401 Garrard	28 10 0

Carriage/Packing 7/6d. all models
Complete range of accessories available
Send for New 8-page brochure 16 17

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY. (list 36)


S.C.R.'s from 5/-
Field Effect Transistors from 7/6
Power Transistors from 5/-
Diodes and Rectifiers from 1/6

Hi-Fi equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE ROAD AND SAVE UP TO £400 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE for all leading makes

AMPLIFIERS
TUNERS
DECKS
SPEAKERS
MICROPHONES
TEST EQUIPMENT
HEADPHONES
CARTRIDGES, etc.

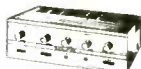All with Terrific Savings
It will PAY YOU to pay us a VISIT!



COMPLETE SYSTEMS from £46—Saves £12.10.0!
Send for new 8-page illustrated Hi-Fi list 16/17.

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10/- worth discount vouchers
FREE WITH EVERY COPY
* 32 pages of transistors and semi-conductor devices, valves and crystals.
* 210 pages of components and equipment.
* 70 pages of microphones, decks and Hi-Fi equipment.



6,500 ITEMS

320 BIG PAGES

Send today 7/6 Post etc 2/-

HENRY'S RADIO LTD

OPEN MON-SAT. 9 a.m.-6 p.m. THURS. 9 a.m.-1 p.m.



303 Edgware Road, London, W.2. Mail Order Dept.
all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-0963