


PRACTICAL WIRELESS

DECEMBER
1970

316
(17½ new
pence)

Double Conversion Amateur Bands

RECEIVER

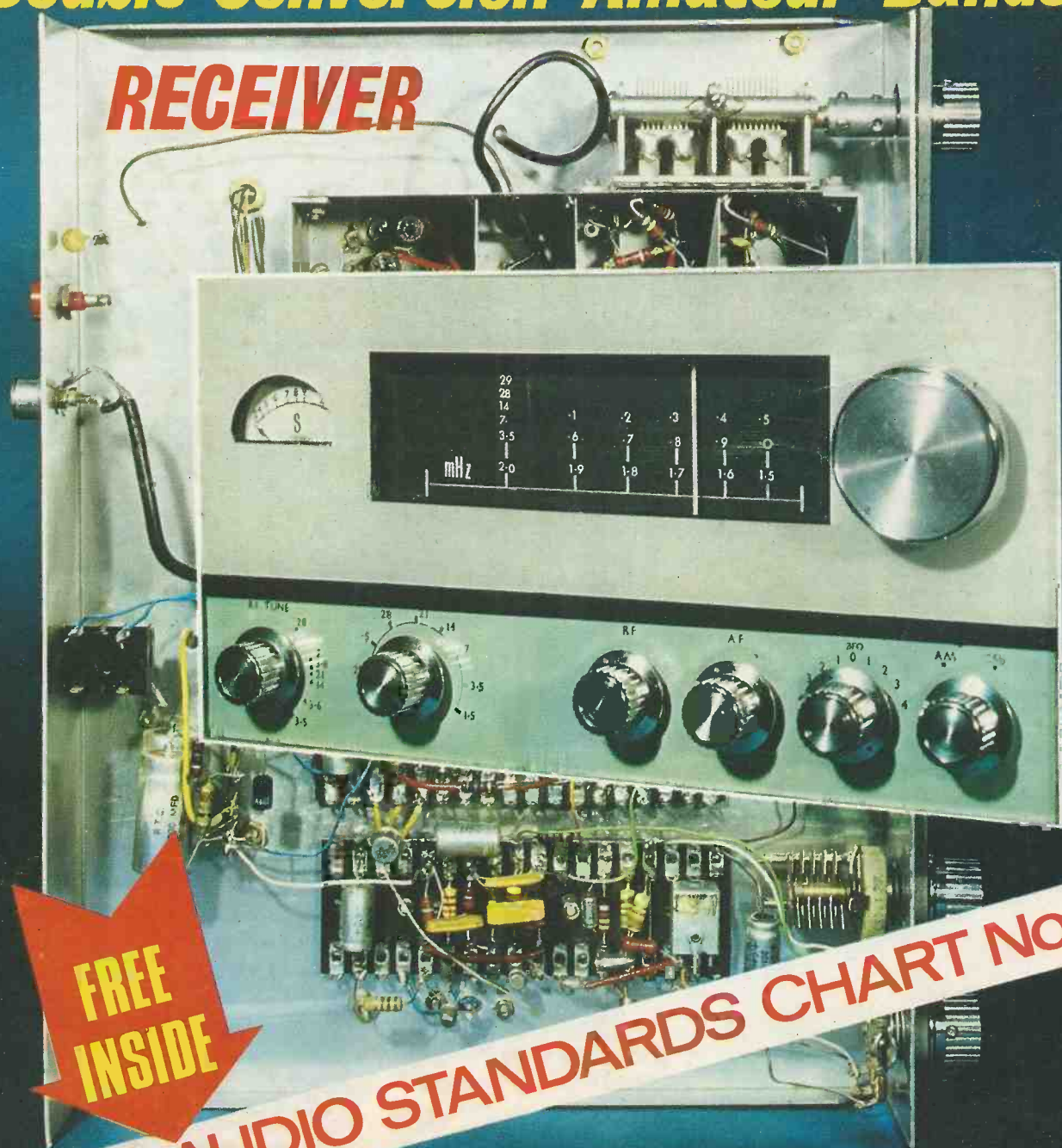

FREE
INSIDE

AUDIO STANDARDS CHART No.1

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits

(illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

*
Write for
price list
and
catalogue

JACKSON BROTHERS


have acquired the manufacturing rights of

WAVEMASTER

VARIABLE CAPACITORS



'Wavemaster' variable capacitors have brass vanes and a single ceramic end plate. All have .248" spindles, extended both ends for ganging by means of our Universal Couplings. All are designed for S.W. working and for one hole fixing. 6mm spindles to order if required. Various capacitances. Largest vane packs 300 pF .017 air gap, 50 pF 0.64 air gap.

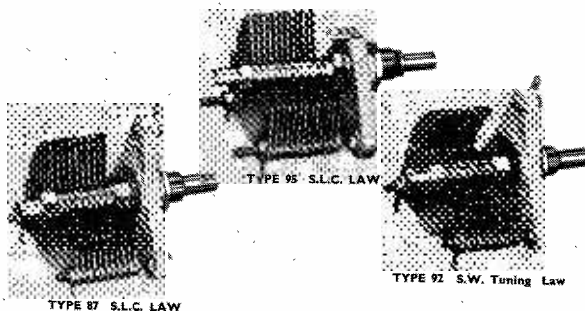

Type 87
S.L.C. Law
Plain bearings $\frac{3}{16}$ "
fixing bush. Front
area $1\frac{1}{2}$ " w. x $1\frac{1}{2}$ " h.

Type 95
S.L.C. Law
Ball bearings $\frac{7}{16}$ "
dia. fixing bush.
Front area $1\frac{1}{2}$ " w. x
 $1\frac{1}{2}$ " h.


Type 92 Modified
S.L.C. Law
(S.W. Tuning)
Plain bearings $\frac{3}{8}$ " dia.
fixing bush. Front
area $1\frac{1}{2}$ " w. x $1\frac{1}{2}$ " h.

JACKSON BROTHERS (London) LTD

Kingsway, Waddon, Croydon, CR9 4DG. 'Phone: 01-688 2754-5
U.S. Office:- M. Swedgal, 258 Broadway, New York. N.Y. 10007

PHOTOELECTRIC KIT

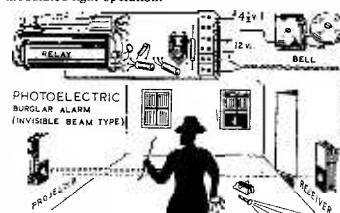CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT

39/6

Postage and Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".

Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

knight-kits

FANTASTIC LOW PRICES!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 7/6 CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

KG-865 50 Watt Stereo Amplifier Kit

DELUXE FEATURES

All Silicon Transistors for Stability, Cleaner Sound ● Extremely Wide Power Bandwidth and Frequency Response ● 50W I.H.F. Power Output ● Specially Selected Low-Noise Preamp Transistors ● Two Printed Circuit Boards for Fast Easy Assembly ● Convenient Front-Panel Stereo Headphone Jack ● Teak-finished Extruded Aluminium Front Panel ● Two A.C. Convenience Outlets



● Output: 50W I.H.F., 25W per channel; 34W continuous sine wave ● Response: $\pm 1\text{dB}$, 18 to 30,000Hz ● Output Impedance: 4 through 16ohms, plus stereo headphones ● T.M. Distortion: under 1% at 60Hz and 7,000Hz mixed 4:1 at rated power ● Input Sensitivity: Magnetic Phono, 5mV; Tuner and Auxiliary, 500mV ● Power Requirement: 230-250V, 50Hz a.c.

Recommended List Price £34.19.6: 24 GNS. Assembled 29 GNS. Teak Case £5 extra

ALL SILICON TRANSISTORS

The NEW KG-980 Stereo FM Receiver Kit

Designed to Satisfy the Most Critical Listener



R.F. and I.F. Panels Assembled and Aligned ● Front Panel Stereo Headphone Jack and Speaker Muting Switch ● Full Controls including Tape Monitor ● 50W I.H.F. Output ● Usable I.H.F. Sensitivity: 3 μV ● Frequency Response: $\pm 1\text{dB}$, 30 to 15,000Hz ● Harmonic Distortion: less than 1.0% ● A.M. Suppression: more than 30dB ● Channel Separation: 30dB ● Complimentary Transformers ● Power Output: 50W I.H.F. (25W per channel); 34W continuous sine wave ● Frequency Response: $\pm 1\text{dB}$, 18 to 30,000Hz ● Power Bandwidth: 20-20,000Hz at 1% harmonic distortion ● Two R.F. Stages ● Stereo indicator light. Recommended List Price £42.19.6: 39 GNS. Assembled 49 GNS. Teak Case 5 GNS. Extra.

KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests


Its several testers in one . . . do all this

Set Engine Idle and Automatic Transmission Shift Points ● Detect Condition of Point Surfaces ● Detect Distributor Wear ● Check Voltage and Current Regulators ● Check Generators for both Current and Voltage Output ● Find Poor or Open Earth Circuits ● Detect Variation in Dwell Angle. Recommended List Price £23.17.6: 16 GNS. Assembled Price: 21 GNS.



KG-625 Deluxe 6in Vacuum Tube Volt Meter Kit

Huge 6in Meter Scale ● Ranges: a.c. 0-0.5-1.6-6-15-50-100-500-1,500V full scale. ● Accuracy: $\pm 3\%$ of full scale reading ● Input Resistance: 11M Ω to 1,500V ● Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale. ● Accuracy: $\pm 5\%$ ● Frequency Response: 1dB, 30Hz to 3MHz; $\pm 3\text{dB}$, 30Hz to 5MHz ● Ohmmeter Ranges: 1-1,000-10,000 ohms; 0-1-10-100-1,000M Ω ● Battery 11V U2. Recommended List Price £24.19.6: 12 GNS. KG 625 as KG 625 (same Ranges) but 4in Scale: Recommended List Price £18.5.6 9: 3NS.

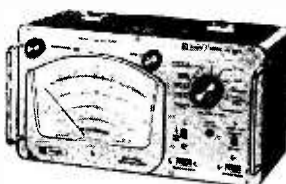

WHY NOT BUY THE PAIR?

KG-371 Deluxe Solid-State Timing Light

Performance surpasses assembled units costing much more

Helps Set Ignition Timing ● Checks Synchronisation of Double Breaker Arms ● Checks for Sticking Automatic Spark-Advance Mechanism ● Checks Distributor Cam Wear ● Built-in D.C. Power Supply ● Reliable Solid-State Circuit ● Your car gives more miles per gallon; improved performance; Greater reliability. Recommended List Price £12.10.0: 9 GNS. Available Assembled Only.



100-in-1 Electronic Science Lab

LOOK AT THE PROJECTS YOU CAN BUILD

Electronic Scale ● Electronic Timer ● Signal Generator ● Hybrid Light Meter ● Signal Injector ● Morse Code Buzzer ● Electronic Cat ● Metronome ● Code Flasher ● CW Monitor ● Ohmmeter ● Boat Horn ● Hybrid Radio ● Hybrid Voice Relay ● Air-Powered Radio ● Polarity Checker ● Valve Checker. Includes: ● Dual Headset ● Photocell ● Speaker ● Meter ● Aerial ● Transistors. Recommended List Price £16.8.0: 9: 3NS.



KG-640 20,000 ohms/Volt VOM Kit

BIG PROFESSIONAL SIZE 62 RANGE MULTIMETER ● A.C. Volts (12 Ranges): 0-2-4-8-16-40-80-300-400-800-1,500-2,000-4,000V ● D.C. Volts (12 Ranges): 0-0.8-1-2-3-16-40-80-400-800-1,600-2,000-4,000V ● Output Volts (8 Ranges): 0-2-4-8-16-40-80-200-400V ● Resistance (8 Ranges): 0-1,000-100,000 ohms-10 megs. Centre scales at 12, 1,200 and 120K Ω ● D.C. Current (10 Ranges): 0-80-160-400-800 μA 8-16-200-400mA 8-16A ● Decibels (12 Ranges): -12 to +74 ● D.C. Sensitivity: 20,000 ohms per volt or 10,000 ohms per volt (function of scale multiplier switch). ● Frequency Response: 20Hz to beyond 200kHz ● Accuracy: D.C. 3%, A.C. 5% ● Test Leads: one red, one black, each 48in long ● Multiplier Resistors: All 1% carbon film. Recommended List Price £16.19.6: 9: 3NS. Assembled Price 12 GNS.



JASON TAPE

We offer you fully tensilised polyester/nylon and P.V.C. tapes of identical quality hi-a, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more pence than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Postage 1/- reel. Post free less 5% on three reels. Quality and Trade enquiries invited. NOTE. Large tape stocks at all branches.

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rodgers, Truvox, Ferrograph, Wharfedale, etc., etc.

TECHNICAL TRADING

- All Mail Orders:—
- ★ ARUNDEL 15-17 Queen Street Tel. 3280
 - ★ BRIGHTON 5 Queen's Road Tel. 23975
 - ★ LONDON 10 Tottenham Court Road Tel. MUSEUM 2639
 - ★ PORTSMOUTH 350-352 Fratton Road Tel. 22034
 - ★ SOUTHAMPTON 72 East Street Tel. 25851

PERSONAL CALLERS Welcomed at all Branches where there are large Hi-Fi and component stocks at the keenest prices including:

GARRARD 1025 Autochangers complete with GARRARD STEREO CARTRIDGE 7 $\frac{1}{2}$ GNS.


MAGNETIC CARTRIDGES Goldring 800H 7 $\frac{1}{2}$ GNS.

Shriro AT33 £7.10.0 (Both listed over £10)

Lasky's

Audio Tronics 70

Send your name and address now to receive immediately the new 1971 Edition of LASKY'S famous Audio-Tronics pictorial catalogue larger and more comprehensive than ever before. Packed with 1000's of items for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Serviceman, and Communications Ham. Covers every aspect of Hi-Fi (including Lasky's budget Stereo Systems, and Package Deals) plus Lasky's amazing money saving vouchers worth over £32. Send your name and address and 2/6 for post and inclusion on our regular mailing list.

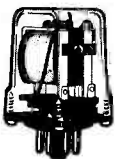

THORN PYGMY PLUG-IN

A compact pygmy relay on an 8-pin base with D.P.D.T. contacts rated to 10A. (Some type 3 P.D.T. on an 11-pin base).

RN TYPE	Contacts	Base	Coil Voltage
215048	D.P.D.T.	8 pin	48V AC/DC
235004	D.P.D.T.	8 pin	40V DC
215060	D.P.D.T.	8 pin	60V AC/DC
305030	3 P.D.T.	11 pin	60V DC
205024	D.P.D.T.	8 pin	24V DC
215042	D.P.D.T.	8 pin	42V DC

Others available in limited quantities.

LASKY'S PRICE 12/6 post 3/6

JUST ARRIVED

Lasky's C60, C90, C120.


Exclusively made for us in U.S.A. Great Savings!

Each	Post	Five for	Ten for
C 60 — 7/6	1/-	33/-	62/-
C 90 — 12/6	1/-	56/-	110/-
C 120 — 17/-	1/-	75/-	139/-

U.S.A. Cassette head cleaner, 10/6, Post 1/-
Post 1/- each, five for 2/-, ten for 3/-



SKYROVER mkII

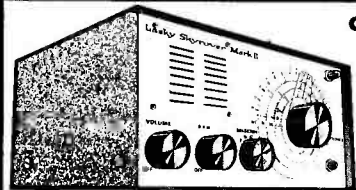

COMMUNICATION RECEIVER

A short wave receiver, exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain. Switch selected SW frequency range cover: 1.5 to 30MHz in three separate bands spread ranges and full AM medium wave-band cover in one range 550-

1,600kHz. Reduction drive tuning with hair line cursor. Controls include volume on/off BFO. Band selector. Power on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 5 1/2 x 5 1/2 in. Complete with mains lead and full instructions.

LASKY'S PRICE £13.13.0

Post 5/-

TMK METER KITS

This meter kit by TMK offers the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinet, movement and range selector mounted in position is supplied with the meter scale. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

MODEL 200

20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3 x 2 in. meter. Full scale accuracy: DCV and current: ± 2%, ACV: ± 3%, resistance ± 3%. Special 0-6V DC range for transistor circuit measurements.

SPECIFICATION

● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV. ● ACV: 0-6-30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-60mA. ● Resistance: 0-10K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0-0.02-0.2μF (AC 6V range). ● Decibels — 20 to ± 63dB. ● Output: 0-0.5μF blocking capacitor. Uses two 1.5V (UT type) batteries. Black bakelite cabinet—Size 5 1/2 x 3 1/2 x 1 1/2 in. Complete with test leads.



KIT PRICE ONLY 92/-

Post 3/6

MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is indicated on the meter face. High speed rotary range selection knob; polarity reversal switch, shielded meter movement with overload protection circuit; Special μA and mA measurement ranges.

SPECIFICATION DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0-25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. DCμA: 0-25μA at 125mA; 0-50μA at 250mA. DCmA: 0-0.25-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV. DC Amps: 0-5A at 125mV; 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0-1μF, 400V) in series with ACV ranges. Decibels: —20 to ± 81.5dB. Operates on two 1.5V batts. Black bakelite cabinet, size 5 1/2 x 6 1/2 x 2 1/2 in. Complete with test leads.



KIT £10.10.0

Post 5/

ALSO AVAILABLE READY BUILT AND TESTED £12.10.0 Post 5/-

EXCLUSIVE TMI & TMS

MODEL TM-1 MINI TESTER

The first of Lasky's new-look top value meters. The TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to —3%, of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero.

- DC/V: 0-10-50-250-1,000 at 1K OPV.
- AC/V: 0-10-50-250-1,000 at 1K OPV.
- DC CURRENT: 0-1mA, 100mA
- Resistance: 0-150kΩ.
- Decibels: —10dB to 22dB.
- Complete with test leads, battery and instructions.




Size Only 3 1/2 in. x 1 1/2 in.

LASKY'S PRICE 39/6 POST 2/6

MODEL TM-5 5K OHMS/V POCKET MULTIMETER

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4 1/2 in x 2 1/2 in x 1 1/2 in, fitted with extra large 2 1/2 in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

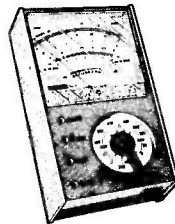- DC/V: 3-15-150-300-1,200 at 5K OPV.
- AC/V: 6-30-300-600 at 2.5K OPV.
- DC Current 0-300μA, 0-300mA.
- Resistance: 0-10kΩ, 0-1MΩ.
- Decibels: —10dB to 16dB.
- Complete with test leads, battery and instructions.



LASKY'S PRICE 49/6 POST 2/6

Garrard

SL-55

OTHER GARRARD UNITS FROM STOCK

AUTOCHANGERS

SL72B	£25 0 0
2025TC with stereo cartridge	£8 17 6
3000 complete with 9TAHC stereo cartridge	£9 19 6
SL65B	£15 10 0
SL95B	£35 0 0
SL75B	£28 0 0

SINGLE PLAYERS

AP 75, £18.10.0. AP75 with AD76K mag. cart., £21.10.0. 401 Transcription Unit, £20.0.0.

BASES AND COVERS FOR GARRARD UNITS

Type WB1 and WB5 for models AT60 Mk II, 2025TC, 3000, SL65B, SL55, 1025, SP25 Mk. II. Price WB1 £3 16 6. WB5 £5 12 6. Type WB4 for models SL72B, SL75B, SL95B Price £5 12 6. Perspex covers: SPCL for WB1 £3 14 1. SPCL for WB4 and WB5 (allows unit to be played with the cover in place)—Price £4 8 6.



SPECIAL SL-55 OFFER

One of the famous Garrard Synchro-Lab Series. Takes 8 L.P.s. Four-speed auto-changer; incorporating a tubular pickup arm and adjustable stylus force. Wired for Mono and Stereo. NOW AT LASKY'S SPECIAL PRICE. Complete with SONOTONE 9TA STEREO CARTRIDGE. £10.19.6

SCOOPMT-65 SPECIAL OFFER

EXCLUSIVE HI-FI STEREO TUNER AMP. OFFER THE MT-65 CHASSIS

Solid state AM/FM multiplex tuner with FET front-end/17 +17 watts stereo amplifier by world famous manufacturer. Frequency response 20-45KHz. Inputs—23mV mag. p/u and 140mV tape play. Tape record output. Controls: Left/right volume, bass, treble, loudness, monitor. Tuning meter and stereo beacon. Stereo 'phone jack. Machined stainless steel front panel. Overall size 20x3½x16in. List Price £75.

SPECIAL PRICE £66.0.0

CARRIAGE 12.6

DE-LUXE "COMPACT" PACKAGE OFFER

MT-65 Chassis £75 0 0
GARRARD AP-75 3,000Hz Single Player £13 6 7
AUDIO DEVELOPMENT AD-36K Magnetic Cartridge £5 18 4
2 WHARFEDALE DENTON Speaker Systems £34 0 0
"Compact" Teak Cabinet (as shown) £7 10 0
TOTAL RECOMMENDED LIST PRICE £148.5.1


**LASKY'S
PACKAGE
PRICE**



£132.0.0

U.K.: carriage 40/-
All units available separately

Sinclair Project 60

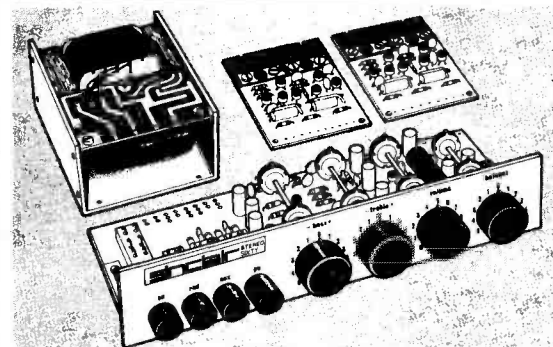

Project 60 is a range of modules which connect together to form a complete stereo amplifier. The modules are: 1. Z-30 high gain power amp. 2. Stereo-60 pre-amp. control unit. 3. The PZ-30 unbalanced and PZ-4 stabilised power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-3 or PZ-4.

STEREO 60 SPECIFICATION

Input sensitivities: Radio up to 3mV, Magnetic Pick-up 3mV: correct to R.I.A.A. curve = 1dB; 20 to 25,000Hz; Ceramic Pick-up up to 3mV
Auxiliary up to 3mV • Output: 1 volt • Signal to noise: better than 70dB • Front panel: brushed aluminium with black knobs and controls • Size: 8¼ x 1½ x 4in. **£9.19.6** post 3/6

Z-30 SPECIFICATION

• Power output: 15 w. R.M.S. into 8 ohms using a 35 volt supply • Frequency response: 30 to 300,000Hz = 1dB • Distortion: 0.02% • Signal to noise: better than 70dB • Input sensitivity: 250mV into 100 K ohms • Loudspeaker imp: 3 to 15 ohms • Power requirements: from 8 to 35V DC (The Z30 will run from batteries if required) • Size: 3½ x 2¼ x 1½in. **89/6** post 3/6

30V unbalanced — sufficient to drive two Z-30's and a Stereo 60 for domestic applications. **99/6** Post 2/6

35V stabilised — ideal for driving two Z-30's and a Stereo 60 for low efficiency speakers. **£7.19.6** Post 2/6

PACKAGE PRICE For Stereo 60, two Z-30 and one PZ-3 **£19.19.6** Post 10/-


INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. Message tape, 150ft.	2 8	5¼in. Long play, 1200ft. Mylar	15 0
3in. Message tape, 225ft.	3 0	5¼in. Triple play, 2400ft.	35 0
3in. Message tape, 300ft.	7 8	7in. Standard play, 1200ft.	12 6
3¼in. Triple play, 600ft. Mylar	10 0	7in. Standard play, 1200ft.	12 6
5in. Double play, 1200ft.	15 0	7in. Long play, 1800ft. Mylar	19 6
5in. Long play, 900ft. Acetate	10 0	7in. Double play, 2400ft. Mylar	25 0
5in. Standard play, 600ft.	8 6	7in. Long play, 1800ft. Acetate	15 0
5¼in. Double play, 1800ft. Mylar	22 8	7in. Triple play, 3600ft. Mylar	30 0
5¼in. Long play, 1200ft. Acetate	15 0		
5¼in. Standard play, 900ft. PVC	12 8		

P. & P. 1/- extra per reel, 4 reels and over Post Free. Special quotes for quantities.

EXCLUSIVE DIGITAL CLOCK SCOOP!

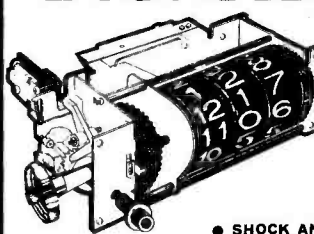

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

SPECIAL QUOTATIONS FOR QUANTITIES

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4½Wx1½Hx3¼D (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.

COMPLETE WITH KNOBS.

LASKY'S PRICE £6.19.6 Post 3/6

AUDIO DEVELOPMENT

AD-309K PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE



The new AUDIO DEVELOPMENT precision counter balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard 3in. mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in. dia. mounting hole.

LASKY'S PRICE £9.19.6 Post 3/6

Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2 Tel: 01 723 3271
33 TOTTENHAM CT. RD, LONDON, WIP 9RB Tel: 01 636 2605
109 FLEET STREET, LONDON, E.C.4 Tel: 01 353 5812
152/3 FLEET STREET, LONDON, E.C.4 Tel: 01 353 2833

HIGH FIDELITY AUDIO CENTRES
42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD Tel: 01 580 2573
118 EDGWARE ROAD, LONDON, W.2 Tel: 01 723 9789

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

This MONTH'S Best Buy...



AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10/90d.) Our Price **£5.18.** + 4/6 p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

* High-fidelity reproduction due to broad frequency response (20-20,000Hz) * Substantially increased stereo effect * Headphones fit the head gently and do not shift * Earpieces fit snugly (Cardanic suspension) * Tone quality superior to conventional loudspeakers. * Only expensive studio loudspeakers can match the reproduction quality of the K50. * Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.




GARRARD SP25

mk II **£10.19.6** Plus 10/- carriage
Normal price £15.11.4

Single record playing unit. Features include cue and pause and automatic pick-up return and switch off.

Wired with mains cable and 5ft. twin screened stereo cable. 5 pin din plug. 10/6 extra. AP75 Complete with base and cover £25 plus 15/- carriage.

PLUGS?

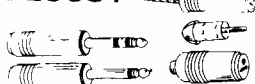

Pack 107 5-Pin Din .. 4/-
Pack 108 3-Pin Din .. 3/6
Pack 135 1/2" Jack .. 5/-
Pack 130 1/2" Jack Stereo .. 9/6
Pack 103 Loudspeaker Plug .. 3/-
Pack 100 Phono Plug .. 1/3
Pack 230 3-Pin Socket .. 4/6
Pack 236 5-Pin Socket .. 6/-
Pack 234 Loudspeaker Socket .. 6/-
Ready-made Leads
3-pin to 3-pin Din .. 12/6
3-pin to open end .. 10/6
5-pin to 5-pin Din .. 16/-
5-pin to open end .. 13/-
5-pin to 4 phone plugs .. 18/6
All leads approx. 6ft. in length.
Post free, by return.

PLINTH & COVER £55.0

Unbeatable Value

plus 10/- p. & p.

Suitable for AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex. Also available for AP75; SL99; SL75 £6.17.6 plus 10/- carr.

Replacement Stereo DIAMOND STYL

8TA 9TA 9TAHC
GP91 ST4 ST9
EV26 GC8
others on request p. & p. 1/6

Countdown SPEAKER

Teak Cabinet

£12 Insurance & carr. 7/6

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.



EMI low matched loudspeaker set 450

Our price 75/- inc. 5/- p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies. Also 350 KIT 20W Frequency range: 20 to 20,000Hz. **£7.10.0.** Normal price £12.10.0 plus 8/- p. & p. Also 150 KIT 10W Decca SX12057 **50/-** plus 8/- p. & p.



SINCLAIR Project 60

SAVE nearly £5 Normal price £23.18.0d.

Designed for building into plinths etc., complete with two Z30 Output stages **£19** 10/- carr.

(20 watt) and power supply unit. Send S.A.E. for full technical brochure. **SINCLAIR 2000 AMPLIFIER** SAVE 6gns. Our price 23gns.

Magnetic cartridges

Diamond **95/-**

styli plus 2/6 p. & p. Today's value £6. Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) 25/- 2/6 p. & p.



SONOTONE Cartridges ...

(Fitted Diamond Styl) (Ceramic) list price 82/-

Sensitivity: 9TA 80mV 9TAHC 55mV/cm/sec rms minimum at 45° at 1,000Hz measured on Decca SX12057 **47/6** plus 2/6 p. & p.

NEW VALVES!

Guaranteed and Tested 24-HOUR SERVICE

IR5 5/6	DAC32 6/9	BCC81 3/6	EL84 4/9	PCF805 12/9	R19 6/3
1B5 4/3	DAF91 4/3	BCC82 4/-	EM34 13/9	PCF806 11/-	U25 12/9
174 2/9	DAF96 7/3	BCC83 4/9	EY51 7/-	PCF82 6/9	U26 11/6
3B4 5/9	DF33 7/6	BCC80 5/9	EY86 6/3	PCL84 7/-	U191 12/-
3Y4 6/6	DF91 2/9	BCC82 5/9	EZ80 4/3	PCL85 8/6	U261 14/-
6/30L2 11/6	DF96 7/-	BCH35 5/6	EZ81 4/6	PCL96 8/3	U329 14/-
6AQ5 5/-	DK32 6/9	BCH81 5/9	KT61 9/3	PFL20011/6	UABC80 6/-
6P23 13/6	DK91 5/6	BCL80 7/6	KT66 18/6	PL36 9/3	UBF89 6/3
6P25 12/-	DK92 8/3	BCL82 6/3	N75 17/-	PL81 9/3	UCC85 7/3
25L6GT 4/9	DK96 7/3	BCL86 4/6	PC86 9/9	PL82 6/3	UCH81 6/6
30C18 12/9	DL35 4/9	EF39 6/9	PC88 9/9	PL83 6/3	UCL82 6/9
30FL1 12/6	DL92 5/9	EF80 4/6	PC97 7/6	PL84 6/-	UF89 6/-
30L15 12/9	DL94 6/6	EF85 5/9	PC900 7/-	PL500 12/9	UL84 6/3
30L17 14/6	DL96 7/3	EF86 4/3	PCC84 6/3	PL504 13/-	UY41 7/-
30P4 12/-	DY86 5/3	EF89 6/9	PCC89 9/3	PY32 10/-	UY85 5/3
30P19 12/-	DY87 5/3	EF91 2/6	PCC189 9/6	PY33 10/-	Z77 3/9
30P11 12/3	EABC80 6/3	EF183 5/6	PCF80 5/11	PY81 5/-	
30PL13 14/-	EB91 2/-	EF184 6/3	PCF86 9/-	PY82 5/-	
30PL14 13/6	EB93 7/9	EH90 7/3	PCF801 6/6	PY800 7/-	
COH35 13/-	EBF89 6/-	EL33 9/3	PCF802 8/9	PY801 7/-	

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83, OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N-16

RSGB Amateur Radio Call Book

1971 Edition now available

Including details of new call signs issued by MPT up to 31st August 1970 and more than 2,100 changes of address, compared with the 1970 edition. 128 pages, including 14 pages of valuable supplementary information.

10s post paid

AMATEUR RADIO TECHNIQUES

By Pat Hawker, G3VA

A source-book for many useful circuits and aeriels, incorporating the latest techniques in the amateur field. Third (1970) Edition. 208 pages. Nearly 500 diagrams.

22s post paid


RADIO COMMUNICATION HANDBOOK

RADIO COMMUNICATION HANDBOOK

over 22,000 copies sold

Now in its second printing

The standard work in its field

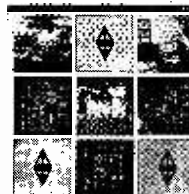

832 pages of everything in the science of radio communication. The handbook's UK origin ensures easy availability of components. **69s post paid**

Obtainable from:

RADIO SOCIETY of GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

When in LUTON, BEDS. you must visit the

SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day
Closed all day Wednesday

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, BEDS


J. J. FRANCIS
(WOOD GREEN) LTD

123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662

Many New Models! in the FREE HEATHKIT 1971 Catalogue..



CONSUMER

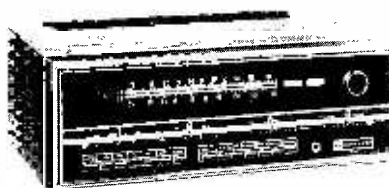

HI-FI & AUDIO



MODEL R/C CARS

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi . . . Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.

- ★ Save up to 50 % over factory built equipment.
- ★ Money saving direct from factory prices.
- ★ They make excellent Christmas gifts.



MARINE



'TRENT' SPEAKER



A Schlumberger Company

HEATH (Gloucester) LTD, GLOUCESTER GL2 6EE

(In block capitals)

Many other models in wide range . . .

**FILL IN THE COUPON FOR YOUR
FREE CATALOGUE TODAY.**

Name

Address

Post Code

R-S-C HIGH FIDELITY STEREO 'PACKAGE' OFFERS

- ★ Four fully wired units ready to 'plug in.'
 - ★ **SUPER 30 AMPLIFIER** (15 + 15 watt) in veneered housing
 - ★ **GARRARD SP25 MK II** Turntable on Plinth with cover
 - ★ **GOLDRING CS90 Ceramic P.U.** Cartridge with diamond stylus
 - ★ **PAIR OF STANWAY II** Loudspeaker units
- 76 Gns.** Carr. 30/-
Units Special Total Price

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



ATTRACTIVE TEAK or AFORMOSIA VENEERED CABINETS and PLINTHS

TERMS AVAILABLE ON ALL PACKAGE OFFERS

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 - ★ Goldring GL69 Transcription Turntable on Plinth as illustrated
 - ★ Shure or Goldring Magnetic P.U. Cartridge.
 - ★ Pair of Stanway II Loudspeaker units
- 92 Gns.** Carr. 30/-
Special Total Price

- ★ **TA12 AMPLIFIER** 6.5 + 6.5 watt in veneered housing
- ★ **GARRARD SP25 MK II** Player unit on Plinth
- ★ **GOLDRING CS90 Ceramic P.U.** Cartridge with diamond stylus
- ★ **PAIR OF DORCHESTER** Loudspeaker Units

Special **54 Gns.** Carr. 25/-
Total Price

Or Deposit £6.19.6 and 9 monthly payments £6.4.6 (Total £60 gns.). Transparent Plastic Cover 3 gns. extra.

AS ABOVE BUT WITH GARRARD 3000 AUTOCHANGER AND SONOTONE 9TA Ceramic Cartridge in lieu of SP25 and CS90 **49 Gns.** Carr. 25/-

Or Deposit £6 and 9 monthly payments £5.14.0 (Total £57.6.0) Trans. Plastic cover 3 gns. extra.

LOW DEPOSIT CREDIT TERMS

Available on purchases over £8
KITS of parts excepted

INTEREST CHARGES REFUNDED


On Credit Sales settled in 3 months

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT

GARRARD 5200 Changer

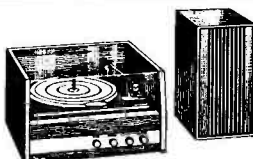with low mass pick-up arm and Stereo Cartridge. CONTROLS: TREBLE, BASS, VOLUME, STEREO BALANCE. Operation on standard 200-250V. A.C. mains. Output rating I.H.F.M.



Luxurious Teak Veneer Finished Cabinets. Transparent plastic (tinted) cover included for main unit. Silver finished fascia plate and matching control knobs.

PAIR OF LOUDSPEAKER UNITS

incorporating high flux 8" x 5" speaker. Size approx. 13 x 7 1/2 x 8 1/2 ins.

Price complete **39 Gns.** Carr. 25/-
ONLY


Terms: Deposit £5 and 9 monthly payments 4 gns (Total £44.18.0)

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICED SYSTEM

RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups etc., and for loudspeaker output impedances of 3 to 16 ohms. For standard 200-250V. A.C. mains operation.

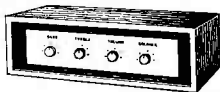Attractive silver finished metal fascia plate and matching controlknobs. Complete KIT of PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9.19.9**



Or FACTORY BUILT in Teak veneered cabinet No leaflet supplied for this unit as illustrated **£12.10.0** carr. 7/9 Or dep. 37/8 and 9 mthly. pymts. 29/6 (Total £15.3.0).

PACKAGE OFFER SAVE £4 approx Above G66 assembled in cabinet, plus pair DORCHESTER LOUDSPEAKER UNITS **£27.10.0** Carr. £1

Or Deposit £5 and 9 monthly payments 57/6 (Total £60.17.6).

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER



★ 200-250V. A.C. Mains operation. ★ High-sensitivity. ★ Rejection x ★ Drift-free reception. ★ Sharp A.M. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. FACTORY BUILT 18 gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit £6.1.0 & 9 mthly pymts. 29/6. Total £24.18.0. STEREO VERSION, 241 gns. Carr. 10/6 extra

HIGH FIDELITY LOUDSPEAKER UNITS Credit terms available.

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate.

DORCHESTER Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High Flux 13 x 8in. Dual Cone speaker. Imp. 3 or 15 ohms. **9 Gns.** Carr. 7/6

STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **17 Gns.** See top of page for illustration

R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION
HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder, 'Mic.' etc. ★ 3 separate switched input sockets on each channel. ★ Separate Bass and Treble controls ★ Slide Switch for mono use. ★ Speaker Output 3-16 ohms ★ For 200-250V. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handmade finish. Fascia plate and knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 months guarantee **17 gns.** or Deposit £3.0.0 and **13 1/2 gns.** 9 mthly pymts. 30/- (Total £22.11.0). Or in Teak or Afrormosia Carr. 7/9 veneer housing **20 1/2 gns.** Dep. 3 Gns. and 9 monthly payments 47/- (Total £24.6.0).



R-S-C SUPER 30 MK II HIGH FIDELITY STEREO AMPLIFIER

High Grade Components, Specifications - comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.

OUTPUT 10 Watts R.M.S. continuous into 16Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.

INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5mV.

FREQUENCY RESPONSE ± 2 dB. 10-20,000 c.p.s.

TREBLE CONTROL +17 dB to -14 dB at 10 Kc/s.

BASS CONTROL +17 dB to -16 dB at 50 c/s.


HUM LEVEL -80 dB.

HARMONIC DISTORTION 0.1% at 10 watts 1,000 c.p.s.

Employing Twin Printed Circuits.

200/250V. A.C. mains operation.

CROSS TALK 52 dB at 1,000 c.p.s.

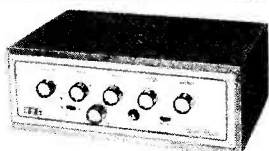

CONTROLS 5 Position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).
CHASSIS Strong Steel construction. Approx. 12 x 3 x 8in.

FACIA PLATE Attractive design in rigid plastic, silver background black lettering. Silver finish matching control knobs as available.

Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

COMPLETE KIT OF PARTS Point to point wiring diagrams and detailed instructions. **22 Gns.** Carr. 15/-

UNIT FACTORY BUILT 29 Gns.

With 12 months guarantee.
Or Deposit £4 and 9 monthly payments 66/6 (Total £53.18.6 or in Teak or Afrormosia veneer housing Carr. 15/- Terms: Deposit £4 and 9 monthly payments of 74/- (Total £57.6.0). Send S.A.E. for leaflet.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
HULL 91 Paragon Street (Half-day Thursday) Tel. 20505

R-S-C
HI-FI CENTRES LTD.

MAIL ORDERS TO: Audio House, Henricer Lane, Leeds 13.
No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. please with enquiries.
Branches open all day Sats.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

32 High Street (Half-day Thurs.) Tel. 56420
5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252
73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573
238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629
60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778
106 Newport Rd. (Half-day Wed.) Tel. 47996
41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469
13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716
LEICESTER
LEEDS
LIVERPOOL
LONDON
MANCHESTER
MIDDLESBROUGH
NEWCASTLE UPON TYNE
SHEFFIELD

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM



★ Moderate size only 25 x 14 x 10in. COMPLETE KIT 21 Gns
★ Response 30-20,000 c.p.s. Impedance 15 ohms
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. 4 Gns. and 9 monthly payments 45/6 (Total £24 Gns.). DEMONSTRATIONS AT ALL BRANCHES

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**

OR SENIOR 15 WATT INC. HF126 15,000 LINE SPEAKER CARR. 6/6 **£6.15.0** Carr. 5/9



AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "F" indicates "F" Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF901D 8" 8W 54/3 HF126D 12" 15W 89/9
HF102D 10" 10W 67/11 HF126 12" 15W £5.5.0
HF120 12" 15W 79/9 HF126D 12" 15W £5.15.0

HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 5/- per enclosure
JES 16 x 11 x 9in. Pressurised. Gives **£4.14.6**
pleasing results with any 8in. Hi-Fi speaker.
SES For optimum performance with any 8in. Hi-Fi speaker. Size 23 x 15 x 9in. Ported **£5.15.0**
SE10 For outstanding results SE12 For excellent performance with 12in. Hi-Fi speaker. Hi-Fi speaker and Tweeter. **£6.19.9**
Size 24x15x10in. P.t.d. **£5.19.9** Size 25 x 16 x 10in.



RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

RP2C Garrard SP25 Mk II (with heavy turntable) fitted Goldring C90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Carr. 9/8 **£24.12.6**

RP5C Garrard 2025 Auto Unit fitted Garrard GOS 23 Stereo Cartridge with diamond tip. Plinth & Cover as RP2C Carr. 9/6. Other types available with Magnetic cartridges and with alternative design plinths. **15 Gns.**

R.S.C. PLINTHS

Superior Solid Natural Wood Construction



AVAILABLE WITH TRANSPARENT PLASTIC COVER Carr. Free

for Record Playing units, cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. **3 gns. 6 gns.** Carr. Free

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES Available at branches only

LINEAR L10 HIGH FIDELITY 10W AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12½ gns.** Carr. 12/6

OR FACTORY BUILT 15 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 21/1 (Total £18.9.9) Available in Teak or Afrormosia veneered housing. 18 Gns.

R.S.C. BATTERY/MAINS CONVERSION UNITS



TYPE BM1 An all-day battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 500c/s is available. Complete kit with diagram 59/9 or assembled 69/9.

R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER



200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -20dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns** Carr. 7/6

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE £8.19.9

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity. 5 valves. Independent Bass and treble controls. Frequency response ± 3dB 30-20,000 c/s. Hum level -60dB. Sensitivity 40 mV. Output rating I.H.F.M. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc. **10. Gns**

Std. A.C. mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. SAR for leaflet. Twin handled metal cover 35/-. Price Factory built 14 gns. or Deposit 23 and 9 monthly payments of 21/6 (Total £17.8.8.)

R.S.C. COLUMN SPEAKERS

ALL TYPES 15 OHMS COVERED IN REXINE/VYNAIR, IDEAL FOR VOCALISTS AND PUBLIC ADDRESS.

TYPE C4100 also suitable for Bass Guitar or Electronic Organ.

TYPE C485 20-30 WATTS Fitted four 8" high flux 8 watt speakers.

Overall size approx 48 x 10 x 5 in. Carr. 10/-

Terms: Dep 23 and 9 monthly payments 35/6 (Total £18.19.8) **16 Gns.**

TYPE C4100 100 watts inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Acoustically filled and pressurised.

Terms: Deposit 23 and 9 monthly payments £5.10.6 (Total £57.14.8).

30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input. 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.A. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £3.14.0 and 9 monthly payments of 42/- (Total £32.12.0) Carr. 12/6



HI-FI CENTRES LTD.



HIGH QUALITY LOUSPEAKER UNITS

IN TEAK OR AFRORMOSIA VENEERED CABINETS


L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required. **5 Gns.** Carr. 7/6

L12 12" 20 WATT 10,000 lines 15 ohms. Carr. 8/9

£8-19-9

L125 50 WATT

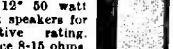Two tone Rexine and vynaair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. 15/- **28 Gns.**



R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar.

vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit horizontal or vertical mounting.

★ Two extra heavy duty 12in. Loudspeakers.

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.

Deposit £13.4.9 and 9 monthly payments of £5.11.9 (Total 60½ gns.)



FAL PHASE 50 AMPLIFIER 50 Watt

Solid state 3 Separately controlled inputs Ind. Bass and Treble Controls. Output for Speaker/s 3-30 ohms.

Size 17" x 7" x 7 1/2" 200-250 A.C. mains. Peak Output rating.

For fuller details of Phase 29 Gns. Carr. Free

50 see Manufacturers advert. page 618 or send S.A.E. for leaflet.

guard against damage from accidental shorts

I.H.F.M. Output rating **59 Gns.**

FAL PHASE 100 AMPLIFIER

100 Watt Solid State 4 Separately controlled inputs Plus master volume Control. Ind. Bass and Treble Controls. Output for speaker/s 3-30 ohms. Protective circuit to

guard against damage from accidental shorts

I.H.F.M. Output rating **59 Gns.**

FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All carr. free.

'POP' 100 18" 100 Watt 14,500 gauss 8/150 **21 gns.**

Dep: 26 and 9 monthly payments 26/6 (Total £16.1.6.)

FOR BASS GUITAR OR ELECT. ORGAN, ETC.

'POP' 60 15" 60 Watt 14,000 gauss 8/150 **£12.18.0.**

Dep: 3 gns. and 9 monthly payments 26/6 (Total £16.1.6.)

FOR BASS GUITAR OR ELECT. ORGAN, ETC.

'POP' 50 12" 50 Watt 14,000 gauss 10 GNS. 150

Dep 22 and 9 monthly payments 22/6 (Total £12.2.6)

Pair suitable all purposes (Total £17.0.)

FOR BASS GUITAR OR ELECT. ORGAN, ETC.

FANE LOUSPEAKERS

'POP' 30C 12in. 25 WATT Dual Cone 15Ω

(For uses other than Bass Guitar or Electronic Organ)

£5-19-9 Carr. free

or Dep. 21 and 9 monthly payments 13/- (Total £17.0.)

FOR BASS GUITAR OR ELECT. ORGAN, ETC.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output with Pre-amp/Tone Control Stages. Hum level -70dB. Frequency response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, EOC83, 807, 807, 0234. Separate Bass and Treble Controls. Sensitivity 36 millivolts. Suitable for High Impedance microphones. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, etc. Complete kit of parts with point to point wiring diagram and instructions. Twin-handled perforated cover 35/-. **15 Gns.**

OR factory built with EL34 output valves and 12 months' guarantee for 18 gns. Carr. 12/6

TERMS: Deposit £3.9.0 and 9 monthly payments of £2 (Total £21.9.0). Send S.A.E. for leaflet.

RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primary 200-250v. 500c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.

250v., 60mA, 6.3v. 2a. 17/11

250-0-250v., 60mA, 6.3v. 2a. 18/11

FULLY SHROUDED UPRIGHT MOUNTING

250-0-250v., 60mA, 6.3v. 2a., 0-5-6.3v. 2a. 24/9

250-0-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 36/8

425-0-425v., 200mA, 6.3v. 4a., e.t., 5v. 3a. 39/9

300-0-300v., 100mA, 6.3v. 4a., e.t., 5v. 3a. 39/9

300-0-300v., 130mA, 6.3v. 4a., e.t., 5v. 3a. 47/11

For Mullard 510 Amplifier

350-0-350v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 39/9

300-0-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a. 47/9

425-0-425v., 200mA, 6.3v. 4a., e.t., 5v. 3a. 89/9

350-0-425v., 200mA, 6.3v. 4a., e.t., 5v. 3a. 93/9

450-0-450v., 250mA, 6.3v. 4a., e.t., 5v. 3a. 99/9

TOP SHROUDED DROP-THERO TYPE

250-0-250v., 70mA, 6.3v. 2a., 0-5-6.3v. 2a. 23/9

250-0-250v., 100mA, 6.3v. 3.5a. 27/11

FILAMENT OR TRANSFORMER POWER PACK

Types 6.3v. 1.6a. 8/9; 6.3v. 2a. 9/9; 6.3v. 3a. 13/9;

6.3v. 6a. 22/9; 12v. 1a. 9/11; 12v. 2a. or 24v. 1.6a. 23/9; 0.9-18v. 1.1a. 19/11; 0-12-25-42v. 2a. 31/9

CHARGER TRANSFORMERS 0-9-15v. 1.1a. 18/9;

24a. 19/11; 3a. 21/11; 5a. 25/11; 6a. 29/9; 8a. 36/9

ATRO (Step Up/Step Down) TRANSFORMERS

0-110/120v. 200-250/350v. 50-80 watts 18/9;

150 watts, 33/6 250 watts 49/9; 500 watts 105/-

OUTPUT TRANSFORMERS

Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 8/9

Push-Pull 8 watts EL34 to 3 Ω or 15 Ω 14/9

Push-Pull 10 watts 6V6, 6CL6 to 3 Ω, 5 Ω, 8 Ω 15/-

Push-Pull EL284 to 3 Ω or 15 Ω 16-12 watt 18/9

Push-Pull Ultra Linear for Mullard 510, etc. 39/9

Push-Pull 15-18 watts, sectionally wound 616, KT66, etc., for 3 Ω or 15 Ω 35/9

Push-Pull 20 watt high quality sectionally wound EL34, 616, KT66 etc. to 3 Ω or 15 Ω 59/9

SMOOTHING CHOKES 150mA, 8-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 19/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11

SELENIUM RECTIFIERS F.W. (Bridged) All 12v. D.C. output. Max. A.C. input 18v. 1a. 4/8. 2a. 6/11. 3a. 9/9. 4a. 12/9. 5a. 16/9.

CRESCENT RADIO LTD.

11 & 40 MAYES RD. N.22 888-3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL



TRANSFORMER SCOOP

Primary 110, 220, 250 v. fused.
Secondary 220 v. at 50mA, 6.3v.
at 1 amp. Overall size 3 1/2" x 2" x
2 1/2" high. 12/6 each. P. & P. 3/-.

2 x 3-15 volt, 1 amp. Secondary
250 volt Primary. Can be used
as 6-3v. heater transformers.
7/6 each. P. & P. 3/-.



SHELF UNIT

Two teak finish shelves on a black frame
(overall size: 28in. x 26in. x 12in.). Ideal for
hi fi equipment: amplifiers, speaker cabinets,
etc. The perfect answer for housing unit audio
and equipment. This unit is wall mounting

50/-

PLEASE NOTE P. & P. IS FREE



WESTON MILLIAMMETER

Modern clear plastic design. 1mA full scale, calibrated
0-100. 2 1/4" x 2 1/4" x 1 1/4" deep.

30/- Plus 2/6 P. & P.

IMPORTED PANEL METERS

KA-38C 1 1/2" x 1 1/2" 50μA,
100μA, 500μA, 1mA,
5mA. 8 meter 1mA, 300v.
All at

29/6 Plus 1/- P. & P.

KA-65C 3 1/4" x 3 1/4". 300v.,
8 meter 500μA, 1mA.
All at

39/6 Plus 1/6 P. & P.

All modern design and made to high standards.



E.M.I. SET 450

3, 8 or 15 Ω, 10 watts.

65/- Plus 7/6 P. & P.


E.M.I. SET 150

This speaker has a flared
centre tweeter cone and
handles up to 10 watts
Size—13" x 5" x 5"
3, 8 & 15 ohms

50/- each
+7/6 P. & P.

SEND FOR FREE LISTS OF SEMI CONDUCTORS

MODEL MAKERS MOTOR

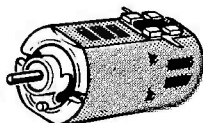

Rated up to 11.5 volt 400mA, torque
12g-cm. Size—1 1/2" long x 7/8" diam.
Shaft—1/8" long x 1/16" diam.
4/6 each. P. & P. 1/6.


COMPONENT CENTRE

8" x 6" one sided printed circuit board	2/- each
BY100 type rectifier 800 pV 750mA	3/3 each
4-pin transistor holders	6d. each
2 1/2" 80 ohm loudspeaker	5/6 each
2 1/2" 8 ohm loudspeaker	6/6 each
2 1/2" 25 ohm loudspeaker	5/6 each
U2 battery holders (blue plastic)	1/- each
10 ohm w/w pots	2/6 each
OC81 double heat clips	6d. each
Tape recorder rev. counters	5/- each
Transistors, Diodes, S.C.B.s etc.	Send for list now

Please include P. & P.

Send 3/- for our Component Catalogue and Flog Lists.

DWELL TIME UNIT

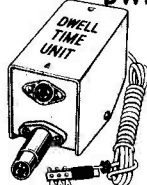

These small units contain the
following components: 700 ohm
DPDT relay with base, 1μF 250v.
paper, 0.01μF 400v. paper, 50μF
35v. electrolytic, 3 diodes, OC200
transistor, a 2N2926 type transi-
stor unmarked, a skeleton pre-set
pot, 4 pin din plug & skt., 4 foot
of 4 core screen. All housed in a
small neat metal box. Can be made
into many timing devices.

12/- Plus 1/6 P. & P.

FLICK SWITCHES




250 volt, 3A Single Pole
on-off. 1 1/2" nylon Toggle.
3/6 Plus 1/- P. & P.

CRESCENT CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

The unit is connected directly across the speaker output of an amplifier, it will
then convert audio signals into a spectacular three colour psychedelic light display.
SEND S.A.E. FOR FURTHER DETAILS

SEND IN S.A.E. WITH YOUR LIST OF COM-
PONENTS FROM THE CONSTRUCTIONAL
PROJECTS OUT OF PRACTICAL WIRELESS/
ELECTRONICS FOR A RETURN OF POST
QUOTE

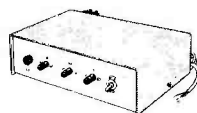WE STILL ARE THE LARGEST COM-
PONENT STOCKIST IN LONDON



Size 8 1/2" x 5 1/2" x 3" high. 500 watts
each channel light output. A total
of 15 x 100 watt lamps can be used!
Input—jack socket. Controls vary
the input to each channel.

£18-10-0 each

Plus 7/6. P. & P.

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

PLUS-3 MAINS UNIT

Provides three separate
switched output voltages
6v., 7.5v. and 9v. DC. attractive
case with indicator
light, mains lead output
socket, plug and lead.

Size 4 1/2" x 3 1/2" x 2 1/2" in.
57/6 P. & P. 2/6



(Extra lead with DIN plug for
Cassette Recorders 7/6)

MAINS UNIT

for transistor equipment
using 7 1/2v. Complete with
DIN plug for power socket.
Can also be supplied for a
6-volt output complete
with suitable plug. (State
make, model and voltage
required.)

45/- P. & P.
2/6

UNIT FOR USE WITH 12v CAR BATTERY
Suitable for running transistor radios etc.
(State output reqd. - 6v., 7 1/2v or 9v) Price 35/- in-
cluding fused lead P. & P. 2/6

MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 20v.
For two separate outputs, 4 1/2v & 4 1/2v,
6v & 6v., 9v & 9v. 42/6. P. & P. 2/6 per
unit. (Please state outputs reqd.).


MAINS UNIT FOR ALL TRANS-
ISTOR RADIOS ETC., USING
PP3 TYPE BATTERY.
(ALSO AVAILABLE FOR 9V.)

20/- P. & P.
2/-

All units are completely isolated from mains by
double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 31 Oliver Road, London, E.17

The Unique MULTI-MINI TWIN-VICE

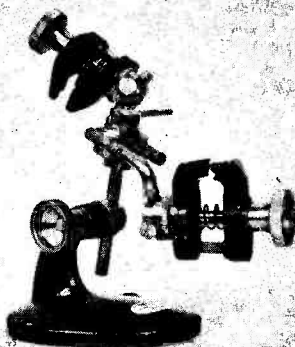

An extra "Pair of hands" for
those tricky jobs

ASSEMBLY—SOLDERING—
GLUING—WIRING—DRILLING
ETC.

- INDEPENDENT ADJUSTMENT OF
THE TWO VICE HEADS TO ANY
ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND,
FLAT, SQUARE, OR HEXAGONAL
PARTS.

TWIN VICE: £5-18-0 (4/6 P & P)

ALSO AVAILABLE

SINGLE VICE: £3-7-6 (3/- P & P)

COVENTRY MOVEMENT CO LTD.
BURNSALL ROAD, COVENTRY
CV5 6BU STD 0203-74363

Learn at home... First Class Radio and TV Courses



After brief, intensely interesting study
—undertaken at home in your spare
time— YOU can secure a recognised
qualification or extend your knowledge
of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120
pages of information of the greatest
importance to both the amateur and
the man employed in the radio industry.
Chambers College provides first rate
postal courses for Radio Amateurs,
Exam., R.T.E.B. Servicing Cert., C. & G.
Telecoms., A.M.S.E.(Elec.). Guide also
gives details of range of certificate
courses in Radio/TV Servicing, Elec-
tronics and other branches of engineer-
ing, together with particulars of our
remarkable terms of

'Satisfaction or Refund of Fee'

Write for your copy of this valuable booklet. It may
well prove to be the turning point in your career.

Founded 1885—Over 150,000 successes

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
(Dept. R15), Aldermaston Court,
Reading, RG7 4PF

Metrosound Audio Products



ST.20 Stereo Amplifier

Good looks apart the ST.20 offers outstanding performance equal to amplifiers selling at two or three times the price which makes it one of the best buys on the High Fidelity market. All silicon solid state circuitry using 20 transistors and 2 diodes provides a full 20 watts r.m.s. output (10 watts r.m.s. per channel). Conservatively rated components are used throughout to ensure long term reliability and stability. Press button selector switches are a feature of the ST.20 for magnetic phono, crystal phono, radio tuner, tape, mono/stereo and on/off facilities. The slimline cabinet in teak veneers and the front panel fascia of

brushed anodised aluminium finish with gleaming silver trims combine to give a look of expensive and stylish elegance.

Size 15½" x 3½" x 10".

Price £36.0.0.

"Its performance is not just on the fringe of the specification – as happens with many low-priced amplifiers – it is well within it and well within the requirements for hi-fi"

F. C. Judd "Hi-Fi Sound" August 1970




ACCEPTED BY THE
COUNCIL OF INDUSTRIAL
DESIGN FOR INCLUSION
IN DESIGN INDEX



Stereo 10-10 Compact System

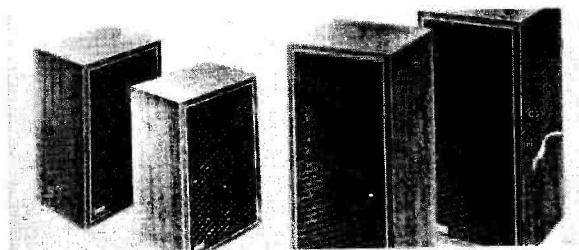Expertly designed and providing outstanding quality reproduction. Not just another compact system but a true "sound centre" incorporating an all silicon transistor amplifier, Garrard 3000 autochanger and two Metrosound HFS.10 speaker systems. Output 20 watts rms. (10 watts rms. per channel) Bass, Treble, Volume and Balance controls. Input for tuner. Tape record outlet. Price £77.6.4.



Metrosound Speaker Systems

MODEL HFS.10 10 watts handling capacity. 8 ohm impedance. Teak finish. Size 14" x 9" x 7". As used in the Stereo 10-10 Compact System and available in matched pairs at £26.3.8.

MODEL HFS.20 20 watts handling capacity. 8 ohm impedance. Teak finish. Size 23" x 11½" x 10½". Price £18.10.0. each.

Available from all leading high fidelity dealers
Designed and Manufactured in England by

metrosound


Metrosound Manufacturing Co. Ltd., Audio Works,
Cartersfield Road, Waltham Abbey, Essex.
Telephone: Waltham Cross 31933

Please send full details of

☐ ST.20 Amplifier ☐ 10-10 Compact ☐ Speakers

NAME _____

ADDRESS _____

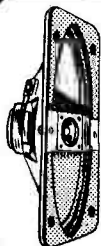

E.M.I. LOUDSPEAKERS
MODEL 450 13 1/2" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price 79/6 P. & P. 4/6.
MODEL 150 13 1/2" x 8" elliptical, 3 and 15 ohm impedance. 10 watts. Lind-Air Price 59/6 P. & P. 4/6.
TEAK FINISH SPEAKER CABINETS
 Size 16" x 10" x 9". Ideal or above units 49/6

C1001 MULTI-TESTER




Overload protection. 20,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-80K, 0-6 Meg ohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1 1/2 in. Complete with case. 85/- P. & P. 3/6

G2D MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2500v. (20,000 ohms per volt). AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-6K, 0-6 Mg (300 ohm and 30K at centre scale). Capacitance: 10f, to .001 mfd. .001 uf to .1 uf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 1/2 in. 71/- P. & P. 3/6.

SINCLAIR PROJECT 60

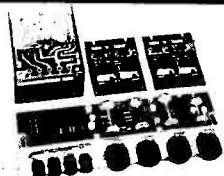

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z30 24 watt Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier 29.19.6 P.Z.5 Power Supply Unit 24.19.6. **SINCLAIR PROJECT 60** Package deal price 19 GNS. P. & P. 12/6. Project 60 is supplied complete with instruction manual and templates for plinth mounting.

SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. **ONLY 59/6 P. & P. 1/6.** **SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10** from A.C. mains 230/250v. Output 13v. at 0.5amp. 16/6 P. & P. 2/6.

"HI-TEN" LOUDSPEAKER

British made full-range 10" unit handles up to 10W. Ceramic magnet. Frequency response, 40Hz-10kHz; imp., 15Ω; flux density, 10,000 lines. 49/6. P. & P. 4/6.



HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001	3"	L.P. PVC	225ft.	5/6	P & P 1/2
J1002	3"	T.P. Poly	600ft.	10/6	P & P 1/2
J1003	5"	L.P. PVC	900ft.	10/-	P & P 1/8
J1004	5"	D.P. Poly	1200ft.	15/-	P & P 1/8
J1005	5 1/2"	L.P. PVC	1200ft.	12/6	P & P 2/-
J1006	5 1/2"	D.P. Poly	1800ft.	22/6	P & P 2/-
J1007	7"	S.P. PVC	1200ft.	12/6	P & P 2/6
J1008	7"	L.P. PVC	1800ft.	17/6	P & P 2/6
J1009	7"	D.P. Poly	2400ft.	25/-	P & P 2/6
J1010	7"	T.P. Poly	3600ft.	50/-	P & P 2/6
C60	Cassette (Library cased)			8/6	P & P 1/-
C90	Cassette (Library cased)			13/-	P & P 1/-
C120	Cassette (Library cased)			18/-	P & P 1/-




DE-LUXE STEREO HEADPHONES
 With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug. **59/6 P. & P. 3/6.**

SOLDERING GUN



Comfortable grip with trigger control. "T" shaped 3/8" bit to multi-mine wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use 230-250 volts. 85 watt element 49/6 P. & P. 3/6.

S-DEC BREADBOARD

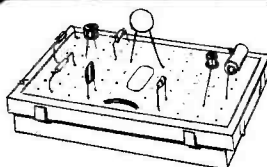

British Made
 Solderless breadboard panels, for fast reliable component connections. Single DeCs. One 8-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on 8-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.
 4-DeC KIT. Four 8-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on 8-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. 25.17.6. P. & P. 3/6.
 T-DeC KIT 22.10.0. P. & P. 3/6.

Garrard HI-FI TURNTABLES



2025 T/C with stereo cartridge .. 28.19.6
 3000 with Sonotone
 9TAHCD stereo cartridge 210.19.6
 SP25 Mk II 210.19.6
 SL65B 215.19.6
 Base and cover for above 45.19.6
 AP78 219.10.0
 SL72B 224.19.6
 SL75B 228.7.0
 SL95B 239.9.0
 401 228.10.0
 Base and cover for above 28.19.6
 P. & P. Decks 12/6. Base & Cover 10/- Deck/Base/Cover 17/6.

SPECIAL OFFERS!

SP25 Mk II with base £14.10.0. P. & P. 15/-.
 SP25 Mk II with Sonotone 9TAHCD cartridge and base £15.15.0. P. & P. 15/-.
 Sonotone 9TAHCD cartridge £2.15.0. P. & P. 1/6.

FIRST TIME EVER! RADIO HEADPHONES



* STEREO EFFECT RADIO
 * POWERFUL TRANSISTOR RADIO
 * BUILT INTO HEADPHONE WITH TUNING AND VOLUME CONTROLS
 * TWIN TELESCOPE AERIAL RODS
 * TWIN MAGNETIC SPEAKERS—ONE IN EACH EARPIECE

Listen to all your favourite radio programmes anywhere and anytime. Lightweight and comfortable to wear. Covers full medium waveband, super-sensitive tuning control and variable volume control. Ideal for outdoors and indoors. **ONLY 12.19.6. P. & P. 4/6.**

600 WATT LIGHT DIMMER SWITCH

Same size as standard wall switch and will dim incandescent lighting from full on to off. Heavy plastic box with control knob. **LIND-AIR PRICE 24.10.0. P. & P. 3/6.**



NEW from Mullard!

UNILEX Audio Modules

Now you can build your own stereo units as you want them, and entirely in your own home.

A good quality stereo amplifier can be built with no electrical knowledge. All solid state—Baxendall tone control circuit—no soldering—terminal block connections throughout.



Everything you need to know about UNILEX SYSTEMS is in the Mullard book "Do it yourself stereo". Superb designs, detailed plans, simple instructions in non-technical language covering 4 systems in 4 price ranges.

Send for your copy now 5/- Post Free.

UNILEX Audio Modules

Amplifier Module EP9000	£2.18.0 each
Pre Amplifier Module EP9001	£3. 2.0 "
Power Supply Module EP9002	£4.12.0 "
Control Panel Assembly and Escutcheon Plate	£3. 5.0

BUILD A STEREO AMPLIFIER FOR ONLY

£16.15.0 P. & P. 7/6

UNILEX PACKAGE DEALS

Unilex Modules	£16.15.0	Unilex Modules	£16.15.0
Garrard 2025	£11.14.1	Garrard SP25 Mk II	£16.11.4
Celestion Speakers	£ 6.17.0	B.S.R. C1 Cartridge	£ 8.17.3
		Celestion Speakers	£ 6.17.0
	£34. 6.1		£34. 6.7
LIND-AIR PRICE 28 gns. P. & P. 20/-		LIND-AIR PRICE 35 1/2 gns. P. & P. 20/-	



LIND-AIR Audio

COLOSSAL REDUCTIONS

OFF AKAI STEREO TAPE RECORDERS

AKAI 4000 STEREO TAPE RECORDER




SAVE
OVER
£20

LIST PRICE £124.10.0

LIND AIR PRICE 99 GNS

A complete stereo tape recorder. 2 speeds 3 1/2 & 7 1/2 i.p.s. and offering full stereo recording and play back facilities.

AKAI 1710 L STEREO TAPE RECORDER

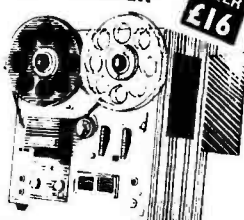

SAVE
OVER
£16

LIST PRICE £89

LIND AIR PRICE 69 GNS

Excellent value for money stereo recorder 3 speeds. Output power 4 watts per channel and every required facility for stereo recording and play back.

AKAI 4000 D STEREO TAPE DECK



SAVE
OVER
£17

LIST PRICE £89.19.1

LIND AIR PRICE 69 GNS

The ideal stereo tape deck for use with existing hi-fi stereo systems to give you the full enjoyment of stereo tape recording and play back.

LA 20 STEREO SYSTEM

SAVE
OVER
£11



Only takes a few minutes to set up ready for use.

**LIND-AIR
PRICE**

39 1/2 gns.

Carr. & Ins. 35/-

Lind-Air LA20 Amplifier **£23.2.0**
Garrard 5-200 Changer with
Sonotone Cartridge **£11.7.6**
Pair of Lind-Air General
Purpose Speakers **£19.0.0**

Recommended Retail Price **£53.9.6**


(Also available with Garrard 3000 changer 4 gns. extra)

SAVE £3-15-6

SCOOP PURCHASE ! !

FAMOUS "SANYO" COLORANO
TRANSISTOR PORTABLE RADIO

Rec. Price **£13.15.0**

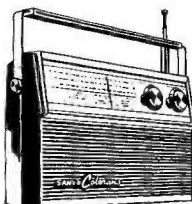

YOURS FOR ONLY **9 1/2 gns.** P. & P. 4/6

(Four HP7 Batteries 3/4 extra)
Elegantly styled quality 10 transistor radio providing wonderful reception of Medium and Long Wave stations plus the new programmes from your local VHF Stations. Grey polystyrene cabinet with silver trim and carrying handle. Size 7" x 4 1/4" x 2 1/4". Fitted with earphone socket which can also be used for extension speaker. Brand New, in maker's cartons. Complete with earphone, instruction manual and Sanyo Guarantee.

HI-FI CATALOGUE NOW READY

5/- P. & P. 1/-



Covers all leading makes plus accessories etc. etc. and full details of Lind-Air money saving systems from 39 1/2 gns.

Over 100 pages, fully illustrated plus 8 page section of P.A. equipment.

NEW BRANCH NOW OPEN AT

**94-96, Upper Parliament Street,
NOTTINGHAM**

Telephone: 40403 (STD 0602)

TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10 watts per channel music power. Inputs for gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oiled walnut cabinet and brushed aluminium front panel.
List Price **£28.7.0**

LIND-AIR PRICE

22 Gns.

P. & P. 10/-


SPECIAL LIND-AIR PURCHASE!

**FANTASTIC SANSUI 200 AM/FM
MULTIPLEX STEREO TUNER
AMPLIFIER**

Solid state 17 watts music power. Fully tunable over Medium wave and VHF/FM Stereo. Inputs for gram and tape etc. Host of outstanding features—details on request. Rec. Retail Price **£89.19.10**.

LIND-AIR PRICE £75.12.0 P. & P. 10/-

BATTERY ELIMINATOR

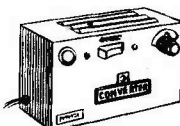

Enables transistor equipment to be operated from AC mains. 0/9/12v. output selector switch and on/off switch. Case size 4 x 2 1/2 x 2 1/2 in. complete with mains lead, connecting leads and instructions. **59/6** P. & P. 3/6.

COMPACT 2-WAY INTERCOMS



For table or wall mounting. Smart two tone grey case size 3 1/2 x 1 1/2 x 2 1/2 in. Complete with lead, staples and 9v battery. **49/6** P. & P. 3/6.

WHARFEDALE SPEAKER KITS



Complete with all components for building into suitable cabinets.

Unit 3 Kit **£11.19.6** each

£21 per pair

Unit 4 Kit **£16.0.0** each

£36 per pair

Unit 5 Kit **£23.10.0** each

£39 per pair

P. & P. 10/- each 15/- pair

18/19, 25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept. L4/12, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

The demands become greater, of course...



and as specialist manufacturers of Loudspeakers we naturally make greater demands—and meet them! Our new kits incorporate the latest progress in the Loudspeaker field and the detailed mounting instructions included in each Kit make the mounting effortless. At the same time you get a quality product at a reasonable price.

For further information please apply to
Messrs. P.F.&A.R. Helme, Summerbridge,
Harrogate, Yorks. HG3 4DR.
Telephone Darley 279 (0423-72-279)

Kit 20-3

Max. Power Input: 40 watts
Frequency Range: 40-20,000 c.p.s.
Standard Impedance: 4 Ω or 8 Ω

Peerless

PEERLESS FABRIKKERNE A/S
11 Gladsaxe Ringvej . 2860 Copenhagen Denmark



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 vols.)** **BASIC ELECTRONICS (6 vols.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"BEST BOOKS IN THIS COUNTRY"

"On going through these books I have found they are the best books I have ever had in this country." S.K.A., London, N.W.2.

"KEY" TO THE KNOWLEDGE"

"Your books have been the 'key' to the knowledge I have needed." J.M., Horsham.

"UNDERSTAND THE BASIC FACTS"

"This is the first time I have been able to understand the basic facts as all other books are too complicated." L.W., Sheffield.

A TECH-PRESS PUBLICATION

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY ☐ BASIC ELECTRONICS ☐

Prices include Postage and Packing.

Signature _____

(If under 21 signature required of parent or guardian)

NAME
BLOCK LETTERS _____

FULL POSTAL
ADDRESS _____

POST NOW FOR THIS OFFER!!

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

MANY ITEMS AT NEW REDUCED PRICES

1N914	1/3	2N3706	2/6	40512	45/6	BC147	3/-	BFY51	4/-
1N3754	4/-	2N3707	2/6	40502	9/6	BC148	3/-	BNX20	3/9
1N4148	1/9	2N3708	2/6	AC107	14/6	BC149	3/-	BY164	10/-
1N5054	4/-	2N3709	2/6	AC126	4/-	BC153	7/-	BY238	3/6
18940	1/-	2N3710	2/6	AC127	4/-	BC154	7/6	C106B1	14/6
2N696	3/6	2N3711	2/6	AC128	4/-	BC167	3/9	MC140	5/-
2N697	3/10	2N3794	24/-	AC176	6/-	BC168	3/6	MJ480	21/-
2N706	2/9	2N3819	7/-	ACY22	4/6	BC169	3/9	MJ481	30/-
2N1131	6/3	2N3820	12/-	ACV41	5/-	BC168	2/3	MJ491	7/6
2N1132	6/2	2N3904	7/6	AD142	14/3	BC169	2/6	NKT403	15/6
2N1302	4/-	2N3906	7/6	AD149	12/-	BC177	6/3	NKT405	16/-
2N1303	4/-	2N4058	4/-	AD161/AD162	14/-	BC178	5/6	OA47	1/3
2N1304	4/6	2N4059	4/9	(matched) 14/-	pr	BC179	6/-	OA90	1/3
2N1305	4/6	2N4060	4/-	AF114	2/-	BC182L	2/6	OA91	1/3
2N1613	6/-	2N4061	4/-	AF115	7/-	BC183L	2/3	OA95	1/3
2N1711	7/-	2N4062	4/-	AF116	6/-	BC184L	2/6	OA99	3/-
2N2147	18/9	2N4284	3/3	AF117	6/6	BC186	8/6	OA200	1/11
2N2218	9/3	2N4286	3/3	AF124	7/6	BC212L	5/-	OA202	2/-
2N2270	12/9	2N4289	3/3	AF127	7/-	BC213L	5/-	OC71	5/6
2N2483	6/3	2N4291	3/3	AF139	9/6	BC214L	5/3	TIP31A	16/-
2N2484	7/6	2N4292	3/3	AF180	18/6	BCY70	4/-	TIP32A	20/-
2N2646	10/9	2N4410	4/9	AF239	9/9	BD121	21/-	TF843	10/6
2N2904	11/-	2N5062	12/3	ASV26	6/6	BD123	21/-	TXF300	3/6
2N2924	4/-	2N5163	5/-	ASV27	8/3	BD124	20/-	ZTX301	3/6
2N2925	4/6	2N5192	25/-	ASV28	8/6	BF167	8/6	ZTX302	4/6
2N2926	2/3	2N5195	28/3	B5041	15/-	BF178	10/6	ZTX303	4/6
2N3053	2/3	2N5457	9/9	HA102	9/-	BF180	12/-	ZTX304	4/6
2N3054	4/6	2N5458	9/9	BA156	4/-	BF194	7/6	ZTX600	5/-
2N3055	15/-	2N5459	9/9	BA130	4/6	BF195	7/6	ZTX601	5/-
2N3325	10/9	40250	14/3	BA156	4/-	BFX29	6/3	ZTX602	6/-
2N3663	11/6	40361	12/6	BC107	2/9	BFX84	5/9	ZTX603	5/-
2N3702	3/6	40362	12/6	BC108	2/6	BFX85	7/-	ZTX604	12/-
2N3703	3/3	40406	10/3	BC109	2/9	BFX87	5/9	ZTX604	12/-
2N3704	2/6	40408	14/6	BC125	11/-	BFX88	6/3	ZTX630	5/5
2N3705	3/5	40430	37/-	BC126	11/-	BFY50	4/6	ZTX531	6/9

PEAK SOUND PRODUCTS

ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo amplifier in modular kit form 12 watts per channel £38/9/-; 25 watts £58/15/- Cabinet kit only £6. These prices nett.

As recently reviewed in Hi Fi Sound.

BAXANDALL SPEAKER SYSTEM

Designed by Peter Baxandall. Superior reproduction for its size. Handles 10 watts with ease. Uses ELAC 15 Ω 50RM109 speaker Unit Kit £13/12/- nett; built £19/8/6 nett.



MAINLINE AMPLIFIER KITS

RCA/818 designed main amplifier kits.

Input sensitivity 500-700mV for full output into 8 Ω.

Power	Kit price including components	Suitable unreg. power supply kit
12W	168/- nett	92/-
25W	190/- nett	N/A
40W	210/- nett	115/1
70W	252/- nett	188/10

30 WATT BAILEY AMP. PARTS

Sensitivity 1.2V for full output into 8 Ω.

Transistors and PCB for one channel £7/5/6 only nett.

Transistors and PCB for two channels £14/11/- only nett. Capacitors and resistors (metal oxide) 40/- per channel nett.

Complete unregulated power supply kit £4.15.0 nett

ZENER DIODES

5% full range E24 values: 400mW; 2.7V to 30V 4/6 each 1W: 6.8V to 82V 9/- each 1.5W: 4.7V to 75V 12/- each Clip to increase 1.5W rating to 3 watts (type 266F) 9d.

CARBON TRACK

POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.

Single gang linear 220 Ω to 2.2M Ω	2/6
Single gang log 4.7K Ω to 2.2M Ω	2/6
Dual gang linear 4.7K Ω to 2.2M Ω	3/6
Dual gang log 4.7K Ω to 2.2M Ω	3/6
Log/anti-log 10K, 47K, 1M Ω only	5/6
Any type with 4 A.D.P. minus switch, extra	2/3

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω Vertical or horizontal mounting 1/- each.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

THE NEW ELECTROVALUE CATALOGUE

48 pages—thousands of items—packed with information generously illustrated with product pictures and technical diagrams. 2/- post free. Add 4/- if required to be sent overseas by air mail.

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	89 Ω-220K Ω	E12	18	16	15
C	1/8W	5%	4.7 Ω-330K Ω	E24	2-5	2	1-75
C	1/4W	10%	4.7 Ω-10M Ω	E12	2-8	2	1-75
C	1/2W	5%	4.7 Ω-10M Ω	E24	3	2-5	2-25
C	1W	10%	4.7 Ω-10M Ω	E12	6	3	4-5
C	1/2W	2%	10 Ω-1M Ω	E24	9	8	7
WW	1W	10% ± 1/20 Ω	0.22 Ω-3.9 Ω	E12		1/6 all quantities	
WW	3W	5%	12 Ω-10K Ω	E12		1/6 all quantities	
WW	7W	5%	12 Ω-10K Ω	E12		1/9 all quantities	

Codes: C = carbon film high stability low noise
MO = metal oxide Electroil TR5 ultra low noise
WW = wire wound Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 59/6 nett.

Components pack for stereo inc. mains transformer, controls etc. £4.15.0 nett.

PLESSEY SL403A Now only 42/8 nett 3W into 7.5 Ω for 18W supply. Application data sent with two more.

WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each
SLIDER SWITCHES D.P.D.T. 3/- each

NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9
Round chrome bezel red, amber, clear 4/9 each

Toggle switches, 250V a.c. 1.5A.
chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/8; D.P.D.T. 5/8; S.P.D.T. centre off 5/-.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC (70 points) only 25/-; Compact T-DeC (increased capacity, may be temperature-cycled, T-DeC (208 points) only 50/- post free. Full range stocked.

Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1d. on total resistor order)

MULLARD polyester C280 series

250V 20%; 0.01; 0.022; 0.033; 0.047 8d ea. 0.068; 0.1 8d ea.; 0.15 11d.; 0.22 1/-; 10/-; 0.33 1/5; 0.47 1/8; 0.68 2/3; 1μF 2/9; 1.5μF 4/2; 2.2μF 4/8.

MULLARD SUB-MIN ELECTROLYTIC

C428 range axial lead 1 1/3 each
Values (μF/V): 0.04/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/64; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 100/2.5; 100/64; 400/10; 400/2.5; 320/64; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 5/8; 1000/50 8/2; 1000/100 18/3; 2000/25 7/4; 2000/50 11/4; 2000/100 11/4; 2000/100 28/8; 2500/64 15/5; 2500/70 18/8; 5000/25 12/8; 5000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/8; 10000/50 44/-; 10000/70 61/-.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 2/-; 100/25 2/-; 100/50 2/8; 250/25 2/8; 330/25 2/8; 250/50 3/9; 500/25 3/9; 500/50 4/8; 1000/25 4/-; 1000/50 6/-; 2000/25 8/-.

SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 5/50 1/- ea. 10/10; 10/25; 10/50; 33/10; 50/10 1/- ea. 22/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

ENAMELLED COPPER WIRE, even No 8 W.G. only. 2oz reels 16-22 S.W.G. 4/3; 24-30 S.W.G. 5/-; 32-34 S.W.G. 5/8; 36-38 S.W.G. 6/3; 4 oz reels 16-22 S.W.G. only 7/6.

ELECTROVALUE

(Dept. PW.12) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475

R+TV

RADIO & TV COMPONENTS (Acton) Ltd.

21c High Street, Acton, London W.3. 6NG

Also at 323 Edgware Road, London, W.2.

ALL ORDERS BY POST TO OUR ACTON BRANCH

Terms C.W.O.

All enquiries S.A.E.

Complete Stereo System £41

WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½in x 6½in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £66.0 each plus 15/- p. & p.

Complete stereo system £41 plus £2 10 p. & p. or with Mk II Amplifier and Magnetic Cartridge £45 & £2 10 p. & p.

The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½in, 6in, 2½in, in simulated

teak case. **BUILT & TESTED.**

MkII (MAG P.U.) £15.15 plus 10/- p. & p. Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

The £29-10-0 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.


SPECIFICATION—

R.M.S. power output 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY. Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30db at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.

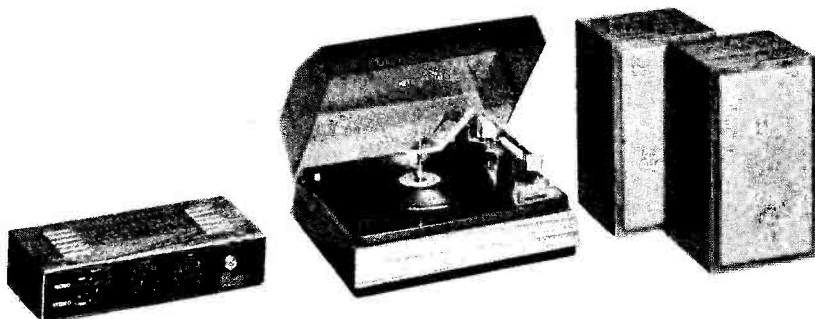TONE CONTROL Treble lift and cut Separate on off switch. A preset balance control.




Duetto integrated transistor stereo Amp. Garrard Changer from Cover and teak finish plinth Duo Type I speakers (see opp. page) The above items purchased together

£9.10.0 + 7/6 p&p.
£7.10.0 + 7/6 p&p.
£4.15.0 + 7/6 p&p.
ea. £4. 4.0 + 7/6 p&p.
£29.10.0 + £1.10 p&p.

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

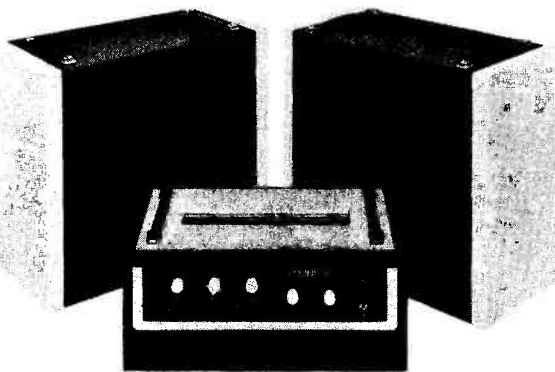

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: \pm 13dB at 60Hz. Treble Control Range: \pm 12dB at 10 KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20" \times 20" \times 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £45 Plus 60/- P. & P.

Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.10.0 plus 20/- P. & P.

Speakers £12.10.0 each plus 30/- P. & P.




The ELEGANT SEVEN Mk. III (350m W Output)

7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

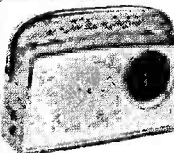Price £5.5.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS



The DORSET (600m W Output)

7-transistor fully tunable M.W.—L.W. superhet portable —with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 extra.

Price £5.5.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS



The Classic


Simulated teak case

£9.10

Plus P. & P. 7/6

SPECIFICATION:

Sensitivities for 10 watt output
at 1KHz into 3 ohms. Tape Head: 3 mV at 31.
p.s.) Mag. F.U.: 2 mV. Cor. P.U.: 80mV. Tuner: 100mV.
Aux: 100mV. Tape/Rec. Output. Equalisation for each
input is correct to within \pm 2dB (R.I.A.A.) from 20Hz to 20KHz.
Tone Control Range: Bass: 13dB at 60Hz. Treble: \pm 14dB at 15KHz. Total Dis-
tortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V.
Size 12 1/2in long, 4 1/2in deep, 2 1/2in high. Built and tested

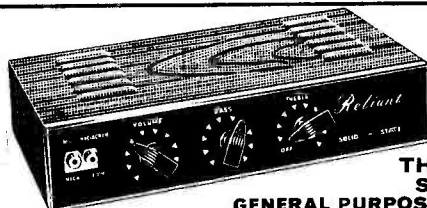

THE RELIANT SOLID-STATE GENERAL PURPOSE AMPLIFIER

SPECIFICATIONS

Output \pm 10 watts. Output impedance—3 to 4 ohms.
Inputs \pm 1. xtal mic 10mV Tone Controls—Treble control range \pm 12dB at 10KHz.
2. gram/radio 250mV. Bass control range \pm 13dB at 100Hz.
Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and
40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar
type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10 1/2in. x
4 1/2in. x 2 1/2in. For use with Std. or L.P. records, musical instruments, all makes of
pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from
gram. and mike. Built and tested.

RELIANT Mk. II in simulated teak case £7.5 plus 7/6 P. & P

THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:—
Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high
flux 6in. x 4in. speaker and 2 1/2in. speaker. Teak finish 12in. x 6 1/2in. x 3 1/2in. 4 guineas
each. 7/6 P. & P.

LIQUIDATED STOCK DANSETTE TOURISTE MK3 CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold completely built for £15.4.6. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4 1/2in deep.

See top of previous page for address



SET OF PARTS

£6.6.0


plus 7/6 P. & P.

Circuit diagram 2/6. Free with parts

Speaker, baffle and fixing kit
25/- extra plus 4/- p. & p. Postage
free when ordered with parts.

RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED

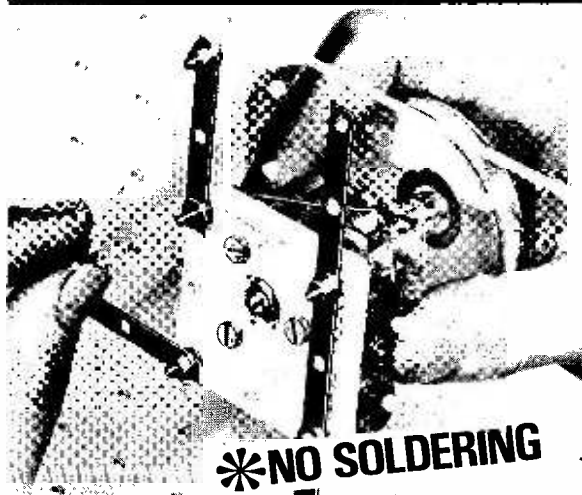Build working radio receivers and electronic circuits in an evening



Beginner or advanced student— you learn fast with Radionic kits

Circuits work first time with the Radionic 'no soldering' method. With the X30 kit, build 33 experiments: a printed circuit transistor radio, burglar alarm, morse code buzzer etc.

The more advanced kits are suitable for G.C.E., City and Guilds, National Certificate and higher. Every set includes construction notes and all circuit diagrams.

It's so easy for you to build *and* learn because you construct circuits that resemble the theoretical diagram. Re-use components easily, too — they're screw-in-mounted.

Send off this coupon today.

TO: RADIONIC PRODUCTS LTD.,
St. Lawrence House, Broad Street, Bristol BS1 2HF

PW4

Please send me full details of all Radionic Kits/please send me one
Radionic Kit X30, for which I enclose £7 19s. 6d.
(delete where inapplicable)

Name _____

Address _____



Adamin

MICRO SOLDERING INSTRUMENTS

A range of micro soldering instruments combining high performance with really small dimensions and providing exceptional versatility.

Weighing about $\frac{1}{2}$ oz. (less flex) these miniature tools ensure the utmost accuracy and safety in use, resulting in consistently high standards of soldering with minimum operator fatigue.

Ultra-slim unbreakable nylon handles give a cool, comfortable grip for sustained delicacy of operation.

Slip-on bits are fitted over the element shaft, so absorbing all the heat produced and giving high performance with rapid heating and recovery. A wide range of interchangeable tip sizes is available to suit different types of work.

There are ADAMIN models from, 8 to 24 watts, in voltages from 6v. to 240v.

Please ask for leaflet A/10.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL
Telephone 01-688 8589 and 4559



CAVE

TOP DISCOUNTS HI FI

5 Bridge Street
Richmond Surrey
01 948 1441 till 8pm

OPEN ALL DAY SATURDAYS
FIRST CLASS REPAIR SERVICE
UP TO 15% DISCOUNT ON
LP RECORDS
SEND FOR LISTS

TURNTABLES, BASES & COVERS

	List Price	Cave's Cash Price
MacDonald MP60 wired to din standard with p. & c.	£23 16 4	£20 0 0
MacDonald 510 wired to din standard with p. & c.	£27 15 10	£23 7 0
MacDonald 510 wired to din standard with p. & c.	£24 16 10	£20 18 0
MacDonald 510 wired to din standard with p. & c.	£21 15 4	£18 6 0
AR Universal Comp., Arm. Base & Cov. (less cart.)	£77 9 0	£71 7 0
Dual 1219 less cart.	£60 8 0	£54 6 0
Dual 1209, less cart.	£42 12 0	£38 6 0
Dual CK6 Base	£9 15 0	£8 16 0
Dual CH5 Cover	£7 5 0	£6 11 0
Dual CK20 Base for 1219	£12 2 0	£11 5 0
Dual CH20 Cover for 1219	£12 2 0	£11 5 0
Trans. Ref. Turnt. w. Arm	£98 2 0	£86 5 0
Trans. Turnt. w. Arm & C.	£57 12 0	£50 19 0
Garrard AP.76	On application	
Garrard 401	£31 14 0	£28 10 0
Garrard SL95B	£45 9 0	£38 19 0
Garrard SL75B	£39 12 0	£33 13 0
Garrard SL65B	£19 8 0	£16 12 0
Garrard 72B	£30 2 0	£25 18 0
Garrard 40B	£12 11 0	£10 16 0
Garrard AP75	£23 12 0	£18 15 0
Garrard SP25 Mk. 2	£15 9 0	£11 12 0
Garrard SP25 Mk. 3	On application	
P & C for SP25	£10 2 0	£4 11 0
SPC4 Cover & WB4 Base	£7 11 0	£6 15 0
SPC4 Cover & WB1 Base	£10 2 0	£9 3 0
SPC4 Cover & WB5 Base (for SP25 playing w. cov.)	£26 12 6	£22 7 0
Golding GL69 Trans. Unit	£39 12 2	£33 12 0
Golding GL69 with P. & C.	£28 13 4	£26 0 0
Golding GL69 with Plinth, Cover & G800	£52 12 3	£42 10 0
Golding GL75 Trans. Unit	£23 9 0	£20 1 0
Golding GL75 with P. & C.	£52 0 0	£46 17 0
Golding GL75 with Plinth, Cover & G800E	£70 16 3	£58 19 0
Plinth for GL75	£28 13 4	£8 0 0
Golding G59 Transcription unit without arm	£26 0 0	£23 8 0
Philips GA202	£69 0 0	£60 14 0
Thorens TD150A Mk. 2 w. Arm.	£43 13 0	£38 19 0
Thorens TD150AB w. Arm & Base	£47 9 0	£41 10 0
Thorens TX11 Cover	£4 2 0	£3 10 0
Thorens TD124/11	£46 16 0	£42 5 0
Thorens TD125	£75 17 0	£66 19 0
Thorens TD124 P & C 9"	£12 0 0	£10 16 0
Thorens TD124 P & C 12"	£15 4 0	£13 13 0
Pioneer PL11AC w. Arm, Base & Cov.	£48 17 0	£40 19 0
Pioneer PL11AC w. AT35X Elipt. Cart.	£73 2 0	£55 18 0

PICK UP ARMS

Golding L69 Arm	£9 18 2	£8 14 0
Golding L75 Arm	£12 12 0	£10 10 0
Transc. Fluid Arm 9 or 10"	£22 6 0	£19 12 0
SME 3009 with S2 Shell	£34 9 0	£29 19 0
SME 3012 with S2 Shell	£36 14 0	£31 19 0
Audio Tech. AT 1005	£19 19 0	£17 0 0

AMPLIFIERS, TUNERS & TUNER AMPS.

Akai AA6600 Tuner/Amp.	£142 10 7	£125 9 0
AR Amplifier	£174 0 0	£156 12 0
Wood Case for above—Walnut	£11 10 0	£10 7 0
AR Receiver Tun./Pre-Amp/Amp.	£380 15 0	£350 14 0
Wood Case for above—Walnut	£18 14 0	£17 5 0
ARD 2000 Amp. Metal	£46 4 0	£39 5 0
ARD 2000 Amp. Wood	£49 7 0	£42 0 0
Armstrong 521	£56 0 0	£48 10 0
Armstrong 523 AM/FM Tun.	£53 15 0	£47 19 0
Armstrong 524 FM Tun.	£41 17 0	£37 14 0
Armstrong 525 Tun./Amp.	£91 17 0	£83 19 0
Armstrong 526 Tun./Amp.	£104 14 0	£93 19 0
Armstrong M8 Decoder	£9 10 0	£7 15 0
Armstrong M8 Decoder	£9 10 0	£7 15 0
Cambridge P40 Amp.	£75 0 0	£63 15 0
Dual CV20 Amp.	£48 10 0	£41 5 0
Dual CV40 Amp.	£73 10 0	£62 10 0
Dual CV80 Amp.	£89 10 0	£76 0 0
Dual CT15 Tun.	£81 15 0	£71 17 0
Dual CT16 Tun.	£106 0 0	£93 3 0
Dual CR40 Tun./Amp.	£178 1 0	£156 10 0
Decca A3000 Amp.	£69 10 0	£60 15 0
Decca T1000 Tun.	£32 0 0	£28 16 0
Decca T2000 Tun.	£59 0 0	£52 19 0
Decca X70 Decoder	£7 7 0	£6 19 0
Dulci 207 Amp. Chassis	£25 0 0	£21 5 0
Dulci 207M Amp. Case	£23 0 0	£20 10 0
Dulci FM77 Tun.	£23 0 0	£20 10 0

LOUDSPEAKERS

Dulci FM77S Tun.	£31 0 0	£27 5 0
Ferrograph F307 Amp. Case	£59 0 0	£46 19 0
Leak 30 Amp. Chassis	£53 0 0	£42 10 0
Leak 30 Amp. Case	£59 10 0	£48 15 0
Leak 70 Amp. Chassis	£63 0 0	£52 0 0
Leak 70 Amp. Case	£69 10 0	£58 10 0
Leak Stereofonic Tun. Chas.	£59 18 0	£52 19 0
Leak Stereofonic Tun. Case	£61 1 0	£53 10 0
Lux SQ1220 Amp.	£124 10 0	£89 13 0
Lux SQ505 Amp.	£97 10 0	£69 12 0
Lux SQ777 Amp.	£66 7 0	£52 10 0
Lux SQ606 Amp.	£84 0 0	£59 19 0
Lux HQ555 Tun./Amp.	£168 0 0	£119 18 0
Lux WL515 Tun.	£108 5 0	£75 15 0
Lux WL313 Tun.	£143 14 0	£92 11 0
Teleton S720 Amp.	£36 0 0	£29 19 0
Sinclair	£4 9 0	£3 16 0
2.30 Amp.	£4 9 0	£3 16 0
2.10 Amp.	£5 9 0	£4 3 0
Stereo 60 Control Unit	£9 19 0	£8 10 0
Stereo 60 Filter Unit	£5 19 0	£5 2 0
PZ-5 Supply Unit	£4 19 0	£4 5 0
PZ-5 Supply Unit	£7 19 0	£6 16 0
PZ-5 Supply Unit	£5 19 0	£4 5 0
IC-10 Amp.	£2 19 0	£2 15 0
Z-12 Amp.	£4 9 0	£3 16 0
PZ4 Power Supply	£4 19 0	£4 5 0
Stereo 25 for 2x12 Amp.	£9 19 0	£8 10 0
2000 Amplifier	£30 9 0	£22 19 0
2000 FM Tuner	£26 14 0	£22 19 0
3000 Amp.	£61 19 0	£52 10 0
Neoteric 60	£25 0 0	£21 19 0
Project 60 FM Tuner	£4 4 0	£3 19 0
Stereo Decoder	£4 4 0	£3 19 0
J. Sugden A21 Amp.	£59 0 0	£47 19 0
Teleton SAQ 203E Amp.	£27 15 0	£19 19 0
Teleton A150 Amp.	£29 0 0	£19 19 0
Teleton CR107 Tun./Amp.	£27 0 0	£26 19 0
Teleton TFS50 Tun./Amp.	£74 0 0	£62 16 0
Teleton GA101 Amp.	£33 15 0	£23 19 0
Teleton GT101 Tun.	£45 10 0	£38 0 0
Teleton CR107 & Speakers	£29 19 0	£29 19 0
Teleton CR24 Tun./Amp.	£35 0 0	£29 19 0
Teleton RA200 Tun./Amp.	£51 15 0	£44 19 0
Teleton CR15 Tun./Amp.	£18 13 0	£13 19 0
Teleton STQ204 Tun./Amp.	£50 10 0	£42 5 0
Teleton T2000 Tun./Amp.	£51 0 0	£32 19 0
Teleton SAQ5015 Amp.	£52 10 0	£43 6 0
Wharfedale Tun./Amp. 100.1	£131 5 0	£112 13 0
Philips RH690 Tuner	£44 10 0	£39 3 0
Philips RH691 Tuner	£89 0 0	£78 4 0
Philips RH781 Tun./Amp.	£74 19 0	£62 4 0
Philips RH790 Tun./Amp.	£135 0 0	£118 16 0
Philips RH580 Amp.	£28 0 0	£23 16 0
Philips RH590 Amp.	£51 15 0	£43 19 0
Philips RH591 Amp.	£76 15 0	£65 5 0
Pioneer SX440 Tun./Amp.	£111 0 0	£92 15 0
Pioneer LX440 Tun./Amp.	£116 9 0	£97 5 0
Pioneer LX800 Tun./Amp.	£206 18 0	£181 16 0
Pioneer SX770 Tun./Amp.	£156 0 0	£130 5 0
Pioneer SX990 Tun./Amp.	£193 2 0	£161 5 0
Pioneer SX1500 Tun./Amp.	£225 17 0	£188 13 0
Pioneer TX500 Tuner	£71 5 0	£56 0 0
Pioneer TX900 Tuner	£151 19 0	£126 15 0
Pioneer SA500 Amp.	£61 19 0	£49 12 0
Pioneer SA700 Amp.	£97 19 0	£78 7 0
Pioneer SA900 Amp.	£133 16 0	£107 0 0
Pioneer SR202 Rereb Amp.	£45 8 0	£36 7 0
Pioneer KX330 Tun./Amp.	£78 15 0	£66 0 0
Quad 303 & 33 Amp.	£98 0 0	£87 19 0
Quad FM Tuner	£51 0 0	£46 0 0
Quad AM3 Tuner	£48 0 0	£44 12 0
Radford SMT3 Tun.	£76 10 0	£64 19 0
Radford SC30 Amp.	£106 0 0	£84 16 0
Revox A50 Amp.	£106 1 0	£92 19 0
Revox A75 Tuner	£162 15 0	£148 0 0
Rogers Ravensbourne	£64 0 0	£54 0 0
Rogers Ravensbrook	£47 10 0	£41 7 0
Rotel 100 Amp.	£45 10 0	£35 19 0
Rotel 120 ST Tuner	£48 17 0	£41 19 0
Rotel 130 Tuner	£79 17 0	£67 12 0
Rotel FAX330 Tun./Amp.	£95 0 0	£79 16 0
Rotel FAX660 Tun./Amp.	£129 0 0	£99 19 0
Secom SA500 Amp.	£31 17 0	£26 19 0
Sansui 350 Tun./Amp.	£129 1 0	£113 10 0
Sansui 400 Tun./Amp.	£127 4 0	£99 0 0
Sansui 500 Tun./Amp.	£145 9 0	£128 9 0
Sansui 2000 Tun./Amp.	£162 3 0	£142 12 0
Sansui AU222 Amp.	£62 17 0	£53 10 0
Sansui AU555 Amp.	£80 9 0	£68 8 0
Sansui TU777 Tuner	£94 5 0	£82 19 0
Sansui TU555 Tuner	£77 9 0	£68 3 0

TAPE RECORDERS

Celestion 15	£29 0 0	£25 8 0
Celestion 25	£59 17 0	£50 17 0
Goodmans Magister	£57 0 0	£49 18 0
Magnum K	£40 2 0	£32 10 0
Mezzo 2 Walnut	£30 18 0	£22 19 0
Mezzo 2 Teak	£30 18 0	£22 19 0
Manbo	£22 8 0	£18 5 0
3005	£22 19 0	£18 19 0
Minister	£25 0 0	Pair
Mezzo 3	Price on application	
Kel Cresta	£22 3 0	£19 5 0
Kel Celeste Mk. 2	£29 0 0	£22 19 0
Kel Concorde	£43 10 0	£33 10 0
Kel Concerto	£53 10 0	£42 19 0
Kel Chale	£34 16 0	£30 17 0
EMI "Richmond"	£32 0 0	£22 19 0
Jordan Watts Module	£12 0 0	£10 10 0
Jordan Watts Jumbo	£19 16 0	£17 7 0
Leak Mini Sandwich	£29 15 0	£20 10 0
Tk/Rswd/Walnut	£29 15 0	£22 10 0
Leak Sandwich Walnut	£45 10 0	£29 19 0
Leak Sandwich Teak	£45 10 0	£31 5 0
Leak Sandwich Mahogany	£45 10 0	£32 10 0
Leads for above		
Lowther PM6	£46 10 0	£33 11 0
Lowther PM7	£58 0 0	£49 7 0
Philips RH491	£23 0 0	£20 5 0
Philips GL561/70 Enc.	£26 19 0	£22 19 0
Philips RH491	£11 0 0	£9 18 0
Philips CS53	£32 0 0	£24 9 0
Quad Electrostatic	£66 0 0	£59 9 0
Radon 404	£13 17 0	£12 5 0
Radon Amethyst	£36 0 0	£31 10 0
Radon Sapphire	£47 10 0	£41 11 0
Rogers Ravensbrook	£31 8 0	£27 13 0
Sansui SP30	£22 10 0	£19 9 0
Sansui SP200	£56 5 0	£53 11 0
Tannoy 12" Lancaster	£63 5 0	£55 7 0
Tannoy 15" Lancaster	£59 10 0	£48 19 0
Tannoy Richmond 12"	£51 0 0	£35 18 0
Tannoy 111LZ	£13 18 0	£10 10 0
Thames Vee Gee	£19 0 0	£16 15 0
Wharfedale Denton	£39 10 0	£32 10 0
Wharfedale Linton	£39 10 0	£32 10 0
Wharfedale Dovedale 3	£29 10 0	£23 19 0
Wharfedale Melton	£59 10 0	£49 18 0
Wharfedale Rosedale		
Speaker Accessories		
Din Speaker Plugs		£0 3 0
Speaker Cable p/d.		£0 1 0

TAPE RECORDERS

Revox 1102/1104	£204 15 0	£180 10 0
Revox 1222/1224	£246 15 0	£217 10 0
Revox 1997 Dust Cover	£5 5 0	£4 18 0
Ferrograph 713	£182 10 0	£166 0 0
Ferrograph 702/704	£207 0 0	£182 10 0
Ferrograph 722/724	£242 10 0	£202 19 0
Ferrograph Cover	£6 5 0	£5 16 0
Akai 4000D	£89 19 0	£72 19 0
Akai 1710L	£89 0 0	£77 12 0
Akai 4000	£124 18 0	£102 19 0
Akai X5000L	£177 19 0	£156 13 0
Akai X5000W	£177 19 0	£156 13 0
Akai M10L	£245 1 0	£215 13 0
Tandberg 64X	£147 13 0	£121 4 0
Philips 4302	£35 17 0	£29 19 0
Philips 4307	£49 10 0	£42 10 0
Philips 4308	£26 7 0	£21 10 0
Philips 4404	£83 0 0	£71 5 0
Philips 4407	£105 0 0	£90 2 0
Philips 4408	£139 0 0	£119 6 0
Philips 2502	£49 10 0	£42 11 0
Philips 2200	£14 18 0	£12 5 0
Philips EL3302	£26 7 0	£21 10 0
Philips 2400	£69 0 0	£60 13 0
Philips 2400 inc. Speakers	£86 0 0	£75 13 0
Philips 2401	£81 0 0	£71 5 0
Philips 2401 inc. Speakers	£99 0 0	£87 0 0
Philips N2202 Car Stereo	£29 18 0	£28 18 0
Cassette Player	£42 0 0	£29 19 0
Sanyo Cassette		£20 19 0
Grundig TK120	£39 5 0	£28 18 0
Grundig TK124	£44 18 0	£35 7 0
Grundig TK144	£49 19 0	£42 5 0
Grundig TK149	£57 12 0	£46 19 0
Grundig TK121	£54 15 0	£45 15 0
Grundig TK141	£59 4 0	£49 14 0
Grundig TK146	£68 2 0	£57 3 0
Truvox R44		£45 10 0
Teleton T710	£34 15 0	£30 10 0
Teleton SL40	£37 10 0	£32 19 0
Teleton FBX 510D	£37 10 0	£32 19 0
Crown CTR8750	£32 11 0	£24 19 0

P & C on most units is 12/8. Insurance: 2/- per £10 value. P & C on Tape Recorders is 17/6. P & C on cartridge is 3/6. Prices quoted above are our selling prices at the time of going to press and are subject to alteration E. & O. E. Special Carriage Charges for 48hr Delivery Services.

it makes SOUND SENSE, buy from CAVES

A COMPLETE STEREO SYSTEM

SAVE OVER £30



L & M STEREO SYSTEM COMPRISES—

Garrard SP25 record player with Goldring G800 magnetic cartridge complete with plinth and cover and ready wired to 5-pin Din plug ...
Teleton SAQ203 Amplifier ...
Two full size 30" x 10" x 7 1/2" internationally acclaimed Musette Speakers...

	Rec. Retail Price	Our Price
Garrard SP25 record player with Goldring G800 magnetic cartridge complete with plinth and cover and ready wired to 5-pin Din plug ...	34 15 0	21 0 0
Teleton SAQ203 Amplifier ...	28 7 0	20 0 0
Two full size 30" x 10" x 7 1/2" internationally acclaimed Musette Speakers...	38 0 0	29 0 0
	£101 2 0	£70 0 0

BARCLAYCARD CREDIT FACILITIES AVAILABLE FOR NEW AND EXISTING HOLDERS

OTHER COMBINATIONS OF HI FI EQUIPMENT AVAILABLE ON REQUEST. AND MORE L & M SENSATIONAL BARGAINS

Plinth and Cover to fit most makes of GARRARD TURNTABLES complete and ready for easy assembly with perspex cover of Neutral Smoke Tint. Spindle can be left in position with cover on.
75/- Carr. Paid
ALSO AVAILABLE L & M Plinths and Covers fully assembled.
85/- Carr. Paid

L & M SUPPLIES

HAINAULT HOUSE, HAINAULT STREET, NEW ELTHAM SE9

Tel. 01-850 0829


Own Car Park. Callers Welcome.

FAL

AMPLIFIERS OF QUALITY AND RELIABILITY at the right price


'PHASE 12'

An extremely attractive solid state stereo amplifier ideal for unit audio use. Facilities include MAGNETIC and CERAMIC P.U. RADIO, TAPE etc. Output 6 watts per channel Freq. Response 40-40,000 c.p.s.—3 dB. Hum level 7—4 dB. Controls include Input Selector, Volume, Balance, Bass, Treble and Stereo/Mono Switch. Black and silver facia panel with satin silver control knobs. Slimline finish enhanced by good quality Teak cabinet housing

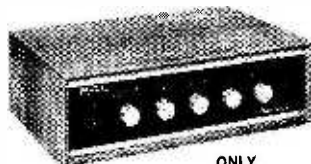

ONLY **24 Gns.**

Recommended Retail Price

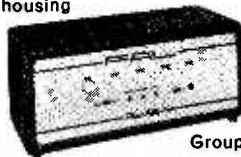

'PHASE 50' P.A. AMPLIFIER

A solid state A.C. mains unit for Vocal and Instrumental Groups and General Public Address use.

29 GNS. ★ 50 watts output (Peak) ★ High sensitivity
★ 3-30 ohms matching
★ 3 separately controlled inputs
★ Freq. Response 22 c.p.s.—30 Kcs

For heavy demands on power, 'Phase 100' will provide 100 watts at music rating. 4 Inputs. Master volume etc.

59 GNS.

For leaflets on the above and other models in the FAL range please send SAE to:—

FUTURISTIC AIDS LTD, 104 Henconner Lane, Leeds 13



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY. ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 15/-



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 15/-



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	3/-
Size 5 (ill. ultra-std)	Savbit	18	3/-
15	60/40	22	4/-

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5.5 Mc/s. Sensitivity 38mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. \$22.10.0. Carriage 30/-.

AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12mA to 1.2 Amp. Resistance 12 ohm to 120 mΩ. HF, VHF, UHF Voltage with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. \$55 each. Carr. 10/-.

CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s to 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V D.C. 0.3A. Excellent condition. \$9/8. Carr. 7/6.

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. \$23.6. Carr. 7/6. Or brand new with accessories. \$7.18.6. Carr. 7/6.

B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. \$27.10.0 each. Carr. 10/-.



Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airco. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. \$45. Carr. 20/-.

AVO CT-38 ELECTRONIC MULTIMETERS

High quality 97 range instrument which measures A.C. and D.C. Voltage, Current, Resistance and Power Output. Ranges D.C. volts 200mV-10,000V. (10 meg Ω -11 meg Ω input). D.C. current 10μA-25 amps. Ohms, 0-1,000 meg Ω. A.C. volt 100mV-250V (with R.F. measuring head up to 250 Mc/s). A.C. current 10μA-25 amps. Power output 500 micro-watts-5 watts. Operation 0/110/200/250V. A.C. Supplied in perfect condition complete with circuit lead and R.F. probe. \$25. Carr. 15/-.

ADMIRALTY B.40 RECEIVERS

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 500Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230 volt A.C. Size 19 1/2 x 13 1/2 x 16in. Weight 114lb. Offered in good working condition. \$22.10.0. Carr. 30/-.



TO-3 PORTABLE OSCILLOSCOPE
8in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.6 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.9v p-p/CM. Bandwidth 1.5 cps-800KHz. Input imp. 2 meg Ω 25pF. Time base. 5 ranges 10 cps-300 KHz. Synchronisation. Internal external. Illuminated scale 140 x 215 x 330 mm. Weight 154 lb. 220/240V. A.C. Supplied brand new with handbook. \$37.10.0. Carr. 10/-.

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW.100	TYPE S-80
100 x 80 mm.	80 mm.
square fronts	square fronts
50μA 69/6	50μA 82/6
50-0-50μA 67/6	50-0-50μA 59/6
100μA 67/6	100μA 59/6
100-0-100μA 65/-	100-0-100μA 57/6
500μA 62/6	500μA 49/6
1mA 59/6	1mA 49/6
20V. D.C. 59/6	20V. D.C. 49/6
50V. D.C. 59/6	50V. D.C. 49/6
300V. D.C. 59/6	300V. D.C. 49/6
1 amp. D.C. 59/6	1 amp. D.C. 49/6
5 amp. D.C. 59/6	5 amp. D.C. 49/6
300V. A.C. 59/6	300V. A.C. 52/6
VU Meter 75/-	VU Meter 67/6

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in. x 4 1/2in. fronts.	Type MR.38P. 1 1/2in. square fronts.
50μA 52/-	200mA 27/6
100μA 52/-	300mA 27/6
500μA 52/-	500mA 27/6
1mA 52/-	750mA 27/6
5mA 52/-	1 amp. 27/6
15mA 52/-	2 amp. 27/6
30 amp. 52/-	5 amp. 27/6
20V. D.C. 52/-	10 amp. 27/6
50V. D.C. 52/-	3V. D.C. 27/6
150V. D.C. 52/-	10V. D.C. 27/6
300V. D.C. 52/-	15V. D.C. 27/6
15V. A.C. 52/-	20V. D.C. 27/6
300V. A.C. 52/-	100V. D.C. 27/6
8 Meter 1mA 52/-	150V. D.C. 27/6
VU Meter 75/-	300V. D.C. 27/6
1 amp. A.C. 52/-	500V. D.C. 27/6
5 amp. A.C. 52/-	750V. D.C. 27/6
10 amp. A.C. 52/-	15V. A.C. 27/6
20 amp. A.C. 52/-	50V. A.C. 27/6
30 amp. A.C. 52/-	10 amp. A.C. 27/6
	20mA 27/6
	50mA 27/6
	100mA 27/6
	150mA 27/6
	S Meter 1mA 32/-
	VU meter 42/-

Type MR.52P. 2 1/2in. square fronts.	Type MR.45P. 2in. square fronts.
50μA 42/-	50μA 45/-
50-0-50μA 42/-	50-0-50μA 42/-
100μA 42/-	100μA 42/-
100-0-100μA 42/-	100-0-100μA 37/6
500μA 42/-	200μA 37/6
1mA 42/-	500μA 32/-
5mA 42/-	500-0-500μA 30/-
15mA 42/-	1mA 30/-
30 amp. 42/-	5mA 30/-
20V. D.C. 42/-	10mA 30/-
50V. D.C. 42/-	50mA 30/-
300V. D.C. 42/-	500mA 30/-
15V. A.C. 42/-	1 amp. 30/-
300V. A.C. 42/-	
8 Meter 1mA 42/-	
VU Meter 42/-	
1 amp. A.C. 42/-	
5 amp. A.C. 42/-	
10 amp. A.C. 42/-	
20 amp. A.C. 42/-	
30 amp. A.C. 42/-	

Type MR.65P. 3 1/2in. x 3 1/2in. fronts.	"SEW" BAKELITE PANEL METERS
50μA 42/-	Type MR.65. 3 1/2in. square fronts.
50-0-50μA 42/-	500mA 35/-
100μA 42/-	1 amp. 35/-
100-0-100μA 42/-	5 amp. 35/-
500μA 42/-	15 amp. 35/-
1mA 42/-	30 amp. 35/-
5mA 42/-	50 amp. 35/-
15mA 42/-	5V. D.C. 35/-
30 amp. 42/-	10V. D.C. 35/-
20V. D.C. 42/-	20V. D.C. 35/-
50V. D.C. 42/-	50V. D.C. 35/-
300V. D.C. 42/-	150V. D.C. 35/-
8 Meter 1mA 42/-	300V. D.C. 35/-
VU meter 42/-	30V. A.C. 35/-
1 amp. A.C. 42/-	150V. A.C. 35/-
5 amp. A.C. 42/-	500mA A.C. 35/-
10 amp. A.C. 42/-	1 amp. A.C. 35/-
15 amp. A.C. 42/-	5 amp. A.C. 35/-
20 amp. A.C. 42/-	10 amp. A.C. 35/-
30 amp. A.C. 42/-	20 amp. A.C. 35/-
50 amp. A.C. 42/-	50 amp. A.C. 35/-
5V. D.C. 42/-	VU meter 62/-

MARCONI
TF885 VIDEO OSCILLATORS
0-5 mc/s Sine Square Wave 245. Carr. 20/-.

MOVING IRON-
ALL OTHERS MOVING COIL
Please add postage

EDGWISE METERS	TYPE PE.70. 3 1/2in. x 1 1/2in. x 1 1/2in. deep.
50μA 60/-	50μA 52/-
50-0-50μA 57/6	1mA 47/6
100μA 57/6	300V. A.C. 47/6
100-0-100μA 55/-	
500μA 55/-	
1mA 55/-	
1-0-1mA 55/-	
5mA 55/-	
10mA 55/-	
100mA 55/-	
	VU meter 65/-

SEND FOR ILLUSTRATED BROCHURE OF SEW PANEL METERS-DISCOUNTS FOR QUANTITIES

POWER RHEOSTATS
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush work. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 14/6. P. & P. 1/6.
50 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 21/- P. & P. 1/6.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms, 27/6 P. & P. 1/6.


FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$26.19.6 P. & P. 3/-.



MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. \$20. Carr. 15/-.

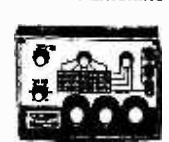TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. 6 Ranges ±1%. L1 μH - 111 HENRY'S. 6 Ranges -2% C. 10pF - 1110mF. 1000-11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. \$20. P. & P. 5/-.

COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES
D.C. coupled. Band width 1Kc/s. Perfect order. \$25. Carr. 30/-.

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. 7/6. Size 140 x 215 x 170 mm.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS
Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. \$12.10.0 Carr. 10/-.

TY75 AUDIO SIGNAL GENERATOR
Sine Wave 20c/s to 200 Kc/s. Square Wave 200c/s to 30Kc/s. High and low impedance output. Output variable up to 6 volts 220/240 volts A.C. Size 210 x 150 x 190 mm. Brand new with instructions. \$16. Carr. 7/6.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER
2 pF-2000 mF
2 ohm-200 megohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New \$17.10.0 Carr. 7/6.



270° 500 MICROAMP METER
Incorporated in Radio Altitude Indicator 1D-14APN. Ideal for rev. counter etc. 15/6. P. & P. 3/-.

ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons
J1B. AUDIO SIGNAL GENERATOR.
15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms \$20.0.0.
VKT75. UHF MILLIVOLT METER.
100 Kc/s to 1,000 Mc/s. A.C. 10mV to 3V. DC 10 mV to 3V. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. \$125.0.0.
T21. TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. \$37.10.0. Carriage 10/- per item.

MARCONI TF195M BEAT FREQUENCY OSCILLATORS
0-40 kc/s. \$20. Carr. 30/-.

G. W. SMITH & CO (RADIO) LTD.
Also see next two pages

SEMI-CONDUCTORS/VALVES


BRAND NEW & FULLY GUARANTEED

TRANSISTORS

IN4001	1/6	AC176	5/6	BSV95A	2/6
IN4014	2/6	AC187	12/6	BY100	3/6
IN4002	2/6	AC188	7/6	BY124	3/6
IN4003	2/6	AC177	5/6	BY126	4/6
IN4004	3/6	AC178	5/6	BY127	4/6
IN4005	3/6	AC179	5/6	BY210	7/6
IN4006	4/6	AC180	5/6	BY211	6/6
IN4007	4/6	AC181	5/6	BY212	6/6
IN4148	1/6	AC222	4/6	BY213	6/6
IN5054	4/6	AC223	4/6	BY214	6/6
2G301	4/6	AC240	4/6	MJ481	25/6
2G302	4/6	AD140	8/6	MPP102	8/6
2G303	4/6	AD149	11/6	MPP103	7/6
2G306	7/6	AD161	7/6	MPP104	7/6
2G308	6/6	AD162	7/6	MPP105	7/6
2G309	6/6	AF114	5/6	NKT213	6/6
2G371	3/6	AF115	6/6	NKT214	4/6
2G374	4/6	AF116	6/6	NKT216	7/6
2G375	4/6	AF117	6/6	NKT217	8/6
2N696	4/6	AF118	12/6	NKT224	5/6
2N697	4/6	AF119	4/6	NKT241	5/6
2N698	5/6	AF124	4/6	NKT261	4/6
2N706	2/6	AF126	4/6	NKT271	4/6
2N706A	2/6	AF127	4/6	NKT272	4/6
2N708	3/6	AF130	6/6	NKT274	4/6
2N914	3/6	AF178	11/6	NKT275	4/6
2N916	3/6	AF180	10/6	NKT278	3/6
2N918	6/6	AF181	8/6	NKT281	5/6
2N929	4/6	AF186	9/6	NKT403	6/6
2N930	5/6	AF239	8/6		
2N1131	5/6	ASV26	5/6	NKT404	6/6
2N1132	6/6	ASV27	7/6		
2N1133	6/6	ASV28	7/6	NKT405	6/6
2N1303	3/6	AY101	20/6	NKT773	5/6
2N1304	4/6	AY131	1/6	NKT1043	6/6
2N1305	4/6	BC107	3/6		
2N1306	5/6	BC108	3/6	OA5	2/6
2N1307	5/6	BC109	3/6	OA10	2/6
2N1308	6/6	BC110	3/6	OA11	2/6
2N1309	6/6	BC111	3/6	OA12	2/6
2N1613	5/6	BC116	12/6	OA70	1/6
2N1711	5/6	BC125	11/6	OA79	1/6
2N1889	6/6	BC126	11/6	OA81	1/6
2N1893	8/6	BC147	3/6	OA85	1/6
2N2147	14/6	BC148	3/6	OA90	1/6
2N2160	11/6	BC149	3/6	OA91	1/6
2N2193	8/6	BC167	3/6	OA92	1/6
2N2217	5/6	BC172	3/6	OA200	2/6
2N2218	6/6	BC177	7/6	OA202	1/6
2N2219	6/6	BC186	7/6	OA210	3/6
2N2368	3/6	BC182L	4/6	OC19	8/6
2N2369	3/6	BC184L	4/6	OC20	15/6
2N2369A	4/6	BC212L	4/6	OC22	10/6
2N2484	6/6	BCY30	6/6	OC23	10/6
2N2613	7/6	BCY31	6/6	OC24	11/6
2N2646	11/6	BCY32	7/6	OC25	10/6
2N2904	7/6	BCY33	4/6	OC26	6/6
2N2923	3/6	BCY34	4/6	OC28	10/6
2N2924	3/6	BCY35	4/6	OC29	12/6
2N2925	3/6	BCY36	4/6	OC30	12/6
2N2926	3/6	BCY37	4/6	OC31	12/6
2N2927	3/6	BCY38	4/6	OC32	12/6
2N2928	3/6	BCY39	4/6	OC33	12/6
2N2929	3/6	BCY40	4/6	OC34	12/6
2N2930	3/6	BCY41	4/6	OC35	12/6
2N2931	3/6	BCY42	4/6	OC36	12/6
2N2932	3/6	BCY43	4/6	OC37	12/6
2N2933	3/6	BCY44	4/6	OC38	12/6
2N2934	3/6	BCY45	4/6	OC39	12/6
2N2935	3/6	BCY46	4/6	OC40	12/6
2N2936	3/6	BCY47	4/6	OC41	12/6
2N2937	3/6	BCY48	4/6	OC42	12/6
2N2938	3/6	BCY49	4/6	OC43	12/6
2N2939	3/6	BCY50	4/6	OC44	12/6
2N2940	3/6	BCY51	4/6	OC45	12/6
2N2941	3/6	BCY52	4/6	OC46	12/6
2N2942	3/6	BCY53	4/6	OC47	12/6
2N2943	3/6	BCY54	4/6	OC48	12/6
2N2944	3/6	BCY55	4/6	OC49	12/6
2N2945	3/6	BCY56	4/6	OC50	12/6
2N2946	3/6	BCY57	4/6	OC51	12/6
2N2947	3/6	BCY58	4/6	OC52	12/6
2N2948	3/6	BCY59	4/6	OC53	12/6
2N2949	3/6	BCY60	4/6	OC54	12/6
2N2950	3/6	BCY61	4/6	OC55	12/6
2N2951	3/6	BCY62	4/6	OC56	12/6
2N2952	3/6	BCY63	4/6	OC57	12/6
2N2953	3/6	BCY64	4/6	OC58	12/6
2N2954	3/6	BCY65	4/6	OC59	12/6
2N2955	3/6	BCY66	4/6	OC60	12/6
2N2956	3/6	BCY67	4/6	OC61	12/6
2N2957	3/6	BCY68	4/6	OC62	12/6
2N2958	3/6	BCY69	4/6	OC63	12/6
2N2959	3/6	BCY70	4/6	OC64	12/6
2N2960	3/6	BCY71	4/6	OC65	12/6
2N2961	3/6	BCY72	4/6	OC66	12/6
2N2962	3/6	BCY73	4/6	OC67	12/6
2N2963	3/6	BCY74	4/6	OC68	12/6
2N2964	3/6	BCY75	4/6	OC69	12/6
2N2965	3/6	BCY76	4/6	OC70	12/6
2N2966	3/6	BCY77	4/6	OC71	12/6
2N2967	3/6	BCY78	4/6	OC72	12/6
2N2968	3/6	BCY79	4/6	OC73	12/6
2N2969	3/6	BCY80	4/6	OC74	12/6
2N2970	3/6	BCY81	4/6	OC75	12/6
2N2971	3/6	BCY82	4/6	OC76	12/6
2N2972	3/6	BCY83	4/6	OC77	12/6
2N2973	3/6	BCY84	4/6	OC78	12/6
2N2974	3/6	BCY85	4/6	OC79	12/6
2N2975	3/6	BCY86	4/6	OC80	12/6
2N2976	3/6	BCY87	4/6	OC81	12/6
2N2977	3/6	BCY88	4/6	OC82	12/6
2N2978	3/6	BCY89	4/6	OC83	12/6
2N2979	3/6	BCY90	4/6	OC84	12/6
2N2980	3/6	BCY91	4/6	OC85	12/6
2N2981	3/6	BCY92	4/6	OC86	12/6
2N2982	3/6	BCY93	4/6	OC87	12/6
2N2983	3/6	BCY94	4/6	OC88	12/6
2N2984	3/6	BCY95	4/6	OC89	12/6
2N2985	3/6	BCY96	4/6	OC90	12/6
2N2986	3/6	BCY97	4/6	OC91	12/6
2N2987	3/6	BCY98	4/6	OC92	12/6
2N2988	3/6	BCY99	4/6	OC93	12/6
2N2989	3/6	BCY00	4/6	OC94	12/6
2N2990	3/6	BCY01	4/6	OC95	12/6
2N2991	3/6	BCY02	4/6	OC96	12/6
2N2992	3/6	BCY03	4/6	OC97	12/6
2N2993	3/6	BCY04	4/6	OC98	12/6
2N2994	3/6	BCY05	4/6	OC99	12/6
2N2995	3/6	BCY06	4/6	OC00	12/6
2N2996	3/6	BCY07	4/6	OC01	12/6
2N2997	3/6	BCY08	4/6	OC02	12/6
2N2998	3/6	BCY09	4/6	OC03	12/6
2N2999	3/6	BCY10	4/6	OC04	12/6
2N3000	3/6	BCY11	4/6	OC05	12/6
2N3001	3/6	BCY12	4/6	OC06	12/6
2N3002	3/6	BCY13	4/6	OC07	12/6
2N3003	3/6	BCY14	4/6	OC08	12/6
2N3004	3/6	BCY15	4/6	OC09	12/6
2N3005	3/6	BCY16	4/6	OC10	12/6
2N3006	3/6	BCY17	4/6	OC11	12/6
2N3007	3/6	BCY18	4/6	OC12	12/6
2N3008	3/6	BCY19	4/6	OC13	12/6
2N3009	3/6	BCY20	4/6	OC14	12/6
2N3010	3/6	BCY21	4/6	OC15	12/6
2N3011	3/6	BCY22	4/6	OC16	12/6
2N3012	3/6	BCY23	4/6	OC17	12/6
2N3013	3/6	BCY24	4/6	OC18	12/6
2N3014	3/6	BCY25	4/6	OC19	12/6
2N3015	3/6	BCY26	4/6	OC20	12/6
2N3016	3/6	BCY27	4/6	OC21	12/6
2N3017	3/6	BCY28	4/6	OC22	12/6
2N3018	3/6	BCY29	4/6	OC23	12/6
2N3019	3/6	BCY30	4/6	OC24	12/6
2N3020	3/6	BCY31	4/6	OC25	12/6
2N3021	3/6	BCY32	4/6	OC26	12/6
2N3022	3/6	BCY33	4/6	OC27	12/6
2N3023	3/6	BCY34	4/6	OC28	12/6
2N3024	3/6	BCY35	4/6	OC29	12/6
2N3025	3/6	BCY36	4/6	OC30	12/6
2N3026	3/6	BCY37	4/6	OC31	12/6
2N3027	3/6	BCY38	4/6	OC32	12/6
2N3028	3/6	BCY39	4/6	OC33	12/6
2N3029	3/6	BCY40	4/6	OC34	12/6
2N3030	3/6	BCY41	4/6	OC35	12/6
2N3031	3/6	BCY42	4/6	OC36	12/6
2N3032	3/6	BCY43	4/6	OC37	12/6
2N3033	3/6	BCY44	4/6	OC38	12/6
2N3034	3/6	BCY45	4/6	OC39	12/6
2N3035	3/6	BCY46	4/6	OC40	12/6
2N3036	3/6	BCY47	4/6	OC41	12/6
2N3037	3/6	BCY48	4/6	OC42	12/6
2N3038	3/6	BCY49	4/6	OC43	12/6
2N3039	3/6	BCY50	4/6	OC44	12/6
2N3040	3/6	BCY51	4/6	OC45	12/6
2N3041	3/6	BCY52	4/6	OC46	12/6
2N3042	3/6	BCY53	4/6	OC47	12/6
2N3043	3/6	BCY54	4/6	OC48	12/6
2N3044	3/6	BCY55	4/6	OC49	12/6
2N3045	3/6	BCY56	4/6	OC50	12/6
2N3046	3/6	BCY57	4/6	OC51	12/6
2N3047	3/6	BCY58	4/6	OC52	12/6
2N3048	3/6	BCY59	4/6	OC53	12/6
2N3049	3/6	BCY60	4/6	OC54	12/6
2N3050	3/6	BCY61	4/6	OC55	12/6
2N3051	3/6	BCY62	4/6	OC56	12/6
2N3052	3/6	BCY63	4/6	OC57	12/6
2N3053	3/6	BCY64	4/6	OC58	12/6
2N3054	3/6	BCY65	4/6	OC59	12/6
2N3055	3/6	BCY66	4/6	OC60	12/6
2N3056	3/6	BCY67	4/6	OC61	12/6
2N3057	3/6	BCY68	4/6	OC62	12/6
2N3058	3/6	BCY69	4/6	OC63	12/6
2N3059	3/6	BCY70	4/6	OC64	12/6
2N3060	3/6	BCY71	4/6	OC65	12/6
2N3061	3/6	BCY72	4/6	OC66	12/6
2N3062	3/6	BCY73	4/6	OC67	12/6
2N3063	3/6	BCY74	4/6	OC68	12/6
2N3064	3/6	BCY75	4/6	OC69	12/6
2N3065	3/6	BCY76	4/6	OC70	12/6
2N3066	3/6	BCY77	4/6	OC71	12/6
2N3067	3/6	BCY78	4/6	OC72	12/6
2N3068	3/6	BCY79	4/6	OC73	12/6
2N3069	3/6	BCY80	4/6	OC74	12/6
2N3070	3/6	BCY81	4/6	OC75	12/6
2N3071	3/6	BCY82	4/6	OC76	12/6
2N3072	3/6	BCY83	4/6	OC77	12/6
2N3073	3/6	BCY84	4/6	OC78	12/6
2N3074	3/6				

LOOK!

PRACTICAL!
VISUAL!
EXCITING!

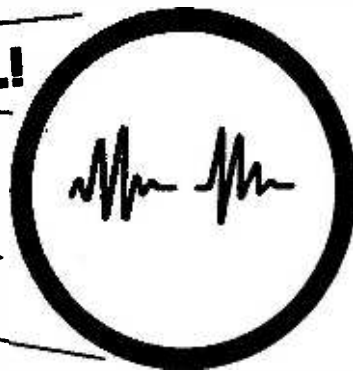


a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .

1

**OWN and
HANDLE a**

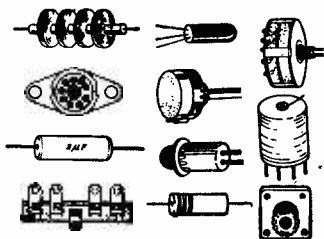complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



2

**BUILD
and USE**


a modern and professional **CATHODE RAY OSCILLOSCOPE**



3

**READ and
DRAW and**

**UNDERSTAND
CIRCUIT DIAGRAMS**

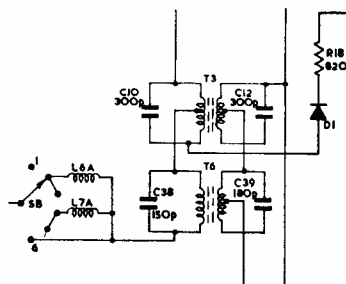

4

CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE

**POST NOW
for
BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS. Please**
send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE P.W. 12

PRACTICAL WIRELESS

VOL 46 NO 8

Issue 766

DECEMBER 1970

TOPIC OF THE MONTH

What went wrong?

WHATEVER happened to the Radio Hobbies Exhibition?" asks an advertiser who has pulled out of the RSGB exhibition. Other journals have posed the same sort of question and readers of Practical Wireless seem to be equally bemused. And viewing the event objectively, we have no hesitation in declaring that to our eyes the recent RSGB show was a bit of a flop.

This is not a dyspeptic editorial gripe. As a major exhibitor, P.W. has a right to be concerned, not only as a participant but as a voice for those at which this exhibition is aimed. It must also be made clear that we are not knocking the RSGB as such; the future of amateur radio relies on a healthy, prosperous and influential RSGB. We do feel, however, that in the organisation and conception of their annual exhibition they have gone sadly adrift. Falling attendance figures and lack of stand support show this clearer than any words.

What has gone wrong? What has caused this downhill spiral of diminishing support both by traders and visitors? The reasons may be complex, but no doubt one contributory cause is the problem of TVI which has resulted in most amateurs buying their equipment rather than making it. This is supported by the appalling lack of support for the RSGB constructional trophies—only *eight* entries all told and none at all for the John Rouse Trophy (which is for constructional entries from the under 16's)! Another contributory reason must surely be the evolution of title from the humble "RSGB Exhibition" to the cumbersome, pompous and pretentious International Radio Engineering and Communications Exhibition. Whoever thought that one up deserves an OBE for sheer effrontery!

But what of the future? The RSGB would be ill-advised to embark on a similar venture next year without a major re-think. What is needed is an all-embracing show revolving around the hobbyist, possibly run by a consortium of interests, covering not only purely amateur radio, but taking in all types of associated interests, be it hi-fi, tape recording, electronics and the like. And give it a title that means something and sounds more attractive than something from 1984. Then we might find companies more willing to take stands and the lost visitors starting to flock back again.

W. N. STEVENS—Editor.

**JANUARY ISSUE WILL BE PUBLISHED
ON DECEMBER 4**

NEWS AND COMMENT

Leader	623
News . . . News . . . News . . .	624
On the Short Waves by <i>Malcolm Connah and David Gibson, G3JDG</i>	631
Letters to the Editor	633
MW Column by <i>Charles Molloy</i>	661
CQ! CQ! CQ! CQ!	669
Practically Wireless by <i>Henry</i>	670

CONSTRUCTIONAL

Amateur Bands Communications Receiver Part 1 by <i>W. Cameron</i>	626
I.C. Stereo Equalisers & Mixers by <i>Caleb Bradley, B.Sc.</i>	634
Audio/Visual Continuity Tester by <i>M. A. Sparks</i>	642
I.C. of the Month (Motorola MC1596G Modulator/Demodulator) by <i>L. A. J. Ireland</i>	646
A Sensitive Telephone Amplifier by <i>C. R. Bradley</i>	648
P.W. 25/25 Stereo Amplifier, Part 2 by <i>F. C. Judd</i>	652
Take 20—Megaphone by <i>Julian Anderson</i>	678

OTHER FEATURES

Going Multiband by <i>Eric Dowdeswell, G4AR</i>	662
Going Back by <i>Colin Riches and Arthur Dow</i>	673

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisements Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS... NEWS... NEWS...


12V Iron

Solderstat Ltd announce a P.V.C. button-down-pack with a 12 volt "HMS Series" soldering iron, with 15 feet of cable fitted with battery clips.

This specially designed soldering iron has a consumption of only 12 watts consuming appreciably less than parking lights.

A unique heatshield/transit cover has been developed to allow the soldering iron to be packed away immediately after use.

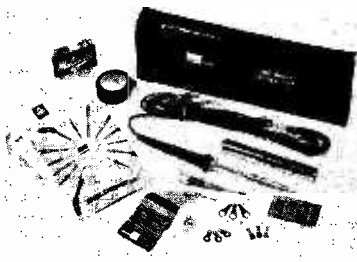Other accessories included are a coil of cored solder, P.V.C. insulation tape, solder tags, wiper pad, screwdriver/wire stripper and a desolder braid dispenser. Recommended List Price is 57s. 6d. *Solderstat Ltd., P.O. Box 10, Bush Fair, Harlow, Essex.*



Magnetic Mic.

A hand microphone has been introduced by the communications division of *S. G. Brown Ltd., of King George Avenue, Watford, Herts.* It can be used with both mobile equipment and for base installations.

Known as the 'Classic', this lightweight instrument has a powerful magnet fitted in the grip which enables it to 'stick' to any ferrous surface. A user in a motor vehicle can place the instrument in the most convenient position on the vehicle's dashboard, eliminating the need for a conventional microphone holder.

Impedance at 1000Hz is 300Ω nominal. Frequency response: Rising at 10dB per decade over the range 100-2000Hz, substantially linear over the range 2000-14000Hz, falling off rapidly thereafter. Sensitivity is 85dB below IV/Dyne/cm² (typical) and output for normal speech is approximately 1mV true r.m.s.

Mr. Mullard

Mullard Ltd. announce that Mr. Stanley Mullard, M.B.E.(Mil.), Hon.C.G.I.A., F.I.E.E., who founded the company 50 years ago, retired from the Board at the end of September, after completing nearly 72 years with the electrical and electronics industry.

Stanley Robert Mullard was born on November 1st, 1883, and was apprenticed to an electrical engineering firm at the age of 15. In 1910 he joined Ediswan. Three years later he became head of their lamp laboratory and in 1915 invented the Pointolite arc lamp, widely used in projection apparatus.

During World War I he enlisted in the Engineers' Battalion of the Royal Naval Division and in 1916 was commissioned in the Royal Naval Volunteer Reserve and attached to the Royal Naval Air Service.

As a member of a small team of scientists and technologists at H.M. Signal School, Portsmouth, he was involved with the invention and development of high-power transmitting valves in fused silica bulbs which were urgently needed by the Navy. In 1920, after his demobilisation, he was invited by the Admiralty to produce these valves in quantity.

The first company to bear his name—the Mullard Radio Valve Company—was founded in 1920. It occupied premises rented from the 'Z' Lamp & Electrical Company of which Mullard had become managing director.

With the spread of radio, Mullard became involved in the manufacture of small receiving valves. Under the trade name



ORA these were soon being turned out at the rate of hundreds a week. Demand rapidly outstripped factory capacity and the firm moved to larger premises at Hammersmith. And in 1923 Mullard acquired still larger accommodation at Balham. By the end of 1924 production stood at 2½ million valves a year.

In 1927 a large factory at Mitcham was purchased and this is still the main centre for silica high-power transmitting valves for industrial electronic applications.

In 1930 Mullard reluctantly decided to relinquish his leadership of the company. He had been working at full pressure since 1910 and his doctors had warned him to ease up.

He has since been far from inactive. He has retained his seat on the Mullard Board and has continued to participate in company affairs. Since 1945 he has also interested himself in new horticultural and other industrial developments. And he has seen the company he founded 50 years ago grow to occupy a leading position in the world electronics industry.

The Tilley Go-Torch

A new product from The Tilley Lamp Company is a useful butane gas blow-lamp complete with paint stripper and soldering bit attachment. Called the Tilley Go-Torch, it operates on a Tilley Go-Gas 6oz disposable cartridge.


Made from high quality chrome-plated steel, brass and aluminium,

the Go-Torch will make a useful addition to the equipment in the radio shack.

Price of the Tilley Go-Torch is £2 19s. 6d., including general purpose burner, soldering bit attachment, a steel flame spreader for paint stripping and a full cartridge of Tilley Go-Gas. The latter is replaceable at around 4s 6d. each. *The Tilley Lamp Company Ltd., Dunmurry, Belfast, Northern Ireland.*

AMATEUR BANDS COMMUNICATIONS RECEIVER

PART 1

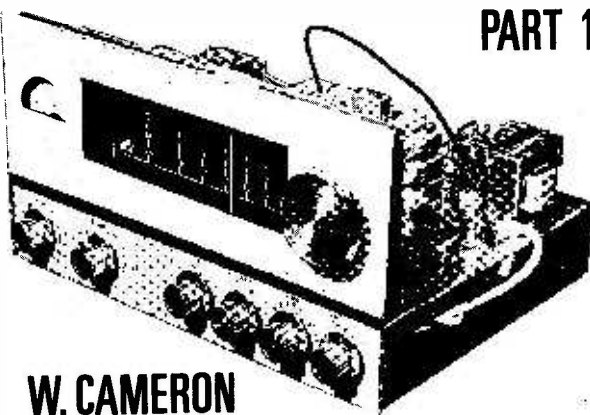

W. CAMERON

- **CIRCUIT** : Double-conversion superhet
- **SYSTEMS** : AM/SSB/CW
- **COVERAGE** : 1.8MHz to 29.5MHz
- **SENSITIVITY** : 1.5 μ V for 0.25V a.g.c. and 100mV into detector and S/N ratio of 12dB
- **I.F. BANDWIDTH** : 4kHz at -6dB points; 10kHz at -30dB points
- **IMAGE REJECTION** : 60dB at 1.5MHz; 80dB at 3.5MHz; 40dB at 28MHz
- **SPURII** : -80dB on all bands
- **INPUT IMPEDANCE** : 300 ohms on 1.5MHz; 80 ohms 3.5 to 28MHz
- **OUTPUT** : 1 Watt into 15 ohms
- **POWER SUPPLY** : 12V d.c. or a.c.mains

A HIGH performance amateur band communications receiver is necessarily rather complex and usually expensive, mainly because of the use of mechanical or crystal i.f. filters, and (in the case of double conversion receivers) crystal controlled oscillators.

The receiver to be described lacks little in selectivity and stability, and in the interests of economy does not use either crystal i.f. filters or crystal controlled oscillators.

The selectivity is not as sharp as can be obtained with a good mechanical filter, but is at least twice as sharp as can be obtained using conventional i.f. circuits, and results in an i.f. bandwidth of less than

4kHz at -6dB. This is just adequate for a.m., while results on s.s.b. are very good indeed.

By taking special care with the oscillators, a stability of a very high order is achieved.

The receiver uses the double conversion principle, in which the second converter is tuned, covering the range 1.5-2.0MHz. This frequency range is chosen so that this unit with the following i.f. amplifier, serves on its own as a complete Top Band receiver.

The oscillator of the first converter is switched to cover all the remaining bands, which are fixed tuned. The r.f. stages are peaked by a front panel control.

This double conversion system has the very great advantage that the same scale calibration, and the same tuning rate, holds good for all bands (with the minor exception that the Top Band calibration is reversed). This means that the entire scale length covers only 500kHz, and is the same on each band.

Another advantage is that because the i.f. has been raised to nominally 1.7MHz (1.5-2.0) from 470 kHz, by the second converter, the image rejection on the h.f. bands is improved. Typically, the image rejection at 2MHz with a 470kHz i.f. can be expected to be -10 or -12dB, but with an i.f. of 1.7MHz improves to -40 to -45dB.

A block diagram of the receiver is shown in Fig. 1, with typical gains per stage.

Important considerations are the avoidance of interference by cross modulation, and unwanted reception of signals caused by beating with oscillator harmonics. These considerations call for good pre-mixer selectivity, and that no oscillator signal or harmonics appear in the r.f. circuits. Also to this end, the r.f. amplifier transistors must always operate in the linear part of their characteristic, which means special methods of applying a.g.c. These considerations are taken care of in the design and will be enlarged on later.

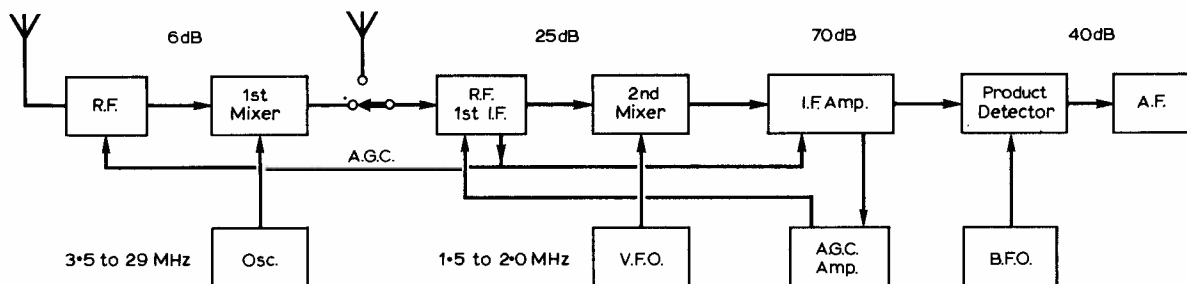


Fig. 1: Block diagram of the complete receiver with typical stage gains.

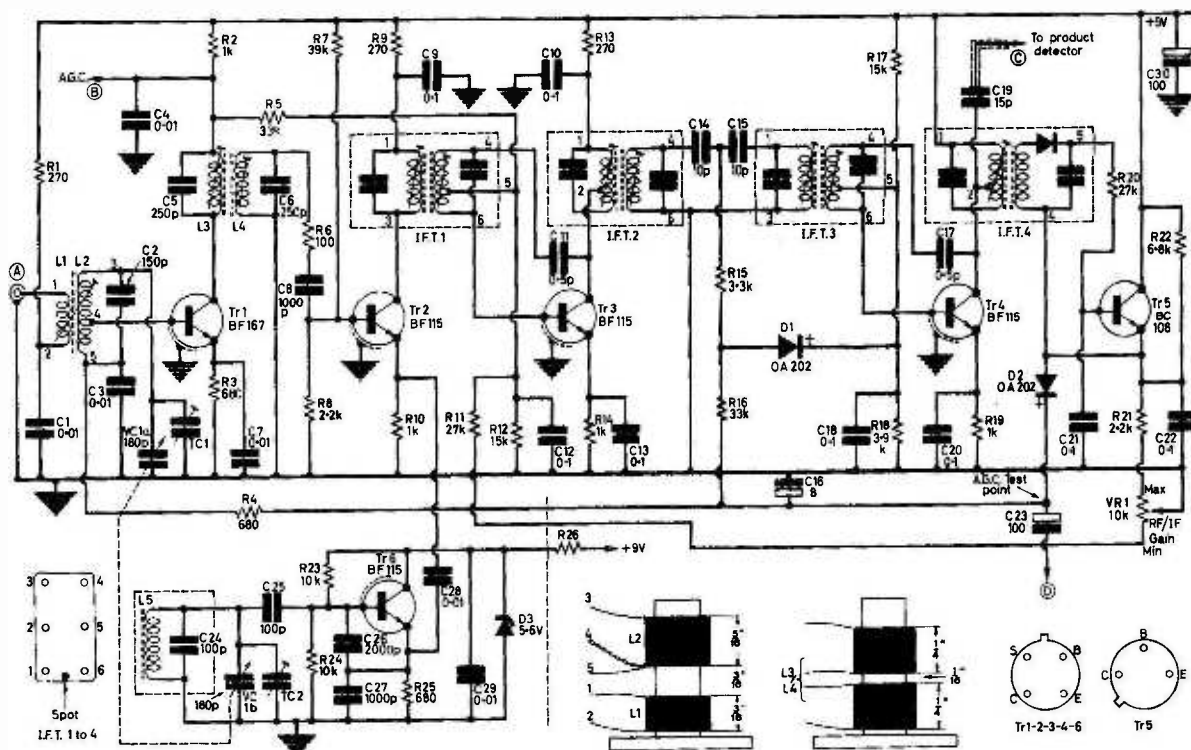


Fig. 2: Circuit of the second converter/i.f. amplifier.

TABLE 1

	Collector	Base	Emitter
Tr1	7.15	1.8	1.15
Tr2	9.0	0.5	0.05
Tr3	8.8	1.6	1.0
Tr4	9.0	1.6	1.0
Tr5	9.0	1.8	2.0
Tr6	5.6	2.6	2.0

Voltages measured with a meter of 20kΩ/V.

INDUCTORS

L1 20 turns pilewound.
 L2 65 turns pilewound, tapped 6 turns from earthy end.
 L3 55 turns pilewound.
 L4 55 turns pilewound.
 See Fig. 2 for winding details.
 L5 55 turns closewound.
 All inductors wound on ½ in. dia. formers, with dust cores (Radiospares), 36 s.w.g. enamelled copper wire.

In order to simplify construction the receiver is built up in units. In the prototype all the completed units are mounted on or within a common chassis 12 x 9 x 2 in. made of 18 s.w.g. aluminium. A panel 12 x 4½ in. (12 x 4½ in. with flange) is bolted to the front to carry the scale, drive and S meter. This panel is mounted with the flange forward so that the scale is recessed behind the front panel proper which can also be of aluminium with cut-outs to show the scale and S meter.

A description of the circuit functions, constructional data and alignment information will be given in the following order:

1. Second converter and i.f. amplifier.
2. B.F.O./product detector, audio amplifier and power supply.
3. Pre-selector and first converter.

Second converter/i.f. amplifier

As already mentioned, this unit, Fig. 2, is, on its own, a receiver covering the 160 metre amateur band

and shipping, in the range 1.5 to 2.0 MHz, the front end of which, in the complete receiver, becomes the second converter (or tunable first i.f.).

To ensure a good Q factor in the aerial tuned circuit, the aerial is loosely coupled to L2 via L1 and similarly the base of Tr1 is tapped well down on L2. L1 is returned to the supply line via R1, as this will later carry the supply voltage to the first mixer. The r.f. stage Tr1 is coupled to the mixer by the wide band transformer L3/L4. This has a relatively flat response over the range 1.5 to 2.0 MHz, with a sharp cut-off at the ends.

The oscillator, Tr6, is a highly stable Colpitts circuit, voltage stabilised by a zener diode, D3. Stability against changes in ambient temperature is achieved by using polystyrene capacitors, which offset the positive temperature coefficients of transistor and coil. If anything, the oscillator may be over compensated, and, if desired, it is not too difficult to be precise by using a combination of polystyrene and silver mica capacitors for C24.

The ganged tuning capacitor VC1a-VC1b must be

a good one, with adequate screening between stators. Most capacitors tried had too much stray coupling between sections so that oscillator voltage appeared on the r.f. section. With the capacitor used no oscillator voltage was measurable on the r.f. section. In the prototype this is a Jackson Bros. Type F, "H" law, but it has later been found that this type can also be supplied in "SLF" and this is specified as it will provide a linear scale calibration.

Two methods of improving i.f. selectivity are adopted: i.f.t.2 and i.f.t.3 are connected back to back to provide four tuned circuits instead of the usual two, and because of the small amount of coupling, the reduced loading results in higher circuit Q's. Also Tr3 and Tr4 are each given a small amount of positive feed-back via capacitors C11 and C17 respectively. These provide only a moderate amount of regeneration, well below the point of oscillation, but give a marked increase in selectivity. The output from the last i.f. is coupled to the product detector via a small capacitor (C19) so that a signal of about 100mV appears at the product detector input.

Tr5 is the a.g.c. amplifier, and in the absence of a signal, only the voltage resulting from the potential divider R21-R22 appears on the a.g.c. line as standing bias for Tr1. With the r.f./i.f. gain control at maximum (R21 to earth) this voltage will be 1.8 volts and is referred to as the a.g.c. reference level. In this condition Tr5 is non-conducting.

On receipt of a signal, the rectified output from the diode in i.f.t.4 is applied between base and emitter of Tr5 and the base will be made positive with respect to the emitter and Tr5 will conduct. The increase in voltage across R21 will be proportional to signal strength and is applied to Tr1 as forward a.g.c.

This reduces the gain of Tr1 in two ways, first, as the transistor is turned more into the "on" mode its current will increase resulting in a greater voltage drop across R2 and R3, so that with a very strong signal the voltage available across the transistor between collector and emitter will be very small. At the same time, the base-emitter impedance becomes very low, further attenuating the signal.

The reducing voltage at R2 serves as reverse a.g.c. for the i.f. amplifier Tr3, and also for the r.f. stage in the pre-selector.

The diode D1 is reverse biased until the voltage on the a.g.c. line rises, when the diode will conduct, attenuating the signal at i.f.t.3.

The result of these a.g.c. combinations is that a good range of a.g.c. is provided, without any of the controlled stages being biased into cut-off.

The purpose of the diode D2 and capacitor C23 is to give the fast attack—slow decay characteristic required for s.s.b. and c.w.

Fig. 3 shows the signal a.g.c. characteristic of the complete receiver. "S" readings are also shown in the scale, relative to signal strength and a.g.c. voltage, which may be found useful in adjusting the "S" meter. This follows accepted practice of 6dB per S point. On the 160 metre band, signals should be given the benefit of another "S" point as the gain is 6dB down compared to the other bands which have the benefit of the pre-selector.

Construction

The second converter and i.f. amplifier unit is built on a chassis 8 x 4 x 1 in. and the main details of

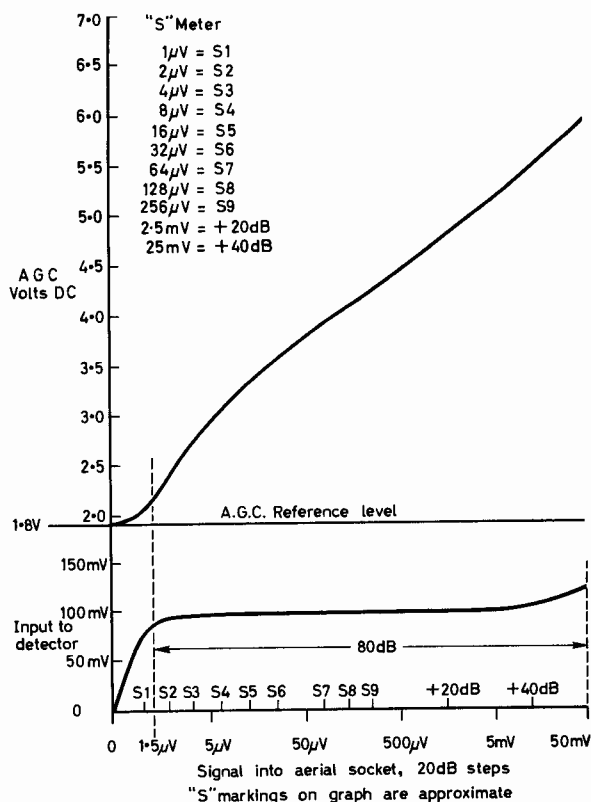



Fig. 3: The signal a.g.c. characteristic of the complete receiver.

this are shown in Fig. 4. The chassis is made from grade 1 tinned plate (about 24 or 26 s.w.g.), with end plates of 18 s.w.g. aluminium. Screened compartments are provided for the r.f. and oscillator sections.

The i.f. transformers are mounted with the identification spots nearest the centre of the chassis.

Paxolin strips are secured under the $\frac{1}{4}$ in. holes as transistor mounts, four tiny holes being drilled through these, through which the transistor leads are passed. The transistors should be pushed right down, and the shield lead bent over and soldered direct to the underside of the chassis.

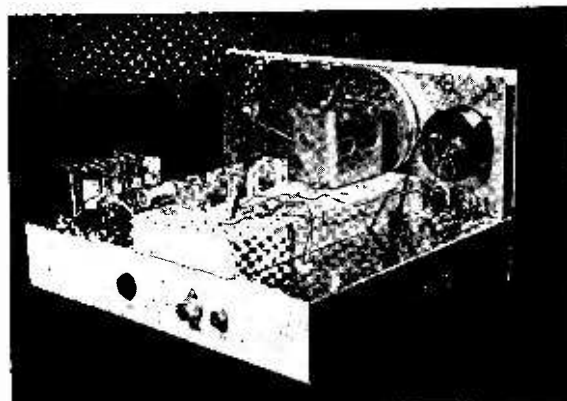After winding, the coils L1/2 and L3/4 and L5 are secured in position on the chassis with a contact adhesive such as Evostik. When winding the close-



A rear view of the completed receiver.

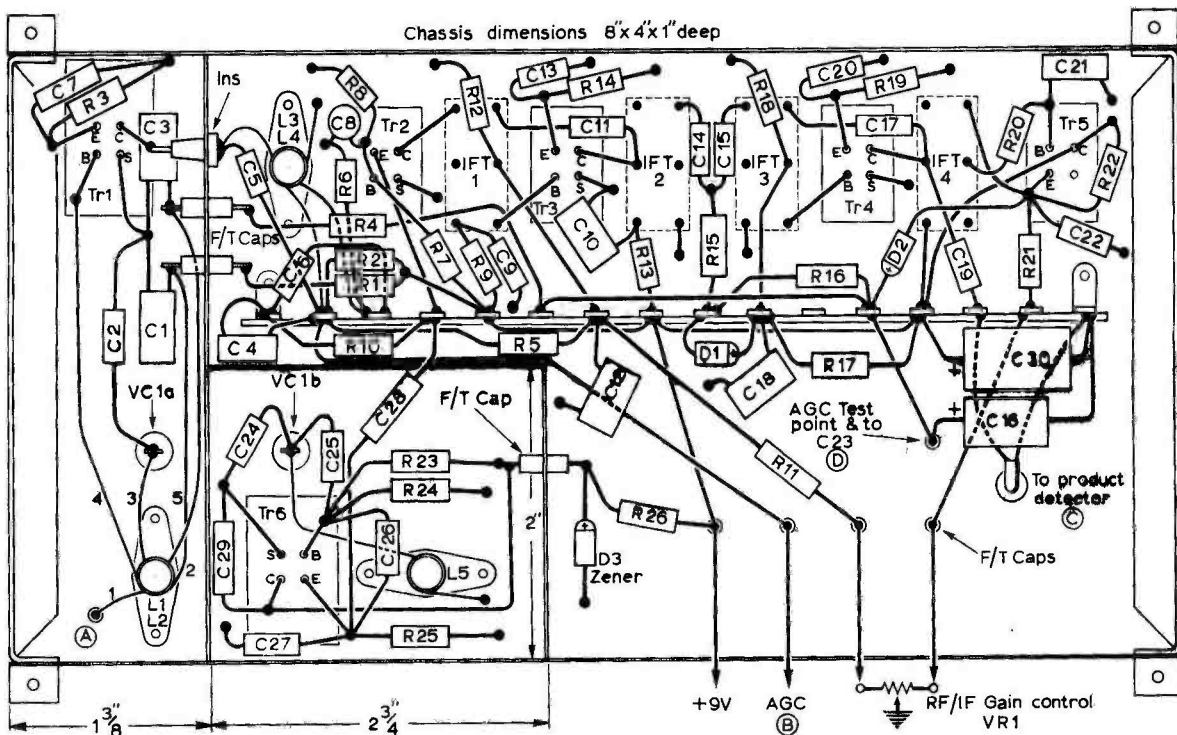


Fig. 4: Underchassis wiring of the second converter (i.f. amplifier).

wound single layer coils, it will be found easier to wind five turns or so at a time, pushing each five turns down before the next five are wound. In this way all the turns of the completed coil are close together and neat. Finish with a spot of polystyrene cement or a coating of wax.

Where d.c. wiring passes through the chassis or screened compartments, it is convenient and good practice to use fed-through capacitors. R.F. wiring can simply pass through holes in the chassis or else feed-through insulators can be used. These can be made by glueing a short length of sleeving in the hole and passing a small piece of thick wire through the sleeving.

Wiring in of components can now proceed as in Fig. 4. The tag strip has 16 tags, mounting lugs being left only at each end, the remainder being cut off. The strip is mounted by soldering each end lug to the chassis. When completed, the unit should be connected to a 9V supply and the voltages checked against Table I.

Alignment

Alignment can be carried out at this stage, or if audible results are required, can wait until the product detector and a.f. amplifier are completed.

Connect a voltmeter between the a.g.c. test-point and chassis, and a signal generator via an isolating capacitor (0.01 μ F) to the base of Tr2 and turn VR1 to maximum.


Inject an unmodulated signal of 470kHz and adjust i.f.t.'s in the order i.f.t.4 to i.f.t.1, for maximum reading on the meter. Reduce the output from the signal generator until the meter reads about 3V and again peak the i.f.t.'s for maximum. Repeat until no improvement can be obtained, and the i.f.'s are then tuned.

As a guide, the output from the signal generator

for the final conditions above will be of the order of 150 μ V.

Transfer the generator to the input of the receiver and inject a signal of 1450kHz. Turn the ganged capacitor to maximum capacity and adjust L5 and then L2 for maximum output. To do this correctly the cores must be screwed in from the top or "hot" end of the coil (furthest from the chassis) as it will be possible to tune the signal twice with L5. The correct signal is the first position.

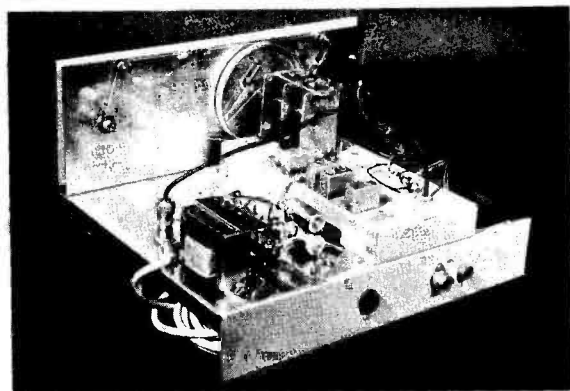Now turn the capacitor to minimum and inject a signal of 2050kHz and adjust TC2 and then TC1



The chassis shown at the top of the page fits on top of the main chassis and it can clearly be seen in this photograph and the one on the facing page

for maximum. Inject a signal of 1800kHz, tune to it, adjust the cores of L3 and L4 for maximum.

Inject a signal of 1600kHz, tune to it, adjust the core of L2 to maximum. Inject 1900kHz and tune to it, adjust TC1 for maximum. Repeat these two last adjustments until no further improvement is obtained.

In all of these adjustments, the output from the signal generator should be kept down so that the meter reading (the voltage at the a.g.c. test-point) does not exceed 3V.

Although the use of a signal generator is strongly recommended, it is possible to align the unit reasonably well without one, but it will then be necessary to complete the product detector and audio amplifier.

The ganged tuning capacitor in the second converter provides the main tuning for the complete

★ components list

Resistors:

R1 270Ω	R10 1kΩ	R19 1kΩ
R2 1kΩ	R11 27kΩ	R20 27kΩ
R3 680Ω	R12 15kΩ	R21 2.2kΩ
R4 680Ω	R13 270Ω	R22 6.8kΩ
R5 33kΩ	R14 1kΩ	R23 10kΩ
R6 100Ω	R15 3.3kΩ	R24 10kΩ
R7 39kΩ	R16 33kΩ	R25 680Ω
R8 2.2kΩ	R17 15kΩ	R26 270Ω
R9 270Ω	R18 3.9kΩ	

All resistors $\frac{1}{2}$ W 10%

VR1 10kΩ potentiometer, linear

Capacitors:

C1 0.01μF ceramic	C16 8μF 12VW/elec
C2 150pF 5% poly	C17 0.5pF *
C3 0.01μF ceramic	C18 0.1μF ceramic
C4 0.01μF ceramic	C19 15pF 5% poly
C5 250pF 5% poly	C20 0.1μF ceramic
C6 250pF 5% poly	C21 0.1μF ceramic
C7 0.01μF ceramic	C22 0.1μF ceramic
C8 1000pF poly	C23 100pF 5% poly
C9 0.1μF ceramic	C24 100pF 5% poly
C10 0.1μF ceramic	C25 100pF 5% poly
C11 0.5pF *	C26 2200pF poly
C12 0.1μF ceramic	C27 1000pF poly
C13 0.1μF ceramic	C28 0.01μF ceramic
C14 10pF 5% poly	C29 0.01μF ceramic
C15 10pF 5% poly	C30 100μF 12VW/elec

* These low value capacitors are obtained by using high value resistors (4.7 MΩ).

VC1a-b 180 + 180pF ganged (Jackson Type F/SLF)

TC1-2 30pF trimmers (part of VC1a-b)

Semi-conductors:

Tr1 BF167	Tr4 BF115
Tr2 BF115	Tr5 BC108
Tr3 BF115	Tr6 BF115
D1 OA202	
D2 OA202	
D3 5.6V 250mW Zener	

IF Transformers:

1FT-1 T41/1E (Weyrad)	1FT-2 T41/2E (Weyrad)
1FT-3 T41/2E (Weyrad)	1FT-4 T41/3T (Weyrad)

Miscellaneous:

Feedthrough capacitors (8). Cord drive with $\frac{3}{4}$ in. drive drum and two $\frac{1}{2}$ in. pulleys. Chassis 8 x 4 x 1 in. (see text). Tag strip, 16 way.

receiver and the scale should be initially calibrated from 1.5 to 2MHz with the aid of the signal generator, in 100kHz steps, which can be subdivided into 10kHz steps if desired.

Note. The cores of L1-4 and L5 must each be treated with a core locking compound or high viscosity grease before they are screwed into the coils. In addition, the core of L5 should have a thin rubber band screwed in with it.

TO BE CONTINUED

NEXT MONTH IN

PRACTICAL WIRELESS

FREE WALL CHART No. 2

In the January issue we shall be presenting free the second wall chart on AUDIO STANDARDS. A must for all hi-fi enthusiasts.

PW. STEREO TAPE RECORDER

A project that has been specifically designed with the constructor in mind, the PW. Stereo Tape Recorder can be used with almost any tape deck which can be fitted with the specified Marriott tape heads. The prototype is based on the R.T.C. 249 push button, three speed deck. Careful thought has been given to both the electronic and constructional design to make it possible for the recorder to be built by the comparative newcomer to electronic construction. Simple switching has been made possible by using an unusual equalisation principle and although 16 transistors are used, the cost of the complete project should be only around £30.

LUXEMBOURG BANDSPREAD POCKET 7

This compact seven transistor superhet radio, in addition to covering the full medium wave-band, has a second band from 1400-1625kHz which enables the user to easily tune the popular stations in this band. The receiver is built in a readily available plastic case using widely available components.

PORTABLE SIGNAL TRACER

This versatile signal tracer is a further addition to our "build your own" test equipment series. This unit has three probes; for checking a.f., r.f. and e.h.t.—the latter for checking corona and high voltage breakdown.

PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" SERIES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the January issue of Practical Wireless—on sale 4th December—price 3s. 6d.

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

The first report this month comes from regular contributor **C. R. S. Stacey** of Tunbridge Wells who used his Lafayette HA-700 receiver and Joystick antenna to hear:

9665 *R. Trans Europe*, ident. in German at 1955
9705 *R. Voice of the Gospel* from 1815 to 1850
15410 *VOA, Tinang* in Chinese from 1611 to 1659.

Ian Howes of Lowestoft used his Unica 30 receiver with a TV aerial to send in an excellent first report which included:

4850 *Mauritania* noted at 2210
4900 *Radio Juventud*, Venezuela at 2240
4940 *R. Abidjan*, Ivory Coast at 2330
4967.5 *Radio Kuwait* noted at 2000
11805 *Radio Globo*, Brazil at 2220
11925 *Radio Bandeirantes*, Brazil at 0030
12175 *Radio Tehran*, Iran at 2000
15245 *Radio Kinshasa*, Congo noted at 2240
15410 *VOA, Philippines* at 1445

Robert Cork of Basingstoke has built the 'PW' modular short-wave receiver and connected it to a 15 foot antenna with the following results:

9540 *Radio New Zealand* to Pacific Islands at 0545

11672 *Radio Pakistan* noted at 2005
11675 *CBC, Radio Canada*, news in English at 0745

11745 *Voice of Nigeria*, news and comment at 2000

11750 *BBC Far East relay*, Tebrau, s-on at 0900

John Trewick of London Colney has sent in another report which contained:

6540 *Radio Pyongyang*, North Korea at 1930
9715 *Radio Nederland*, Bonaire at 0800
15330 *United Nations Radio Service* at 2100

Chris Vernon of South Ruislip made his own super-het receiver and used it with a 20ft. long-wire to hear:

6620 *Radio Peking* in English from 2155 to 2215
9625 *CBC, Radio Canada* in English from 0715 to 0745

11710 *ABC, Australia* in English from 0840 to 0920

11950 *Radio Japan* in English from 2030 to 2100
15255 *Radio Vilnius*, Lithuania in English at 2235-2300.

Simon Hamer of New Radnor in Wales has two receivers, a Mullard domestic receiver and a 10 transistor portable and two aerials, 25 and 60 foot long-wires. This line-up enabled him to hear:

11710 *ABC, Australia* from 0645 to 0915 in English

11790 *ABC, Australia* in Vietnamese, Eng. ID. at 2130

15105 *BBC, Atlantic relay*, Ascension Island at 0730

21690 *Windward Islands* to U.K., s-off at 2200

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

Colin Blanchard of Sutton Coldfield has a 5 valve Mullard domestic superhet and a 50 foot long-wire and he has heard the following stations:

9625 *Radio Israel* with news in English at 2100
9912 *All India Radio* with music, Id. in Eng. at 2050

11720 *VOA, Tangier* with Jazz Hour from 2345 to 2400

11725 *Radio Peking* in English from 2100 to 2130
15320 *ABC, Australia*, Id. at 2255, news in Eng. at 2300

Nicholas Brooks of Naseby used his Astrad Auriga receiver and 120 foot long wire to hear several stations including:

11620 *All India Radio*, Delhi in English at 1930
11660 *Radio Pakistan*, Karachi in English at 2110
21440 *HCJB, Quito*, Ecuador in English at 2055
21650 *Radio Nederland*, Bonaire in English at 2030.

Roy Patrick of Derby has sent in some more interesting items including:

SOUTH KOREA, The Voice of Free Korea in Seoul has been heard in English at 0900 on the frequency of 9646kHz.

SYRIA, Radio Damascus is now on 9670 and the frequency of 15165 has been dropped.

DXing Tips

Now that the winter season is with us once again I have decided to give some hints about the tricks of the trade to help newcomers to become better DXers.

The subject for this month is the identification of stations using languages other than English. I have noticed that the majority of reports to this page concern broadcasts in English whereas the most interesting stations use other languages.

It is easier to catch the name of a station if one knows the words which precede the name. In English the most frequently used expressions are: This is... You are tuned to... You are listening to... In Spanish we have: Esta es... Aqui... Habla... In Portuguese: Aqui... Fala... Fala-vos... In French: Ici... Vous écoutez... Vous êtes à l'écoute. In Italian: Qui... Transmette... Questa é... In German: Hier ist... Hier spricht... In Russian: Govorit... Vy slushaite... In Arabic: Huna... Hadha... Hadihi... In Standard Chinese: po tien tai... Cantonese: bor deen toy... Vietnamese: Day la... Thai: Thini... Japanese: Kochirawa... desu. Mongolian: ...yarsh; Swahili: Hii ni... Afrikaans: Dit is... Hindi, Urdu: Yeh...hai. I hope that the above will be of use to some of you.

All reports, which should be in frequency order, must reach me by the 17th. of the month at the following address: 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

CONDITIONS have varied quite a lot this past month. The l.f. bands, true to form, have begun to improve and it can only be hoped that this will continue thus enabling Santa to fill waiting ears with Christmas DX.

Talking l.f., **Paul Leach** (Cheshire) informs that a listen on 1880kHz in the evenings will often be rewarded by sigs from HBØXKZ (QSL via G3TXF). Paul hopes to take the R.A.E. in December before going to school in GD-land.

Twenty metres have proved its worth for those who were prepared to go on owl watch. Late nights and early mornings appear the most fruitful times to QRX.

Surprise of the month was undoubtedly ten metres. True its a temperamental old band with a character all of its own, but there were some very good openings especially towards the end of the month. North America and Japan were heard on two occasions.

P. Fereyear (Essex), Marconi No. 9 set built in 1943, no mention of any antenna (boy, they really knew how to build sets in 1943). He says that PAØPN can usually be logged at 1100 around 1805kHz.

On 3500kHz, Paul logged; CR7GJ, F6ACM/FC, OY7JD, PY1HA, VO1FG, VS6DO, WA1IKG, 9V1PP.

The majority of logs this month owe their existence to either 14 or 21MHz. Certainly these are nearly always the easiest bands to pick up DX although the EU stations sometimes make the going a bit rough.

K. Hastie (Roxburghshire), CR100, 60ft. long-wire, Joymatch a.t.u., had a peep at 14MHz and got: HC8KKU, HS3ACV, HV3SJ, K6GUY, KJ6CF, MP4BBA, VE2BM, 5Z4KL, all s.s.b. except the two sidebands from the HC station.

Twenty-one megahertz was found to be harbouring; CR6FP, CX4CR, K7UIT, OHØNI, WBØDIR, 4S7TB and 9V1NR all on s.s.b.

J. Moore (Leicester), still titivating the dial on his CR100/2 fed with 130ft. of wire via an a.t.u. managed to bag these on 14MHz; AX2AAR, AX2AGN, AX3JW, AX4KS, C31CY, CN8BG, EA6BN, ET3USA, FM7WW, HT6GAF, LU2FAO, OB4OS (another prefix for Peru), OHØNK, PY2DSC, PY3AHJ, PY7VGP, TI2RSR, VK3AM, VK3QX/M, VK5FM, VK7AZ, YS1O, YV1ON, YV1ACT/5, YV5DFI, ZB2A, ZM4FX, 4N2KO (Korcula Island), 4X4RW, 6Y5GA, 9G1BF, 9Y4KR.

Fifteen metres gave a good account of itself where John heard; CR4BB, CR6GA, CR6JW, CR7AF, CT3AS, EL2BU, EP2DX, HK3AUE, HS1ABC, IT1SEZ/P (Ustica), fifteen JA stations, JH1JLR, JR1HRX, KC6RS, KR6JU, KS6DH, LU1ZE, OD5EP, PZ1AP, TI2ALG, VP8KL, VP9MI, VU2BEO, VU2OLK, WB6WQV, W7HFD, XW8DM, ZC4CB, ZM6QK, ZS5OE, 5N2AAE, 5R8AS, 5VZWT, 7Z3AB, 9E3USA, 9G1BF, 9H1BX, 9H1CB, 9J2PV, 9V1PA.

A. Crooks (Leicester), RA1, PR30, 45ft. end-fed,

reports 20 metre sigs from; AX2DD, AX2OZ, AX3AYT, AX5EJ, CR6MT, CR7IC, CT3AN, EP2DA, ET3DS, FG7TD, HBØXJK/M, HK3BLD, JA3XPO, LU8DX, MP4QBK, OHØNI, PJ2HT, PZ1AC, PZ1DF, TA1KT, TF2WKI, TI2ES, TU2BB, VE1YY, VE3FKD, VP8HZ, VP8KL, VU2BEO, VU2VAE, YA1MLX, YV4AU, ZD7SD, 4N2KO, 4S7PB, 5X5MP, 5Z4MO, 6W8DY, 6Y5GA, 7Z3AB, 9Y4VV.

On 21MHz Andy hooked; CE7DW, CR6LC, CR7IZ, CT2AK, CX9CO, JA7BSD, K5TSR, KP4BBK, KR6JU, KV4AD, LG5LG, LU7SE, PZ1AP, SV1CC, SVØWY, VE3AIU, VP2MM, VP2VI, VP8KD, VP8KL, VS5RG, W6MSM, W7APA, ZD8AB, ZE1DG, ZS1NL, 3V8AL, 4N2LO, 4Z4AQ/MM (20°N 18°W), 5N2AAE, 5VZWT, 5Z4KM, 6W8AL, 9G1GT/M, 9H1CB, 9J2PV, 9M2VI, 9Q5QR, 9U5DP, 9V1PQ.

A. Trelinski (Warks.) has a Lasky's Skyrover with a b.f.o. Hoards of G stations logged on 3.5MHz while on 14MHz; CE1FF, K6DXX, 5T5AD, VK9NT, WB6NDC. Alexander says that some of these stations were stronger than Radio 4 (I don't know that callsign—new country?).

T Thornton (Berks.), CR7OA, 132ft. end-fed, is pleased with the results of an eavesdrop on 28MHz. Stations immediately responsible for causing such pleasure are; CR6GA, CX9CO, DU1FH, EA8GZ, FG7XT, KV4CM, LU5FEH, MP4BFO, PY8GES, TR8MC, ZC4IK, 4X4WP, 9H1BL.

S. Davies (S. Wales), Murphy B40C, "full-wave" dipole for 28MHz at 20ft. claims great activity on ten metres. Included in his log are; CE8AA, CR6FA, CR7AF, CX8DM, CT1UN, EL2AW, HK3VK, KG4AM, KP4ATS, K4EBW, K8SMC, LU2DEK, LU7AAG, PY2DSQ, VE3BPX/4, WB4OSW, WB6ODA, W5BY, ZE2JO, ZK5DV, ZP5GS, ZS1UF, ZS4MZ, 7Q7AA, 9J2RO, 9J2AG.

N. Richardson (Bucks.) reckons that conditions have been good on 144MHz. The gear comprises an 8-element Yagi, Garex converter, PR30, CR7OA tuning 28-30MHz. Signals of the a.m. variety were received from; F1APQ, F1BCI, F5VH, F6ALH, ON4RY, ON5HH, ON5NY, PAØCML, PAØFHV, PAØTLX, PAØJHT. Solitary sidebands squeaks from; GM3OXD/P, HB9ADJ/P, PAØFWS.

November offers a good choice for the contest enthusiast and s.w.b. The diary reads, November 7-8th, 40 metre phone contest; 7-8th, two metre c.w. contest; 14-15th, top-band contest; 20-21st, Malta Independence Day phone/c.w. contest; 27-28th, CQ world-wide DX contest; December 6th, 2 metre fixed-station contest.

Please note. The address for all communications, which includes logs, for The Amateur Bands is now:

14, Manland Avenue, Harpenden, Herts.

Logs in alphabetical order please, to arrive by the 15th of the month.

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents

Light communication

Concerning the article in the June P.W. concerning the Light-Operated Telephone, I have some comments to make:

Some years ago I had cause to experiment with light-modulated beams and whilst doing this I noted the restriction of h.f. due to the delay in the bulb filament heating and cooling at h.f. The amplifiers used at this time to drive the bulb were ECC83/6V6 valved units with an output of about 2-3W into 3 ohms. I drove the bulb from the secondary of the output transformer. I experimented with various bulbs and found the pre-focus type gave the best performance (I recall I used a 6V type). To overcome the h.f. heating lag, I included a battery in series with the bulb/transformer secondary, under-running the bulb just enough to see the filament glowing. The battery was bypassed to a.f. with a 25 μ F capacitor. When signals were transmitted, the filament, already hot, was able to pass considerably more h.f., and overall a better performance was obtained.—**Roger Bunney** (*Hampshire*).

Musical pollution

I think it's about time something was done about piped music and background music. Music is supposed to soothe the savage breast but when one gets a juke box blaring in a pub when one is trying to talk business or has musical "inducement" when trying to buy clothes and to cap it all, music in the Hilton's lifts, it makes one's breast all the more savage to think that some cretin somewhere has conned some morons somewhere else into thinking that this intrusion induces sales and adds to enjoyment.—**M. Casey** (*London*).

Wiring colours

I am sorry about Mr. Gallacher's colour blindness but feel that this minority affliction hardly constitutes a valid argument against the well-recognised colour coding for mains wiring, red, black and green.

He does not mention the other widespread use of green and

red—namely road signs. I do not know if he drives a car, but if he does, although traffic signals can be recognised by position, what of the single lamps used at traffic control of roadworks, and the very many danger signs and direction signs. Also, what about the compulsory red rear lights on cars?




Although we now have to accept the new colours for mains wiring, I still cannot see the reason for the modification, or for the choice of these colours.

Often, I feel, they get together and decide on some new way, or new regulation (particularly on cars) to boost sales and profits.—**E. W. Baigent** (*Buckinghamshire*).

Printed circuits

I read Mr. R. A. Yates' article in the May edition of *Practical Wireless* concerning the making of printed circuit boards with some interest. However, Mr. Yates' advice to bend the ends of the leads to the wire becoming bonded to the copper laminate with a film of solder which does not remove easily on desoldering and removal of the component becomes more difficult and can result in a damaged laminate.

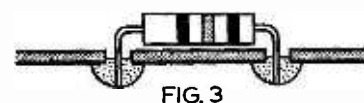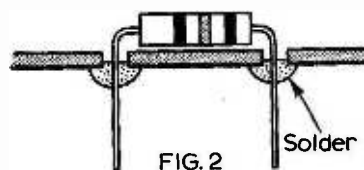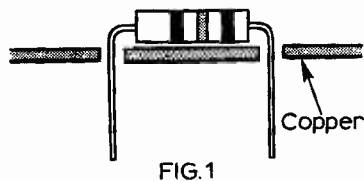The method taught me is to leave the leads long and to push the leads through the holes drilled in the board as in Fig. 1. The iron is then rested with the



side of the bit on the laminate and the end on the lead. A quick application of the solder results in a neat mound of solder as in Fig. 2. It only remains then to cut off the lead at the top of the mound giving the result shown in Fig. 3 which can be desoldered quite easily for the component removal if this should become necessary at some later stage.

This is a well-tried method and I hope it may help readers to make better printed circuit boards.—**A. Morgan** (*Berkshire*).

Born too soon?

I am now 71 years of age and I fear have entered my second childhood. Some time ago, I found my old toy box with relics of my younger days and in it was a book by Maurice Child called "Small Power Wireless Installations," price 1s. There was another book entitled "Wireless Telegraphy for Amateurs," by Hawgrave Graham. I put the books down, rested my old head in my hands and lapsed into reverie. I remembered my first set, built in a cigar box from instructions from the "Scout." Next came a more ambitious one in a Hudson soap box with sliders, etc. I had a fine aerial with broomsticks as spreaders and aluminium wire. Alas, near me lived a police sergeant and when the 1914 War broke out, I was ordered to hand in the lot. When 2LO came on the air, I was off again!

Some time later I remembered an old domestic set for medium and long waves under the bench. I stripped the coils out, got new ones from Denco with a 3-gang 300pF capacitor and re-built the chassis for long, medium, short and trawler reception. It worked, but the hum was nearly as loud as the signal!

Now, I spend hours in my shed with this set and copies of P.W., wondering if I'll ever be able to master all this n.p.n. and p.n.p. business and zeners and all the other mysterious things happening today in the world of radio. So please tell those "size 8 heads" to have pity on us old ones—we can't help it—we were just born 60 years too soon!—**W. Wickins** (*Norfolk*).

I.C. Stereo Equalisers & Mixers

CALEB BRADLEY B.Sc.

INTEGRATED circuit flatpacks are now available containing two or more linear amplifiers with sufficient isolation for multi-channel audio use. Possible applications are in equalisers for stereo signal sources where two preamps with identical frequency responses are required and in audio mixers where two or more preamp stages are needed (two for each signal source for stereo). Each of the circuits described here consists of one i.c. and a few discrete components and can be constructed inside a very small space; for example, the equaliser circuits can be fitted easily into a matchbox. More space is occupied by the controls in the case of the mixers. Power requirements are small and are simply met by batteries which will have many months' useful life. Alternatively, these circuits will generally be feeding a main amplifier from which power can be taken.

The i.c.'s used here are the Motorola MC1303P which contains two linear amplifiers, and the R.C.A. CA3048 which contains four linear amplifiers.

MC1303P

This device forms an ideal basis for a stereo preamplifier. By adding suitable feedback components, the two amplifiers can be given a suitable frequency response for equalisation of stereo signal sources such as magnetic pickups or tape playback heads; alternatively, the MC1303P can serve as a high-gain, low-noise and low-distortion preamp stage with a flat frequency response suitable for two inputs from tuner, microphone, electric guitar, etc. The equaliser circuits can be added to any valve or transistor amplifier as the MC1303P has a low impedance output to suit both high and low impedance amplifier inputs. An output swing of up to 5.5V is available, enough to drive almost any audio amplifier. Lower distortion is obtained with smaller outputs, however.

The MC1303P consists of two separate high gain amplifiers in a 14-lead flatpack. The two amplifiers are arbitrarily labelled for left and right stereo channels in the circuit shown in Fig. 1, but there is no reason why they should not be used for any pair of mono signals. Only the power supply connections are common to both channels. From the characteristics listed in Table 1, it can be seen that the channel separation is high. The circuit consists of 16 transistors and 18 resistors, not an exceptionally large total to squeeze on a tiny silicon chip inside a plastic slab only $\frac{1}{4}$ in. long, by today's standards. Component references are given for the 'left' channel only as both amplifiers are identical. Operation is as follows.

Positive and inverted inputs are received by the long-tailed pair amplifier Tr1, Tr2. This is directly coupled to a second similar amplifier Tr4, Tr5. The tail current of Tr4, Tr5 is sampled by Tr3 which is a constant current source in the tail of Tr1, Tr2. This

MOTOROLA MC1303P Summary of Characteristics

Type:	Monolithic two-channel amplifier, silicon epitaxial structure, in standard 14-lead flatpack.
Max. supply voltage (25°C)	-15-0-15V d.c.
Temperature range	0-75°C
Channel separation (10kHz)	>60dB
Characteristics each channel:	
Open loop gain	>8000 (78dB)
Output voltage swing	4.5-5.5V r.m.s. max.
Input noise volts	0.5µV typical
Input bias current (mean of +ve & -ve inputs)	1-10µA
Input offset current	0.2-0.4µA
D.C. Power dissipation	300mW max.

TABLE 1

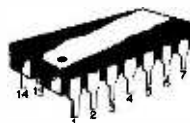
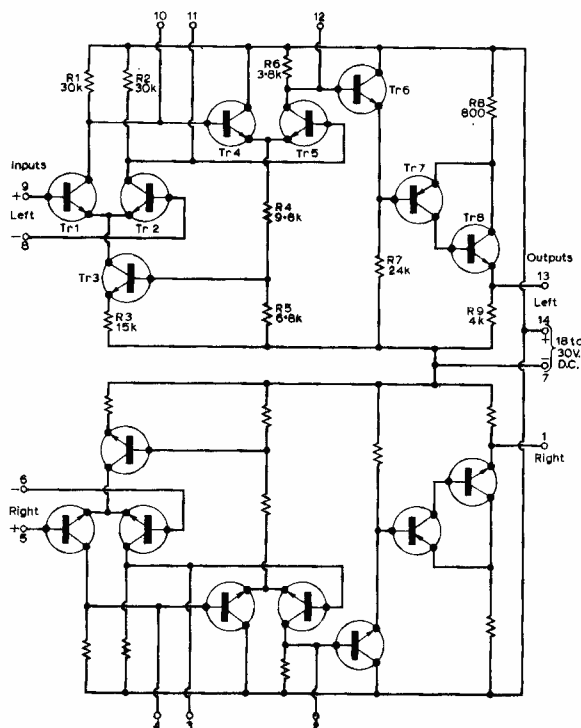


Fig. 1: The internal circuitry and packaging of the MC1303P i.c. two-channel amplifier.

Merry Christmas from Antex

Complete Soldering Kit 55/-

This contains the iron fitted with a $\frac{1}{16}$ " bit, interchangeable spare bits $\frac{3}{32}$ " and $\frac{1}{8}$ ", resin cored solder; felt cleaning pad; stand for soldering iron, and a booklet "How to solder." From Electrical and Radio Shops or send cash to Antex.

Model CN 240/2
15 watts - 240 volts 34/-
Fitted with nickel plated bit $\frac{3}{32}$ "
and in handy transparent pack. From
Electrical and Radio Shops or send
cash to Antex.

PRECISION MINIATURE SOLDERING IRONS
Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 61371/8.
Telex: 45296. Giro No. 2581000.

☐ Please send me the
Soldering Kit
I enclose cheque/P.O./cash value

NAME
ADDRESS

☐ Please send me the
Model CN 240/2 Pack

ROC ELECTRONICS

50 PROJECT ELECTRONIC KIT

Model R.130



King of the Roc Electronic Kits is the Giant R.130 which makes up into no less than 50 separate projects including Radio Receivers, Transmitters, Tachometer, Rain Alarm, Testers, Electronic Switches, Amplifiers and even an Electronic Target Game. As well as earphone, speaker, meter, relay, transformer, solar cell, buzzer, etc., etc., the R.130 is supplied complete with a fitted hardwood case and clear detailed instructions for all 50 projects.

PRICE £7.19.0

4 BAND SHORT WAVE RECEIVER KIT Mod. R.140



This excellent transistorised battery operated kit will not only provide hours of entertainment when made up but also in its construction. It receives the normal broadcast band 550 KhZ-1.6MHz and on shortwave 1.5 MHz-30 MHz in three bands. The 32 page manual not only shows step by step instructions on how to assemble the kit but also includes a guide on broadcasting stations throughout the world.

PRICE: £9.8.0

PROFESSIONAL SOLID STATE FOUR BAND COMMUNICATION RECEIVER Model R.135

This is the communication receiver that you have long been waiting for. Fully transistorised and continuous coverage from 555 KhZ-3 MHz in four bands including illuminated electronic bandspread for 160-10 metres. Also incorporated is an internal speaker, automatic noise limiter, SSB/AM/CW Switch, AVC Switch, S Meter, Receive and Standby Switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. The R.135 will run off of 240v AC, dry batteries or any 12v DC negative ground source.



PRICE: £45.0.0

20 PROJECT SOLAR ELECTRONIC KIT Model R.128

This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/2 in capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a Morse set complete with key and Morse training code. Supplied complete with easy to follow instructions and even the cement to assemble this unique electronic space capsule.

PRICE £4.10.0

2 OCTAVE ELECTRONIC ORGAN KIT Model R.129

Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves. Slotting into a fitted hardwood case the top panel carries the key assemblies and all the components including the loudspeaker. Like all Roc Electronic Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

PRICE £4.10.0

10 PROJECT INTEGRATED CIRCUIT KIT

Model R.127

Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio. (2) Test Oscillator. (3) Morse Telegraph Training Set. (4) I.C.T. Transistor Radio. (5) Germanium 1 Transistor Radio. (6) Record Player Amp. (7) Continuity Tester. (8) AF Signal Tracer. (9) Radio Transmitter. (10) Water Purity Tester.

PRICE £3.10.0

2 TRANSISTOR SOLAR RADIO KIT Model R.126

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.

PRICE £2.10.0

CRYSTAL RADIO KIT

Model R.125

This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite aerial for maximum efficiency. A perfect introduction to Radio Theory.


PRICE £1.10.0

5 WATT STEREO INTEGRATED AMPLIFIER CHASSIS Model R.123

Mounted on a heavy gauge chassis the fully transistorised R.123 stereo amplifier is completely self-contained even down to ganged volume and separate tone controls. For a simple stereo amplifier of excellent quality all you have to provide is the cabinet and control knobs.

SPECIFICATION: Output: 5W total, 2.5W per channel. Input sensitivity: 600mV at 2.2Mohms. A.C. 240v. operation

PRICE £4.19.0

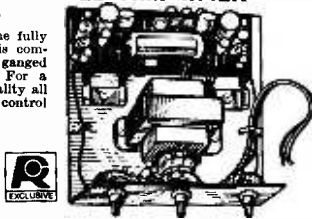

5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service. SPECIFICATION—Tape speed: 9.5 cm/sec (3 1/2 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 45dB at 1,000Hz. Output: 5W total, 2.5W per channel. Amplifier outputs: 200mV.

PRICE £36.0.0



AM/FM/MPX STEREO TUNER

Model R.134



Perfect Matching Unit to the R.136 Amplifier. The R.134 Stereo Tuner is designed to give years of reliable performance. The Tuning Band covers AM & FM with a separate stereo beacon to indicate when stereo broadcasts are being received.

SPECIFICATION: FM: Frequency Range: 88-108MHz. Usable Sensitivity: 18µV. Stereo Separation: 26dB at 1kHz. Image Rejection: 50dB. AM: Frequency Range: 535-1,605kHz. Usable Sensitivity: 280µV.

PRICE: £21.0.0

4 WATT STEREO FM/AM/MPX TUNER AMPLIFIER

Model R.124

Another Roc Exclusive offering top value for money performance the R.124 is a Stereo Tuner/Amp with facilities only usually found in much more expensive units. Features like separate bass and treble controls, automatic frequency control switch and stereo headphone socket give the R.124 a price to specification ratio second to none. Housed in a handsome walnut cabinet the classical low line styling of the R.124 will grace any home.



SPECIFICATION: FM: Frequency Range: 88-108 MHz; Usable sensitivity: 20µV; Stereo Separation: 26dB at 1 KHz, 20dB Minimum; Image Rejection: 55 dB; AM: Frequency Range: 535-1605 KHz; Usable Sensitivity: 300µV; Audio Section: Total Output Power: 4 Watts; Phono Input: 200mV at 1 megohm. Tape Input: 100mV at 100 Kohm.

PRICE £29.19.0



STEREO HEADPHONES Model R.328

Built up to a standard not down to a price, the R.328 stereo headphones represent a breakthrough in value for money.

A valuable addition to any stereo installation they will provide many hours of listening pleasure.

SPECIFICATION: Matching impedance: 8-16 ohms. Frequency range: 30-15,000Hz.

PRICE £2.8.0

H.P. Terms available for personal callers on purchases over £30



RETURN OF POST MAIL ORDER SERVICE (Dept. PW)

Orders under £10 please add 5/- post and packing. Orders over £10 sent post free.

ROC ELECTRONICS LIMITED

193 EDGWARE ROAD LONDON W2 1ET

TELEPHONE: 01-723 8211
Shop open 9-6 Monday - Saturday (Thurs 1pm)

arrangement provides d.c. feedback for stability and gives a high input impedance. As the circuit has a high gain extending far into the radio frequencies, some top cut must be introduced to ensure stability for audio use. This can be done by connecting an external capacitor (up to 1000pF) between tags 10 and 11.

The amplified signal across R6 is fed by emitter follower Tr6 to the complementary p-n-p/n-p-n amplifier Tr7, Tr8. This provides a low impedance emitter follower output on pin 13.

The basic wiring needed to operate the i.c. as a stereo preamp is shown in Fig. 2. Each channel has a feedback network wired from the output to the invert input to give an overall frequency response

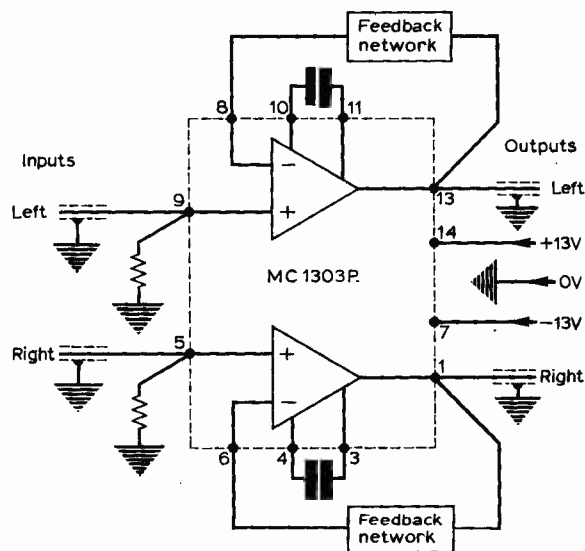


Fig. 2: Basic wiring of MC1303P for stereo preamp use.

appropriate to the signal source. The device needs a centre-tapped power supply of between $-9/0/9V$ and $-15/0/15V$ d.c. and the current drawn is only 22mA approx. The centre tap is needed to provide a bias connection for the input stages, and is a suitable earth point for the input and output cable screens.

PREAMP WITH LEVEL RESPONSE

The circuit in Fig. 3 is suitable for low level signal sources which do not require equalisation. It gives a signal gain of 40 dB (i.e. 100) with a response of 10Hz - 50kHz, $-3dB$. Since the lower end of R2 is returned to earth at a.f. by C3, the proportion of the output signal fed back to the invert input is approximately $R2/R3 = 1/100$. Since the open loop gain of the amplifier is very high, this sets the gain of this channel at 100 at audio frequencies. At higher frequencies, additional feedback is provided by C4 and the gain falls off.

Only 0.05V r.m.s. input is sufficient to drive either channel to full output (5V r.m.s.); beyond this distortion increases rapidly. Larger inputs can be handled if the gain is reduced by reducing the values of R3 and R6. The gain can be recalculated from the relation given.

MAGNETIC CARTRIDGE EQUALISER

The circuit in Fig. 4 is a useful addition to audio amplifiers with no provision for magnetic pickups,

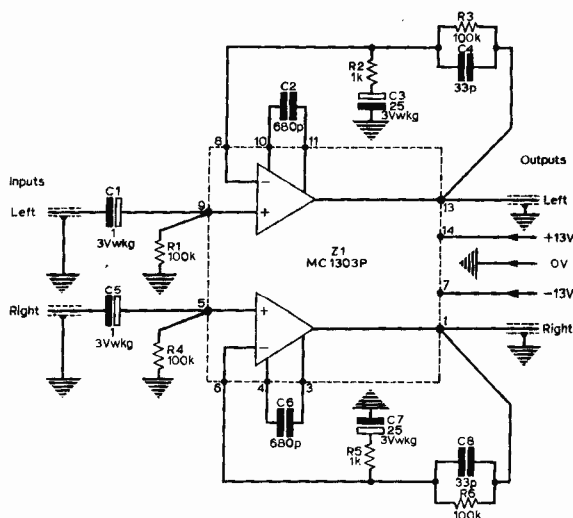


Fig. 3: General purpose stereo preamp with level frequency response.

and it also enables a record player to be improved by conversion to a magnetic pickup. The feedback network R3, R4, C4, C5 is chosen to give the standard RIAA LP record playback curve frequency response. Gain is 34dB (50) at 1kHz. For a maximum output of 5V r.m.s. at 1kHz, 100mV r.m.s. input is required and total harmonic distortion is 0.1 %. Noise

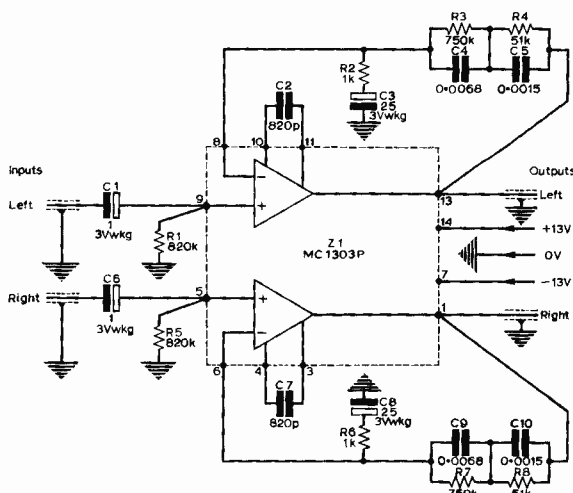


Fig. 4: R.I.A.A. equalised preamp for magnetic pickups.

is 70 dB below a 10mV input and hence the circuit is suitable for the lowest output stereo cartridges. As the input impedance is high, special care must be given to adequate screening of the input leads from the record deck to minimise hum pickup.

TAPE HEAD EQUALISATION

Very few commercial amplifiers or preamps provide for low level inputs from stereo (i.e. $\frac{1}{4}$ track) tape playback heads; an input labelled 'tape' is generally for medium level signals that have already been equalised in a tape recorder. The circuit in Fig. 5 provides NAB tape playback equalisation for either $7\frac{1}{2}$ or $3\frac{3}{4}$ inches per second playing speeds, depending on the values of feedback components R4, C4, etc.

For $1\frac{1}{2}$ i.p.s. speed, the values given for $3\frac{3}{4}$ i.p.s. are fairly satisfactory, or optimum values can be found by experiment. A two pole, three way switch will enable the component values to be switched for different speeds; on many tape decks this switch can be mechanically coupled to the deck speed selector.

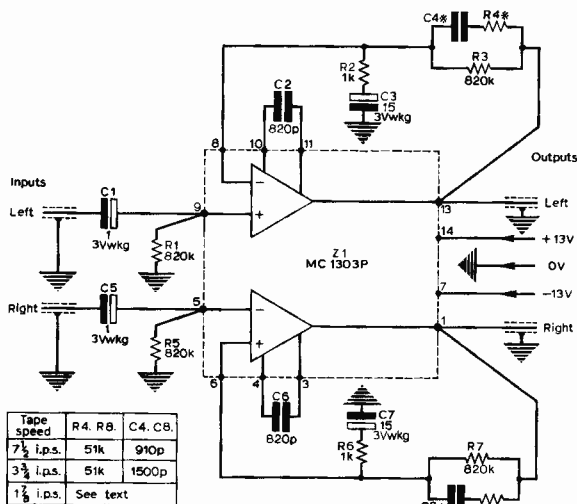


Fig. 5: Equaliser for stereo tape playback.

TWO-CHANNEL MIXERS

The MC1303P can serve as an active mixer for two mono signals if the two outputs in Fig. 3 are connected to potentiometers as in Fig. 6. Such a circuit would be useful for mixing two microphone signals. The $6.8k\Omega$ resistors serve to reduce interaction of the two level controls, and can be increased

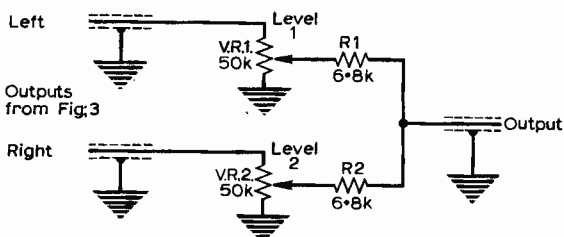


Fig. 6: Additional circuitry to convert Fig. 3 to an active two channel audio mixer.


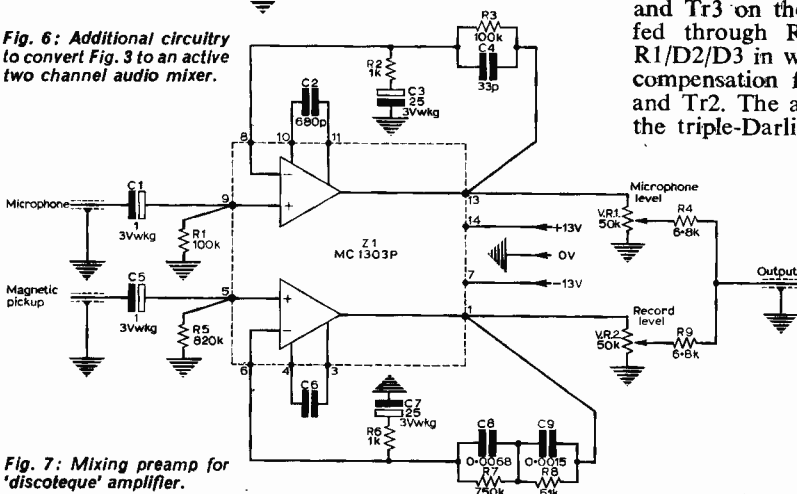


Fig. 7: Mixing preamp for 'discotheque' amplifier.

to $10k\Omega$ if the output loading is more than $50k\Omega$. The output loading should be not less than $10k\Omega$ unless lower values are chosen for VR1, R1, etc. Either amplifier in the MC1303P may be independently equalised using the component values in Figs. 4 or 5. An example is the mixer circuit in Fig. 7 which was designed for a 'discotheque' amplifier. One amplifier has a flat response and takes the signal from a disc jockey's microphone, the other amplifier provides RIAA equalisation for a mono magnetic record pickup.

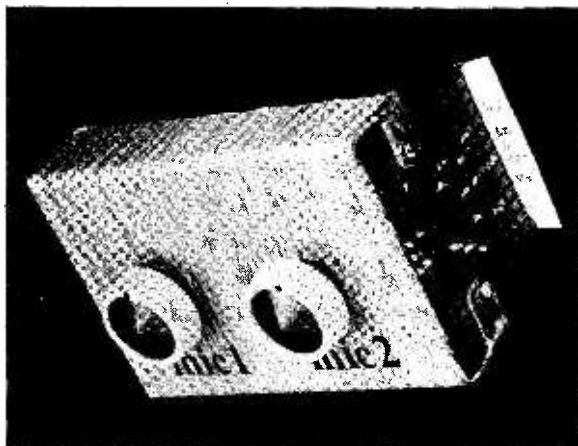

The small physical size of the i.c.s. makes it possible to build the equalisers and mixers very small.

CA3048

The RCA CA3048 is a 16-lead flatpack containing no less than four separate identical amplifiers. Characteristics of each amplifier are shown in Table 2. The circuit of half the device (i.e. two amplifiers) is shown in Fig. 8 where component references are given for one amplifier only. The circuit of the other two amplifiers is identical and separate, except that all the earth connections are to one pin, pin 5. Each amplifier operates as follows.

Positive and inverted inputs are received by a long-tailed pair amplifier consisting of Darlington-connected pair Tr1, Tr2 on the positive input side, and Tr3 on the other. Base bias current for Tr1 is fed through R3 from the potential divider R2/R1/D2/D3 in which D2 and D3 provide temperature compensation for the emitter/base junctions of Tr1 and Tr2. The amplified signal across R6 is taken to the triple-Darlington amplifier Tr4, Tr5, Tr6 which provides a low impedance output at pin 1 with a voltage gain equal to $(R11+R12)/R10 = 5$ (14 dB).

Unlike the amplifiers in the MC1303P, each amplifier in the CA3048 has an in-built a.c. and d.c. negative feedback loop R7, R9 between the output and the inverted input. Temperature compensation for the emitter/base junction of Tr3 is provided by D1. The effect of this feedback is to give each

The 'KIT IDEA' by HEATHKIT

kit building is so easy the
Heathkit way.



TRY IT FOR YOURSELF

**START WITH A SMALL
BUT VERY USEFUL KIT**

**THE NEW HEATHKIT
BATTERY CHARGER**

PRICE ONLY
£2.18.0. plus carr. 6/-

**POWERFUL OUTPUT—UP TO 4 AMPS • FULLY FUSED • SOLID KNOCKABOUT CASE •
SAFE DOUBLE WOUND TRANSFORMER • FOR 6V OR 12V CARS • ROBUST AMMETER**

Here's the easy to build, inexpensive kit to introduce you to kit building. As well as the fun and fascination of building it yourself you get Do-it-Yourself savings. The clear, simple, fully illustrated instructions make assembly foolproof. This is the battery charger to keep your car battery in top working condition.

Hurry, and make sure of your order today.

P.S. This also makes an excellent seasonal present . . .



A Schlumberger Company

HEATH (Gloucester) LTD GLOUCESTER GL2 6EE

(Block capitals please)

Name.....

Address.....

.....

Post Code.....

Please send me a battery charger kit for
which I enclose £3.4.0, including carriage.

DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master inter-com. Simply plugs together. Originally sold at £10. Special snail price 49/6, plus 3/6 postage.



Be first this year! SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden frame. Post and ins. 3/6. **19/6**

12V EXTRACTOR FAN BY DELCO

Caravan, Car or Boat. 6 Bladed 5" diameter fan inside heavy duty cylinder with 3 point fixing flange. 5 1/2" diameter fixing hole. Length approx. 8 1/2". Exceptional bargain 27/6 plus 5/6 post and insurance.

HAPPY FISH

and lively indoor Plants have 'LUX GROWTH' lighting which gives U.V. and other rays essential to healthy flora & fauna—Special Trial Offer. 9" U.V. tube complete with choke, starter tube, connections and spring clips—all you need incl. wiring diagram 39/6 plus 4/6 post & ins.



MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 1/2. 19/6 each.



2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £13.15. Post and ins. 7/6.



THIS MONTHS WORKSHOP AID

RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 10 or 15 amp—simply fit in place of switch.



VARIAC CONTROLLERS



With these you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to film lighting. We offer a range of these, ex-equipment but little used and in every way as good as new. Any not so, will be exchanged or cash refunded. 2 amp £4.19.6, 5 amp £7.19.6, 8 amp £12.19.6, 10 amp £15.19.6

STANDARD WAFER SWITCHES

No of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
6 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
7 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
8 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
9 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
10 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
11 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
12 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6

THE FULL-FI STEREO SIX

The amplifier



Sensation of the year. You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses over the two channels. The amplifier is ideal for use with reproduction and at the same time, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include 'treble lift and cut', 'balance' and separate mains on/off switch. UNREPEATABLE PRICE is £28.19.6 plus 7/6 post and insurance.

Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. S.A.E. with enquires please.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. At the pull of a cord it extracts grease, grime and cooking smells before they dirty decorations. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Suitable wherever it is necessary to move air fast. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. 39/6 + 6/6 post and ins.

MULTI-SPEED MOTOR

Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (while the beaters of the food mixers normally go) and 8,000, 12,000 & 15,500 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1" diameter and approximately 1" long. A further point about this motor is that being 230/240v AC-DC series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2 1/2" dia. x 5" long, mains 230/240v. Price 17/6 plus 4/6 postage and insurance. 12 or more post free.

'CORONET' CAMERA

at a fraction of maker's price Plus this FREE over-ready drop-front case and shoulder strap. British made with precision auto-focus lens. Perfect pictures in colour and B & W. 12 pictures on Kodak 127 film. Extremely strong and robust. 14 days' free trial. We guarantee to return your money in full if you can't take perfect pictures. 19/6 + 2/6 p & p.



12v 1/2 amp POWER PACK

Comprises double wound mains transformer with full wave rectifier and 2,000 mfd smoothing. 27/6 + 4/6 P & P

ELECTRONICS (CROYDON) LTD

Dept. PW, 266 London Rd., Croydon CRO 2TH
Also 102/3 Tamworth Road, Croydon

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEM (0702) 46344

FULLY TESTED AND MARKED

AC107	3/-	OC170	4/6
AC126	3/6	OC171	4/6
AC127	3/6	OC200	5/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF239	7/6	2N1302-3	4/-
AF186	10/-	2N1304-5	4/-
AF139	7/6	2N1306-7	7/-
BC154	5/-	2N1308-9	7/-
BC171 = BC107	2/6	2N3819 FET.	7/-
BC172 = BC108	2/6	2N3844A	5/-
BF194	3/-	Power Transistors	10/-
BF274	3/-	OC20	10/-
BPY50	4/-	OC25	10/-
BSY25	7/6	OC26	10/-
BSY26	3/-	OC28	7/6
BSY27	3/-	OC29	7/6
BSY28	3/-	OC30	5/-
BSY29	3/-	OC36	7/6
BSY95A	2/6	AD149	10/-
OC41	2/6	AUY 10	30/-
OC44	2/6	2N3055	12/6
OC45	2/6	28034	2/-
OC71	2/6	Diodes	10/-
OC72	2/6	AAY42	2/-
OC73	3/6	OA91	2/-
OC81	2/6	OA79	1/9
OC81D	2/6	OA81	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

FREE!

Packs of your own choice up to the value of 10/- with orders over £4.

RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors, PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

PI PLEASE ASK FOR PAK P.I. ONLY 10/-
2/- P. & P. on this Pak

NEW UNMARKED UNTESTED PAKS

H10	25	Mixed volts 1 1/2 watt Zeners Top Hat type.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
H11	30	Mat series "Alloy" PNP Transistors.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
H15	30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
H16	8	Experimenters' Pak of Integrated circuits. Data supplied.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N705A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H20	20	BY126/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type. AV.40% Good.	10/-

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	10/-
H8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	10/-
B79	4	IN4007 Sil. Rec. Diodes. 1000 P.I.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	58P5 Light Sensitive Cells. Light Res. 400 Ohm Dark 1M Ohm	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN. Sil. Trans. A06 B8X20 2N2369 500 MHz, 360mW.	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B99	200	Mixed Capacitors, Post and packing 2/6. Approx. Quantity counted by weight.	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC172, NK271, etc.	10/-
H4	250	Mixed Resistors, Post and packing 2/6. Approx. Quantity counted by weight.	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-
H9	2	OCPT1 Light Sensitive Photo Transistors.	10/-

1970 Mullard Data Books, Data and Equivalents on Semiconductors, Valves and Tubes. Price 4/- each. P. & P. 6d.

P.O. RELAYS 8 FOR
Various Contacts and Coils
Resistances.
Post & Packaging 5/-
20/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA POSTAGE.

R.C.A. CA3048 Summary of Characteristics

Type: Monolithic four-channel amplifier, silicon epitaxial structure, in standard 16-lead flatpack. Each amplifier has a.c. and temperature-compensating d.c. feedback.

Max. supply voltage (25°C) +16V d.c.

Temperature range -25°C to 85°C

Channel separation (1kHz) >45dB

Characteristics each channel:

Open loop gain (a.c. feedback bypassed) >500 (54dB)

Gain with feedback 6 (16dB) approx

D.C. Power dissipation 150mW

TABLE 2

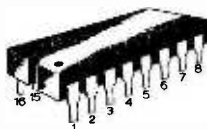
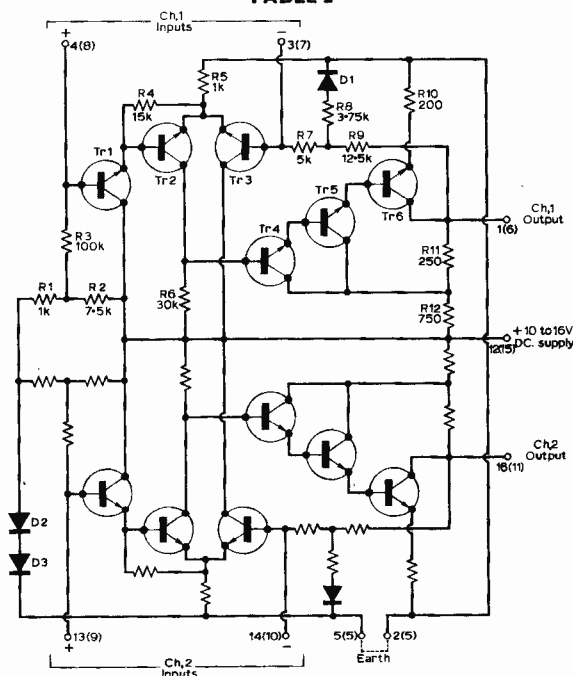


Fig. 8 (above): Internal circuit and pin identification of the CA3048 i.c. 4-channel amplifier. The circuit of half the device is shown; the other half is similar with connections to the pin numbers in brackets.

Fig. 9 (right): (a) Four channel active audio mixer using CA3048 (b) Modification for mixing two stereo signals (see text).

amplifier a very linear frequency response and a high input impedance of nearly 100k Ω , the value of R3. It also produces very low impedance at the inverted input. By bypassing pin 3 to earth through a large capacitor (50 - 100 μ F for audio frequencies), the feedback is removed at a.f. and the gain of the amplifier rises from about 16dB (6) to 57dB (700). A variable resistor

of 25k Ω in series with the capacitor can be used as a gain control over this range.

4-CHANNEL AUDIO MIXER


The circuit of a 4-channel active audio mixer based on the CA3048 is shown in Fig. 9a. Each input signal is brought through a level control (VR1 etc.) to an amplifier providing 34dB (50) gain, set by the value of R1, etc. The four outputs are combined by R9, etc. to produce a single output; the effect of these combining resistors is to reduce each channel's gain to approximately 20dB (10). As for the two -channel mixers described, the output loading should not be less than 10k Ω .


Instead of mixing four mono signals, the CA3048 can be used to mix two stereo signals. For this, double ganged potentiometers are used for VR1/VR3 and VR2/VR4, and the output arrangement is modified as shown in Fig. 9b. Each double ganged potentiometer then gives simultaneous control of the left and right channels of one stereo signal, and the maintenance of left/right balance will be as good as the tracking accuracy of the potentiometers used.

CONSTRUCTION

Since each of the circuits given consists of one i.c. and only a handful of discrete components, no firm layouts need be given. The pin arrangements of the i.c.s will suggest suitable layouts, and provided component leads are kept short there should be no stability problems. The circuits can be wired up conveniently on a small piece of drilled paxolin sheet or Veroboard, and put in a metal lozenge or tobacco box for screening. The screens of the input and output leads and the power supply earth should be connected to the metal box, ideally at the same point. The author's preference is to connect the i.c. in 'dead insect' fashion, i.e. on its 'back' with the pins sticking up. It is then possible to desolder the pins one by one at a later date and remove the i.c. intact.

—continued on page 651

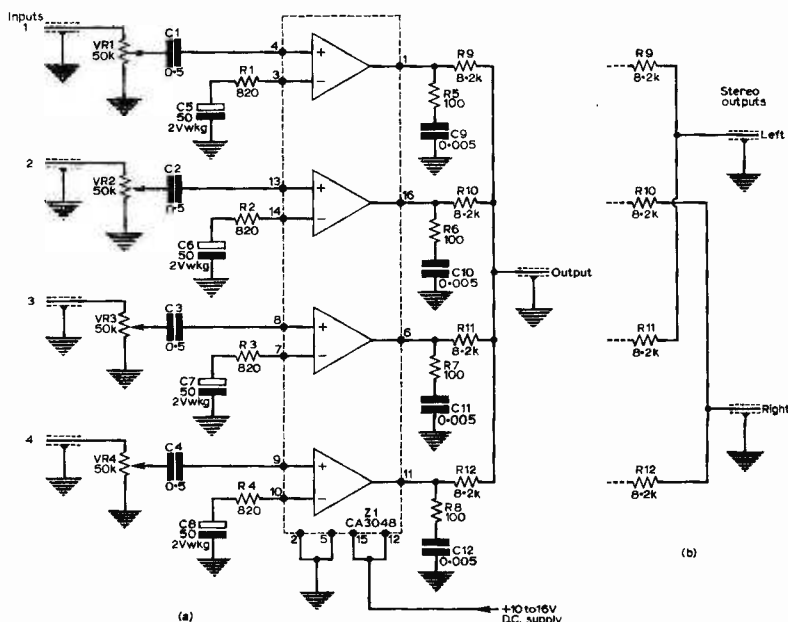

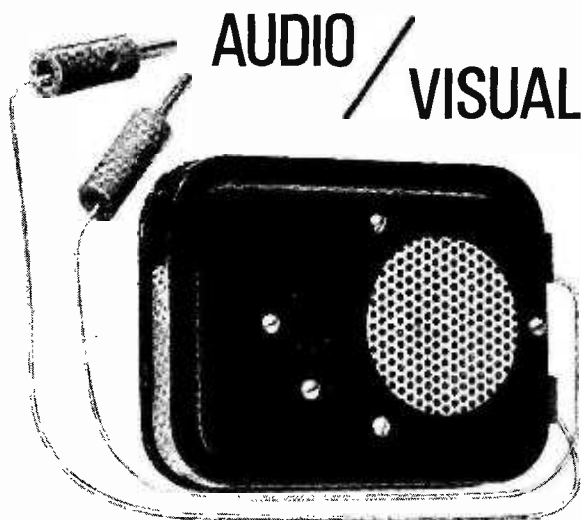

CONTINUITY TESTER

M.A.SPARKS

WHEN only a few points have to be checked for continuity an ordinary ohm-meter is as convenient as any instrument to use. But if a large number of continuity tests have to be made, then the continued looking from test points to meter scale and back again can become rather tedious.

Sometimes, too, it is useful to be able to make continuity tests in a situation where a conventional meter would be inconvenient or even dangerous; at the top of an aerial mast for example. The unit to be described gives both an audible and visual indication of continuity between two points and will also give some indication of intermittent contacts and resistances in circuit up to about 1k Ω .

CIRCUIT

As can be seen from the circuit diagram in Fig.1, the tester consists basically of a low frequency free-running or astable multivibrator. Because the circuit is not exactly symmetrical, when the current

supply is completed through the probes the current through one transistor (say Tr1) increases faster than the current through the other. The collector voltage of Tr1 will rise to almost zero.

This voltage change will be fed to the base of Tr2, so reducing its collector current and making its collector voltage more negative. This change is fed back to the base of Tr1, so causing a further increase in the collector current of Tr1. This regenerative action will continue until Tr1 is hard on and Tr2 cut off.

Capacitor C1 now charges up through R2 until the base of Tr2 becomes sufficiently negative that Tr2 begins to conduct, regenerative feedback causing Tr2 to turn hard on and Tr1 to cut off. C2 now charges up through R3 and the cycle repeats.

With the values of C1, C2 and R2, R3 given in Fig.1 the circuit oscillates a few times per second, causing the bulb in the collector circuit of Tr2 to flash on and off, alternating with a pulse of sound from the speaker in the collector circuit of Tr1.

CONSTRUCTION

Almost any p-n-p transistors with a collector current rating of about 100mA. or more can be used. The frequency of oscillation can be varied by altering the values of C1 and C2. Increasing the value will

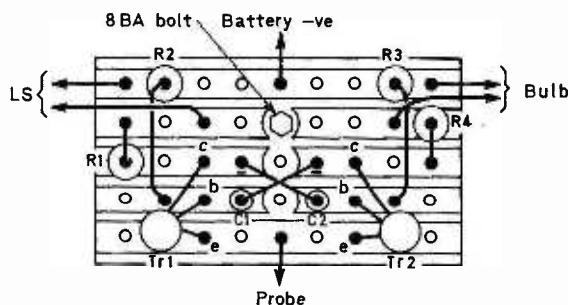


Fig. 2: Wiring of circuit board.

reduce the frequency; decreasing it will increase the frequency. If the frequency is increased very much, however, the bulb will appear to be on continuously owing to the thermal lag of the filament.

The small components are mounted vertically on a piece of Veroboard 9 holes long by 5 rows wide as shown in Fig.2. The centre hole of row two is


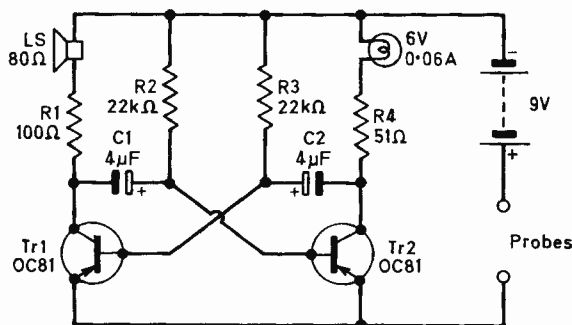


Fig. 1: Circuit of tester. All resistors are $\frac{1}{4}W$.

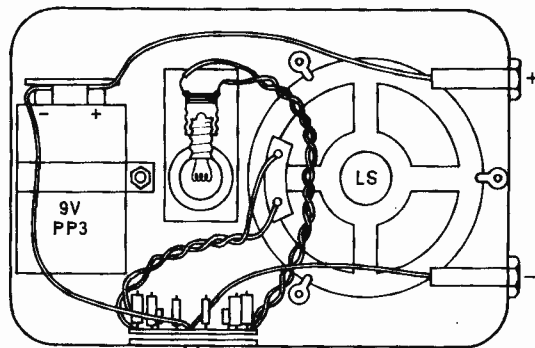

Positioning of major components and circuit board.

CODAR CR.70A

Communications Receiver 540 to metres





who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

NOT as a **PROGRAMMER** but an **OPERATOR**—No maths and no special education.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 437 9906 NOW!

Or post the coupon today for full details FREE and without obligation.



London Computer Operators Training Centre,
B31 Oxford House, 9/15 Oxford Street, London W.1.
Telephone: (01) 437 9906.
127/131 The Piazza, Dept. B32, Piccadilly Plaza,
Manchester 1.
Telephone: (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____

Address _____

Tel: _____

LOW COST ELECTRONIC AND SCIENTIFIC EQUIPMENT AND COMPONENTS

BRAND NEW HI-VAC NUMERATORS

Fig. size 16mm.
Cold cathode gas filled in line 0-9 digital display tubes. Long life expectancy. Minimum striking voltage 180V. Side reading Type XN 3, XN 7, XN 12 and XN 23. Specify amber, clear or red. Price 18/6 each. P. & P. 2/6.

KEYNECTOR

Connects anything electrical in seconds without plugs or sockets. No more worries about dangerous live wires. Now you can make electrical connections safely, in seconds with the revolutionary new Keynector. Cuts out plugs, sockets and saves time. A hundred different uses in the home, and a must for the do-it-yourself enthusiast. Only 46/6 plus p. and p. 5/- Or send for a leaflet

LAMPS

250V, 15W, MBC. Panel lamps. Ideal making up displays, etc. Length 2 1/2 in. x 1 1/4 in. Special offer, 10 for 21. P. & P. 6/-.

SYNCHRONOUS MOTORS

200/250V 50Hz. self starting. Model S7 1 RPH 30/-, Model S7 1 RPM 30/-, Clock Motor 2 RPH 20/-, Type MA 23 Low Torque Hysteresis Motors 1/60 RPM. 1/30 RPM. 1/12 RPM. 1/5 RPM. 1/4 RPM. 25/- each. Fitted one-way clutch 1/12 RPM. 1/6 RPM. 1/4 RPM. 1/3 RPM. 30/- each. P. & P. on any of above 5/- each.

NEW COMPLETE TELEPHONE DIAL ASSEMBLIES

Clear Perspex dials—no markings. 20/- each. P. & P. 5/-.

HIGH SPEED IMPULSE COUNTERS

by Davis, Wynn & Andrews. 4in. dial and pointer registers up to 100 and 4-digit counter, both manually re-settable. The drive to the counter is by air inverse escapement so that there is no loading of the pointer mechanism when digits are changed and adjustable pawls are unnecessary. Coil resistance 100 ohms for nominal volt operation, but the device works reliably from 20 volts at rates up to 10 impulses/sec. In circuit with a thyatron or neontron counting rates up to 100 impulses/sec. are possible provided pulse width is restricted to keep mean current to 100mA. Brand new in individually sealed boxes. Price 26.0.0. P. & P. 7/6.

LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW


High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in. conduit box. 240V, 50Hz, 600W. Price 59/6. P. & P. 2/6.

MEMORY CORE STORES

42 x 52 2K bit ferrite core store complete with 84 OA 10 load diodes. Ideal for building computer store or holding information in binary form. Price 45/- P. & P. 7/6. Handbook on use of core stores 2/6.

RIGHT ANGLED GEAR BOXES Suitable for rotating transmitter aerials

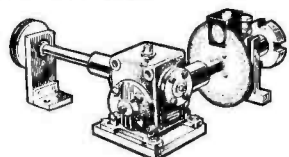Gear boxes give a drive of 14.5:1 at right angles to the input. Driveable through the 1/2 shaft only. Dimensions 4" wide, 3 1/2" deep, 4 1/2" high. Robust construction in cast iron. Price 59/6. With pulley and ball race shaft mountings. Price 79/6, carr. 15/-.



MINIATURE SQUARE COUNTER 6 DIGIT

By Veeder Root. Rotary ratchet type, adds 1 count for each 36° movement of shaft. 9/6 plus 2/6 P. & P.

ELECTRIC CLOCK MOTOR


NEW 200-250V, 60Hz, 2W. Synchronous induction motor. 2 revs. per hour. O/P shaft, 1/2 in. dia. x 1/2 in. long. Clockwise rotation. Three-holed mounting at 120° on 2in. P.O.D. Price 20/- P. & P. 4/-.

DELAY LINE

2 microsecond, 4,000 ohm. Type MON 2484D. Length 2 1/2 in. x 1/2 in. x 1/2 in. Encapsulated module. Price 30/- P. & P. 5/-.

4 DIGIT NON-RESETTABLE COUNTER

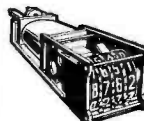Totalising 10 impulses per second. Length 3 1/2 in. x 1 1/2 in. x 1 1/2 in. 24V d.c., 300 ohm. Price 6/6. P. & P. 6/-.



OSCILLOSCOPE TYPE CT 52

A very handy miniature portable instrument for general purpose applications. 2 1/2 in. diam. tube. Wave form investigation from 10Hz-20MHz. Pulse monitoring duration 50 microseconds to 0.1 microsecond. Time base free running 10Hz-40KHz. Also single sweep facility from 50 microseconds to 3 microseconds. "Y" Amplifier. Delay Line Calibration Voltage. Power supply 110-250V, 40/60Hz, 60W. Supplied with metal carrying case. L. 13in. H. 8in. W. 5 1/2 in. Weight 14 1/2 lb. Price £22. P. & P. 30/-.



MINIATURE MOVING COIL RELAY 5115

By Sangamo Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance. 310 micro amps. 316 Ohm. List price £4.10. Our price 20/- P. & P. 3/-.



BRAND NEW MOVING COIL DC TEST METERS

Compact and portable. W 2 1/2 in. H 1 1/2 in. D 3 in. In black plastic case. Available as follows: 3-0.3 Volts. Prod on Base. 0-15 and 0-300V Dual Range Voltmeter 0-3 and 0-300V Dual Range Voltmeter 0-7.5 Amps Ammeter. Our Price £11.10.0 each. P. & P. 5/-.

PANEL LAMPS.

Robust superior design. 1" dia. to fit 1/2" hole. 1" O/A Length. Available Red or Green. 15 for 30/- P. & P. 5/- With Press to Test facility. 1" dia. to fit 1" hole. 1 1/2" O/A Length. Available White or Red. 12 for 30/- P. & P. 5/- Both types take 6mm Midget Flange Bulbs.

ELECTRONIC BROKERS (Dept. P.W.) 49-53 PANCAS ROAD, LONDON N.W.1 Tel. 01-837 7781 Telex. 267307

OPEN MON-FRI, 9-6pm

drilled out to take an 8BA mounting bolt and the copper strip cut well back so that the two halves do not short circuit across the nut.

A two ounce tobacco tin makes a convenient case for the tester with holes for the speaker and bulb cut in the base. The speaker is protected by a piece of perforated zinc across the opening and the hole for the bulb to show through is covered by a thin piece of coloured plastic sheet which is also large enough to insulate the bulb holder from the tin case. To prevent the copper strips of the Veroboard from shorting to the tin they are covered by a piece of thin s.r.b.p. sheet.

NOTES ON USE

Any convenient pair of test leads plugged into the sockets form the probes. Continuity between the probes is indicated by the regular bleeping and flashing emitted by the tester. As the resistance between the probes increases, so the bleeps and flashes become weaker and cease altogether if the resistance is more than about $1k\Omega$.



Rear view of tester and cover with magnet attached.

Intermittent contacts are shown by random crackling noises from the speaker. A shallow pot magnet bolted to the lid of the tin enables the tester to be 'stuck' to any convenient iron or steel surface and thus leave both hands free for more important tasks. ■

BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.

QUERY COUPON

This coupon is available until 4th Dec. 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, DEC. 1970

PW WALLCHARTS ON AUDIO STANDARDS

Standards are set to assist us. Too often they confuse. Somewhere in an isolated office a committee of notables sits around a table and fail to agree. Given the terms of reference to define a horse they come up with the specifications for a Bactrian camel.

Or so it appears to the engineer and enthusiast working in and around the field of audio and high fidelity.

There are so many standards, each valid in its own right, each different. Reading the specifications of a number of pieces of audio equipment, one could be forgiven for concluding that manufacturers set out deliberately to confuse. Usually, the reason for the great discrepancies is simply that each applies the standard to suit his own test procedures.

In an effort to clarify matters—or at least, to present the most important tests and measurements to the audiophile—*Practical Wireless* has whittled away the mass of standards and revealed the bare bones of facts and figures relating to international audio standards, and has included, where such inclusion may help, the methods and limits of testing and the types of test gear that must be used.

There are at least eighteen standards organisations publishing audio specifications. Space forbids their being listed here. Fuller details, including the addresses of standards-making organisations can be furnished to readers who apply to the Query Service in the usual way.


PRACTICAL WIRELESS QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard textbooks. In order to prevent unnecessary disappointment, prospective users of the service should note that:

- (a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.
- (b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.
- (c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.
- (d) We regret we are unable to answer technical queries over the telephone.
- (e) It helps us if queries are clear and concise.

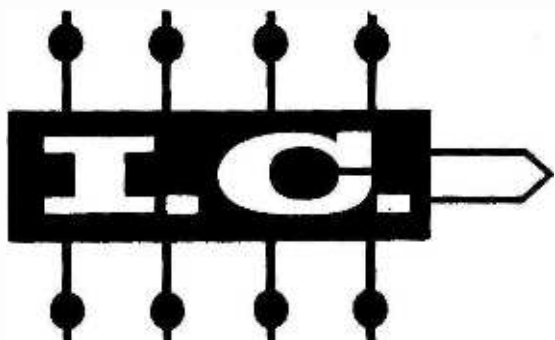(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.



OF THE MONTH

L.A.J. IRELAND

Number 14

The Motorola MC1596G Modulator/Demodulator

A NEW special purpose i.c. which will be of interest to the amateur radio fraternity is the Motorola MC1596G modulator/demodulator circuit. It can be applied to communications problems, in particular the generation of suppressed carrier signals; however, it will also act as a standard a.m. modulator, and in receiver circuits as a detector, not to mention its possibilities in laboratory instrumentation.

Circuit

The basic mode of operation can be deduced from the circuit diagram, Fig. 1. It should be remembered that in standard applications, a signal of considerable amplitude is supplied as the carrier, with the result that Tr1-Tr4 act in a switching, rather than a linear mode. The output is therefore the product of the signal input and a "square wave" of a frequency determined by the carrier signal; the signal input alone determines the amplitude of the output signal.

Theory

At this stage it is necessary to introduce a little mathematics. The Fourier analysis of a square wave is a sine wave of the same frequency plus a series of sine waves whose frequencies are the odd harmonics (multiples) of the basic square wave frequency, or fundamental. It follows then that if the modulator circuit is followed by a filter which passes the fundamental but blocks all the harmonics, the output of the complete assembly will be a sine wave whose amplitude is determined by the signal input. All the applications of the MC1596G are elaborations on this theoretical scheme.

A concept frequently found in electronics text books enters here, the idea of bandwidth. Only an infinitely long series of sine waves is definitively fixed in frequency: this, a further conclusion from Fourier theory, can be illustrated approximately as follows. To determine frequency, a number of sine waves must be counted and the corresponding time measured, from which the Hertz number (or cycles per second) can be calculated. The more cycles included in the count the more accurate the result will be; therefore to determine the frequency with absolute accuracy (zero bandwidth) an infinite series is required.

In a modulated signal the characteristics are constantly changing, in a manner determined by the modulating waveform; as a result only brief intervals are available for frequency determination, and the more complex the modulation the briefer the intervals, and therefore the greater the possible deviation from the precise frequency.

This deviation takes the name bandwidth, and it evidently applies as much to amplitude modulated signals as to f.m. transmissions. Those parts of the signal lying at frequencies other than the precise carrier frequency are referred to as the sidebands of the signal. Now, as it is the modulation which is responsible for producing the sidebands, it follows that the information can be reconstituted from the sidebands and the carrier may be regarded simply as a means of locating them. Therefore to transmit a given amount of information with the minimum radiated power, the carrier frequency should be omitted, and in a balanced circuit this is precisely the function the i.c. performs.

Moreover, as the sidebands are present symmetrically on each side of the carrier, either one carries

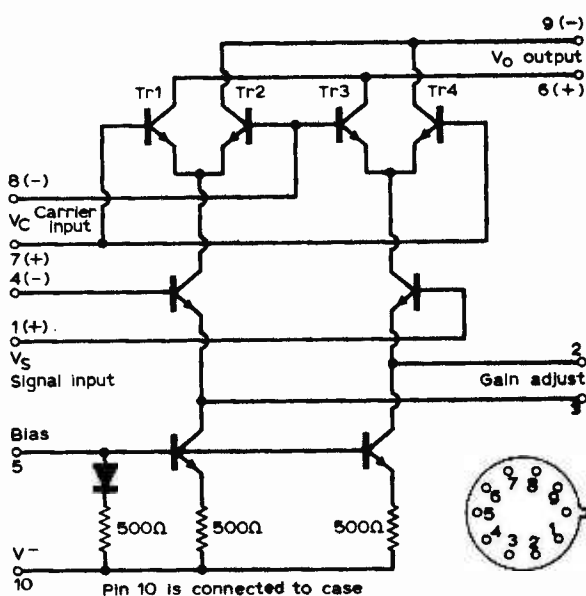



Fig. 1: Circuit of the MC1596G. Pin 10 is adjacent to the spigot.

the full information, so for even more effective use of available power, and to limit the bandwidth demands even further, one of the sidebands may be filtered out. The transmitted signal finally produced is referred to as "single sideband suppressed carrier" or s.s.b. (Sideband rejection, of course, is carried out by a series of LC circuits, not in the balanced modulator).

It should be noted that the analysis given above assumes accurate switching operation in the full wave gate section of the i.e. (Tr1-Tr4) so that the Fourier series of sine waves is produced. This is obviously dependent on the amplitude of the carrier signal applied to the modulator; should this be significantly lower than 300mV the transistors do not switch cleanly, with a consequent departure from precise squaring of the waveform, and therefore from the Fourier series. This implies a residual carrier-frequency component, to a degree determined by the extent of linear operation in the gate transistors, so the circuit output approaches the conventional amplitude modulation.

Applications

For use as a detector of either a.m. or s.s.b. signals, a carrier wave must be supplied in the same way as in the modulator case; however, this time the carrier is selected to be at the same frequency as the carrier of the signal to be detected. In a practical example, the signal is delivered by the final i.f. stage of a receiver, while the local carrier is generated by the receiver b.f.o. (beat frequency oscillator). The sideband will be displaced from the carrier by the amount of the modulation frequency, so it follows that if all the high frequency components of the i.c. output are rejected, the system output will be the audio modulation alone.

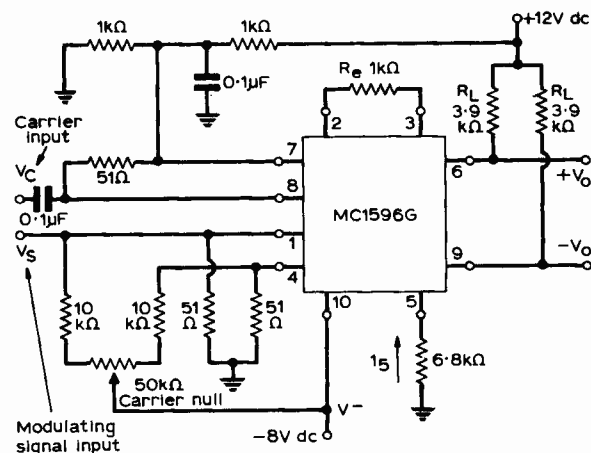


Operation of the MC1596G as a balanced modulator. If the circuit is unbalanced with the "carrier null" control a component at carrier frequency is introduced and a conventional a.m. signal results.

For morse reception, the b.f.o. is offset from the carrier, and the signal will be heard at a frequency determined by the extent of the offset. As before, for optimum results the b.f.o. amplitude should be 300mV and the a.m. or s.s.b. may be at any level between 5 and 500mV.

It will come as something of a surprise to find that this unit is also adaptable as a f.m. detector. In this case the i.f. output is applied to the carrier input of the i.c.; the signal input is fed through a linear phase shift network which may be adapted from an old f.m. i.f.t. The extent of the phase shift is frequency-dependent, and therefore varies with the audio modulation; the output of the i.c. will be a sum of the audio signal and a series of high frequency components which are rejected.

Other Uses

Those interested in instrumentation will recognise in the MC1596G the essential elements of a lock-in or phase sensitive amplifier, widely used in research and industry to recognise and identify synchronous signals once a reference frequency is available. In cases where a wideband, or even a tuned, amplifier is swamped with noise, a lock-in system is still able to follow a signal, since it switches in phase with that signal and adds the outputs, with the result that the signal becomes more evident while the noise, on average, cancels out.

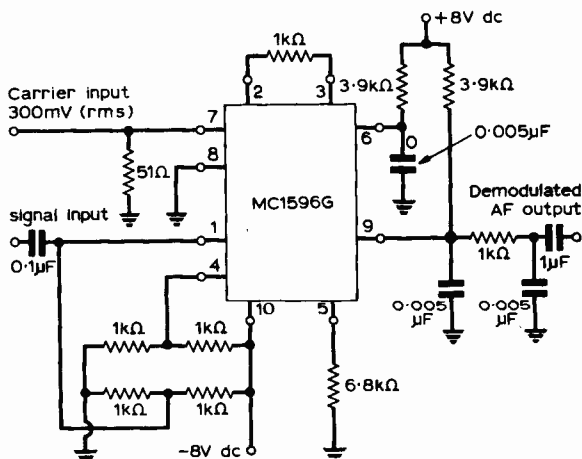

The MC1596G as an s.s.b. demodulator or product detector. A carrier input (b.f.o.) level of 300mV (r.m.s.) is optimum. The composite s.s.b. signal input may be between 5 and 500mV (r.m.s.).

One point of caution: under certain circumstances, depending on driving source impedances, instability may occur. If this is a problem, the inputs should be shunted by suppressor networks, made up of a 510 ohm resistor and a 10pF capacitor in series.

Notes

It is also worth noting the wide bandwidth of the basic device: the signal input is only 3dB down at 80MHz, while the carrier response only drops at 300MHz. The price of around £3 is something of an inhibition, but if past experience with i.c.'s is any guide, it should drop rapidly, particularly in view of the versatility of the device.

The unit is currently available from Motorola distributors in the U.K., including:

Jermyn Industries, Vestry Estate, Sevenoaks, Kent.
Celdis Ltd., 43/45 Milford Road, Reading, Berks. ■

a sensitive telephone amplifier



ALMOST everybody who regularly uses a telephone will know the frustration caused by a poorly connected call where words are heard faintly and have to be repeated, making conversation difficult. In addition, use of the telephone can present a serious problem to the hard of hearing. The unit described here is a compact device which relieves these problems by amplifying telephone calls to loudspeaker volume. Its design was prompted by the author's frequent need to take down notes during telephone conversations. It can reduce the strain of using the telephone, and it could be especially useful in a noisy environment such as a factory. The unit can actually save money on long distance calls since it allows a conversation to flow faster. It also enables more than one person to listen to a telephone, making conferences by telephone possible.

The unit is portable and can be attached to a Post Office or private intercom in seconds, without any unauthorized electrical connection or modification to the telephone. It works by detecting the stray magnetic field which exists around a telephone. A special magnetic detector, which attaches to the telephone by a built-in rubber suction cup, produces a signal which the unit amplifies to loudspeaker volume. Depending on where the detector is attached to the telephone, the unit may deliver both sides of the conversation, or almost solely the incoming speech. Since it is hardly likely to be used for quality music reproduction, the unit's frequency response is deliberately restricted to give the best intelligibility of telephone speech. A somewhat unconventional volume control circuit is used to this end.

circuit

The circuit of the telephone amplifier is shown in Fig. 1, where typical voltage readings are shown. A silicon integrated circuit flatpack is used in the audio output stage. Besides simplifying construction, this tiny unit proves cheaper than the equivalent discrete components. It delivers just under one watt of audio power, quite adequate for this use, and operates here with the absolute minimum of external components.

The signal from the telephone pickup L is first amplified by two conventional common emitter

stages Tr1 and Tr2, coupled by C4. These transistors are very high gain but inexpensive silicon planar types and they are run at a fairly low collector current of about $200\mu\text{A}$ to minimise noise. High frequencies are attenuated by collector-base feedback capacitors C2 and C5 in each stage. This both ensures stability and gives a useful reduction in noise when the amplifier is used at full gain on a weak signal—there is no point in trying to amplify treble frequencies which simply are not present on the telephone line. For the same reason, bass is restricted by the values of C3 and C6 which are not large enough to decouple the transistor emitters at low frequencies.


The amplified signal is coupled by C10 to the General Electric PA234 integrated circuit. This contains all the active components of a conventional Class B audio amplifier, equivalent to six n-p-n transistors, one p-n-p transistor, three diodes and three resistors. The voltage drop across the chain of diodes provides sufficient standing current in the output transistors to minimise crossover distortion, with automatic temperature compensation to prevent thermal runaway.

A.C. and d.c. negative feedback from the output to the input of the i.c. is provided by preset potentiometer VR2. This must be adjusted to obtain half the supply voltage at the i.c. output (pin 12).

The 15Ω loudspeaker is fed via d.c. blocking capacitor C11. Overall negative feedback is taken from the speaker to Tr1 base by R9 and VR1 to form the unusual volume control which operates as follows.

The arrow on VR1 indicates the direction of clockwise rotation. When this control is set fully clockwise, the slider is at earth and there is no feedback from R9. The amplifier then works at maximum gain. As the control is rotated anticlockwise, the amplifier gain is progressively reduced as more negative feedback is introduced from R9 into Tr1 base. The advantage over a conventional volume control in this application is that the advantages of negative feedback, namely reduced distortion and extended frequency response, are gained to the maximum at all volume settings. There is also an economy in components. At the high volume setting used with a very weak, noisy telephone signal, there is little or no feedback and the resulting restricted frequency response of the unit aids intelligibility.

small polythene soap box, sold by most chemists. The volume control, a standard miniature Japanese radio type, and most of the components are mounted on a small piece of Veroboard. This is shaped so it wedges tightly into the smaller half of the box, together with the loudspeaker and battery, without any other fixing being needed. The Veroboard layout is shown in Fig. 2 and is not critical. The components need not be so closely packed if a larger box is used, and the Veroboard can be shaped to suit the box. Careful soldering with a small, hot iron is essential. Resistors should be small $\frac{1}{4}$ watt types. The author chose to use a fractionally under-rated electrolytic capacitor (only 6.4V working) for C9 as this value is available in a very small size.

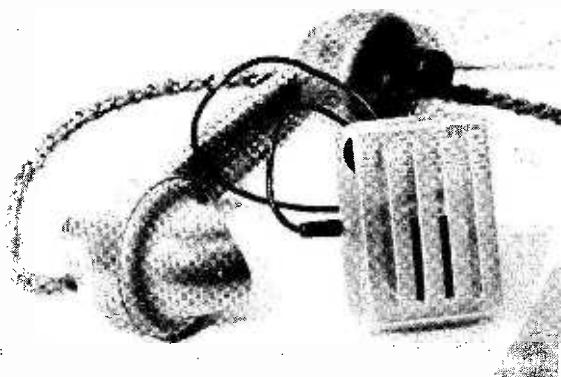

The sucker of the pickup coil should be located for best reception.

There are two breaks to be made in the Veroboard conductors, one of which is a break between two holes. These breaks can be made with a razor blade, which is also useful for cutting holes in the box for the loudspeaker, input socket, and the protruding volume control knob. The author intended to glue the i.c. to the Veroboard (there is still room there), but then succeeded in soldering it to the back of the loudspeaker by the heat sink tab. This way of mounting was thought more elegant, even though there is no indication that the i.c. needs the extra heatsink thereby obtained.

By choosing the smallest type of skeleton preset for VR2, it is possible to mount this component directly onto the i.c. pins. Capacitor C11 is the only remaining component and this is wired directly from the i.c. to the speaker. A piece of plastic insulating tape prevents any of the Veroboard conductors shorting against the speaker frame.

The only wires which have to be kept short are those from the input socket to the Veroboard. These should be tightly twisted. If, with some other layout, more than an inch or so length is required, a small screened cable should be used, with the screen connected to the earth side. The space occupied by the socket can be reduced if necessary by breaking off the shorting contact which is not needed.

After checking the wiring, with special attention to the lead connections of transistors, electrolytics and the i.c., and to possible shorts between Veroboard conductors caused by stray solder blobs, switch on. Check that the voltage at pin 12 of the i.c. can be varied by VR2, and set it to half the supply voltage. The unit should produce some hiss at

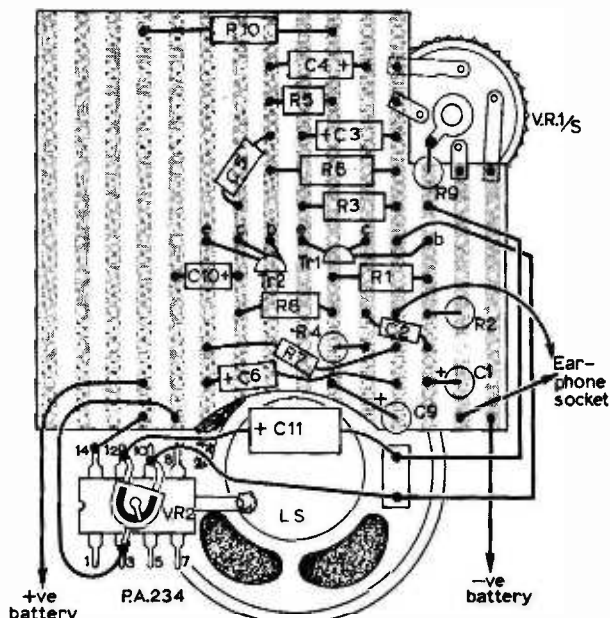


Fig. 2: The component layout. The heat sink tab of the i.c. is soldered to the magnet of the loudspeaker.


full volume. If not, check the remaining voltages in Fig. 1. Injecting an audio signal, or just touching with a screwdriver, at i.c. pin 3, Tr2 base, and Tr1 base should produce progressively louder response from the speaker.

With the pickup plugged in, some stray hum will probably be picked up from the mains. Loud positive feedback squeals will be produced if the pickup is brought near the unit, as it is sensitive enough to detect the stray field of the loudspeaker voice coil.

uses

The telephone pickup is extremely sensitive to stray field from the mains, and the unit will produce a loud hum if the pickup is near any mains appliance. This hum can always be minimised by setting the pickup at a certain angle.

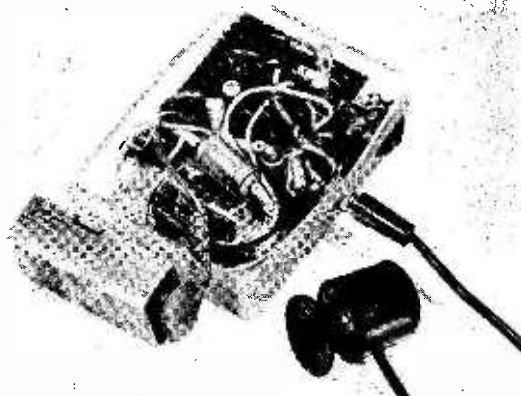On the modern pattern Post Office desk telephone, the best place to attach the pickup is usually high on the right hand side. On the older types it is at the back, and on STD pay telephones it is at about an



An internal view of the completed telephone amplifier.

inch below the cord entry on the left hand side of the case. In these positions, both sides of the conversation will be amplified to loudspeaker volume. The best point is easily found by experimenting for the loudest volume from the unit with the telephone producing a continuous sound, such as a dialling tone.

The maximum volume that can be used is limited by the onset of feedback whistles caused by the telephone handset picking up the sound from the loudspeaker. Feedback should be avoided as it sounds most perplexing to your caller! There is less danger of feedback if the pickup is attached to the telephone earpiece—the stray field is not very strong here, but there is the advantage that less of one's own speech is amplified. The best position for the pickup will be found slightly off the axis of the earpiece.

other uses

The pickup is extremely sensitive to any alternating magnetic field; it will pick up hum anywhere near a mains transformer, and will actually reproduce the signal from a radio if placed near the voice coil of the radio loudspeaker, or near the output transformer. Also, both field buzz and line whistle can be detected near a television set.

The unit can also be used for experiments in communication over short distances by magnetic field. As a starter, if about 12 yards of single core wire is laid under a carpet in a large coil of about 6 turns, and the ends of the wire connected to the loudspeaker output of an amplifier or radio, the telephone amplifier will pick up the signal several feet away from the coil. This is one form of 'wireless' communication for which no licence is required.

Without the telephone pickup the unit is an extremely sensitive amplifier plus speaker combination with a multitude of uses. It can be connected to any low level audio source, such as a radio tuner, microphone, record cartridge, tape playback head, or electric guitar, as long as hi-fi quality is not expected.

CORRIGENDA

Mini Organ—October 1970

In the circuit diagram, Fig. 1 the top end of the pre-set potentiometer network should not be returned to the negative rail. As shown the oscillator will function continuously. The circuit is completed only through the stylus.

The Genetracer—August 1970

The "brackets" at the top of Fig. 1. should be amended to show R1 to R4 inclusive as "Generator" and R5/C4 etc. as "Tracer". The earthy end of D1 and VR2 should be shown connected to the positive line of the "tracer" (i.e. SW2) and not that of the generator (SW1) as shown.

Delete the second wire from the right-hand tag of SW1, Fig. 2. "To positive", the necessary connection to the positive line is already provided by the lead from SW1 to the output socket (outer shield), as shown in Fig. 4.

I.C. Stereo Equalisers and Mixers

—continued from page 641

If the circuits are used to drive an amplifier with a d.c. blocking capacitor at the input, they can be connected directly to it. However, if they are to feed directly to a valve grid or a transistor base, a blocking capacitor of 0.1μF or 1μF 3V respectively should be inserted.

The voltage ratings of the d.c. blocking capacitors at the inputs of the circuits must naturally be sufficient to withstand any d.c. level present in the input signal, or the i.c. will be damaged.

POWER REQUIREMENTS

If a d.c. supply of somewhat higher voltage than the i.c. requirements can be "borrowed" from the main amplifier, a simple zener diode regulator circuit as shown in Fig. 10a can be used to power the i.c. Such a supply might be the positive h.t. line of a

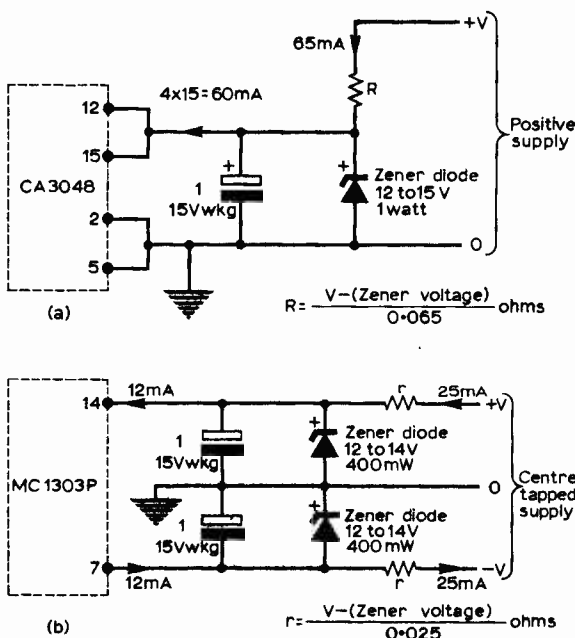


Fig. 10: Zener regulator power supply circuits for (a) CA3048 and (b) MC1303P.

transistor amplifier, or the voltage across a cathode bypass capacitor in a valve amplifier. The earth connection of the i.c. should be at the same potential as the chassis of the main amplifier, or else considerable attention will be needed to suitable decoupling arrangements. When the MC1303P is used in a preamp feeding a valve amplifier with a push-pull output stage, the bypassed output valve cathodes can generally provide the centre tapped supply needed for Fig. 10b.

The value of the dropping resistor(s) R or r depend(s) on the actual supply voltage and zener diode voltage; select the nearest 5% tolerance value to the resistance calculated from Fig. 10. The power dissipated in the resistor is, as always, the product of the voltage across it and the current flowing through it (answer in watts if the current is in amps).



STEREO AMPLIFIER

F.C. JUDD

PART 2

Circuit Boards

Details for the size and assembly of the pre-amplifier circuit boards and their internal screens are given in Fig. 7a, b and c. The boards are cut to size as in Fig. 7b, together with the 20s.w.g. aluminium (or tinplate) screens that are fitted between the boards as in Fig. 7a. The boards and screen are spaced $\frac{1}{2}$ in. apart from each other with spacers but note that one board has attached to it a length of $\frac{1}{8}$ x $\frac{3}{8}$ in. aluminium angle for securing the assembly to the chassis.

These angles must be fitted so that when each assembly is placed in position as in Fig. 7c the angles will be facing toward each other. It is best to assemble the blank circuit boards together with their screens and try them in position on the chassis to ensure that they comply with Fig. 7c. Then mark each board so that it can be identified as to which channel it belongs and which ends will be used for input and output respectively.

Although the circuitry for the right- and left-hand channels is identical *the component layout on the board is in opposition* as they are mounted back to back, hence the reason for identification with respect to channel allocation and input and output ends. The component layout and connection diagrams given in Fig. 8 should help in getting the boards the right way round and as can be seen, the layouts are virtually mirror copies of each other.

The input pre-amplifier for the right-hand channel is an exception however, as it also carries the large 5000 μ F positive rail decoupling capacitor C24 and the 1.5 k Ω voltage dropping resistor R35.

When the boards have been assembled and wired they should fit back-to-back with the wiring inside, the components outside and of course the screen in the middle.

Completion of the pre-amplifier circuit boards is by soldering flying leads to components and other points on the boards that connect with front panel controls, the selector switch S1 and S2 and supply



and earthing points. It is most essential that these leads are fitted before the circuit boards are mounted on the chassis as it would be very difficult to connect them afterwards. All leads shown coming away from the circuit boards as in Fig. 8 should be regarded as flying leads and the best way to identify them is to use coloured wires.

Panel Controls and Selector Switch

Connections to the volume, balance and tone controls etc., are shown in Fig. 9. Providing the leads from the input pre-amplifier boards (via R18) to the balance control VR1 are short, and they should be no more than two or three inches long, they need not be screened. This also applies to leads connecting the tone controls and the filter switches. The leads from the output of the tone control/drive amplifier boards (C23) to the volume controls and from these to the power output modules and to S5 the stereo/mono switch, must be screened. This is to prevent instability due to capacitive coupling since these leads are fairly long and pass close to the input ends of the boards.

Next come the wires connecting the selector switch S1 and S2 to the input pre-amplifier boards. Again no screening is necessary providing the leads are as short as possible and are kept clear of the other circuit boards. The connections are shown in Fig. 10 but note that the pictorial diagrams of the switch wafers may not agree with those actually purchased i.e., the contacts may be differently orientated. The remainder of the wiring is to S1A and B from the input sockets and this includes the input attenuators (R1, R2, R3, R4 etc.). The leads between the tape recording output sockets and the output from the pre-amplifiers (C23) need not be screened but must be as short as possible and kept clear of leads going to the input sockets.

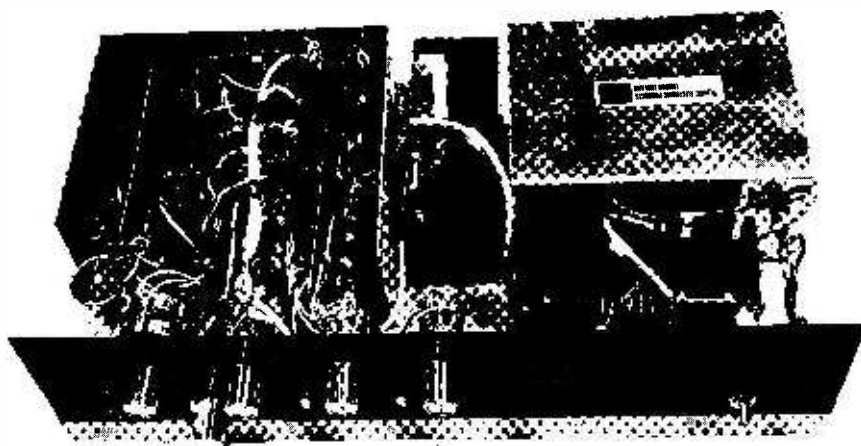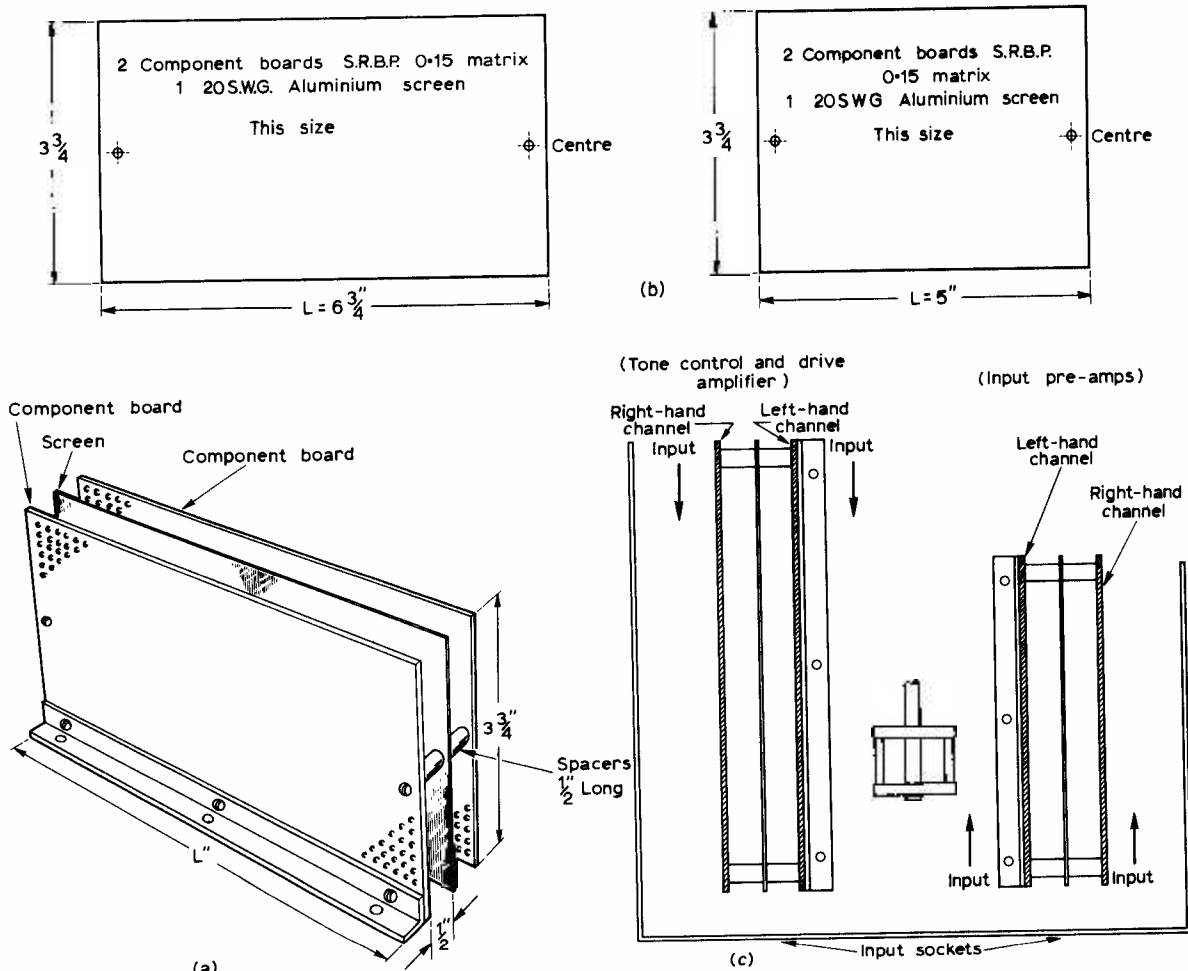Those who have test equipment such as an audio



Another view of the completed PW25/25 Stereo Amplifier in which the wiring to the Henelec Type PA25 output modules can be seen.



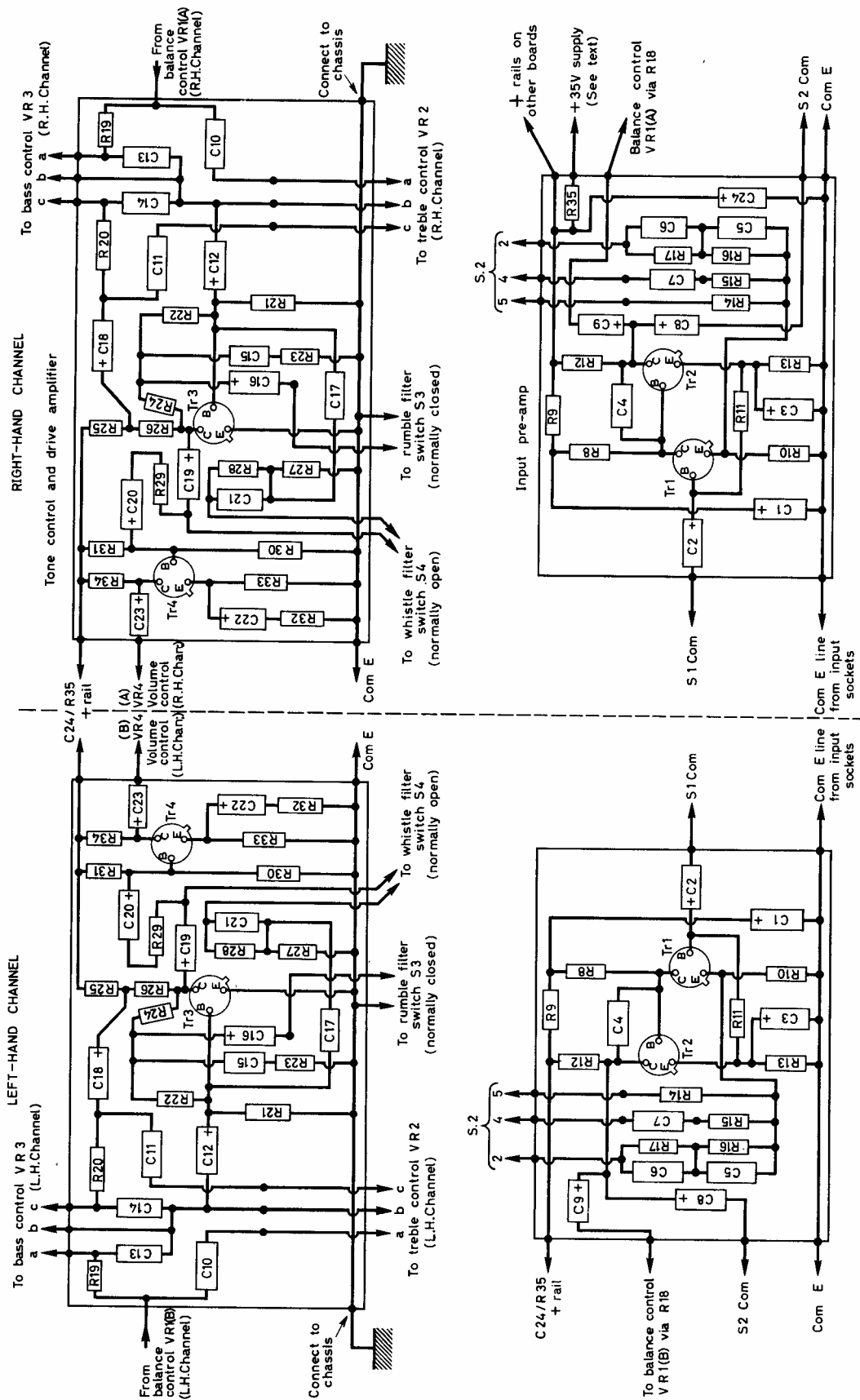


Fig. 8. Component layout of the pre-amplifier circuit boards. Note that, left to right, one is the mirror image of the other, except for C24/R35 on the R.H. channel input pre-amplifier board.

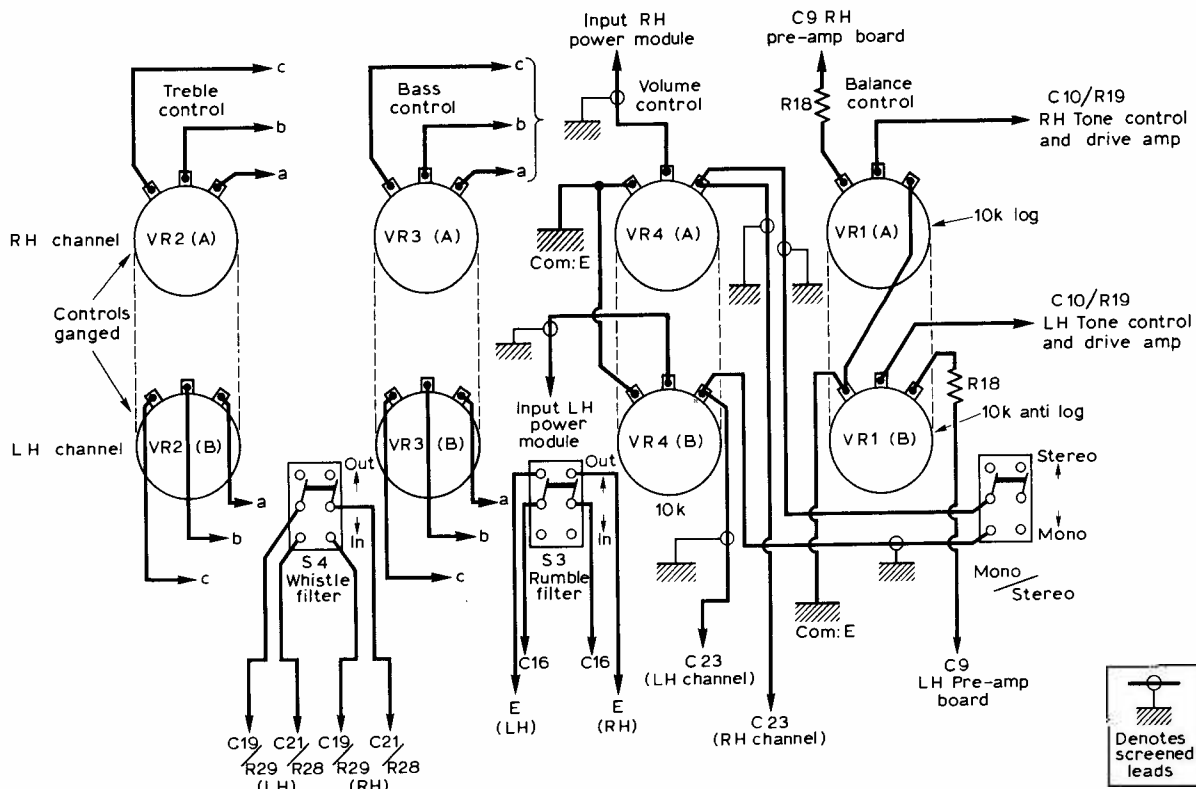

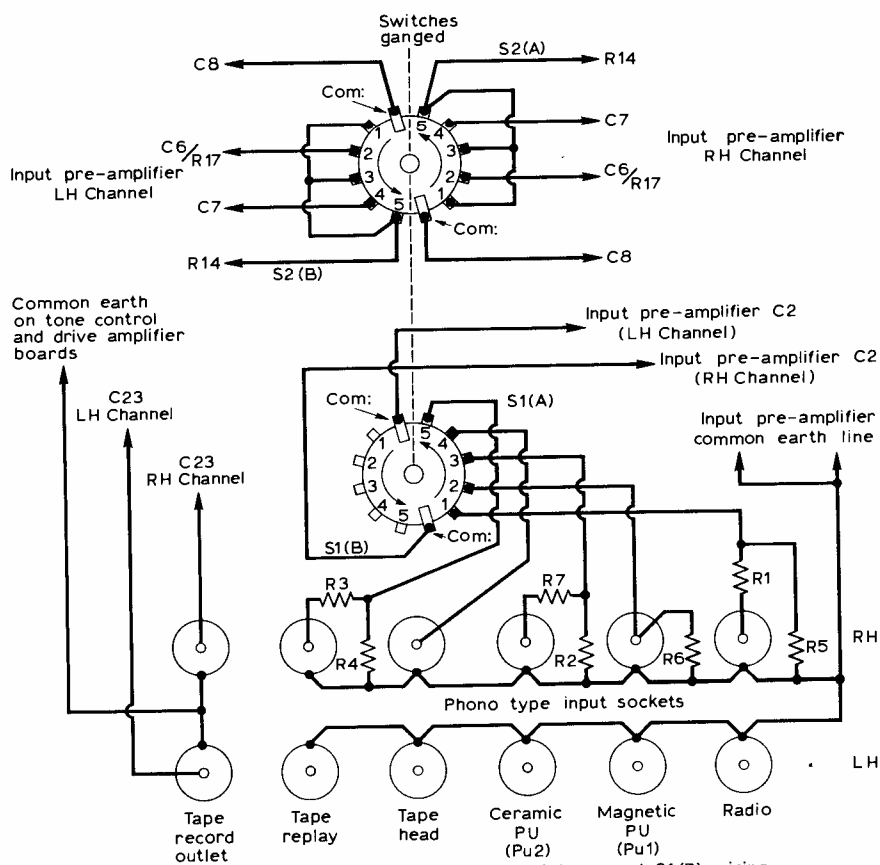▲ Fig. 9. Rear view of the wiring to the various panel controls. See text for comments on the use of screened leads.



◀ Fig. 10. Wiring of the input selector switch wafers and the associated input sockets. For clarity the wiring to the L.H. channel input sockets is omitted but is similar to the R.H. channel.

signal generator and an audio milli-volt meter would do well to connect the pre-amplifiers to a 22V battery supply (5 x 4½V torch batteries) and check them for performance before connecting them to the power output modules and the MU442 power unit.

Output Modules and Power Supply



The power supply unit MU442 is supplied with a 3-pin mains input socket and the leads from this run internally to the mains and earth connections respectively on the printed circuit board inside. First remove the cover to obtain access to the mains connections inside which will be as shown in Fig. 11a. The 'red' lead to what is effectively the 240V terminal is disconnected and extended as shown in Fig. 11b to the mains on/off switch on the front panel. The return lead from the switch is connected to the 240V terminal. Two leads are then connected

as shown in Fig 11b to the mains neon pilot light. These and the leads going to the on/off switch should be taken out through the left hand side (looking from the rear) of the power supply unit.

Finally comes the connection of the PA25 power output modules to the output from the pre-amplifiers via the volume controls VR4. The PA25 modules and MU442 unit are supplied with connecting cables and plugs. The two screened leads between the PA25 modules and the power supply are disconnected from the plugs on the power supply itself. These are now taken to VR4 for the right and left hand channels respectively as in Fig. 12. The remaining connection is that of the positive supply line for the pre-amplifiers. This picks up the +35V rail from the right-hand channel PA25 module input plug as shown in Fig. 12. The negative supply line is obtained by contact between the power unit case and the main chassis.

Fig. 11. Modifications to the mains input wiring of the MU442 power supply unit.

Fig. 12. Details of the wiring to the inputs of the power modules together with the socket arrangement on the back of the power supply unit.

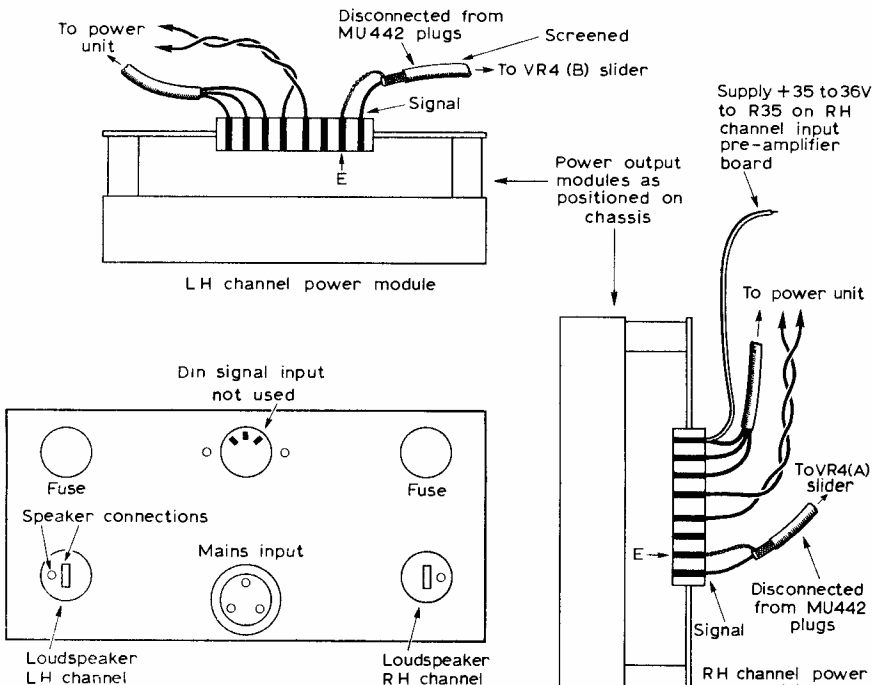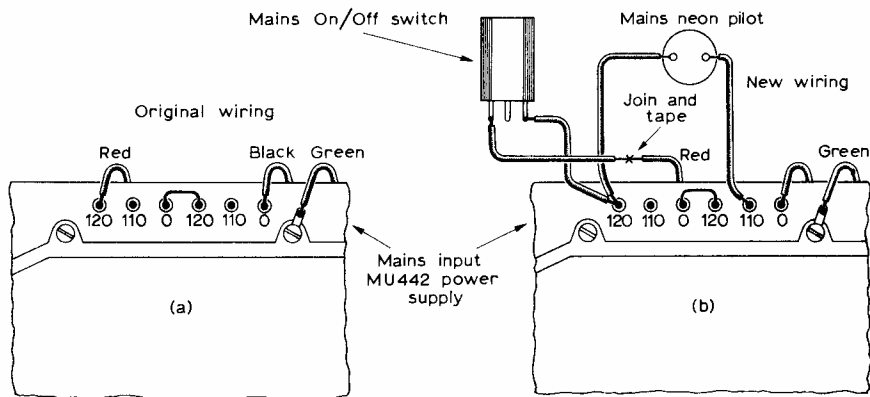

An outline of the rear of the MU442 power supply is also shown in Fig. 12. Note that the DIN signal input socket is not used, as the signal inputs to the PA25 modules have been re-routed to the volume controls (VR4). The loudspeaker sockets are also DIN type and the connections are as shown. Do *not* earth the loudspeakers at any point and do not connect one output to the other in any way. Do not short circuit the outputs with the amplifier running and developing power. There are fuses on the power supply and the modules which will protect them against voltage surges and accidental overloading. Do not tempt providence by poking around with a screwdriver whilst the units are running.

WAY OUT- of the component finding maze

It may be fun finding your way out of the maze at Hampton Court, but it's not so funny trying to locate and obtain just the components you need for a particular job. In fact, the number of problems and frustrations you can meet is quite a-maze-ing!

There is an easy way out however. Simply get a copy of the Home Radio Catalogue and order whatever you need from the comfort of your easy chair. This famous radio and electronic constructor's "Bible" lists over 8,000 items, more than 1,500 of them illustrated. At only 12/6d. (8/6d plus 4/- post & packing) it's a gift—especially as each copy contains 6 vouchers, each worth 1/- when used as directed.

Once you have your Home Radio Catalogue you can make life even easier for yourself by joining our **Credit Account Service**. Then you can order by telephone any time of day or night, Sundays included! No need to bother with postal orders, cheques, registering envelopes every time you order. We send prepaid envelopes and you make only one payment each month. So simple! Write for details or telephone 01-648 8422.

YOUR FIRST STEP out of the maze—Post the Coupon with your cheque or P.O. for 12/6d


The price of 12/6d applies only to catalogues purchased by customers residing in the U.K.

Please write your Name and Address in block capitals

NAME

ADDRESS

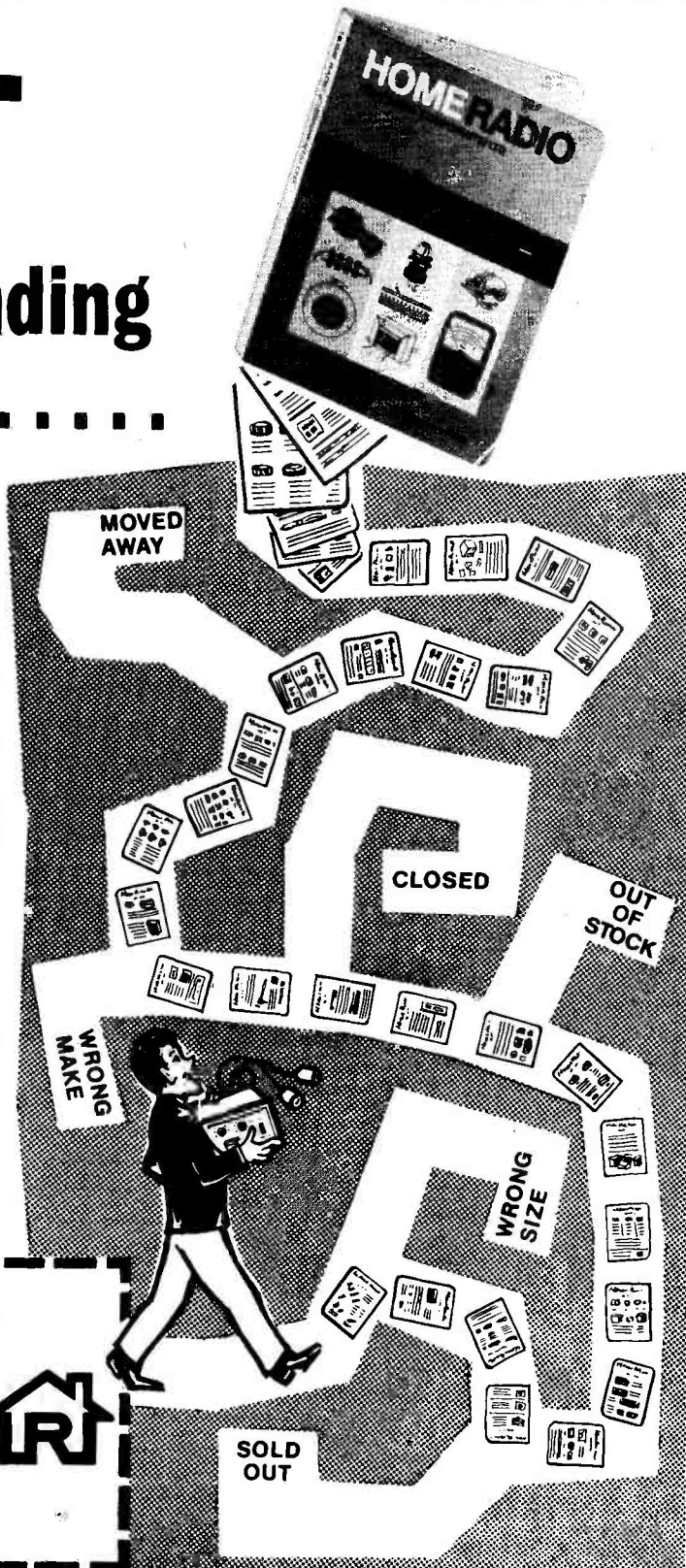HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey, CR4 3HD



Testing and Performance

In constructing and wiring a fairly complex piece of equipment like the PW 25-25 amplifier there is always the risk of a faulty component, wrong connection or dry soldered joint etc., hence the earlier suggestion that it might be worthwhile testing the pre-amplifiers before connecting the power output modules and supply. In making the prototype as shown in the photographs the writer tested each circuit board individually before assembling them and then again after assembly and wiring as a complete pre-amplifier on the chassis. This is quite easy to do if an audio signal generator and audio voltmeter are available. The tone controls etc., can be temporarily connected for individual testing and each board hooked up to a 22V battery. Those able to do this will find the table of input and output signal levels of some use.

Before switching on the completed amplifier ensure that loudspeakers and/or suitable dummy resistive loads are connected at the output (speaker) sockets. Set the volume control to zero and inject a signal at the 'radio' input—preferably a 90 to 100mV sine-wave at 1000Hz. Advance the volume control just sufficiently to lightly load the output stage and then repeat the procedure for the other channel. For those without an audio signal generator and audio voltmeter, further tests can only be made by listening and using appropriate signals from a radio tuner or pick-up etc., to ensure that the amplifier is operating correctly on both channels.

TEST CONDITIONS Input signal—1000 Hz sine-wave

Input Pre-amplifier (one only)

Input at C2 10mV

Output at C9 300mV

With equalising network switch S2 connected and set to 'Radio'.

Tone Control/Drive amplifier

Input at C10/R19 10mV

Output at C23 400mV

With tone controls connected and set at neutral. Filter switches connected and set to 'Off'.

Complete Pre-amplifier

	Input		Input
Radio	70/75mV	Tape Head	8/10mV
Mag.PU	6/7mV	Tape Replay	150/200mV
Cer.PU	70/80mV		

All inputs for 1 volt r.m.s. output at C23/VR4. Volume controls off. Balance control at neutral. Tone controls at neutral. Signal level at module inputs (sliders of VR4) for full output should be 700 to 800mV r.m.s.

DC Supply

Positive point on module/take-off point for pre-amplifiers 35/36V

Pre-amplifiers positive rail/junction of C24/R35 22/24V

Current consumption, pre-amplifiers only 2.5/3mA

Total consumption, both pre-amplifiers, complete, at 22V 8/9mA


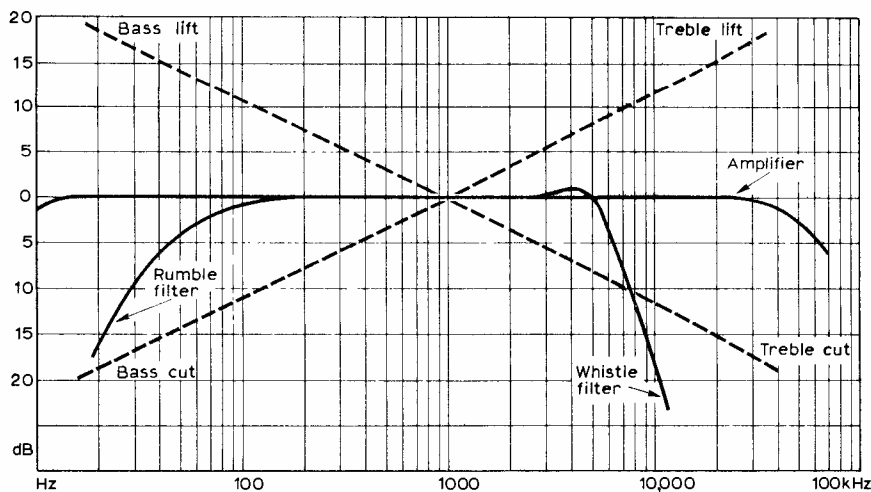
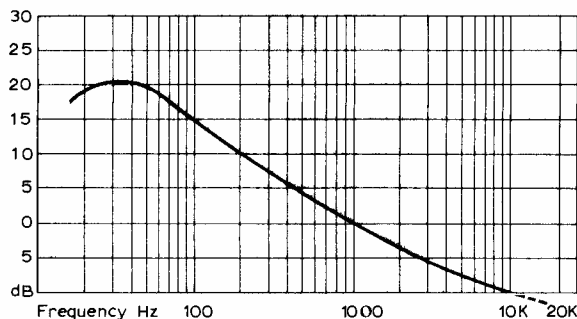


Fig. 13. Graph showing effect of the various controls on the amplifier's basic response curve.

Fig. 14. (below, left) Response from tape head input (CCIR). Fig. 15 (below, right) Response from magnetic pick-up input (RIAA).

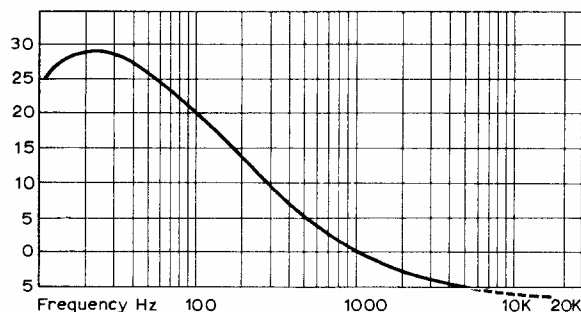

COMET

Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Over 1000 items in stock. Complete Free price list on request.



Customers Welcome
Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

STEREO AMPLIFIERS

	Rec. Price	Retail Price	Comet Price
ARMSTRONG 521	£256	0 0	£46 0 0
DULCI 207	£25	0 0	£17 0 0
DULCI 207M	£30	0 0	£20 10 0
GOODMANS Maxamp	£54	0 0	£39 10 0
HL 505	£23	2 0	£16 10 0
LEAK Stereo 30 Plus	£53	0 0	£42 10 0
LEAK Stereo 30 Plus (cased)	£59	0 0	£47 10 0
LEAK Stereo 70	£65	0 0	£52 0 0
LEAK Stereo 70 in teak case	£71	10 0	£58 10 0
LINEAR LT 66	£21	0 0	£16 10 0
LL Stereo Amp.	£23	10 0	£16 10 0
METRO SOUND ST 20	£36	0 0	£28 10 0
PHILIPS RH 591	£73	0 0	£55 10 0
PHILIPS RH 590	£49	0 0	£37 12 0
PHILIPS RH 580	£26	0 0	£19 10 0
PIONEER SA500	£82	1 11	£45 0 0
PIONEER SA700	£98	0 0	£74 10 0
PIONEER SA900	£134	2 0	£99 10 0
PIONEER Reverberation	£45	9 11	£35 10 0
QUAD 33 Pre-amplifier	£43	0 0	£38 10 0
QUAD 303 Main Amplifier	£55	0 0	£48 10 0
ROGERS Ravensbourne	£59	10 0	£46 10 0
Ravensbourne (cased)	£54	0 0	£49 10 0
Ravensbrook	£44	0 0	£36 10 0
Ravensbrook (cased)	£49	0 0	£39 10 0
TELETON 150 (replaces 203)	£29	0 0	£19 10 0
TELETON GA101 30w. RMS	£33	15 0	£25 10 0
SINCLAIR 2000	£30	9 0	£23 10 0
VOLTEX 100 watt stereo			
discotheque 8 electronically mixed inputs	£185	0 0	£139 0 0

TUNERS

*ARMSTRONG 593 AM/FM	£53	15 3	£44 10 0
*ARMSTRONG 524 FM	£41	17 8	£34 10 0
ARMSTRONG M8 decoder	£9	10 0	£7 10 0
*DULCI FMT. 7FM	£22	1 0	£17 10 0
DULCI FMT. 7S Stereo	£31	0 0	£25 5 0
GOODMANS Stereomax	£92	10 5	£63 10 0
LEAK Stereofonic Chassis	£29	18 0	£22 10 0
LEAK Stereofonic in teak case	£67	3 6	£58 10 0
PHILIPS RH 590	£39	0 0	£31 10 0
PHILIPS RH691	£83	0 0	£70 10 0
PIONEER TX500 AM/FM	£77	18 9	£63 10 0
PIONEER TX900 AM/FM	£153	13 10	£125 0 0
QUAD Stereo FM	£51	0 0	£39 10 0
ROGERS Ravensbourne	£61	17 8	£48 10 0
ROGERS Ravensbrook	£45	0 2	£39 10 0
ROGERS Ravensbrook (cased)	£51	5 3	£42 10 0
*SINCLAIR 2000	£26	14 6	£19 10 0
TELETON G100	£47	10 0	£33 10 0
TELETON 201X FM	£36	0 0	£29 10 0
TRUVOX FM 200/1C	£60	11 10	£39 10 0

All above tuners are complete with MPX stereo decoder except where starred.

TUNER/AMPLIFIERS

ARENA 2400	£90	6 0	£71 10 0
ARENA 2600 Stereo AM/FM	£111	6 0	£94 0 0
ARENA 2700 Stereo	£105	0 0	£85 0 0
ARENA T1500F	£72	9 0	£59 10 0
ARENA T900	£93	9 0	£78 10 0
*ARMSTRONG 525	£91	17 9	£76 10 0
*ARMSTRONG 526	£104	14 3	£86 10 0
ARMSTRONG M8 decoder	£9	10 0	£7 10 0
GOODMANS 3000	£77	14 7	£65 10 0
PHILIPS RH781	£74	19 6	£64 10 0
PHILIPS RH790	£125	0 0	£101 10 0
PIONEER KX300 AM/FM/SW	£78	12 4	£62 10 0
PIONEER SX770 AM/FM	£160	8 6	£129 10 0
PIONEER SX900 AM/FM	£194	14 8	£155 0 0
TELETON 7AT1	£15	10 0	£49 10 0
TELETON R400	£103	19 0	£85 10 0
TELETON CR10T	£39	15 0	£39 10 0
TELETON TF550	£75	10 0	£49 10 0
TELETON 7AT20	£105	0 0	£79 10 0
TELETON MTX1150w. RMS	£160	0 0	£109 0 0
TELETON 10A90 with speakers	£67	5 0	£48 10 0
TELETON R8000 with speakers	£63	5 0	£49 10 0
WHARFEDALE 1001	£131	5 0	£105 0 0

All above Tuner Amplifiers are complete with MPX stereo decoder except where starred.

TURNTABLES

ARENA SP25 with base, cover	£22	1 0	£17 10 0
B.S.R. McDONALD MP60	£15	0 0	£10 10 0
B.S.R. McDONALD D10	£18	19 8	£15 10 0
DUAL 1219 transcription	£60	8 0	£50 10 0
DUAL 1209 transcription	£42	12 4	£35 10 0

COMET for after-sales service

THROUGHOUT THE U.K.

SERVICE DEPOTS at LEEDS, GOOLE WAKEFIELD DONCASTER HULL and BRIDLINGTON

	Rec. Price	Retail Price	Comet Price
GARRARD SP25, fully wired with Goldring G800 magnetic cartridge, complete with base, plinth and cover	£21	15 0	£19 6 0
GARRARD SP 25 Mk II	£15	11 4	£10 10 0
GARRARD AP.75	£23	16 0	£17 10 0
GARRARD SL.55	£13	17 9	£11 12 0
GARRARD SL.65B	£19	6 5	£14 10 0
GARRARD SL.75	£35	12 4	£28 10 0
GARRARD SL.95B	£45	9 1	£36 10 0
GARRARD 401	£31	14 2	£25 10 0
GARRARD SL.72	£30	2 0	£24 10 0
GARRARD 3500 with GKS Cartridge	£15	15 0	£11 19 6
GARRARD base and cover to fit SP25, SL55, SL65B and 3500	£26	12 6	£21 10 0
GOLDRING GL69 Mk. II	£26	12 6	£21 10 0
GOLDRING GL69P Mk. II	£36	8 2	£29 10 0
GOLDRING GL75	£46	18 8	£39 10 0
GOLDRING GL75P	£4	4 3	£3 8 0
GOLDRING Covers for 69P and 75P	£27	19 0	£23 19 6
GOLDRING GL75, complete with plinth, cover and G800 cartridge	£57	19 0	£53 19 6
GOODMANS MT1000 Turntable	£78	15 3	£65 0 0
GOODMANS 3025	£37	14 9	£25 19 6
PHILIPS 228	£19	19 6	£16 19 6
PHILIPS GA146	£29	19 6	£24 19 6
PHILIPS 217	£32	9 0	£27 4 0
PHILIPS 202 Electronic	£64	0 0	£54 0 0
THORENS TD.125	£75	17 8	£61 10 0
THORENS 125AB	£120	3 11	£99 10 0
THORENS 150A Mk II	£43	12 7	£32 10 0
THORENS 150AB Mk II	£47	8 7	£40 10 0
THORENS TX11 Cover	£24	3 2	£23 10 0
THORENS TD.124/11	£46	15 10	£39 19 6

Bases, plinths, and covers stocked.

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

DELIVERY BY SECURICOR WITHIN 72 HOURS

ALL IN-STOCK items delivered by SECURICOR within 72 hrs. (Add 20/- only for Securicor delivery). All goods fully insured against loss or damage whilst in transit.

SPEAKERS

ARENA HT 27	£18	18 0	£13 19 6
ARENA HT 28	£17	17 0	£12 19 6
ARENA HT 21	£10	10 0	£9 5 0
ARENA HT 7	£19	19 0	£16 19 6
ARENA HT 10	£22	1 1	£18 19 6
ARENA HT 20	£22	11 0	£26 19 6
ARENA HT 26	£78	15 0	£65 19 6
B & W DM3	£63	0 0	£53 6 0
B & W P2H	£94	10 0	£79 0 0
B & W DM1	£32	0 0	£25 19 6
CELESTION Ditton 10	£21	3 2	£16 19 6
CELESTION Ditton 15	£29	0 0	£22 19 6
CELESTION Ditton 25	£59	17 0	£46 19 6
DULCI AS 3	£8	8 0	£6 19 6
GOODMANS Majesta	£57	0 0	£44 19 6
GOODMANS Maxim	£20	7 9	£16 19 6
GOODMANS Mezzo II	£30	19 0	£22 19 6
GOODMANS Magnum-K	£40	2 0	£28 19 6
GOODMANS Marimba	£24	0 1	£18 19 6
GOODMANS Mambo	£22	5 6	£17 19 6
GOODMANS 3005 (pair)	£25	0 0	£21 19 6
KEF Celeste	£29	0 0	£28 19 6
KEF Concord	£53	10 0	£41 19 6
KEF Concerto	£22	3 4	£17 19 6
KEF Cresta	£45	10 0	£29 19 6
LEAK Sandwich	£29	15 0	£21 19 6
LEAK Mini-Sandwich	£27	10 0	£20 19 6
LEAK 300	£23	10 0	£17 19 6
LEAK 200	£45	0 0	£32 19 6
LEAK 500	£45	0 0	£32 19 6
LOWTHER Acousta (with PM5)	£45	10 0	£38 7 6

LOWTHER Ideal Baffle	£35	10 0	£29 17 6
Acousta (with PM7)	£53	0 0	£45 19 6
QUAD Electrostatic	£66	0 0	£52 19 6
PHILIPS RH 481	£11	0 0	£9 2 6
PHILIPS RH 482	£18	0 0	£14 19 6

WHARFEDALE Speakers

Airedale	£69	10 0	£55 19 6
Denton	£19	0 0	£14 19 6
Super Linton	£22	10 0	£18 19 6
Mellon	£29	10 0	£22 19 6
Dovedale 3	£39	10 0	£29 19 6
Rosedale	£33	10 0	£26 19 6
UNIT 3 Speaker Kit	£11	19 6	£9 10 0
UNIT 4 Speaker Kit	£16	0 0	£13 5 0
UNIT 5 Speaker Kit	£23	10 0	£18 19 6

CHASSIS SPEAKERS

GOODMANS Axlette 8	£7	9 6	£5 19 6
GOODMANS Twinnaxette 8	£8	8 8	£6 19 6
GOODMANS Twinnaxiom 10	£9	8 5	£7 15 0
GOODMANS Axium 10	£28	16 8	£26 19 6
GOODMANS Axium 301	£19	5 0	£14 10 0
GOODMANS Axium 51	£12	3 0	£9 10 0
GOODMANS Axium 61	£17	12 0	£12 19 6
GOODMANS Axium 81	£29	13 0	£22 19 6
GOODMANS Axium 91	£33	10 0	£26 19 6
GOODMANS Axium 80	£26	1 4	£21 12 0
GOODMANS Axium 91/100	£34	17 0	£26 2 0
GOODMANS ARU 180	£37	17 8	£28 19 6
GOODMANS ARU 280	£37	17 8	£28 19 6
GOODMANS ARU 480	£5	8 5	£4 3 0
GOODMANS ARU 172	£27	17 0	£21 19 6
GOODMANS Trebas 100	£17	0 0	£11 10 0
GOODMANS Trebas 5K/20KL	£8	8 0	£6 8 0
GOODMANS Midax	£11	4 0	£8 8 0
GOODMANS Attenuator	£3	1 4	£2 8 0
GOODMANS Crossover			
Networks X/950/5000	£8	7 9	£6 6 0
GOODMANS Crossover			
Networks X/500	£6	7 9	£4 15 0
GOODMANS Crossover			
Networks X/5000	£2	6 0	£1 14 6
WHARFEDALE 8 inch Bronze/RS/DD	£4	8 0	£3 13 6

HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

AKAI X-360	£339	0 0	£284 0 0
AKAI X-360D deck	£290	0 0	£243 0 0
AKAI 1710L	£89	17 0	£68 19 6
AKAI 1800	£158	0 0	£133 0 0
AKAI 1800SD	£199	0 0	£167 0 0
AKAI 4000	£124	18 0	£99 10 0
AKAI 4000 D deck	£89	19 0	£69 10 0
ALBA R22 Battery/Main	£50	5 0	£29 10 0
BUSH TP 60 Cassette	£29	8 0	£24 19 6
BUSH TP 70 Cassette			
Battery/Main	£29	19 0	£23 19 6
FERGUSON 3246	£43	0 0	£33 19 6
FERGUSON 3247 4-track	£48	9 0	£38 19 6
FERGUSON 3248 4-track	£54	6 0	£41 19 6
FERGUSON 3249 4-track	£64	6 0	£49 19 6
FERGUSON 3244 Stereo 4-track			
GRUNDIG C200 Cassette	£97	18 0	£79 19 6
GRUNDIG TK 124	£37	10 0	£29 19 6
GRUNDIG TK 124	£44	18 0	£34 19 6
GRUNDIG TK 144	£49	19 6	£38 19 6
GRUNDIG TK 144	£57	12 8	£47 19 6
MARCONI TK 4218 Stereo tape Recorder	£89	11 0	£68 19 6
PHILIPS 290 Cassette Recorder with Radio	£34	0 0	£26 19 6
PHILIPS 3302 Cassette	£28	7 0	£19 10 0
PHILIPS 4302 Twin Track			
PHILIPS 4307 4-track	£39	0 0	£31 19 6
PHILIPS N4404 (4 track stereo)	£49	10 0	£38 19 6
PHILIPS N4407 Stereo	£87	0 0	£69 19 6
PHILIPS 4408 4tk stereo	£105	0 0	£85 19 6
PHILIPS N4306	£129	0 0	£109 0 0
PHILIPS N4306	£60	10 0	£49 19 6
PHILIPS 4500	£126	0 0	£96 19 6
SANYO Stereo Tape Deck MR 800	£89	0 0	£59 19 6
TELETON FXB 510D Stereo	£52	10 0	£43 19 6
TOSHIBA GT601V	£45	3 0	£29 19 6

PICKUP ARMS

GOLDRING Lenco L75	£12	6 6	£10 10 0
GOLDRING Lenco L69	£9	5 9	£7 0 0
SME 3009 with S2 shell	£31	6 3	£25 19 6
SME 3012 with S2 shell	£33	7 3	£28 19 6

COMET Hi-Fi DISCOUNT WAREHOUSES

Reservoir Road, Clough Road, Hull HU6 7QD. Tel 407906 & 407877
also at 68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055 (5 lines)

Customer guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Comprehensive Hi-Fi Catalogue available 5/- Add 9/- for post and packing on all orders (cartridges 4/-). Make cheques Money Orders payable to "COMET". If Securicor Delivery Required add 20/- only.

WELBROOK HI-FI AMPLIFIER KIT

During last year Welbrook introduced to the Hi-Fi field their unique output stage which was a completely new break-through in high-fidelity Audio Design. It enabled us to produce an amplifier, giving a level of distortion at low output levels, normally associated with CLASS A or truly complimentary output stages, but still retaining the low relative cost and advantages of a CLASS B quasi-complimentary stage.

To maintain our position as a forerunner in the audio field, we now introduce this amplifier in kit form.

Consider the following brief specification and then note the price.

POWER OUTPUT:

10 watts R.M.S. per channel (8 ohms).

T.H.D.:

Typically less than 0.1% for all output levels up to 10 watts.

INPUTS:

Magnetic — ceramic — crystal P.U.
Tuner.
Tape.

OUTPUTS:

4 — 8 — 15 ohms.
Tape Output.

The kit consists of a fibre-glass P.C.B., 20 silicon transistors, 12 silicon diodes, approximately 140 electronic components, and all materials required to complete a chassis mounted amplifier, including front panel and knobs.

PRICE: £32 0s. 0d.
(Cabinet Extra).

Further details and fully illustrated leaflets available.

**Welbrook Engineering
and
Electronics Limited**
Brooks Street, Hr. Hillgate,
Stockport, Ches.
Phone: 061-480 4268.

DIMMASWITCH



This is an attractive dimmer unit which fits in place of the normal modern light switch. The ivory mounting plate matches modern fittings and the control knob is bright chrome. An ON/OFF switch is incorporated to control 40-600 watts of all lights except fluorescents at mains voltages from 200-250V, 50 Hz.

Competitive products sell at £4.19.6d. — our price is £3 4s. We also offer at £2 14s. a complete kit of parts with instructions enabling you to build this dimmer yourself.

The circuit uses a miniature RCA triac and a diac triggering device to give complete reliability. Radio interference suppression is included.

Post and Packing 1/6d. extra.

Please send Cash with Order to:—

DEXTER & COMPANY
ULVER HOUSE, 19 KING STREET,
CHESTER CH1 2AH.

Tel: Chester 25883

As supplied to H.M. Govt. Departments, Hospitals
Local Authorities, etc.

4-STATION INTERCOM



£6.15.0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.12.0. P. & P. 9/- extra.

INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.



Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (PW. 12)
189 KENSINGTON HIGH STREET, LONDON, W.8.

BRAND NEW AR88D COMMUNICATIONS RECEIVERS.
AC mains input 110 volts or 250 volts. Frequency in 6 bands 535 Kcs up to 32 megs, output impedance 2.5-600 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

COMPUTER BOARDS Min 30 transistors and diodes and res. etc. 10 boards at 10/- plus 2/6 p.p.; 25 boards at 22/6 plus 4/6 p.p.

BARGAIN PARCELS 14lb at 29/- plus 6/6 p.p.; 28lb at 55/- plus 12/6 p.p.; 56lb at 90/- plus 25/- p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££s. Lucky Dip Service.

FURZILL BEAT FREQUENCY OSCILLATOR 0-10 Kcs, 110/250 volt. Good condition complete with spares. £5.10.0 plus 25/- p.p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3.0.0 plus £1 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1—1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 5 1/2" x 4 1/2" x 5" Sealed. Price 27/6 p.p. 5/-

CRYSTALS AS NEW: Hc 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,680; 4,660; 4,520; 4,510; 2,300; 2,295 Kcs and 10 x J465 Kcs. 10/- each plus 1/6 p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance 1/2 & 1/4 watt. Preferred values in packets of 10. Our price 10/- per 100, 19/- per 200, 27/- per 300, 50/- per 400. Our selection. p.p. 1/6 per 100 and 6d. per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details; Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 Mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal — 12/- per doz. plus 3/6 p.p.
Trimmers with Xtal — 15/- per doz. plus 3/6 p.p.
Also 20 PF min. brand new air spaced. 10/- per doz. plus 3/6 p.p.

MURPHY MOBILE MR 820 TRANS/RECEIVER. Low band, not tested, but complete with valves. Built-in speaker. Less crystals and mike. 12 volt input. RF output 4-6 watt. £5.0.0 + 15/- p.p.

NEW TOGGLE SWITCHES. 250 volt 3-5 amps. 2 pole 2 way. 12/6 dozen, 2/6 post and packing.

SIGNAL GENERATORS OSCILLATOR No. 2. Size 12in. x 8 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kcs RF meter. Measuring levels; RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories; 230V AC 12V DC. £20.0.0 plus 15/- p.p.

TF 144 G Signal Generators 85 Kcs/s to 25 Mc/s. Good condition and complete with accessories. £22.0.0 plus 30/- p.p.

AERIALS. New Condition. Whip type 11ft 12/6 each. Used condition 12ft 10/- each. All collapsible type. Post and packing 3/6. Bases for the above 5/-, post and packing 2/6.

PYE VANGUARD TRANS/RECEIVER. Boot mounted. Low band (app. 20 watts), 20 valve QQV3-20A, QQV3-10 etc. less crystals. 12 volt input. Not tested. Used condition with speaker and mike £8.16.0 carr. 30/-. As above less mike and speaker £5 each + 30/- carr.

New lengths 50ft Coaxial cable 70 ohms (approx.), coax plugs each end, price 20/- each post and packing 2/6.

Magnetic Transducers new, price 7/6 post and packing 2/-

New Aerial Wire on boards 7/22 uncovered. Length 75ft 8/- post and packing 2/6.

New small fuse boxes 250 volts 15 amps. 17/6 each post and packing 3/-.

Headphones, ex Gov. DLR No. 5 high impedance. New 17/6 3/6 p.p. Used condition 12/6 3/6 p.p.

Meters moving coil ex equipment, good condition. Also 20 amp DC, 40 amp DC, and RF Therm-Couple Meters 0-1 amp and 0-2.5 amp, 2in. diameter. 10/-, post and packing 5/-.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

A. H. THACKER,
Radio Dept.,
HIGH STREET, CHESLYN HAY,
Nr. Walsall, Staffs.

If the necessary test equipment is available the amplifier can be checked for overall frequency response, input sensitivity and power output. The frequency response curves given in Fig. 13, 14 and 15 were taken from the original amplifier and performance should agree closely with these. If an oscilloscope is available the power output can be checked at just below clipping point with an 8 ohm high wattage resistor across each output. Clipping, when it occurs at just over 25 watts r.m.s. should be quite symmetrical i.e., the same at top and bottom of the wave-form. The voltage across an 8 ohm load at just below clipping will be between 14 and 15V r.m.s.


The amplifier will of course only develop its maximum power output of 25 watts per channel with 8 ohm loudspeakers. Nevertheless the output power of 15 to 18 watts that would be developed across 15 ohm speakers is still quite considerable for a domestic stereo hi-fi amplifier. At average listening power levels the difference in performance between 8 and 15 ohm speakers would be barely noticeable. It is only really necessary to use 8 ohm loudspeakers if one wants the resultant full power with life-size sound and thereby run the certain risk of becoming unpopular with neighbours.

When the amplifier has been finally tested the legends for the controls can be put on with Letraset or similar transfer lettering and a strip of thin aluminium (20 s.w.g.) glued along the lower edge of the panel. For the original amplifier, this strip was cut and polished, given one coat of clear varnish and glued on with Evostik. The upper section of the panel was painted matt black.

For its final listening tests the amplifier was used with a Lenco record transcription unit and Elac stereo magnetic cartridge, radio tuner (stereo output) a Ferrograph Series 7 half-track stereo recorder, and a pair of Goodmans Magnum 15 ohm speakers. The excellent performance of the amplifier did more than justice to the above signal sources and to the time and effort involved in construction. ■

introducing **MAXWELL**

by G8DSH

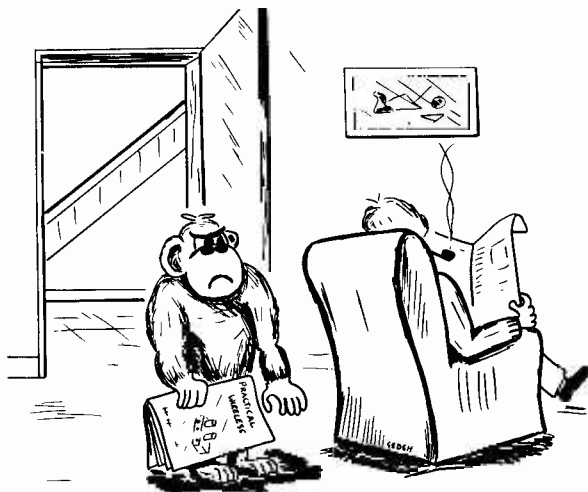

"I don't care how much Mr. Anderson says it costs to build.
I'm not lending you a quid."

THE MW COLUMN

DURING November, medium wave stations in Middle East countries will be prominent in the late evening long after their normal signing-off times. The should be quite noticeable after 2230 hrs GMT when the band is becoming quiet. This situation is caused by Ramadan which ends this year on the 29th of the month. It provides the MW DXer with an opportunity to log the more difficult countries from this area while newcomers to the band should be able to hear several North Africans without difficulty. Look for Oujda 593kHz, Sebba Aioun 611 and 1043, Agadir 935, Tangiers 1232, all in Morocco; Ain Beida 529, Oran 548, Algiers 890, in Algeria; Tunis 629 and 962, Sfax 719 in Tunisia; Benghazi 674, Tripoli 1052, Beida 1124 and 1250, in Libya; Batra 620 and 818, Cairo 773, in Egypt. These stations stand out from their neighbours on account of the Arabic style programming though a few in Morocco, Algeria and Tunisia have European programmes with announcements in French. Farther east and rather more difficult are Riyadh 588kHz in Saudi Arabia; Jerusalem 677, Amman 800, in Jordan; Jeddah 647 in Saudi Arabia; Beirut 836 in Lebanon; Damascus 665, Dayr az Zawr 957 in Syria; Ankara Turkey on 1061; Kuwait 1345 in the Persian Gulf. Although many of these stations can be logged when using a non-directional aerial, a MW loop will give an added advantage when DXing to the east. The writer has heard Tunis 962kHz on a transistor portable, simply by rotating the receiver until interference is at a minimum.

The out of band Greek station reported recently, has been tracked down to Amphissa. It is privately owned, located near Delphi and signs-off daily at 2100 hrs GMT. The latest issue of the FBIS list gives the frequency as 1611kHz but variable. Reporters to Sweden Calling DXers from Austria, Germany, Italy and South Africa have heard Amphissa so it ought to be audible in the country in the winter. The highest authorised MW frequency is 1602kHz (187.3m), which is off-scale on many domestic receivers so it is rather surprising to learn of broadcasting beyond the band edge.

The sea path across the north and mid Atlantic favours reception of Latin American MW stations on the east coast of South America. After midnight is the time to search for the Venezuelan stations YVLH 650kHz Radio Giradot in Maracay, YVKS 750 Radio Caracas, YVRB 960 R. Monagas in Maturin, YVRS 1020 R. Margarita on the island of Margarita, YVMV 1150 Ondas del Caribe in Punto Fijo, YVOZ 1200 R. Tiempo Caracas. From the nearby Dutch island of Bonaire, Trans World Radio operates PJB on 800kHz with a power of 500kW and it is often a strong signal. HJED 820 La Voz de Rio Cauca in Cali, HJHN 960 R. Sutatenza in Barranquilla, HJCC 1010 Bogota, HJAH 1070 R. Atlantico Barranquilla are regularly heard Colombians. ZFY 760 in Georgetown Guyana and SRS 725 Paramaribo Surinam are heard regularly though a loop is essential for SRS on account of European QRM from 728kHz.

Charles Molloy

GOING MULTIBAND

ERIC DOWDESWELL G4AR

HAVING seen many amateur stations over the years it is apparent that the majority of operators do not make the most of the equipment that they possess. There is invariably a reasonable communications receiver capable of resolving c.w., a.m. and s.s.b. on the majority of the h.f. amateur bands but the transmitter is so often a one-band affair, usually for the 20 metre band, and then for the c.w. mode only.

While 20 metres is considered *the* band for DX working there are times when it can go dead for various reasons and when this happens the single-band operator can only switch off and go and join the family around the TV!

With a little effort and at almost no cost at all the transmitter could be modified to cover at least two more bands, thus permitting operation over much longer periods, by selection of the appropriate band that is active at the time.

The only other factor to be considered in going in for multiband operation is of course the aerial system but a suitable one is no more difficult to construct than the one-band dipole and certainly need not deter anyone from going multiband.

Basically the idea is to alter the various tuned circuits in the transmitter so that they each cover more than one band either by changing the inductance/capacitance ratio of the existing circuit or by simple switching.

With some circuits it is possible to obtain coverage of the 10, 15 and 20 metre bands with a single inductor and capacitor. While the L/C ratio may not be the optimum on each band this is mainly a theoretical consideration that will have little effect on the practical results. Grid drive to the following stage may be less than that which would be obtained with a properly designed circuit but the modern beam tetrode generally used in transmitters is very tolerant in this respect.

Practical Considerations

Consider a relatively simple transmitter designed for single band operation on 20 metres consisting of a v.f.o. on 40 metres followed by a buffer amplifier, frequency doubler and power amplifier and how it can be modified for multiband operation. Typical valve types are shown, Fig. 1. If the modifications are carried out over a period the transmitter need not be off the air for any significant time.

VFO/Buffer Amplifier

The v.f.o. will usually consist of an oscillator in which the circuit, components and construction have been carefully integrated in order to get the maximum degree of stability, and working, in this case, on the 40 metre band.

The buffer amplifier is a "must" in order to isolate the v.f.o. from the following stage which can influence the stability of the v.f.o. This is particularly so if the following stage is keyed. In general the lower the operating frequency of the v.f.o. the better will be its stability. However, there is no objection to tuning the output circuit of the buffer amplifier to the 20 metre band as a first step to improving the versatility of the transmitter. Fig. 2.

It is recommended that, at a later date, the v.f.o. itself be modified to function on 80 metres so that operation on 40 metres becomes possible.


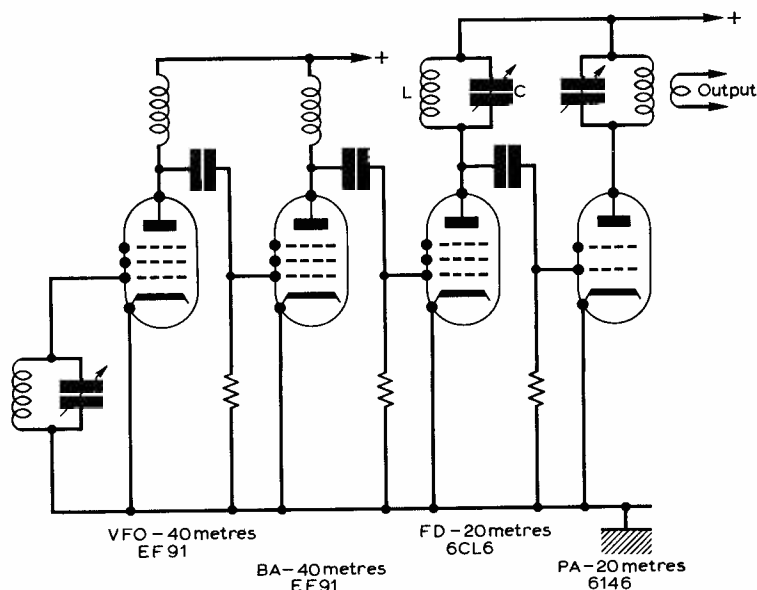


Fig. 1. A typical arrangement of a four valve transmitter for the 20m. band.

STEREO 8 + 8 MK II HI-FI AMPLIFIER KIT

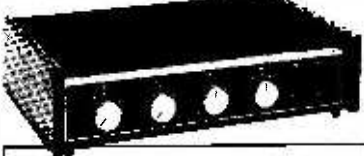

Our popular Stereo 8 + 8 Mk II now further improved incorporating high quality ready drilled printed circuit board for easy construction.

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of.

Brief specification:
Power output: 8.5 watts r.m.s. per channel into 5 ohms.
Frequency response: $\pm 3\text{dB}$ 15-30,000 Hz
Sensitivity: 50 mV into 1 meg ohm
Full power bandwidth: 30 Hz to 20,000 Hz
(Readings taken at 8.5 watts into 5 ohms)
Bass boost approx. to $\pm 12\text{dB}$. Treble cut approx. to -16dB . Negative feedback 18dB over main amp.
Power requirements 25V at 0.6 amp.
PRICES: AMPLIFIER KIT £10.10.0. P. & P. 3/-
POWER PACK KIT £3.0.0. P. & P. 5/- CABINET £3.0.0. P. & P. 5/- (Post Free if all units purchased at same time)

Also available STEREO 10 + 10. As above but 10 watts per channel. PRICES: AMPLIFIER KIT £12. P. & P. 3/- POWER PACK KIT £3.10.0. P. & P. 5/-

LOUDSPEAKER BARGAINS

3" x 4in 10m/- P. & P. 1/6. 5in. 3 ohm 16/- P. & P. 3/-
7" x 4in. 3 ohm 21/- P. & P. 4/- 10" x 6in. 3 or 15 ohm 35/- P. & P. 6/- E.M.I. 8" x 5in. 3 ohm with high flux magnet 26/- P. & P. 4/- E.M.I. 13 1/2" x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-) P. & P. 6/- E.M.I. 13" x 8in. 3 or 15 ohm with two built in tweeters and crossover network 4 gns. P. & P. 6/-
BRAND NEW. 12in. 15w. Hi-Fi Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hi-Fi ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6 Guitar models: 25w. £6.10.0. 35w. £8.10.0. E.M.I. 3in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 18/6 each. P. & P. 2/6.
12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm 37/6. P. & P. 6/-
35 OHM SPEAKERS 3 1/4in. 14/- P. & P. 2/6

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Medium imp. Brand New. Special Price 42/- P. & P. 2/-
SINGLE HEADPHONE
With aluminium headband. Approx 200 ohm 5/- P. & P. 1/6

BALANCED ARMATURE EARPHONE
Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY 3/6. P. & P. 1/6.
CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity 15/6. P. & P. 1/6.
HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE 21/- P. & P. 1/6.
HIGH IMPEDANCE DYNAMIC STICK MIKES.
High sensitivity, 39/6. P. & P. 2/6.

HONEYWELL MICROSWITCHES. S.P. C/O. Push button action. Rating 250V. AC at 15 amps. Size approx. 1 1/4" x 1/2" x 1/2". 5/- each. P. & P. 1/- (6 or more post free).

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 140pF fitted with trimmers and 5:1 integral slot motion. Suitable for nominal 470 k/c L.F. Size approx. 2 x 1 1/4". Only 8/6. P. & P. 2/6.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1 1/2in. 5/- each. P. & P. 1/-

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-50V. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30V. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price 35/- P. & P. 6/-

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240V. Sec. 9-0-9 at 500mA. 14/- P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 17/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21.5V. at 500mA. 12/6. P. & P. 2/6.

BATTERY CHARGER TRANSFORMERS. 200/240V. input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3" x 2 1/4" x 2 1/4". Brand New. Price 21/- P. & P. 5/-

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4in. FIVE for 10/- P. & P. 2/-

SPECIAL OFFER!

HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 8" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohms impedance.

OUR PRICE £8.8.0. Carr. 10/-

Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.10.0. Carr. 10/-

STOCKISTS OF SINCLAIR EQUIPMENT


Z30 Amplifier 39/6. P. & P. 2/6
Stereo 60 Pre. Amplifier 29 19 8 p. & p. 5/-
PZ5 Power Supply 24 19 6 p. & p. 3/6
PZ6 Power Supply 27 19 6 p. & p. 3/6
IC10 Integratee Circuit 59/6 p. & p. 2/-

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18V battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/4" x 1 1/4" x 1 1/4". Brand new complete with instructions. Price 17/6 P. & P. 2/6.

SPECIAL PURCHASE! E.M.I.

4-SPEED PLAYER

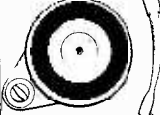

Heavy 8 1/2in. metal turntable. Low flutter performance 200/250v. shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with 4/5 styli for LP/78. ONLY 63/- P. & P. 6/6.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST, (as above.) Fitted mono to styli and cartridge for LP/78. ONLY 20/- P. & P. 1/6.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE 75/- P. & P. 6/-
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.
DELUXE QUALITY PORTABLE R/P CABINET MK II. Uncut motor board size 14 1/2" x 12in. clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.B. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6. P. & P. 9/6.

10/14 WATT HI-FI

AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, E86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.19.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets. 29.19.6. P. & P. 8/6.

BRAND NEW TRANSISTOR BARGAINS. GET 15 matched pair 15/- 175/10p 10/- OCT1 5/- OCT6 6/- AF117 3/6; 2G339 (NPN) 3/-
Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/- ORP12 Cadmium Sulphide Cells 10/6. All post free.

VERY POWERFUL CAPACITOR MOTOR

For 12V. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" x 1 1/2" dia. Free shaft 1/4" dia. x 1/8" Ideal for Model Makers, etc. ONLY 7/6 each P. & P. 1/-
3 or more post free (A few 6v. versions also available)

DE LUXE STEREO AMPLIFIER

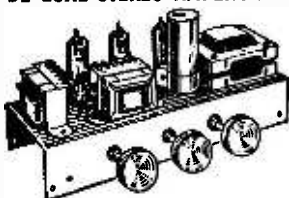

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up: -2 x ECL86 Triode Pentodes. 1 x E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11 1/2" x 4 1/2". Overall height including valves 5". Ready built and tested to a high standard. PRICE £8.18.6 P. & P. 8/-

4-SPEED RECORD PLAYER BARGAINS

Main models. All brand new in maker's packing.
SPECIAL OFFER! Famous GARRARD 3500 fitted Sonotone 9TAHCD Diamond Stereo Cartridge. List price over £16. Limited Number at £10. Carr. 8/6.
LATEST B.S.E. C109/A21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £28.19.6. Carr. 6/6.
With stereo cartridge £27.19.6. Carr. 6/6.
LATEST GARRARD MODELS. All types available 1925, 2025, SP25, 3000, AT60 etc. S.A.E. for latest Prices! PLINTH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.15.0 complete. P. & P. 8/6.

LATEST AGC G6P1/180 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/- P. & P. 1/6

SONOTONE STAHC compatible Stereo Cartridge with diamond stylus 50/- P. & P. 2/-

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. 32/6. P. & P. 2/-

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/- P. & P. 2/-

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI
Peak output in excess of 14 watts. All standard British components.
Built on printed circuit panel size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or S1 Mullard AC128D and matched pair of AC128 o/p) 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 49/6. P. & P. 3/-
Also ready built and tested, 55/- P. & P. 3/-

3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates EOC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only £4.15.0. P. & P. 6/-

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

FEW ONLY. BARGAIN PRICE 55/- P. & P. 6/-

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Frequency Multiplier

Provided that the output tuning capacitor C of the frequency multiplier stage has a value of at least 100pF it is possible to reduce the value of the associated inductor L (Fig. 2) until the circuit is resonating at 20 metres with the capacitor at almost its maximum capacitance. It will then be found possible to tune the circuit to the 15 metre band and to the 10 metre band when the capacitor is almost at its minimum value.

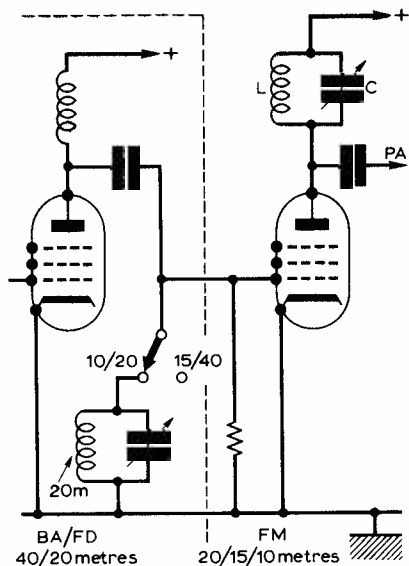


Fig. 2. Adding a 20m. tuned circuit to the buffer amplifier stage.

In setting up this circuit, first remove the h.t. from the p.a. stage and provide drive at 7MHz to the grid of the multiplier stage and tune the output circuit to 14MHz for maximum grid current to the p.a. stage. Check by means of a calibrated absorption wavemeter that the correct harmonic has been chosen. Now remove turns from the inductor L, one at a time, until the circuit resonates at 14MHz with the capacitor almost at maximum. If L is fitted with a dust core it may be possible to reach this condition by simply adjusting the core.

Now reduce the capacitance until another peak in grid current is found, which should correspond to the third harmonic on 21MHz but check again with the wavemeter. Reduce the capacitance still further, when the fourth harmonic on 28MHz should appear with the capacitor at almost minimum capacitance. Check again with the wavemeter.

If difficulty is experienced in reaching or covering all the 10 metre band, check the circuitry for stray capacitances such as those due to the tuned circuit wiring not being the shortest possible or being too close to earthed objects. The valveholder should be of ceramic or similar low-loss material.

The drive will fall off with increasing frequency but it should still be possible to get sufficient drive to permit the p.a. to be driven to a reasonable input on 10 metres. Twenty-five watts input is better than no input at all! If operation on 40 metres is contemplated, and the author thoroughly recommends it,

it will be necessary to add a switch to bring in a separate tuned circuit for this band, but this presumes that the v.f.o. has been modified to provide output on 80 metres, as previously suggested.

Power Amplifier

If the existing output circuit of the p.a. is of the type shown in Fig. 1 and designed solely for 20 metres this alone is sufficient reason to adopt the pi-network circuit shown in Fig. 3 which provides greater attenuation of harmonics and easier matching of the load to the p.a. valve.

Where TVI is a problem this could very well be the only circuit which is acceptable. The only additional component required is the loading capacitor which is usually of the broadcast receiving type and readily available.

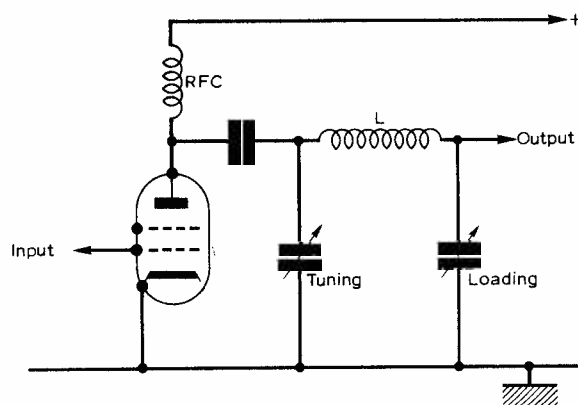


Fig. 3. Conventional pi-network circuit for the power amplifier.

All that is now required to convert this circuit into multiband capability is a band switch selecting appropriate taps on the inductor. A typical circuit with component values is shown in Fig. 4.

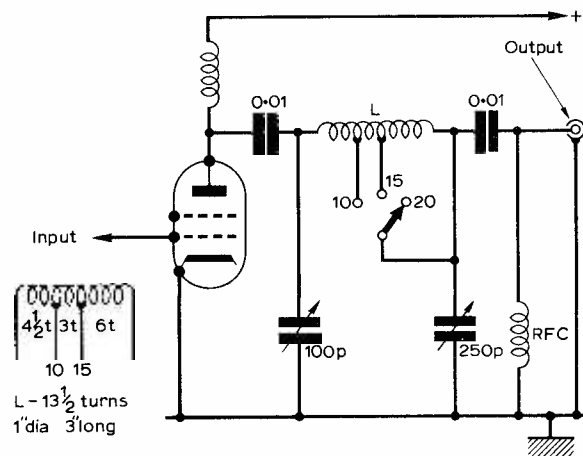


Fig. 4. Component values for a 10/15/20m. pi-network circuit using a 6146 valve.

other supports are not to be had then the extra wires may be sloped below the existing wires and secured to the same supports, Fig. 7.

If the basic dipole is cut for 40 metres then extra dipoles for 10 and 20 metres only are required since the 40 metre dipole will act as a $3/2$ wavelength aerial on 15 metres. There will be a slight mismatch but not enough to prevent satisfactory loading of the p.a.

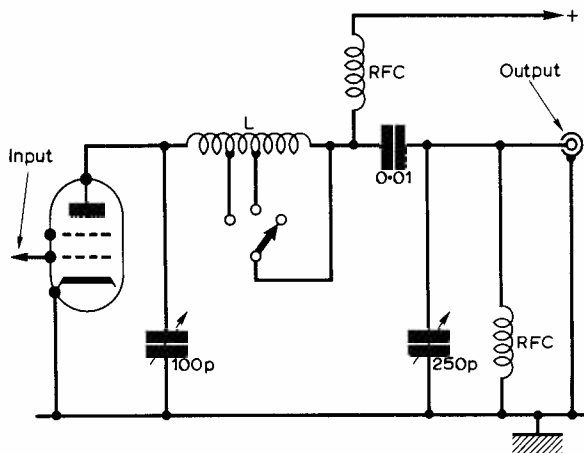


Fig. 5. A receiving type r.f.c. can be used in this circuit to feed h.t. to the p.a. valve.

A variation of this circuit, not often encountered, is shown in Fig. 5 in which a conventional receiving type r.f.c. can be used since it is now placed at a point of low r.f. potential. However the anode tuning capacitor and the bandswitch are now subject to the applied h.t.

Aerials

Converting the transmitter to multiband operation is fairly simple but it is not of much use unless the existing aerial system can also be converted by an equally simple method.

Assuming a conventional dipole aerial is already available for the 20 metre band it is very easy to add additional dipoles for the 15 and 10 metre bands in parallel with the existing wires, tying off the ends to the nearest available supports such as trees or chimney stacks or poles. Fig. 6. If such

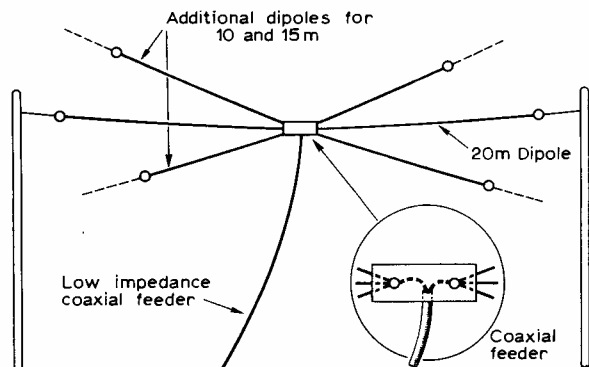


Fig. 6. Possibly the simplest method of converting a 20m. dipole to multiband operation.

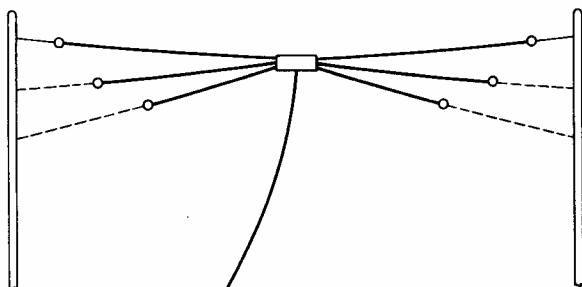


Fig. 7. If the ends of the additional dipoles are tied off to the supports used for the 20m. dipole the direction of maximum radiation will be the same for all three dipoles.

A very effective aerial, often neglected, is the ground plane, Fig. 8, which is simplicity itself to erect yet can provide very low-angle radiation which is so essential for DX working. It is omni-directional, however, and so will not give any discrimination against very strong Continental stations under conditions of short skip. A multiband version of the ground plane is shown in Fig. 9.

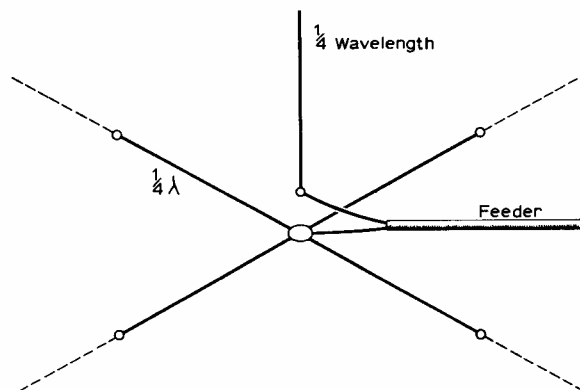


Fig. 8. The ground plane aerial. The four radials may be sloped downwards and may even be used as stays with a lightweight mast.

Provided the ground plane wires for 20 metres are fitted the others are not essential, although they should be erected if possible. Coaxial feeder of 50 Ω impedance should be used and the match between the aerial and the feeder can be much improved if the ground plane wires are sloped down at about 45 degrees to the horizontal.

Another useful multiband aerial that can be erected and forgotten is the well tried G5RV, Fig. 10. While the matching to the feeder is a compromise, no trouble will be found in loading the transmitter satisfactorily on all bands. On 160 metres the feeders may be joined together at the bottom and

COMPLETE STEREO SYSTEM

FOR ONLY 39 GNS


CARRIAGE 35/-

PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5 1/4 x 3 1/2 in. high (Amplifier available separately if required £14.19.6 Carr. 7/6.) **NOW AVAILABLE - MATCHING FM TUNER 21 GNS.**

PREMIER STEREO SYSTEM "TWO"
As system "ONE" above but with Garrard SP25.
PREMIER PRICE 45 Gns. Carr. 35/-


AURIGA 8 WAVEBAND TRANSISTOR PORTABLE

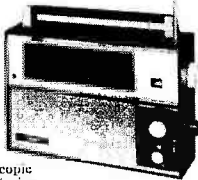Covers Medium, Long and 6 Short Waves and includes many features not normally found in this price range. 10 transistors and 2 diodes. Push Pull output. Press button dial illumination. Volume, tone, tuning and wave-change controls. Telescopic aerial. Uses 6 x 1 1/2 batteries. Sockets for external batteries, tape recorder and aerial. Elegant black and chrome cabinet. Size 11" x 2 1/4" x 7 1/2".



Premier Price 15 Gns.
P. & P. 7/6

TELETON SAQ203E STEREO AMPLIFIER

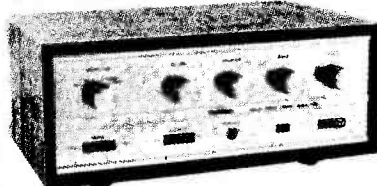


A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0

PREMIER PRICE 22 Gns. P. & P. 10/-

TWO STATION TRANSISTOR INTERCOMS.

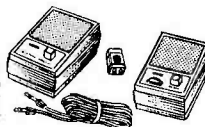Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc.




65/- P. & P. 4/-



HI-FI STEREO HEADPHONES
Designed to the highest possible standard. Fitted 2 1/2 in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft lead and stereo jack plug.
49/6 P. & P. 5/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-

SPECIAL OFFER!

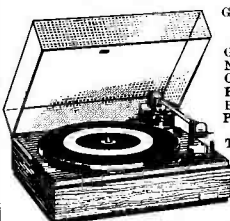

GARRARD SP25 MK II SINGLE RECORD PLAYER FITTED GOLDRING 850 MAGNETIC STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.

Total list price over £24.
PREMIER PRICE 18 Gns.
P. & P. 10/-

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case.



MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped attractively boxed.

LP3 3" 250' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/6
TT3 3" 450' POLYESTER 7/6		DT6 5 1/2" 1800' POLYESTER 22/6	
DT3 3 1/2" 600' POLYESTER 11/6		TT6 5 1/2" 2400' POLYESTER 37/6	
SP5 5" 600' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5 1/2" 1200' POLYESTER 15/-		DT7 7" 2400' POLYESTER 25/-	
		TT7 7 3/8" 3600' POLYESTER 50/-	


TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/6.
Post and Packing 3" 1/-, 5", 5 1/2", 1/6, 7" 2/-. (3 reels and over Post Free).



E.M.I. 13x8in. HI-FI SPEAKERS
Fitted two 2 1/2 in tweeters and crossover network. Impedance 8 or 16 ohm. Handling capacity 10W. Brand new.
79/6 P. & P. 7/6



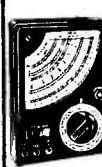WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. **67/6** P. & P. 2/-
"Markanan" Soldering Iron. Lightweight, pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. **31/6** P. & P. 2/-



POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C.
19 Ranges: 0.5-25-50-250-500-2500 volts DC. 0.10-50-100-500-1000 volts AC.
0-50uA-2.5 mA-250 mA DC. 0-5000 ohms. 6 megohms. 10uA 25-0-001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. **£4. 19. 6** P. & P. 3/6.

PREMIER EXCLUSIVE MIDLAND CASSETTE TAPE RECORDER 12-115



Solid state incorporating piano key controls for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with battery. **£16.10.0**
Size 10 1/2" x 5 1/2" x 2 1/2". P. & P. 7/6.



TAPE CASSETTES
C60 (60 min.) 7/6 3 for 21/-
C90 (90 min.) 12/6 3 for 36/-
C120 (120 min.) 17/6 3 for 51/-
P. & P. 1/-

All cassettes can be supplied with library cases at 6d. extra each

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



We'll make you a £2,000 a year technician.

We're going to give 175 men just about the finest apprenticeship in the world.

If you're 15½ to 17½ (and bright at Science or Maths) you could be one of them.

We'll train you to be a top Navy technician, in electronic, air or marine engineering.

And that means you'll take equipment like radar, missiles, helicopters, diesels, computers and automation in your stride.

Our training will make you a £2,000 a year man. With more to come.

And some of the best firms in the country will be keen to sign you on, when you leave us.

Send the coupon for your free booklet. With 175 top technicians to train, you're in with a chance.

RN
ROYAL NAVY

Royal Naval Careers Service (Apprenticeships)
(636 XS2), Old Admiralty Building, Whitehall,
London, S.W.1.

Please send me, without obligation, the free booklet on
Artificer Apprenticeships.

Name

Address

Date of birth

(Enquiries from U.K. residents only)



TRANSISTORS, DIODES & SEMI-CONDUCTORS

AA120 2/-	BSY95A 3/6	OC23 6/6	OC140 5/-	XK143 (Gerrin. up to 70 meg) 2/6
AC107 2/6	GET113 2/6	OC25 6/-	OC189 3/6	PL4003 (200v. P/I 1A) 4/6
AC126 2/6	GET872 4/6	OC26 7/6	*OC170 4/-	2202 (1A P/I) 4/6
AC128 2/6	GET875 2/6	OC28 3/6	OC171 2/3	GET120 (with Ht. 8k. & Wshr.) 4/6
AC167 5/-	GET882 4/6	OC29 10/-	OC202 4/6	CR5001 (50V. 6A. Cond. Rectr.) 8/6
AC217 10/6	GET885 4/6	OC35 8/6	2G240 40/-	CRYSTAL DIODE. MIX for 2/6. (Up to six packets of 6 for 1/-)
AD149 10/6	NK216 7/-	OC44 2/9	2G302 3/6	
AF115 3/-	NKT279A 3/-	OC45 2/3	2N1302 3/6	
AF116 3/-	(8"G.D.)	OC71 2/3	2N1306 4/6	
*AF117 4/-	NKT453 6/8	OC72 2/3	28303 7/6	
BC108 3/6	(P.N.F.)	OC73 2/3	TK200 5/-	
BFY18 4/6	OA10 1/6	OC74 2/3	(V.H.F.)	
BFY51 4/6	OA10 1/6	OC75 2/3	TK20 1/-	
BSY18 3/6	OA47 1/9	OC76 2/3	TK22C 1/6	
BSY26 3/6	OA81 1/9	OC81 2/6	(Gen. Purpose)	
BSY28 3/6	OA85 1/3	OC81D 2/6	TK6023 2/-	
BSY29 3/6	OA95 1/3	OC82D 2/6	XA701 3/6	
BSY65 3/6	OA202 4/-	OC139 5/-		

* WITH 4 LEADS. (Charges: Up to one dozen, can be assorted, 1/- Over 12 charges paid)

S.D.P.'s	BYZ10	TEN AMP SERIES	TWENTY AMP SERIES	THIRTY AMP SERIES
BY100 800piv 2/10 each	1200piv 7/-	50 piv 10/-	50 piv 9/6	100 piv 12/6
SIX AMP SERIES	TRANSISTORS FIVE AMP SERIES	100 piv 12/6	500 piv 13/6	400 piv 20/-
BYZ13 300piv 4/-	100 piv 7/6		800 piv 20/-	600 piv 22/6
BYZ12 600piv 5/-	200 piv 9/-			
BYZ11 900piv 6/-	300 piv 10/6			
	400 piv 12/6			
	500 piv 25/-			

Charges: up to 3 for 1/-, 3 to 11/6, 12 and over paid. Orders received after Nov. 12th will not be despatched until Nov. 23rd, nor will any mail be dealt with between these dates.

ELECTROLYTIC CONDENSERS

Full details of many types from 6d each in our list (see below).
SUB-MIN TRANSFORMER: Output (3 V for OC72 etc) 2/9 driver, 3/- (up to 6 either 1/-).
MULTIMETER: 20,000 Ω/V D.C., 24, 12, 6, (2/6), 1000 Ω/V 47/6 (2/6). Full details both in list.

SOLDERING IRON. Slim Mod. British High speed, 8½in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use, 21/- (1/6).

DIAMONDSTYLII Replacements for BSR TC8LP, TC8/S and TC8LP/STEREO: COLLARO "O"; RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67; all at 7/6 each (1/-). ACOS GP73 and GP91; BSR BT4 (ST3, ST5, ST8 (ST9); SONOTONE RTA, 9TA and 9TAHC; PHILIPS AG3306, 3060, (3063, 3069, 3301, 3302, 3304), all at 15/- (1/-). All are of the very highest quality.

DOUBLE DIAMOND Types: If you don't use the 78 side - this is the best buy - now available only in ST4 (ST3, ST5), ST9 (ST8), 9TA, 9TAHC, 3306, GP91 (for GP92, 93 and 94 Cartridges) and GP918C for GP918C cartridges. 30/- each (1/-).
SAPPHIRE all the above 77 types only, also ACOS GP27 at 3/8 each (1/-). ACOS GP91 at 7/6 (1/-). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES

All fitted 8styl and Standard fittings. Mono GP67/2, 15/-. Stereo compatible - Mono which also plays Stereo records monaurally with min. wear. **GP91/8C**, 21/- latest Stereo **GP98**, 25/6. **Ceramic Stereo**, top quality for expensive outfits, **GP94**, 35/6. **Sonotone stereo** 9TAHC diamond fitted cartridge 55/- (all at 1/-). More diamond types in list. Goldring cartridges, magnetic types, 850, 800, 800E & 800 Super E in stock. If in doubt which cartridge suits your player, write us with details of existing cartridge and make of deck with S.A.E. All postage refunded with despatch of cartridge ordered.

TWO STATION TRANS. INTER-COM. Excellent baby alarm. Instant, easy fitting with leads plug and button. 20/- (1/6).

TRANSISTORISED AMPLIFIER, 3 watt, 9V operation, Size 2½ x 2½ x 1½ 52/6 (1/6).

Extra High Torque MINI-MOTOR, 4½ to 12V, 1½ x ½ in. 5/- (1/-), 9,000 r.p.m.

SUBSTITUTION BOXES. Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range and complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24in. Red and Black leads, thin 4½in. prods, 14in. Plugs 4/6 (1/-). CROC CLIPS: Plated with screw, or with red/black handles, 6d. each, 5/- doz. (1/-). Many other types in list.

RECORDING TAPE. Finest quality British Mylar. STANDARD: 5in. 600ft. 7/3

5½in. 900ft 10/-, 7in 1200ft. 11/3, LONG PLAY 5in. 900ft 10/-, 5½in. 1200ft. 11/3, 7in. 1800ft. 18/- (1/3 reel). Still the finest quality and value obtainable.

MICROPHONES - CRYSTAL MIC91, Hand/Desk, 16/3; MIC45, curved hand grip 19/6; CM21, two tone grey hand/Desk 10/6 (1/3), Stick "60" 20/3; (1/6 each type). Cream plastic hand type with "Strut" stand, switch and 2 leads with 2.5 and 3.5 plugs 12/6 (1/3). Lapel (or hand) with clip 6/6 (1/-). CM70. Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands. 29/6 (1/6).

DYNAMIC: Cream hand/table 15/6 (1/6). ME10 50K Ω, 3½" x 1" with Base. Adaptor 39/6 (2/6). ME11, similar but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6).

CARDIODYNAMIC OMNI-DIRECTIONAL: Highly successful "BALL" type, 209, 50K/600 ohms imp. Built in vol. control, on/off switch, special lead, handle 26.6.0.

Non-directional Ball type, 20K Ω, with on/off slide switch, 20" cable & connector & stand holder (½" thread) type DM160 23.17.6 (on both types 5/-).

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in., either size 5/6 (1/-).

SPEAKERS: 12in. round, 16Ω, 6W, 3 or 1Ω (state which), 37/6 (5/6); or for stereo, 30/- per pair (charges paid), 2½in. 3 1/2 7/6 (1/-). Limited quantity powerful 24in. PM transistor replacement speaker, high ohms, excellent 6/- (1/-). HEADPHONES: Stereo Dyn 8-16 Ω 63/- (3/-). EARPIECES with lead and min. jack plug, magnetic 1/9. Crystal 4/9 (up to 3 for 1/- on either). State if 2.5 mm. of 3.5mm. plug required. (Crystal 3.5mm. only).

AERIALS CAR TYPES - Telescopic vandal proof locks retracted, 2 keys and all fittings 27/6 (2/6). Superior type, slightly longer, 30/- (2/6).

Extending Aerials for Portables & P.M. Sets - 4-section 61-23", 1" sliding threaded base, needs 1" hole 4/-; 6-section 54-25½", screw hole in base 4/-; 7-section 54-32", screw hole in base 7/6. DISAPPEARING, with swivel and sliding threaded socket, fixing nut on bottom section - 8-section 54-29½", 1 1/2 dia. 18/6; 10-section 74-56½", 1 1/2 dia. 18/6. All are strongly plated (P.P. & on all above, up to the 10" type).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 3/9, DPST 3/9 DPDT 3/6. Slide type, Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre "off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d each additional). Rotary Switches etc. in list. Example: 4 pole 3 way 3/9 (1/-).

VIBRATORS: 12v 4 pin non-synch. 1½" x 3½" (EXCL. PINS) 4/6. Genuine PLESSEY 12v 4 pin non-synch. heavy duty type 121 HD4, 1½" x 2½" (EXCL. PINS) 8/6; 12v, 7 pin synch. type 12SR7, 12/6; 6v 7 pin, type 6SR7, 12/6 (All types 1/- per vibrator) a few other types in our list.

MAINS NEON TESTER: Fly leads 2/-; Pocket screwdriver type 3/6, (1/-).

CONNECTING WIRE: Packets of 5 coils asstd. cols., each coil 5 yds. Solid Core 2/9 (1/-). Flexible 3/3 (1/3). Super thin for transistor wiring etc. 3/3 (1/-). PICK-UP WIRE: Twin Super thin Flex, Screened, Sheathed, 1/3 yd. (6d up to 6 yds, over 6 yds. post free). TWIN NICK CABLE: 6d & 1. SINGLE MIKE CABLE: 9d. yd. Both flexible, screened and sheathed. (Up to 3 yds. 8d., each additional yard 1d. extra.)

RETRACTABLE FLEXIBLE LEADS, Space saving "Curly", many uses in car and home: with phono plug each end, 6ft., 4/6; 12ft., 7/6; With phono plug one end, phono socket at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

CURRENT LIST: With full range and special offers sent if requested with all orders or free for S.A.E. (Post free overseas.) This advertisement cancels all previous ones and lists supplied prior to October 30th, 1970.

FELSTEAD ELECTRONICS (Dept PW37)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted. Minimum charge of 1/- Charges apply to G.B. and Eire only, overseas orders welcome. S.A.E. please for all enquiries, otherwise regret cannot be replied to.

the whole system resonated against earth with a suitable tuning unit. This applies equally well to almost any aerial system of course.

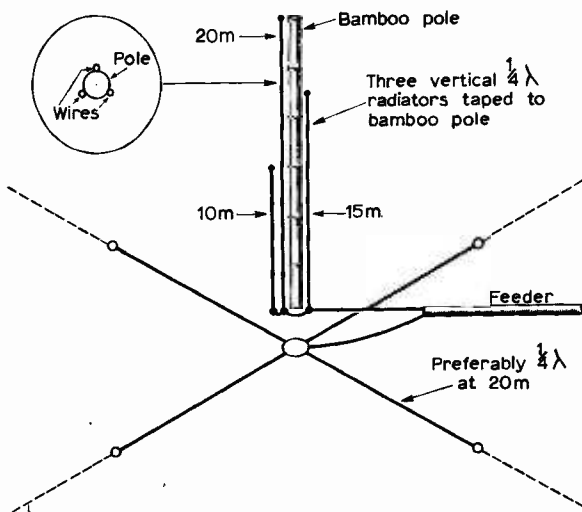


Fig. 9. Construction of a ground plane aerial for 10/15/20m.

If TVI is a problem, the use of open wire feeders or a long wire with a tuning unit should be avoided. Rather a low impedance coaxial feeder should be used, together with a balun transformer in order to reduce the radiation from the feeder. A balun can be made quite easily and cheaply and it will be effective over all the h.f. bands. (See RSGB Radio Communications Handbook p.13.30.)

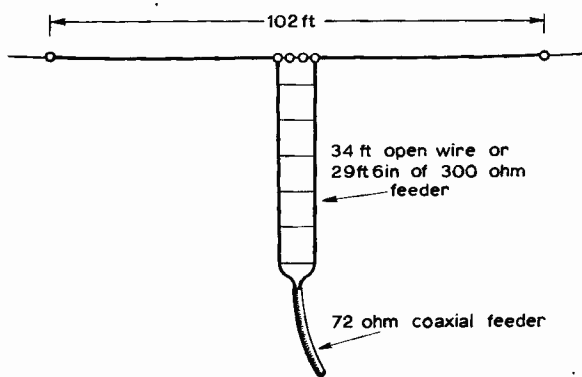


Fig. 10. The G5RV multiband dipole. At a height of about 32 feet the best match between aerial and feeder will be obtained on the 20m. band. If accurate matching is required on the other bands an aerial tuning unit may be interposed at the junction of the co-axial and open wire feeders.

Conclusions

These simple modifications to transmitter and aerial will permit operation on the 10, 15 and 20 metres bands which will greatly increase interest in DX working and often enable contacts to be made with those countries that have proved so elusive on 20 metres.



CORRESPONDENTS WANTED

... anyone of my own age (18) interested in Amateur Radio and Aeronautics.—P. Jones, 28 St. Fagans, Cardiff, CF5 4SP.
... penfriend of my own age (12) who is interested in short wave listening.—Stephen Champion, 16 The Orchard, Kings Langley, Herts., WD4 8JR.
... anyone who knows how to wire up a crossover network in an audio system. The unit I am particularly interested in is a Harrow 3-way crossover network, model MN-3.
—T. M. Bles, 'Tillings', Fair Mile, Henley-on-Thames, Oxon.
... anyone of my own age (18) who is interested in short wave listening.—I. Simpson, 2 Taylor Cottages, Derryhale, Portadown, Co. Armagh, N. Ireland.
... someone who speaks English, is about 17 years old and who likes anything connected with electronics.—B. Cameron, 84 Pownall Street, Masterton, New Zealand.

TAPESONDENTS WANTED

... boy or girl of my own age (17). I have Phillips cassette recorder and a Grundig 4-track machine with speeds of $\frac{1}{2}$, $3\frac{1}{2}$ and $7\frac{1}{2}$ i.p.s.—Louis Smit, 42 Langton Road, Montclair, Durban, South Africa.
... girl with interest in Amateur radio or electronics. About 16 years old.—R. Collins, 17 Heathfield, Chippingham, Wilts.
... near my own age (17) from the Hong Kong, Kowloon area who are living in this country. I already have a pen friend in Causway Bay, Hong Kong and know a little about the area. My tape speeds are: $\frac{1}{2}$, $3\frac{1}{2}$ and $7\frac{1}{2}$ i.p.s. and my hobbies are short wave listening, tape recording and photography and electronics.—A. M. N. Hoare, 4 Fairfield Drive, Whitburn, Sunderland, Co. Durham.
... someone of my own age (18) who is interested in electronics and radio. I have a Ferguson 2-track machine with speeds of $\frac{1}{2}$ and $3\frac{1}{2}$ i.p.s.—R. Richards, 33 Rogers Road, Canning Town, London, E.16.
... boy of 13 would like to tapespond at $3\frac{1}{2}$ i.p.s. Interested in pop records, disc jockeys (would like to be disc jockey himself one day). Can send interesting tape to someone own age.—Reggie Preston Jr., 7 Gordon House, Tarves Way, Greenwich, London, S.E.10.

ISSUES WANTED

... June, September and October 1961 and May, July and August 1962 issues of Practical Wireless.—A. Giles, 20 Fieldway, Dagenham, Essex.
... borrow only copies of P.W. for April, May and December 1966.—J. A. Foll, 104 Burnley Road, Rawtenstall, Rossendale, Lancashire, BB4 8HH.
... Issues of Practical Electronics containing plans for a bass guitar (May and July 1966).—J. Miller, 10 Cortina Avenue, High Barnes, Sunderland, Co. Durham.
... June 1968 issue of P.W.—A. D. Beales, 45 Railway Street, Southport, Lancs.
... November 1967 issue of P.E. containing fuzz box article.—John, 23 Manor Park Crescent, Edgware, Middx.
... copy of P.E. for May 1967, P.W. for July 1969 and P.T.V. for June 1962.—J. Glavin, North Lodge, Northlands, Salthill, Chichester, Sussex.
... issue of P.W. containing 7MHz Transceiver article.—A. Sutton, 11 Bennett Grove, Lewisham, London, S.E.13.
... April, May, June, July, August and October 1968 and February, April, May and June 1969 issues of P.W.—H. Lewis, c/o 18 Vickers Street, Motherwell, Lanarkshire, Scotland.
... Issues of P.W. containing articles on mods for No. 62 Mk. 2 transceiver.—Wim Kloosterman, P.O. Box 203 Penrith, N.S.W., 2750, Australia.
... January 1967 issue and all other issues of 1967 containing details of the "Explorer".—R. L. J. Winston, 82 Stephen's Firs, Mortimer, Reading, RG7 3UY.
... March 1965 issue of P.W. containing details of the key mechanism of the Solo Organ.—R. J. Perry, 42 Kirkstall Mount, Leeds, 5, LS5 3DP, Yorks.
... March 1969 issue of P.W.—H. E. Dunford, 10 Mounts Bay Road, Penzance, Cornwall.
... Issues of P.W. containing articles on the Pedal Steel Guitar.—T. J. Woods, 16 Bermuda Terrace, Deepcut, Camberley, Surrey.
... December 1969 issue of P.W. dealing with the Noise Limiter article.—H. N. S. Colborn, Court Cottage, Horton, Nr. Bristol, BS17 6QR.

EXCHANGE

... Practical Wireless and Television, Basic Electricity, Short Wave Mag., Tape Recorder, Wireless World, 40m transceiver, b.f.o. unit, aerial tuner, Morse code kit, 7W amplifier, Grundig TK23, and Radio & Television Servicing Vols.—Cummins, 14 Munster Sq., N.W.1.

INFORMATION WANTED

... handbook and circuit diagram for R209 Mk. 2 together with info. on mods.—A. A. Lightbody, 42 The Uplands, Harpenden, Herts.
... gen on converting the 38 set for Amateur band reception.—S. L. Lumb, 4 Rydall Street, Leeds, 11.
... info or mods to the Indicator unit type 26.—A. Milne, 67/1 Dumbryden Gardens, Edinburgh, EH14 2NU.
... info on the Armstrong A10 Mk. 2 amplifier and control unit.—P. L. Manley, 85 Nursery Drive, Sanbury, Oxon.
... any info on the Rectograph 500 tape recorder.—R. Marks, Cotswold, Barnet Lane, Elstree, Herts.
... copy of fault-finding chart No. 1 issued with April 1968 P.W.—S. M. Rashid, 49-M, Block-6 P.E.C.H.S., Drigh Road, Karachi, Pakistan.
... manual for Sony tape recorder TC771 not 777A.—S. Coles, Shatterly, Kingsley Avenue, Camberley, Surrey.
... circuit for Ekco RF364 record player.—G. Davies, Mochen Foch Farm, Lower Mochen, Nr. Newport, Mon., NP1 8UW.
... service manual on Philips TV model M236-805 which uses a A59-11W picture tube and works on 625-lines.—Lool Kok Cheow, Radio Malasia, Kajang, Selangor, Malaysia.
... circuit diagram and information on B44 Mk. 2 transceiver with or without mods.—G. Wheeler, 45 Kings Way, Billericay, Essex.
... information or manual for Hallicrafters Sky Champion and Canadian Mk. 1 58 Tx/Rx.—G. Whitwell, 90 Milverton Road, Erdington, Birmingham, 23.
... information, circuit, handbook, etc. on the indicator unit type 300.—Bell, 82 St. Catherine's Avenue, Luton, Beds.
... circuit of Nordie Mende 9050 radio.—D. P. Bourne, 25 Green Street, Georgetown, Guyana, South America.
... circuit diagram of the Veritone Vega unit.—M. J. Power, 66 Oakdale, Harrogate, Yorkshire.
... service sheet for an Ultra T491 radio.—D. Gregory, 53 Wellington Way, Leicester, LE3 1RG.
... the addresses of the agents for Japanese transistor receivers and in particular "Challenge" agent. Also details of connections to amplifier and switching connections of the Minister Transistor Royal 410 tape recorder.—G. Kingston, Kruse Cottage, Trevidland, Liskeard, Cornwall.
... loan of theoretical circuit of Sound Sales amplifier type A-Z serial A.50/75 and tone unit C51/2.—R. V. Flexman, Horseshoe Cottage, The Haven, Billingshurst, Sussex.

practically wireless

commentary by HENRY

IT will not have escaped the notice of our vigilant readers that there has been a gap in Henry's contributions lately.

Although these immortal lines will not be sullied with your marmalade until the jaunting season is over, they are being written—with the stub of a pencil on the back of an hotel bill—at the height of the holiday season. Henry's absence from the August issue was nothing to do with this.

That was a different matter! What our Editor, that mean and scrimping curmudgeon of a—ahem! sorry—what his "Highness" calls 'the exigencies of publication space.' Well, *he* knows what he means. So, to avoid another omission of this column, Henry is squatting atop a high mountain seeking inspiration.

The deadline happens to come smack in the middle of our annual fortnight, already curtailed to ten days by some last-minute panics in the workshop. A local Education Authority decided that the best time to wire out a derelict class room for visual aids and audio reinforcement was while the pupils were under the feet of the parents rather than the teachers.

But eventually the job was sorted out and the kiddiwinkies will be able to Watch with

Teacher when the term comes around again. And Mrs. Henry finally stopped huffing with impatience, went back to make sure the gas was turned off, collected yet another piece of luggage that we simply could not do without, and the Henries sailed off into the wild blue yonder.

Well, wild grey actually, for the vac. was spent in Snowdonia, and you may have read about the gales that uprooted venerable druidic trees and dismantled the weekender's small boats, around the middle of August. We were there, lad, we were there.

One of the structures that the wild wind uprooted must have been the local radio mast, for Henry's holiday punishment has been to 'maintain a radio silence.'

Despite Mrs. H. and her feminine tendency to bring along half the domestic equipage, we have landed in an alien world that appears not to believe in communications. There is no radio in the hotel bedrooms—and a portable wireless set is the one amenity we did not bring.

Musak there is, true, burbling away in its sugary fashion in the unreachable corners of lounge, dining room and hallway. Television there is with a picture that leaves too much to be desired. The mountains breed telegenic ghosts that make all programmes more interesting than informative—if you happen to have a taste for surrealism. But no wireless.

It could be argued that 'Top of the Pops' would sound sacrilegious in such surroundings. Perhaps the rural bumbblings of Walter Gabriel could be tolerated but we cannot even get that.

Gasping for news, we tried the car radio. We were even prepared to put up with Tony Brandon. But we then found the answer to the wireless-less community—those dratted mountains, no less. Reception varies between the impossible and the outlandish.



Gleefully skinning a heretic

You should worry, down there in Centralshire, about the vestige of a 19kHz beat. Up here, if Woman's Hour comes through with any clarity, the locals forecast rain.

So the Henries basked in back-to-Nature silence, relying on social encounters for the saving of sanity. And—guess what—the first family that we met included a teenage son who turned out to be a rabid P.W. fan. Intelligent type, obviously, with a father who works out mathematical problems to put himself to sleep, and a mother who is as erudite as she is charming.

But in the course of conversation this column was mentioned and Henry had his gaff blown—by the little woman, who else?

With painful memories of the chaffing and criticism suffered in his workshop, where colleagues have long since peeled off his aliases, like gleeful Inquisitors skinning a heretic, Henry was loth to stand up manfully and confess: 'I did it.' But we were soon launched on the sort of conversation that goes: '...do you remember...?'

You will be happy to know, Mr. Editor, that in the wilds of N. Wales, at least, Henry's absence was noted, and will have no excuse to do it again—if only I can find a carrier pigeon to help me make this deadline.



Squatting atop a high mountain

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service


NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs
£6.19.6

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P. & P. 7/6

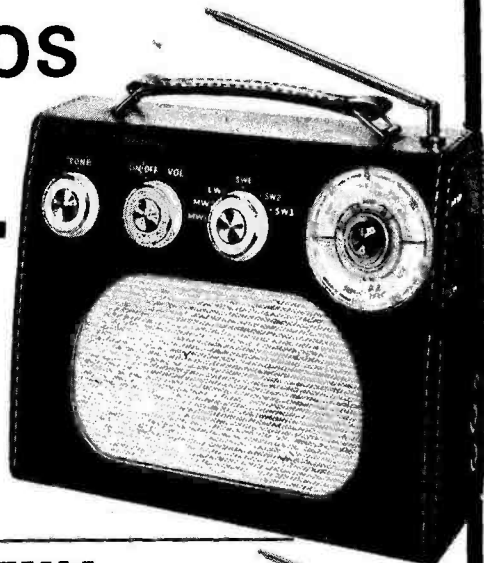


roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

£5.19.6

P. & P. 7/6

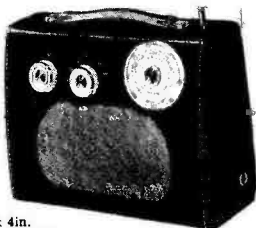


NEW! trans eight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

Total building costs

89/6

P. & P. 5/6

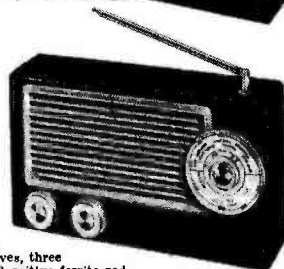

pocket five


MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND PORTABLE
WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs

44/6

P. & P.
3/6

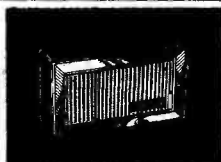

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND
PORTABLE
WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs

47/6

P. & P.
3/9



IMPROVED MODEL!

roamer six


SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive black case with red grille and cream knobs and dial polished brass inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 2/6 extra). Easy build plans and parts price list 2/- (FREE with parts).

Total building costs

79/6

P. & P.
4/6

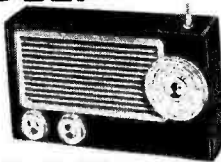

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW.24

★ Callers side entrance Stylo Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

LIFETIME ACHIEVEMENT IN 75 DAYS OPERATING! DXCC (100 Countries Worked)—SWLs THIS ALSO MEANS 100 Countries Heard!!

By G3DCS, E. H. CHAUDRI, C.ENG., F.I.E.R.E., CHARTERED ENGR. USING THE



TYPE SM JOYMATCH

Peaks throughout medium & short wave spectrum—used with joystick or conventional aerial.
£5-10-6 + 5/6 p.p.

G. W. SMITH & CO., at
LONDON 3 & 34 Lisie St. WC2.
311 Edgware Rd. W2.

IMHOFF'S (Eddystone Distributors)
LONDON. New Oxford St. WC1

LASKY'S RADIO at:
LONDON. 207 Edgware Rd.
33 Tott. Ct. Rd.
152-153 Fleet St.

DAVIS & KAYS, Turnpike Pde. N15

RSC HI-FI CENTRES at:

BIRMINGHAM. Gt. Western Pde.

BRADFORD. 10 N. Parade.

DARLINGTON. 16 Priestgate.

DERBY. 16 Osmaston Rd.

EDINBURGH. 133 Leith St.

GLASGOW. 326 Argyle St.

HULL. 91 Paragon St.

LEEDS. 5-7 County Pde.

LEICESTER. 92 High St.

LIVERPOOL. 73 Dale St.

MANCHESTER. 60A Oldham St.

MIDDLESBROUGH. Newport Rd.

NEWCASTLE/TYNE. 41 Blackett St.

SHEFFIELD. 13 Exchange St.

LONDON. 238 Edgware Rd.

WORLD'S MOST VERSATILE & COMPACT ALL BAND AERIAL

JOYSTICK

REGD.

VARIABLE FREQUENCY ANTENNA

PARTRIDGE MAKE DX EASY! OBTAINABLE FROM:—

ALSO AT:

ABERDEEN. L. Hardie, George St.

ASHFORD (MIDD.). Echelford Coms.

BATH. Ryland Huntley, 15 Old Bond St.

BIRMINGHAM. Amateur Electronics,

Chas. H. Young Ltd.

BLACKBURN. Holdings, Mincing Lane.

BOURNEMOUTH. Forrester's Nat. RDO.

BRADFORD. Radio Ham Shack, Godwin St.

BRIGHTON. Arthur Sallis, Gardner St.

BURNLEY. Trafalgar Supplies.

CARDIFF. Wesak Radio, Cathays.

CHELMSFORD. Radio Service, New St.

CHESTERFIELD. J. & A. Tweedy Ltd.

EDINBURGH. F. Brown & Co. Geo. IV Bdge.

FRASERBURGH. Murray Mackie.

GLASGOW. RME Surplus Supplies.

GOODMAYES. Unique Radio, Facade.

GT. YARMOUTH. The Record Shop.

HALIFAX. Albert Hind. Ltd.

HARTLEPOOL. Specialist Radio.

HERNE BAY. Purdeys.

HUDDERSFIELD. Radio Craft Ltd.


ILLFORD. Short Wave, Newland Ave.

ILFORD. Radio Day, Clayhall Ave.

IPSWICH. Eagle Elect. (Dunsell)

LEICESTER. S. May 12-14 Church Gate.

(FREE BROCHURE 5d. STAMP)

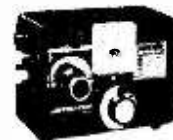

TYPE LO-Z JOYMATCH

New one knob joystick VFA
tuner, 1/2 kw 80 thru 10m. 100W on
160m. Excellent S.W.R. all bands.
£7-19-6 + 5/6 p.p.

LIVERPOOL. Stephens-James, Priory Rd.

Super Radio (Whitechapel).

LONDON. City Radio, Ealing, W5.

Newbury Radio, Forest Gate.

R. T. & I. Ashville Rd. E11.

LUTON. Coventry Radio, Dunstable Rd.

NEWCASTLE/LYME. Sydney T. Chadwick.

NEWCASTLE/TYNE. Richley & Freeman.

NEWPORT (MON.). K.F. Paull, Dock St.

NEWQUAY. R. V. Heming Ltd.

NORWICH. Radiomatics, St. Benedicts St.

NOTTINGHAM. Pete's Elect. Arkwright St.

OLDHAM. The Electronic Centre, The Mumps.

PLYMOUTH. Radio Parts, 5 Market Way.

PRESTON. Croftfilm, 48 Friargate.

ROMFORD. Newbury Radio, 120 North St.

SCARBOROUGH. Derwent Rdo. Hillcrest Ave.

SOUTHAMPTON. Frank Victor, Northam.

S. SHIELDS. J. R. Gough Elect. Imeary St.

SUNDERLAND. Red Radio Shop. Crowtree Rd.

SWANSEA. Holt High Fidelity.

WATFORD. Davis & Kays, Woodlands Pde.

WESTCLIFF-ON-SEA. Radio Constructor Co.

WEYMOUTH. Dorset Radio Electronic.

WORCESTER. Jack Porter, College St.

WOLVERHAMPTON. Lings Radio, Snow Hill.

WORTHING. G.W.M. Radio, Portland Rd.

G3VFA

OR DIRECT FROM: PARTRIDGE ELECTRONICS LTD. (P.W.), BROADSTAIRS, KENT. (Tel: THANET 62535)

G3CED

GOLDRING & GARRARD PRICES SLASHED

G.850 £4.17.6d p.p. 2/6. SP25 Mk 11 £10.15.0d p.p. 10/-

SEE BELOW FOR OTHER MODELS

Golding 800/E Elliptical Transcription Arm Cart. £11.15.0d p.p. 4/-



PLINTHS AND COVERS

Suitable for AT60, SP25, 3000, 2500,
3500. Superbly finished Plinth, ready
cut for use, complete with Tinted
Perspex Cover. This unit is finished
in Teak Polish and will blend in any
modern home. 79/6 p.p. 7/6.

TURNTABLES

Garrard 8025 TC	Son 9 TAHC Diamond	£9.10.0d
Garrard 3000	Son 9 TAHC Diamond	£9.12.6d
Garrard A70	Mk 11 Less Cart.	£11.15.0d
Garrard SL65B	Less Cart.	£13.19.6d
Garrard AP75	Less Cart.	£13.19.6d
Garrard SL72B	Less Cart.	£24.0.0d
Garrard SL75	Less Cart.	£25.0.0d

10/- P.P. FOR DECKS

SPEAKERS, AMPLIFIERS, ETC.

Teleton CR 107 £29.0.0d p.p. 10/-
Teleton F4200 £42.0.0d p.p. 10/-
Best Stereo Headphones £2/8 p.p. 5/-
"Master" Magnetic Cart. Diamond Stylus
65/- p.p. 5/-
LL Nova Amp. 5 + 5 Mag and Cer-Input
£15.10.0d p.p. 10/-
3-Way Speaker System Teak Cabinet, size
14 1/2 x 8 1/2 x 6", 10 Watts Peak, each £5.19.6d
p.p. 7/6
Nova 7500 VHF Tuner Plus 7 x 7 Amp.
£39.0.0d p.p. 10/-
3-Way Speaker System Teak Cabinet, size
21" x 14 1/2 x 9 1/2", 20 Watts Peak, each
£11.19.6d p.p. 10/-
Prices for good not listed, sent by return
of post. S.A.E. please.

LEAK SANDWICH (SPEAKER)

Enclosure (26" x 15" x 12") oiled
(mat) walnut 8 ohms—up to 35w
handling capacity.
List price £45. 10. each.
Our price £32 each p.p. 10/-

GARRARD SP25 ON PLINTH WITH COVER

Complete, not wired, £14.12.6d
p.p. 15/- Ready wired with 5-pin
Din or Phono, 10/6 extra.

For any other Deck, 3000, 2025TC,
add price of Plinth and Cover to
Deck and add 15/- p.p.

Send P.O. Order, Cheques, etc., to:

AUDIO SUPPLIES

Callers welcome: 50 STAMFORD HILL, LONDON, N.16
Phone: 01-895 3611


Open Sun. 10 a.m. to 2 p.m. Mon. to Sat. 9.30 to 6 p.m. Thurs. 1 p.m.

M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

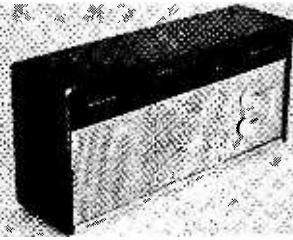VHF FM/MW/LW
TRANSISTOR RADIO
BRAND NEW 10 transistor plus 4 diode table
model of well known
British manufacture. The
highly polished wood
cabinet, speaker and pre-
assembled chassis are
supplied separate and
only require fitting to-
gether and the 2 speaker
connections making.
CHASSIS & CABINET
£9.10.0. SPEAKER 25/-
carr. paid.



STC STEREO/MONO HEADPHONES. Brand new lightweight high
quality comfortable padded headphones for stereo or mono use. Weight
10 oz. 20 c/s to 20 Kc/s 300 ohms per earpiece. Supplied with details of
matching circuit for 15 ohms using only 3 resistors. 54/- plus 4/- pp.
12 VOLT TRANSISTOR INVERTERS. 12vdc input. 270vdc at 150mA
approx output. Transformer 2in x 2in x 1 1/2in mounted on aluminium
case 1 1/2in x 2 1/2in x 4in. Weight 15oz. 65/- plus 4/- pp.

TRANSISTOR MODULATOR PRE-AMP PANEL. BRAND NEW 4
transistors plus 1 diode. 4 1/2in x 2 1/2in. Fitted with pre-set microphone gain
control and mod filter. Originally used to drive an NKT404 which
drove a pair of NKT404s. Supplied brand new c/w circuit of complete
modulator. 22/6d plus 1/6 pp.

TRANSISTOR AUDIO AND MUTING PANELS. Brand new set of
3 panels. Audio panel with transistor gate originally used to drive an
NKT404 output transistor. 2 muting panels with Schmitt trigger circuit
to operate the gate on the audio panel. 8 transistors in all. Supplied with
full circuit 22/6d plus 2/6 pp.

455Kc/s FM LF PANEL. Brand new but faulty 6 transistor panel
usually low in gain. 12/6 plus 1/6 pp.


HAND TELEPHONES. Brand new radiotelephone type press to talk
handsets. 12/6 plus 1/6 pp.

VHF AERIAL C/O RELAYS. Used but OK. 6 or 12v. 4/- plus 1/6 pp
60 UNTESTED MIXED TRANSISTORS 5/- plus 1/- pp.

60 UNTESTED MIXED DIODES 2/6 plus 1/- pp.
USED TESTED VALVES. 12AX7/ECC83 2/6. 6BJ6 1/6. 6AQ5/EL90
2/6. ECF80 2/-, 6AT6 1/6.

ALSO VARIOUS VHF EQUIPMENT IN STOCK
S.A.E. AND 6d. STAMP FOR LISTS

GOING BACK...

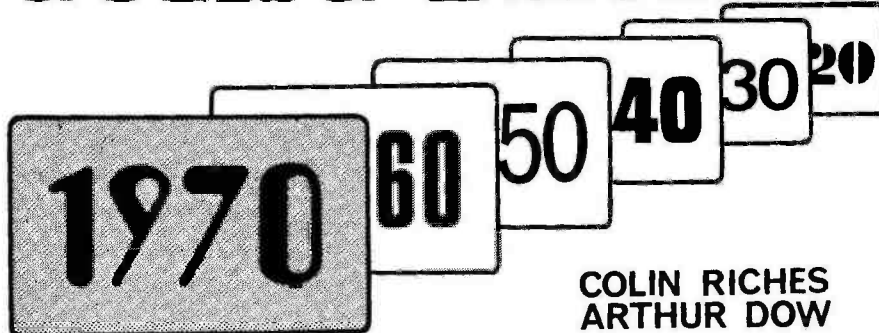

COLIN RICHES
ARTHUR DOW



AT 6.0 p.m. on November 2nd, 1920 switches were thrown in a small shack on top of the Westinghouse Company's building in Pittsburgh, Pennsylvania, U.S.A. and the first broadcast was about to begin. Throughout the day, the American people had been to the election booths to cast their votes in the 1920 Presidential election and the broadcasting of the results had been chosen for the opening programme.

There were very few receivers, but the station had arranged for the programme to be relayed over loudspeakers to a nearby civic centre. These listeners were privileged to be the first to hear the famous station call-letters . . . "KDKA, East Pittsburgh".

The programme continued for some eighteen hours—long by even present day standards—and a few hours later the station was again on the air and has continued to this present day with regular programmes, still using the same call-sign.

The origins of KDKA dated many years earlier than 1920. As early as 1915 a Dr. Frank Conrad (who later became Assistant Chief Engineer of

Westinghouse) had built a radio receiver to enable him to hear the time signals broadcast from the Naval Observatory at Arlington. He did this primarily to test the accuracy of the watch and a \$5 bet was the motivating factor. The reception of these signals sparked the enthusiasm of Dr. Conrad and by July 1916 he was on the air with his amateur station, 8XK. Dr. Conrad was however unable to pursue his hobby for long because the entry of the United States into the First World War caused cancellation of amateur licences in April 1917.

During the emergency both Westinghouse and Dr. Conrad were able to gain invaluable experience as the station was allowed to operate under a special authorisation for the testing of new radio equipment for the British and U.S. Governments.

The ban on transmissions was lifted on October 1st 1919 and very shortly afterwards 8XK was back on the air incorporating all the advances made during the War, making it an extremely well equipped station for the times.

On the 17th of the same month Dr. Conrad



Harold W. Arlin, the world's first full-time radio announcer.



Picture taken during the first broadcast of KDKA.

became bored with continually speaking into the microphone and to enable him to make adjustments on his equipment while it was operating, he placed the microphone near his gramophone. During the next few days he made considerable use of this trick and was amazed to find that listeners began writing in to ask him to play a particular record, to convince sceptics that music could be transmitted over the radio.

The demand however became so heavy that Dr. Conrad had to stop playing individual requests and

instead went over to "broadcasting" gramophone records over the station for two hours every Wednesday and Saturday. Dr. Conrad's use of the term "broadcast" to describe these transmissions is the first recorded use of the word.

With four hours a week of transmission time to fill, the supply of records was soon exhausted and a local music store agreed to supply the records as long as Dr. Conrad agreed to announce where they could be bought, and so the first "commercial" was born.

The popularity of these programmes grew rapidly and from time to time live singers and bands were included in the programme with one of Dr. Conrad's two sons acting as the master of ceremonies. By the late summer of 1920 the broadcasts had grown so popular that a Pittsburgh store ran an advertisement in a daily newspaper for the sale of radio receivers on the strength of being able to hear these transmissions. The date was September 29th, 1920 and it was probably the one single event that brought about the first broadcast.

Among the people who saw the advertisement was H. P. Davies, Vice-President of Westinghouse. He was already a keen follower of the work being done

The Aeriola Jr. had range of 15 miles and used to cost about £10.



First orchestra developed for exclusive radio work was KDKA Little Symphony Orchestra, with Victor Saudek conducting.



How the family used to listen in.

by their company employee and the advertisement made him realise that if regular programmes were provided for the people, they would quickly want to buy receivers of their own.

Mr. Davies began by winning over the other officials of Westinghouse and this was done so quickly that the application for a licence was submitted to the authorities on October 16th and the forthcoming election night was chosen for the grand opening. The enthusiasm of the small group was such that it was under five weeks between the newspaper advertisement and the station opening.

For this first scheduled broadcast there was no studio; a single room accommodated the transmitter, the record turntable and the staff. William Thomas acted as the technician, L. H. Rosenberg as the announcer and John Frazier and R. S. McClelland handled the telephone lines to the newspaper offices. The chief engineer was D. G. Little, a long standing friend of Dr. Conrad. Oddly enough the main force behind the project was not there on that night. Fearful less the new equipment should fail Dr. Conrad was standing by with his station 8XK, five miles away, ready to take over in the event of trouble.

Between the election returns and the occasional music, listeners heard the same request over and over again: "Will anyone hearing this broadcast communicate with us as we are anxious to know how far and how well this programme is being heard".

The broadcast was a national sensation and newspapers all over the country carried reports on the broadcast. The mailbag over the next few days was massive. One of the reports came from H. W. Irving, now transmitter supervisor of KDKA. He heard the broadcast on the ship "Antigone", then off the coast of Virginia.

KDKA had a fair lead on other stations, and it was not until several months later that the second station came on the air, this one being WBZ in Springfield, Massachusetts which made its first trans-

—continued on page 677

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 23/6. Kit D—65 w. 23/6. Kit F for 8ft. 125 w. tube 35/-. Kit MF1 is for 6in., 9in. and 12in. miniature tubes. 19/6. Kit MF2 for 21in. 13 w. miniature tube 29/-. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit F 6/6 then 4/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

BLANKET SWITCH

Double pole with neon jet into side so luminous in dark. Ideal for dark room light or for use with waterproof element, new plastic case. 5/6 each. 3 heat model 7/6.



BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each we offer these while our stocks last at only 12/6 each.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each. 24/- doz.

Standard. 2in. long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each. 18/- per dozen.

Flat. Flat type, 2in. long, just over 1/16in. thick. Approximately 1/2in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. 25 per dozen.

Small ceramic magnets to operate these reed switches 1/6 each. 18/- dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment.

100 mfd. 25v., 1/6 each 12/- doz.

200 mfd. 25v., 1/8 each 15/- doz.

250 mfd. 50v., 3/8 each 33/- doz.

400 mfd. 40v., 4/4 each 46/- doz.

500 mfd. 12v., 2/- each 21.0 doz.

500 mfd. 25v., 3/6 each 33/- doz.

500 mfd. 50v., 4/6 each 48/- doz.

500 mfd. 350v., 8/6 each 24.10 doz.

1000 mfd. 12v., 3/- each 31.10 doz.

1000 mfd. 18v., 3/4 each 34/- doz.

1000 mfd. 64v., 7/4 each 34/- doz.

2000 mfd. 25v., 6/6 each 79/- doz.

5000 mfd. 12v., 4/6 each 22.50 doz.

10,000 mfd. 6v., 5/6 each 23.00 doz.

10,000 mfd. 15v., 8/6 each 24.10 doz.

15,000 mfd. 10v., 10/6 each 25.00 doz.

60,000 mfd. 8v., 22/- each 210.00 doz.

70,000 mfd. 18v., 40/- each 220.00 doz.

TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7ft to 47in. Hole in bottom for 6BA screw 7/6. KNUCKLED MODEL FOR P.M. 10/-.

TOGGLE SWITCH

3 amp 250v. with fixing ring 1/6 each. 15/- doz.

80 OHM BALANCED ARMATURE EAR PIECE

Usable as a microphone or loudspeaker. 4/6 each.

3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Clydon" Company for the equally famous Radiomobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra (if required) with a frequency coverage 1620 Kc/s-525 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2 x 2 1/2 in.) with reduction gear for fine tuning. Snip price this month 12/6, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post free.



Horstmann "Time and Set" Switch


(A 15 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around 45. Special snip price 29/6, p. & ins. 4/6.

DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 8/6 each, plus 3/6 post and insurance, 6 or more post free.



ATLAS SLIMLINE FLUORESCENTS

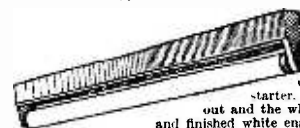

Fluorescent lighting units made by the famous Atlas company, with super silent, polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. Postage and insurance 6/6 extra. 4ft. twin model 59/6, post & ins. 6/6. 5ft. twin with diffuser, sharp price 2/1, our price 210, carr. 21.

230 VOLT MAINS OPERATED KLAXON HORN



This is small (about 10in. long) but has a very piercing and effective note hence it would make good Fire Alarm or Works stop and start Siren. Also useful for instance to scare birds off crops. Made for the G.P.O. so obviously best quality. Slightly used but OK. 39/6 plus 1/6 p.p.

THIS MONTH'S SNIP

40 WATT 12in. HI-FI SPEAKER. Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 40 watts R.M.S.—Cone moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms. Chassis diam. 12in.—12 1/2in. over mounting lugs. Overall height 5 1/4in. A £10 speaker offered this month for 25.15/6 plus 7/6 post and ins.



MOTORISED CAM SWITCH

Made by the famous meter company Chamberlain and Hookham, these have a normal mains 200-240V motor which drives a ratchet mechanism so geared to give one ratchet action per minute on a wheel with 60 teeth thus a complete revolution of the cam takes place in one hour. The cam operates 8 switches (6 changerover and 2 on/off thus 480 circuit changes per hour are possible). Contacts, rated at 15 amps have been set for certain switch combinations but can, no doubt, be altered to suit a special job. Also other switch wipers or devices can be attached to the shaft which extend approximately one inch. 47/6, p. & ins. 4/6.



BARGAIN OF THE YEAR


MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/4 x 2 1/4 x 1 1/4in.—complete with soft leather zipped bag. Specification—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kc/s. Sensitivity: 465 Kc/s or 485 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only 24/6 less batteries plus 2/6 post for 27 post free. Rechargeable batteries 8/6 pair.



1 HOUR MINUTE TIMER

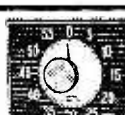Made by famous Smith's companies, these have a large clear dial, size 4 1/4 x 3 1/4, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch 22/6.



3kW TANGENTIAL HEATER UNIT




This heater unit is the very latest type, most efficient and quiet running. It is fitted in Heater and blower heaters costing £15 and more. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 79/8. Postage and insurance 6/6. 2kW. model 49/6 plus 6/6 p. & p. 2kW model 59/6 plus 6/6 p. & p.

MICRO SWITCH

5 amp. changerover contacts, 1/9 each. 18/- doz. 15 amp Model 2/- each or 21/- doz.



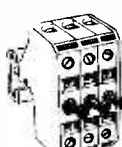Mains Connector. A quick way to connect equipment to the mains safely and firmly—disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold bare wire on up to four 7,028 cables. 12/6 each.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 37/6, plus 2/6 post & p.



BALANCED ARMATURE UNIT

500 ohm. operates speaker or microphone, so useful in intercom or similar circuits. 6/6 ea, 23.10.0 doz. 80 ohm model 5/6.



BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2 in. deep. Has three piano key type controls for Record, Play, back and Rewind. Motor is a special heavy duty type intended for operation off 4.5 volts. Supplied complete with 2 spools ready to install. Record. Replayhead is the sensitive M4 type intended for use with transistor amplifier. Price 79/8. Post and insurance 4/6. Unused ex-equipment.



PROTECT VALUABLE DEVICES FROM THERMAL RUN-AWAY OR OVERHEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostats part of the heat-sink. Motors and equipment can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removal range setting is between 80 to 800deg.F. Price 10/-



THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch, so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob 59/6.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: P1, P3, P4, P6, P7, P9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

ELECTRONICS (CROYDON) LTD
Dept. PW, 266 London Rd., Croydon CRO 2TH
Also 102/3 Tamworth Road, Croydon

VALVES

1A7	7/9	6B16	9/-	6K7	1/9	787	45/-	20P4	20/-	78	5/-	D992	3/6	ECF80	6/6	EM84	7/6	PCCR9	10/6	PY800	9/6	UCH81	7/-
1D5	7/8	6B17	17/-	6K7G	6/6	7Y4	9/6	20P5	20/-	80	7/6	D996	7/6	ECF82	6/6	ESU150	20/-	PCCR19	10/6	PY801	9/6	UCH82	7/6
1H5	7/8	6B87	25/-	6K8	2/9	10C1	20/-	25L6GT	7/-	150B2	11/6	DH77	4/9	ECH31	12/6	EY51	7/6	PCF80	9/6	R3	7/6	UCH83	11/6
1L7D5	6/-	6B87	25/-	6K8	2/9	10C2	12/6	25V5	6/6	150C4	9/6	DK91	6/-	ECH42	13/-	EZ35	6/-	PCF82	9/6	R19	7/6	UF41	10/6
IN6GT	6/-	6C4	5/-	6K8GT	11/6	10P1	14/9	25Z4	6/6	801	9/6	DK92	9/-	ECH81	5/9	EZ40	9/-	PCF84	8/-	RG5/500	80/-	UF49	7/6
IR5	6/-	6C5G	5/-	6K25	15/-	10P18	8/-	28D7	9/3		120/-	DK96	7/9	ECH85	8/6	EZ41	9/6	PCF86	9/-	S130	40/-	UL41	12/-
IR4	5/6	6C6	3/9	6L1	12/-	10L1	8/-	38C1	6/9	813	75/-	DL92	25/-	ECL80	7/-	EZ80	5/6	PCF88	9/-	SP4	8/-	UL84	7/-
IR5	4/6	6C8G	6/-	6L6G	7/9	10L1D11	10/6	30C15	15/-	864	15/-	DL93	6/3	ECL82	7/-	EZ81	5/6	PCF89	9/-	SP41	8/-	UM80	6/6
IT4	4/6	6C8G	24/-	6L18	6/-	10P13	13/6	30C17	15/-	864	15/-	DL94	6/3	ECL83	10/3	EY61	15/-	PCF90	15/-	SP61	8/-	UM81	6/6
3A4	4/6	6CH6	7/8	6Q7G	6/-	11B3	70/-	30C18	15/-	1825	6/3	DL95	7/9	ECL86	9/-	EY62	15/-	PCF91	15/-	SP62	8/-	UM82	6/6
3Q4	7/9	6CW4	13/6	6Q7GT	8/6	12AT6	4/9	30P5	17/-	4022AR	67/-	DM70	6/-	ECL87	10/3	EY63	15/-	PCF92	15/-	SP63	8/-	UM83	6/6
3Q5	7/9	6D6	3/9	6A7M	7/-	12AT7	6/-	30PL1	15/-	6763	12/-	DX86	6/-	ECL88	10/3	EY64	15/-	PCF93	15/-	SP64	8/-	UM84	6/6
384	6/3	6E5	7/6	68C7	7/-	12AU6	5/9	30PL12	19/-	7193	2/-	DX87	6/-	ECL89	10/3	EY65	15/-	PCF94	15/-	SP65	8/-	UM85	6/6
3V4	6/3	6F1	12/6	68G7	6/-	12AU7	5/9	30PL14	15/-	7475	14/-	DX88	12/-	ECL90	10/3	EY66	15/-	PCF95	15/-	SP66	8/-	UM86	6/6
5R4GY	10/6	6F5G	8/-	68H7	3/3	12AX7	6/3	30L15	17/-	A61	9/6	EAS0	3/6	ECL91	10/3	EY67	15/-	PCF96	15/-	SP67	8/-	UM87	6/6
5V4G	5/6	6F6G	5/-	68J7	6/-	12BA6	6/-	30L17	17/-	ATP4	2/3	EAB8C0	6/6	ECL92	10/3	EY68	15/-	PCF97	15/-	SP68	8/-	UM88	6/6
5V4G	8/-	6F8G	5/6	68K7GT	4/9	12BE6	6/3	30P4	22/6	ATP5	12/-	EAF42	10/-	ECL93	10/3	EY69	15/-	PCF98	15/-	SP69	8/-	UM89	6/6
5Y3GT	6/-	6F11	6/6	68L7GT	6/-	12C8GT	6/-	30P12	18/-	ATP7	8/6	EAF43	10/-	ECL94	10/3	EY70	15/-	PCF99	15/-	SP70	8/-	UM90	6/6
5Z4G	7/-	6F13	6/6	68N7GT	5/6	12E1	20/-	30P19	15/-	AU2	8/6	EAF44	10/-	ECL95	10/3	EY71	15/-	PCF100	15/-	SP71	8/-	UM91	6/6
630L2	15/-	6P23	15/-	6Q4GT	12/-	12J7GT	6/6	30PL13	18/-	AU5	8/6	EBC33	6/6	ECL96	10/3	EY72	15/-	PCF101	15/-	SP72	8/-	UM92	6/6
6A8G	12/6	6P24	15/-	6UG6	7/9	12K7GT	7/-	30PL14	15/-	AZ31	8/-	EBC41	9/6	ECL97	10/3	EY73	15/-	PCF102	15/-	SP73	8/-	UM93	6/6
6AC7	4/6	6F25	14/-	6V6M	12/-	12K8GT	8/-	35A5	12/6	CBL31	16/-	EBC90	9/6	ECL98	10/3	EY74	15/-	PCF103	15/-	SP74	8/-	UM94	6/6
6AK5	5/-	6F28	14/-	6V6G	4/6	12Q7GT	6/-	35L6	9/-	COH35	15/-	EBC91	9/6	ECL99	10/3	EY75	15/-	PCF104	15/-	SP75	8/-	UM95	6/6
6AM5	4/6	6F22	20/-	6V6GT	6/6	12SA7	8/-	35W4	4/6	CL39	20/-	EBC92	9/6	ECL100	10/3	EY76	15/-	PCF105	15/-	SP76	8/-	UM96	6/6
6AM6	3/6	6G6	3/6	6X4	4/6	12S8GT	6/-	35Z3	10/-	CV450	25/-	EBC93	9/6	ECL101	10/3	EY77	15/-	PCF106	15/-	SP77	8/-	UM97	6/6
6AQ5	3/6	6H6	3/-	6X3G	4/6	12SH7	3/-	35Z4GT	9/6	CV30	12/6	EBC94	9/6	ECL102	10/3	EY78	15/-	PCF107	15/-	SP78	8/-	UM98	6/6
6AS7G	15/-	6J5M	9/-	6X5GT	4/6	12SJT	3/9	35Z5	10/-	CV31	8/6	EBC95	9/6	ECL103	10/3	EY79	15/-	PCF108	15/-	SP79	8/-	UM99	6/6
6AT6	4/9	6J5G	4/-	7B6	11/6	12SRK7	4/9	37	6/6	DAC32	7/-	EBC96	9/6	ECL104	10/3	EY80	15/-	PCF109	15/-	SP80	8/-	UM100	6/6
6AT6	5/6	6J5GT	5/6	7B7	7/6	12SRK7	5/-	42	6/6	DAF91	4/6	EBC97	9/6	ECL105	10/3	EY81	15/-	PCF110	15/-	SP81	8/-	UM101	6/6
6B4G	20/-	6J6	3/6	7C5	22/6	14H7	9/6	50B5	6/6	DAF96	7/6	EBC98	9/6	ECL106	10/3	EY82	15/-	PCF111	15/-	SP82	8/-	UM102	6/6
6BS8	20/-	6J7M	8/6	7C6	15/-	19AQ5	5/-	50C5	6/3	DOCC90	20/-	EBC99	9/6	ECL107	10/3	EY83	15/-	PCF112	15/-	SP83	8/-	UM103	6/6
6BA6	5/-	6J7G	6/-	7D5	8/-	20D1	10/-	50C6GT	31/-	DP33	8/-	EBC100	9/6	ECL108	10/3	EY84	15/-	PCF113	15/-	SP84	8/-	UM104	6/6
6BE6	5/-	6J7GT	7/6	7H7	6/6	20P2	14/-	50L6GT	8/-	DP70	9/-	EBC101	9/6	ECL109	10/3	EY85	15/-	PCF114	15/-	SP85	8/-	UM105	6/6
6BH6	9/-	6K6GT	8/-	7R7	13/-	20L1	20/-	75	9/6	DP91	4/-	EBC102	9/6	ECL110	10/3	EY86	15/-	PCF115	15/-	SP86	8/-	UM106	6/6

TRANSISTORS

2N2147	15/-	AC107	7/6	AD149	10/-	AF117	5/-	BC157	4/-	BFY51	4/-	NKT213	5/-	OA5	3/-	OA95	1/6	OC35	10/-	OC76	5/-	OC82D	5/-
2N2160	12/6	AC128	5/-	AD161	7/6	AF118	5/-	BC158	4/-	BFY52	4/-	NKT214	5/-	OA10	3/6	OA200	1/6	OC36	10/-	OC77	8/-	OC83	4/6
2N2369A	4/-	AC17	6/-	AD162	7/6	AF119	5/-	BC159	4/-	BFY53	4/-	NKT215	5/-	OA15	2/6	OA202	2/-	OC44	3/6	OC78	5/-	OC84	4/6
2N2926	2/6	AC18	5/-	AD163	7/6	AF120	5/-	BC160	4/-	BFY54	4/-	NKT216	5/-	OA20	2/6	OA210	2/-	OC45	3/6	OC79	5/-	OC85	4/6
2N3055	14/6	AC19	5/-	AD164	7/6	AF121	5/-	BC161	4/-	BFY55	4/-	NKT217	5/-	OA25	2/6	OA215	2/-	OC46	3/6	OC80	5/-	OC86	4/6
2N3819	7/-	AD140	8/-	AF116	6/6	BC109	2/6	BFY50	5/-			NKT218	5/-	OA30	2/6	OC23	5/-	OC75	5/-				

SEND S.A.E. FOR LIST OF 3,000 TYPES

Express Postage Insurance 9d per valve.

6,000 types in stock send for lists, S.A.E.

R.S.T.

"Renowned for Service"

BLACKWOOD HALL, WELLFIELD ROAD., STREATHAM, S.W.16

Tel. 769-0199/1649. Open to callers 9 a.m.—5.30 p.m. Closed Saturday 1.00—2.30 p.m.

INTRODUCING THE FANE 'CRESCENDO' 12

SUPER SENSITIVE
12" LOUDSPEAKER

Rec. Retail Price **£28.15.0**

Incorporating the Fane specially developed High Power Voice Coil

HIGHER SENSITIVITY
HIGHER ACOUSTIC OUTPUT
HIGHER POWER HANDLING
WIDER FREQUENCY RANGE

Available in alternative models

TYPE 'A' (General Purpose)
Flux Density 20,000 lines
Power Handling **100 Watts**
(continuous)
Frequency Response 30-16,000 Hz
Voice Coil Impedance 8 or 15Ω
Weight 18 lb
Voice Coil Diameter 2 in.
Cone: Single with
Plastiflex surround

TYPE 'B' (Bass Guitar, etc.)
Flux Density 20,000 lines
Power Handling **75 Watts**
(continuous)
Frequency Response 40-10,000 Hz
Voice Coil Impedance 8 or 15Ω
Weight 18 lb
Voice Coil Diameter 2 in.
Cone: Single with
Plastiflex treated surround

ALSO AVAILABLE 'CRESCENDO' 15 Full Frequency Range £35.18.0

Manufacturers' enquiries to—

FANE ACOUSTICS LTD. Hick Lane, Batley, Yorks.

Sole Distributors to wholesale and retail trades

LINEAR PRODUCTS LTD. Electron Works, Armley, Leeds.



BAKER 12in. MAJOR £9

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 6 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle 19 x 12 1/2 in. and instructions. £11.10.0

Latest Catalogue 1/- with enclosure plan

Baker Reproducers Ltd
Bensham Manor Road Passage, Thornton Heath, Surrey.
Telephone 01-684-1665

multi-drawer storage units

NEW! HANDY! TIDY! I-N-T-E-R-L-O-C-K-I-N-G

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots—removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins x 2 1/2ins x 2 1/2ins)

Usually 2/6 each. Our Price 24/- dozen

DOUBLE UNITS (5ins x 4 1/2ins x 2 1/2ins)

Usually 4/6 each. Our Price 40/- dozen

PLUS QUANTITY DISCOUNTS!

Orders £5 and over Deduct 1/- in the £

Orders £10 and over Deduct 1/6 in the £

Orders £20 and over Deduct 2/- in the £


Packing/Postage/Carriage: Add 6/- to all orders under £3. Orders £3 and over, Packing/postage/carriage free

Quotations for Larger Quantities

IVORYET LIMITED

(Dpt. PW10) 31 ALBERT RD. HENDON - LONDON NW4

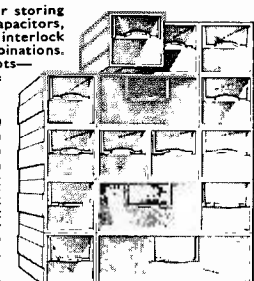A place for everything Everything in its place!



TECHNICAL TRAINING

*in radio television
and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- Radio operator Certs
- General Certificate of Education, etc.

Now available Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL
CORRESPONDENCE SCHOOLS**

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS

AGE.....12/70

INTERNATIONAL CORRESPONDENCE SCHOOLS

Going Back

—continued from page 674

RADIO BROADCASTING NEWS

Fourth Week Broadcasting

March 26, 1922

KDKA Edition. Vol. 1. No.



Early copy of KDKA'S "Radio Times".

mission on September 19th, 1921. After that stations were opening every few days and within a year over a hundred stations were regularly broadcasting and a million receivers had been sold.

Even before the opening of WBZ, KDKA had broken ground with all sorts of transmissions. On January 2nd 1921 a religious service was relayed from a local church, on March 4th the inaugural address of the newly elected President Harding was read out on the station at the same time as the speech proper was being made in Washington. On April 11th the first sports commentary was carried, a boxing match, and on May 19th the first farm programme was started.

For the first six months programmes originated from the transmitter room, there was little need for a studio as most programmes consisted of either gramophone records or were relays from outside points. In May, however, regular live music was added to the schedule and although these at first took place in a small auditorium in the building, room resonance proved so serious that they were transferred to a tent on top of the main building and it was not until October 3rd that the first proper studio was built.

Dr. Frank Conrad however was a true innovator and having seen that the station was properly established he turned his interest to the short-wave bands. In conjunction with a few other amateurs he began some of the first tests on wavelengths below 100 metres, then considered of little value. In August 1922 8XK began relaying the programmes of KDKA and a year later all programmes were relayed on short waves and these were heard in Great Britain.

Conrad died in 1941 but in the intervening years did a great deal of research into f.m. and television. Others were also working in these fields but Dr. Conrad's contribution was considerable and he was the holder of innumerable patents.

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.

SINCE this series started we have had many requests for particular circuits. The less serious have asked for colour TV circuits and stereo systems but the vast majority have asked for simple circuits that are functional when finished.

One such request from a reader in Manchester asked for a megaphone or loudhailer suitable for use with a car battery. At first this seemed almost impossible, bearing in mind our limitations on a maximum of twenty components and twenty shillings, but after a little thought the circuit in Fig. 1 was evolved. Let me state straight away that the loudspeaker and the various items needed to form the cabinet and chassis are not included in the price and even so it will be a tight squeeze to stay under our price limit.

THE CIRCUIT

A careful study of the circuit in Fig. 1 will show that it is basically a mating together of two previously published circuits, the Gramophone Amplifier and last month's General Purpose Preamplifier; there are some minor differences but the basic circuit is the same. The amplifier produces an output in the order of 1 watt—quite adequate for a megaphone.

Megaphones—or loudhailers as they are often called—are designed so that both high and low frequencies are not only unnecessary but actually undesirable. The microphone used is one of the balanced armature earpieces that we used in our intercom circuit some time ago. These used to be used in military telephones and are not only very sensitive and cheap but have an ideal frequency response for our requirements here. Since there is little bass content in the voice and little output from the microphone in this region, a high value coupling capacitor is unnecessary, a $0.5\mu\text{F}$ one was used in the prototype, low value electrolytics ($1\mu\text{F}$ to $5\mu\text{F}$) are however much smaller physically and cheaper and they could be used instead. In this case the negative connection would go to the microphone.

One of the problems in building a megaphone is acoustic feedback, that is the sounds of the loudspeaker getting back into the microphone and causing a "howl-round". This problem can be reduced by attenuating the upper frequencies and C2, connected between the base of Tr1 and the negative line, achieves this.

R1 provides base bias. Note that if an electrolytic is used for C1 the value of R1 may have to be altered to allow for leakage. R2 acts as the collector supply and load and the output is coupled via C3 to the volume control VR1. C3 is $0.5\mu\text{F}$ and the same rules apply to it as to C1, that is an electrolytic could be used in its place.

C4 acts as a d.c. blocking capacitor and feeds the

No. 20

MEGAPHONE

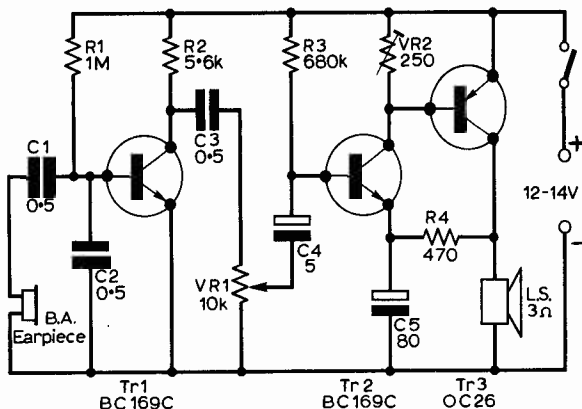


Fig. 1.: The circuit of the "Take 20" Megaphone

signal to the second transistor, Tr2 which, like Tr1, is a BC169C. The emitter of Tr2 is connected to the negative line via a 470Ω resistor connected through the loudspeaker; this tends to d.c. stabilise the conditions in the output stage. A positive feedback loop exists and it is essential that C5 is included to decouple the audio. VR2 is a small preset potentiometer which acts as the collector load, this sets the quiescent current through the output stage, Tr3. An OC26 has been specified for Tr3 but in fact almost any germanium power transistor would do—some of those available as unmarked surplus types would do well here.

The loudspeaker impedance is not all that important and a 3Ω type has been specified here only because these are more common than others, it is however essential that it has a cone diameter of over 6in. Speakers with smaller diameters will have their cones biased one way by the quiescent current through the output transistor and whereas this is acceptable on larger speakers it will cause intolerable distortion in smaller types.

The power supply is nominally 12V and the internal impedance of this will usually mean that no decoupling is needed, however, if stability problems arise a $250\mu\text{F}$ 16V capacitor connected across the two supply rails will probably cure this.

CONSTRUCTION

As the loudspeaker has to be fairly large it will be difficult to build a handheld unit and in any case it is far simpler to build the amplifier into the loudspeaker cabinet. Tr3 must be heat sunk. VR2 requires setting only once; before switching on set it to *minimum* resistance (so Tr3 base and emitter are shorted) and after applying the supply current increase this slowly until signals are relatively undistorted—increasing beyond this point will only raise the quiescent current.

In the region of high quiescent current the quality is good but Tr3 will become very hot and may blow, so care should be taken with the setting. ■

MAKE 5 DIFFERENT TRANSISTOR RADIOS Last 250




TOTAL BUILDING PRICE 39/6

Amazing Radio Construction set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed.

Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loud-speaker, personal

phone, knobs, screws, etc., all you need. Box size 14" x 10" x 2" (parts avail. separately). Send only 39/6 + 4/6 P. & P. Money back guarantee. Makes exciting Christmas Present.

REAL WORKING ELECTRONIC ORGAN

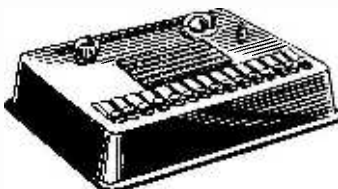

ONLY 55/-

simple as a.b.c. to make. Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low building price. **ONLY 55/- + 4/6d. P. & P.** for all parts, including case, loud-speaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, (but full) instructions, etc. etc. uses standard PP3 battery (parts available separately) *Nicely boxed makes thrilling Christmas present.* Have all the pleasure of making it yourself, finish with an exciting gift for someone. Money back guarantee.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13½ x 10 x 2½. Uses standard battery. You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. *Take it anywhere—play it anywhere.*

NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as


"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS—TEST THEIR MENTAL ABILITY, ETC. WITH THIS ASTONISHING ELECTRONIC BRAIN-BOX



ONLY 57/6

puta your friends to a very lively test. It gives out full and finish signals the weakest to strongest person. **THE ELECTRONIC MAZE tests the mental ability of the player** because it uses psychology with an electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof, uses standard battery. Size 18" x 12" x 6" (Max.) You can play all these games and more beside after building the "Brainbox". **WE GUARANTEE THAT ANYONE FROM NINE TO NINETY CAN EASILY ASSEMBLE ALL THESE PROJECTS IN UNDER ONE HOUR!** You can't go wrong, no soldering, you get pictorial, easy as a.b.c. step-by-step simple instructions. **ONLY 57/6d + 6/6d P. & P.** for all parts including chassis, switches, stylus, signaling lights, wire, nuts, screws etc. etc. Uses standard U2 battery. (PARTS AVAILABLE SEPARATELY) **FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.** **MONEY BACK GUARANTEE.**

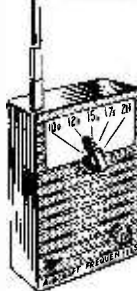EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



ONLY 47/6

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach, ground control, tower. Hear for yourself the disciplined voices hiding tensions on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. **CLEAR AS A BELL.** This fantastic fully transistorized instrument can be built by anyone with a minimum of under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4½ x 3 x 1½. All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables). **NO CONNECTIONS WHATSOEVER EVER NEEDED.** Use indoors or outdoors. **THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN.** **SEND NOW. ONLY 47/6** for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately). **NICELY BOXED MAKES THRILLING CHRISTMAS PRESENT.** Money back guarantee.

FIND BURIED TREASURE! TREASURE LOCATOR FULLY TRANSISTORIZED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different designs, carrying out actual field tests with prototypes, our design team have come up with this real winner.

This fully portable transistorized metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used). **FINDS GOLD, SILVER, LOSE COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC.** Outdoors or indoors. *Extremely sensitive, will signal presence of certain objects buried several feet below ground!* No knowledge of radio or electronics required. *Can be built with ease in one short evening by anybody from nine years of age upwards,* with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is easy as A.B.C. Fully transistorized—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13½ x 10 x 2½. Great demand expected at this remarkably low price—**ORDER WHILE PRESENT STOCKS LAST.** All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. **ONLY 47/6d + 6/6d P. & P.** (Telescopic handle as illustrated 25/- extra). Parts available separately. Nicely boxed makes fantastic Christmas gift! Made up looks worth £15! Money back guarantee.

ONLY 47/6




UNIQUE RADIO FOR BEDROOM OR OFFICE

No batteries, no electricity, never wears out

Tune in your favourite programmes or the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode which evolved from wartime radar. Never buy a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4½ x 2½ x 1½ in beautiful case. **ONLY 7 CONNECTIONS AND IT'S WORKING.** No soldering necessary. **CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES!** Ideal for absolute beginner from 8 years of age upwards.

ONLY 19/6

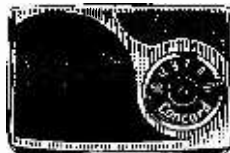
SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS ONLY 19/6d + 2/6d P. & P. for all parts including beautiful case, germanium semi-conductor, tuning condenser, personal phone, wire, nuts, screws. **SIMPLE AS A.B.C. INSTRUCTIONS.** Will make an exceptional Christmas present. (Parts available separately). Money Back Guarantee.



SHORTWAVE TRANSISTOR RADIO

Can be built in one evening

At last! After trying countless circuits searching for easy build, work-first-time short wave. Giving advanced world-wide performance, this "Sky Hunter". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorized (no valves). Size only 3½ x 4½ x 1½. As tremendous demand anticipated price held to only 45/- + 3/6 P. & P. for all parts incl. Cabinet, screws, instr. etc. (Parts available separately). Money back guarantee.

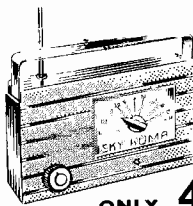

ONLY 45/-

AMAZING TRANSISTORIZED CIGARETTE RADIO

Yes, a perfectly ordinary packet of cigarettes! But watch your friends' astonishment on hearing its range of stations loud and clear. Holds 10 cigarettes yet conceals sensitive, fully transistorized circuit (including tiny battery). A young boy can assemble it in under 2 hours. No soldering. Only 16 connections to make. **ALL PARTS** including semi-conductors. Simple as ABC Illustrated Plans, etc. **ONLY 29/6** plus 2/6 post, etc. Parts available separately. Money back guarantee.




TOTAL BUILDING PRICE

29/6



CONCORD ELECTRONICS LTD (Dept. PW14) 8 Westbourne Grove, London W.2. (Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema) Callers 9-6 Inc. Sat.

Project 60

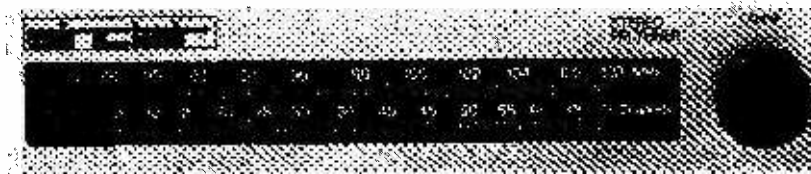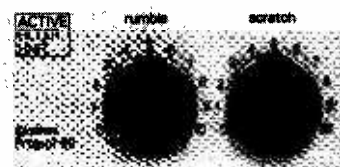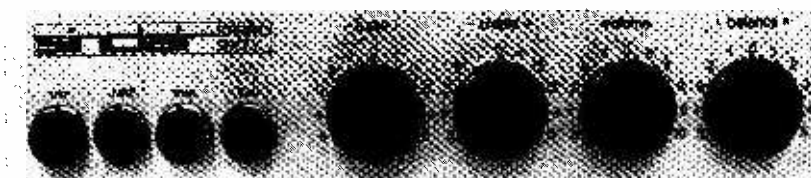

the world's most advanced high fidelity modules

With the introduction of an entirely new and original high fidelity stereo F.M. tuner, the Project 60 range can be said at this stage to be complete. It offers the constructor a most attractive choice of modular arrangements whereby a high fidelity system can be selected to suit the user's personal requirements. Equally, it is possible to use any Project 60 modules separately or partially grouped and so benefit greatly from the flexibility in use these modules afford. The chart below shows some of the most popular applications for constructors to assemble. The Project 60 manual (free with the modules) suggests others as well and its 48 pages are packed with valuable information. The new tuner, for example can be used with any good high fidelity system as well as Project 60.

Project 60 now falls into four interdependent groups: - 1. The Z.30 and Z.50 amplifiers which have only 0.02% distortion at all output levels and are useful in a wide variety of other applications. 2. The control units comprising the Stereo 60 preamp and control unit and the Active Filter Unit (A.F.U.) with which both high pass and low pass filtering can be introduced between control unit and power amplifiers. 3. The Stereo F.M. tuner as described opposite, and 4. The power supply units PZ.5.

PZ.6 and PZ.8. For most requirements when using Z.30 power amplifiers, the PZ.5 will be perfectly adequate; if low efficiency (high quality) loud speakers are used, the PZ.6 stabilised power supply unit will be used. The PZ.8 will be needed with Z.50s which can be used for any Project 60 system.

Project 60 modules incorporate some of the most advanced circuitry in the world to achieve unsurpassed standards of high fidelity and modern manufacturing techniques enable these modules to be sold at exceptionally attractive prices. Assembling the modules requires no skill or previous experience since the manual supplied with the modules explains clearly how everything can be done with nothing more than the simplest of domestic tools.

Project 60 manuals

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

System	The Units to use	In conjunction with	Cost of Units	+ Project 60 tuner
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6	
B Simple battery powered record player	Z.30	Crystal pick-up, 12V or more battery supply and volume control	89/6	
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Volume control etc.	£9.9.0	£34.9.0
D 20+20 watts R.M.S. stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, F.M. tuner etc.	£23.18.0	£48.18.0
E 20+20 watts R.M.S. stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc. All dynamic speakers	£26.18.0	£51.18.9
F 40+40 watts R.M.S. de-luxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6	£57.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with converter, or 45V d.c., controls	£5.9.6	
H Indoor P.A.	One Z.50, PZ.8 and mains transformer	Microphone, guitar, heavy duty speakers etc., controls	£17.8.6.	
J High pass and low pass filters	A.F.U.	D, E or F as above	£5.19.6	

sinclair

Sinclair Radionics Limited, 22 Newmarket Road, Cambridge

Telephone (0223) 52731

Z.30 & Z.50 power amplifiers

The Z.30 together with the Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are the same physical size and may be used with other units in the Project 60 range equally well. For operating from mains, for the Z.30 use PZ 5 for most domestic requirements, or PZ 6 if you have very low efficiency loudspeakers. For Z.50, use the PZ 8 described below.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms from 40 volts 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response 30 to 300,000 Hz \pm 1dB

Distortion 0.02% into 8 ohms

Signal to noise ratio better than 70 dB unweighted

Input sensitivity 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size $3\frac{1}{2} \times 2\frac{1}{4} \times \frac{1}{2}$ ins.



Z.30

Built, tested and guaranteed with circuits and instructions manual

Z.50

Z.30

Z.50

Built, tested and guaranteed with circuits and instructions manual

89/6

109/6

Stereo 60 pre amp/control unit

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS

● Input sensitivities — Radio — up to 3mV, Mag. p.u. — 3mV; correct to R.I.A.A. curve \pm 1dB; 20 to 25,000Hz Ceramic p.u. — up to 3mV; Aux. — up to 3mV.

● Output — 250mV.

● Signal-to-noise ratio — better than 70dB.

● Channel matching — within 1dB.

● Tone controls — TREBLE +15 to —15dB at 10kHz; BASS +15 to —15dB at 100Hz.



● Front panel — brushed aluminium with black knobs and controls.
● Size $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ ins.


Built, tested and guaranteed

£9.19.6

Active Filter Unit

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The Sinclair A.F.U. is suitable also for use with any other amplifier system.

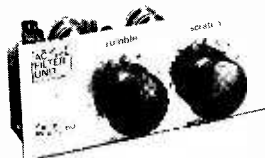Two stages of filtering are incorporated — rumble (high pass) and scratch (low pass). Supply voltage — 15 to 35V. Current — 3mA. H.F. cut-off (—3dB)



variable from 28kHz to 5kHz. L.F. cut-off (—3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output

Built, tested and guaranteed

£5.19.6

Power Supply Units

The units below are designed specially for use with the Project 60 system of your choice.

Illustration shows PZ 5 power supply unit to left and PZ 8 (for use with Z.50s) to the right. Use PZ 5 for normal Z.30 assemblies and PZ 6 where a stabilised supply is essential.


PZ-5 30 volts unstabilised £4.19.6

PZ-6 35 volts stabilised £7.19.6

PZ-8 45 volts stabilised

(less mains transformers) **£5.19.6**

PZ-8 mains transformer £6.19.6

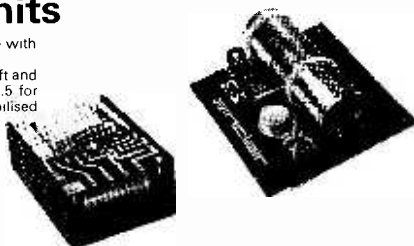

GUARANTEE If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

sinclair

Stereo FM tuner



first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time the principle has been applied to an FM tuner with fantastically good results. By the inclusion of other original features such as varicap diode tuning, printed circuit coils and an I.C. in the specially designed stereo decoder, the tuner has an unsurpassed specification, which also incorporates a squelch circuit for silent tuning between stations, A.F.C. and A.G.C. Sensitivity is such that good reception becomes possible in difficult areas, foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of high fidelity, this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. Although the tuner is intended primarily for use with a Project 60 system, it can be used to advantage with any other high fidelity system. It is easily mounted into any cabinet as shown in the manual supplied with it.

Specifications

Number of transistors 16 plus 20 in I.C.

Tuning range 87.5 to 108 MHz

Capture ratio 1.5dB

Sensitivity 2μV for 30dB quieting
7μV for full limiting

Squelch level 20μV

A.F.C. range \pm 200 KHz

Signal to noise ratio > 65dB

Audio frequency response 10Hz—15kHz (\pm 1dB)

Total harmonic distortion 0.15% for 30% modulation

Stereo decoder operating level 2μV

Pilot tone suppression 30dB

Cross talk 40dB

I.F. frequency 10.7 MHz


Output voltage 2 x 150mV R.M.S.

Aerial Impedance 75 Ohms

Indicators Mains on, Stereo on, tuning indicator

Operating voltage 25-30 VDC

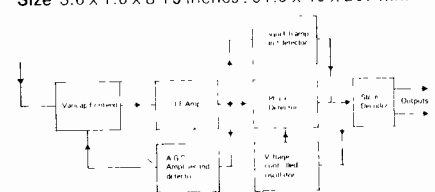Size 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: £25 built and tested. Post free.

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge

Please send



NAME

ADDRESS

for which I enclose cash/cheque money order

PW. 12A

Sinclair IC-10

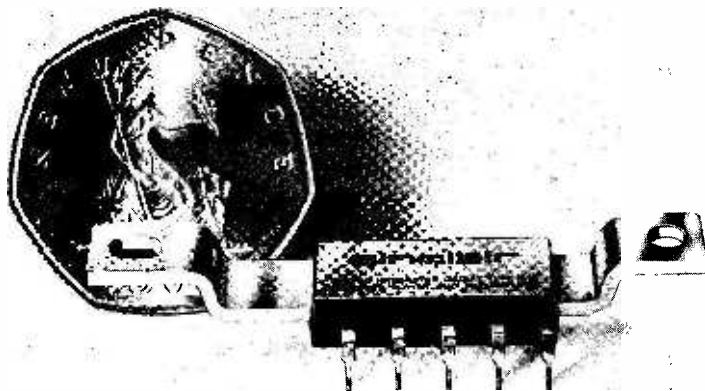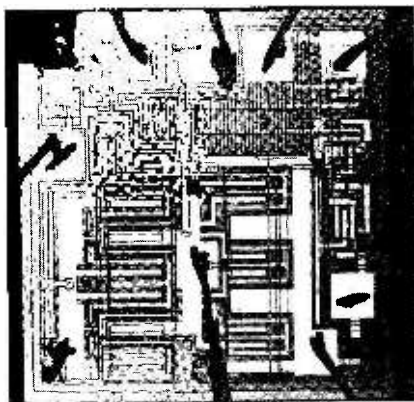

the world's most advanced high fidelity amplifier

Specifications

Output 10 Watts peak, 5 Watts R.M.S. continuous
 Frequency response 5 Hz to 100 KHz \pm 1dB
 Total harmonic distortion Less than 1% at full output
 Load impedance 3 to 15 ohms
 Power gain 110dB (100,000,000,000 times) total
 Supply voltage 8 to 18 volts.
 Size 1 x 0.4 x 0.2 inches
 Sensitivity 5mV
 Input impedance Adjustable externally up to 2.5 M ohms

Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a full guarantee on every IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

SINCLAIR

IC-10 with IC-10 manual
Post free.

59/6

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge

Please send

NAME

ADDRESS

for which I enclose cash/cheque money
order

PW. 12A

sinclair


Q.16 High fidelity loudspeaker

Developed out of the revolutionary and much praised design of the original Sinclair Q 14 comes this more advanced version to meet the requirements of even greater numbers of high fidelity enthusiasts. The Q.16 employs the same well proven acoustic principles in which a special driver assembly is meticulously matched to the physical characteristics of the uniquely designed housing. In reviewing this exclusive Sinclair design, technical journals have been loud in their praise for it and it comfortably stands comparison with very much more expensive loudspeakers. The shape of the Q.16 enables it to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures, and with its improved styling, the Q.16 presents an entirely new and attractive appearance. A solid teak surround is used with a special all-over cellular black foam front chosen as much for its appearance as for its ability to pass all audio frequencies unimpaired.

The Q.16 is compact and slim and is the ideal shelf-mounted speaker, and brings genuine high fidelity within reach of every music lover.

Specifications

Construction:	A sealed seamless sound or pressure chamber is used with internal baffle, all of materials carefully chosen to ensure freedom from spurious tone coloration.
Loading:	Up to 14 watts R.M.S.
Input impedance:	8 ohms.
Frequency response:	From 60 to 16,000Hz. as confirmed by independently plotted B & K curve.
Driver unit:	Specially designed high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension. Excellent transient response is achieved.
Size and styling:	9 $\frac{1}{2}$ " square on face \times 4 $\frac{3}{4}$ " deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
Price:	£8 19 6.

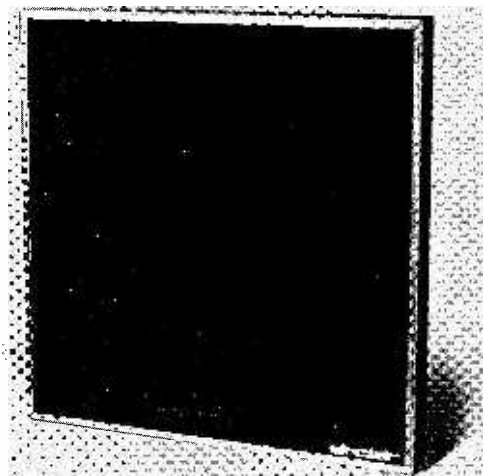

Micromatic Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation very much easier than with many larger sets. The plug-in high fidelity type magnetic earpiece which matches exactly with the output of the Micromatic provides wonderful standards of reproduction both for speech and for music. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.


Specifications

Size:	1 $\frac{1}{8}$ " \times 1 $\frac{7}{8}$ " \times $\frac{1}{2}$ " (46 \times 33 \times 13mm).
Weight including batteries:	1 oz. (28.35gm) approx.
Tuning:	Medium wave band with bandspread at higher frequency end.
Earpiece:	High-fidelity magnetic type.
Battery requirements:	Two Mallory Mercury Cells, type R.M. 675, for long working life.
Case:	Black plastic with anodised aluminium front panel, spun aluminium dial.
Controls:	Tuning dial, and on/off switching by means of earpiece plug.
Price:	Available in kit form complete with earpiece, case, instructions and supply of solder in fitted pack. 49/6. Ready built, tested and guaranteed. 59/6.



H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

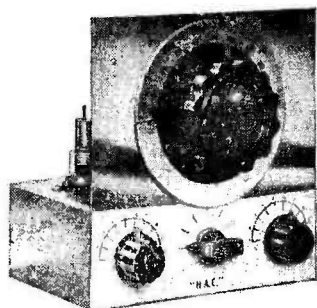

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hains, etc.

NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price 66/- (post & packing 4/-). Customer writes: "Australia, India and America at loud volume." "I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world." Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays. 7 element 45/-, 11 element 52/6, 14 element 60/-, 18 element 70/-, Wall Mounting with Cranked Arm. 7 element 65/-, 11 element 75/-, 14 element 82/6, 18 element 90/-, Chimney Mounting Arrays complete. 7 element 80/-, 11 element 87/6, 14 element 95/-, 18 element 105/-, Complete assembly instructions with every aerial. Low Loss co-axial cable 1/8 yd. King Teleboosters—Labgear U.H.F. Boosters from 75/-, Belling Lee "Concord" all Band V.H.F./U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8/-, Accessories 3/-, C.W.O. or C.O.D.

BBC-ITV-FM AERIALS




B.B.C. (Band 1) Loft. 25/-, Wall S/D. 32/6, 'H' array 60/-, I.T.V. (Band 3) 5 element loft array 45/-, 7 element 55/-, Wall mounting 5 element 65/-, Combined BBC/ITV loft 1 + 5 55/-, 1 + 7 67/6, Wall mounting 1 + 5 77/6, Chimney mounting 1 + 5 90/-, Preamps from 75/-, Combined BBC/ITV/BBC2 Aerials. 1 + 5 + 9 80/-, 1 + 5 + 14 90/-, 1 + 7 + 14 100/-, Available loft only. F.M. Radio Loft S/D 19/6, 'H' 38/6, 3 element array 57/6, Standard co-axial cable 1/- yd. Coax plugs 1/8, Outlet boxes 6/-, Diplexer crossover boxes 17/6, p.p. Aerials 8/-, accessories 3/-, C.W.O. or C.O.D. (min. C.O.D. charge 3/6). 1/- for fully illustrated Lists.

Callers welcomed—open all day Saturday.

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE,
LONDON ROAD, MITCHAM,
SURREY O1-648 4884

THE RADIO CONSTRUCTOR

IN NOVEMBER ISSUE

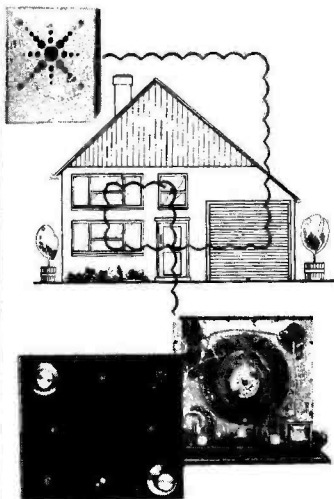

THE 'DOORCOM'

This simple but effective transistorised unit allows loudspeaker communication between one Master and two Slave positions. If desired, both Slave positions may be switched into the system at the same time. Printed circuit board assembly.

★ SPECIAL WORKSHOP ★
EQUIPMENT OFFER

PLUS

● MANY OTHER
PROJECTS AND
FEATURES

● DATA SHEET No. 44

ON SALE NOW 3/6

Copies may also be obtained
direct from the Publishers
4/- including postage.
Published by:

Data Publications Ltd.
57 Maids Vale, London, W.9

THE RADIO CONSTRUCTOR

THORNBURY TRADE DISPOSALS BRADFORD

£5 TELEVISIONS £5

Delivered anywhere in Great Britain

17" 12 channel. Complete & tested. Excellent condition
Carriage and ins. £1

17" Untested T.V.s 12 channel. 30/- Carriage £1. All makes

TUBES! TUBES!

Guaranteed 6 months

17" & 19" All makes 30/-
23" 50/-
19" Bonded 70/-
23" Bonded 90/-

Plus 10/- carriage

SPEAKERS P.M. 3, Ohm. PERFECT CONDITION EX
T.V. 5" Round 2/-, 6" x 4" 2/-, 7" x 4" 4/-

VALVES EX EQUIPMENT

Guaranteed 6 months

APR12	1/-	PCC84	1/6	PL36	4/6	688	1/-
EB91	3d	PCF80	1/6	PL81	3/6	68W7	2/-
EBF89	2/6	PCC89	2/6	PY81	1/-	6U4	3/6
EC82	2/6	PCL85	4/6	PY800	3/-	20D1	2/6
ECL80	1/-	PCL84	3/6	PY82	4/6	20P1	4/6
EF183	2/6	PCL82	3/6	PY33	4/6	20P3	2/-
EF184	2/6	PCF86	3/6	U191	3/6	30PL1	4/6
EY86	3/6	PCL83	2/6	6F23	3/6	30P12	4/-
						30F5	2/3

On 2 valves or more 6d. postage & packaging

UHF TUNERS TO SUIT MOST MODELS

i.e. FERGUSON 850 900 Chassis
K.B. G.E.C. etc. 50/-, P. & P. 10/-

VHF TUNERS MOST MAKES

20/- delivered. (Discount for quantity)

Dept. T.S.

THORNBURY TRADE
DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford, Tel. 665670

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

JOHNSONS (RADIO)
St. Martin's Gate, Worcester
WR1 2DT

KEYNECTOR

The safe quick
way to connect
electrical
equipment
to the
mains



Send for full details

EB INSTRUMENTS

49-53 PANCRAS ROAD, LONDON NW1

Tel: 01-837 7781

BRAND NEW FULLY GUARANTEED TRANSISTORS

SEND
FOR

NEW LIST

NEW PRICES

1N4001	1/6	AAZ12	4/-	BPY10	19/6
1N4002	1/6	AAZ13	2/6	B8X20	3/6
1N4003	2/-	AAZ17	2/-	B8X21	7/6
1N4004	2/-	AC126	5/-	B8X22	5/-
1N4005	2/6	AC127	5/-	B8Y27	4/-
1N4006	3/-	AC127Z	10/-	B8Y28	6/-
1N4007	4/-	AC128	5/-	B8Y29	5/-
1N4009	1/6	AC153	4/-	B8Y50	5/-
1N4148	1/6	AC154	3/-	B8Y53	5/-
2G210	12/6	AC169	3/-	B8Y66	5/-
2G240	48/6	AC176	5/-	B8Y67	5/-
2G261	4/-	AC187	6/-	B8Y68	5/-
2G292	4/6	AC188	6/-	B8Y69	5/-
2G303	5/-	AC17	6/-	BY100	3/6
2G306	6/-	AC18	4/-	BY103	4/6
2G308	6/-	AC19	5/-	BY126	3/-
2G309	6/-	AC20	4/-	BY127	4/-
2G371	4/6	AC21	4/6	BY210	8/-
2G374	4/6	AC22	3/6	BY211	7/-
2G381	5/-	AC28	3/6	BY212	6/-
2G382	6/-	AC34	4/-	BY213	6/-
2G383	5/-	AC36	5/-	BY215	20/-
2N404	4/6	AC39	11/-	BY216	12/6
2N686	3/6	AC40	3/-	GET102	6/-
2N687	3/6	AD140	10/-	GET103	4/6
2N688	3/6	AD149	10/-	WFF102	8/6
2N706	2/-	AD161	7/6	MFF103	7/-
2N706A	2/6	AD162	7/6	MFF104	7/6
2N707	9/6	AF102	12/6	MFF105	8/-
2N708	3/-	AF114	6/6	OA5	3/-
2N914	4/6	AF115	6/-	OA7	4/-
2N916	4/6	AF116	6/6	OA9	4/-
2N918	7/6	AF117	5/-	OA10	5/-
2N919	4/-	AF118	12/6	OA47	2/-
2N920	5/-	AF124	6/-	OA70	2/-
2N922	8/6	AF125	5/-	OA71	2/-
2N930	5/6	AF126	4/-	OA73	2/-
2N1131	6/-	AF127	4/-	OA74	2/-
2N1132	6/6	AF139	6/-	OA79	2/-
2N1303	4/6	AF178	8/6	OA81	2/-
2N1304	5/-	AF181	8/6	OA85	2/6
2N1305	5/-	AF186	8/-	OA86	4/-
2N1306	5/-	AF239	8/-	OA90	2/-
2N1307	5/-	AF219	20/6	OA91	1/6
2N1308	6/-	AF211	12/6	OA95	1/6
2N1309	5/-	AF212	15/-	OA200	1/6
2N1613	4/6	ABY23	5/-	OA202	2/-
2N2147	15/-	ABY27	6/6	OA210	5/-
2N2160	12/6	ABY28	5/-	OA211	7/6
2N2287	20/-	ABY29	7/6	OA225	7/6
2N2646	10/6	ABY27	9/6	OA228	7/6
2N2904	6/-	ASZ21	8/6	OA229	9/6
2N2906	7/6	AUY10	19/6	OA231	9/6
2N2925	4/-	B3M	19/6	OA234	7/6
2N2926	2/6	BA110	5/-	OA238	8/6
2N3011	5/-	BAV31	2/-	OC18	8/6
2N3053	4/6	BC107	2/6	OC19	7/6
2N3054	10/-	BC108	2/6	OC20	19/6
2N3055	15/-	BC109	2/6	OC22	9/6
2N3702	2/6	BC113	5/-	OC23	10/-
2N3703	2/6	BC116	2/6	OC24	10/-
2N3704	3/6	BC118	7/6	OC25	7/6
2N3705	3/6	BC134	7/6	OC26	5/-
2N3707	3/-	BC135	6/-	OC28	12/6
2N3709	2/6	BC136	7/-	OC29	12/6
2N3710	2/6	BC137	8/-	OC25	10/-
2N3711	2/6	BC138	8/-	OC36	12/6
2N3730	10/-	BCY30	5/6	OC41	5/-
2N3731	12/6	BCY31	6/-	OC42	6/-
2N3734	2/6	BCY32	10/-	OC43	8/-
2N3819	7/-	BCY33	4/-	OC44	4/6
2N3820	17/6	BCY34	4/6	OC45	5/6
2N3823	17/6	BCY38	6/-	OC46	5/6
2N4058	8/6	BCY39	9/6	OC70	2/6
2N4561	3/-	BCY40	8/6	OC71	3/-
2N4286	3/-	BCY42	4/-	OC72	5/-
2N4288	3/-	BCY43	4/-	OC73	6/-
2N4289	3/6	BCY70	4/-	OC74	6/-
2N4290	3/-	BCZ11	7/6	OC75	5/-
2N4291	3/-	BC147	8/6	OC76	5/-
2N4292	3/-	BC145	2/6	OC77	8/-
40381	11/-	BC149	4/-	OC78	5/-
40382	12/-	BF152	6/-	OC81	5/-
58001	10/-	BF194	3/6	OC81D	4/-
58002	10/6	BF195	3/-	OC82	4/-
58003	9/6	BD124	12/6	OC83	5/-
58004	9/6	BDN3000	5/-	OC84	5/-
58005	14/-	RF115	10/-	OC82	10/-
58012	25/-	BF164	8/-	OC123	5/-
58013	20/-	BF158	6/-	OC139	5/-
58017	18/-	BF159	12/-	OC140	7/6
58034	12/6	BF163	8/-	OC141	15/-
58036	25/-	BF167	5/-	OC169	4/-
58020	9/-	BF173	6/-	OC170	5/-
58231	6/-	BF180	7/6	OC171	6/-
58232	7/6	BF181	7/6	OC200	7/6
58233	10/-	BFX30	6/-	OC201	9/6
58234	12/6	BFX88	5/-	OC202	12/6
58232	9/6	BFY20	12/6	OC203	7/6
58201	8/6	BFY50	4/6	OC204	8/-
58202	11/-	BFY51	4/6	OC205	12/6
58203	8/6	BFY52	4/6	OC206	15/-
58232	8/6	BFY53	3/6	OC207	15/-
58233	9/6	BFY64	8/6	OC207	18/6
AA178	8/6	BLY10	20/-	OC12	19/6
AAV12	5/-	BLV11	28/6	ORP60	8/-

INTEGRATED CIRCUITS

Type	I	12+	25+	100+	500+
UL914	8/6	7/7	7/3	6/9	6/6
UL923	12/6	11/9	11/-	10/-	9/3
SL403A	42/6	41/-	40/-	37/6	35/-
MC1303	52/6	48/-	45/-	40/-	35/-
MC1304	55/-	50/-	47/6	42/6	37/6
PA246	52/6	48/-	45/-	40/-	35/-

2N3055	15/-
Mullard 115watt	
Silicon Power	
25 + 13/-	
100 + 11/-	

2N3819	7/-
Texas F.E.T.	
25 + 6/-	
100 + 5/3	
500 + 4/9	

IN4003 and 4 2/-	
1 AMP 300-400v	
25 + 1/9	
100 + 1/6	
500 + 1/3	

2N2646	10/6
Motorola	
Unijunction	
25 + 8/9	
100 + 7/6	
500 + 6/9	

AF139	6/-
Siemens V.H.F.	
25 + 5/3	
100 + 4/6	
500 + 3/9	

AF186	8/-
Mullard V.H.F.	
25 + 7/-	
100 + 6/-	
500 + 5/-	

OC170	5/-
25 + 4/3	
100 + 3/6	

BY126	3/-
Mullard 800v	
1 amp Plastic	
25 + 2/6	
100 + 2/3	

BY127	4/-
1 amp 1000v	
1 amp Plastic	
25 + 3/3	
100 + 3/-	

BY213	5/-
Mullard 6a 200v	
25 + 4/-	
100 + 3/6	
500 + 3/-	

AF239	8/-
Siemens VHF	
25 + 7/-	
100 + 5/3	
500 + 5/-	
1000 + 4/-	

BC107/8/9	2/6 ea.
I.T.T. or Mullard	
25 + 2/3	
100 + 2/3	
500 + 1/9	

OA200/OA202	2/-
Silicon Diodes	
25 + 1/6	
100 + 1/3	
500 + 1/1	

OC28	12/6
Mullard Power	
25 + 1/1	
100 + 10/-	
500 + 8/6	

OC42	6/-
Mullard	
25 + 5/3	
100 + 4/9	
500 + 4/3	

OC71	3/-
Mullard	
25 + 2/3	
100 + 2/-	
500 + 1/9	

OC45	3/6
Mullard	
25 + 3/-	
100 + 2/6	
500 + 2/-	

OC75	5/-
Mullard	
25 + 4/3	
100 + 3/6	
500 + 3/-	

BCY38	6/-
Mullard	
25 + 5/3	
100 + 4/6	
500 + 4/-	

IN4001 and 21/6	
1 amp 100-200v	
25 + 1/4	
100 + 1/2	
500 + 1/-	

IN4005	2/6
600v 1 amp	
25 + 2/-	
100 + 1/9	
500 + 1/6	


ZENER DIODES	
400 MW 5%	
BZY88 Range	
All Voltages	
3.3v-33v	3/6

IN4006	
800v 3/1000v 4/3	
25 + 2/10	3/3
100 + 2/5	3/3
500 + 2/3	2/6

IN4007	
800v 3/1000v 4/3	
25 + 2/10	3/3
100 + 2/5	3/3
500 + 2/3	2/6

OC139	5/-
Mullard	
25 + 4/-	
100 + 3/3	
500 + 3/-	

OC140	7/6
Mullard	
25 + 6/-	
100 + 5/-	
500 + 4/-	

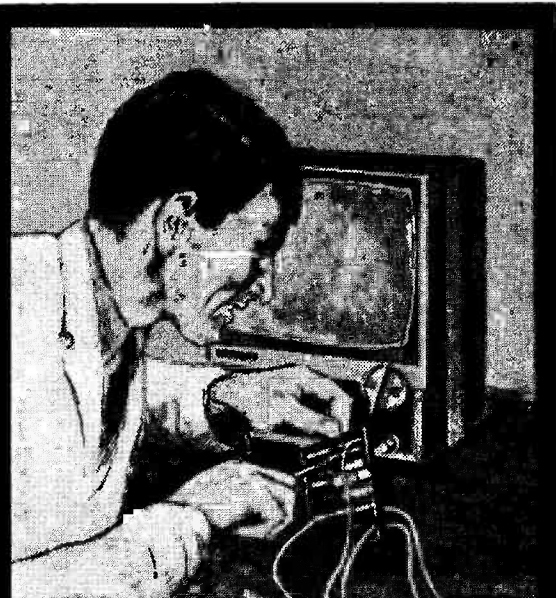

Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full-time 2 year College Diploma Course which gives a thorough fundamental training for radio and television engineers starts on 5th January, 1971.

The course includes theoretical and practical instruction on Colour Television receivers and is designed to cover the syllabus of the new City and Guilds Radio, Television and Electronics Technicians' Course. Pembridge College diplomas are awarded to successful students.

The way to get ahead in this fast growing industry — an industry that gives you many far-reaching opportunities—is to enrol now. Minimum entrance requirements Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

To: The Pembridge College of Electronics (Dept. PW17), 34a Hereford Road, London, W2. 5AJ

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME.....

ADDRESS.....

PLEASE NOTE MINIMUM

Quantity Prices 100+ Phone (01) 723 0401 Ex. 4. All listed devices are from stock at time of going to press Please add 1/6 post packing to your order

ORDER SHOULD BE 10/-

New Autumn List. New devices, New prices. Ask for List 36. Send for free copy today! Discounts 10% on 12+ any one type 15% on 25+ any one type

HENRY'S RADIO

Mail Order Dept. Components Organ Dept.
303 EDGWARE ROAD, LONDON W2
Telephone: 01-723 1008 9

DISCOSOUND



DISCOSOUND 40 PRE-AMP

The Discosound 40 offers the same specification as the D.J. Disco Amp without the power output stage. Size 16in x 7in x 7in. Self powered and ideal for use with the Discosound 100 Power Amplifier below and one of the outstanding features is that it is capable of running ten of these Power Amplifiers (Total 1,000W).

PRICE £40.10.0 inc. P. & P.


DISCOSOUND 100 POWER AMPLIFIER



A 100W RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response 20-20,000Hz ± 2dB. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound 40, or can be used with any other high quality pre-amp control unit. Completely built and tested on steel Chassis.

PRICE £49.10.0 inc. P. & P.

DJ70S INTEGRATED MIXER- AMPLIFIER

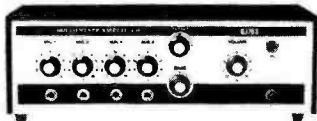

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70W R.M.S.), a frequency response (30-20,000Hz ± 3dB) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs, etc., or anywhere that high quality high output is required. Size: 15in x 5in x 6in.

PRICE £63.0.0 inc. P. & P.

Also available DJ105S 30W PA Amplifier. Similar specification to above.

PRICE £41.0.0 inc. P. & P.

For full details of these and all Discosound Products write direct to:-

DISCOSOUND,

122 BALLS POND ROAD, LONDON, N.1.
Telephone: 01-254 5779

Full money back guarantee if returned within 10 days.
All Discosound Products are guaranteed for 12 months.
Demonstrations given at any time.

VALVES

**SAME DAY SERVICE
NEW! TESTED! GUARANTEED**

SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6, DAF96, DF96, DK96, DL96, 4 FOR 29/-.


1A7GT 7/6	30C1 6/6	DL94 6/9	EM34 14/6	PCL85 9/-	URM1 10/6
1H5GT 7/8	30C15 13/-	DL96 7/8	EM80 8/3	PCL86 8/3	UBF80 5/9
1N5GT 7/9	30C17 13/-	DY86 5/9	EM81 8/3	PCL88 14/6	UBF89 6/9
1R5 5/9	30C18 16/6	DY87 5/9	EM84 6/9	PCL800 15/6	UCC84 7/-
185 4/3	30F5 15/9	EAC80 6/6	EM87 7/6	PEN44 8/6	UCC85 7/3
1T4 2/9	30FL12 12/9	EAF42 10/-	EY61 7/3	PEN36C14/-	UCF80 7/6
384 5/9	30FL13 12/9	EB01 8/3	EY86 6/6	PFL20011/9	UCH42 12/6
3V4 6/9	30FL14 14/-	ECB3 8/-	EZ40 8/-	PL81 9/3	UCL81 6/6
5Y3GT 6/-	30L1 6/6	EB41 10/6	EZ41 8/-	PL81 9/3	UCL82 7/-
5Z40 7/6	30L15 13/-	EBF80 6/9	EZ80 4/6	PL81A 10/3	UCL83 11/-
6/30L2 11/9	30L17 14/9	EBF89 6/3	EZ81 4/6	PL82 6/-	UF41 10/6
6AL5 2/3	30P4 13/-	EC081 3/9	GZ39 8/9	PL83 6/6	UF85 6/9
6AM6 2/9	30P12 13/9	EC082 4/9	GZ34 9/9	PL84 6/6	UF89 6/9
6AQ5 5/3	30P19 13/-	EC083 7/-	KT41 15/6	PL500 13/-	UL41 12/-
6AT8 4/6	30PL1 12/9	EC085 5/9	KT61 9/9	PL504 12/6	UL44 20/-
6BA6 4/6	30PL13 14/6	EC084 12/-	KT66 16/9	PL508 23/6	UL44 7/-
6BE6 4/9	30PL14 14/-	ECF80 6/-	LN329 14/6	PM84 7/6	UM80 5/-
6BJ6 8/6	35L6GT 8/9	ECF82 6/-	N78 17/6	PX25 23/6	UM84 4/6
6CD6G 22/-	35W4 4/6	ECB35 6/-	P61 10/-	PY32 10/-	UY41 7/6
6F14 9/-	36Z4GT 5/-	ECB42 12/9	PAB080 7/-	PY33 10/-	UY85 5/9
6F23 13/9	180BE 13/6	ECB81 5/9	PC86 10/3	PY81 5/3	VP48 15/6
6F35 12/6	607 8/6	ECB83 5/3	PC88 10/3	PY82 5/3	W119 7/-
6J5G 4/9	6063 12/6	ECB84 7/6	PC88 8/6	PY83 5/9	Z77 4/6
6K7G 2/6	AC/VP215/6	ECB80 7/-	PC97 8/-	PY88 6/9	Transistors
6K8G 8/6	AZ31 9/6	ECL82 6/9	PC900 7/6	PY800 7/6	AC107 3/6
6M6 8/6	B349 13/-	ECL86 8/-	PC84 6/6	PY801 7/6	AC127 2/6
6V8GT 6/6	B729 12/6	EF37A 6/6	PC85 6/-	R19 6/6	AD140 7/6
6X4 4/9	ECB35 13/6	EF39 4/9	PC88 8/-	R20 12/6	AF116 3/-
6X5GT 5/9	CL33 18/6	EF41 11/9	PC89 9/9	SC2150A	AF117 4/-
10F18 7/-	CY31 6/9	EF80 4/6	PC189 9/9	U25 13/-	AF125 3/6
10F13 12/-	DAC39 7/3	EF85 6/3	PC805 13/-	U26 12/-	AF127 3/6
12AH8 45/-	DAF91 4/3	EF86 6/3	PC86 6/6	U26 12/-	AF127 3/6
12AT7 3/9	DAF96 7/3	EF89 5/3	PCF82 6/6	U47 13/6	OC26 5/6
12AU6 4/8	DF33 7/9	EF91 2/9	PCF86 9/6	U49 12/-	OC44 2/-
12A07 4/9	DF01 2/9	EF183 5/9	PCF80 13/6	U78 4/6	OC46 2/6
12AX7 4/9	DF96 7/3	EF184 6/6	PCF801 8/9	U191 12/6	OC71 2/6
12K8GT 7/3	DH77 4/6	EL190 3/6	PCF802 9/-	U193 8/6	OC72 2/6
19BG6G17/6	DK32 7/6	EL33 9/9	PCF805 13/6	U251 14/6	OC75 2/6
20F2 13/6	DK91 5/9	EL34 9/6	PCF806 11/3	U301 10/6	OC81 2/6
20F3 11/9	DK92 8/6	EL41 11/-	PCF808 13/-	U329 14/6	OC81D 2/6
20F4 13/6	DK96 7/3	EL43 4/9	PCL82 7/3	U801 19/6	OC82 2/6
26L6GT 5/-	DL35 5/-	EL90 5/3	PCL83 12/-	UAC80 8/6	OC82D 2/6
25U4GT11/6	DL92 5/9	EL500 12/6	PCL84 7/6	UAF42 10/3	OC170 4/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.

Tel. 01-550 7441.

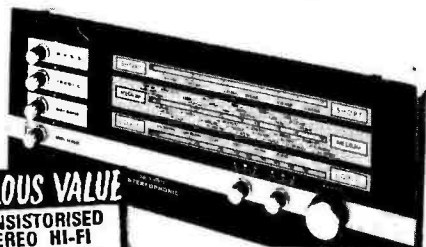Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Sarnade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED

Only 28 Gns. + P & P 17/6
Credit terms available, first monthly payment £3.62 followed by 9 monthly payments of £3.62. (Total "Credit Sale" Price £33.18). Send £4.3.8 today.

FANTASTIC BARGAIN OFFER!


"TRANSCONTINENTAL" FULLY TRANSISTORISED STEREO PHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer - a complete radiogram at half normal price ONLY

10 Watts Total output
17 Transistors & 10 diodes

38 Gns. P & P 17/6

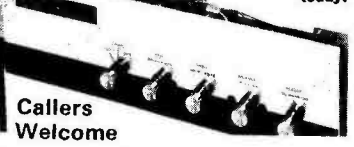EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
Credit Terms available. First monthly payment £4.9.10 followed by 9 monthly payments of £4.9.10. (Total "Credit Sale" Price £44.10.4.) Send £5.7.4 today.



Callers
Welcome

POST
THIS
COUPON
NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name _____
Address _____

LEWIS radio

100 CHASE SIDE, SOUTHGATE DEP. P1170
LONDON, N.14. TELEPHONE 686 3733/9666

BI-PAK SEMICONDUCTORS

NEW LOW PRICED TESTED S.C.R.'s.

1A 3A 7A 16A 30A	(TO-5) (TO-66) (TO-48) (TO-48)	(TO-48) (TO-48)
PIV each case	each case	each case
50 4/6 5/-	9/6 10/6 25 20/-	
100 5/- 6/6	10/6 12/6 50 23/-	
200 7/- 7/6	11/6 15/- 100 28/-	
400 8/6 9/6	13/6 18/6 200 32/-	
600 10/6 11/6	15/6 25/- 400 35/-	
800 12/6 14/-	18/- 30/- 800 80/-	

PRINTED CIRCUITS EX-COMPUTER
Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/-, Plus 2/- p. & p.

TRANSISTOR EQUIVANT BOOK
A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

2N3060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 6/- each.	Sil. trans. suitable for P.E. Organ, Metal TO-18. Eqty. ZTX300 1/- each. Any Qty.
180VCE NIXIE DRIVER TRANSISTOR. 8im. 88X21 & C407, 2N1893 FULLY TESTED AND CODED ND120 1-24. 3/6 each. TO-5 NPN 25 up 3/- each.	

MULLARD I.C. AMPLIFIERS
TAA243, Operational amplifier, 70/- each.
TAA263, Linear AF amplifier, 18/6 each.
TAA293, General purpose amplifier, 21/- each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS
Audio Power Amplifier, 30/- each.

SIL. RECTS. TESTED

PIV 750mA 3A 10A 30A	50 1/- 2/9 4/3 9/6	100 1/3 3/3 4/6 15/-	200 1/9 4/- 4/9 20/-	300 2/3 4/6 6/6 22/-	400 2/6 5/6 7/6 25/-	500 3/- 6/- 8/6 30/-	600 3/3 6/9 9/- 37/-	800 3/6 7/6 11/- 40/-	1000 5/- 9/3 12/6 50/-	1200 5/6 11/6 15/-
----------------------	--------------------	----------------------	----------------------	----------------------	----------------------	----------------------	----------------------	-----------------------	------------------------	--------------------

TRIACS
VBOM 2A 6A 10A (TO-1) (TO-66) (TO-88)
100 14/- 15/- 22/6
200 17/6 20/- 28/-
400 20/- 25/- 35/-
VBOM = Blocking voltage in either direction.

2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH

FULL RANGE OP ZENER DIODES RANGE 2-18V. 400mW (DO-7 Case) 2/6 ea. 1-5W (up-Hat) 3/6 ea. 10W. (HO-10 Stud) 5/- ea. All fully tested, 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed.

Pak No.	EQVT
T1 8 26371A	OC71
T2 8 26374	OC75
T3 8 26374A	OC81D
T4 8 26381A	OC81
T5 8 26382T	OC82
T6 8 26344A	OC44
T7 8 26345A	OC45
T8 8 26378	OC78
T9 8 26399A	2N1392
T10 8 26417	AF117

All 10/- each pack

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequalled Value and Quality
Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	80 Mixed Germanium Transistors AF/RP	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. 8BY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U13	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 3N997	10/-
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Ser. & OC71	10/-
U23	30 Madu's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, 8BY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experiments' Assortment of Integrated Circuits, untested, Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1-amp BCR's TO-5 can up to 600 PIV CR81/25-600	20/-
U31	20 Sil. Planar NPN trans. low noise AMP 2N3707	10/-
U32	25 Zener diodes 400mW DO7 case mixed Volts, 3-18	10/-
U33	16 Plastic case 1 amp Silicon Rectifiers IN4000 series	10/-
U34	30 BCR's PNP alloy trans. TO-5 BCY26, 28303/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY 50/51/53	10/-
U37	30 Sil. alloy trans. BO-2 PNP, OC200 28322	10/-
U38	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303 & 2N3011	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	25 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

I.C. AMPLIFIER

Identical encapsulation and pin configuration to the following: 8LA02-2, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

AD161 NPN AD162 PNP
MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS. For mains driven output stages of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 12/6 PER PAIR.

UNIJUNCTION
UT46. Eqty. 2N2646
Eqvt. T543, BEN3000
5/6 EACH
25-99 5/- 100 UP 4/-

NPN SILICON PLANAR
BC107/8/9, 2/- each 50-99 1/10 100 up 1/8 each, 1,000 off 1/6 each. Fully tested and coded TO-18 case.

NPNDIFFUSED SILICON PHOTO-DUODIODE
TYPE IS701 (2N2175) for Tape Readout, high switching and measurement indicators, 50V, 10mA V. OUR PRICE 10/- EACH 50 OR OVER 8/6 EACH. FULL DETAILS.

FET's	Price each
2N 3819	8/-
2N 3820	20/-
MPF105	8/6

BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	SIM-TYPE.	Description	Price and qty. prices 1-24	25-99	100 up
BP00 7400N	Quad 2-Input NAND GATE	..	6/6	5/6	4/6
BP01 7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	..	6/6	5/6	4/6
BP04 7404N	HEX INVERTER	..	6/6	5/6	4/6
BP10 7410N	Triple 3-Input NAND GATE	..	6/6	5/6	4/6
BP20 7420N	Dual 4-Input NAND GATE	..	6/6	5/6	4/6
BP30 7430N	Single 8-Input NAND GATE	..	6/6	5/6	4/6
BP40 7440N	Dual 4-Input BUFFER GATE	..	6/6	5/6	4/6
BP41 7441AN	BCD to decimal decoder and NIT Driver	..	22/6	20/-	17/6
BP42 7442N	BCD to decimal decode (TTL 0/1)	..	22/6	20/-	17/6
BP50 7450N	Dual 2-Input AND/OR/NOT GATE —expandable	..	6/6	5/6	4/6
BP53 7453N	Expandable 4-wide 2 Input and-or- nor gate.	..	6/6	5/6	4/6
BP60 7460N	Dual 4-Input—expandable	..	6/6	5/6	4/6
BP70 7470N	Single JK Flip-flop—edge triggered	..	9/-	8/-	7/-
BP72 7472N	Single Master Slave JK Flip-flop	..	9/-	8/-	7/-
BP73 7473N	Dual Master Slave JK Flip-flop	..	10/-	9/-	8/6
BP74 7474N	Dual D Flip-flop	..	10/-	9/-	8/6
BP75 7475N	Quad Bistable Latch	..	11/-	10/-	9/6
BP76 7476N	Dual Master Slave Flip-flop with preset and clear	..	11/-	10/-	9/6
BP83 7483N	Four Bit Binary Adder	..	26/-	22/6	20/-
BP90 7490N	BCD Decade Counter	..	22/6	20/-	17/6
BP92 7492N	Divide by 12 4 Bit binary counter	..	22/6	20/-	17/6
BP93 7493N	Divide by 16 4 Bit binary counter	..	22/6	20/-	17/6
BP94 7494N	Dual Entry 4 Bit Shift Register	..	22/6	20/-	17/6
BP95 7495N	4 Bit Up-Down Shift Register	..	22/6	20/-	17/6
BP96 7496N	5 Bit shift register	..	24/-	21/-	18/6

Data is available for the above Series of Integrated circuits in booklet form, price 2/6

BRAND NEW. FULL TO MANUFACTURERS' SPECIFICATION
BP709 Operational Amplifier, dual-in-line 14 pin package—BN72709 and similar to MC1709 and ZLD709C
This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

	Price each 1-24 25-99 100 up
BP709	10/6 9/- 8/-

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very ridged specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	PAK No.	PAK No.
UIC00 = 5 x 7400N	UIC42 = 5 x 7442N	UIC80 = 5 x 7480N
UIC01 = 5 x 7401N	UIC43 = 5 x 7403N	UIC82 = 5 x 7482N
UIC02 = 5 x 7402N	UIC44 = 5 x 7404N	UIC83 = 5 x 7483N
UIC03 = 5 x 7403N	UIC45 = 5 x 7405N	UIC86 = 5 x 7486N
UIC04 = 5 x 7404N	UIC46 = 5 x 7406N	UIC90 = 5 x 7490N
UIC05 = 5 x 7405N	UIC47 = 5 x 7407N	UIC92 = 5 x 7492N
UIC06 = 5 x 7406N	UIC48 = 5 x 7408N	UIC93 = 5 x 7493N
UIC07 = 5 x 7407N	UIC49 = 5 x 7409N	UIC94 = 5 x 7494N
UIC10 = 5 x 7410N	UIC50 = 5 x 7410N	UIC95 = 5 x 7495N
UIC20 = 5 x 7420N	UIC51 = 5 x 7411N	UIC96 = 5 x 7496N
UIC30 = 5 x 7430N	UIC52 = 5 x 7412N	UIC97 = 5 x 7497N
UIC40 = 5 x 7440N	UIC53 = 5 x 7413N	UIC98 = 5 x 7498N
UIC41 = 5 x 7441N	UIC54 = 5 x 7414N	UIC99 = 5 x 7499N

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DUAL-IN-LINE LOW PROFILE SOCKETS

14 AND 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.

Order No.			1-24	25-99	100up
TS014	14 pin type	7/6	6/-	5/3
TS016	16 pin type	10/-	8/6	7/9

RTL. FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits
Epoxys case Tu-5 temp range 15°C to 55°C.

	Qty. prices each 1-11 12-24 25-99 100 +
μL 900 Buffer	8/- 7/- 6/6 5/6
μL 914 Dual two-input GATE	8/- 7/- 6/6 5/6
μL 923 J-K Flip-flop	10/8 10/- 9/6 9/-

Full data and circuits for IC's in booklet form price 1/6 each.
μA709C Linear R-P-I AMPLIFIER 11/- 10/- 9/- 8/3
PLASTIC CASE TO-5 6 lead up to 100 m.c/s.

DTL. DIGITAL I.C.'s

DTL dual in-line package.

Type	Price each 1-11 12-24 25-99 100 +
Type MC844P expandable dual 4-input NAND Power Gate	15/- 15/- 15/- 15/-
Type MC844P Clock Flip-flop	15/- 15/- 15/- 15/-
Type 862 Triple 3-input NAND/NOR Gate	15/- 15/- 15/- 15/-

Full DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

MW/LW TRANSISTOR RADIO

Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-555m + 1070-1870m. 41 loudspeaker. Transistors 3 x AF117, OC81D + 2 OC81. Also works off car-aerial. Full instruction book 2/6, free with parts. State preference red, blue or tan and give alternative. Requires PP7 battery, price 4/6 extra. All parts **£6.17.6** + 4/6 post or **£10.10.0** fully built + 4/6 post. A few left of Super Six Kit (see previous issues) at **£4.5.0** (+ 4/6 post). 9 volt 6 transistor superhet using 3HF AA17 in RF and IF stages powered by a two-stage AF amplifier using OC81D. 2 x OC81. Output approx. 500mW.


STEREO AMPLIFIER type HV—2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4½ x 6in. high. EZ80, 2 x ECL86; for 3 ohm speakers, double wound main trans; fixing flange and base plate, suitable for crystal cart, tuner etc. **£6.10.0** (8/- p. & p., 200-250V. A.C.). Superior version separate base, treble & vol each channel with mono/stereo switch 15/- extra.



MULLARD STEREO "DO IT YOURSELF"

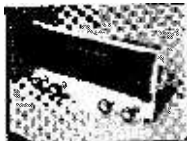Pre-amplifier EP9001 **£3.2.0**, 2 amps. EP9000 **£2.18.0** each. Power Supply EP9002 **£4.12.0**. Control panel **£2.10.0** or the lot for **£15.10.0** post paid. Booklet 5/- (6d post)



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short, Gram., 200-250V A.C. Ferrite aerial, Chassis 13 x 7 x 5in. Dial 13 x 4in. Double wound mains transformer 5 valves ECH81, EF89, EBC81, EL84, EZ80. Price **£10.12.6**. (7/6 p. & p.) Output trans. for 3-ohm speaker

NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans 10" x 6" x 4" overall. Rect; ECC83, EL84. Mike and Gram Inputs. **£7.5.0**. (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)

6 PUSH-BUTTON STEREOGRAM CHASSIS



M.W.; S.W.1; S.W.2; V.H.F. Gram: Stereo Gram Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6½in. high. Dial silver and black 15 x 3in. 190-550M; 18-51M; 60-187M; VHF 86-100 Mc/s. Valves. ECC85, ECH81, EF89, 2x ECL86, EM84 and Rect. Price **£19.19.0** carr. paid With Stereo Decoder fitted **£7.10.0** extra.

1½W MAINS GRAMOPHONE AMPLIFIERS

EZ80, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2½ x 2½ x 2½in. separate but wired to chassis, 4 x 2½ x 4½in. over valves 67/6 including 5in. Speaker (55/- less speaker). (Post paid.) (Two less 10%). ECL82 with metal rect. O.P. Transformer for 3-ohm speaker. Size 8 x 5½ x 2½in. overall. Bass, treble & vol./on-off on separate panel, 6 x 1½in. with fixing holes. Price **67/6** (+ 3/6 p. & p.). Not for low output cartridge. (Two less 10%).

MAINS TRANSFORMERS (200-250V AC INPUT)

Postage. Postage in brackets. Out 250V at 50mA and 6.3V at 1½A. 10/- (2/6) 22V at 1A + 6.3V at 2A and 250V at 50mA 15/- (3/6) 250V at 40mA, 24V at 1A and 6.3V at 1½A 12/6 (2/6). 250V at 50mA, 22V at 1A and 6.3V at 1½A 17/6 (3/6). 90V at 20mA and 1.4V at 250 mA 10/- (2/6).

USEFUL BOX 3½" x 3½" x 1½" with fixing bracket 2/6 (Postage 2/-). 25/- per dozen post free.

NEW F.M. TUNER

Range 87 to 107 MHz Attractively finished metal container with cast front escutcheon. Case size 13in. x 7in. x 3½in. high. Mains transformer. Metal Rectifier and Valves ECC83, EF89, EF80, ECC82 as cathode follower. EM84 tuning indicator, 2 x AF117 and 2 diodes. A really fantastic performer. Price **£10**, tax paid and carr. paid or with Stereo Decoder, **£24**.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY. S.A.E. for enquiries please.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

Please
1/70

BRITISH NATIONAL RADIO SCHOOL

Thinking of High Fidelity?

You should read the Goodmans High Fidelity Manuals

Goodmans High Fidelity Manuals are of vital interest to you, and contain constructive and informative articles on all aspects of High Fidelity sound. One manual contains specifications, descriptions and full colour illustrations of the entire current range of loudspeaker cabinets, systems, amplifiers and F.M. tuners. The construction manual contains the information needed by those enthusiasts who prefer to make their own High Fidelity or musical instrument loudspeaker systems.

These manuals are available free from

Goodmans Loudspeakers Limited

Axion Works Lancelot Road Wembley Middx. Tel: 01-902 1200

Please send me
Full colour manual ☐ (Tick as required)
Construction manual ☐

Name
Address

PW. 12

BRAND NEW

SEMICONDUCTORS & COMPONENTS

GUARANTEED

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

TRANSISTORS

2G901	4/-	2N3402	4/6	3N143	13/6	BC168C	3/-	BFY75	6/-	NKT237	7/-
2G902	4/-	2N3403	4/6	3N152	17/6	BC169	3/-	BFY76	6/-	NKT238	5/-
2G903	4/-	2N3404	6/6			BC169B	2/6	BFY77	11/6	NKT240	5/6
2G906	8/6	2N3405	9/-	R.C.A.:-		BC169C	3/-	BFY85	9/-	NKT241	5/6
2G908	6/6	2N3414	4/6	40050	10/6	BC170	2/6	BFY90	13/6	NKT 281	5/6
2G909	6/6	2N3415	4/6	40251	17/6	BC171	3/-	BFY25	37/-	NKT 713	4/-
2G971	8/6	2N3416	7/6	40305	6/6	BC172	3/-	BFY29	36/-	NKT 781	5/6
2G974	4/-	2N3417	7/6	40310	9/6	BC175	4/6	BFY10	29/-	NKT10419	6/-
2G981	4/6	2N3570	25/-	40311	7/-	BC182	2/6	BRX39	9/6	NKT10439	7/6
2N404	4/6	2N3572	19/6	40312	9/6	BC182L	2/6	BRX19	3/6	NKT10519	
2N696	4/-	2N3605	5/6	40314	7/6	BC183	2/6	BRX20	3/6		6/6
2N697	4/-	2N3606	5/6	40320	7/6	BC184	3/-	BRX21	7/6	NKT20329	
2N698	5/6	2N3607	4/6	40323	6/6	BC121L	2/6	BRX26	9/-		9/6
2N706	2/6	2N3702	4/6	40324	9/6	BCY30	5/6	BRX27	6/6	NKT20339	
2N708	3/6	2N3703	2/6	40326	7/6	BCY31	5/6	BRX28	6/6		7/6
2N708	3/6	2N3704	3/6	40329	6/6	BCY32	7/6	BRX60	16/6	NKT80111	
2N709	12/6	2N3705	3/-	40344	5/6	BCY33	4/6	BRX61	12/6		15/6
2N718	5/6	2N3706	2/6	40347	7/6	BCY34	4/6	BRX76	4/6	NKT80112	
2N726	6/6	2N3707	3/-	40348	10/6	BCY38	4/6	BRX77	5/6		19/6
2N727	6/6	2N3708	2/-	40360	8/6	BCY39	10/6	BRX78	5/6	NKT80113	
2N914	3/6	2N3709	2/6	40361	7/6	BCY40	7/6	BRX24	3/-		22/6
2N919	3/6	2N3710	2/6	40363	14/6	BCY42	7/6	BRX25	3/-	NKT80211	
2N918	6/6	2N3711	2/6	40370	6/6	BCY43	3/-	BRX26	3/6		18/6
2N929	4/6	2N3715	44/6	40406	11/6	BCY64	6/6	BRX27	3/6	NKT80212	
2N930	5/6	2N3716	58/-	40407	8/6	BCY65	4/6	BRX28	3/6		18/6
2N987	10/6	2N3773	48/-	40408	10/6	BCY69	4/6	BRX29	3/6	NKT80213	
2N1060	4/6	2N3819	7/6	40410	12/6	BCY70	19/6	BRX32	5/-		18/6
2N1091	4/6	2N3823	19/6	40474	11/6	BCY71	19/6	BRX37	5/-	NKT80214	
2N1131	4/6	2N3854	5/6	40484	7/6	BCY71	3/6	BRX37	5/-		18/6
2N1132	5/6	2N3854A	5/6	40600	14/6	BCY72	3/6	BRX38	4/6	NKT80215	
2N1302	3/6	2N3855	5/6	AC107	6/6	BCZ10	5/6	BRX39	4/6		18/6
2N1303	3/6	2N3855A	6/-	AC126	4/-	BCZ11	6/6	BRX40	6/6	NKT80216	
2N1304	4/6	2N3856	6/-	AC127	5/-	BD116	22/6	BRX51	6/6		18/6
2N1306	4/6	2N3856A	7/-	AC128	4/-	BD121	13/6	BRX52	6/6	OC20	35/-
2N1306	5/6	2N3856	5/6	AC134	4/6	BD123	6/6	BRX53	7/6	OC22	10/-
2N1307	5/6	2N3858A	6/-	AC176	5/6	BD124	12/-	BRX54	8/6	OC23	10/-
2N1308	6/6	2N3859	5/6	AC187	12/-	BD131	19/6	BRX56	18/-	OC24	10/-
2N1309	6/6	2N3859A	6/6	AC188	7/6	BD132	19/6	BRX79	9/6	OC25	8/6
2N1307	3/6	2N3860	6/-	AC177	5/6	BDY10	27/6	BRX82	10/6	OC26	5/6
2N1613	5/6	2N3866	30/-	ACY18	5/6	BDY11	27/6	BRX83	11/6	OC28	12/6
2N1631	7/6	2N3868	5/6	ACY19	30/-	BDY17	30/-	BRX95A	7/6	OC29	12/6
2N1632	6/6	2N3877A	8/6	ACY20	5/-	BDY18	35/-	BRW41	5/6	OC30	8/-
2N1637	6/6	2N388A	12/6	ACY21	5/-	BDY19	38/6	BSW70	5/6	OC35	10/-
2N1638	5/6	2N3900	7/6	ACY22	4/6	BDY20	22/6	C111	15/-	OC38	12/6
2N1639	5/6	2N3900A	8/6	ACY28	4/6	BDY38	10/6	C424	5/6	OC38	10/6
2N1711	5/6	2N3901	19/6	ACY40	4/6	BDY60	25/-	C435	11/-	OC41	4/6
2N1809	6/6	2N3906	8/6	ACY41	5/6	BDY61	25/-	C436	8/6	OC42	8/6
2N1893	7/6	2N3904	7/6	ACY44	8/6	BDY62	20/-	C744	6/6	OC44	4/6
2N2147	16/6	2N3905	7/6	AD140	10/6	BF115	5/6	D16P1	7/6	OC45	2/6
2N2148	11/6	2N3906	7/6	AD149	11/6	BF117	9/6	D16P2	8/6	OC46	3/6
2N2160	11/6	2N4058	3/6	AD150	12/6	BF163	7/6	D16P3	7/6	OC70	3/6
2N2193	8/6	2N4059	2/6	AD161	7/6	BF167	5/6	D16P4	8/6	OC71	2/6
2N2193A	8/6	2N4060	2/6	AD162	7/6	BF178	6/6	GET102	5/6	OC72	2/6
2N2194A	6/6	2N4061	2/6	AP106	8/6	BF177	6/6	GET113	4/6	OC74	6/6
2N2217	6/6	2N4062	2/6	AP114	5/6	BF178	10/6	GET114	4/6	OC75	4/6
2N2218	6/6	2N4244	9/6	AP115	6/6	BF179	14/6	GET118	4/6	OC76	4/6
2N2219	6/6	2N4255	8/6	AP116	5/6	BF180	7/6	ET119	4/6	OC77	6/6
2N2220	6/6	2N4285	3/6	AP117	5/6	BF181	6/6	GET120	6/6	OC81	4/6
2N2221	6/6	2N4286	3/6	AP118	12/6	BF184	5/6	GET187	3/6	OC82	4/6
2N2222	6/6	2N4287	3/6	AP119	4/6	BF185	8/6	GET188	6/6	OC83	5/6
2N2287	21/6	2N4288	3/6	AP124	4/6	BF194	3/6	GET187	4/6	OC84	5/6
2N2297	6/6	2N4289	3/6	AP125	4/6	BF195	4/6	GET189	4/6	OC139	6/6
2N2303	5/6	2N4290	3/6	AP126	4/6	BF196	8/6	GET189	4/6	OC140	6/6
2N2308	6/6	2N4291	3/6	AP127	5/6	BF197	8/6	GET189	4/6	OC171	6/6
2N2369	6/6	2N4292	3/6	AP128	5/6	BF198	8/6	GET189	4/6	OC171	6/6
2N2369A	3/6	2N4303	9/6	AP178	8/6	BF200	10/6	GET189	4/6	OC200	7/6
2N2410	8/6	2N5027	10/6	AP179	14/6	BF224	4/6	MAT100	6/6	OC201	9/6
2N2483	5/6	2N5028	11/6	AP180	10/6	BF225	4/6	MAT101	6/6	OC202	12/6
2N2484	6/6	2N5029	9/6	AP239	8/6	BF237	4/6	MAT120	6/6	OC203	8/6
2N2535	4/6	2N5030	9/6	AP238	9/6	BF238	4/6	MAT121	6/6	OC204	8/6
2N2540	4/6	2N5172	2/6	PF280	12/6	BF244	6/6	MC140	6/6	OC205	12/6
2N2613	7/6	2N5174	10/6	AP211	6/6	BFW58	5/6	MJ400	21/6	OC207	15/-
2N2614	5/6	2N5175	10/6	ASY26	5/6	BFW69	5/6	MJ420	22/6	OCRP1	8/6
2N2646	11/6	2N5176	9/6	ASY27	7/6	BFW60	5/6	MJ421	22/6	OCRP12	12/6
2N2696	6/6	2N5232	5/6	ASY28	5/6	BFW61	9/6	MJ430	20/6	OCRP1	10/-
2N2711	5/6	2N5233	5/6	ASY29	5/6	BFW62	9/6	MJ440	19/6	P346A	4/6
2N2712	5/6	2N5245	9/6	ASY36	5/6	BFX13	4/6	MJ480	19/6	TIP31A	16/6
2N2713	5/6	2N5246	8/6	ASY30	5/6	BFX29	6/6	MJ481	25/-	TIP32A	19/6
2N2714	6/6	2N5249	13/6	ASY34	5/6	BFX30	6/6	MJ490	20/6	T1834	12/6
2N2865	12/6	2N5265	55/-	ASY36	8/6	BFX43	7/6	MJ491	27/6	T1845	9/6
2N2904	6/6	2N5266	55/-	ASY20	7/6	BFX44	7/6	MJ1800	43/6	T1844	2/6
2N2904A	6/6	2N5267	52/6	ASY21	8/6	BFX68	13/6	MFJ340	12/6	T1845	2/6
2N2905	7/6	2N5305	7/6	AUY10	30/-	BFX68A	13/6	MJE520	17/6	T1846	2/6
2N2906A	5/6	2N5306	8/6	BC107	2/6	BFX84	5/6	MJE521	17/6	T1847	2/6
2N2906	5/6	2N5307	7/6	BC108	2/6	BFX85	6/6	MPF102	8/6	T1848	2/6
2N2906A	5/6	2N5308	7/6	BC109	2/6	BFX86	5/6	MPF103	7/6	T1849	2/6
2N2907	6/6	2N5309	12/6	BC113	5/6	BFX87	6/6	MPF104	7/6	T1850	3/6
2N2923	3/6	2N5310	8/6	BC115	8/6	BFX88	5/6	MPF105	7/6	T1851	2/6
2N2924	3/6	2N5354	5/6	BC116A	7/6	BFX89	12/6	MP83638	6/6	T1852	2/6
2N2925	3/6	2N5355	5/6	BC118	6/6	BFX92A	12/6	NKT0013	9/6	T1853	4/6
2N2926	3/6	2N5356	5/6	BC121	4/6	BFX93A	14/6	NKT124	8/6	T1860	4/6
" Green	2/6	2N5365	9/6	BC122	4/6	BFY10	6/6	NKT125	8/6	T1861	5/6
" Yellow	2/6	2N5366	9/6	BC125	11/6	BFY11	6/6	NKT126	5/6	T1862	5/6
" Orange	2/6	2N5367	11/6	BC126	11/6	BFY12	4/6	NKT128	5/6	ZTX107	3/6
2N3011	6/6	2N5457	7/6	BC134	6/6	BFY13	4/6	NKT135	5/6	ZTX108	3/6
2N3014	6/6	2N718A	6/6	BC135	8/6	BFY17	4/6	NKT137	6/6	ZTX109	3/6
2N3053	5/6	2N8005	15/-	BC136	7/6	BFY18	6/6	NKT140	6/6	ZTX300	3/6
2N3054	10/6	2N8020	40/-	BC140	7/6	BFY19	6/6	NKT141	6/6	ZTX301	3/6
2N3085	15/6	2N8102	10/6	BC147	3/6	BFY21	8/6	NKT212	6/6	ZTX302	4/6
2N3133	6/6	2N8103	5/6	BC148	2/6	BFY24	9/6	NKT213	6/6	ZTX303	4/6
2N3134	6/6	2N8104	5/6	BC149	3/6	BFY29	10/6	NKT214	4/6	ZTX304	4/6
2N3135	5/6	2N8501	6/6	BC152	3/6	BFY30	10/6	NKT215	4/6	ZTX500	4/6
2N3136	5/6	2N8502	7/6	BC154	8/6	BFY41	10/6	NKT216	7/6	ZTX501	5/6
2N3390	5/6	2N8503	5/6	BC157	4/6	BFY43	12/6	NKT217	6/6	ZTX502	5/6
2N3391	5/6	2N8504	5/6	BC158	3/6	BFY60	4/6	NKT219	6/6	ZTX503	5/6
2N3391A	6/6	2N128	14/6	BC159	4/6	BFY61	4/6	NKT223	5/6	ZTX504	12/6
2N3392	3/6	2N140	15/6	BC160	12/6	BFY52	4/6	NKT224	5/6		
2N3393	3/6	2N141	14/6	BC167	3/6	BFY53	3/6	NKT225	4/6		
2N3394	3/6	2N142	11/6	BC168B	2/6	BFY66A	11/6	NKT229	5/6		

Fully guaranteed Individually packed VALVES

CY31	7/-	ECL86	8/-	PC97	8/-
DAF96	7/9	EF36	3/6	PC900	9/6
DF96	7/6	EF37A	7/-	PC984	6/6
DK96	7/6	EF39	7/6	PC989	9/6
DL92	6/6	EF40	10/-	PC1189	11/-
DL94	6/6	EF41	12/6	PC1800	15/-
DM70	6/-	EF80	5/-	PCF80	6/6
DM71	6/-	EF83	9/7	PCF82	9/6
DY86	6/6	EF85	6/6	PCF84	9/3
DY87	6/6	EF86	6/3	PCF86	11/-
DY89	6/6	EF89	5/3	PCF91	15/6
DY892	9/9	EF91	7/6	PCF801	9/9
ES8CC/01		EF95	5/-	PCF802	9/9
		EF183	6/6	PCF805	14/6
EAB80	6/6	EF184	7/-	PCF806	13/-
EA243	10/-	EF1200	15/6	PCF808	14/6
EB33	8/-	EL34	10/6	PCF200	14/6
EB33	8/-	EL41	11/6	PCF81	9/6
EB34	10/6	EL42	10/6	PCF82	9/6
EB34	10/6	EL43	4/9	PCF83	13/6
EB38	7/6	EL45	7/3	PCF84	8/6
EB38	7/6	EL46	8/6	PCF85	8/6
EB38	7/6	EL47	6/6	PCF86	8/6
EB38	7/6	EL48	6/6	PCF87	11/6
EB38	7/6	EL49	6/6	PCF88	11/6
EB38	7/6	EL50	6/6	PCF89	11/6
EB38	7/6	EL161	6/6	PCF200	11/6

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
01-743 4946

Open 9-12-30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to £1.2/-; over £1.2/- per £1; over £3 post free. C.O.D. 4/- extra

TRANSISTORS, ZENER DIODES etc.

DA5	2/6	OC29	15/-	OC172	7/6	3FR5	6/6	AF118	10/-	CR83/20	10/-
DA10	6/-	OC35	8/6	OC200	6/6	3N128	17/6	AF139	10/-	CR83/30	11/6
DA70	2/-	OC38	8/6	OC201	7/6	3N139	35/-	AF178	12/6	CR825/025	
DA71	2/-	OC44	4/-	OC206	10/-	3N140	19/6	AFY19	22/6		15/-
DA79	1/9	OC45	2/6	IN21	3/6	3N154	19/-	AS26	5/6	CR83/40	12/6
DA81	1/6	OC70	3/-	IN21B	5/-	3N159	29/-	AS28	5/6	GET103	4/6
DA200	1/9	OC71	2/6	IN23	12/-	6FR5	29/-	BAW19	5/6	GET115	9/6
DA202	2/-	OC72	4/-	IN43	4/-	12FR60	14/9	BC107	3/6	GET116	8/6
DA203	1/6	OC73	11/-	IN70	4/-	DI1	3/-	BC108	4/-	BD185	5/6
DA211	9/6	OC75	4/6	IN70A	4/-	38303	10/-	BCY10	9/-	BD928	6/6
DA2200	11/-	OC76	5/-	IN746A	4/6	40594	27/6	BCY72	7/9	BD948	6/6
DA2201	10/-	OC81	4/-	series	5/3	40695	27/6	BFY61	4/6	BD968	7/9
DA2202	10/-	OC81D	3/-	IN821A	21/-	40636	29/-	BFY62	4/6	BD988	9/3
DA2206	9/6	OC81DM	3/-	IN823A	28/-	40668	27/-	BS05	7/6	V405A	7/9
DA2207	8/6	OC82	3/-	IN825A	21/-	40669	29/-	BS1	9/-	Z Range	
DA2208	8/6	OC83	3/-	IN826A	21/-	40670	29/-	BS2	9/3	Zener diodes	
DA2213	6/6	OC83A	3/-	IN827A	21/-	40671	29/-	BU100	36/-	3/6 ea.	
DA2223	10/-	OC83B	3/-	IN828A	21/-	40672	29/-	BU13	5/-	Z2A range	
DA2225	10/-	OC84	5/-	IN829A	6/6	40673	29/-	BYZ16	15/-	7/6 ea.	
OC16	15/-	OC122	10/-	IN21307	6/6	ACV28	4/-	CRS1/10	5/-	Z3B range	
OC22	8/6	OC139	6/6	IN23053	6/6	AD149	11/-	CRS1/20	9/6		
OC23	7/6	OC140	6/6	IN23054	6/6	AD150	11/-	CRS1/30	10/-	ZL range	
OC28	12/6	OC171	6/6	IN23055	15/-	AD162	7/6	CRS1/35	11/6	5/- ea.	
OC28	12/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	ZS range	
								CRS1/45	13/6	7/6 ea.	
								CRS1/50	14/6		
QVQ03-10	25/-	UAF4C0	7/6	VR150/30	35/-	5144G	10/6	6A87G	16/-	6D6	8/11
QVQ06-40	85/-	UBC41	9/6	Z759	35/-	5144G	10/6	6A76	4/6	6EA8	11/12
QVQ06-40A	85/-	UBF80	7/6	Z800U	29/-	5X4G	7/6	6AUX	8/-	6EU7	7/7
QVQ06-40A	10/-	UF89	7/6	Z800U	29/-	5X4G	7/6	6AUX	8/-	6F23	15/16
RI7	8/-	UCH42	12/6	Z906T	12/-	5144GT	12/-	6B7	5/6	6H6M	3/4
RI7	8/-	UCH42	12/6	IR5	5/6	524	14/-	6BK7	8/-	6J4WA	14/15
RI7	17/6	UCH81	6/-	IR5	5/6	6A87	3/-	6BEA	4/6	6J5	7/7
STV280-40	60/-	UCL82	7/6	184	4/6	6AC7	3/-	6B8	5/-	6J5GT	5/6
STV280-40	60/-	UCL83	12/6	174	3/-	6A16	11/6	6B6G	11/6	6J7G	5/6
STV280-40	180/-	UP80	7/6	1X2B	7/6	6AK8	8/-	6BQ7A	6/6	6J7M	8/8
UT21	51/-	UP89	6/-	34A	4/-	6AL5	3/-	6BR7	16/-	6K6GT	8/8
UT25	14/6	UL41	12/-	3D6	3/-	6AL5W	7/-	6Bw6	16/-	6K7	8/8
UT26	14/6	UL84	6/-	304	7/6	6A86	8/-	6BW7	13/-	6K8GT	7/7
UT27	3/-	U5	7/6	6FR5	29/-	6A86	8/-	6C6	4/6	6C8	4/4
UT29	11/-	U6	11/6	5V4	3/6	6AQ3	6/-	6C9	4/-	6K8GT	7/7
UT301	6/6	U85	5/6	5B254A	36/-	6AQ5W	9/-	6CL6	11/6	6K23	14/14
U801	20/-	VR105/30	6/-	5B255M	35/-	6A86	6/-	6CL9	9/-	6LGT	9/9

EX-RENTAL TELEVISIONS

TWO-YEAR GUARANTEE

17" SLIMLINE 405 only
£11 10 0

19" SLIMLINE 405/625
39 Gns.


Carriage and Insurance 30/-

FREE ILLUSTRATED LIST OF
TELEVISIONS

17"-19"-21"-23"

WIDE RANGE OF MODELS,
SIZES AND PRICES

DEMONSTRATIONS DAILY

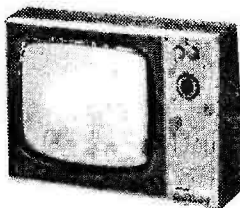

TWO-YEAR GUARANTEED TUBES 100% REGUNDED

Slim Line Tubes 110" 17" and 19" 109/6, 21" and 23" 129/6.

Normal Tubes 70" and 90" 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

SPEAKERS 10"-, 2 1/2" 8Ω, 3 1/2" 25Ω,
4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x
3" 3Ω. BRAND NEW. P. & P. 2/-.

Transistors: Mullard matched output
kit 7/6, OC81D—2 OC81's. P. & P.
FREE.

Transistor Radio Cases: 4 for £1.
Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 9/6.

Ferrite Rods 3/6: 6" and 8" complete
with LW/MW Coils. P. & P. FREE.

STRIP LIGHT TUBES 3/9 each.
11" (284mm). 230/240 volts, 30 watts.
Ideal for cocktail cabinets, illuminating
pictures, diffused lighting, etc.
6 for £1. P. & P. free.

RECORD PLAYER CABINET 49/6



Cloth covered. Size 16 1/2" x 14 1/2" x
7 1/2". Takes any modern auto-
changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

£21/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

Sensational News from Russia! for Every Lover of HI-FI!

**SUPERB COMPLETE DE-LUXE STEREO
RADIOGRAM System**
Comprising 4 magnificent UNITS!

*** GUARANTEED
£140
PERFORMANCE!**

**LISTED IN U.K. Sept 65
AT £79-
AND THAT WAS A
RUSSIAN MIRACLE!**

**NOW FROM US
FANTASTIC!
ONLY 49! GNS.
2 COMPLETE
FOR £26/8**

(comparable with specifications costing around £140) to be
sold by others in U.K. at £79 as recently as Sept. '69! NOW—unbelievable but true—
We are able to offer 500 only. **BRAND SPARKING NEW** with written 12 months
guarantee, for only 49! gns., carriage, etc., 2 gns. You'll never appreciate the wonderful
reproduction possible from your old stereo or mono records until you listen to them on
this superb Hi-Fi Audio Unit. It's a breath-taking experience! But wait. With the 6
Waveband Radio you can get thousands of transmissions from all over the world
including ham radio, ships at sea, continental and international stations. Amazing
clarity of tone & incredible station selection. Just read the magnificent specification
of this compact fully transistorised, high quality sound reproduction equipment in
matching unit form:—Four-speed single Record Player deck, lightweight arm with
'turnover' sapphire stylus and transparent deck cover. etc. (16 1/2" x 12" x 6 1/2" approx.).
Two Speaker Cabinets (each 18 1/2" x 9 1/2" x 8" approx.), each containing 8" high efficiency
unit and 3" cone tweeter. Fully transistorised Tuner/Amplifier (26 transistors 11 diodes)
(18 1/2" x 9 1/2" x 8" approx.) incorporating VHF/FM, Long, Medium and 3 Short wave-
bands. All instantaneous Press Button top panel controls! Push-pull output stage.
Frontally controlled rotatable ferrite rod aerial, internal F.M. aerial, meter type tuning
indicator, stereo balance control, separate variable bass and treble controls give
superb balance and tone. Plus all usual extension sockets. 110, 127, 220, 240V. A.C.
All cabinets very strongly constructed—with beautiful high gloss walnut polyester
finish. Long negotiations and a final purchase for cash made this incredible offer
possible! Please don't ask questions—just hurry! Only 500 will be lucky! SPARES &
UK SERVICE CONSTANTLY AVAILABLE. Only 49! gns plus carriage, crating,
handling, etc. 2 gns., and test on 7 days approx. No more to pay! *U.K. Trade distribu-
tors claim that British models comparing with this specification could cost you £140!
We guarantee to refund your money if you don't agree!

**BRAND NEW!
BANG
UP-TO-DATE!**

RUSSIAN WORLD BEATER!

**WE COULDN'T EVEN MAKE THEM FOR
THIS FANTASTIC PRICE!**

BATTERY/MAINS!

8 WAVEBAND 10 TRANSISTOR
PLUS 2 DIODES
PORTABLE RADIO

WORLD WIDE BATTERY MODEL
RECEPTION **£13.19.6**
THOUSANDS OF TRANSMISSIONS.
AND STATIONS THE WORLD OVER! BOX POST ETC. 8/6

(OR WITH MAINS/BATTERY ELIMINATOR 20/- extra)

This fantastic brand new Astrad Auriga Russian 8 Waveband
Portable Radio, designed for world-wide reception, will
probably make your present radio seem like a "crystal set".
Better than any other 8 wave radio that even they have
produced! With optional battery eliminator for both battery
and mains use! We're almost giving them away at only £13.19.6— a mere fraction of
even today's Russian miracle price! In fact, we challenge you to compare the perform-
ance and value with that of 39 1/2 gns. radios! *You just can't lose, we'll refund your
money if you are not astounded! Purer and sweeter tone than ever! Wider band spread
for absolute 'pin-point' station selection! Yes, the Russians have really surpassed
themselves this time, proving once again their fantastic ability in the field of elec-
tronics and brilliantly reflecting their advanced micro circuitry techniques in the
field of space communications. YOU GET THIS AMAZING SET FROM US AT A
PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE! Yes, 8 separate
wavebands, including Standard Long, Medium and Short Waves to cover the entire
world! Unique side control waveband selection unit gives incredible ease of station
tuning! Thousands of different transmissions and stations at your fingertips 24 hours
a day, including ships at sea and messages from all over the world—truly nothing
is secret. You must hear it to believe it! Superb, sweet tone—controlled from a
whisper to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF
volume and Treble-Bass tone controls! Press-button dial illumination! Take it any-
where, runs economically on standard batteries (obtainable everywhere) or direct
through battery eliminator from 220/240V. A.C. mains supply. Internal ferrite rod
aerial plus built-in telescopic aerial extending to full 31in. length. It's also a fabulous
CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black
Chrome finish case. SIZE 11in. x 9in. x 3 1/2in. overall approx. Made to give years of
perfect service. WRITTEN GUARANTEE, manual with simple operating instruc-
tions and circuit diagram. ONLY £13.19.6 (mains/battery eliminator 20/- extra).
POST ETC. 8/6. Standard batteries 5/- extra. Can also be used through extension
amplifier, tape-recorder, public address.

*COMPARE
IT'S PERFORMANCE WITH
39 1/2 GNS RADIOS!

LEARN HOW COMPUTERS WORK WITH COMPUKIT



CompuKIT 1 is a practical do-it-
yourself teaching aid designed to
remove the mystery from digital
computers, logic and Boolean algebra.
"Cheap, Quick and Clean... and,
clear winner on all counts" says the
Times Educational Supplement
Accompanied by easy-to-follow
instruction book.

Ideal as a gift to amateurs, intelligent teenagers, teachers etc.
Unassembled kit, complete, Type CK1/U £10-10-0 (P. & P. 6/-)
Assembled, fully tested, ready to use Type CK1/A £13-5-0 (P. & P. 6/-)
Also available CompuKIT 1 Deluxe Model and CompuKIT 2 I.C. Patch-
board.

Cash with order, or further information, from

LIMROSE ELECTRONICS (PW), Lymm, Cheshire

BUILD YOUR CIRCUITS on VEROBOARD

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.

8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD.

Industrial Estate, Chandler's Ford, Hants

SHOPERTUNITIES LTD. S.L.

Dpt. WP/1, 164 UXBRIDGE RD.,
(facing Shepherd's Bush Green),
London, W12 8AQ. (Thur. 1 Fri 7). Also 37 High Holborn, London, WC1 (opp. Chancery
Lane). (Wed. Thurs 7). Mon.-Sat. 9-6.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £6 0s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

MISCELLANEOUS

2 WATT TRANSISTOR AMPLIFIERS (not a kit). Standard 3 ohm output. Frequency response = 2db from 12 to 12000 cps, on board measuring 2½ x 3½ in. Ideal record players, etc., 22s 6d each, pp 1s 6d. A. Manley, 13 Randishorne Gardens, Bromley Road, London, S.E.6.

TOP TRANSISTORS

ACV22 1/9	OC72 1/9	2N2926 1/9
BFY51 1/9	OC200 1/9	2N3702 1/9
BFY52 1/9	OC201 1/9	2N3703 1/9
BSY27 1/9	OC202 1/9	2N3705 1/9
OC45 1/9	ZTX300 1/9	2N3706 1/9
OC71 1/9	2N706 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested, unmarked but guaranteed to be within their correct specification, or money refunded.

ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act Now, Only 29/11

MONEY BACK GUARANTEE. P. & P. 1/-

J. M. KING (K)

17 Buckridge, Portpool Lane, London, E.C.1

ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22.	11/3d	16/6d
23-30.	11/9d	17/6d
31-35.	12/3d	18/6d
36-40.	15/-	24/-
41-44.	17/9d	29/6d

Orders despatched by return of post. Please add 1/- per item P. & P.

Supplied by: Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

TRADE ENQUIRIES INVITED

BUILD IT in a DEWBOX quality cabinet. 2in. x 2½in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

BIG BARGAIN PARCEL 13/-

POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6 PAID**

SALOP ELECTRONICS
23 Wyke Cop, Shrewsbury,
Shropshire

S.A.E. for lists

MISCELLANEOUS

(continued)

MUSICAL MIRACLES! Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches etc. Send S.A.E. NOW!—D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

DO-IT-YOURSELF PRINTED CIRCUIT KITS

AMAZING VALUE! Each pack contains

★ P. C. Boards (assorted sizes)

★ Etchant

★ Resist

★ Etching Tank

★ Full instructions

Price 16/- and 30/- (extra large). C.W.O.

CLIFFORD ELECTRONICS, (Dept. P.W.)

14 Lynford Gardens, Edgware, Middx.

VICTORIA STREET'S unique magazine and paperback centre, Hills Westminster. "Practical Wireless" always in stock. **HILLS WESTMINSTER LTD.**, 5 Artillery Row, Victoria Street, S.W.1 (01-222 6165).

TV NOTES for UFO Detection, and 2 Optical Circuits, 9/6. Optical/radiation Detector Circuit (electronic "memory") 9/6. UFO Daily Flight Patterns (American, British) 7/6. Radar & Electronic Publications, "Highlands", Needham Market, Suffolk.

6 or 12 volt FLUORESCENT LIGHTS 12 ins. 8 watt tube, ample light for camping, caravan or boats, etc. fully transistorised, low battery drain.

Only 65/- post paid.

or in kit form 57/6 post paid

4 watt GRAM AMPS

Quality gram amplifier, volume/on, off and tone controls, A.C. mains operation, 3Ω output, dimensions 4½x4½ ins. app. new and boxed.

Unbeatable at 67/6 post paid

or in kit form 59/6 post paid

ELECTRONIC INDUSTRIES (SHROPSHIRE)

4 Longden Green, Shrewsbury, Shropshire

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 5 x 5d stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 10s). No callers please, mail-order ONLY.

AUDIOSCAN Dept. PW12
4, PRINCES SQUARE,
HARROGATE, YORKS.

COMPUTER PANELS AT BARGAIN PRICE. Few hundred left at 5/- each. 8 x OC43 or GET 875+24 OA81. Useful length leads. C.W.O. P. & P. 6d each. Mail order only. F. & H. Guy Ltd., 80 High Street, Ware, Herts.

MISCELLANEOUS

(continued)

PARAPHYSICAL LABORATORY, Downton, Wilts. Fascinating international magazines. S.A.E. for list. Parcel 20s.

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

WANTED

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WE BUY New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED NEW VALVES, televisions, radiograms, transistors, etc. **STAN WILLIAMS**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED, Pye Radiotelephones types F27AM, Cambridge, Bantam, Westminster, Motaphone. Phone Caterham 46692.

HIGHEST CASH PRICES for good quality Tape Recorders. 9.30-5.00. Immediate quotations. 01-472 2185.

HI-FI EQUIPMENT

SHURE GOLDRING Cartridges Post Free G800, M44/5/7 £7.17.6, M3D £5.5.0, M44E £8.19.6, M55E £9.19.6, M75E/2 £16.10.0, GARRARD SP25/2 £10.17.6. AP 75 £16.17.6 p. & p. 7/6. Ultimate Electronics, 38 Achilles Road, London, N.W.6. Mail Order Only.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.



TELEVISION

This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in Sept., January and April, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—
London Electronics College, Dept. LX/4. 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE** prospectus and find out how ICS can help you in your career.

**ICS, DEPT. 541 INTERTEXT HOUSE,
STEWARTS ROAD, LONDON. SW8**

R.T.E.B. Certs., City & Guilds, Colour TV, Radio, Computers, Radio Amateurs' Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—**FREE**. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 137K, Aldermaston Court, Reading RG7 4PF.**

COLOUR TV SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV engineer technician, and approved by leading manufacturer. Full details from:

ICS (D.562), Intertext House, London SW8, or 'phone 01-720 1983.

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on 'Satisfaction or Refund' terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio & TV, etc. Send for full details and illustrated book—**FREE**. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 168K, Aldermaston Court, Reading RG7 4PF.**

APPOINTMENTS

**NORTH EAST LONDON
POLYTECHNIC
AUDIO TECHNICIAN
(Grade T 4)**

required to manage Language Laboratory complex. Must have several years practical experience in sound, radio, television and/or language laboratory work, H.N.C. or C.G.L.I. final certificate desired.

Salary: £1,362-£1,603.

Qualification allowance £50 or £30 may also be paid.

Apply by letter in first instance to the Staffing Officer, North East London Polytechnic, Romford Road, Stratford, E.15.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

BAKER AND BAINES

UHF Aerials BBC and ITV 625 Colour
 10 ele 42/-, 14 ele 47/-, 18 ele 65/-, 22 ele 76/-,
 Double 22 ele 180/-.
BBC Aerials: Dipole 35/-, X 43/-, H 48/-.
ITA Aerials: 5 ele 38/-, 8 ele 54/-, 11 ele 66/-,
 double 5 array 99/-.
Combination Aerials: Dipole plus 5 54/-,
 H plus 5 82/-, X plus 5 80/-. Special Loft Dipole
 plus 5 42/-.
Diplexers — Triplexers — Matched Diplexers
 UHF — VHF.
 Poles, Lashings, Clamps, Couplers, etc. Co-Ax
 1/3 and 2/3.
 Postage paid inland on Aerials only. Please state
 channels when ordering. **SAB** for full lists.

11 Dale Crescent, Tupton, Chesterfield

SITUATIONS VACANT

Radiomobile

BRITAIN'S CAR RADIO SPECIALISTS

RADIO SERVICE ENGINEER

As duties will include the servicing of our complete range of products (both valve and transistorised), the successful applicant will have a good working knowledge of radio theory, together with a number of years, practical experience.

TRAINEE RADIO MECHANICS

A number of vacancies have arisen for young men between the ages of 15 and 20 years who wish to be trained as Radio Technicians.

Previous experience is not necessary but a genuine interest in radio work and a willingness to be taught are essential. As Day Release facilities will be offered in appropriate instances, a good general education, particularly mathematics, is desirable.

Applications should be made in writing in the first instance to: **MISS I. S. THOM, A.M.I.P.M., INDUSTRIAL RELATIONS/PERSONNEL MANAGER, RADIOMOBILE LIMITED, GOODWOOD WORKS, NORTH CIRCULAR ROAD, LONDON, N.W.2.**

RECEIVERS & COMPONENTS

(continued)

"AUDIO 1" 3 WATT AMPLIFIER

Ready built, tested and guaranteed. Very attractive Cabinet in black leatherette with light grey front, size 10" x 4 1/2" x 4". Fitted large speaker, Jack Socket and Volume Control. Many uses e.g. Radio Kit Amplifier, Intercom, Record Player, Public Address or even Crystal Set Amplifier. OUR PRICE ONLY 97/- P. & P. 4/6d.

EXTENSION SPEAKER CABINET

The same Cabinet that houses our Amplifier. ONLY 28/- P. & P. 3/- Or with fitted Speaker 34/- P. & P. 3/6d.




NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only 68/- P. & P. Free U.K. only

"MAY FLOWER" 5 Wave Band Short Wave Kit

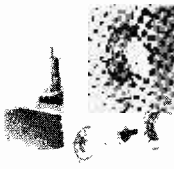

As illustrated above our all wave band one valve easy to build kit. Complete with one short wave and one medium wave plug in coil. Extra coils available at 7/- each. Price 75/- P. & P. included. This kit contains the very best in components. Drilled chassis, bandspread tuning, step by step instructions and of course first class reception and value for money. Illustrated Catalogue of Selected Kits and Components 2/6 P. & P. Free.

Cheques, Postal Orders to:

Dept. F.W.,
Galleon Trading Co., 25 Avelon Road,
Romford, Essex

E.M.I. LOUDSPEAKERS, 13in x 8in Bass, 2 Tweeters & Crossover, 75/-; Longthrow Bass 6 1/2in, 47/6; 5in, 37/6; Tweeters 3 1/2in, 16/6; Crossovers 16/-. Available in 3, 8, 15 ohms. Teak Cabinets to exact E.M.I. spec. Metrosound ST20 Amplifiers £27/10. All P&P Free. S.A.E. full list. 'SONTEL'. 183 Clapham Manor St., London, S.W.4. Tel. 01-720 3559.

BC108B 2/3; **BC109C** 2/6; **2N3705**, 50V, 800mA, 100MHz, 2/9. Postage 1/-, SAE list. **GREENWELD**, 24 Goodhart Way, W. Wickham, Kent.

AERIAL BOOSTERS

We make four types of r.f. high gain transistorized pre-amplifiers

Wideband Radio Type L10 39/-
This covers the Medium and Short Wave.
V.H.F. F.M. Radio Type L11 59/-
This covers the V.H.F. radio band.
V.H.F. Television Type L12 59/-
Please state Band and I and III.
U.H.F. Television Type L45 59/-
Tunable over the U.H.F. band.
S.A.E. for Details. P. and P. 1/-

VALVE BARGAINS

Any 5—9/-; 10—14/-; 100—£5 10s; **ECC82**, **ECL80**, **EF80**, **EF85**, **EF183**, **EFB98**, **EB91**, **EY86**, **PCC84**, **PCC89**, **PC97**, **PCF80**, **PCF86**, **PCL82**, **PCL83**, **PCL84**, **PCL85**, **PL36**, **PY33**, **PY81**, **PY82**, **PY801**, **PY800**, **30L15**.

7 day Money Back Guarantee.

VELCO ELECTRONICS

62 Bridge St, Ramsbottom, via Bury, Lancs.

EXPERIMENTERS

NEW VHF AERIAL KIT

Unique push-pull colour coded adjustable element system gives coverage of 2 metre Amateur band, Aircraft, BBC VHF FM and the new "local" stations, plus Stereo! For use in or outdoors, easy to instal with universal mounting bracket and mast, together with rotary ball clamp, VHF boom and four elements. S.A.E. for leaflet.

Complete kit, direct from makers, or from your local dealers, 52/- post and packing paid.

TUBULAR METAL PRODUCTS
7 Lowesmoor Terrace, Worcester

COMPUTER PANELS 5-BC108. Diodes 4-10/-, American, total transistors. Minimum 30. Details types. First grade components. 3-10/6. Post 1/6. Assorted Components. 7lb 20/- C.P. J.W.B. Radio, 75 Hayfield Road, Salford 6, Lancs.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW. NEW MILLS, Stockport.

MORSE MADE !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to:

68GHS (BOX 11), 46 GREEN LANE, FURLEY, SURREY

1925 WORKING RADIO, P.W. July '61 to May '70, 102 volumes. Offers: 37 Priolo Road, Charlton, London, S.E.7.

"MULLARD", "BRIMAR" E180F valves (gold plated pins), guaranteed, 5/6d post paid. Jack Porter Limited, "Electronics," College Street, Worcester.

INTEGRATED CIRCUIT AUDIO AMPLIFIER KIT

Power output: 3 Watts R.M.S. per channel.

Sensitivity: 160 mv. input for 3 watts output.

Output load: 7.5 to 15.

Frequency response: — 15 Hz to 50 kHz (3db down).

Treble cut and boost: — 18 db to + 12 db.

Bass cut and boost: — 14 db to + 12 db.

Noise level: — 80 db max. (referred to 3 watts output).

Hum: — 70 db max. (referred to 3 watts output).

Crosstalk: — 40 db.

Distortion at 3 watts output 1% max. (Total harmonic).

Price of kit of parts and full constructional details £15.

TELEVISION CITY,
Dept. PW1, 50 Richmond Road,
Kingston-upon-Thames, Surrey
Tel. 01-546 3961 (100 yards from Station)
Daily 9.30-5.30; Friday 9.30-7; Closed Monday

ELECTRICAL

**240 VOLT
ELECTRICITY
ANYWHERE**



BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY

Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested, only £4.19.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW. **STANFORD ELECTRONICS**
Rear Derby Road, North Promenade,
Blackpool, Lancashire.

LADDERS

VARNISHED TIMBER LADDERS from manufacturer, **LOWEST PRICES** anywhere. 15 1/2ft. ext. £5.10. 17ft. ext. £5.15. 20ft. ext. £6.5. 21 1/2ft. ext. £7. 24ft. ext. £8.2. 29ft. ext. £9.5. 31 1/2ft. Triple ext. £11.2.6. 36ft. triple ext. £14.10. Carr. 13/6. Free Lists. Also Aluminium Ext. and Loft Ladders. **CALLERS WELCOME.** Dept. W.L.S. **HOME SALES, BALDWIN ROAD, STOURPORT, WORCS.** Phone Stourport 2574.

PADGETTS RADIO STORE

**OLD TOWN HALL,
LIVERSEGE, YORKS**

TEL. HECKMONDWIKE 4285

AIR POSITION INDICATORS. Contains gears, Ball Races, Dinner units, Lamps, four numbered Counters. 24 Volt motor, etc. Great interest to the model makers, in good condition, 15/-, Carriage 10/-.

GROUND POSITION INDICATOR. Contains 24 Volt Lamp, Prisms, mirror, gears. Could interest schools and model makers, 15/-, Carriage 15/-.

NEW BOXED UNIT TYPE 8197. Contains two Toggle D.P.S.T. switches, also one press Toggle D.P.S.T. Sixteen miniature 500 Ohm. Pre-set Pots. RX, TX, Switches, etc. 5/-, P/P 4/6. £3 per dozen. Carriage paid.

TOGGLE SWITCHES. D.P.S.T. 1/-, P/P 9d. on any Switch. 1 doz. Post Free. Ex Units. **D.E.D.T. SWITCHES** 1/8. **PRESS BUTTON** D.P.S.T. 1/8.

G.P.O. RELAYS, EX-UNITS 400 Ohms. Doz. 10/- P/P 5/-. Sample, 1/3, P/P 1/6.

SPECIAL OFFER. Bush 17" T.V. Sets Series 75. 12 Channels. Complete and Tested with good Tube £6.10.0. Cabinet Fair. Carriage and Insurance Passenger Train G.B. only 35/-. Untested 17" T.V. Complete 12 Channel 50/- Carriage £1.

Speakers Removed from T.V. Sets. All P.M. 3 Ohms. 5" round 3/- each 6 x 4, 3/- each 7 x 4, 5/- each. Small Speakers 8 x 2 1/2 5/- each. Post on any Speaker 4/-.

8" P.M. Speakers in Cabinet with Volume Control 3 Ohm. Cabinet Condition Poor, Speaker First Class. 10/- Post and Packing 10/-. Reclaimed T.V. Tubes with 6 month Guarantee 17" AW 43/80, AW 43/88 40/-, MW 43/69 30/- each. All Tubes 15/- Carriage.

VALVE LIST—Ex Equipment, 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12	1/6	PCL85	4/-	6B8	1/8
EB91	9d.	EF183	4/-	6BW7	2/6
EF85	3/-	EF184	4/-	6K7	1/8
EBF80	3/-	PCL82	4/-	6U4	5/-
BCC81	3/-	PCL83	5/-	6P28	5/-
BCC82	3/-	PL56	5/-	10P13	2/6
BCC83	4/-	PL81	4/-	18SBT	8/6
ECL80	1/6	PY33	5/-	20D1	3/-
EF60	1/6	PY61	1/6	20P1	5/-
EF80	1/6	PY62	1/6	20P3	2/6
EF91	9d.	PZ30	5/-	30P1L	5/-
RY86	5/-	UY19	5/-	30P12	5/-
PCC84	2/-	UY21	5/-	30P5	5/-
PCF80	2/-	UY22	5/-	40P1L	5/-
PCL84	4/-	UY21	5/-	6/30L2	5/-

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5441/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
 When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/6. No C.O.D. orders accepted

PLEASE NOTE THAT THE VALVES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

PLEASE NOTE THAT ALL PRICES ARE IN DECIMAL PARTS OF £, I.E. IN NEW PENCE

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

0A2	0.38	6AR5	0.35	6EJ7	0.85	6Y6G	0.85
0A3	0.45	6AR6	0.40	6EW6	0.85	7Y4	0.80
0B2	0.35	6AS5	0.35	6F1	0.70	9BW6	0.50
0B3	0.80	6A87G	0.80	6F5	0.50	10C2	0.50
0C3	0.38	6AT6	0.30	6F6G	0.30	10D1	0.50
0D3	0.35	6AU6	0.25	6F11	0.38	10D2	0.40
1B3GT	0.38	6AV6	0.30	6F13	0.38	10F1	0.90
IL4	0.20	6AW8A	0.55	6F14	0.65	10F9	0.50
IR4	0.35	6BA6	0.25	6F15	0.65	10F18	0.45
IR5	0.35	6BE6	0.30	6F18	0.45	10L1	0.45
IS4	0.27	6BF5	0.80	6F23	0.80	10LD1	0.60
IS6	0.25	6BF8	0.60	6F24	0.75	10P13	0.50
IT4	0.25	6BH6	0.45	6F25	0.75	10P14	1.10
IU4	0.27	6BJ6	0.45	6F26	0.85	12AB3	0.60
IU5	0.50	6BK7A	0.55	6F28	0.80	12AC6	0.40
IX2	0.45	6BL7GT		6J4	0.50	12AD6	0.40
IX2B	0.40		0.85	6J5GT	0.30	12AL5	0.45
2D21	0.35	6BN5	0.43	6J7	0.45	12AQ5	0.43
3A4	0.35	6BN6	0.40	6K6GT	0.55	12AT6	0.80
3B28	2.15	6BQ5	0.25	6K7	0.75	12A7	0.38
3BP1	2.75	6BR8	0.65	6K8G	0.85	12AU6	0.30
384	0.40	6BR7	1.30	6K23	0.55	12AU7	0.30
384	0.35	6BW6	0.85	6K25	0.75	12AV6	0.38
3V4	0.45	6BW7	0.70	6L6GT	0.45	12AV7	0.50
5R4G	0.60	6BX6	0.25	6L7	0.40	12AX7	0.30
5U4G	0.38	6BZ6	0.35	6L8	0.45	12AX7	0.30
5U4GB	0.42		0.40	6L9	0.45	12B4A	0.55
5Y3GT	0.32	6C5GT	0.40	6N7GT	0.40	12B6A	0.35
5Y3GT	0.32	6CA4	0.28	6P1	0.60	12BA7	0.35
5Z3	0.50	6CA7	0.50	6P28	0.85	12B66	0.35
5Z4G	0.40	6C16	0.30	6Q7	0.40	12B7H	0.40
6B0L2	0.75	6C6DGA		68A7	0.40	12B7T	0.55
6A14	0.35		0.15	68G7	0.35	12K7	0.55
6A14A	0.50	6C6T	0.50	68K7	0.35	12K7GT	0.35
6A07	0.40	6CH6	0.55	68L7GT	0.35	12Q7G	0.30
6A116	0.50	6CL5	0.50	68N7GT	0.35	12R7	0.35
6A18	0.30	6CW4	0.83	68Q7	0.40	1487	0.80
6A18	0.30	6C16	0.45	68R7	0.40	20D1	0.45
6AK6	0.67	6D3	0.45	6T8T	0.35	20L1	1.10
6AL3	0.43	6DK6	0.75	6U6G	0.60	20P1	0.50
6AL5	0.20	6DK6	0.48	6U8A	0.40	20P4	1.10
6AM5	0.2	6DQKB	0.83	6V6GT	0.88	20P5	1.20
6AM6	0.35	6D94	0.75	6X3	0.30	25C5	0.50
6A00	0.35	6E18	0.48	6X5GT	0.65	25ZGT	0.70
6A00	0.35	6E18	0.70	6X8	0.55	25ZGT	0.30

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home – equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast – makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION – OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.
C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero
A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education
Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled... my life is fuller and happier." – Case History G/321.

"In addition to having my salary doubled, my future is assured." – Case History H/493.

"A turning point in my career – you have almost doubled my standard of living." – Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." – Case History B/461.

FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



POST THIS COUPON TODAY

To: B.I.E.T., Dept D258, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

B.I.E.T. – IN ASSOCIATION WITH THE SCHOOL OF CAREERS – ALDERMASTON COURT, BERKSHIRE

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/asia) Ltd.; South Africa – Central News Agency Ltd.; Rhodesia and Zambia – Kingston Ltd.; East Africa – Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 15s 0d. (22-25) PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LTD • MAIL ORDER AND INDUSTRIAL SALES DEPT 303, EDGWARE ROAD LONDON W.2 01 723 1008 9

● **ELECTRONIC COMPONENTS AND EQUIPMENT**
AUDIO AND TEST GEAR
356 EDGWARE ROAD LONDON W.2
TEL 01-402 4736


● **ELECTRONIC ORGANS. PUBLIC ADDRESS**
DISCOTHEQUE EQUIPMENT
309 EDGWARE ROAD LONDON W.2
TEL 01-723 6963

● **HIGH FIDELITY SALES**
AND DEMONSTRATIONS
354, EDGWARE ROAD LONDON W.2
TEL 01-402 5854

OPEN MONDAY TO SATURDAY 9AM TO 6PM. THURS 9AM TO 1PM. OPEN ALL DAY SATURDAY

COMPLETE STEREO SYSTEM FOR £39.10-0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge. Aux./Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12" x 3 1/2" x 6 1/2". Fitted headphone socket. Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover.

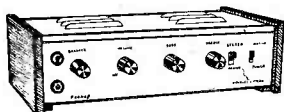

● **COMPLETE STEREO SYSTEM**
(Rec. Price £50), **£39.10-0**
p.p. 20/-

● **AMPLIFIER ONLY** £13.19-6,
p.p. 7/6


● **TE1035 RECOMMENDED**
STEREO PHONES 39/6

UNBEATABLE VALUE !!

BUILD THIS VHF FM TUNER


5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

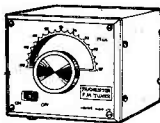PARTS TOTAL COST £6.19.6, p.p. 3/6
DECODER £5.19.6, (FOR STEREO) p.p. 3/-
ASK FOR BROCHURE No. 3.



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted Sin. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.

BUILD YOURSELF A QUALITY RADIO

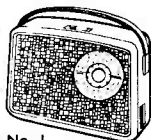

Total cost £6.19.6, p.p. 6/6

Ask for Leaflet No. 1.

SINCLAIR EQUIPMENT Z30 75/- each, stereo 60 £8.10-0, PZ5 79/6, PZ6 £6.19-6, Z50 £5-9-6, PZ8 £5-19-6.

SPECIAL OFFER 2 of Z30, stereo 60, PZ5 (usually £23.10) **£19**
or with PZ6 in place of PZ5 £21

WHEN IN LONDON visit the new Disco Centre at "354" and component shop at "356" Edgware Road, W.2.

TEST EQUIPMENT FOR YOUR HOME



AF105 50k/v multimeter (illus.), price £8.10, p.p. 3/6, leather case 28/6
200M 20k/v multimeter price £3.17-6, p.p. 3/-, case 12/6
TE20D RF Generator (illus.), price £15, p.p. 7/6
TE22D Matching Audio Generator, price £17, p.p. 7/6
TE65 Valve Voltmeter, price £17.10-0, p.p. 7/6
Full details and complete range in catalogue



SLIM POCKET TEST GEAR

● **SIGNAL INJECTOR** 35/- p.p. 1/6
● **SIGNAL TRACER** 29/6 p.p. 1/6

NEW WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV. 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended for Quality and Performance. Price 79/6 Model 940



FREE Stock List No. 16/17 on request
BEST VALUE IN U.K.

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day. Visit the new Hi-Fi Store

100 STEREO SYSTEMS

LOW CASH AND CREDIT/HP PRICES (Credit terms from £30 purchase-callers only).



HENRY'S LATEST CATALOGUE

New print. Now 350 pages. 6th Impression

★ **COMPONENTS, TEST GEAR**
★ **EQUIPMENT, MODULES**
★ **SPECIAL OFFERS ETC. ETC.**

Everything for the constructor
Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

WHY NOT SEND AWAY TODAY?

NEW. 8 page SEMICONDUCTOR LIST FREE no: 36 new ranges and a few circuits.



YOU CAN SAVE 25% brand new GARRARD


(Post 7/6) COMPLETE LIST FREE ON REQUEST AND GOLDRING

SP25mkII £10.19-6, AP75 £16.19-6, SL65B £14.19-6, SL72B £25 GL69 £22

SPECIAL Above with Sonotone 9tahc diam. Add £2, with magnetic add 70/-, with Goldring G800 add £7.10-0

Also Fitted with 9tahc diamond 2025TC £9.15-0, 3000LM £9.15-0, Model 50 £9.15-0
Plinths/Covers: Standard 99/6, p.p. 4/6. De luxe £8.10-0, p.p. 6/-, SL72B type £8.10-0, p.p. 6/-, GL69 Type £9.15-0 p.p. 6/6.

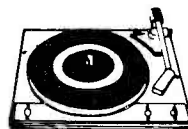
● **Goldring GL69** with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.




NEW 25watt and 50watt RMS SILICON AMPLIFIERS

LOOK AT THE SPECIFICATIONS !

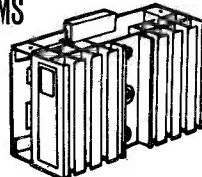- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s



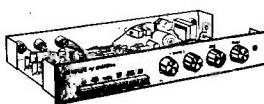PA25 10 Silicon Transistors Differential input, 25watts rms into 8ohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing. 12watts into 15ohms. Supplied with edge connector and harness.
PA50 12-Transistor Version, 50watts rms into 3 to 4ohms
MU442 Power supply for one or two PA25 or one PA50
● PA25 £7.10-0, ● PA50 £9.10-0, ● MU442 £6



NEW SELF POWERED PREAMPLIFIERS

Mains operated slim design. Preamplifiers for use with any Power Amplifier. All Silicon FET/Transistor designs. Capable of driving up to 4-PA50 Amplifiers. Push Button selection. All facilities.

MODEL FET154 STEREO PREAMPLIFIER

Inputs for mag. Pickup, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. ±20dB Boost or Cutout Controls. Slim design. Size 12" x 5 1/2" x 1 1/2". Price £16.10-0

MODEL FET 9/4


Mono Preamplifier with built-in MIC MC XEC. Inputs for all Crystal and Ceramic cartridges, Tuner/Tape in and out. O/P and Response as FET154. Size 10 1/2" x 4 1/2" x 1 1/2". Price £12.10-0

NO SOLDERING. JUST PLUG-IN CONNECTORS

ELECTRONIC ORGANS

COMPLETE RANGE OF COMPONENTS IN STOCK FOR ALL PURPOSES

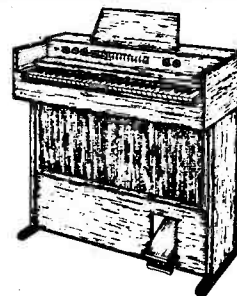- ★ **MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT VENEERED CABINETS FOR ALL MODELS**
- ★ **49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE**
- ★ **KITS AVAILABLE IN SECTIONS AS REQUIRED**
- ★ **NEW PAX DISCOTHEQUE CENTRE AT "309"**



HENRY'S RADIO LTD **FOUR ELECTRONICS CENTRES** **ALL WITHIN 100 YARDS**
303-309-354-356 EDGWARE ROAD LONDON W.2