


# PRACTICAL WIRELESS

JUNE  
1972

20p

## 12W RECORD PLAYER

Estelle

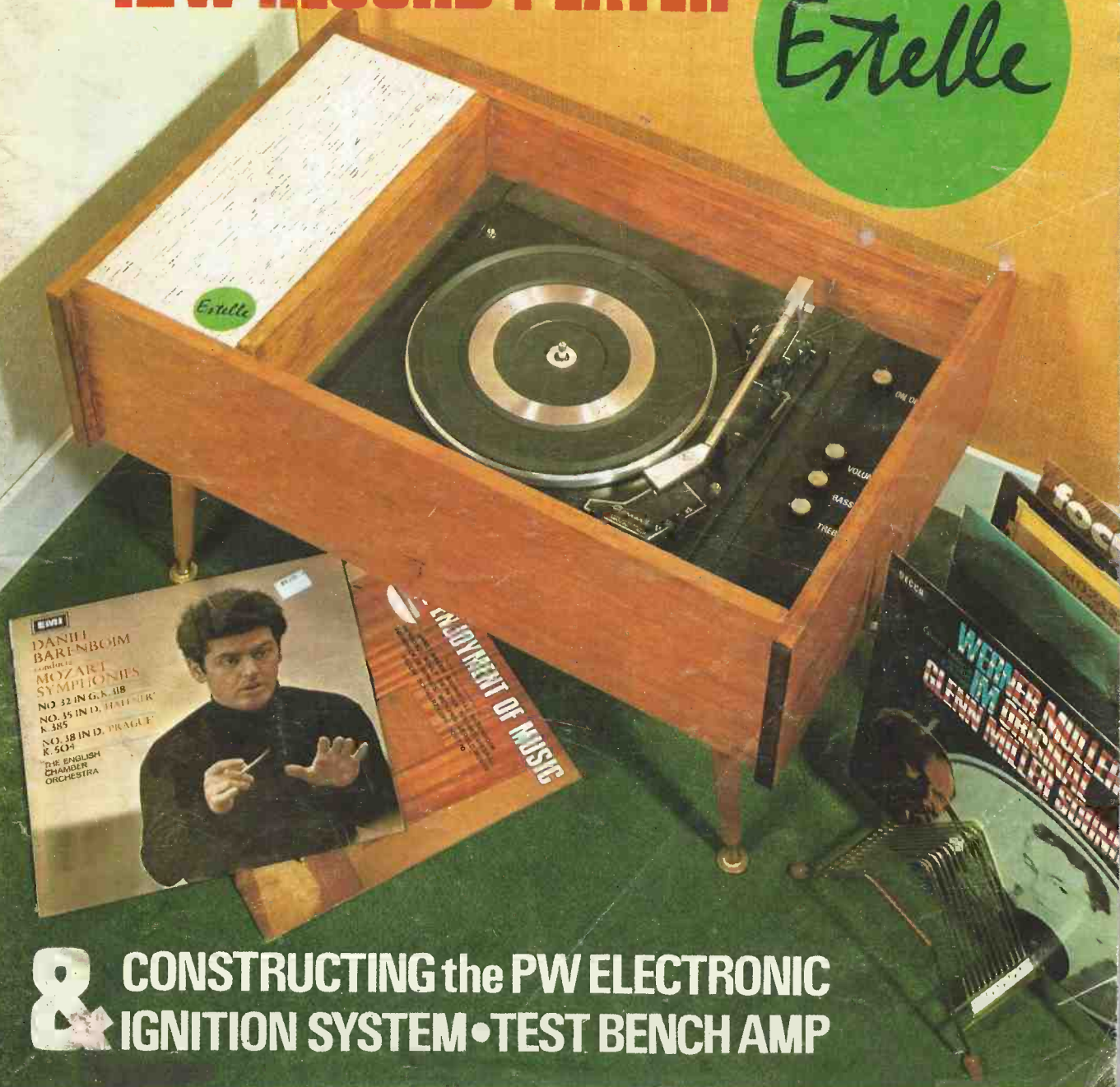

**& CONSTRUCTING the PW ELECTRONIC  
IGNITION SYSTEM • TEST BENCH AMP**

# RSC HIGH-FIDELITY STEREO PACKAGE OFFERS

Four fully wired units ready to 'plug in'.

- ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
- ★ GARRARD SP25 MK III Turntable on Plinth with cover
- ★ GOLDRING G850 Magnetic cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units

Special Total Price **£87.75**  
Carr. £1.50

Terms: Deposit £12.75 and 9 monthly payments £9.37 (Total £97.08).

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
- ★ Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II speaker units.

Special Total Price **£99.75** Carr. £1.50

Terms: Deposit £14.75 and 9 monthly payments £10.52 (Total £110.33).



ATTRACTIVE TEAK OR AFRORMOSIA VENEERED CABINETS AND PLINTHS

Send S.A.E. for coloured brochure showing other money saving offers.

- ★ TA12 AMPLIFIER 6.5 + 6.5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ PAIR OF DORCHESTER Loudspeaker Units

Special Total Price **£59**

Or Deposit £9 and 9 monthly payments £6.25 (Total £65.25). Carr. £1.25  
Trans. Plastic Cover £3.15 extra.

PACKAGE AS ABOVE but with Garrard 3000 Autochanger and Sonotone 9TA Ceramic Cartridge in lieu of SP25 and CS90 Carr. £1.25

Or Deposit £8 and 9 monthly payments £5.58 (Total £58.22)  
Trans. Plastic cover £3.15 extra.

## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in.
- ★ Response 30-20,000 c.p.s.
- ★ Impedance 15 ohms


COMPLETE KIT **£23**  
Carr. 65p

★ Performance comparable with units costing considerably more.

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.60 and 9 monthly payments £2.47 (Total £28.83).

DEMONSTRATIONS AT ALL BRANCHES

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs.

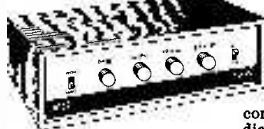


COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£11.50** Carr. 40p

Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £14.99 or dep. £2.20 and 9 monthly payments £1.70 (Total £17.50).
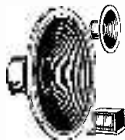
## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.95** Carr. 30p  
OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6.95** Carr. 35p



## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performance at low cost.

HF808T 8" 10W £2.88	HF120D 12" 15W £4.75
HF102D 10" 10W £3.40	HF126 12" 15W £5.50
HF120 12" 15W £4.25	HF128D 12" 15W £5.90



## FANE 807 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. STATE **£3.85**  
WHEN ORDERING



## HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16 x 11 x 9in. approx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. **£9.45** Carr. 40p.

STANWAY II Size 20 x 10 1/2 x 9 1/2 in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for illustration **£17.85**

## R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION  
HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. **£15.50** Carr. 40p. Factory built with Deposit £3 and 9 mthly pymts £2.15 (Total £22.35). Or in Teak veneer housing Dep. £3 & 9 mthly payments £2.55 (Total £25.95). Send S.A.E. for leaflet. **£23**



## HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. All sizes approx. Carr. 35p. per enclosure.

JES Size 16 x 11 x 9in. Pressurised. **£5.35** Carr. 30p. For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£6.47**

SE10 For outstanding results with 10in. Hi-Fi spkr. **£6.74** Carr. 30p. Size 24 x 15 x 10in. P.t.d. **£7.87**



## R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 90v. to battery radio where A.C. mains 200/250v. 50c/s is available. COMPLETE KIT **£3.25** ASSEMBLED READY **£3.75**  
WITH DIAGRAM FOR USE

## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. - 2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p.  
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£9.75**




# R.S.C. MKIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

A COMPLETELY NEW DESIGN  
FURTHER IMPROVED IN BOTH  
APPEARANCE AND PERFORMANCE.  
REPRESENTING VALUE  
FAR HIGHER THAN THE  
PRICES SUGGEST.

Only high grade components by leading manufacturers: **£25** Carr. 65p

COMPLETE KIT OF PARTS  
Or FACTORY BUILT with 12 months guarantee. Dep. £5.75 and 9 monthly payments £3.50 (Total £37.25). **£33.75**  
Or FACTORY BUILT in cabinet as illustrated. Dep. £7 and 9 monthly payments £3.99 (Total £42.91) **£38.75**

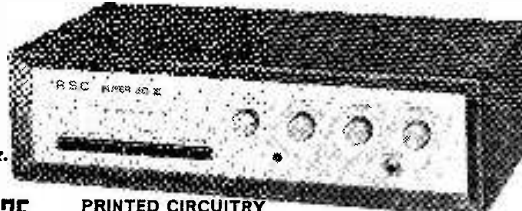TECHNICAL DETAILS (Applying to each channel where appropriate)  
CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble and Balance. Plus Ceramic Mag P.U. Switch.



PRINTED CIRCUITRY  
TWENTY SILICON  
TRANSISTORS.  
FOUR DIODES.  
FOUR RECTIFIERS

- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE. WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms. HARMONIC DISTORTION: -3dB 7Hz to 70kHz 0.1% at 1000 Hz 10 Watts  
TREBLE CONTROL: +16dB to -12dB at 14kHz  
BASS CONTROL: +17dB to -16dB at 40Hz  
CROSS TALK -58dB  
SENSITIVITIES: Disc Mag. 2.5 mV. Ceramic 35mV. Radio 120mV. Tape 120mV.  
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.





**CN.240/2** Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. **Price £1.70**

**CN.240** Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. **Price £1.70**

**G.240** Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. **Price £1.83.**




**CCN.240** New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" iron coated bit. Spare bits 1/8", 3/16" and 1/4" available. Can also be supplied for 220 volts. **Price £1.80**

**CCN.240/7** The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. **Price £1.95**



**E.240** 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. **Price £1.80.**

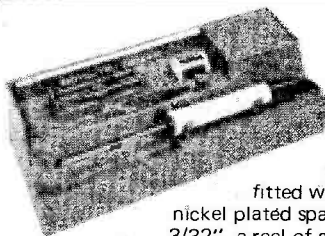**ES.240** 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. **Price £1.83**



### SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.


**Price £2.75**



### SK.2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

**Price  
£2.40.**

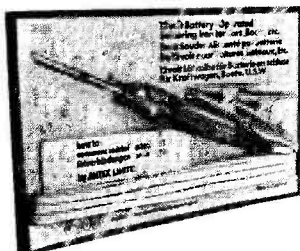

### MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. **Price £1.95.**

# sign here

## to answer all your soldering problems

I enclose cheque/P.O./Cash  
(Giro No. 2581000)

Name \_\_\_\_\_

Address \_\_\_\_\_

PW6

☐ Please send the Antex  
colour catalogue.

Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_



from electrical, radio or car accessory  
shops or from **Antex Ltd., Freepost**  
(no stamp required) **Plymouth**

**PL1 1BR** Telephone 0752 67377/8





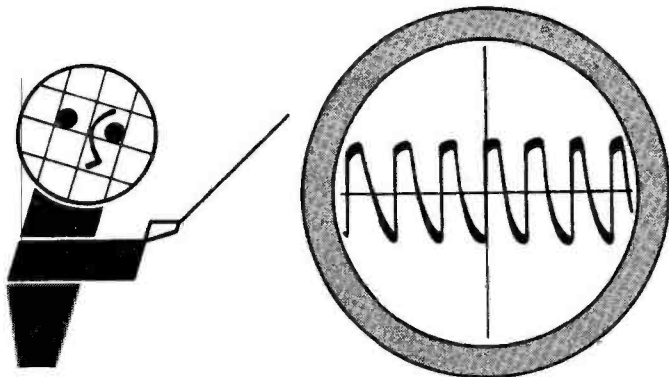
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
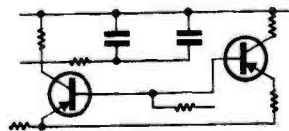
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL62

**special free gift also to all our students**

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
TO-5	TO-6	TO-6	TO-6	TO-48	TO-48	TO-48
\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.33	0.53	0.58	0.63	1.40
200	0.35	0.37	0.57	0.61	0.75	1.80
400	0.43	0.47	0.67	0.75	0.93	1.75
600	0.53	0.57	0.77	0.97	1.25	
800	0.63	0.70	0.90	1.20	1.50	4.00

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.40	0.05	0.05	0.07	0.14	0.21	0.47
100	0.44	0.08	0.05	0.13	0.16	0.23	0.75
200	0.45	0.09	0.06	0.14	0.20	0.24	1.00
400	0.48	0.13	0.07	0.20	0.27	0.37	1.25
600	0.47	0.18	0.10	0.23	0.34	0.45	1.80
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.83	2.50
1200		0.33		0.33	0.57	0.83	

## TRIACS

VBOM	2A	6A	10A
TO-1	TO-66	TO-88	
\$p	\$p	\$p	\$p
100	30	50	70
200	50	60	80
400	70	75	1-10

FOR USE WITH TRIACS  
BR100 (D32) 37p each

UNIJUNCTION  
UT46. Eqt. 2N2646, Eqt. T1843. BEN3000 27p each. Fully tested and cooled TO-18 case.

NPN SILICON PLANAR  
BC107/108, 10p each;  
50-99 8p; 100 up, 8p each; 1000 off, 7p each. Fully tested and cooled TO-18 case.

**FREE**  
One 50p Pak of your own choice free with orders valued \$4 or over.

**SPECIAL OFFER**  
2N2926 (Y) (O)  
10 for 50p, 25 for \$1  
20,000 TO CLEAR

**CADMIUM CELLS**  
ORP12 43p  
ORP60, ORP61 40p each

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18**  
SIM. TO 2N706/8. BSY-27/28/55A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.  
20 For 0.50  
50 For 1.00  
100 For 1.75  
500 For 7.50  
1000 For 13.00

**PHOTO TRANS.**  
OCPT1 Type. 43p

**SIL. G.P. DIODES** 4p  
300mV 300, 0.50  
40pV(Min.) 100, 1.50  
Sub-Min. 500, 5.00  
Full Tested 1000, 9.00  
Ideal for Organ Builders.

**D13D1 Silicon Unilateral switch** 50p each.  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**FULL RANGE OF ZENER DIODES VOLTAGE RANGE**  
2-33V, 400mV (DO-7 Case) 13p ea. 11W (Top Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

**10 amp POTTED BRIDGE RECTIFIER**  
on heat sink.  
100PIV. 90p each

**JUMBO COMPONENT PAKS**  
MIXED ELECTRONIC COMPONENTS  
Exceptionally good value

Resistors, capacitors, p.c.s., electrolytics and coils, plus many other useful items. Approximately 3lbs in weight. Price incl. P. & P. \$1.50 only

Plus your satisfaction or money back guarantee.

**BRAND NEW TEXAS GERM. TRANSISTORS**

Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1316 OC81D
T4	8 2G3817 OC81
T5	8 2G3827 OC82
T6	8 2G3441 OC44
T7	8 2G3456 OC45
T8	8 2G3478 OC78
T9	8 2G3589A 2N562
T10	8 2G417 AF117

All 50p each pak

**2N2060 NPN SIL. DUAL TRANS. CODE D1699**  
TEXAS. Our price 25p each.

**120 VCB MIXIE DRIVER TRANSISTOR.** Sim. B5X21 & C407. 2N1893 FULLY TESTED AND CODED ND 120, 1-24 17p each. TO 5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 5p each. Any Qty.

**NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS.**  
50 v RMS 32p each  
100 v RMS 37p ..  
400 v RMS 46p ..  
Size 15 mm x 6 mm.

## KING OF THE PAKS Unequalled Value and Quality

## SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	\$p
U1	120 Glass sub-min. general purpose germanium diodes .....
U2	60 Mixed germanium transistors AF/RF .....
U3	75 Germanium gold bonded diodes sim. OA5, OA47 .....
U4	40 Germanium transistors like OC81, AC12S .....
U5	60 200mA sub-min. Sil. diodes .....
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706 .....
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V .....
U8	50 Sil. planar diodes 250mA, OA/200/202 .....
U9	20 Mixed volts 1 watt Zener diodes .....
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132 .....
U13	25 PNP-NPN sil. transistors OC200 & 2N104 .....
U14	150 Mixed silicon and germanium diodes .....
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697 .....
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV .....
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22 .....
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV .....
U19	25 Silicon NPN transistors like BC109 .....
U20	12 1.5 Amp silicon rectifiers Top-Hat up to 1,000 PIV .....
U21	30 A.F. germanium alloy transistors 2G300 series & OC71 .....
U23	30 Mad's like MAT series PNP transistors .....
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV .....
U25	25 300 Mc/s NPN silicon transistors 2N708, BSY27 .....
U26	30 Fast switching silicon diodes like IN914 micro-min .....
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600 .....
U31	20 Sil. Planar NPN trans. low noise amp 8N3707 .....
U32	25 Zener diodes 400mV DO7 case mixed volts. 3-18 .....
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series .....
U34	30 Sil. PNP alloy trans. TO-6 BCY26, 2S302/4 .....
U35	25 Sil. planar trans. PNP TO-18 2N2906 .....
U36	25 Sil. planar PNP trans. TO-5 BFY50/51/52 .....
U37	30 Sil. alloy trans. 80-2 PNP, OC200 2S322 .....
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011 .....
U39	30 RF germ. PNP trans. 2N1303 TO-5 TO-5 .....
U40	10 Dual trans. 6 lead TO-5 2N2906 .....
U41	25 RF germ. trans. TO-1 OC45 NK772 .....
U42	10 VHF germ. PNP trans. TO-1 NKT667, AF117 .....
U43	25 Sil. trans. plastic TO-18 A.F. BC113/114 .....
U44	20 Sil. trans. plastic TO-5 BC115/116 .....
U45	7 3A SCR's TO-66 up to 600 PIV .....

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## NEW QUALITY TESTED PAKS

Pak Description	Price
Q1	20 Red spot trans. PNP AF .....
Q2	16 White spot R.F. trans. PNP .....
Q3	4 OC77 type trans. .....
Q4	6 Matched trans. OC44/45/81/81D .....
Q5	4 OC75 transistors .....
Q6	4 OC72 transistors .....
Q7	4 AC128 trans. PNP high gain .....
Q8	4 AC126 trans. PNP .....
Q9	7 OC81 type trans. .....
Q10	7 OC71 type trans. .....
Q11	2 AC127/128 comp. pairs PNP/NPN .....
Q12	3 AF116 type trans. .....
Q13	3 AF117 type trans. A.F. .....
Q14	3 OC171 H.F. type trans. .....
Q15	2 2N2926 sil. epoxy trans. .....
Q16	2 GET880 low noise germ. trans. .....
Q17	3 NPN 1ST141 & 2ST140 .....
Q18	4 Mad's 2 MAT 100 & 2 MAT 120 .....
Q19	3 Mad's 2 MAT 101 & 2 MAT 121 .....
Q20	4 OC44 germ. trans. A.F. .....
Q21	3 AC127 NPN germ. trans. .....
Q22	20 NKT trans. A.F. R.F. cooled .....
Q23	10 OA202 sil. diodes sub-min. .....
Q24	8 OA81 diodes .....
Q25	6 IN914 sil. diodes 75PIV 75mA .....
Q26	8 OA95 germ. diodes sub-min. IN69 .....
Q27	2 10A 800PIV sil. rect. 1845R .....
Q28	2 Sil. power rect. BYZ13 .....
Q29	4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698 .....
Q30	7 Sil. switch trans. 2N706 PNP .....
Q31	6 Sil. switch trans. 2N708 NPN .....
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132 .....
Q33	3 Sil. NPN trans. 2N1711 .....
Q34	7 Sil. NPN trans. 2N2369, 500MHZ .....
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2N2905 .....
Q36	7 2N3446 TO-18 plastic 300MHZ NPN .....
Q37	5 2N3053 NPN sil. trans. .....
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702 .....
Q39	7 NPN trans. 4 x 2N3704, 3 x 2N3705 .....
Q40	7 NPN amp. 4 x 2N3707, 3 x 2N3708 .....
Q41	3 Plastic PNP TO-18 2N3904 .....
Q42	6 NPN trans. 2N5172 .....
Q43	7 BC107 NPN trans. .....
Q44	7 NPN trans. 4 x BC108, 3 x BC109 .....
Q45	3 BC113 NPN TO-18 trans. .....
Q46	3 BC115 NPN TO-5 trans. .....
Q47	6 NPN high gain 3 x BC167, 3 x BC168 .....
Q48	4 BCY70 NPN trans. TO-18 .....
Q49	4 NPN trans. 2 x BFY51, 2 x BFY52 .....
Q50	7 BSY28 NPN switch TO-18 .....
Q51	7 BSY28A NPN trans. 300MHZ .....
Q52	8 BY100 type sil. rect. .....
Q53	25 Sil. & germ. trans. mixed all marked new .....

## PRINTED CIRCUITS-EX-COMPUTER

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p Plus 10p P. & P. 100 Boards \$3, P. & P. 30p.

## POWER TRANSISTOR BONANZA!

GENERAL PURPOSE GERM. PNP			
Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE. - OC25-28-29-30-35-36, NKT 401-403-404-405-406-430-451-452-453, T13027-3028, 2N250A, 2N466A-467A-468A, 2N511 A & B, 2G220-222, ETC. VCEO 80V VCEO 50V IC 10A PT. 30 WATTS Hie 30-170.			
PRICE	1-24	25-99	100 up
	43p each	40p each	36p each
<b>SILICON High Voltage 250V NPN</b> TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCEO 250V VCEO 100/IC 6A/30 Watts. HFE type 20/IT 5MHZ. OUR PRICE EACH : 1-24 25-99 100 up 50p 45p 40p			
<b>EX-STOCK TYPE EACH AS PRICED</b> OC25 50p OC28 40p AD140 43p BD131 70p BD139 75p OC230 50p OC29 40p AL102 85p BD132 80p BD140 85p OC23 83p OC35 33p AL103 85p BD135 70p BD156 75p OC24 45p OC36 40p BD121 80p BD136 80p BU105 23 OC25 25p AD140 40p BD123 75p BD137 70p 2N3054 445p OC26 25p AD142 40p BD124 70p BD138 80p			

PNP

PNP

M/P COMP  
GERM TRANS.  
OUR LOWEST PRICE  
OF 55p PER PAIR

**2N3055**  
115 WATT SIL  
POWER NPN  
50p EACH

**SILICON 50 WATTS MATCHED NPN/PNP**  
BIP 19 NPN TO-3 Plastic.  
BIP 20 PNP. Brand new.  
VCEO 100V VCEO 50V TO 10A. HFE type 100/IT 3mHZ.  
OUR PRICE PER PAIR:  
1-24 25-99 100  
prs. prs. prs.  
80p 55p 50p

**SILICON PHOTO TRANSISTOR.** TO-18 Lens and NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up  
Price each 45p 40p 35p

## F.E.T.'S

2N3819	85p	2N5468	50p
2N3830	50p	2N6459	40p
2N3831	35p	BFY10	40p
2N3823	50p	MPPI05	40p

## NEW EDITION 1971

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference. and equivalents book for European American and Japanese Transistors. Exclusive to BI-PAK 90p each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.**

**OUR STOCKS** of individual devices are now too numerous to mention in this advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

# -the lowest prices!

## 74 Series T.T.L. I.C.'S DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed

BI-PAK				BI-PAK			
Order No.				Order No.			
Price and qty. prices				Price and qty. prices			
1-24 25-99 100 up				1-24 25-99 100 up			
£p £p £p				£p £p £p			
BP00-SN7400	0-15	0-14	0-12	BP86-SN7486	0-82	0-30	0-28
BP01-SN7401	0-15	0-14	0-12	BP90-SN7490	0-87	0-84	0-58
BP02-SN7402	0-15	0-14	0-12	BP91-SN7491AN	0-87	0-84	0-73
BP03-SN7403	0-15	0-14	0-12	BP92-SN7492	0-87	0-84	0-58
BP04-SN7404	0-15	0-14	0-12	BP93-SN7493	0-87	0-84	0-58
BP05-SN7405	0-15	0-14	0-12	BP94-SN7494	0-77	0-74	0-68
BP07-SN7407	0-18	0-17	0-16	BP95-SN7495	0-77	0-74	0-68
BP08-SN7408	0-18	0-17	0-16	BP96-SN7496	0-77	0-74	0-68
BP09-SN7409	0-18	0-17	0-16	BP100-SN74100	1-75	1-65	1-55
BP10-SN7410	0-15	0-14	0-12	BP104-SN74104	0-97	0-94	0-83
BP13-SN7413	0-29	0-28	0-24	BP105-SN74105	0-97	0-94	0-83
BP16-SN7416	0-43	0-40	0-38	BP107-SN74107	0-40	0-38	0-36
BP17-SN7417	0-43	0-40	0-38	BP110-SN74110	0-55	0-53	0-50
BP20-SN7420	0-15	0-14	0-12	BP111-SN74111	1-25	1-15	1-10
BP30-SN7430	0-15	0-14	0-12	BP113-SN74113	1-00	0-95	0-90
BP40-SN7440	0-15	0-14	0-12	BP119-SN74119	1-35	1-25	1-10
BP41-SN7441	0-87	0-84	0-83	BP121-SN74121	0-87	0-84	0-58
BP42-SN7442	0-87	0-84	0-58	BP141-SN74141	0-87	0-84	0-58
BP43-SN7443	1-95	1-85	1-75	BP145-SN74145	1-50	1-40	1-30
BP44-SN7444	1-95	1-85	1-75	BP160-SN74160	1-80	1-70	1-60
BP45-SN7445	1-95	1-85	1-75	BP151-SN74151	1-00	0-95	0-90
BP46-SN7446	0-87	0-84	0-83	BP153-SN74153	1-20	1-10	0-95
BP47-SN7447	0-87	0-84	0-83	BP154-SN74154	1-80	1-70	1-60
BP48-SN7448	0-97	0-94	0-83	BP155-SN74155	1-40	1-30	1-20
BP50-SN7450	0-15	0-14	0-12	BP156-SN74156	1-40	1-30	1-20
BP51-SN7451	0-15	0-14	0-12	BP160-SN74160	1-80	1-70	1-60
BP53-SN7453	0-15	0-14	0-12	BP161-SN74161	1-80	1-70	1-60
BP54-SN7454	0-16	0-14	0-12	BP164-SN74164	2-00	1-90	1-80
				BP165-SN74165	2-00	1-90	1-80
BP60-SN7460	0-15	0-14	0-12	BP181-SN74181	2-75	2-60	2-40
BP70-SN7470	0-29	0-28	0-24	BP182-SN74182	0-97	0-94	0-83
BP72-SN7472	0-29	0-28	0-24	BP190-SN74190	3-50	3-25	3-00
BP73-SN7473	0-37	0-35	0-32	BP191-SN74191	3-50	3-25	3-00
BP74-SN7474	0-37	0-35	0-32	BP192-SN74192	2-10	1-95	1-75
BP75-SN7475	0-47	0-45	0-42	BP193-SN74193	2-10	1-95	1-75
BP76-SN7476	0-43	0-40	0-38	BP195-SN74195	1-10	1-05	0-95
BP80-SN7480	0-87	0-84	0-58	BP196-SN74196	1-80	1-70	1-60
BP81-SN7481	0-97	0-94	0-83	BP197-SN74197	1-80	1-70	1-60
BP82-SN7482	0-97	0-94	0-83	BP198-SN74198	5-50	5-00	4-00
BP83-SN7483	1-10	1-05	0-85	BP199-SN74199	5-50	5-00	4-00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.  
PRICES for quantities in excess of 500 pieces mixed, on application.  
Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442

### LINEAR I.C.'s-FULL SPEC.

Type No.	Price		
	1-24	25-99	100 up
BP 201C-SL201C	63p	53p	45p
BP701C-SL701C	63p	53p	45p
BP 702C-SL702C	63p	53p	45p
BP 702-SL702	63p	53p	45p
BP 709-SL709	63p	53p	45p
BP 709P-SL709C	63p	53p	45p
BP 710-SL710	53p	45p	40p
BP 711-SL711	53p	45p	40p
BP 741-SL741	75p	60p	50p
BP 741-SL741C	75p	60p	50p
BP 741-SL741C	75p	60p	50p
TAA 293	80p	75p	70p
TAA 350	170p	158p	150p

S.G.S. EA1000 2-63

### ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price		
	1-24	25-99	100 up
BP930	15p	11p	10p
BP932	15p	11p	10p
BP933	15p	11p	11p
BP935	15p	11p	11p
BP936	15p	11p	11p
BP944	15p	11p	11p
BP945	25p	24p	22p
BP946	15p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP9093	40p	38p	35p
BP9094	40p	38p	35p
BP9097	40p	38p	35p
BP9099	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minutron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

## STOP PRESS! NOW OPEN

BI-PAKS NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices.

18, BALDOCK ST. (A10), WARE, HERTS. Tel.: 61593  
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.

## BI-PAK DO IT AGAIN!

### 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER

## THE AL50



★ Frequency Response 15Hz to 100,000-1dB.

★ Loan-3, 4, 8 or 16 ohms.

★ Distortion-better than -1% at 1KHz.

★ Signal to noise ratio 80dB.

ONLY  
**£3.25p each**

★ Supply voltage 10-35 Volts.

★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.  
FULLY BUILT - TESTED - GUARANTEED.

### STABILISED POWER MODULE

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5amps at 35volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units etc. Handbook available 10p.

### STABILISED POWER MODULE SPM80 £2-95

TRANSFORMER BMT80 £1-95 p. & p. 25p.

SPECIAL COMPLETE KIT COMPRISING 2, AL50's, 1, SPM80 & 1, BMT80 ONLY £11 FREE p. & p.

### DTL & TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"-out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	UIC930 = 12 x $\mu$ A 930	50p	Pak No.	UIC948 = 8 x $\mu$ A 948	50p
UIC932 = 12 x $\mu$ A 932	50p	UIC951 = 5 x $\mu$ A 951	50p		
UIC933 = 12 x $\mu$ A 933	50p	UIC961 = 12 x $\mu$ A 961	50p		
UIC935 = 12 x $\mu$ A 935	50p	UIC962 = 5 x $\mu$ A 962	50p		
UIC936 = 12 x $\mu$ A 936	50p	UIC963 = 5 x $\mu$ A 963	50p		
UIC944 = 12 x $\mu$ A 944	50p	UIC964 = 5 x $\mu$ A 964	50p		
UIC945 = 8 x $\mu$ A 945	50p	UIC965 = 5 x $\mu$ A 965	50p		
UIC946 = 12 x $\mu$ A 946	50p	UIC966 = 5 x $\mu$ A 966	50p		

Packs cannot be split but 25 Assorted Pieces (our mix) is available as Pack UICX9 Data Booklet available for the BP930 Series, PRICE 15p

UIC00 = 12 x 7400N	50p	UIC46 = 5 x 7446N	50p	UIC81 = 5 x 7481N	50p
UIC01 = 12 x 7401N	50p	UIC47 = 5 x 7447N	50p	UIC82 = 5 x 7482N	50p
UIC02 = 12 x 7402N	50p	UIC48 = 5 x 7448N	50p	UIC83 = 5 x 7483N	50p
UIC03 = 12 x 7403N	50p	UIC49 = 5 x 7449N	50p	UIC84 = 5 x 7484N	50p
UIC04 = 12 x 7404N	50p	UIC50 = 5 x 7450N	50p	UIC85 = 5 x 7485N	50p
UIC05 = 12 x 7405N	50p	UIC51 = 5 x 7451N	50p	UIC86 = 5 x 7486N	50p
UIC06 = 12 x 7406N	50p	UIC52 = 5 x 7452N	50p	UIC87 = 5 x 7487N	50p
UIC07 = 12 x 7407N	50p	UIC53 = 5 x 7453N	50p	UIC88 = 5 x 7488N	50p
UIC08 = 12 x 7408N	50p	UIC54 = 5 x 7454N	50p	UIC89 = 5 x 7489N	50p
UIC09 = 12 x 7409N	50p	UIC55 = 5 x 7455N	50p	UIC90 = 5 x 7490N	50p
UIC10 = 12 x 7410N	50p	UIC56 = 5 x 7456N	50p	UIC91 = 5 x 7491N	50p
UIC11 = 12 x 7411N	50p	UIC57 = 5 x 7457N	50p	UIC92 = 5 x 7492N	50p
UIC12 = 12 x 7412N	50p	UIC58 = 5 x 7458N	50p	UIC93 = 5 x 7493N	50p
UIC13 = 12 x 7413N	50p	UIC59 = 5 x 7459N	50p	UIC94 = 5 x 7494N	50p
UIC14 = 12 x 7414N	50p	UIC60 = 5 x 7460N	50p	UIC95 = 5 x 7495N	50p
UIC15 = 12 x 7415N	50p	UIC61 = 5 x 7461N	50p	UIC96 = 5 x 7496N	50p
UIC16 = 12 x 7416N	50p	UIC62 = 5 x 7462N	50p	UIC97 = 5 x 7497N	50p
UIC17 = 12 x 7417N	50p	UIC63 = 5 x 7463N	50p	UIC98 = 5 x 7498N	50p
UIC18 = 12 x 7418N	50p	UIC64 = 5 x 7464N	50p	UIC99 = 5 x 7499N	50p
UIC19 = 12 x 7419N	50p	UIC65 = 5 x 7465N	50p	UIC100 = 5 x 7500N	50p
UIC20 = 12 x 7420N	50p	UIC66 = 5 x 7466N	50p		
UIC21 = 12 x 7421N	50p	UIC67 = 5 x 7467N	50p		
UIC22 = 12 x 7422N	50p	UIC68 = 5 x 7468N	50p		
UIC23 = 12 x 7423N	50p	UIC69 = 5 x 7469N	50p		
UIC24 = 12 x 7424N	50p	UIC70 = 5 x 7470N	50p		
UIC25 = 12 x 7425N	50p	UIC71 = 5 x 7471N	50p		
UIC26 = 12 x 7426N	50p	UIC72 = 5 x 7472N	50p		
UIC27 = 12 x 7427N	50p	UIC73 = 5 x 7473N	50p		
UIC28 = 12 x 7428N	50p	UIC74 = 5 x 7474N	50p		
UIC29 = 12 x 7429N	50p	UIC75 = 5 x 7475N	50p		
UIC30 = 12 x 7430N	50p	UIC76 = 5 x 7476N	50p		
UIC31 = 12 x 7431N	50p	UIC77 = 5 x 7477N	50p		
UIC32 = 12 x 7432N	50p	UIC78 = 5 x 7478N	50p		
UIC33 = 12 x 7433N	50p	UIC79 = 5 x 7479N	50p		
UIC34 = 12 x 7434N	50p	UIC80 = 5 x 7480N	50p		

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail.  
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back



# TOKAI/TUNER AMPLIFIER

AM/FM MULTIPLEX  
20/20 RMS PER CHANNEL  
Made to sell over £100  
Only £60.00



## MAIL ORDERS ONLY

### CARTRIDGES

Goldring G850	£4.50
Goldring G800	£7.50
Goldring G800E	£12.00
Goldring G800SE	£16.00
Shure M3DM	£5.50
Shure M44.5	£7.50
Shure M44.7	£7.50
Shure M55E	£10.00
Audio technical AT66	£5.00

### AMPLIFIERS

Armstrong 521	£45.50
MetroSound ST201	£26.00
Sinclair 2000	£24.00
Sinclair 605	£25.00
Heco HA50	£50.00
Femograph F307(T)	£48.00
Cambridge Audio P40	£66.00
Sansui AU101	£33.00
Sansui AU555A	£57.00
Sansui AU666	£74.00

### HEADPHONES

AKG K60 (600Ω)	£12.50
K120	£7.50
Koss KR7 711	£8.50
Nivico STH10E	£10.50
Pioneer SEE30	£10.50
SE50	£15.00
Sansui SS2	£7.50
SS10	£10.50
SS20	£13.50
Sennheiser HD414	£10.50
Teac HP101	£8.50
Wharfedale DD1	£9.50

### TURNTABLES

Garrard SP25/3	£11.50
BSR MP60	£11.50
Pioneer PL12AC	£35.00
Garrard 401	£28.95
Goldring GL69	£21.50
Goldring GL72/P	£27.00
Goldring GL75	£31.50
Sansui 1050C	£62.00

### GRUNDIG

#### CLEARANCE

TK 121	£43.00
TK 141	£47.00
TK 146	£52.00
TK 248	£120.00
TK 3200	£100.00
SV 85	£100.00
RT 100	£140.00
Yacht Boy 210	£33.00


### HECO

#### HSW330

Baffle Unit  
Freq. Response 45-25,000Hz  
Power Handling 30 watts RMS  
Retail £20.22  
Our Price £15.00
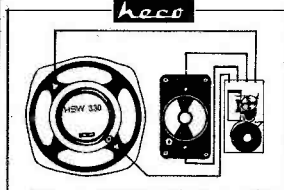
#### HSW320

Baffle Unit  
Freq. Response 48-25,000Hz  
Power Handling 20 watts RMS  
Retail £16.65  
Our Price £12.00



## SOUTHERN AUDIO SERVICES

43, High Street, Kingston-on-Thames, Surrey  
Tel: 01-549 3194 (3 lines)

All equipment guaranteed new and in makers' own boxes.  
Finest after sales services, First year, parts and labour free.  
Money credited within 7 days if not satisfied. Majority of orders by return post.


Under the personal Direction of Mr. Joseph PAO, BRIT.I.R.E.,  
POST GRAD. DIPLOMA IN ELECTRONICS (SOUTHAMPTON)



## for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

### IDEAL FOR HOME CONSTRUCTORS

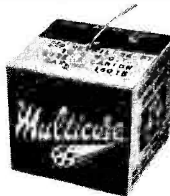

Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

### EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)

Size 19A (60/40 alloy) 18swg, 18p

Size 15 (60/40 alloy) 22swg, 22p

### BIB WIRE STRIPPER AND CUTTER



**NEW!**

Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4 & 6 BA spanner ends, ground cutting edges. Price 32p. Also available, de luxe Model 8. Price 58p.

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

## MINIATURE POWER DRILLS

Capable of Drilling Mild Steel

IDEAL FOR PRINTED CIRCUITS  
PRECISION DRILLING,  
CUTTING, GRINDING

12 volt D.C.;



PRICES FROM £3.00

### EXPO DRILLS LTD.,

DEPT. PW1, 62 NEAL STREET, LONDON, W.C.2

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.

### AERIAL BOOSTERS

We make four types of Aerial Boosters.  
L45 525 U.H.F., L12 V.H.F. TV.  
L11 V.H.F. Radio, L10 M/W & S/W.  
Price L45, L12 & L11 £2.95, L10 £2.45.

### VALVE BARGAINS

Any 5 = 45p, 10 = 70p:  
ECC82, ECL80, EF80, EF85, EF183,  
EF184, EF89, EB91, EY86, PCC84,  
PCC89, PC97, PCF80, PCF86, PCL82,  
PCL83, PCL84, PCL85, PL36, PY32,  
PY82, PY800, PY801, 30L15, 30C15,  
6-30L2.

### 19" TV £6.50

19" 405 Slimline Televisions in good working order, with complete set of spare valves.  
Price £6.50. Carriage £1.50.

### AERIAL BOOSTERS KITS £1.60

Complete kit with all parts and case. Will cover from 30 mcs. to 300 mcs.

### 500MFD CAPACITORS

500mfd-25v/w Brand New Electrolytic with long leads. 11p each.


POST & PACKING under £1-5p Over £1-10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

## VELCO ELECTRONICS

62A Bridge Street, Ramsbottom, Bury, Lancs.
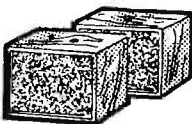
## FANTASTIC! WHARFEDALE BARGAINS

**SAVE £8.90 ON DENTON 2**  
Sold in matched pairs. Each Denton contains an 8in. bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 18 watts maximum. Frequency response: 65-17,000 Hz. Impedance: 4/8 ohms. Cabinet 9 1/2 in. x 14 in. x 8 1/2 in.



List Price £39.90 Per Pair  
LASKY'S PRICE £31.00 C&P £2.00

List Price	Lasky's Price	C&P
LINTON 2 Pair £49.90	£38.75	£2
TRITON 3 Pair £65.00	£51.50	£2
MELTON 2 each £35.00	£25.50	£1
DOVEDALE 3 each £45.00	£33.00	£1
ROSEDALE, each £65.00	£50.00	£1
UNIT 3 each £12.50	£9.50	50p
UNIT 4 each £18.00	£12.50	50p
UNIT 5 each £26.00	£18.50	50p

## DIGITAL CLOCK SCOOP

**EXCLUSIVELY FROM LASKY'S**  
The lock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. **HUNDREDS OF APPLICATIONS COMPLETE WITH KNOBS. FEATURES:**  
• MAINS OPERATION • 12-HOUR ALARM  
• AUTO "SLEEP" SWITCH • HOURS, MINUTES AND SECONDS READ-OFF  
• FORWARD AND BACKWARD TIME ADJUSTMENT • SILENT OPERATION  
• SHOCK AND VIBRATION PROOF  
• BUILT IN ALARM BUZZER  
SPECIAL QUOTES LASKY'S £6.50 C&P 25p FOR QUANTITIES




## BSR TD8S

**8 TRACK STEREO CARTRIDGE PLAYER**  
The unit is switched on and off by the insertion of the cartridge. The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250V AC, 50Hz. Frequency response: 50Hz-10KHz. 4 pole dynamically balanced synchronous motor maintains unwavering speed accuracy - independent of mains fluctuations. Compact in size the TD8S is housed in black and woodgrain plastic cabinet. Size: 8 1/2 (W) x 3 1/2 (H) x 10 1/2 (D) in.  
List Price £24.20 LASKY'S PRICE £17.95 C&P 35p


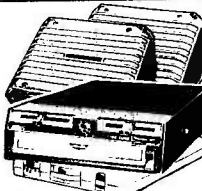
## BELTEX 8 TRACK

**Stereo car Player**  
Accepts all standard pre-recorded 8 track stereo cartridges and other features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance control. Tech spec. max output 10W (5 watts per channel), frequency response 50Hz-10KHz. Output imp. 4 ohms. size 4 1/2 (W) x 1 1/2 (H) x 6 1/2 (D) in. Operates on 12V DC negative earth systems. Beautifully styled with black ivory and chrome trim finish.  
BELTEX C5700 complete with mounting brackets and 8-track pre-recorded demonstration cartridge £19.75 C&P 25p each £24.95  
Beltek SP24 speakers are available perfectly matching the C5700 in performance and finish specially designed for optimum performance in heavily damped car interior. Size: 7 1/2 (W) x 6 (D) x 4 1/2 in. rear, 2 1/2 in front (H). Comp with connecting leads. £5.95 Pair C&P 25p



## TM-1 TEST METER

1000 ohms/volt  
Lasky's new look top value TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to +3% of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment. 1000's IN USE. SIZE ONLY 2 1/2 x 3 1/2 x 1 1/2  
• DC/V: 0-10-50-250-1000 at 1K/ohms/V. • AC/V: 0-10-50-250-1000 at 1K/ohms/V. • DC Current: 0-1mA, 100mA. • Resistance: 0-150K ohms. • Decibels: -10 + 22dB. • Complete with test leads.  
LASKY'S PRICE £1.85 C.&P. 15p



## TM-5 TEST METER

5000 ohms/volt  
Another pocket multimeter from Lasky's. The "slimline" impact resistant case size 4 1/2 in x 2 1/2 in x 1 1/2 in fitted with extra large 2 1/2 in square meter. Readability is superior on all low ranges, making this an excellent instrument for servicing transistorised equipment. Zero ohms adjustment. Buff finish with crystal clear meter cover. • DC/V: 3-15-150-300-1,200 at 5K ohms/V. • AC/V: 6-30-300-600 at 2.5K/ohms/V. • DC Current: 0-300µA, 0-300mA. • Resistance: 0-10K/ohms, 0-1M/ohms. • Decibels: -10dB to 16dB. • Complete with test leads, battery and instructions.  
LASKY'S PRICE £2.55 C.&P. 35p



## BSR McDONALD MP60

High precision low-mass counter-balanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.  
LASKY'S PRICE £10.95 C.&P. 50p



## BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.  
MODEL A B C D E  
MP.60 10.95 15.50 18.50 18.75 22.00  
HT.70 15.90 19.90 23.50 23.75 27.00  
610 14.50 17.50 21.00 22.25 25.50  
310 12.10 16.50 18.85 20.00 22.85  
310 9.75 14.00 16.50 17.25 20.25  
MP.60 TPD2 Styrene base 17.50 21.00  
210 Complete with plinth, cover & BSR cartridge £9.95

## FANTAVOX CAR RADIO

W1/700 MW/LW  
A new two waveband all transistor car radio that covers full medium and long wavebands with slide switch wave change. Large easy to grip controls. Illuminated dial with "easy to read" lining scale. Externally adjustable aerial trimmer ensures maximum output. Powerful output stage gives perfect reproduction through either one or two speakers. Operates on all through either one or two speakers. Operates on all 12 volt D.C. system. Negative or positive earth. Standard size 6 1/2 in (W) x 4 1/2 in (D) x 2 in (H). Black with chrome trim. Complete with speaker, baffle, leads, mounting brackets and instructions. Fully guaranteed. Complete with speaker, baffle & mounting bracket.  
LASKY'S PRICE £7.50 C.&P. 25p



## TAPE SCOOP

EMI 2,400ft Professional Tape on 10 1/2 in metal NAB spools. Fully guaranteed brand new.  
Today's value over £5.00 each £1.25 each 5 for £5.00 C.&P. each 20p 5 for 50p

## LEAK BARGAINS STEREO 30 PLUS amplifier (cased)

List Price LASKY'S £45.00 C & P £62.50 PRICE £1.00

## STEREO 70 amplifier (cased)

List Price LASKY'S £55.00 C & P £75.00 PRICE £1.00

## LEAK TEAK CASES

Teak case for Stereo 30 or Stereo 70, please state which is required.  
List Price LASKY'S £2.75 C & P £7.37 PRICE 35p

## Teak case for Stereofetic tuner only.

List Price LASKY'S £2.50 C & P £7.37 PRICE 35p

## Double case for 30 or 70 and stereofetic tuner.

List Price LASKY'S £4.95 C & P £10.37 PRICE 35p

## LEAK TRUSPEED TURNTABLE SYSTEM

List £69.50 Lasky's Price £47.50 C & P £1.50

## CAR RADIOS FROM PHILIPS

MODEL RN 214/15

RN214 is a triumph of micro-miniaturisation. So compact and light, mounted on its spindles only, it needs no real support. The RN214 can be fixed quickly and easily. Spec: Power supply: 13 volt D.C. negative earth operation only. Power output: 5 watts. Wave ranges: Medium wave: 185m-586m (1622-512kHz). Long wave: 1030m-2000m (290-150 kHz). Intermediate frequency: 470kHz. Size: 7in x 1 1/2 in x 3 1/2 in. EN8893/05 general purpose mounting kit with loudspeaker £2.70 extra.  
List Price £19.25 LASKY'S PRICE £15.50 C.&P. 25p



Model RN 314/15  
The RN314 gives you big sound because of the high sensitivity from the tuned RF stage. Due to its compact size it can be mounted without any rear support. Spec: power supply: 12V DC neg earth only. Power output: 5 watts RMS. Wave ranges: Medium 185m-585m (1622-512kHz); Long 1030m-2000m (290-150kHz). Intermediate frequency: 470kHz. Size: 7in x 1 1/2 in x 3 1/2 in. EN8893/05 general purpose mounting kit with loudspeaker £2.70 extra.  
List Price £25.25 LASKY'S PRICE £21.00 C.&P. 25p



## BARGAIN SCOOP

PYE S.W. CAR RADIO CONVERTER

High quality transistorised and ultra compact Shortwave Converter for use with any suitable MW(AM) Car Radio. Self powered for use on 12V positive or negative earth systems. The model 2649 is simply connected to the radio via the push button selected band spread ranges (13, 16, 19, 25, 31, 41, 49, 60 & 90 M) combined with the normal radio tuning to give full cover from 3-2MHz-21-75 MHz. On/off switch and by-pass switch for normal M.W. radio use. Complete with mounting bracket fitting and alignment instructions. Black hammer crackle finished case—size: 6(W) x 1 1/2(H) x 3 1/2(D) in. Made to sell at Approx. £20.00  
LASKY'S PRICE £8.75 C.&P. 20p.

## OUT NOW! 1972

## AUDIO TRONICS NEW REVISED EDITION

The great new 1972 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with details of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss LASKY'S offering holders one month interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

# Lasky's Radio Limited

Branches  
207 EDGWARE ROAD, LONDON. W.2 Tel: 01-723 3271.  
33 TOTENHAM CT. RD., LONDON. W.1 Tel: 01-636 2605  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
152/3 FLEET STREET, LONDON. E.C.4 Tel: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity  
42-45 TOTENHAM CT. RD., LONDON. W.1 Tel: 01-580 2573  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
**NEW CITY BRANCH NOW OPEN**  
109 FLEET STREET, LONDON. E.C.4 Tel: 01-353 5312  
Open all day Thursday, early closing 1 p.m. Saturday  
ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON. E.1 Tel: 01-790 4821



## BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,  
LONDON S.W.17 01-672 3984

(Nr. Tooting Broadway Underground Station)  
(Closed all Wednesday)

### SPEAKERS

E.M.I. 13½ x 8in. 3 ohm £2.50, 15 ohm P. & P. 30np. E.M.I. 13½ x 8in. fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 98p. P. & P. 7p.

### CARTRIDGES-Stereo


Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SXIM, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.

### CARTRIDGES—Mono

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.
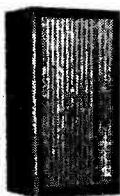
### FARRA-DAY


5½" x 11" x 4½" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front £2.90 P & P 25p



### VYNAIR

Widths from 50 to 54in., 75np yd. off roll. P. & P. 10np, ¼ yard 40np. P. & P. 10np. Send 5np stamps for samples.

### ELF

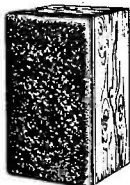

An extension speaker of quality; 9 x 5½ x 3½in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm speaker. The baffle is half inch thick. A real bargain at £1.92½. Post and packing, 37½p.

### SPEAKER MATCHING TRANSFORMERS

3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.

### HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms. frequency range 30-15,000 Hz 6ft. cord and standard stereo plug. Only £2.57½. P. & P. 27½p.




### STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.50. P. & P. 13p.
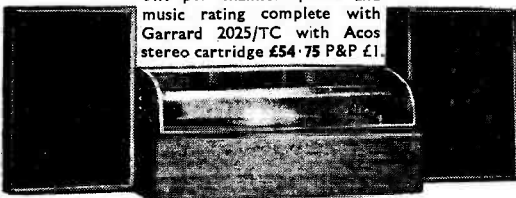
### NOCTURNE 73 STEREO SYSTEM

6w. per channel speech and music rating complete with Garrard 2025/TC with Acos stereo cartridge £54.75 P&P £1.



# Toshiba

## HI-FI STEREO AMPLIFIERS

We are now supplying a printed circuit board (for the pre-amplifier circuit) to achieve instant success with this fabulous amplifier kit.



Typical distortion level at 1,000 Hz for 20 watts mean power is approximately 0.3% of third harmonic. Tone controls: 15 dB (typical) cut and lift in bass and treble regions. Input sensitivity; suitable for 4 mV magnetic pickup. Output: 20 watts (RMS).

*Toshiba*

—TH9013P 20 watt Hi-Fi Power Amplifier

£4.57 each

*Toshiba*

—TH9014P. Pre-Amplifier. Voltage gain 75 dB

(typical). Output noise voltage 0.1 mV (typical) £1.50 each.

Printed Circuit Board £1.50 each  
Complete Kits of all Capacitors & Resistors, £6.95 each  
& Ganged Potentiometers £5.00 each  
Transformer Kit (Including Rectifier)  
Comprehensive instructions, circuit diagrams & suggested layout etc., supplied with each kit.

SEND LARGE S.A.E. FOR DATA

# Hawnt

Officially appointed distributors for ERIE, MULLARD, Etc.

HAWNT & CO. LTD., DEPT. PW2

112-114 Pritchett Street,


Birmingham B6 4EN Telephone 021 359 4301

## THE ULTIMATE IN COMMUNICATIONS RECEIVERS
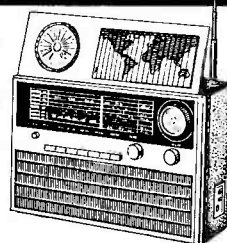
# WORLD MASTER 8 WAVE BANDS

+ WORLD MAP & TIME ZONE DIAL

Brings INSTANT WORLD-WIDE RECEPTION at the press of a button. Sensational scoop purchase of this just-released model enables us to offer a truly advanced communications receiver at a previously unheard of price. (Similar models can cost £120 or more.) The 8 WAVE BANDS enable you to cover the world at the press of a button. You might even pick up a world scoop on this world-wide receiver! As well as all the usual BBC Programmes you can pick up Local Radio Stations (including new stations yet to be introduced). \*Pop Pirates. \*Aircraft (control to pilot—pilot to control). \*Shipping. \*Taxis. \*RAC. \*A.A. \*Fire and Ambulances; \*Continental and 100s more too numerous to list. from Australia, Africa, America, India, Europe. You'll get hour after hour of enjoyable listening on this superb receiver 24 hours a day—7 days a week. A complete hobby in itself. Enjoy the exciting cross-talk between control towers and airline pilots—listen to the progress of an ambulance on its way to an accident—hear the deep-sea trawler captain's ship-to-ship and ship-to-shore conversations. PLUS many more exciting and absorbing Public Service Band transmissions we are not allowed to mention. This set has been manufactured by one of the most advanced companies in radio and electronic communications and carries their FULL WRITTEN GUARANTEE. Attractively finished in Leatherette and stainless steel to add quality and distinction to any living-room. Completely portable using standard batteries (obtainable anywhere)—or can be plugged directly into mains. 14 Transistors, 9 diodes, 1 thermistor, internal ferrite rod antenna and external Telescopic Antenna. Tone, volume and tuning controls. Very latest keyboard push-button waveband selector. Dial light (enabling use in darkness). Special WORLD-WIDE DIAL and WORLD MAP enables you to tell the correct time in any country of the world (essential for world listening). Hi-fidelity ear-phone automatically cuts out main speaker when in use. Freqs.: Long Wave 150-350 Kcs. Medium 535-1605 Kcs. Marine 1.6-4.5 Mcs. Short Wave 4-12 Mcs. Short Wave 12-24 Mcs. FM/VHF 88-108 Mcs. AIRCRAFT 108-135 Mcs. PUBLIC SERVICE BANDS 135-174 Mcs.



CASH PRICE £29.50

+ 50p p. & p. or sent for £7.50 deposit and 50p. p & p and 6 monthly payments of £4.40 (Total £33.90)

## SCIENTIFIC AND TECHNICAL (PW6) 507-511 LONDON ROAD, WESTCLIFF, ESSEX

NOTE.—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc., but there is no licence needed to buy.



# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

### CLEAR PLASTIC METERS

#### TYPE SW.100

100 x 80 mm.

50μA	...	\$2.60
50-0-50μA	...	\$2.45
100μA	...	\$2.45
100-0-100μA	...	\$2.35
500μA	...	\$2.30
1mA	...	\$2.10

20V D.C.	...	\$3.10
50V D.C.	...	\$3.10
300V D.C.	...	\$3.10
1 amp. D.C.	...	\$3.10
5 amp. D.C.	...	\$3.10
300V A.C.	...	\$3.10
VU Meter	...	\$2.75

### BAKELITE PANEL METERS

#### TYPE S-80

80 mm.

square fronts

50μA	...	\$2.30
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.00
500μA	...	\$2.75
1mA	...	\$2.60
20V D.C.	...	\$2.20
VU Meter	...	\$3.37

50V D.C.	...	\$2.60
300V D.C.	...	\$2.60
1 amp. D.C.	...	\$2.60
5 amp. D.C.	...	\$2.60
300V A.C.	...	\$2.60
VU Meter	...	\$3.37

## "SEW" CLEAR PLASTIC METERS

### Type MR.85P. 4 1/2in. x 4 1/2in. fronts.

50μA	...	\$2.60
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.00
500μA	...	\$2.30
1mA	...	\$2.10
1-0-1mA	...	\$2.10
3mA	...	\$2.10
10mA	...	\$2.10

20V D.C.	...	\$2.80
50V D.C.	...	\$2.80
300V D.C.	...	\$2.80
1 amp. D.C.	...	\$2.80
5 amp. D.C.	...	\$2.80
300V A.C.	...	\$2.80
VU Meter	...	\$2.80

### Type MR.88P. 1 21/32in. square fronts.

50μA	...	\$2.10
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.10
500μA	...	\$2.10
1mA	...	\$2.10
1-0-1mA	...	\$2.10
2mA	...	\$2.10
5mA	...	\$2.10
10mA	...	\$2.10
20mA	...	\$2.10
50mA	...	\$2.10
100mA	...	\$2.10
150mA	...	\$2.10

200mA	...	\$2.10
300mA	...	\$2.10
500mA	...	\$2.10
750mA	...	\$2.10
1 amp.	...	\$2.10
2 amp.	...	\$2.10
5 amp.	...	\$2.10
10 amp.	...	\$2.10
3V D.C.	...	\$2.10
10V D.C.	...	\$2.10
15V D.C.	...	\$2.10
20V D.C.	...	\$2.10
100V D.C.	...	\$2.10
150V D.C.	...	\$2.10
160V D.C.	...	\$2.10
300V D.C.	...	\$2.10
500V D.C.	...	\$2.10
900V D.C.	...	\$2.10
750V D.C.	...	\$2.10
15V A.C.	...	\$2.10
50V A.C.	...	\$2.10
150V A.C.	...	\$2.10
300V A.C.	...	\$2.10
500V A.C.	...	\$2.10
8 Meter 1mA	...	\$2.10
VU Meter	...	\$2.10

### Type MR.85P. 2 1/2in. square fronts.

50μA	...	\$2.10
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.10
500μA	...	\$2.10
1mA	...	\$2.10
1-0-1mA	...	\$2.10
3mA	...	\$2.10
10mA	...	\$2.10
20mA	...	\$2.10
50mA	...	\$2.10
100mA	...	\$2.10
150mA	...	\$2.10

10V D.C.	...	\$2.00
20V D.C.	...	\$2.00
50V D.C.	...	\$2.00
300V D.C.	...	\$2.00
15V A.C.	...	\$2.10
300V A.C.	...	\$2.10
8 Meter 1mA	...	\$2.10
VU Meter	...	\$2.10
1 amp. A.C.*	...	\$2.00
5 amp. A.C.*	...	\$2.00
10 amp. A.C.*	...	\$2.00
20 amp. A.C.*	...	\$2.00
30 amp. A.C.*	...	\$2.00

### Type MR.45P. 2 1/2in. square fronts.

50μA	...	\$2.25
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.10
500μA	...	\$2.10
1mA	...	\$2.10
1-0-1mA	...	\$2.10
2mA	...	\$2.10
5mA	...	\$2.10
10mA	...	\$2.10
20mA	...	\$2.10
50mA	...	\$2.10
100mA	...	\$2.10
150mA	...	\$2.10

5 amp.	...	\$1.70
10V D.C.	...	\$1.50
20V D.C.	...	\$1.50
50V D.C.	...	\$1.50
300V D.C.	...	\$1.50
15V A.C.	...	\$1.50
300V A.C.	...	\$1.50
8 Meter 1mA	...	\$1.55
VU Meter	...	\$2.25
1 amp. A.C.*	...	\$1.70
5 amp. A.C.*	...	\$1.70
10 amp. A.C.*	...	\$1.70
20 amp. A.C.*	...	\$1.70
30 amp. A.C.*	...	\$1.70

### Type MR.65P. 3 1/2in. x 3 1/2in. fronts.

50μA	...	\$2.37
50-0-50μA	...	\$2.25
100μA	...	\$2.25
100-0-100μA	...	\$2.25
500μA	...	\$2.25
1mA	...	\$2.25
1-0-1mA	...	\$2.25
3mA	...	\$2.25
10mA	...	\$2.25
20mA	...	\$2.25
50mA	...	\$2.25
100mA	...	\$2.25
150mA	...	\$2.25

10V D.C.	...	\$2.80
20V D.C.	...	\$2.80
50V D.C.	...	\$2.80
300V D.C.	...	\$2.80
15V A.C.	...	\$2.80
300V A.C.	...	\$2.80
8 Meter 1mA	...	\$2.80
VU Meter	...	\$2.80
1 amp. A.C.*	...	\$2.20
5 amp. A.C.*	...	\$2.20
10 amp. A.C.*	...	\$2.20
20 amp. A.C.*	...	\$2.20
30 amp. A.C.*	...	\$2.20

## "SEW" BAKELITE PANEL METER

### Type MR.65. 3 1/2in. square fronts.

25μA	...	\$2.50
50μA	...	\$2.75
100μA	...	\$2.35
100-0-100μA	...	\$2.25
500μA	...	\$2.20
1mA	...	\$2.15
1-0-1mA	...	\$2.15
5mA	...	\$2.15
10mA	...	\$2.15
20mA	...	\$2.15
50mA	...	\$2.15
100mA	...	\$2.15
500mA	...	\$2.15

1 amp.	...	\$1.95
2 amp.	...	\$1.95
5 amp.	...	\$1.95
15 amp.	...	\$1.95
30 amp.	...	\$1.95
50 amp.	...	\$1.95
5V D.C.	...	\$1.95
10V D.C.	...	\$1.95
20V D.C.	...	\$1.95
50V D.C.	...	\$1.95
150V D.C.	...	\$1.95
300V D.C.	...	\$1.95
30V A.C.*	...	\$1.95
50V A.C.*	...	\$1.95
150V A.C.*	...	\$1.95
300V A.C.*	...	\$1.95
500mA A.C.*	...	\$1.95
1 amp. A.C.*	...	\$1.95
5 amp. A.C.*	...	\$1.95
10 amp. A.C.*	...	\$1.95
20 amp. A.C.*	...	\$1.95
30 amp. A.C.*	...	\$1.95
50 amp. A.C.*	...	\$1.95
VU Meter	...	\$3.10

**\*MOVING—IRON**  
**ALLOTHERS MOVING COIL**  
 Please add postage

## SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm.  
 A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	...	\$5.00
100μA	...	\$4.65
1mA	...	\$4.40
50-0-50μA	...	\$4.65
1-0-1mA	...	\$4.40
1A d.c.	...	\$4.40
5A d.c.	...	\$4.40
10V d.c.	...	\$4.40

## EDGWISE METERS

### Type PE.70. 3 1/2in. x 1 1/2in. x 2 1/2in. deep

50μA	...	\$2.10
50-0-50μA	...	\$2.10
100μA	...	\$2.10
100-0-100μA	...	\$2.10
500μA	...	\$2.10
1mA	...	\$2.10
1-0-1mA	...	\$2.10
5mA	...	\$2.10
10mA	...	\$2.10
20mA	...	\$2.10
50mA	...	\$2.10
100mA	...	\$2.10
500mA	...	\$2.10

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

# MULTIMETERS for EVERY purpose!

## ROUND SCALE TYPE PENCIL TESTER

### MODEL TS.68



Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 ohms. Resistance 0-20K ohms. ONLY \$1.97 P. & P. 15p



**HIOKI MODEL 780X**  
 20,000 O.P.V.  
 Overload protection  
 5/25/100/500/1000 VDC.  
 10/50/250/1000 VAC.  
 50mA/250mA. 20K/2 meg ohm.  
 -5 to +62db.  
 \$4.97. P. & P. 15p.

## Models 100TR MULTIMETER/TRANSISTOR

TESTER. 100,000 p.v. mirror scale/overload protection. 0/12/1/6/3/12/30/120/500 VDC. 0/6/30/120/500 VAC. 0/12/500μA/12/300mA/12 AMP DC. 0/10 K/1MEG/100MEG. -20to+50 db. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. \$13.50. P/P 25p.

**SKYWOOD SW-500**  
 50K Ω/Volt. Mirror scale DC Volts 0-6/3/12/30/120/500. DC current 20μA/6/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. \$7.50. P. & P. 15p.




## 370 WTR MULTI-METER

Features A.C. current ranges. 20,000 o.p.v. 0/5/2/10/50/250/500 1000 V DC. 0/2/5/10/50/250/500/1000 V AC. 0/50μA/1/10/100mA/1/10 Amp DC. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5MEG/50MEG. -20 +62db. \$15. P. & P. 25p.


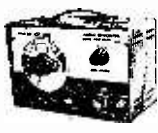
## TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 5000 ohms, 200/250V. A.C. operation. Supplied brand new with guaranteed instruction manual and leads. \$17.50. Carr. 37p.

## TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. 37p. Size 140 x 215 x 170 mm.

## BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR



New high quality portable instrument. Sine 1 Hz to 100 kHz. Square 20 Hz to 20 kHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price \$27.50. Carr. 25p.

**240° Wide Angle 1mA Meters**  
 MW1-6 60mm square \$2.97  
 MW1-8 80mm square \$4.97  
 P. & P. extra

## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: E 1 Ω-1 M meg Ω. 6 Ranges ±1% L1 μ H - 111 6 Ranges ±2% TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 1/2 in. \$20. P. & P. 25p

## 230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 60 RPM CW: 30 RPH CW: 2R/HR ACW: 2R/HR CW: 5R/HR 20R/HR ACW. 50p each Post 12p.



## TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.5v p-p/CM. Bandwidth 1-5 cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. \$40.00. Carr. 50p.

## HONEYWELL DIGITAL VOLTMETER VT.100



Can be panel or bench mounted. Basic meter measures 1 volt DC. but can be used to measure a wide range of AC and DC volt., current and ohms with optional plug in cards. Specification: Accuracy: ±0.2, ±1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 13/16 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49.97. Carr. 50p.

**G. W. SMITH & CO (RADIO) LTD.**  
 Also see next two pages

**SEMI-CONDUCTORS/VALVES**  
ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3414	2N3416	2N3445	2N3459	BC114	15P	BFW90	22P	NKT129	30P	
2G301	20P	2N3417	27P	28102	25P	BC115	15P <td>BFW91</td> <td>22P</td> <td>NKT223</td> <td>27P</td>	BFW91	22P	NKT223	27P
2G302	20P	2N3439	130P	28103	25P	BC116	15P <td>BFX12</td> <td>22P</td> <td>NKT224</td> <td>28P</td>	BFX12	22P	NKT224	28P
2G303	20P	2N3440	97P	28104	25P	BC119	30P <td>BFZ29</td> <td>25P</td> <td>NKT225</td> <td>28P</td>	BFZ29	25P	NKT225	28P
2G304	48P	2N3464	17P	28105	25P	BC120	30P <td>BFZ30</td> <td>25P</td> <td>NKT226</td> <td>28P</td>	BFZ30	25P	NKT226	28P
2G308	30P	2N3465	17P	28302	50P	BC122	20P <td>BFZ37</td> <td>25P</td> <td>NKT233</td> <td>28P</td>	BFZ37	25P	NKT233	28P
2G309	30P	2N3566	22P	28303	60P	BC125	15P <td>BFZ44</td> <td>37P</td> <td>NKT240</td> <td>27P</td>	BFZ44	37P	NKT240	27P
2G371	20P	2N3568	25P	28304	75P	BC126	20P <td>BFZ68</td> <td>47P</td> <td>NKT241</td> <td>27P</td>	BFZ68	47P	NKT241	27P
2G374	20P	2N3569	25P	28501	32P	BC134	12P <td>BFZ84</td> <td>25P</td> <td>NKT242</td> <td>20P</td>	BFZ84	25P	NKT242	20P
2G381	22P	2N3570	125P	28502	35P	BC135	12P <td>BFZ85</td> <td>30P</td> <td>NKT243</td> <td>62P</td>	BFZ85	30P	NKT243	62P
2N388A	48P	2N3572	97P	28503	27P	BC136	25P <td>BFZ86</td> <td>35P</td> <td>NKT244</td> <td>17P</td>	BFZ86	35P	NKT244	17P
2N389	30P	2N3573	104P	28504	30P	BC137	15P <td>BFZ87</td> <td>25P</td> <td>NKT245</td> <td>25P</td>	BFZ87	25P	NKT245	25P
2N396	15P	2N3606	27P	3N128	70P	BC138	20P <td>BFZ88</td> <td>30P</td> <td>NKT261</td> <td>20P</td>	BFZ88	30P	NKT261	20P
2N397	15P	2N3607	22P	3N140	77P	BC140	35P <td>BFZ89</td> <td>62P</td> <td>NKT262</td> <td>20P</td>	BFZ89	62P	NKT262	20P
2N398	25P	2N3638	18P	3N141	72P	BC141	35P <td>BFZ93A</td> <td>70P</td> <td>NKT284</td> <td>30P</td>	BFZ93A	70P	NKT284	30P
2N399	30P	2N3638A	20P	3N142	55P	BC147	10P <td>BFY11</td> <td>42P</td> <td>NKT371</td> <td>20P</td>	BFY11	42P	NKT371	20P
2N706	10P	2N3641	18P	3N143	45P	BC148	12P <td>BFY12</td> <td>42P</td> <td>NKT372</td> <td>20P</td>	BFY12	42P	NKT372	20P
2N706A	10P	2N3642	18P	3N144	35P	BC152	12P <td>BFY19</td> <td>25P</td> <td>NKT274</td> <td>20P</td>	BFY19	25P	NKT274	20P
2N708	15P	2N3643	20P	40050	55P	BC152	17P <td>BFY21</td> <td>42P</td> <td>NKT275</td> <td>20P</td>	BFY21	42P	NKT275	20P
2N709	68P	2N3644	25P	40050	50P	BC153	20P <td>BFY24</td> <td>45P</td> <td>NKT278</td> <td>25P</td>	BFY24	45P	NKT278	25P
2N718	25P	2N3645	25P	40251	32P	BC164	20P <td>BFY29</td> <td>20P</td> <td>NKT281</td> <td>27P</td>	BFY29	20P	NKT281	27P
2N718A	30P	2N3691	15P	40309	32P	BC165	15P <td>BFY30</td> <td>40P</td> <td>NKT401</td> <td>87P</td>	BFY30	40P	NKT401	87P
2N726	30P	2N3692	15P	40310	32P	BC168	15P <td>BFY31</td> <td>40P</td> <td>NKT402</td> <td>87P</td>	BFY31	40P	NKT402	87P
2N727	30P	2N3693	15P	40311	35P	BC169	15P <td>BFY43</td> <td>62P</td> <td>MKT403</td> <td>75P</td>	BFY43	62P	MKT403	75P
2N914	17P	2N3694	18P	40312	47P	BC169	35P <td>BFY50</td> <td>20P</td> <td>NKT404</td> <td>55P</td>	BFY50	20P	NKT404	55P
2N916	17P	2N3702	10P	40314	37P	BC167	11P <td>BFY51</td> <td>20P</td> <td>NKT405</td> <td>75P</td>	BFY51	20P	NKT405	75P
2N918	80P	2N3703	10P	40315	87P	BC168B	10P <td>BFY62</td> <td>20P</td> <td>NKT406</td> <td>68P</td>	BFY62	20P	NKT406	68P
2N929	22P	2N3704	11P	40316	47P	BC169B	11P <td>BFY63</td> <td>15P</td> <td>NKT451</td> <td>62P</td>	BFY63	15P	NKT451	62P
2N930	22P	2N3705	11P	40317	45P	BC169B	11P <td>BFY74</td> <td>42P</td> <td>NKT452</td> <td>62P</td>	BFY74	42P	NKT452	62P
2N987	40P	2N3706	9P	40320	55P	BC190	12P <td>BFY76</td> <td>42P</td> <td>NKT453</td> <td>47P</td>	BFY76	42P	NKT453	47P
2N1090	22P	2N3707	11P	40320	20P	BC170	12P <td>BFY77</td> <td>57P</td> <td>NKT713</td> <td>20P</td>	BFY77	57P	NKT713	20P
2N1091	22P	2N3708	7P	40323	32P	BC171	15P <td>BFY90</td> <td>95P</td> <td>NKT717</td> <td>42P</td>	BFY90	95P	NKT717	42P
2N1311	25P	2N3709	9P	40324	27P	BC172	15P <td>B8X19</td> <td>17P</td> <td>NKT734</td> <td>27P</td>	B8X19	17P	NKT734	27P
2N1332	25P	2N3710	9P	40326	47P	BC175	20P	B8X21	20P	NKT786	87P
2N1333	25P	2N3711	15P	40329	47P	BC176	20P	B8X22	20P	NKT787	87P
2N1303	17P	2N3713	18P	40344	27P	BC178	20P	B8X26	45P	NKT781	30P
2N1304	22P	2N3714	20P	40347	87P	BC179	20P	B8X37	47P	OC16	50P
2N1305	22P	2N3715	125P	40348	52P	BC182	10P	B8X38	32P	OC19	37P
2N1306	25P	2N3716	130P	40360	40P	BC182L	10P	B8X61	32P	OC20	78P
2N1307	25P	2N3773	240P	40361	40P	BC183	10P	B8X62	32P	OC21	78P
2N1308	25P	2N3774	240P	40362	40P	BC183L	10P	B8X77	15P	OC23	60P
2N1309	25P	2N3819	34P	40370	32P	BC184	11P	B8X77	20P	OC24	60P
2N1507	17P	2N3820	55P	40406	57P	BC184L	11P	B8X78	25P	OC25	40P
2N1613	20P	2N3823	50P	40407	40P	BC186	25P	B8Y44	15P	OC26	25P
2N1631	35P	2N3854	47P	40408	52P	BC187	27P	B8Y26	15P	OC28	60P
2N1632	30P	2N3854A	27P	40409	52P	BC187L	27P	B8Y27	15P	OC28	60P
2N1633	27P	2N3855	30P	40410	85P	BC213L	12P	B8Y32	15P	OC35	50P
2N1638	27P	2N3855A	30P	40412	50P	BC214L	15P	B8Y28	17P	OC36	60P
2N1639	27P	2N3856	30P	40467A	57P	BCY10	17P	B8Y29	17P	OC41	28P
2N1701	16P	2N3856A	35P	40468A	35P	BCY30	27P	B8Y32	25P	OC42	28P
2N1711	24P	2N3856S	25P	40526	75P	BCY32	30P <td>B8Y36</td> <td>25P</td> <td>OC45</td> <td>15P</td>	B8Y36	25P	OC45	15P
2N1839	30P	2N3859	27P	40603	30P <td>BCY33</td> <td>30P<td>B8Y37</td><td>25P</td><td>OC46</td><td>15P</td></td>	BCY33	30P <td>B8Y37</td> <td>25P</td> <td>OC46</td> <td>15P</td>	B8Y37	25P	OC46	15P
2N1893	37P	2N3859	27P	40603	30P <td>BCY35</td> <td>30P<td>B8Y38</td><td>25P</td><td>OC46</td><td>15P</td></td>	BCY35	30P <td>B8Y38</td> <td>25P</td> <td>OC46</td> <td>15P</td>	B8Y38	25P	OC46	15P
2N2147	72P	2N3859A	32P	40C197	30P <td>BCY34</td> <td>30P<td>B8Y39</td><td>22P</td><td>OC70</td><td>15P</td></td>	BCY34	30P <td>B8Y39</td> <td>22P</td> <td>OC70</td> <td>15P</td>	B8Y39	22P	OC70	15P
2N2160	57P	2N3860	30P	40C126	20P <td>BCY38</td> <td>30P<td>BCY41</td><td>30P<td>OC71</td><td>12P</td></td></td>	BCY38	30P <td>BCY41</td> <td>30P<td>OC71</td><td>12P</td></td>	BCY41	30P <td>OC71</td> <td>12P</td>	OC71	12P
2N2193	40P	2N3866	150P	40C127	24P <td>BCY39</td> <td>30P<td>BCY43</td><td>32P</td><td>OC72</td><td>12P</td></td>	BCY39	30P <td>BCY43</td> <td>32P</td> <td>OC72</td> <td>12P</td>	BCY43	32P	OC72	12P
2N2194A	42P	2N3877	40P	40C128	22P	BCY40	50P <td>BCY45</td> <td>30P<td>OC73</td><td>30P</td></td>	BCY45	30P <td>OC73</td> <td>30P</td>	OC73	30P
2N2195	42P	2N3878	74P	40C129	18P	BCY41	50P <td>BCY46</td> <td>30P<td>OC74</td><td>30P</td></td>	BCY46	30P <td>OC74</td> <td>30P</td>	OC74	30P
2N2194A	42P	2N3900	37P	40C152	22P	BCY41	50P <td>BCY54</td> <td>40P</td> <td>OC75</td> <td>22P</td>	BCY54	40P	OC75	22P
2N2217	25P	2N3900A	40P	40C154	22P	BCY43	35P <td>BCY56</td> <td>80P</td> <td>OC76</td> <td>22P</td>	BCY56	80P	OC76	22P
2N2218	20P	2N3901	97P	40C176	20P <td>BCY54</td> <td>32P<td>BSY79</td><td>45P</td><td>OC77</td><td>30P</td></td>	BCY54	32P <td>BSY79</td> <td>45P</td> <td>OC77</td> <td>30P</td>	BSY79	45P	OC77	30P
2N2319	20P	2N3903	20P	40C187	25P <td>BCY58</td> <td>22P<td>BSY90</td><td>37P</td><td>OC78</td><td>20P</td></td>	BCY58	22P <td>BSY90</td> <td>37P</td> <td>OC78</td> <td>20P</td>	BSY90	37P	OC78	20P
2N2320	25P	2N3904	25P	40C188	25P <td>BCY59</td> <td>27P<td>BSY95A</td><td>42P<td>OC79</td><td>20P</td></td></td>	BCY59	27P <td>BSY95A</td> <td>42P<td>OC79</td><td>20P</td></td>	BSY95A	42P <td>OC79</td> <td>20P</td>	OC79	20P
2N2221	20P	2N3905	25P	40C177	27P <td>BCY60</td> <td>87P</td> <td>BSY96</td> <td>15P<td>OC81D</td><td>15P</td></td>	BCY60	87P	BSY96	15P <td>OC81D</td> <td>15P</td>	OC81D	15P
2N2222	25P	2N3906	25P	40C18	84P <td>BCY70</td> <td>15P</td> <td>C450</td> <td>15P<td>OC82</td><td>25P</td></td>	BCY70	15P	C450	15P <td>OC82</td> <td>25P</td>	OC82	25P
2N2222A	25P	2N4058	12P	40C19	24P <td>BCY71</td> <td>20P<td>GT102</td><td>30P<td>OC82D</td><td>15P</td></td></td>	BCY71	20P <td>GT102</td> <td>30P<td>OC82D</td><td>15P</td></td>	GT102	30P <td>OC82D</td> <td>15P</td>	OC82D	15P
2N2267	30P	2N4059	10P	40C20	20P <td>BCY72</td> <td>15P<td>GT113</td><td>30P<td>OC83</td><td>25P</td></td></td>	BCY72	15P <td>GT113</td> <td>30P<td>OC83</td><td>25P</td></td>	GT113	30P <td>OC83</td> <td>25P</td>	OC83	25P
2N2368	15P	2N4060	12P	40C22	20P <td>BCY73</td> <td>15P<td>GT114</td><td>30P<td>OC84</td><td>25P</td></td></td>	BCY73	15P <td>GT114</td> <td>30P<td>OC84</td><td>25P</td></td>	GT114	30P <td>OC84</td> <td>25P</td>	OC84	25P
2N3606	15P	2N4061	12P	40C23	20P <td>BCY79</td> <td>30P<td>GT118</td><td>30P<td>OC139</td><td>25P</td></td></td>	BCY79	30P <td>GT118</td> <td>30P<td>OC139</td><td>25P</td></td>	GT118	30P <td>OC139</td> <td>25P</td>	OC139	25P
2N2369A	15P	2N4062	12P	40C28	17P <td>BCZ10</td> <td>27P<td>GT120</td><td>25P</td><td>OC140</td><td>25P</td></td>	BCZ10	27P <td>GT120</td> <td>25P</td> <td>OC140</td> <td>25P</td>	GT120	25P	OC140	25P
2N2410	42P	2N4244	47P	40C39	47P <td>BCZ11</td> <td>27P<td>GT183</td><td>12P</td><td>OC170</td><td>38P</td></td>	BCZ11	27P <td>GT183</td> <td>12P</td> <td>OC170</td> <td>38P</td>	GT183	12P	OC170	38P
2N4833	27P	2N4248	15P	40C40	20P <td>BD112</td> <td>50P<td>GT680</td><td>80P<td>OC171</td><td>30P</td></td></td>	BD112	50P <td>GT680</td> <td>80P<td>OC171</td><td>30P</td></td>	GT680	80P <td>OC171</td> <td>30P</td>	OC171	30P
2N4843	27P	2N4249	15P	40C41	15P <td>BD117</td> <td>50P<td>GT687</td><td>80P<td>OC172</td><td>30P</td></td></td>	BD117	50P <td>GT687</td> <td>80P<td>OC172</td><td>30P</td></td>	GT687	80P <td>OC172</td> <td>30P</td>	OC172	30P
2N4844	27P	2N4249	15P	40C41	15P <td>BD121</td> <td>50P<td>GT689</td><td>80P<td>OC173</td><td>30P</td></td></td>	BD121	50P <td>GT689</td> <td>80P<td>OC173</td><td>30P</td></td>	GT689	80P <td>OC173</td> <td>30P</td>	OC173	30P
2N5439	22P	2N4250	42P	40C42	15P <td>BD123</td> <td>80P<td>GT689</td><td>80P<td>OC202</td><td>75P</td></td></td>	BD123	80P <td>GT689</td> <td>80P<td>OC202</td><td>75P</td></td>	GT689	80P <td>OC202</td> <td>75P</td>	OC202	75P
2N5440	22P	2N4254	42P	40C43	15P <td>BD123</td> <td>80P<td>GT689</td><td>80P<td>OC202</td><td>75P</td></td></td>	BD123	80P <td>GT689</td> <td>80P<td>OC202</td><td>75P</td></td>	GT689	80P <td>OC202</td> <td>75P</td>	OC202	75P
2N2613	35P	2N4255	42P	40C49	47P <td>BD124</td> <td>80P<td>GT689</td><td>25P<td>OC245</td><td>75P</td></td></td>	BD124	80P <td>GT689</td> <td>25P<td>OC245</td><td>75P</td></td>	GT689	25P <td>OC245</td> <td>75P</td>	OC245	75P
2N2614	30P	2N4284	17P	40C50	82P <td>BD131</td> <td>75P<td>GT687</td><td>22P<td>OC246</td><td>40P</td></td></td>	BD131	75P <td>GT687</td> <td>22P<td>OC246</td><td>40P</td></td>	GT687	22P <td>OC246</td> <td>40P</td>	OC246	40P
2N2646	40P	2N4285	17P	40C51	82P <td>BD132</td> <td>80P<td>GT688</td><td>22P<td>OC249</td><td>75P</td></td></td>	BD132	80P <td>GT688</td> <td>22P<td>OC249</td><td>75P</td></td>	GT688	22P <td>OC249</td> <td>75P</td>	OC249	75P
2N2712	25P	2N4286	17P	40C52	82P <td>BD133</td> <td>80P<td>GT689</td><td>22P<td>OC250</td><td>75P</td></td></td>	BD133	80P <td>GT689</td> <td>22P<td>OC250</td><td>75P</td></td>	GT689	22P <td>OC250</td> <td>75P</td>	OC250	75P
2N2712	25P	2N4287	17P	40C53	82P <td>BDY20</td> <td>105P<td>MAT101</td><td>25P</td><td>OC270</td><td>75P</td></td>	BDY20	105P <td>MAT101</td> <td>25P</td> <td>OC270</td> <td>75P</td>	MAT101	25P	OC270	75P
2N2713	25P	2N4288	15P	40C54	25P <td>BDY61</td> <td>105P<td>MAT120</td><td>25P</td><td>OC271</td><td>75P</td></td>	BDY61	105P <td>MAT120</td> <td>25P</td> <td>OC271</td> <td>75P</td>	MAT120	25P	OC271	75P
2N2714	30P	2N4289	17P	40C55	25P <td>BDY62</td> <td>105P<td>MAT121</td><td>25P</td><td>ORP12</td><td>50P</td></td>	BDY62	105P <td>MAT121</td> <td>25P</td> <td>ORP12</td> <td>50P</td>	MAT121	25P	ORP12	50P
2N2904	20P	2N4290	12P	40C56	25P <td>BF115</td> <td>25P<td>MJ400</td><td>107P<td>ORP60</td><td>40P</td></td></td>	BF115	25P <td>MJ400</td> <td>107P<td>ORP60</td><td>40P</td></td>	MJ400	107P <td>ORP60</td> <td>40P</td>	ORP60	40P
2N2904A	25P	2N4291	15P	40C57	20P <td>BF117</td> <td>47P<td>MJ401</td><td>80P<td>ORP61</td><td>42P</td></td></td>	BF117	47P <td>MJ401</td> <td>80P<td>ORP61</td><td>42P</td></td>	MJ401	80P <td>ORP61</td> <td>42P</td>	ORP61	42P
2N2905	25P	2N4292	15P	40C58	20P <td>BF118</td> <td>47P<td>MJ402</td><td>80P<td>ORP62</td><td>42P</td></td></td>	BF118	47P <td>MJ402</td> <td>80P<td>ORP62</td><td>42P</td></td>	MJ402	80P <td>ORP62</td> <td>42P</td>	ORP62	42P
2N2905A	25P	2N4293	15P	40C59	20P <td>BF119</td> <td>47P<td>MJ403</td><td>102P<td>ST140</td><td>15P</td></td></td>	BF119	47P <td>MJ403</td> <td>102P<td>ST140</td><td>15P</td></td>	MJ403	102P <td>ST140</td> <td>15P</td>	ST140	15P
2N2906	25P	2N4304	47P	40C124	22P <td>BF158</td> <td>15P<td>MJ440</td><td>95P</td><td>ST141</td><td>20P</td></td>	BF158	15P <td>MJ440</td> <td>95P</td> <td>ST141</td> <td>20P</td>	MJ440	95P	ST141	20P
2N2906A	25P	2N4305	47P	40C125	19P <td>BF159</td> <td>35P<td>MJ450</td><td>97P<td>TS184</td><td>62P</td></td></td>	BF159	35P <td>MJ450</td> <td>97P<td>TS184</td><td>62P</td></td>	MJ450	97P <td>TS184</td> <td>62P</td>	TS184	62P
2N2907	23P	2N4306	47P	40C126	19P <td>BF163</td> <td>35P<td>MJ460</td><td>125P<td>TS184</td><td>40P</td></td></td>	BF163	35P <td>MJ460</td> <td>125P<td>TS184</td><td>40P</td></td>	MJ460	125P <td>TS184</td> <td>40P</td>	TS184	40P
2N2908	23P	2N4307	47P	40C127	19P <td>BF164</td> <td>35P<td>MJ470</td><td>125P<td>TS184</td><td>40P</td></td></td>	BF164	35P <td>MJ470</td> <td>125P<td>TS184</td><td>40P</td></td>	MJ470	125P <td>TS184</td> <td>40P</td>	TS184	40P
2N2909	23P	2N4308	47P	40C128	19P <td>BF165</td> <td>35P<td>MJ480</td><td>125P<td>TS184</td><td>40P</td></td></td>	BF165	35P <td>MJ480</td> <td>125P<td>TS184</td><td>40P</td></td>	MJ480	125P <td>TS184</td> <td>40P</td>	TS184	40P
2N2925	15P	2N5029	47P	40C129	42P <td>BF170</td> <td>35P<td>MJ491</td><td>137P<td>TS184</td><td>40P</td></td></td>	BF170	35P <td>MJ491</td> <td>137P<td>TS184</td><td>40P</td></td>	MJ491	137P <td>TS184</td> <td>40P</td>	TS184	40P
2N2925	15P	2N5030	47P	40C130	42P <td>BF173</td> <td>19P<td>MJ3430</td><td>50P<td>TS186</td><td>11P</td></td></td>	BF173	19P <td>MJ3430</td> <td>50P<td>TS186</td><td>11P</td></td>	MJ3430	50P <td>TS186</td> <td>11P</td>	TS186	11P
2N2926	10P	2N5039	42P	40C179	45P <td>BF177</td> <td>15P<td>MJ3370</td><td>80P<td>TS187</td><td>11P</td></td></td>	BF177	15P <td>MJ3370</td> <td>80P<td>TS187</td><td>11P</td></td>	MJ3370	80P <td>TS187</td> <td>11P</td>	TS187	11P
2N2926	10P	2N5172	12P	40C180	50P <td>BF178</td> <td>25P<td>MJ3370</td><td>80P<td>TS188</td><td>12P</td></td></td>	BF178	25P <td>MJ3370</td> <td>80P<td>TS188</td><td>12P</td></td>	MJ3370	80P <td>TS188</td> <td>12P</td>	TS188	12P
2N2926V	10P	2N5174	12P	40C181	40P <td>BF179</td> <td>30P<td>MJ3370</td><td>80P<td>TS189</td><td>12P</td></td></td>	BF179	30P <td>MJ3370</td> <td>80P<td>TS189</td><td>12P</td></td>	MJ3370	80P <td>TS189</td> <td>12P</td>	TS189	12P
2N3011	12P	2N5175	12P	40C182	40P <td>BF180</td> <td>30P<td>MJ3370</td><td>80P<td>TS190</td><td>12P</td></td></td>	BF180	30P <td>MJ3370</td> <td>80P<td>TS190</td><td>12P</td></td>	MJ3370	80P <td>TS190</td> <td>12P</td>	TS190	12P
2N3012	12P	2N5176	12P	40C183	40P <td>BF181</td> <td>30P<td>MJ3370</td><td>80P<td>TS191</td><td>12P</td></td></td>	BF181	30P <td>MJ3370</td> <td>80P<td>TS191</td><td>12P</td></td>	MJ3370	80P <td>TS191</td> <td>12P</td>	TS191	12P
2N3053	18P	2N5224	30P	40C184	40P <td>BF182</td> <td>30P<td>MJ3370</td><td>80P<td>TS192</td><td>12P</td></td></td>	BF182	30P <td>MJ3370</td> <td>80P<td>TS192</td><td>12P</td></td>	MJ3370	80P <td>TS192</td> <td>12P</td>	TS192	12P
2N3054	46P	2N5245	45P	40C185	40P <td>BF183</td> <td>30P<td>MJ3370</td><td>80P<td>TS193</td><td>12P</td></td></td>	BF183	30P <td>MJ3370</td> <td>80P<td>TS193</td><td>12P</td></td>	MJ3370	80P <td>TS193</td> <td>12P</td>	TS193	12P
2N3055	46P	2N5246	45P	40C186	40P <td>BF184</td> <td>30P<td>MJ3370</td><td>80P<td>TS194</td><td>12P</td></td></td>	BF184	30P <td>MJ3370</td> <td>80P<td>TS194</td><td>12P</td></td>	MJ3370	80P <td>TS194</td> <td>12P</td>	TS194	12P
2N3133	30P	2N5249	57P	40C187	40P <td>BF185</td> <td>20P<td>MJ3370</td><td>80P<td>TS195</td><td>12P</td></td></td>	BF185	20P <td>MJ3370</td> <td>80P<td>TS195</td><td>12P</td></td>	MJ3370	80P <td>TS195</td> <td>12P</td>	TS195	12P
2N3134	30P	2N5250	57P	40C188	40P <td>BF186</td> <td>20P<td>MJ3370</td><td>80P<td>TS196</td><td>12P</td></td></td>	BF186	20P <td>MJ3370</td> <td>80P<td>TS196</td><td>12P</td></td>	MJ3370	80P <td>TS196</td> <td>12P</td>	TS196	12P
2N3135	30P	2N5251	57P	40C189	40P <td>BF187</td> <td>20P<td>MJ3370</td><td>80P<td>TS197</td><td>12P</td></td></td>	BF187	20P <td>MJ3370</td> <td>80P<td>TS197</td><td>12P</td></td>	MJ3370	80P <td>TS197</td> <td>12P</td>	TS197	12P
2N3136	30P	2N5252	57P	40C190	40P <td>BF188</td> <td>20P<td>MJ3370</td><td>80P<td>TS198</td><td>12P</td></td></td>	BF188	20P <td>MJ3370</td> <td>80P<td>TS198</td><td>12P</td></td>	MJ3370	80P <td>TS198</td> <td>12P</td>	TS198	12P
2N3137	30P	2N5253	57P	40C191	40P <td>BF189</td> <td>20P<td>MJ3370</td><td>80P<td>TS199</td><td>12P</td></td></td>	BF189	20P <td>MJ3370</td> <td>80P<td>TS199</td><td>12P</td></td>	MJ3370	80P <td>TS199</td> <td>12P</td>	TS199	12P
2N3138	30P	2N5254	57P	40C192	40P <td>BF190</td> <td>20P<td>MJ3370</td><td>80P<td>TS200</td><td>12P</td></td></td>	BF190	20P <td>MJ3370</td> <td>80P<td>TS200</td><td>12P</td></td>	MJ3370	80P <td>TS200</td> <td>12P</td>	TS200	12P
2N3139	30P	2N5255	57P	40C193	40P <td>BF191</td> <td>20P<td>MJ3370</td><td>80P<td>TS201</td><td>12P</td></td></td>	BF191	20P <td>MJ3370</td> <td>80P<td>TS201</td><td>12P</td></td>	MJ3370	80P <td>TS201</td> <td>12P</td>	TS201	12P
2N3140	30P	2N5256	57P	40C194	40P <td>BF192</td> <td>20P<td>MJ3370</td><td>80P<td>TS202</td><td>12P</td></td></td>	BF192	20P <td>MJ3370</td> <td>80P<td>TS202</td><td>12P</td></td>	MJ3370	80P <td>TS202</td> <td>12P</td>	TS202	12P
2N3141	30P	2N5257	57P	40C195	40P <td>BF193</td> <td>20P<td>MJ3370</td><td>80P<td>TS203</td><td>12P</td></td></td>	BF193	20P <td>MJ3370</td> <td>80P<td>TS203</td><td>12P</td></td>	MJ3370	80P <td>TS203</td> <td>12P</td>	TS203	12P
2N3142	30P	2N5258									

## Integrated Circuits

CA3000	180p	FJH131	25p	SN7441AN	
CA3005	170p	FJH141	25p		75p
CA3005	170p	FJH151	25p	SN7442	105p
CA3007	825p	FJH161	25p	SN7446	105p
CA3007	825p	FJH171	25p	SN7467	135p
CA3012	85p	FJH181	25p	SN7448	120p
CA3013	105p	FJH221	25p	SN7450	20p
CA3014	124p	FJH231	25p	SN7451	20p
CA3018	84p	FJH241	25p	SN7453	20p
CA3018A		FJH251	25p	SN7454	20p
CA3019	84p	FJH261	25p	SN7472	20p
CA3020	120p	FJH31	60p	SN7473	40p
CA3020A		FJH321	60p	SN7474	40p
CA3021	156p	FJH141	135p	SN7475	45p
CA3022	156p	FJH191	60p	SN7476	45p
CA3023	126p	FJH211	125p	SN7486	33p
CA3026	100p	FJH251	125p	SN7490	87p
CA3028A	74p	FJH101	125p	SN7492	87p
CA3028B		FJY101	25p	SN7493	87p
CA3029	87p	IC12	250p	SN7496	87p
CA3029A		L900	40p	SN74107	52p
	165p	L914	40p	SN74153	
CA3030	137p	L923	40p		135p
CA3035	182p	LM380	22p	SN74154	
CA3036	182p	MC7940P	25p		200p
CA3039	82p	MC7940P	25p	SN74160	
CA3041	105p	MC788P	145p		180p
CA3042	109p	MC790P	145p		20p
CA3043	137p	MC792P	68p	SN7463	25p
CA3044	130p	MC799P	68p	SN7464	20p
CA3045	137p	MC1304P	200p	SN74165	25p
CA3046	81p	MC1305P	225p	SN74192	
CA3048	804p	MC1305P	225p	SN74193	175p
CA3049	180p	MC838P	58p	TA2A21	175p
CA3052	185p	MC1435P	345p	TA2A42	
CA3053	46p	MC1552G	455p		455p
CA3054	105p	MC1709C	94p	TA2A43	
CA3055	140p	MC1709C	94p	TA2A93	87p
FCH101	85p	MC4000P	25p	TA3000	175p
FCH112	105p	PA222	55p	TA3010	125p
FCH131	59p	PA222	55p	TA3020	125p
FCH131	59p	PA222	55p	TA3030	125p
FCH151	105p	PA237	81p	TA4A35	147p
FCH171	105p	PA237	81p	TA5A21	132p
FCH181	105p	PA246	150p	TA5A22	380p
FCH191	105p	PA424	235p	TA5A30	360p
FCH201	180p	PA264	180p	TA5A11	445p
FCH221	180p	SN7400	20p	TA5A10	155p
FCH231	150p	SN7401	20p	TA5A10	155p
FCH241	180p	SN7402	20p	TL403D	15p
FCH251	180p	SN7403	20p	SL792C	147p
FCH261	180p	SN7404	20p	UA702A	285p
FCH271	180p	SN7405	20p	UA703C	137p
FCH281	180p	SN7406	20p	UA703C	137p
FCH291	180p	SN7407	20p	UA703C	137p
FCH301	180p	SN7408	20p	UA710C	125p
FCH311	180p	SN7409	20p	UA710C	125p
FCH321	180p	SN7410	20p	UA716C	187p
FCH331	180p	SN7411	20p	UA716C	187p
FCH341	180p	SN7412	20p	UA730C	160p
FCH351		SN7413	20p	UA741C	80p
FJH101	25p	SN7420	20p		

## BRIDGE

RECTIFIERS	100 PIV 4A	50p
PLASTIC	200 PIV 4A	55p
ENCAPSULATED	400 PIV 4A	65p
	600 PIV 4A	70p
600 PIV 1A	50 PIV 6A	45p
50 PIV 2A	100 PIV 6A	55p
100 PIV 2A	200 PIV 6A	65p
200 PIV 2A	400 PIV 6A	75p
400 PIV 2A	600 PIV 6A	85p

## SILICON RECTIFIERS

MINIATURE SERIES	WIRE ENDED PLASTIC		
	IN	PL	CL
	1 AMP	1.5 AMP	3 AMP
4001 50PIV	7p	8p	18p
4002 100PIV	7p	9p	20p
4003 200PIV	8p	10p	22p
4004 400PIV	8p	10p	25p
4005 600PIV	10p	12p	26p
4006 800PIV	12p	15p	27p

4007	1000PIV	15p	18p	30p
		50+ less 15%	100+ less 20%	

SILICON RECTIFIERS STUD MOUNTING				
	6A	10A	17-5A	35A
100PIV	—	45p	50p	\$1.22
200PIV	25p	50p	55p	\$1.42
400PIV	30p	55p	62p	\$1.77
600PIV	32p	60p	72p	\$2.12
800PIV	35p	75p	87p	\$2.47

1000PIV	40p	85p	£1.05	£2.77
	50+ less 15%	100+ less 20%		

ZENER DIODES		
400MW	1.5 WATT	10 WATT
3.3-33 V	2.4-100	3.9-100V
10p each	25p each	40p each
25+ less 15%	100+ less 20%	

**TRANSISTOR DISCOUNTS:-** 12 + 10%

**S.A.E. FOR FULL LISTS.**


## VALVES

OA2	35p	25Z4	80p	EL95	35p
OB2	45p	25Z5	42p	EM80	45p
OZ4	30p	35Z6	65p	EM81	60p
LL4	20p	30C15	80p	EM84	35p
IR5	40p	30C17	90p	EM85	£1.00
IR5	30p	30C18	80p	EM87	70p
IR5	25p	30C19	80p	EY51	40p
IU4	30p	30FL12	75p	EP82	40p
IU5	30p	30FL12	120p	EY87	42p
2D21	35p	30FL14	95p	EZ40	55p
3Q4	50p	30L15	85p	EZ41	50p
384	35p	30L17	80p	EZ80	27p
3B4	35p	30L19	80p	EZ81	28p
3B4	75p	30L20	80p	EZ82	45p
JU4	35p	30PL1	75p	GZ34	30p
JY3	40p	30PL13	83p	KT66	£2.05
JY3	40p	30PL14	90p	KT88	£2.00
3Z4G	40p	35L6	50p	MU14	75p
930/2L2	80p	35W4	35p	PAB080	40p
930/2L2	40p	35Z4	35p	PC80	50p
9A67	40p	35Z5	50p	PC85	80p
9AG7	40p	35Z6	50p	PC88	60p
6AK5	35p	50B5	50p	PC97	45p
6AK6	60p	50C5	50p	PC900	45p
6AL5	20p	80	55p	PC84	40p
6AM6	30p	85A2	40p	PC85	40p
6AM7	35p	85C2	50p	PC88	50p
6AS7	40p	19Z5	50p	PC89	50p
6AT6	35p	5763	70p	PCCI89	55p
6AU6	25p	6146	160	PCF80	80p
6AV6	30p	AZ31	55p	PCF82	34p
6BA6	25p	CY21	35p	PCF84	80p
6BE6	30p	DAF91	30p	PCF86	80p
6BF6	35p	DAF96	30p	PCF900	80p
6BJ6	50p	DF91	22p	PCF901	50p
6BQ7A	40p	DF96	45p	PCF802	50p
6BR7	50p	DK91	40p	PCF805	80p
6BR8	70p	DK92	55p	PCF806	70p
6BW6	55p	DK96	50p	PCF808	75p
6BZ6	35p	DL91	35p	PCF83	40p
6BZ8	40p	DL94	45p	PCF83	45p
6C4	33p	DL96	45p	PCF84	45p
6C0D6	125p	DM70	40p	PLC85	40p
6CL6	50p	DY86	32p	PLC86	45p
6CW4	65p	DY87	33p	PFL200	85p
6E6	65p	ELB0C	100p	PL85	50p
6F6G	35p	ELB0F	100p	PL86	50p
6F13	45p	EABC80	35p	PL82	45p
6F14	70p	EAF42	35p	PL83	45p
6F15	65p	EB91	20p	PL84	40p
6F18	35p	EBF41	55p	PL500	75p
6F19	35p	EBF41	50p	PL504	80p
6H6	17p	EBC0	40p	PY33	65p
6J4	50p	EBF83	40p	PY33	63p
6J5	25p	EBF89	32p	PY80	40p
6J5GT	30p	EBL21	60p	PY81	30p
6J7	20p	EC06	80p	PY82	35p
6J7	45p	EC08	60p	PY83	35p
6K6G	40p	ECG40	65p	PY81	40p
6L6GT	30p	ECG40	30p	PY800	40p
6LD20	50p	EC085	40p	PY801	50p
6Q7	40p	EC088	40p	U25	80p
6SA7	40p	ECF80	35p	U26	80p
6SG7	40p	ECF82	35p	U30	40p
6S7	40p	ECF86	65p	U35	35p
6S7	40p	ECF87	50p	U191	75p
6SL7	35p	ECH35	100p	U281	40p
6SN7	35p	ECH42	75p	U282	40p
6SQ7	40p	ECH81	30p	U301	40p
6T4	65p	ECH83	45p	U301	£1.30
6T6	65p	ECG80	45p	UABC80	40p
6V6GT	35p	ECB82	35p	UAF42	55p
6X4	35p	ECL83	70p	UBC41	50p
6X5G	30p	ECL86	40p	UBC81	40p
6X6GT	40p	EP37A	120p	UBR80	40p
102	50p	EP89	50p	UCB99	35p
10E1	75p	EP81	80p	UCB84	50p
10P13	60p	EP41	65p	UCB85	40p
10P14	£1.10	EP42	70p	UCF80	55p
12A26	30p	EP80	25p	UCB82	60p
12AT7	30p	EP86	35p	UCH42	70p
12AU7	30p	EP80	80p	UCB81	40p
12AX7	35p	EP81	80p	UCL82	35p
12AV6	40p	EP91	30p	UCL83	60p
12BA6	40p	EP92	35p	UF41	60p
12BE6	40p	EP183	35p	UF80	35p
12BH7	45p	EP184	35p	UF89	40p
12AQ5	35p	EH90	40p	UF85	40p
20E1	75p	EL38	50p	U1	75p
20F2	65p	EL38	£1.25	UL84	40p
20L1	£1.10	EL41	60p	UY41	48p
20P1	50p	EL42	65p	UY85	40p
20G	60p	EL81	55p	VR105/30	38p
20P4	£2.10	EL84	25p	VR150/30	35p
20P5	£1.20	EL84	25p	VR151/30	35p
25L6	60p	EL91	65p	<i>for postage</i>	

DIODES & RECTIFIERS					
1N34A	10p	BA164	15p	7JM7M	37p
1N35A	10p	BA165	15p	OA5	17p
1N916	10p	BA166	7p	OA6	12p
AA119	7p	BAY31	7p	OA10	20p
AA129	10p	BAY38	15p	OA9	19p
AAZ13	10p	BY100	10p	OA47	10p
AAZ15	10p	BY110	25p	OA70	10p
BA101	15p	BY232	3p	OA73	10p
BA102	30p	BY124	15p	OA79	75p
BA110	25p	BY126	12p	OA81	85p
BA111	27p	BY127	15p	OA85	75p
BA112	70p	BY164	63p	OA90	75p
BA115	7p	BY210	85p	OA91	75p
BA116	32p	BY211	85p	OA95	75p
BA142	32p	BY212	85p	OA900	75p
BA144	12p	BYZ13	25p	OA202	10p
RI445	20p	BYZ16	40p	OA210	17p
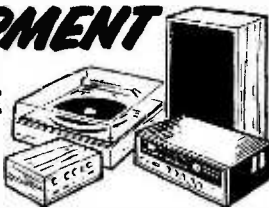
# HI-FI EQUIPMENT

**SAVE UP TO  
33 1/3% OR MORE  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!**



## RECORD DECKS

BSR	
UA80†	\$4.97
CI29†	\$8.50
MP60	\$10.40
610	\$14.07
510	\$11.50
810	\$22.95
810	\$23.45
MP60 TPD1	\$17.12
MP60 TPD2	\$15.40
610 TPD1	\$20.35
510 TPD1	\$18.20
210 Package	\$9.55
HT 70	\$14.99
HT 70 Pack	\$21.60

GARRARD	
2025 T/C*	\$8.50
405*	\$9.25
3-300*	\$8.50
SP25 III	\$10.50
SP25/G800*	\$14.50
SL45B	\$13.45
AP76	\$18.95
AP76/G800*	\$22.50
SL75B	\$23.25
SL75B	\$23.00
SL95B	\$32.50
401	\$26.80
ZERO 1004	\$41.95
ZERO 1008	\$37.50

\* Stereo Cartridge + Mono  
All others less cartridge  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied with  
cartridge ready  
wired in teak  
veneered plinth with  
cover.

Garrard 2025T/C/TAHCD  
Garrard SP25 III/TAHCD  
Garrard SP25 III/G800  
Garrard SP25 III/M75-6  
Garrard SP25 III/M75-4  
Garrard SP25 III/M75-5  
SP25 III/G800 (Playden P&C)  
Garrard AP76/G800  
Garrard AP76/M75-6  
Garrard AP76/M55E  
Garrard AP76/M75-4  
BSR McDonald MP60/AT55  
Golding GL75/G800  
Golding GL75/G800E  
Carriage 50p any item

## SINCLAIR EQUIPMENT

Project 60  
Package  
offers.

2 x Z30 amplifier, stereo 60 pre-amp, P25  
power supply. £15.95 Carr. 37p. Or with  
P26 power supply £18.00 Carr. 37p. 2 x Z30  
amplifier, stereo 60 pre-amp, P28 power  
supply. £20.25 Carr. 37p.  
Transformer for P25. £2.97† extra.  
Add to any of the above £4.45 for active  
filter unit and £13.90 for pair of Q16 speakers.  
Project 60 FM Tuner £16.95, Carr. 37p.  
All other Sinclair products in stock.  
2000 Amp £23.50 Carr. 37p.; 3000 Amp  
£30.95 Carr. 37p.; Neoteric Amp £43.95  
Carr. 37p. IC12 £1.80 p. & p. 10p.

NEW PROJECT 605 - £20.97, Carr. 37p.

## LATEST CATALOGUE


Our new 6th edition gives full details of a  
comprehensive range of HI-FI EQUIP-  
MENT, COMPONENTS, TEST EQUIP-  
MENT AND COMMUNICATIONS EQUIP-  
MENT. FREE DISCOUNT COUPONS

VALUE 50p  
272 pages  
fully illus-  
trated and  
detailing  
thousands of  
bargains.

SEND NOW


ONLY  
37p  
P & P  
10p

## TELETON SAQ-206B STEREO AMPLIFIER

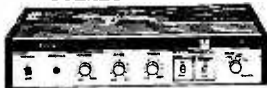

Latest exciting release. Brand new model.  
6 + 6 watts rms. Inputs for mag, xtal, aux.  
tape. Volume, bass, treble, sliding balance,  
scratch filter and loudness controls.  
OUR PRICE £18.50 Carr. 37p.

## SKYWOOD CXK03 COMMUNICATION RECEIVER

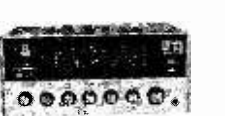

Solid state. Coverage on 5 bands 200-420  
KHz and .55 to 30 MHz. Illuminated slide  
rule dial. Bandspread. Aerial tuning. BFO.  
AVC. ANL. 'S' meter. AM/CW/SSB. Integrated  
speaker and phone socket. Operation  
220/240V AC or 12V DC. Size 325 x 266 x 150  
mm. Complete with instructions and circuit.  
£28.50. Carr. 50p

## LAFAYETTE LA. 324 STEREO



Compares with amplifiers up to £40.  
OUR PRICE £24. Carr. 37p.

## TAPE CASSETTES

Top quality in plastic library boxes.  
C60 60 min 30p. 3 for 75p. 10 for £2.95  
C90 90 min 45p. 3 for £1.95 10 for £2.30  
C120 120 min 52p. 3 for £1.35 10 for £2.20  
Cassette Head Cleaner 30p. P. & P. 10p. Extra

## ★ TRANSISTORISED FM TUNER



6 TRANSISTOR  
HIGH QUALITY  
TUNER. SIZE  
ONLY 6 1/4 x 4 1/4 in.  
3 I.F. stages.  
Double tuned dis-  
criminator. Ample  
output to feed most  
amplifiers. Operates on 9 V battery. Coverage  
88-108Mc/s. Ready built ready for use. P&P  
£8.00 multiplex adaptors £4.97†.



Battery operated,  
11 meg input. 26  
ranges. Large 4 1/2"  
mirror scale. Size  
5 1/2" x 4 1/2" x 2 1/2".  
DC VOLTS 0.3 -  
1200V. AC VOLTS  
2 - 300V RMS 50 -  
800V P-P. D.C. CUR-  
RENT 12 - 12MA.  
Resistance up to 2000M ohm. Decibels  
-20 to +51 db. Complete with leads/instruc-  
tions. £17.50. P. & P. 20p.



## 230 VOLT A.C. 50 CYCLES RELAYS


Brand new. 3 sets of  
chanceux contacts at  
5 amp rating. 50p each.  
P. & P. 10p (100 lots £40)  
Quantities available.
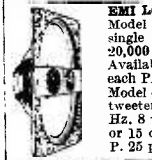
## HOMER INTERCOMS



Ideal for home,  
office, stores, fac-  
tories, etc. Supplied  
complete with bat-  
teries, cable and  
free instructions.


2 Station £2.97, 3 Station £5.25, P. & P. 15p.  
4 Station £6.62, P. & P. 17p.




EMI LOUDSPEAKERS  
Model 350. 13" x 8" with  
single tweeter/crossover. 20-  
20,000 Hz. 15 watt RMS.  
Available 8 or 15 ohms. £7.50  
each P. & P. 37p.  
Model 450. 13" x 8" with twin  
tweeter/crossover. 55-13,000  
Hz. 8 watt RMS. Available 8  
or 15 ohms. £3.50 each. P. & P. 25 p.



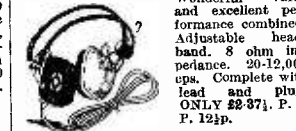
TE 1018 DE-LUXE  
MONO HIGH IMPE-  
DANCE HEADSET  
Sensitive, soft earpads.  
adjustable headband.  
Magnetic impedance  
2,600 ohms.  
£1.97, P. & P. 15p.



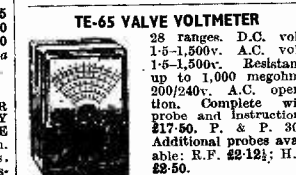
HOSIDEN DHO-25 STEREO HEADPHONES  
Wonderful value  
and excellent per-  
formance combined.  
Adjustable head-  
band. 8 ohm im-  
pedance. 20-12,000  
cps. Complete with  
lead and plug.  
ONLY £2.37, P. & P. 12p.



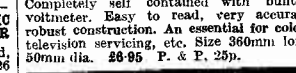TE-65 VALVE VOLTMETER  
28 ranges. D.C. volts  
1.5-1,500V. A.C. volts  
1.5-1,500V. Resistance  
up to 1,000 megohms.  
200/240V. A.C. opera-  
tion. Complete with  
probe and instructions.  
£17.50. P. & P. 30p.  
Additional probes avail-  
able: R.F. £2.12; H.V.  
£2.50.



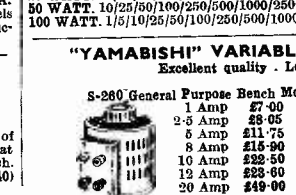
E.H.T. TESTER 0-30KV  
Completely self contained with built-in  
voltmeter. Easy to use, very accurate.  
Robust construction. An essential for colour  
television servicing, etc. Size 360mm long.  
50mm dia. £8.95 P. & P. 25p.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS  
Excellent quality - Low price - Immediate delivery

S-260 General Purpose Bench Mounting	
1 Amp	£7.00
2.5 Amp	£8.00
5 Amp	£11.75
8 Amp	£15.90
10 Amp	£22.50
12 Amp	£23.60
20 Amp	£49.00

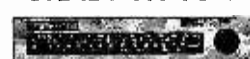
## SPECIAL OFFER! SINCLAIR PROJECT 60 STEREO FM TUNER



The first tuner in the world to use the phas-  
lock loop principle - as used for receiving  
signals from space craft because of its vastly  
improved signal to noise ratio. Provides  
fantastic results even in difficult areas.  
Tuning range 87.5 to 108MHz. Automatic  
stereo indicator. Sensitivity: 2µV. AFC  
range ± 200KHz. Signal to noise ratio:  
60dB. Output voltage 2 x 150mV. Operating  
voltage 25-30V DC. Size 93 x 40 x  
207 mm. REC. LIST PRICE £25.  
OUR PRICE £16.95 P. & P. 25p  
ONLY  
Unrepeatable offer - buy now and save over £8.



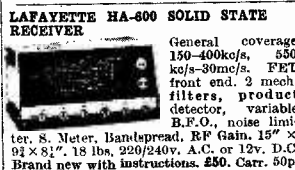UR-1A SOLID STATE COMMUNICATION  
RECEIVER  
4 Bands covering 550kc/s-30mc/s. FET.  
S Meter. Variable BFO for SSB. Built-in  
Speaker. Bandspread. Bandwidth Control.  
220/240V. A.C. or 12V. D.C. 12 1/2" x 4 1/2" x 7".  
Brand new with instructions. £25. Carr. 37p.



LAFAYETTE HA-800 SOLID STATE  
RECEIVER  
General coverage  
150-400kc/s. 550  
kc/s-30mc/s. FET  
front end. 2 mech.  
filters. product  
detector. variable  
B.F.O. noise limit-  
ter. S. Meter. Bandspread. RF Gain. 15" x  
9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C.  
Brand new with instructions. £50. Carr. 50p.



U4812 MULTIMETER  
Extremely sturdy instrument for general  
electrical use. 607 o.p.v.  
0/31/3/7.5/30/60/150/300/  
600/900 VDC and 75mV.  
0/3/1.5/7.5/30/60/150/300  
600/900 VAC.  
0/300mA/1/1.5/6/15/60/150  
600MA/1/5/6 AMP. D.C.  
0/1.5/6/15/60/150/600MA/  
1/5/6 AMP. AC.  
0/200 Ω/3K/20K Ω.  
Accuracy DC 1%. AC 1-5%.



TE-1035 STEREO  
HEADPHONES  
Low cost high performance  
stereo headphones.  
Foam rubber ear cups.  
Adjustable head-band.  
8 ohm impedance. 25-  
18,000 Hz. With lead and  
stereo jack plug. ONLY  
£1.97, P. & P. 12p.



MCA-250 AUTOMATIC  
VOLTAGE  
STABILISER  
Input 88-125 VAC. or  
175-250VAC. Output 120V  
AC, or 240 VAC. 200 VA  
rating. £1.97. Carr. 50p.

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous  
enamel. Heavy duty brush wiper. Continuous rating. Wide range  
ex-stock. Single hole fixing. 3in. dia. shafts. Bulk quantities available.  
25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 72p. P. & P. 7p.  
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.05 P. & P. 7p.  
100 WATT. 10/25/50/100/250/500/1000 or 2500 ohms. £1.37 P. & P. 7p.

# G.W.SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON. W.1  
27 TOTTENHAM CT. RD. LONDON. W.1  
3 LISLE STREET, LONDON. W.C.2  
34 LISLE STREET, LONDON. W.C.2  
311 EDGWARE ROAD, LONDON. W.2

Tel: 01-637 2232  
Tel: 01-636 3715  
Tel: 01-437 8204  
Tel: 01-437 9155  
Tel: 01-262 0387

CALLERS  
WELCOME  
MONDAY TO  
SATURDAY  
9AM-6PM

All Mail Orders to -  
11-12, Paddington Green,  
London, W.2  
Tel: 01-262 6592



# TECHNICAL TRAINING

*in radio television  
and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunications Techns'. Certs.
- Radio Amateurs' Examination
- General Radiocommunications Certificate
- C. & G. Radio Servicing Theory
- General Certificate of Education, etc.

Now available Colour T.V. Servicing

**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics

Accredited by the CACC.

Member of the ABCC.

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam) .....

NAME .....  
(BLOCK CAPITAL PLEASE)

ADDRESS .....

AGE.....OCCUPATION .....

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
Dept. LA28 Intertext House, Stewarts Road,  
London, S.W.8 4UJ



## "PACK UP YOUR TROUBLES IN OUR NEW KIT BAG"

Chadacre Electronics Limited, are pleased to announce that the following modules, may now be purchased in Kit-Form\*:

MODULE	BUILT & TESTED KIT	
	£	£
4300 Phase Simulator	9.00	5.50
4310 Microphone Amp	11.00	7.00
4311 Equaliser	9.00	5.50
4312 Stereo Output Amp	9.00	5.50
4315 Stereo V.U. Driver Amp	9.00	5.50
4316 Mixing Amp	7.00	3.75
6301 I.C. Ring Modulator	15.00	7.50
4317 Stereo Headphone Amp	4.25	—
4318 Stereo Buffer/Bridging Amp	4.00	—



\* Kits are complete with all Capacitors, Resistors, Inductors, Transistors, Printed Circuit Board & Illustrated Data Sheet. All orders despatched by return. If you require further information about these and other modules, send just 25p for our illustrated catalogue.  
20% Discount on quantities of 10 or more mixed units.  
P & P Allow 25p/Module.  
Free on all orders of £20 or more.

**chadacre  
electronics Ltd**

43 CHADACRE AVENUE, CLAYHALL,  
ILFORD, ESSEX. TEL. 01-550 7119.



## M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

**NEW RETAIL PREMISES NOW OPEN IN BISHOPGATE STREET.** Near City Station. Everything for the Ham. Give us a call, G8BUU at your service.

**PYE AM25B VANGUARDS.** 12 volt Boot mounting radio-telephones. 20 watts RF output from QV03/20A. High-band and low-band in stock. Ideal for 2 or 4 metre mobile operation. Less mike, control box and speaker. £20 each plus carr. 90p. U.K.  
24 volt High-band version of above. £17.50 plus carr. 90p. U.K.

**EDDYSTONE 770U Mk. II RECEIVERS.** As new. £120

**EDDYSTONE 770R.** 19 to 165 Mc/s in 6 Bands. AM, NBFM, FM, CW, and noise limiter. £85 plus £2 P./P.

**EDDYSTONE 770U.** As above but covers 145 to 500 Mc/s. £100 plus £2 P./P.

**HAMMARLUND SP600 RECEIVERS** in clean condition. £90 plus £2 P./P.

**PYE CAMBRIDGE.** Boot Mounting High-band and low-band. Less mike, control-box and speaker. Ideal for mobile on 2 metres. £27.50 plus carr. 50p. U.K.

**QZ06-20.** Brand new quick heat version of the 6146. Ideal for low drain mobile rigs. £1.75 plus carr. 10p. U.K.

**BRAND NEW 2 1/2sq. 500uA METERS.** Only £1.20 plus carr. 10p. U.K.

**BRAND NEW COSSOR PA UNITS** with YL1020 and YL1000 quick heat valves. Hi/low band. Ideal mobile work. £6 each plus 25p. carr. U.K.

**MOTOROLA 1N4007 DIODES.** 1000 P.I.V. 1 Amp. 12p each. 3p postage

**1lb. REELS OF SOLDER.** 24 S.W.G. 60/40. 75p Reel plus 10p postage

**REV. COUNTERS.** Tape recorder type. 35p each plus 5p carr.

Send SAE for full lists with many bargains of general interest.

# BI-PRE-PAK



## TELEPHONE DIALS

Standard Post Office type.  
Guaranteed in working order.

**ONLY 50p**

## COMPLETE TELEPHONES

EX-G.P.O. NORMAL HOUSEHOLD TYPE



**95p**

EACH  
P. & P.  
35p  
each.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries, 0-3 to 0-5V, 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, approx. quantity, counted by weight	50p
H4	250	Mixed Resistors, approx. quantity counted by weight	50p
H7	40	Wirewound Resistors, Mixed types and values.	50p
H8	4	BY127 Sil. Recs, 1000 PIV, 1 amp, plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/112/13 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



## OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.

## FULLY TESTED AND MARKED SEMICONDUCTORS

	6p		6p
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
AC177	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF186	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-20	2N1306-7	0-20
BC107	0-10	2N1308-9	0-22
BC108	0-10	2N3819FET	0-45
BC109	0-10		
BF194	0-15		
BF274	0-20	Power Transistors	0-50
BFY50	0-15	OC20	0-30
BSY25	0-13	OC23	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-10	AD149	0-30
OC41	0-15	AU710	1-25
OC44	0-13	2S034	0-25
OC45	0-10	2N3055	0-50
OC71	0-10		
OC72	0-10	Diodes	
OC81	0-13	AA742	0-10
OC81D	0-13	OA95	0-09
OC83	0-18	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-15	IN9114	0-07

## F.E.T. PRICE

## BREAKTHROUGH !!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+20p each.



## BULK BUYING CORNER

NPN/PPN Silicon Planar Transistors, mixed, untested, similar to 2N705/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BY31-36, £4-30 per 1,000.

NPN/PPN Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

## 1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.  
IN4004, 500+ at 3p each; 1,000+ at 4p each.  
IN4006, 500+ at 6p each; 1,000+ at 5p each.  
IN4007, 500+ at 8p each; 1,000+ at 7p each.

## FREE CATALOGUE FOR



TRANSISTORS,  
RECTIFIERS,  
DIODES,  
INTEGRATED  
CIRCUITS,  
FULL PRE-PAK  
LISTS

## 8 RELAYS FOR VARIOUS TYPES P & P 25p £1

## COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each**  
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested			
Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	50p	25p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

## INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	10p	9p	8p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	20p	18p	15p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 1/2 P Gate	40p	35p	30p

## LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 16p each.

## BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

**B.P.I. Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. **The Ilika Radio Valve & Transistor Data Book 9th Edition;** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.


NAME.....

ADDRESS .....

MINIMUM ORDER 50p. CASH WITH ORDER  
PLEASE. Add 10p post and packing per order  
OVERSEAS ADD EXTRA FOR POSTAGE
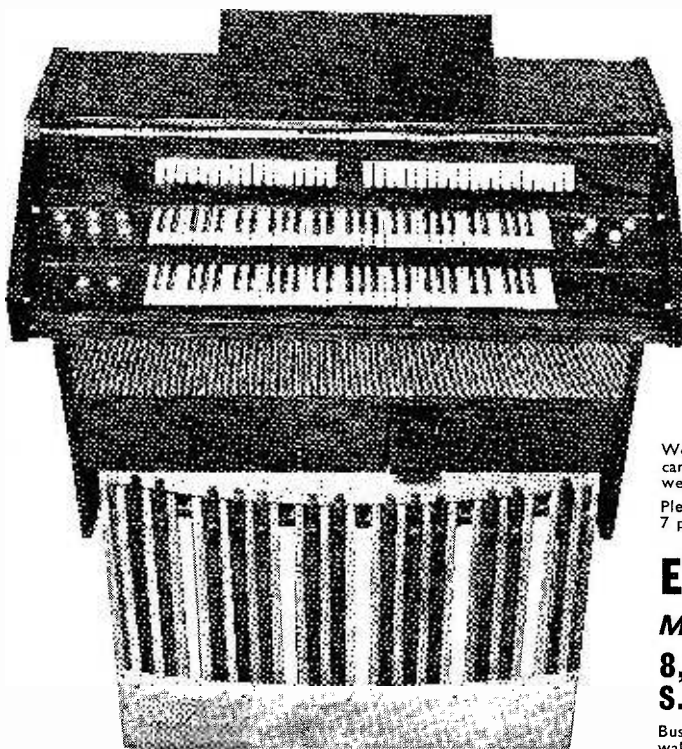
# BI-PRE-PAK LTD

DEPT. D 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344



## ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £103.00, P/P £1.50.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £167.00, P/P £5.00.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, Wah Wah, etc. at £406.00. Carr. paid on complete kit U.K. only.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55 carr. paid on complete kit U.K. only.

We regret H.P. facilities are not available, but components can be bought separately. Trade and overseas enquiries welcomed. Send 15p for latest catalogue.

Please call in for demonstration. Business hours: 10 a.m. to 7 p.m. Monday to Saturday. Thursday closed.


## ELVINS ELECTRONIC

### MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE RD., LONDON  
S.W.18 TEL: 01-870 4949

Bus numbers 37, 220, 225, 168 pass the door. 10 minutes walk from East Putney or 15 minutes walk from Putney Bridge Underground Stations.

## RADIO BARGAINS

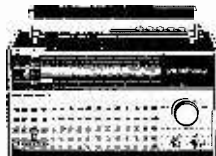

Grundig Mariner 865	£35.00
Grundig Solo Boy	£17.50
Grundig Party Boy	£22.50
Grundig Music Boy	£26.00
Grundig TR600	£28.50
Grundig Elite Boy	£29.50
Grundig Yacht Boy	£34.50
Grundig Satellit Univ.	£112.00
Grundig Melody Boy	£41.50
Grundig 3005	£64.00
Koyo KTR1661 8w.b.	£40.25
Koyo KTR 1664 8w.b.	£47.50
Koyo KTR1770 11w.b.	£66.00
Aiwa AR158	£31.00
Toshiba IC70	£16.50
Hitachi WH1160	£22.50
ITT/KB Golf	£26.50
ITT/KB Touring Int. Marine	£45.00

**FREE** With each set "Guide to Broadcasting Stations" (160 pages)

**WILMSLOW**  
**AUDIO, Dept. PW,**  
10 Swan St., Wilmslow,  
Cheshire, SK9 1HF

## PRACTICAL WIRELESS ELECTRONIC IGNITION SYSTEM



This Capacitor-discharge Electronic Ignition system was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the Standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the De-luxe version containing a ready-drilled roller-trimmed printed circuit board and fully machined die-cast case with electrical connection block. Each kit is supplied with a custom wound transformer, first-grade components and full construction details. Suitable for 12V. systems only, pos. or neg. earth. All components available separately. Case size 4 1/2" x 3 1/2" x 2" Complete assembly and wiring manual 25p, refundable on purchase of kit.


Price: Standard kit ... £7.25 post free  
De-luxe ... £8.75 post free  
Trade enquiries invited. Mail order only.

State pos. or neg. earth when ordering.

## DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ  
Tel. Walsall 34365
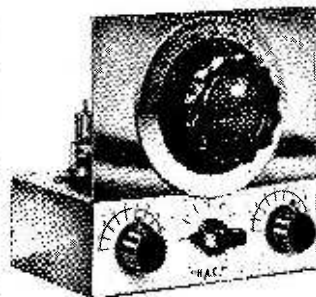
## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Home, etc.

### NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £3.50 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

**"H.A.C." SHORT-WAVE PRODUCTS**  
29 Old Bond Street, London W.1



## BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 18" x 11 1/2". Above motor board 3 1/2". below motor board 2 1/2". with STEREO and MONO XTAL MONO-COMPATIBLE Plays all records



£8-75 Post 25p.  
£7-75 Post 25p.

RCS 3 WATT AMPLIFIER. Ready made tested. 2-state triode pentode valve UCL82. 3 watts output. Tone and volume controls. Rectifier valve UY85. Knobs. With high performance Loudspeaker. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

## R.C.S. PORTABLE PLAYER CABINET

£4

Post 25p.



Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18" x 15" x 5 1/2". Metal Hittings. Carrying handle. Popular colours. Two-tone rexine covered.

GARRARD SINGLE PLAT TO MK II Complete with stereo/mono plug in head. Ideal Discotheque or Hi-Fi. £10

GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 8500 Stereo and Mono Autochanger £14. Post 25p.

BSR JOURNALS SINGLE PLAYER Turntable, 4-speed motor and separate pick-up £4-50

EMI PICK-UP ARM with mono xtal and stylus £1-25. HI-FI PICK-UP CARTRIDGES. Diamond LP/Stereo Stereo/Mono 9TA £2-50; GP84 £2-50; GP83 £2-00; Sapphire Mono GP81 £1-50; Power-point LP/78 £6-00.

## E.M.I. WOOFER AND TWEETER KIT

£5-75 Post 25p

Comprising a fine example of a Woofer 10" x 8 1/2" with a massive Ceramic Magnet, 440z. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 8 1/2" in. square has a special lightweight paper cone and magnet flux 10,000 lines. Impedance Standard 8 ohms Maximum Power 12 watts Useful Response 85 to 18,000 cps Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 1/2", £9 POST 25p

## WEYRAD P50-TRANSISTOR COILS

RA2W Ferrite Aerial 72p	Spare Cores 3p
Osc. P50/1A0 33p	Driver Trans. LFDT4 58p
I.F. P50/200 470 k.c/s. 38p	Printed Circuit, P0A1 58p
3rd L.F. P50/300 36p	1.5 Tuning Gangs 68p
P51/1 or P51/2 36p	Weyrad Booklet 10p
P50/3V 38p	OPTI 58p

Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 20p.

VOLUME CONTROLS 80ohm Coax 4p. yd. Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edges 5K. S.P. Transistor 25p. Ideal 625 and colour.

## 8in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power. £4-80



BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 1/2 in. sides. 7 x 4 in. 45p; 9 x 7 in. 60p; 11 x 7 in. 70p; 13 x 9 in. 90p; 14 x 11 in. 95p; 15 x 14 in. 99p; 11 x 3 in. 50p; 16 x 10 in. 41p. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 29p; 14 x 9 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2 p. 2-way, or 2 p. 4-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p. TOGGLE SWITCHES. sp. 14p; dp. 18p; dp. dt. 28p.

"THE INSTANT" BULK TAP ERASER & HEAD DEMAGNETISER 200/250V. A.C. £2-35 Post Leaflet S.A.E. 15p



## HIFI STOCKISTS RETURN OF POST DESPATCH RADIO COMPONENT SPECIALISTS

Radio Books & Component Lists 5p. Written guarantee. (Export: Remit cash and extra postage.)

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or £2. PLEASE STATE VOLTAGE REQUIRED. Post Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in. FREE

## GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12V or H.T. line 200-300V D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2". Response 25 cps. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Post Full instructions supplied. Details S.A.E. 90p 10p

## NEW TUBULAR ELECTROLYTICS

2/350V 14p	250/25V 14p	50+50/350V 85p
4/350V 14p	500/25V 20p	60+100/350V 58p
8/450V 14p	1000/25V 35p	82+32/250V 15p
16/450V 15p	1000/50V 47p	32+32/450V 38p
32/450V 20p	8+8/450V 15p	50+50/325V 50p
25/25V 10p	8+16/450V 20p	32+82+32/350V 43p
50/50V 10p	16+16/450V 25p	100+50+50/350V 48p
100/25V 10p	32+32/350V 25p	

LOW VOLTAGE ELECTROLYTICS  
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.  
500mF. 12V. 25p. 25V. 20p. 50V. 30p.  
1000mF. 12V. 17p. 25V. 35p. 50V. 47p. 100V. 70p.  
2000mF. 6V. 25p. 25V. 42p. 50V. 57p.  
2500mF. 50V. 22p. 3000mF. 25V. 47p. 50V. 65p.  
5000mF. 6V. 25p. 12V. 42p. 25V. 75p. 35V. 85p. 50V. 86p.

CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p. 0.5 13p. 1mF 15p. 2mF 150p. 500V-0.001 to 0.05 4p. 0.1 5p. 0.25 8p. 0.47 25p. SILVER MICA. Close tolerance 1%. 2.2-500pF 8p. 500-2.200 pF 10p. 2.700-6.800pF 20p. 6.800pF-0.01 mfd 30p. each. TWIN GANG. "0-0" 20pF-170pF. 65p. Slow motion drive 365+365 with 25+25pF. 50p 500pF slow motion, standard 45p; small 8-gang 500pF £1.00.

SHORT WAVE, SINGLE. 10pF 30p. 25pF 55p. 50pF 55p.

NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.

RESISTORS 1 w., 1/2 w., 20p. 1/2 w. 2p. 10 ohms to 1 meg. 10p.

DIODES. Preferred values 10 ohms to 10 meg. 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K. 10p each; 2 1/2 watt, 1 ohm to 82 ohms 10p.

## DECCA DECADEC GARRARD MOTOR UNIT MKII

Single play Stereo Mono Deram transcription head and arm Four speeds 10in. turntable. Anti-rumble filter Bias compensation. Laboratory motor.



SPECIAL PRICE £18-50 Post 25p

## METAL PLINTH & PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12" x 14" x 7 1/2 in. Post 25p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE

## MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp. £1-50  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2-50  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3-00  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £2-25  
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 3 a. 2 1/2 x 2 1/2 in. 90p  
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 6.3v. 3 a. 60p  
Ditto tapped sec. 1.4 v., 2.3 v., 3.4 v. 6.3 v. 1 1/2 amp. 80p  
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25  
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-25  
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-25  
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-75  
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. £2-25  
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12v. 1 1/2 amp. £1-50; 2 amp. £1-80; 4 amp. £2-50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p  
LUCAS 2DS500 Bridge 70V 5 amp £1.



## E.M.I. 13 1/2 x 8in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As Illustrated) Post 15p  
With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-80 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p

Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

## ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free  
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

## BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20 x 15 x 9 in. 25. Post 25p For 13 x 8 in. or 8in. speaker 18 x 10 x 9 in. 25. Post 25p For 10 x 6 in. or 6in. speaker 16 x 8 x 6 in. 24. Post 25p LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.

## GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambria cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosures Systems, etc. £4



## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1-90 Post 10p.

## SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16k/s. 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kc/s. 15W. 15 ohm £2. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm 2 1/2 in., 2 1/2 in., 35 ohm, 2 in., 3 in 25 ohm, 3 1/2 in. dia.; 3 in dia.; 6 x 4 in.; 8 x 5 in. £1 EACH 15 ohm, 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 3 ohm, 2 1/2 in. 5 x 8 in. LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 1/2 in. £1-50; 8 x 5 in. £1-60; 8 x 2 1/2 in. £1-50; 11-75 10 x 6 in. £1-80. RICHARD ALLAN TWIN CONE LOUDSPEAKERS. Sin. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.

## BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £39 Post Free



## BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4-50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4-50. £3-50

## BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt

Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12-50

## BARGAIN FM TUNER as above less cabinet £8-85

## BARGAIN 3 WATT AMPLIFIER. 4 Transistor

Push-Pull Ready built, with volume control. 9v. £3-50

## COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p.

OUTLET BOXES, SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 6mm Chrome 14p. DIN SOCKETS Chassis 3 pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CANS 5p.

## E.M.I. TAPE MOTORS Post 15p.

120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.76in. Size 2 1/2 x 2 1/2 x 2 1/2 in. (Illustrated) £1-25  
BALFOUR GRAM MOTORS 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/32. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p 85p





# The Specification sounds fine the System sounds great

## Viscount 117 Audio Suite complete £49

**14 + 14W per channel 40Hz to 40kHz  $\pm$  3dB Total distortion at 10 watts at 1kHz -0.1%.**

This is real value for money! We have designed 3 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. It is available in 2 versions — R100 for ceramic cartridges, and R101 for magnetic and ceramic. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For all systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with teak finished plinth and perspex cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

### PRICES

**SYSTEM I**  
Viscount III R101 amplifier  
2 x Duo Type II speakers  
Garrard SP25 Mk. III with MAG.  
cartridge plinth and cover

£22.00 + 90p p&p  
£14.00 + £2 p&p  
£23.00 + £1.50 p&p  
£59.00

### Available complete

**SYSTEM 2**  
Viscount R101 amplifier  
2 x Duo Type III speakers  
Garrard SP25 Mk. III with MAG.  
cartridge, plinth and cover

£22.00 + 90p p&p  
£32.00 + £3 p&p  
£23.00 + £1.50 p&p  
£77.00

### Available complete

**SYSTEM 3**  
Viscount III Amplifier R100  
2 x Duo Type II speakers, pair  
Garrard SP25 Mk. III with CER.  
diamond cartridge, plinth  
and cover

£17.00 + 90p p&p  
£14.00 + £2 p&p  
£21.00 + £1.50 p&p  
£52.00

### Available complete

**for only £69 + £4 p&p**

### Available complete


**for only £49 + £3.50 p&p**

### SPEAKERS Duo Type II

Size approx. 17" x 10" x 6". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet.  
£14 pair + £2 p&p.

Duo Type III. Size approx. 23" x 11" x 9". Drive unit 13" x 8" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

**SPECIFICATION R101**  
14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 9%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within  $\pm$  1dB R.I.A.A. Radio 150mV into 220K. (Sensitivity given at full power). Tape out facilities: head-phone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass:  $\pm$  12dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble  $\pm$  12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2—58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13" x 9" x 3".

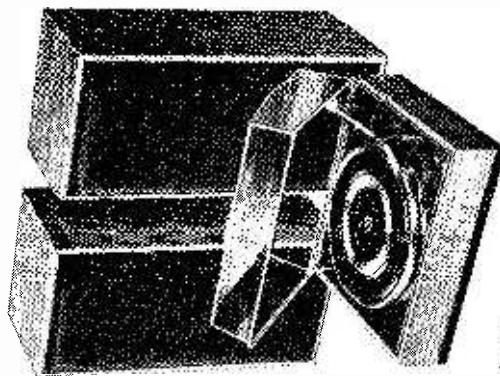


Goods not  
despatched outside U.K.



Radio and TV Components (Acton) Ltd.,  
21c High Street, Acton, London W3 6NG,  
323 Edgware Road, London, W2. Mail orders  
to Acton. Terms C.W.O. All enquiries S.A.E.

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

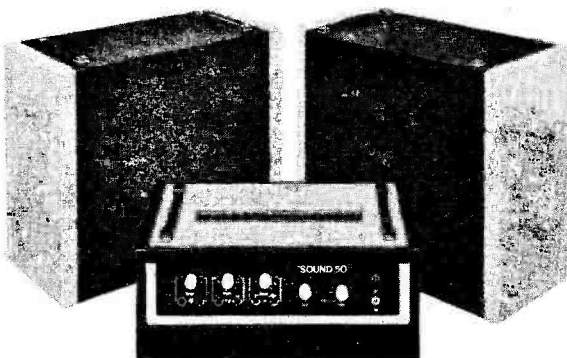

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range:  $\pm 13$ dB at 60Hz. Treble Control Range:  $\pm 12$ dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.


**SPEAKERS!** Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £6 P. & P.  
Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.  
Speakers £12.50 each plus £2.25 P. & P.

## RELIANT mk. IV

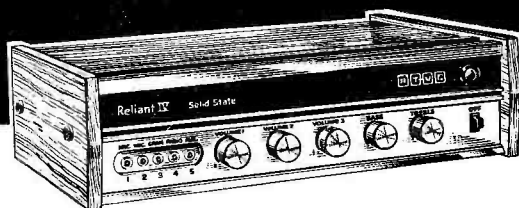

Provides a high standard of sound reproduction, with full mixing facilities. Its versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate base and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry ★ Attractive Styling


**£9.50** plus P. & P. 60p.

**INPUTS:**—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.). All 250mV sensitivity.  
**CONTROLS:**—3 Volume controls. Bass control range: 13dB @ 60Hz. Treble control range  $\pm 12$ dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator.  
**POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker  
**SIGNAL/NOISE:**—Better than —60dB on inputs 3, 4 and 5 & —50dB on 1 & 2  
**SUPPLY:**—220 - 250 AC Mains. **SIZE:**—12½" x 6" x 3½"
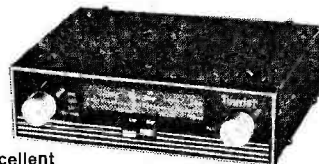
## TOURIST MK3 CAR RADIO

ALL TRANSISTOR


Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.



SET OF PARTS

**£6.30** plus P. & P. 50p. Circuit diagram 13p. Free with parts. Speaker, baffle and fixing kit £1.25 extra plus 25p. p. & p. Postage free when ordered with parts.
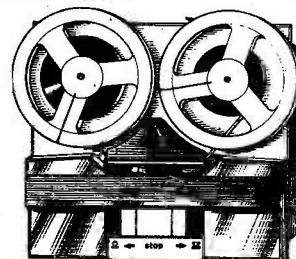
## CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK



with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips. 4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.


Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

**£15.00.** Plus 75p P. & P.

## DUETTO mk. II I.C.

STEREO AMPLIFIER

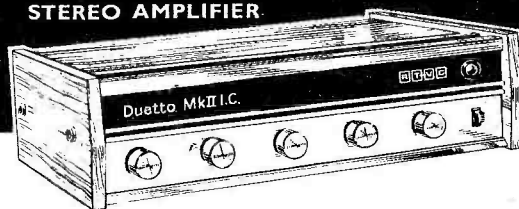

Sophisticated styling combined with up-to-date electronics means Hi-Fi. This is what the Duetto Mk.II offers at a realistic price. Mullard built stereo pre-amplifier/tone control module and the highly efficient I.C. monolithic power chips ensure: reliability, very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum etc.

Inputs : P.U. 150mV. @ 2.2 Meg (for cer. cartridge)

Auxiliary 100mV. @ 1 Meg (for radio, tape etc.)

Outputs : 5 watts rms per channel into 8-15Ω speakers.

Switched stereo headphone socket with power correction.

Controls : Mono/stereo switch, selector switch, treble, bass, volume, balance and on/off switch. Neon indicator.

Tone Controls : Treble  $\pm 14$ dB @ 15KHz

Bass  $\pm 14$ dB @ 60Hz

Power Bandwidth :  $\pm 2$ dB 20Hz-25KHz Size 12½" x 6" x 3½"

**£10.50**

plus P. & P. 60p

**RTVC**  
See opposite page for addresses

# DISCOUNTS UP TO

# 60%\* ON BRANDED GOODS

ALL BRAND NEW  
in manufacturer's sealed cartons.  
GUARANTEED 12 MONTHS.

## SPECIAL OFFER £17.95

Garrard SP25 Mk. III  
Goldring G800  
Teak plinth and tinted cover. All  
leads supplied.  
Please add £1.25 for P & P.

## TURNTABLES

Please add 75p for P. & P.  
Garrard SP25 Mk. III £9.45  
Garrard AP76 £18.75  
Garrard SL65B £12.70  
Garrard 401 £26.50  
Garrard Zero 100 (Auto) £38.25  
Garrard Zero 100 (Single) £36.25  
Garrard SL72B £23.50  
Garrard SL75B £25.50  
Garrard SL95B £34.50  
BSR MP60 £9.50  
Goldring GL72 £21.95  
Goldring GL72/P £29.00  
Goldring GL75 £26.95  
Goldring GL75/P £34.25  
Wharfedale Linton & cart. £26.95  
Thorens TD125 £37.50  
Thorens TD125AB £80.00  
Thorens TD150 Mk. II £27.25  
Thorens TD150A Mk. II £33.30

## AMPLIFIERS

Please add 75p P. & P.  
Amstrad 8000 Mk. II £16.25  
Amstrad IC2000 £26.95  
Armstrong 521 (teak cased) £43.95  
Alpha Highgate 212 £25.00  
Alpha Highgate FA300 £27.95  
Alpha Highgate FA400 £31.95  
Ferrograph F307 Mk. II  
(Wood cased) £47.50  
Ferrograph F307 Mk. II  
(Metal cased) £45.00  
Leak Delta 30 £47.50  
Leak Delta 70 £55.50  
Metrosound ST20E £24.45  
Metrosound ST60 £46.25  
Pioneer SA600 £58.00  
Pioneer SA700 £66.50  
Pioneer SA800 £73.95  
Pioneer SA900 £92.00  
Pioneer SA1000 £94.00  
Rogers R/brook (Chassis) £35.00  
Rogers R/brook (Cased) £37.00  
Rogers R/brook (Chassis) £41.50  
Rogers R/brook (Cased) £46.50  
Sinclair PRO602 x Z30/PZ5 £15.00  
Sinclair PRO602 x Z30/PZ6 £17.35  
Sinclair PRO602 x  
Z30/PZ8/Trans £21.50  
Sinclair AFU (Filter Unit) £41.50  
Sinclair 608 £18.50  
Sinclair 2000 Mk. II £21.50  
Sinclair 3000 Mk. II £29.50  
Wharfedale Linton £37.50  
Goodmans Max Amp £37.95  
Teleton SAQ306B £22.50  
Europhon 10 + 10 £16.95

All prices correct  
at time of press  
E. & O.E.



## GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. 174 Pentonville Road, London, N1. Telephone 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue,  
Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to  
6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque,  
Money Order, Bank Draft, Giro or Cash by Registered  
Mail. CALLERS: Please note that cheques can only be accepted together  
with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS  
on main road leading to the East and West Country

## TUNERS

Please add 75p P. & P.  
Armstrong 253 £39.00  
Armstrong 524 £30.50  
Rogers Ravensbrook FET4  
(Chassis) £31.00  
Rogers Ravensbrook FET4  
(Cased) £35.00  
Rogers Ravensbourne FET4  
(Chassis) £43.00  
Rogers Ravensbourne FET4  
(Cased) £48.00  
Sinclair PRO60 (Module) £10.25  
Sinclair 2000/3000 Tuner £32.50  
Philips RH690 £43.00  
Leak Delta FM (Cased) £54.25  
Leak Delta AM/FM (Cased) £65.25

## TUNER/AMPLIFIERS

Please add 75p for P. & P.  
Alpha Highgate 150 £44.95  
Alpha Highgate R500 £64.50  
Armstrong 525 (Teak cased) £67.95  
Armstrong 526 AM/FM £77.95  
(Teak cased) £127.25  
Leak Delta 75 £120.00  
Philips RH781 £57.50  
Philips RH 882 (+cass head) £72.00  
Philips RH702 £82.50  
Teleton 2100 £103.25  
Goodmans One Ten £79.50  
Rogers R/brook (Teak) £73.95  
Rogers R/brook (Chassis) £73.95

## SPEAKERS

Please add £1.25 P. & P. per pair  
Amstrad 138 £19.95  
Wharfedale Denton 2 £27.95  
Wharfedale Linton 2 £36.25  
Wharfedale Melton 2 £47.25  
Wharfedale Dovedale 3 £60.50  
Celestion Ditton 120 £38.00  
Celestion Ditton 15 £33.95  
Celestion Ditton 25 £29.95  
Goodmans Double Maxim £47.50  
Goodmans Mezzo 3 £44.00  
Goodmans Magister £74.00  
Sinclair Q16 £12.50

£3.20\*



Plus 35p p. & p.  
Finished in teak veneer with tinted  
dust cover fully assembled.  
For Garrard SP25; 2025TC; 3000;  
AT60; 2000; 2500; 3500; 5100;  
1025; SL65B; Also for  
McDonald MP60 and others.  
For AP76; A75; SL72B; SL75;  
SL95B; £4.20 plus 55p P. & P.  
Also finished in walnut to match  
Japanese equipment—at no extra.

## CARTRIDGES

Please add 10p for P. & P.  
Goldring G850 £3.45  
Goldring G800 £5.95  
Goldring G800E £10.00  
Goldring G800 Super E £15.15  
Shure M3D £3.75  
Shure M44E £5.70  
Shure M55E £6.50  
Shure M75E Type 2 £10.25  
Sontone 9TAC £1.55

## VALVES

SAME DAY SERVICE  
NEW! TESTED! GUARANTEED!

## SETS


1K5, 185, 1T4, 384, 3V4, 6AF91, DF91, DK91, DL92, DL94.  
Set of 4 for £1.12. DAF96, DF96, DK96, DL96, 4 for £1.65.

1R5	-28	30C1	-28	DY802	-40	EL500	-62	PCL82	-32	UAC80	-82
185	-22	30C16	-58	EAC80	-32	EM80	-38	PCL83	-67	UAF42	-60
1T4	-18	30C17	-78	EAP40	-80	EM81	-38	PCL84	-34	UAC41	-52
384	-28	30C18	-61	EB91	-10	EM84	-32	PCL85	-38	UBF80	-84
3V4	-47	30F5	-64	EB93	-40	EM87	-32	PCL86	-38	UBF89	-82
5U4G	-31	30FL1	-61	EB41	-54	EY61	-36	PCL88	-63	UC84	-82
5V4G	-35	30FL12	-69	EB90	-32	EY86	-29	PCL800	-75	UC86	-85
5Y3GT	-34	30FL14	-68	EBF80	-32	EZ40	-43	PEN44	-77	UCF80	-88
5Z4G	-35	30L1	-29	EBF89	-29	EZ41	-43	PEN38C	-70	UCF42	-58
630L2	-54	30L15	-87	ECC81	-17	EZ80	-22	PFL200	-52	UCL81	-32
6AL5	-11	30L17	-87	ECC82	-20	EZ81	-22	PL36	-49	UCL82	-32
6AM8	-18	30P4	-57	ECC83	-35	GZ30	-34	PL81	-44	UCL83	-55
6AQ5	-22	30P12	-72	ECC85	-34	GZ32	-40	PL81A	-47	UF41	-66
6AT6	-20	30P19	-57	ECC804	-34	GZ34	-48	PL82	-31	UF89	-30
6AU6	-20	30P1	-60	ECP80	-31	KT41	-77	PL83	-83	UL41	-57
6BA6	-20	30P13	-89	ECP82	-28	KT61	-55	PL84	-30	UL84	-80
6BE6	-21	30P14	-65	ECH35	-55	KT66	-77	PL500	-63	UM84	-22
6BJ6	-41	35L6GT	-45	ECH42	-59	LN319	-63	PL504	-63	UY41	-89
6BW7	-52	35W4	-25	ECH81	-59	LN329	-72	PM84	-33	UY85	-25
6F14	-40	35Z4GT	-25	ECH83	-40	LN339	-63	PX26	-66	VP48	-77
6P28	-88	807	-45	ECH84	-38	N78	-87	PY32	-55	W77	-43
6P28	-53	AC/VP2	-77	ECL80	-35	PAC80	-34	PY33	-55	Z77	-22
6P70	-84	B349	-65	ECL82	-31	PC86	-47	PY81	-25	Transistors	-17
6KT6	-12	B729	-62	ECL86	-35	PC88	-47	PY82	-25	AC107	-17
6K8G	-17	CC835	-67	EF39	-38	PC96	-42	PY83	-28	AC127	-18
6QT6	-35	CY31	-60	EF41	-60	PC97	-39	PY88	-33	AD140	-87
68N7GT	-30	DAF91	-22	EF80	-33	PC900	-31	PY900	-34	AF115	-20
6V8GT	-28	DAF96	-22	EF85	-28	PC94	-29	PY901	-34	AF116	-20
8X4	-23	DF91	-16	EF89	-26	PC98	-40	R20	-56	AF118	-48
8X6GT	-28	DF96	-38	EF91	-13	PC989	-45	U25	-64	AF125	-17
10P19	-58	DH77	-20	EP92	-30	PC189	-48	U26	-56	AF127	-17
12AH6	-29	DK32	-28	EF94	-25	PC1805	-56	U47	-64	OC26	-55
12AT7	-17	DK91	-25	EF183	-29	PC180	-28	U49	-56	OC44	-12
12AU7	-20	DK92	-50	EF184	-31	PCF82	-33	U52	-31	OC45	-12
12AX7	-22	DK96	-45	EH90	-35	PCF86	-48	U78	-24	OC71	-12
19B6GT	-80	DL36	-40	FL33	-55	PCF800	-58	U91	-59	OC72	-12
20P2	-87	DL92	-26	FL34	-45	PCF801	-28	U93	-42	OC75	-12
20P3	-77	DL94	-47	EL41	-54	PCF802	-40	U261	-64	OC81	-12
20P4	-98	DL95	-38	EL84	-23	PCF805	-61	U301	-38	OC82	-12
25L6GT	-19	DY86	-24	EL90	-26	PCF806	-58	U329	-66	OC82D	-12
25U4GT	-57	DY87	-24	EL95	-33	PCF808	-68	U801	-80	OC170	-28
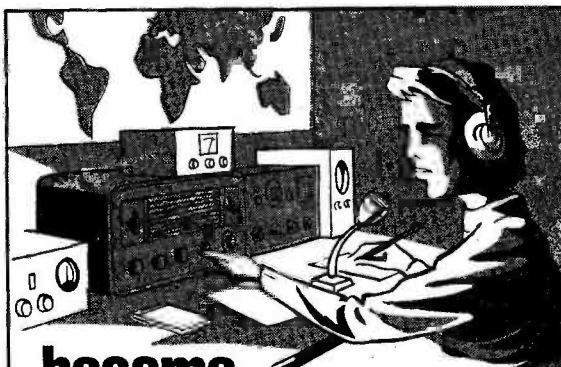
## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD,  
ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve,  
(3p. per. valve extra)  
Any parcel insured against damage in transit 3p. extra.



## become a RADIO-AMATEUR!

learn how to become a radio-amateur  
in contact with the whole world. We give  
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO &  
ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME :

ADDRESS :

WB62

BLOCK CAPS please



# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome 7 section Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 8" x 2 1/2" Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8-50**


P. P. & Ins. 50p

(Overseas P. & P. £1)

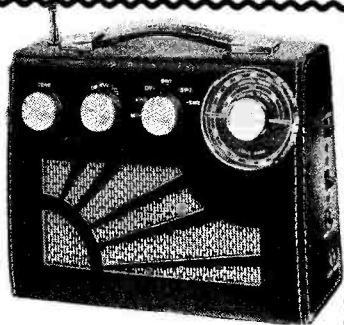

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

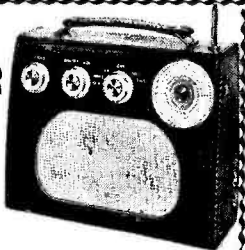

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


## ROAMER SEVEN MK IV



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

## ROAMER SIX

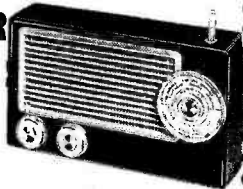

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)


## POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 63p)

## TRANSONA FIVE

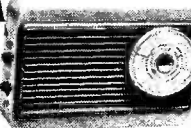


5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 23p. (Overseas P. & P. 63p)

## TRANS EIGHT

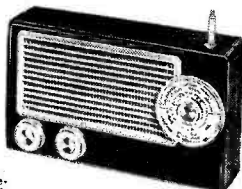

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)

## NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4" x 2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

\* Callers side entrance Barratts Shoe Shop  
\* Open 10-11, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

# COMET

## HI-FI DISCOUNT WAREHOUSES

# NEW LOW



	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ALBA UA 700	37-93	24-95
ALPHA 212 By Highgate	37-75	25-95
AMSTRAD Stereo 8000 Mk 2	27-95	14-95
AMSTRAD I.C. 2000	42-95	27-50
ARMSTRONG 521	59-00	44-95
DULCI 207	26-00	16-50
DULCI 207M	32-00	19-50
FERROGRAPH F307 Mk. II (cased)	84-00	46-95
FERROGRAPH F307 Mk. II (Metal case)	60-00	42-95
GOODMANS Maxamp	54-00	34-95
LEAK Delta 30 (cased)	65-00	48-25
LEAK Delta 70 (cased)	75-50	58-95
METROSOUND ST20E	39-50	24-95
METROSOUND ST60	70-00	46-25
PHILIPS RH 591	79-00	53-95
PHILIPS RH 580	52-00	35-50
PHILIPS RH 580	29-00	19-95
PIONEER SA500A	58-78	39-95
PIONEER SA600	89-60	58-95
PIONEER SA800	119-85	75-95
PIONEER SA900	133-83	90-95
PIONEER SA1000	147-83	95-95
PIONEER QL600 Quadraphonic con.	94-43	65-95
PIONEER Revolution 202W	61-05	34-95
RANK Rotel 210	34-90	24-95
RANK Rotel 310	47-50	32-95
RANK Rotel 610	74-50	49-50
ROGERS Ravensbourne	64-50	45-50
ROGERS Ravensbourne (cased)	69-50	49-50
ROGERS Ravensbrook Mk. II	50-50	35-95
ROGERS Ravensbrook (cased) Mk. II	55-50	39-95
SINCLAIR 2000	35-00	24-25
SINCLAIR Project 60/2 x Z30/P25	23-90	15-95
SINCLAIR PROJECT 60/2 x Z50/P28/Trans	34-88	21-95
SINCLAIR PROJECT 605	29-95	20-25
SINCLAIR AFJ	5-98	4-25
SINCLAIR Neoteric	61-95	42-93
SINCLAIR 3000	45-00	29-50
TELETON SAQ 206	33-00	19-50
TELETON 307	33-00	20-95
WHARFEDALE Linton Amplifier	60-00	42-95
TELETON GA202 15 watt RMS P.Chan.		Spec Price 28-50

All take both ceramic and magnetic cartridges.

### TUNERS


*ARMSTRONG 523 AM/FM	52-68	39-50
*ARMSTRONG 524 FM	40-97	30-95
ARMSTRONG M8 Decoder	9-50	6-95
*DULCI FMT.7 FM	24-43	17-50
DULCI FMT.7S Stereo	32-89	24-50
GOODMANS Stereomax	75-74	46-95
LEAK Delta FM	73-00	53-95
LEAK Delta AM/FM	87-00	65-95
PHILIPS RH 690	44-15	33-50
PHILIPS RH 691	83-40	67-25
PIONEER TX500 AM/FM	70-93	52-50
PIONEER TX600 AM/FM	100-37	77-95
RANK ROTEL 320	53-33	38-50
ROGERS Ravensbourne chassis	57-95	42-50
ROGERS Ravensbourne in teak case	62-63	47-25
ROGERS Ravensbrook chassis	42-14	31-25
ROGERS Ravensbrook (cased)	48-00	35-25
SINCLAIR 2000	45-00	33-50
SINCLAIR 3000	45-00	34-25
SINCLAIR Pro 60 tuner (stereo)	25-00	19-95

All above Tuners are complete with MPX Stereo Decoder except where starred.

### TUNER/AMPLIFIERS

AKAI AA 8500	228-34	169-95
AKAI 6600	145-26	105-50
AKAI 6300	125-83	92-50
AKAI 6200	97-09	72-50
ARENA 2600	111-30	59-95
ARMSTRONG M8 Decoder	9-50	6-95
ARMSTRONG 525	90-14	67-95
ARMSTRONG 526	102-72	77-50
GOODMANS Module 80, 35w. RMS	89-02	67-75
GOODMANS Module 80 Compact	130-38	125-95
GOODMANS Module 110 FM/MW/LW/SW 100W RMS	131-22	104-95
LEAK Delta 75	160-00	127-95
MIDLAND 19/542	49-56	36-75
PHILIPS RH 790	134-00	74-95
PIONEER SX440 AM/FM	135-80	104-95
ROGERS Ravensbrook Chassis	101-69	79-95
ROGERS Ravensbrook (cased)	105-35	82-95
ROTEL RX150	67-93	51-95
TANDBERG 1171 MPX	103-03	84-95
TANDBERG TR200 MPX	99-23	79-95
TELETON F2000	51-50	27-25
TELETON CR55	125-26	98-50
TELETON R3000 AM/FM	42-16	21-95

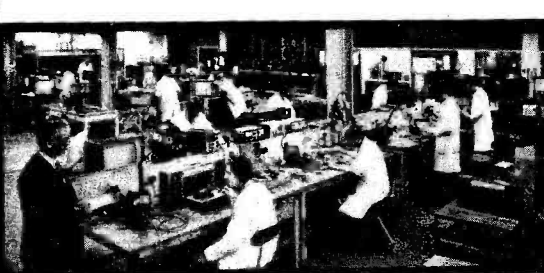All the above Tuners and Tuner/Amplifiers take both ceramic and magnetic cartridges except Teleton F2000, 8000 which take ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.



### COMET for after-sales service

THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, Bridlington, Birmingham, Edinburgh, Leicester and Rochdale

### CARTRIDGES

	Rec. Retail Price	Comet Price
AUDIO TECHNICA AT66	6-47	4-20
GOLDRING G850	6-10	3-45
GOLDRING G800	12-21	5-80
GOLDRING G800E	17-67	9-70
GOLDRING G800 Super E	24-41	14-40
*GOLDRING CS90 Stereo	4-88	4-20
*GOLDRING CS91/E	7-33	6-20
EMPIRE 1000ZE/X	59-12	45-95
EMPIRE 999VE/X	42-14	33-25
EMPIRE 999TE/X	24-58	19-50
EMPIRE 999SE/X	19-90	15-60
EMPIRE 999E/X	15-57	11-70
EMPIRE 909E/X	12-12	9-40
EMPIRE 90EE/X	9-37	7-15
ORBIT Magnetic NM 22	Spec Price 2-85	
ORTOFON M1SE	27-60	22-95
SHURE M3DE	6-10	4-20
SHURE M31E	11-63	8-50
SHURE M32E	10-73	7-85
SHURE M32-3	9-84	7-65
SHURE M44-5	8-30	5-65
SHURE M44-G	8-30	5-65
SHURE M44-7	7-90	5-40
SHURE M44E	8-60	5-60
SHURE M55E	9-70	6-80
SHURE M75G	14-70	9-70
SHURE M75-6	13-60	8-25
SHURE M75EJ	15-40	10-50
SHURE M75EJ	19-00	12-70
SHURE M75E/95C	20-80	14-60
SHURE V15-11	39-40	26-95
SONOTONE 9TAHC Diam/Saph...	3-75	1-95

Starred cartridges above are ceramic. All others are magnetic.

### PICKUP ARMS

GOLDRING Lenco 75	13-51	9-30
GOLDRING Lenco L69	9-77	6-40
SME 3009 with S2 Shell	32-34	24-50
SME 3012 with S2 Shell	34-44	26-50

### TURNABLES

The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.		
GARRARD SP25 Mk III with Goldring G.800	Special Price £19.50	
GARRARD SP25 Mk III with Shure M.44/7	Special Price £20.50	
GARRARD SP25 Mk III with Shure M.44/E	Special Price £21.95	
GARRARD AP76 with Goldring G800	Special Price £29.90	
GARRARD AP76 with Shure M55E	Special Price £32.95	
GARRARD AP76 with Shure M75EJ	Special Price £34.95	
GARRARD 2025 with Sonotone 9TAHC	Special Price £13.90	
GOLDRING 705/P with G850	£26.00	£10.95
GOLDRING GL75 with G800	Special Price £39.95	
THORENS 150 AB complete with TX11 cover Shure M55E cartridge	£60.46	£47.95

GARRARD SP25 Mk III	16-17	10-25
GARRARD SL65 B	20-93	13-95
GARRARD SL95 B	49-21	32-75
GARRARD 401	39-04	27-50
GARRARD SL72 B	32-60	22-95
GARRARD Zero 100A	57-42	39-95
GARRARD Zero 100S	52-83	38-95
GARRARD CB4 base Mk II/2 to fit Zero 100 & Zero 100S	6-55	4-95
Base and Cover to fit GARRARD AP25, SL55, SL65B	Special Price 3-60	
GARRARD 40B	13-63	10-95

	Rec. Retail Price	Comet Price
GARRARD AP76	28-44	19-50
GOLDRING GL69 Mk. II	26-86	18-50
GOLDRING GL69P Mk. II	35-23	25-25
GOLDRING GL75	39-06	28-25
GOLDRING GL75P	47-43	35-25
GOLDRING Covers for 69P and 72P	4-36	3-75
Cover for 75P Deluxe	4-88	3-95
GOLDRING C99-plinth and cover for 69P	10-75	9-75
GOLDRING C99	27-90	19-50
GOLDRING G101P/C	27-90	22-50
GOLDRING GL72 Chassis	27-90	20-95
GOLDRING GL72P	36-27	29-25
GOLDRING GL85	61-03	46-50
GOLDRING GL85P	70-80	54-75
LEAK Delta	67-50	54-75
McDONALD MP60	14-80	10-25
McDONALD 610	18-79	14-50
McDONALD HT70	20-68	15-25
McDONALD HT70 inc. plinth & cov. Base and Cover for MP60 and 610	29-89	22-50
PHILIPS 202 Electronic	Spec Price 3-95	
PHILIPS 308 transcription unit complete with base and cover	64-65	51-75
PIONEER PL2AC with base & cover	36-55	28-25
THORENS TX25 cover	47-15	36-25
THORENS TD125	8-26	6-60
THORENS TD125AB	73-78	58-25
THORENS TD150 Mk. II	112-14	91-95
THORENS TD150 Mk. II	33-64	28-25
THORENS TD150A Mk. II	43-09	33-50
THORENS TD150AB Mk. II	46-63	38-25
THORENS TX11 Cover	4-13	3-75
WHARFEDALE Linton with base and cover and Shure M44/7 cart.	34-50	27-25

### SPEAKERS

AMSTRAD 138 (pair) 13"x8" twin cone teak	26-00	15-95
AKAI SW 155	59-50	39-95
B & W Model 70	159-50	111-95
B & W DM2	62-80	51-95
B & W DM3	63-00	47-95
B & W DM4 (pair)	75-20	59-95
CELESTION COUNTY	23-97	19-50
CELESTION Ditton 120 (pair)	56-40	42-95
CELESTION Ditton 15	37-60	26-50
CELESTION Ditton 25	65-00	44-95
CELESTION Ditton 44	54-00	39-95
CELESTION Ditton 66	99-00	74-95
GOODMANS Minister (pair)	45-86	36-95
GOODMANS Havant (pair)	54-42	42-95
GOODMANS Magister	65-63	41-95
GOODMANS Double Maxim	32-27	25-25
GOODMANS Mezzo 3	35-70	23-95
GOODMANS Magnum K2	46-20	30-95
GOODMANS Dimension 8	72-44	49-95
GOODMANS DIN 20NT kit	12-19	9-70
KELETRON KN400 2-speaker System (pair)	15-86	12-50
KN600 3-speaker System (pair)	26-46	17-50
KN100 4-speaker System	15-30	10-25
KN1600 3-speaker System	20-40	13-95
KN2100 3-speaker System	25-20	15-95
KN2100 3-speaker System	30-60	20-45
LEAK 150 (pair)	49-00	37-00
LEAK 250 (pair)	63-00	46-50
LEAK 600	48-50	34-50
METROSOUND HPS 103 (pair)	29-21	23-50
METROSOUND 202	21-50	15-25
METROSOUND Duplex 15	32-00	23-95
METROSOUND Duplex 25	52-00	36-95
PHILIPS RH 411 (pair)	20-60	16-10
PHILIPS RH 402 (pair)	44-70	27-20
PHILIPS 406	34-00	28-20
SINCLAIR 016	8-98	6-95
STE-MA 450	25-00	16-95
TANDBERG Tan 7	27-22	23-40
TANDBERG Tan 11 (pair)	36-94	31-20
TANDBERG Tan 12 teak (pair)	45-82	43-83
TANDBERG Tan 25 teak (pair)	66-08	56-50
TANDBERG Tan 50 teak	65-00	49-95

# PRICES!



## OVER 1000 ITEMS ALWAYS IN STOCK ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Price	Relail Price	Comet Price
TELETON 8000 (pair) .....	21-08	11-95	
WHARFEDALE Speakers			
Denton Mark II (pair) .....	39-00	29-50	
Linton Mark II (pair) .....	49-00	37-50	
Melton Mark II .....	35-00	24-45	
Dovedale 3 Mark II .....	45-00	30-50	
Rosdale .....	65-00	44-95	
Triton (III) (pair) .....	63-00	50-95	
Unit 3 Speaker Kit .....	12-00	9-25	
Unit 4 Speaker Kit .....	18-00	11-95	
Unit 5 Speaker Kit .....	26-00	17-50	

<b>CHASSIS SPEAKERS</b>			
GOODMANS Twin-Axiom 8.....	8-65	7-10	
GOODMANS Twin-Axiom 10 .....	9-58	7-75	
GOODMANS Axion 401 .....	17-68	12-25	
GOODMANS Axion 8P .....	5-20	4-15	
GOODMANS Axion 10P .....	5-67	4-70	
GOODMANS Axion 12P .....	13-00	9-90	
GOODMANS Axion 15P .....	21-00	15-75	
GOODMANS Axion 18P .....	35-70	25-95	
GOODMANS Axion 100 40 watts	12-00	9-50	
GOODMANS ARU 172 .....	4-50	3-20	
GOODMANS Axent 100 .....	6-90	4-90	
GOODMANS Midax 650 .....	13-59	9-30	
GOODMANS Attenuator .....	3-73	2-70	
GOODMANS Crossover Network	7-77	5-25	
XO/50 .....			
WHARFEDALE 8in. Bronze/RS/DD .....	4-50	3-40	
WHARFEDALE Super 8/RS/DD .....	8-00	6-60	
WHARFEDALE Super 10/RS/DD .....	13-00	11-00	
WHARFEDALE WMT1 Matching	0-84	0-70	
Transformer .....			

<b>HI-FI STEREO SYSTEMS COMPLETE</b>			
ALBA UA552 .....	47-75	34-65	
AMSTRAD Stereo 1000 .....	48-00	33-95	
DANSETTE Consort Stereo .....	34-43	24-95	
DECCA Sound 813 .....	Special Price	53-95	
DECCA Sound 814 .....	Special Price	57-95	
DECCA Sound 1204 .....	Special Price	76-95	
DECCA Compact 3 .....	Special Price	102-35	
DECCA 403 .....	Special Price	47-75	
ELIZABETHAN LZ101 .....	58-33	41-85	
FERGUSON 3450 with Radio .....	70-45	51-95	
FERGUSON 3451 with Radio .....	96-80	76-95	
FIDELITY UA2 Music Master .....	44-50	33-95	
FIDELITY UA1 Music Master with			
Radio .....	107-00	78-95	
FIDELITY stereo nine .....	38-50	24-95	
GOODMANS Module 80 compact			
system FM/5 watts RMS (Less			
L/S) .....	165-00	125-75	
HMV 2404/5/6 with Radio .....	194-40	159-00	
HMV 2451 .....	115-95	89-95	
HMV 2452 .....	63-90	49-95	
HMV 2450 with Stereo Radio .....	130-60	103-00	
KB1025 with 657 speakers .....	49-50	37-95	
MURPHY 902 Studio 1, AM/VHF			
Radio .....	86-84	65-95	
MARCONI 4452 .....	73-95	56-50	
PHILCO FORD M1500 .....	97-96	66-75	
PHILIPS 808 .....	93-50	71-95	
PHILIPS GF824 .....	65-30	49-65	
PYE black box unit stereo 1022 .....	90-93	68-25	
RIGONDA party time .....	27-50	21-95	
STEEPLETONE stereo system .....	41-75	31-95	
TELETON STP 8 track stereo system	17-50	38-95	
ULTRA 6026 .....	36-10	29-95	

<b>TAPE RECORDERS AND TAPE DECKS</b>			
AKAI 1720L 4-track Stereo .....	87-36	66-25	
AKAI 4000D 4-track stereo deck .....	93-65	60-45	
AKAI CR80D 4-track stereo tape			
deck .....	65-02	58-45	
AKAI CR80 4-track stereo recorder	106-39	74-00	
AKAI X200D .....	157-93	100-45	
AKAI 1800SD .....	162-79	102-35	
AKAI 2000SD .....	289-07	223-30	

	Rec. Price	Relail Price	Comet Price
AKAI GXC 40D Cassette Tape Deck	92-26	65-25	
AKAI GXC 40 Cassette recorder	111-75	83-85	
BUSH Discassette DC70 .....	20-62	16-55	
BUSH TP 66 Batt./Mains Cassette			
Recorder .....	28-18	21-95	
BUSH TP70 Cassette, battery/mains			
Recorder .....	28-13	21-95	
EKCO 350 Battery/Mains Cassette			
VHF/MW Radio .....	37-42	28-75	
EKCO 351 Battery/Mains Cassette	23-23	18-45	
FERGUSON 3245 Twin track .....	36-70	25-95	
FERGUSON 3246 4-track .....	42-55	30-95	
FERGUSON 3247 4-track .....	47-95	34-95	
FERGUSON 3248 4-track .....	53-75	39-95	
FERGUSON 3252 4-track .....	100-52	74-95	
FERGUSON 3253 .....	43-55	31-95	
FERGUSON 3258 4-track .....	72-40	53-95	
FERGUSON 3262 .....	30-15	23-95	
FERROGRAPH 702 2-track tape deck	224-43	170-65	
FERROGRAPH 704/W 4-track tape			
deck .....	224-43	170-65	
FERROGRAPH 722 .....	224-43	190-15	
FERROGRAPH 724 .....	262-03	190-15	
GRUNDIG C200 De Luxe Cassette	37-55	27-95	
GRUNDIG TK 121 twin track .....	56-25	38-95	
GRUNDIG TK 141 4-track .....	62-10	45-75	
GRUNDIG TK 146 4-track Auto .....	66-95	49-95	
GRUNDIG TK 147 4-track Auto .....	93-05	71-95	
GRUNDIG C410 Cassette recorder	42-50	32-95	
PHILIPS R.R. 392 MW/VHF Radio			
and Cassette Recorder .....	49-95	36-55	
PHILIPS 2204 cassette, battery/mains	29-10	22-90	
PHILIPS 2202 cassette .....	49-95	36-55	
PHILIPS 3302 cassette .....	20-35	15-95	
PHILIPS 4307 4-track .....	48-65	34-95	
PHILIPS 4308 De Luxe 4-track .....	56-85	41-45	
PHILIPS 4404 4-track stereo recorder	89-25	65-95	
PHILIPS 4407 4-track stereo recorder	108-50	81-85	
PHILIPS 4500 4-track stereo tape			
deck .....	124-30	91-65	
PHILIPS 4408 4-track stereo .....	130-60	98-95	
PHILIPS 2503 Cassette Stereo			
tape deck .....	52-05	42-95	
PHILIPS 2400 stereo cassette less			
L/S .....	66-10	51-95	
PYE 9109 cassette .....	20-37	18-45	
PYE 9116 Stereo cassette .....	66-10	60-95	
PYE 9118 .....	29-11	22-95	
TANDBERG 1841 4-track stereo			
tape deck .....	66-09	48-75	
TANDBERG 3021X twin track stereo	104-00	80-85	
TANDBERG 3041X 4-track stereo .....	104-00	80-85	
TANDBERG 4021X twin track stereo	174-00	135-50	
TANDBERG 4041X 4-track stereo .....	174-00	135-50	
TANDBERG 6041X 4-track stereo .....	188-00	145-25	
TANDBERG 6021X 4-track stereo .....	188-00	145-25	
TELETON TC110 cassette battery/			
mains .....	26-76	18-50	
TELETON TRC 130 cassette with			
VHF/AM radio battery/mains .....	41-32	28-00	
WHARFEDALE Dolby DC9 cas-			
sette stereo tape deck .....	107-50	87-75	
<b>BASES AND COVERS</b>			
GARRARD WB1 Base .....	3-78	3-20	
GARRARD WB4 Base .....	5-60	4-70	
GARRARD SP1 Cover .....	3-68	2-90	
GARRARD SP4 Cover .....	4-38	3-50	
Special offer of Base and Cover to fit			
GARRARD SP25, SL55, SL65B and 3500			
Special Price 3-60 .....			
GARRARD WB4 base Mk II to fit			
Zero 100 & Zero 100S .....	6-55	4-95	
GOLDRING Plinth 75 .....	8-37	7-00	
GOLDRING Plinth 69 .....	8-37	7-00	
GOLDRING Covers for 69P and 72P	4-36	3-75	
Cover for 75P De Luxe .....	4-88	3-95	
THORENS TX25 (for TD125AB) .....	8-26	6-60	
THORENS TX11 Cover .....	4-13	3-75	
Base and Cover for TD 105 .....	12-39	10-50	
SME Plint System 2000 with motor			
board .....	46-20	37-00	
MOTORBOARDS only .....	5-85	3-95	

## COMPLETE HI-FI SYSTEMS

Completely wired mounted  
and ready for use

	Rec. Price	Relail Price	Comet Price
<b>GOODMANS AUDIO SUITE,</b>			
Goodmans Maxamp stereo ampli-			
fier, Goodmans stereomax AM/			
FM Tuner with decoder, Pair of			
Goodmans Magnum K2 speakers,			
Garrard AP75 turntable in base,			
complete with cover and Gold-			
ring G800 Cartridge. Beautifully			
finished in walnut .....	251-80	182-95	

<b>THORENS TD 150AB Mk. II with</b>			
TX11 dust cover, SHURE M55E			
Cartridge, LEAK Delta 70 Ampli-			
fier, 2 Wharfedale Dovedale 3			
Speakers .....	229-96	174-95	

<b>PHILIPS 790 tuner/amp 20 watts</b>			
RMS per channel, FM/MW/LW/			
SW & Stereo decoder, Electronic			
tuning, Goldring G175 turn-			
table on plinth with cover and			
G800 magnetic cartridge, fully			
wired, 2 Mezzo III speakers....	269-19	158-95	

<b>GARRARD AP76 with base</b>			
cover and Shure M55E Cartridge			
Arena 2800 AM/FM and SW Tuner/			
AMP and 2 Goodmans Havant			
speakers .....	214-95	133-95	

<b>GOODMANS Module 80 Tuner/</b>			
Amplifier, Garrard AP76 Turn-			
table with Goldring G800 Car-			
tridge and 2 Goodmans Havant			
Speakers .....	192-97	138-95	

<b>LEAK Delta 30 amp in teak case,</b>			
15 watts RMS channel, Garrard			
AP76 transcription deck with			
plinth, cover & G800 magnetic			
cartridge, fully wired, 2 Dilton 15			
speakers .....	189-36	126-95	

<b>LINTON System with Wharfedale</b>			
Linton Amplifier, Linton Turntable			
with Shure M44-T Cartridge and pair			
of Linton Mk II Speakers .....	143-50	106-95	

<b>AMSTRAD I.C. 2000 integrated</b>			
circuit 20 watts RMS into 8 ohms			
per channel amp, Garrard SP 25			
turntable with plinth, cover &			
Goldring G800 magnetic car-			
tridge, fully wired, 2 Wharfedale			
Denton Speakers .....	114-95	74-50	

<b>AMSTRAD 8000 Mk. II Amplifier,</b>			
watts RMS per channel, Garrard			
SP25 with G800 cartridge including			
base, plinth and cover and pair of			
Amstrad 138 13" x 8" twin cone teak			
finish speakers .....	86-95	48-50	

<b>GOLDRING 705P Turntable, fully</b>			
wired complete with Goldring 850			
cartridge, Amstrad stereo 8000			
amplifier and 2 Amstrad 138, 13"			
x 8" twin cone speakers .....	79-95	39-95	

Complete Price List FREE on request!

## COMET HIGH FIDELITY DISCOUNT WAREHOUSES

- (Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 46441 (6 lines)  
 (Dept. P.W.) 78 Armley Rd., Leeds LS12 2EF Tel. 40551 (10 lines)  
 (Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside,  
 TS18 2RH Tel. 66132 and 65215  
 (Dept. P.W.) Heeley Road, Selly Oak, Birmingham B29 6EY Tel. 021-472 6181  
 (Dept. P.W.) Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley, Birmingham  
 Tel. 021-706 0684  
 (Dept. P.W.) I. Newhaven Road, Edinburgh EH6 5XQ Tel. 554 8501  
 (Dept. P.W.) Syson Street, Leicester Tel. 52234  
 (Dept. P.W.) Corner of Well i' th' Lane and Queensway, Rochdale  
 Tel. 50606

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or if Securicor delivery required add £1-75 only. Make cheques, Money Orders payable to "COMET"



All in-stock items delivered by  
**SECURICOR**  
WITHIN 72 HOURS

(Add £1-75 only for Securicor delivery)

ALL GOODS FULLY INSURED AGAINST  
LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to  
the public from  
9-0 a.m. until  
5-30 p.m. Mon.  
9-0 a.m. until  
1-0 p.m. Tues.  
9-0 a.m. until  
8-0 p.m. Wed.  
9-0 a.m. until  
8-0 p.m. Thurs.  
9-0 a.m. until  
8-0 p.m. Fri.  
9-0 a.m. until  
5-30 p.m. Sat.  
Customers are  
welcome to call  
Ample car  
parking facilities

Free  
Technical  
Advisory  
Service. If  
in doubt,  
ask us!



## SOLE AGENT REQUIRED



**UK 450**

The Amtron range of products will shortly be available in the U.K. and a sole agent is required to handle distribution. These are just four examples from their extensive range of equipment.

### TV SWEEP GENERATOR

Variable frequency signal generator for T.V. alignment; both frequency and amplitude can be modulated. Output voltage 100mV - Frequency range: 34 to 50 MHz - Attenuator: Continuous variation - Amplitude modulation: at 1 kHz depth 30%. Can be operated on 120, 160, 220 and 240V A.C. Power Supplies.




**UK 470**

### CRYSTAL CALIBRATOR MARKER GENERATOR

When a sweep signal is applied to a circuit the curves obtained on an oscilloscope are easier to analyse if they have the precise frequency reference. The UK740 marker generator provides an answer to this problem.

Ratings and characteristics; Radio frequency output voltage; 100mV Output frequency: 27.5 to 47 MHz fundamental 55 to 94 MHz second harmonic: 84 to 140 MHz third harmonic: 140 to 345 MHz fifth harmonic.

Attenuator: continuous variation - Amplitude modulation: internal 1000 Hz with possibility of cutting out the external one by UK 495 - Crystal calibrator - Output frequency: 5.5 MHz - Output voltage at 5.5 MHz: 100mV - Power: 9V battery - Transistors used: 2 x AF106—AC128.

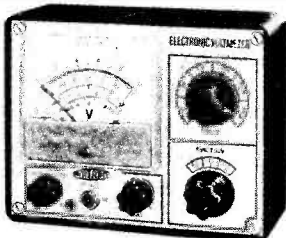

**UK 475**

### ELECTRONIC VOLTMETER

Using FET transistors which give better stability than the conventional valve instrument. Can be used with a 9V battery.

Ratings and Characteristics - Continuous voltage range: from 20mV to 300V D.C. Bandwidth 20 Hz to 1 MHz



**UK 495**

### BAR GENERATOR

The UK 495 can be used for setting up TV sets without the help of the broadcast test pattern.

Vertical bars: variable from 8 to 16; duration: 0.5  $\mu$ s approx. - Horizontal bars: variable from 7 to 13; duration 200  $\mu$ s approx. - Line synchronism: repetition rate 64  $\mu$ s (15625 Hz); duration: 5  $\mu$ s approx. Frame synchronism: repetition rate: 20 ms (50 Hz), duration: 600  $\mu$ s approx. - Power: 9V D.C.

Applications are invited from well established companies able to offer distribution facilities throughout the U.K.  
Please write with full details to:—

**Box No. 102**

**Advertisement Dept., Practical Wireless,  
Fleetway House, Farringdon Street, London EC44AD.**



# PRACTICAL WIRELESS

VOL 48 NO 2

Issue 784

JUNE 1972

## All the Winners!

By a unanimous decision, the panel of judges, comprising the Editor and editorial staff of P.W., selected as the winner of the Project Autumn competition the following article:

1. **Digital Frequency Counter/Timer**, by J. Thornton-Lawrence (September-December 1971).

Congratulations are therefore due to author John Thornton-Lawrence for the design, construction and preparation of his most successful project since he started writing for us. Apart from the opinion of the judges, the Digital Frequency Counter/Timer has enjoyed a great success with readers, as confirmed by correspondence. John will soon be travelling to London to officially receive the Designer's Trophy and we hope that he has cleared a prominent space on the sideboard to display the cup!

The selection of runners-up was more difficult. There were twelve nominations to be considered and placed in order of merit. In the event, these were the articles selected:

2. **Linear Ohmmeter**, J. N. Watt (Sept. 71)

3. **Quality Hi-fi System**, C. R. Bradley (Feb.-April 72)

4. **Gate Dip Oscillator**, B. Wood (February 72)

5. **Cube Radio**, R. F. Graham (March 72)

6. **Modular Audio Mixing System**, F. C. Judd (Oct.-Dec. 71)

While congratulating the runners-up, we must also offer our sympathy to the several authors who very nearly squeezed into the final list—some by a very narrow margin.

As mentioned last month, and detailed elsewhere in this issue, our next writer's competition is restricted to those who have never written for P.W. before. This should provide a keen incentive to readers who have hitherto felt that the opposition might be too strong!

We will, of course, continue to publish articles by our established authors, but they will not be eligible for the competition itself. In this way, if we achieve nothing else, it will be seen that the pages of P.W. are open to anyone producing the right kind of material. A study of the winning articles in the last competition will be helpful in assessing chances and will also show that a long and complex article is not necessarily the route to a prize. And for new writers who need a little guidance on preparing articles for publication, some handy notes are available from this office on request. Now it is up to you!

W. N. STEVENS—Editor.

## NEWS AND COMMENT

Leader	121
News . . . News . . . News . . .	122
Mobile Rally Diary	149
Letters	153
CQ! CQ! CQ!	156
MW Column by Charles Molloy	156
Electronotes by S. Ginsberg	157
Practically Wireless by Henry	158
On the Short Waves by Malcolm Connah and David Gibson, G3JDG	169

## CONSTRUCTIONAL

Estelle 12-Watt Record Player by H. T. Kitchen	124
Modifications to the Transistorised Oscilloscope by J. Ransome	130
Constructing the P.W. Electronic Ignition System, Part 1, by D. G. Fripp	133
Take 20, No. 37, Burglar Alarm by Julian Anderson	142
The Texan 20+20W IC Stereo Amplifier, Part 2, by Richard Mann	144
MW/IF Wobbulator by A. J. Birkinshaw	150
Test Bench Amplifier by E. Buckland	154

## OTHER FEATURES

Transistor Circuitry for Beginners, Part 8 by H. W. Hellyer and Michael Hollier	161
IC of the Month RCA CA3090Q Stereo Decoder by L. A. J. Ireland	173
Going Back by Colin Riches and Arthur Dow	175

**JULY ISSUE WILL BE  
PUBLISHED ON JUNE 2nd**


©IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS...

# NEWS...


# NEWS...

## Push-button wonder

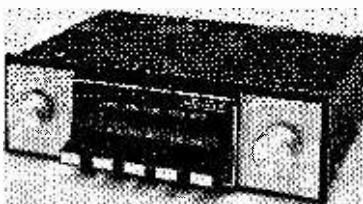

It's a "wonder" because it's a push-button car radio in kit form retailing for only £7! Step-by-step assembly instructions are provided with the kit, and the manufacturers, Radio & TV Components Limited, maintain that anyone with a little experience in wielding a soldering iron can complete the unit in an evening—or if you go to bed very early, two evenings! An integrated circuit and a printed circuit board simplify construction and cut down the number of components to be soldered. The "Tourist" car radio, as it has been called, features five push buttons which can be tuned to four preset medium wave stations. The fifth button is for use on long wave. Spun aluminium knobs are used and the tuning scale is illuminated.

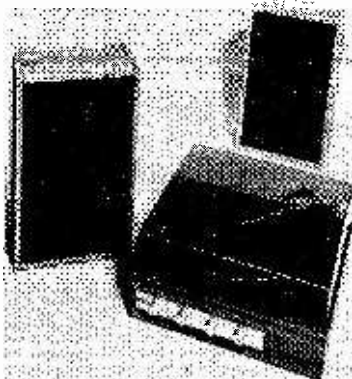Permeability tuning is employed and r.f. sensitivity is said to be better than  $15\mu\text{V}$  at 1MHz. Power output into an  $8\Omega$  speaker is better than 2.5W. The i.f. module and the tuner are pre-aligned and




the kit is suitable for 12V positive or negative operation.

Also announced by Radio & TV Components is the £25 stereo system designated Unisound 505. This comprises pre-assembled units which can be wired together in about an hour by means of a screwdriver (no soldering iron being needed). Basically the units used in this system are the Mullard Unilex modules modified by the addition of ATEs integrated circuits on the amplifier output stages to provide increased output. The turntable supplied is a Garrard 2025 TC and speakers are dual cone  $13\times\text{in.}$  ellipticals in kit form, manufactured by EMI.

Further information on both of these units may be obtained from Radio & TV Components, (Acton) Limited, 21 High Street, Acton, London, W.3.

## Saba radio

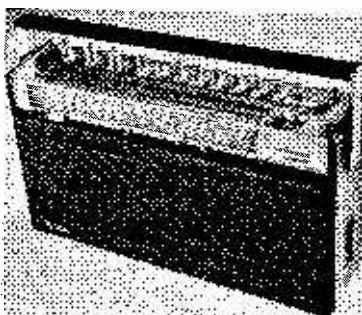

One receiver in the new Saba range is the Transeuropa Automatic G Radio mains/battery/car portable radio. Waveband ranges are: f.m. 87.5MHz-104MHz, SW1

6.8MHz-18.9MHz, SW2 15MHz-15.5MHz, SW3 5.9MHz-6.23MHz, SW4 2.8MHz-7.5MHz, MW1 510kHz-1220kHz, MW2 1180kHz-1630kHz, LW 150kHz-300kHz.

Twelve transistors are used and the f.m. tuner employs two transistors and vari-cap diode tuning. There are common i.f. stages for a.m. and f.m.: 460kHz 10.7MHz.

A five transistor audio amplifier provides 3.6W and 6W when operating from 12V car battery. There are  $2\times 5\Omega$  Ohm speakers—7 &  $2\frac{1}{2}\text{in.}$ —the  $2\frac{1}{2}\text{in.}$  speaker is switchable. Treble and base controls are provided amongst many other features. Recommended retail price is £55. U.K. Distributors are Lampitt Electronics Limited, Manchester.


## Burnt fingers

We mentioned it once before, and we're mentioning it again because it's useful stuff. Burneze, priced at 39p, is an aerosol preparation which gives instant relief to minor burns. Available through all branches of Boots and most good chemists, it should have a place in every workshop, or home first aid kit, ready for instant action the moment you grab hold of the wrong end of the soldering iron!
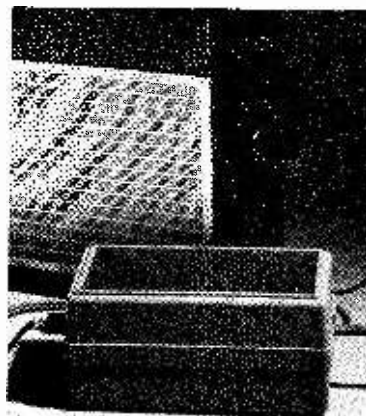
## Hacker power

The VP408 is a fully-stabilized power unit designed to plug into the mains electricity supply and give a d.c. output adjustable from 6 to 18 volts.

Selection of the voltage required by the equipment to be operated is very simple. Set flush in the underside of the unit is a circular control which may readily be turned by a small screwdriver until the pointer on the control is in line with the voltage indicated on the scale.



The VP408 is intended primarily as an alternative to batteries as the power source for Hacker portable radios, but its wide range of stabilized voltages makes it an ideal power source for portable radios generally, some cassette tape recorders and other equipment requiring low voltage d.c. current within the capabilities of the unit. The VP408 costs £6.90p. Hacker Radio Limited, Norreys Drive, Cox Green, Maidenhead, Berks.

# NEWS... NEWS... NEWS...

## Record rack

The record rack shown on the front cover was kindly loaned to us by *Civil Service Stores, Strand, London.*

## TEAC amplifier


Acoustico Enterprises Ltd., inform us that they now have stocks of Teac equipment and in the picture we show the Teac Amplifier type AS-200S, retailing at £170.48. This is an all silicon transistor stereo amplifier having a rated power of 60W per channel  $\pm 0.5\text{dB}$  into a  $4\Omega$  load or 50W per channel  $\pm 0.5\text{dB}$  in an  $8\Omega$  load. Harmonic distortion is under 0.5%, rated output, under 0.1%, 30W output and under 0.1% 100mW. Frequency response is 20-80,000kHz  $+0\text{dB}$   $-1\text{dB}$  and power bandwidth is 20-30,000Hz. Input impedance is  $25\text{k}\Omega$  or more and sensitivity is 0.7V for rated output.

Elimination of capacitance from the output circuit plus the very stable dual p.s.u. results in an 'unprecedented' flat frequency response which is very noticeable in the low frequency ranges.


A precision 3dB step selection tone control is employed to eliminate any tonal imbalance between channels.

So that the speakers are protected from surge voltage when the unit is first switched on, Teac have included a muting circuit that prevents any current flow to the speakers until the unit has stabilized—usually 3-4 seconds after switch-on.

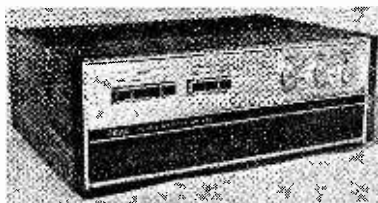
A matching and very smart looking a.m./f.m. stereo tuner designated AT-200S is also available from Acoustico for £220.41. For further information on Teac equipment contact *Acoustico Enterprises Ltd., 6-8 Union Street, Kingston Upon Thames, Surrey.*



## Drills for printed circuit boards

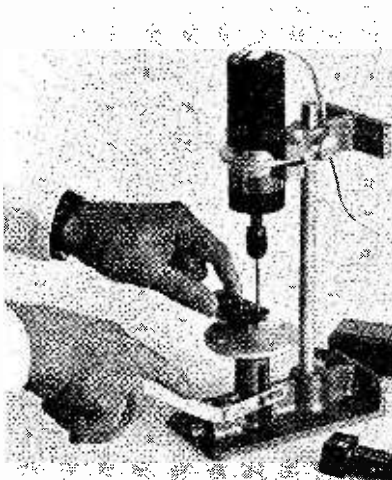

Last October we gave details of two miniature electric drills, made by Expo (Drills) Ltd., which have proven very useful indeed to constructors faced with the problem of drilling a multitude of small holes in circuit boards. The Reliant, and its big brother the Titan Super, are intended to run from a 12V battery or a mains rectifier unit. Now a drillstand-cum-lathe bed is available capable of accommodating either drill. The drill is attached to the stand by a fixed clamp, the work table rising up to the drill by means of a small hand lever against a spring action.

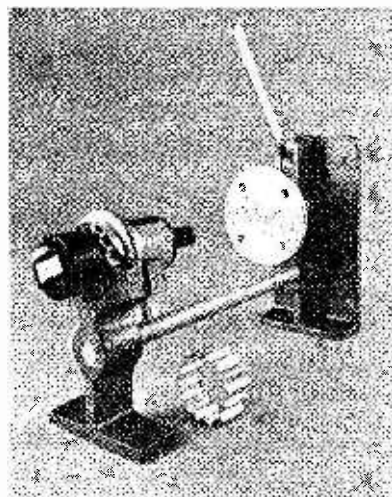

Holes are provided in the stand body to enable it to be screwed down to a bench or to a moveable wooden base. The stand can also be screwed down with the drill and main post horizontal when it may be used as a simple lathe bed for polishing, grinding or cutting. Apart from standard twist drills various cutters, burrs and saws are available as accessories. All these can be accommodated in a set of three collets with a maximum capacity of  $\frac{1}{8}\text{in}$ . A three jaw chuck of unique design is expected to be available in the near future. Details from *Expo Ltd., 62 Neal Street, London, W.C.2.*

## Texan transformers

Gardners Transformers Limited announce a new range of low-profile transformers which are designed to overcome the transformer problems associated with the modern tendency towards slimmer electronic equipment.

Use of a Solo Series Transformer (Gardners Type SL 20) in the "Texan" stereo-amplifier designed by Richard Mann, of Texas Instruments, enabled the designer to achieve a remarkably compact design.

Further details of the new SOLO Series (Drawing A.3869) are readily available to industrial users, while a separate Advance Technical Data Sheet (AT.23)

describing the Texan 20W transformer will gladly be forwarded upon request to *Gardners Transformers Limited, Christchurch, Hampshire, BH23 3PN.*





H.T. KITCHEN

**T**HIS is a project that really got out of hand! Originally I had an old Garrard 4HF turntable that had seen better days and the intention was to put it in a home-made cabinet with a simple mono amplifier and hand it over to my daughter Estelle for her birthday. Her chief criterion of quality is the level obtainable, "the louder the better"!

In the end a second hand Garrard SP25 deck was fitted carrying a ceramic cartridge of unknown history. The "simple" amplifier finished up with ten transistors and at least "mid-fi" performance. The relatively small elliptical speaker in the cabinet has

become more of a monitor speaker, the amplifier output being taken to a larger external speaker better able to handle the amplifier output of 12W r.m.s.

## THE PREAMPLIFIER

A pre-amplifier performs two basic functions. It must raise the usually low voltages fed into it to a level suitable for feeding the power amplifier, and it must be capable of altering the frequency response of the signals passing through it to fulfil two essential requirements. First, to equalise or com-

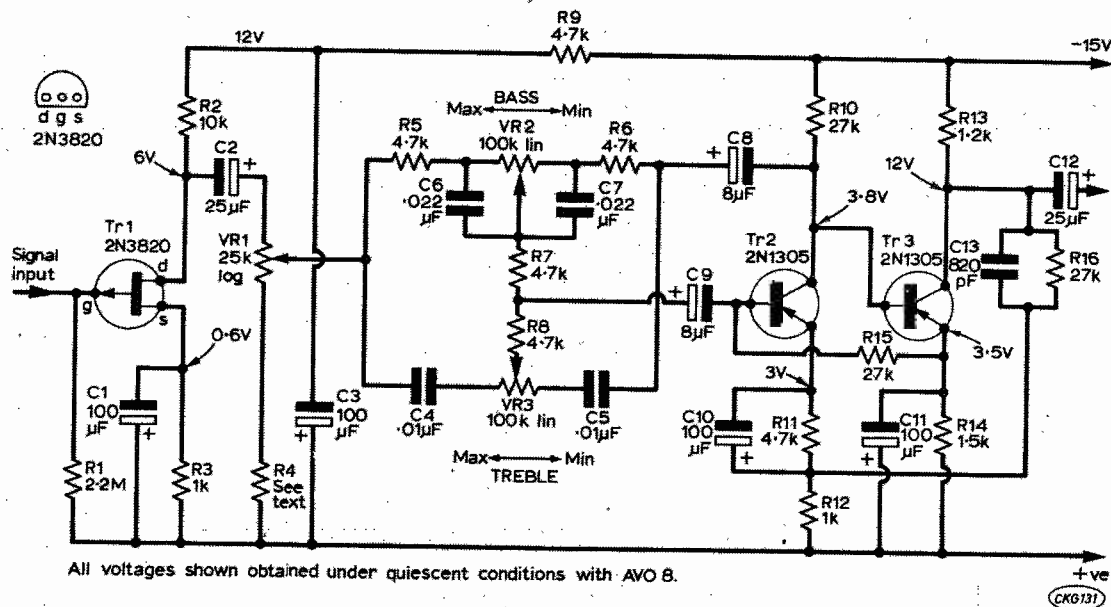


Fig. 1: The circuit of the preamplifier and tone control sections.




The first requirement is a fixed frequency response to the RIAA standard. The second requirement is to provide a variable frequency response, the limits of which follow long established practice. The paradox referred to earlier is a necessary one, for the flat ideal response may result in a sound output from the loudspeaker that is aurally totally unacceptable. The variable frequency response that results from the use of correctly designed tone controls allows the user to modify the response so that a more pleasing sound can be obtained from the loudspeaker, even though a graph of the same response may well depart, perhaps greatly, from the theoretically "correct" flat line response.



Tr1 feeds the volume control VR1 at the earthy end of which is a low value resistor, R4, allowing a low level signal from the loudspeaker whilst a record is being played with the volume control at minimum.

The output of the volume control feeds the tone controls which are of the well known and highly regarded Baxandall configuration. A further stage of amplification follows the tone controls before the signal is ready to be passed on to the power amplifier. The degree of amplification required is quite modest but nevertheless two transistors are allotted to this task. The configuration of Tr2 and Tr3 however, allows the overall gain (of the two) to be closely controlled, and is therefore far superior to a single transistor. Direct coupling from Tr2 collector to Tr3 base goes a long way towards eliminating low frequency phase shifts which can occasionally prove troublesome.

 A further advantage of the two transistor circuit is the ability to "tailor" the a.c. feedback such that it becomes frequency selective. This can be effected by





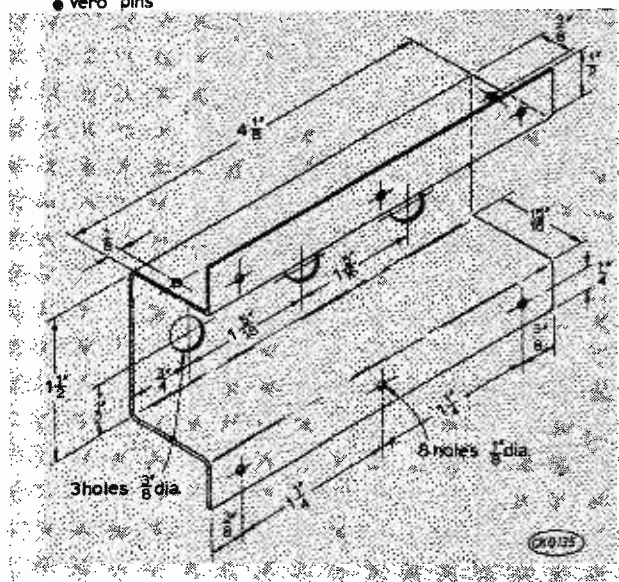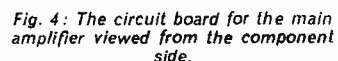

mounted Tr10 with an insulating mica washer. D2, R31 and C22 are grouped round the pins of Tr10. The ends of the aluminium panel protrude either side of the mains transformer body, and carry C21 and C23, one at each end.

The end of the transformer, remote from the power transistor heat sink, Fig. 6, carries a small panel of s.r.b.p. on to which are mounted eight tags.

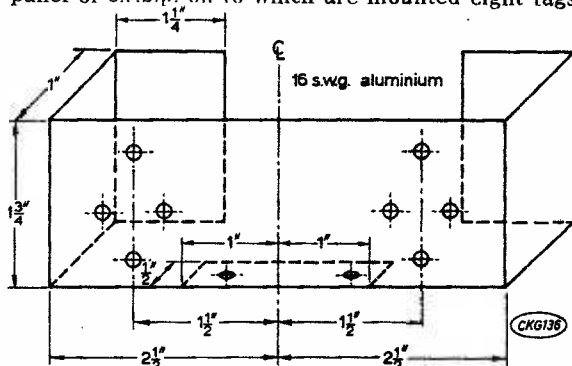


Fig. 6: The heatsink for the output transistors made from 16 s.w.g. aluminium.

Diodes D3 to D6 are soldered to these turret tags, the interconnections being on the reverse side. Since the current demands are heavy (relatively speaking) wire of a suitably heavy gauge must be used such as 14/01in.


## COMPONENTS

It must be borne in mind that the power amplifier and the latter two transistors of the pre-amp are directly coupled; any faulty transistors, or transistors well outside the published specifications, can lead to fault conditions developing. At best these conditions will prevent correct operation of the equipment; at worst they will cause the destruction of the power transistors. The "cure" is to buy only new transistors from a reputable supplier.


With the exception of R29, R30, and R31, all the resistors used are 5% 1/2W carbon film types since these are now freely and inexpensively available from many suppliers. The use of these resistors makes subsequent fault finding very much easier, should the need arise, since any deviation from correct operation can almost certainly be attributed to the semiconductors whose manufacturing "spreads" are so much wider than those of the resistors.

The mains transformer, as already explained, was purchased with a 30V secondary. If the expense of the simple series stabiliser is unacceptable, then the conventional power supply (transformer—rectifier—capacitor) can be used. Under these conditions, the transformer should be rated at 18 to 20V at 800mA for a single amplifier, or at 1.5A for a stereo pair. Since smoothing is now dependent upon C23 alone, it should be increased in value to 2000μF or 2500μF. An anti-surge resistor of about 1Ω should be interposed between the rectifiers and C23.

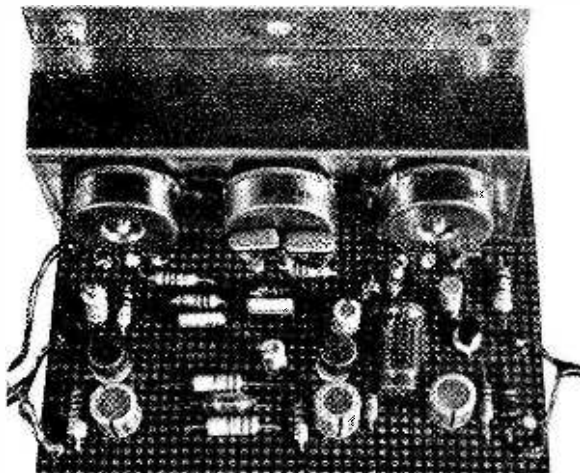
When the amplifier is delivering its full rated power, transistors Tr8, Tr9, and Tr10 get very hot under sustained drive conditions, and adequately rated heat sinks are necessary. Under normal conditions, when music is being reproduced at a reasonable level, through speakers of average efficiency, the heat generated is very much less, and smaller



A view of preamplifier.

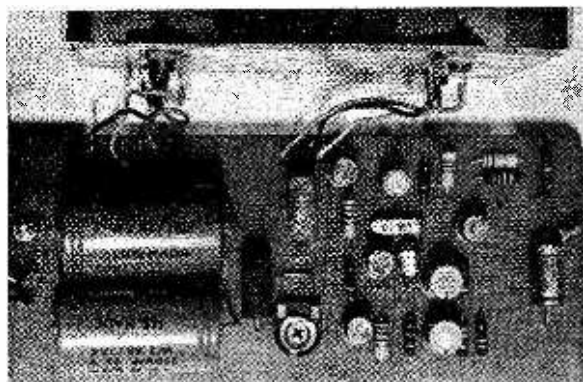

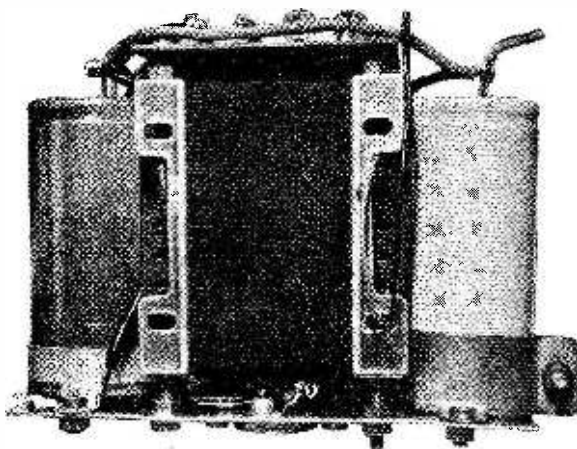The main amplifier. The wires to the output transistors can be seen at the top.



The power supply.

heat sinks can be used, providing an adequate air flow is ensured.

When the various units are completed, they must be thoroughly checked over; wiring errors, shorting wires, etc., can be disastrous, so time spent in careful checking is time well spent.



The first item to be checked can be the power supply. Assuming a series stabiliser is used with a transformer having a 30V secondary, the voltages should agree closely with those shown in Fig. 3.

Having allowed C21 ample time to discharge completely, the power amplifier can be connected to the power supply. A fairly high wattage resistor of some 10 to 20Ω should be connected in series with the negative line to limit the maximum current that can be drawn in the event of the power amplifier having a fault condition. Power can now be applied.

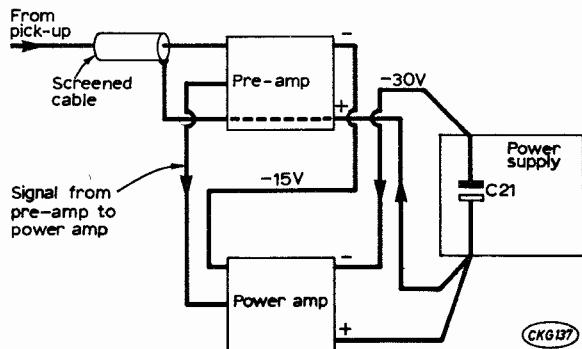


Fig. 7: The interconnection of the individual sections.

An accurate voltmeter should be connected to the centre point and VR4 adjusted to provide a centrepoint voltage of approximately 18V. The remaining voltages can also be checked and should agree with those shown in Fig. 2. If voltages differ considerably from those shown, or if the centrepoint cannot be set to 18V, then a semiconductor is the most likely cause, and the easiest course of action is to remove them all from circuit and have them checked on a reliable tester. It is no good pressing on in the hope that the fault will "go away". It won't, it will remain or get worse. If all appears to be well, the series resistor can now be removed.

The centre point voltage, under quiescent conditions, is set to exceed half the supply voltage by a small margin, so that at maximum drive the centre

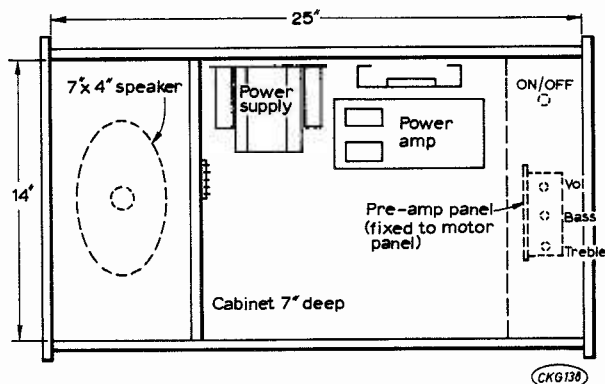


Fig. 8: The general layout employed in the prototype.

point falls to exactly half the supply voltage. Limiting, under conditions of excess drive, will therefore be symmetrical.

If an audio oscillator and oscilloscope are available, VR4 can be set even more accurately. A 1kHz

signal is injected into the base of Tr4, and the oscilloscope is connected from the centrepoint to earth. The input from the generator is increased to the point where limiting becomes visible on the oscilloscope. VR4 is then adjusted until the limiting become symmetrical, i.e. positive and negative peaks are evenly clipped. Since VR4 has an effect upon the overall gain of the amplifier, the input signal may require altering to compensate.

As explained earlier, the output transistors are liable to be damaged, or even completely destroyed if indiscriminate high power testing is indulged in. For this reason, sine wave testing at full power *must not be attempted beyond 1 or 2kHz*. High frequency testing can be attempted, but at greatly reduced power outputs. Even then, a series ammeter should be used to continuously monitor the current consumption. If this is done at a carefully chosen output then it will become apparent that I<sup>2</sup>R as a function of *actual power output*, and I<sup>2</sup>R as a function of *power consumed*, are two very different quantities, the power consumed being, of course, greater than the power output, the difference increasing with an increase in frequency.

When the power amplifier has been satisfactorily set up, attention can be turned to the pre-amp. Again, an audio oscillator and oscilloscope are invaluable. A voltage at 1kHz., equal to the peak output of the cartridge to be used, is fed into the input of the pre-amp and R16 is selected such that, with the volume control fully advanced, the output waveform from the power amplifier just starts to limit. This will ensure that distortion due to overloading cannot occur, even at maximum output.

## CONNECTING UP

AC currents of over 1<sub>2</sub>A flow through the output stages under maximum drive conditions and incorrect earthing can result in instability or the formation of hum loops. Some thought to interconnections must therefore be given, the circuit of Fig. 7 having been found satisfactory. The pickup lead should only be earthed at the pre-amp, the other end being left disconnected. The turntable should be earthed separately to the main earth. On the prototype, a separate mains on-off switch is used, sited well away from pre-amp to preclude any possibility of mains induced hum. This switches the mains to the player as well as to the amplifier power supply.

Although the amplifier has been described as a mono or single channel unit, reference has occasionally been made to stereo operation. This is, of course, quite possible. All that is required is a doubling up of everything, with a revised physical layout. Separate heat sinks should be used for the two power amplifiers, and if continual high power operation is envisaged, these should be of the commercially produced extruded type.

The power supply will require revision, since a single NKT404 will probably be overrun. Its maximum collector dissipation in the present application is in the region of 8W and this will be doubled for stereo. The easiest course, if a regulator is desired, is to replace the NKT404 with a 2N3055 in the positive side, and to turn the power supply circuit "up side down". The 2N3055 must be mounted on an extruded heat sink to dissipate the heat generated safely, this being mounted in a position where an adequate air flow is possible.

# MODIFICATIONS TO THE TRANSISTORISED OSCILLOSCOPE

FEBRUARY-MARCH 1972

SINCE publication of the constructional details of the Transistorised Oscilloscope in the February and March editions of *Practical Wireless*, many readers have written in to say that they have had difficulty in obtaining the VCR 139A cathode ray tube. When the unit was first designed, stocks of this tube appeared to be adequate to meet the anticipated demand, but the response to the article has been very much greater than expected and consequently the VCR 139A has become a very rare specimen! In reply to readers' requests several alternative tubes have been tried but, to date, only two which are readily available in quantity have proved to be satisfactory—the surplus 2A P1 and the Mullard DG 7-5.

The 2A P1 can be used as a direct electrical replacement with only one circuit modification (change R12) but suffers from two mechanical disadvantages:

1. The tube face is only 2in. diameter rather than 2½in. of VCR 139A.
2. Some versions are slightly too long to be accommodated into the original chassis design. Early versions of the tube are just over 10in. long and will require extensive modification to the metalwork before they can be used. The later, and fortunately much more common version, is 7½in. long and fits perfectly well into the cradle as designed.


The pin connections for the 2A P1 are shown in Fig. 1 together with the corresponding connections for the VCR 139A. The only electrical modification is the changing of R12 (Fig. 5 page 887 of February issue) which should now be 10Ω 5 watt.

The Mullard DG 7-5 is listed by its makers (Philips of Eindhoven) as being obsolete, but, on checking with wholesalers, it still seems to be very widely stocked throughout the country and should be available to special order from any good component retailer. This tube works very well in the revised circuit and gives, if anything, a slightly brighter and better focussed trace than the VCR 139A.

The modified display unit is shown in Fig. 2 and this should be compared with the original circuit (Fig. 5—page 887). As will be seen the main change to the original circuit is the provision of a negative supply for the tube grid. This supply is required because the heater and the cathode of the DG 7-5 are internally connected, so that instead of being able to take the grid to chassis and running the cathode at a positive potential with respect to the chassis, we are obliged to hold the cathode at chassis potential and make the grid negative. The additional components required for this modification are prefixed with the figure 4 in the revised circuit diagram.

The major points concerning construction and testing are unaffected by this modification and the few additional components are easily accommodated on the tag-strips mounted on the back panel.

DN 0669

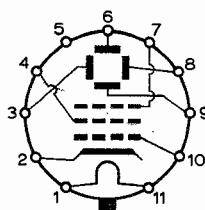

Tube 2A P1  
Base USM11

	2A P1	VCR139A
Heater	1,11	3,4
Cathode	2	1
Grid	10	2
Focus electrode	4	5
Anode	7	9
X plates	3,8	8,10
Y plates	9,6	7,11

Fig. 1: Pins connections of the 2A P1.

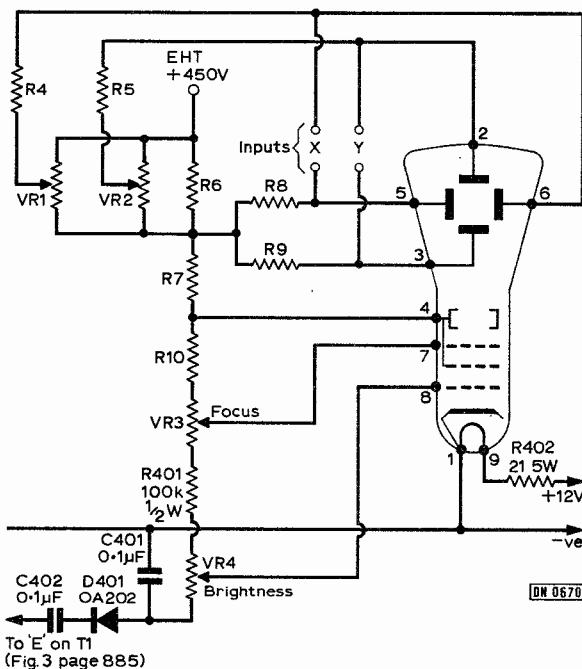


Fig. 2: Circuit changes when using the DG 7-5 tube.


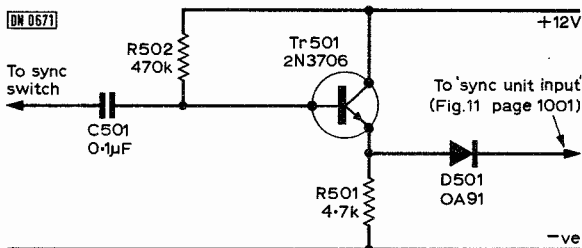


Fig. 3: Modification of the sync circuit.

Many readers have expressed a preference for a more conventional synchronisation circuit than the gated system used in the prototype. The most obvious method is to feed negative going pulses into B<sub>2</sub> of Tr9 (Fig. 11 page 1001) but unfortunately this seems to have a rather distressing effect on linearity. A simple and effective circuit is shown in Fig. 3—the only disadvantage being a lack of sensitivity to very fast pulses.

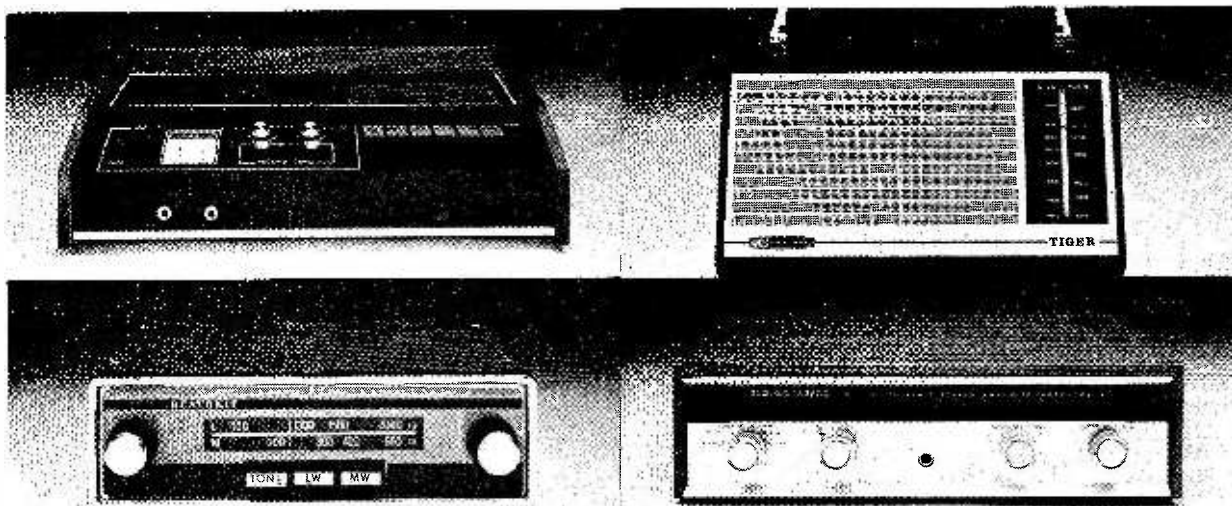

If you can use a soldering iron and follow simple instructions, you can assemble any of these high performance products in a few hours. And save a lot of money

Heathkit have the world's widest range of top quality electronic products designed specifically for home assembly.

Of which we show just 4 above.

The AD110 is our new stereo cassette recorder. It gives you cassette convenience, reel performance and Heathkit quality. Designed to complement various other Heathkit Hi Fi products, it costs only £74.80 + £8.45 for twin matched stereo mikes.

Another new product, the Tiger transistor radio kit

costs £10.90. It gives long life from every large PP9 battery, weighs just 3 lbs, and gives really good reception on Long & Medium wavebands.



And, as you can see, it looks pretty good too.

Costing just £18.45 complete with speaker and aerial, the CR1 car radio gives unsurpassed reception. A 6 transistor, 2 diode circuit gives 4 watts output, pre-assembled and aligned tuning unit makes assembly easy, and push-button controls give instant selection.

The AA14 30 watt stereo amplifier is an established

product, proven in use by thousands of satisfied customers. Featuring a 17 transistor, 6 diode circuit, it costs £30.00 less cabinet.

These products and all the others in the Heathkit range are easily assembled by anyone who can use a soldering iron and follow our superbly clear, step-by-step instructions. Furthermore, in the unlikely event that you get stuck, we guarantee to help you out.

Find out more. Send for our free 1972 catalogue. Now.



*Guaranteed  
Fault Proof*



You can make it if you try.

Please send me the FREE New 1972 Heathkit catalogue.


Name .....

Address .....

PW06/72

HEATH (Gloucester) Ltd., Gloucester GL2 6EE


# LINDAIR (ELECTRO-TECH) LTD

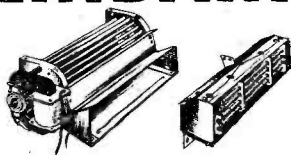

## TANGENTIAL HEATER

Silently driven by a shaded pole Mylex motor. Compact, powerful and quiet running with aluminium impeller (outlet 5/8" x 1/4"). Mains voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts. **PRICE ONLY £1.60** P. & P. 40p

## SYNCHRONOUS AUTO-RESET PROCESS TIMER

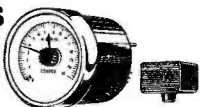

By LONDEX LIMITED

Type IMP Mk. 2. Brand New and Boxed. These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing. Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes. 230/250v. 50Hz, also available 60Hz. 15 minutes full scale, 15 secs. per division. Driven by self-starting sync. motor. Contact rating 5 amp at 250v. a.c. incorporates solenoid operated clutch. Also, lever actuated micro switches. Normal price probably in excess of £18. Complete with multi-pin connector as illustrated.

OUR PRICE ONLY

£6.50

## SEEN THIS ?

This is the only way we could illustrate this fabulous item.

## NORPLEX

the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec. conductive properties. Heat Resistant. Ideal for P.C.s, etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST. Sizes: 12" x 12", 24" x 12", 24" x 24", FULL SHEET 43" x 37" (11 sq. ft.). Single sided copper with thicknesses of 1/32", 3/64", 1/16", 3/32", also Double sided 1/32", 1/16", 3/32".

**PRICE ONLY £1** per sq. ft. 58 per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only £1 one or more sheets.

## MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.5v, 10-15ma. Size 4.4 x 1.4mm. dia. Leads 22mm. These fantastic lamps have a life expectancy of 1,000 hrs.

OUR PRICE

£3.25

per doz. Free p. & p.

## NEW AND UNUSED

Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50, cash with order please.

## FURTHER BULK PURCHASE

## SILVANA MAGNETIC SWITCH




NOW COMPLETE WITH REFERENCE

MAGNET! A magnificently activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v. 13 amp at 240v. Size (approx.) 1 1/8" long 1/2" dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. **New Lower Price.** Only £2.10 for 12, £3 for 50 or £15 for 100 complete with magnet.

£2.10

## PROGRAMMER TIMER

BY HONEYWELL

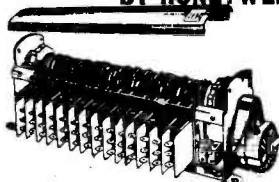

A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £15.00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p P. & P.

£5.75

301 EDGWARE ROAD, LONDON W2. Tel: 01-262 2251. Open 9 a.m.-6 p.m. MON to SAT

## SOUND BARGAINS



## GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM  
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

£10.50 + 40p. P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention. Even TV Sound in certain areas. PLUS A SPECIAL WEATHERBAND. Frequency ranges: MW540-1600 KHZ, FM88-108 MHz, Airband 108-145 MHz, VHF 145-175 MHz, 23 semi-conductors—12 transistors 11 diodes and thermistors. Automatic frequency control stops irritating station drift. Built-in adjustable 8-section 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 V2 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2" x 6 1/2" x 3 1/2". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. HURRY! Limited quantity only from Markytme. Money back guarantee.

OUR PRICE £28.95 + 50p P. & P.



8 WAVEBANDS AND WORLD MAP & TIME ZONE DIAL

Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with Stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermister. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 350-1500Kcs. Marine 1.6-4.5Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. Aircraft 108-135Mcs. PUBLIC SERVICE BANDS 135-174Mcs. Fully guaranteed.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

**MARKYTME**

(DEPT. FW1), 372 EDGWARE ROAD, LONDON, W.2 Tel. 01-723 0084. Callers welcome Monday to Saturday 9 a.m. to 6 p.m.

## NEW - NEW - NEW

\*YOUR FEARS! — ARE THEY GROUNDESS? PARTRIDGE, THE PIONEERS OF THE SPACE-AGE COMPACT, VERSATILE, WORLD RECORD AWARD WINNING

## JOYSTICK V.F.A.

REGD.

ANNOUNCE THE INTRODUCTION OF TWO MORE PIONEER PRODUCTS FOR THE TRANSMITTING AMATEUR AND S.W.L. (utilising our well-known small plastic containers).

1. \*THE JOYMATCH ARTIFICIAL EARTH: BAND-SWITCHED. EFFECTIVELY REPLACES OUTDOOR EARTH SYSTEMS. FITS COMPLETELY INSIDE THE SHACK. FANTASTIC RESULTS. £4.50 (plus 30p P/P).
2. THE JOYMATCH AERIAL BANDSWITCH: A COMPLETE foolproof indoor or outdoor AERIAL SYSTEM suitable for ALL TYPES OF RADIO RECEIVERS. FULL SW AMATEUR & B'CAST plus MARINE BAND coverage. Single control function switch brings that signal roaring in. £4.50 (plus 30p P/P).
3. For the D.I.Y. SWL & TRANSMITTING AMATEUR: A triple purpose 6 band A.T.U. in Kit form, easily assembled (using step-by-step instructions) in 45 mins. Tunes communications RXs and TXs (300W P.E.P.—PA input) 160 thru 10m on TX and 1-2 to 32 MHz on Receive. Most attractive appearance £4.50 (plus 30p P/P) or ready assembled and tested. £5.50 (plus 30p P/P).
4. JOYSTICK V.F.A. latest model now £11.00 plus 30p P/P (gold stove enamel) or £8.00 plus 30p P/P (white stove enamel—earlier model).
5. NATURAL GROUND SYSTEMS—DETAILS ON REQUEST.
6. JOYMATCH III (one-eleven) now £11.00 plus 40p P/P.

Send 3p stamp for full details to:

**PARTRIDGE ELECTRONICS LTD. (PF)**

BROADSTAIRS, KENT, ENGLAND.

Telephone (Thanet) 0843 62535 (C.O.D. orders accepted by telephone). Cheap telephone period—Ring 0843 62839 7-8 p.m. Monday-Friday.




# constructing THE PW ELECTRONIC

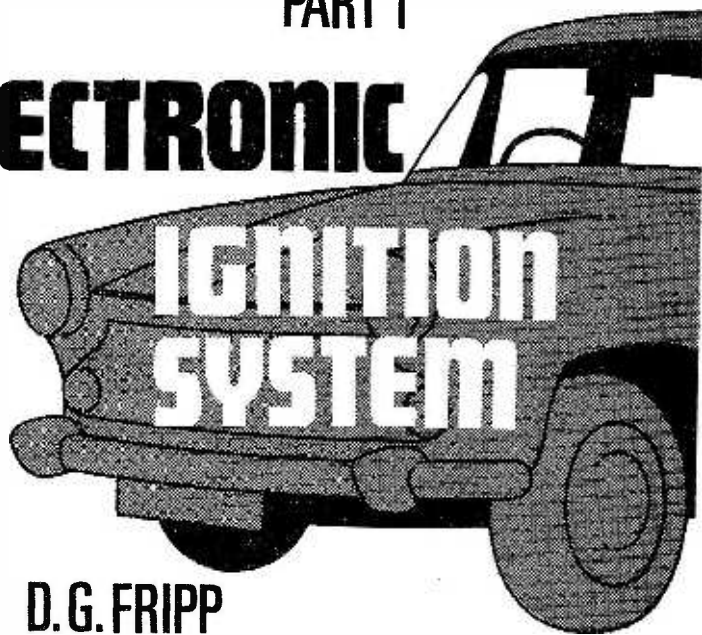PART 1

Last June we published a short article on the PW Electronic Ignition System little realising the tremendous interest it would arouse. Thousands of these units have been built but many readers wrote in saying "I've got all the parts, what do I do next?" Here is all the information they could possibly need, based on the experiences of a reader.

THE advantages of an electronic ignition system are now quite well known, and of the various systems available perhaps the "capacitor discharge" system is the most widely popular. This constructional article deals with such a system and follows closely the circuitry as described under this heading in the June 1971 issue in which most of the advantages were fully explained with the exception of one fact of paramount importance to the constructor; as this system uses the contact breaker as already fitted to the car, it in no way alters the timing; thus in the unlikely event of a component failure, a quick rearrangement of the connecting leads taking less than thirty seconds enables the car ignition to be returned to normal and the journey resumed.



D.G. FRIPP

Unlike many other systems employing specialised components which are not always readily available even from agents without some delay, this system with its inherent safety factor of easy reversion has much to commend it, as no doubt anyone who has been stranded by an ignition fault would hasten to agree.

## SOME ADVANTAGES

Some not quite so obvious advantages not previously mentioned may be of interest to would be constructors, not least of which is the fact that owing to the more powerful spark delivered to the plugs by this electronic ignition unit—this may vary from 20 per cent to 40 per cent depending on the coil used—the firing of the petrol-air mixture is ensured, thus a slightly weaker mixture can often be used to enhance the economy already achieved by this form of ignition due to more complete combustion. This of course means that as up to 25 per cent more of the fuel used is burnt in the engine, where it develops more power, there is a correspondingly significant decrease in the pollution emission in the form of unburnt exhaust gases. In these days of a growing awareness of the desirability of reducing the amount of pollution, as is typified by the lowering of the limits of exhaust emission which must be complied with for the importation of cars into the U.S.A. in the near future, it would seem that the future of electronic ignition may well be assured if only from this one important aspect.

Another advantage of this type of ignition is that because of the faster rise time (as against conventional inductive systems) there is much less time for the current to leak away through any leakage paths which may exist on any of the insulated parts of the ignition components such as plug insulators, leads, distributor cap, rotor arm, and coil h.t. stack, also any conductive deposits which may have accumulated on the plug firing points. Thus plug fouling is virtually eliminated and therefore the heat range grading can be ignored. From this it can be

seen that a vehicle using this electronic ignition unit, which is driven under widely varying conditions, should not exhibit any plug trouble even if it were prone to with normal ignition, assuming plugs of reasonable condition.


Largely because of the reasons just mentioned at least one well known plug manufacturer has developed a plug specifically for use with electronic ignition. This plug has an annular gap, which has the effect of greatly increasing the mass of the outer electrode, so its erosion should be slower. It should be realised that the effect of a high energy spark is likely to cause more erosion of the electrodes—especially the outer—although this seems to be offset to some degree by using wider gaps as is advocated later in this article, and is probably nullified by the fact that this high energy spark is of much shorter duration—approximately one fifth of a conventional system—and contains nearly equal positive and negative half cycles so that metal migration of the plug firing electrodes should be very much less.

Certainly these conditions would appear to prolong spark plug life, and this is borne out by one such car fitted with new plugs when one of these ignition units was installed, as careful examination of the plugs over 5,000 miles later showed no observable deterioration of the firing electrodes.

From this it can be seen that the normal plugs as quoted by the car manufacturer can be used with confidence, provided that they are in reasonable condition and the gaps are reset.
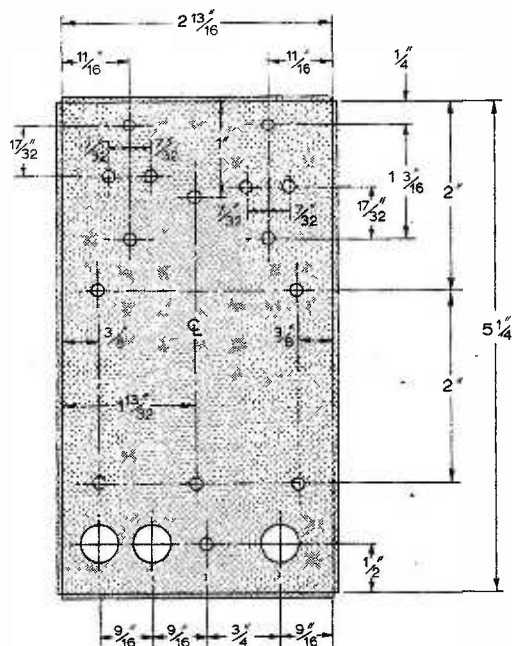
## POLARITY

The unit as shown is the one as used for positive earth supply, but the method of construction and the placing of components is identical for the negative



18 s.w.g. aluminium  
Small holes .04 BA clearance. Large holes  $\frac{3}{8}$  dia.  
View looking into box lid  
(CKG072)

Fig. 1 Drilling details for the lid of the box on which all the components are mounted.

## ★ components list

### Resistors

R1 82Ω 3W wirewound	R5 1kΩ ½W
R2 1kΩ ½W	R6 8-2kΩ ½W
R3 1kΩ ½W	R7 39Ω 5W wirewound
R4 82Ω 3W wirewound	R8 2.2 MΩ ½W

### Capacitors

C1 0.47μF 600V	C2 0.22μF 250V
----------------	----------------

### Semiconductors

Tr1, Tr2 2N3055 Positive earth system  
2N3614 Negative earth system  
D1, 2, 4, 5 1N4001 D3 4 x BY100 or 1N4006  
ZD1, ZD2 BZY94C30 SCR TAG1/500 or TAG1/600  
(see text)  
Semiconductors available from Jermyn Industries,  
Sevenoaks, Kent

### Transformer

T1 Type P1/6 Available from Magtor Ltd., 68 Dale  
Street, Manchester (£1.50 inc. p/p.)

### Miscellaneous

Aluminium box and lid (Type AB7), see text. Tag  
strips .01 in. spacing, 8 way with earthing tag each  
end, 2 way with one earth tag, 3 way with centre  
earth tag (R.S. Components Ltd.). 4 right angle  
male push-on connectors (Lucar type).

earth type except for the transistor types and the polarity of the associated diodes as has been explained in the original article. The actual connections from the unit to the coil and contact breaker remain the same in both models as the polarity of the pulse fed to the ignition coil is identical.

When wiring in the unit see that the pulse feed from the discharge capacitor is connected to that terminal on the coil marked positive, as this terminal should correspond to the single end of the primary winding whilst the terminal marked negative should be the end of the primary winding which is common with the earthy end of the secondary on a correctly marked coil.

## CONSTRUCTION

This unit has been designed to be as compact as possible without undue cramping of the specified components, but there is little room to spare; high voltage points are adequately spaced and their positions relative to other components considered so the constructor is urged to follow the layout as closely as possible.

Having made a box and lid to the required dimensions, Fig. 1 or purchased a ready made one the lid is marked out to the dimensions given in Fig. 1 and all the holes drilled. Extra holes may be required in the box and lid if extra self tapping screws will be needed to hold the unit together when the box is mounted in the car owing to the possible inaccessibility of the one screw top and bottom provided on the ready made box.


At this stage it is prudent to ascertain the mounting position of the unit and the method to be adopted. Pan head self-tapping screws straight through the back of the box, or alternatively small pieces of aluminium angle may be affixed to the sides of the box to secure fixing points. Whichever

## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £10.50. P. & P. 25p.

## DE LUXE STEREO AMPLIFIER

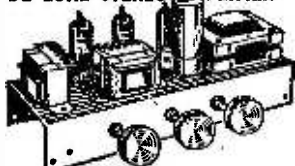

A.C. mains 200-240 v. A single heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up: -2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono). Into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8.99 P.&P. 45p.

## SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!

All Transistor F.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. FM RF Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional APC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/4" h x 1 1/4" w x 2 1/4" d. For 6V D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.25 post free. Connection details supplied.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/16 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1/4 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half watt at 1 amp. or 10-10-10, 20-20-20, 30-30-30v. at 2 amps full wave. Size 3 1/2 in. long x 3 1/2 in. wide x 3 in. deep. Price £1.75 P. & P. 50p.

MAIDS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 75p. P. & P. 13p. Pri 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri 200/240v. Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p.

4 AMP BATTERY CHARGER TRANSFORMER. Brand new. For 6 or 12v. 240v. Primary. Secondary volts rms off load 10v and 16-5v. Overall size approx. 2 1/2" x 2 1/2" x 3". Weight 2lbs. Limited number at £1.55. P. & P. 35p.

## HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

4-SPEED RECORD PLAYER BARGAINS. Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C128 4-SPEED AUTOCHANGER. With latest mono compatible cartridge. £6.97 Carr. 50p. With stereo cartridge £7.97 Carr. 50p. LATEST GARRARD MODELS. S.A.E. for latest Prices!

## PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1925, 2000, 2025, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). PRICE £25.50. P. & P. 60p.

LATEST ACOS GP91/150 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 8p.

SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for LP/EP/78. £1.63 P. & P. 10p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 10p.

## QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2 in. wide x 3 in. deep x 6 in. high. Ready built and tested. PRICE £27.75 P. & P. 40p.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £24.95 P. & P. 50p.

## DELUXE QUALITY PORTABLE R/P CABINET MK II

Uncut motor board size 14 1/2 x 12 in. clearance 2 in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8 in. PRICE £24.75. P. & P. 50p.

## SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosures with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8.40 Carr. 65p

Cabinet Available Separately £4.50 Carr. 60p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £6.50 Carr. 65p

## LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05. P. & P. 15p. 7 x 4in. 3 ohm £1.15. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet £2.10 (15 ohm) £2.25. P. & P. 30p. E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13 x 8in. twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobase magnet assembly £6.25. (guitar models £5.50. £6.50. £8.50. P. & P. 30p. E.M.I. 8in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 95p each. P. & P. 13p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm £2.20. P. & P. 30p. 35 ohm SPEAKERS 3in. only 63p. P. & P. 13p.

## "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS ap. 54 in. wide. Usually £1.75 yd. our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 1/4 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2.95. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES.


OUR PRICE £1.05. P. & P. 8p

## GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 13p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.
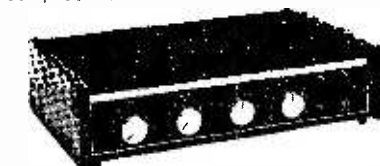
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1 amp. Overall Size 12" w x 8" d x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES  
AMPLIFIER KIT . . . £10.50 P. & P. 15p  
POWER PACK KIT . . . £3.00 P. & P. 30p  
CABINET . . . £3.00 P. & P. 30p

(Post Free if all units purchased at same time Full after sales service)

Also available ready built and tested £20.50. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.



## 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records, A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4" d x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.


## HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

FEW ONLY. £2.75 P. & P. BARGAIN PRICE 35p
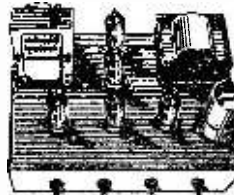
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. ONLY £7.97 P. & P. 55p.



(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



**Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.**

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

**Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!**

... and what’s more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it’s as fascinating as a hobby**

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

## New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.’s full range of courses.



# FREE

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

## POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF  
Please send book and full information — FREE and without obligation.



NAME \_\_\_\_\_ AGE \_\_\_\_\_

BLOCK CAPITALS PLEASE

ADDRESS \_\_\_\_\_

Subj. of interest \_\_\_\_\_

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Accredited by the C.A.C.C.

## GEIGER COUNTERS

(FOR MAINS OR PORTABLE BATTERY USE)

Latest Home Office release and probably the last, of this well known Contamination Meter No. 1, this very useful instrument is used for the measurement of Radio-Activity. Indicated on an Internal Meter scaled 0/1 to 10 mill Rontgens/Hour, a socket is also provided for additional sound Monitoring on Headphones. This instrument is housed in a Strong light Alloy Case, placed in a carrying Haversack with shoulder strap. Containing Cable and Hand held Probe, Instruction Card, plus the latest plug in Vibrator Power Unit, which uses current small Transistor Radio Batteries (4 Mallory Long Life RM12 or 4 EverReady H.P.7 or equivalent makes).

For Mobile use anywhere. (Cost Gov. approx. £70 each). Supplied Brand New in Carton only £55.00 carr. 50p. An additional plug in Power Unit for Laboratory use, operating from 100-120 volts or 200-250 volts A.C. Mains is available. Supplied Brand New in Carton at only £25.00 post 25p. Headphones (not necessary) if required £1.50. A few Geiger Counters as above but not boxed in cardboard cartons, available at only £4.50.



### Meter Dose Rate Portable Trainer NO. 1

This was used to train in the use of Geiger Counters. A very compact self-contained Geiger Counter, being very sensitive. Radiation indicated on Internal Meter scaled 0 to 3 Rontgens /Hour x 10-4. Unit contained in Waterproof Alloy Case, which is hand held. Uses Internal Batteries (4 EverReady B105 and 1 U2 or equivalent makes) Not Supplied. These have had little or practically no use, supplied as New in Cartons. Few only £35.00 carr. 50p.

Due to Warehouse clearance, we have for disposal few only Trans-Receivers No. 62 MX2. Made by Pye for the Navy and Army. Using a total of 11 Valves, 1 RF and 2 I.F. stages, A.V.C., B.F.O. covering 1.5 mc/s to 10 mc/s (approx 200 to 30 metres) in two switched Bands. Can be used on RT or CW M.O. or Crystal. A very good Internal ATU made of a rotating Silver wire coil. Tuneable over the complete range, suitable for Aerials 4ft to 100ft. Internal P.U. for 12 volt D.C. A meter is fitted for checking voltages A.V.C. etc. Housed in a Metal Waterproof Case approx size 18" x 10 1/2" x 12 1/2". Supplied in very good condition with Headphones & Mike two spare Valves, circuit boxed, only at £12.50. Carr. £1. Air Tested £1 extra. A few Grade 2 sets £9.50. Carr. £1. Air Tested £1 extra. CRYSTAL CALIBRATOR No. 10. Range 500 Kc/s to 10 mc/s, up to 30 mc/s on Harmonics. Size 7" x 7 1/4" x 4". Power 300 volts RT, 12 volts LT. The Calibrator can plug into a Power Socket on the 62 Trans-Receiver which it was normally used with. Supplied in Good used condition with circuit £2.50. Post 50p or Brand New in Carton with operating Manual & Circuit Connectors to set £5.00. Post 50p.

**JOHNS RADIO** Dept. D, 424 Bradford Road, Batley, Yorks. Phone Morley 69696

## SURPLUS

**THOUSANDS OF VARIETIES IN ELECTRONIC COMPONENTS AT THROWAWAY PRICES. SAVE ££££££ HERE**

### EEC PRODUCT AC/DC CONVERTER

Input 240 Volts. Output 3V, 4.5V, 6V, 7.5V, 9V and 12V DC  
Current 500 MA Price £4.47 Postage Paid

### EEC CAR ADAPTOR

Input 12 Volts  
Output 6V, 7.5V, 9V

Price £5.10 Postage Paid

MD 800 Sound Headphones with volume Control £3.90

Garrard 2025 with Plinth Cover & Cartridge £12.30

Shiramatic Car Radio MW/LW	Manual	£8.50
	Twinspeaker	£8.95
	Pushbutton	£10.45

Plinth & Cover Suitable for Garrard SP25 £3.25

Headphones DH025 £2.25

Siran Battery Chargers 6V & 12V £2.87

Top Quality Audio Cassetts	C 60	—	35p
	C 90	—	47p
	C120	—	60p

Please Send 25p for Postage & Packing

## EDGWARE

### ELECTRONIC CENTRE

194 EDGWARE ROAD, LONDON, W2

Phone: 723-1465



way is used, remember that any metal protrusions in the shape of screw or rivet heads must be shallow and positioned only in close proximity to earthed parts of the circuit, and also that the unit relies on its mounting for earth return operation which keeps the number of leads to a minimum and the reversionary facility less confusing.

The three heat sink fins, having been made to the sizes given in Fig. 2, are then mounted by means of  $\frac{3}{8}$ "  $\times$  4BA screws as is also the transformer (five leads toward transistors), the two-way tag strip, the three-way centre earth leg tag strip and the discharge capacitor clip which is made from a piece of thin scrap aluminium. The eight-way tag strip is not mounted at this stage as it is more easily fitted after the tag panel.

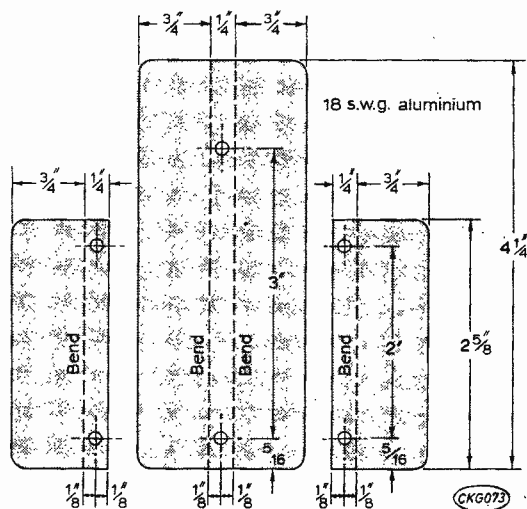


Fig. 2. These three heat sink fins are fitted to the lid of the box.

When mounting the heat sink fins and the transformer it is a sound idea to give those sides which come in contact with the chassis a smear of silicone grease to ensure thermal conductivity. Likewise the transistors when they are mounted.

To obtain a professional finish to the unit now is the time to give it a few coats of matt black paint after masking the transistor mounting positions with two small pieces of masking tape or something similar cut to the required shape using the actual transistors as templates. One of the popular aerosols is ideal for this job and the results are well worth the small effort involved, not only as regards the final appearance of the unit but this process effectively assists the even dissipation of heat besides preventing corrosion.

The paxolin strips and washers are next prepared as in Fig. 3 and assembled to form the tag panel in the manner indicated not forgetting to include a soldering tag under the nuts of connectors marked coil +, -, and CB and the earth tag of the eight-way tag strip under the nut of the remaining connector marked IG/SW., the nut on that side of the transformer being removed to take the other earth tag of the eight-way tag strip which should have the adjacent tag completely removed as reference to Fig. 4 makes clear.

The two transistors of the type required for the particular polarity unit being constructed should

next be mounted (with silicone grease on mating surfaces) and also the thyristor heat sink by soldering the doubled over tag in the position indicated in Fig. 4. This heat sink may either be made from thin springy brass or copper 0.020" thick to the dimensions given in Fig. 5 or it can be formed from a commercial heat sink as supplied for OC81 type transistors as was done in the prototype. It serves as a convenient anchorage for the s.c.r. as well as providing a safety factor which, although not absolutely necessary, is an added precaution.

Wiring can now be begun and is largely achieved with the wire ends of the components. The long wire from the discharge capacitor should be well insulated with plastic sleeving and dressed as in Fig. 4. Careful checks especially on the polarity of the various diodes and the use of a heat sink is strongly recommended whilst soldering operations are in progress.

With regard to the components around the transistors, which were soldered into circuit so as to preclude any intermittent contacts which might occur with spring contacts on transistor holders (imagine an ignition fault impairing performance whilst overtaking), it may be found advantageous to solder the components together one by one so that the final connection to the appropriate transistor pin consists of only one wire end which simplifies construction, replacement of transistors should this ever be necessary, or if the unit is ever altered to the opposite polarity working.

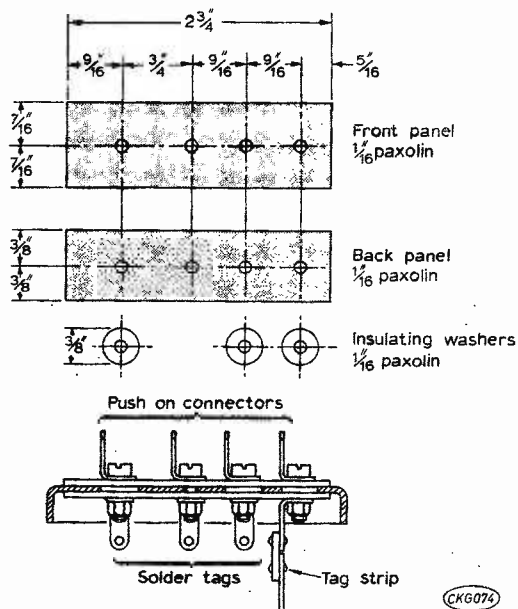


Fig. 3. Assembly details of tag panel.

The next few paragraphs may be ignored by the competent constructor, but are included for those who prefer to work from a step by step outline.

**NOTE:** The following instructions refer to a unit with a **positive** earthed vehicle. They also apply to the construction of a unit for negative earth use if the reference to polarities of D1, D2, D4, ZD1, ZD2 are reversed, D5 is not required, and of course TR1 and TR2 are of the type specified in the components list. The gate and cathode connections are also reversed for the negative earth unit.

Start by terminating the two black wires of the transformer to the third and fourth tag of the eight-way tag strip (counting earth tags and removed tag from transformer towards IG/SW connector) followed by blue transformer lead and one side of R1 to right tag, and yellow transformer lead and one side of R4 to left tag of three-way strip on transistor side of transformer.

Connect one side of R2, R3 and positive side of ZD1, ZD2 to the central earth tag of the same three-way strip; join free end of R2 to free end of R1 fairly close to R1 body in a T form thus leaving the wire from R1 full length, then using this tee technique again join the positive end of D1 to the R1 wire, the end of this R1 wire is now formed into a small loop to fit on the Base pin of Tr1. By using this method there is only one connection to be made to Tr1 base pin with the advantages already mentioned.

Repeat this process with R3, R4, and D2 to Base pin of Tr2. Connect the free end of D1 (negative) to the free end of ZD1 (negative) and also green lead of T1 using same T method, again forming small loop on the ultimate wire of these junctions for connection to emitter pin of Tr1.

Repeat with D2, ZD2, red transformer lead and emitter pin of Tr2. The four BY100 which form bridge rectifier D3 are next wired in position, Fig. 4, by joining two negative wires of two BY100's together and to the earth tag on strip held by T1 bolt, one positive going to tag 3 where black T1

#### Colour code

B-Blue  
G-Green  
R-Red  
W-White  
Y-Yellow

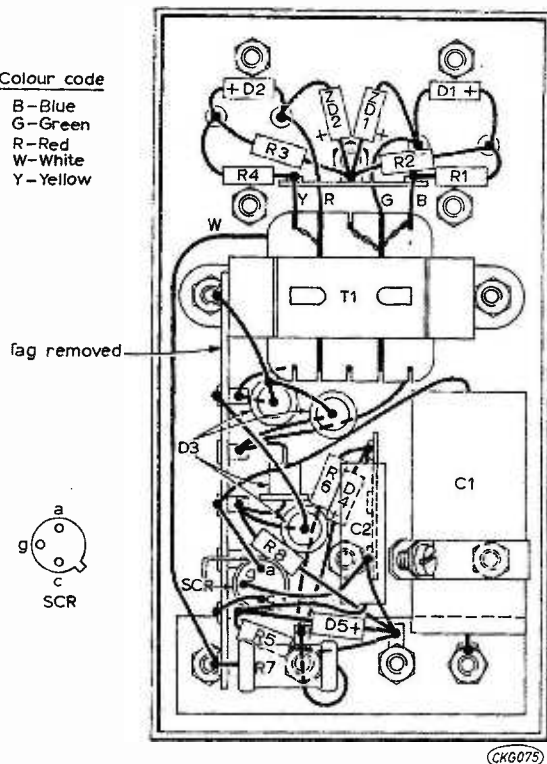


Fig. 4. Complete wiring diagram for a positive earth unit which may be compared with the photograph, below left.

lead joins. The other positive goes to tag 4 where the other black T1 lead has been soldered and from this point is connected the negative of the third BY100. Its positive wire goes to tag 5 as also does the positive of the fourth BY100 together with one side of R8. The negative of the fourth BY100 is returned to tag 3, upper half of tag. Use the lower half of tags for all previous connections except the earth one.


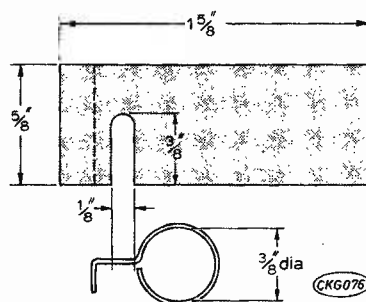


Fig. 5. Heat sink for the SCR made from springy brass or copper.

The two-way tag strip should now be mounted by means of the central heat sink fin fixing bolt and a short piece of wire soldered from the unit tag marked Coil negative to the earth tag on the two-way strip, in the form of a bus bar. Several earth joints can then be comfortably accommodated the first of which is the free end of R8.

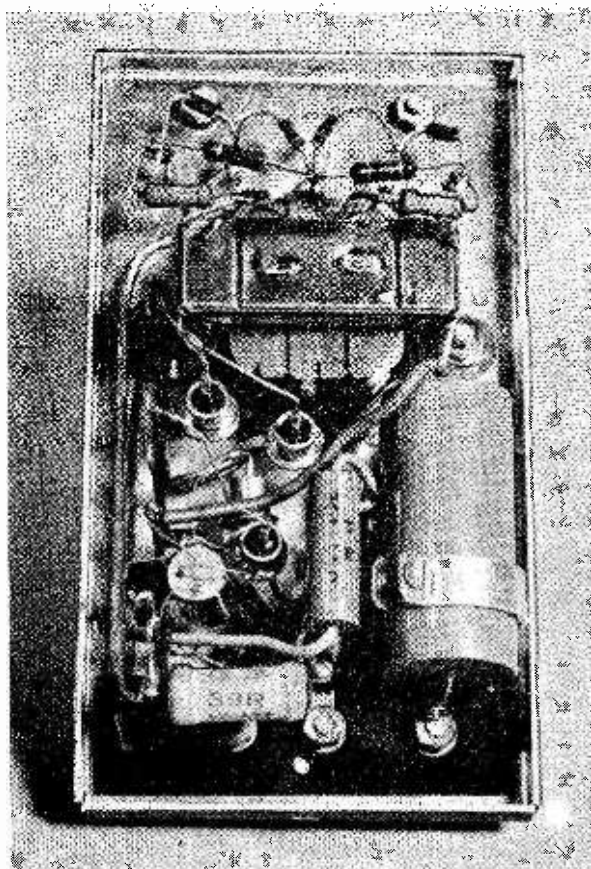To the lower half of tag 7 solder one end of R5 and the negative end of D5, the other end of R5 and the positive end of D5 are then earthed at the bus bar.



## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. \$2.25 plus 25p post and ins.

## MULTI-SPEED MOTOR

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000; 12,000 and 15,500 r.p.m. shaft is  $\frac{1}{8}$  in. dia. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor, size approx. 2in dia. x 5in long. Price 88p plus 25p postage and insurance.



## MAINS MOTOR

Precision made — as used in record decks and tape recorders — ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



## TELEPHONE HAND SET

Ex-G.P.O. Perfect order. 50p each plus 20p p. & p.



## 12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50V smoothing. Price £1.50, plus 20p post & packing.

## NEW LIGHT DIMMER

This uses the latest technique from America, a self triggering device known as the thermo tab and has enabled us to produce a really reliable dimmer at a remarkably low price—namely £2.50 each or 10 for £22.50.



## ROCKER SWITCHES

3 new types to offer this month, all snap in fixing into oblong holes. Type 1 S.P. on/off 10 amp 250V. Size approx. 1 1/2 x 3 1/2. Made by Arrow electric. (93 series). Price 12p each. 10 for £1.08.

Type 2 D.P. on/off 10 amp 250V with neon indicator in the lever. Again Arrow 93 series. Price 25p each or 10 for £2.25.

Type 3 Double pole change over spring return, made by the French Eussenberg Company. Size approx. 1 1/2 x 4 1/2. Price 15p each. 10 for £1.35.

## CARD OPERATED SAFE

All electronic parts to make this £4.50.

## AMPLIFIER CASE

Teak veneer on 3/4 ply, modern appearance and design. Size—front 13" x 4 1/2" deep x 8 1/2". Limited quantity £1.25 each plus 25p post and insurance.

## MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

## PRESSURE SWITCH

Made by Bailey and Maceay Ltd., Type 108R. Adjustable up to 15lb. per square inch. (Instructions included). Set to trip at 8lb. per square inch. Changeover switch rated at 2amp 250V A.C. with re-set button. Electrical connections in box with conduit entry. Price £1.50 each plus 20p post and insurance.

## 20 WATT INVERTER

Smart and Brown—For van lighting or camping etc. Will light a 2ft. 20 watt standard fluorescent tube from a 12V car battery, current approx. 2A. Very well made unit using the cast chassis. Size 11 1/2" x 2" x 1 1/2". Price £5.50 complete with lamp holders and test clips.

## FLEX CABLE SNIP

3 core heavy circular T.R.S. waterproof flex, ideal for running down the garden to pool or shed. 1.5mm cores (5 amp) 100 yard coils £4.25 plus carriage 75p up to 200 miles. £1—300 miles. £1.50—500 miles.



## DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master intercom. Simply plugs together. Originally sold at £10. Special snip price £3.50 plus 20p postage.

## AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and insurance.




## NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic pushrod suitable for operating, 5p each, 45p doz.


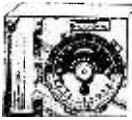
## NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN.3. Price 98p each. 10 for £9.



## 24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 20p. Additional time contacts 50p pair.

## TREASURE TRACER MARK II

Complete Kit (except wooden battens) to make the metal detector similar to the circuit in Practical Wireless August issue. £2.95 plus 20p post and insurance.



## MULLARD IF MODULE

This is a fully screened intermediate frequency module for amplification and detection of f.m. signals at 10.7MHz and a.m. signals at 470kHz. The first stage is used as an i.f. amplifier for f.m. and a self oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 75p each. 10 for £6.75. 100 for £62.50p. With connection dig.



## COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in wide £1.00 plus 33p post and insurance with cassette. 3/4in wide £1.00 plus 30p post and insurance with cassette. 5/8in wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p, 1in 75p each plus 20p post and insurance.

## ERGOTROL UNITS

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains.

Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods.

The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control.


4 models are available—all are brand new in makers cases:

Model 2410 for up to 5 amps £17.50

Model 2411 for up to 10 amps £27.50

Model 2415 for up to 80 amps £95.00

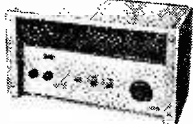
Note: 2415 is a floor mounting 3 phase unit.



## THIS MONTH'S SNIP
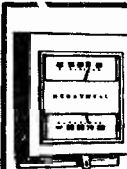
### HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40°-90°F (5-26°C). This is a precision instrument with a differential which can be adjusted to better than 1-5°F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bi-metal element and adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows thermometer above and switch setting scale below—size approx. 3 1/2" x 3 1/2" x 1 1/4" deep—can be mounted on conduit box or directly on wall. Price £1.25 each or ten for £11.25.



## CENTRIFUGAL FAN

Mains operated, turbo-blower type. Pressed steel Housing contains motor and aluminium impeller. Motor is 1/10th hp giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2" wide by 12 1/2" dia. Outlet into trunking 10 1/2" x 4 1/2". £4.95 - £1.



## THE FULL-FI STEREO SIX

### THE AMPLIFIER

#### SENSATION OF THE YEAR



You will be amazed at the fullness of reproduction and at the added quality your records or tuner will reproduce. Built into metal chassis ready for mounting on plinth this amplifier uses an integrated solid state circuit with an output power of 6W R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. UNREPEATABLE PRICE is £6.50 plus 20p post and insurance. Simulated Teak cabinet ready for mounting amplifier £1.50 (posted free when ordered with chassis).

### P.E. GEMINI

Dual purpose twin 30 watt stereo amplifier for exceptional performance. Complete kit of parts less case £45 or reprint of data & parts list 55p.



## MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 500mW into 8 ohms speakers. Input suitable for crystal mic. or pick-up 9V battery operated. Size 2in long x 1 1/2in wide x 1 1/2in high.


SPECIAL SNIP PRICE 80p each. 10 for £5.40. 100 for £50.

## CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical Wireless, June). Price £5.95 plus 20p post. When ordering please state whether for positive or negative systems. De-lux model including printed circuit board etc. £6.95.
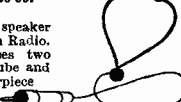
## RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.



## ELECTRONIC IGNITION

20p post. When ordering please state whether for positive or negative systems. De-lux model including printed circuit board etc. £6.95.

## QUICK CUPPA

Mini Immersion Heater. 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, 12v. car model also available same price. Jug heater £1.50 (mains only)



## MAINS OPERATED SOLENOIDS



Model T12—small but powerful. 1 1/2" pull—approx. size 1 1/2" x 1 1/2" x 1 1/2". Price 60p. Model 400/1 1/2" pull. Size 2 1/2" x 2 1/2" x 7 1/2".

Model TT10 1 1/2" pull. Size 3 x 2 1/2 x 2 1/2" £1.80 plus 20p post and ins.

## MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V. A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction.



Single pole 25p each 10 for £2.25 Double pole 35p each 10 for £3.15



## DRILL CONTROLLER

### NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p post & p.

## SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6BA screws. Size approx. 1in x 2in rated 250V 1amp. 6p each. 10 for 54p, 100 for £5.10, 500 for £24. Ditto as above but for printed circuit. 5p each 10 for 45p, 100 for £4.25. Sub Miniature Slide Switch. DPDT 19mm (1in approx.) between fixing centres. 12p. each or 10 for £1.08.




## LIGHT CELL

Almost zero resistant in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in dia. by 1/2in thick. Rated at 500 MW. wire ended. 43p with circuit. Also ORP12 light cell 45p.


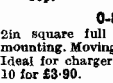
## TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—6 sections. extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 88p. KNUCKLED MODEL FOR F.M. 50p.



## 0-8 AMMETER

2in square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 43p each. 10 for £3.90.



## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchen, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact. 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2 plus 33p post and ins.



## DIGITAL CLOCK

As featured this issue, send for parts list.

## MICRO SWITCH

5A changeover contacts. 8p each. £1 doz. 15 amp Model 10p each or £1.05 doz.



## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 2 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole. 12 way. All at 20p each £1.80 for ten, your assortment.



## REED SWITCHES


Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types.


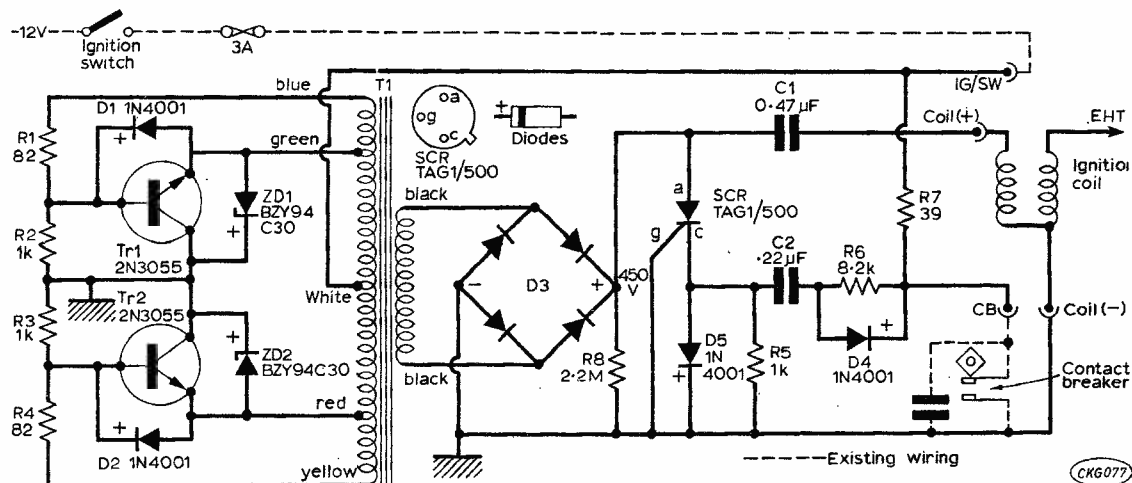
# J. BULL (ELECTRICAL) LTD.

(Dept. P.W.), 7 Park Street, Croydon CRO 1YD

Callers to: 102/3 Tamworth Road. Croydon.



Only minor amendments have been made to the original circuit. This one is for **POSITIVE** earth vehicles.

One end of R6, the negative end of D4, and one end of C2 are soldered to the free tag on the two-way strip; the free end of R6 and the positive end of D4 are then connected to the unit tag marked CB as is also one side of R7, the other side of R7 and the white T1 lead solder to the earth tag 8 which is unit tag marked IG/SW.

The free end of C2 connects to lower half of tag 7 on eight-way strip.

Capacitor C1 fixing clamp should now be fixed in position and C1 secured by means of the clamping bolt—not forgetting to use a small piece of aluminium as a crush guard. One end of C1 connects to unit tag marked coil positive and the other end covered with good quality plastic sleeving and dressed as in Fig. 4 and connected to tag 5 on eight-way strip.

The thyristor heat sink is then fixed by bending both upper and lower portions of tag 6 (on eight-way strip) in such a manner as to form an almost complete wrap around the strip, the slot in the heat sink is then pushed down centrally over this wrap and soldered in position as shown in Fig. 4.

The last component to be fitted is the thyristor


SCR and reference to Fig. 4, clearly shows how this is connected, namely anode to tag 5 cathode to tag 7 on eight-way strip whilst the gate is connected to the earth bus bar adjacent to unit tag marked Coil negative.

The TAG 1/500 has proved eminently suitable for use with most ignition coils as fitted to British cars and far superior to those s.c.r.'s obtained from other sources, in freedom from breakdown, but some foreign-made ignition coils require the TAG 1/600 to be used owing to the primary inductance generating excessive oscillatory peaks. However, this subject is too extensive to go into in this article and the foregoing remarks can be taken as a reliable guide.
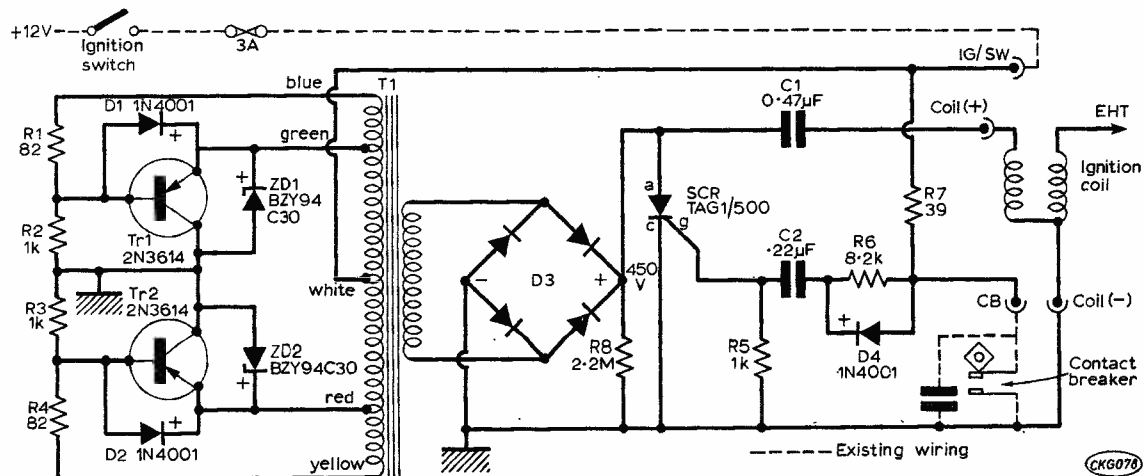
## TESTING

When the unit is complete it should be tested by applying the car battery to connectors IG/SW and -ve (IG/SW to live feed and -ve to that pole of the battery which is earthed on the particular car and unit) when a whistle should be heard indicating that the oscillator section is working. The voltage

This circuit is for **NEGATIVE** earth vehicles. Certain diode polarities are reversed as well as the gate and cathode connections to the SCR. Diode D5 is omitted.





across the bridge rectifier is then measured and should be approximately 450V, this reading may increase to approximately 480V when the connections to the ignition coil are made but it depends on coil characteristics.

Assuming these initial tests to be satisfactory the unit is then fixed to the car in a suitable place, all connections checked, and the unit is ready for use.

## CONNECTING UP

The connections of the ignition unit to the vehicle are quite simple but are given here in full for guidance of any constructor who may be doubtful.

After mounting the unit (preferably on side of wing or bulkhead so as to keep leads from the unit to the Ignition coil as short as practicable) remove the existing ignition switch to ignition coil wire—that is the thin lead which does *not* go to the contact breaker—and connect to unit tag marked IG/SW (see notes in text about ballast resistor if cold start coil is fitted).

Remove the thin lead from the ignition coil which connects to the contact breaker, and connect this lead to unit tag marked 'CB'.

Two short extra leads are now required and are connected one lead from unit tag marked 'coil negative' to ignition coil terminal marked 'negative,' the other lead goes from unit tag marked 'coil positive' to ignition coil terminal marked 'positive.' These connections are identical for both negative and positive earthed vehicles.

For coils marked SW and CB, this corresponds to positive and negative respectively—see circuit diagram.

Should the reversionary facility be required—due to component fault, although this should not occur if the recommended components are used—simply remove the two short leads connecting the unit tags marked 'coil positive' and 'negative' to the ignition coil positive and negative.

Remove the lead from the unit tag marked CB and connect it to the ignition coil terminal which is the same polarity as that terminal of the battery which is earthed to the chassis.

The remaining lead which is left on the unit tag marked IG/SW is removed and connected to the remaining free terminal on the ignition coil.

## PLUGS

It is recommended that the sparking plug gaps be reset to around 0.050" instead of the usual gap which is about 0.025", as the higher resistance load thus presented enables the greater output available from the electronic ignition unit to be used to the fullest advantage.

The prototype of this unit is in use on the writer's car and has proved a worthwhile accessory.

**NEXT MONTH** Part 2 reviews the various types of ignition coil available today and how they can be used with the PW Electronic Ignition System plus information on using your tachometer with this unit. Finally, a discussion of the various advantages of the PW unit as obtained in actual road tests.



## Practical Wireless Designer's Trophy

**1972**

To encourage new authors, entries for the 1972 Trophy will be restricted to readers who have not previously had an article published in PW. This leaves the field wide open for those wanting to try their hand at writing technical constructional articles. Contestants will not be in competition with well-known authors, only with other newcomers, so the cup can only be won by a new writer. **It Could Be You.**

## TURN YOUR CONSTRUCTIONAL PROJECT INTO CASH—AND MAYBE WIN THE CUP! RULES

1. The winning entry will be chosen by a panel of judges from among articles published in issues of PW dated September 1972 to August 1973 inclusive. The Editor's decision on all matters arising will be final.
2. The winner of the competition will receive and retain outright the PW Designer's Trophy 1972. Other prizes will be awarded to the best runners-up. Articles will be paid for shortly after publication.
3. The competition is open only to authors who have not previously had any work published in PW.
4. Articles submitted for the competition should conform to the general style of material published in PW and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
5. Articles should, preferably, be typed using double spacing, leaving wide margins, on one side only of each sheet. Circuit diagrams and any other drawings must be separate and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Components list must also be separate and laid out to the standard PW format.
6. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Photographs may be identified by sticking a label on the reverse instead of writing on the back of the photograph itself.
7. Components used in the design must be readily available from retail sources.
8. Articles should be sent to the Editor, Practical Wireless, Old Fleetway House, Farringdon Street, London, E.C.4. Authors will be advised as soon as possible of the acceptance or rejection of their articles. Equipment, the subject of an article, must not be sent to the Editor until advised to do so.
9. Employees and staff of PW are not eligible for entry to this competition.

**SUBMIT YOUR ARTICLES NOW**

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.**

**M**AGAZINES such as *Practical Wireless* require a continual supply of new ideas and new articles in order to attract readers; this is not always easy as new and original projects are rare. There is one field however which seems to have been almost ignored—that of burglar and security alarms. A few have been published but I can only recall three in the past ten years.

This is all the more extraordinary when one considers how useful (and how simple) a burglar alarm can be. Admittedly the electronics side is only the tip of the iceberg as the hard part is the fitting and wiring of the alarm circuit rather than the construction of the alarm itself. This can present problems but some guides will be given.

The circuit of the alarm itself is shown in Fig. 1. This is a simple, but reliable audio oscillator whose output is fed to a loudspeaker. The alarm circuit wire is shown as a shorting link between the base and emitter of Tr1; this cuts off the transistor. This link will, of course, be very long; it may be up to 100 yards but even so its resistance will not be more than a few ohms assuming that reasonable quality wire is used. This will have virtually no effect on the circuit and may, for our purposes, be considered as a dead short.

When this link is broken Tr1 will be biased by R1 and when conducting this will in turn provide bias for Tr2 causing a considerable current to be passed through the primary of the transistor output transformer T1 and so to the speaker. However the inclusion of C1 causes this current to appear as a series of pulses and this sounds like an audio note in the speaker.

When the alarm circuit is closed the only current passing will be that through R1 plus the tiny leakage currents through the transistors. This will be below 20µA in total and this sort of current can be taken from a battery almost indefinitely; it will decay of old age before running down.

Note that the output of the speaker, while being more than sufficient to scare off a burglar, is not all that high and so an efficient speaker should be used. This excludes the use of miniature types and the larger the diameter, the greater will be the output.

The construction of this circuit should present few problems but a suggested layout on a small tagboard is shown in Fig. 2.

The alarm circuit comprises a single wire running between the doors and windows to be protected. The contacts can take many forms. Microswitches can be used, most of these have changeover contacts and so can be arranged to break the circuit when a window or door is opened. A springy metal can also be used to make the contacts. All of the switches must be in series of course so that if any one of them is opened the alarm will sound.

## No. 37 BURGLAR ALARM

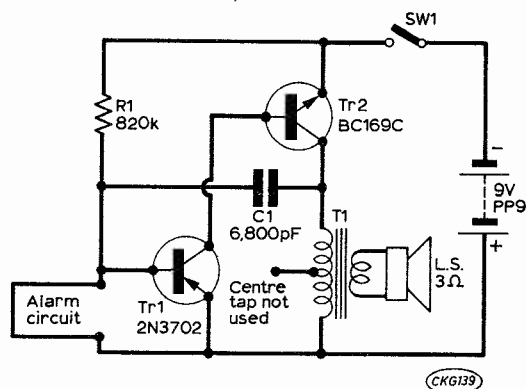


Fig. 1: The circuit of the Take 20 Burglar Alarm.

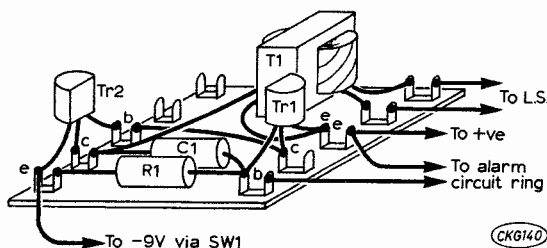


Fig. 2: A suggested component layout on tagboard.

R1	820kΩ, ½W, 5%	1p
C1	6,800pF, polystyrene	4p
Tr1	2N3702	13p
Tr2	BC169C	11p
T1	Transistor output transformer (Eagle Type LT700 or similar)	20p
LS	3Ω loudspeaker (ex-TV type)	15p
SW1	On-off switch	5p
	Tagboard	11p
		80p

Prices are those recently advertised in *Practical Wireless* and may have changed. No allowance is made for minimum order costs or for postage and packing and these should be checked carefully before ordering.

In addition to acting as a burglar alarm, this arrangement will also provide a rapid check to ensure that all the necessary windows and doors are shut. It is also a fail-safe circuit; any faults in the circuit will cause the alarm to sound.

Although battery operation is perfectly satisfactory if the battery is replaced regularly, it is far better to operate this circuit from a mains power supply. In the long run this will be cheaper and more reliable.



**IN NEXT MONTH'S**

**PRACTICAL  
WIRELESS**

# AUDIO Test TRIO



**DON'T  
MISS  
YOUR  
COPY!**

\*  
PLUS  
MANY  
OTHER  
CONSTRUCTIONAL  
ARTICLES  
AND  
ALL THE  
REGULAR  
FEATURES


Either of these audio signal generators plus the calibrated switched attenuator will enable the constructor to carry out accurate performance tests and measurements on audio equipment. Output amplitude is stabilised using an FET rather than the usual power-consuming thermistor, permitting operation with self-contained batteries. The series starts with a full description of the more sophisticated, full-facility, sine square-wave version.

## DX'ERS AUDIO AID



This unit will greatly improve the intelligibility of weak DX signals—by filtering the a.f. rather than working at r.f. It incorporates a highly efficient adjustable noise limiter together with an audio filter which will virtually eliminate heterodynes, whatever the strength.

## 2 METRE F.E.T. CONVERTER

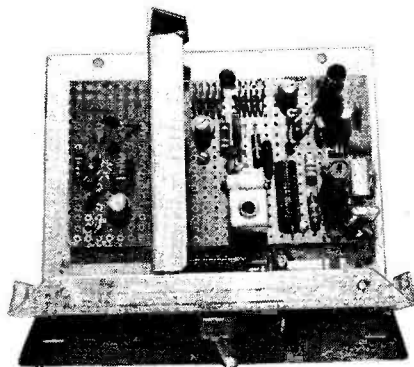


This simple 4-transistor crystal controlled converter permits reception of the entire 2 metre amateur band (144-146MHz) on any receiver capable of covering from 4 to 6MHz. A suitable choice of crystal frequency allows direct frequency read-out on 2 metres from the calibration on the main receiver.

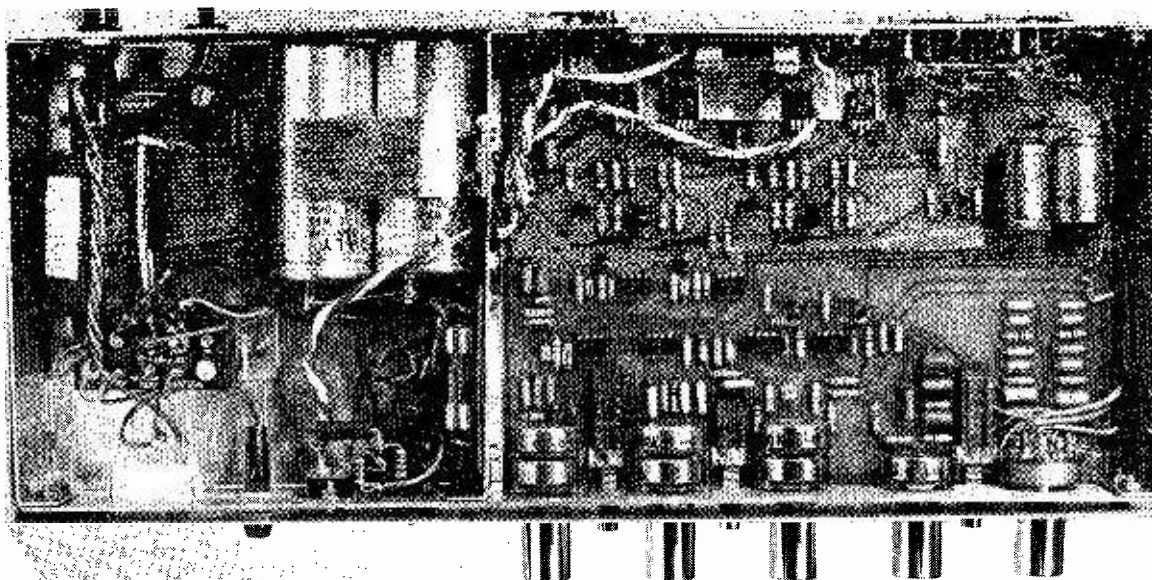**ALL IN THE JULY ISSUE  
ON SALE 2nd JUNE**








The complete Texan amplifier. The power supply section is to the left of the dividing screen.

approximately  $1k\Omega$ . However it seems a pity to lose the rumble filter especially as ceramic cartridges are more likely to be used with the sort of turntables which require a rumble filter most.

Therefore, the best approach is to use a low impedance loading circuit on the ceramic cartridge such as shown in Fig. 15. This will give a characteristic which approximates to the velocity characteristic of a magnetic cartridge and the output level will also be similar so that the amplifier can be used without modification to its feedback components. This circuit allows some variation of the shunt capacitor to improve the linearity of the response and some manufacturers will quote the circuit values which give the best "magnetic" characteristic from their particular cartridge. If this approach is adopted the constructor can wire the attenuator quite neatly across the pins of the DIN pickup socket.
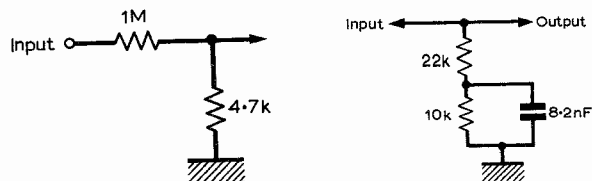
### Input Impedance

In the specification the input impedance of the amplifier is quoted as  $47k\Omega$  at  $1kHz$ . This nominal figure is modified when the rumble filter is inserted in circuit partly due to the shunting effect of  $R1$  and partly to the series reactance of  $C1$  and  $C2$ . This will not normally have any effect on a magnetic pickup cartridge but it may have some loading effect if a ceramic/magnetic conversion network is used so the variation of input impedance is plotted in Fig. 16.



### Auxiliary

The Texan was originally designed to give an equalized output directly from a tape head without external amplifiers. For this reason the circuit shows  $R8$ ,  $R9$  and  $C9$  and the printed circuit board is laid out to take these components. However, the present

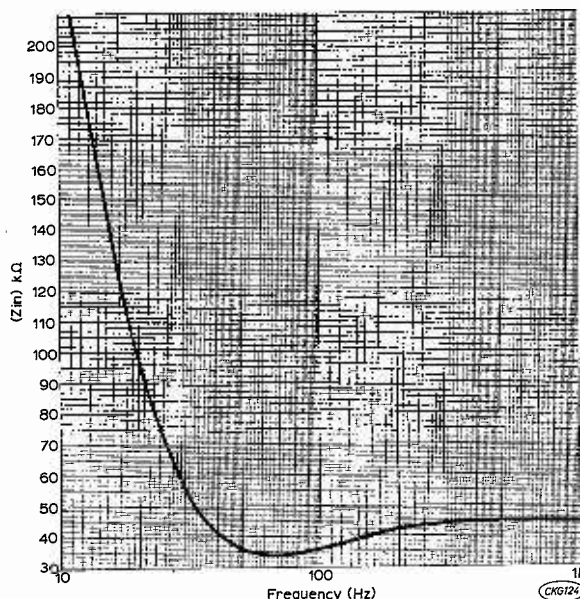


Fig. 14: (far left) Equalisation circuitry for high output crystal/ceramic pickup cartridges.

Fig. 15: (left) Equalisation circuitry for low output crystal/ceramic cartridges.

Fig. 16: (above) Variation of input impedance with frequency (rumble filter in).

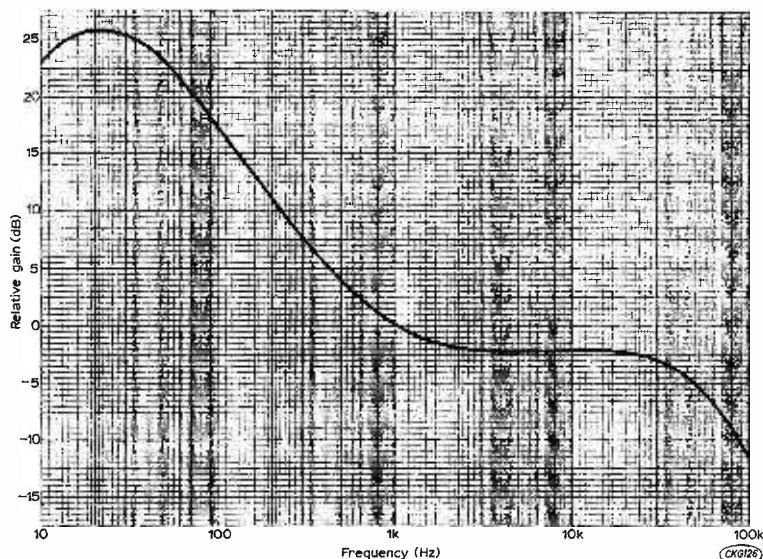


Fig. 17: Tape replay characteristic (direct from head).

day tendency is for a separate tape unit, having internal amplifiers. If it is intended to use such a unit, R8 and C9 should be omitted and R9 reduced to approximately  $1.2\text{k}\Omega$  giving a flat characteristic and sensitivity similar to that of the radio position.

Nevertheless I feel that many home constructors may be interested in a tape head facility so the following table gives the appropriate values for a few of the standard replay characteristics.

TABLE 1

	R8	R9	C9	Standard time constants
D.I.N. $1\frac{1}{2}$ ips	$33\text{k}\Omega$	$890\text{k}\Omega$	$3.9\text{nF}$	$1590\mu\text{S}$ $120\mu\text{S}$
D.I.N. $3\frac{1}{2}$ ips	$33\text{k}\Omega$	$820\text{k}\Omega$	$3.9\text{nF}$	$3180\mu\text{S}$ $120\mu\text{S}$
D.I.N. $7\frac{1}{2}$ ips	$22\text{k}\Omega$	—	$3.3\text{nF}$	— $70\mu\text{S}$
N.A.B. $7\frac{1}{2}$ ips	$15\text{k}\Omega$	$1\text{M}\Omega$	$3.3\text{nF}$	$3180\mu\text{S}$ $50\mu\text{S}$
N.A.B. $3\frac{1}{2}$ ips	$27\text{k}\Omega$	$1\text{M}\Omega$	$3.3\text{nF}$	$3180\mu\text{S}$ $90\mu\text{S}$
N.A.B. $1\frac{1}{2}$ ips				
As for $3\frac{1}{2}$ ips N.A.B.				

The overall response of the amplifier when using components for DIN  $3\frac{1}{2}$  i.p.s. is shown in Fig. 17. The sensitivity of the amplifier with this characteristic was  $1\text{mV}$  approx. Once more the very high loop gain of the operational amplifier is valuable for producing the large amount of bass boost which is required.

## Performance

A number of facts and figures have already been quoted regarding the performance of the *Texan* so that distortion is the main topic left for discussion.

Apart from the money the other good thing about writing an article is the opportunity it gives for liberating a few proverbial bees from one's bonnet. My personal "bee" is concerned with the vicious

circle of "specmanship" which sets Hi-Fi designers chasing each others' tails (or should it be "tales"). Now I am all in favour of pickups which track, noise reduction systems for tape recorders, f.m. broadcasting and electrostatic loudspeakers—on the whole I am sure that they are worth the money. But I cannot see much point in paying more and more for better and better amplifiers when they are already too good for the transducers coupled to them. When the most experienced ears can barely detect 0.1% distortion on pure tones why spend money struggling for 0.01%, especially when all transducers and recording media introduce about 2 or 3% in themselves. This is a generalisation, of course, and it is always easy to find a specific flaw in such an argument. However, I feel the basic principle is good. Namely, consider the system as a whole and don't spend a lot more money unless you are going to

hear the difference. With that said, here are a few more figures:

TABLE 2

Load	Fundamental frequency	Power output (watts)	Harmonic output (dB)			T.H.D. %
			2nd	3rd	4th	
$15\Omega$	1kHz	15	76	67	—	0.047
		10	74	80	86	0.023
		5	74	80	80	0.024
		0.5	71	77	80	0.033
		0.05	59	61	62	0.164
		0.005	15	51	48	0.488
	10kHz	10	54	53	70	0.302
		5	56	57	64	0.221
		0.5	57	57	67	0.205
		0.05	61	70	75	0.096
$8\Omega$	1kHz	25	63	61	69	0.114
		20	65	63	—	0.09
		15	66	65	—	0.075
		5	69	75	—	0.04
		0.5	75	75	—	0.025
		0.05	65	68	69	0.077
	10kHz	25	50	43	63	0.779
		20	52	46	69	0.562
		15	54	50	70	0.375
		5	60	56	65	0.196
		0.5	60	77	—	0.101
		0.05	60	—	—	0.10
$4\Omega$	1kHz	25	61	50	75	0.329
		20	63	50	—	0.324
		15	65	52	—	0.257
		10	67	55	90	0.183
		5	68	61	81	0.098
		0.5	66	70	71	0.066
		0.05	55	58	59	0.245

Distortion: Harmonic distortion was measured using a Radford Low Distortion Oscillator and a Hewlett Packard 3590A Wave Analyzer with a 3593A Sweeper.

This measurement technique is far more accurate and gives more useful information due to the subjective nature of harmonic distortion. The harmonics

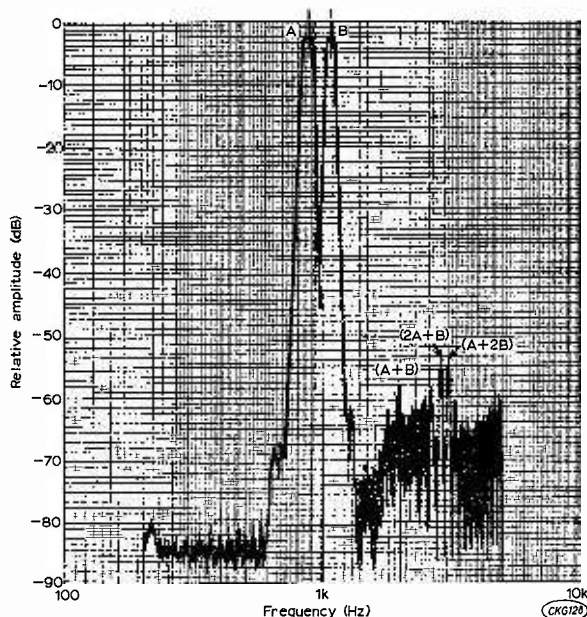


Fig. 18: Wave analysis for input frequencies of 900Hz and 1.1kHz.

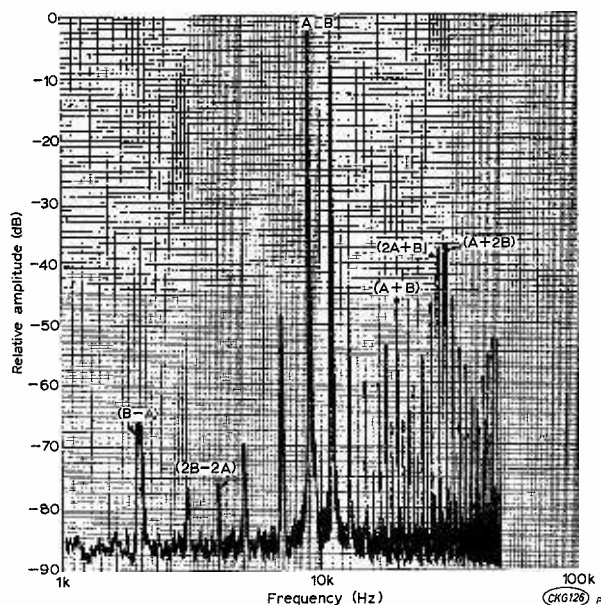


Fig. 19: Wave analysis for input frequencies of 9kHz and 11kHz

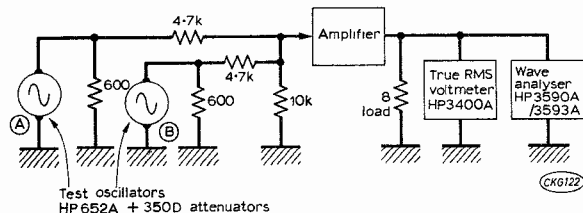


Fig. 20: Test set-up that was used for measurements of intermodulation products (I.P.).

are therefore tabulated in some detail in Table 2 along with total harmonic distortion figures. So you pay your money and you take your choice. The harmonics are quoted in dB below the fundamental. The total harmonic figures are given as a percentage and calculated from

$$\text{T.H.D.} = \sqrt{V_2^2 + V_3^2 + V_4^2} \dots$$

where  $V_2$ ,  $V_3$ ,  $V_4$  etc are the percentage values of the harmonic components.

It can be seen that the percentage T.H.D. does not leap up at the levels where crossover distortion would be apparent so the amplifier has a good clean sound.

The *Texan* is primarily designed to work into 15Ω or 8Ω speakers but, for interest, some distortion figures are also quoted for 4Ω loads.

All the measurements were made on the complete amplifiers so they include any distortion due to the preamplifier.

### Intermodulation Distortion

The intermodulation products (I.P.) in an amplifier's output result from non linearity of the transfer characteristic which causes multiplication of the components of a complex input waveform so that a spectrum of sum and difference frequencies may be produced across the entire amplifier bandwidth. Thus with only two sinusoidal inputs with frequencies A and B we may get I.P.'s at frequencies of A+B, A-B, 2A+B, 2A-B, A+2B, A-2B etc. If the spectrum is analyzed there will also be components at 2A, 2B, 3A, 3B which are due to harmonic distortion in the signal source and those harmonics produce their own I.P.s resulting in the general mish-mash shown in Figs. 18 and 19.

However, after a bit of mental arithmetic, it is fairly easy to sort out the I.P.s which really count. The total intermodulation distortion is calculated from:

$$\text{I.D.} = \frac{\sqrt{I_P^2 + I_P^2 + I_P^2}}{A+B} \times 100\%$$

where I.P., etc are the amplitudes of the intermodulation products A and B are the amplitudes of the input waveforms.

Therefore any I.P. which is 10 to 20dB below the major I.P. in level can virtually be ignored.

The method of measurement was as follows: With the apparatus shown in Fig. 20, oscillator A was temporarily disconnected and the level from oscillator B was adjusted to give 12.6 volts across the 8Ω load (ie 20 watts). The B attenuator was then set back 3dB. This procedure was repeated for oscillator A alone. The two inputs were then mixed together and the output checked on the true r.m.s. meter to ensure that the power was still 20 watts.

The input frequencies were 900Hz and 1.1kHz in one case (Fig. 18) and 9kHz and 11kHz in the other case (Fig. 19). The analyzer was set to sweep from 200Hz to 5kHz for the low frequency test and from 2kHz to 50kHz for the higher frequency test with an analyzer bandwidth of 100Hz in each case.

Fig. 18 shows that with inputs 900Hz and 1.1kHz the predominant I.P.s occur at 2kHz (A+B), 2.9kHz (2A+B) and 3.1kHz (A+2B). These components give a percentage I.D. of 0.19% approximately.

At the higher frequencies it is easier to pick out I.P.s due to the amplifier and again it can be seen

from Fig. 19 that the dominant components are at 20kHz, 29kHz and 31kHz. The difference frequency I.P.s are also clearly seen at 2kHz (B-A), 4kHz (2B-2A) etc but they are insignificant compared with the sum products so that an I.D. figure of 1.0% is obtained.

These distortions may seem rather high but the method of measurement was rather unkind since the *peak* voltage for the combined waveform is  $\sqrt{2}$  times greater than the *peak* voltage for a pure sine input due to the beating of the two waves. The peak output voltage is thus 25.2 volts giving a peak power of 80 watts instead of 40 watts.

### Noise and Crosstalk

The wave analyzer which was used for the distortion measurements is also a very valuable instrument for measuring noise and crosstalk. It gives more accurate and meaningful results and since one has only to insert the graph paper and push the button it appeals to my lazy nature.

The noise versus frequency plot shown in Fig. 21 was made with the *Texan* switched to the radio input and the volume control turned up to nearly maximum so that the input sensitivity was exactly 30mV. The input was then grounded via 600Ω and the wave analyzer was connected across the amplifier output.

Between 20Hz and 1kHz an analyzer bandwidth of 10Hz was used, necessitating an automatic sweep rate of 1Hz/Sec. To avoid spending six hours or so completing the plot to 25kHz, the bandwidth was increased to 100Hz after 1kHz. This allowed the sweep rate to be increased to 10Hz/Sec.

The ordinate scaling of the graph is relative to the full output voltage (12.6V) and it can be seen that between 20Hz and 1kHz the mean level is approximately -110dB. Above 1kHz the level jumps by 10dB since noise is proportional to  $\sqrt{\text{Bandwidth}}$

$$100 \\ \text{(and } 20 \log_{10} \frac{100}{10} = 10\text{dB)}$$

However, the absolute noise/root cycle is still the same, about  $38\mu\text{V}/\sqrt{\text{Hz}}$ . To get a full bandwidth signal/noise ratio we must add 33dB to the plotted level:

$$\frac{20\text{kHz}}{10\text{Hz}} \text{ (i.e. } 20 \log_{10} \frac{20\text{kHz}}{10\text{Hz}} \text{) giving a figure of 77dB.}$$

The wave analyzer allows the hum components to be measured separately since peaks are obvious at 50Hz and particularly at the odd harmonics of 50Hz indicating that they originate in the power supply. Adding these components together gives a separate

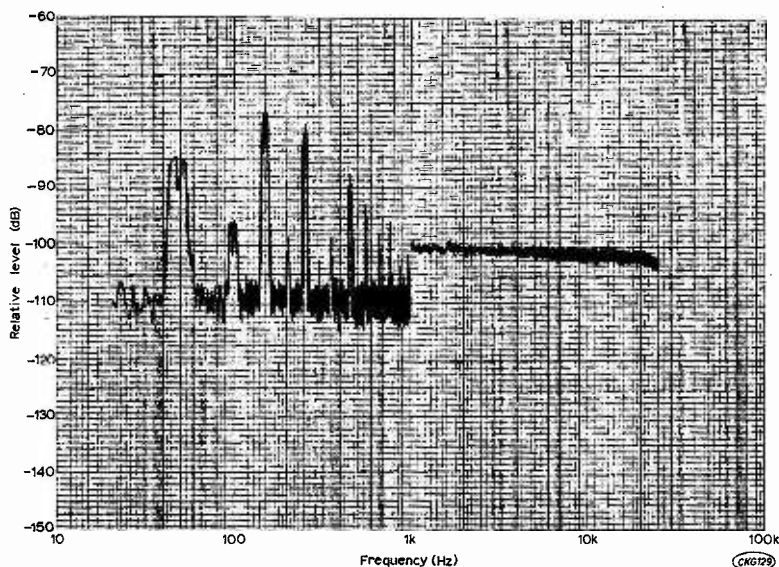


Fig. 21: Noise v. frequency.

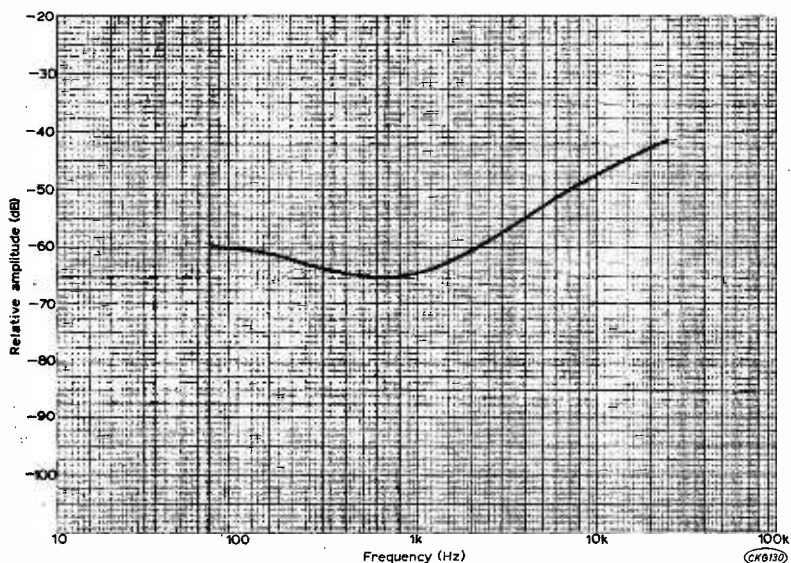


Fig. 22: Interchannel crosstalk v. frequency.

figure of 75dB for the signal/hum ratio.

More subjectively I have found that for normal listening in domestic surroundings one has to put an ear fairly close to the loudspeaker to decide if the amplifier is switched on or not and that is really the acid test.

To measure crosstalk versus frequency the b.f.o. output of the wave analyzer was used to provide a 30mV input to one channel of the amplifier. The input of the other channel was grounded via 600Ω and the balance control was set to its mid-way position. The volume control was adjusted to give 20 watts into one load so that any extra coupling via the power supply would be included. The analyzer input was then connected to the output of the other channel. A continuous sweep was made between



60Hz and 25kHz at a bandwidth of 100Hz. The ordinates of the plot are again relative to full output voltage giving an inter-channel crosstalk figure of  $-65\text{dB}$  at 1kHz and  $-48\text{dB}$  at 10kHz. The crosstalk figures quoted in the specification were measured with an r.m.s. voltmeter at full bandwidth—hence the difference of 14dB at 1kHz. This shows the merit of using a selective voltmeter at low signal levels if other spurious signals are likely to be present. At 10kHz the crosstalk becomes the predominant signal so that the specification figure is not in error at this frequency.

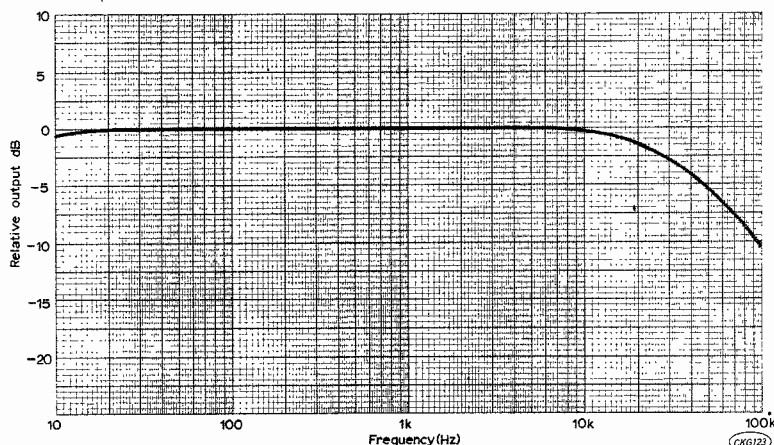


Fig. 23: Power response (20W into  $8\Omega$  resistive load).

## Power response

The frequency response of the *Texan* was plotted with the selector switch in the flat radio position and with the input and gain adjusted to give a power output of 20 watts at 1kHz into an  $8\Omega$  resistive load. The response is almost identical to the low level response shown in Fig. 5 (part 1). This indicates that the gain of the amplifier is still determined by the passive feedback components in the circuit and is not effected by changes in the parameters of the transistors in the power stage. The phase advance capacitor C18 produces a smooth roll-off outside the audio band to eliminate r.f. signals from the output which could cause intermodulation problems with stereo multiplex decoders, tape oscillators and

so-forth. In response to numerous enquiries, readers are reminded that all components for the *Texan*—including drilled fibre glass p.c. board, drilled and punched metalwork, finished front panel, will be available from Henry's Radio Limited.

Kits will also contain pre-formed wire packs to facilitate assembly and complete hardware—in fact everything will be included even down to the last nut and bolt.

A slimline version of the teak sleeve—slimmer than the type shown in the photographs will be available during July/August.

Henry's Radio Limited are the sole U.K. distributors for the "TEXAN", to the trade and retail outlets.

## TO BE CONTINUED

**May 7**— Spalding "Tulip Time" at picnic site, Surfleet, 4 miles north of Spalding on the A16 Spalding-Boston road. Talk-in stations will be G3VPR/P on top band (1980kHz). Something for all the family. Free admittance.

**May 21**— Northern Mobile Rally, at Moore Grange School, Parkstone Avenue, off Ring Road, West Park, Leeds. Refreshments will be available. Further details from D. Binns, G3MGI, 80 Gipton Wood Road, Leeds 8, Yorkshire.

**May 28**— Chiltern Mobile Rally, organized by the Chiltern Amateur Radio Club, and held in the grounds of Sir Francis Dashwood, at West Wycombe, near High Wycombe, on the same day as an annual steam rally. Talk-in on 160m and 2m. Further details from: P. Perkins, G3OUV, Loakes House, Loakes Park, High Wycombe, Bucks. High Wycombe (0494) 21612.

**May 28**— Hull & District Amateur Radio Society held in grounds of the East Riding College of Education, Bishops Burton, on the A.1079 York to Beverley. Further information from L. D. Colley, G3AGX, Micasa, Ferry Road.

## MOBILE RALLY DIARY

Wawne, Hull, Yorkshire.

**June 11**— Third Elvaston Castle, Elvaston Castle Countryside Park, Nr. Derby.

**June 18**— Anglian Mobile Rally, at the Suffolk Show Ground, Ipswich. Further details from D. W. Thomas, G3ZLN, The Old Peoples Home, 9 Burlington Road, Ipswich, Suffolk.

**June 25**— Bristol City & County RSGB Group, at Longleat, Warminster, Wilts.

**June 25**— West of England Mobile Rally, at Longleat, near Warminster, Wiltshire. Information from D. Iles, G3COP, 23 Dryleaze Road, Stapleton, Bristol.

**July 2**— South Shields & District Amateur Radio Club.

**July 9**— Cornish Mobile Rally, organized by the Cornish Radio Amateur Club, will be held at the Truro Rugby Football Ground. Talk-in stations will be operational

on 1.875kHz a.m. and 2m a.m.

**July 16**— Upton-on-Severn Mobile Rally organised by the Worcester & District Amateur Radio Club. Further information from B. A. Jones, G8ASO, 12 Woodside Road, Larkill, Worcester.

**August 6**— Woburn Abbey Rally.

**August 13**— Torbay Amateur Radio Society Mobile Rally at Newton Abbot Rugby Ground.


**August 13**— Annual Derby Mobile Rally at Rykneld Schools. Details from T. Darn, G3FGY, 1, Sandham Lane, Ripley, Derby.

**August 20**— Saltash & District Amateur Radio Club Rally at Saltash Grammar School, with side-shows etc. Ample free parking on site. Details from: 1 Aldridge, G4AJU, 302 St. Peter's Road, Manadon, Plymouth, Devon, PL5 3DU.

**August 26-27**— Stratford-on-Avon Radio Club Mobile Rally at the National Agricultural Centre, Kenilworth, Warwickshire. Hq. of the 'Royal Agricultural Society of England. Further details M. J. W. Webb, G3OOQ, 14 Townsend Road, Tiddington, Stratford-on-Avon, Warwickshire. Or ring Stratford-on-Avon 5973.



# MW/IF

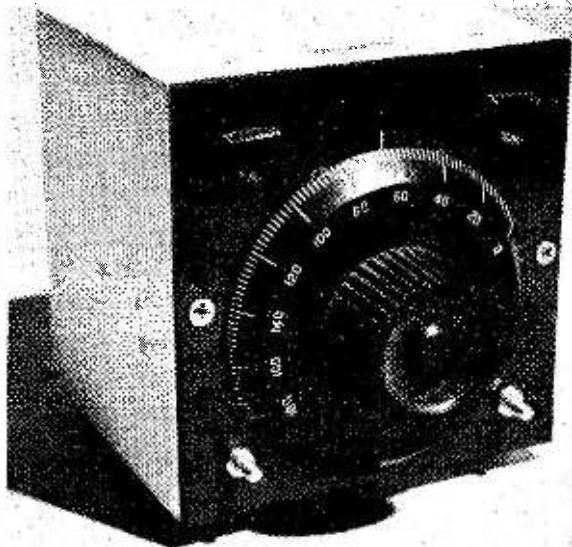

## WOBBULATOR

A.J. BIRKINSHAW

**A** WOBBULATOR is a signal generating oscillator which is frequency modulated by the sawtooth timebase sweep of an oscilloscope. The band of frequency swept is designed to cover the pass band of tuned radio frequency coupled circuits such as the intermediate frequency transformers of a superhet receiver.

### THE REQUIREMENT

The response curve of an i.f. amplifier may be plotted by gradually shifting the frequency of a calibrated signal generator of constant amplitude applied to the amplifier input and recording the detector output voltage relative to input frequency as in Fig. 1.

We could use a pen recorder to trace output voltage on a moving paper chart if there were a mechanical linkage from chart drive to the tuning control of the oscillator with linear rotation relative to frequency.

One would plot many graphs before deciding which give the best or required performance and as preset controls on i.f. transformers are not designed to give an indication of electromechanical value and in some instances a certain amount of hysteresis between electrical and mechanical value may exist, the process of resetting may become somewhat tedious.

Most of us have at some time or other taken the easy way out and tuned for maximum aural response which is reasonably effective under the circumstances because we do not have the manufacturers resources in the way of special equipment

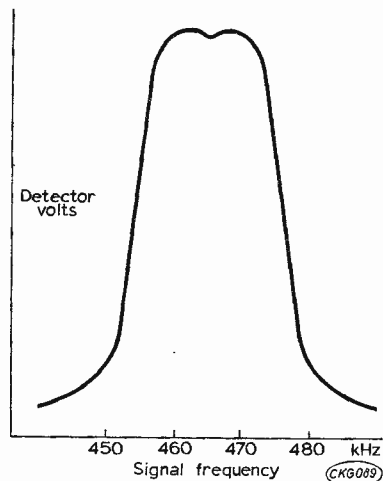


Fig. 1: A typical response of an i.f. amplifier.

designed to set-up a particular model.

However, because radio receivers depend largely on their i.f. response curves for the quality of reproduction, both bandwidth and amplitude have to be considered. We are in deeper trouble if we have just substituted a transformer of higher Q where maximum amplitude may lead to instability. So we require to see the behaviour of the circuit during adjustment.

We can display the band-pass response on an oscilloscope screen during alignment operations if we automatically sweep the signal in synchronism with the 'scope's time base using the detector output voltage for vertical deflection of the trace, Fig. 2.

Sweep may be obtained if the time base voltage controls the reactance of the oscillatory circuit of the signal generator to swing its resonant frequency a known amount equally above and below a mean value, the mean being the dial frequency setting of the generator.

Frequency modulated signal generators which, with the aid of a cathode ray oscilloscope, were designed for the visual examination of band-pass response curves and the alignment and testing of radio receivers have used various methods to obtain the required sweep as technology advanced. First the motor driven condenser, then the Miller reactance valve and nowadays we have the much

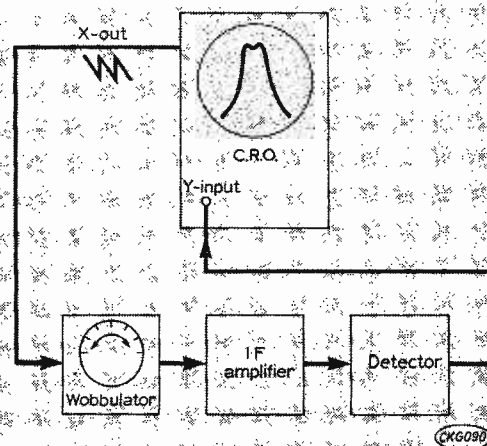


Fig. 2: The arrangement used for displaying the curve shown in Fig. 1.

simpler semiconductor diode whose reverse bias capacitance varies with voltage.

The author is indebted to D. Bollen who described, in the January 1970 issue of *Practical Wireless*, how the common silicon power rectifier shows useful varactor properties. The author has found by experiment that we may dispense with the bias battery for the oscillator application.

For amateur receiver projects the wobulator to be described will repay its simple cost even if the oscilloscope required as an accessory has to be borrowed. Its output is 100 to 370mV peak to peak over the tuning range of 370kHz to 1.2MHz which covers normal intermediate and medium-wave frequencies.

The minimum requirements of the oscilloscope are moderate, a vertical sensitivity of 0.1 to 1V per centimeter and a time base speed range covering 10mS to 1mS per centimeter being all that is required.

## THE CIRCUIT

A single OC44 germanium PNP transistor is used in a circuit configuration popularly employed as a common base oscillator found as part of self-oscillating mixers in medium-wave superhet transistor radios. The emitter resistor is smaller in value than usually employed to allow for greater r.f. output.

The diode requires a negative reverse bias which is not apparent by first examination of the circuit diagram shown in Fig. 3. The bias is provided by rectification of oscillatory power developed across R4 and R5.

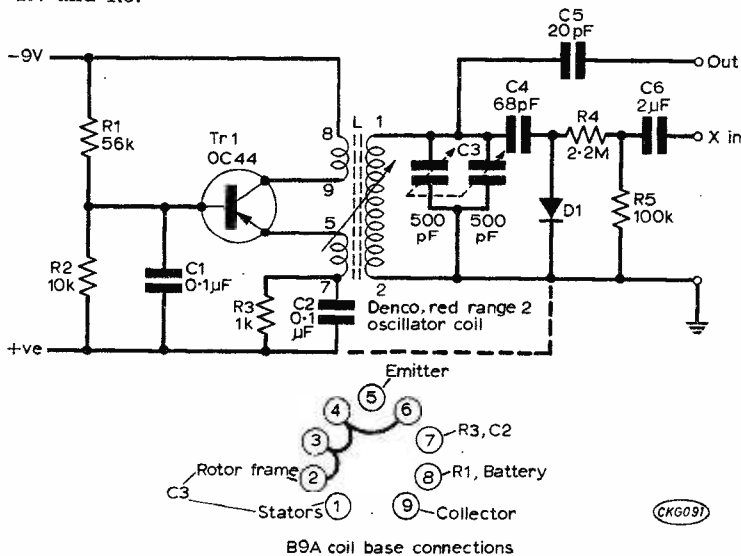


Fig. 3: The circuit of the m.w./i.f. wobulator.

The X input in a sawtooth waveform is applied via C6 to preserve the waveshape. Sawtooth amplitude should be in the region of 20V peak to peak which is required to swing the diode capacitance and thereby frequency modulate the oscillator.

A lead via a 20pF capacitor connects to the signal input of the receiver being examined. A screened lead from the detector load connects to the Y input of the oscilloscope in use (screening is essential to avoid instability).

With the Denco coil specified, a twin gang 500pF tuning capacitor connected in parallel covers the

## ★ components list

Resistors	
R1 56kΩ	R4 2.2MΩ
R2 10kΩ	R5 100kΩ
R3 1kΩ	All ½W, 10% types
Capacitors	
C1 0.1µF	C4 68pF
C2 0.1µF	C5 20pF
C3 500~500pF variable	C6 2µF 250V polyester
Semiconductors	
Tr1 OC44	
D1 Silicon diode BY127, FST3/4 AF etc.	
Miscellaneous	
L1 Oscillator coil, Denco red, Range 2; Veroboard;	
B9A valve holder	

range depicted in Fig. 4. A twin 365pF unit may be substituted with an acceptable shift of frequency coverage.

## CALIBRATION

The dial can be an engraved knob marked every two degrees from 0 to 180°, an alternative is to use a small protractor and pointer knob. With the case removed, connect the battery and place near a broadcast receiver tuned to the medium wave-

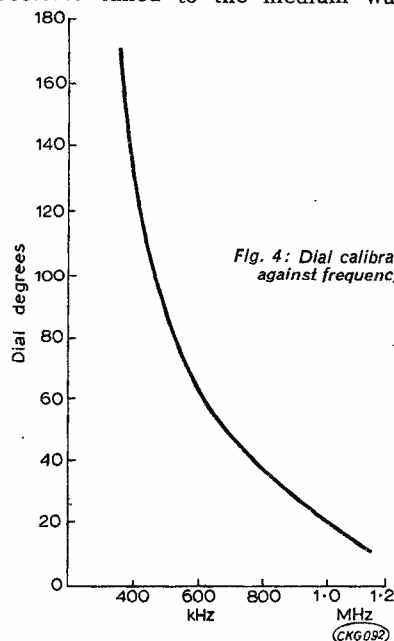



Fig. 4: Dial calibration against frequency

band. Select a programme of known frequency and rotate the wobulator tuning control to obtain a beat whistle. Check with the calibration graph shown in Fig. 4 and adjust the core of the coil to obtain a similar calibration.

Construction should present no problems and the layout adopted by the author may be seen from the photographs. The Denco coil is best mounted on a B9A valveholder, this will avoid the necessity of soldering directly to the pins.

The simple wobulator project can be put to further use by the addition of an audio modulating

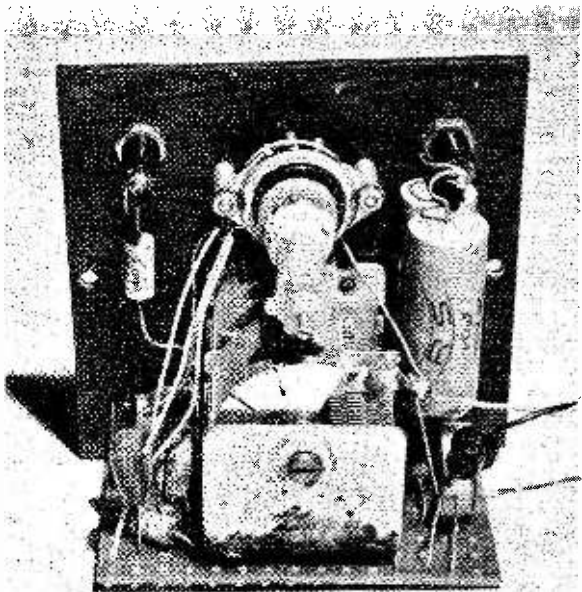oscillator operating at about 440Hz. We do not of course require modulation when using the wobblator but there are many occasions where a modulated oscillator with reasonably pure sine wave characteristics is an asset, having successfully



An internal view of the prototype.

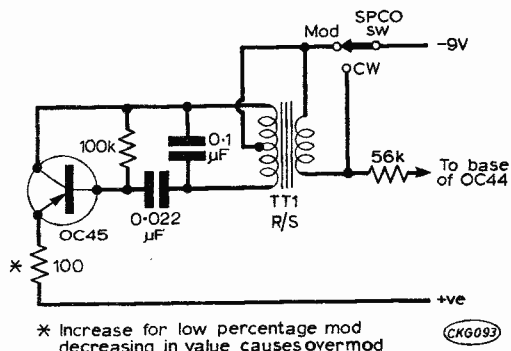


Fig. 5: A simple modulator circuit which may be added.

aligned our receiver i.f. stages we may prefer to adjust the signal r.f. stages and also to note the aural response through the amplifiers driving the loudspeaker. A tunable modulated oscillator enables us to do this, conversion is a simple matter for if we do not apply a sawtooth input, the r.f. oscillator provides c.w. output which may be base modulated by a single transistor oscillator as shown in Fig. 5.

The additional stage may be constructed on a small piece of Veroboard, this and a single pole changeover switch may easily be accommodated in the space at the rear of the cabinet.

Modulation depth may be adjusted by altering the value of the 100Ω emitter resistor but the value given is a reasonable compromise to allow sufficient tolerance in the performance of the component parts. Reducing the value gives overmodulation and poor waveform, increasing the value decreases modulation amplitude but provides a sine wave without distortion.

**JUNE ISSUE**

# TELEVISION

## COLOUR IF STRIP

The i.f. strip of a colour receiver must be particularly carefully designed if the chrominance, luminance and sound signals are to be handled without distortion and interference, so this is a crucial part of the colour receiver project. The strip on which we start next month uses separate sound/chrominance and luminance detectors to reduce sound-chrominance beat patterning. The former detector also drives an a.f.c. circuit and the strip incorporates a two-stage a.g.c. circuit—a third stage providing delayed a.g.c. for the tuner. The strip incorporates an intercarrier sound channel using a TAA350 i.c., a controlled tuned chrominance stage and the luminance channel and delay line.

## C AND L IN TV SERVICING

Many TV set faults are caused by faulty capacitors and inductors. A condensed summary of fault conditions, test methods and suggested stocks to hold will be given.

## TRANSISTOR SYNC STAGES

Transistors are now widely used as sync separators and amongst developments are two-transistor sync stages. The features of importance in the use of transistors in this part of the circuit will be investigated.

## RENOVATIONS: COLOUR!

A few ex-rental colour sets are now appearing on the market. Caleb Bradley discusses the likely problems, the equipment required and initial checks and adjustments. Including details of an easy to construct e.h.t. meter and a degaussing coil.

## PLUS ALL THE REGULAR FEATURES

**ORDER YOUR COPY ON THE FORM BELOW**

TO..... (Name of Newsagent)

Please reserve/deliver the JUNE issue of TELEVISION (20p), on sale MAY 15, and continue every month until further notice.

NAME.....

ADDRESS.....

# LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents

## On the bottle

Like your four correspondents of March '72 "Letters" I, too, was bottle-fed on valves. However, they should try to recapture the spirit of adventure and voyage into the New World of electronics. More than 50 years ago valves were also unreliable (and costly) remember? but we persevered until better days came along. Now transistors and other solid state devices have opened the door very widely indeed. Transistors unreliable? Not any more when properly used and treated. A transistor radio designed and built in 1958 by the writer is still working 100 per cent without any breakdowns. Blame the faults on designers and manufacturers of commercially made equipment built to a price-profit formula: to the lack of a new kind of servicing expertise which many persons cannot be bothered to acquire. The craze for making equipment for ordinary purposes smaller and yet smaller, added to the profit motive regardless, one must expect shoddy goods. No, Valves, the day of the bottles—good as they were and blessed their memory—is gone forever. Space travel, satellite communications, etc, would not have been possible without solid state devices—nor would there have been any moon walk on television. Greatest boon of all is possibly the contributions these devices have made to Medical electronics.—**A. V. Nash**, (London, S.W.12).

## N.Z. prices

I have just read a letter in your magazine, from K. B. Moore, dated December, 1971, and I feel I must point out that the prices for the items listed are as follows: BC109 transistor—\$0.84c (42np) not \$1.85c. BC169C transistor—\$1.10c (55np) not \$2.25c. 5μF 12V capacitor—.14c (7np) not .20c. 1.5M resistor—.05c (2½np) not .10c. If Mr. Moore was actually charged the prices he mentions, I would suggest that next time he buys components, he shops around first.

As you will see from the corrected list, semiconductors are about 4 to 5 times their cost in

the U.K., but passive components are very similar in price. The major reason for the difference is that the N.Z. Government places a rather large import duty and sales tax on all semi-conductors.—**A. R. Millar**, (Auckland 10, New Zealand).

## Fight Back

As a human being, I am open to susceptibility, and it is with great reluctance that I resist a tirade against "bottles," induced by the first four letters in your March issue. However, as an unbiased electronics enthusiast it would be wrong to omit to mention that valves have their uses. Indeed, only a fool would suggest using transistors in the output stages of a high power radio transmitter, for example. But semiconductor devices also have a place. Who, for instance, would even consider building a computer of valves, or even of discrete components?

In his letter in the March issue Mr. Martin gives no evidence against transistors, nor any in support of valves; it would be interesting to know the reasons for his electronic reactionism! By comparison, Mr Freeby gives difficulty of servicing as his reason for preferring valves. He mentions "transistor radios which almost fall to pieces when you try to service them," but this is the fault of their physical construction, not the transistors therein. However, he does conclude "or blow up half a dozen transistors when searching for one faulty one", and *this* 'fault' can be cured by practise on the serviceman's part.

"Valves are best for starting people off on electronics," writes Mr. Watton, but here I must beg to differ, for the following reasons:

(i) Transistors are *very* cheap—those used by beginners that is, which can be obtained for less than 1p each (the transistors, not the beginners!)

(ii) There is no risk of electric shock or of burns in beginner's transistors circuits.

(iii) The electrical fragility of transistors encourages care on the part of the constructor, surely

an important part of electronics.

Finally, Mr. Wode's only argument seems to be the average size of loudspeakers in transistor radio sets giving poor tone. I am sure we all agree that large loudspeakers are essential for good quality sound, but where do transistors come in? Admittedly, transistors are electrically fragile, and a transistor class B amplifier needs careful design, for it to be successful, but the fact that all the audio amplifiers I know of on the market today are transistor amplifiers, prove that, in this field at least, transistors are supreme!—**R. D. Broome**, (Warwickshire).

## U.S.A. — 1940

Further to your Leader in the March issue, your younger readers may be interested to know that prior to 1940, reception of U.S.A. stations in the S.W. Bands was so good that the London evening newspapers used to print the radio programmes of Boston, New York, Schenectady etc. in addition to B.B.C.—**G. Snewin**, (London, E.17).

## Quality speakers

British beaches may soon have no sand judging by the number of people who seem to be building the Quality Hi-Fi speakers! But here's a useful bit of information which may help readers.


The SI-1020A hybrid amplifier specified for the system has been discontinued but may be replaced by the SI-1025A which is for all practical purposes identical in performance and mounting. The plinth specification is unchanged. Amplifiers available from Photain Controls Ltd., Randalls Road, Leatherhead. Tel. 2776.—**Caleb Bradley**, (Essex).

## Company policy

I couldn't agree more with the many views on poor workmanship and bad after-sales service that have been published in *Practical Wireless*. It's about time that high standards of the above were adopted as company policy to ensure value for money.—**Ian Vine**, (Middlesex).

# test bench amp

E. BUCKLAND

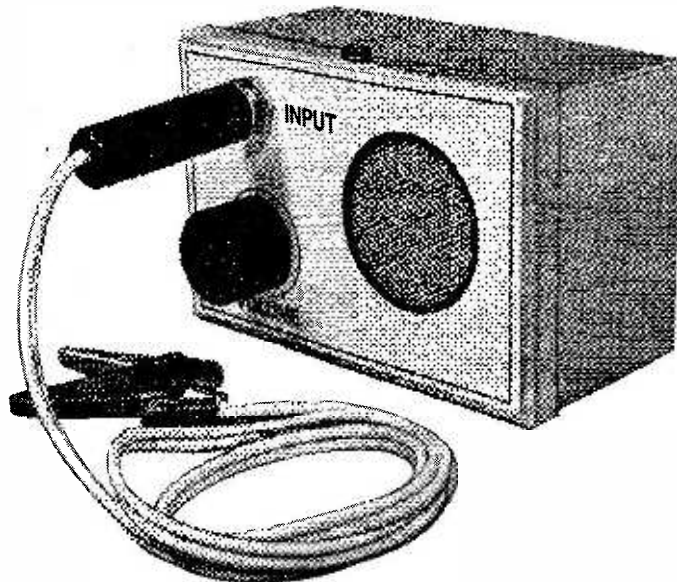

ANYONE who has more than a passing interest in the construction of radio and electronic projects will have acquired a fair number of items of test gear. A multimeter is essential but an r.f. and a.f. signal generator will also be found very useful. These items, plus others which will be required for one's own particular field of interest, are used mainly to test and trouble-shoot finished or partially finished equipment.

One of the most useful items in the author's opinion, however, is none of the above but a simple straightforward audio amplifier; this is rarely considered as an item of test gear. This is surprising when one considers how useful it can be.

A high proportion of the projects published in this magazine are fitted with an amplifier as the final stage; a quick check shows that 30 of the last 36 projects featured on the cover of *P.W.* either used an audio amplifier or were designed to feed one. This gives a rough indication of how often a test bench amplifier could be used for checking that either the early stages of such a project are operating properly or even that an amplifier is working correctly. The circuit shown here can equally well be used as a signal tracer at audio frequencies.

To be of maximum use such an amplifier has to meet certain requirements. Portability was considered important and so the circuit is battery operated. Small size was also high on the list of priorities as this will mean less shelf space and will make it easy to carry around in a brief case for instance. It had to be of reasonable quality, at least good enough to be able to distinguish between correct and incorrect operation of the equipment to which it is coupled. High input impedance and high sensitivity are also desirable features for such a circuit. The output level is of less importance as long as it is to be used mainly as a monitor. The output is in the order of 200mW but small speakers are not very efficient and this output is less than it sounds. Even so, this compares favourably with the output from normal small transistor radios using the same type of battery and has been found to be more

than adequate for the intended purpose. In fact many of the design features were controlled by the use of a PP3 battery. This is used to meet the requirements of portability and small physical size. The permissible current drain from this battery limits the output to the level mentioned above.

All the components used are widely available and the cost of this project is not high—certainly not over £2 in total.

## THE CIRCUIT

The circuit of the Test Bench Amplifier is shown in Fig. 1. The input is applied directly across the volume control VR1 which is rather higher in value than one would normally encounter in a circuit of this type. This high value has the advantage here of presenting a high impedance input at low volume control settings—this approaches 500kΩ, though this is somewhat reduced for high volume settings where

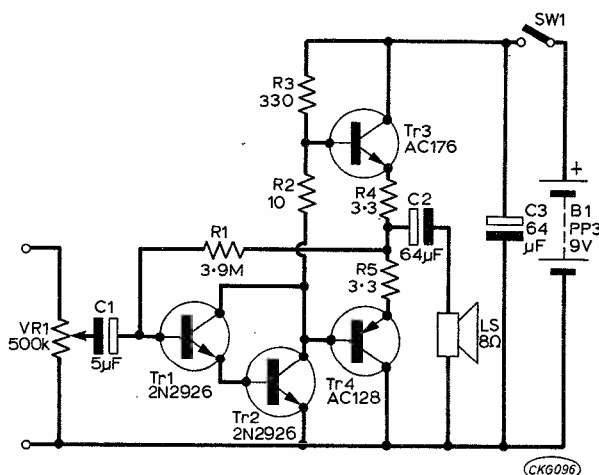


Fig. 1: The complete circuit of the Test Bench Amplifier.



the input impedance of the first transistor is in parallel with the volume control.

The slider connects to the base of the first transistor via the d.c. blocking capacitor C1. Tr1 and Tr2 are connected as a Darlington Pair, a configuration which gives very high gains and also a higher input impedance than a conventional common-emitter amplifier would present.

This stage drives the output pair Tr3 and Tr4. These are conventionally connected as a complementary output pair; one is an NPN and the other a PNP with the bases connected together by R2, a 10Ω resistor. This is necessary to provide a small bias to avoid cross-over distortion.

When Tr2 is conducting heavily (when it is driven on by a positive swing in the signal), Tr4 is driven into conduction. When Tr2 approaches cut-off (due to a negative going swing) the voltage at the base of Tr3 rises (R3 providing the bias) and it conducts. This explanation is far from complete but descriptions of the operation of this type of output stage are described more completely from time to time in other articles.


Note that Tr3 and Tr4 must be a matched pair of transistors but are not otherwise critical. Any similar complementary pair of germanium transistors can be substituted without any circuit modifications.

The bias for the Darlington Pair is provided by R1 which also introduces both a.c. and d.c. feedback. If difficulty is experienced in making the circuit work, a slight change in this value may be helpful. However four prototypes have been built of this circuit and this value has proved satisfactory in each case.

The low value of C2 certainly reduces the bass response but this makes very little difference in practice—miniature loudspeakers are not normally renowned for their good bass response; there seems little point in providing a signal which cannot be handled by the speaker. This smaller value than one would normally find has the added advantage that it is physically small.
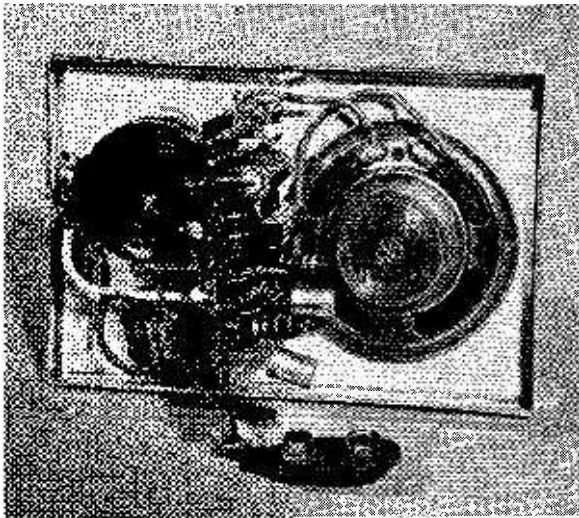
## CONSTRUCTION

The majority of the components are mounted on



An internal view of the prototype.

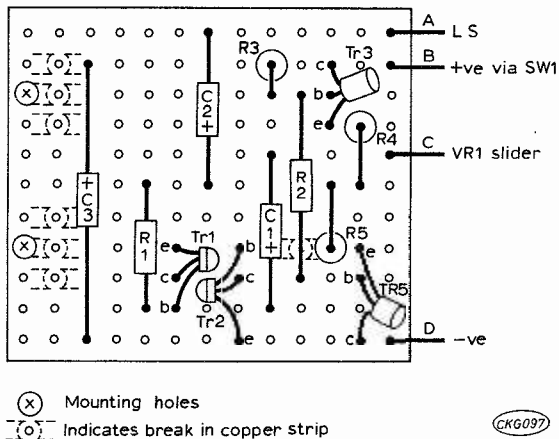


Fig. 2: The component layout on Veroboard.

## ★ components list

R1 3.9MΩ R4 3.3Ω  
R2 10Ω R5 3.3Ω  
R3 330Ω  
All ½W, 10% types  
VR1 500kΩ log. pot. with switch

### Capacitors

C1 5μF 10V C3 64μF 10V  
C2 64μF 10V

### Transistors

Tr1 2N2926 Tr3 AC176†  
Tr2 2N2926 Tr4 AC128†  
† Matched Pair.

Any "colour" of 2N2926 transistor may be used for Tr1 and Tr2.

### Miscellaneous

L.S. Miniature 8Ω loudspeaker  
B1 PP3 battery, 9V  
Battery clip; Veroboard 0.15in. matrix, 13 x 11 holes; metal or plastic case—see text; Jack plug and socket; Crocodile clips.

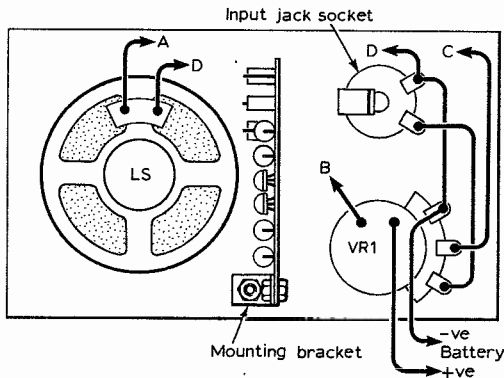


Fig. 3: The wiring details. The wires marked A to D connect to the appropriate points on the circuit board.

a small piece of Veroboard, 0.15in matrix, 13 x 11 holes. One end is left free of components to leave room for a small mounting bracket. The components layout is shown in Fig. 2. The copper conducting

strip has to be cut away around the mounting holes for obvious reasons but other than this only one additional break is needed.

Due to the low output and the protection afforded the output pair by R4 and R5, heatsinks are not really necessary on Tr3 and Tr4 when operating from the specified battery.

The circuit can be fitted into almost any small case. The author originally built his into a plastic case but this was dropped several times and eventually broke. For this reason it was replaced by a small metal case which proved much more satisfactory. The one used in the prototype was 4 x 2½ x 2in. fitted with a lid; this is available by mail order from Henry's Radio.

The lid carries the components and a wiring diagram for the final connections is shown in Fig. 3. Of course, any convenient case can be used. The loudspeaker is glued to the face; this method of fixing has been found to be very simple and quite strong enough.

The input to the amplifier is through a jack socket and two wires from the associated jack plug can be fitted with croc clips for rapid connection to any circuit. A band of tape was wound around one of these wires to identify the "earthy" connection.

Proper distortion and frequency response figures have not been taken from this circuit but the amplifier introduces no noticeable distortion and the frequency response has proved to be quite adequate for the designated purpose. ■



#### BOOKS WANTED

...Mullard Circuits for Audio Amplifiers. Second Edn. 1962.—George W. Saunders.  
...Any volumes 3 to 10 "Wireless World", RSGB T & R Bulletin, July 1933 (with covers), RSGB 1928 Annual Log Book. "History of Radio Telegraphy & Telephony", Blake, 1927.—Allan Hertridge, 631DG, 96 George Street, Basingstoke, Hants.  
...Oscilloscope equipment circuits by Easterling buy or borrow.—F. Cosgrove, Rowan Chalet, Lower Road, Postcombe, Oxford, OX9 7DU.  
..."Simple Radio Circuits" by A. T. Collins.—J. Wheelton, 41 Chorley Road, Burntwood, Walsall, Staffs.  
...Young Schoolboy requires a second-hand copy of the Radio Communication Handbook about £1? Phone Harpenden 5910.—Huw Hallybone, 78 Sauncey Avenue, Harpenden, Herts.

#### INFORMATION AVAILABLE

...I have in my possession an Italian Magazine dated the Year 1953 called "Bollettino Tecnico Jeloso", it also has English Translation of contents. I would be pleased to send to any reader who may have a need for it, if they send S.A.E. 12" x 4"—it has full diagrams, of circuits and components, for the following: TRANS: 9,212-TR, TRANS: 9,222-TR, REC: 9,209-R.—R. Peel, 57 Tangmere Drive, Castle Vale, Birmingham, 35.

#### EXCHANGE

...P.E. April, 70 to Nov. 70 & March 71 to Dec. 71. Also P.T. Jan. 71 to Oct. 71. 27 issues. All good condition. Would exchange all these for Vol. 43 & 44 P.W.—G. J. David, 32 Trebeferad, Llantwit Major, Glam.  
...I have the Aug. 1966 edition of P.W. twice so am willing to exchange one copy for any interesting bit of electronic junk.—L. Cook, 7 Plum Tree Close, Eccleston Park, Prescot, Lancs., L35 7JT.  
...Swap, buy or sell P.W. back issues. Large quantity for disposal. S.A.E. for lists.—R. Forsbert, 123 Harestone Hill, Caterham, Surrey, CR3 6DL.  
...June 1968, July and Aug. 1968 issues of P.E.—S. Tucker, 8 Hawkswell Gardens, Oxford, OX2 7EX.  
...May 1971 issue of P.W.—C. H. Cheah, 17 Hargrave Road, Archway, London, N19 5SH.  
...Aug. 1968 P.W. or photocopy of Portable Keyless Organ.—G. E. Dutton, Buckth-Vine-Inn, Burscough Street, Ormskirk, L39 2EG, Lancs.  
...P.W. Volume 45 (May 69–April 70), P.W. Volume 47 No. 7 (Nov. 71), P.E. Volume 5 (Jan. 69–Dec. 69 inc.).—M. Ridger, 25 Broomfield Crescent, Leeds, LS6 3DD.  
...P.W. for Jan. 1971 with Part 1 of the Stereo Tape Recorder.—R. W. Andrews, 7 Bracken Grove, Wellington, Salop.  
...The issue of P.W. containing the circuits, operating info, for the electric organ published circa 1964.—A. J. L. Brown, 9 Rullion Road, Penicuik, Midlothian.  
...The blueprint for the P.W. 35W Guitar Amplifier.—P. Winkley, 96 Leopold Avenue, Handsworth Wood, Birmingham, 20.  
...July 1971 issue and any 1969 issues of P.W.—N. A. Dent, Middle House, Lockner Holt, Chilworth, Guildford, Surrey.

CHARLES MOLLOY

## THE Medium Wave Column

**TOMMY CROSBIE** who lives in Broseley, Cheshire writes "I do not think a communications receiver is necessary for a beginner. I only use a domestic receiver (removed from an old radiogram) though some modifications must be made." He then describes how he traced the a.g.c. line and connected it to chassis via a switch. When the switch is operated the a.v.c. is off and the receiver is ready for DXing. Stations heard by Tommy on his modified receiver and MW loop include RNE Tenerife, Canary Islands on 620kHz; Godhavn, Greenland 650kHz; PJB TransWorld Radio, Bonaire 800kHz; EFJ57 Tenerife 890kHz; WINS New York 1010kHz; WBMJ San Juan, Puerto Rico 1190kHz; Radio Afghanistan, Kabul 1280kHz; PJD St Maartin, Netherlands Antilles 1295kHz (this station often broadcasts in English).

DXers will find it an advantage to switch-off the a.v.c. when operating on the medium waves. Two or more stations can often be heard simultaneously on a channel and the slight difference in frequency between them gives rise to a beat. If the a.v.c. is switched on, then the receiver gain will follow this beat, giving rise to an unpleasant flutter which makes reception difficult. The writer invariably has the a.v.c. switched on, then the receiver gain will follow this while the receiver gain is adjusted with the r.f. gain control.

**Paul Swain**, while on a visit to Tudweilog on the coast of Wales, used his Sanyo 7 transistor portable between 0003hrs and 0330hrs GMT on the 12th February to log CBN St John's, Newfoundland 640kHz; WOR New York 710kHz; CJON St John's 930kHz; WINS New York 1010kHz; WNEW New York 1130kHz; WWVA Wheeling, West Virginia 1170kHz; WHAM Rochester, New York 1180kHz; WOWO Fort Wayne, Indiana 1190kHz; WCAU Philadelphia, 1210kHz; WTOP Washington, D.C. 1500kHz; WMEX Boston 1510kHz; WKBW Buffalo, N.Y. 1520kHz.

**Richard Coyle** of Glasgow sends a log heard on a Lafayette KT340 and an antenna of 200ft of wire wound round the loft in a triangular coil. R. Caracas, Venezuela 750kHz; WHDH Boston 850kHz; WCBS New York 880kHz; CBM Montreal 940kHz; R. Sutatenza, Colombia 960kHz; WBZ Boston 1030kHz; WHN New York 1050kHz; Radio Globo, Rio 1180kHz; R. Tupi, Rio 1280kHz.

A new high power outlet at Bissau, Portuguese Guinea has appeared on 1070kHz. According to a QSL received by the writer it is on the air daily until 0100hrs GMT and has been heard as a strong signal with deep fading, after 2300hrs. The address for reception reports (which may be in English) is Emissora da Guine Portuguesa, Caixa Postal 191, Bissau, Portuguese Guinea.

Send logs and information about the Medium Waves to the writer at 132 Segars Lane, Southport, PR8 3JG.

# Electronotes..

**S. GINSBERG**

**T**HINGS are hotting up in the television field. Hitachi have launched a 20in. colour tube with 110° deflection angle and with a 29mm neck. The Japanese market version of the tube will have a black matrix but because of Zenith patents the one for Europe will not. Hitachi have plans to follow this tube up with smaller versions in 18in. and 16in. One interesting thing about the Hitachi tubes is a change in the approach to avoid a form of distortion.

A problem with many 110° tubes is that the static convergence at the edges of the tube is upset because of the large convergence angle near the edges of the tube. The electrons passing through the aperture in the shadowmask do not land accurately on the corners of an equilateral triangle and thus colour purity is degraded. While some people might claim that corrective action during tube manufacture tends to eliminate this defect, Hitachi claims that these remedies are inadequate.

Hitachi are fabricating tubes to match this electron distortion rather than trying to correct the placing of the electron beam itself. The resultant tube permits components such as those used with 90° tubes to be used rather than require special deflection coils and special components.

Back to computers. Memories are very much in the news but perhaps the most interesting one is not a semiconductor memory nor a magnetic core. It is a ferroelectric one which, if researchers are right, will pack some 10<sup>13</sup> bits of information. The idea came originally from holograms. These are three-dimensional images. It was reasoned that perhaps information could be stored in three dimensions, one layer behind the other. Now comes the idea that this could be done with ferroelectric materials and the suggestion is for one called barium titanate which has been doped with impurities. The doping causes the individual crystals to become photosensitive besides being transparent. Thus they could be used to record the interference waves from a holographic image. They could easily be "read out" by using a beam of light and they can also be erased and new information "written" in. So it looks like another twist in the memories stakes with a serious competitor for the memory elements; semiconductor, hologram, plated wire, magnetic core etc.

RCA are recorded as having done some work on ferroelectric crystals but this method used a great deal of heat (some 300°C required for erasure) and there were few problems. The newer method just announced, using barium titanate, uses only an electric field for erasure and thus looks promising. Experiments, incidentally, are taking place in France.

# Would YOU pay 50 pence for a components catalogue?



## You'll be glad you did when you get THIS one!

A components catalogue is so vital to any keen constructor that it simply does not pay to make do with less than the best. True, the best may cost a little more... but it's the cheapest in the end. So invest in a Home Radio Components Catalogue, listing over 8,000 items, more than 1,500 of them illustrated. If you call at our shop the catalogue is yours for just 50 pence. If you order by post—70 pence, including postage and packing. You also get 10 Vouchers, each worth 5 pence when used as instructed—so you can get the cost of the catalogue back in any case!

**Send the Coupon today, with your cheque or P.O. for 70p.**

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

HOME RADIO (Components) LTD., Dept. PW,  
234-240 London Road, Mitcham, Surrey CR4 3HD **01-648 8422**



# practically wireless commentary by HENRY

No. 90  
Nothing  
if not  
Informative

**S**HATTERED, not a little disabused, Henry sits hunched in the corner of his workshop trying to work out where he went wrong.

No, it is not another classic case of diagnosing power supply, regulator and control circuit malfunction when the heat-fuse in the mains transformer had parted. Not a mere inability to restring a dial drive cord that goes twice round the town hall and back between tuning gang and pointer pulley. Not even, not especially, another case of reading *nano* for *micro* or *milli* for *Meg*.

Worse than that, Henry has been accused by a close colleague—nay, a collaborator—of being too literary, not factual enough. ‘People pick up PW,’ he says, ‘to be informed, not to be led through the pages of the dictionary.’

Oh dear—I plead guilt. *Mea culpa*, and all that. Verbal diarrhoea has afflicted your scribe.

There—you see? Put into plain-song, the foregoing should read: Henry talks too much, and to little effect.

‘Tis true, ‘tis true. Which is why Henry, in this lazy month between Spring and Summer, wants to acquaint you with a few of the

facts he has stumbled upon during a recent browse through the trade and enthusiast magazines.

In the April 1972 issue of *Studio Sound* there are two equipment reviews. First is of a Crown DC 300 amplifier, imported from Indiana, U.S.A. A cool 600 watts into 4 ohms, is all. Or, to be a little more realistic, 150W RMS per channel into 8 ohms. The reviewer, P. A. Lomas, had little to say about it except that it ‘exceeded specification’ for every test made. And, believe me, those specifications are very impressive, as one would expect for a bit of hardware costing £360.

What interests Henry more is the methods he used to determine how good this amplifier really was. . . . Harmonic distortion of 0.008% at 500Hz, Crosstalk at 10kHz, 95dB below full output, and noise at -113dB, forsooth!

He does report—and Henry applauds the touch of humanity—‘Short circuit tests merely produced large frightening sparks, pitted screwdrivers and a shaking hand.’

But the accompanying review was rich. It dealt with the Edison Phonograph, and could have been better if a perfectly straight-faced approach had been maintained. Instead, we read such specifications as:—Wow and Flutter: dependent on alcohol level in blood of operator. (The Phonograph is a cylindrical-scan tinfoil clad machine operated by a hand crank, or hadn’t you guessed?)

In fact, the review goes into nice detail about the construction, with diagrams, and nowhere does T. T. Wittering mention April 1. If David Kirk, the Editor of *Studio Sound*, intends to continue with the April Fool insert, as Radio-Electronics used to do (still does?), T. T. W. will have to get together with Henry Scruggs or George Izzard O’Veering and write about the Super-Crown.

On second thoughts, he need only quote from some specifications as boldly published by the



The ‘ultimate’ Hi-Fi system.

makers of system audio equipment. And if he wants more power, what about the Marantz at 250 watts, or the Phase Linear, 750 watts?

Power alone isn’t everything, as any owner of an earache generator can tell you. But it does seem to be the tendency for makers of powerful amplifiers to make, also, equipment that performs to the highest standards.

Bert Whyte’s piece in the February *Audio* talks about Joe Audiophile, in his seventh heaven because his Aunt Nelly remembered him in her will. He purchases the ‘ultimate’ hi-fi system, super megawatt amplifiers, preamps with a plethora of controls, which can be corrective or creative, digital readout tuner—naturally, Joe’s system is quadrophonic—and ultra-wide range speakers with low frequency response down in the sub-basement.

Developing his theme, Bert describes that Joe’s aim is to listen to his 15 ips copies of classical masters. ‘The first faint susurrations (sic) of Ravel’s “Daphnis and Chloe” are heard from the speakers . . . *molto pianissimo* . . . and Joe is in a transport of delight.’ no tape hiss—but then—WHUMP! RUMBLE’

Joe has been the victim of monitoring techniques. The discs made from those master tapes have been ‘rolled off rapidly’ below 60Hz.



Large frightening sparks.

So many of the components you need for PW designs are in the new 1972 Electrovalue catalogue. Bigger, better than ever—Post free—10p.

# ELECTROVALUE

## Electronic Component Specialists

### TRANSISTORS

Wide range. Up to date. Brand new—no 'seconds' or surplus. Highest quality and reliability.

No.	Type	Purpose	Price
2N697	Sil. NPN	General	18p
2N1304	Ger. NPN	"	28p
2N1305	PNP	"	28p
2N2946	Sil. UJT	Oscillator, SCR driver	47p
2N2928	NPN	Small sig. amp	11p
2N3055	NPN	High power	50p
2N3702	PNP	Low power	10p
2N3704	NPN	Low power	10p
AC126	Ger. PNP	Small sig./driver	23p
AC188	PNP	Low power	20p
AC176	NPN	Low power	16p
AD149	PNP	High power	58p
*AD181	NPN	Med. power	35p
*AD182	PNP	Med. power	35p
BC108	Sil. NPN	Small signal	11p
BC109	NPN	Low noise	12p
BC168	NPN	Small signal	10p
BC169	NPN	Low noise	11p
BF194	NPN	RF amp.	14p
BF151	NPN	Med. current	20p
OA50	Ger. diode	RF detector	6p
OA81	"	General	5p
SD1	"	Silicon Rectifier 1 amp	10p
W02	"	Silicon bridge 1 amp	30p

\*Matched pair AD181/AD182  
Sil. = Silicon. Ger. = Germanium.



### MINITRON DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available.

£2.00  
£1.36

Suitable BCD decoder driver type FLL121T  
Dil Socket: 16 lead 30p.

No. 3015G showing + or - and fig. 1 and decimal point £2.00.

### We are official distributors for SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eimco-Wolf "Solderstat" irons we offer this light weight model HMS in 16 or 24 watt, ratings 220/240V a.c. £1-87 nett

### INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON

Designed essentially for micro-miniature and printed circuit board assemblies. Temperature is adjusted as required by control on base and remains constant whether tiding or on load. Although for working to very delicate standards, the iron is of rugged construction and is exceptionally reliable. Price, complete with base, nett

£9-20

### DE-SOLDER BRAID

The efficient money saving way to de-solder solder joints. per 6 ft. length, nett

50 p

TYGAN 36" x 27" £1-58; 18" x 27" 88p,  
VYNALR 36" x 23" 93p. 15" x 25" 60p.  
(Pattern Book 3p & S.A.E.)

### RESISTORS 10%—5%—2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up
				(see note below)		
C	1/20W	5%	82-220K	E12 9	8	7
C	1/8W	5%	4.7-470K	E24 1	0.8	0.7
C	1/4W	10%	4.7-10M	E12 1	0.8	0.7
C	1/2W	5%	4.7-10M	E24 1-2	1	0.9
C	1W	5%	4.7-10M	E12 2-5	2	1.8
MO	1/2W	2%	10-1M	E24 4	3	2 nett
WW	1W	10%	0.22-3.9	E12 7	7	6
			+1/20Ω			
WW	3W	5%	10Ω-10K	E12 7	7	6
WW	7W	5%	10Ω-10K	E12 9	9	8


Codes: C = carbon film high stability low noise  
MO = metal oxide Electrosl TR5 ultra low noise  
WW = wire wound Plessey

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 = an E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 82, 91 and their decades. Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p on total value of resistor order).

### RIVLIN PRECISION RESISTORS

0-1% to 0-01% tolerance. Prices and delivery details on request. Example—values up to 100K, between £1 and £2 nett.

### SLIDE POTENTIOMETERS

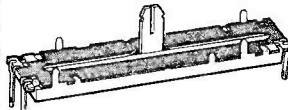

Robust construction, smooth silent action. In values from 47K to 1 megohm, linear or log, each 50p.  
Knobs flat, grip type in black/Red/Green/Yellow/Blue/Lt. Grey/Dark Grey or White each 5p.

### SIEMENS TTL INTEGRATED CIRCUITS

FLH101 (7400)	20p	FLJ121 (7473)	45p
FLH201 (7401)	20p	FLJ141 (7474)	45p
FLH191 (7402)	20p	FLJ151 (7475)	45p
FLH291 (7403)	20p	FLJ181 (7476)	45p
FLH211 (7404)	25p	FLH221 (7480)	68p
FLH271 (7405)	25p	FLH231 (7482)	87p
FLH381 (7408)	25p	FLH241 (7483)	132p
FLH391 (7409)	25p	FLH341 (7486)	33p
FLH111 (7410)	20p	FLJ161 (7490)	80p
FLH351 (7413)	35p	FLJ221 (7491)	AN
FLH121 (7420)	20p	FLJ171 (7492)	85p
FLH131 (7430)	20p	FLJ181 (7493)	80p
FLH141 (7440)	24p	FLJ231 (7494)	132p
FLH101 (7414)	132p	FLJ191 (7495)	87p
FLH281 (7442)	1-16	FLJ261 (7496)	1-48
FLH361 (7443)	1-45	FLJ301 (74100)	1-64
FLH371 (7444)	1-45	FLJ281 (74104)	43p
FLH251 (7450)	20p	FLJ271 (74107)	62p
FLH161 (7451)	20p	FLK101 (74121)	48p
FLH171 (7452)	20p	FLJ201 (74190)	1-80
FLY101 (7465)	20p	FLJ211 (74191)	1-80
FLJ101 (7470)	45p	FLJ241 (74192)	1-74
FLJ111 (7472)	32p	FLJ251 (74193)	1-74

### BAXANDALL SPEAKER

As designed by P. J. Baxandall and originally described in "Wireless World". Complete kit inc. spkr. equaliser and special cabinet kit (18" x 12" x 10") cut to size. 10 watt RMS/15Ω loading. Carr. free in U.K. Nett

£31.81

Speaker unit and equaliser kit with instructions £4.81. Pack flat cabinet assembly (all cut to shape) natural teak finish £9.00.

### MISCELLANEOUS

**CARBON SKELETON PRE-SETS**  
Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

**ZENER DIODES** 5% full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 76V, 45p each.  
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

**MINIATURE TOGGLE SWITCHES**  
2A/250V, DP/DT, 45p.

**MAIN LINE AMPLIFIER KITS**

70 watt power amp. module kit, £12-60 nett. Power supply kit, £8-00 nett. Matching pre-amp kit, £3-30 nett. (Above prices for mono.) Stereo Kit, 2 power amps, pre-amp kit, power supply kit and matched controls for building your own cabinet, £38-40 nett.

### SIEMENS CAPACITORS

#### POLYCARBONATE—5% TOLERANCE

250V, up to 0.1μF: 100V/0.1μF and above  
0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056 each 3p.  
0-068; 0-082; 0-1; 0-12; 0-15 each 4p.  
0-18; 0-22; each 5p.  
0-27; 0-33; 6p; 0-39 7p; 0-47 8p; 0-56 10p; 0-68 11p; 1μF 13p.

**ELECTROLYTIC CAPACITORS** (values in μF/V)  
0-47/100; 1/100; 2-2/63; 4-7/35; 10/25; 22/16; 47/10; 100/10; 220/5—each 5p.  
10/63; 22/35; 47/35; 100/16; 100/25; 220/6; 220/10; 220/16; 470/5 each 6p.  
47/50; 47/63; 100/35; 470/10 each 7p.  
100/50; 220/35; each 9p; 100/63; 470/25; 100/10 each 10p.  
220/63; 470/35; 1000/16; each 14p.  
1000/25—16p; 470/63; 1000/35 each 18p; 2000/200—28p.  
1000/63; 2-200/35; 4-700/16—each 33p.  
Tantalum and other capacitors etc.—see latest 1972 Catalogue—Issue No. 6.

## 1972 ELECTROVALUE CATALOGUE (NO.6)

Now enlarged to 96 pages plus cover. More items, more information, more diagrams than ever. Post free—10p.

### NEWMARKET LINEAR I.C.s

LIC 709C/14 Dual in line—84p.  
LIC 741C/14 Dual in line—40p  
T05 version also available

### CARBON TRACK POTENTIOMETERS

long spindles. Double wipers for low noise.  
**SINGLE GANG** linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7KΩ to 2.2MΩ, 15p; Dual gang linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 22K, 47K, 1MΩ only 42p. Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.  
Only decades of 10, 22 & 47 available in ranges quoted. **DUAL CONCENTRIC** in any combination of above values, 60p; with switch, 72p.

### DISCOUNTS

10% on orders £5 to £15.  
15% on orders over £15. No discount on items marked Nett. Prices subject to alteration without notice.

### POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders: carr. & insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

# ELECTROVALUE

(Dept. P.W. 672) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 OHB  
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475  
ELECTROVALUE—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT IN 1965



# Shoptertunities save you £££'s and £££'s

## RUSSIAN WORLD BEATER!

**JUST ARRIVED!**

THE FABULOUS  
**BRAND NEW**  
**VEF 204**

**THIS OFFER ONLY FROM US!**

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

**8 WAVEBAND**  
10 TRANSISTOR PLUS 2 DIODES  
PORTABLE RADIO

AND "SHIP-TO-SHORE"  
NOW WITH MARINE BAND

NOT JUST A RADIO BUT A TECHNOLOGICAL MAGIC!

BATTERY MODEL **£13.97**

MAINS/BATTERY ELIMINATOR **£1.48p** Extra

WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

\*COMPARE IT'S PERFORMANCE WITH **£42 RADIOS!**

**IMPORTANT: THIS VERY LATEST MODEL INCORPORATES ALL THE LATEST TECHNOLOGICAL IMPROVEMENTS AND SUPERSEDES ALL EARLIER MODELS: DESIGNED FOR WORLDWIDE RECEPTION**—it'll probably make your present radio seem like "crystal set"! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore. We're almost giving them away at only **£13.97**—a fraction of today's Russian miracle price! Compare performance with **£42 radios!** \*Refund if not astounded. Furer and sweeter tone than ever! Wider band spread for "pinpoint" station selection. The Russians have really surpassed themselves this time, proving again their ability in the field of space communications. Yes, 8 separate wavebands, including standard Long, Medium and Short Waves to cover the world. PLUS special "ship-to-shore" MARINE BAND! Thousands of different transmissions and stations, including ships at sea, etc., and messages from all over the world. You must hear it to believe it! Superb sweet tone—from a whisper to a roar! Push-pull output! Separate ON/OFF volume & Treble/Bass tone controls! Press button dial illumination! Take it anywhere—runs on standard batteries or through battery eliminator from 220/240V. AC mains. Internal ferrite rod plus telescopic aerial. It's also a fabulous **CAR RADIO!** Black & Chrome case, 11in. x 9in. x 3 1/2in. overall approx. Made to give years of service. **WRITTEN G'TEE**, manual with instructions & circuit diagram. **ONLY £13.97** (with mains/battery eliminator £1.48 extra). **POST 50p**. Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. (SOBRY—we cannot exchange these radios for any earlier model already purchased!) **NOTE**—The Ministry of Posts & Telecommunications has pointed out that a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

## SAVE £20.25 NOW!

**THIS FANTASTIC OFFER ONLY FROM US!**

fabulous BRAND NEW

**SOLID STATE**

This equipment's got EVERYTHING!

**BATTERY/MAINS AC**

**Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**



WITH REMOTE CONTROL MICROPHONE

**OUR PRICE £23.75** CARR. ETC. 35p

**FANTASTIC** (even by our standards!) Brand new—the latest sensation in the world of sound! First class makers! Not only a fabulous VHF AM/FM Radio AND Cassette Tape Recorder and Player combined, but it also runs off standard batteries or mains (simply plug in 220/240V a.c. line cord). Now you can record and play back anything, anywhere! You can even tape direct from the Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44 YET WE OFFER AT ALMOST HALF PRICE!** Just look at these wonderful features:—"Press-button Keyboard Control panel or latest MASTER SWITCH CONTROL "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic leveller! \*Separate ON/OFF, and HI-LO volume controls! Heavy duty built-in speaker! \*Earphone (for personal listening or "monitoring") and extension speaker! \*socket! \*Remote control microphone! \*Built-in swivel telescopic extension aerial (24in approx)! Magnificently made case, with carry handle (DESIGNS VARY SLIGHTLY). Takes standard 30, 60, 90 or 120 minute Philips Cassette Tapes obtainable everywhere. But wait, the amazing built-in full circuit VHF AM/FM Radio gives you superb clarity of tone and incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC National VHF. Picks up dozens of foreign stations. Also fabulous in your car! You can pay £££'s more for a Car Radio or Car Cassette Player ALONE! **ONLY £23.75**, carr. etc. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE. BONUS OFFER—Standard Batteries and Cassette Tape 25p extra if required. Send quickly or call.**

## MOTORING SENSATION! SAVE £24 NOW!

**Complete 8-TRACK CAR STEREO SYSTEM**

Yes! **superb CARTRIDGE CASSETTE PLAYER!** Plus **TWO MATCHED SPEAKERS!** Plus **ALL CONNECTIONS and FITTINGS!**

**LIST PRICE £39.97! ONLY £15.97 CARR. ETC 33p**

**SHOPERTUNITIES LTD. SL**

**ASTRONOMICAL REDUCTION!** Frustrated import order must be turned into cash! Brand New, from first class makers—we must not mention name! Absolutely the ultimate in luxury car equipment! The sort of offer that you can only dream about, but **THIS** is true! Yes, for the incredible price of **£15.97** carr., etc. 33p, you can have this magnificent complete 8-track stereo system. Superb Cartridge cassette player beautifully made—no compact, overall size 8 1/2in. x 6 1/2in. x 2 1/2in. approx. for easy mounting in any car, boat or truck—or even in the home. (Runs off 12v battery.) Just "snap-in" a Cartridge cassette (takes all standard 8-track Cartridge cassettes—gives hours of continuous playing) and experience rich true-fidelity stereo sound! Autopilot, automatic track changer plus manual programme selector. Separate thumbwheel volume and treble/bass tone controls, sliding balance control. Outstanding 80-10,000 c/s frequency response! Circuit—10Tr. OTL system! Playback system—8-track 4 channel! Speaker impedance—4-8 ohms each channel! Output power—3 watts (2.5 watts per channel). Plus 2 compact matched stereo speakers, each 4 1/2in. diam. approx. plus all leads, connections, fittings, etc. Designed for fast, easy mounting. With simple instructions. **WRITTEN GUARANTEE. Yes, everything for £15.97** carr., etc. 33p but please hurry—limited stock only! Refund G'tee. **ADDITIONAL STOP PRESS OFFER. Super Deluxe with FAST FORWARD and automatic track changer INDICATOR—only 22 extra.**

Dept. WP/19, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.). BOTH STORES OPEN FROM MONDAY TO SATURDAY 9 a.m.—6 p.m.

## poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction permits new installation ideas.

Power capability: 20 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1 7/16" x 1 3/4" x 1 11/16". Weight: 19 ounces.


£6.50 each Stereo pair £12.50 post free

**web europa**

P.O. Box 162, Watford WD1 1AA

## WILSIC SOUND EFFECTS KITS

**WAH-WAH PEDAL KIT (illustrated)**

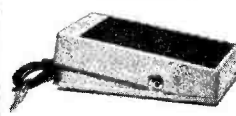


Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13, COMPLETE KIT £6.50 add 38p for assembly of module, but please note we cannot supply kits fully built.

**REVERBERATION UNIT KIT.** For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9.50 (excluding case £7.50). Assembled and tested £12.50. **VIBRATO UNIT KIT.** Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5.25.

SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

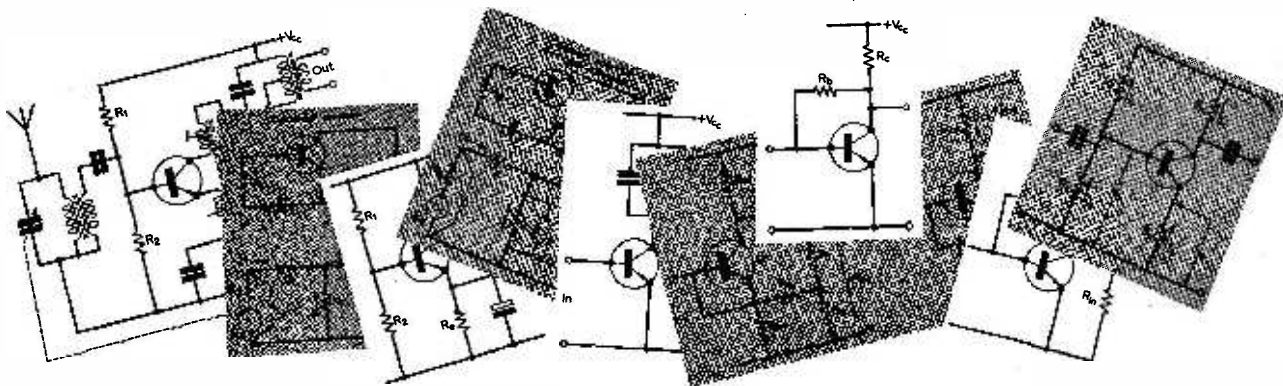LATEST CATALOGUE 5p (stamps)  
**WILSIC ELECTRONICS LTD.**  
6 COPLEY ROAD, DONCASTER, YORKS.



# TRANSISTOR CIRCUITRY for beginners

H.W. HELLYER & MICHAEL HOLLIER

## PART 8

### Buffer links

It has become obvious in recent months, from the polite noises made over the editorial hot-line, and correspondence we have received, that our chosen method of dealing with simple transistor circuitry meets with some approval.

Simplicity can be deceptive. This month, for instance, we have chosen as our subject a single-transistor collector-follower circuit. One transistor, a few components, a little bit of board, and a few moments of your time. But if we were to cover, fully, all the parameters affecting the calculated performance of this 'simple' circuit, half the adverts would be squeezed out of *PW*. More important, such an approach would frighten off the beginner—and he's the chap at whom this series was aimed, remember?

The buffer-link can be used between two pieces of equipment when discrepancies of impedance and voltage are such that gain as well as matching is needed. A typical example is the case of the tape recorder connected to the 'Tape' outlet of a radio-gramophone. Quite often, specifications make it appear that the simple connecting lead will do the job adequately. The significant point omitted from those specifications (or, at best, skated over), is that the impedance of the load drastically affects the available signal voltage from the radiogram. A glance at Fig. 39 shows why this should be.

To prevent the load (i.e., the tape recorder) from robbing the main equipment of some signal voltage and to save the extra cost of a properly designed feed stage, such as we have already described, a fairly high resistor is used to connect the signal take-off point to the socket.

If a direct connection is now made to the socket, the relatively low impedance of the tape recorder will not affect the performance of the radiogram. But, and it's a big but, a potential divider is now formed, with the smaller resistance section being the tape recorder, so the available voltage is reduced in proportion to the two resistors.

If there is not enough voltage available, we are not going to be able to make a decent recording. No amount of ingenuity with external resistive networks will produce sufficient modulation. What we need is a little amplifier between the radiogram and the tape recorder. We need, in fact, a buffer to prevent interaction of one upon the other and a link to join their circuits together—a buffer-link.

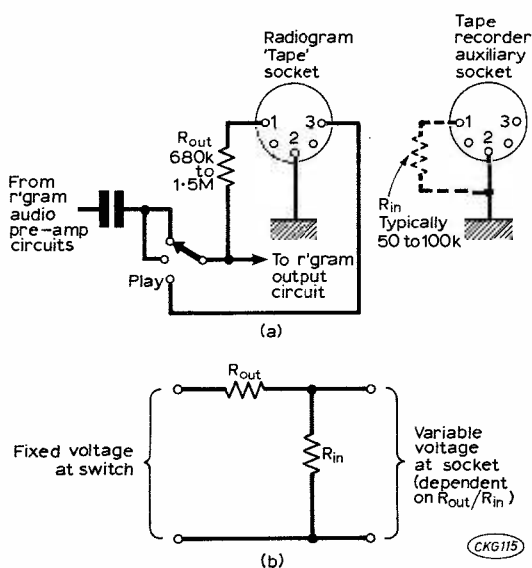


Fig. 39. (a) A single channel of a typical radiogram 'tape' outlet showing the presence of  $R_{out}$  which affects the matching. (b) is the equivalent of (a).

### Simple circuit

Emitter-follower circuits make excellent buffers, but do not allow us to obtain any voltage improvement. A two-stage circuit would do the trick, maybe; like the Darlington Pair of Part 6; or even more elaborate circuitry, like the single-double device of Part 7. Here, we can obtain the gain we require and make a suitable match with the very simple circuit of Fig. 40.

This is the single-transistor collector follower stage. If you have read Part 5, page 913, it should

not be necessary for me to explain those terms. Such a stage has a medium impedance input, certainly lower than the emitter follower we previously discussed, but still not too low for our purpose. It has a fairly high output impedance, but again, not too high for our purpose. Component changes can modify the performance to suit our requirements, as we shall show. Voltage gain is quite reasonable, and the signal inverts  $180^\circ$  between input and output. All these are conditions that we want.

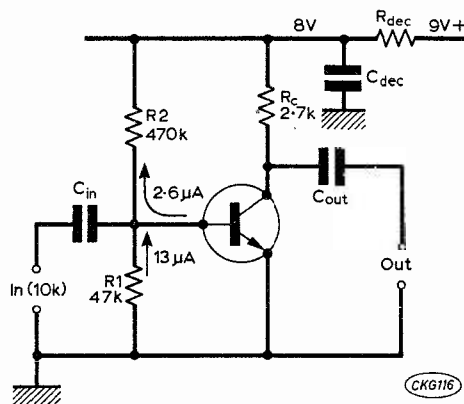


Fig. 40. Basic buffer-link circuit. Essentially a collector-follower the emitter is taken directly to the negative line.

R1 and R2 form the potential divider to give us base bias, just as we have seen in previous months.  $R_c$  is the collector load resistor, and this time, our a.c. signal is developed across this load. The emitter in our first example is taken directly to chassis.

The input signal to the base is coupled by  $C_{in}$ , with  $C_{out}$  performing its coupling function at the other end of the stage, taking the signal to the input of the tape recorder.

## Recap

Recapping a little: previous dealings with the emitter follower and Darlington circuits have taught us that the output signal is a little less than the signal voltage fed in to the circuit. In technical terms, the gain is less than unity. This time, we have acquired a bit of gain, and the price we pay is an input impedance lower than before, and an output impedance higher than before. In addition, we now have a phase inversion, which the emitter follower did not have. A signal at the input of the stage is inverted, i.e., receives a phase change of  $180^\circ$ . If the input signal is positive-going, the output signal will be negative-going. This doesn't much matter to us in our present application, but can be quite important for some applications.

On the subject of impedance, the terms high, low and medium are, of course, only relative. Impedance is the resistance to an a.c. signal, usually at a specified frequency. Where no frequency is specified, as in the case of an amplifier, it is assumed that the impedance is constant over the frequency range of interest: example, 20Hz to 20kHz. A reference frequency of 1kHz is generally assumed, except in the case of microphones and loudspeakers, when 400Hz is more often employed. In general, an a.c. resistance of  $1k\Omega$  and below would be called low, up to  $100k\Omega$  would be medium and above  $100k\Omega$  referred to as 'high impedance'.

## Circuit details

We should begin with some modest requirements, bearing in mind that a wide variation of performance can be expected with certain circuit changes. Battery supply—again 9 volts, allowing for 1 volt being dropped across the decoupling resistor, so the stage supply  $V_{cc}$  is 8V. The collector current we shall choose is 1mA. And with these simple starters we can choose a transistor.

Our choice is determined by the need more for low noise than high gain, although it is nice to have both. So, to get the best of both worlds, back to old faithful, BC109. Referring to Figs 41 and 42, we can work out the more detailed figures.

The transistor will be operating at a collector current of 1mA, and the voltage between collector and emitter,  $V_{CE}$ , will be about 5 volts. (Refer to previous articles in this series for reasons for these quoted figures—an expansion of the argument). From Fig. 41, we can see that the a.c. current gain,  $h_{fe}$ , can be determined at somewhere around 450. Similarly, from Fig. 42, we find that the d.c. current gain,  $h_{FE}$ , is around 380.

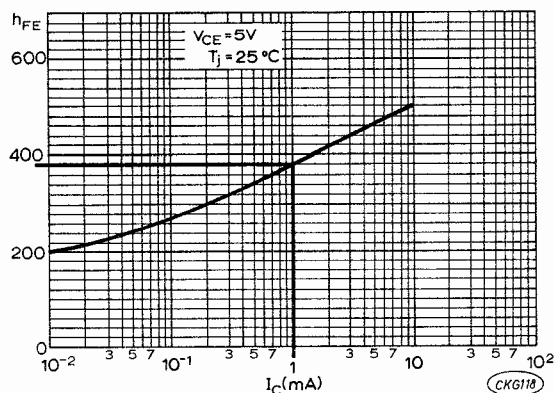
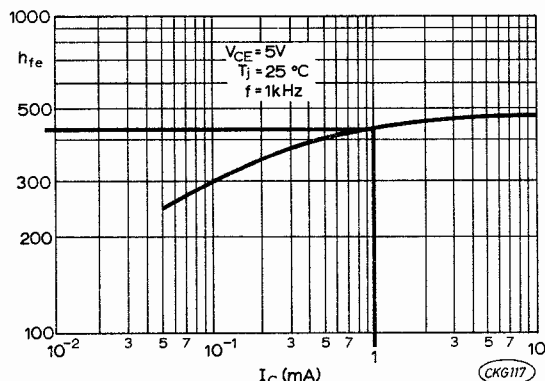


Fig. 41. (top) Graph to determine  $h_{fe}$ , the a.c. current gain. Fig. 42 (bottom) is the graph to find the d.c. current gain  $h_{FE}$ .

The base current of the transistor is determined by the formula:

$$I_b = \frac{I_c}{h_{FE}}$$

We have determined  $h_{FE}$  and the  $I_c$  we chose, for best conditions and easy working, to be 1mA. Putting these figures in the above formula, we arrive at the conclusion  $I_b = 2.6 \mu A$ .

**HENRY'S** FOR LOW COST **FIRST GRADE BRAND NEW** **BRANDED** GERMANIUM AND SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES AND INTEGRATED CIRCUITS  
BY ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS

## TRANSISTORS

A SELECTION FROM OUR LIST

AAV30 10p	BD115 75p	OC16 50p	2N1303 18p
AAV42 15p	BD123 85p	OC20 85p	2N1304 22p
AAV15 10p	BD131 75p	OC22 80p	2N1305 22p
AAV17 10p	BD132 80p	OC24 80p	2N1306 25p
AC107 35p	BDY11 1.50	OC25 40p	2N1307 25p
AC126 30p	BDY17 1.50	OC26 25p	2N1308 25p
AC127 25p	BDY36 55p	OC28 60p	2N1309 25p
AC127Z 50p	BDY60 1.00	OC29 60p	2N1613 20p
AC128 20p		OC35 60p	2N2147 75p
AC176 20p		OC39 60p	2N2160 60p
AC187 25p		OC42 40p	2N2217 20p
AC188 25p		OC48 50p	2N2218 20p
ACV17 30p	BF115 25p	OC44 15p	2N2219A 20p
ACV18 30p	BF154 25p	OC45 12p	
ACV19 25p	BF158 15p	OC70 12p	2N2219 20p
ACV20 20p	BF199 35p	OC71 12p	2N2220 25p
ACV21 20p	BF180 35p	OC72 20p	2N2221 20p
ACV22 10p	BF194 15p	OC75 25p	2N2222 20p
ACV23 55p	BF195 15p	OC76 25p	2N2223 20p
ACV40 20p	BF196 15p	OC77 40p	2N2224 20p
ACV41 15p	BF197 15p	OC81 20p	2N2225 25p
ACV44 25p	BF213 25p	OC82 20p	2N2226 20p
AD140 50p	BFX29 25p	OC83 25p	2N2227 20p
AD149 50p	BFX30 25p	OC83 25p	2N2228 20p
AD161 35p	BFX84 25p	OC84 25p	2N2269 15p
AD162 35p	BFX85 25p	OC139 25p	2N2269A 15p
AF114 25p	BFX86 25p	OC140 40p	2N2645 15p
AF115 25p	BFX87 25p	OC141 40p	2N2646 15p
AF116 25p	BFX88 25p	OC170 25p	2N2904 20p
AF117 20p	BFY18 25p	OC171 30p	2N2904A 20p
AF118 20p	BFY50 20p	OC200 40p	
AF124 25p	BFY51 20p	OC201 75p	2N2905 25p
AF125 25p	BFY52 20p	OC202 80p	2N2905A 25p
AF126 20p	BFY53 20p	OC206 60p	
AF127 20p	BFY90 65p	OCF71 97p	2N2906 20p
AF129 30p	BRX20 15p	ORP12 50p	2N2906A 20p
AF180 50p	BRX21 20p	ORP60 40p	
AF181 45p	BRX27 15p	ST140 15p	2N2907 25p
AF185 50p	BS705A 12p	ST141 20p	2N2907A 25p
AF186 40p	BT108 45p	TIP30A 80p	2N2925 25p
AF289 40p	BU105 42.25p	TIP30A 80p	2N2926 10p
ASV26 25p	BY100 15p	TIP31A 60p	2N3011 20p
ASV27 25p	BY126 12p	TIP32A 70p	2N3011 20p
ASV28 25p	BY124 15p	TIP33A 80p	2N3033 20p
ASV29 30p	BY192 80p		2N3054 50p
ASV31 30p	BY193 80p		2N3055 75p
BA100 15p	BY211 30p	TIP34A 1.50	2N3525 75p
BA102 30p	BY212 30p	TIS43 40p	
BA110 25p	BY213 25p	TIS50 12p	2N3614 55p
BA115 7p	BZY781-90 15p	TIS51 10p	2N3702 10p
BA118 5p	GET103 35p	TIS52 10p	2N3703 10p
BA118 7p	GET104 35p	TIS53 10p	2N3704 10p
BA131 7p	GET111 45p	TIS61 20p	2N3705 10p
BA138 15p	GET112 35p	TIS62 20p	2N3707 12p
BC107 10p	GET114 20p	V405A 25p	2N3708 10p
BC108 10p	GET115 50p	V405B 25p	2N3714
BC109 10p	GET116 55p	W01 30p	
BC109G 12p	GET117 55p	W06 20p	2N3715 22.00
BC113 10p	GET182 20p	ZTX107 15p	2N3716 22.00
BC114 20p	GET183 20p	ZTX108 12p	2N3716 22.00
BC115 20p	GET184 20p	ZTX109 15p	2N3716 22.00
BC116 20p	GET185 20p	ZTX110 15p	2N3716 22.00
BC116A 25p	GM378A 55p	ZTX301 15p	2N3717 22.00
BC117 20p	MAT101 25p	ZTX302 20p	2N3717 22.00
BC117 20p	MAT121 25p	ZTX303 20p	2N3717 22.00
BC118 20p	MC724F 60p	ZTX304 20p	2N3717 22.00
BC119 30p	MJ420 80p	ZTX305 20p	2N3717 22.00
BC134 20p	MJ421 80p	ZTX500 15p	2N3717 22.00
BC135 15p	MJ2801 1.10	ZTX501 15p	2N3717 22.00
BC136 20p		ZTX502 20p	2N3717 22.00
BC137 20p	MJ2901 1.10	ZTX503 17p	2N3717 22.00
BC138 20p		ZTX504 40p	2N3717 22.00
BC147 12p	MJE340 50p	ZTX531 20p	2N3717 22.00
BC148 10p	MJE370 20p	IN914 7p	2N3824 95p
BC149 10p	MJE417 80p	IN918 10p	2N3824 95p
BC153 20p	MJE520 75p	IN918 10p	2N3824 95p
BC154 20p	MJE521 70p	IS44 7p	2N4058 12p
BC167 15p	MJE2855 18921 7p	IN2091 12p	2N4058 12p
BC168 12p		IN2092 12p	2N4058 12p
BC169 12p		IN2093 12p	2N4058 12p
BC177 20p	MJE3055 36301 25p	IN2094 12p	2N4058 12p
BC178 20p	MPSA06 25p	IN2095 12p	2N4058 12p
BC179 20p	MPSA06 25p	IN2096 12p	2N4058 12p
BC182L 10p	MPSA07 15p	IN2097 12p	2N4058 12p
BC183L 10p	MPSA08 15p	IN2098 12p	2N4058 12p
BC184L 12p	MPSA09 55p	IN2099 12p	2N4058 12p
BC212L 12p	MPSA10 55p	IN2100 12p	2N4058 12p
BC213L 12p	NKT216 35p	IN2101 12p	2N4058 12p
BC214L 15p	NKT403 75p	IN2102 12p	2N4058 12p
BCY30 35p	NKT404 55p	IN2103 12p	2N4058 12p
BCY31 40p	OA5 25p	IN2104 12p	2N4058 12p
BCY32 60p	OA10 25p	IN2105 12p	2N4058 12p
BCY33 30p	OA17 10p	IN2106 12p	2N4058 12p
BCY34 35p	OA70 10p	IN2107 12p	2N4058 12p
BCY38 40p	OA79 10p	IN2108 12p	2N4058 12p
BCY39 40p	OA81 8p	IN2109 12p	2N4058 12p
BCY40 50p	OA80 8p	IN2110 12p	2N4058 12p
BCY70 15p	OA85 7p	IN2111 25p	40594 21.05
BCY71 20p	OA90 7p	IN2112 25p	40594 21.05
BCY72 15p	OA200 7p	IN2113 25p	40594 21.05
	OA202 10p	IN2114 25p	40594 21.05

## HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES  
BRANDED FAIRCHILD, I.T.T. AND TEXAS  
DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quadruple 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	14p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7404	Hexuple Inverters	20p	18p	14p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	14p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	14p	14p	12p
7413	Dual 4-input Schmitt triggers	20p	27p	25p	22p	20p
7420	Dual 4-input NAND gates	20p	18p	14p	14p	12p
7421	Single 3-input NAND gates	20p	18p	14p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	14p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	72p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7443	Excess 3-Decimal decoder/TTL outputs	1.00	85p	80p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	1.75	1.00	1.45	1.30	1.15
7448	BCD-Decimal 7 seg. decoder/indicator driver	1.75	1.00	1.45	1.30	1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7460	Dual 4-input expanders	20p	18p	14p	14p	12p
7470	Single J-K flip-flop (gated inputs)	20p	27p	25p	22p	20p
7472	Single J-K flip-flop (gated inputs)	20p	27p	25p	22p	20p
7473	Dual J-K flip-flop	40p	37p	35p	33p	30p
7474	Dual J-K flip-flop	40p	37p	35p	33p	30p
7475	Quadruple bistable latch	45p	42p	40p	38p	35p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	34p	31p	28p
7480	Gated Full Adder	80p	72p	67p	59p	55p
7481	16-bit read/write memory	1.05	1.15	1.10	1.00	0.90
7482	2-bit binary Full Adder	87p	80p	70p	65p	60p
7483	4-bit binary Full Adder	1.00	90p	85p	80p	73p
7484	16-bit RAN with gated write inputs	90p	85p	80p	75p	71p
7486	Quadruple 2-input Exclusive OR gates	45p	41p	38p	35p	33p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	1.00	90p	85p	80p	73p
7492	Divide twelve counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual entry 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	8-bit parallel/serial in/out shift register	1.00	90p	85p	80p	73p
74100	8-bit bistable latch	1.00	90p	85p	80p	73p
74118	Hexuple Set-Reset latches	1.00	95p	80p	75p	70p
74121	Monostable multivibrators	80p	55p	50p	46p	41p
74141	BCD-Decimal decoder/Nixie driver	1.00	85p	80p	80p	70p
74145	BCD-Decimal decoder (1-4-line) TTL O/P	1.50	1.40	1.30	1.10	1.00
74150	16-bit data selector/multiplexer	23.25	23.20	22.25	22.15	22.05
74151	8-bit data selector/multiplexer	1.10	80p	80p	80p	80p
74153	Dual 4-line to 1-line data selector/multiplexer	1.35	1.27	1.20	1.15	1.10
74154	16-bit decoder/demultiplexer	22.00	1.75	1.55	1.30	1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.10	1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.10	1.05
74190	Sync decade up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74191	Sync 4-bit up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74192	Sync decade up-down counter, 2-line mode	22.00	1.90	1.80	1.65	1.55
74193	Sync 4-bit up-down counter, 2-line mode	22.00	1.90	1.80	1.60	1.40
74198	Asynchronous presettable decade counter	1.50	1.40	1.30	1.10	1.00
74197	Asynchronous presettable 4-bit binary counter	1.50	1.40	1.30	1.10	1.00

Complete data on the above in booklet 20 pages. Ref. 24, issue 2 at 15p post paid.  
Texas I.C. Handbook. Complete information on 100 types. 40p. Post 10p.  
Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

### INTEGRATED CIRCUITS

MFC4001	55p
MFC4010P	80p
IC12	22.50
PA246	1.50
TAD100	1.50
TAD110	1.50
MC741P	55p
702C (TOS)	75p
708C (TOS)	45p
708C (D.I.L.)	45p
723C(TOS)	1.00
741C(TOS)	80p
MC1803P	22.00
MC1304P	22.25
SL403D	1.50
741C(DIL)	75p
914(TOS)	40p
923(TOS)	40p
TO81BA	40p
20 watt amp.	44.47
TO81BA	40p
Pre amp	1.50

### PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier SL403D

Complete with 6-page booklet, circuits and data  
**£1.50**

### ZENER DIODES

	1	25	100	500	1000
400m/w					
BZY 88					
series*	12p	10p	8p	7p	6p
1 1/2 watt					
25p	23p	20p	17p	15p	
3 watt					
30p	27p	25p	22p	20p	
10 watt					
25 series					
+40p	37p	35p	30p	25p	
All types are 5% W. Indented + these					
Stud. in voltages 3.3-100 volt in all					
standard values. *3-33 volt.					

### TRIACS

TRIACS			
Stud with accessories		P.I.	Current 1-11
Type	volts		
SC35A	100	3 amps	80p
SC36B	200	3 amps	85p
SC35D	400	3 amps	90p
SC40A	100	6 amps	90p
SC40B	200	6 amps	1.05
SC40D	400	6 amps	1.00
SC45A	100	10 amps	1.05
SC45B	200	10 amps	1.15
SC45D	400	10 amps	1.25
SC50A	100	15 amps	1.35
SC50B	200	15 amps	1.45
SC50D	400	15 amps	1.75
SC40E	500	6 amps	1.25
SC46E	500	10 amps	1.45
SC50E	500	15 amps	1.95
DIAC	SD2		25p

# WICKS FOR BARGAINS

## ELAC SPEAKERS

8N 8" Round  
£3.50. P. & P. 25p.  
TW4/16 3" Tweeter  
£1.00. P. & P. 20p.

## Special Offer!

Grundig GDM312  
Dynamic Micro-  
phones. List £7.35  
OUR PRICE £3.  
P & P 30p

## Hi-Fi Stereo Headphones

(Value £5.00)  
Only £2.25 inc. post.

## Speaker Cloth

Best quality. Width  
36". Under half price at  
55p per yd. Black with  
silver fleck, will blend  
with any room setting.  
End of stock line, yds  
and yds must go.  
Send S.A.E. for  
other samples.

## Plugs, Sockets and Leads.

Phono plugs: 3p each  
30p per dozen.  
2 pin Din spkr. plugs  
15p each.  
3 pin Din plugs.  
15p each  
5 pin Din plugs.  
15p each.  
5 pin Din sockets  
(chassis) 7p each.  
Stereo Jack Sockets  
c/cct. 13p each.  
Phono sockets  
(chassis) 2 way 3p; 3  
way 4p; 4 way 5p.  
6ft. stereo lead 5 pin  
Din to open end. 45p  
6ft. stereo lead 2  
phono to open end. 37p  
12ft. spkr. lead 2 pin  
Din to open end. 40p.  
Please add P & P 5p.

## 100 Mixed Resistors

1 watt 10% all best  
quality (no ex govern-  
ment) 40p.

## Pots

100K x 100K Ilns & Logs.  
stereo. 35p inc. post.  
100K DP switch stereo,  
log. 45p inc. post.  
50K single Balance.  
15p inc. post.

## 4 B.A. brass nuts

50 for 25p inc. post.

## E.A. STEREO AMPLIFIER:

All transistor. 5 watts per channel; In attractive  
teak veneered sleeve. Frequency response  
40-20,000 Hz  $\pm$  3dB. Controls: On-off volume;  
Bass: Treble; Balance; Selector: Headphone  
Jack. Ceramic or Magnetic PU. Radio and  
Tape inputs: Tape output and 8 ohm speaker  
output. Fully guaranteed 12 months parts.  
6 months free service. Size 14 1/2"W x 9 1/2"D x 4 1/2"H  
approx.  
£16.50 inc. post.

## 2 WAY SPEAKER SYSTEM:

Ideal for use with above amplifier. 8" twin cone  
Bass speaker and 3" tweeter, fitted in extremely  
elegant teak veneered cabinet. Size: 16 1/2"H x  
10 1/2"W x 9"D. 8 ohms handle 10 watts.  
£7.50 each inc. Carr.

## STEREO PACKAGE DEAL

E.A. Stereo Amplifier with pair of 2-way  
Speaker Systems (detailed above) plus Garrard  
2025TC with stereo cartridge, teak plinth and  
cover and all leads and plugs.

ONLY £44.00. CARR. PAID.

## GARRARD OFFERS

Garrard SP25 Mk III (Rec. Price £15.85)  
Our Price £11.25 Carr. 50p.

Garrard SP25 Mk III ready wired in beautiful  
teak plinth with tinted perspex cover. (Fitted  
with 5-pin DIN plug or phono plugs—state  
choice). (Rec. Price £23.19). Our Price £16.  
Carr. 75p.

Or with choice of fitted cartridges.

SP25 Mk III/Sonotone 9TAHC (Rec. Price  
£27.29) Our Price £18. Carr. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31.02)  
Our Price £26. Carr. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36.19)  
Our Price £21. Carr. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36.16)  
Our Price £21. Carr. & Ins. 75p.

Note! Garrard SL65B (Automatic Changer  
version of SP25 Mk III) alternatively supplied—  
please add £3 to above prices.

Garrard AP76 (Rec. Price £27.85)  
Our Price £19.85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak  
plinth with perspex cover (fitted with 5 pin  
DIN or Phono plugs). Please state choice.  
(Rec. Price £39.85). Our Price £23.94  
Carr. & Ins. 75p.

## OR WITH CHOICE OF FITTED CARTRIDGES.

Garrard AP76/Shure M3D (Rec. Price £47.26)  
Our Price £29.94. Carr. & Ins. 75p.

Garrard AP76/Shure M55E (Rec. Price £52.82).  
Our Price £32.35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52.82)  
Our Price £32.35. Carr. & Ins. 75p.

Garrard 2025TC fitted with stereo/mono  
cartridge. £8.99. Carr. Paid.

## TEAK PLINTH & PERSPEX COVER

Ready cut to take 2025TC. SP25 III, SL65B  
available at £4.99. Carr. & Ins. 35p.

## STEREO DIAMOND CARTRIDGES

SHURE M3DM £5.00; M44-7 £6.97; M44E £7.50;  
M55E £9.50; M75EJ £16.00

SONOTONE 9TAHCD £1.99

GOLDRING 850 £5.50; 800 £9.00; 800E £12.50;  
800 SUPER £16.65.

P. & P. 18p any type.

## SPECIAL PURCHASE! GRUNDIG HI-FI TAPE IN LIBRARY BOXES

GL15. 5 1/2" LP 1200 ft.

(Rec. Price £1.97)

OUR PRICE £1.25. Post 16p  
(3 or more post free)

● Guaranteed all brand new best quality goods.

● All enquiries SAE please.

**D. T. WICKS & CO.** 49 North Station Rd,  
Colchester, Essex.

Tel: (0206) 78807

CALLERS WELCOME—Monday-Saturday—9 a.m. to 1 p.m., 2.15 p.m. to  
6 p.m., Thursdays, 9 a.m. to 1 p.m.

# LOWE ELECTRONICS

119 CAVENDISH ROAD, MATLOCK,  
DERBYSHIRE. DE4 3HE

TEL. MATLOCK 2817 or 2430 9 a.m.—9 p.m.

## G3UBO & G3MME

For the few who have learnt the rather bitter lesson that "fantastic  
and fabulous bargains" usually carry a built-in catch, that for junk  
prices you usually get junk, and that the nice dealer isn't really  
giving you something for nothing. To those few who feel that if  
they get what they pay for they haven't done too badly, we would  
like to mention that in the field of Amateur Communications and  
allied equipment, our name is top of the list.

We are the actual importers of Yaesu Musen Amateur Band  
Receivers, Transmitters and Transceivers, along with a wide range  
of accessories such as Aerials (beams, verticals, mobile whips),  
Filters (mechanical, crystal, high pass, low pass), Digital Voltmeters,  
Digital clocks, Digital frequency meters, Headsets, Morse keys,  
Electronic keyers, Microphones, Valves, R.F. wattmeter/dummy  
loads to mention just a few. We have a very good second-hand  
selection of the best Amateur equipment and can service your  
communications equipment for you. Everything we sell carries a  
full money-back guarantee.

To mention just one specific piece of equipment that we feel is  
unbeatable:—Yaesu YC-305 Counter. A frequency meter counting  
to over 30 MHz and reading to cycles, mains or battery, 5 digit  
readout. A professional piece of laboratory equipment at a very  
low price. Brand new £97.50.

SEND us a **LARGE** s.a.e. and we'll fill it with guff on all our gear.  
For Amateur Radio products of high quality at fair prices—you  
want us. Psst!! You want earth shattering bargains? Free gifts!  
Enormous discounts? Try further down the road, sir.

Hours: Tuesday to Saturday 9-5.30 (closed for lunch 1-2 and all day  
Monday).

# RSGB BOOKS FOR YOU

## RADIO DATA REFERENCE BOOK

Third (1972) edition

Compiled by G. R. Jessop, CEng, MIERE, G6JP  
Completely revised and updated

An invaluable source of essential radio data conven-  
iently gathered into one hard-bound volume.

150 pages £1 post paid

## VHF-UHF MANUAL

By G. R. Jessop, CEng, MIERE, G6JP

Transmitters, receivers and test equipment for use  
at vhf and uhf are all fully covered on a practical  
basis in this second edition. £1.80 post paid

## RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio  
communication. The Handbook's U.K. origin en-  
sures easy availability of components. Complete  
coverage of the technical & constructional fields.  
A superb hard-bound volume. £4.10 post paid

These are three of a complete range of technical  
publications, log books and maps, all obtainable from:

**RADIO SOCIETY OF GREAT BRITAIN**

35 DOUGHTY STREET, LONDON, WC1N 2AE



Referring again to our previous arguments, we say that the current flowing in the base bias chain, R1 and R2, should be about five times the base current of the transistor. In our circuit, we have the emitter taken directly to the negative line, and we know that the base-emitter voltage of a silicon transistor is normally 0.6V. So we can calculate the value of R1, since the voltage across it must be 0.6V and the current through it five times the base current of  $2.6\mu\text{A}$ . If we do our sums correctly, the answer will be:

$$R1 = \frac{0.6\text{V}}{5 \times I_b(2.6\mu\text{A})} = \frac{0.6 \times 10^6}{13} = 46,154\Omega.$$

The nearest preferred value in the 5% range will be 47k $\Omega$ .

The voltage across R2 will be the supply voltage, 8 volts, minus the base voltage of 0.6V = 7.4V. The current will be six times  $I_b$ , that is the current in R1 plus the original base current. So:

$$R2 = \frac{V_{cc} - V_b}{6 \times I_b} = \frac{8 - 0.6}{15.6 \times 10^{-6}} = \frac{74 \times 10^6}{156} = 474,359\Omega.$$

The nearest preferred value is 470k $\Omega$ .

## Input resistance

We have talked before about input resistance and our own experiences in trying to match equipment, about which manufacturers have given inadequate information, show that this is a difficult field. 'Fings ain't always wot they seem ter be!'

The input resistance of the transistor (looking into its base and ignoring R1 and R2) is  $h_{ie}$ . Fig. 43 shows that Mullard graph for the BC109, idealised for the conditions under which we are using the transistor—that is, with unnecessary information omitted. We have done this here, at Michael's insistence, because, to the layman, there is nothing more confusing than a graph filled with curves and references he is not called upon to use.

Here, we have indicated that the  $h_{ie}$  is a little over 10k $\Omega$ . If we had no graph, we should have to calculate:

$$h_{ie} = r_e \times h_{fe} \text{ where } r_e = \frac{25}{I_c(\text{mA})}$$

$$\text{so } h_{ie} = \frac{25}{1} \times 450 \text{ or } 11.25\text{k}\Omega, \text{ which is reasonably near}$$

the plotted figure in this case.

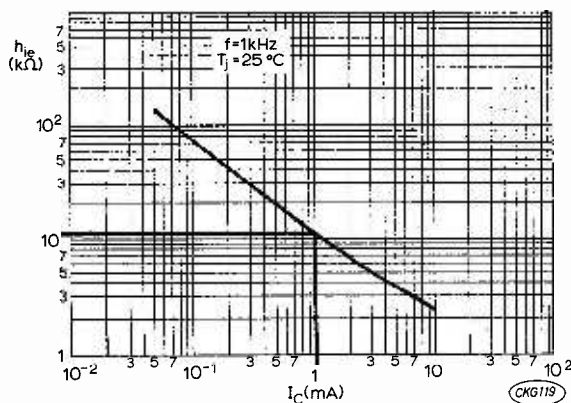


Fig. 43. This graph will give the input resistance,  $h_{ie}$ , of the transistor.

The input resistance of the stage, and not just the  $h_{ie}$ , is the latter shunted by the parallel combination of R1 and R2. This is as far as a.c. is concerned. (In parallel, because to a.c. signals, by reason of the low impedance of  $C_{dec}$ , the top of R2 is effectively connected to the bottom of R1.)

So we calculate for  $h_{ie}$ , R1 and R2 in parallel, arriving at:

$$\frac{1}{11\text{k}\Omega} + \frac{1}{47\text{k}\Omega} + \frac{1}{470\text{k}\Omega} = 8.7\text{k}\Omega \text{ approx.}$$

If there are to be 5 volts between collector and emitter, then we must have a voltage drop across  $R_c$  of 8-5 ( $V_{cc} - V_{CE}$ ). This works out to 3 volts and if the collector current is chosen to be 1mA, the resistance of the load  $R_c$ :

$$\frac{3 \text{ volts}}{1\text{mA}} = 3,000$$

The nearest preferred value to a 3k $\Omega$  resistor we shall get in the 5% range is 2.7k $\Omega$ . That's near enough.

## Gain

Stage voltage gain ( $A_v$ ) is equal to  $R_c$  divided by the emitter resistance. In this case we are concerned with the **effective internal** emitter resistance,  $r_e$ , which you will remember, caused some confusion earlier, and is calculated from the formula:

$$r_e = \frac{25}{I_c(\text{mA})} = 25\Omega.$$

The stage gain,  $A_v$ , becomes:

$$\frac{R_c}{r_e} = \frac{2,700}{25} = 108$$

We made some comment on the principle of selecting transistors so this may be the place to underline the importance of parameter variations on the validity of some associated calculations. In this case, if  $I_c$  changes, so does  $r_e$ . We chose our collector current and took a 'typical'  $h_{FE}$  from the graph. But collector current (actual) depends on base current and actual  $h_{FE}$ . So if the selected transistor has an  $h_{FE}$  that differs,  $I_c$  will differ,  $r_e$  will be affected and the stage gain may be quite different from that calculated. Hard world, isn't it?


## Adding an external $R_e$ .

In the previous case, that of Fig. 40, we had the emitter firmly strapped to 'earth' so the emitter voltage was the same as the negative supply line. What happens to the stage and its performance if we now insert a resistance in this emitter, in the position  $R_e$  of Figs 44 (a and b)?

Quite simply, the stage gain is altered and at the same time the input resistance,  $R_{ix}$ , is increased.

Basing our calculations on some of the factors we have already, we can choose a convenient value of resistor for  $R_e$  and work out what differences it will make. First,  $V_{cc}$  is 8V;  $I_c$ , 1mA;  $R_c$ , 2.7k $\Omega$  and our  $R_e$  will be, let us say 47 $\Omega$ . Then  $V_e = I_e \times R_e = 1\text{mA} \times 47 \text{ ohms} = 0.047\text{V}$ .

The emitter current is the collector current plus base current, or  $I_e = I_c + I_b$ . Since the base current of the transistor ( $2.6\mu\text{A}$ ) is very small in comparison with the collector current of 1mA, it is convenient to ignore it, satisfied that there will be only a negligible amount of error. So we can say, effectively,

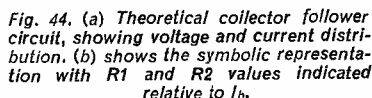
$$R_1 = \frac{V_b}{5 \times I_b} = \frac{0.65}{5 \times 2.6 \times 10^{-6}} = 50 \text{ k}\Omega, \text{ approx.}$$
$$R_2 = \frac{V_{cc} - V_b}{6 \times I_b} = \frac{8 - 0.65}{15.6 \times 10^{-6}} = 471.154 \text{ k}\Omega$$
$$\frac{R_c}{(R_c + r_a)} = \frac{2,700}{47 + 25} = 37.5$$

Negative feedback enters into matters at this point. We have not fitted any bypass capacitor across

To demonstrate the differences that are obtained when  $R_0$  is inserted, and then altered, the accompanying table has been prepared. Calculations which back these figures are based on the foregoing formulae, as worked out for an  $R_0$  of  $47\Omega$ , which we have used. We are assuming a  $V_{cc}$  of 8V, and  $R_0$  of  $2.7k\Omega$ , using a BC109 transistor. We have taken the figures calculated and measured for no  $R_0$  and for four different resistive values.

$R_0 \Omega$	0	47	100	220	470
Output impedance	<2.7k	2.7k	2.7k	2.7k	2.7k
R1 (k $\Omega$ )	47	47	47	56	82
R2 (k $\Omega$ )	470	470	470	470	390
R <sub>IN</sub> (k $\Omega$ ) measured	8.6	19.5	26	36.3	52
R <sub>IN</sub> (k $\Omega$ ) calculated	8.7	18.3	25	34.3	52
A <sub>v</sub> (voltage gain) measured	120	35	19	10.5	5.4
A <sub>v</sub> calculated	108	37.5	21.6	11	5.74

Finally, a paragraph on coupling and decoupling. We have already stated that  $R_{dec}$  is dropping 1V and we know that the approximate current through it will be 1mA so from this we can calculate its value.

$$R_{dec} = \frac{1V}{1mA} = 1k\Omega$$

We can take it that the decoupling capacitor,  $C_{dec}$  is as before, that is  $100\mu F$ .  $C_{out}$  is similar, at  $10\mu F$  and  $C_{in}$  will vary with the stage input resistance for optimum value. Using the rule-of-thumb method,  $1\mu F$  into  $100k\Omega$ , and applying this to measured values of  $R_{IN}$ , we can see that this will vary from a mere  $0.1\mu F$  (actual value  $0.086\mu F$ ) to greater than  $0.5\mu F$ .

**TO BE CONTINUED**

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CO" column which appears in most issues.

## RETURN OF POST SERVICE

## TTL LOGIC I.C. NEW PRICES

	1-11 12-24			1-11 12-24			1-11 12-24	
	$\hat{p}_p$	$\hat{p}_n$		$\hat{p}_p$	$\hat{p}_n$		$\hat{p}_p$	$\hat{p}_n$
SN7400	0.20	0.18	SN7433	0.80	0.75	SN7472	0.32	0.30
SN7401	0.20	0.18	SN7437	0.64	0.60	SN7473	0.43	0.41
SN7402	0.20	0.18	SN7438	0.64	0.60	SN7474	0.43	0.41
SN7403	0.20	0.18	SN7440	0.23	0.21	SN7475	0.45	0.43
SN7405	0.20	0.18	SN7441	0.87	0.83	SN7476	0.45	0.44
SN7406	0.80	0.75	SN7442	0.85	0.81	SN7480	0.70	0.65
SN7407	0.80	0.75	SN7443	2.88	2.70	SN7481	1.40	1.38
SN7408	0.20	0.18	SN7444	2.86	2.70	SN7482	0.87	0.82
SN7409	0.20	0.18	SN7445	2.50	2.40	SN7483	0.87	0.82
SN7410	0.20	0.18	SN7446	1.00	0.95	SN7484	2.00	1.85
SN7411	0.23	0.21	SN7447	1.00	0.95	SN7485	3.82	3.40
SN7412	0.48	0.46	SN7448	1.00	0.95	SN7486	0.33	0.30
SN7413	0.40	0.38	SN7449	1.00	0.95	SN7490	0.87	0.84
SN7430	0.20	0.18	SN7451	0.20	0.18	SN7491	1.21	1.10
SN7423	0.51	0.47	SN7452	0.20	0.18	SN7492	0.87	0.84
SN7427	0.48	0.45	SN7453	0.20	0.18	SN7493	0.87	0.84
SN7428	0.80	0.75	SN7454	0.20	0.18	SN7494	0.87	0.84
SN7430	0.23	0.15	SN7460	0.20	0.18	SN7495	0.87	0.84
SN7432	0.48	0.42	SN7470	0.40	0.38	SN7496	0.87	0.84

**C425 range axial lead** 6p each  
 Values: ( $\mu\text{F/V}$ ): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40;  
 6.4/6.4; 6.4/25; 8/40; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4;  
 25/25; 32/10; 32/40; 40/16; 50/6.4; 50/25; 50/40; 64/10; 80/2.5; 80/16;  
 80/25; 100/6.4; 125/10; 125/16; 200/10.

PIV	50	100	200	400	600	800	1000	1200
1A	8p	9p	10p	11p	13p	15p	20p	—
3A	15p	17p	20p	22p	25p	27p	30p	35p
4A	—	—	25p	35p	35p	—	—	—
5A	—	52½p	57p	65p	77½p	84p	97½p	\$1.25
15A	—	57½p	62½p	77½p	90p	97½p	\$1.20	\$1.57½
35A	—	80p	90p	\$1.00	\$1.25	\$1.50	\$2.50	—

1 amp and 3 amp are plastic encapsulation.

IN34A	10p	AA119	7p	BAX16	121p	FST3/4	221p
IN914	7p	AA139	15p	BAY18	171p	OA5	17p
IN916	7p	AAZ13	12p	BAY31	7p	OA10	10p
IN4007	20p	AAZ15	12p	BAY38	25p	OA9	20p
IS44	7p	AAZ17	10p	BY100	15p	OA47	8p
IS113	15p	BA100	15p	BY103	22p	OA70	7p
IS120	12p	BA102	25p	BY132	471p	OA78	10p
IS121	14p	BA103	25p	BY137	45p	OA70	7p
IS130	8p	BA114	15p	BY126	15p	OA81	8p
IS131	10p	BA115	7p	BY127	17p	OA82	10p
IS132	12p	BA141	17p	BY164	57p	OA90	7p
JS890	7p	BA142	17p	BYX10	22p	OA91	7p
IR922	8p	BA144	12p	BYZ10	35p	OA95	7p
IS923	12p	BA145	7p	BYZ11	33p	OA300	7p
IS940	5p	BA154	12p	BYZ12	80p	OA202	10p
		BAX13	5p	BYZ13	25p	UIY307	50p

**MINITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) £2.00**  
May be driven by SN7447

**GNP-7AH COLD CATHODE TUBE SIDE VIEWING, 0-9 and TWO DECIMAL POINTS.** May be driven by SN7447N. 75p

TIL 209 LIGHT EMITTING  
DIODE. Made by TEXAS INST.  
(Red). 85p

0.15, 0.22, 0.33	..	..	5p each
0.47	..	..	9p

0.68	..	..	..	11p
1μF	..	..	..	14p

1.5μF	..	..	..	21p
2.2μF	.	..	..	25p

## WIRE-WOUND RESISTORS

2.5 watt 5% (up to 270 ohms  
only) 7p

5 watt 5% (up to 8.2k  $\Omega$  only), 9p  
10 watt 5% (up to 26k  $\Omega$  only).

10p

## POTENTIOMETERS

Carbon:  
Log. or Lin., less switch, 16p

Log. or Lin., with switch, 25p  
Wire-wound Pots (3W), 38p

Twin Ganged Stereo Pots, Log.  
or Lin. 40p.

## PRESETS (CARBON)

0.1 Watt 8p VERTICAL  
OR

0.3 Watt 7½p HORIZONTAL

**P.W. Digital Clock**

Complete Kit (less box) as in

**£20.50** April '72 issue.  
(inc. P. & P.)



**CALLERS WELCOME**  
TUE. 8.5.00 MON. FRI.

9-5.0 SAT.

**Table 1**

## 16


TOP QUALITY — LOW COST



AMATEUR RADIO EQUIPMENT



**NEW!**

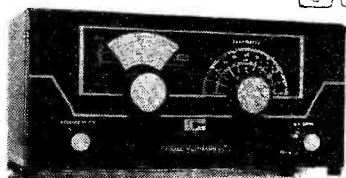

### MULTIBAND-6 TRF SHORT WAVE RECEIVER KIT

This new all transistor T.R.F. Receiver tunes 550 KHz-30 Mhz (540-10 metres) complete coverage, no gaps. Trawlers, Ship to Shore telephone, Six Amateur Bands, 160-10 metres, International Broadcast, Australia, Far East, Russia, USA, etc. etc., using miniature plug in coils. Hi-Gain FET Regen. Det./Pre-Amp A.F./A.F. Module giving full loud speaker output to any external 2/3 ohm speaker. Two separate Tuning Dials, Calibrated Mhz and Degrees. Electrical Bands spread on all bands. Regen. det. receives CW/SSB signals also. Handsome styling with Black Perspex Panel, Steel Cabinet in Charcoal finish with Chrome Trim.

This is a quality CODAR-KIT with full 12 months guarantee. No technical knowledge required, printed circuit construction, Instruction Manual with pictorial drawings backed by friendly Help-U After Sales Service if you have any queries.

Complete Kit (even to the resin-cored solder) with 3 Coils. £11.50 Carriage 70p.

Available NOW. NEW PR40 FET Pre-Selector. Stamp brings illustrated leaflets.



**CR 70A**

**COMMUNICATION RECEIVER**

**WORLD RANGE PERFORMANCE  
SUPERB STYLING**

The new Mark 2 CODAR CR70A general coverage Communications receiver now embodies the following extra features: Printed Circuit construction of all valve stages for peak performance and reliability. Switched phone jack for speaker muting.

It tunes 540 to 10 metres continuous coverage, no gaps. Covers Shipping and distress frequencies, and six amateur bands 160-80-40-20-15-10 metres, Met stations, World Wide broadcast.

Exclusive specially wound Air spaced CODARCOIL Hi "O" aerial input, "S" meter, two speed vernier tuning, switched BFO for CW/SSB signals. Monitored output for tape recorder.

It only needs your aerial and a 2/3 ohms loudspeaker to bring its outstanding performance to your fingertips. 12 months full guarantee. Complete £27.50 carriage 50p.

Ask the chap who's got one—there's plenty of them! Start your own Short Wave Listening Station now!

ON THE DESIGN STAFF—  
G3SZM G3IRE G8BBI

WE HAVE MOVED TO OUR NEW FACTORY • PLEASE NOTE OUR NEW ADDRESS

**CODAR**



**VALCON WORKS • BURRELL BUILDINGS • CHURCHILL INDUSTRIAL ESTATE • LANCING • SUSSEX**

## CAPACITOR DISCHARGE IGNITION KIT

PW JUNE 71

A comprehensive kit of parts with detailed constructional details, ready drilled diecast case, screws, leads, terminals etc.



Available in both 6 and 12v versions. State whether positive or negative earth.

£8.75 incl. p. & p.

De-coupling kit for impulse tachometer and interference suppression. £1.00 incl. p. & p.

All our kits use guaranteed quality components and have been approved by the Author.

**MAGTOR LTD.**

68 DALE ST., MANCHESTER, M1 2HS.

## C. T. ELECTRONICS

267 ACTON LANE, LONDON, W.4  
01-994 6275

OUR RETAIL COMPONENT SHOP IS NOW  
OPEN FROM 9.30 a.m.-6 p.m. MON-SAT.

FREE COMPONENT PRICE LISTS  
NOW AVAILABLE  
PLEASE SEND LARGE S.A.E.

HUNDREDS OF SURPLUS BARGAINS FOR  
THE PERSONAL CALLER


## BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts  
Bass Resonance 45 c.p.s.  
Flux Density 12,000 gauss  
Voice Coil impedance 3 or 8 or 15 ohm models  
Useful response 45-13,000 c.p.s.

Nett weight 5 lbs. POST FREE  
GUITAR MODEL "GROUP 25" £7  
25 watt rating  
Latest catalogue 5p with enclosure plans.

**£7**

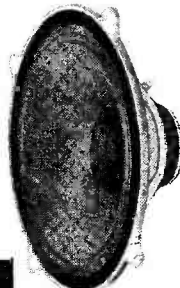

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE first reporter this month is **Hugh Cocks** of Mayfield in Sussex who has a Unica UNR-30 receiver and a 70 foot long-wire. Hugh sent in a special log of South American stations as follows:

- 9515 R. Roquete, Pinto, Brazil at 2200.
- 9530 R. Calendario, Venezuela at 2230.
- 9595 R. Cultura de Bahia, Brazil at 2130.
- 9620 R. Novo de Julho, Brazil at 2150.
- 9635 R. Aparecida, Brazil at 2225.
- 9665 R. Nac. Brasilia, Brazil at 2230.
- 9705 R. Maua, Brazil at 2100.
- 11720 R. Nac. Brasilia, Brazil at 2100.
- 11785 R. Guaiba, Brazil at 2058.
- 11795 R. Nac. Rio, Brazil at 2100.
- 11805 R. Globo, Brazil at 2100.
- 11865 R. Cl. de Pernambuco, Brazil at 2100.
- 11875 R. Soc. de Bahia, Brazil at 2100.
- 11915 R. TV. Gaucha, Brazil at 2115.
- 11925 R. Bandeirantes, Brazil at 2200.
- 11950 R. Min. Educaco, Brazil at 2130.
- 15105 R. Rural Brasileira, Brazil at 2200.
- 15145 R. Jornal do Comercio, Brazil at 2150.
- 15155 R. Dif. de Sao Paulo, Brazil at 2200.
- 15190 R. Inconfidencia, Brazil at 2230.
- 15415 R. Cl. Ribeirao, Brazil at 2130.

**Ian Howes** of Lowestoft used a TV antenna with his R209 Mk. 2 receiver to log the following very interesting stations:

- 4500 Urumchi, China with music at 0010.
- 4665 Pathet Lao, Laos in Laotian at 1545.
- 4790 R. Ondas Portenas Venezuela at 0010.
- 4800 AIR, Hyderabad, India at 1545.
- 4840 AIR, Bombay, India at 1510.
- 4965 R. Santa Fe, Colombia news at 0000.
- 9680 VLH/R9 ABC, Melbourne, Australia at 1100.
- 11875 R. Dif. Nacional, Nicaragua at 0000.
- 11880 R. Splendid, Argentina in Spanish at 0045.

**Peter Herman** of New South Wales, Australia has an equipment line-up which includes a Trio 9R-59DS receiver, a 9MHz. dipole, a 15MHz. dipole, and a Hitachi SCT-1150R 3-band radio/cassette with a telescopic and 12 foot long-wire antenna. Peter's log included:

- 3322 R. Bougainville, N. Guin. at 1143.
- 4820 R. Gambia at 1800.
- 6145 AIR, India at 1540.
- 7100 R. Budapest, Hungary at 1630.
- 7235 All India Radio at 1500.
- 7285 R. Berlin International at 1730.
- 7290 R. Kuwait at 1630.
- 11920 R. Abidjan, Ivory Coast at 1830.

**D. A. Hairon** of St. Clement, Jersey has sent in another report using the usual equipment, this time he has heard:

- 9570 ABC, Australia in English at 1015.
- 9625 Israel B.C. in English at 2130.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 11730 R. Nederland, Bonaire at 0525.
- 11760 R. Habana, Cuba, sign off at 0200.
- 11815 TWR, Bonaire in English at 0045.
- 11860 BBC, Ascension Is. relay at 0815.
- 11875 R. Nacional, Nicaragua, Spanish at 0130.
- 15160 R. Ankara in Arabic at 0530.
- 15532 R. Bangladesh in English at 1245.
- 17855 NHK, Japan in English at 0900.
- 21605 R. Kuwait in Arabic at 1100.

**Alastair Nimmo** is only eleven years old but this extract from his log, using a Meridian 10 transistor portable and 100 foot long-wire shows distinct promise:

- 5960 HCJB, Quito, Ecuador, English at 0830.
- 6040 VOA, Rhodes relay at 2100.
- 9515 R. Ankara in English at 2200.
- 9525 RSA, South Africa in English at 2215.
- 9530 AIR, Delhi in English at 1900.
- 9530 VOA, Monrovia relay, English at 2230.

In order to mention as many reporters as possible I will end this article with a few short extracts from the many received:

**Richard Coyle**, Glasgow, Lafayette KT340:

- 4965 R. Santa Fe, Colombia at 0550.
- 4970 R. Rumbos, Venezuela at 0345.
- 4990 R. Barquisimeto, Venezuela at 0400.
- 5038 R. Bangui, Ident. in French at 0500.
- 5075 R. Sutatenza, Colombia at 0100.

**Adrian Pell**, Wareham, Dorset:

- 12025 Voice of Vietnam, English at 2015.
- 15165 Danish Radio in Danish at 1400.
- 15295 TWR, Bonaire in Norwegian at 2145.
- 15370 VOA, Greenville in French at 2200.

**Ian Newbold**, Birmingham, R209 Mk. 2, 95 foot aerial:

- 3340 R. El Mar, Ecuador at 2000.
- 4550 R. Nacional, Colombia at 2005.
- 9735 NHK, Japan in Japanese at 2018.
- 15170 ELWA, Liberia in French at 2007.

**Fred Wall**, E.17, PR155, 20 foot long-wire:

- 3380 R. Malawi in English at 1800.
- 9510 R. Barquisimeto, Venezuela at 2350.
- 9520 R. New Zealand in English at 0900.
- 11930 Windward Is. B.S. cricket at 2120.

**Philip Sokell**, Barnsley, Romer 10, telescopic antenna:

- 6125 VOA noted at 1610.
- 6185 Radio Australia at 2045.
- 7215 Radio Cairo, Egypt at 0254.
- 7230 Radio Kiev, Ukraine at 0045.

Reports should arrive by the 15th of the month and be addressed to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.



# SHORT WAVES

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

**I**N theory, it should have been a very good month for keen listeners since almost every log sent in was for bands which were at either end of the r.f. spectrum. Quite a few queries in the post bag, many asking questions which would require a text book, blackboard and a couple of years at evening classes to answer. Many people who have queries have a very simple way out—join the nearest radio club. You can ask a question and get an immediate answer. There is nearly always someone at the club who specialises in an area where your question is aimed at. If one person doesn't know the full answer, then it is virtually certain that someone else will.

Join the R.S.G.B., too. This organisation will give you all the help you need, and will also tell you the name and address of the secretary of your nearest radio club. The Society also publishes a number of "booklets" especially for the radio enthusiast and some are aimed specifically at the beginner.

Having joined a club, you will get a chance to visit other people's 'stations' and see gear which, at present, is only a number, like PR40 or R107. Better still, you can have a twiddle with the gear and make up your own mind as to whether a particular piece of equipment is very good or just mediocre.

So you don't hear any DX in spite of all those lovely logs you read in *Practical Wireless*? One way to latch on to some DX is to listen for a DX net which has European stations either in it or even running it. Listen for a good European station calling a DX station. Once you have found the right frequency it is highly probable that other stations will come up also calling the DX station. Eighty metres is a common hunting ground for this type of DX net.

Combined efforts of the Ipswich and Colchester clubs will result in the Anglian Mobile rally to be held at Ipswich on June 18. Talk-in stations on 160, 80, 4 and 2 metres. Colchester club also runs slow morse practice sessions. Anyone in the area might like to drop to Hon. Sec. a line at 26 Pondfield Road, Colchester, Essex. See you at the rally?

An appeal from **Sam Elsdon** for Amateur stations to use "standard" phonetics. I agree. Only way seems to be to make an accepted phonetic alphabet compulsory and written into all Amateur licences throughout the world. Sam has just finished off the CQ2 v.h.f. receiver which appeared in the September edition of *Practical Wireless* back in 1969. He runs a CR70A and PR40 plus a 310ft end-fed. A listen on eighty metres s.s.b. raised: DJ9NW, PJ4AQ, W5ILR/TF, XE1CV, 9H1D. Log for 20 metres reads: BY4AP, EA3AKE, FG7TC, IS1KLO, VE3MR, VK2AVA, VK3OEL, VK5OB, VO4HW, ZS5KY, 4X4DK, 7X2PK, 7X3ORU.

**Kevin Lamb** has seen thirteen summers pass and resides at Ashford. Gear consists of a two-valve homebrew receiver, a.t.u. (also homebrew) and a 50ft end-fed. Goodies heard on topband include: HB9CM, OK1FT, OK1MAC, OL1APC, 4U1ITU.

Twenty metres using an R107 (that's cheating) raised: CX2XA, EA8GZ, EA8DI, HK5ASM, PY7AZQ, VK3ALL, VK4NB, VK4UC, VK5FH, VK6HE, VP9GK, ZL1HD, ZL3AH, ZL3AR, ZL3HA. Kevin asks about some four metre activity. This is a band which the Amateur could so easily lose unless there is a lot more activity. If the two metre addicts would come down, the G8 plus threes take the trouble to learn c.w., and the h.f. DX types go up another band, we might just save it—or is it worth the effort?

One hundred and thirty-two feet of wire stretching into the sunset but anchored to the aerial terminal of an R107 is a feature at a house in Melbourne Road, Chester. **Mike Purcell** loiters thereabouts and heard the following on 3.5MHz s.s.b.: CR4BS, CT1UN, HB9LQS, VE1QM, VP2LAT, VO1CU, WB0FFG/TF, W1AA, 4X4UF.

Another CQ2 v.h.f. receiver builder is **David Lawley** (Gravesend). He has heard a fair number of Amateur two-metre stations already but although he is only ten miles from the beacon station GB3VHF, he can't hear it at all. (V-e-r-y interesting.) Ten metres is the band which has brought a lot of stations in for David using the School Radio Society's B40 plus 500ft long, long, long wire. Log reads: JA8GWA, JR1INC, OD5HI, PZ1DV, VE3DOR, VE7HC, VU2JM, K1BCD, hoards of W stations, ZC4BJ, 4X4GH, 4X4HK, 9X5MS all mostly on s.s.b.

Down on topband, David reports signals from: E19J, GM3YOR, GW3UCB, GW3UPK, GW4AHN/A, HB9CM, HB9NL, OL1AOH, OL5ANJ, PA0PN. These were all on c.w. but PA0PN is on most Sunday mornings on s.s.b.

Eighty-three W stations start off the eight metre log of **Richard Coyle** (Glasgow). Additional appearances from: VE1ANZ, VE2WA, VE3GCS, VE3VE, ZL3GS, 6W8DY.

Fifty-nine W stations in the ten-metre log from an unknown listener at Henrietta Street, Girvan in Ayrshire. OK, don't sign your name, but I know you've got a CR70A and a ten-metre dipole. Incidentally, it is surprising how many logs don't get in because no receiver is mentioned, or the aerial hasn't been divulged or the whole list is not in alphabetical order. (Hint! hint!!)


**John Guy** (Wimborne), B40C, 70ft end-fed, 28MHz, mode unspecified: CR4BS, CR611, ET3USA, FL8MM, HC2GG/P, KP4DHD, VS6DO, YV1AMX, YV3SZ, 7Q7BC, 8R1G.

More news from **John Stevenson** (Woking) about his d.c. (direct conversion) receiver. A number of mods have given a large increase in sensitivity. Log for 14MHz s.s.b. reads: CT1BZ, HR1RS, HV3SI, KP4BSA, PY1CAD, PY2YRS, PY4AS, VK2NN, VK2RV, VQ9R, ZL1BE, 3A2CP, 4X4BL, 4X4NJ, 4Z4TV, 9H1CZ.

Happenings for the merry month of May include: 6-7, 432MHz contest; 21, 2 metres contest. June: 3-4, National Field Day; 10-11, 4 metre contest.

## Discoscene

EFFECTS LIGHTING EQUIPMENT

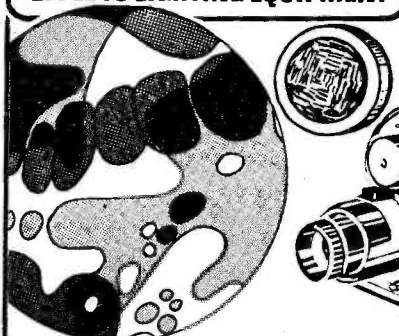

Wheel and Cassette Projectors  
Moire — Liquid — Graphic — Polaroid  
Strobes — Kaleidoscope Lenses — Lamps  
and Fittings — Spot Banks

Your enquiries welcomed

### EFFECTS PROJECTORS

DISCO COLT, 150 watt

LIQUIMATIC MINI, 50 watt QI with  
6" wheel

DISCOWHEEL, 50 watt QI with  
quick change Cassette

GNOME 150, 150 watt QI with  
Cassette

LIQUIMATIC, 150 watt QI with 6"  
wheel

PLUTO TUTOR-2, 250 watt QI with  
Cassette and 6" wheel

TUTOR-2, with Liquisplode Tank

KALEIDOSCOPE LENS (for Tutor-2)


6" Liquid Wheel and Crystal Wheel

Liquid Cassette and Moire (24

different types to choose from)

Portable Hi-Power Strobes


TRADE & RETAIL SUPPLIED

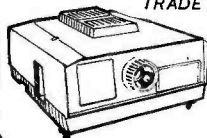

## DISCOTHEQUE EQUIPMENT

### PA SOUND & LIGHTING

### from 4 SPECIALISED DISCO STUDIOS

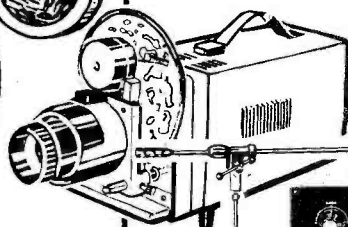

Illustrated above:

**DISCO SUPER.** Two high quality turntables, pre-amp, cross-fade between decks, pre-fade and listen facilities, mic over-ride, aux inputs, full controls for all facilities; deck inputs via break-jacks. And VU meter for visual monitoring of inputs and outputs. Headphone monitor socket. Output 100 watts r.m.s. DJ 30L Mk. II Sound to Light Unit incorporated. Also available **DISCO-PLINTH, DISCO-IMP, DISCO MINI** and **DISCO STANDARD**, as 'Super' less Light Unit, 100 watts r.m.s.

**DISCO SUPREME**, 3 turntable version of 'Super', 100 watts r.m.s. Power output can be increased in multiples of 100 watts to suit customers' requirements.

**DJ DISCO AMPLIFIER**, 100 watts r.m.s. with all facilities

**SOUND CONTROLLED PSYCHEDELIC LIGHT UNIT DJ 40L Mk. II**, 1,000 watts per channel over three channels—bass, mid, and treble

**PSYCHEDELIC SOUND TO LIGHT CONTROL UNIT DJ 30L Mk. II**, 1,000 watts per channel over three channels—bass, mid, and treble

**70WATT P.A. MIXER-AMP DJ 70S.** One of the finest available — 30-20,000 Hz  $\pm 3$ db

**CONSORT SPEAKER**, 2 x 12" 100 watt system

**MICROPHONES STANDS & BOOMS EFFECTS PROJECTORS SPARES & ACCESSORIES STROBES**  
**COLOUR DISPLAYS MIXERS AMPLIFIERS AND ALL**  
**P.A. DISCOTHEQUE GEAR — DESIGNED AND ESPECIALLY**  
**MADE TO GET THE BEST FROM YOUR MOBILE OR**  
**PERMANENT INSTALLATION.**

PACKAGE  
DEAL PRICES  
ON REQUEST  
CREDIT TERMS  
FOR CALLERS

SEE HEAR AND SELECT FROM A COMPLETE RANGE OF SOUND AND  
LIGHTING EQUIPMENT AT ANY OF THESE FOUR DISCO CENTRES.  
LITERATURE AND QUOTATIONS ON REQUEST.

OPEN 6 DAYS A WEEK WITH VALUE-FOR-  
MONEY PRICES—12 MONTHS' GUARANTEE  
CREDIT TERMS AVAILABLE FOR CALLERS

## Discoscene

536, Sutton Road,  
Southend, Essex.  
(0702) 611577

## Discosound

122, Balls Pond Road,  
London, N.1.  
(01) 254 5779

## Discosound

(Birmingham) Ltd.  
494, Bristol Road,  
Selly Oak, B'ham 29.  
(021) 472 1141

## Henry's Disco

309, Edgware Road,  
London, W.2.  
(01) 723 6963

### P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S.) per Channel into 8 Ohms!!  
Total Harmonic Distortion 0.02%!!  
Frequency Response (-3 dB) 20Hz-100kHz!!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

All Parts available separately.



### ELECTRO SPARES

21 BROOKSIDE BAR,  
CHESTERFIELD, DERBYSHIRE.  
QUALITY • SERVICE • VALUE

### REED COILS

3, 6, 9, 12, 24V Miniature 27p  
Small 27p  
Standard 34p

P & P. 7p on all orders.

### REED SWITCHES

Large range of many sizes, types  
and manufacture

Popular types:  
E Small n/o 10 for 50p  
A Miniature n/o 24p each  
B Standard c/o 40p each

### REED PUSH BUTTON SWITCHES

Momentary Action  
1 contact £1.00  
2 contacts £1.25  
Illuminated 1 contact £1.30  
Illuminated 2 contacts £1.55

### REED RELAYS

Many versions available, popular  
types: 3, 6, 9, 12, 24V

Miniature 1/A normally open 56p  
Small 2/E 1 contact 36p  
2/EE 2 contacts 44p  
2/EEE 3 contacts 52p  
STD 3/B change over 87p


### REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g. 50, 100 & 200 grams. Send for prices

### C.B.M. ELECTRONIC COMPONENTS LTD.

26 Avon Trading Estate, Avonmore Road, London, W.14

## BETTER GET 'SET'

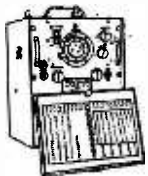

**FAMOUS BC.221  
FREQUENCY METER**  
125 KHz-20 MHz. Complete  
with valves, crystal and charts.  
ONLY £19.50. Carr. £1.50.  
**No. 22 TM/RC.** 2-8 Mc/s. Com-  
plete with 12V. D.C. P.S.U., head-  
phones, mike and all cables £28.50.  
Carr. £2.50.

### CRYSTAL CALIBRATOR

**No. 10** Crystal controlled hetero-  
dyne wave-meter covering 500KHz-10 MHz (Harmonics  
up to 30 MHz). Power required 300V. D.C. 15mA. 12V.  
0-3A D.C. Test equipment for 62TM/RC. SPECIAL  
OFFER £28.50. P. & p. 50p.  
FEW ONLY—No. 62 TM/RC 1-5-10 MHz £17.50.  
Carr. £2.



**MARCONI 801A SIGNAL GENERATOR**  
10-310 MHz. In original transit case. £45. Carr. £2.50

### AERIAL MAST EQUIPMENT

#### 20' TELESCOPIC MASTS

£3.75. Carr. £1

5' 2" Extension Sections to

fit bottom of above mast to

increase height. £1.25 each

(any number supplied).

35' MAST 7' 6" inter-

locking sections) with base


plate and 12 nylon guys with

semi-auto tensioner.

£19.50. Carr. £1.50.

70' MAST. Ditto. 16 guys, block

and tackle. £37.50. Carr. £2.50.

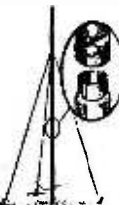

**AERIAL RODS 3ft.** Screw-in 1" dia. sections. Brand  
New, green finish. Suitable for many other uses. 10 for £2.  
Carr. 50p. 25 for £5. Carr. £1.50.

### R.F. ANTENNA TUNER (A.T.U.)

Cylinder design 10" x 4 1/2". Pre-  
cision calibrated scale. Suitable  
for tuning most aerials for  
increased signal strength. A must  
for serious operators for RC or  
TM. Full instructions.  
ONLY £28.00. P. & p. 25p.



### R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller  
Coaster" design 16 G silver or  
silver plated wheel traversing  
on wire on ceramic former. Will  
handle considerable R.F.  
In original packing. As used  
with No. 53 Transmitter.  
ONLY £28.00. P. & p. 50p.



### No. 17 SET TRANSMITTER

Receiver Rebuilt. Complete station  
with P8U, Cables, Mic, Aerial, etc.  
£22.50. Carr. £3.

### No. 19 SET 500uA METERS

Scaled 0-500 and 0-15V. Brand new,  
boxed £1.25 Post Paid. (Quantity  
prices on request.)



### R.F. AMPLIFIER. To increase

output of No. 19 Set.  
ONLY £23.75. Carr. £1.25.  
Instruction Book for R.F. Amp.  
£7.1p Post Paid.



### ALL No. 19 SPARES IN STOCK

Complete instruction book  
with circuits for No. 19  
Equipment. £7.1p Post Paid.

### HEAVY DUTY BATTERIES

New in metal cases with  
carrying handles.  
6V. 100/125AH. 15" x 11" x 7" £5.50. Carr. £1.25.  
6V. 170AH. 15 1/2" x 13" x 7" £8.50. Carr. £1.25.

### LIQUID PRISMATIC COMPASSES

2" diameter £7.50, p. & p. 25p

### FAMOUS TELE 'F' FIELD TELEPHONES

Suitable for Farms, Building  
Sites etc. Communication up  
to 5 miles or more. Rugged  
construction. Will last a lifetime.  
ONLY £6.25 PAIR. Carr. £1.25  
(Twin telephone wire for above available—ask for price.)  
Many other Ex-Govt. Surplus Equipment items in stock.  
Receivers etc. in small quantities too numerous to mention.  
Enquiries invited. LIST £5p Post Paid. (Refundable  
against purchases over £25.)  
C.W.O. Carriage charges apply to Mainland only.  
Minimum Export Order £50.



**Surplus Electronic Trading**

DRIVERS END LANE, CODICOTE,

HITCHIN, HERTS, SG4 8TP

Hours of business: 8-5 Mon.-Fri., 8-12 Sat.  
Telephone: Codicote 242 for appointment



### 6 or 12 Watt QUALITY AMPLIFIERS

Look at our special Summer Prices!

This powerful range of Stereo Amplifiers,  
currently being used in O.E.M.'s production  
equipments, are genuine high quality low  
distortion (averaging 0.2%) units using  
high grade components, based on the well  
proven Plessey integrated circuit ampli-  
fiers. Each is fully tested and assembled on  
a silk screened printed circuit board with  
tone control pre-amp section and power  
amplifiers. The circuit features printed  
circuit mounted controls for volume,  
balance and tone, together with bridge  
rectifier and smoothing capacitor and only  
needs extra: 13 to 15V A.C. from any  
transformer rated at about 1A (2A for  
12watt models). Input sensitivity (100mV  
at full gain) and impedance are chosen to  
suit crystal pick-ups and tuners to provide  
a level frequency response from 50 to  
15KHz.

601 Amplifier, 3+3watts r.m.s. for 8Ω  
load, with treble control. Size: Front  
8 1/2" x 2 1/2" h x 2 1/2" d. Price £4.90\*

602 Amplifier, 3+3watts r.m.s. for 8Ω  
load, with separate bass and treble con-  
trols, size: Front 5 1/2" x 1 1/2" h x 6 1/2" d.  
Price £7.49

1202 Amplifier, 6+6watts r.m.s. for 15Ω  
with separate bass and treble controls,  
size: Front 5 1/2" x 2 1/2" h x 6 1/2" d.  
Price £10.50\*

Mains transformers:  
for use with 600 series amplifiers. Price 98p

for use with 1200 series amplifiers. Price £1.75

Also available in KIT form for price of  
amplifier less 12.5%.

Cheques, P.O.s. plus 16p per item post and  
packing.

### THE AUTOTRON COMPANY, HIXON, STAFFORD

Discount quotations for quantity  
orders, 5 to 1000. Trade enquiries  
invited.

## TRANSFORMERS

### DOUGLAS GUARANTEED

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS*†	£9.91 9p
12V x 2 500 mA x 2	MT213 CT*†	£9.91 16p
12V x 2 1A x 2	MT214 AT*†	£1.48 24p
12V x 2 2A x 2	MT 18 AT	£2.06 30p
12V x 2 3A x 2	MT 70 AT	£2.59 32p
12V x 2 4A x 2	MT 108 AT	£2.82 34p
12V x 2 5A x 2	MT 72 AT	£3.35 42p

30 volts. All tapped at 0-12-15-20-24-30V.  
put Price P.P. Out-Ref. No. Price P.P.

500 mA MT 113 CT† 1-12 16p 3A MT 20 AT 2-64 32p  
1A MT 79 AT† 1-55 29p 4A MT 51 AT 8-10 40p

2A MT 3 AT 2-23 30p 5A MT 51 AT 4-81 45p  
50 volts. All tapped at 0-19-25-32-40-50V.

500 mA MT 102 AT† 1-45 24p 3A MT 105 AT 8-81 41p  
1A MT 103 AT 2-06 32p 4A MT 106 AT 5-06 41p

2A MT 104 AT 3-10 32p 6A MT 107 AT 7-47 50p  
60 Volts. All tapped at 0-24-30-40-45-50V.

500 mA MT 124 AT† 1-46 30p 2A MT 127 AT 8-16 41p  
1A MT 128 AT 2-24 32p 3A MT 125 AT 4-59 41p

### AUTO-WOUND RANGE

Power Winding tapped at Ref. No. Price P. & P.

20 VA 0-115-210-240 MT 113 CT £9.99 16p  
75 VA MT 13 CS† £9.91 8p

150 VA 0-115-200-220-240 MT 4 AT £21.15 2p  
200 VA MT 5 AT £29.00 32p

400 V. Output at 50 Hz. Ref. 173 AT Price P. & P.  
C-D Ignition system by E. M. Marston £29.30 29p

### EQUIPMENT RANGE

Sec. Output (r.m.s.) Ref. No. Price P. & P.

3-0-3 V. 200 mA MT 209 CS\*† £9.99 8p  
3-0-9 V. 100 mA MT 13 CS† £9.91 8p

12-0-12 50 mA MT 210 CS† £9.91 8p  
26-0-26 30 mA MT 211 CS† £9.91 8p

0-20 x 2 300 x 2 MT 214 CT† £1.21 16p  
0-8-9 x 2 500 mA x 2 MT 207 CT† £1.48 19p

0-15-20 x 2 500 mA x 2 MT 205 AT† £2.12 23p  
0-15-27 x 2 500 mA x 2 MT 203 AT £2.45 29p

0-15-27 x 2 1A x 2 MT 204 AT\* £2.42 30p  
10-12-0-12-20 700 mA (d.c.) MT 221 AT\* £1.11 26p

AT indicates open universal fixing with tags; CT is  
open U-clamp fixing with tags; CS is open U-clamp  
fixing with P.C. splices; †: Transformer with screen; ‡: un-  
tapped 240V Primary; †: Primary tapped at 210-240V;  
over 200 types in stock through agents or direct. Send for  
list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.,  
(Dept. M08FW), Thames Street, LOUTH, Lincs.


## PROJECT 60 FM TUNERS

ONLY \*£19.50

### MULLARD UNILEX

EP9000 Amp £2.40. EP9001 Pre-amp £2.00.  
EP9002 Power Unit £3.00. Control Unit £2.00.  
Unilex Booklet £0.25.

### SINCLAIR SUPER IC12

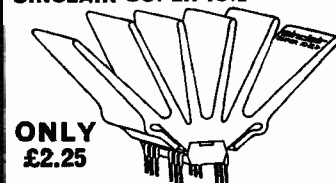

ONLY  
£2.25

Complete with free printed circuit board and  
44 page instruction book.

### IC12 KITS

**MONO  
KIT** £1.20 Contains all the parts required for  
the printed circuit board and  
simple tone and volume controls.

**STEREO  
KIT** £2.00 As above, but contains parts for  
two printed circuit boards and also  
contains a balance control.

**POWER  
KIT** £2.50 A set of components to construct  
a 28V 0.5Amp power unit. Ideal for  
both the stereo and mono versions.

**PZ5  
UNIT** \*£4.00 This fully constructed, compact,  
robust, modern power supply is  
also ideal for both versions.

### S-DECS AND T-DECS

The breadboards for the translator age.

S-DECS  
£1.40  
T-DECS  
£2.00



All orders from this section are post free and  
are subject to a 10% discount if over £5.00 and  
15% if over £15.00. Official credit orders from  
educational establishments welcome.

### SINCLAIR PROJECT 60

Z30	£3.00
Z50	£4.35
PZ5	*£4.00
PZ6	*£5.40
PZ8	*£6.40
Q16	*£7.40
AFU	£4.00



Stereo 60 Preamp/Control Unit	£7.80
Project 60 kit (see below)	*£2.50
Stereo 60/2 Z30/PZ5	*£16.75
***Above package deal if sold with	
Project 60 kit and one other unit	
e.g. AFU, tuner or Q16 speaker	*£15.85
Stereo 60/2 Z30/PZ6	*£17.85
***Similar special deal for above	
Stereo 60/2 Z50/PZ8	*£20.25
Transformer for PZ8 (42V 2Amps)	*£2.45
Project 605	*£20.95
Project 60 FM tuner	*£19.50

### PROJECT 60 KIT

Our extremely popular kit contains the extra  
capacitors, DIN plugs and sockets, cables and  
fuse holder needed to complete Project 60 at the  
attractive price of \*£2.50.

## SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent.

Mail order only. Postage 37p per order on orders  
containing one or more items with prices marked  
with an\*. Postage on other orders 10p.

# I.C. OF THE MONTH

## L.A.J. IRELAND

Number 30

RCA CA3090Q Stereo Decoder

IN AUGUST 1970 this column reported on the introduction of a stereo decoder i.c., the Motorola type MC1303. In the interval this unit has proved very successful and certain commercial concerns are marketing decoder units based on this device. However, technology does not stand still; it was recognised that the elimination of the set of coils required in a standard stereo decoder would facilitate the assembly of units on a commercial basis.

Successful decoding demands the selection of the 19kHz pilot tone from the audio signal developed by the discriminator stage of the f.m. tuner, followed by the reconstruction of the 38kHz carrier by frequency doubling without degrading the phase relationship with the pilot tone. Replacement of the carrier into the 38kHz sideband permits demodulation of the "difference" signal; the audio components of the discriminator output provide the "sum" signal.

The final stage in decoding is the reconstruction of the separate right and left channels from the "sum" and "difference" signals supplied. To reduce noise in the subcarrier (38kHz) regeneration process, it is desirable that sharply tuned circuits be used to reduce the bandwidth about 19kHz when determining the pilot tone. This however, is in conflict with the requirement of phase coherence, since then slight detuning can introduce significant phase shift. Remembering that a channel separation of at least 20dB is the minimum acceptable in a stereo decoder and that less than 10° of phase shift in each of the three inductors alone can cause a reduction in channel separation approaching this figure, the care necessary in designing and aligning the coils can be estimated, even with a sound basic system such as the MC1303.

At this point it may be recalled that the introduc-

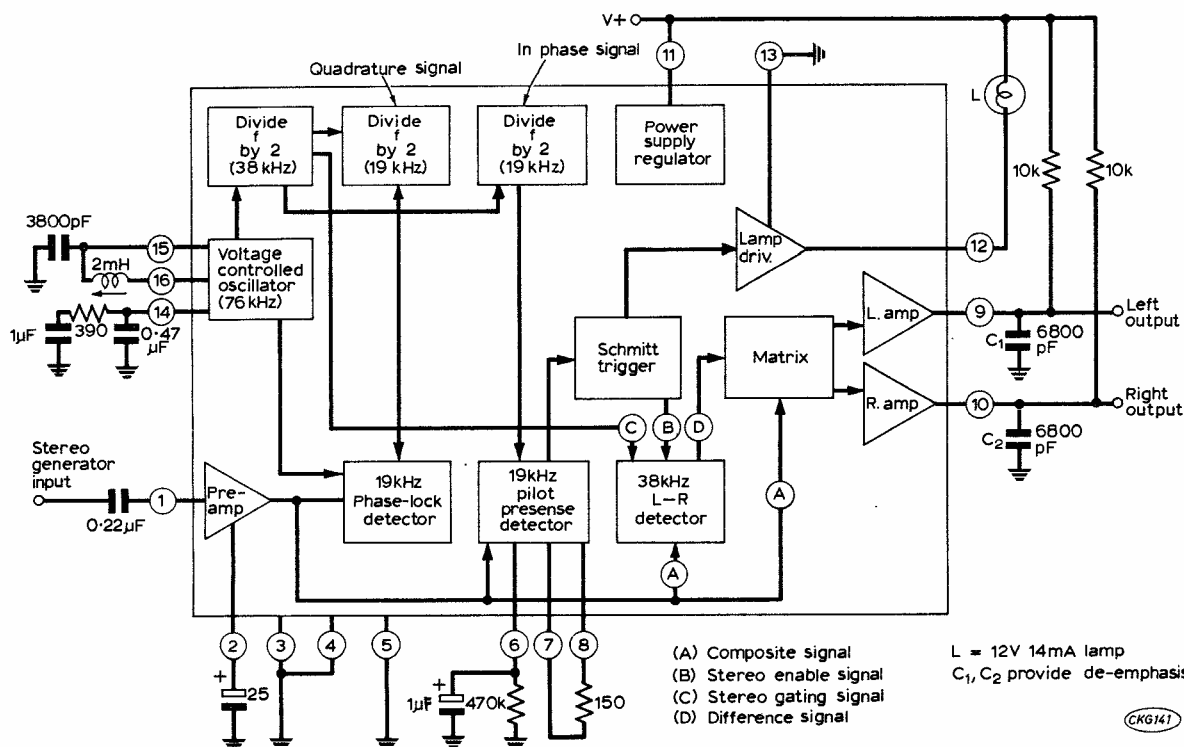


Fig. 1: The R.C.A. type CA3090Q phase-locked loop i.c. stereo decoder block diagram and applications circuit. In domestic tuner systems the f.m. discriminator is applied across the 0.22 μF capacitor.

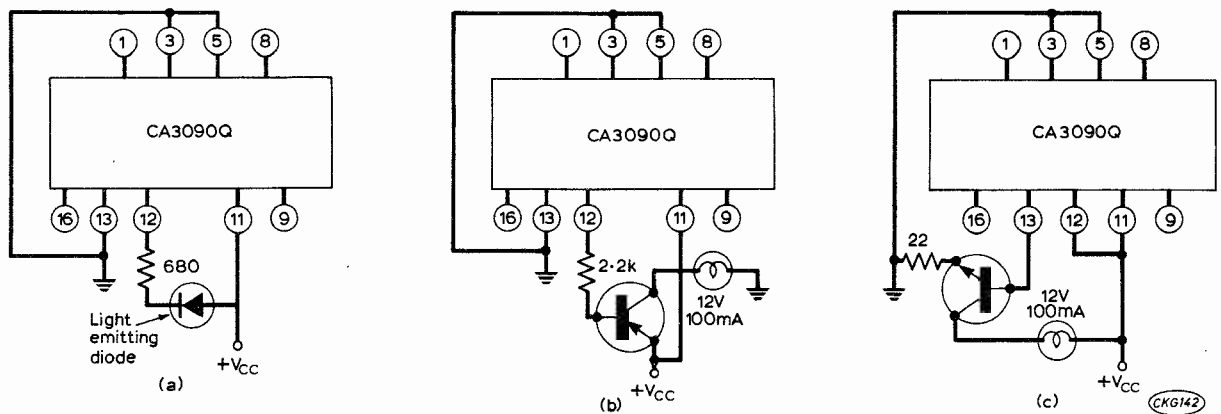


Fig. 2: Various methods of light indication (a) using a light emitting diode (b) PNP lamp driver (c) NPN lamp driver.

tion of monolithic silicon technology has opened an alternative route to the operation of tuned circuits, capable of eliminating to a great extent the requirements for precision LC circuits. It is, of course, the phase-locked loop circuit, first dealt with in "I.C. of the Month" in July 1971. Here, a local oscillator, whose operating frequency can be shifted by a limited amount by the application of an external voltage bias, drives a phase comparison circuit. The other input to the comparator is the external reference signal. The comparator output, a measure of frequency and phase separation of the local and the reference signal, feeds back to the local oscillator as an error voltage, correcting the local oscillator frequency.

The phase-locked loop i.c. considered last July was the Signetics NE561B system, suitable as an a.m./f.m. demodulator. This month exactly the same circuit concept is applied to the stereo decoder problem in the new R.C.A. Type CA3090Q. It is perhaps unnecessary to point out that by a phase-lock method, the problem of phase-shift degradation of channel separation is clearly avoided, and the need for design compromise between subcarrier circuit bandwidth and signal/noise ratio circumvented.

In the CA3090Q the loop local oscillator operates at a centre frequency of 76kHz and is followed by bistable frequency dividers, producing the 38kHz subcarrier at first division and 19kHz, the pilot tone frequency, at the second division. The frequency and phase comparison operation is carried out at 19kHz by reference to the received pilot tone, and the d.c. error voltage fed back to the local oscillator to maintain phase lock. Unlike the Signetics unit, the voltage controlled local oscillator of the CA3090Q is an LC oscillator, but the coil for this circuit is the only inductor required in the whole stereo decoder system, and even then alignment is non-critical. In point of fact, a 4kHz shift in local oscillator free-running frequency requires a correction voltage representing some 10° total subcarrier phase shift; the 40dB channel separation figure then achieved is highly satisfactory, Fig. 1.

Signals at 19kHz are derived from the local oscillator by division independently for the phase comparator already mentioned and for a stereo signal presence detector circuit. When the pilot tone exceeds a preset value, corresponding to an f.m. detector output (i.e. the "composite" stereo signal comprising a.f. "sum" signal, 19kHz pilot tone and 38kHz suppressed carrier "difference" signal) of 40

mV, a Schmitt trigger operates, switching the i.c. into stereo mode, with demodulation of the 38kHz signal and matrixing for channel separation, together with a suitable stereo reception signal. External indication of stereo operation is therefore directly available in a dial light, with the attractive possibility that this may be an l.e.d. solid state indicator, rather than a mere bulb, Fig. 2. A manual override to the automatic mono/stereo switching operation may be incorporated; the control voltage to secure this function is applied at pin 4 (shown earthed in Fig. 1).


The circuit incorporates an internal voltage regulator, a feature widely accepted in complex function i.c.'s since it eliminates the need for external decoupling of power supply lines, a decoupling which could well be ineffective anyway due to internal "crosstalk" on the chip. Further, in a complex circuit, the availability of pins for external connections is often a limiting factor, and economically more significant in production than a few extra transistors on the chip, which require consideration once and for all only at the design stage. The effectiveness of the internal regulation is indicated by the capability of the unit to function over a power supply voltage range of 10 to 16 volts.

Design of the actual decoder can be based on Fig. 1, which shows the actual circuit for a phase locked loop automatic stereo decoder with function indicator lamp. The coil is a 2mH unit, and may be wound on an adjustable pot core. The complexity of the unit can be judged by the fact that it has 128 transistors! Clearly an itemised analysis of circuit function would not find a place in this note, so Fig. 1 also provides a block diagram to assist the constructor who wishes to study the system more fully. For the majority of readers, though, it will be sufficient that in this i.c. there is available a first-rate stereo decoder which is simple to apply even if highly sophisticated in design.

The unit is supplied in a 16-pin quad-in-line plastic package, i.e. differing from the d.i.p. package in that alternate pins are displaced to provide four lines each of four pins. This facilitates the design and construction of suitable p.c. boards; it is recommended that an earth strip be left down the centre of the i.c., screening contacts on one side of the i.c. from those on the other. However, no difficulty should be experienced, even by the relative newcomer to construction, in achieving success with this unit. ■



# GOING BACK...

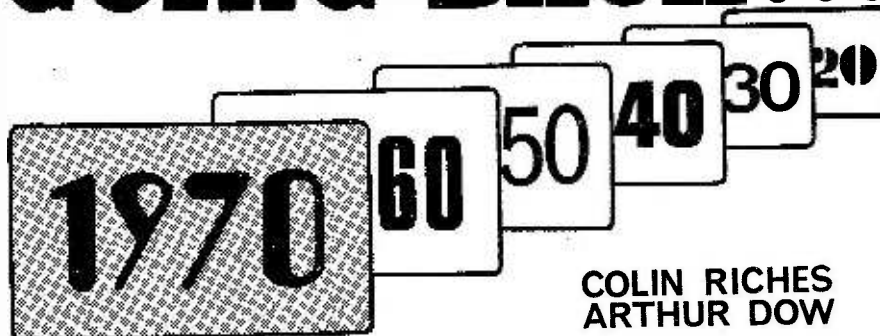


COLIN RICHES  
ARTHUR DOW


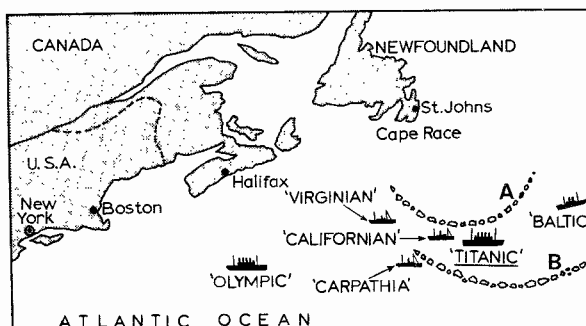
## TITANIC DISASTER - PART 2

Mr. Cyril Evans, examined by the Solicitor-General at the Court of Enquiry on the disaster, stated that he was the sole Marconi operator in the *Californian*. At 5.35 p.m. New York time, or 7.30 ship's time, he received a message from the steamship *Antillian* that an hour before she had seen three large icebergs to the southward. A little later he heard from the *Titanic* and offered her the report about the ice, and she replied, "All right, I heard the same thing from the *Antillian*". At 9.5 New York time, or 11 o'clock ship's time, the captain directed him to tell the *Titanic* that the *Californian* was stopped and surrounded by ice. He sent the message to the *Titanic* and got the reply, "Keep out." That was because the *Titanic* was at that moment in communication with Cape Race, and his message had caused an interruption. The *Titanic*, however, must have heard what he had said about the ice, because his signals were much stronger than the Cape Race signals. He next heard the *Titanic* say to Cape Race, "Sorry, please repeat". The messages from the *Titanic* to Cape Race were private messages from the passengers.

Mr. John Durrant, Marconi operator of the *Mount Temple*, was another witness. In reply to the Solicitor-General, he stated that the range of his wireless installation was 150 miles by day and 200 miles by night. On the evening of Saturday, April 13th—the day before the foundering of the *Titanic*—he got



Map showing the approximate positions of the *Titanic* and other ships.


an official message from the captain of the *Mount Temple* that ice had been seen. This was the only message he received in regard to ice before the wreck.

The witness then proceeded to give from his log-book the various calls he heard sent by the *Titanic* and the replies to them by ships which they reached.

The first thing he heard of the *Titanic* was at 11 minutes past 12 o'clock (ship's time) on Sunday night, when he got the message "C.Q.D." from the *Titanic*, giving her position, and adding, "Come at once. Struck berg. Advise captain." He told his captain at once. After the lapse of ten minutes he had the entry, "*Titanic* still calling C.Q.D.", that she was asked by the *Carpathia* what was wrong, and replied, "Struck iceberg. Come to our position," which was given. At 12.26 a.m. he made the entry—" *Titanic* still calling C.Q.D." At this time the *Mount Temple* had altered her course, and was speeding to the assistance of the *Titanic*. This had been done about 15 minutes after getting the first signal. At 12.34 he heard the *Frankfurt* answering the *Titanic* and the *Titanic* giving her position to the *Frankfurt*. The *Titanic* asked, "Are you coming to our assistance?" The *Frankfurt* said, "What is the matter with you?" and the *Titanic* answered, "Have struck an iceberg. Sinking. Come to our help. Tell captain." The *Frankfurt* then said, "O.K. Will tell bridge at once", and the *Titanic* replied, "O.K. Yes. Quick." At 12.42 he heard the *Titanic* calling "S.O.S."

At a quarter to 1 o'clock he heard the *Titanic* sending out both calls. She then got into touch with the *Coronia*, and next with the *Virginian*.

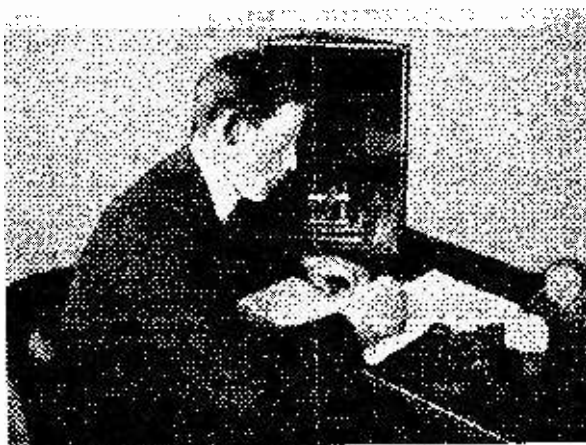The Solicitor-General then asked if Mr. Durrant had broken in and talked to the *Titanic* would he



H. T. Cottam, wireless operator on board the "*Carpathia*".

have interrupted her messages to other ships? Yes, I never said a word after I got her position. The first rule in wireless telegraphy is "Never Interfere".

The witness, continuing the narrative from his log-book, said the *Titanic* called the *Olympic* at 12.43 a.m. The *Olympic* replied at 1.06 a.m. and got the message, "Get your boats ready. Going down fast by the head." At 1.11 the *Frankfurt* sent a message to the *Titanic*, "Our captain will go for you". At 1.13 he heard the *Titanic* working the *Baltic*.

The witness said the *Titanic* answered the *Olympic*, "We are putting the women off in the boats". At 1.29 the *Titanic* sent out a general call. "C.Q.D. Engine-room flooded". The *Titanic* also informed the *Olympic* that the sea was clear and calm. At 1.31 he heard the *Frankfurt* say to the *Titanic*, "Are there any boats round you already?" and to this the *Titanic* made no reply. At 1.33 he heard the *Olympic* send a message to the *Titanic* asking whether the *Titanic* was steering south to meet the *Olympic* and the reply of the *Titanic* was simply the code word for "Received". That was the last message that he heard from the *Titanic*. The messages from the *Titanic* did not get fainter towards the end. When the messages ceased, he thought the flooding of the engine-room had put the wireless out of condition. Most ships, including his own, carried storage batteries for use when power could not be obtained from the dynamos, and the wireless apparatus could be changed from the dynamos to the storage batteries in a minute: but the range of a wireless using storage batteries would be less than that of a wireless using dynamos.

At 1.41 a.m. he heard the *Frankfurt* and the Russian ship, the *Birma*, calling the *Titanic* and there was no reply. At 1.56 the *Olympic*, the *Frankfurt*, and the *Baltic* called, and again there was no

answer from the *Titanic*. At 2.11 the *Birma* informed the *Frankfurt* that she was 70 miles from the *Titanic*. At 2.36 he made the entry, "All quiet now. The *Titanic* has not spoken since 1.33." At 3.11 he heard the *Carthia* say, "If you are there, we are firing rockets." At 3.26 the *Carthia* again called the *Titanic*. At 3.44 the *Birma* told the *Frankfurt* that he thought he heard the *Titanic* and calling her, said, "Steaming full speed to you. Shall arrive 6 in the morning. Hope you are safe. We are only 50 miles away." At 3.46 he heard the *Carthia* calling again. At 4.40 he made the entry, "All quiet. We are stopped away. Pack ice." At 5.11 the *Californian* called "C.Q.", and he answered telling her that the *Titanic* had struck an iceberg and sunk, and he gave her the position. At 5.26 he heard the *Californian* speaking to the *Frankfurt*, and she replied to the same effect. His last entry was, "8 a.m. Heard from *Carthia* that she had rescued 20 boatloads".

## P.M.G. Comments

The Right Honourable Herbert Samuel, M.P., Postmaster-General, referring to the disaster at the dinner of the London Chamber of Commerce on April 18th, 1912, said:

"Those who had been saved had been saved through one man, Mr. Marconi, whose wonderful invention was proving not only of infinite social and commercial value, but of the highest humanitarian values as well." He had seen it stated that in the United States of America the efficiency of the wireless telegraphy service had been impaired by lack of regulation. He did not know whether that was well founded or not, but as Postmaster-General he could assure them that such disturbance was impossible here. Parliament had given the Postmaster-General a complete control over the use of wireless telegraphy, and no one could operate or establish a station without the Postmaster-General's licence, which was only very sparingly given, and for purposes of experiment and research and under such conditions which precluded disturbance of commercial or humanitarian messages. Round the coast, in charge of his department, there was a girdle of wireless stations which were in constant communication with the telegraphic services of the country and with the life-saving stations. No fewer than 400 liners had been equipped with wireless apparatus, including a certain number of cargo vessels. All the operators on these ships were required to hold a Post Office Certificate of Efficiency, and to answer immediately any signals of distress, and under conditions which, as far as possible, precluded interference with one another.

## David Sarnoff

David Sarnoff was on duty at the Marconi Wireless Telegraph Co. of America station at Saisconset on Nantucket Island. On the night of April 14, 1912, he picked up the messages that told of *Titanic's* distress signals and he stayed on duty continuously for 72 hours so that he could relay messages from the rescue ship to the rest of the world.

Brig. General David Sarnoff, born in a small village near Minsk in Russia, in 1891, and former Chairman of the Board of R.C.A. passed away on December 12th, 1971.



Mr. John Durrant, operator on the "Mount Temple".

# See the world as a skilled technician.

## 250 apprenticeships available

Apply now for a skilled technician apprenticeship in the Royal Navy. You'll be given just about the finest technician training – with the opportunity to take your O.N.C.

Within a few years you'll be maintaining and operating vital Navy equipment: radar, missiles, electronic systems, computers, gas turbines, aircraft.


Completion of training will bring you a salary over £2,000 a year. With plenty more to come.

You'll have a great time, with world travel, sport and adventure.

And, with your training, you'd be sure to get a good job when you return to civilian life.

So, if you're 15½-21, and of 'O' level standard in Maths, and Science or English – or have a good C.S.E. in certain subjects – there's a great future for you in the Navy. Send now for the free booklet.

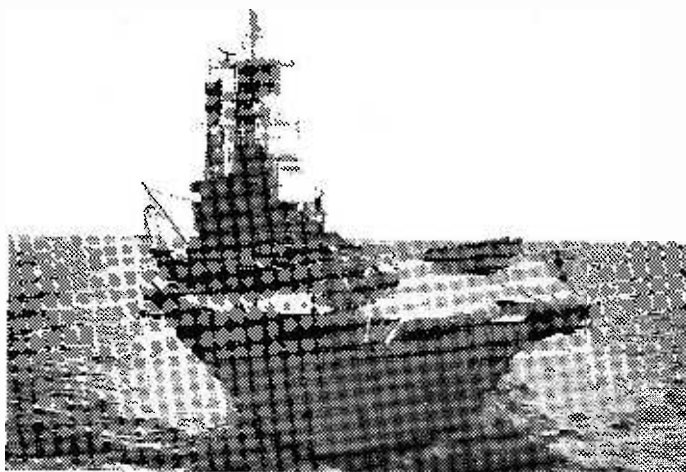*Our next Apprentice entry is in September.*



### SEND FOR FREE BOOK

Name \_\_\_\_\_

Address \_\_\_\_\_

Date of birth \_\_\_\_\_

Royal Naval Careers Service (Apprenticeships)  
(830FL1), Old Admiralty Building,  
Whitehall, London, SW1A 2BE.  
Please send me, without obligation,  
my free "Navy Technician  
Apprenticeships" Booklet.



## BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9090

0A2	30	6BW6	72	6RT6	35	12807	35	30EH5	55	EB34	20	EL32	18	KTW61	63	PL83	30	UF41	30	AC107	15	BCV12	50	0A85	09		
0B2	30	6BW7	50	6BA7GT	35	12807	23	50L6GT	45	EB91	10	EL35	1.00	KTW63	50	PL504/500	0F80	35	AC126	13	BCV34	23	0A202	10			
0Z4	25	6BZ6	31	6BA7M	35	128H7	15	85A2	43	EB41	48	EL37	74	MHL06	75	0F85	34	AC127	17	BCV38	23	0C22	38				
1A3	32	6CB6A	32	6BC7GT	33	128J7	23	90C1	59	EB681	29	EL41	53	N78	2.05	PL505	1.30	PF86	63	AC128	20	BCV39	95	0C23	38		
1A7GT	32	6C4	28	6BC7GT	33	128K7	24	150B2	58	EBF80	30	EL42	53	N308	1.30	PL508	1.30	PF89	27	AC132	20	BCV41	95	0C24	38		
1B3GT	35	6C9	73	6BH7	53	128Q7GT	307	59	EBF83	36	EL81	50	N339	1.44	PL509	1.30	UL41	54	AC154	25	BCV58	29	0C25	38			
1H5GT	33	6CD6G	1.08	6BJ7	35	50	50	50702	80	EBF89	26	EL83	39	P61	44	PL802	75	UL84	28	AC156	20	BCV59	25	0C26	60		
1L4	13	6CH8A	50	6BK7GT	23	14H7	48	5763	50	EBL21	60	EL84	41	PABCS0	32	PM84	31	UM30	33	AC157	25	BCV63	20	0C29	63		
1N5GT	37	6CH6	38	6BQ7GT	38	1487	75	AC2/PEN	EC86	59	EL85	59	EL86	40	PC86	44	PM4	1.16	UY41	38	AC165	25	BCV67	38	0C30	32	
1R5	26	6CL6	43	6L4GT	60	19A05	24	98	EC88	59	EL86	38	PC88	44	PM4	1.16	UY41	38	AC166	25	BCV68	30	0C36	43			
1S4	22	6CM7	50	6V6G	27	19B06G	80	AC2/PEN	EC92	34	EL91	23	PC95	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63			
1U4	29	6CU5	30	6V6GT	20	19G6	50	DD	98	EC93	1.50	EL93	32	PC97	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63		
1U5	45	6CW4	35	6X4	20	20D4	1.05	AC6/PEN	EC93	1.50	EL93	32	PC97	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63			
2D21	35	6DE7	50	6X4GT	25	20F2	65	AC6/PEN	EC94	60	EL94	32	PC98	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63			
2GK5	50	6DT6A	50	7A7	28	20L1	95	98	EC98	1.16	EM80	37	PC98	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63			
3A4	25	6EW6	55	7B6	58	20P1	50	AC/TTP	EC98	1.16	EM81	37	PC98	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63			
3D6	19	6F1	59	7B7	32	20P2	78	AL60	78	EC93	21	EM81	37	PC98	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63		
3Q4	35	6F6	63	7C6	30	20P4	89	ATP4	12	EC94	28	EM84	31	PC98	53	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63		
3Q6GT	35	6F6G	25	7H7	28	20P5	1.00	AZ1	40	EC95	32	EM85	1.00	PCF80	26	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63		
3S4	25	6F13	33	7H7	28	20P5	1.00	AZ1	40	EC95	32	EM85	1.00	PCF80	26	PM36	2	UY10	45	AC168	38	BCV68	40	0C42	63		
3V4	35	6F14	40	7Y4	60	25L6G	20	AZ41	53	EC98	35	EY51	29	PCF84	40	QQV03/10	1.20	UC81	40	AD140	36	RY127	18	0C76	15		
4CB6	50	6F18	45	7Z4	50	25Y3	38	CL33	90	EC98	35	EY81	35	PCF86	44	1.20	UC82	40	AD149	50	RY210	25	0C77	27			
5C6G	50	6P23	68	9D7	78	25Y3G	49	CV63	53	EC98	35	EY82	34	PCP200	67	Q895/10	49	UC301	40	AD161	45	RY211	25	0C78	15		
5V4G	33	6P24	68	10C2	49	25Z4G	28	CV10	53	EC98	35	EY84	50	PCP801	28	QV04/7	43	UC403	33	AD162	45	RY212	25	0C79	15		
5Y3GT	25	6P25	51	10D1E7	50	25Z5	40	CV11	29	EC98	35	EY87/67	27	PCP802	37	R10	75	UC404	38	AD163	40	RY213	25	0C80	11		
5Z4G	33	6P28	60	10F9	75	25Z6G	43	DAF91	25	EC98	35	EY88	50	PCP803	37	R10	75	UC405	38	AD164	40	RY214	25	0C81	11		
6A8A	50	6P32	68	10P13	54	30A05	44	DAF95	25	EC98	35	EY91	53	PCP804	37	R10	75	UC406	38	AD165	40	RY215	25	0C82	11		
6A8G	33	6G8H8A	50	10F18	35	30C15	53	DF91	14	EC98	35	EZ40	40	PCL82	29	R17	88	VP23	40	AD115	15	FSY41A	23	0C82D	11		
6ACT	15	6GK5	50	10D1E7	50	30C17	74	DP96	34	2.10	EZ41	42	PCL83	54	R19	28	VP41	38	AD117	19	G89	20	0C83	20			
6AG5	25	6GUT	50	10P13	54	30C18	58	DH76	28	EC98	35	EZ80	19	PCL84	32	SP42	75	VT61A	35	AD121	30	G8T113	20	0C84	24		
6AK6	30	6H6GT	15	10P14	1.08	30F2	61	DK40	55	EC98	35	EZ82	19	PCL85/63	32	SP41	75	VT611	44	AD124	25	G8T118	20	0C85	23		
6AM5A	50	6K7G	22	12A67	19	30P12	87	EH0F	1.20	EC98	35	EZ84	30	PCL86	32	TP23	50	VT612	50	AD125	25	G8T119	20	0C86	23		
6AN8	40	6JGT	39	12A6	40	30P12	87	EH0F	1.20	EC98	35	EZ85	30	PCL86	32	TP23	50	VT613	50	AD126	18	G8T123	38	0C140	95		
6AN5	21	6J6	18	12A65	40	30P12	87	DL96	55	EC98	35	EZ86	34	GZ30	33	PCL86	32	TP23	50	AD129	35	AF139	65	G8T587	43	0C169	95
6AR5	30	6J7G	24	12A66	40	30P12	87	DM70	30	EC98	35	EZ88	33	GZ32	39	PENADD	1.38	UCF80	30	W167	50	AF178	68	G8T873	15	0C172	35
6AT6	18	6J7GT	24	12A67	19	30P12	87	DM71	38	EC98	35	EZ89	33	GZ33	70	1.38	UCF42	49	W279	60	AF180	48	G8T887	23	0C200	32	
6AUF6	19	6J7A8A	50	12A7	19	30P12	87	DP96	34	2.10	EZ89	33	GZ34	67	PEN45D1D	1.38	UCB41	45	X41	50	AF186	55	G8T897	23	0C201	38	
6AV6	28	6K7G	10	12A7	19	30P12	87	DP96	34	2.10	EZ90	33	GZ37	67	75	UCB81	40	Transistors	40	AF239	55	G8T898	23	0C202	43		
6AW8A	50	6K7GT	22	12A7	19	30P12	87	DP96	34	2.10	EZ90	33	GZ38	67	75	UCB81	40	Transistors	40	AF239	55	G8T898	23	0C202	43		
6AX4	30	6K8G	18	12A7	19	30P12	87	DP96	34	2.10	EZ90	33	GZ39	67	75	UCB81	40	Transistors	40	AF239	55	G8T898	23	0C202	43		
6B8G	13	6L1	98	12A7	19	30P12	87	DP96	34	2.10	EZ90	33	GZ40	67	75	UCB81	40	Transistors	40	AF239	55	G8T898	23	0C202	43		
6BA6	20	6L6GT	39	12A6A	30	30P11	57	E92CC	40	EF40	49	HL42DD	40	4020	38	UC92	35	2N2927	22	BA116	25	OA5	28	0C204	30		
6BC8	50	6L7	38	12B6	30	30P13	75	E180F	90	EF41	58	HL42DD	40	4020	38	UC92	35	2N2927	22	BA116	25	OA5	28	0C204	30		
6BE6	20	6L18	44	12B7	27	30P14	62	E182CC1	00	EF42	58	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BG6G	1.05	6L19	1.38	12J5GT	30	30P15	87	E1148	35	EF54	58	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BH6	43	6L2D	48	12K5GT	33	35A3	49	EAB0	18	EF73	75	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BJ6	39	6L7GT	40	12K3	50	35L6GT	42	EAB6	18	EF73	75	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BQ7A	39	6Q7	49	12K7GT	34	35W4	42	EABCS0	29	EF80	48	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BR7	79	6Q7G	27	12S7GT	35	35Z4GT	24	EAC91	38	EF85	25	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53		
6BR8	63	6R7	55	40	35Z5GT	30	EAF42	48	EF86	27	HL42DD	40	4020	38	UC92	35	2N2927	22	BA130	10	OA10	43	ORP12	53			

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business -- Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p. per order. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale price 7p. post paid. Business hours Mon-Fri, 9-5.30 p.m. Sats, 9-1 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

**BELLING LEE INSULATED TERMINALS.** Red or Black, 5 amp. max. 10p pair, pp 3p

**BERCOSTAT WIREWOUND RHEOSTAT.** 50 volt, 800  $\Omega$  25 watts, 2" dia. 25p. pp 7p.

**FINNED ALUMINIUM HEATSINK** 9" x 1 1/2", Ready Drilled. 20p, pp 6p

**SMITHS CIRCULAR TAPE POSITION INDICATORS** Resettable, 50p, pp 5p.

**G.E.C. 5 AMP 240 VOLT A.C. CIRCUIT BREAKER.** 75p, pp 10p

**SUB MIN CROC CLIPS.** Red or Black, insulated 4p. Min. quantity, 6 pp 3p.

**GARRARD MAG TAPE DECKS:** 11ps, 50v solenoid operated brakes etc., Mains voltage motors £7-50 each, pp £1-23.

**4 1/2" PLANNAIR FANS.** Complete, capacitor, ex-equip. 2,800 r.p.m. £3-50, pp 40p.

**ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON.** 250v. Single Phase A.C.  
 1 h.p. 1,440 r.p.m. £3-75 pp £1-00  
 1 h.p. 1,425 r.p.m. or 2,800 r.p.m. £6-75 pp £1-25  
 1 h.p. 1,410 r.p.m. £3-75 pp £1-25

**AUDIO CONNECTORS**  
 3 pin Din Plug .. 13p each  
 5 pin Din Plug A type, B type .. 13p ..  
 2 pin Din Speaker Plug/socket .. 10p ..  
 3 pin Din Line Socket .. 13p ..  
 3-5mm Jack Plug Screened .. 10p ..  
 Standard Jack Plug .. 10p ..  
 Screened Standard Jack Plugs .. 15p ..  
 Stereo Jack Plug .. 13p ..  
 Screened Stereo Jack Plug .. 18p ..

**Phono Plugs:** Red or Black 3p each.  
 pp on above items 3p.

**B.S.R. MINI AUTO-CHANGER.**  
 Mono Cartridge £4-75 pp 30p.

**MAINS NEONS.**  
 Red or Green. Size: 1" x 1 1/2" 15p, pp 3p

**LEVER ACTION P.O.1000 TYPE SWITCHES.**  
 Lock 4-pole changeover 15p, pp 3p. (ex-equip.)

**Lock 2 Pole Changeover 10p pp 3p.** (ex-equip.)

**AUDIO LEADS**  
 Screened Phono Leads 46" long, 15p  
 3-5 mm JACK/3-5mm JACK 7' 6" long 40p  
 5-Pin Din A Type, 5-PIN A TYPE. Approx 5' long 70p. pp above items 5p.

**PIEZO DYNAMIC MICROPHONE**  
 50k  $\Omega$  £1-00 pp 8p.

**MULLARD SCREW TERMINAL CAPACITORS.**  
 4,500 uf 64v. 7100 uf 40v. 50p each pp 10p.

**BELLING LEE 1-5 amp** line rubber covered interference suppressor 25p pp 8p.

**RUBBER 3 PIN 5 AMP NON REVERSIBLE CABLE CONNECTORS** 20p pp 5p.

**FIBRE GLASS TAPE 3" wide 50 yd. roll.** 50p pp 20p.

**SOLENOIDS 12 VOLT PULL ACTION**  
 2" x 1" x 4" 40p pp 8p.

**STC SEALED RELAYS DOUBLE POLE CHANGEOVER**  
 48v 2500 Ex-equip. 15p pp 5p.

**SIMMENS MINIATURE RELAY.** Double pole changeover dust cover/base 48v 2500 50p pp 5p new.

**STC MINIATURE RELAY 280 Ohm Perspex Cover** 6-15v new. 35p pp 5p.

**GARDNER'S POTTED TRANSFORMER** 0-250v Input: 18v 500mA 50v 150 mA, 6v 250 mA Output. Size 3" x 2 1/2" x 2 1/2". £1-00, pp 20p. Ex equip tested.

**TELESCOPIC AERIALS**  
 Chromed 7" closed 28" extended 6 section ball jointed base 23p pp 8p new.

**MULLARD 4 DM 160 INDICATORS** in plastic holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 1 1/2" 36p pp 8p.

**PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200**  
 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/ resistors. Power supply 22v 250 mA DC. Output 240v. AC £1 pp 20p ex-equip.

**TOGGLE SWITCHES.** Single pole Double Throw ex-equip. new condition. 50p doz. pp 18p.

**PAINTON PLUG SOCKETS** Type 159 series working voltage 350v AC/DC current max. 3 amp AC/DC 7 pin plug & socket 50p pp 6p. 15 pin plug & socket £1 pp 6p. 31 WAY PLUG & SOCKET. £1-50 pp 6p.

CASH WITH ORDER PLEASE

## FIELD ELECTRIC LIMITED

3 Shenley Road,  
 Borehamwood, Herts.  
 Adjacent Elstree Mainline Station  
 Tel: 01-953 6009.

# C. HADLEY

24, WOODHILL,  
 HARLOW, ESSEX

Add 5p. P. & P. Price list 10p  
 or free with orders.

All our stocks are brand new with money back guarantee

AC107 15p	BC108 8p	BFY51 12p	OC72 13p	2N2646 47p	AD161, AD162 M/P 58p
AC126 13p	BC109 8p	BSY95A 15p	OC81 13p	2N2926 10p	1-9 58p
AC127 17p	BC154 20p	ME0402 18p	OC81D 13p	2N3053 20p	10 plus 55p
AC128 13p	BC168 10p	ME0404 14p	OC83 20p	2N3055 49p	
AC176 25p	BC169 11p	ME4101 10p	OC170 24p	2N3702 13p	
AC141K 20p	BC182L 8p	ME4102 12p	OC200 25p	2N3704 13p	
AC142K 20p	BC185L 8p	ME6002 14p	OC201 25p	40531 49p	
AD145 40p	BC184L 8p	ME6101 14p	OC25 25p	40636 55p	
AD150 44p	BC212L 8p	ME6102 15p	OC28 32p	IN4601 4p	
AD161 M/P58p	BC214L 8p	MP8111 32p	OC29 36p	IN4602 4p	
AD162 58p	BD116 78p	MP8511 34p	OC35 28p	IN4603 5p	
AL102 58p	BD121 50p	MP8513 45p	OC36 38p	IN4604 7p	
AL103 49p	BD130 46p	OC41 13p	2N697 18p	OA90 6p	
AL103 85p	BD131 59p	OC44 13p	2N1171 24p	OA91 6p	
AL111 85p	BF194 15p	OC45 13p	2N1304 25p	IN4148 4p	
BC107 8p	BFY50 15p	OC71 12p	2N1305 25p	WO2 32p	

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
 250V F.C. mounting: 0-01 $\mu$ F, 0-015 $\mu$ F, 0-022 $\mu$ F, 3p. 0-033 $\mu$ F, 0-047 $\mu$ F, 0-068 $\mu$ F 3p. 1 $\mu$ F, 4p. 0-15 $\mu$ F, 0-22 $\mu$ F, 5p. 0-33 $\mu$ F, 6p. 0-47 $\mu$ F, 8p. 0-68 $\mu$ F, 11p. 1-0 $\mu$ F, 13p. 1-5 $\mu$ F, 20p, 2-2 $\mu$ F, 24p.

**Miniature Fixed Ceramic Plate. C333 Series, 3p each.**  
 63V dc wkg. 1-5pF, 2-2pF, 2-7pF, 3-3pF, 3-9pF, 4-7pF, 5-6pF, 6-8pF, 8-2pF, 10pF, 12pF, 15pF, 18pF, 22pF, 23pF, 33pF, 39pF, 47pF, 56pF, 68pF, 82pF, 100pF, 120pF, 150pF, 180pF, 220pF, 270pF, 330pF.

**ELECTROLYTIC CAPACITORS MULLARD C426 SERIES**  
 6p each  
 ( $\mu$ F/V) 10/2-5, 40/2-5, 80/2-5, 160/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 35/6-4, 50/3-4, 100/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 250/10, 500/10, 10/15, 20/15, 40/15, 80/15, 125/15, 1-6/25, 0-4/25, 12-5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

**MULLARD C437 SERIES**  
 100/40, 160/25, 250/16, 400/10, 640/6-4, 800/4, 1000/2-5, 9p. 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/6-4, 1600/2-5, 12p. 160/64, 250/40, 400/2-5, 640/16, 2000/4, 1000/10, 1600/6-4, 2500/2-5, 15p. 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6-4, 4000/2-5, 18p.

<b>RESISTORS</b>	<b>BARGAIN TTL's</b>	15p each
1 watt 10% carbon	7400, 01, 02, 03, 04, 10, 20, 30, 40, 50,	
1 watt 10% carbon	51, 53, 54	35p each
range 2-20 ohms to 10 megohms type TR5	7442, 70, 72, 73, 74, 76, 86.	
triple rated 1-1/3, tin oxide $\pm 2\%$	<b>★ Super Low Priced Linear I.C.'s</b>	
range 10 ohms to 1 meg.	709c TO99 .. 28p	
	709c DIL .. 32p	
	741c TO99 .. 38p	
	741c DIL .. 36p	
	747c DIL .. 42p	

**MINIATURE NEON LAMPS** 5p each  
 HB1725 1-9mA 230v.  
 SB1725 0-6mA or 115v.

## LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8-15 ohm ..	£19-50
Fane Pop 60 watt 15" 8/15 ohm ..	£11-15
Fane Pop 50 watt 12" 8/15 ohm ..	£9-25
Fane Pop 25/12" 20 watts ..	£5-40
Fane Pop 15 12" 10 watts ..	£4-00
Top 20 12" 25 watt 8 or 15 ohm ..	£5-75
Hiten 10" 10 watt 8 or 15 ohm ..	£3-00
Baker Group 25 12" 25 watt 8 or 15 ohm ..	£5-75
EMI 13 x 8, 3 or 15 ohm ..	£2-00
EMI 13 x 8 with Tweeter 3, 8 or 15 ohm ..	£2-50
EMI 13 x 8 twin tweeter 3, 8 or 15 ohm ..	£3-60
Celestion 8" Round 15 ohm ..	£2-05
Celestion PS8 for Unilux ..	£2-35
Richard Allan 8" 3 or 15 ohm ..	£2-35
Fane 8" dual cone 8 ohm ..	£2-75
Elac 6 1/2" dual cone 8 ohm Cer. mag. ..	£2-25
Philips Hi-Fi 20 watt type EL7032 dual cone 12" 35-17000 hz. ..	£3-50
Elac 59RM109 ..	£2-70
2", 2 1/2" or 3" 80 ohm ..	£6-50
7 x 4, 3 or 8 ohm ..	£1-50
10 x 6, 3, 8 or 15 ohms ..	£1-80
Elac 8 x 5 58E/172 3 ohm ..	£1-60
Goodmans 8P, 8 or 15 ohm ..	£4-50
Goodmans 10P, 8 or 15 ohm ..	£4-50
Goodmans 12P, 8 or 15 ohm ..	£5-95
Goodmans 15P, 8 or 15 ohm ..	£16-00
Goodmans 18P, 8 or 15 ohm ..	£25-00
12" round 3 or 15 ohms ..	£2-50

FREE with orders over £6—"Hi-Fi Loudspeakers Enclosures" book.

All units guaranteed new and perfect.  
 Prompt despatch p. & p. 25p per speaker.

**WILMSLOW AUDIO, M. O. Dept.**  
 10 Swan St., Wilmslow,  
 Cheshire, SK9 1HF

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
 7 element 2-25, 11 element 2-75, 14 element 3-18, 18 element 3-75.  
**WALL MOUNTING c/w WALL ARM & BRACKET**  
 7 element 3-25, 11 element 3-75, 14 element 4-25, 18 element 4-75, CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT, 7 element 4-00, 11 element 4-50, 14 element 4-75, 18 element 5-25, MAST MOUNTING arrays only, 7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd. KING TELEBOOSTERS from 3-75. LABGEAR all band U.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. Static clearly channel number, required on all orders. P.p. on all aerials 50p. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

**BBC—ITV—FM AERIALS**  
 BBC (band 1) Wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00. ITV (band 3) 5 element loft array 2-50. 7 element 3-00. COMBINED BBC—ITV, loft 1-5 2-75, 1-7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3-75. COMBINED U.H.F.—V.H.F. aerials 1-5+9-4 4-00, 1-5+14 4-50, 1-7+14 5-00. F.M. RADIO loft S/D 1-00 3 element 3-25, 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

**CALLERS WELCOMED**  
 OPEN ALL DAY SATURDAY  
**K.V.A. ELECTRONICS**  
 40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
 Telephone 01-648 4884

### E.M.I. 13 1/2" x 8" LOUDSPEAKERS

10 watts, 8 ohms with crossover and two tweeters.  
£3.25. P. & P. 40p.

### GOODMANS AXIOM 301

20 watts, 8 ohms, 12" 30-16kcs.  
£21.00. P. & P. 50p. Limited number. Cancelled export order.

### 7" E.M.I. PROFESSIONAL LONG PLAY TAP 1,200 ft

£1.25. P. & P. 25p.

### FANE 13" x 8"

15 watt, 8 ohms. Dual cone.  
£3.00. P. & P. 40p.

### BUSH ARENA HI-FI

### STEREO AMPLIFIER

10 watts R.M.S. per channel. 25-20,000Hz. -3db.  
Harmonic distortion less than 1%.  
£32.00. P. & P. 75p.

### TRIO AMPLIFIERKA 2000A

£37.50. P. & P. 75p.

### TRIO KT 1000A TUNER

£56.50. P. & P. 75p.

### TRIO KT 2001 TUNER

£63.50. P. & P. 75p.

### TRIO KA 4002 AMP.

£57.50. P. & P. 75p.

### E.M.I. SPEAKERS

13" x 8" Tweeters. Fitted in Teak cabinets. 10 watts, 8 ohms.  
£22.50 Pair. P. & P. 75p.

## 100 WATT ALL-PURPOSE AMPLIFIER

- ★100 watts continuous sine wave output into 8 ohms.
- ★4 high impedance inputs, allowing mixing facilities for all types of equipment to match any signal.  
Input 1 250mV } Suitable for crystal or ceramic  
Input 2 100mV } cartridge radio tuner, etc.  
Input 3 5mV } Suitable for all mics and guitars.  
Input 4 5mV } Input impedance 100K.
- ★Separate volume controls on each input.
- ★Master volume, treble and bass controls.
- ★40db variation on treble control at 12KHz.  
40db variation on bass control at 60Hz.
- ★Frequency response 20Hz-25KHz ±2db.
- ★Short and open circuit protection on output stage
- ★Standard 240V-120V mains operation.  
£34.20. Post paid.

## 50 WATT ALL-PURPOSE AMPLIFIER

- ★50 watts continuous sine wave output into 8-15 ohms.
- ★One dual input high gain channel with individual volume control, matches any mic, guitar, etc.  
Sensitivity 5mV into 500K.
- ★One dual input low gain channel with individual volume control, matches crystal or ceramic cartridge, radio tuner, etc. Sensitivity 100mV into 500K.
- ★Master volume, treble and bass controls.
- ★35db variation on treble control at 12KHz.  
34db variation on bass control at 60Hz.
- ★Frequency response 20Hz-30KHz ±2db.
- ★Short and open circuit protection on output.
- ★Standard 240 volt mains operation.  
£36.65. Post paid.

### AMSTRAD 8000 MK II

£16.50. P. & P. 50p.

### AMSTRAD IC2000

£27.50. P. & P. 50p.

### H.L. AUDIO SA707

£16.50. P. & P. 50p.

### AMSTRAD 138 SPEAKER SYSTEM

£19.90 Pair. P. & P. £1.25

### PLYNTHS & COVERS

For SP25, MP60, 2025, SL5B5, 3000.  
£3.20. P. & P. 35p.

### STEREO HEAD PHONES

Binatone £2.60.  
Amstrad HP5, 5A £6.95  
Amstrad HP5, 7A £12.95.  
Post free.

### E.M.I. 13" x 8" BASS SPEAKERS

12 watts R.M.S. 8 ohms with cross over.  
£5.00. P. & P. 50p.

### ELAC

10 watts. With 8" round metal tweeter. 8 ohms.  
£3.00. P. & P. 40p.

### SP25 MK III

£12.00. P. & P. 50p.


### 2025T/C

with cartridge £9.00. P. & P. 50p.

S.A.E. FOR LEAFLETS

*Linovale Radio Ltd.* 48 HOE STREET LONDON E.17 01-520-7546

## SHORTWAVE TRANSISTOR RADIO

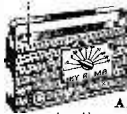

only  
£2.75

Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 74 stations logged on rod aerial in 30 mins. — Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" Only £2.75 + 20p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

## INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY  
£3.25



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even steps by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. SEND £3.25 + 20p p. & p. (parts available separately).

## ELECTRONIC ORGAN



ONLY £3.25

Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. SELF CONTAINED LOUDSPEAKER. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions. ONLY £3.25 + 20p p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4.95



FULLY TRANSLATORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! £4.95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2.75 extra if required.) EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

## FIND BURIED TREASURE!

### Transistorised Treasure Locator



ONLY £2.85

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2.85 + 20p p. & p. (Sectional handle as illustrated 30p extra). Parts available separately. Made up looks worth £15!

## Eavesdrop on the exciting world of Aircraft Communications

### V.H.F. AIRCRAFT BAND CONVERTOR



ONLY £2.85

Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripping decisions in emergency—Tune into the international distress frequency. Cover the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). NO CONNECTIONS WHAT-EVER NEEDED. SEND ONLY £2.85 + 20p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON



Only £2.75

CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to make out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost self-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, components, nuts, screws, wire, etc. no soldering. £2.75 + 20p p. & p. Parts available separately.

## BUILD 5 RADIO AND ELECTRONIC PROJECTS

only £2.45




Amazing Radio Construction set! Become a radio expert for £2.45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send £2.45 + 20p p. & p.

CONCORD ELECTRONICS LTD. (PW6U) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.-6 p.m. inc. Saturday





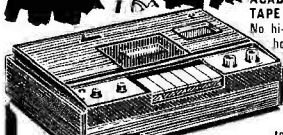
# "Where can I get exclusive ROC ELECTRONICS!"



**ROC PRICE**  
**£42.00**  
Including two pencil microphones and all connecting leads  
Normal Price £65.00
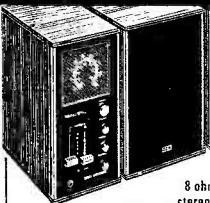
## ACADEMY STEREO CASSETTE TAPE DECK, MODEL CS-2000D

No hi-fi system is complete without one—hook it up to any ROC or other good quality amplifier, and the results are fantastic! The CS-2000D records and plays back. A big feature is its easy-to-use piano-key controls. Easy-to-get-at mic inputs are on top; line inputs and outputs at the rear. Dual-channel recording level meter. Pop-up cassette ejection. Stereo/Mono button. Tape counter. Pause control. Tape speed 1½ ips (4-75 cms). Frequency response 100-10,000 Hz. Wow and flutter better than 0.3%. Rewind time better than 60 sec with C60 cassette. Engineered throughout to the highest electrical and mechanical standards. Size 18" wide, 4½" high and 8" deep. Walnut cabinet with satin aluminium trims.



**ROC PRICE**  
**£70.99**  
Including connecting leads  
Normal Price £115.00

## REALISTIC HI-FI 36-WATT STEREO CONCERTMASTER FM-AM RECEIVER SYSTEM, MODEL 12-694

Brilliantly designed tuner/amplifier with two matching speakers. All three units in beautifully finished walnut cabinets with smart aluminium vertical trims. The tuning dial is fronted by unique black glass. Figures light up behind it in green when the unit is on. Separate easy-to-operate Left and Right volume controls. Microswitch for on/off, Programme selector. Separate bass and treble controls. Headphone socket on front panel for easy access. Single tuning knob for FM and AM. Built-in aerials, facilities for external FM aerial. Illuminated dial. Stereo broadcast indicator light. Each speaker has 8½" bass and 3" treble units. Output: 9 watts r.m.s. per channel into 8 ohms. Frequency response: 30 to 20,000 Hz. FM: frequency range 80-108 MHz, sensitivity 2.5µV, stereo separation 30dB, image rejection 40dB. AM: frequency range 530-1605 kHz, sensitivity 100µV. Sizes: speakers 8" wide, 12" high and 9½" deep; receiver 6" wide, 12" high and 9½" deep. And their sophisticated appearance matches the excellence of the specification.



**ROC PRICE**  
**£27.25**  
Normal Price £39.95 each

## REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted—for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slide controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls—magnetic phono (high/low) tuner, aux. mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts r.m.s. per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono—50dB; tuner/aux—65dB. How's that for a specification! Size 14½" wide, 3½" high, 10½" deep.



As reviewed in "POPULAR HI-FI" February 1972  
**ROC PRICE**  
**£35.20**  
Normal Price £55.50

## OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivity: FM 3µV; AM 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11½" wide, 4" high, 7½" deep.



**ROC PRICE**  
**£31.20**  
Normal Price £50.00

## 8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST

The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual override. Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in preamp. Tape speed 3½ ips (9.5 cms). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect in a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut, including connecting leads.




**ROC PRICE**  
**£31.20**  
Normal Price £49.00

**8-TRACK HOME STEREO CARTRIDGE PLAYER MODEL E1**  
With this unit, you can play any standard 8-track cartridge on the market—at a fraction of the normal retail value! It gives you a total of 5 watts of power, to feed into two 8-ohm speakers. The frequency response is 50 to 10,000 Hz, giving you a fine tonal quality that can't be bettered at anything near this price. The E1 has separate tone, balance and volume controls, giving you complete freedom to select the sound you want to hear. Tape speed is 3½ ips, and wow and flutter are both less than 0.3%. Size: 11½" wide, 5" high, 11" deep.
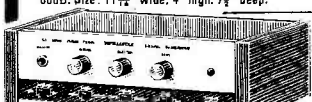
## REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5½" deep. And yet it has separate gated volume, balance and tone controls. Plus speaker in/put, mono/stereo, phono/enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.



**ROC PRICE**  
**£12.45**  
Normal Price £21.00

## REALISTIC TM-100 AM/FM/MPX STEREO TUNER

Here's another unit that gives you fabulous value in miniature! Designed specifically to match the Realistic SA-100B in both appearance, size and performance, the TM-100 is superb value-for-money. It gives you the full FM and AM ranges—FM, 80-108 MHz; AM, 535-1605 kHz. Sensitivity: FM 5µV; AM 250µV. Image rejection 50dB.



**ROC PRICE**  
**£17.55**  
Normal Price £28.00

## OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the Olson AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11½" wide, 4" high, 7½" deep. The specification reads well—sounds even better!



**ROC PRICE**  
**£24.10**  
Normal Price £39.00



**ROC PRICE**  
**£17.80**  
Normal Price £25.00 per pair

## R.445 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier—and to your pocket. At only £17.80 a pair, they are real value-for-money. Each cabinet is heavily legged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6½" deep.

## OLSON AM-357 4-WATT STEREO AMPLIFIER

Here's the marvellous value for someone just starting to set themselves up in audio! At only £9.00 you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for tunable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2½" high, 4½" wide.



## OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price—nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you—reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12½" wide, 3½" high, 7½" deep.



**ROC PRICE**  
**£9.00**  
Normal Price £14.70

## PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16

This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received—that's the time to switch to "Stereo"! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much—separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz. AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4½" high, 8" deep.



**ROC PRICE**  
**£5.50**  
Normal Price £7.75

## ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5½" wide, 1½" high and 6½" deep. It contains its own mains power supply, and has a gated tone control and separate volume controls for each channel. Specification: frequency response 40-17,000 Hz ± 3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise (ratio better than 45dB).



## OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price—nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you—reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12½" wide, 3½" high, 7½" deep.



**ROC PRICE**  
**£9.00**  
Normal Price £14.70

# units at lowest prices?..."

## TOP VALUE • TOP QUALITY ACCESSORIES THAT EVERY HI-FI ENTHUSIAST NEEDS TO COMPLETE HIS SYSTEM



**R.328 STEREO HEADPHONE**  
If you're starting in hi-fi, and you discover the need for a pair of really good stereo headphones, the R.328 is ideal, at a price you can afford. They have padded ear cushions, a 6-foot cord and jack plug. Frequency range 30-15,000 Hz. Impedance 8 ohms per channel. **ROC PRICE £2-95**

### EAGLE SE-30 STEREO HEADPHONE

This model is for the more discriminating listener. For a start the frequency range extends from 30 to 16,000 Hz. And you can adjust the volume of each earpiece independently. There's also a mono/stereo switch. For maximum comfort, the ear cushions are covered in soft leathers. **ROC PRICE £7-95**



**TEC HR-007 HEADPHONE RADIO**  
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. Normal Price £9.45 **ROC PRICE £5-80**



**EAGLE 8-TRACK CAR STEREO PLAYER, CS.8**  
Drive to the sound of music - with this fabulous 8-Track Car Stereo Player. It gives you superb tone and power to fill the car with stereo sound. Ideal for use with R.151 or R.152 speakers. Complete with all mounting accessories. For negative earth electrical systems only. Output: 2.5 watts per channel. Frequency range: 70-10,000 Hz. Wow and flutter: less than 0.3%. Tape speed: 3.5 cm/sec. Channel selector: automatic with manual over-ride. Mounting dimensions: 6 1/2" x 5 1/2" x 2 1/2". **ROC PRICE £27-20**

**"WATTS" RECORD CLEANER**  
The original "Dust Bug" Automatic Record Cleaner keeps your records clean as they play. £1.20 Watts Disc Pre-amp. Keeps new records like new - for perfect record reproduction. 35p

**R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER**  
Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalisation: RIAA. Output: 200-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/2". Supply: 140 VAC. **ROC PRICE £4-97**

**15-FOOT STEREO HEADPHONE EXTENSION CORD R.362**  
Fitted with heavy duty 3-circuit stereo plug at one end and a matching stereo socket at the other. **ROC PRICE £1-30**

**STEREO HEADPHONE "Y" ADAPTOR R.361**  
Enables you to use two sets of stereo headphones from a single socket. Fitted with male plug and two female sockets. **ROC PRICE £1-30**

Every item shown here is the best of its kind within its price range. Buy them separately or at the same time as the other top-value audio products listed.



**R.186 STEREO HEADPHONE JUNCTION BOX**  
If you want easy, fingertip control of headphones and loudspeakers, here's the ideal solution to the problem. All you do is connect it to your speakers and amplifier, plug in your headphones - and you're ready to take over! At the flick of a slide switch, you can have headphones alone, or speakers alone, or both together. Input: suitable for use with amplifiers rated up to 20 watts. Size: 2 1/2" x 3 1/2" x 1 1/2". **ROC PRICE £1-50**



**R.151 STEREO CAR SPEAKERS**  
Smart black, tough, plastic cases, each containing a high flux 110mm diameter speaker unit. Just what you need to go with the CS.8 Cartridge Player or any other car stereo system. Fitted with over three yards of connecting cable. Dimensions: 6 1/4" x 5 1/4" x 3 1/4". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker. **ROC PRICE £3-72**


**R.152 STEREO CAR SPEAKERS**  
These sloping front speakers match the CS.8 Cartridge Player or any other car stereo system. Fitted with high flux 110mm diameter speaker unit, and over three yards of connecting cable. Dimensions: 6 1/4" x 6 1/4" x 3 1/4". Impedance: 8 ohms per speaker. Rating: 5 watts max. per speaker. **ROC PRICE £4-96**

**EAGLE LC.06 STEREO MAGNETIC CARTRIDGE**  
For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: ±1.5dB. Channel separation: 20dB. Recommended stylus pressure: 2.4 grams. Compliance: 9 x 10-6 cm/dyne. **ROC PRICE £4-75**

**EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE**  
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ±1dB. Channel separation: 28dB. Compliance: 12 x 10-6 cm/dyne. **ROC PRICE £6-37**

**R.088 MATCHED STEREO LOUD-SPEAKERS**  
Here's real value stereo speakers! Each unit comes complete with 10-foot lead and phone plug, and look really smart. Power handling per speaker: 4 watts rms. 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9-50 pair**
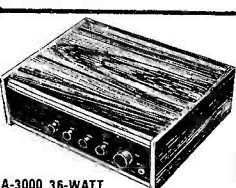
## SPECIAL PURCHASES! OFFERED AT EVEN LOWER PRICES! EXCLUSIVE TO ROC



**A-3000 36-WATT SOLID STATE STEREO AMPLIFIER**  
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm x 300mm x 130mm. Normal Price £30-70. **ROC PRICE £28-00**

**SAO-501 50-WATT SOLID STATE STEREO AMPLIFIER** A really powerful unit with all the facilities you need for home entertainment - inputs for magnetic cartridge, tape, radio tuner and auxiliary.

Controls for bass, treble, balance and volume. Headphone socket on the front panel for easy access. Loudness switch. Rumble and scratch filters. Specifications: 25 watts rms per channel into 8 ohms. Inputs: Magnetic, Tuner, Tape/Aux. Tape play. Frequency response 20-20,000 Hz (± 1db). Size: 333mm x 102mm x 285mm. Normal Price £33-60. **ROC PRICE £26-40**




**A-5000 60-WATT SOLID STATE STEREO AMPLIFIER**  
With the A-5000, you're in the big-sound class - 30 watts rms per channel into 8 ohms! The circuit is all-silicon-transistor, giving you top quality sound and a mere 0.2% distortion at 25 watts output. And optimum stereo input balance is derived from the use of an IC (integrated circuit). There's no need to worry about overload or short-circuiting the output - the A-5000 has built-in protection. Specifications: 30 watts rms per channel into 8 ohms. Frequency response 15-40,000 Hz (± 2db) Inputs: Magnetic, Tuner, Tape/Aux. Tape Play. Normal Price £43-40. **ROC PRICE £34-00**




**R-200 20-WATT AM/FM/MPX STEREO TUNER AMPLIFIER** What more could a hi-fi enthusiast want! The R-200 gives you top quality reproduction of both AM and FM programmes, including all the stereo broadcasts now available on FM. And you have built-in facilities for recording your favourite programmes on an external tape recorder. The front panel is carefully designed, with the latest slider controls for bass, treble, volume and balance. Alongside the dial are a meter for accurate tuning and a stereo indicator lamp that automatically lights up when you're tuned in to a stereo signal. Dozens of other brilliant facilities including main and remote speaker terminals. Specifications: 10 watts rms per channel into 8 ohms. Frequency response: 25-40,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tape, Aux. Tape Play. Size: 398mm x 287mm x 106mm. Normal Price. **£50-00. ROC PRICE £42-00**



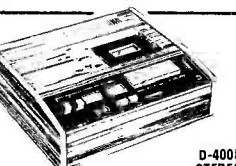**R-150 12-WATT AM/FM/MPX STEREO TUNER AMPLIFIER** You couldn't get better value-for-money in Stereo Tuner Amplifiers anywhere! Just look at all the facilities the R-150 gives you - bass, treble, balance, volume, switchable AFC for drift-less reception on FM, socket for headphones on the front panel. A tuning meter. Stereo indicator. Tape output, so that you can record your favourite programmes. To name but a few, AM section covers the medium waveband - 535-1605 kHz, and the FM band 88-108 MHz. Specifications: 6 watts rms per channel into 8 ohms. Frequency response: 40-20,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Aux. Size: 107mm x 385mm x 283mm. Normal Price £38-30. **ROC PRICE £29-90**



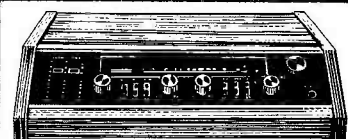**D-400B STEREO CASSETTE DECK** Precision engineered for trouble-free performance, this Stereo Cassette Deck has a fantastic range of facilities, making it a real value-for-money unit. Left and right level meters for recording, the latest slider controls for record level, switchable playback noise filter, aux/mic switch, mic input sockets, piano-key controls for record, rewind, play, fast-forward, and stop/eject. Index counter with reset button. Specifications: Frequency response: 35-12,000 Hz. Wow and flutter: less than 0.25%. Inputs: Mike, Aux, Din Socket. Size: 345mm x 300mm x 100mm. Normal Price £39-50. **ROC PRICE £34-00**



**MR-15 AM/FM/MPX STEREO TUNER AMPLIFIER** Here's a beautifully styled AM/FM Stereo Tuner Amplifier. Featuring FET (Field Effect Transistor) front end FM tuner, and dual-channel IC equalizer for perfect balance. The MR-15 incorporates professional style vertical sliding controls for bass and treble. All the input/output facilities you need. Covers FM 88-108 MHz. AM 535-1605 kHz. Output 16 watts rms per channel into 8 ohms. Inputs: Magnetic, Tape, Aux. Tape Play. Size: 467mm x 458mm x 130mm. Normal Price £67-60. **ROC PRICE £54-00**

## ROCELECTRONICS LTD

M. JORY, Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME 9-6 MON TO SAT.

LATE NIGHT THURSDAY 7 PM

Buy it with your  
BANK CARD

Return-of-post mail order service. Orders over £10 post free (UK only).  
Add 25p for p & p to orders under £10.  
HP terms available for callers

Compare our prices with any other unit on the hi-fi market, and you'll find you won't beat ROC unit prices. No matter where you live, London or Land's End!

Take a good look at all these super audio equipment bargains. They're all on demonstration at our Shop from 9 to 6 p.m. Monday to Saturday, late night Thursday until 7 p.m. But don't worry if you can't get there yourself. Our Mail Order service is at your disposal. With the same exclusive ROC equipment - and at the same super value-for-money prices!

When you invest in ROC equipment, you're getting much more than an exclusive product. You're getting value for money that is literally unbeatable. ROC units are bought direct from the manufacturer, and ALL the savings ROC derive from this are passed on to you!

At ROC Electronics, we take extra care to select only the best buys. We check everything before you do - and it's fully guaranteed whether you buy at the shop or by Mail Order.


ROC  
exclusive unit

## Fully guaranteed Individually packed VALVES

B12H \$1.75p	ECH84 45p	OA2 35p
CY31 35p	12BH300 62p	OB2 35p
DAF96 38p	12BH300 62p	PACB80 37p
DF96 42p	ECL82 35p	PC97 37p
DK96 41p	ECL83 65p	PC900 48p
DL92 32p	ECL86 42p	PC84 40p
DL94 40p	EFC36 45p	PC88 40p
DL96 41p	EFC37 45p	PC89 40p
DM70 30p	EFC38 45p	PC90 40p
DY86 32p	EFC39 45p	PC91 40p
DY87 32p	EFC40 45p	PC92 40p
DY88 32p	EFC41 45p	PC93 40p
DY89 32p	EFC42 45p	PC94 40p
DY90 32p	EFC43 45p	PC95 40p
EB80C/01	EFC44 45p	PC96 40p
E180C 42p	EFC45 45p	PC97 40p
E181C 40p	EFC46 45p	PC98 40p
E182C 40p	EFC47 45p	PC99 40p
E183C 40p	EFC48 45p	PC100 40p
E439C 40p	EFC304 45p	PC356 40p
E440C 40p	EFC305	
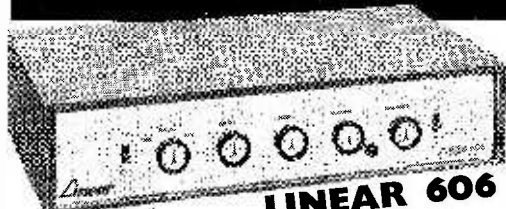
# NEW FROM LINEAR TWO STEREO AMPLIFIERS

Representing really exceptional value IN ELEGANT TEAK FINISH CASES!



0-200-230-250v. 50 Hz A.C. mains operation. Inputs for magnetic or Ceramic Pickup, Tape or Radio Tuner.

**LINEAR 606**  
6+6 WATTS  
Recommended Retail Price  
**£22.50**

## TECHNICAL DETAILS


**Bass Control**  $\pm 12$  dB at 40 Hz.  
**Treble Control**  $\pm 12$  dB at 14 KHz.  
**Sensitivities** Mag. P.U. 3.5 m.v. into 47K ohm R.I.A.A. Ceramic P.U. 35 m.v. into 100K ohm. Tape Amp. 100 m.v. into 100K. Radio Tuner 400 m.v. into 400K ohm.  
**Crosstalk** 53 dB.  
**Hum and Noise** -75 dB min. vol. -65 dB max. vol.  
**Total Harmonic Distortion** 0.1% at 1 watt into 15 ohms.  
**Output** (per channel) 6.5 watts I.H.F.M.

- ★ Individual Bass and Treble Controls.
- ★ Frequency Response  $\pm 1\frac{1}{2}$  dB 20 Hz to 65 KHz.
- ★ Outputs for Speaker impedances between 3 and 15 ohms.
- ★ Stereo/Mono Switch.
- ★ Input Selector Switch.
- ★ Solid State Circuitry.
- ★ Attractive silver finished metal fascia and matching control knobs.

- ★ A modestly priced solid state unit.
- ★ The Silver Facia with black lettering enhanced by matching control knobs, provides a high standard of appearance.
- ★ Suitable for crystal or ceramic Gram. Pick-up cartridges, and Radio input.
- ★ A wide range of tone variation is provided by the separate Bass and Treble 'lift' and 'cut' controls.
- ★ A selector switch permits instantaneous selection of Gram. or Radio.
- ★ Speaker impedances between 3 and 15 ohms are suitable.
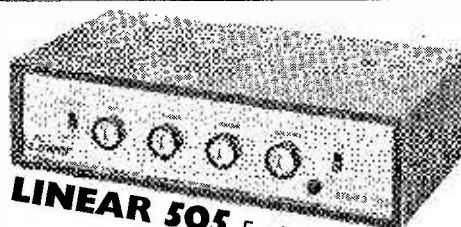
## TECHNICAL DETAILS

**Frequency Range** 20 Hz to 20 KHz  
**Output** (per channel) 5 watts I.H.F.M.  
**Bass Control**  $\pm 12$  dB at 60 Hz.  
**Treble Control**  $\pm 14$  dB. at 14 KHz.



Recommended Retail Price

**£17.50**

0-200-250v. 50 Hz A.C. mains operation

Wholesale and Retail enquiries to the Manufacturers

PRINTED CIRCUIT CONSTRUCTION  
EMPLOYING 10 TRANSISTORS

ALL LINEAR AMPLIFIERS GUARANTEED FOR 12 MONTHS

**LINEAR PRODUCTS LTD.,** Electron Works, Armley, Leeds LS12 3SA Tel. 630126

## PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ TEL. HECKMONDWIKE 4285

**Few only Famous Receiver Type 1155B.** Fitted with N type S.M. Drive, Complete Clean Condition, but untested. £8. Carriage & Ins. £1.

**Valve Voltmeter. Type CT54.** Ohms Range 1K To 10 Meg in 5 Ranges. Volts Range 2.5 To 480 V AC DC. Untested Clean Condition. Less Batteries. £5 Carriage & Ins. £1.

**Amplifier Type A413.** Complete with 5Z4 & 6V6gt Valves. 250/230 Volt Transformer. Clean Condition. Untested. £1.25p. Carriage 75p.

**Latest Air Ministry Release Radio Receiver. Type R4187.** 2.8 To 18 MHz In Three Bands. Complete with 17 Miniature Valves. 26 Volt Motor. Power supply Motor and Manually Tuned. Very Clean, But not tested. £5. Carriage and Ins. 75p.

**Control Unit. Type 4190.** Complete with three miniature valves.  $1\frac{1}{2}$  500µA meter. Six relays. model makers motor with gears. 24 press buttons. Lots of spares. Clean condition. £1.50. Carriage and Ins. 75p.

**Every one loves a bargain. And these T.V. sets we offer are the best you will find at the price.**

Complete untested T.V. sets with all valves back and knobs BBC1 and ITV. 17" 90p tube £2. 17" 110p tube £3. 19" slim £5. Carriage and Ins. £1.50. We are now breaking up many Slimline Sets. Send S.A.E. and please quote model and serial number and part you require.

For example tested L.O.P.T. £1.45. Fireball Tuners with Valves 75p. Droppers all types 50p.

**Breaking up Ferguson Type 506T.** Tested L.O.P.T. £1.45. Post paid. Fireball Tuner Unit with Valves less knobs 75p post paid. S.A.E. for other spares for this set.

**Reclaimed T.V. Tubes. All with 12 months guarantee.**

AW43/88, £1.50. AW43/80 £1.50. MW43/69 £1. Special Offer, Brand New Brimar Tubes C17PM £1. Many older types in stock. Carriage and Ins. on any tube £1.50.

**Valve list of equipment. All valves tested on a Mullard valve tester before despatched. 3 months guarantee on all valves. Single valves P/P 3p. Over post paid.**

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12p
EF80	8p	PCL82	12p	6BW7	10p
EF85	12p	PCL83	12p	6U4	10p
EBF80	12p	PCL84	12p	20P1	20p
EBF89	12p	PL36	20p	20P3	10p
ECC81	10p	PL81	17p	20D1	10p
ECC82	12p	PY81	8p	30P4	20p
ECC83	12p	PY33	17p	30F5	10p
ECL80	8p	PY82	8p	30P12	20p
EF91	4p	PL82	8p	30FL1	20p
EY86	20p	PL83	8p	6/30L2	20p
EP50	60p per doz.				

# Train for television

Course commences 6th September, 1972

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:




Name \_\_\_\_\_

Address \_\_\_\_\_

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**  
(Dept. PW9) 34a Hereford Rd., London W2 5AJ
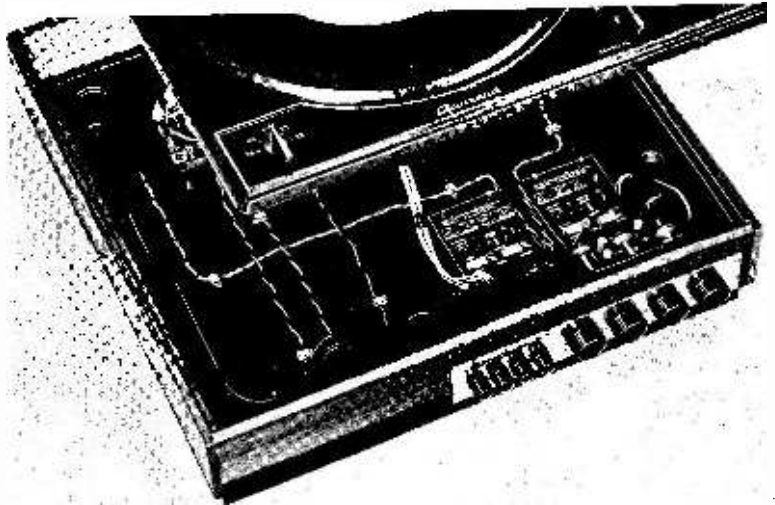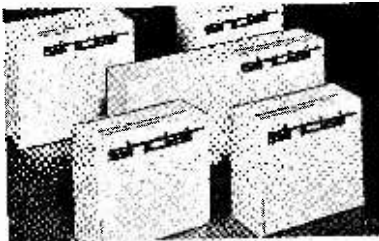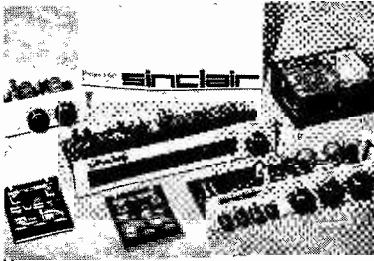
# Sinclair Project 60

The World's leading range of high fidelity modules



## New!

### Project 605

The easy way to buy and build Project 60



Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

## Sinclair

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world. Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile — using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all — price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

#### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
20 + 20 W. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
20 + 20 W. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
40 + 40 W. R.M.S. de-luxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.



## Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**



The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS**—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** 20µV. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz—15 KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

## Stereo 60 Pre-amp/control unit

Built, tested and guaranteed. **£9.98**




Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

**SPECIFICATIONS**—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A curve ±1dB: 20 to 25,000 Hz. Ceramic p.u. — up to 3mV: Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 12 to —12dB at 10 KHz; BASS + 12 to —12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

## A.F.U. High & Low Pass Filter Unit

Built tested and guaranteed. **£5.98**

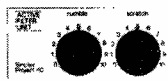

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages — rumble (high pass) and scratch (low pass). Supply voltage — 15 to 35V. Current — 3mA. H.F. cut-off (—3dB) variable from 28KHz to 5KHz. L.F. cut-off (—3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. **Size:** 66 x 40 x 90 mm.

## Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48 Z.50 £5.48**



The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you

use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts: 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts: 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz ±1dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω)

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

## Power Supply Units



Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ.5 30 volts un stabilised £4.98**

**PZ.6 35 volts stabilised £7.98**

**PZ.8 45 volts stabilised**

**(less mains transformer) £7.98**

**PZ.8 mains transformer £5.98**

## Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

**sinclair**

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

# Practical Wireless Classified Advertisements

## Miscellaneous

**R.W. QUALITY HI-FI SYSTEM pre-amplifier**

Build this simple module for the plinth unit on Type 2A (mono) or 4AS (stereo) Edge connector not needed

**NIPBOARD**

also R.W. CAR WINDSCREEN WIPER DELAY UNIT on 1A  
Wiring connections also provided with Nipboard  
SRBP 1A-15p; 2A-28p; 4AS-44p; F/glass 1B-18p; 2B-34p

**SPECIAL OFFER** Integrated circuit £1.20 TWO for £2.35  
OFFER £1.40 3D with circuit each

**NIP ELECTRONICS** P.O. BOX 11 ST ALBANS

**ELECTRONIC MUSIC**

Build your own units or even a complete sound machine from our circuit assemblies. These include I-C Ring Modulator, Phasing amps, White Sound effects, auto Waa-Waa, an amazing V-C oscillator, and many others. Send 10p for catalogue; mail-order only.

**Taylor Electronic Music Devices**  
Greyfriars House, Chester

**BUILD IT in a DEWBOX quality cabinet.** 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can set one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW

(S.A.E. for details)

TO: 'BOFFIN PROJECTS'  
DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

## JOHN SAYS...

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8.90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2.95. AUTO RHYTHM from Dewtron modules. Simple unit for waltz, foxtrots etc. costs under £20 in modules. SYNTHESIZER MODULES and other miracles. Send 15p for illust. list.

**D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.**

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free.

**CROWBOROUGH ELECTRONICS (P.W.),** Eridge Road, Crowborough, Sussex.

**"WORLD RADIO TV HANDBOOK,"** £2.80; "SWL Address Book," Stations' QSL Policy, £1.37. "Confidential Frequency List," published shortly, thousands of private stations, £1.55. "How to Listen to the World," £1.35. IRC/3p for price list (Mail only). Under £2, carriage 10p. E & OE. McGarvey, Chambers Street Union, Edinburgh 1.

Classified advertisements 9p per word (minimum 12 words). Semi-display setting £6.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, **PRACTICAL WIRELESS**, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to **PRACTICAL WIRELESS** and crossed "Lloyds Bank Ltd."

## SYNTHESIZER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to **D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.**

## THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to **C. & S., 20 Maude Street, Darlington, Durham.** Send 21p stamp.

## TAPE HEADS PICK-UP CARTRIDGES

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required.

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

**R. D. I. LTD.,**  
Chilton Works, Garden Road,  
Richmond, Surrey.

## TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACV22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

**J. M. KING (B)**

17 Buckridge, Portpool Lane, London, E.C.1

**ALUMINIUM SHEET.** Cut sizes 20 swg 33p square foot and min. charge. C.W.O. Postage 15p per order. **OPEN SATURDAY.** Berkshire Metals, 10-12 Armour Road, Tilehurst, Reading.

## Miscellaneous

### 12 VOLT FLUORESCENT LIGHTS

(as illustrated)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v. is available. Guaranteed for six months.

READY TO USE at

12 ins. 8 watt **£3.60** post paid

21 ins. 13 watt **£4.60** post paid

**SALOP ELECTRONICS,**  
23 Wyle Cop, Shrewsbury, Shropshire  
Callers welcome. For Lists or enquiries lge. s.a.e.

### PRINTED CIRCUIT BOARD

In 6 standard widths: 2in, 2½in, 3in, 3½in, 4in, and 5in x any length. 1/16in Fibreglass, single sided, 2p per 3 sq. inches. Doublesided, 1p per sq. inch. P. & P. 5p per order. S.A.E. Quotations for other sizes and quantity discounts.

**J. KNOPP,** 11 Connaught Gardens, Braintree, Essex, CM7 6LY. Tel. Braintree 25254.

**CHROMASONIC ELECTRONICS** is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

### CAR RADIOS

12 Volt Neg/Pos earth complete with speaker and fixing kit. £8.50 P & P 50p Retractable aerials with two keys £1.20 post paid. 6 Transistor 2 wave superhete radios built and tested £4.50 P & P 25p Mail order only Written Guarantee.

**D. WESTON,** 6 Byron Rd., Eastfield Park, Swadlincote, Burton-on-Trent.

### Ladders

**LADDERS.** Timber 20ft, £7.80; 29ft, £11.20. Carr. 80p. Brochure (Dept. WLS), Home Sales, Baldwin Road, Stourport, Worcs. Callers Welcome. Phone 02-993 5222. Ansafone installed.

### Educational

### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs) RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

**ICS, DEPT. 541 INTERTEXT HOUSE,**  
STEWARTS RD., LONDON, SW8 4UJ

## Educational

# TELEVISION TRAINING

(MONOCHROME AND COLOUR)

**LEC**

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing September 11th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A/6, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

**CIE, AMSE, City & Guilds, etc.** Thousands of exam successes. Postal Courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept H.8), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**RADIO, TV, RTEB CERTS., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit).** Thousands of successes. Details of home study courses and illustrated book FREE: BIET (Dept. H.7), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

## For Sale

**YUKON SELF-SPRAY**  
Get these NOW! OR GREY HAMMER BLACK WRINKLE (CRACKLE) FINISHES

Yukan Aerosol spraykit contains 4538, fine quaz, durable easy instant spray. No stove baking required. Hammerz, available in grey, blue, Modern Eggshell Black Wrinkle (Crackle) all at 85p in our counter or 90p carriage paid per push-button self-spray can. Also Durable, heat and water resistant Black Matt, fin sh (3399) self-spray cans only 75p carriage paid.

**SPECIAL OFFER:** 1 can plus optional transferable strap on trigger handle value 25p (50p) carry age paid. Choice of 1: self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

**YUKAN, 307A, EDWARDS ROAD, LONDON, W2 1EN**  
We supply many Government Departments, Municipal Authorities, bus garages and leading individual Organisations. We can supply you too.  
Open all day Saturday, Closed Thursday afternoons.

## MORSE MADE EASY!!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Complete Course £4.50 (Overseas £1.00 extra) details only, 4p stamp. 01-660 2896.

**GSNSC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K.R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**TELEPHONE ANSWERING machines.** New and Reconditioned. £55/160. STAM Co., 182a New North Road, N1. 01-286 6119.

**PANDA CUB TRANSMITTER.** Mike stand and key, £20. Pye International Receiver, £20. Exchange for good oscilloscope or Test Equipment. Box 104.

**ELECTRONIC COMPONENTS,** very cheap. Clearing laboratory. For details write: G. Smith, 3 Hart Road, Old Harlow, Essex.

## Situations Vacant

# RADIO OPERATORS

**DO YOU HAVE PMG I, PMG II, MPT 2 YEARS OPERATING EXPERIENCE?**

Possession of one of these qualifies you for consideration for a Radio Operator post with the Composite Signals Organisation.

**On satisfactory completion of a 7-month specialist training course, successful applicants are paid on scale rising to £2365 pa; commencing salary according to age—25 years and over £1664 pa. During training salary also by age, 25 and over £1238 pa with free accommodation.**

The future holds good opportunities for established (i.e. pensionable) status, service overseas and promotion. Training courses commence every January, April and September. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

**RECRUITMENT OFFICER, GOVERNMENT COMMUNICATIONS HEADQUARTERS,**

Room A/1105, Oakley Priors Road, CHELTENHAM, Glos. GL52 5AJ (Telephone: Cheltenham 21491, Ext. 2270)

**MEN! £50 p.w. can be yours**

Now for the first time anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a computer operator in only 4 weeks—and can earn £2,000++ p.a. **JOBS GALORE!** 144,000 new operators will be needed over the next 5 years alone! Write, without obligation for FREE details or telephone TODAY.

**London Computer Operators Training Centre**  
E89, Oxford House, 9/15, Oxford Street, London W.1.  
Telephone: 01-734 2874

127 The Piazza, Dept. E89, Piccadilly Plaza, Manchester 1,  
Telephone: 061 236 2935

## Aerials

### BAINES for HIGH FREQUENCY AERIALS

Postage paid on all aerials inland

#### MULTIBEAMS UHF

MBM 10 £1.90, MBM 18 £2.65, MBM 30 £3.60, MBM 38 £5.10, MBM 46 £5.50, 2MBM 46 £12.50, 4MBM 46 £28.50. Log Periodic £4.50.

#### VHF AERIALS

BBC Dipole £1.75, H £2.50, BBC/ITA Dipole and 5 £2.70, ITA 5 Element £2.00, ITA 8 Element £2.70, FM H £2.00.

**ACCESSORIES:** SAE for full list.

**Pre-amps:** Masthead mains £6.00, Colourbooster £3.88, Co-Ax. 5p and 9p, UHF Duplexers 65p.

Please state channels on all orders.

**R. BAINES, 11 Dale Cress., Tupton Chesterfield S42 6DR**

#### AERIALS

UHF 8e £1.90, 14e £2.25, 18e £3.25, 22e £3.75.

BBC Dipole £1.75, H £2.40, X £2.15, ITA 5e £1.95, 8e £2.70, 11e £3.30, 13e £4.05, Combined 1+5 £2.70, H+5 £4.10, X+5 £4.50.

FM dipole £1.13, 2el £2, 3e £3.75, Stereo £6.

Battery powered. Mains models £2 extra. Boosters, FM £4.35, UHF £3.75, VHF £3.75.

Low loss coax 6p/yd, plugs 8p.

SAE enquiries. Full catalogue 10p refundable.

**BAKER, BONTNEWYDD, CARDS, SY23 4JH**

Direct from the Manufacturers  
**U.K.F. AERIALS**  
EASY ASSEMBLY KITS  
10 Element **SAVE** 40%  
**£125** on normal retail price  
14 Element 18 Element  
**£150 £175**  
Ready assembled also 20p  
plus 20p carriage and packing.  
Please state which amount or group.  
**APEX AERIALS (P.W.)**  
6, BAA WORKS, NABY ST., JUNKYNTON, RENFREWSHIRE

## Tape Recorders

### ROBIN HOOD

(NOTTM) LTD.

Special Offer—Post Free. First Class British Made

Non-stretch Mylar Tapes

5mins. 1/2" x 900ft. 55p

5mins. 1/2" x 1200ft. 60p

7mins. 1/2" x 1200ft. 60p

7mins. 1/2" x 1800ft. 85p

10% discount on orders over £5

**23 Wadham Road, Woodthorpe, Nottingham**

## Amplifiers

### TAPE AMPLIFIERS

Made by Clarke & Smith, these sensitive amplifiers with vol. and tone controls use 2 x ECC83, EL84, EZ80, and give 2 watts into 7in x 4in 3 ohm speaker. Contained in oak-faced cabinet with non-standard deck using single a.c. motor. Only £3 + £1 carr. Complete with circuit diagram. List free.

**GREENWELD ELECTRONICS**

(PW1)  
24 Goodhart Way, West Wickham, Kent.

## PICTURE BOOK WAY OF LEARNING

BASIC ELECTRICITY 5 Vols. £4.50 post paid. BASIC ELECTRONICS 6 Vols. £5.40 post paid.  
OVER 1,000,000 PARTS ALREADY SOLD

Available on our 100% Guarantee Money Back if not completely satisfied.

Illustrated Prospectus Free on request.

SELRAY BOOK COMPANY, 60, Hayes Hill, Bromley BR2 7HP

### Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID for NEW VALVES popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),  
367 Kensington Street, Bradford 8,  
Yorkshire.

HIGHEST POSSIBLE cash prices for Akai, B. & O., Brenell, Ferrograph, Revex, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

CASH PAID for New Valves. Payment by return. WILLOW VALE, ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WANTED. Murphy A 74 or A 78C. Condition immaterial, but must be complete. Box No. 103.

### Service Sheets

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"  
Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

### Service Sheets

#### A.L.S. SERVICE SHEET SERVICE

OUR STOCKS NOW COVER OVER 10,000 MAKES AND MODELS  
1972 TV list covering mono and colour—price 25p, plus SAE  
1972 Radio, Tape, Record Players, etc. List price 25p, plus SAE  
Service Sheets—price 25p. PO and LARGE SAE. Manuals for many makes  
Enquiries welcome but please—a SAE  
Always state make, model number and whether TV, radio, tape, etc.

#### BARGAIN CORNER

Bag of 100 1/2 watt Resistors (our selection) 25p.  
Bag of 50 1 watt Resistors (our selection) 25p.  
Metal box containing Heavy Duty 12V 2PCO Relay OC35 (type) transistor and other components (originally fluid level control unit) price 50p.

MAIL ORDER ONLY

A.L.S.

21c Dryden Chambers, 119 Oxford Street, London W1R 1PB

### \* SERVICE SHEETS • MANUALS • BOOKS \*

ON RADIOS, TELEVISIONS, AMPLIFIERS, SERVICING DATA AND FAULT-FINDING ETC.  
SERVICE SHEETS 40p EACH. 1972 SERVICE SHEET CATALOGUE 20p. SEND S.A.E. WITH ENQUIRIES

#### NEW BOOKS & PUBLICATIONS

	PRICE + P & P
TRANSISTOR EQUIVALENTS & SUBSTITUTES HANDBOOK by B.B. Babani. 78 pages . . . . .	£0.40 7p
RADIO, T.V. VALVE & TUBE EQUIVALENTS HANDBOOK by B.B. Babani. 64 pages . . . . .	£0.40 7p
1972 MULLARD DATA BOOK. Data on Valves, Semiconductors & Equivalents . . . . .	£0.30 7p
HI-FI, PA & DISCOTHEQUE AMPLIFIER DESIGN HANDBOOK. (5 to 1,000 Watts). 112 pages. . . . .	£0.75 10p
AUDIO AMPLIFIERS by Data Publications Ltd. 16 Amplifier Projects. 128 pages. . . . .	£0.55 10p
TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. 205 pages. . . . .	£1.50 15p
QUESTIONS & ANSWERS ON RADIO & TELEVISION by H.W. Hellyer. 128 pages. . . . .	£0.60 10p
BEGINNERS GUIDE TO RADIO by Gordon J. King. 7th Edition. 204 pages. . . . .	£1.00 10p
BEGINNERS GUIDE TO ELECTRICITY by Clement Brown. Assoc. Brit. IRE. 185 pages. . . . .	£1.00 10p
BEGINNERS GUIDE TO ELECTRONICS by Terence L. Squires. AMIERE. 194 pages. . . . .	£1.00 10p
BEGINNERS GUIDE TO TRANSISTORS by J.A. Reddihough. 160 pages. . . . .	£1.00 10p
BEGINNERS GUIDE TO HI-FI by J.R. Hey. ASERT. An Introduction to Hi-Fi Equipment. . . . .	£0.35 7p
RADIO CONTROL FOR MODELS by Data Publications Ltd. Circuits, Servo's Etc. 192 pages. . . . .	£0.75 10p
POWER ENGINEERING USING THERYSTRIDS. VOL. 1. by Mullard Ltd. 228 pages. . . . .	£1.50 15p
RADIO SERVICING by G.N. Patchett. Vol. 4. Fault-Finding. 92 pages. . . . .	£0.70 10p
FAULT LOCATION EXERCISES IN RADIO & T.V. SERVICING by K.J. Bohlman. AM Inst F. . . . .	£0.80 10p
CONSUMER ELECTRONICS HANDBOOK by Mullard. Part 1. Semiconductor Devices. . . . .	£1.50 30p
CONSUMER ELECTRONICS HANDBOOK by Mullard. Part 2. Valves, Tubes & Components. . . . .	£1.50 30p
GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Data on Trans/Receivers Etc. . . . .	£2.85 20p

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to

### BELL'S TELEVISION SERVICES

\* Albert Place, Harrogate, Yorks. Tel. 0423-86844 \*

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

### Receivers and Components

#### NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p.&p 10p U.K. only.

Illustrated catalogue of selected kits and components. 15p P&P free.

Galleon Trading Co.,  
12, Burns Way,  
Corringham,  
Stanford-Le-Hope,  
Essex.

MINI MAINS PACK KIT. Safe double-wound mini transformer, silicon rectifiers, 1,000uF smoothing, instructions. Buildable to size of PP6 etc. 9V, 120mA 90p. UK post 5p. Mail order only. Amatronics Ltd., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

Mixed component parcels contain Toggle, Slide Switches, Plugs, Sockets, Electrolytic Capacitors, Valveholders, Tag Strips, Transistors, Diodes, Potentiometers, I.F.s Plus a good selection of other components. Save yourself £'s on these well-selected parcels 6lb nett weight £1 p & p 40p. (Approx 10 Days Delivery)

Assorted brand new wire wound resistors 1-10 watts 100 for £1 post free.

Assorted capacitors (no rubbish) includes Silver Mica, Ceramic and Polystyrene types 100 for 50p p & p 10p.

P.V.C. connecting wire 10 different colours 30 x 1 yd lengths 30p post free.

Electrolytic Capacitors 32 uF 500v 25p Also 100uF 500v (limited quantity) 35p

Mullard Ferrite Cores Type LA 2100 50p Post free.

We apologise for any delay in despatching goods.

Mail order only


XEROZA RADIO  
1 East Street,  
Bishops Tawton  
Devon

BRAND NEW COMPONENTS by return. Electrolytics 15 or 25V 1, 2, 5, 10 mfd. 3-5p; 25, 50-4p; 100-5p. Mylar Film 100V .001, .002, .005 .01, .02-2p; .04, .05-2.5p; .068, .1-3p. Mullard miniature Carbon Film resistors E.12 series 1/4W 10-10MΩ 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

## Receivers and Components
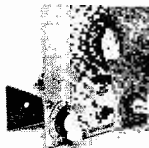
### LOOK

**"GALLEON" DOES IT AGAIN**  
**"MAYFLOWER MK 2" SHORT-**  
**WAVE KIT. WHOLE WORLD AT**  
**YOUR FINGER TIPS. 5 WAVE**  
**BANDS**



As illustrated above, our all-wave band one valve easy to build kit. This kit contains the very best in components. Drilled chassis, Bandsread tuning, step-by-step instructions, plus a bonus: one medium plug-in coil and of course, money back if not satisfied.

£3.75 +15p P & P. Cheques and postal orders to:

**GALLEON TRADING CO.,**  
 12 Burrs Way, Corringham,  
 Stanford-le-Hope, Essex.

**IMPROVE THE SSB AND DX PERFORMANCE OF YOUR B40 OR 62B RECEIVER**  
 All components, hardware, and step-by-step instructions included. Prices post paid. **PRODUCT DETECTOR KIT.** Type A with AGC switch for B40/A £2.85. Type B for B40B/C and 62B £2.50. **VERNIER FINE-TUNING KIT.** Includes handsome S/M dial for precise and easy tuning of SSB and weak DX. All models (except B40D) £2.10. **S-METER KIT.** Type A for B40 and B40A. With 1.7" meter £2.95. With 2" meter £3.20. **S-METER KIT.** Type B for B40B/C/D and 62B. With 1.7" meter £2.75. With 2" meter £3.95. Duplicated **NOTES/CCTS:** B40A/B/C 75p. 62B 75p. I specialise in surplus naval RX's. Send SAE for list of these and other items including B40D. B41. CR150, CR300, CAS, CAT, R209, R1392A.

**P. R. GOLLEGE G3EDW**  
 Glen Tor, Torrington, Devon.  
 Tel: 08-052 2411

**RADIO SPARES COMPONENTS** specified for projects in this, and other magazines supplied on request. SAE with all enquiries. The Hobbies Shop, 32 The Parade, Cwmbran Town Centre, Cwmbran, Mon.

## WITWORTH TRANSFORMERS

### TV LINE OUT-PUT TRANSFORMERS

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue

Modern **BAIRD, BUSH, GEC, PHILIPS** Replacement types ex-stock.

For "By-return" service, contact:

London: 01-948 3702

**Tidman Mail Order Ltd., Dept. PW,**  
 235 Sandycroft Rd., Richmond, Surrey  
**TW9 2EQ**

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked. (182)

CALLERS WELCOME

## JUST TWO

of our many bargains, S.A.E. lists at giveaway prices. 1 WATT 5 transistor Amplifiers, complementary output 2-250m. 9-12v supply. Measures 1 1/2" x 2 1/2" approx. Only £1.25 each.

**ZENERS—312v 400mw types 5p each, 50p doz.**

Mail order only. P. & P. 10p.

**A. J. MANLEY, 13 Randisbourne Gardens,**  
 Bromley Road, London S.E.6.

**EX COMPUTER PRINTED CIRCUIT PANELS**  
 2in X 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 8p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 22p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 X OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 25 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875, All long leaded on panels 13in X 4in. 4 for £1, P. & P. 25p.

**709C OPERATIONAL AMPLIFIER**  
 705 8 lead I.C. 1 off 50p; 50 off 35p; 100 off 20p.

**250 MIXED RESISTORS** 62p  
 1/2, 1/4 & 1 watt.

**150 MIXED HI STABS** 62p  
 1/2, 1/4 & 1 watt 5% & better

### QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

### GPO EXTENSION TELEPHONES

with dial but without bell.  
 85p each, P. & P. 30p.  
 £1.75 for 2, P. & P. 50p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

### KEYTRONICS mail order only

**44 EARLS COURT ROAD,**  
**LONDON W.8 01-478 8499**

### B.H. COMPONENT FACTORS LTD. DEPT. PW.

For Eagle, Sinclair, Data Books and Components. 1/4 W 5% resistors 1p, or 50p/100. Electrolytic C426 4/40, 8/40, 10/16, 32/10, 25/25, 100/6.4, all 4p. IN914 6p, 100V 1A Bridge 35p. Panel neon 15p. Mains Transformers 32-0-32 at 150mA 50p. 150V at 25mA and 8v at 650mA 75p. Electrolytic 100/50 10p, 500/50 12p, 1000/12 12p. 1.000/25 25p. 1.000/50 35p. uL914 30p. 7.400/01/10/50 15p. Free list, CWO. pp UK 10p. Discount £10—10%. Money back guarantee. Brand new to spec. PO Box 18, Luton, Beds, LU1 1SU.

**ELECTRONIC COMPONENTS.** Send SAE for list. Radnor Supplies, 23 Arbury Road, Nuneaton, Warwickshire.

### SOUND SUPPLIES (LOUGHTON) CO. LTD.

for Eagle International and International Rectifier Products. TOA P.A. Equipment and Mikes. Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Semiconductors, Valves. Vero Board, etc., for the constructor.

**ELECTRONICS DEPARTMENT.**  
 12 Smarts Lane, Loughton, Essex.  
 Tel. 01-508 2715.

Hours: 9.30 a.m.—1 p.m. 2-6 p.m. Mon., Tues., Wed. & Fri. 9.30 a.m.—1 p.m. 2-5.30 p.m. Sat. Closed all day Thurs.

N-CHANNEL	WOT A PRICE	P-CHANNEL
2N3819 @ 29p		2N3820 @ 49p
X6 @ 28p		X6 @ 48p
X10 @ 27p		X10 @ 47p
X25 @ 26p		X25 @ 46p

P & P 6p

10 years makers guarantee  
 Copy of F.E.T. design ideas by Texas 12p  
 Free to all 10 up customers.

**THE FET KING**  
 518 Neistrop Road, M/C 19 3JL.  
 Tips:—short leads while soldering.

## NEW

**15 Watt Hi-Fi**  
**£3.75** plus 25p postage  
**each**  
**AMPLIFIERS**

**7 TRANSISTORS GUARANTEED**  
**PRINTED CIRCUIT-TESTED**  
**DESIGN BUILT- INSTRUCTIONS**

A great new 15 watt HiFi amplifier is now available at the low cost of £3.75. Just look at the specification —Power 15 Watts R.M.S., frequency response 15-cs 19000 cs. Signal to noise ratio better than 70 db, Harmonic distortion 0.1%, Input sensitivity 750mv into 2k. These factors make the H Electronics HiFi amplifier the best at its price—order now.

**H ELECTRONICS.**  
 105, Grange Road, London. S.E.25

### EX-RENTAL TV's (UNTESTED)

Complete with 13 channel tuners. Good cabinets. Carriage £1.50 extra.

19"/21" slimline (110° tube) .. £5-00  
 23" slimline .. £7-50  
 19" BBC 2 sets .. £14-50

### TUBES EX EQUIPMENT (Tested)

#### SINGLE PANEL

19"/21" any type .. £3-00  
 23" any type .. £4-00

#### TWIN PANEL (BONDED)

19" bonded .. £5-00  
 All tubes add £1 carriage.

### VALVES EX EQUIPMENT

EB91	5p	30L15	12p	PL36	22p
EBF89	12p	30P4	12p	PL31	17p
ECC82	12p	FC97	17p	PY81	15p
EC180	7p	PCF86	17p	PY800	15p
EF80	12p	PC84	7p	PY82	7p
EF85	12p	PCF80	7p	PY33	22p
EF183	12p	PCC89	12p	U191	17p
EF184	12p	PCL85	22p	6F23	17p
EY86	17p	PCL82	17p	30PL1	22p
30PL13	20p	PCL86	17p	30P12	20p
630LZ	12p	PCL83	12p	30F5	10p

Add 24p per valve p. & p., orders over £1 p. & p. free

### UHF TUNERS

For Ferguson 850 900 chassis. Adaptable for most UHF Chassis £2-50, p. & p. 50p.

### SLOT METERS

Smiths reconditioned switchmaster MK III. Decimalized, Perfect working order. 12 for £25 delivered. For sample send £2-50 c.w.o.

## TRADE DISPOSALS (Dept. PW/TS)

Thornbury Roundabout, Leeds Rd., Bradford.  
 Telephone 0274/685670

### HARDWARE AND COMPONENTS

AVAILABLE from ONE Supplier

**FACIA PANELS : CHASSIS**  
**BRACKETS : NUTS & BOLTS**  
**WIRE : SPACERS**

**LARGE STOCK of COMPONENTS**  
 Resistors, Transistors, Capacitors

### CRYSLON INDUSTRIES

Rother St., Stratford-upon-Avon,  
 Warwickshire



## Receivers and Components

### ELECTRONICS CENTRE HARROGATE

Components, test meters, Hi Fi, SW  
receivers

48 DRAGON AVENUE. Tel. 60259

New Branded Guaranteed Top Quality

### MICROCIRCUITS & TRANSISTORS

All complete with Data  
2N2926—red and orange 6p; green 8p;  
BC109C 9p; 2N3055 48p; 741 33p; 723 75p;  
BFY 50/51/52 10p; ME0412 19p; ME4101 10p;  
MP8111 33p; SOLDERCON I.C. Pin Sockets  
0-7p per pin.

### JEF ELECTRONICS (P.W.5)

York House, 12 York Drive, Grappenhall,  
Warrington, WA4 2EJ. Mail Order Only.  
C.W.O. P & P 7p per order. Overseas 65p.  
Money back if not satisfied. Discounts begin  
at 10 off. List free on application.

**RECEIVERS**, test gear, meters, govern-  
ment surplus equipment, valves,  
masts, rotator crystals, components.  
SAE list. Kerby, 46 Manor Road,  
Selsey, Chichester, Sussex.

**AARVAK ELECTRONICS** Soundlight.  
Convertors 3 Channel 1.2kW £17. 3kW  
£25. Strobes 1 Joule £16. 4 Joule £25.  
Mail or call, 74 Bedford Ave., Barnet,  
Herts. 01-449 1268.

### INCOMPARABLE V.H.F. KIT

Johnsons CV2—unique triple-purpose (Con-  
verter, Receiver, Tuner-Feeder) kit for the  
Amateur enthusiast. Fantastic transistorized  
performance, World Wide Sales. Complete  
kit of top grade parts with coils covering  
80-180 MHz, plus easy/build diagrams and  
instructions. £4 direct from makers or  
S.A.E. for free literature.

### JOHNSONS (RADIO)

ST. MARTINS GATE

WORCESTER WRI 2DT

Est. 1943 Tel. 24864  
(A division of the G-BAN Organization)

RETURN

OF THE WORLD FAMOUS GLOBE-KING  
S.W. KIT & CRYSTAL SET KITS IS IMMINENT.

## Trampus electronics

All Brand New, to spec. Money Back  
Guaranteed. **DIL. SOCKETS**. Plastic,  
14 & 16 pin 12p 40kes **ULTRASONIC**  
**TRANSDUCER**. Max 100yd. transmit/  
receive £2 data 9p. Nixie £1.25. Numeri-  
cal Indicator 0-9DP 5v 8mA bar £1.89.  
**LIGHT EMITTING DIODES**: Visible  
Red 2v 67p. Infrared £1.49. IC Photo/  
Detector/amp 44p. 1A RECTS: 50v 6p.  
400v 9p. 50v bridge 31p. 2N3055, 44p.  
BC107 7p. BC108 7p. BC109 7p. 2N3702/  
3/4/5/6/7 11p. 2N3708/9/10/11 9p. ME  
0404-2 17p. ME 0411 18p. ME 0412 19p.  
ME 4001 12p. ME 4102 11p. BC177/8/9  
12p. 2N3819 29p. IN914 6p. Zeners  
400mW 12p. 3-5 WATT IC AUDIO AMP  
& data. Hi Fi etc. £1.49. 741 0P AMP  
33p. SCR 400v 4A 59p. **CAPACITORS**:  
C426 range 16/25/40v 5p. Mini 5/10/50/  
100 uf 6p. Mylar .01 to .2uf 6p. Resis-  
tors 1½ p. SANWA JP5D Multimeter  
£5.99. **STEREO AMPLIFIERS** complete  
in case. 8w (4+4w) £13.67 10w (5+5w)  
14-99p. **FREE CATALIST**, SAE. C.W.O.  
P. & P. UK 7p. Discount 10+ one  
type 10%.

P.O. BOX 29, BRACKNELL, BERKS.

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

1R5	-25	DF96	-35	EF91	-12	PFL200	-51
1R5	-21	DK91	-25	EF92	-28	PL36	-47
1T4	-14	DK92	-47	EF183	-28	PL81	-43
3R4	-24	DK96	-43	EF184	28	PL82	-29
3Y4	-48	DL92	-24	EL33	-54	PL83	-31
6/30L2	-58	DL94	-48	EL84	-22	PL84	-29
6AQ5	-21	DL96	-38	EY51	-38	PL500	-61
6BW7	-50	DY86	-23	EY86	-28	PL504	-61
6F1	-57	DY87	-23	EZ80	-20	PY81	-23
6F23	-67	DY802	-30	EZ91	-21	PY82	-24
6F25	-51	EABC80	-30	KT61	-54	PY800	-32
6SN7GT	-28	EB91	-9	KT66	-78	PY801	-32
26L6GT	-18	EB93	-58	N78	-85	R19	-29
30C15	-58	EBF89	-27	PC68	-45	U25	-63
30C17	-75	EC081	-15	PC88	-45	U26	-55
30C18	-59	EC082	-15	PC900	-30	U191	-57
30F5	-63	EC083	-21	PC84	-28	U251	-63
30FL1	-59	ECF82	-26	PC89	-43	U329	-65
30FL14	-67	ECF85	-53	PC189	-47	U801	-78
30LL5	-58	EOH42	-58	PCF80	-27	U809	-29
30LL7	-68	EOH81	-26	PCF86	-48	UCC85	-34
30P4	-58	EC080	-35	PCF801	-27	UCH81	-30
30P19	-58	EC082	-29	PCF802	-38	UCL82	-31
30PL1	-58	EC086	-34	PCF805	-59	UF89	-28
30PL13	-87	ECF89	-38	PCF82	-30	UL84	-29
30PL14	-63	EP80	-22	PC83	-55	UY41	-37
DAF91	21	EP85	-28	PC84	-50	UX85	-24
DAF96	35	EP86	-28	PC85	-37	W77	-42
DE91	-14	EP89	-24	PC86	-37	Z77	-18

Post/Packing on 1 valve 7p., plus 3p. per valve on each  
extra. valve Any parcel insured against damage in transit  
3p. extra. Office address, no callers.

### GERALD BERNARD

83 OSBALDESTON ROAD,  
STOKE NEWINGTON, LONDON N.16

### BARGAIN PRICE

**BRAND NEW HARTLEY OSCILLOSCOPES** CT316 in  
original packing. Band width up to 5 Mc/s. Mains  
supply. Price £40, p. & p. £150p.

**NEW 3in. SPEAKERS** 15 ohms 75p. p. & p. 10p.

**BARGAIN PARCELS** 14lb at £1.45 plus 32p p.p.: 28lb at  
£2.75 plus 52p p.p.: 56lb at £4.50 plus £1.25 p.p. Contain  
posts, Res, Valves, Diodes, Tagboards, Chassis, Valve-  
holders, etc. Good value save £22s. Lucky Dip Service.

**FANTASTIC BARGAIN**. New 6 inch tubes. E450 4B/16  
4VH, medium Persistence, green. Ideal scope tube. List  
price £5. Our price £1.40 carriage paid.

**500 µ AMP METERS**. Approx. 1½" on panel with plug  
and switch ex new equip. 75p p. & p. paid.

**NEW HEAVY COAX CABLE** dia. ¾" 70 ohms approx.  
50ft. lengths £1.40, p. & p. 30p. 100 ft. lengths £2.70,  
p. & p. 50p.

**AERIALS**. New Condition Whip Type, 4ft. 20p; 11ft.  
75p, all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New  
bases on adjustable clamp for the above, 62p. p. & p. 25p.  
New matching unit coax connection for above, 30p,  
p. & p. 5p.

**CRYSTALS AS NEW**: Hc 6u, 5,345; 5,030; 5,005; 4,945;  
4,875; 4,840; 4,795; 4,680; 4,660; 4,520; 4,510; 2,300;  
2,295 Kc/s. 80p each plus 8p. p.p.

**BRAND NEW CARBON RESISTORS**. 1-½ watt 10%,  
tolerance, mixed, 250 for 87p. p. & p. 12p. 500 for £1 60  
(you save 15p), p. & p. 20p.

**TRIMMER BARGAINS**. These are 10PF sub-min. air-  
spaced trimmers on board with min. wire ended Xtal.  
Brand new. No details: Contents 12 trimmers, some  
ceramic caps. Xtal frequency 3RD overtone 249 mc/s-  
250 Mc/s, 255 Mc/s. No choice.  
Trimmers without Xtal—60p per doz. plus 17p p.p.  
Trimmers with Xtal—75p per doz. plus 17p p.p.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** ½" dia  
x 3 ft. long. Brass screw in ends, copper coated and  
plated. Good condition. 20p, p. & p. 5p each. Minimum  
order 6.

**AS NEW AERIAL TUNER UNIT No. 6 RF**, consisting of  
1½ inch 500 micro/ampmeter 3 gang tuner 75 PF  
geared BNC type socket size 5½" x 4½" x 5". Price £1 50  
carriage paid.

Huge release of valves for the 62 set TX/RX, in original  
rubber packing consisting of QV04/7 x 61M, ARP12 etc.  
10 valves in all at the bargain price as seen  
87p plus 17p p.p.

R209. Set of valves 62p. p.p. 25p.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED**.  
75ft. 40p, 90ft. 47p, 100ft. 55p, p. & p. 20p.

### MUIRHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:  
1. To Measure Gain up to 50 db.  
2. To Measure Loss up to 45 db.  
3. To compare Power levels (A.F.).  
4. As an Audio Frequency Generator covering 100 Hz.  
to 41 kHz. With a dial setting accuracy of ±0.5 Hz.  
Output: —1 M/W into 600 SL. Complete with mains  
power unit. Tested. Good Condition. £12, p. & p. 75p.

**AERIAL MAST POLES** approx. 5ft high 2" dia. Inter-  
locking ends. Minimum order three. New condition.  
£1 each section. Carriage 35p each section.

½" 75 ohms Coax in 50ft coils with BNC plugs good  
condition. Price £1 + 30p. p.p.

**NEW BOXED AMP METERS** 1½" 20-0-20 dc. 65p,  
p. & p. 5p.

**AS NEW UNUSED REJECTOR UNITS** for rejecting  
unwanted signals. Four ranges 1-2-10 Mc/s. £1 50  
p. & p. 20p each.

**AS NEW UNUSED AERIAL VARIOMETER**. Cylinder  
design 10" x 4½" suitable for tuning most aerials for  
signal strength. £1 50 p. & p. 25p.

**NEW HEADPHONES AND MIKE RUBBER** muff type  
low impedance 87p p. & p. 17p.

**TF1449 SIGNAL GENERATORS**. Good condition £12  
p. & p. £1 50

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

**WOULD CUSTOMERS PLEASE ENSURE THAT ALL  
ORDERS ARE PRINTED IN BLOCK CAPITALS AND  
INCLUDE YOUR ADDRESS.**

## A. H. THACKER,

Radio Dept.,

HIGH STREET, CHESLYN HAY,

Nr. Walsall. Staffs.



## AIRCRAFT BAND RADIOS

Meteor	MW/VHF	£9.50
Ross	MW/VHF	£10.00
Three Band	FM/MW/VHF	
	88-145	£12.00
Five Band	MW/SW/FM- VHF/PSB	£29.00
Constellation	MW/LW/FM/VHF	£30.00

Waltham	LW/SW/MW/FM/VHF/PSB	88-174	£33.00
Aiwa	MW/MB/SW/FM/VHF/PSB		£35.00
Juliette 6	MW/MB/SW/FM/VHF/PSB		£41.50
Koyo 8	SW/12/MB/LW/MW/FM/VHF/ PSB		£40.00
Koyo 8 De Luxe	I663		£46.00

### Special Offers

Flight 4. MW/FM (88-108)/Air (108-140)/Public (140-175). £15.00  
II Band. SW/1-4/MB/LW/MW/FM/AIR/PB 76-86/PB 148-176. £75.00  
Koyo 1664 BFO. SW/12/MB/LW/MW/FM/VHF/PSB £48.00

Money-Back  
Guarantee  
Mail Order

## LANGTON'S RADIO

58 HIGH STREET, ROCESTER, STAFFS. ST14 5JU. Tel. 388

Full Lists Free  
Counter  
Service

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home – equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast – makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Dic & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." – Case History G/321.

"In addition to having my salary doubled, my future is assured." – Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." – Case History B/461.

## FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.  
Please send me book and details of your Courses in

Name.....  
BLOCK CAPITALS PLEASE  
Address.....

Subj. of interest ..... AGE .....  
Accredited by C.A.C.C.

**B.I.E.T. – IN ASSOCIATION WITH THE SCHOOL OF CAREERS – ALDERMASTON COURT, BERKSHIRE**

# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST · PA · DISCOTHEQUE · LIGHTING · MAIL ORDER



### 20 + 20 WATT I.C. STEREO AMPLIFIER

As featured by "Practical Wireless" May/June 1972

**DEVELOPED BY "TEXAS" ENGINEERS FOR PERFORMANCE, RELIABILITY AND POWER FEATURES INCLUDE:** Low profile with specially designed Gardners Transformer. 6—I.C.'s, 10 Transistors, 4 Diodes, 2 Zeners, fibreglass P.C. panel. Multi protection. Stabilised supply. DIN input/output. Complete chassis work.

**FUNCTIONS:** Separate Treble/Bass/Volume/Balance controls. Input selector, Mag. pu, Radio, Tape in and out. Headphone socket. Scratch and rumble filters. Mono/Stereo switch.

**SLIM DESIGN WITH SILVER TRIM**—Chassis size overall 14½" x 6" x 2" max.

**TOTAL COST TO BUILD £28.50** Post 45p.

(Optional teak sleeve available July/August)

**TEXAS—HENRY'S VALUE & PERFORMANCE**

Henry's are sole U.K. trade and retail suppliers of the Texas—enquiries invited.

## LATEST EDITION CATALOGUE



**FULLY** detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

**PRICE 55p** POST PAID (40p FOR CALLERS)

**10,000** Stock lines at Special Low Prices and Fully Guaranteed

## PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303" see below

### PUBLIC ADDRESS, LIGHTING & DISCOTHEQUE EQUIPMENT

**DJ1055** 30 watt rms Amplifier, 4 inputs, master tone and volume controls etc. 8 ohm output. Cased portable. £33.50. Post 40p.

**DJ1705** 70 watt rms version. Cased portable. £49.75. Post 40p.

**DISCOAMP** 100 watt rms to 8 ohms. 4 inputs, separate bass and treble controls, PFL etc. Cased for cabinet or rack mounting. £67.50. Post 40p.

**McDONALD MP60** fitted to plinth with cover, SC5MD cartridge to match above amplifiers. £17.25. Post 70p.

**DJ3011** 3 changing light control unit for above amplifiers. 3 x 1 K Watt. Treble, Bass and Mid range. £28.50. P. 35p. DJ40L as 30L plus mike £37.50

**EFFECTS PROJECTORS**—Coloured rotating light patterns. DISCO COLT 150 watt Tungsten £22.50 LIQ1 50—50 watt Q.I. £32.50 LIQ1 150—150 watt Q.I. £50.00

Complete range of Disco/PA/Lighting on display at "303"

**TEST EQUIPMENT**  
Huge range in stock—too much to list here. It's all in the latest catalogue—prices, specifications etc. Also Panel Meters and Edge Meters.



**GARRARD MEDAL GOLDING TURNABLES**  
CHASSIS (Post 50p)  
SP25/3 £10.50 HT70 £15.00  
MP60 £10.40 MP610 £14.15  
AP76 £18.85 Zero 1005 £40.75

With PLINTH/COVER (Post 70p)  
MP60 PC £17.20 TD150 AB/TX11 £40.75

HL75 PC £21.60 PL12AC £40.75  
HT70 PC £35.25 £35.25  
GL72P £29.25 BD2 £32.25

CART/PLINTH/COVER (Post 70p)  
GL72PC/G800 £34.50  
(HL)AP76/G800 £29.95  
HT70 PC/G800 £27.90  
MP60 PC/SCSM £17.25  
(HL)SP25/3/G800H £18.95  
(HL)2025 TC/9TAHCD £13.50

**ULTRASONIC TRANSDUCERS**  
Operate at 40Kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.

PRICE PAIR £5.90 Post 10p

**POWER INTEGRATED CIRCUITS**  
SL403D—3 watt with 8 page data, layouts & circuits £1.50 P.C. Board 60p; Heat Sink 14p IC12—6 watt with data and circuits £1.80  
TH9013P—20 watt Power Amp Module £4.57  
TH9014P—IC Preamp £1.50 Data/Circuits Book for above No. 42 10p

**TEXAS PUBLICATIONS**  
1-100 watt Amplifiers and Pre-Amplifier. Layouts and data £1.25 (Free List No.48A) 700 pp 16 I.C. Data Book (No.2) (All TTL I.C.'s) 60p  
420 page Transistor Data (No. 3) 60p  
340 page Transistor Data (No. 4) 60p (Post etc. 20p each.)

**7 SEG & NIXIE TUBES**  
(Post .50p per 1 to 6)  
XN3, XN13, GNE 0-9. Side view with data 85p.  
GNP-7, GNP-8 0-9. Side view with decimal units data 95p  
3015F. 7-segment £7 per 4 with data.  
New Digital Clocks Circuits. Nixie and 7 segment, Ref. No. 31 15p  
TRANSISTORS, IC's etc. Free list No.36 on request

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

**TRANSISTORS, IC's etc. Free list No.36 on request**

### LOW COST HI-FI SPEAKERS



E.M.I. Size 13½" x 8½". Large Ceramic Magnet.  
**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.  
**TYPE 150 TC** Twin cone version £2.75. Post 22p.  
**TYPE 450** 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.85. Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70. Post 28p.



**POLISHED CABINETS** For 150, 150TC and 450 £4.60. Post 30p.

### HIGH POWER AMPLIFIER MODULES



Quality transformerless low noise amplifiers suitable for all Audio, PA and Hi Fi use. Modern compact designs. PA25 and PA50 supplied with plug harness for use with MU442 Power Supply.  
MPA12/13 18v. 0.8A. 12W. 3-4 ohm. £4.50  
MPA12/15 30v. 0.5A. 12W. 12-16 ohm. £5.25  
MU24/40 Mains unit for 1 or 2 MPA12/3 or 15. £4.50  
PA25 22-0-22v. 1A. 25W. 8 ohm. £7.50  
PA50 22-0-22v. 2A. 50W. 2-4 ohm. £9.50  
MU442 Mains unit for 1 or 2 PA25 or 1 only PA50. £6.00  
Post 20p per unit

### ALL SILICON-FET PREAMPLIFIER AND MIXER SELF POWERED



All inputs. Adjustable input and output. DIN sockets. Tape in and out. Microphone mixing. Suitable up to 4-PA25 or 2-PA50.

Price £10.50 Post 30p


### 300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled STR Amplifier. Size 5½ x 1½ x 2½ in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost.  
Price £1.75, p.p. 15p (or 2 for £3.25, p.p. 15p)


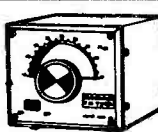
### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 Kcs. BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.  
**TOTAL £6.97**, p.p. 20p. Decoder Kit £5.97.  
Tuning meter unit £1.75  
Mains unit (optional) Model PS900 £2.47. Post 20p  
Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p



### SINCLAIR PROJECT 60 MODULES

#### —SAVE POUNDS!

Z30 £3.57; Z50 £4.37  
STEREO PZ5 £3.97  
60 £9.97; PZ8 £4.77  
PZ6 £6.37



Transformer for PZ8 £2.95  
Active Filter Unit £4.45  
Stereo FM Tuner £16.95  
IC12 £1.80; Q16's £15 pr.  
Post etc. 20p per item

**PACKAGE DEALS**  
2 x Z30, Stereo 60, PZ5 £15.95  
2 x Z30, Stereo 60, PZ6 £18.00  
2 x Z50, Stereo 60, PZ8 £20.25  
Post 25p  
Transformer for PZ8 £2.95  
Post 20p

**ALSO IN STOCK**  
2000 £23.50; 3000 £30.95  
Post 50p each

**NEW PROJECT 605 KIT £19.95**  
Post 25p

### "BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
**TOTAL COST TO BUILD £7.98**, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2  
**7" MEDIUM AND LONG WAVE PORTABLE** (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

### SLIDER CONTROLS

Top quality. 60mm/singles and ganged. Complete with knobs. 5K, 10K, 25K, 50K, 100K, 500K, 1 meg, Log and Lin. 45p each. 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each. Post 1-5 15p; 6 or more 20p.

### MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S

Send large S.A.E. with list for parts quote for your circuit or get a Catalogue—it's all in there!

**Electronic Components, Audio and Test Gear Centre**  
356 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 4736

**High Fidelity Sales & Demonstrations Centre**  
354 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 5854

**P.A., Disco & Lighting Centre**  
309 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 6963

**Mail Orders, Special Bargain Shop, Industrial Sales**  
303 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 1008/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY