

practical WIRELESS

FEBRUARY 1979
VOLUME 55
NUMBER 2
ISSUE 864

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "*Practical Wireless*" Subscription Department, Oakfield House, Perry Mount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

□ NEWS & VIEWS

- 20 **Editorial**
Our Role
- 20 **PW Personality**
Alan Martin
- 21 **News . . . News . . . News . . .**
- 32 **Special Product Report**
Sinclair DM235 Digital Multimeter
- 40 **Hotlines** Ginsberg
Recent developments in electronics
- 47, 58 **Production Lines** Alan Martin
Information on the latest products
- 61 **New Books**
Comments on recent books in the electronics field
- 71 **RAE Reprint Announcement**

□ FOR OUR CONSTRUCTORS

- 22 **12V Fluorescent Light**
An economical emergency light source
- 30 **Follow-up to the Wide-range Capacitance Meter** . Ian Hickman
Extending the range of measurement to 30 000 μ F
- 41 **PW "Hythe" Marine Band Receiver—1** . M. Tooley & D. Whitfield
A simple multi-mode receiver
- 59 **PW "Dorchester" All-band Tuner—3** W. S. Poel
Mechanical details and alternative applications

□ GENERAL INTEREST

- 26 **Digital Audio Amplification** Gordon J. King
A look at pulse-width-modulated amplifiers
- 34 **FM Receivers—Devices & Circuits—2** M. J. Darby
The i.f. stages
- 48 **IC of the Month** Brian Dance
The LM391N-60 audio power driver
- 52 **Introduction to Logic—7** S. A. Money
LSI and microprocessors
- 62 **On the Air**
Amateur Bands Eric Dowdeswell
MW Broadcast Bands Charles Molloy
SW Broadcast Bands Charles Molloy
VHF Bands Ron Ham

○ EXTRA

Index to Volume 54
Contents of our issues dated May—December 1978

Our March issue will be published on 2 February
(for details see page 33)

FABULOUS PROFESSIONAL DISCO SYSTEM

F.A.I. De Luxe PROFESSIONAL Carr. etc. £15
CONSOLE (Powered)

Slide Fade Controls. Autofade with Music Override on both mic. and jingle inputs. Headphone pre-fade monitor with 5 Push-button selector. Illuminated V.U. meters. Illuminated rocker switches. LED cue indicators. Tape or Jingle inputs, unity gain. Mic. channel with Bass & Treble. Slave outlet.

Treble Control (Music Channel) Output into line (Slave)
Treble Control (Mic. Channel) Autofade Recovery
Bass Control (Music Channel) Microphone Input.
Bass Control (Mic. Channel) Tape/Jingle. 1/P

£399
SAVE £100

DEPOSIT £28.88
and
38 weekly
payments of
£9.74
(Total £399)

TURNABLES: Garrard 125SB Belt-drive with Low-Mass 'S' arm and Magnetic Cartridge.

POWER: 120 watts continuous RMS into 4 ohms

DECK LIGHTS: Fully adjustable flexi-beams over each turntable with independent switching.

CABINET: Solidly made to withstand the rigours of transporting. Covered in heavy duty leather cloth type material in attractive colour combinations. Corner cap protectors. Recessed carrying handles.

List £320.76

INTEREST FREE CREDIT
on this system only

ALL THREE UNITS PRODUCED BY BRITAIN'S LARGEST MAKERS OF DISCO EQUIPMENT



PAIR MATCHING FULL RANGE De Luxe 80w LOUDSPEAKERS

Each inc. Pair of Powerful 12" Bass units (with aluminium centre domes), and High Frequency Horn unit to extend frequency range to above 17 kHz. Normally £89.95 ea.



Make your own Console with these

DISCO MODULES

CONTROL UNIT (mains powered)

Vol. (Left) Vol. (Right) Tape input and volume control. Bass, Treble, ON/OFF switch for each Table. **£25.00**
Carr. £1

MONITOR UNIT With H/Phone **£7.95**
Socket and Vol. Control Carr Free

FADER UNIT Carr Free **£7.95**

100w OUTPUT UNIT **£29.95**
Mains powered Carr. £1.50

TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£15.00	£12.95
T12/60R 12" 60w	£22.50	£14.95
T12/100 12" 100w	£36.00	£25.95
T15/60 15" 60w	£26.00	£17.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95

Carr. £1.20, under £18, over this add 6p per £1.

CABINETS FOR ABOVE Heavy duty, finished in black Vynide with Vynair fronts, protective corner pieces, various sizes cut-outs. TE1 1 x 12" £11.95. TE2 2 x 12" £16.95. Deposit Terms orders over £20.



Rating RMS
Imp 8-15
ohms

FANTASTIC SPEAKER OFFER

TWIN 12" SPEAKER CABINET PLUS PAIR 12" SPEAKERS

of Robust vibration-proof construction. Fitted protective corner pieces. Removable Vynair covered front with silver effect trim. Sunken jack socket with escutcheon at the rear.

Pair 12" 20w speakers for wiring in series and front mounting in above supplied to complete a 40 watt unit for lead guitar or P.A.

While stocks last
Three items

£19.95



Carr. £2.50

RSC 100 WATT DISCO SYSTEM



Consisting of
(1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUDSPEAKERS including 12" UNITS

£169.95

Carr. £4.75

ALL RSC PRICES INCLUDE VAT

50 WATT AMPLIFIER SACRIFICE

Limited stocks of
TITAN TA/50A

to be cleared
to make way
for a re-styled
model.

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. Value £60. Terms: Dep. £7.95 & 8 monthly payments £4.72 (Total £45.71). Matching Cabinets 1 x 12" £29.95, 2 x 12" £49.95 Carr. £1 **£39.95**



New Branches at

***LEEDS, *LIVERPOOL & *WOLVERHAMPTON**



Barclaycard & Access
PHONE ORDERS quoting
CARD NUMBER accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS, 18.
Tel: 0532 577831.

MAIL ORDERS MUST NOT BE SENT TO SHOPS

TERMS C.W.O. or C.O.D. No. C.O.D. under £3. POSTAGE 60p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

OPEN ALL DAY SATS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BIRMINGHAM 30/31 Great Western Arcade.
(Closed Wed.) Tel. 021-236 1279

CARLISLE 8 English Street (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq., The Precinct.
(Closed Thurs.) Tel. 25983

DERBY 97 St. Peter's Street (Closed Wed.). Tel. 41361
DEWSBURY 9/11 Kingsway (Closed Tues.). Tel. 488058

DONCASTER 3 Queensgate, Waterdale Centre.
(Closed Thurs.) Tel. 63069

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501

Prices correct at 11.12.78 E. & O.E. All items subject to availability

GLASGOW 326 Argyle St. (Closed Tues.). Tel. 041-248 4158
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LONDON 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

***LEEDS** 16-18 County (Mecca) Arcade, Briggate
(Closed Wed.). Tel. 449609

***LIVERPOOL** 35 Dawson Way, St. John's Precinct
(Closed Wed.). Tel. 708 9380

***MANCHESTER** 60A Oldham Street
(Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 103 Linthorpe Rd. (Cl. Wed.) Tel. 247096
***NEWCASTLE UPON TYNE** 59 Grainger St.
(Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street
(Closed Thurs.). Tel. 48088

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.)
(Closed Thurs.). Tel. 20718

***WOLVERHAMPTON** 5 Wulfrun Way
(Closed Thurs.). Tel. 28612

***MUSICAL INSTRUMENTS & ACCESSORIES**
in stock at these branches

RADIO EXCHANGE LIMITED

NEW ELECTRONIC MASTER KIT



With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeve, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

Projects:

V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

£14.99 + P & P £1.10

V.H.F. AIR CONVERTER KIT



Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3½". All parts including case and plans.

£4.95 + P & P and Ins. 60p

ELECTRONIC CONSTRUCTION KIT E.C.K. 2




Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3 in. loudspeaker, gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit).

Complete kit of parts

£7.95 + P & P and Ins. 90p


NEW MODEL R.K.1.

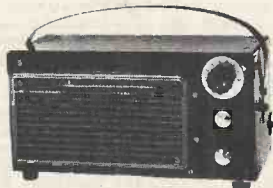

MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

£8.99 + P & P 90p

EDU KIT JUNIOR

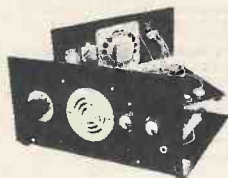


Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
 - ★ One Transistor Radio
 - ★ 2 Transistor Regenerative Radio
 - ★ 3 Transistor Earpiece Radio Medium Wave Coverage
 - ★ 4 Transistor Medium Wave Loudspeaker Radio
 - ★ Electronic Noise Generator
 - ★ Electronic Metronome
 - ★ 4 Transistor Push/Pull Amplifier
- All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.95 + P & P and Ins. 90p

NEW ROAMER TEN MODEL R.K.3.

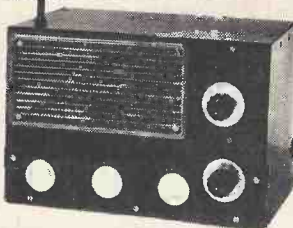


Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality 6" x 3" Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain. Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9—9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

£14.79 + P & P £1.10


E.V.6 PLUS ONE

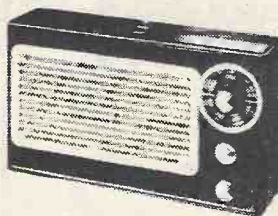

Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.

Total Building Costs:
£6.95 + P & P and Ins. 90p

EDU-KIT MAJOR

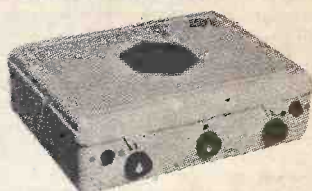

Completely solderless Electronic Construction Kit. Build fifteen projects including:—

- Signal Injector
- Transistor Tester NPN-PNP
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio.

Components include:

- 24 Resistors
 - 21 Capacitors
 - 10 Transistors
 - 5" x 3" Loudspeaker
 - Earpiece
 - Mica Base-board
 - 3 12-way Connectors
 - 2 Volume Controls
 - 2 Slider Switches
 - 1 Tuning Condenser
 - 3 Knobs
 - Ready Wound MW/LW/SW Coils
 - Ferrite Rod
 - 6½ yards of wire
 - 1 yard of sleeving, etc.
- Complete kit of parts including construction plans.

Total building costs:

£9.99 + P & P and Ins. £1.10

RADIO CONSTRUCTION KIT Q7



A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micanite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans excluding 9v PP7 Battery.

£6.25 + P & P and Ins. 75p

POCKET FIVE



NOW WITH 2½" LOUDSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs
£4.95 + P & P and Ins. 80p

To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 1SA

Tel.: 0234 52367

- Callers side entrance "Lavells" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Reg. No. 788372

I enclose £.....for.....

Name

Address

PW279

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

practical WIRELESS

50p

Australia 85c
New Zealand 85c
South Africa 80c
Malaysia \$2.25

FEB 1979

Build the
Pw HYTHE
marine
band
receiver

also:
12 Volt Fluorescent
Lamp
&
Digital Audio
Amplification



TTL ★ ★

7400	10p	74109	25p
7401	10p	74118	75p
7402	10p	74120	00p
7403	10p	74121	25p
7404	10p	74122	35p
7405	12p	74123	40p
7406	25p	74125	35p
7407	25p	74126	35p
7408	12p	74128	60p
7409	12p	74130	120p
7410	10p	74131	60p
7411	10p	74132	45p
7412	15p	74135	90p
7413	25p	74136	80p
7414	45p	74137	90p
7415	25p	74138	100p
7416	25p	74141	50p
7417	25p	74142	180p
7420	12p	74143	270p
7421	10p	74144	270p
7422	15p	74145	55p
7423	20p	74147	100p
7424	20p	74148	90p
7425	22p	74150	65p
7426	22p	74151	45p
7427	22p	74153	45p
7428	22p	74154	70p
7430	20p	74155	45p
7432	20p	74156	45p
7433	20p	74157	45p
7437	20p	74160	55p
7438	12p	74161	55p
7440	12p	74162	55p
7441	45p	74163	55p
7442	40p	74164	60p
7443	60p	74165	60p
7444	60p	74166	75p
7445	65p	74167	75p
7446	50p	74170	100p
7447	50p	74173	80p
7448	50p	74174	80p
7450	12p	74176	80p
7451	12p	74177	80p
7452	12p	74178	75p
7453	12p	74179	120p
7454	12p	74180	90p
7455	12p	74181	130p
7456	12p	74182	50p
7457	25p	74183	120p
7458	25p	74184	120p
7459	25p	74185	100p
7460	25p	74186	100p
7461	25p	74187	100p
7462	25p	74188	100p
7463	25p	74189	100p
7464	25p	74190	100p
7465	25p	74191	100p
7466	25p	74192	100p
7467	25p	74193	100p
7468	25p	74194	100p
7469	25p	74195	100p
7470	25p	74196	100p
7471	25p	74197	100p
7472	25p	74198	100p
7473	25p	74199	100p
7474	25p	74200	100p
7475	25p	74201	100p
7476	25p	74202	100p
7477	25p	74203	100p
7478	25p	74204	100p
7479	25p	74205	100p
7480	25p	74206	100p
7481	25p	74207	100p
7482	25p	74208	100p
7483	25p	74209	100p
7484	25p	74210	100p
7485	25p	74211	100p
7486	25p	74212	100p
7487	25p	74213	100p
7488	25p	74214	100p
7489	25p	74215	100p
7490	25p	74216	100p
7491	25p	74217	100p
7492	25p	74218	100p
7493	25p	74219	100p
7494	25p	74220	100p
7495	25p	74221	100p
7496	25p	74222	100p
7497	25p	74223	100p
7498	25p	74224	100p
7499	25p	74225	100p
7500	25p	74226	100p

POWER SUPPLY CAPACITORS

2200/16	35p	4700/63	120p
2200/63	80p	4700/70	135p
2200/100	150p	10000/10	100p
3300/30	50p	10000/25	150p
3300/63	80p	15000/15	150p
4700/25	50p	22000/25	200p
4700/40	65p		

ENQUIRIES FOR ALL OTHER TYPES

CMOS

4000	12p	4047	80p
4001	12p	4048	50p
4002	12p	4049	25p
4003	12p	4050	25p
4004	12p	4051	100p
4005	12p	4052	130p
4006	12p	4053	120p
4007	12p	4054	100p
4008	12p	4055	130p
4009	12p	4056	120p
4010	12p	4057	100p
4011	12p	4058	100p
4012	12p	4059	100p
4013	12p	4060	100p
4014	12p	4061	100p
4015	12p	4062	100p
4016	12p	4063	100p
4017	12p	4064	100p
4018	12p	4065	100p
4019	12p	4066	100p
4020	12p	4067	100p
4021	12p	4068	100p
4022	12p	4069	100p
4023	12p	4070	100p
4024	12p	4071	100p
4025	12p	4072	100p
4026	12p	4073	100p
4027	12p	4074	100p
4028	12p	4075	100p
4029	12p	4076	100p
4030	12p	4077	100p
4031	12p	4078	100p
4032	12p	4079	100p
4033	12p	4080	100p
4034	12p	4081	100p
4035	12p	4082	100p
4036	12p	4083	100p
4037	12p	4084	100p
4038	12p	4085	100p
4039	12p	4086	100p
4040	12p	4087	100p
4041	12p	4088	100p
4042	12p	4089	100p
4043	12p	4090	100p
4044	12p	4091	100p
4045	12p	4092	100p
4046	12p	4093	100p

FX1593 FERRITE RINGS

O/D 12mm, I/D 6mm
10 for 70p

TOGGLE SWITCHES

SUB MIN
Single Pole C.O. 85p
Single Pole C.O. Biased 85p

RESISTORS 1/3RDW

100 of 1 type £1.00p E12 only

LINEAR

A73850	450p	NE556	90p
CA3039	70p	NE562B	400p
CA3046	60p	SAD1024	1800p
CA3048	60p	SI9178	65p
CA3065	200p	SN76003N	150p
CA3076	250p	SN76013N	110p
CA3080	75p	SN76013ND	125p
CA3084	250p	SN76023N	110p
CA3085	85p	SN76023ND	125p
CA3086	80p	SN76033N	150p
CA3088	190p	SN76227N	160p
CA3089	160p	SN766228N	180p
CA3090A	360p	SN7668DN	75p
CA3123E	130p	TAA300	100p
CA3130	100p	TAA350	190p
CA3140	60p	TAA350	35p
CA3140	60p	TAA350	220p
LF357	80p	TAA651B	140p
LM211H	250p	TAA700	350p
LM300TR5	170p	TAD100	150p
LM301AN	30p	TAD110	130p
LM304	200p	TBA120T	85p
LM307N	85p	TBA480Q	200p
LM308TQ5	100p	TBA520Q	200p
LM308DIL	100p	TBA530Q	200p
LM309K	100p	TBA540	200p
LM310T05	150p	TBA550Q	250p
LM317K	325p	TBA580C	250p
LM324	20p	TBA641A12	250p
LM339	60p	TBA700	225p
LM348N	90p	TBA720Q	200p
LM380	90p	TBA800	80p
LM381N	90p	TBA810	100p
LM382	90p	TBA820	100p
LM383	180p	TBA820	100p
LM385	20p	TBA820	100p
LM389	20p	TBA820	100p
LM390N	65p	TBA820	100p
MC1310P	140p	TBA820	100p
MC1312P	150p	TBA820	100p
MC1314P	190p	TBA820	100p
MC1315P	230p	TBA820	100p
MM50398	650p	TBA820	100p
MM5314	380p	TBA820	100p
MM5316	480p	TBA820	100p
NE529K	150p	TBA820	100p
NE555	25p	TBA820	100p

ELEC CAPACITORS

0-47/25	7p	47/10	8p
1/16	7p	47/16	8p
1/25	7p	47/25	8p
1/50	7p	47/50	8p
2-2/25	7p	47/50	8p
2-2/35	7p	100/10	8p
3-3/25	7p	100/16	8p
4-7/10	7p	100/25	8p
4-7/16	7p	100/50	8p
4-7/25	7p	100/63	15p
4-7/50	7p	220/16	12p
6-8/25	7p	220/25	14p
10/10	7p	220/50	22p
10/16	7p	330/25	17p
10/25	7p	330/35	18p
10/50	7p	330/50	20p
22/63	7p	470/10	15p
22/16	7p	470/25	19p
22/25	7p	470/35	20p
22/50	7p	470/50	24p
22/100	7p	1000/16	27p
33/63	7p	1000/35	35p
33/16	7p	1000/40	40p
33/25	7p	1000/63	50p
33/50	7p	1000/100	60p

POLY CAPS

1000 PF	5p	0-1 uF	6p
2200	5p	0-22 uF	7p
3300	5p	0-33 uF	7p
4700	5p	0-47 uF	12p
8200	5p	1-0 uF	20p
0-01 uF	5p	2-2 uF	25p
0-022 uF	5p	4-7 uF	35p
0-033 uF	5p	6-8 uF	40p
0-047 uF	5p	10 uF	60p

TANT. BEADS

0-1/35V	14p	3-3/16V	14p
0-15/35V	14p	4-7/16V	14p
0-22/35V	14p	4-7/25V	14p
0-33/35V	14p	4-7/35V	14p
0-47/10V	14p	6-8/63V	14p
0-47/35V	14p	6-8/35V	14p
0-68/35V	14p	1-0/35V	14p
1-00/10V	14p	22/15V	21p
1-00/35V	14p	33/16V	25p
1-5/35V	14p	47/3V	20p
2-2/25V	14p	47/16V	25p
2-2/35V	14p	100/3V	25p

SPECIAL OFFER

2000uF 35v 40p 100/£30

REED INSERTS

One Price
26MM Long 10 for £1.00p
50MM Long

TRANSISTORS


AA113	10p	BC171	12p
AA217	10p	BC172	12p
AC121	30p	BC177	15p
AC126	20p	BC178	15p
AC127	20p	BC182	10p
AC127/01	25p	BC182L	12p
AC128	20p	BC183	10p
AC151	25p	BC183L	12p
AC153	30p	BC184	15p
AC153K	40p	BC184L	12p
AC154	30p	BC186	20p
AC157	20p	BC204	12p
AC158	20p	BC205	12p
AC159	35p	BC207	12p
AC160	35p	BC212	11p
AC161	35p	BC213	12p
AC162	30p	BC213L	15p
AC163	30p	BC214	15p
AC164	30p	BC214L	15p
AC165	30p	BC237	10p
AC166	30p	BC237B	15p
AC167	30p	BC238	15p
AC168	30p	BC239	15p
AC169	30p	BC240	15p
AC170	30p	BC241	15p
AC171	30p	BC242	15p
AC172	30p	BC243	15p
AC173	30p	BC244	15p
AC174	30p	BC245	15p
AC175	30p	BC246	15p
AC176	30p	BC247	15p
AC177	30p	BC248	15p
AC178	30p	BC249	15p
AC179	30p	BC250	15p

The latest kit innovation!

from **Sparkrite**

Sparkrite - was featured by Shaw Taylor in "DRIVE IN"

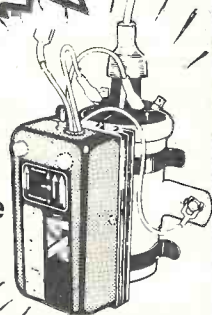the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE U.K. only.

Electronics Design Associates, Dept. PW2
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

Inc. V.A.T. and P.P.

QUANTITY REQ'D

I enclose cheque/PD's for

X4 KIT £16.65

TACHOPULSE SLAVE UNIT £3.85

£ Cheque No.

Please state polarity pos. or neg. earth
Access or Barclaycard No.

Random FLASHER UNIT

Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random.

£21.95

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches

B.C. Fitting and E.S. Fitting

£12.50 EACH

Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT
(less lamp)

B.C. Fitting and E.S. Fitting

£2.55 EACH

TYPE B 3 BANK UNIT
(Less Lamps)

B.C. £8.80 Fitting - EACH - E.S. £8.80 Fitting - EACH -

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE CLEAR £1.65 each
Maximum 3 lamps
E4-95
B.C. or E.S. Fitting

TWIN BANK 12 LIGHT UNIT
(less lamps) Length 31 1/2

B.C. £20.35 Fitting - EACH - E.S. £20.35 Fitting - EACH -

ALL PRICES INCLUDE V.A.T. and POST & PACKING
(These prices apply to the United Kingdom only)
Reg No. 174 3303 80

ALBEN ENGINEERING CO. LTD.
DEPT. PW THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel. Burnley 20940

VALVES											
A1065	1.25	EF80	0.40	PC900	1.25	SP61	0.85	3E29	5.50	6F17	1.00
AR6	0.60	EF83	0.50	PCC84	0.45	TT21	7.50	3S4	0.50	6F24	0.90
ARP3	0.60	EF85	0.55	PCC89	0.55	U25	1.00	3V4	0.85	6F33	4.20
ATP4	0.50	EF86	0.50	PCC189	0.65	U26	0.85	5B/254M	0.85	6H6	4.20
B12H	3.00	EF91	0.85	PCF80	0.80	U27	1.00	6J4/WA	1.75	13D6	0.40
CY31	0.50	EF92	0.75	PCF80	0.80	U301	0.50	6J5	0.75	14S7	1.00
DAF96	0.60	EF95	0.45	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DET22	19.50	EF163	0.65	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DF96	0.60	EF184	1.40	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DH76	0.40	EF804	2.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DK96	0.40	EF804	2.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DL92	0.50	EF90	0.80	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DY88/870	55	EL32	0.90	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
DY802	0.55	EL34	2.20	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
E55L	7.50	EL37	3.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
E88 CC/01	1.30	EL41	1.05	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
E180CC	1.30	EL82	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
E180E	0.60	EL84	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
E182CC	3.50	EL85	0.95	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EAT6	2.00	EL90	1.30	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EACB800	50	EL91	1.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EB91	0.40	EL95	0.70	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EB93	1.00	EL95	0.70	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EB95	1.00	EL95	0.70	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EB98	0.50	EL95	0.70	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EC52	0.40	EM80	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EC82	0.55	EM81	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC81	0.50	EM84	0.40	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC83	1.15	EM87	1.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC84	0.45	EY51	0.45	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC85	0.50	EY81	0.45	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC86	1.25	EY86/87	0.55	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC88	0.60	EY88	0.55	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC189	0.80	EZ80	0.45	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECC80	0.50	EZ81	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECF80	0.45	EY301	0.90	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECF801	0.75	GZ32	0.65	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECH34	0.95	GZ33	3.50	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECH35	1.50	GZ34	2.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECH42	0.85	GZ37	2.50	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECH81	0.45	KT68	4.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECH84	0.95	KT88	5.75	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECL80	0.60	MH4	1.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECL82	0.55	ML6	1.00	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECL83	1.20	OA2	0.55	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECL85	0.65	OB2	0.60	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
ECL86	0.55	PABC80	0.40	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
FC17A	1.50			PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EF39	2.90	PC85	0.50	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EF40	0.70	PC86	0.85	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75
EF41	0.75	PC88	0.75	PCF80	0.80	U301	0.50	6J5GT	0.95	19AQ5	0.75

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavailable.

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc.: retail 749 3934, trade and export 749 0899.

COLOMOR (ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

LOUDSPEAKER BARGAINS

3 ohm. 7 x 4in. £1.50. 8 x 5in. £1.90. 9in. £1.80. 8in. £2.
15 ohm 7 x 4in. £1.50. 8 x 4in. £1.60. 5in. £1.50. 5 x 3in. £1.50.

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape
reels. A.O. mains 200/240V.
Leaflet S.A.E. **£4.95** Post
50p

HEAD DEMAGNETISER £4.75



A.C. ELECTRIC MOTORS

2 Pole, 240V, 2 Amp. Spindle—1.43 x 0.212in. £1.75. 2 Pole,
240V, 15 Amp. Double Spindle—1.75 x 0.16in. Each £1.50.
2 Pole, 120V, 5 Amp. Spindle—0.75 x 0.2in. Two in series
—240V, 75p each. Brush Motor. From a Food Mixer 240V,
3 Amp. High Speed and Powerful Spindle—0.5 x 0.25in.
£2.95 each.

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p;
8 x 6in. £1.40; 10 x 7in. £1.55; 14 x 9in. £1.90; 16 x 6in. £1.85;
12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p;
10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p;
14 x 9in. 94p; 12 x 12in. £1.16 x 10in. £1.16.

ALUMINIUM ANGLE BRACKET 6 x 1/2 x 1/2in. 15p.

ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1;
8 x 6 x 3in. £1.90; 12 x 6 x 3in. £2; 6 x 4 x 4in. £1.80.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records
Auto or Manual. A high quality
unit backed by BSR reliability
with 12 months guarantee. A.C.
200/250V. Size 13 1/2 x 11 1/2in.
Above motor board 3 1/2in.
Below motor board 2 1/2in.



With MAGNETIC STEREO CARTRIDGE **£21.50**
Cueing Device, Bias Compensator, Balanced Arm, All Post 75p

BSR Budget Autochanger with ceramic cartridge. £14.95

Garrard 5300. Autochanger with ceramic cartridge. £14.95

Garrard Minichanger. Plays all size records.
Ceramic cartridge. Stereo. £9.95

BSR, P182. Snake arm, flared turntable, ceramic
cartridge. Latest model. Stereo £19.95

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for
disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing.
Master treble, bass and volume controls. 3 speaker output sockets
to suit various combinations of speakers.

4-8-16 ohm. Slave output. Guaranteed. **£85** Carr.
Details S.A.E. A/O mains 120V. and 240V. £1.50

BAKER 50 Watt AMPLIFIER 2 inputs £59.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to
build kit. Will control up to 480 watts AC mains. **£3.25**
Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp. 8 inputs
for high medium or low gain per channel, with volume control
and P.O. Board. Can be ganged to make multi-way
stereo mixers. **£2.95** Post 35p

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.O.S. printed circuit. Three
channels. 600 to 1,000 watts each. Will operate from 200WV.
to 100 watts signal source. Suitable for home use. **£17**
Cabinet extra £4.

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco
Lights. Edison Screw 75p each or 6 for £4.

MAINS TRANSFORMERS

6 VOLT 1 AMP. £1.00 3 AMP. £1.95 9 VOLT 3 AMP. £2.75
12 VOLT 300 MA. £1.00 750 MA. £1.30 20 VOLT 2 AMP. £2.50
30 VOLT 8 AMP. AND 34 VOLT 2 AMP. O.T. £3.45
20 VOLT 1 AMP. £2.00 20-0-20 VOLT 1 AMP. £2.95
30 VOLT 1 1/2 AMP. £2.75 40 VOLT 2 AMP. £2.95 30V 2 AMP. £3
0-20-40-60 VOLT 1 AMP. £3.60 2 x 18 VOLT 6 AMP. £9.

GENERAL PURPOSE LOW VOLTAGE. Voltages available at
2A. 3. 4. 5. 6. 8. 9. 10. 12. 16. 18. 24 and 80V **£5.80**
1A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60 **£5.80**
2A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60 **£5.80**
3A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60 **£11.00**
5A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60 **£14.60**

R.C.S. TEAK COMPACT SPEAKERS



13 x 10 x 6in.
50 to 14,000 cps.
12 watts rms. 8 ohms

£19 pair Post £1.50

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long
periods of electronic power.
Useful response 30-13,000 cps.
Bass resonance 55 cps.

GROUP "35" **£15.12**

12in. 40 watt
4. 8 or 16 ohms.

GROUP "50/12" **£22.68**

12in. 60 watt professional
model. 4. 8 or 16 ohms.

Response ~ 30 - 16,000 cps.

With aluminium pressure dome.

GROUP "50/15" **£34.50**

16in. 75 watt
8 or 16 ohms.

Send for leaflets on Disco, P.A. and Group Gear.



R.C.S. MINI MODULE HI-FI KIT

15 x 8 1/2in 3-way Loudspeaker
System, EMI 5in, Bass 5in, Middle
5in, Tweeter with 3-way Crossover
and Ready Cut Baffle. Full assembly
instructions supplied. Response =
60 to 20000cps 12 watt RMS.
8 ohm. £10.95 per kit. Two kits £20.
Postage 75p.

E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover.
10W. State 3 or 8 ohm. **£7.95**
Post 45p

15W model **£10.50**

8 ohms. **£10.50**

GOODMANS 20W Woofer **£9.95**

Size 12 x 10in 4 ohms.

Rubber cone surround.

Hi-Fi Bass unit. **£9.95**
Post 65p



RADIO COMPONENT SPECIALISTS

Minimum post 30p.

Components List 20p.

H.P. available.

Access & Barclay VISA welcome.

337 WHITEHORSE ROAD, CROYDON

Open 9-6

Sat. 9-5

(Closed all day Wednesday)

Phone your order.

Tel. 01-684 1665.

You know it's easy with Heathkit.

Electronics Courses

New series of courses on car
electrical systems.

New series of courses on electronic
equipment.

DC electronics.

AC electronics.

Semi-conductors.

Electronic circuits.

Digital techniques.

Microprocessors.

Heathkit self-instruction electronics courses are
complete, low-cost learning systems. All you need is the
will to learn and the Heathkit courses will teach you at
your own pace.

It's easy because the courses are based on step-by-
step programmed instructions, with audio records (or
optional cassettes), self evaluation quizzes to test your
understanding, and interesting experiments that
encourage you to learn the easy "hands-on" way with
the optional Heathkit experimenter-trainers.

Thousands of people just like you have already
learnt electronics the easy Heathkit way - at home,
in educational establishments and
in industry throughout the world.

You'll find it easy too. Full
details are in the Heathkit catalogue,
together with hundreds of kits you
can build yourself; for the home,
car and workshop.

Send for your copy now.

BARCLAYCARD

VISA

Access



New Kits

Line printer.

Dual floppy disc.

Dual trace 5MHz and 35MHz
oscilloscopes.

Memory expansion for digital trainer.

2M hand-held transceiver.

To Heath (Gloucester) Limited, Dept PW 2/79, Bristol Road,
Gloucester GL2 6EE. Please send the items I have ticked.

☐ Heathkit catalogue (enclose 20p in stamps). ☐ Computer
brochure (enclose 20p in stamps).

Name _____

Address _____

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue
without having to use this coupon. Registered in England, number 606177.

HEATH
Schlumberger

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester. (Gloucester 29451).

ROOM THERMOSTAT

Famous Satchwell, elegant design. Intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0.30 C. Special snip this month £3.25.

ROD THERMOSTAT—£3.00.

WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make £3.75.

MICRO SWITCH BARGAINS

Rated at 5 amps 250V. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 (two types) for £1.25.

RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £3.95.

MULTISPEED MOTORS

Six speeds are available 500, 800 and 1,000 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/2 in. diameter and approximately 1 in. long. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £2.

12V MINIATURE RELAY

dc operated with two sets of change over contacts. The unique feature of this relay is its heavy lead out wires; these provide adequate support and therefore the relay needs no fitting on the other hand there is a fixing bolt protruding through one side so if you wish you can fix the relay and use its very strong lead outs to secure circuit components—an expensive relay; but we are offering it for only 7p each. Don't miss this exceptional bargain!

EXTRACTOR FAN

Ex computers—made by Woods of Colchester. Ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £5.25.

MAINS RELAYS

With triple 10 amp changeover contacts—operating coil wound for 230V a.c. Chassis mounting one screw fixing. Price £1.25

BURGLAR ALARM ITEMS

(Circuit free on application)

Trigger mats 24" x 18" 13" x 10" £2.45
Relay 24 volt £1.95
5-12 volt 95p
Alarm Bell 24 volt 95p
9-12 volt £2.25
Mains on application
Reset, Switch, ordinary 45p
Secret type with key 95p
Wire—100 metres £1.50
24V Power unit mains operated £3.35

MERCURY BATTERIES

Bank of 7 Mercury cells type 625 which are approx. 1 1/2 in. diameter by 1 1/2 in. thick in plastic tube giving a total of 10.7V. Being in a plastic tube it is very easy to break up the battery into separate cells and use these for radio control and similar equipment. Carton of 25 batteries £1.60.

PP3/PP9 REPLACEMENT

Japanese made in plastic container with leads size 2in. x 1 1/2in. x 1 1/2in., this is ideal to power a calculator or radio. It has a full wave rectifier and smoothed output of 9V suitable for loading of up to 100mA. £2.53.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in. x 18in. £2.50. 13in. x 10in. £1.95.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.95.

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45

Made up model £1.00 extra

8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats, etc. £2.

ROTARY PUMP

Self priming, portable, fits drill or electric motor, pumps up to 200 gallons per hour depending upon revs. Virtually uncorrodible, use to suck water, oil, petrol, fertilizer, chemicals, anything liquid. Hose connectors each end. £2.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 10, 25, 29, 31 metre bands. Kit contains chassis, front panel and all the parts £1.94—crystal earphone 55p including VAT and postage.

MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of speakers this should sell at about £30—but due to a special bulk-buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.

HUMIDITY SWITCH

American made by Ranco, their type No. J11. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive micro-switch adjustable by a screw, quite sensitive—breathing on it for instance will switch it on. Micro 3 amp. at 250V a.c. Overall size of the device approx. 3 1/2 in. long, 1 in. wide and 1 1/2 in. deep 75p.

DELAY SWITCH

Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 95p.

25A ELECTRIC PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to.

All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours independent 60 minute memory jogger. A beautiful unit. £3.95.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied Model 1153 500mW power, output £1.69
Model 1172—10 watts power output £3.94
Model 1172 1W. power output £2.25
Model EP9000 4 watt power output £2.90
EP 9001 twin channel or stereo pre-amp £2.90

TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron—same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—price £4.95 post £1.50 control switch to give 2kw, 1kw, cold blow or off available 50p extra.

2 k.w. model made in metal case with control switch £12.00

THERMOSTATS

Refrigeration as illustrated with 36" capillary £1.62.
Limpet Stat must be mounted in close contact calibrated 90°-190°F 15 amp contacts £1.62.
Appliance Stat fix like a volume control—15 amp contact 30°-80°F 85p.
Ditto but for high temps £1.25.
Over Stat—with Serson and capillary 85p

Wall Mounting by Satchwell £3.00
Boiler Stat. with control 20°-80°C £2.16

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.

MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument jewelled bearings—1000 opv—mirrored scale.

11 instant ranges measure:—DC volts 10, 50, 250, 1000 by AC volts 10, 50, 250, 1000 by DC amps 0-1 mA and 0-100 mA Continuity and resistance 0-150K ohms.

Complete with insulated probes, leads, battery, circuit diagram and instructions.

Unbelievable value only £6.50 + 50p post and insurance.
FREE Amps ranges kit enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send £1.50p.

TERMS: Cash with order—but orders under £6 must add 50p to offset packing, etc.

BULK ENQUIRIES INVITED. PHONE: 01-688 1833.

J. BULL (ELECTRICAL) LTD
(Dept. P.W.), 103 TAMWORTH RD., CROYDON CR9 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

Telephone Ringing Mains Unit Rather than unit as it not only reduces mains to 50 volts but also reduces the mains frequency to 25 Hz, this frequency gives correct ringing note for GPO bells. These units were made for the GPO so obviously are first class. Completely enclosed and safe to mount on the wall or stand on a shelf. Price £3.20.

Telephone Extension Bells in bakelite wall box, these will save you missing calls when you are out in the garden or shed, etc. Price £3.16.

Variable Mains Supply A bench mounting unit which contains an isolation transformer for safety and a 2 amp variac for adaptability. With this you will be able to get continuously variable mains supply from zero to full voltage at 2 amps. A real time saving device, price only £20.75.

Answering Machines still available as last month's newsletter but supplies are going down rapidly and this may well be your last chance to acquire one of these.

A very large purchase this month enables us to offer a range of radio items. You will find the prices well below average:

Cassette Recorder/Player Japanese or Hong Kong made, these have all the normal facilities record, playback, fast rewind, etc., also sockets for stop/start, microphone, earphone and lead for mains as these operate from mains or HP1 batteries. £12.50.

8 Track to Cassette Adaptors Cartridges are going out of popularity, cassettes on the other hand are being made in increasing numbers and cover practically every field of sound entertainment. Cassettes can be played in 8 track if you have an adaptor. We offer these adaptors complete in carrying case and the price is only £8.50.

AM/FM Radios There's no doubt that FM does give better reproduction in good areas so a more adult member of the family will be pleased with one of these. The ones we have are in leatherette cases and are battery/mains radios having the mains unit built in and are complete with mains plug. These cover medium wave and VHF with optional AFC. Price £6.75.

8 Track to Cassette Adaptors Cartridges are going out of popularity, cassettes on the other hand are being made in increasing numbers and cover practically every field of sound entertainment. Cassettes can be played in 8 track if you have an adaptor. We offer these adaptors complete in carrying case and the price is only £8.50.

Soft Toy Radios Not necessarily only for the younger members of the family as these are soft and cute and have universal appeal. Dolls, poodles, elephants and rabbits each with zip compartment at the bottom where the radio fits. Medium wave only, working from PP3 batteries. When ordering please state preference and if possible give an alternative. £4.50.

5 Band Portable. A very impressive radio in black imitation crocodile case, size approx. 12in. wide x 7in. high. This has metal embellished carrying handle and a pullout chrome plated FM aerial, covers the following bands AM 535 to 1605 kHz. FM 88 to 108 MHz weather band 162.5 MHz and it has a logging scale. This battery/mains radio has the built in mains unit also serves as a charger if you use rechargeable batteries. The mains lead with plug locks away in its own compartment, another feature is a dial indicator which shows state of batteries. A real snip at £10.50.

Car Battery Power Unit made for Rank Radio. This unit has been designed to operate 6V battery powered equipment from a 12V car battery, it provides a reliable source of stabilised voltage and gives protection to your equipment. It can also be used as a source of connections also against excessive car battery voltage should this occur. The unit is very robust and virtually everlasting if used sensibly. It uses a negative earth circuit but it will operate in a positive earth car providing the instrument being played is not connected to the car chassis. A real bargain at £2.20.

Extension Speaker Cabinets—new delivery of these enables us to bring down the price quite a lot. We can now supply smaller ones (11in. x 8in. x 4 1/2in. approx.) at £1.95. Post £1.00 and we have a larger one with a silver finish size approximately 12 1/2in. x 9in. x 5 1/2in. Price of this is £1.69, post £1.50. If you can call and collect these cabinets you can save yourself the quite considerable postage and you only have to buy a few to get a discount as well. The quantity discount for these is a special rate of 25% if you buy four or more. Note these cabinets are very good quality (made for Rank Audio Systems) the grill material is Dacron.

Slide Switch Bargain Double pole changeover standard size with good length of connecting wire soldered to each tag—10 for £1.35.

Six Digit Counter Mains operated, 1 pulse moves counter through one digit, not resettable but all you have to do is make note of the numbers before the start of each count. Real bargain at 80p.

Be Prepared for possible blackouts and interruptions in electricity supply this winter! I have some very good lighting nearby. We still have the fluorescent outfits for operating 12in tubes from 12V car battery and the price is still the same £3.95 plus 50p post complete with a 21in tube.

Stereo Car Speakers usual type in neat compact enclosures for the rear shelf of the car. 8 ohms 5 Watt £5.50 per pair.

Bleepers 6/12V battery or transformer operated, ideal for using in many alarm circuits but particularly for car and motor cycle alarms. These give a loud shrill note. American made by Delta Alarms. Price £1.08 + 8p. Large quantities available.

Most Useful Timer Up to 12 on/off's per 24 hours is what you can get from the Verner time switch if you fit our adaptor. The shortest on/off time is one hour but you can use any combinations of on/off to make up the 24 hours. An obvious use for this is to control immersion heaters. These are real current consumers and even though the thermostats are working properly, economies can be quite considerable if a time switch is used. Our Venners are all capable of 20 amp switching. There are of course many other applications for the time switch, which you will remember in its basic form follows the sun switching on at dusk and off at dawn. Price £3.24 plus 50p post. We have a 12V adaptor, extra for plastic case £1.08 or metal case £2.16 + 16p.

Safe Soilstat For growers who use soil heating on benches, economies can be made by using a thermostat but if mains voltage equipment is used then the thermostat must be enclosed in a waterproof and earthable container. We can now supply this price £3.78 + 28p. This container will accept the normal immersion heater type thermostat but for soil heating you want one which covers 50 deg. fahrenheit and upwards, we can supply these at £3.20.

Motorised Light Flasher We can offer two motorised units both capable of 2 000V of light. Our 1/2 second flasher changes every 1/2 second and the 2 second flasher changes every 2 seconds. Either type £6.40.

Frightening Fuel Bills could lose some of their sting if you fit double glazing but even if the fuel bill does not come down much you will have a more comfortable home less draughts, etc. Double glazing frames, movable in the Spring, can be quite easily made using rigid PVC sheetings. We have this, it is as clear as glass and virtually as everlasting. It is easy to fit as you can cut, bend it, nail it, etc. A recent purchase enables us to offer this at well below current price. It is 600mm (23 1/2in wide) and available in any length (it rolls up like lino). Price 15p per sq ft. Minimum order 20 sq ft for £1.05 post 50p orders over £6.00 post free, longer lengths price negotiable.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept C276 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest.....
Name.....
Address.....
Telephone Number.....

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices—signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of £1.25 /1000—or a bag of 2500 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £62. 50 Diode Circuits Book 75p.

PC ETCHING KIT Mk III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride. DALO etch resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25.

RELAYS

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil, SPCO 3A contacts. 93p.

W832 Sub. min type, 10 x 19 x 10mm 12V coil DPCO 2A contacts £1.15.

W701 6V SPCO 1A contacts 20 x 30 x 25mm. Only 56p.

W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A. 95p.

W819 12V 1250R DPCO 1A contacts. Size 29 x 22 x 18mm. Min plug-in type 72p.

1979 CATALOGUE

64 big pages with 50p discount vouchers + qty prices for bulk buyers + reply paid envelope—All this for just 45p inc. post.

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third their original list price!

18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p.

All prices include VAT—just add 25p post

RESISTOR PACK

Carbon Film 5% mostly 1W, few 1/2W resistors. Brand new, but have pre-formed leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of £2.50 per 1000; £11 per 5000.

DIN SOCKET OFFER

2 pin switched speaker socket. PC mounting; 5 pin 180° PC mntg or chassis mntg (clip fix). All the same price, any mix: 10 for 70p, 25 for £1.60, 100 for £5.50.

BC182B OFFER

Special Offer for quantity users 1k .035 + VAT; 5k .032 + VAT. Price negotiable on 10k Approx. 100k available.

POLYTHENE SHEET

Size 36 x 18" 200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £19.

AIR FRESHENER KIT

As featured in Nov. EE. Complete kit inc. case and instructions. Only £7.95 + 55p p & p.

74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

TRANSFORMERS

All mains primary: 12.0-12V 50mA 85p; 100mA 95p; 1A £2.50. 6.0-6V 100mA 85p; 1 1/2A £2.40. 9.0-9V 75mA 85p; 1A £2.10.

Multitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.9 20V 2 1/2A £3.90; 25V 1 1/2A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V + 300mA twice £2.50; 12V @ 250mA twice £2.00.

HEAT SINK OFFER

Copper TOS sink 17mm dia. x 20mm. 10 for 40p; 100 for £3; 1000 for £25.

GREENWELD

443 Millbrook Road Southampton SO1 0HX

FANE NEW "POP" RANGE SPEAKERS

Improved appearance — higher sensitivity



		Rec. Price
12" 'POP'	40T Dual Cone 45w	£14.95
12" 'POP'	50H 50w	£16.99
12" 'POP'	75 75w	£23.95
15" 'POP'	65 70w	£25.95
15" 'POP'	80 80w	£31.95
18" 'POP'	100 100w	£52.75
18" 'POP'	150 150w	£57.95

SPECIALIST RANGE

		Rec. Price
12" DISCO/80 80w*	Fitted large Tweeter Cone	£29.95
12" DISCO/100 100w		£31.95
12" GUITAR/80L 80w*	For Lead Guitar	£28.95
12" GUITAR/80B "	Prs rec for Bass Guitar	£29.95
12" PA/80 80w	Dual Cone. For general purpose P.A.	£28.95
15" BASS/85* 85w	For Bass Guitar	£41.95
15" BASS/100 100w		£44.50

● Linen Cone surround

HIGH FREQUENCY HORNS

J44 Range:

2.5KHz-15KHz Power: 50w with HPX2R

30w with HPX1R

Imp: 8 ohms

Size approx 3 1/2" x 3 1/2" x 3"

Rec Price £7.95

J73 Range:

2.5KHz-20KHz Power: 50w with HPX1R

Imp: 8 ohms

Size approx: 7 1/2" x 3" x 6 1/2"

Rec Price £11.95



J104 Range:

2KHz-15KHz Power: 50watt with HPX1R

70 watt with HPX2R

Imp: 8 ohms

Size approx 10 1/2" x 3 1/2" x 7 1/2"

Rec Price £16.95

920/2 Range:

1 KHz-18KHz Power: 100w with HPX1. Imp: 8 ohms

Size approx 14" x 9" x 15"

Rec Price £62.95

HIGH POWER "CROSS-OVERS"

HPX1R (3.5KHz)

HPX2R (5KHz)

£3.65

Impedance or total impedance of Bass Drivers not to exceed 8Ω. Otherwise use series Horns or attenuation provided with HPX1R and HPX2R.

FANE SPEAKERS—SUPPLIED TO MOST LEADING U.K. MANUFACTURERS OF GROUP & DISCO EQUIPMENT

2 years guarantee on speakers & Horns
Distributors (Wholesale & Retail)
Rec. Prices INCLUDE VAT.
Rec. prices shown correct at 20/11/78

LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS
Manufacturers & Export enquiries to:—
FANE ACOUSTICS LTD, HICK LANE, BATLEY, YORKSHIRE

ambit[®] international

Production of the new catalogue has been held up for a few weeks - since we have just been appointed as distributors for two of the most exciting ranges of radio components products yet: The Micrometals range of iron dust torroids cores and formers, and the OKI range of VLSI for digital frequency displays for receivers. We apologize for any inconvenience, but these two ranges are really worth the wait, and include some products you will find hard to believe, like the MSM5523 IC, an IC with less than ten external components that gives AM frequency readout to 1kHz from LW to 39.999MHz, FM frequency readout in 100kHz steps - (all usual IF offsets programmable by diodes), a 24 hour format clock with 12 hour display, independent on and off timers, time signals on the hours, stopwatch facility and a sleep timer. This costs £14 with its timebase crystal, and makes all that has gone before an expensive and time wasting exercise. Rather like the way the Intersil ICM7216 has revolutionized the instrument counter market. (See the OSTS ad.) And those of you familiar with Amidon and IG dust torroids, favoured in many new RF designs, will be pleased to know Ambit will be stocking a broad range of the Micrometals types for applications from EMI filters to RF PA stages.

OKI frequency counter ICs: details in cat2
MSM5523 for CA LEDs with RHDP such as FND507 £14 inc xtal
MSM5525 for 3 1/2 digit LCD AM/FM with direct segment drive, no clock or timers £11 inc xtal
Other types for fluorescent displays etc OA

Other new semiconductor additions:
KB4437 pilot cancel mpx decoder 4.35
KB4438 muting stereo preamp 2.22
HA1370 supercodes TDA2020 2.99
TDA1090 HiFi AM/FM 3.35
TDA1220 low cost AM/FM 1.45

PRICES DOWN ON VMOS: as expected, this new technology in power transistors is getting cheaper. 120v comp pairs /100W for £10.00
Price reduction on CA3189Enow £2.20
New varicaps: to add to the biggest range.....
KV1211 2.9v bias to tune MW, like the KV1210, but a double double £1.75

New pilot tone filters from TOKO.....
208BL series, individual per channel with a 26/38kHz version for pilot cancel decoder applications. Flat to 15kHz £0.90
New crystal filter for amateur NBFM.....
TOYO 10M481 with over 90dB adjacent ch. rejection for 2m NBFM. 10.7MHz £14
New ceramic IF filters for 455kHz.....
CFM455H 6kHz/6dB, 15kHz max./60dB - ideal for MC3357 etc. £10

A brief summary of some of our range of ICs:
TDA1062/1.95; TDA1083/1.95; HA1197/£1.40
CA3123E/£1.40; TBA651/£1.81; CA3089/1.94
HA1137/£2.20; MC1310/£2.20; HA1196/£3.95
KB4424/£2.75; KB4423/£2.53; SD6000/£3.75
KB4412/£2.55; KB4413/£2.75; KB4417/£2.55
MC1495L/£3.86; MC1496P/£1.25
LM381N/£1.81; LM1303/£0.99; ULN2283B/£1.00; LM380N/£1; TBA810AS/£1.09
TCA940E/£1.80; TDA2002/£1.95;
ICL8038CC/£4.50; NE566/£2.50; NE567/£2.50; NE5608/£3.50; NE561B/£3.50;
NE562B/£3.50; NE565A/£2.50

SEE THE OSTS ADVERT FOR CMOS/TTL REGULATORS, OPTO DISPLAYS, and other types of linear devices.

Some transistors for RF specifically:
BF256L/0.34; 40822/0.43; 40823/0.51 *
40673/0.55; BF900/96/0.80; BF960/1.60 *
BF224/0.22; BF274/0.18; BF195/0.18;
BF240/0.22; BF241/0.22; BF362/0.70;
BF479/0.86; BF679S/0.70; BFY90/0.90 *

PIN and other Varicap diodes:

BA102/0.30; BA121/0.30; ITT210/0.30
BB104B/0.40; MVAM2/£1.48; MVAM115/£1.05; MVAM125/1.05; KV1210/£2.75
BA479/0.35; TDA1061/0.95; BA182/0.21

METER MADE low cost panel meters:
3 x 930 series with blanks and dry transfer sheet of scales and legends for £12.5 *

TERMS etc: CWO please, VAT on Ambit items is generally 12 1/2%, except where marked (*). Catalogue part 1:45p, part 2:50p all inclusive. Postage 25p per order, carriage on taker kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if it isn't. It's something else.....

- ★ Exceptionally high performance - exceptionally straightforward assembly
- ★ Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- ★ Various options and module line-ups possible to enable an installment approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- ★ Matching both the style and design concepts of the MkIII HiFi FM tuner
- ★ Hitachi VMOS power fets - characterized especially for HiFi applications
- ★ Power output readily multiplied by the addition of further MOSFETs
- ★ VU meters on the preamp - not simply dancing according to vol level
- ★ Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester LW, MW, SW, & FM stereo tuner



In much the same way as we have swept away the 'old technology' in frequency/timer counters - with the OKI and Intersil single IC counters, we now offer a single IC "All Band" radio tuner. Don't confuse this one chip radio with things like the ZN414 - for this is a genuine superhet receiver with a mechanical AM IF filter, and ceramic IF filters for FM. The AM section employs a balanced input mixer section, covering all broadcast bands - plus a BFO and MOSFET product detector for SSB/CW - though at this price, the tuner is not intended as a "communications receiver" - although we know of many lesser designs that make that claim. The AM sensitivity is nevertheless better than 5uV, and FM sensitivity is 1.2uV for 30dB S/N. As a multiband broadcast superhet receiver, it is a unique constructor project that fulfills the requests we very frequently get for a general coverage circuit that isn't over complicated. The set has CA3089E FM performance, with mute etc., and a PLL stereo decoder with full pilot tone filtering.

The tuner board - with "on board" PCB mounted switching, all components etc : £33.00
The case/cabinet with PSU, meter and mechanics etc £25.00
An SAE for full details please. See the feature article in Practical Wireless (Dec/Jan)

2 Gresham Road, Brentwood, Essex.

FF1 WALL MOUNTING KIT FOR HI-FI SPEAKERS

Fidelity Fastenings FF1 is a precision made, vibration damped wall fastening for Hi-Fi and Stereo Speakers of up to 50lbs weight each. Almost undetectable when fitted, the FF1 allows easy adjustment of speaker angle, and the rubber mounting ensures that they do not move accidentally. Speakers can also be quickly and easily lifted off for dusting, cleaning and redecorating.

Available from all good Audio, Hi-Fi and electrical shops at

£6.49

in case of difficulty, direct from the manufacturer at £6.89 inc P & P

PRECISION AUDIO PRODUCTS FROM

Fidelity Fastenings

The Ridgeway, Iwer, Buckinghamshire
Tel: (0753) 654222

★ Holds up to 50lbs weight per speaker.

★ Precision cast mounting brackets.

★ Rubber friction mounting for complete stability.

★ Easy adjustment of angle for precise stereo image.



SINCLAIR PRODUCTS microvision tv £90. PDM35 £27.25. mains adaptor £3.24. case £3.25. DM235 £48-30. rechargeable battery units £8. adaptor/charger £3.70. case £8.50. cambridge prog calculator £13.13. prog library £3.45. mains adaptor £3.20. enterprise prog calculator £21.95. DM350. DM450 p.o.a.
COMPONENTS send sae for full list. 1 lb FE1 £1.05. dolo pen 73p. 60 sq ins pcb 55p. laminate cutter 75p. small drill 20p. zn414 £1.05. pcb and extra parts for radio £3.85. case £1. IN4148 1.4p. IN4002 2.9p. 723 29p. 741 15p. NE555 23p. bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p. plastic equivs bc107, bc109 4.8p. 1W 5% E2 resistors 10R to 10M 1p. 0.8p for 50+. of one value. 16v electrolytics 5/12/5/10/22mf 5p. 100mf 6p. 1000mf 10p. polyesters 250v .015. .068. .1mf 13p. ceramics 50v E6 22pf to 47n 2p. polystyrenes 63v E12 10pf to 10n 3p. zeners 400mV E24 2v7 to 33v 7p.

TV GAMES send sae for data. AY-3-8500 + kit £8.95. AY-3-8600 + kit £12.50. tank battles chip £6.90, kit £7.05. stunt cycle chip £6.90, kit £5.60. rifle kit £4.95.
TRANSFORMERS 6-0-6v 100ma 74p. 1 1/2 £2.35. 6-3v 1 1/2 £1.89. 9-0-9v 75ma

74p, 1a E2, 2a £2.60. 12-0-12v 100ma 90p, 1a £2.49.

IC AUDIO AMPS with pcb JC12 6W £1.60. JC20 10W £2.95. JC40 20W £2.95.

BATTERY ELIMINATORS 3-way type 6/7/9v 300ma £2.95. 100ma radio type with press-studs 9v £3.35. 9+9v £4.50. stabilized type 3/6/7/9v 400ma £6.40. 12v car converters 3/4/6/7/9v 800ma £2.50.

BATTERY ELIMINATOR KITS send sae for data. 100ma radio types with press-studs 4v £1.40. 6v £1.40. 9v £1.40. 4 1/2+4 1/2v £1.80. 6+6v £1.80. 9+9v £1.80. stabilized 8-way types 3/4/6/7/9/12/15/18v 100ma £2.80. 1Amp £6.40. stabilized power kits 2-18v 100ma £3.60. 2-30v 1A £6.95. 2-30v 2a £10.95. 12v car converter 6/7/9v 1a £1.35.

T-DEC AND CSC BREADBOARDS s-dec £3.17. t-dec £4.02. u-dec £4.40. u-dec £6.73. 16 di adaptor £2.14. exp300 £6.21. exp350 £3.40. exp650 £3.89. exp4b £2.48.

BI-PAK AUDIO MODULES s450 £23.51. AL60 £4.86. pa100 £16.71. spm80 £4.47. bmt80 £5.95. stereo 30 £2.10.

SWANLEY ELECTRONICS (Dept PW)
32 Goldsall Rd., Swanley, Kent
Post 30p extra. prices include VAT.

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA
ENGLAND

Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp.

Yaesu FRG7-FRG7000-FR101

Drake SSR-1 SPR-4 R4C *

Secondhand Equipment
Our secondhand equipment stock changes daily. Send S.A.E. for latest price list. Part exchanges welcome. Access-Barclaycard and H.P. facilities.

TRIO R-300 - R599D - R820S

Antenna Multituners
Designed and manufactured by ourselves. Over 1000 sold in over 50 countries.

Antenna Switches
Mk2 covers 550kHz 30MHz £25.00
Prices include VAT and postage.
Send SAE for Test report.

OSTS**CD4000 CMOS**

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE
AMBIT AO TOOL!**Micromarket****PRICES
SLASHED****TTL: Standard AND LP Schottky**

4000	17p	4059	563p	4522	149p	6800 series	8216	1.95	2114	£10
4001	17p	4060	115p	4527	157p	6800P	8224	3.50	2708	£10.55
4002	17p	4063	109p	4528	102p	6820P	8228	4.78		
4006	109p	4066	53p	4529	141p	6850P	8251	6.25		
4007	18p	4067	400p	4530	90p	6810P	8255	5.40		
4008	80p	4068	25p	4531	141p	6852	3.65			
4009	58p	4069	20p	4532	125p	8080 series	2102	£1.70		
4010	58p	4070	20p	4534	614p	8080	2112	£3.40		
4011	17p	4071	20p	4536	38p	8212	2513	£7.54		
4012	17p	4072	20p	4538	150p		4027	£5.78		
4013	55p	4073	20p	4539	110p					
4016	52p	4075	20p	4541	141p					
4017	80p	4076	90p	4543	174p					
4018	80p	4077	20p	4549	399p					
4019	60p	4078	20p	4553	440p					
4020	93p	4081	20p	4554	153p					
4021	82p	4082	20p	4556	77p					
4022	90p	4085	82p	4557	38p					
4023	17p	4086	82p	4558	117p					
4024	76p	4089	150p	4559	38p					
4025	17p	4093	50p	4560	218p					
4026	180p	4094	190p	4561	65p					
4027	55p	4096	105p	4562	530p					
4028	72p	4097	372p	4566	159p					
4029	100p	4098	110p	4568	281p					
4030	58p	4099	122p	4569	303p					
4031	250p	4160	90p	4572	25p					
4032	100p	4161	90p	4580	600p					
4033	145p	4162	90p	4581	319p					
4034	200p	4163	90p	4582	164p					
4035	120p	4174	104p	4583	84p					
4036	250p	4175	95p	4584	63p					
4037	100p	4194	95p	4585	100p					
4038	105p	4501	23p							
4039	250p	4502	91p							
4040	83p	4503	69p							
4041	90p	4506	51p							
4042	85p	4507	55p							
4043	85p	4508	248p							
4044	80p	4510	99p							
4045	150p	4511	149p							
4046	130p	4512	98p							
4047	99p	4513	206p							
4048	60p	4514	260p							
4049	55p	4515	300p							
4050	55p	4516	125p							
4051	65p	4517	382p							
4052	65p	4518	103p							
4053	65p	4519	57p							
4054	120p	4520	109p							
4055	135p	4521	236p							

Voltage Regs

NEW LOW PRICES	
7800 series UC TO220 package 1A	all 95p
7900 series UC TO220 package 1A	all £1
78MUC series TO220 package 1/2A	all 90p
78LCP series TO92 100mA	all 35p
L200 up to 3A/adjustable V/A	
78MGT2C 1/2amp adjustable volts	175p
79MGT2C 1/2amp adjustable volts	175p
723C precision controller	65p
MAINS FILTERS FOR NOISE/RFI etc	
1 amp in IEC connector	£4.83
5 amp in 'wire in' case	£3.87
NE550A	73p

LINEARS non-consumer

BIMOS	
CA3130E	84p
CA3130T	90p
CA3140E	35p
CA3140T	72p
CA3160E	90p
CA3160T	99p
Op amps	
LM301AH	67p
LM301AN	30p
LM308H	121p
LM308N	97p
LM318H	279p
LM318N	224p

OPTO 7 seg displays

0.43" High Efficiency HP:	
5082-7650 red CA	233p
5082-7653 red CC	
5082-7660 yellow CA	
5082-7663 yellow CC	
5082-7670 green CA	
5082-7673 green CC	
0.3" Standard HP	
5082-7730 red CA	147p
5082-7740 red CC	
0.5" Fairchild	
FND500 red CC	150p
FND507 red CA	150p

TERMS: CWO psc., VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTS and Ambit - a single combined remittance and pp charge is sufficient. Account details OA.

2 Gresham Road, Brentwood, Essex.**PRACTICAL WIRELESS T.V. SOUND TUNER**

(Nov. 75 article by A. C. Ainslie)

Copy of original article supplied on request

IF Sub-Assembly (G8) £6.80. P & P 75p.
Mullard ELC1043 V'cap UHF Tuner £5.50. P & P 35p.
3-way Station Control Unit £1.20. P & P 25p.
6-way Station Control Unit (Special Offer) £1.00.
Power Supply Prtd Circuit Board £1.00. P & P 30p.
Res, Caps, Semiconds, etc. for above £5.80.
Mains Transformer for above £2.50. P & P 30p.
Add 12½% VAT to price of goods. P & P all items 85p.

Callers welcome at shop premises.

MANOR SUPPLIES**172 WEST END LANE, LONDON NW6**

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

TOPS THE PACK!


COMPONENTS	— Now over 1,000 types in stock!
KITS	— See the new range of low-cost 'ELEKITS'.
MODULES	— New ready-built functions.
SERVICE	— 1st Class same day despatch.
QUALITY	— All guaranteed products.
PRICES	— Many reductions!
MAGAZINE	
PROJECTS	— Trouble-free!

I enclose 30p*, please send catalogue.

Name

Address

*Refundable with future orders over £5.00.

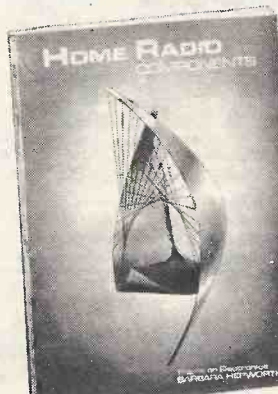**START THE NEW YEAR WELL
by treating yourself to this
famous
Components
Catalogue**

- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., Dept. P.W., 234-240 London Road, Mitcham, Surrey CR4 3HD**POST THIS COUPON**
with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME

ADDRESS

**HOME RADIO (Components) LTD.,** Dept. P.W., 234-240 London Road, Mitcham, Surrey CR4 3HD.

(Regn. No. London 912966)

B. BAMBER ELECTRONICS

Dept. P.W. 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

OSMOR 10V REED RELAY COILS 1k ohm coil) to fit 1" reeds (not supplied) 2 for 50p.
HF CHOKES wound on 1" x 1" long ferrites. 4 for 50p.

VHF CHOKES wound on 6-hole tubular ferrites. 5 for 40p.

DUAL TONE HEATSINKS 1" x 1" x 1" with screw-in clamps. 3 for 50p.

MAINS TESTER SCREWDRIVERS 100 to 500V. Standard size 50p. Large 70p.

RADIO PLIERS 5 1/2" £1.80, 6 1/2" £2.00, SMALL SIDE CUTTERS (with wire holding device) £4.50.

MINIATURE FILE SETS. Set of 6 £2.20.

TAP AND DIE SETS (18 piece) contain 1 each of 0, 2, 4, 6, 8, BA Sizes in Dies, Plug Taps, Taper Taps + American type tap wrench, 1 type tap wrench, Die Holder. £12.50.

LARGE ELECTROLYTIC CAPS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3.90 per pack (+12 1/2% VAT).

Slider Switches. 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

Due to a change of supplier, our stock aluminium boxes and vinyl covered equipment cases will be as follows

Aluminium boxes with lids

AL1 3" x 2" x 1" 60p
AL2 4" x 3" x 1" 70p
AL3 4" x 3" x 2" 80p
AL4 6" x 4" x 2" 90p
AL5 6" x 4" x 3" £1.25
AL6 8" x 6" x 3" £1.50
AL7 8" x 6" x 2" £1.75

Vinyl Equipment Cases

Blue Vinyl covered steel tops with plain aluminium lower sections.

BC0 5" x 2 1/2" x 2 1/2" £1.00
BC1 6" x 4 1/2" x 2 1/2" £2.00
BC2 6" x 4" x 3 1/2" £2.25
BC3 8" x 5 1/2" x 3 1/2" £3.00
BC4 10" x 6 1/2" x 3 1/2" £3.25
BC7 12" x 6 1/2" x 5" £3.25

MAINS TRANSFORMERS. Type 15/300 240V input. 15V at 300mA output. £1.50 each.

MAINS TRANSFORMERS. Type 45/100, 240, 220, 110, 0V input. 45V at 100mA output. £1.50 each.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

CELESTION 8" x 5" ELIPTICAL SPEAKERS. 20 ohm, 3 watts rated, £1.50 each + 12 1/2% VAT.

IC AUDIO AMP PCB. Output 2 watts into 3 ohm speaker, 12V DC supply, size approx. 5 1/2" x 1 1/2" x 1" high, with integral heatsink, complete with circuits, £2.00 each.

NICAD CONVERTER PCB. (Low power inverter). Size approx. 4" x 1 1/2" x 1" high, 12V DC supply, 60V DC output, through pot on pcb, for charging Nicads, etc. (ideal for charging portable batteries from mobile supply). Only needs one BFY50/51/52 or similar transistor, which can be mounted direct on the pcb pins on board, fitted with a star-type heatsink (Not Supplied). £2.00 each.

THE NEW EAGLE INTERNATIONAL CATALOGUE IS AVAILABLE ON REQUEST containing Audio, In-car, and test equipment, etc.

DECIMAL KEYBOARDS, pressure sensitive type, when pressed contacts go from O/C to approx. 25 ohms. Switches only, no encoders. Size approx. 3" x 3", with large square touch plates. 0-9 + Clear, A, B, Dual Watch, and spare. Few only, £2.00 while stocks last.

TYPE 8079 FULL RANGE SPEAKER, 10" dia, 15 ohm, £5.00 each (or 2 for £9.00) + 12 1/2% VAT.

SEMICONDUCTORS

BSX20 (VHF Osc/Mult). 3 for 50p.
BC108 (metal can). 4 for 50p.
PBC108 (plastic BC108). 5 for 50p.
BFY51 Transistors. 4 for 60p.
BCY72 Transistors. 4 for 50p.
PNP audio type TOS Transistors, 12 for 25p.
BF152 (UHF amp/mixer). 3 for 50p.
2N3819 FET. 3 for 60p.
BC148 NPN SILICON. 4 for 50p.
BC158 PNP SILICON. 4 for 50p.
BAY 31 Signal Diodes, 10 for 35p.
IN4148 (IN914) 10 for 25p.
BC107 (Metal can) 4 for 50p.
SCRs 400V at 3A, stud type, 2 for £1.00.
TIP2955 Silicon PNP power transistor, 60V at 15A, 90 Watts. Flat pack type, 2 for £1.50.
GERMANIUM DIODES, approx 30 for 30p.
741C op amps by RCA, 4 for £1.
RED LEDs (Min. type) 5 for 70p.
T03 transistor Insulator sets, 10 for 50p

SPECIAL OFFER FOR COMPUTER BUILDERS, ETC.

19 way ribbon cable, decimal coded, 4 metres for £1.25
13 way heavy-duty ribbon cable, decimal coded, (ideal for PSU runs) 3 metres for £1.50

CLAREED REED RELAYS, complete with reeds, TYPE 1, Size approx. 2 1/2" x 1/2" x 1/2", 2 pole make, 9V 400 ohm coil, 35p each. TYPE 2, Size approx. 2 1/2" x 1/2" x 1/2", 2 pole make + 2 pole break, 2 x 9V 200 ohm coils, 60p each.

VIDICON SCAN COILS (Translator type, but no data) complete with vidicon base £6.50 each. Brand New.

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold-plated pins. Ideal for experimenters or service engineers. 28 pin DIL £1.75, 40 pin DIL £2.00. Or save by buying one of each for £3.50.

GLASS BEAD FEEDTHROUGH INSULATORS. Solder-in type, overall dia. approx. 5mm. Pack of approx. 50 for 50p.

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.

Type N81 approx 3 1/2" x 2 1/2" x 1 1/2" 45p each
Type N82 approx 4" x 3" x 1 1/2" 55p each
Type N83 approx 4 1/2" x 3 1/2" x 1 1/2" 65p each
Type N84 approx 5 1/2" x 5 1/2" x 3 1/2" £1.50.

DIE-CAST ALUMINIUM BOXES Send for Latest Price List.

PLUGS AND SOCKETS

BNC Plugs, 10 for 50p each.
N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
PL259 Plugs (PTFE) brand new, packed with reducers, 75p each.
SO239 Sockets (PTFE), brand new (4-hole fixing type). 60p each.

SOLDER SUCKERS (Plunger type). Standard Model £5.50. Skirted Model £6. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS:

S140D 40W 240V £4.50.
S125K 25W 240V + bits etc., KIT £5.30.

BENCH STAND with spring and sponge for Marksmen Irons £2.70.

Spare bits MT9 (for 15W) 60p. MT5 (for 25W) 60p. MT10 (for 40W) 55p.

ALL PRICES + 8% VAT.

TC2P TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. £30 + VAT (£2.40).

SPARE TIPS

Type CC single flat. Type K double flat fine tip, Type P, very fine tip £1.50 each + VAT (8p). MOST SPARES AVAILABLE.

WELLER SOLDERING IRONS

EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN 8100D £12.00.

EXPERT SOLDER GUN KIT (spare bits, case, etc.) £15.00. Spare bits 40p pair.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

BSR AUTOCHANGE RECORD PLAYER DECKS with cue device, 33-45-78RPM, for 7", 10", 12" records. Fitted with SC12M Stereo Ceramic cartridge and styl. Brand new £14.00 + 12 1/2% VAT.

GARRARD AUTOCHANGE RECORD PLAYER DECKS, Model 6-300, with cue device, 33-45-78 r.p.m., for 7", 10", 12" records. Fitted with K5418 Stereo Ceramic cartridge and styl. Brand new £16.00 + 12 1/2% VAT. Please note, record decks sent by Roadline, allow 14 days for delivery.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

VARIAC TUNERS Mullard type ELC1043/05. Brand new, £5.00 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Seatronic Manufacture. Approx 100. £1.50 per pack + 12 1/2% VAT.

Dubilier Electrolytics, 50uF, 450V, 2 for 50p.
Dubilier Electrolytics, 100uF, 275V, 2 for 50p.
Pleasay Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.
Dubilier Electrolytics, 5000uF, 35V, 50p each.
Dubilier Electrolytics, 5000uF, 50V, 60p each.
ITT Electrolytics, 6800uF, 25V, high grade screw terminals, with mounting clips, 50p each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY) SAE with ALL ENQUIRIES Please PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN CALLERS WELCOME BY APPOINTMENT ONLY

SOUTHERN VALVE CO. SECOND FLOOR, 8 POTTERS ROAD, NEW BARNET, HERTS.

Telephone 01-440/8841 MAIL ORDER ONLY. MINIMUM ORDER 60p

Some leading makes available. VAT invoices issued on request.

All New and Boxed. "Quality" Branded Valves. Guaranteed 3 months. BVA etc.

6% Allowed in lieu of Guarantee! Already deducted from our Prices!

NOTE: PLEASE VERIFY CURRENT PRICES. Correct only at time of going to press.

DY86/7 53p	EF86 55p	GY501 £1.40	PCF802 80p	PL36 £1.00	PY500A £1.80
DY802 53p	EF89 55p	PC86 78p	PCF805 £1.70	PL81A 65p	UBF89 42p
ECC81 54p	EF183 55p	PC88 78p	PCF806 75p	PL83 50p	UCC85 50p
ECC82 60p	EF184 55p	PC97 75p	PCF808 £1.70	PL84 50p	UCH81 58p
ECC83 60p	EH90 60p	PC900 65p	PCL82 85p	PL500 £1.15	UCL82 72p
ECC85 50p	EL34 £1.85	PC834 55p	PCL83 80p	PL504 £1.15	UCL83 95p
ECH81 55p	EL84 50p	PC85 50p	PCL84 85p	PL508 £1.60	UF89 60p
ECH84 85p	EL509 £2.30	PC899 50p	PCL805 £1.85	PL509 £3.05	UL41 99p
ECL80 52p	EM84 90p	PC189 55p	PCL85 £1.85	PL519 £3.30	UL84 90p
ECL82 62p	EY86-7 46p	PCF80 80p	PCL86 85p	PL802 £2.80	UY85 60p
ECL86 72p	EY500A £1.60	PCF86 60p	PCL200 £1.40	PY88 85p	U25 60p
EF80 41p	EL280 42p	PCF200 £1.60	PD500 £3.60	PY800 63p	U26 60p
EF85 45p	EZ61 44p	PCF301 60p	PFL200 £1.35	PY801 63p	

We offer return of post service. CWO ONLY. No C.O.D. MANY OTHERS Post free over £20. £5 to £20-80p (max.) AVAILABLE

Items in stock at time of going to press but subject to possible market fluctuations

STOP PRESS One valve post 13p, each extra valve 6p. Large valves 2p each extra.

EL519, etc. MAX 75p. LISTS AND ENQUIRIES, S.A.E. PLEASE!

EX STOCK ALL PRICES INCLUDE VAT @ 12 1/2%.

ENQUIRIES WELCOMED FROM TRADE AND RETAIL (same prices)

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL L2 2DY

MICROPHONES: EM506 Electret Dual Imp (50K + 600K) Imp Stick Mic, with Battery £11.00. Electret Model ECM105 Pencil Hand Mics 1K Ohm impedance, with standard Jack £2.85. EM104 Tie Clip, Electret supplied with battery 1K Imp £4.95. UD130 Dual Imp (50K + 600K) moving-coil dynamic mic, cardioid response £2.25p.

B buzzers, GPO open type 3-6V 30p. Large plastic domed type loud note 6 or 12 volts 50p. Solid state buzzers, miniature, 6-9-12-24 volt 15ma 75p each.

MAINS TRANSFORMERS, all 240V AC primary, postage shown in brackets per transformer. 6-0-6 100ma, 9-0-9 75ma, 12-0-12 50ma 75p each (15p). 0-4-6-9 150ma no mounting bracket, 65p (20p). 12-0-12 100ma 95p (15p). 12V 500ma 95p (22p). 12V 2 amp £2.25 (45p). 12V 4 amp £2.75 (54p). 15-0-15V 1 amp £2.10 (45p). 30-0-30V 1 amp £2.75 (54p). 0-12-15-20-24-30V tapped at 2 amp £4.50 (54p). 20-0-20V 2 amp £3.50 (54p). 25V 1.5 amp £4.45 (45p). 18V 1.5 amp rectified £2.00 (45p). 35V 2 amp, 2-5V 2 amp Toroid £2.95 (54p). 20V 2-5 amp, £2.20 (54p). Murata MA401L 40KHz rec/send transducers £3.25 pair.

SMITHS TRANSISTORISED AUDIO WARNING DEVICE, 6-12V 30p.

BOARDS SURPLUS. Reed Board with 14 12v Reed SP c/o RLAS £1.75. LM309K 5v Regulator Panel 65p.

NEW LOW COST MULTIMETERS.

KRT100, 1000Ω, P.V. 1kv AC/DC, 150mA DC current, 0-100KΩ res. mirror scale, switched range selector, £4.65.

KRT101, same as KRT100 but range selection is by prod insertion, £3.50.

TAPE HEADS Mono Cassette £1.30. Stereo version £3.00.

SOLDER SUCKER, high suction eye protection shield £4.95.

PROJECT BOXES, black plastic ABS with lid 75 x 56 x 35 44p; 95 x 71 x 35, 52p 115 x 95 x 36 60p.

TERMS: cash with order, (or official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost. VAT inclusive prices. New Illustrated Catalogue now ready. S.A.E. please.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051 235 0982.

G.T.ELECTRONICS (ACTON) LTD.

WEST LONDON'S LARGEST RETAIL ELECTRONIC COMPONENT STOCKISTS

WE ARE ONLY A PHONE CALL AWAY

01-994 6275

FOR

RESISTORS
INCLUDING
METAL FILM
METAL OXIDE
CARBON FILM
WIRE WOUND
POTENTIO-
METERS
PRESETS
CAPACITORS

POLYESTER
POLY-
CARBONATE
POLYSTYRENE
SILVER MICA
TANTALUM
ELECTROLYTIC
TUNING CAPS
TRIMMERS

FUSES

TRANSISTOR
PADS
TRANSISTOR
SKTS
METERS
MANY SURPLUS
BARGAINS

FOR

HARDWARE
KNOBS
CASES
SLEEVEING
WIRE AND CABLE
VERO PRODUCTS
P.C.B.

FOR

TRANSISTORS
DIODES
THYRISTORS
SCR's L.E.D.'s
TTL CMOS
LINEAR IC's
CRYSTALS
INDUCTORS
IF CANS

CHOKES

FORMERS
FERRITES
RELAYS
TRANSFORMERS
BULBS & HOLDERS
LENSES & NEONS

G.T.ELECTRONICS (ACTON) LTD.

Trade: 270 ACTON LANE, CHISWICK, LONDON. W4 5DG.

Retail: 267 ACTON LANE, CHISWICK, LONDON. W4 5DG.

TEL: 01-994 6275. Registered in England 1179820.

LOOK!

Here's how you master electronics.

.... the **practical** way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2. Read, draw and understand circuit diagrams.


In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

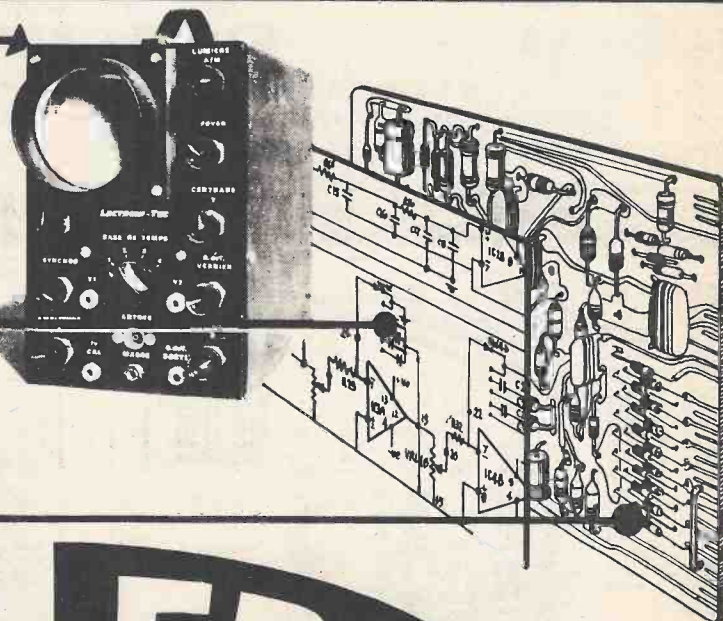4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



FREE

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WB279

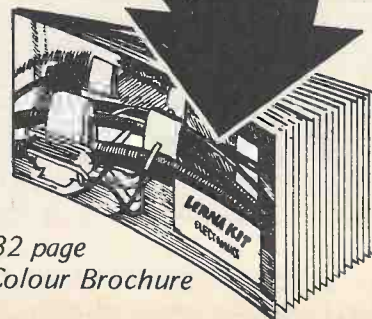


32 page
Colour Brochure

I.C.E. MULTIMETERS

TWICE the information in HALF the size

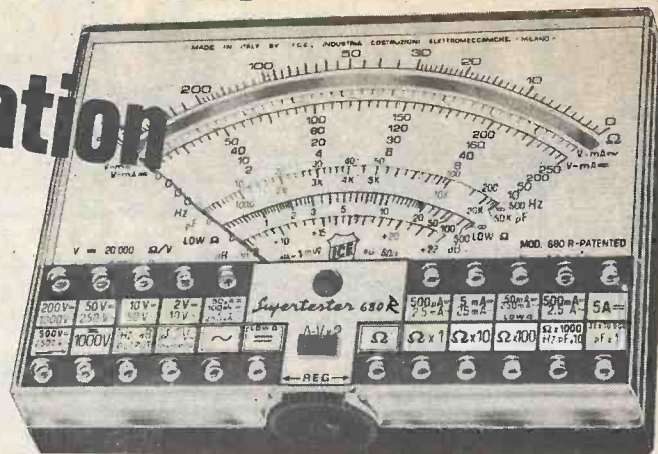The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



Supertester 680R (illustrated)

- * 20kΩ/V, ±1% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 80 Ranges – 10 Functions
- * 140 × 105 × 55mm

£32.00 + VAT

(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.

Supertester 680G

- * 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 48 Ranges – 10 Functions
- * 109 × 113 × 37mm

£24.50 + VAT

(For Mail Order add 80p P&P)

Microtest 80

- * 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 40 Ranges – 8 Functions
- * Complete with case – only 93 × 95 × 23mm

£16.60 + VAT

(For Mail Order add 80p P&P)



Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF. Tel: 20767

400mW ZENERS Unmarked Good 3-6, 6-8, 10, 11, 12, 13, 16, 18, 24, 30, 33, 36v. All at 10 for 40p.

ERIE RED CAP .01uf 100v.w. SUB-MINIATURE CAPACITORS @ 5p each.

BD187 4 Amp NPN PLASTIC POWER NPN TRANSISTORS @ 5 for £1.

MURATA 10.7MHz CERAMIC FILTERS @ 27p, VERNITRON FM4 10.7MHz FILTER @ 50p, MURATA 455kHz BFB FILTER @ 30p.

10 Amp S.C.R.s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.

DAU TRIMMERS 2 to 9pf @ 10p, 6 to 45pf @ 10p, 0 to 125pf @ 12p, 8 to 140pf @ 15p, TETTER VHF TRIMMERS 10pf @ 18p.

VHF POWER TRANSISTORS unmarked Good 2N 3375 @ £1, 2N 3866 @ 3 for 75p, 2N 3553 @ 3 for £1.10.

ELECTROLYTIC CAPACITORS 1000uf 100v.w. @ 50p, 2200uf 100v.w. @ 60p, 3300uf 64v.w. @ 60p, 3300uf 40v.w. @ 50p.

HC6U CRYSTALS 38MHz, 40MHz, 44-3MHz, 45-9MHz, 46-5MHz, 46-7MHz, 48-3MHz, 50-1MHz. All at 50p each.

3 PIN PLUG AND SOCKET like R.S. European Type with Two Metres of Cable @ 75p pair.

10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.

SUB-MINIATURE TANTALUM 4-7uf 10v.w. @ 5p, 6 for 25p.

50 2 Watt ZENERS assorted untested @ 57p.

DISC CERAMICS .01uf 50v.w. @ 20p doz. 1uf 18v.w. @ 25p doz.

100 MINIATURE DIODES CV 9637 pre-formed leads @ 57p.

VHF FETS 40673T @ 33p, E304 @ 25p, J310 @ 20p, MFE 131 @ 60p, BF 256 @ 25p, 2N 3819T @ 20p.

MINIATURE BUTTERFLY PRE-SET VARIABLE CAPACITORS spindles easily extended 25 × 25pf @ 50p, 38 × 38pf @ 60p, 38 × 38pf Wide Spaced @ 65p.

50 VARI-CAP DIODES LIKE BA 102 untested @ 57p.

200 1/2 Watt RESISTORS assorted for 75p.

MULLARD VARIABLE CAPACITORS Solid Dielectric 195 +80pf @ 40p.

30 ASSORTED 10XAJ CRYSTALS @ £1.10, 20 FT 243 CRYSTALS assorted @ £1.50, 20 FT 241A CRYSTALS assorted @ £1.10.

50 10X CRYSTALS assorted @ £1.50 (P & P £1.50).

TRANSISTORS BC 548 @ 10p, 6 for 50p, BC 549 @ 10p, 6 for 50p.

PLASTIC TRIACS 400 PIV 6 Amp @ 60p each.

COIL FORMERS 1/2" Dia. with core at 6 for 25p.

McMURDO 8 PIN PLUGS @ 20p, 8 PIN SOCKETS @ 20p, COVERS @ 15p.

600MHz FREQUENCY 8 DIGIT COUNTERS HFC 600 @ £115.

2 GHz STRIPLINE NPN TRANSISTORS @ £1 each.

100uf 100v.w. WIRE ENDED ELECTROLYTICS 10p, 5 for 35p.

MC 3340 ELECTRONIC ATTENUATOR I.C. with data @ 50p.

1uf 25v.w. ELECTROLYTICS at 6 for 25p.

20 PHOTOTRANSISTORS AND DARLINGTONS assorted untested @ £1.

SOLDER-IN FEED THRU's 5-8pf, 1000pf all 20p doz.

MULLARD T PACK 800MHz TRANSISTORS 9F 362 @ 25p.


CRYSTALS 10X 8010kHz @ 40p, 10XAJ 7010kHz @ 30p.

VARIABLE CAPACITORS 25 + 25 + 25pf 1" Spindle direct drive @ 75p.

ELECTRET MICROPHONE INSERTS with FET Pre-amp @ £1.85.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas post at cost.

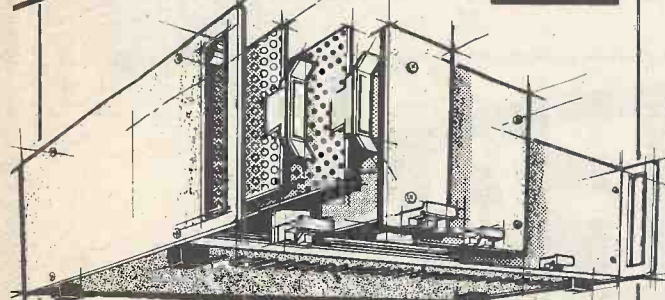OUR RANGE OF
PRODUCTS ARE NOW INDIVIDUALLY
AND ATTRACTIVELY PACKAGED



Our new 1978 catalogue lists a card frame system that's ideal for all your module projects — they used it in the ETI System 68 Computer. And we've got circuit boards, accessories, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

RST VALVE MAIL ORDER CO.

CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

SPECIAL EXPRESS MAIL ORDER SERVICE

SEMICONDUCTORS

AA119 0-10	AS226 0-40	BC159 0-10*	BCY72 0-13	BF194 0-09*	BZX61 0-18	OA70 0-30	OC82 0-65	ZS271 0-23*	2N697 0-25	2N3055 0-70
AA330 0-27	AS227 0-40	BC167 0-12*	BCZ11 1-50	BF195 0-09*	Series 0-13	OA79 0-30	OC83 0-65	ZS278 0-57*	2N698 0-30	2N3440 0-60
AA332 0-42	AS215 1-25	BC170 0-11*	BD121 1-20	BF197 0-12*	BZY88 0-13	OA81 0-30	OC84 0-65	ZTX107 0-14*	2N705 1-20	2N3441 0-80
AA313 0-18	AS216 1-25	BC171 0-10*	BD123 1-20	BF200 0-27	CRS/105 0-40	OA85 0-30	OC122 1-50	ZTX109 0-10*	2N708 0-15	2N3442 1-10
AA215 0-34	AS217 1-25	BC172 0-10*	BD124 1-30	BF224 0-20*	CRS/140 0-60	OA91 0-08	OC139 2-25	ZTX300 0-12*	2N930 0-20	2N3614 1-50
AC107 0-60	AS221 2-00	BC173 0-12*	BD135 0-38*	BF258 0-26	CRS/305 0-45	OA95 0-08	OC140 2-75	ZTX301 0-13*	2N1131 0-26	2N3702 0-11*
AC125 0-20	AU110 1-70*	BC178 0-14	BD136 0-34*	BF259 0-32	CRS/340 0-70	OA200 0-09	OC141 3-25	ZTX302 0-15*	2N1132 0-26	2N3703 0-13*
AC126 0-20	AU113 1-70*	BC179 0-16	BD138 0-35*	BF336 0-20*	GEK66 1-50	OA202 0-09	OC170 1-00	ZTX303 0-17*	2N1302 0-26	2N3704 0-13*
AC127 0-20	AU110 1-70*	BC182 0-11*	BD139 0-43*	BF338 0-21*	GEK541 1-75	OA211 1-00	OC171 1-00	ZTX304 0-19*	2N1303 0-35	2N3705 0-13*
AC128 0-20	BA145 0-13*	BC183 0-10*	BD140 0-44*	BF339 0-21*	GJ3M 0-75	OA220 1-00	OC200 1-50	ZTX311 0-12*	2N1304 0-45	2N3706 0-13*
AC141 0-25	BA148 0-13*	BC184 0-11*	BD144 2-00	BF321 3-96	GM0378A 1-75	OA2208 1-00	OC201 1-75	ZTX500 0-13*	2N1305 0-45	2N3707 0-13*
AC141K 0-35	BA154 0-09	BC212 0-13*	BD181 1-10	BF528 2-23	K5100A 0-45*	OA2207 1-00	OC203 1-75	ZTX501 0-14*	2N1306 0-50	2N3708 0-10*
AC142 0-20	BA155 0-10	BC213 0-12*	BD182 1-18	BF529 0-20*	MJE370 1-17	OC204 2-50	OC205 2-50	ZTX502 0-16*	2N1307 0-50	2N3709 0-13*
AC142K 0-30	BA156 0-09	BC214 0-15*	BD237 0-10	BFV10 0-65	MJE371 0-61	OC206 2-50	OC207 1-75	ZTX503 0-17*	2N1308 0-55	2N3710 0-10*
AC176 0-20	BAW62 0-05	BC237 0-09*	BD238 0-55	BFV11 0-65	MJE371 0-61	OC208 2-50	OC209 2-50	ZTX504 0-20*	2N1309 0-55	2N3711 0-10*
AC187 0-20	BAX13 0-06	BC238 0-12*	BDX10 0-91	BFX64 0-22	MJE520 0-52	OC21 3-00	OC212 1-75	ZTX505 0-15*	2N1613 0-25	2N3712 1-75
AC188 0-20	BAX16 0-09	BC301 0-25	BDX32 0-20	BFX85 0-23	MJE521 0-55	OC22 3-00	OC223 1-75	ZTX506 0-16*	2N1671 0-50	2N3713 0-20
AC187 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC23 3-00	OC234 0-08	ZTX507 0-17*	2N1993 0-25	2N3714 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC24 3-00	OC235 0-08	ZTX508 0-18*	2N2147 1-75	2N3715 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC25 3-00	OC236 0-08	ZTX509 0-19*	2N2148 1-85	2N3716 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC26 3-00	OC237 0-08	ZTX510 0-20*	2N2149 0-25	2N3717 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC27 3-00	OC238 0-08	ZTX511 0-21*	2N2150 0-25	2N3718 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC28 3-00	OC239 0-08	ZTX512 0-22*	2N2151 0-25	2N3719 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC29 3-00	OC240 0-08	ZTX513 0-23*	2N2152 0-25	2N3720 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC30 3-00	OC241 0-08	ZTX514 0-24*	2N2153 0-25	2N3721 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC31 3-00	OC242 0-08	ZTX515 0-25*	2N2154 0-25	2N3722 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC32 3-00	OC243 0-08	ZTX516 0-26*	2N2155 0-25	2N3723 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC33 3-00	OC244 0-08	ZTX517 0-27*	2N2156 0-25	2N3724 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC34 3-00	OC245 0-08	ZTX518 0-28*	2N2157 0-25	2N3725 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC35 3-00	OC246 0-08	ZTX519 0-29*	2N2158 0-25	2N3726 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC36 3-00	OC247 0-08	ZTX520 0-30*	2N2159 0-25	2N3727 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC37 3-00	OC248 0-08	ZTX521 0-31*	2N2160 0-25	2N3728 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC38 3-00	OC249 0-08	ZTX522 0-32*	2N2161 0-25	2N3729 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC39 3-00	OC250 0-08	ZTX523 0-33*	2N2162 0-25	2N3730 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC40 3-00	OC251 0-08	ZTX524 0-34*	2N2163 0-25	2N3731 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC41 3-00	OC252 0-08	ZTX525 0-35*	2N2164 0-25	2N3732 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC42 3-00	OC253 0-08	ZTX526 0-36*	2N2165 0-25	2N3733 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC43 3-00	OC254 0-08	ZTX527 0-37*	2N2166 0-25	2N3734 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC44 3-00	OC255 0-08	ZTX528 0-38*	2N2167 0-25	2N3735 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC45 3-00	OC256 0-08	ZTX529 0-39*	2N2168 0-25	2N3736 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC46 3-00	OC257 0-08	ZTX530 0-40*	2N2169 0-25	2N3737 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC47 3-00	OC258 0-08	ZTX531 0-41*	2N2170 0-25	2N3738 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC48 3-00	OC259 0-08	ZTX532 0-42*	2N2171 0-25	2N3739 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC49 3-00	OC260 0-08	ZTX533 0-43*	2N2172 0-25	2N3740 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC50 3-00	OC261 0-08	ZTX534 0-44*	2N2173 0-25	2N3741 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC51 3-00	OC262 0-08	ZTX535 0-45*	2N2174 0-25	2N3742 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC52 3-00	OC263 0-08	ZTX536 0-46*	2N2175 0-25	2N3743 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC53 3-00	OC264 0-08	ZTX537 0-47*	2N2176 0-25	2N3744 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC54 3-00	OC265 0-08	ZTX538 0-48*	2N2177 0-25	2N3745 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC55 3-00	OC266 0-08	ZTX539 0-49*	2N2178 0-25	2N3746 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC56 3-00	OC267 0-08	ZTX540 0-50*	2N2179 0-25	2N3747 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC57 3-00	OC268 0-08	ZTX541 0-51*	2N2180 0-25	2N3748 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC58 3-00	OC269 0-08	ZTX542 0-52*	2N2181 0-25	2N3749 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC59 3-00	OC270 0-08	ZTX543 0-53*	2N2182 0-25	2N3750 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC60 3-00	OC271 0-08	ZTX544 0-54*	2N2183 0-25	2N3751 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC61 3-00	OC272 0-08	ZTX545 0-55*	2N2184 0-25	2N3752 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC62 3-00	OC273 0-08	ZTX546 0-56*	2N2185 0-25	2N3753 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC63 3-00	OC274 0-08	ZTX547 0-57*	2N2186 0-25	2N3754 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC64 3-00	OC275 0-08	ZTX548 0-58*	2N2187 0-25	2N3755 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC65 3-00	OC276 0-08	ZTX549 0-59*	2N2188 0-25	2N3756 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC66 3-00	OC277 0-08	ZTX550 0-60*	2N2189 0-25	2N3757 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC67 3-00	OC278 0-08	ZTX551 0-61*	2N2190 0-25	2N3758 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC68 3-00	OC279 0-08	ZTX552 0-62*	2N2191 0-25	2N3759 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC69 3-00	OC280 0-08	ZTX553 0-63*	2N2192 0-25	2N3760 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC70 3-00	OC281 0-08	ZTX554 0-64*	2N2193 0-25	2N3761 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC71 3-00	OC282 0-08	ZTX555 0-65*	2N2194 0-25	2N3762 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC72 3-00	OC283 0-08	ZTX556 0-66*	2N2195 0-25	2N3763 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC73 3-00	OC284 0-08	ZTX557 0-67*	2N2196 0-25	2N3764 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC74 3-00	OC285 0-08	ZTX558 0-68*	2N2197 0-25	2N3765 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC75 3-00	OC286 0-08	ZTX559 0-69*	2N2198 0-25	2N3766 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC76 3-00	OC287 0-08	ZTX560 0-70*	2N2199 0-25	2N3767 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC77 3-00	OC288 0-08	ZTX561 0-71*	2N2200 0-25	2N3768 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC78 3-00	OC289 0-08	ZTX562 0-72*	2N2201 0-25	2N3769 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC79 3-00	OC290 0-08	ZTX563 0-73*	2N2202 0-25	2N3770 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY20 0-15	BFX87 0-21	MJE525 1-25	OC80 3-00	OC291 0-08	ZTX564 0-74*	2N2203 0-25	2N3771 0-10*
AC188 0-20	BAX16 0-09	BC301 0-25	BDY2							

Marshall's Electronics



A. Marshall (London) Ltd., Dept: PW Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805 Retail Sales
London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, B516 2LX. Tel: 0272 654201.

2N929 0-37	2N3417 0-25	2N4062 0-20	2N5245 0-37	AF106 0-60	BC182L 0-15	AY-3-8500 6-50	CA3051 1-83	LM340T5 0-83	LM741C 0-70	LM7805KC 1-75	SN76013N 1-50
2N930 0-37	2N3439 0-35	2N4121 0-27	2N5248 0-44	AF109 0-32	BC183A 0-12	CA3000 3-30	CA3052 1-78	LM340T12 0-83	LM741C-8 0-30	LM7812KC 1-75	SN76012NO 1-30
2N1131 0-32	2N3441 0-92	2N4122 0-27	2N5253 0-44	AF114 0-70	BC183LA 0-15	CA3001 4-25	CA3053 0-77	LM340T15 0-83	LM741C74 0-30	LM7815KC 1-75	SN76018KE 1-80
2N1303 0-30	2N3442 1-45	2N4123 0-19	2N5259 0-44	AF115 0-70	BC184 0-12	CA3002 3-30	CA3054 1-10	LM340T24 0-83	LM747CN 0-89	LM7824KC 1-75	SN76023N 1-50
2N1305 0-30	2N3456 0-25	2N4124 0-19	2N5401 0-44	AF118 0-70	BC184L 0-15	CA3005 2-50	CA3059 2-10	LM341P5 0-80	LM748-8 0-50	LM7812CZ 0-30	SN76023NO 1-30
2N1501 0-35	2N3566 0-25	2N4125 0-19	2N5445 1-65	AF124 0-70	BC205 0-17	CA3006 4-60	CA3062 3-75	LM341P12 0-80	LM748-14 0-50	LM7815CZ 0-30	SN76033N 2-35
2N1613 0-30	2N3567 0-25	2N4126 0-19	2N5447 0-16	AF139 0-75	BC212A 0-15	CA3007 4-15	CA3064 1-10	LM341P15 0-80	LM748-18 0-50	LM7815CZ 0-30	SN76033N 2-35
2N1637 0-72	2N3538 0-17	2N4235 1-35	2N5448 0-16	AF200 1-30	BC212LA 0-13	CA3008 2-55	CA3065 1-10	LM341P24 0-80	LM748-20 0-50	LM7815CZ 0-30	SN76033N 2-35
2N1890 0-30	2N3539 0-38	2N4236 1-65	2N5449 0-20	AF201 1-30	BC213B 0-15	CA3012 1-65	CA3068 3-80	LM348N 0-95	LM748-24 0-50	LM7815CZ 0-30	SN76033N 2-35
2N1893 0-30	2N3544 0-40	2N4237 1-65	2N5458 0-35	AF239 0-70	BC213LA 0-17	CA3013 1-85	CA3070 1-90	LM348N 0-95	LM748-28 0-50	LM7815CZ 0-30	SN76033N 2-35
2N1991 0-10	2N3662 0-25	2N4240 1-70	2N5555 0-85	AF279 0-88	BC214 0-18	CA3014 2-20	CA3071 1-90	LM348N 0-95	LM748-32 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2193 0-50	2N3663 0-29	2N4250 0-26	2N6109 0-55	AF280 0-95	BC237B 0-15	CA3018 0-75	CA3072 1-90	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2194 0-42	2N3702 0-14	2N4250 0-26	2N6109 0-55	AF280 0-95	BC237B 0-15	CA3018 0-75	CA3072 1-90	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2217 0-55	2N3703 0-14	2N4256 0-32	2N6122 0-44	AS278 1-30	BC239B 0-13	CA3018A 1-10	CA3075 1-70	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2218 0-55	2N3704 0-14	2N4284 0-38	2N6123 0-48	AS278 1-30	BC239B 0-13	CA3018A 1-10	CA3075 1-70	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2219 0-38	2N3705 0-14	2N4285 0-32	2N6124 0-46	AS278 1-30	BC239B 0-13	CA3018A 1-10	CA3075 1-70	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2221 0-25	2N3706 0-14	2N4287 0-22	2N6125 0-47	AS278 1-30	BC239B 0-13	CA3018A 1-10	CA3075 1-70	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2222 0-55	2N3707 0-14	2N4288 0-22	2N6126 0-48	AS278 1-30	BC239B 0-13	CA3018A 1-10	CA3075 1-70	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2270 0-49	2N3708 0-12	2N4292 0-27	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2388 0-27	2N3709 0-12	2N4302 0-31	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2369 0-27	2N3710 0-12	2N4303 0-33	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2483 0-30	2N3711 0-12	2N4342 0-60	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2613 0-80	2N3712 1-39	2N4401 0-20	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2645 0-80	2N3714 1-55	2N4402 0-20	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2648 1-10	2N3716 1-70	2N4403 0-20	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2904 0-31	2N3719 0-21	2N4822 0-83	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2905 0-31	2N3819 0-36	2N4870L 0-58	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2906 0-25	2N3820 0-39	2N4871L 0-51	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2907 0-25	2N3821 0-95	2N4888 1-55	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2923 0-17	2N3827 0-27	2N4901 1-65	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2924 0-17	2N3854A 0-19	2N4902 2-20	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N2925 0-19	2N3855 0-30	2N4903 2-75	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3011 0-37	2N3856A 0-19	2N4904 1-85	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3020 0-75	2N3858A 0-20	2N4905 2-40	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3053 0-25	2N3859A 0-22	2N4920 0-83	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3054 0-72	2N3860 0-18	2N5086 0-30	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3055 0-75	2N3866 1-98	2N5087 0-30	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3108 0-75	2N3901 0-30	2N5088 0-30	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3133 0-50	2N3904 0-18	2N5089 0-30	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3242 0-68	2N3905 0-18	2N5129 0-62	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3250 0-35	2N3906 0-18	2N5130 0-22	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3301 0-45	2N3962 0-95	2N5131 0-22	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3302 0-39	2N4031 0-55	2N5137 0-22	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3392 0-17	2N4032 0-65	2N5143 0-22	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3394 0-17	2N4033 0-65	2N5180 0-58	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35
2N3397 0-19	2N4036 0-72	2N5190 0-65	2N6288 0-50	BC113 0-22	BC259B 0-19	CA3021 2-40	CA3086 0-50	LM348N 0-95	LM748-36 0-50	LM7815CZ 0-30	SN76033N 2-35

1979 CATALOGUE IS AVAILABLE NOW!
LOTS OF NEW PRODUCTS AND IDEAS.
PRICE 50p POST PAID OR 40p TO CALLERS.

Prices correct at 7 Dec. 1978. All prices include VAT. P & P 40p.

+ BATTERY FLUORESCENT LIGHTING —

Type "A"




Type "C"



Type "B"



Type "D"

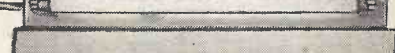

White Enamel cases as shown above, including lampholders. Type "A" or "B" £1.50. Case only, £1.00. Plastic Lampholders to suit 50p pair. Ceramic (adaptable) 40p pair. Tubes to fit (21 in.) £1.00. (These can only be supplied when cases are ordered due to risk of postal damage.) Case type "C" (18 in.) or Case type "D" (12 in.) including lampholders £1.25.

INVERTER TRANSFORMERS, special design for maximum efficiency
Transistor, Heat Sink, Circuit board cut to size, Resistor, Capacitors etc £1.00 each
21 in. Fittings built and tested £4.95
12 in. ditto (Batten type) £3.95

THIS IS ABOUT HALF THE PRICE THAT A SIMILAR FITTING WOULD COST YOU ELSEWHERE!!!!
WHY NOT DO AS MANY OTHERS ARE DOING, BUILD THEM AND SELL THEM TO YOUR CAMPING FRIENDS?

PRINTED CIRCUITS. WHY NOT MAKE YOUR OWN WITH FOTOLAK POSITIVE LIGHT SENSITIVE LACQUER

Now you can produce perfect printed circuits in minutes! Method: Spray cleaned board lightly with lacquer. When dry, place positive master of required circuit on now sensitised surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK Aerosol	£1.50	Plain Copper-clad Fibre-glass	Single-sided	Double
Developer	30	Approx. 3-18mm thick, sq. ft.	£1.25	£1.50
Ferric Chloride	40	Approx. 2-00mm thick, sq. ft.	£2.00	£2.50
Clear Acetate Sheet	12	Approx. 1-00mm thick, sq. ft.	£1.50	£1.75
Daylo Pens	98	Approx. .79mm thick, sq. ft.	£1.25	£1.50
		Single-sided Copper-clad paxolin.		
		Pack of 10 sheets each 245mm x 150mm		£2.50

Giant packs of unused mixed components! Weight 4lbs., these contain an assortment of resistors (carbon and wire-wound), capacitors, (electrolytic, paper, silver-mica, polyester and polystyrene), transistors, diodes, volume and pre-set controls and hosts of other 'bits and pieces'. No two bags are the same, but all contain a jolly good mixture of parts. Ideal for the odds and ends box!!! Per bag £3.00

SPECIAL OFFER! Few only 3-channel (each 750 watts) Sound-to-light units. Fantastic value for money! Plug into any loudspeaker socket and create your own disco-type light show! Any mains lamps may be used £17.95

Brand new printed circuit boards containing I.C.'s, transistors, diodes, resistors, capacitors etc. etc. It is quite impossible to list these so we are selling by weight at £1.00 per lb. This could include upwards of 100 integrated circuits! Send as many £1's as you wish, we will weigh as varied a parcel as possible and refund your change!

PLEASE NOTE: All lighting and printed-circuit materials plus 8% VAT. Other goods 12½%. No VAT on overseas orders. Postage INLAND 6p per order. Overseas include extra to cover. We will refund any excess paid. Any enquiries for further details MUST include stamped addressed envelope!


G. F. MILWARD

(ELECTRONIC COMPONENTS LTD.), 369 Alum Rock Road, B'Ham B8 3DR. 021-327 2339

The Logic Probes

When you see what these new CSC logic probes can do, in such a small size, and at such small prices, there's only one word for it:-

Amazing!

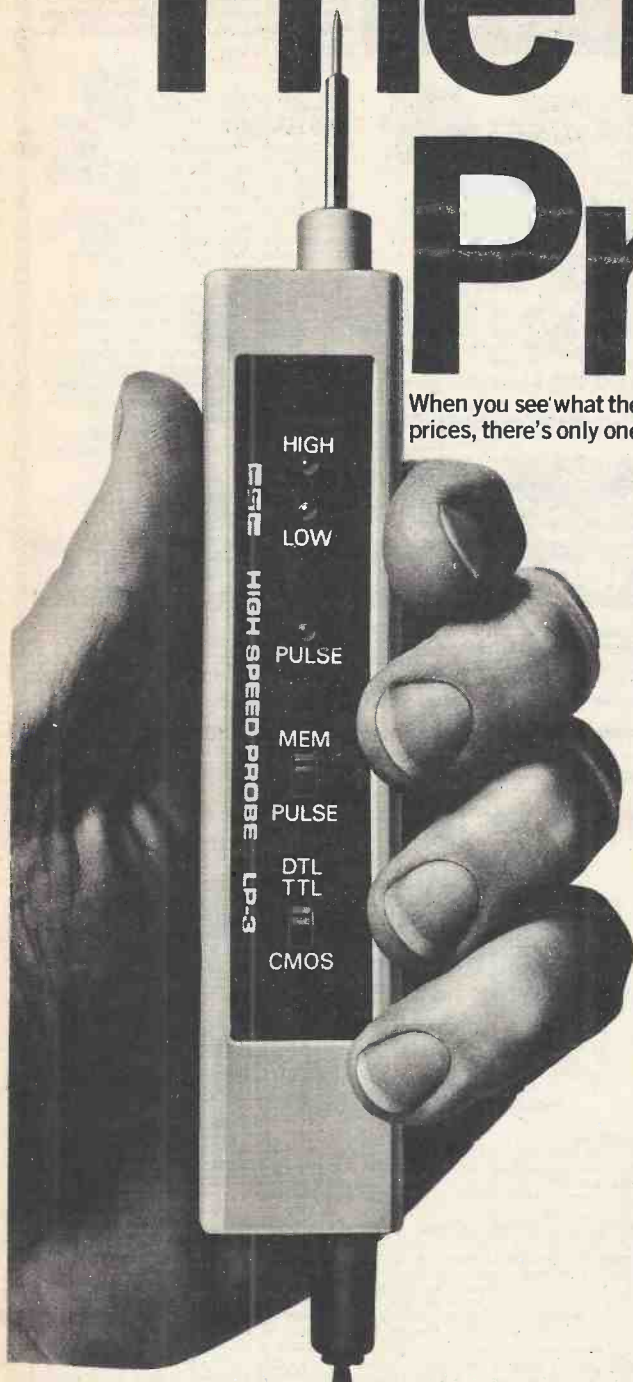

LP-1 Unit Price £31.00 • Post & Package £1.50 • VAT £2.60 • **Total £35.10.**

Clip the leads to the power supply of the circuit under test, touch the probe tip to any pin, pad or component and you're in business. The 'HIGH' and 'LOW' LEDs show logic states 1 or 0, if neither come on you've got open circuit, tri-state, signal out of tolerance (or no power!).

The 'PULSE' LED flashes once for any pulse 50nsec or longer, and flashes regularly at 3Hz for high frequency trains. Then, while 'PULSE' is flashing, 'HIGH' will come on alone to show duty-cycles over 85%, 'LOW' alone to show less than 15%, and with both on together duty-cycles can be estimated between 15% and 85% by relative brightness.

In the MEMORY mode, the leading edge (positive- or negative-going) of any pulse will latch a flip-flop on and keep the PULSE LED lit as long as power is applied to the probe. You can catch events that are hard to see even with a high quality scope!

LP-1 is switch-selectable for DTL/TTL and HTL/CMOS circuits.

LP-2 Unit Price £18.00 • Post & Package £1.25 • VAT £1.54 • **Total £20.79.**

Economy version of LP-1, with the same HTL/CMOS and DTL/TTL capability. 'HIGH' or 'LOW' LEDs function as in LP-1, 'PULSE' catches pulses as short as 300nsec and shows pulse trains as 10Hz blink. When pulsing, 'HIGH' comes on to show duty-cycles above 70%, 'LOW' shows below 30%, both on together show between 30% and 70%. 300,000 Ohm input impedance protects your circuit under test, and the low price brings the advantages of our quick, easy LOGIC PROBE technique to anyone interested in logic circuitry.

LP-3 Unit Price £49.00 • Post & Package £1.50 • VAT £4.04 • **Total £54.54.**

Super-high speed version, captures pulses as short as 10nsec, and monitors pulse trains as rapid as 50MHz. That's better performance than many oscilloscopes! And no bulky instruments, no set-up time. At frequencies up to 1.5MHz you can estimate duty-cycles by the High/Low relative intensity, as with LP-1. DTL/TTL and HTL/CMOS are switch-selectable, of course, plus 'MEM' memory mode to latch on to any pulse, pulse train or passing transient. LP-3 is the ideal trouble-shooter for your fastest logic circuits, and like all CSC probes is well-designed, handy and easy to use, robust, reliable and individually tested before it leaves the factory.

And the new pulser DP-1 Unit Price £51.00 • Post & Package £1.50 • VAT £4.20 • **Total £56.70.**

The Digital Pulser: another new idea from CSC. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 100Hz. The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And a very reasonable price.

How to order. Telephone 0799-21682 and give us your Access, Barclaycard or American Express number, and your order will be in the post that night. Or, write your order, enclosing cheque or postal order, or stating credit card number and expiry date. (Don't post the card!). Alternatively, ask for our latest catalogue, showing all CSC products for the engineer and the home hobbyist.

(Prices are for UK only. For Europe add 10%, outside Europe add 12½% to total prices.)

Specification	LP-1	LP-2	LP-3	DP-1
Input Impedance	100,000Ω	300,000Ω	500,000Ω	Output Tri State
Minimum Detectable Pulse	50ns	300ns	10ns	Autopolarity Pulse Sensing
Max. Input Signal (Freq.)	10 MHz	1.5 MHz	50 MHz	Sink and Source 100 ma
Pulse Detector (LED)	High Speed Train or Single Event	High Speed Train or Single Event	High Speed Train or Single Event	Pulse Train: 100pps
Pulse Memory	Pulse or Level Transition Detected and Stored	None	Pulse or Level Transition Detected and Stored	LED indicator flashes in Single Pulse. Stays lit on Pulse Train

CONTINENTAL SPECIALTIES CORPORATION (UK) LTD.,
UNIT 1, SHIRE HILL INDUSTRIAL ESTATE, DEPT 6J
SAFFRON WALDEN, ESSEX CB11 3AQ TEL: 0799-21682




REGISTERED IN LONDON: 1303780 VAT No: 224 8074 71
DEALER ENQUIRIES WELCOME.

TRADE MARK APPLIED FOR © CSC (UK) LTD 1977.

ANNOUNCING

THE NEW EUROREADBOARD

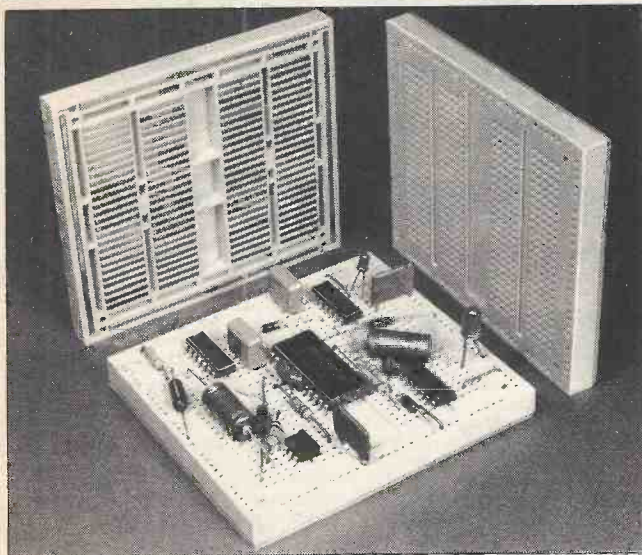

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points.

4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

Double-sided, nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m.ohms)

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

What other breadboarding system has as many individual contacts, offers all these features and only costs £5.80 inclusive of VAT and P.P. — NONE.

At £5.80 each The EuroBreadBoard is unique value for money. At £11 for 2 The EuroBreadBoard is an indispensable design aid.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent, DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroBreadBoard @ £5.80 ☐ Please
or 2 EuroBreadBoards @ £11.00 ☐ Tick

(All prices include VAT and P.P., but add 15% for overseas orders).

Name.

Company.

Address.

.....

.....

Tel. No. PW179

Please make cheque/P.O.'s payable to David George Sales

NO DISCO SYSTEM IS COMPLETE WITHOUT...



CITRONIC MM313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono, inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU
£80.46 inc. VAT (P.P. £1.50)

PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF PRACTICAL WIRELESS

Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K. No X over required. They can be used in any PA system up to 100W. Why pay more? OUR PRICE ONLY **£4.99** each (P&P 35p each)



BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET **£0.65** (P&P 35p) P551 PLUG **£1.84** (P&P 35p) Carriage on 10 or more nominal **£1.00** Also available 6-way multicore cable (6 Amps per core) ex stock. **£0.65** per metre. Please phone for carriage quote.



PROJECTORS

SQUIRE MULTIFECT 150

including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use.

A BARGAIN AT £40.50 (P&P £1.00)



STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250 W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only **£65.00 + VAT** attachments extra

PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H/H Disco Speakers 12" and 15" BSR and Garrard decks at discount prices.



Plus sockets, Fuses, Plugs, etc etc.

Roger Squire's DISCO GEAR

Personal callers: ROGER SQUIRE'S DISCO CENTRES

LONDON: 175 Junction Road, Tufnell Park N18 5QQ. 01-272 7474

BRISTOL: 125 Church Road, Redfield, Bristol BS6 9JR. 0272-550550

MANCHESTER: 251 Deansgate M3 4EN. 081-831 7676

GLASGOW: 1 Queen Margaret Rd., (off Queen Margaret Drive) Kelvinside, Glasgow G20 6DP

Open from 10-5 Tues-Sat
10-8 Weds.
Closed Mondays.

Tel. 041 946 3303

OPEN UP THE EXCITING WORLD OF SHORT WAVE LISTENING



SRX-30

For the advanced, keen short wave listener, the choice of receiver has usually been between cheap and nasty or very good but very expensive equipment. We think that the SRX-30 will provide that listener with excellent performance at a reasonable cost and is the answer to this eternal problem.

The SRX-30 provides AM, CW, USB and LSB reception on all frequencies from 500 kHz to 30MHz. All right, so does your Sooper Blooper Mk. 3 but you can't set the Sooper Blooper dial to the frequency you want and be sure that it's correct! The SRX-30 tuning system is so simple to operate. You have a dial reading in MHz from 0.29 and a main tuning dial reading 0-1000 kHz. So—if you know that Radio Siobovia is broadcasting on 10.295 MHz, you set the MHz dial to 10, the kHz dial to 295 and there you are. The MHz dial setting is not critical, as stability is guaranteed by a triple mixing drift cancelling system, thereby overcoming another problem in your Sooper Blooper Mk. 3: drift.

A further drawback to cheap receivers is massive image interference on the higher frequencies due to the use of a low IF, typically 455 kHz. The cure for this problem is the use of a high IF and the SRX-30 employs a first IF of around 40 MHz—so goodbye to first IF images. You could of course find the same system as this in the Racal RA17 series receivers; after all, the SRX-30 has copied the basic idea from this very receiver. The big drawback to the RA17 (apart from the price !!) is that unless you have the muscles of a prize fighter, lifting the RA17 may send you for a holiday at Hernia Bay (staying at the Truss House?).

To summarize, the SRX-30 covers 500 kHz to 30 MHz with excellent dial readout and reset accuracy; it has all mode (AM, CW, SSB) reception and is equally at home in broadcast or amateur bands: it has all the facilities of a top class communications receiver, RF gain, fine tuning, selectable sidebands, built in loud-speaker, operation from ac mains or 12v. Dc, rugged construction and super styling and all at an attractive price—£175 inc. VAT. Carr £3.

See it soon at your nearest stockist, you will be agreeably impressed.

For all that's good in Amateur Radio, contact:

LOWE ELECTRONICS LTD., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.

For full catalogue, simply send 45p in stamps and request catalogue CPW.

PROFESSIONAL KITS THAT SAVE YOU MONEY!!



MC020

AN ADVANCED MUSIC CENTRE for the experienced constructor. This unit is available as a fully wired chassis, in modular form or as a kit. It can be built in easy stages or as a complete unit. A variety of cassette decks are suitable.

SPECIFICATIONS

AMPLIFIER	Nominal	Intermediate Frequency:
Power Output:	2 x 25 watts RMS.	AM 475KHz
Distortion:	THD @ 2 x 20 watts 0.7%	FM 10.7KHz
Frequency Range:	@ -1.5dB 30Hz-15KHz	Aerial input: AM (Internal) Ferrite Rod 2 pin DIN Co-axial 75 ohm unbalanced!
Tone Control Range:	18dB	AGC: For 6dB audio change 46dB
VC-20dB	@ 100Hz-14dB	IF Bandwidth @ max sensitivity ± 1.5KHz @ 6dB
Basic Electrical centre	@ 10KHz-8dB	RF Sensitivity: @ 20dB S/N Ratio
Treble Electrical centre	@ 10KHz-14dB	200KHz 1500V/m
Loudness Control:	VC30dB @ 100Hz-14dB	600KHz 500V/m
VC30dB	@ 10KHz-11dB	1400KHz 200V/m
Filters:	VC30dB @ 10KHz-6dB	FM: RF Sensitivity: @ 26dB S/N (mono) 2.5V
Controls:	5 rotary: volume, balance, bass, treble tuning.	88MHz 100KHz
Switches:	0 push button: phono, tape, radio, aux. input, mono/stereo, loudness, filter, speaker switching, separate mains switch.	@ 46dB S/N (mono) 16V
Meters:	2 signal strength: FM tuning	@ 46dB S/N (stereo) 125V
Sockets:	Headphones: 5 pin DIN Aux: AM aerial (ext) FM aerial (co-axial): 4 x 2 pin DIN/L/S	Distortion: @ Decoder O/P 0.9%

SUITABLE SURPLUS MODULES. Fully Wired

Stereo power amp 25w rms P/channel	£7.50
Low noise pre amp. Full freq correction	£5.99
RF Board MW/LW/MPX Fet. 3 x IC	£9.99
P.S.U. £3.50 Transformer £5.50	
Selector Board 8 way	£3.99
Complete chassis massive 22 Inches	£8.50




TU020

A Hi Fi tuner amplifier

This unit can be built from our modules or as a complete kit. Input for mag cartridge, tape record/playback, MW/LW/VHF stereo, tuner. Uses the same R F Board as does the Wimborne with birdie filters, multiplex filter, varicap tuning on MW and LW. Items from the Wimborne numbers 2 and 3 can be used for different performance specifications.

SPECIFICATIONS

Power output 25 Watts RMS per channel (both channels driven)	FM sensitivity 1.0V for 26 dB S/N ratio
Total harmonic distortion 0.05%	IF rejection 60 dB image rejection 60 dB
Bass 100 Hz ± 12 dB	Stereo separation 40 dB
Treble 10 KHz ± 12 dB	AM sensitivity 200V at 1600 KHz 20 dB S/N ratio.
Frequency response ± 1.5 dB 30 Hz-20 KHz	
Fully wired modules, Preamplifier,	Magnetic PU amp £2.99
Power amplifier £6.99	Hardware kit £7.99
RF Board £9.50	PLEASE ADD £1 for postage and packaging for each item except the mag PU amp which is 30p.
Power supply unit £33.99	
Transformer £4.50	

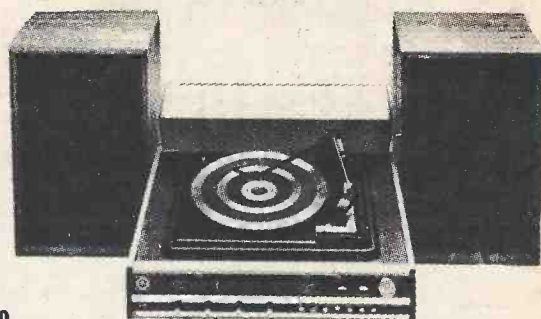

AU10

A Radio Record Player Kit which has everything you need to make a first class three band STEREO unit. Can be assembled in modular form or from scratch. A professional finish is guaranteed.

SPECIFICATIONS

Amplifier	2 x 10W RMS, both channels driven
Output	1% ± 2 x 5 watts
Distortion:	Four rotary
Controls:	1. OFF/ON/VOLUME
	2. Balance
	3. Treble
	4. Bass
Tone Control Range:	Bass @ 100 Hz ± 9dB
	Treble @ 10 kHz ± 9dB
Outputs:	2 x 2-pin DIN for 8 ohm loudspeakers
	1 switched stereo headphone socket
	1 5-pin DIN Aux. Tape in/out socket
Stereo Performance:	Frequency response @ ± 1.5dB 30 Hz-15KHz
	Separation 40dB
	Audio Filter—flat to 55 kHz-50dB @ 130 kHz
Controls:	7 Push Button: Phono, Tape, Mono, FM, MW, LW, AFC
	1 Rotary: Tuning
Radio Tuner	
Waveband Coverage:	Medium Wave 525-1620 kHz
	Long Wave 155-280 kHz
	FM VHF 88-108 kHz
Price Hardware Kit	8.90
Amplifier & Pots	8.75
PSU & Transformer	3.99
	RF Board 21.95
	Record Deck 13.95
	Dust cover 6.00



PW WIMBORNE

The most versatile music centre ever.

Complete kit price approximately £110 comparable price £180.

- 1 Hardware Kit, for a professional finish, trim, knobs, extrusions, sockets, top moulding 50 plus parts. £9.95.
 - 2 Amplifier Module (11-14) watts RMS per channel, wired and tested, £19.95, kit price £13.95.
 - 3 Mechanically tuned RF Board, absolutely complete and tested 1.5V sensitivity FET front end 7 way switch, MW, LW, stereo VHF, only requires 13 VDC. £21.95.
 - 4 Stereo cassette module, with CRO2 switching, low noise devices, ALC tape counter, excellent specification, incredible price £24.95.
 - 5 Varicap tuned RF Board, the ultimate AM/FM Receiver kit, MOSFET front end, Deviation mute, interstation mute, fantastic performance 1.0V sensitivity, Hitachi, AM receiver Ic, excellent MW/LW performance, complete with 7 way switch, The basis of the finest Hi Fi system, fully wired and tested. £33.95. Kit £26.95.
 - 6 Magnetic PU Amp with LM387 or discrete (BC 149). Both £2.99 each.
 - 7 Wooden Plinth plus base board £9.95.
 - 8 Perspex dust cover plus hinges £6.50.
 - 9 Mains transformer £2.99.
- All items include VAT. Please add £1 per item for postage and packaging, item 6 30p. For further details please send 15p.

REED HAMPTON LTD.

19 CHURCH LANE, WALLINGTON SURREY. Tel: (01) 647 0851

It's W-W-WINTER S-S

74 SERIES TTL IC'S

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.07	7427	£0.21	7472	£0.19	74107	£0.22	74165	£0.65
7401	£0.09	7428	£0.25	7473	£0.22	74110	£0.35	74166	£0.75
7402	£0.09	7430	£0.28	7474	£0.22	74111	£0.55	74167	£2.00
7403	£0.09	7432	£0.20	7475	£0.27	74118	£0.75	74174	£0.60
7404	£0.09	7433	£0.28	7476	£0.22	74119	£1.10	74175	£0.60
7405	£0.09	7437	£0.20	7480	£0.40	74121	£0.22	74176	£0.55
7406	£0.22	7438	£0.20	7481	£0.80	74122	£0.35	74177	£0.55
7407	£0.22	7440	£0.10	7482	£0.65	74123	£0.38	74180	£0.80
7408	£0.12	7441	£0.45	7483	£0.55	74136	£0.50	74181	£1.25
7409	£0.12	7442	£0.38	7484	£0.82	74141	£0.50	74182	£0.55
7410	£0.09	7443	£0.68	7485	£0.65	74145	£0.54	74184	£1.00
7411	£0.15	7444	£0.68	7486	£0.22	74150	£0.65	74190	£0.68
7412	£0.14	7445	£0.64	7489	£1.60	74151	£0.45	74191	£0.68
7413	£0.22	7446	£0.60	7490	£0.30	74152	£0.45	74192	£0.65
7414	£0.45	7447	£0.45	7491	£0.60	74154	£0.80	74193	£0.60
7416	£0.22	7448	£0.52	7492	£0.32	74155	£0.48	74194	£0.55
7417	£0.22	7450	£0.09	7493	£0.28	74156	£0.48	74195	£0.55
7420	£0.09	7451	£0.09	7494	£0.70	74157	£0.48	74196	£0.60
7421	£0.19	7452	£0.09	7495	£0.45	74160	£0.55	74197	£0.58
7422	£0.15	7453	£0.09	7496	£0.48	74161	£0.60	74198	£1.00
7423	£0.20	7454	£0.09	74100	£0.80	74162	£0.60	74199	£1.00
7425	£0.18	7460	£0.09	74104	£0.35	74163	£0.60	74279	£1.00
7426	£0.21	7470	£0.24	74105	£0.35	74164	£0.65		

CMOS I.C.'s

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.12	CD4017	£0.65	CD4031	£1.60	CD4055	£1.00
CD4001	£0.13	CD4018	£0.70	CD4035	£0.90	CD4056	£1.15
CD4002	£0.13	CD4019	£0.35	CD4037	£0.78	CD4059	£0.15
CD4006	£0.80	CD4020	£0.80	CD4040	£0.78	CD4070	£0.15
CD4007	£0.14	CD4021	£0.75	CD4041	£0.68	CD4071	£0.15
CD4008	£0.80	CD4022	£0.75	CD4042	£0.68	CD4072	£0.15
CD4009	£0.40	CD4023	£0.13	CD4043	£0.78	CD4081	£0.15
CD4010	£0.42	CD4024	£0.55	CD4044	£0.78	CD4082	£0.15
CD4011	£0.13	CD4025	£0.13	CD4045	£1.15	CD4510	£0.80
CD4012	£0.14	CD4026	£1.00	CD4046	£0.95	CD4511	£0.80
CD4013	£0.35	CD4027	£0.45	CD4047	£0.75	CD4516	£0.85
CD4014	£0.70	CD4028	£0.60	CD4049	£0.35	CD4518	£0.85
CD4015	£0.70	CD4029	£0.75	CD4050	£0.35	CD4520	£0.85
CD4016	£0.35	CD4030	£0.40	CD4054	£0.95		

BOOKS BY BABANI

The following books are offered at 10% off their normal retail price

		Sale Price
BP2	Handbook of Radio, TV and Industrial Transmittng Tube and Valve Equivalents	£0.54
BP6	Engineers and Machinists Reference Tables	£0.36
BP7	Radio and Electronic Colour Codes and Data	£0.14
BP10	Modern Crystal and Transistor Set Circuits for Beginners	£0.32
BP14	Second Book of Transistor Equivalents and Substitutes	£0.99
BP15	Constructors Manual of Electronic Circuits for the Home	£0.45
BP22	79 Electronic Novelty Circuits	£0.68
BP23	First Book of Practical Electronic Projects	£0.68
BP24	52 Projects Using IC741 (or equivalents)	£0.68
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	£0.77
BP27	Giant Chart of Radio Electronic Semi-conductor and Logic Symbols	£0.54
BP29	Major Solid State Audio Hi-Fi Construction Projects	£0.77
BP32	How to Build Your Own Metal and Treasure Locators	£0.77
BP34	Practical Repair and Renovation of Colour TV's	£0.86
BP35	Handbook of IC Audio Preamplifier and Power Amplifier Construction	£0.86
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	£0.99
BP37	50 Projects Using Relays SCR's and Triacs	£1.13
BP39	50 (FET) Field Effect Transistor Projects	£1.13
BP43	How to make Walkie-Talkie	£1.31
BP44	IC 555 Timer Projects	£1.22
BP47	Mobile Discotheque Handbook	£0.68
BP49	Popular Electronic Projects	£0.68
BP160	Coil Design and Construction Manual	£0.14
BP196	AF-RF Reactance Frequency Chart for Constructors	£0.68
BP202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	£0.68
BP205	First Book of Hi-Fi Loudspeaker Enclosures	£0.77
BP213	Electronic Circuits for Model Railways	£0.77
BP214	Audio Enthusiasts Handbook	£0.77
BP215	Shortwave Circuits and Gear for Experimenters and Radio Hams	£0.77
BP216	Electronic Gadgets and Games	£0.77
BP217	Solid State Power Supply Handbook	£0.77
BP219	Solid State Novelty Projects	£0.77
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	£0.86
BP222	Solid State Short Wave Receivers for Beginners	£0.86
BP223	50 Projects Using IC Ca3130	£0.86
BP224	50 CMOS IC Projects	£0.86
BP225	A Practical Introduction to Digital IC's	£1.08
BP226	How to Build Advanced Short Wave Receivers	£1.08

VPS30 Variable Regulated Stabilised Power Supply Module

Incorporating a short circuit protection and current limiting:
Voltage Regulation 2-30V
Regulated Current 0-2A
AC Input Maximum 25V
Eliminates the use of batteries and thus saves £1's—can be used time and time again.
ONLY £7.60 + V.A.T.

Brand New

ITT 923 Silicon Diodes 200mA 200V
100 off — £2.00
500 off — £9.00
1000 off — £15.00
10,000 off — £130.00

Single-Sided Fibre Glass Board
12" x 3 1/2" approx. 2 pcs £0.60

THYRISTORS

No. THY1A/50	1 Amp. 50 volt T05	18p
No. THY1A/400	1 Amp. 400 volt T05	32p
No. THY3A/50	3 Amp. 50 volt T064	25p
No. THY3A/200	3 Amp. 200 volt T064	32p
No. THY3A/400	3 Amp. 400 volt T064	40p
No. THY5A/50	5 Amp. 50 volt T066	25p
No. THY5A/400	5 Amp. 400 volt T066	40p
No. THY5A/600	5 Amp. 600 volt T066	50p
No. C106/4	6 Amp. 400 volt T0220	42p

TRIAC

S84	8 Amp. 400 volt T0220 Plastic	80p
-----	-------------------------------	-----

DIACS

1TT	V413 equit	12p
8R100	D32 each	12p

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF - 10µF
16202	18 Electrolytics	10µF - 100µF
16203	18 Electrolytics	100µF - 680µF

All 3 at SPECIAL PRICE of £1.20*

16160	24 Ceramic Caps	22pF - 82pF
16161	24 Ceramic Caps	100pF - 390pF
16162	24 Ceramic Caps	470pF - 3300pF
16163	21 Ceramic Caps	4700pF - 0.047µF

All 4 at SPECIAL PRICE of £1.60

RESISTOR PAKS

Order No.	60ΩW.	100 ohm - 820 ohm
16213	60ΩW.	1K - 8.2K
16214	60ΩW.	10K - 82K
16215	60ΩW.	100K - 820K
16216	60ΩW.	100 ohm - 820 ohm

All 4 at SPECIAL PRICE of £1.60*

16217	40ΩW.	1W - 8.2K
16218	40ΩW.	1K - 8.2K
16219	40ΩW.	10K - 82K
16220	40ΩW.	100K - 820K

All 4 at SPECIAL PRICE of £1.60*

VOLTAGE REGULATORS

Positive			
No. MVR7805	µA7805	T0220	55
No. MVR7812	µA7812	T0220	55
No. MVR7815	µA7815	T0220	55
No. MVR7818	µA7818	T0220	55
No. MVR7824	µA7824	T0220	55

Negative			
No. MVR7905	µA7905	TO220	75
No. MVR7912	µA7912	TO220	75
No. MVR7915	µA7915	TO220	75
No. MVR7918	µA7918	TO220	75
No. MVR7924	µA7924	TO220	75

µA723C T099	38p
LM309K T03	£1.20

SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak bank and singles Latching and non-Latching	£1.00*

AUDIO LEADS

Order No.	Description	Price
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug Mirror image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*

AUDIO PLUG AND SOCKET PAKS

Order No.	Description	Price
S1	5 x 3.5 mm Plastic Jack Plugs	40p*
S2	5 x 2.5 mm Plastic Jack Plugs	40p*
S3	4 x Std. Plastic Jack Plugs	50p*
S4	2 x Stereo Jack Plugs	30p*
S5	5 x 5 Pin 180° DIN Plugs	50p*
S6	8 x 2 Pin Loudspeaker Plugs	50p*
S7	8 x Phono Plugs Plastic	50p*
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*
S11	2 x Stereo Jack Sockets with instruction leaflet for Hi/Phone connection	50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*
S13	8 x 2 Pin DIN Chassis Sockets	50p*
S14	6 x Single Phono Sockets	40p*

P.C. BOARD

S110	Mixed Bundle. P.C.B. Fibre-glass/paper, single and double-sided. Fantastic value	75p
------	--	-----

SPECIAL OFFER!

UNTESTED

SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like 1N4148	40p
No. 16134	50 750mA Sil. top hat Rects.	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mw Zeners D.O.7 case	40p
No. 16137	30 NPN Plastic trans. like BC107/8	40p*
No. 16138	30 PNP Plastic trans. like BC177/8	40p*
No. 16139	25 NPN trans. like 2N697/2N1711 T039	40p
No. 16140	25 PNP trans. like 2N2905 T039	40p
No. 16141	30 NPN trans. like 2N706 T018	40p
No. 16143	30 NPN Plastic trans. like 2N3906	40p*
No. 16144	30 PNP Plastic trans. like 2N3905	40p*
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN T03 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 20 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

MAMMOTH I.C. PAK

Approx. 200 Pieces. Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked—you to identify.

Order No. 16223 £1.00

MATCHED PAIRS OF PNP GERMANIUM

MED. POWER TRANS

	VCE	VCB	HFE	Price
NKT301	40	60	30-100	35p per pair
NKT302	40	60	50-150	35p per pair
NKT303	20	30	30-100	25p per pair
NKT304	20	30	50-150	25p per pair

From U.S.A. by

DINDY

SCREW CASED

LOW NOISE

CASSETTES

Order No. S53 10 for £3.50* C90

HEAD-CLEANING

CASSETTE 45p each

RETURN OF THE AL20A

By popular demand—this useful 5W RMS power amplifier is offered at the re-introduitory price of £2.75 + V.A.T.—Hook-up and data supplied.

ETCH RESIST PENS

Order No. 1609 50p each

UNIUNCTION TRANSISTORS

	UT46	TIS43	20p
2N3819	15p	2N5458	18p

2 AMP. BRIDGE RECTIFIERS

Metal Stud Mounting			
No. S45	50V	(K8S 005)	28p
No. S46	100V	(K8S 01)	30p
No. S47	200V	(K8S 02)	34p

SALE T-T-TIME again!

SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	Price
16168	5 pieces Assorted Ferrite rods	40p
16169	2 pieces Tuning gangs MW/LW	40p
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p
16172	3 Micro switches	40p
16176	20 Assorted electrolytics	40p
16177	Trans types 1 pack Assorted Hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p
16184	15 Assorted Fuses 100mA 5 amp	40p
16188	60 1/2W resistors mixed values	40p
16187	30 metres stranded wire assorted colours	40p
S100	120 1/2W resistors. Pre-formed 1978 Prod. Our mix	60p*
S101	120 1/2W resistors. Pre-formed 1978 Prod. Mixed values	60p*
S102	250 1/2W resistors Range 100 ohms - 10 meg.	£2.00*
S103	220 1/2W resistors Range 100 ohms - 10 meg.	£2.00*
S104	60 Low ohms 1/2 watt resistors 10 - 100 ohms	60p*
S105	40 Low ohms 1/2 watt resistors 10 - 100 ohms	60p*
S106	25 Mixed wirewound resistors 20 Tantalum bead caps	£1.00*
S107	High quality electrolytics 10mF - 500mF voltage range 15 50V	£1.00*
S108	Our mix 40 for	£1.00*
16204	C280 Pak Contains 50 metal foil caps	£1.00*

POTENTIOMETERS

Slider 40mm TRAVEL

Order No.	Price
16191	6 x 470 Ohm LIN Single 40p*
S24	6 x 1 K LIN Single 40p*
S25	6 x 5 K LIN Single 40p*
16193	6 x 22 K LIN Single 40p*
16196	6 x 47 K LOG Single 40p*
16194	6 x 47 K LIN Single 40p*
S27	6 x 100 K LIN Single 40p*
S28	6 x 100 K LOG Single 40p*
S29	6 x 500 K LOG Single 40p*
S32	6 x 50 K LIN Single 40p*

Slider 60mm TRAVEL

S30	6 x 2.5 K LOG Single 40p*
S34	4 x 5 K LOG Dual 40p*
S36	4 x 100 K LOG Dual 40p*
S37	4 x 4.3 MEG LOG Dual 40p*
S34	6 x 220 K LIN Single 40p*
S95	6 x 100 K LOG Single 40p*
S96	6 x 500 K LIN Single 40p*
S38	Mixed slider pots, various values and sizes. Our mix only £1.00*
S39	6 x Chrome slider knobs 40p*

WIREWOUND

S90	Wirewound Pots Linear 1 Watt rating Mixed useful values 5 for £1.00*
-----	--

CARBON TYPES

S91	Car Radio type Dual Switched Pot P.C. mounting 100 K Lin switched 2.5 K Lin each 60p*
-----	---

DUAL POTS P.C. MOUNTING

6mm Shaft	Price
S92	4 x 100 K Lin £1.00*
S93	4 x 100 K Log £1.00*
16173	15 Rotary Pot Assorted 40p*
16186	25 Pre-set Assorted Values 40p*

ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

SILICON POWER TRANS. N.P.N.

S97	BD371 2 Amp 1.2w. 60Vceo Hfe 40-400. Case T092 with heat tab. 5 for	60p*
S98	2N5293 R.C.A. 36w 4 Amps 75Vceo Hfe 30-120. 5 for	£1.00*

CRYSTAL EAR PIECES

S126 Less plug £0.20

Plugs for above	Price
No. 16106 2.5 plastic	£0.09
No. 1697 3.5 plastic	£0.11

Mono Crystal Cartridge

S127	GP91/1SC Special Offer	£1.00
------	------------------------	-------

Nickel Cadmium Rechargeable Batteries 1.25V

S128	35000 Cell size = U2	£2.50
S129	900C Cell size = J1U1	£0.90
S130	Complete kit of parts to build nickel cadmium charger	£3.50

Super Save Pak

S124	5 x 741P	£1.00
S125	5 x 555	£1.00

S138 Surplus/ends of manufacturers line/pre-amp. with base, treble, volume control and circuit diagram supplied. ONCE ONLY OFFER

S137	20 Assorted Slider Knobs—chrome/Black	£1.25
------	---------------------------------------	-------

S131	2 x 12V Relays plastic case	£1.00
------	-----------------------------	-------

S132	2 x 24V Relays plastic case	£0.60
------	-----------------------------	-------

S133	A switch bank 5-way incl silver knob	£0.75
------	--------------------------------------	-------

S134	2 x Magnets suitable for reed switches	£0.10
------	--	-------

S135	1 Veroboard pak 2 pcs 45sq. ins. approx.	£0.80
------	--	-------

S136	15 Veroboard pak 2 pcs 60sq. ins. approx.	£1.10
------	---	-------

16199	1 Veroboard pak 30sq. ins. approx.	£0.50
-------	------------------------------------	-------

16200	15 Veroboard pak 30sq. ins. approx.	£0.50
-------	-------------------------------------	-------

Tools	No. 2011 5 in. wire cutters	£1.55
-------	-----------------------------	-------

	No. 2012 5 in. long wire pliers	£1.45
--	---------------------------------	-------

SUPER DUPER COMPONENT BOX

Min. 310 in weight consisting of a fantastic assortment of Electronic Components—Pots, Resistors, Condensers, Switches, Relays, Board—Semiconductors, wire, hardware, etc., etc., etc.
*This is a large box and is sent separate to your order.
£2.50 including p. & p.

TRANSFORMERS SALE OFFER

S141	0.35 240V primary 0-55V at 2A secondary	£4.50* + £1.00 p. & p.
S142	0.349 240V primary 0-20V at 2A secondary	£3.50* + £0.86 p. & p.

COMPLETE AMPLIFIER KITS:

STA 15	15 watts per channel amplifier kit Consists: 2 x AL60; 1 x PA100; 1 x SPM80; 1 x 2034; transformer; 2 x coupling capacitors. £37.70 inc. VAT. 85p P&P.
STA25	25 watts per channel amplifier kit Consists: 2 x AL60; 1 x PA100; 1 x SPM120/45 - 1 x 2040; transformer; 1 x reservoir capacitor; 2 x coupling capacitors. £41.45 inc. VAT. £1.16 P&P.

STA35	35 watts per channel amplifier kit Consists: 2 x AL80; 1 x PA100; 1 x SPM120; 1 x 2041; transformer; 1 x reservoir capacitor; 2 x coupling capacitors. £48.45 inc. VAT. £1.16 P&P.
-------	--

STA50	50 watts per channel amplifier kit Consists: 2 x AL120; 1 x PA200; 1 x SPM120/65 - 1 x 2041; transformer; 1 x reservoir capacitor; 2 x coupling capacitors. £58.20 inc. VAT. £1.10 P&P.
-------	---

STA125	125 watts per channel amplifier kit Consists: 2 x AL250; 1 x PA200; 2 x SPM120/65 - 2 x 2041; transformers; 1 x reservoir capacitor; 2 x coupling capacitors. £72.85 inc. VAT. £1.25 P&P.
--------	---

TRANSISTORS

BRAND NEW—FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	*9p	BF200	*25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	*9p	BFX29	22p	TIP41C	36p	2N2219	15p
AC176K	24p	BC183L	*9p	BFX84	18p	TIP42A	36p	2N2219A	18p
AC187	16p	BC184	*9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	*9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	BC1212	*10p	8FY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	BC1212L	*10p			TIP3055	42p	2N2222A	16p
AD161/1		BC213	*10p	MPSA05	*22p	ZTX107	*6p	2N2369	10p
162 MP	80p	BC213L	*10p	MPSA06	*22p	ZTX108	*6p	2N2904	14p
AF139	30p	BC214	*10p	MPSA55	*22p	ZTX109	*7p	2N2904A	15p
AF239	30p	BC214L	*10p	MPSA56	*22p	ZTX300	*7p	2N2905	14p
BC107	6p	BC251	*10p	OC44	12p	ZTX301	*7p	2N2905A	15p
BC108	6p	BCY70	12p	OC45	12p	ZTX302	*7p	2N2906	12p
BC109	6p	BCY71	12p	OC71	9p	ZTX500	*8p	2N2906A	14p
BC118	*10p	BCY72	12p	OC72	12p	ZTX501	*10p	2N2907	12p
BC147	*8p	BD115	40p	OC75	10p	ZTX502	*12p	2N2907A	13p
BC148	*8p	BD131	*35p	OCB1	14p	2N696	10p	2N2926G	*8p
BC149	*8p	BD132	*37p			2N697	10p	2N2926Y	*7p
BC154	*16p	BF115	11p	TIP29A	35p	2N706	7p	2N3053	12p
BC157	*9p	BF167	19p	TIP29B	36p	2N706A	8p	2N3055	35p
BC158	*9p	BF173	20p	TIP29C	38p	2N708	8p	2N3702	*7p
BC159	*9p	BF180	25p	TIP30A	36p	2N1302	12p	2N3703	*7p
BC169	*10p	BF181	25p	TIP30B	37p	2N1303	15p	2N3704	*6p
BC170	6p	BF182	25p	TIP30C	38p	2N1304	15p	2N3903	*11p
BC171	*6p	BF183	25p	TIP31A	32p	2N1307	18p	2N3904	*11p
BC172	*6p	BF184	25p	TIP31B	33p	2N1308	22p	2N3905	*11p
BC173	7p	BF185	25p	TIP31C	34p	2N1309	22p	2N3906	*11p

DIODES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	BAX16/		BYZ16	30p	OA85	7p	1S44	3p
AA213	4p	OA202		BYZ17	28p	OA90	6p		
BA100	6p			BYZ18	28p	OA91	7p	IN5400	10p
BA115	5p	BY100	15p	BYZ19	28p	OA95	7p	IN5401	11p
BA144	5p	BY127	*10p					IN5402	12p
BA148	10p	BY210	32p	OA47	5p	IN34	5p	IN5404	13p
BA173	10p	BY211	32p	OA70	5p	IN60	6p	IN5406	16p
BAX13/		BY212	32p	OA79	7p	IN914	4p	IN5407	17p
QA200	5p	BY213	30p	OA81	7p	IN414B	4p	IN5408	19p

LINEAR I.C.'s

TBA800	*£0.75	µA711	£0.25	µA748	£0.28
TBA810	*£0.85	µA703	£0.20	72558	£0.45
TBA820	*£0.65	741P	£0.18	MC1310P	£1.25
LM380	*£0.80	72741	£0.20	76115	£1.25
LM381	*£1.25	µA741C	£0.20	NE555	£0.22
72709	*£0.20	72747	£0.55	SL414A	£1.80
µA709	£0.20	748P	£0.28		

ZN 414 RADIO CHIP 75p*

OPTOELECTRONICS

Displays	Price	LED CLIPS	Price
No. 1510	707 LED Display £0.70	No. 1508/125 .125	5 for £0.12
No. 1511	747 LED Display £1.50	No. 1508/2 .2	5 for £0.15
No. 1512	727 Dual LED Display £1.55	No. S139	Infra Red Detector Fairchild FP100 £0.50

LED's	Price
No. S120	.125 Bright Red £0.09
No. S121	.2 Bright Red £0.09
No. S102	.125 Green £0.12
No. S105	.2 Green £0.12
No. S103	.125 Yellow £0.12
No. S106	.2 Yellow £0.12
No. S82	Clear .2 illuminating Red £0.10

2nd QUALITY LED PAKS	Price
No. 1507	10 Assorted Colours & Size £0.75
No. S122	10 x .125 Red £0.60
No. S123	10 x .2 Red £0.60

P.O. RELAYS

S85 - 2 Off Post Office relays	40p
--------------------------------	-----

BATTERY HOLDERS

to take 6 x HP7's	
Order No. 202	10p each

EX. G.P.O. MICROSWITCHES

Order No. S51	4 for 50p
---------------	-----------

CABLE CLIPS

S65 - 50 2mm round single pin fixing	30p
--------------------------------------	-----

MAMMOTH I.C. PAK

Approx. 200 Pieces. Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked—you to identify.
Order No. 16223 £1.00

POWER SUPPLY STABILIZER BOARD

Unused ex-equipment stabilizer board. Input 30V. D.C. Output 20V. Complete with circuit diagram.
Order No. S81 £1.25

ORDERING

Minimum postage and packing for Sale Orders £0.50 PLUS any further postage as stated as per this Sale Advertisement.

Overseas Orders—ADD extra for Air-mail.

V.A.T.

Please ADD V.A.T. as follows:
12 1/2% to items marked *.
8% to unmarked items.
NO V.A.T. on Books.

I.C.
INSERTION
EXTRACTION
TOOL
O/D 2015
30p each

BI-PAK
DEPT. PW2, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK
STREET, WARE, HERTS.



EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR

Dick Ganderton C. Eng., MIERE

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Ted Parratt, BA

NEWS & PRODUCTION EDITOR

Alan Martin

TECHNICAL SUB-EDITOR

Peter Preston

TECHNICAL ARTIST

Rob Mackie

ASSISTANT ART EDITOR

Keith Woodruff

SECRETARIAL

Sylvia Barrett
Debbie Chapman

EDITORIAL OFFICES

Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER

Telephone: 01-261 6671 Roy Smith

REPRESENTATIVE

Telephone: 01-261 6636 Dennis Brough

CLASSIFIED ADVERTISEMENTS

Telephone: 01-261 5762 Colin R. Brown

MAKE UP & COPY DEPARTMENT

Telephone: 01-261 6570 Dave Kerindi

ADVERTISEMENT OFFICES

Kings Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

Our Role

OBVIOUSLY, with a title like *Practical Wireless*, our main aim in life must be to impart practical information—working designs, with instructions on building and using them. We don't see that as the whole story, though. We think we're here to educate you too, and this side of things takes many forms.

First there is the item which is straight theory, though often incorporating practical hints such as the *Introduction to Logic* series which concludes in this issue. This sort of article is intended to help you to understand text-books or manufacturer's data sheets, which often assume a fairly advanced level of knowledge and tend to be somewhat obscure in their treatment, or simply to keep you up to date with developments.

A second type of article is typified by the "*FM Receivers—Devices and Circuits*" series, and by its predecessor on a.m. receivers. These present outline circuits and explain how they work, but do not give constructional information. Their intention is to provide a basis for further experimentation by interested readers.

Of course, the constructional articles also have quite a big teaching role, too, either in "learning by doing" or "learning by reading". This last category is particularly important, as some part of a circuit will often trigger off an idea for another project in someone's mind, or will provide a solution to a design problem that has been bugging them. And it is the reason that we sometimes publish articles which will, we think, only have direct appeal to a limited number of readers, but where the principles involved are of wider interest. The *Videowriter* project published in *PW* in 1976 was rather in this category, though as it turned out, it was built in quite large numbers and used in applications which we never foresaw.

As already hinted at above, we want to help you to understand text-books etc., and part of that understanding is the ability to take in the various abbreviations and symbols used. This is part of the reason for our decision to change, over the next few issues, to a new but now widely-adopted convention for quoting component values on circuit diagrams. This involves using the unit multiplier instead of the decimal point, so that for example $4.7\text{k}\Omega$ becomes $4\text{k}7$, and $2.2\mu\text{F}$ becomes $2\mu 2$. The decimal point, being just a small dot on the paper, is so easily missed, and this new method is intended to overcome the problem. Note also that the unit, which is obvious anyway, has been dropped, thus saving space on congested circuit diagrams. More details will be given in our next issue, for the benefit of those unfamiliar with the scheme.

PERSONALITY



Alan Martin—News & Production Editor

Following technical college, Alan began his working life as a draughtsman. His first contact with *PW* was as a technical artist in the latter days of F. J. Camm—the founder. After a spell in the technical publications dept. of a large electronics firm, Alan started his own company, specialising in the preparation of technical literature. He joined the staff of *PW* in 1973.

Having lived in West London for most of his life the move to Poole proved quite an upheaval for himself, wife and two daughters. However, the move has been a great success and the family have settled very happily in Christchurch.

Alan's interests include darts, swimming, the countryside and lately gardening, mainly the labouring aspect!

New Battery

Chloride Silent Power Ltd. has received a £1.9 million grant from the Government to support the continued development of a revolutionary new battery in which Britain has a world lead.

This is the sodium sulphur battery, which has been under development by Chloride Silent Power, at its Runcorn research establishment, since the formation of the company—jointly owned by the Electricity Council and the Chloride Group—in 1974.

With at least three times the energy of the lead acid batteries now used in battery-operated vehicles, the new battery would give road vehicles a range of well over 100 miles compared with the 60-mile range of the present advanced Silent Karrier vehicles.

Among the many advantages of this new battery is that it uses two materials which are relatively cheap and plentiful throughout the world—sodium and sulphur. Demand for this battery will accordingly not affect supply or cost of these raw materials.

The £1.9 million grant is from the Department of Industry, under the Science and Technology Act 1965, from funds being made available under the Government's new Product and Process Development Scheme.

To date, £2.6 million has been spent by Chloride Silent Power Ltd. on sodium sulphur development, and the DOI grant is a contribution towards further development expenditure over the next four years, including the building of a pilot manufacturing plant. *Chloride Group Ltd., 52 Grosvenor Gardens, London SW1W 0AU. Tel: 01-730 0866.*

New Catalogues

Greenweld Electronics, the wholesale/retail suppliers of electronic components and equipment, have recently published their new 64 page catalogue. Also provided is an order form and reply paid envelope, five 10p discount vouchers and a bargain list. The catalogue costs 30p plus 15p P&P and is obtainable from: *Greenweld Electronics, 443 Millbrook Road, Southampton SO1 0HX. Tel: (0703) 772501.*

Crellon Electronics announce the publication of their largest stock list

ever. This 30 page edition covers over 8000 different items and is available free of charge from: *Crellon Electronics, 380 Bath Road, Slough, Berkshire. Tel: (06286) 4300.*

Electronic Brokers' latest catalogue is the largest the company has ever produced, with 86 pages devoted to second user electronic test equipment, computers and peripherals, plus new electronic products. Copies of the catalogue are available, free, to bona fide companies writing in on their letter heads. For private individuals, the charge is £1, and overseas enquiries £2—to cover P&P. From: *Electronic Brokers Ltd., 49/53 Pancras Road, London NW1 2QB. Tel: 01-837 7781.*

Heathkit have their latest 40 page catalogue ready, containing scores of electronic kits dealing with radios, digital clocks, test instruments, metal locators, car tune-up systems—and a new range of personal computers. Also available is their 16 page computer brochure. Both the catalogue and brochure are obtainable for 20p each, from: *Heath (Gloucester) Ltd., Dept. PW, Bristol Road, Gloucester GL2 6EE. Tel: (0452) 29451.*

Club news

Ormskirk Amateur Radio Club will be holding their A.G.M. on Wednesday 17 January 1979. The club meets on Wednesday evenings at members' homes; often there is a talk-in on 145.000MHz at about 2000 GMT. New members are very welcome. For further details contact: *Peter J. Kay G4GCB, Hon. Sec. OARC, 24 Laurel Avenue, Burscough, Ormskirk, Lancs. Tel: Burscough 89 2416.*

Verulam Amateur Radio Club will be holding the 1979 G3PAO Memorial Lecture in the Ex Civil Defence Hall, Chequers Street Car Park, St Albans, Herts on Thursday 25 January at 7.30 for 8.00 pm. This event is held in memory of their former Chairman and Founder Member, George Slaughter, who passed away in 1977. The lecture entitled "EME Transmissions" will be delivered by Peter Blair G3LTF, and will be illustrated with slides and tape recordings. Interested parties are welcome to attend. Further details from: *Hon. Sec. G4DUS QTHR. Tel: Rickmansworth 77616.*

Microprocessor Courses

Bleasdale Computer Systems in conjunction with Texas Instruments Ltd. is expanding its existing range of Microprocessor courses to cover the TI9900 family of microprocessors and TI990 microcomputers.

The courses are run by consultants who are actively involved in designing and building m.p.u. based systems. They are designed to give the participants in-depth practical experience in designing and building such systems. To achieve this, Bleasdale has designed and developed a range of Input/Output devices which can readily interface with microprocessors.

Currently available there is a one-week course for people with little or no previous microprocessor experience entitled "The Fundamentals of the 9900". Also a 2-week workshop entitled "Designing Systems with 9900", which is an advanced workshop for people with knowledge of microprocessors and their operation. For further information contact: *Bleasdale Computer Systems Ltd., 7 Church Path, Merton Park, London SW19. Tel: 01-540 8611.*

Sound and Video 79

Arrangements for Sound and Video 79, the North West's Audio, Hi-Fi and Video exhibition are now well under way and more exhibitors than last year have agreed to participate.

The exhibition will be held for the 3rd year at the Excelsior Hotel, Manchester Airport from Thursday, 18 January until Sunday, 21 January and entrance will be free. For further information: *R. J. Taylor, Advertising & Promotions Manager, Hardman Radio Ltd., Head Office & Accounts, 26 Exchange Street East, Liverpool L2 3PH. Tel: 051-236 2828.*

RAE Reprint

A reprint of the complete series—So You Want to Pass the RAE?—including details of the new examination format being introduced this year, is now available.





Order your copy by completing and returning the coupon on page 71.

12V FLUORESCENT LIGHT

Low-voltage fluorescent lamp fittings have many applications. For boats and caravans, where often the only power supply is an accumulator, they form a permanent light source. For emergency or other intermittent use, the scope is even wider: in the home, when power failures or cuts occur; in the car, for breakdowns and punctures; when camping.

A 13 watt, 21 inch tube will provide a very useful level of lighting for a consumption of about 1 ampere from a 12 volt battery, when driven via a suitable inverter circuit such as that shown in Fig. 1. Transistor Tr1 operates as a blocking oscillator, with feedback from the primary winding (1-2) to the secondary winding (3-4) of transformer T1 applied to its base. Resistor R1 sets the base current for Tr1, with C2 providing decoupling to ensure maximum feedback efficiency.

The pulses at Tr1 collector are also coupled to T1 tertiary winding (5-6-7-8) which is connected to the fluorescent tube LP1. At switch-on, all power will be directed to the tube heaters. When operating temperature is reached the high voltage present across the secondary of the transformer will cause rapid striking of the tube and the heaters will be extinguished. Operation in this manner prevents the tube "blackening" at the ends. When the tube has struck, this voltage drops to a much lower value due to the load then imposed on T1.

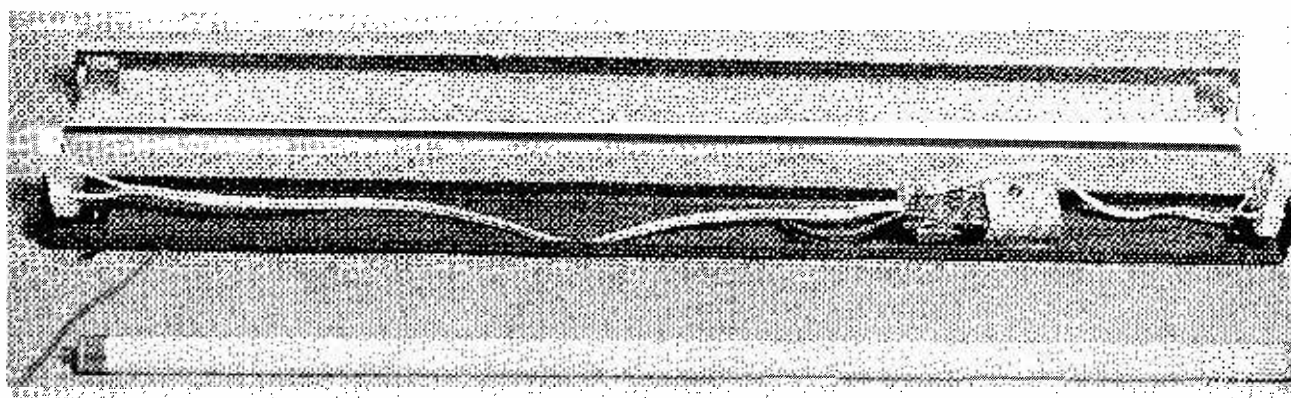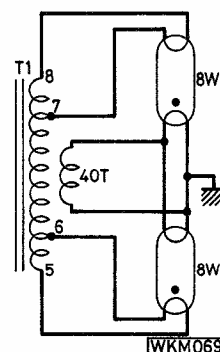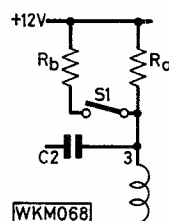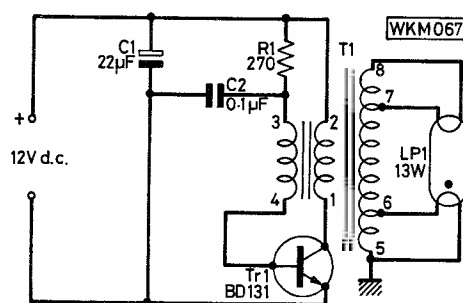

Interior view of the complete unit



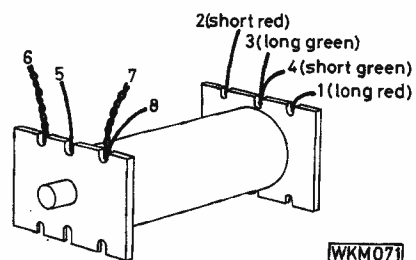
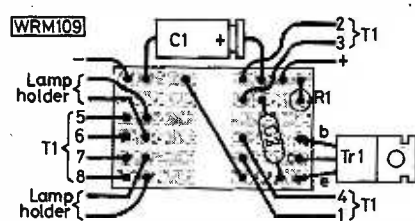



Fig. 4: Board layout and transformer terminations

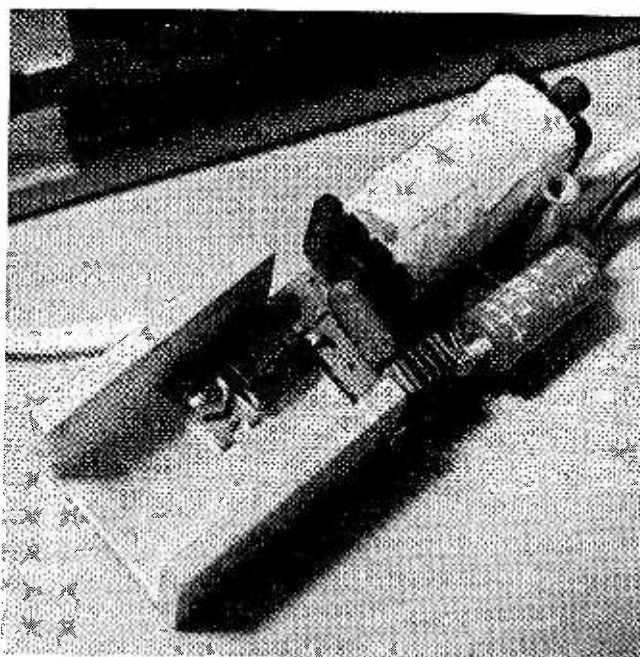

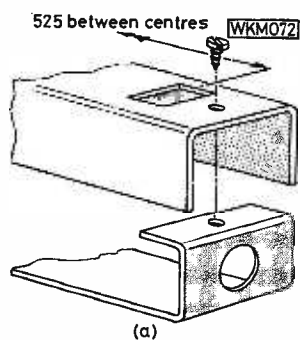
Assembly of board, transformer and heatsink



(a)

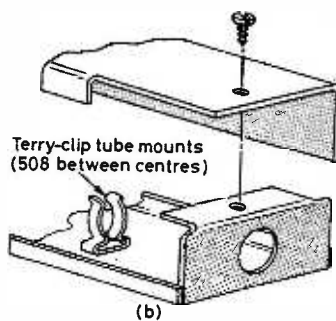

(b)

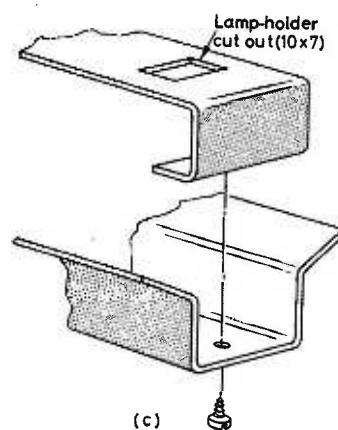

(c)

Fig. 5: Some suggested case forms: (a) standard open type (b) side-reflector type (c) large reflector type

Components

The type of transistor used in this circuit is not too critical and any h.f. *npn* power transistor can be used. Some types (for instance the 2N3055) will tend to self-destruct if run off-load. In this case, a cure is to connect an 82V Zener diode between the emitter and collector of Tr1 (cathode to collector). With transistor types other than that specified, it may be necessary to alter the values of R1 and C2 for optimum working.

The transformer is of a special design for use with this inverter circuit, and it is not practicable for the home constructor to wind a component to meet the required tolerances.

Dry Battery Operation


For operation from dry batteries, say two 6V hand-lamp batteries in series, the load of 1A is rather heavy, and in this application, the consumption can be reduced somewhat by increasing the value of R1. The light output will, of course, be reduced also, but a more serious drawback is a possible reluctance of the tube to strike. The easiest way to overcome this is to fit a "Start/Run" switch, which will provide increased bias current to Tr1 to get the circuit going. A suggested arrangement is shown in Fig. 2, where R_A is of the value required to give the desired running current, and R_B is switched in parallel with it for starting, by closing switch S1. The value of R_B should be chosen so that in parallel with R_A it provides a resistance of about 270 Ω .

From the point of view of the mechanical design of a portable lantern powered from dry batteries, it is probably more convenient to use a shorter fluorescent tube. This may be done without loss of light output by using two 8 watt tubes. These should be connected as shown in Fig. 3, with the centre pair of heaters powered from an additional winding of about 40 turns of 34 s.w.g. enamelled wire wound on the outside of T1.

Construction

The circuit is so simple that a printed circuit board is hardly justified. Instead, the components are mounted on a small piece of Verostrip or Veroboard. A suitable layout is shown in Fig. 4. The transformer and board may be held together by means of a double-sided sticky pad. Take care not to break the transformer leads, as these are fragile, particularly on the tertiary winding. The transistor heat-sink can be secured and insulated from the case with another double-sided sticky pad.

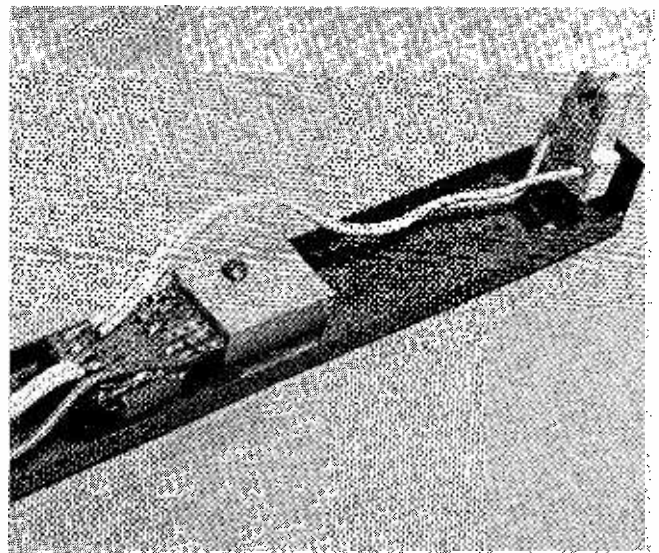The exact form of the case metalwork will depend to a large extent on what metalworking facilities are available to the constructor. The only critical dimension is the spacing of the two lampholders. Some suggested designs are shown in Fig. 5.



★ components

Resistors

R1 270 Ω 1W (or 2 x 560 Ω 1/2W in parallel)

Capacitors

C1 22 μ F 50V tubular electrolytic

C2 0.1 μ F 250V polyester

Transistors

Tr1 BD140

Miscellaneous


T1 12V 13W inverter transformer (G. F. Milward, 369 Alum Rock Road, Birmingham B8 3DR)

LP1 13W 2ft fluorescent tube with 2 bi-pin holders

Verostrip or Veroboard, 0.1in matrix, 16 x 26mm

Materials for case and heat-sink

To ensure reliable starting, one end of the tube must be connected to one side of the 12V supply and/or the lamp case. This is achieved in the layout of Fig. 4 by the circuit board mounting screw. If the lamp is to be used in a vehicle on which the positive supply line is connected to vehicle chassis, then care must be taken that no connection exists between the 12V negative supply line and the lamp case. In the two-tube version, this "earthing" connection should be made to one side of the centre pair of heaters, as shown in Fig. 3. ●

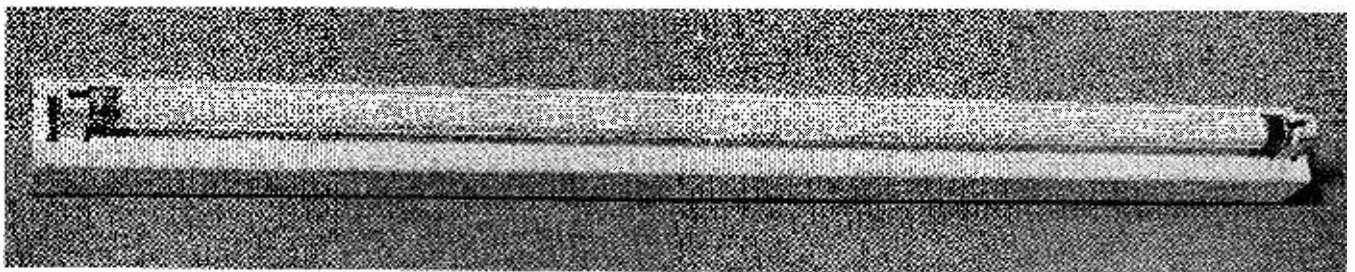


EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

★ As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. Size approx 20" x 11" x 9 1/2".

£28.00 Per stereo pair + £5.00 p&p.

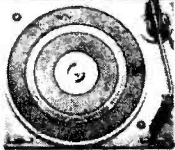

BSR Manual single play record deck with auto-return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 + p.m. spindle adaptor ideally suited from home or disco use.

OUR PRICE £10.95 £2.55

TURNTABLE BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck

£26.95

GARRARD SP25 MKIV Deck

with Shure head £25.95

Plinth and cover for BSR decks £6.00

BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO CASSETTE RECORDER



UNREPEATABLE

MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation.

160 16 VOLT MAINS TRANSFORMER, 2 1/2 amp.

BSR Record auto deck on plinth with stereo cartridge ready wired.

LED 5 function men's digital watch

stainless steel finish

LCD 5 function men's digital watch

stainless steel finish

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish.

POCKET CALCULATOR. With LED display, memory and percentage key.

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

£11.95

125 Watt Power Amp Module

Mains power supply for above unit.

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/2" x 14 1/2" x 7 1/2" approx.

MULLARD Built power supply

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape heads.

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3/4" approx. tweeter inc. crossovers

VIDEOMASTER Super Score TV Game with pistol mains operation

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock. LW, MW, SW, VHF mains/battery operation.

7" TAPE TRANSPORT Mechanism—a selection of models from

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

£7.50 p+p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vo. On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary selection switch.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 1dB Radio. FM sensitivity for 3dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre Size approx length 16" x height 2 1/4" x depth 4 1/4"

240 Volts AC Complete with Circuit diagram.

£19.95 p&p £2.50

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE

PRICE £25 AT OVER PER PACK

SEE OUR PRICES

1 PACK 1.2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

OUR PRICE p+p £1.00 £4.95

2 PACK 2.2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.

illus. OUR PRICE p+p £1.00 £7.45

ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors.

£1.00 p+p £1.95

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE.

p+p 50p 95p



GARRARD BARGAIN

LIST PRICE £95.00

OUR PRICE £39.95

86 SB MKII. Belt drive, 2 speed turntable module with plinth and cover.



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90 + £2.50 p&p

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

£23.00 + £2.50 (NOTE Cabinet not without cabinet. p&p available separately) £29.00 + £2.50 complete with cabinet.

SPECIAL OFFER Complete with 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3 1/4" approx. tweeters and crossovers.

£49.00 + p&p £4.00

BUILT AND READY TO PLAY

30x30 Viscount. Available fully built and tested.

39.00 + p&p £2.50

50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx.

13 1/2" x 5 1/2" x 6 1/2"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P 8" speakers. Package price £45.00 + £4.00 P&P

70 & 100 WATT MONO DISCO AMP

Size approx.

14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls: master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level.

Output 100 watts RMS 200 watts peak. 100 watt £65

140 watt peak p & p £4.00

Output 100 watts RMS 200 watts peak. 100 watt £65

STEREO CASSETTE TAPE DECK ASSEMBLY

Consisting of ready built tape transport system/mechanism, mated to the electronics.

Unit is ready built for installing into cabinet of own choice. Features include

pause control, solenoid assisted auto-stop, 3 digit tape counter, belt driven balanced fly wheel by DC motor

with electronic speed control, twin VU meters. Specification Power

Output, more than 0.5v, mic. -65dB 10KHz, DIN -47dB 100KHz

Track-2 channel stereo record play-back. Tape speed 4.8cm/sec. Freq.

response 50-12000 Hz signal to noise ratio 42dB Recording system AC bias

Erasing system AC erase Bias freq. 57KHz Compatible for both normal and chrome dioxide tapes. Size of mechanism only 4 1/4" x 6 1/4" x 11 1/4" approx.,

included a moulded top-plate as illustrated

13 1/4" x 9 1/4" approx with circuit diagram.

£25.00 P&P £2.50

Opt. extras: Mains transformer to suite £2.50 + £1 p & p.



323 EDGWARE ROAD, LONDON W2
210 HIGH STREET, ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 1.12.78 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK



Almost all audio and hi-fi amplifiers employ a push-pull output stage biased either to class A or quasi-class B (which is rather like class AB), so that the analogue input signal swings over a fairly linear part of the transfer characteristic. To combat residual non-linearity and hence to reduce the distortion a liberal amount of negative feedback is commonly used, and with quasi-class B designs, which are currently the most common, the output transistors are biased for a small quiescent current to avoid transfer characteristic discontinuity at the centre, low-level point where the characteristics of the two output transistors join. Power amplifiers of this kind are well known and it is not here intended to dwell on their design.

A less well-known technique converts the analogue input signal to a digital format which is used merely to switch the push-pull output transistors on and off. The digital format is a pulse train derived from a stable squarewave generator, and the width of the pulses is caused to vary in direct sympathy with the audio information carried by the analogue signal, which is the usual output from a gramophone pickup, tape deck, radio tuner, etc.

The analogue signal is reconstituted for driving the loudspeaker by passing the encoded pulse chain through a low-pass filter which, while greatly attenuating the relatively high-frequency pulses, yields an output which is proportional to the average value of the pulse chain at any instant. Because the squarewave pulse chain is effectively modulated by the analogue signal, the system is generally referred to as pulse width modulation, or p.w.m. for short.

It is not new from the technical point of view, for amplifiers adopting the principle were referred to way back in 1947¹, well before the days of fast-switching transistors, and more recently in 1960 in terms of a practical design². Since then one or two commercial amplifiers have appeared for a short time, later to be taken off the market as the result of various shortcomings, not the least of which being a high level of radiation of the harmonics of the squarewave switching signals. Audio amplifiers are designated class A, class B and class AB, and since class C refers to r.f. amplification, the next class in line was class D, so in the early days the first p.w.m. amplifiers were designated class D.

It is of interest to note that the Dynaharmony range of amplifiers by Japanese Hitachi have been designated class E in the US. This is because they employ an auxiliary output amplifier which automatically switches to a higher voltage supply on high amplitude signals as a means of combating bad distortion on the peaks, which other am-

plifiers of similar main-amplifier power may well clip; also, of course, because the letter "E" was the next in line! This range of amplifiers is also referred to as class "G" (mainly in the UK), but there is no connection with class D.

Principle of PWM

With the advent of fast-switching power transistors and more sophisticated circuit techniques there has been a revival of interest in p.w.m. amplifiers, and one or two excellent designs, including the recent Sony TA-N88³, are on the market. The time is now ripe to explore the basic principle of class D operation, to see whether there are advantages (or, indeed, disadvantages) with respect to ordinary analogue power amplification, and to investigate some of the performance parameters of a commercial design.

An impression of the make-up of a p.w.m. amplifier is given by the elementary block diagram in Fig. 1. Here the switching devices are *p*- and *n*-channel V-type junction f.e.t.s (a complementary pair) which are switched on and off by the driver stage feeding the gates.

There are various ways in which the pulse chain can be modulated by the analogue signal, such as by a Miller integrator (an arrangement similar to this being found in the Sony TA-N88) or by a "comparator" stage, shown in the diagram by the block labelled Modulator.

The pulse chain starts life as a high-frequency sinewave, and is then changed to a square or triangle wave, depending on the nature of the modulation, after which it is buffered before being applied to the modulating system. A transformer feedback type of oscillator may be used, though, from the point of view of subsequent filtering, there can be merit in using a crystal-controlled oscillator. One design⁴, in fact, employs a television subcarrier reference crystal which runs at 4.433618MHz, which is followed by a divide-by-ten TTL stage to yield a frequency of 443kHz. The Sony TA-N88 amplifier employs a transformer-coupled oscillator running at 500kHz.

Clearly, the switching rate must be much higher than the highest audio frequency. The higher the frequency the better, since this makes it easier to achieve high attenuation of residual ripple signal at the loudspeaker terminals. However, there are constraints related to the switching speed of the output devices and the losses involved if the switching rate is too high. With contemporary power transistors a fundamental switching rate of about 500kHz, corresponding to 2μs, seems appropriate. This also satisfies the requirement for an upper-frequency response extending to around 50kHz before the analogue output is unduly affected by the low-pass filter action. Moreover, if negative feedback is taken after the low-pass filter, as shown in the diagram, the phase shift of the filter at the frequency of unity gain must not be so large as to incite instability. The use of a high switching rate also helps in this respect. When the pulse chain is derived from a very stable oscillator, such as a crystal-controlled oscillator, very high-*Q* filtering can be employed for ripple rejection which, of course, is not possible if the oscillator is likely to drift slightly in frequency.

With the Miller integrator type of modulator, the tops of the pulses widen and the spaces between them shorten as the amplitude of the analogue signal increases and, conversely, as the amplitude of the signal falls so the tops of the pulses shorten and the spaces between them widen. Analogue signal is continuously changing in amplitude as the information carried by the signal changes, so this is encoded in terms of the pulse chain continuously changing in effective mark/space ratio. Information on the frequency components (rise-time, etc.) of the analogue signal is encoded in terms of rate-of-change of the mark/space ratio

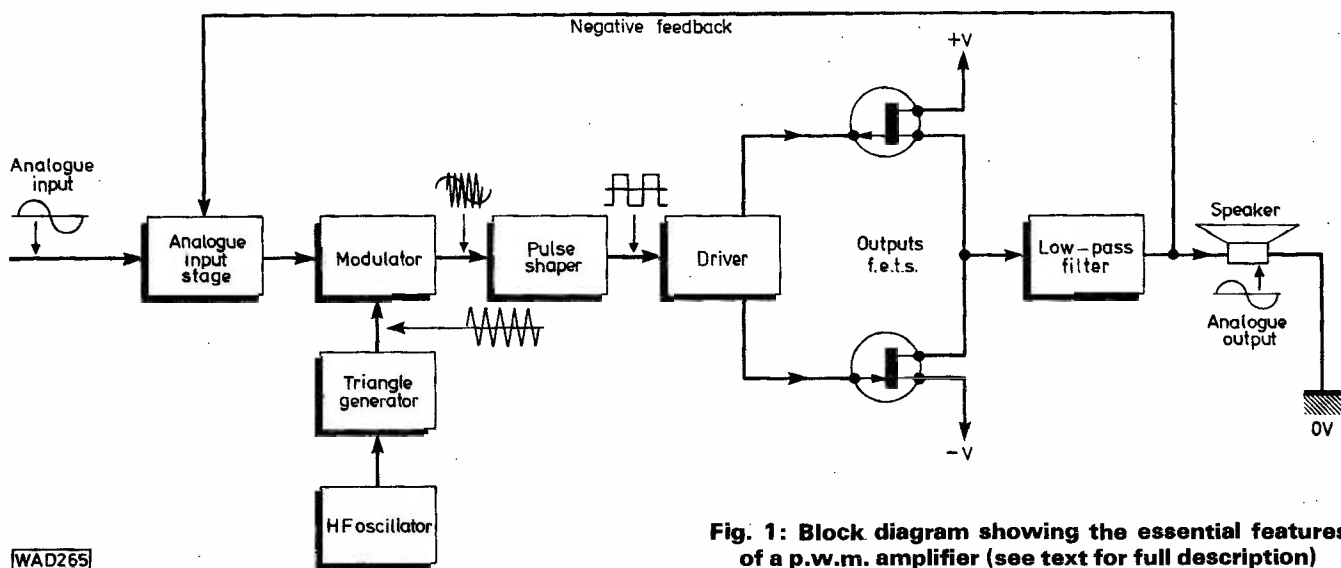


Fig. 1: Block diagram showing the essential features of a p.w.m. amplifier (see text for full description)

of the pulse chain. When there is no analogue input the pulse chain assumes a steady-state 50:50 mark/space ratio, which means that the tops of the pulses and the spaces between them are equal.

The Sony p.w.m. amplifier uses a dual-f.e.t. in differential configuration which, with current regulators and a bipolar stage, forms an integrator to which are applied the analogue and squarewave signals. It works by subtracting the inputs from the output, and has a bandwidth from d.c. to several megahertz. This is followed by a comparator composed of an i.c. containing three differential amplifiers, and its job is to produce the modulated pulse chain for switching the output devices via a driver amplifier. The configuration ensures that the rise-time of the pulse formation is less than 20ns.

Another method of modulation⁴, which is that shown in Fig. 1, works in the manner shown in Fig. 2. As already noted, the analogue and pulse information, the latter first converted to a triangular wave format, are fed to the two input ports of the comparator or modulator. A simple sinewave analogue signal is shown in the diagram for the sake of rendering the description more apparent. In a practical situation, of course, the analogue signal would be continuously changing in amplitude and rate in accordance with the audio information. To ensure a faithful conversion to digital, and hence to minimise the amount of false information on the reconstituted analogue signal, a primary requirement is for the triangle wave to be very linear.

The diagram reveals that the output pulse chain encoding is a function of the amplitude of the analogue input

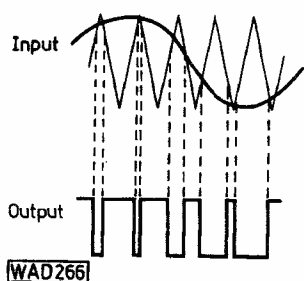


Fig. 2: Showing one method of encoding a pulse chain with information carried by an analogue signal

at any instant resulting from the corresponding changes in "slicing" level with respect to the constant-rate triangle wave input. The implication here is that the triangle wave rate is about four and a half times greater than the frequency of the analogue signal. Thus, if the triangle wave repetition rate were, say, 500kHz, then the analogue signal being encoded would have a frequency of around 111kHz. At lower analogue frequencies, of course, there would be many more triangle wave cycles per analogue cycle.

To avoid the former happening, the frequency of the analogue signal fed to the modulator for encoding is deliberately restricted by low-pass filtering. The audio spectrum is generally regarded as extending from 20Hz to 20kHz, and an amplifier with a small-signal response, at least, of less than this would certainly not be regarded as "hi-fi" by the devotees. However, having said that, it is of interest to note that even a high-quality stereo f.m. transmission carries little or no information below about 30Hz, while at the upper end of the spectrum the output is swiftly attenuated above about 15kHz or, perhaps, a trifle higher owing to the demands of pilot tone filtering.

Well-recorded gramophone records played with a top-flight pickup system fail to extend noticeably above the f.m. audio spectrum. Output below 50Hz is tamed by the specified low-frequency 3180μs time-constant of the RIAA equalisation, while the more recent IEC requirement calls for further filtering at 20Hz, corresponding to a time-constant of 7957μs. It is thus unlikely whether the equivalent rise-time of most of the best programme material fed into a hi-fi amplifier is quicker than about 15μs.

Nevertheless, to avoid this rise-time being further slowed down by rise-time limitations of the amplifier to which the programme material is fed, it is generally considered that the amplifier's small-signal frequency response at the -3dB points should extend to about 40kHz, corresponding to a rise-time of just under 9μs. Some amplifiers boast a small-signal rise-time of less than 2μs, corresponding to an upper-frequency response around 200kHz. It is my judgement that this is totally unnecessary and can detract from, rather than enhance, the reproduction.

It is not unreasonable, therefore, to filter the analogue signal before it is applied to the modulator so that the small-signal response is down to -3dB at 40kHz or, perhaps, a little higher (say, 50kHz). The p.w.m. amplifier design in Ref. 4 specifies a Bessel input filter for control-

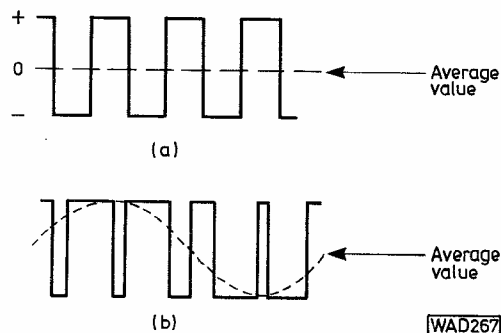


Fig. 3: The analogue of the pulse chain is represented by the average value of the pulse chain, which is shown at (a) with respect to 50:50 mark/space ratio (zero analogue) and at (b) when the pulse chain is encoded with sine wave signal, as produced by the process shown in Fig. 2

ling the input signal rise-time. As with any hi-fi amplifier, the design should aim for the widest open-loop bandwidth of the **power amplifier** section to prevent the effects of so-called transient intermodulation distortion (t.i.d.) which, to some extent, establishes the small-signal upper-frequency response of the analogue signal at the modulator input. To avoid phase distortion at infra-bass frequencies it is now common practice to employ direct coupling throughout the power amplifier system; this presents no problem.

Digital-to-Analogue Conversion

Referring to Fig. 1, the encoded pulse chain is fed to the output f.e.t.s merely to switch them on and off. In Fig. 3 a pulse chain of 50:50 mark/space ratio is shown at (a). Since this chain is perfectly symmetrical its average value is equal to half the peak-to-peak value which is zero. This is the condition when there is no analogue signal input.

Since this chain is fed to the loudspeaker through the low-pass output filter the current flowing through the loudspeaker is zero (the symmetrical switching of the complementary output f.e.t.s also ensures that this is the case). The filter, of course, greatly attenuates the switching component, and when the pulse chain is encoded the average value corresponds to the analogue input signal, as shown at (b) in Fig. 3, which is the pulse chain resulting from the sine wave modulation in Fig. 2. The result is that current corresponding to the analogue signal flows through the loudspeaker, along with a little switching residual, as shown in Fig. 4.

With a suitably high switching rate and well-designed filtering the switching residual is generally much lower than that implied by Fig. 4. The design aim is for a rejection ratio of 100dB which, referred to 100W output into 8 ohms, corresponds to a residual as small as 283 μ V; but not all commercial designs appear yet to be meeting this aim. The design in Ref. 4, aided by the crystal-controlled switching rate source, is one which has, at least, achieved the aim.

Although a higher level of ripple appears not to affect the reproduction (since it is well outside the response capability of the loudspeaker and up in the r.f. realm), it can cause medium-frequency radio interference owing to radiation from the amplifier direct and from the loudspeaker cables. This was one of the major problems with early p.w.m. amplifier designs. Some produced more than 1V of ripple signal, which is well above the requirements of international standards.

Advantages and Disadvantages of PWM

What are the advantages of p.w.m.? Probably the main advantage is high efficiency, which means that powerful amplifiers can be made in small size without undue overheating. With "linear" amplification the power transistors are not working very efficiently because a relatively high average power is dissipated by them. The maximum efficiency of push-pull class A working is only 50%. The efficiency is improved by class B, it working out to 78.5% excluding the driving and pre-amplifiers, of course⁵.

Because the output transistors of p.w.m. remain either bottomed or cut-off for most of the time the efficiency is very high. Maximum theoretical efficiency is 100% (output power the same as the input power). In a practical design an efficiency of up to 90% is realisable. The loss stems mainly from the saturation voltage and the peak current in the "on" state. If it is assumed that these are respectively 1V and 6A, then the power dissipated by the transistors would be a mere 6W, while the peak power into an 8 Ω load would be 288W. Other small losses result from transient switching dissipation.

The Sony TA-N88 p.w.m. power amplifier will deliver 2 \times 160W average power into 8 Ω loads yet its size is only about half that of a 2 \times 100W quasi-class B amplifier. In comparison with a class A amplifier of similar power yield, the Sony has a power-to-weight ratio advantage of four or five times!

A quasi-class B amplifier is inherently a very non-linear animal in open-loop mode, which means that a high degree of negative feedback needs to be applied to bring its performance up to an acceptable hi-fi standard. Sadly, negative feedback is not a cure for all amplifier troubles and, contrary to some opinion, there are times when an increase in feedback can actually impair the performance.

On the other hand, a class A amplifier behaves much more linearly in open-loop mode, which means that it requires less feedback for a given fidelity. This is undoubtedly one of the reasons why class A power amplification has been favoured by devotees over the years. When a lot of power is required for driving very inefficient loudspeakers in large rooms, for example, then the major disadvantage of this type of amplifier is the abysmal power-to-weight ratio—very large and massive heat sinks being required by the output transistors along with large transformers to yield the high standing power.

A well-designed p.w.m. amplifier is endowed with virtually the same open-loop linearity as a class A amplifier yet it possesses a far more acceptable power-to-weight ratio. Hence, a p.w.m. amplifier calls for a relatively small amount of negative feedback merely to improve upon an already good intrinsic linearity rather than to correct for the shortcomings of some quasi-class B designs, which is the hallmark of favourable auditioning.

The greatest disadvantage is really related to the switching signal and the probability of this being radiated

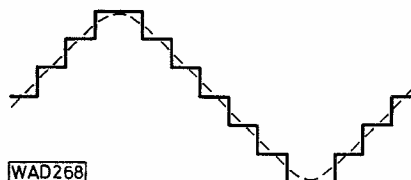


Fig. 4: Reconstituted analogue signal at the output carrying residual switching signal. In practice, the level of the residual is well below that implied by the waveform

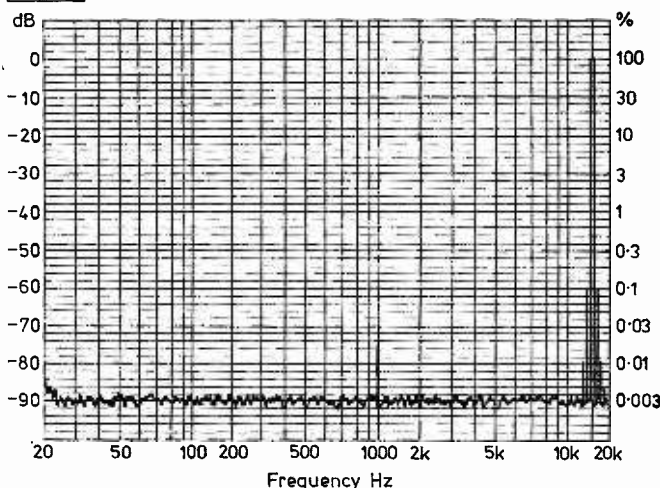


Fig. 5: CCIF intermodulation distortion produced by the Sony TA-N88 p.w.m. amplifier when delivering 38V peak composite signal across a load corresponding to a "difficult" loudspeaker of about 5 ohms modulus of impedance and 60 degrees phase-angle

if it is not suppressed properly. Most of the earlier problems have been resolved by the advent of new solid-state devices, including fast-switching i.c.s and power transistors.

Non-linearity arises when the pulse chain varies in amplitude or width from causes which are not directly related to the analogue modulation process. When this happens harmonic and intermodulation components and products appear across the output load, but by the use of suitably fast switching devices allied with competent design these aberrations are minimised. Normal feedback is possible from the analogue output to the analogue input, as shown in Fig. 1.

In some designs the feedback voltage is obtained prior to the output low-pass filter, as in the Sony, and with others the voltage is picked up after the filter, as in Fig. 1. The latter would appear to have merit, provided the filter does not cause phase shift likely to evoke instability, because it keeps the source impedance low and hence the damping factor high.

Limiting and Protection

Input overload can result in the loss of switching pulses at the extremes of modulation, accompanied by a severe rise in distortion and an increase in r.f. emission. To avoid this, most p.w.m. amplifiers are equipped with a "soft limiting" circuit in series with the analogue input signal. In the Sony, for example, this consists of a high-speed f.e.t. attenuator whose gate is connected to current sensors in the output stage. When the current threshold is exceeded the attenuator is activated so that the level of analogue signal reaching the modulator is reduced.

Thermal and short-circuit protection circuit are also included. These operate a relay whose contacts are in series with the loudspeaker, so that in the event of an output short-circuit under heavy drive or an abnormal rise in temperature the contacts open and disconnect the load. The relay is also connected to an energising delay circuit so that the contacts close after the power supply has fully

stabilised. This avoids the switch-on "thump" from the loudspeaker when the power switch is turned on.

Auditioning

How do p.w.m. amplifiers compare in reproduction with more conventional class A and quasi-class B designs? Of the p.w.m. amplifiers that we have auditioned we have found the sound quality to be very close to that expected from a well-designed class A transistor or valve amplifier.

Lab Performance

As already noted, the Sony TA-N88 produced a full 160+160W into 8Ω loads to the threshold of heavy distortion rise (just prior to the peak clipping point) at any frequency, at least, within 20Hz to 20kHz. Second harmonic distortion at 1kHz and with both channels delivering 160W was -70dB, corresponding to about 0.03%. Odd-order and higher-order distortion was negligible, being equal to or below the residual of the switching signal at the output.

At 10kHz and the same two-channel power the distortion was, as would be expected, higher, corresponding to about 0.25% second harmonic, which predominated. The third harmonic was about 64dB down, corresponding to about 0.063%.

At lesser output power all distortion components shrank towards the level of the switching signal residual, which measured about 100mV r.m.s. across the output of one channel (less across the other). Although rather on the high side, the reproduction was not affected, but radio interference could just be detected on medium frequencies when a receiver with a ferrite rod aerial was placed a short distance away from the amplifier (a really tough test!).

The spectrogram in Fig. 5 shows the measured CCIF intermodulation distortion with 38V peak of composite two-tone signal across an impedance load corresponding to a "difficult" loudspeaker. There was a rise in amplitude of the IM products with increasing output voltage.

The amplifier required just under 1.5V r.m.s. for full drive; stereo separation was as high as 88dB, and residual mains ripple below 90dB. The damping factor was not too good, being 28 at 40Hz and 2.3 at 20kHz. This could possibly be improved by taking the feedback from the output side of the low-pass filter. Small-signal bandwidth was from d.c. to almost 90kHz (-3dB), after which the roll-off rate was 12dB/octave, corresponding to about 4μs, which we regarded as unnecessarily fast.

The amplifier is equipped with two pairs of complementary junction V-f.e.t.s in parallel. These devices or MOSFET power devices are ideally suitable for p.w.m. amplifiers, as also are fast-switching power bipolar transistors. However, with the inevitable price reduction of the V-f.e.t. species of power transistors, such as the Hitachi V-MOSFET, we are almost certain to experience a revival of the p.w.m. amplifier, especially when the pundits fully realise just how fine such an amplifier can audition. ●

References

1. Fitch, group of papers *Journ.IEE*, Vol. 94, Part IIIA, No. 13, 1974.
2. Ettinger and Cooper, *Proc.IEEE*, Paper No. 3092E, April 1960, Vol. 106B, 18, p. 1285.
3. Gordon J. King, *Hi-Fi News & RR*, Sept. 1978, pp. 173-177.
4. Brian E. Attwood, PWM Systems, Horsham, England, Very High Fidelity Quartz Controlled PWM (class D) Stereo Amplifiers for Consumer and Professional Use, paper presented at the 59th Convention of the *Audio Engineering Society*, February 28 to March 3 1978 at Hamburg.
5. Gordon J. King, *The Audio Handbook*, pp. 84-87, Newnes-Butterworths, 2nd printing 1978.

Follow-up to

P_W Wide range CAPACITANCE METER

Ian HICKMAN

Requests from readers for an even wider capacitance measurement range set the author thinking and here is the result—an add-on unit which enables the Wide Range Capacitance Meter (PW Sept '76 issue) to measure capacitors up to 30 millifarads, i.e. 30 000 μ F. Modifications to build the extra ranges into the original capacitance meter were hardly practical and this add-on unit involves only minimal changes, namely the addition of two 2mm sockets to the front panel.

To avoid possible confusion, component references for the extender follow on from those of the original capacitance meter.

Circuit Description

Fig. 2 shows the circuit diagram of the extender. It works on the same principle as described in the original article. The capacitance under test shunts a voltage waveform generator of known source impedance. The lowest impedance available in the original circuit was about 220 Ω , limiting the measurement range to 10 μ F or 30 μ F with the function switch at x3. The extender unit takes the test waveform (at 220 Ω source impedance) via an extra socket on the front panel of the meter and feeds it to a 220 Ω attenuator chain; the extra loading of this chain attenuates the test waveform by 6dB. The chain is tapped at points where, looking in, one 'sees' a 22 Ω source resistance (x10 socket) and a 2.2 Ω source resistance (x100 socket). The latter point represents a further 40dB of attenuation of the test waveform and IC1 provides 46dB of gain, so producing the same voltage at its output as would have appeared at the red C_x terminal originally. The op. amp. output has a d.c. blocking capacitor whose reactance at the frequency of the test waveform is very low, and by setting the range switch to 10–100pF, the f.e.t. Tr5 is biased via R22 but 'sees' a.c. signals only from the op. amp. Clearly, a 100 μ F capacitor connected to the x10 terminal, or 1000 μ F at the x100 terminal, will produce the same attenuation (in dB) of the test waveform as 10 μ F connected to the original meter (on the 1–10 μ F range).

Push button S3 reduces the source resistance at the x100 socket from 2.2 Ω to 0.22 Ω and raises the gain from the op. amp. to 66dB (x2000) to compensate. This provides a x1000 range, at reduced accuracy. This is because of the reduced bandwidth of the op. amp. when supplying the extra 20dB of gain. In particular, the x1000 range should only be used in conjunction with the x3 range of the function switch, as on x3 the test waveform frequency is reduced by a factor of 3. Even so, R46 has been set at 430k Ω instead of the theoretical 390k Ω . The latter value should be used if you use a high-speed op. amp. such as the LM318 instead of a 741. If using a 741,

it should be a full spec. device from a reputable source—not a 'reject' or 'fall out'!

Note that no polarising voltage is applied to the capacitor under test, thus avoiding the inconvenience of a 6 seconds time constant for charging when measuring 30 000 μ F! The amplitude of the test wave form applied to the capacitor under test is so small that the absence of a polarising voltage is of no consequence.

Construction

The author used a diecast box and though only just deep enough internally, this fits neatly in front of the capacitance meter leaving the controls unobstructed. Any similar sized box would do, but metal is preferable to plastic. The box is connected to the black C_x terminal, i.e. the case of the capacitance meter. Two additional connectors are required on the capacitance meter, one to make the 12V supply available to the extender and one to

This unit is an add-on extender for the Wide Range Capacitance Meter described in Practical Wireless September 1976. It is presented for the benefit of those readers who have already built the main instrument. We regret that the issue in which the meter originally appeared is no longer available.

supply the test waveform. These were added one either side of the existing C_x terminals.

The circuitry of the extender was made up on a piece of 0.1 inch pitch Veroboard as shown in the component layout drawing Fig. 1 and mounted on the three 4mm sockets and S3 along one edge of the board, the other edge being supported by a long 6BA bolt fastened to the back of the front panel with Araldite.

Resistors R41 and R42 may be wound using Eureka wire: 126mm of 36 s.w.g. gives 1.98 Ω and 124mm of 24 s.w.g. gives 0.22 Ω . This allows 2.5mm each end for soldering. Alternatives are to use 3.9 Ω , 4.7 Ω and 27 Ω in parallel for R41 and a 0.22 Ω $\frac{1}{2}$ W metal film resistor for R42.

On completion of the extender, check that it will not short the stabilised supply of the Capacitance Meter, connect up and switch the Meter to x1 and 10–100 μ F. Check that the voltage at the junction of R45 and C13 is about 6V. The meter should read off-scale to the right. Connect a 20 μ F capacitor between the x10 terminal and common and check that the meter reads in the region of 20 μ F (i.e., 2 on the upper scale). Note that the tolerance on electrolytics is typically $-20 + 50\%$, so precision cannot be expected!

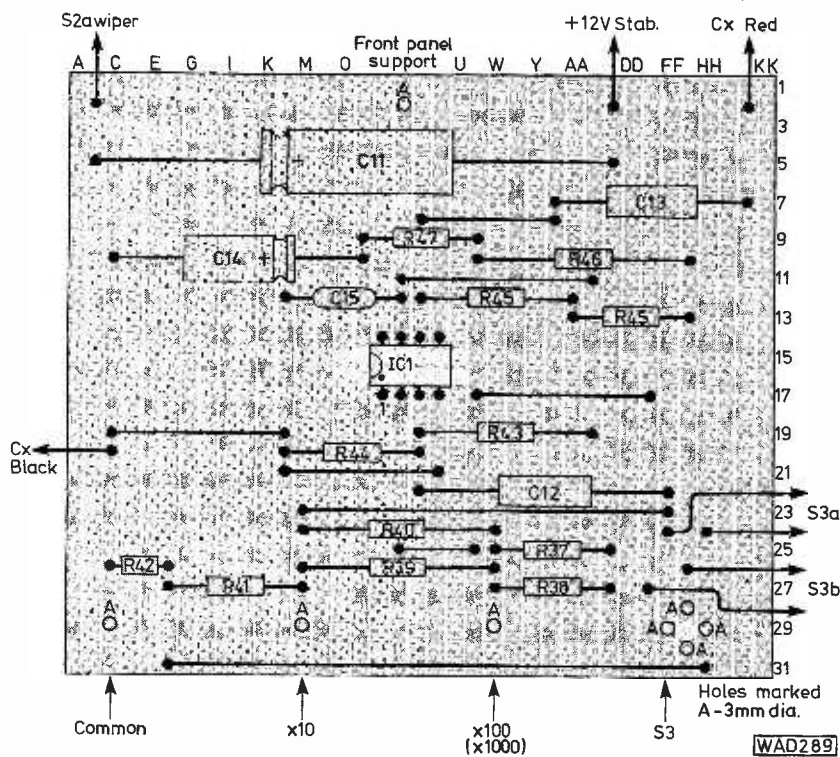


Fig. 1: The component layout of the add-on millifarad extender unit. 0.1 inch pitch Veroboard is used. The 741 op. amp. i.c. is shown as an 8 pin d.i.l. package but the alternative 14 pin d.i.l. package can also be used on the same board layout

Fig. 2: The circuit diagram of the extender unit

★ components

Resistors

2% $\frac{1}{2}W$ metal oxide or thick film

22 Ω	1	R39
220 Ω	2	R37, 47
22k Ω	2	R45a, b
430k Ω	1	R46

5% $\frac{1}{2}W$

470 Ω	1	R40
1.8k Ω	1	R38
390k Ω	2	R43, 44

see text for R41 and R42

Capacitors

Disc ceramic

0.1 μ F	1	C15
-------------	---	-----

Polyester

0.04 μ F	1	C13
--------------	---	-----

0.47 μ F	1	C12
--------------	---	-----

Electrolytic

47 μ F 10V	1	C14
----------------	---	-----

220 μ F 10V	1	C11
-----------------	---	-----


Semiconductors

Integrated Circuits

741	1	IC1
-----	---	-----

Miscellaneous

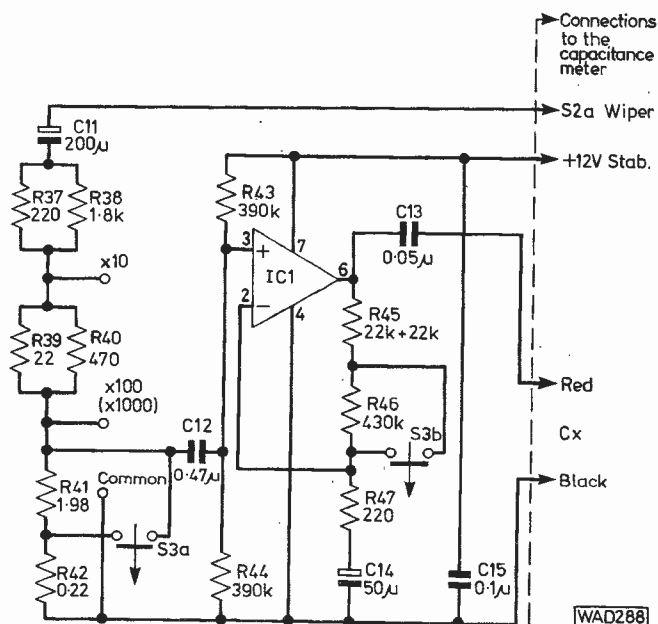- 2 pole min. push button switch (RS 337-942) (1)
- Diecast box 114 x 89 x 55mm approx. (1)
- Veroboard 0.1 inch pitch 36 tracks x 32 holes
- 2mm sockets (5)



Use

Following the above checks, the unit is ready for use, as there is no calibration to carry out. Capacitors in the range 10–100 μ F can be measured by connecting between 'common' and 'x10', whilst capacitors between 100 μ F and 1000 μ F (3000 μ F with the function switch at x3) are connected between 'common' and 'x100'. These terminals are also used for measuring capacitors between 3000 μ F and 30 000 μ F, with press button S3 depressed and the function switch at x3. As the reactance of 30 000 μ F at the test frequency is only tens of milliohms, good quality plugs and crocodile clips with short stout leads should be used for connecting the capacitance under test to the extender.

SPECIAL PRODUCT REPORT

Sinclair

DM235 DIGITAL MULTIMETER



Every person who claims to be actively interested in wireless or electronics needs some form of multi-test meter. If you are richer than most then this will probably be the ubiquitous Avo Model 8, for long regarded as the Rolls Royce of conventional multimeters. For the not quite so well off a lower priced oriental meter will suffice, some of them having a bewildering array of ranges—my own one even tests transistors.

The digital multimeter, or d.m.m. for short, is relatively new to the amateur scene mainly because of its very high initial cost for an instrument with a limited number of ranges.

Recently, however, several such instruments have been launched by manufacturers obviously aimed at the amateur segment of the market. The Sinclair DM235 is such an instrument and forms the subject of this test report.

A 3½ digit, six function multimeter, the DM235 is both a bench-top and a fully portable unit. The carrying handle is arranged to act as a leg to tilt the case for easier reading of the display. With a set of dry batteries in the rear mounted


compartment the instrument can be carried very easily with the front uppermost. The test leads fit neatly into a space behind the battery compartment panel when not in use. If you intend to carry the meter around a lot then an ever-ready carrying case is available as an extra. In use the DM235 proved to be simple to operate and the display was easily read with the unit on the bench top. Range selection is by two rotary switches, one of which acts as a function selector and other determines the full scale reading. A slide switch selects d.c./Ω or a.c. readings and a second slide switch controls the power to the unit.

The test leads provided are the usual type with a banana plug at one end and a spring-loaded hook-grip at the other end. I found these to be more of a nuisance than useful. They never seemed to grip properly when I tried to hook them over a test point but when finally in position they seemed reluctant to let go. Also they proved difficult to use as a probe as the wire hook tends to get hidden inside the plastic end. The wander plugs fitted tightly into the two sockets provided on the front panel.

★ specifications

Voltage:	1mV to 1kV d.c. 1mV to 750V a.c.
Current:	1μA to 1A d.c. 1μA to 1A a.c.
Resistance:	1Ω to 20MΩ
Diode test:	0.1μA to 1mA
Input impedance:	10MΩ
Basic accuracy:	0.5% on 2V range; 1% on all other d.c. ranges and resistance; 1.5% 30Hz to 10kHz a.c. ranges
Size:	254 × 147 × 41mm
Weight:	682gm

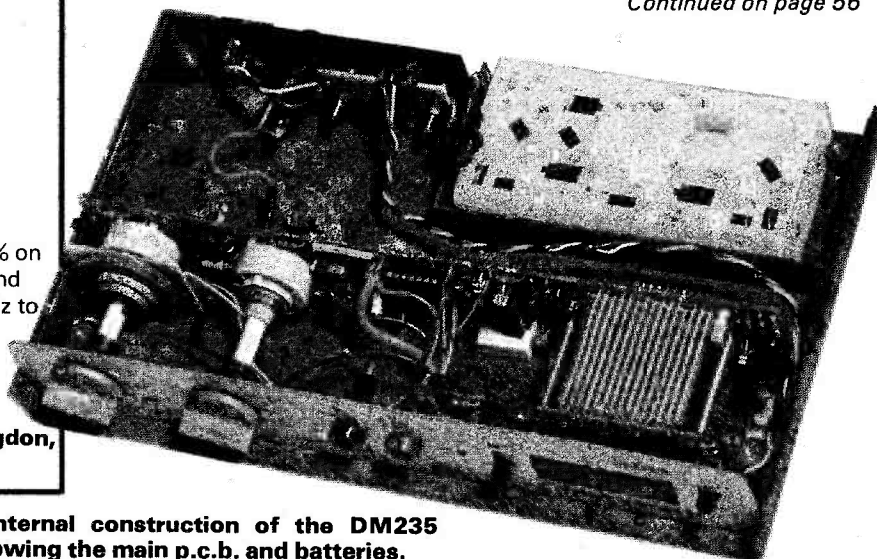Sinclair Radionics Ltd., St. Ives, Huntingdon, Cambs. PE17 4HJ.



The internal construction of the DM235 showing the main p.c.b. and batteries.

Continued on page 56

NEXT MONTH IN...

practical

WIRELESS

ON SALE 2ND. FEB.

We proudly present

THE




WINTON

STEREO AMPLIFIER

Using power FETs in the output stage, the "Winton" produces 50 watts per channel with harmonic distortion around 0.015% and sounds as good as its spec.

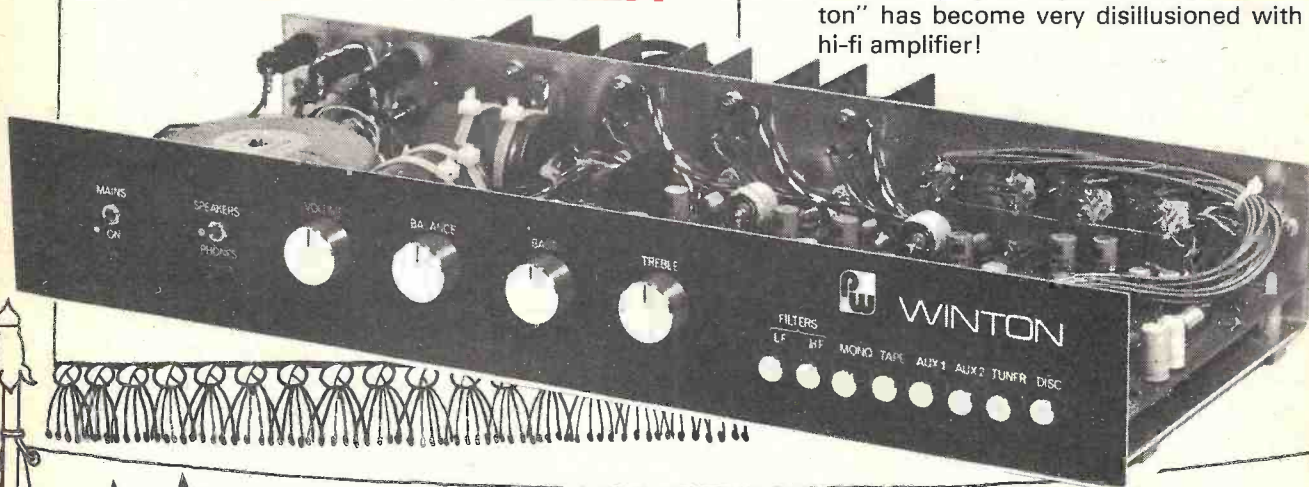We warn you—everyone who has heard the "Winton" has become very disillusioned with their own hi-fi amplifier!



★ ★ ★
EXTRA 8 PAGE SUPPLEMENT
'Data for
CONSTRUCTORS'

All the information you have ever wanted on such topics as soldering, front panels, component markings, cases and cabinets, handling CMOS and more besides, is yours free in our special supplement.

ALSO:

THE



'SOUNDLITE'

**SOUND TO
LIGHT UNIT**

A three-channel sound-to-light converter incorporating zero-voltage switching, a.g.c. and active filters.

DEVICES & CIRCUITS

PART 2

M.J. DARBY

In the first part of this feature we saw that the front-end unit of a receiver provides a 10.7MHz intermediate frequency output signal. The i.f. stages must amplify, filter and limit this signal before it is demodulated. Current trends are strongly towards the use of one or two integrated circuits in the i.f. stages rather than the use of discrete components, whilst ceramic filters are generally employed rather than inductance-capacitance tuned circuits, since they provide the required selectivity without the necessity for alignment.

In most designs a single quadrature-tuned circuit is employed in the demodulator circuit and this must be aligned so that it resonates at 10.7MHz. A few years ago Signetics produced an integrated circuit phase-locked loop, the NE563, which required no tuned circuits in the i.f. or demodulator stages, but this device is no longer available. Nevertheless, when using a commercially manufactured front-end unit, the alignment of the receiver is very simple—only the demodulator circuit need be adjusted. The position is very different to the alignment of the many tuned circuits in the older valve type of receiver where any slight mis-alignment of the band-pass tuned circuits or of the ratio detector circuit could result in considerably greater distortion.

Available Devices

There are quite a number of integrated circuits available which include all the devices required for the i.f. amplifier/limiter and demodulator stages of an f.m. receiver. The decoder required for stereo reception is always a separate circuit, normally a phase-locked loop i.c., but some amplifier/limiter/demodulator devices incorporate an audio amplifier. Many of the devices designed for use as amplifier/limiter/demodulators in the sound section of television receivers are suitable for use in f.m. radio receivers. A selection of typical amplifier/limiter/demodulator devices is shown in Table 1. These devices are suitable for the f.m. section only of receivers which cover both the f.m. and a.m. bands. However, some details will be given later of devices which can be used in both parts of an a.m./f.m. receiver.

Sensitivity

It is quite reasonable to feed the output from a high gain front-end unit through a single ceramic filter into a high gain i.f. device (such as the 3089) for local station reception, but in a situation using a relatively insensitive device, such as the μ A2136 or the LM2111, it is almost essential to employ an interfacing amplifier in order to obtain adequate gain, reasonable a.m. rejection, etc. The amplifier used may employ one or two discrete transistors, but an integrated circuit amplifier is often much more convenient.

The sensitivity of the devices shown in Table 1 is expressed as a value which is known as "the input limiting voltage at the -3dB point" or sometimes as the "limiting sensitivity" or the "input limiting threshold", any of these terms being used in various data sheets. Let us consider what this definition means. If the input signal level to a device is relatively high, the amplitude of the output signal will be unaffected by any reasonable variations of the input signal, since the output amplitude is controlled only by the limiter circuit. As the input voltage falls, a point is eventually reached at which the input to the limiter is inadequate for it to operate correctly and the output amplitude must then fall. When this fall is equal to -3dB, the input signal level to the device is known as the "input limiting voltage at the -3dB point" or one of the other terms mentioned. The lower the value of the input limiting voltage, the more sensitive the device.

It can be seen from Table 1 that the input limiting voltage ranges from about 12 μ V up to about 450 μ V.

The main difference in the internal circuits of such devices is the use of a more sensitive amplifier-limiter with more amplifying stages in the more sensitive devices. Although it must be remembered that the more sensitive devices are likely to become unstable if the circuit layout is unsuitable, all of the devices should be stable if used in a reasonable circuit layout with the input well away from the output. The input to a sensitive device should not consist of a length of copper strip on a board, but rather a miniature coaxial lead or at least a short wire.

Facilities

Another important factor to be considered when choosing an amplifier/limiter/demodulator device is the range of facilities provided by each of the integrated circuits concerned. The 3089 device, the TDA1200 and the CA3189E offer a very wide range of facilities, including a.g.c. output, a.f.c. output, muting of noise when tuning between stations and generally a very high performance for high quality equipment. A few devices, such as the LM1808, are available with an incorporated audio amplifier and this can be useful when space is at a premium.

Gain Block

Before we consider typical amplifier/limiter/demodulator circuits, we will look at an integrated circuit gain block which will provide ample gain between the front-end unit of the receiver and any of the devices shown in Table 1.

The circuit of this 10.7MHz amplifier is shown in Fig. 7. A Fairchild μ A753 integrated circuit (in a plastic 8 pin dual-in-line package) is very convenient for use in this type of circuit for a number of reasons. There is a choice of a

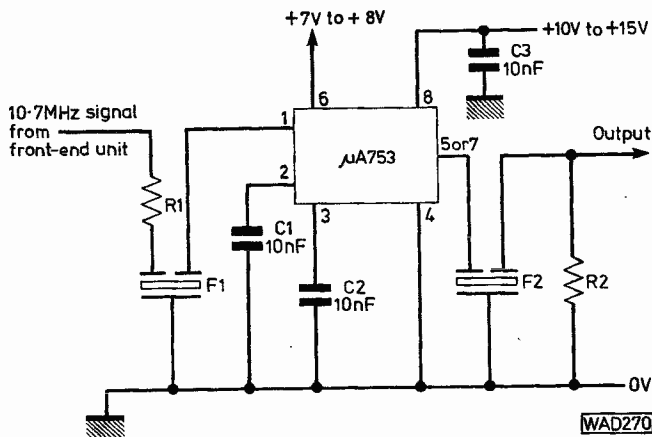


Fig. 7: A simple $\mu A753$ 10-7MHz amplifier with ceramic filters

gain of about 34dB if the output is taken from pin 7 or a higher gain of about 50dB if the output is taken from pin 5. Another feature of the $\mu A753$ is that its input and output impedance have been chosen to match those of the ceramic filters normally used in the input and output circuits.

It is important that the filters (marked F1 and F2 in Fig. 7) should be reasonably closely matched with the circuit impedances. The 10-7MHz filters now available from Toko, Vernitron and Murata have been designed to operate with their inputs and outputs connected to circuits of 330 Ω impedance; if the "in" and "out" impedance is far from this value, the band-pass characteristics of the filters will be impaired.

The input impedance of F1 can be matched by making the value of R1 equal to 330 Ω minus the output impedance of the front-end. Similarly the value of R2 is selected so that this resistor, in parallel with any load which the circuit feeds, forms the required 330 Ω value across the output of F2. The values of these resistors are not at all critical and R1 can often be 270 Ω whilst R2 may be about 390 Ω .

Ceramic filters are marked with a colour code to indicate the approximate resonant frequency. It is vitally important that the two filters used in the Fig. 7 circuit should both have the same colour coding or they will not match one another accurately enough in frequency; they must also come from the same manufacturer. Two such filters provide almost the ideal band-pass characteristic with a rejection of around 100dB at frequencies 0-2MHz or more from the resonant frequency. However, it is possible to omit F2 and to couple pin 5 or pin 7 through a small capacitor (perhaps 1nF) directly to the input of an amplifier/limiter/demodulator device. The rejection of unwanted frequencies will then be of the order of 55dB—which is adequate for many locations.

The $\mu A753$ provides a stabilised output of +7-8V from pin 6. This is ideal for use as a power supply to certain front-end units (such as the Mullard LP1186), but some of the Toko front-end units require a higher voltage supply which can be conveniently obtained using a Zener diode. The maximum current which can be taken from pin 6 of the $\mu A753$ is about 10mA.

The $\mu A753$ has been designed to operate over a wide temperature range, namely -40°C to +85°C, at almost constant gain. Naturally care must be taken to ensure that the leads to the decoupling capacitors C1, C2 and C3 in Fig. 7 are kept as short as possible.

There are a few other similar gain blocks available. The Fairchild $\mu A3076$ (available from Arrow Electronics Ltd.)

provides a relatively high gain (around 80dB) for use with a demodulator of moderate sensitivity.

Amplifier/Limiter/Demodulators

The output from the circuit of Fig. 7 may be fed into one of the amplifier/limiter/demodulator devices listed in Table 1. We will now consider some typical applications circuits using some of these devices. Although the principles of operation of each type of device are the same, the individual features of the devices (and therefore practical circuits) differ considerably. A common feature is that they all require a phase shifting "quadrature" tuned circuit.

The $\mu A2136$

The Fairchild $\mu A2136$ is a relatively simple device with moderate gain, three stage input amplifier/limiter, a quadrature demodulator circuit, an audio output amplifier, an internal voltage regulator and other circuitry. The connections of this device are shown in Fig. 8; it is available in a standard 14 pin dual-in-line case from Arrow Electronics Ltd., Coptfold Road, Brentwood, CM14 4BN at a price of about £2.

The basic circuit for a limiter/demodulator using a device such as the $\mu A2136$ is shown in block form in Fig. 9, whilst a full typical circuit is shown in Fig. 10. The input from the amplifier which follows the front-end may be coupled through C1 to L2 and hence into the limiter of the $\mu A2136$ device. Although inductor coupling is used in this circuit, other types of input coupling can be employed, such as in the examples used with other circuits in this article. It is important to note, however, that the maximum resistance between pins 4 and 6 is about 300 Ω ; in Fig. 10, this resistance is that of the winding L2 which is very low.

The output of the limiter is fed to the quadrature detector and appears at pin 10; after attenuation by a factor of about seven times, it also appears at pin 9. The quadrature tuned circuit is connected between pins 2 and 12, R1 damping the resonance of the circuit. The value chosen for R1 is a compromise between obtaining a relatively high audio output voltage and obtaining the lowest possible distortion at the output.

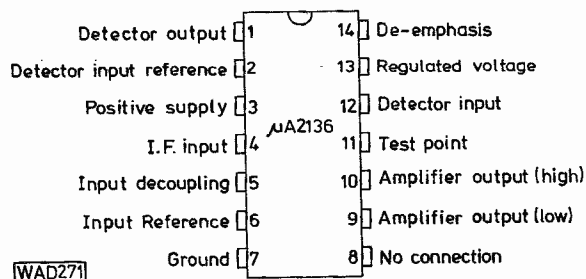


Fig. 8: The $\mu A2136$ connections


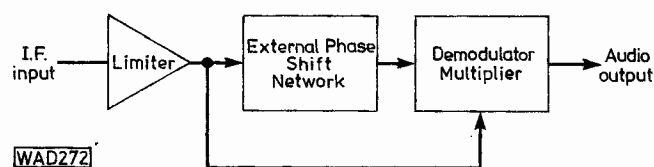


Fig. 9: Basic circuit in block form for a limiter and f.m. demodulator

Fig. 10: A limiter-demodulator circuit using the μ A2136

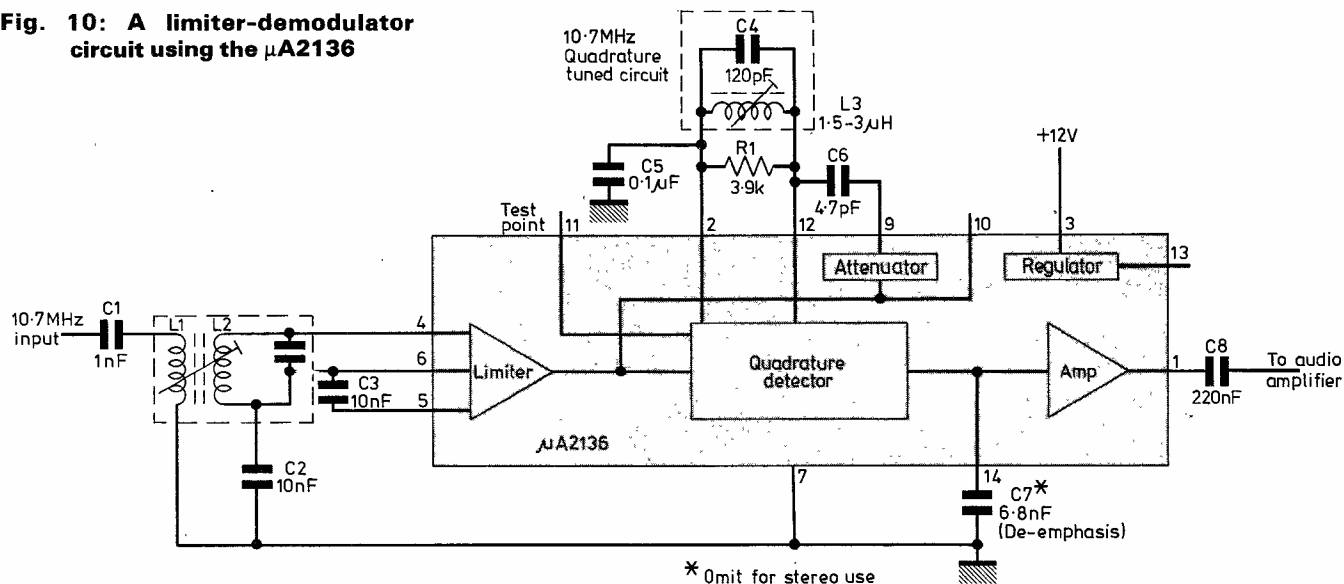

The output from the quadrature circuit is amplified and fed to pin 1. A de-emphasis capacitor should be connected from pin 14 to ground, the internal resistance of the device at pin 14 providing the required resistive component of the de-emphasis network.

The regulated voltage appears at pin 13, but this voltage is also used to power the input limiter and the quadrature detector; the internal connections are not shown in Fig. 10 in order to keep the circuit as simple as possible. No external connection need be made to pin 13.


It may be noted that the μ A2136 device is an improved version of the earlier ULN2111 14 pin dual-in-line device. The Sprague ULN2111 has no internal voltage regulator and the positive supply of about 12V must be connected directly to pin 13 instead of to pin 3. Otherwise, the connections are the same. Further similar devices are the ULN2111A (Sprague), the CA2111AE and its quad-in-line version the CA2111AQ (RCA) and the MC1357 (Motorola). The μ A2136 is a direct equivalent of the Sprague ULN2136.

The 3075

The Fairchild μ A3075 (available from Arrow Electronics Ltd.), the National Semiconductor LM3075 and the RCA CA3075 are somewhat similar devices to the μ A2136, but an audio pre-amplifier is incorporated on the same chip as the i.f. circuitry. These are 14 pin dual-in-line plastic devices.

A typical 3075 circuit is shown in Fig 11. The i.f. input circuit may be similar to that of Fig. 10 or one of the other circuits, but the effective resistance between pins 1 and 2 must be fairly small so that pin 2 is correctly biased from pin 1. The 3-stage limiter has a gain of about 60dB and feeds a quadrature detector, the output from which feeds an emitter-follower before being coupled to the input of an audio pre-amplifier at pin 14. The output from the pre-amplifier stage is fed to pin 12. The capacitor C7 of Fig. 11 is for de-emphasis and should be omitted from a stereo circuit. The audio pre-amplifier provides a gain of about 21dB, but there is a loss in the coupling network between the emitter follower and the pre-amplifier.

Fig. 11: A limiter-demodulator circuit using the 3075 device

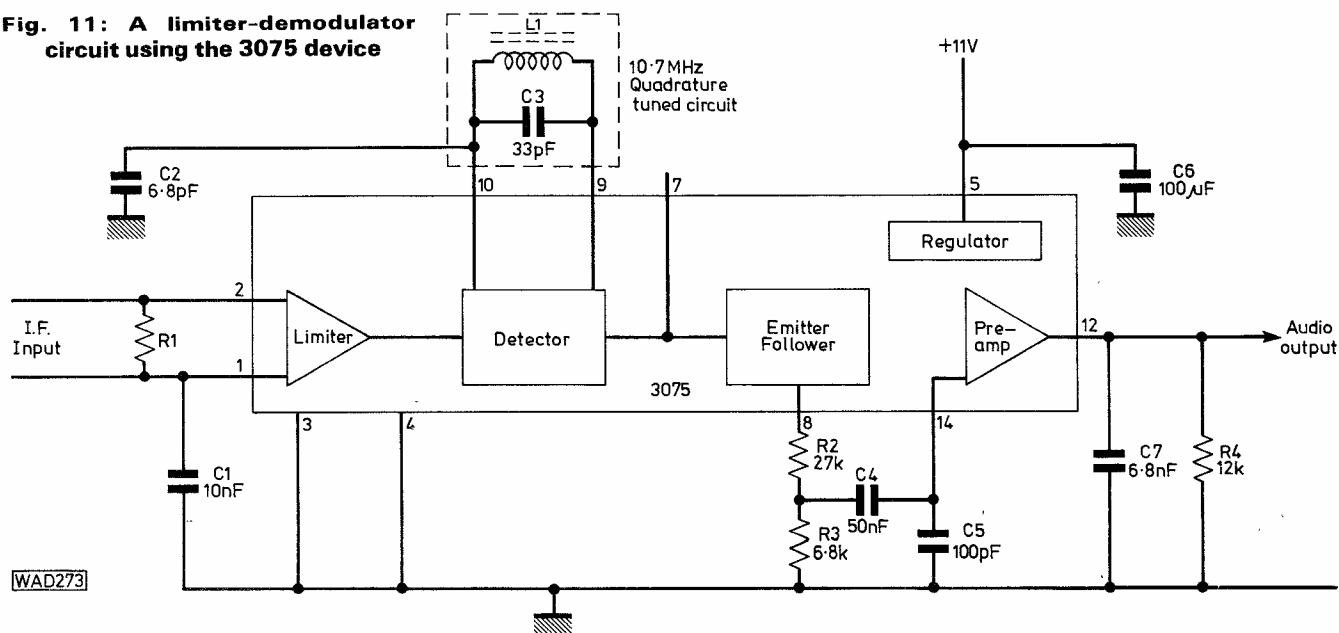

TBA 120 series

The TBA120 device was developed for television sound circuits and contains a six stage limiter, but the more sensitive TBA120S with an eight stage limiter is normally preferred for f.m. receiver applications (available from Chromasonic Electronics, 56 Fortis Green Road, N10 3HN). The TBA120T is similar to the TBA120S, but has an 820Ω input resistor to match it to the 5.5MHz ceramic filters used in television receivers; the TBA120U is another device in this series designed to be used with L/C tuned circuits. These devices are manufactured by Siemens, AEG-Telefunken, etc.

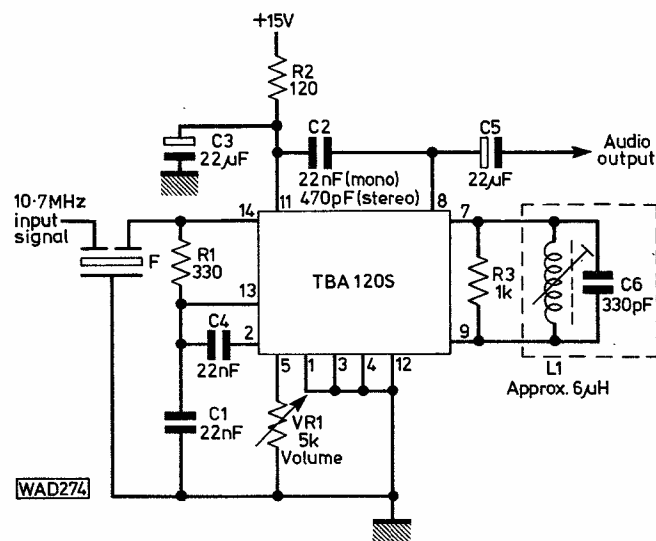


Fig. 12: A limiter-demodulator using the TBA120S device with an electronic volume control

A typical TBA120S amplifier/limiter/demodulator circuit is shown in Fig. 12. A particular feature of all the TBA120 series of devices is an electronic attenuator in the circuit shown. VR1 will provide a variation of about 70dB in volume and since only d.c. levels are involved the volume control leads need not be screened—this is another feature of the TBA120 and the LM1808 devices.

The filter F in Fig. 12 may well be the output filter F2 of the circuit of Fig. 7. L1 and C4 form the normal quadrature circuit of the demodulator.


The 3089

The 3089 type of device (equivalent to the TDA1200) is probably the best known of all limiter/demodulator integrated circuits for 10.7MHz f.m. i.f. use; it is an "industry standard" type available from many manufacturers and provides a wide range of facilities for use in high quality equipment. It has been included in many circuit designs which have appeared in this magazine. It is a sensitive device with a 12μV limiting sensitivity.

A 3089 circuit is shown in Fig. 13. The input to pin 1 is obtained from the 10.7MHz ceramic filter F (which may be the output filter F2 of Fig. 7). Inside the device the signal passes through three cascaded amplifier/limiter circuits and hence to the quadrature detector circuit. This part of the circuit requires a 22μH choke (L1 in Fig. 13), but a miniature Toko component is available for this application. The Toko Company also produces a KACS-K-586HM 10.7MHz tuned circuit in a miniature can which has been especially designed for use as the quadrature detector tuned circuit with 3089 devices.

The output impedance of the 3089 device at pin 6 is about 5kΩ, so when the value of the series resistor R6 is added to this, the total of nearly 10kΩ produces the required 50μs de-emphasis time-constant with C8. The capacitor C8 should be omitted in stereo circuits.

Fig. 13: A 3089 circuit which provides very comprehensive facilities

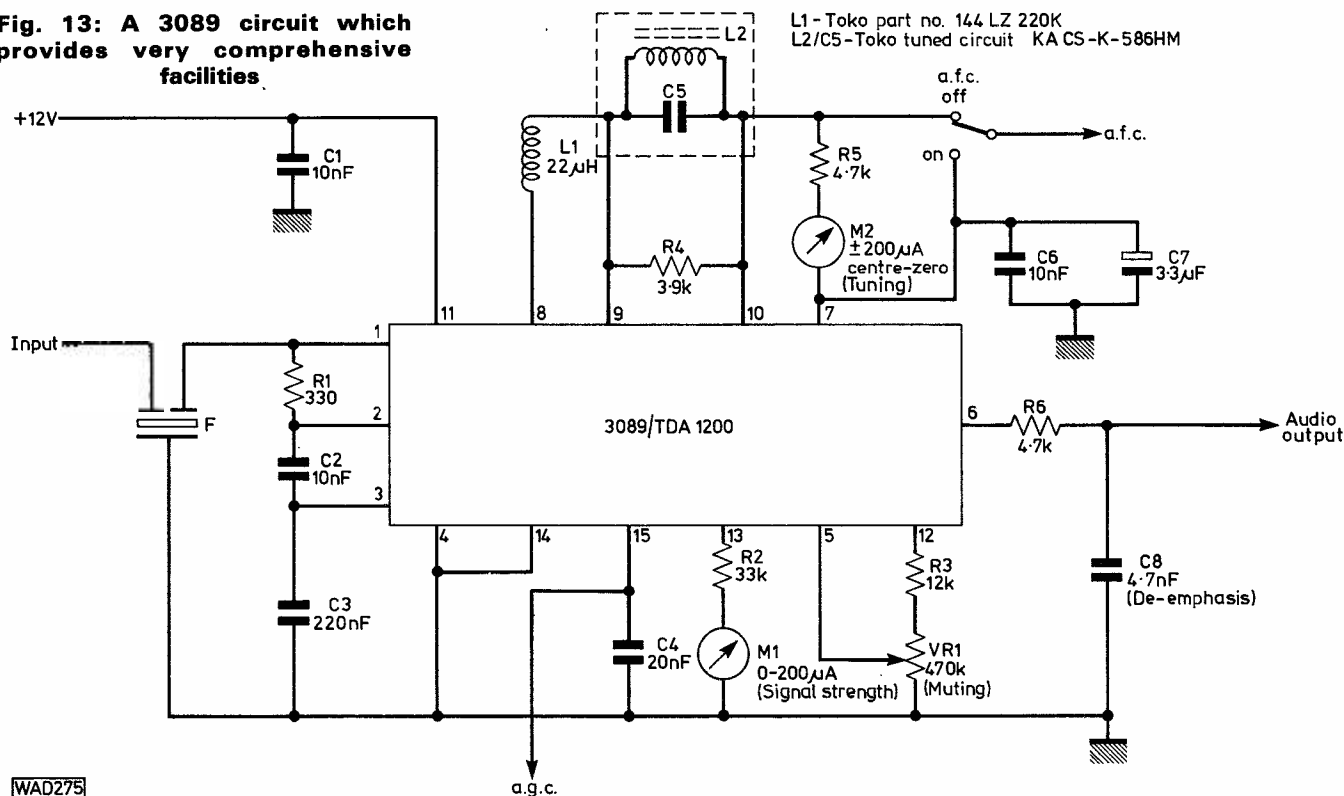

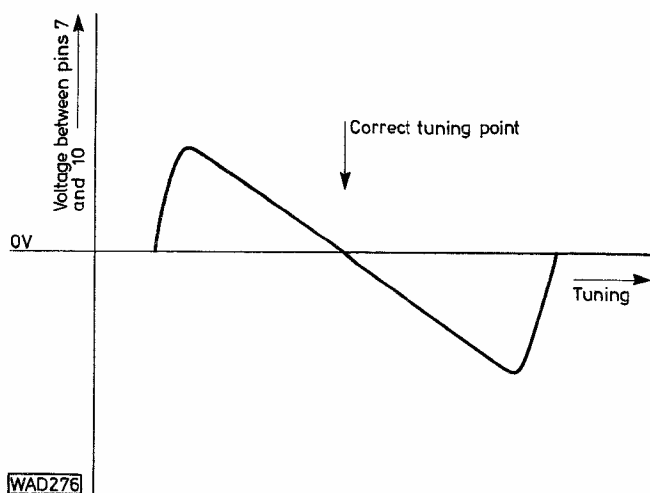


Fig. 14: Variation of the 3089 pin 7 potential with tuning

The meter M1 provides an indication of the signal strength of the i.f. signal at pin 1 of the device. The potential at pin 13 of the device increases approximately as the logarithm of the signal strength and the meter reading increases in proportion to this voltage. The logarithm scale has been chosen so that a very wide range of signal strengths can be accommodated and shown on the meter. In practice, the circuit can indicate any input signal level between about 5 μ V and 100mV by means of M1.

Each of the three cascaded amplifier/limiter circuits in the input of the device has a signal level detector

associated with it. The combined outputs of these signal level detectors control the deflection of the signal strength meter. The first level detection circuit also provides the a.g.c. control signal from pin 15 which may be fed to the front-end unit.

The centre-reading meter M2 can be used as a tuning meter. When tuning towards the centre frequency of the signal, the meter needle is deflected to one side, but as tuning becomes closer to that of the signal, the meter needle returns through the centre position (when tuning should be exact) and is displaced to the other side. This variation of the potential at pin 7 with the tuning is shown in Fig. 14.

All the phase quadrature circuits discussed in this article must be aligned before use by adjusting the position of the core of the phase quadrature coil, whilst the extra input coil used in Fig. 10 must also be aligned. The alignment is greatly facilitated by the use of the meters shown in Fig. 13. When L2-C5 is correctly tuned, the meter M2 will show almost a symmetrical response when tuning through the signal (see Fig. 14) with optimum results when the receiver is tuned to the centre point of the curve.

The use of the meters in the Fig. 13 circuit is optional and some readers may wish to construct the circuit so that a meter is used only during the alignment of the receiver, since the incorporation of a meter permanently into a circuit does increase the cost of the receiver. The full scale reading of M1 and of M2 is not at all critical, as the values of the series resistors R2 and R5 can be adjusted to obtain suitable deflections with the meters available. However, the full scale deflection should not exceed a few mA or the device operation may be affected.

When tuning an f.m. receiver, a considerable amount of unpleasant random noise ("hiss") is formed when tuned to

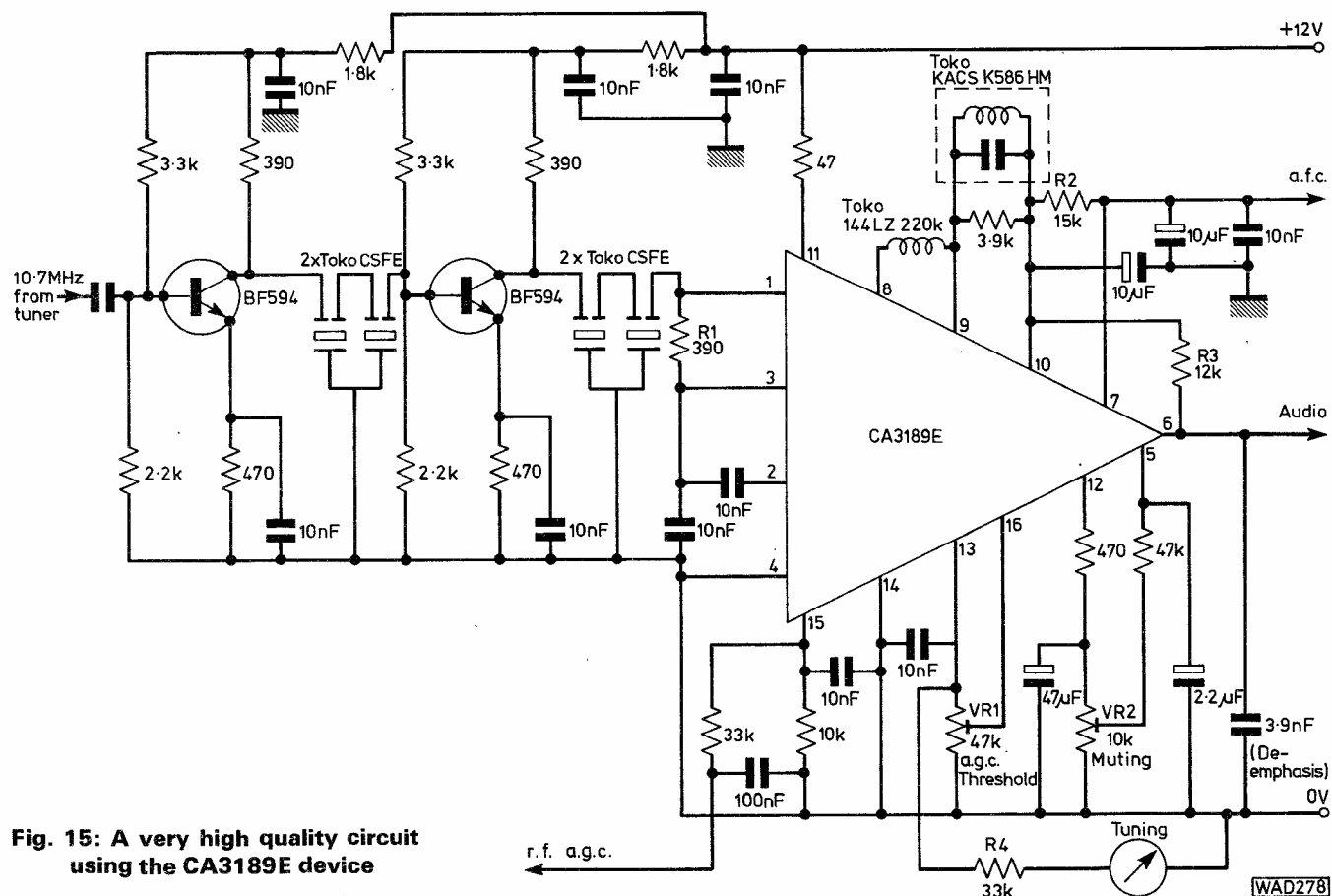


Fig. 15: A very high quality circuit using the CA3189E device

Device	Package	Sensitivity (Input voltage at -3dB point)	Supply Voltage	Supply Current (in mA at 12V)	AM Rejection (dB)	Total Harmonic Distortion	AFC Output	AGC Output	Muting	On-chip Audio Pre-amp	Electronic Volume Control range (dB)	Remarks
μ A2136	14 pin d.i.l.	450 μ V (max. 800 μ V)	12V (20V max.)	17 (max. 22)	40	1% (max. 3%)	—	—	None	—	—	—
3075	14 pin d.i.l.	250 μ V (max. 600 μ V)	12V (max. 18V)	17 (max. 28)	50 (min. 40)	1% (max. 2%)	—	—	None	Yes	—	—
3089 or TDA1200	16 pin d.i.l.	12 μ V (max. 25 μ V)	12V (max. 18V)	23 (max. 30)	55 (min. 45)	0.5% (max. 1%)	yes	yes	Noise only	—	—	Industry standard type
CA3189E	16 pin d.i.l.	12 μ V (max. 25 μ V)	12V (max. 18V)	14 (max. 18)	55 (min. 45)	0.5% (max. 1%)	yes	yes	Noise and deviation	—	—	used in high quality receivers
TBA120	14 pin d.i.l.	80 μ V	12V (max. 14V)	14 (max. 20)	60 (min. 50)	—	—	—	none	—	60	designed for television sound
TBA120S	14 pin d.i.l.	50 μ V (max. 100 μ V)	12V (max. 18V)	14 (max. 20)	68	0.2%	—	—	none	single transistor available	85 (min. 70)	Internal transistor and Zener diode
LM1808	18 pin d.i.l.	200 μ V (max. 400 μ V)	18V (max. 26V)	11 (i.f. only)	min. 40	1.2% (max. 2%)	—	—	none	2W power amplifier	75	On-chip power amplifier with protection
2111A	14 pin d.i.l.	300 μ V	12V (max. 15V)	17 (max. 22)	40	0.3%	—	—	none	—	—	—
Parameters may vary from one manufacturer to another—consult data sheets						Devices suitable for use as 10.7MHz Limiter/Demodulators						

frequencies between the incoming required signals. The 3089 device incorporates a circuit which is able to mute or silence the receiver when no signal is being received. A muting signal is obtained from a level detector connected to the quadrature circuit which feeds a steady output voltage to pin 12, this voltage varying according to whether an input signal or only noise is being received.

A fraction of the voltage from pin 12 is tapped off by VR1 and fed to pin 5, the muting input. The voltage fed into pin 5 can mute the audio pre-amplifier inside the 3089 so that no audio output is obtained whilst tuning between input signals.

The total harmonic distortion at the output of the 3089 device is about 0.3%, this being lower than that of most other similar devices. This distortion level is mainly a function of the phase linearity characteristic of the quadrature tuned circuit. A considerable reduction in the distortion level can be obtained by employing two tuned circuits instead of one between pins 9 and 10, but the alignment is then far more difficult and suitable test equipment is required to set up the double tuned circuit correctly. However, it is possible to reduce the total harmonic distortion at the output to a level of less than 0.1%.

The CA3189E

The RCA device type CA3189E is a recent development of the 3089 type of device. Like the 3089, it is encapsulated in a 16 pin dual-in-line package and the connections to the two devices are almost identical (except for pin 16), but the external circuits which must be used with the two devices are somewhat different. The CA3189E is the latest device for use in equipment of the highest quality.

The bandwidth of the CA3189E circuit has been restricted to about 15MHz (as opposed to the 25MHz of

the 3089 type devices); this not only improves the noise level by reducing the amount of "in-band" noise generated by two signals outside the pass band, but also renders the circuit layout less critical and improves stability.

Unlike the 3089, the CA3189E includes an adjustable delay for the a.g.c. system; this means that the signal level at which the a.g.c. voltage commences to reduce the gain of the device is adjustable. Improvements in the design of the CA3189E internal circuit have resulted in the signal-to-noise ratio being increased to over 70dB. Another feature unique to the CA3189E is the inclusion of a "deviation" muting circuit in addition to the normal noise muting circuit used in the 3089 devices. This deviation muting circuit results in the muting of the "thump" noise when turning rapidly through a fairly powerful signal.

A typical CA3189E circuit is shown in Fig. 15. The limiting sensitivity of the CA3189E is about the same as that of the 3089 device and a similar input circuit can be employed. However, Fig. 15 shows a different type of input circuit using two BF594 npn transistors and a total of four Toko CSFE ceramic 10.7MHz filters which provide a band-pass characteristic which enables a signal-to-noise ratio of about 40dB to be obtained at an input signal level of only 3 μ V.

It is possible to omit one of the BF594 amplifier stages and two of the ceramic filters; the input signal is then fed directly (through a capacitor) to the base of the second BF594 transistor. In this simpler circuit the signal-to-noise ratio is appreciably lower, being rather over 20dB at the same input signal level of 3 μ V.

The similarity between the CA3189E and 3089 circuits can be seen from Figs. 15 and 13. An important difference between the two is the use of an external audio load resistor 12k Ω between pins 6 and 10 in the CA3189E circuit, whereas the load resistor is fabricated on the

continued on page 71

HOT LINES

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article.

MPU bank cards

A popular cheque scheme on the Continent is one in which the owner's photograph is printed on each cheque. This gives a useful security "cheque"! The Continental bankers have again been looking at services to customers and on French electronics company has warmed to this theme by proposing to stick a microprocessor into everyone's bank credit card.

Cards in current use can store only a limited amount of information in magnetic stripes. The proposal is that, by using a microprocessor, every transaction could be recorded and the holders bank balance could be updated at each transaction.

While all this "with-it, latest, state-of-the-art" approach might be applauded by electronics pundits, I keep hearing about electronic accounting systems charging people idiotic amounts, like the £8 million gas bill etc. The Ginsberg abacus rules—OK?

What is an 1154?

Say 1154 to most Lisle Street electronics buffs and they will draw you a picture of an enormous ex-RAF transmitter, complete with coloured knobs and a couple of PT15 directly heated valves in the p.a. stage.

Contrast this nostalgic colossus with the new i.c. that incorporates its own 4MHz oscillator. The chip uses silicon gate techniques (not to mention a touch of c.m.o.s.) and sips only a dainty 6µA at 1.55V. It is aimed at the watch market and deliveries are now rumoured to be rife.

Meter magic

So now I've heard it all, Magic Meters—well, they appear to be magic to me. A new range of analogue panel meters just out on the British market look all very smart in their black edged cases and large white dials with black lettering. The scale reads 0–150A (on the one I'm looking at). But if I want it to read 0–15kV, I can simply unplug one scale, and insert another. And the readings are guaranteed to be accurate to Class 1.5 accuracy. There's virtually dozens of scales; another reads 0–1000kW.

The nice thing about these meters is that they are dustproof, the scales have a positive "click" insert mechanism, and you can change scales without

taking the meter to pieces or, indeed meddling with anything else on the instrument.

The range of scales available is truly enormous, ranging from milliamps to Megavolts. These meters are intended for the professional who should look for the IMO J Series instruments.

Confucius—II dit

Someone in History is always having his magic phrase "Damned clever these Chinese" repeated. Alas, to bring it up to date we must substitute French. An electronics company in Toulouse has been watching the growing market in home computing and business computing. Now, it is to launch its X1 system which is based on the Motorola 6800. The X1 offers 8K of memory, two minifloppy discs, keyboard, and 12in display monitor all for around £2000. The display can handle 24 rows of 80 characters. Strong rumours persist that a basic version will be made available for around £500.

The murky depths revealed

Television cameras on the seabed are all very well—until there's turbulence, or the water gets murky, then they're blind and virtually useless.

A British company has come up with a solution—use an ultrasonic TV camera. While the possibility has been argued about since the late 1930's, it is only now that a practical solution has been achieved. In use, an array of ultrasonic transducers fire forward to "illuminate" the screen at ultrasonic frequencies.

The reflections are focused onto a special converter tube. A half-wavelength piece of quartz is embedded in the faceplate of the converter tube and it is this that accepts the ultrasonic echoes and translates them into a voltage pattern. The new unit is said to operate at depths down to 30 metres, but can be used down to 300 metres with an added pressure window.

The TV scan details are 12½ frames/second 201 lines/frame. Using a frequency of 2MHz it is claimed to see clearly through several metres of very murky water.

While underwater enthusiasts celebrate, doubtless Hams will wonder about further QRM at the high end of Topband!

Hothouse transducers

If you're interested in checking relative humidity, then you might be pleased to hear about a special relative humidity transducer that has recently appeared on the American market. It measures only 41 x 22 x 1.6mm and the humidity is sensed by an electrically conductive surface. It can monitor from 0% to 100% relative humidity over the temperature range –60°F to +200°F. Useful, perhaps, for electronics gardeners or budding sauna enthusiasts.

Optical disc store

In previous Ginsberg writings I mentioned that video discs were a reality and that many manufacturers were producing these. It now seems that these discs will have another application—for storage in computers. A European company has produced an optical disc memory system that looks very promising. One, single 12 inch double sided disc can store the equivalent of half a million pages of typewritten matter. This is considerably more than magnetic discs. The mean access time to any address anywhere on the disc is 250ms.

Self checking

When using computers and computer systems it is not unusual to find a thing called "self-diagnostic". This is where the computer (or system) fires signals around its own circuitry to check that all its circuits are functioning correctly. This usually happens in those fractions of a second that the system isn't being used.

The latest digital multimeter to arrive on the market does the same thing. It will self-check itself and, if it does find something it shouldn't, it will isolate the fault to one of the five basic boards. It will also function as a d.m.m. to an accuracy of better than ±2 p.p.m. of reading, and 1 p.p.m. of full scale (6½ digits). Input impedance of this truly magnificent beast is 1000MΩ and the input is also fully protected against overloads to 1kV. And the price!

Ginsberg

Pw HYTHE marine band receiver **Part 1**

M. TOOLEY & D. WHITFIELD



This modern receiver design offers very good performance at low cost, is easy to build and uses readily available components. The receiver provides for the reception of a.m., c.w. and s.s.b. signals. The construction of the receiver unit makes use of a single printed circuit board and the alignment procedure is simplified by the use of a pre-tuned ceramic i.f. filter. The resulting performance is more than adequate to satisfy the needs of the discerning short wave listener or medium wave DXer.

Although the basic receiver design is for a frequency coverage of 1.5 to 3.5 MHz, coil winding details are also given for alternative frequency bands in the range 1 to 12 MHz. Only two coils need to be wound by constructors and, to further simplify this task, they each make use of only a single tuned winding.

The multi-mode capability and the 2 MHz tuning range of the receiver also makes it ideally suited for use as a 'tunable i.f.' in conjunction with a front-end converter for the v.h.f. aircraft or amateur bands.

The receiver utilises the National Semiconductor LM373N i.f. amplifier. This versatile device, designed specifically for communications subsystems, provides all

the necessary facilities for a complete multi-mode i.f. amplifier and detector. The LM373N is a 14-pin dual-in-line integrated circuit which comprises a gain-controlled i.f. preamplifier, main i.f. amplifier, f.m./c.w./s.s.b. product detector, a.m. peak detector and an a.g.c. system.

The product detector operates in an unbalanced mode for a.m. reception and functions as an amplifier followed by an envelope detector. For f.m. reception, the product detector is supplied with a signal which is in phase quadrature with the original i.f. signal (i.e. 90° out of phase). The product detector inputs for s.s.b. operation are the i.f. signal and the b.f.o. output. The audio output is then derived before the envelope detector. The envelope detector then acts as an audio frequency peak detector and the output of this stage is used for a.g.c. purposes.

Circuit Description

An overall block diagram of the receiver is shown in Fig. 1. It is a conventional single-conversion superhet which makes use of five transistor stages and two integrated circuits. The circuit diagram is shown in Fig. 2.



For this external view, the receiver has been fitted with satin-finish aluminium knobs, contrasting the black front panel

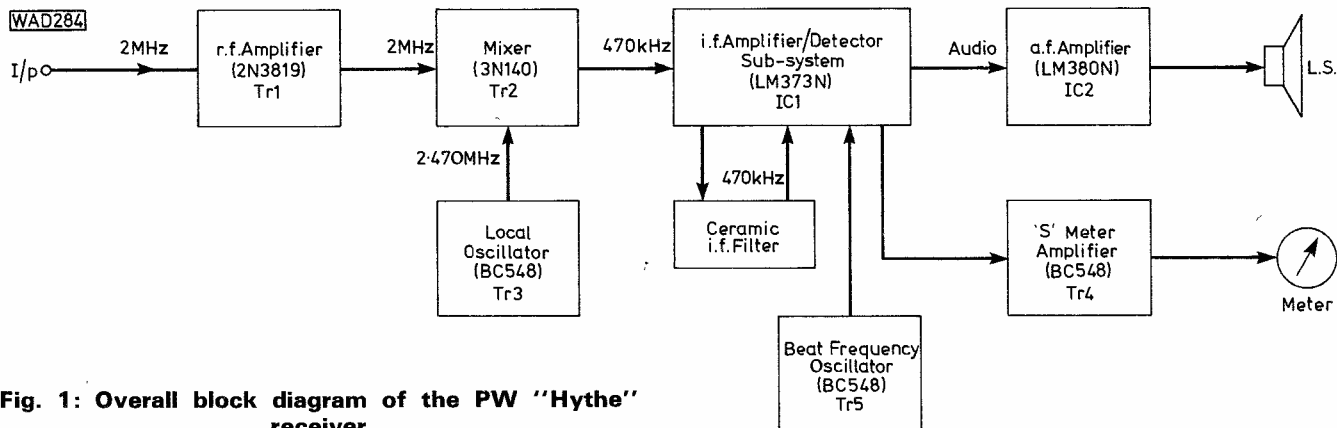


Fig. 1: Overall block diagram of the PW "Hythe" receiver

Amplification at r.f. is provided by a junction gate field effect transistor, Tr1, operating in common gate configuration. This stage exhibits a low input impedance, ideal for matching long wire aerials, and a high output im-

pedance, which is necessary to reduce the loading on the r.f. tuned circuit, L1 and VC1.


A dual gate field effect device, Tr2, is used in the mixer stage. The signal from Tr1 is applied to gate 1 and the

★ specification

Frequency Coverage: 1.5 to 3.5MHz
Modes of Operation: AM, FM, CW and SSB
Intermediate Frequency: 455kHz (nominal)
Sensitivity: 1.5µV RMS typical for 10dB S+N/N ratio measured at 2.5MHz (30% modulation at 100Hz)
Selectivity: 5.6kHz at -3dB points
 11.9kHz at -20dB points
AF Power Output: 500mW maximum into 8Ω loudspeaker at 1kHz
AF Response: 130Hz to 3.5kHz at -6dB
Image Channel Rejection: Greater than 20dB at 2MHz. This figure is considerably improved with the aid of an aerial tuning unit or preselector.
IF Rejection: Greater than 55dB at 2.5MHz
AGC Range: AM; less than 3dB change in audio output for 40dB change in input. Measured at 2.5MHz, 30% modulation.
BFO Tuning Range: 2kHz centred on 455kHz (nominal)
Input Impedance: 600Ω (nominal)
Output Impedance: 8Ω to 16Ω (nominal)

Table of component changes for alternative frequency coverage

Frequency coverage	L1		L2		C28
	Turns	SWG	Turns	SWG	
1.0-2.5MHz	140	34	105	34	4.7nF
2.5-6.0MHz	65	30	50	30	1nF
5.0-12.0MHz	40	30	38	30	470pF

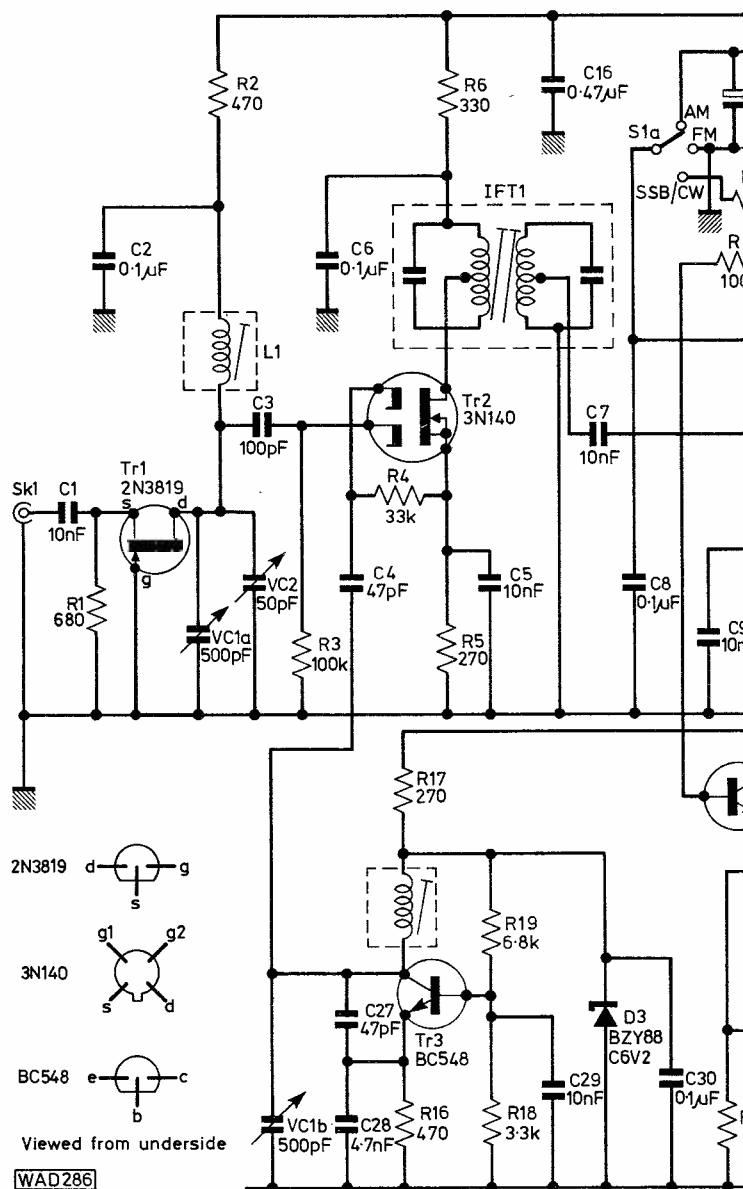

local oscillator signal to gate 2. This type of mixer offers very good performance, providing considerable conversion gain and minimising the loading on the r.f. amplifier and local oscillator tuned circuits. The drain load of Tr2 is a double-tuned i.f. transformer, used to select the desired intermediate frequency signal.

The local oscillator stage is somewhat unconventional in design. A bipolar transistor, Tr3, is connected in common base configuration in a modified form of Colpitts oscillator. This arrangement provides an almost constant output level over a very wide tuning range, with the added advantage of requiring only a simple untapped inductor. The power supply to the oscillator is stabilised by a Zener diode, D1.

The i.f. amplifier and detector functions are provided by IC1. A ceramic filter is used to define the overall selectivity of the receiver. The LM373N is ideally suited for filters of this type having medium level input and output impedances.

External switching is used to select the different modes of operation. This switching is important, not only to

select the appropriate signal paths, but also to ensure that the correct a.g.c. characteristics are provided.

As the LM373N uses only a relatively small a.g.c. voltage swing compared with a conventional i.f. amplifier, it is necessary to provide additional d.c. amplification in order to drive the signal strength meter. The current amplifier, Tr4, operates as an emitter follower which has a high input impedance in order to minimise the loading effect on the a.g.c. line. Pre-set potentiometers, VR4 and VR5, are respectively used to allow calibration and balancing of the 'S' meter.

The beat frequency oscillator (b.f.o.) stage uses a transistor, Tr5, operating as a conventional common emitter, tuned-collector oscillator. The emitter load, however, is left un-bypassed in order to improve the purity of the output waveform. The operating frequency of the b.f.o. is pre-adjusted by the core setting of IFT4. Fine frequency adjustment is achieved by means of a conventional silicon diode D3, connected as a "varicap"—i.e., to a variable reverse bias potential derived from a potentiometer across the supply. The b.f.o., a.g.c. amplifier and local oscillator

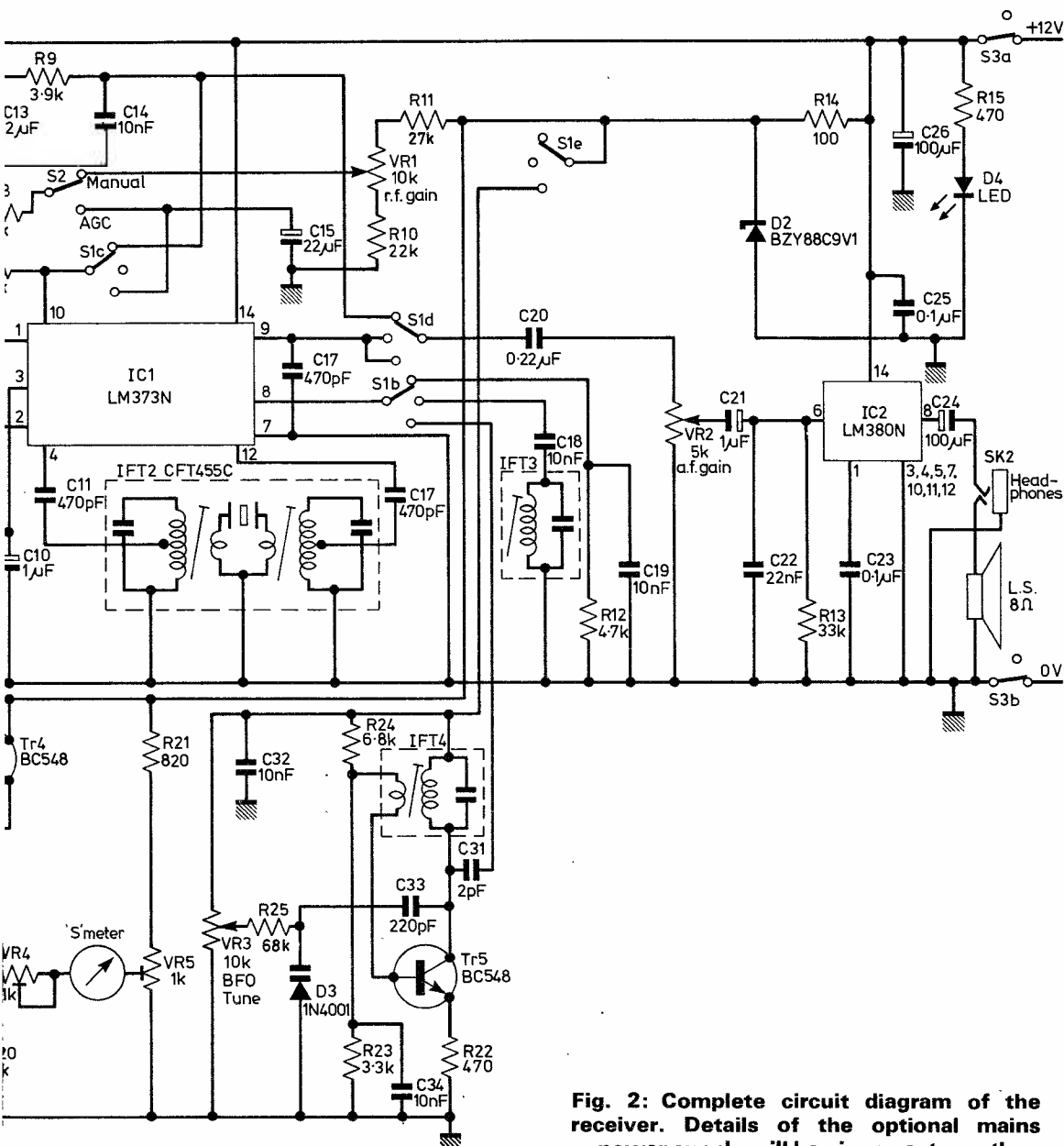


Fig. 2: Complete circuit diagram of the receiver. Details of the optional mains power supply will be given next month


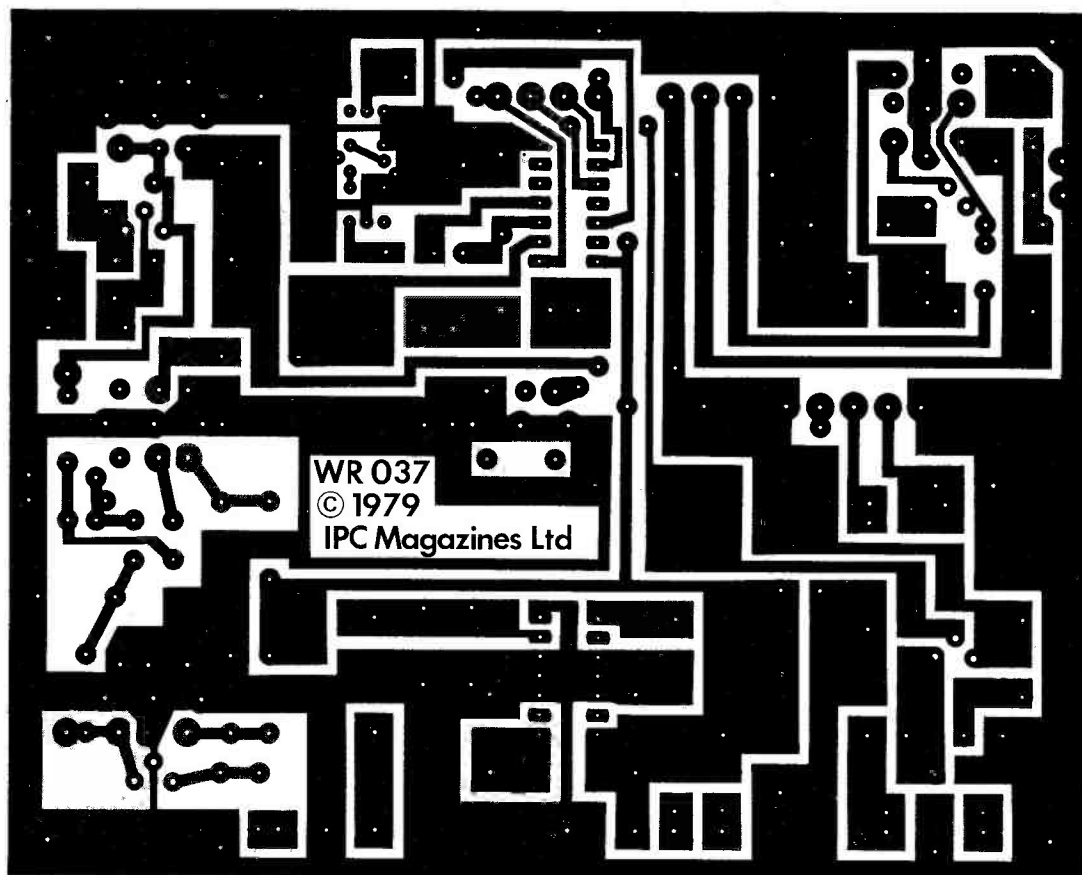


Fig. 3: Printed circuit board track pattern, shown full size

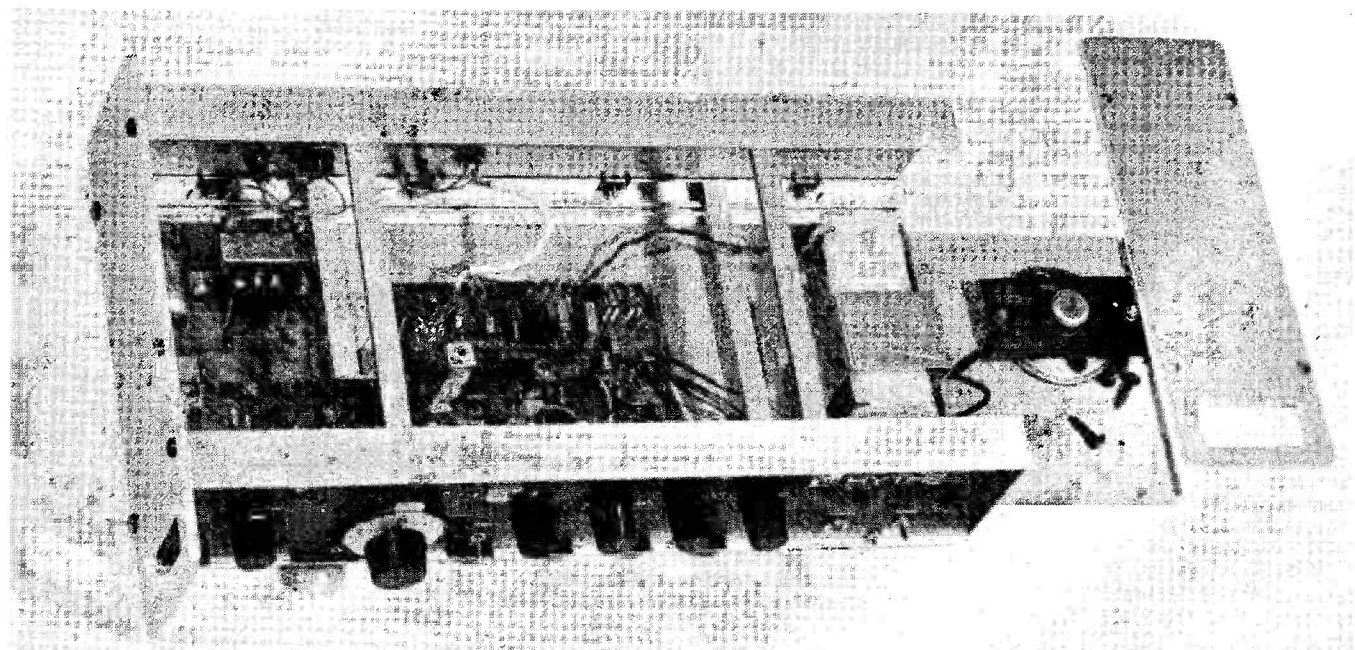

Internal view of the PW "Hythe". Access to the internal battery pack is by removing the right-hand end of the case. The case specified is also suitable for mounting in a standard 19 inch rack cabinet

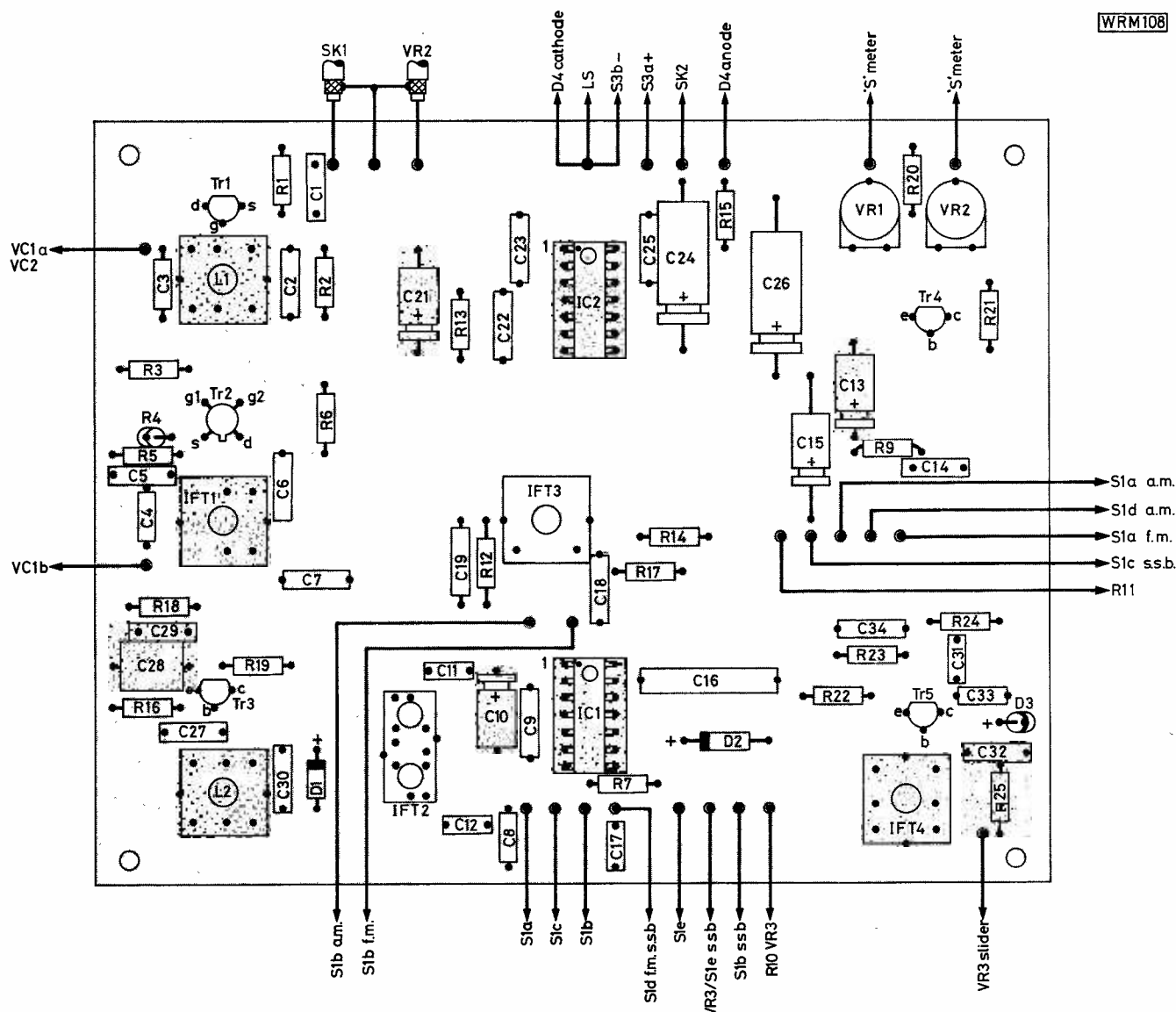


Fig. 4: Component location and external connections for the receiver printed circuit board

stages are all powered from a nominal 9V stabilised supply provided by D2.

Audio amplification of the detected signal is provided by IC2. This is a conventional arrangement using an LM380N. Little comment is needed, save to mention that this arrangement provides an adequate power output, with a fixed voltage gain of around 50, and uses an absolute minimum of external components.

Construction

The majority of components are located on the p.c.b. with

controls and switches mounted on the front panel. After completing the assembly of the p.c.b. a careful visual check should be carried out in order to ensure that all components have been soldered correctly into place and that no dry joints or inadvertent short circuits exist. It is essential that the p.c.b. should be thoroughly checked at this stage since it is difficult to remove it for inspection once it has been wired to the front panel components. Push-fit terminal pins may be inserted into the p.c.b. to readily facilitate connections to the rest of the circuit. The p.c.b. is secured above the base of the chassis close to the front panel by means of four short stand-off pillars. The wiring from the main p.c.b. to the front panel, and par-

★ components

Resistors

all $\frac{1}{4}$ W 10% carbon

100 Ω	1	R14
270 Ω	2	R5, 17
330 Ω	1	R6
470 Ω	4	R2, 15, 16, 22
680 Ω	1	R1
820 Ω	1	R21
1k Ω	2	R8, 20
3.3k Ω	2	R18, 23
3.9k Ω	1	R9
4.7k Ω	1	R12
6.8k Ω	2	R19, 24
22k Ω	1	R10
27k Ω	1	R11
33k Ω	2	R4, 13
68k Ω	1	R25
100k Ω	2	R3, 7

Miscellaneous

S1 miniature Maka-switch, two 4p 3w wafers and spacers, S2 s.p.d.t. miniature toggle switch, S3 d.p.d.t. miniature toggle switch, IFT1 Denco IFT18, IFT2, IFT3 Denco IFT13, VC1 dual gang 500pF (365pF if reduced frequency coverage acceptable). VC2 50pF variable. Ceramic filter CFT455C (6kHz bandwidth) Ambit International. Coil formers 4.8mm dia \times 27mm in length 2 off, base plates, cans and dust cores to suit. 8 Ω speaker ($2\frac{1}{2}$ in dia), moving coil meter (see text), 50mm vernier drive, terminal pins, stand-off pillars, round BNC socket, countersunk 4BA screws, 15mm long (min.) 3 off, 4BA clearance spacers $12\frac{1}{2}$ mm long (min.) 3 off, standard jack, battery holders (optional), West Hyde "Brightcase" BC2121, front panel (D. J. Pattle).

Potentiometers

all carbon track

1k Ω lin	2	VR4, 5
5k Ω log	1	VR2
10k Ω lin	2	VR1, 3

Capacitors

Silvered mica

2pF	1	C31
-----	---	-----

Polystyrene

47pF	2	C4, 27
100pF	1	C3
220pF	1	C33
470pF	3	C11, 12, 17

Polyester min dipped

4.7nF	1	C28
10nF	10	C1, 5, 7, 9, 14, 18, 19, 29, 32, 34
22nF	1	C22
0.1 μ F	6	C2, 6, 8, 23, 25, 30
0.22 μ F	1	C20
0.47 μ F	1	C16

Electrolytics

63V tubular

1 μ F	2	C10, 21
22 μ F	2	C13, 15
100 μ F	2	C24, 26

Semiconductors

LM373N	1	IC1
LM380N	1	IC2
2N3819	1	Tr1
3N140	1	Tr2
BC548	3	Tr3, 4, 5
BZY88 C6V2	1	D1
BZY88 C9V1	1	D2
1N4001	1	D3
TIL 209	1	D4

ticularly that associated with the tuning capacitor VC1, should be as short and direct as possible, and wiring from the board to the volume control, and from the aerial socket to the board, should employ short lengths of screened cable. Some care is needed here in order to ensure that the control spindle of VC1 is correctly aligned to the shaft of the drive. If this alignment is not correct, undue wear may be placed on the vernier drive mechanism and also the tuning may be found to be somewhat erratic.

Inductors L1 and L2 consist respectively of 120 turns and 80 turns of 32 s.w.g. enamelled copper wire wound in two layers on a 4.8 mm diameter former fitted with a base, screening can, and dust core. In each case, care should be taken to ensure that the terminal pins of the base align correctly with the p.c.b. connections. After completing the winding of the coils, they should be liberally coated with a polystyrene impregnant in order to hold the windings in place. The screening can is then fitted and the entire assembly is located and soldered to the p.c.b. If an alter-

native frequency coverage is required, coil winding details are provided in the table shown. The moving coil meter used in the prototype was a miniature edgewise tuning indicator of approximately 200 μ A full-scale deflection. The receiver will, however, operate satisfactorily with moving coil meters having anything between 100 μ A and 1mA full-scale deflection and, if desired, constructors may choose to use a properly calibrated 'S' meter. In the authors' experience, however, the calibration of such meters in all but the most expensive of receivers has been found to be somewhat arbitrary and, for most purposes, a conventional linear meter scale will be found to be quite satisfactory.


The second part of this article will deal with the two optional items involved—the power supply, and an aerial matching unit, the latter providing an improvement both in image rejection and impedance matching. Details will also be given for setting up and operation of the receiver generally.

PRODUCTION LINES

alan martin

If you please

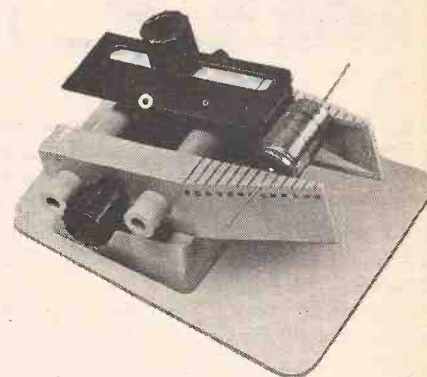Would readers kindly mention "Production Lines", when applying to manufacturers or suppliers featured on this page.



Neat job

With the home constructor demanding a highly professional standard of finish to his projects, a useful tool has been introduced by Litesold.

The Opsec component lead bending tool is designed for simple and accurate preforming of component leads prior to insertion into the p.c.b.

The jaws may be adjusted, up to a maximum of 45mm, to accommodate most lengths of components likely to be used on circuit boards. An adjustable stop and numbered slots on the jaws ensure accurate positioning of the component prior to bending. The base is engraved in steps of 2.5mm to aid initial setting-up.

Manufactured in Deroton, a tough, high impact plastic and with the base fitted with non-slip feet, which may be drilled through and the unit screwed securely to the bench, the Opsec tool costs £4.99 plus 8% VAT and 15p P&P. *Light Soldering Developments Ltd., 97/99 Gloucester Road, Croydon, Surrey CRO 2DN. Tel: 01-689 0574.*

Cases Galore


West Hyde Developments, the Aylesbury based electronic hardware suppliers, inform me, that they can supply from stock a case to house virtually all projects likely to appear in journals such as *Practical Wireless*. The photograph shows a selection of the various families of cases available, however, the combination of sizes multiply this selection enormously.

West Hyde can also offer a full range

of accessories such as knobs, handles, switches, indicators and tools.

With the aid of a computer, designed to complement West Hyde's accounting system, they are able to provide a speedy turnaround of orders.

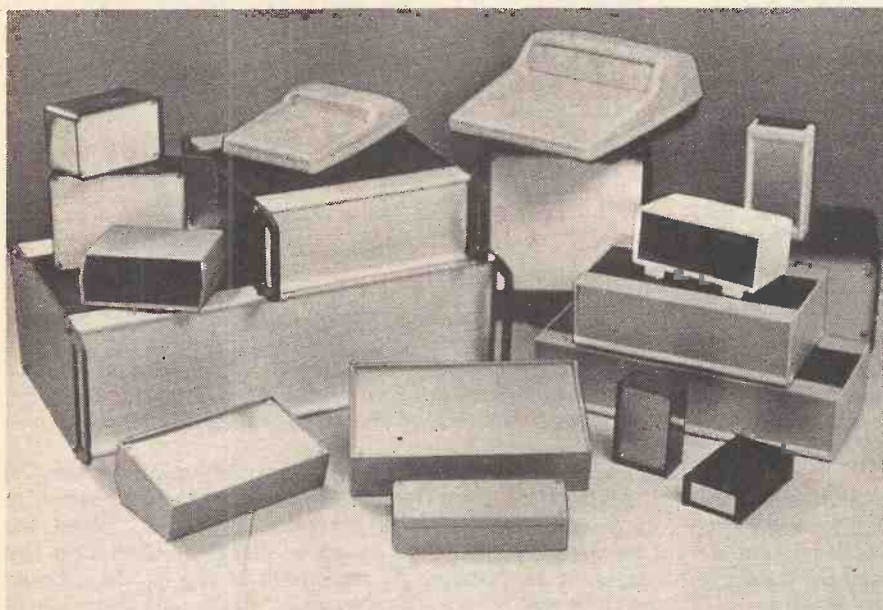To obtain their latest, free catalogue and price list, applications should be sent to: *West Hyde Developments Ltd., Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET. Tel: (0296) 20341/4.*



Drill stand

Recently introduced by Mega Electronics Ltd., a new low-cost p.c.b. drill stand designed for use with conventional hand-held p.c.b. drill units.


Designated the Photolab PLST-12A, the drill stand is constructed with a strong base of machined cast iron supporting precision steel guides by means of which the standard 12V drill is raised and lowered.


Important features are its combined simplicity and accuracy, and the fact that it will accept both the Mega and

other proprietary drills of 34mm body diameter. Additionally, the same basic drill stand is available to special order from Mega, capable of accepting drills between 20mm and 41mm diameter, at marginal extra cost.

Printed circuit boards of up to 254 x 228mm (10 x 9in.) overall will be accepted by the drill stand.

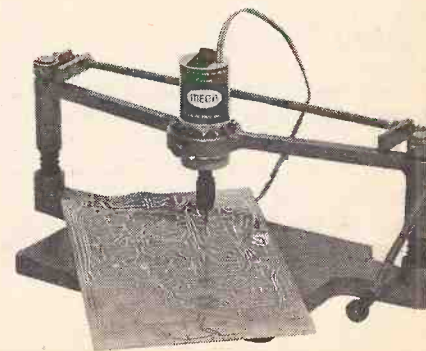The Photolab drill stand is priced at £16.50 which includes VAT, and is available from: *Mega Electronics Ltd., 9 Radwinter Road, Saffron Walden, Essex CB10 1EP. Tel: 0799 21918.*



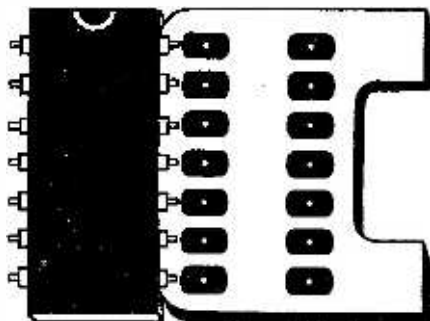

OF THE MONTH 73

Brian DANCE M.Sc

NATIONAL LM391N-60 AUDIO DRIVER

The design of high quality audio power amplifiers is quite complex, and poorly constructed circuits may develop distortion or even burn out if used in a warm room. To avoid the problems associated with the construction of a complete amplifier using discrete semiconductor devices, a complete audio hybrid module or integrated circuit power amplifier can be used.

However, another approach involves the use of an audio power driver i.c. which contains most of the circuitry required for the early stages of the amplifier, but which is not itself designed to supply high power levels. This device will provide signals which can be used to drive external power transistors feeding the load.

Unfortunately very few audio power driver devices have been manufactured, but recently the new LM391N-60 has become available to the home constructor. This is a 16 pin dual-in-line device with the connections shown in Fig. 1 which can be used to construct audio power amplifiers producing only about 0.01% total harmonic distortion. It has the advantage that it is internally protected against output faults causing excessive current flow. In addition, it is protected against thermal overloading, and also protects the external power transistors.

A typical LM391N-60 amplifier which will deliver up to 20W into an 8Ω loudspeaker or up to 30W into a 4Ω loudspeaker when operated from suitable power supplies is shown in Fig. 2. Pin 8 of the LM391N-60 can deliver an output current of up to 5mA to the base of the BD345 driver transistor Tr1; this latter device amplifies the current before it is again amplified by the BD346 power transistor, Tr2. Pin 8 is a current source, but pin 5 accepts current and is therefore known as a current sink. The current is withdrawn from the base of the BD344 transistor Tr3 into pin 5; Tr3 drives the BD347 power transistor Tr4.

The positive half cycles of the waveform are handled by the BD346 power device, the current passing through R9, L1 and the loudspeaker to ground, but during negative half cycles current flows from ground through the speaker, L1, and R10, to the BD347 and hence to the negative supply line. This is a normal type of Class B operation in which each output transistor conducts alternately.


Circuit Details

The audio input signal is coupled by C1 to pin 1 of the device, R1 being the ground return resistor. The values of these components must not be too low or the bass response will be reduced. The amplifier input impedance is approximately equal to R1, but if this resistor has a very high value, board layout problems may occur when designing for stability. In addition, the use of a very high value for R1 may result in a high offset voltage at the output.

Negative feedback is taken from the output through R4 to pin 2. The gain at audio frequencies is equal to $(1 +$

$R4/R2)$ or about 20 (26dB) with the component values shown. However, the value of R2 can be altered (within reasonable limits) to obtain various values of gain. The input voltage required for full output power is about 630mV with the values shown. The value of R4 should be approximately equal to R1 for minimum offset voltage.

Capacitor C2 prevents the flow of a steady direct current in the feedback circuit so that there is 100% negative feedback at zero frequency; this reduces the gain of the circuit to unity at zero frequency with the result that any small input offset voltage is not amplified to produce a large output offset. Such an output offset would not only reduce the output voltage swing in one direction (and hence limit the maximum output power), but would also drive a steady current through the loudspeaker so that the loudspeaker coil would be displaced in its magnet gap or perhaps even burnt out. The value of C2 should be adequate to prevent the attenuation of bass frequencies.

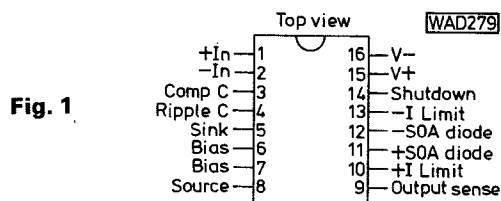

The 5pF capacitor C4 is for frequency compensation (as in an operational amplifier) and sets the high frequency gain-bandwidth product. This component is required for high frequency stability. Capacitor C3 connected to pin 4 improves the rejection of mid-band and high frequencies (see Fig. 3) and if used should have a value equal to that of C4.

The potentiometer VR1 between pins 6 and 7 sets the bias for the external transistor output stages. Too little bias will result in excessive crossover distortion, whilst too much will result in an excessive power consumption and possible overheating. In the circuit of Fig. 2, VR1 should be adjusted for a quiescent current in the output devices of about 15mA, since this is just a little more than is required for minimum crossover distortion (as shown in Fig. 4). Crossover distortion is best detected at high frequencies and at low signal amplitude. The component C5 is a bias by-pass capacitor which reduces high frequency distortion and improves the transient response.

The components L1 and R14 connected in parallel may be made as a single item by wrapping about 25 turns of 19 s.w.g. wire around a 10Ω 2 watt resistor and soldering the ends of the wire to the resistor leads. It is possible to omit these two components completely with some loads, but the inductance L1 greatly improves the stability of the circuit with a capacitive load. Almost all the load current flows through the wire of the inductance (except at very high frequencies) rather than through the resistor R14. The value of this inductance is not at all critical, 2 to 12μH being suitable, but the wire used for L1 must be able to carry the

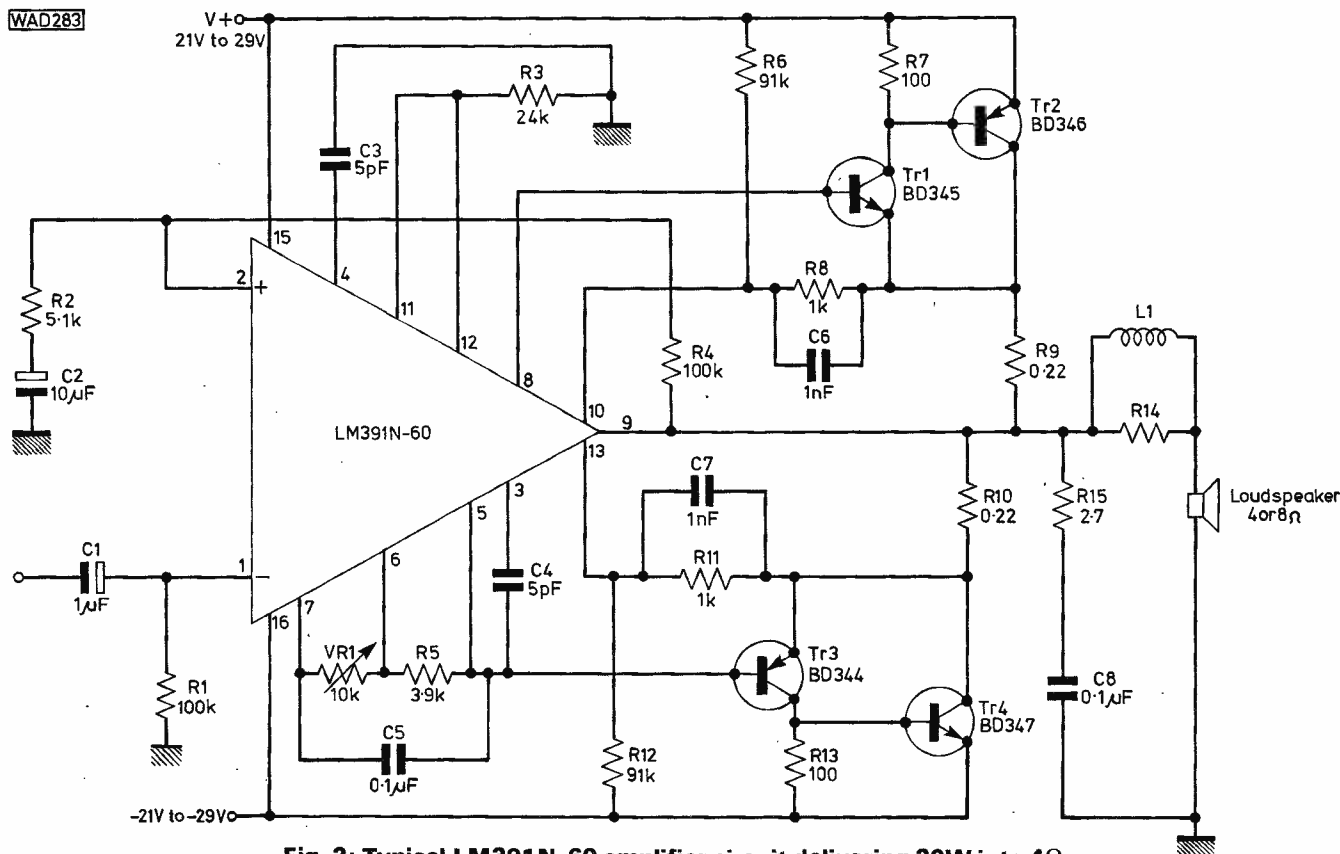


Fig. 2: Typical LM391N-60 amplifier circuit delivering 30W into 4Ω

peak current required by the loudspeaker.

The components R15 and C8 form the normal Zobel network which improves the stability at very high frequencies with certain types of load. Although the circuit may possibly operate satisfactorily without these two components, it is wise to include them rather than risk having trouble with the finished amplifier.

The resistors R9 and R10 are the emitter stabilising resistors for the power output transistors Tr2 and Tr4 respectively. They can easily be wound from a short length of resistance wire (possibly around a resistor of higher value), but the resistance wire used must be able to carry the peak current passed by the transistors. R9 and R10 stabilise the output stage quiescent current against variations of temperature.

The resistors R7 and R13 are bleed resistors which remove the charge stored in the base of the output transistors and thereby speed up the operation of these components.

Protection Circuit

If an excessive current passes through R9, the voltage drop across this resistor will be passed to pin 10 of the LM391N-60. The internal circuit of the device will then cause the current drive to pin 8 to be reduced so that the current passing through R9 is limited to a safe value. Similarly, a high current through R10 results in an increased voltage being applied to pin 13; this results in a reduction of the pin 5 current so that the current in Tr4 is limited to a safe value.

The limiting action of this protective circuit commences when the voltage between pins 10 and 9 or between pins 9 and 13 exceeds about 0.65V. When the component values shown are used, this means the output current in each transistor is limited to a few amps.

The safe operating area (s.o.a.) protective diodes connected in the pin 11 and pin 12 circuits are not used in the relatively simple circuit of Fig. 2 and neither is the device shutdown facility of pin 14. However, a thermal switch may be fitted to one of the output device heat sinks so that this switch closes when the temperature rises above a certain level and connects pin 14 directly to ground. A current of less than 0.5mA in the pin 14 circuit is adequate to shut the device down.

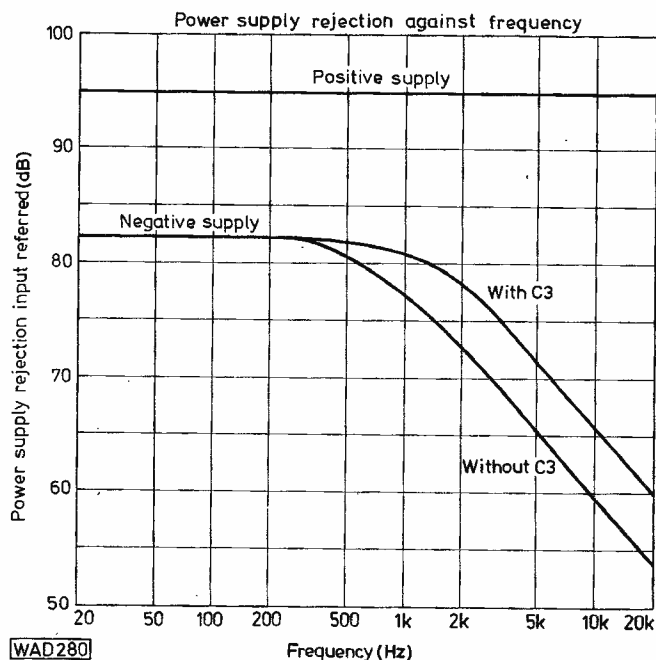


Fig. 3

Power Supply

The maximum power supply voltage which can be safely applied to the LM391N-60 is $\pm 30\text{V}$. However, it is wise to keep the applied voltage appreciably below this value so as to provide a margin of safety to allow for any normal increases in the mains supply voltage producing a higher supply line voltage. An upper limit of 27V is suggested unless stabilised supplies are employed. If the power supply voltage is low, the maximum output power may be reduced. The LM391N-60 draws a quiescent current of about 3mA (maximum 10mA for any device of this type).

The output voltage of a typical LM391N-60 can swing to within 5V of the potential of either of the supply lines. When using a supply of $\pm 21\text{V}$, the maximum output voltage swing will therefore be about $\pm 16\text{V}$. The current in a 4Ω load will be $16 \div 4 = 4\text{A}$ peak, whilst the peak power

will be $16 \times 4 = 64\text{W}$. In Europe amplifiers are rated according to the maximum mean power they can deliver; the mean power is one half of the peak power in the case of a sine wave, so the peak power could be about 32W provided the current limiting circuit does not limit at a current under 4A .

When employing an 8Ω loudspeaker with $\pm 21\text{V}$ power supplies, the peak current is $16 \div 8 = 2\text{A}$ and the peak power $16 \times 2 = 32\text{W}$. Thus the maximum mean power is about 16W . A little more power can be obtained with an 8Ω load if the power supply voltage is increased to about $\pm 23\text{V}$.

The LM391N-60 provides excellent rejection of noise and hum present on the power supply lines. The amplitude of any such noise and hum signals at the output of the device is typically 31 600 times (or 90dB) less than their amplitude on the power supply lines; the typical variation of the rejection with frequency is shown in Fig. 3. The minimum rejection figure for any LM391N-60 is 70dB or 3160 times.

The noise generated by the LM391N-60 is only $3\mu\text{V}$ referred to the input.

Performance

The total harmonic distortion in a LM391N-60 circuit is about 0.01% at 1kHz when the circuit gain is 20, but it increases with frequency as shown in Fig. 4. The distortion is also higher in circuits employing higher gain, since the amount of negative feedback is smaller. Typical values of the total harmonic distortion at two values of gain are shown in Fig. 5. The intermodulation distortion has been measured as 0.01% for signals of 60Hz and 7kHz simultaneously present.

External transistors

Various types of complementary output transistor ($\text{Tr}2$ and $\text{Tr}4$ in Fig. 2) may be used with various types of driver device ($\text{Tr}1$ and $\text{Tr}3$). The transistors used must have a V_{CEO} breakdown voltage rating which is not less than the total voltage applied across the circuit (namely the sum of the positive and negative supply voltages). The maximum current at the LM391N-60 outputs is 5mA . The gain of the driver transistor multiplied by the gain of the output stage must be adequate to bring up this 5mA current to a value which is great enough to drive the loudspeaker at the required power level.

The complementary driver transistors in the circuit shown have a gain of 40 at 200mA collector current. Thus they can bring the 5mA output up to the 200mA level. The output transistors have a minimum gain of 30 at a current of 4A , so this is adequate for the purpose. The driver transistors should have a much higher transition frequency (f_T) than the output transistors to prevent instability.

It is recommended by the device manufacturers that the output transistors of the Fig. 2 circuit should each be mounted on a heatsink of thermal resistance not more than 4.8°C/W or alternatively both could be mounted on the same heat sink which should not have a higher thermal resistance than 2.4°C/W . No heat sinks are required for the driver transistors. These heat sinks are not designed to cope with long duration short circuiting of the output to ground.

The LM391N-60 can be used together with external transistors in high fidelity amplifiers which are reasonably simple to construct. The device is available from Arrow Electronics Ltd., Coptfold Road, Brentwood, Essex, CM14 4BN.


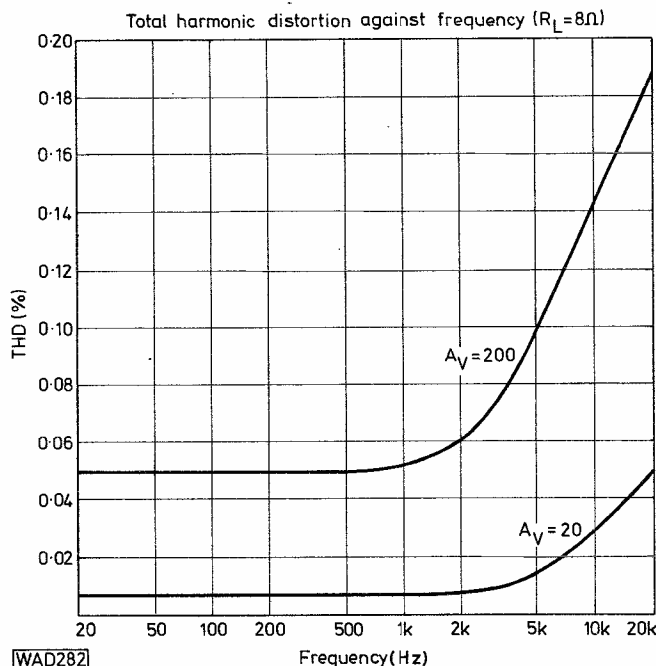


Fig. 4: Above

Fig. 5: Below

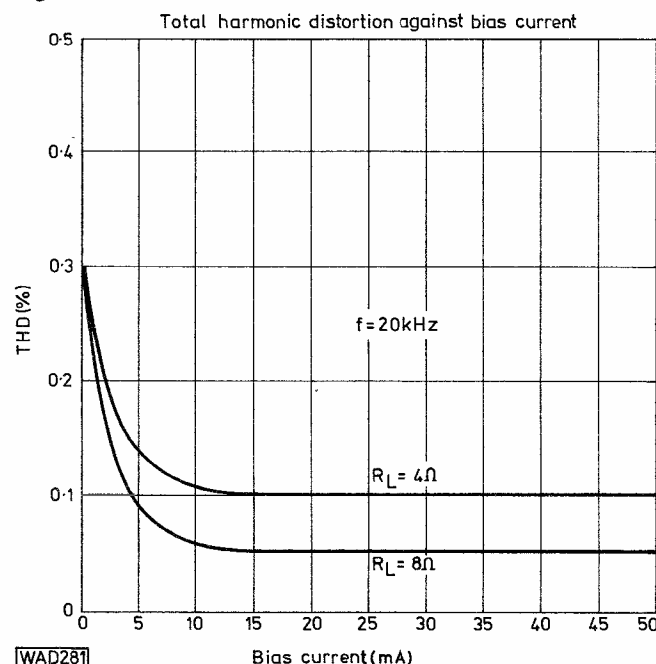

WAD281

Introduction to

S.A.MONEY

LOGIC ~ 7

Having examined the various types of logic element and some typical applications it may now be interesting to look at some of the more recent developments in digital integrated circuits and see how they might affect amateur projects in the future.

Probably one of the more significant advances in the technology of integrated circuits in recent years has been the development of Large Scale Integrated (LSI) circuits in which there might be a thousand or more gates, or flip-flops, on a single silicon chip. This has been made possible by using larger chips, maybe 4mm square, and better photographic and etching techniques allowing more components to be packed into the chip. These complex chips make it possible to build a complete logic system into a single i.c. package. Even more complex devices, having tens of thousands of gates on a chip, known as Very Large Scale Integrated (VLSI) circuits are now being developed which promise to reduce complete computer systems to little more than a handful of i.c. chips.

MOS Logic

Most of the LSI logic devices currently being built use MOSFETs to form the logic elements. Unlike CMOS logic, which uses both *p*- and *n*-channel devices, the MOS logic in LSI chips uses either all *p*-channel or all *n*-channel type transistors.

The earliest LSI chips used *p*-channel transistors and this type of logic is generally referred to as PMOS logic. Power supplies for PMOS devices are negative and often there are two or three different voltages required to produce the correct bias conditions. Typical devices might use supply lines of $-5V$ and $-12V$ although some circuits may need as much as $-20V$ for the supply rail. Because the logic signals are of different amplitude and opposite polarity there can be problems in interfacing PMOS logic with normal TTL and CMOS circuits. Discrete transistor circuits are normally used to match the PMOS outputs to TTL inputs and vice-versa.

Production of LSI circuits using *n*-channel transistors was initially more difficult than that of PMOS devices, but, once the fabrication problems have been overcome, these new NMOS devices, as they came to be called, were found to be better than their PMOS counterparts.


Initially NMOS devices, like the PMOS types, used two or three positive power supply rails but in many of the new NMOS circuits the bias supplies are derived inside the chip so that only a single supply voltage is required. One big advantage of NMOS circuits is that they can easily match up with TTL or CMOS logic and in many cases direct connection between the two types of logic is possible. Most NMOS logic circuits are faster in operation than PMOS equivalents.

A typical NAND gate in NMOS logic would have a circuit arranged as shown in Fig. 77(a) whilst a NOR gate

would be as shown in Fig. 77(b). As with CMOS the input impedance of PMOS or NMOS circuits is very high so static electricity can be a problem. Most modern LSI chips will have protection diodes built in to minimise the possibility of damage due to static. Nevertheless it is wise to handle all MOS LSI type devices with the same care as CMOS, and they should be stored with all device pins shorted together by aluminium foil or conductive plastic foam.


Semiconductor Memories

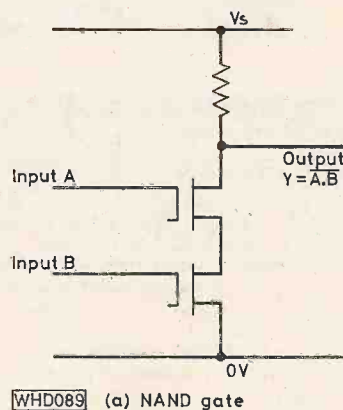Among the earliest applications of LSI techniques was the production of semiconductor memory systems for use



WHD089 (a) NAND gate

Fig. 77 (a): Typical MOS LSI NAND gate

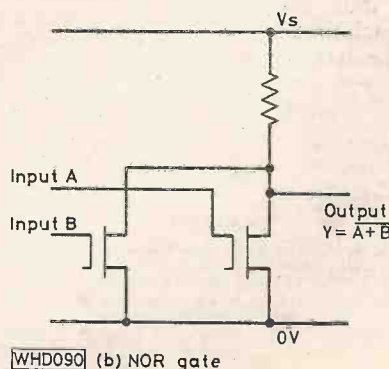

WHD090 (b) NOR gate

Fig. 77 (b): Typical MOS LSI NOR gate

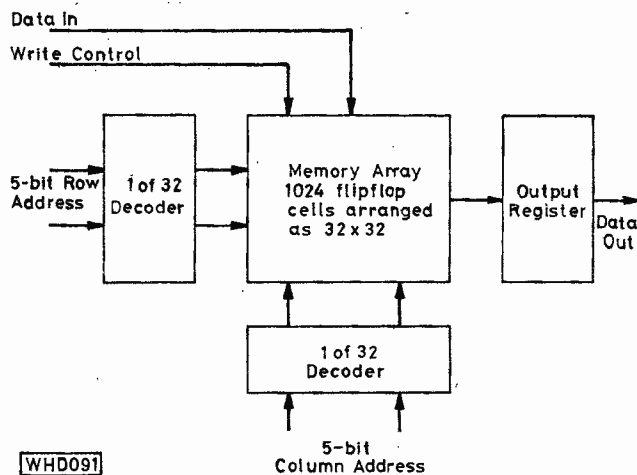


Fig. 78: Organisation of a typical 1024-bit (1K) memory

with small computers. Prior to the mid-1970s virtually all of the digital computer systems used ferrite cores as memory cells. These small ferrite ring cores were magnetised one way to represent a logic 1 state and the magnetisation polarity was reversed to represent a 0 state. A vast array of these tiny magnetic cores would be used to store the states of perhaps thousands of bits of data. Complex addressing logic had to be used to select a particular core in the array, to read its state or to write in new data. Because the windings often consisted of only one turn quite large current pulses were needed to magnetise the cores, so power supplies tended to be rather large.

A semiconductor memory can readily be produced by using a flip-flop for each memory cell. Using LSI techniques it is possible to build 1 000 or more such cells on a single chip and with MOS logic the power requirements will be relatively small.

To simplify the addressing logic the array of flip-flop cells in an MOS memory would be arranged as, say, 32 rows and 32 columns, and the general arrangement of the chip would be as shown in Fig. 78. To select a particular memory cell a 32-way decoder is used to select one row of flip-flops. Next a second decoder is used to select one of the 32 columns and hence will select one flip-flop in the chosen row. The input and output circuits of this selected flip-flop will now be routed to the input and output pins of the chip. When a clock pulse (called the Write input) is applied, the selected flip-flop will take up the state of the data input line thus allowing data to be written into the memory. Each time a flip-flop is selected, its output will be routed to the data output line of the memory chip allowing the data to be read out.

In a typical memory device, such as the 2102, there might be 1024 cells arranged as a 32×32 array. Such a chip would be called a 1K memory. Note the convention by which the "binary thousand" (1024) is denoted by a capital K. Thus a 4K memory would hold $4 \times 1024 = 4096$ bits, a 16K memory would hold 16 384 bits and so on. The address decoders would each be 32-way devices and would be controlled by a pair of 5-bit binary codes, giving a total of 10 pins allocated to address signals for the memory. Apart from the address and power supply there will also be data input and output and a Read/Write control signal to be accommodated. Some chips also have a Chip Enable (CE) line and provide a tri-state output signal. The connections for a 2102 memory are shown in Fig. 79.

Larger memory devices use capacitors as the storage device and the 0 or 1 state is determined by whether the capacitor is discharged or charged. A typical memory cell of this type is shown in Fig. 80.

One problem with capacitor-type memories is that, due to leakage paths on the chip, the charge on the capacitor is slowly leaked away and memory would be lost unless the cell could be topped up. In fact this process of "refreshing" the state of the memory cell is achieved by regularly reading the state of the cell and rewriting this state back into it. This refresh process needs to be carried out at about 2ms intervals and for this reason such memories are called dynamic memories, whereas the normal flip-flop types are referred to as static memories.

In a dynamic memory the capacitors used for storage of data are very small and in a typical chip there may be as many as 16 384 cells together with the addressing logic. Newer types with 65 536 cells are already starting to appear. Static memories, with their more complex cell structure, tend to be less dense and may have perhaps 4096 cells, although here too larger devices are being developed.

Digital Calculators

Until a few years ago most engineers used slide rules or mathematical tables to carry out their calculations. Today they almost invariably use an electronic calculator and even the housewife shopping at the local supermarket may be found using a pocket electronic calculator to check prices.

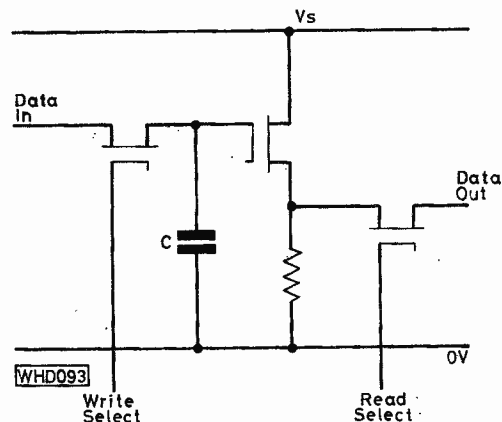
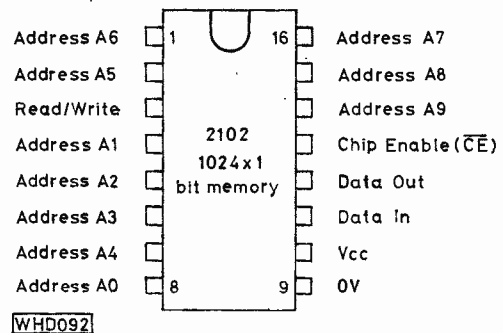


Fig. 80: A typical dynamic memory cell

Prior to 1971 calculators were desk-top machines which were either mechanical or used a vast array of SSI devices. The complex logic of these machines was however an ideal application for the new LSI techniques. In 1971 MOSTEK were to produce the first calculator chip which could add, subtract, multiply and divide numbers. The LSI revolution had begun.

Early calculator chips used PMOS logic and needed a number of extra circuits around them to drive the displays and communicate with the keyboard but despite this it was possible to build a complete four-function calculator unit into a case that would fit into a coat pocket and run from a set of batteries.

The basic logic scheme inside a typical calculator is shown in Fig. 81. At the heart of the device is the ALU (arithmetic and logic unit). This is a complex logic array which can add or subtract two numbers and perform one or two simple tests on the result. For convenience the numbers are represented in the BCD format and the ALU deals with them four bits (one BCD digit) at a time. For multiplication and division a sequence of successive additions or subtractions is carried out in much the same way as if the sum were being worked out on paper.

Apart from the ALU there are flip-flop registers which will hold the two numbers to be operated upon and the result of the operation. An 8- or 10-digit l.e.d. or l.c.d. seven-segment display is provided to present the numbers in visible form. To minimise the number of pins needed on the calculator, chip display is multiplexed with the digits flashing up in sequence at a sufficiently high rate to produce a flicker-free display. A further complex section of logic controls the activities of the ALU, registers, keyboard and display to produce the desired results.

Suppose we are going to add two numbers. At the start the control logic connects the keyboard and display to the "A" register, and as numbers are keyed in their 4-bit data patterns are shifted into this register one digit at a time. The display will show the contents as the number is fed in. When the "+" function key is pressed, a flip-flop is set to select the addition process whilst the keyboard and display are switched to the "B" register where the second number will be stored. When the second number has been entered and the "=" key is pressed, the numbers from the "A" and "B" registers are routed to the inputs of the ALU which adds them together, and the result from the ALU is fed to the display. Digits are switched in sequence by the control logic and any carry bits from one decade are added in as the next decade is dealt with.

In the case of multiplication and division, a sequence of add or subtract operations is carried out in the ALU as the control logic works its way through a preset sequence of commands. These commands switch the operation of the ALU and control the transfer of numbers between it and the other registers. A similar complex sequence of operations is used in some modern calculators to work out trigonometric and other mathematic functions. Sometimes additional registers will be included to allow intermediate results of a complex calculation to be stored temporarily.

LSI in Television

Another application of LSI devices which has come into prominence in the past year or two has been the TV game. In the early 1970s TV based games, such as Pong (or TV tennis), began to make their appearance in the amusement arcades. In these early games conventional logic devices were used, but soon GI introduced an LSI chip which could provide a choice of several different games such as tennis, hockey and squash. Recently much more sophisticated games such as tank battle, which would have needed hundreds of TTL devices, have been introduced.

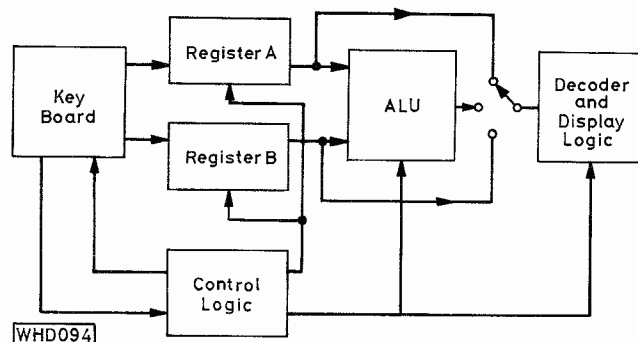


Fig. 81: Block diagram of a digital calculator

The games chip itself has to generate a complete video signal for the game display including sync pulses and in some cases colour signals. Sound effects, such as the ball striking the bat, are generated as bursts of pulses by the games chip. Apart from producing the display the chip must control the motion of bats, balls, etc., and also detect scoring moves and keep the score for both players. Further logic is needed to display the score on the screen and to control the selection of the various games.

External controls for bats, tanks, etc., are normally potentiometers which alter the timing of delay circuits in the chip and hence alter the position of objects on the TV screen. Sometimes the speed of movement may be controlled in a similar way as in the stunt rider and racing car games.

Another recent application of LSI devices in television has been in building decoder systems for the Ceefax and Oracle teletext transmissions now being broadcast by the BBC and ITV.

In teletext decoders the logic must select out the data signals from the television picture signal and decode them. A particular page of text, selected by the viewer, must then be detected and removed from the incoming data stream. The selected page of text is stored as a set of binary data words in a memory and data from this memory is regularly read out and converted into video signals to produce a text display on the screen in place of the programme picture. Using conventional logic such a decoder system might require about a hundred TTL devices whereas by using LSI it is possible to reduce this to perhaps six to ten chips which will fit conveniently on to a small card mounted in the back of the television receiver.

Universal Logic Chips

One of the problems facing the manufacturer of LSI chips is to decide what to put into them. As the logic gets more complex the number of options also increases as each user will want his own favourite features. Unfortunately it costs a lot of money to design an LSI chip and unless it can be made in thousands or even millions it will not be economic to produce it.

One solution to this problem adopted by the chip makers was to build a standard chip which contained a large array of identical gates and to tailor the devices to the user's requirements by interconnecting the gates as required during the final stages of making the device. Thus only the final interconnection pattern needed to be designed for each new application and the overall cost of a new device could be kept down.

Another approach was to make the circuit on the chip more versatile so that it might satisfy a number of varied applications. The limit here is in the number of pins that can be used on the chip package and typically a 40-pin

d.i.l. is about the biggest practical container for normal use.

Intel faced this basic problem when they were making calculator chips for various designs of calculator unit. It occurred to their engineers, however, that basically all of the systems were the same but the control sequence used in each calculator was different. Since most logic systems can be broken down into a sequence of separate logic operations, a universal logic chip might now be produced where the set of commands to the ALU and control logic was fed in from an external memory. Now the basic calculator or logic operation chip could be standard and mass produced, whilst its action could be tailored to suit the user's needs by supplying the appropriate sequence of instructions from some external memory device. The basic idea of the microprocessor has been born and Intel's 4004 device became the world's first microprocessor chip which could handle 4-bit data words and process them in any way the user desired.

Microprocessors

Recently, microprocessors have been very much in the news and in some circles have taken on the aura of being a kind of magical device which can solve all of our problems. In practice, as we shall see, the microprocessor is nothing more than a very versatile logic element that will respond to a set of external commands to perform a wide variety of logic functions. In essence the device works in virtually the same way as the central processing unit of any digital computer system.

Internally a microprocessor will be arranged more or less as shown in Fig. 82. It consists basically of some control logic, an ALU and a set of registers which connect to two external data bus systems. At any time the signal interconnections between the internal circuits are set up by the control logic in response to the external commands, and the internal circuits can communicate with one another via an internal data bus system. Outside the chip an 8-bit-wide data bus is used to carry data to and from the processor chip. A second bus, usually 16 bits wide, carries address signals from the processor which define the particular external circuit that is to talk to the 8-bit data bus. Usually most of the external circuits are memory arrays and the address bus will select the particular memory location where the desired data is to be found or sent to.

The ALU is perhaps the heart of the processor since it can add or subtract numbers, carry out AND, OR, INVERT and EXCLUSIVE OR logic operations or act as a counter or shift register. This is the versatile logic element. The control logic decodes the command instructions fed in from the external memory and sets up the appropriate operation in the ALU and the interconnections between the registers.

The Accumulator register is used to take data from the external data bus and process it via the ALU, after which the result is held in the Accumulator. A second register, called the Program Counter, keeps track of the memory address where the next instruction is to be found. The Program Counter also controls the transfer of instructions from the data bus into the instruction register, from whence they pass to the control logic for decoding and execution.

An Address register is used to hold the current memory address for any data or instructions that are to be passed from the data bus into or out of the processor. Two other registers may also affect this address signal. One is the Index register which allows the processor to modify the memory address during program execution whilst the

Stack Pointer register is used to hold the address of a special area of memory used as a scratchpad by the processor as it executes the program. Finally there is usually a Status register which provides information on the state of play within the processor device. This register can for instance indicate if the result of the last arithmetic operation was zero or negative.

Microcomputers

A microprocessor chip by itself is totally useless, apart from its value as an objet d'art or collectors item. To produce a working system it needs the addition of some memory to hold program and data information and also there must be input-output circuits to allow the device to talk to the outside world. A typical microcomputer system might be as shown in Fig. 83.

To make the system work, a set of program instructions must be written into the memory system and the program counter register is then loaded with the address of the first instruction of the sequence. Each instruction may consist of from one to three 8-bit data words. The first word is always an Operation code which will tell the processor what to do. The second and third words convey the address in the memory where any data needed is to be found or stored. As each of the instructions is executed the Program counter register is updated automatically so that

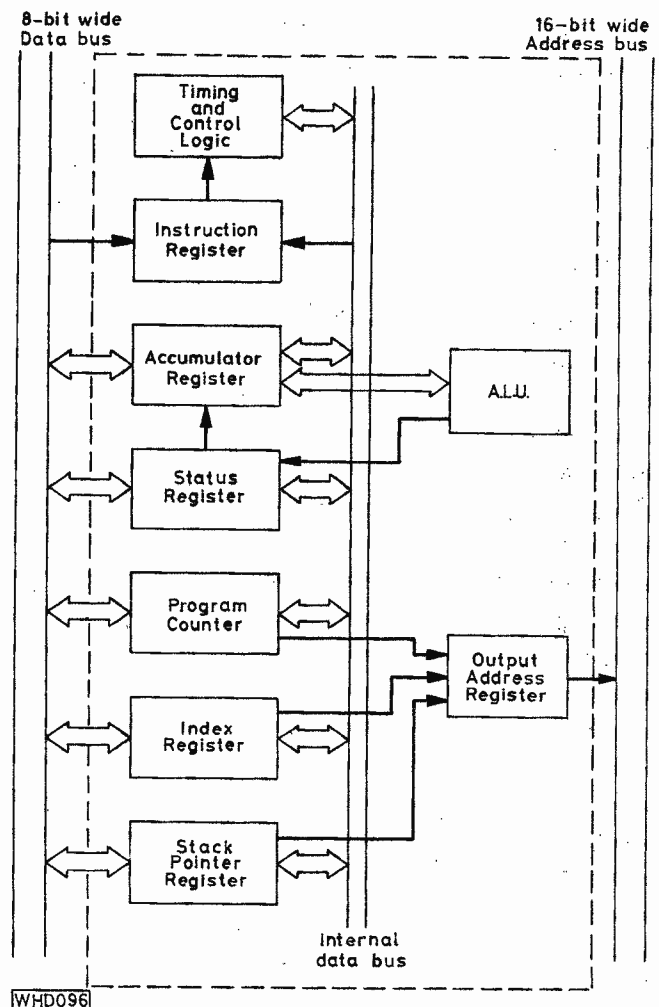


Fig. 82: Block diagram of a simple microprocessor chip

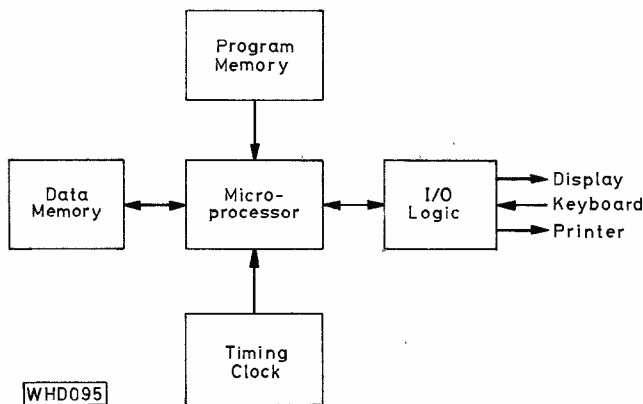


Fig. 83: Block diagram of a typical microcomputer system

it now contains the address in memory where the next instruction to be executed is to be found.

Programming

Perhaps the most important part in designing a system using microprocessors is the process of writing the program of instructions, or software as it is called in computing circles.

Actual instruction codes stored in the memory are just 8-bit binary numbers which represent instruction codes and addresses. Programming in this machine code is difficult and definitely not recommended. To overcome this problem a new language called Assembly code is normally used for writing the programs for a microprocessor. Here each operation code is given a mnemonic name such as ADD, SUB or LDA (Load the Accumulator) and the memory addresses can be given names, such as TEMP, SPEED or SUM.

Suppose we want to add two numbers together. The set of instructions might be;

```

LDA N01      (Load N01 into accumulator)
ADD N02      (ADD N02 to accumulator)
STA SUM      (Store the result in SUM)
  
```

When the complete program has been written in this mnemonic language it must next be translated into the 8-bit binary words of the machine code before it can be loaded into the microcomputer's memory system for execution. The translation is carried out by a complex program called an Assembler. This translation process may be carried out on a similar microcomputer system or on a full-size digital computer system. Once the machine code data has been generated it may be put on to a cassette tape or written into a Read Only Memory. In the small microcomputer system the program is either loaded from cassette tape into a normal read/write memory or read directly from the programmed ROM in order to make the microprocessor carry out its required operations.

Where the microprocessor is being used as a calculator or computer it is convenient to use a higher level language than the Assembly code. Typical of these are the FORTRAN and BASIC languages used on larger digital computers. In this case our simple addition program is reduced to the statement:

$$C = A + B$$

where A and B are the two numbers and C is the answer. These high level languages also need to be translated. In the case of BASIC this is done by using an interpreter-type program to translate each instruction as it is executed, but FORTRAN is translated to machine code in much the same way as the Assembly code.

Where do we go from Here?

In this series the basic principles of logic have been discussed and some of the applications of these devices to amateur electronic projects have been touched upon. It is to be hoped that the reader will now be in a position to understand how a logic system works and perhaps to follow the descriptions of logic operation in books and articles, though it must be admitted that some books on logic tend to be a bit obscure.

How will microprocessors and LSI affect our projects? It is certain that microprocessors are here to stay and that they will feature in the more advanced amateur projects such as RTTY systems, Morse decoders, control systems and various types of electronic games.

LSI devices are already making themselves felt in the field of amateur electronics. It is now possible to buy a single LSI chip which, with a suitable display, makes a very nice digital voltmeter. The counter and control logic for a digital frequency meter can now be reduced to a handful of LSI chips whilst text displays can readily be produced on the domestic TV screen using a few LSI devices.

Small logic circuits and discrete transistors will not disappear however, and still have their uses in the simpler applications. It's foolish to use a microprocessor when a few simple gates will do the job, unless of course the microprocessor is already in the system somewhere. It's always a good idea to look at the simple approach first before a microprocessor or LSI chip is considered. The problems are all out there waiting to be solved so why not see if you can put those logic chips in the junk box to some good use?

SPECIAL PRODUCT REPORT—DM235

continued from page 32

The readout is a full $3\frac{1}{2}$ digit i.e.d. display with 8mm high red digits reading up to ± 1999 . The digits are bright and well formed giving a good angle of view.

The instrument is well built with most of the components on one main printed circuit board. The two halves of the plastics case are held together by several screws. The display board is mounted onto the main board.

For use in the lab it would make sense to use the a.c. mains adaptor which is built into a 13A plug. This small unit was a shade tight fitting into a standard mains socket but otherwise was satisfactory, and should repay its cost by saving on dry batteries. Rechargeable batteries are also available and can be recharged from the mains adaptor while the instrument is being used.

The advantages of a d.m.m. over the conventional analogue type is the unambiguous readings given by the digital display. Even with a mirror scale such as provided by the Avo 8 type of instrument it is difficult to obtain an accurate reading and almost impossible if you cannot stand right over the scale. The d.m.m. eliminates any parallax error as well as any misreading of ranges or scales. Against this, however, is the comparatively slow scanning rate of the DM235. It can be a little disconcerting for the newcomer to digital meters to have to wait for three or four changes of the display before the true reading is shown. With an analogue meter the reading is instantaneous. Also, if you are used to using your conventional meter to indicate maximum or minimum voltages, such as when tuning a circuit, then the digital readout will be no real substitute, as it is difficult to interpret trends.

However, taken all round the DM235 represents good value for the enthusiast and should prove to be a useful addition to his workshop test equipment.

Dick Ganderton

MAIL ORDER DEPT.

CRESCENT RADIO LTD

1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ. 01-888 3206



"FLIP"

PUSH BUTTON HEADS OR TAILS
Complete kit and full instructions supplied.
A pocket game, easy to build and great to play.
KIT PRICE = £5.25 + 8% VAT. Post free.

75 OHM

2 1/2" (57mm) LOUSPEAKER BARGAIN
This ever popular many project loudspeaker.
Only while stocks last. 65p + 12 1/2% VAT.

REAR SHELF CAR SPEAKERS

5W 8 ohm good quality car stereo
loudspeakers.
Still only £3.75 + 12 1/2% per pair.

HEAVY DUTY XOVER 2 WAY 8 OHM

A 2 way 8 ohm H/D Xover suitable
for L/S systems up to 100 watt.
Fitted with screw terminals for
input and a three position 'HF
LEVEL' switch which selects either
Flat, -3dB or -6dB.

ONLY £3.00 + 8% VAT

A CRESCENT 'SUPERBUY'
Goodmans 5" 8 ohm long throw
H/D loudspeaker.

Mounting plate is integral with L/S
chassis and has fixing holes with
centres spaced at 5 1/4" (diagonally).

ONLY £5.00 + 12 1/2% VAT



P & P. Orders up to £5, add 30p. Orders
£5-£10, add 50p. All orders over £10
post free! Please add V.A.T. as shown.
S.A.E. with all enquiries please.



Personal callers welcome at: 21 Green Lanes, Palmers Green N13.
Also 13 South Mall, Edmonton Green, Edmonton.

LOUDSPEAKERS + 12 1/2% VAT

2 1/2" (57mm) 8 ohm 90p
5" 8 ohm Ceramic £1.50
8" "ELAC" 8 ohm 15W dual
cone £5.00
8" "GOODMANS" 'Audiom
8PA' 8 ohm 15W £4.95
7" x 4" 8 ohm 4W £2.00

EFFECTS PROJECTOR "150"

Ideal for disco work, this versatile
low price machine, is of a sturdy
metal construction. Comes com-
plete with bulb (150 watt) and 6"
Liquid Wheel.

A must for parties, the ideal
machine to set the mood for your
music.

ONLY £37.50 + 8% VAT

LOUDSPEAKERS + 8% VAT

12" "McKENZIE" 8 ohm 75W
Bass £23.62
12" "McKENZIE" 8 ohm 75W dual
cone £23.62
12" "McKENZIE" 8 ohm 75W
general purpose £18.75
12" "GOODMANS" 'Audiom 12P'
8 ohm 50W £23.73
12" "FANE" POP 33T 16 ohm 33W
£12.92
12" "FANE" POP 50/2 16 ohm 50W
£15.70

A great Antenna and no mistake!

And even if there are mistakes—inadvertently and
without any intent to confuse—our JOYSTICK VFA
remains good value for money—giving continuous
coverage 0.5–30 MHz in a space saving package (only
7' 6" long) installed anywhere, instantly ready for use.

We do, however, have to apologise for errors in published
prices in PW for December—the correct prices appear in
this issue.

In use by Amateur Transmitting and SWL Stations world-
wide and in government communication.

JOYSTICK ANTENNAS

SYSTEM "A"

£41.00

200 w. p.e.p. OR for the SWL

SYSTEM "J"

£47.95

500 w. p.e.p. (improved 'Q' on receive)

"PACKAGE DEALS"

COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all
necessary cables, matching communication headphones. Delivery
Securicor our risk. ASSEMBLED IN SECONDS. You SAVE £14.15 on
each PACKAGE DEAL!

PACKAGE No. 1

Features R.300 Rx.

£222.00

PACKAGE No. 2

Features FRG7 Rx.

£237.45

PACKAGE No. 3

Features SRX30 Rx.

£212.45

PACKAGE No. 4

Our "Rolls"—Rx. FRG7000

£402.00

RECEIVERS ONLY

R.300	£184.50	FRG7	£199.95
SRX30	£174.95	FRG7000	£364.50

All prices are correct at time of going to press
and include VAT at 12 1/2% and carriage.



Just telephone
your card number
Phone 0843 62535 (ext.5)
(or 62839 after
office hours)



or write for details, send 9p stamp

G3CED



G3VFA

5, Partridge House, Prospect Road, Broadstairs,
CT10 1LD. (Callers by appointment).

the MIGHTY MIDGETS



MINIATURE

SOLDERING IRONS AND ACCESSORIES



	RETAIL PRICE each inc. v.a.t.	POSTAGE extra.
18 WATT IRON inc. No. 20 BIT	£3.78	22p
SPARE BITS	44p	—
STANDS	£3.25	65p
SOLDER: SAVBIT 20'	52p	9p
" 10'	26p	4p
LOWMELT 10'	65p	9p
I.C. DESOLDERING BIT	88p	9p

BIT SIZES: No. 19 (1.5 mm) No. 20 (3 mm)
No. 21 (4.5 mm) No. 22 (6 mm)

From your Local Dealer or Direct from Manufacturers

S & R BREWSTER LTD

86-88 Union St. Plymouth PL1 3HG

Tel: 0752 65011 TRADE ENQUIRIES WELCOME

PRODUCTION LINES

alan martin

High power batteries

A new heavy-duty battery has been added to the range of transistor and high-power types from the Vidor division of Crompton Parkinson Ltd., a Hawker Siddeley company.

The new Vidor battery, which is known as the VT3C, is identical in size to the "small" transistor type currently available. It has been designed for use in portable electronic and electrical equipment and is particularly suitable for heavy-duty applications where sustained high power is required.

Typical applications for the VT3C include calculators, TV games, toys, remote TV programme selectors and small battery-powered domestic appliances.

The new VT3C complements the recently introduced HP7C calculator battery. *Crompton Parkinson Ltd., 50/52 Marefair, Northampton NN1 1NY. Tel: (0604) 30201.*

Alarm watch

If you feel like treating yourself to a really nice present, the Casio Alarm watch (25CS-14B) should fit the bill.

Presented with a superb stainless steel case and strap, the watch displays in the normal time mode—hours, minutes, seconds, a.m./p.m. and day, with a claimed accuracy of ± 10 seconds per month.

The calendar mode displays day, date, month, year and is pre-programmed until the year 2009.

Also the watch features an alarm facility with a rather piercing voice.

Powered by one silver oxide battery (type UCC393) with an operating life of approx. 15 months, calculated on the basis of 5 pushes of the light button per day for 1 second duration each, and the alarm running for 60 seconds.

The recommended retail price is £74.95, but Tempus offer the watch at a discounted price of £59.95 which includes VAT. *Tempus, Dept. PW, 19/21 Fitzroy Street, Cambridge CB1 1EH. Tel: 0223 312866.*



Every month is the right frequency

When you're building a major project from a PW design, you want to be sure of getting every issue in sequence! Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) U.K. £10.60. Overseas £10.60.

**practical
WIRELESS**

SUBSCRIPTION ORDER FORM

Please send me Practical Wireless each month for one year. I enclose a Sterling cheque/international money order for..... (amount),

PLEASE USE BLOCK LETTERS


NAME Mr/Mrs/Miss.....

ADDRESS.....

POSTCODE.....

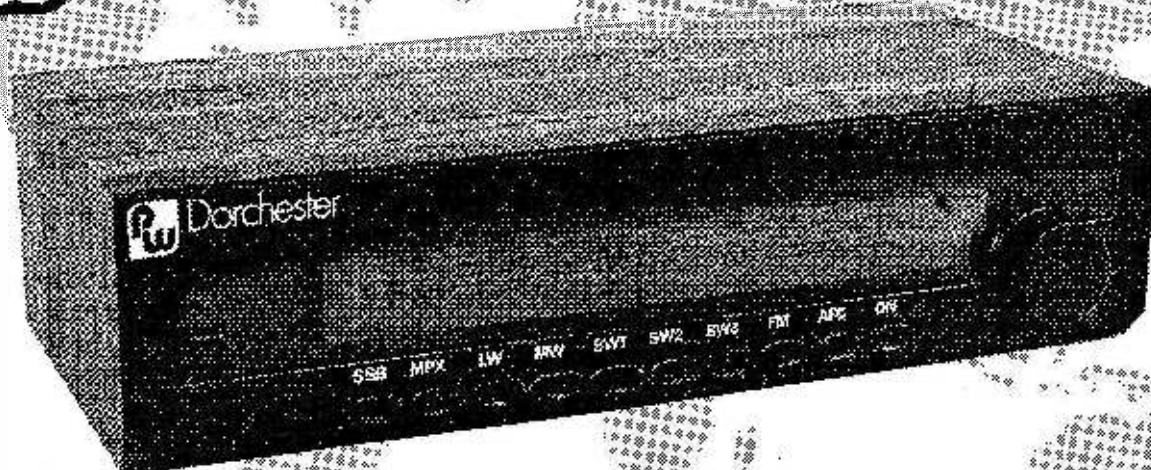Make your crossed cheque/MO payable to IPC Magazines Ltd., and post to: Practical Wireless, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.





ALL-BAND TUNER

W.S. POEL

This part deals with the extensions and accessories that you may wish to consider in connection with the "Dorchester" tunerboard, some of which are likely to be methods of housing, powering and tuning the receiver, in a manner which will not disgrace your sitting room.

The case housing the Author's unit was modified from parts used for a commercial design which is no longer produced. In this way, a professional standard of presentation, with a neatly sculptured front panel and proven mechanics were available instead of the usual combination of folded aluminium and Dymo tape.

The basic mechanical layout of the prototype is given in Fig. 11: subsequent versions had the chassis deepened slightly to accommodate the tuner with a little more ease. An extension shaft is required which is fitted to the tuning capacitor spindle and held rigid by means of a bush mounted on a bracket.

The tested tuner board—remember not to expect a completely un-ried unit to work first time, no matter how carefully you may have constructed it—is fitted to the base plate by means of pillars mounted in the bottom of the chassis. The Author prefers spacers which are

designed for use with self-tapping screws so that the pillars are fixed down independently of the tuner board. The approach whereby the bolt is simultaneously passed through a pillar and fixed through the p.c.b. is usually frustrating and tedious to perform.

Tuner Power Supply

This unit (Fig. 12) is simply a mains transformer, followed by a rectifier and three-terminal voltage regulator from the 7812 series, or the SGS TDA1412. Radio frequency interference from this type of regulator needs to be suppressed with additional filtering circuitry, so note the extra decoupling.

The current-handling capacity of the power supply needs to be about 150mA—but in the prototype, a degree of headroom has been left, so that the illumination of the meter and tuning scale may be included. Before you consider attaching any sort of audio power amplification to the tuner supply, make absolutely certain that there is sufficient reserve to prevent the voltage from falling below the minimum at which regulation takes place.

Where a steel chassis is used, it is desirable to mount the ferrite rod antenna on the back panel (outside) or the efficiency will be greatly impaired. There are various methods employed in commercial designs, the most elegant of which is to mount the rod in a non-ferrous tube on some form of infinitely-adjustable pivot so that the angle may be adjusted to the user's requirements. A long wire antenna coupled to the rod tends to reduce directional effects and can be the conveyor of problems arising from one of the many thousands of sources of r.f.i. This design makes a simple approach, using proprietary parts and tubing—since it seems the more intricate mechanical arrangements are exclusively customised to individual manufacturers' specifications.

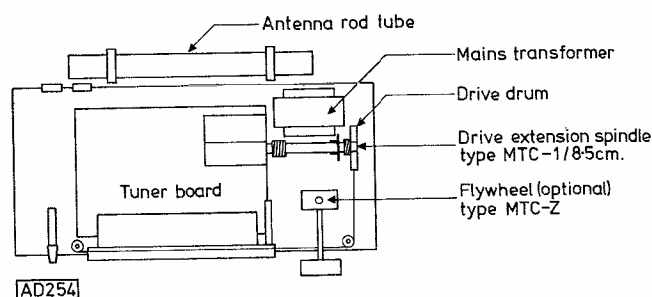


Fig. 11: Mechanical layout of the tuner

Coverage and Sensitivity

In the Author's prototype, SW3 was restricted to a maximum of approximately 22MHz. In this way, the main broadcast bands are given a bit more spread on the dial. No modification of the circuit is necessary, since the adjustment is simply carried out using the trimming adjustments of capacitors and tuning slugs.

A preselector is frequently suggested for use in conjunction with receivers that are to be fed with nondescript antenna arrangements and have broad coverage—and before considering a suitable design here, it is very important to bear in mind that gain and h.f. receivers are not necessarily the best of companions. Certainly everyone likes to think their set can resolve s.s.b. below 1 μ V, but then, there isn't much point if the set overloads when another station a few kilohertz away flattens the whole thing with a 1mV input!

The basic tuner has excellent sensitivity for a unit of this type—a broadcast transmission receiver, first and foremost. An antenna of some twenty feet in length proved to be more than adequate, so before getting carried away with antennae it must be borne in mind that some selectivity in the tuner is called for, to limit cross-modulation of the mixer by strong adjacent channels.

The average casual listener usually has a length of wire for an antenna, and as far as receiving is concerned, this can be turned into a beautifully effective and versatile arrangement with a simple pi-network tuner. Various designs have been featured over the years (Fig. 13 shows two examples) and so we will not go into too much detail here. By switching coil taps at various positions along an inductor, almost any piece of wire can be tuned to resonance at h.f. Wires that are much shorter than a wavelength tend to exhibit a high impedance—and the pi-network is one of the best ways of matching.

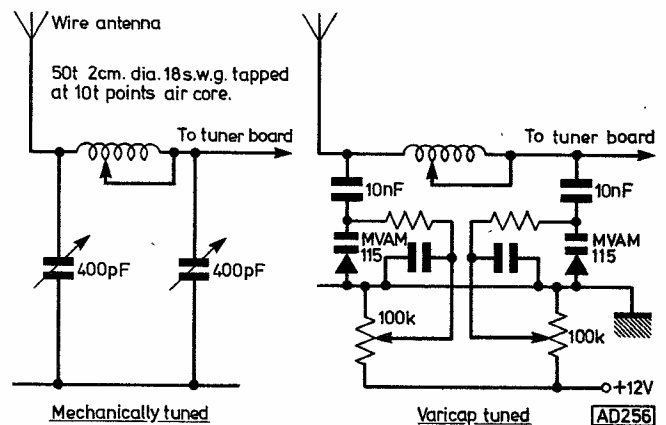


Fig. 13: Typical pi-network aerial tuning arrangements with (left) ganged variable capacitor and (right) varicap diodes

If you still want more gain with your tuner, then the circuit of Fig. 14 is suitable, but remember that the gain control is not merely an adornment, but a necessity—since the preselector may be used as a tuned attenuator when things get out of hand simply by backing-off the gain control.

If you are a keen s.w.l. then a digital frequency-readout is a virtual must these days. The recently-published PW design will readily suit this receiver. Take the oscillator from pin 20 of the i.c.—or by f.e.t. buffering from the oscillator section of the tuning capacitor.


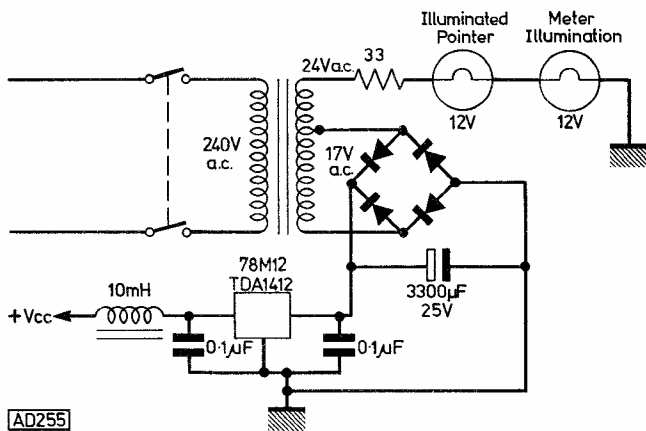


Fig. 12: Power supply arrangements

In stretching the wiring feeding the ferrite rod, the possibility of extraneous pickup on the coupling leads has been greatly increased, so this wiring must be tightly wound and kept to an absolute minimum. It is not feasible to use fully screened connections of this length, since their additional capacitance would restrict the necessary bandwidth.

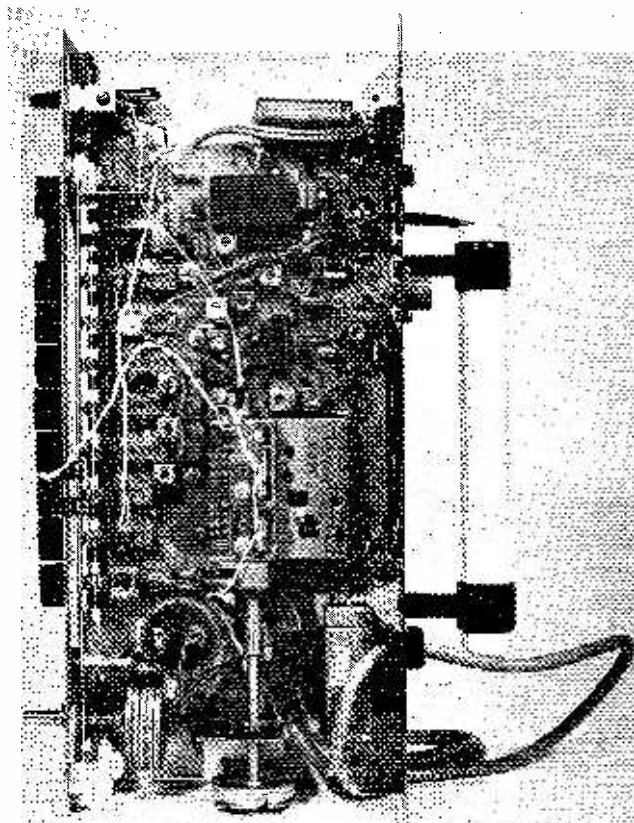Remember to secure the coils on the rod when you have adjusted them. This should be carried out whilst the rod is in place at the rear of the chassis, since the presence of adjacent metal will tend to modify the aerial tuning characteristics somewhat.



A view of the completed unit prior to the outer case being fitted

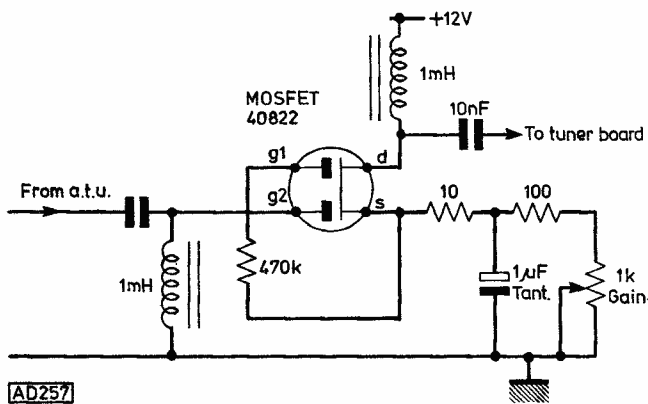


Fig. 14: R.F. pre-amplifier

Audio

Some readers may wish to include audio amplification within the tuner—and the many i.c.s that exist to fulfil this requirement scarcely need additional comment here. However, there is one point to watch, and that is the almost universal tendency of such amplifiers to exhibit h.f. oscillation at their output. Remember to decouple the power supply carefully—and feed the loudspeaker/headphones using screened audio cable, taking care to follow manufacturers' recommendations concerning Zobel networks, ferrite bead suppressors, etc. The high gain of the tuner makes it susceptible even to quite low levels of spurious radiation that most applications could quite easily ignore.

The question of using the tuner in a portable configuration was briefly discussed in the first part of this article. The main i.c. consumes a fair amount of current for this application—especially in the a.m., mode; but in f.m. the consumption reaches around 23mA, with another 12mA for the tunerhead. This is not necessarily unreasonable by modern standards, and indeed, many of the larger portables have a much higher consumption.

Thus the unit makes the basis of a very fine portable. The really superfluous part of the circuit would then be the stereo decoder, for however desirable the idea of a stereo portable may seem, it is usually a wasteful extravagance. In units incorporating mains/external 12V options, the decoder arrangement should be locked out when the internal batteries are used. All scale lighting functions should be wired so that they only illuminate on the operation of biased switch or pushbutton.


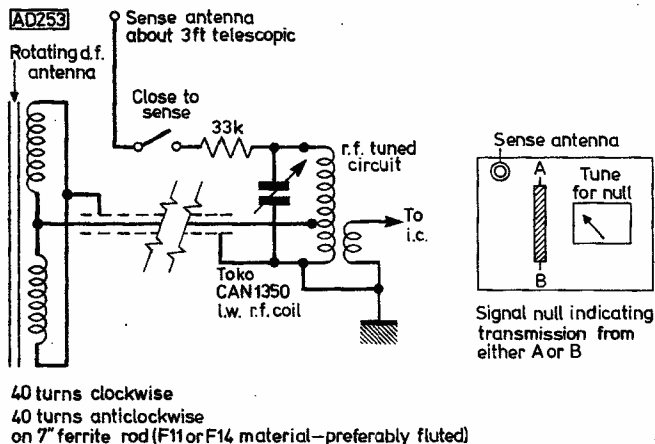


Fig. 15: Typical arrangements when direction-finding facilities are to be incorporated


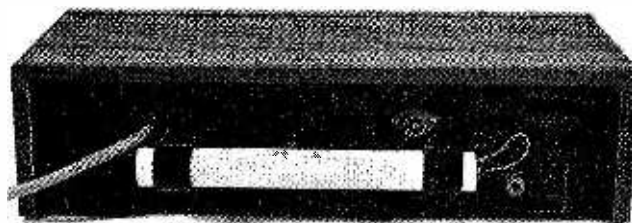


A rear view of the Dorchester showing the ferrite rod aerial and other connections

The question of direction-finding has recently been raised, and since the nautical and aero transmissions are located in the only section omitted from the standard broadcast range of 175kHz to 30MHz (250–400kHz approx.) one of the s.w. bands has to be sacrificed if the facility is to be accommodated. This will probably be SW3 and oscillator coil is changed for a 632μH DF band type. The antenna coil is also changed, and a second ferrite rod antenna for the DF band fitted—or, as an alternative, the “loopstick” arrangement used to permit sensing of the rod position relative to the transmission (Fig. 15).

The tuned circuit for DF is then the l.w. r.f. coil, with the DF rod coupled to the tap.

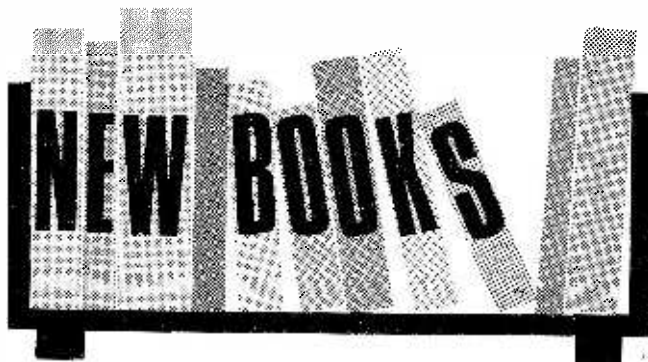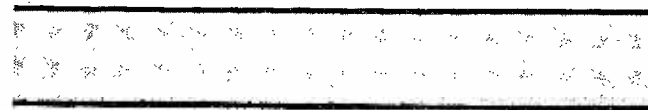Work on DF applications is far from finalised as yet, but if sufficient reader-interest is apparent, then further developments will be published at a later date.



ELECTRONICS—an elementary introduction for beginners

by L. W. Owers

Published by Talbot House Press

Freeland, Oxford OX7 2AP


119 pages. 209 × 149mm. Price £2.95

This book sets out to give a broad introduction to the subject of electronics, providing a background for more advanced study. This is achieved well, starting with the discovery of electric charge and ending with semiconductors.

Moving away from electrostatics into the realm of moving charges and conduction we meet resistors, capacitors and inductors, progressing through valves and the cathode ray tube into semiconductors and the doping of semiconductor materials to form transistors and integrated circuits.

The whole book is well illustrated with some excellent diagrams which are available as 35mm slides for teaching purposes.

KA

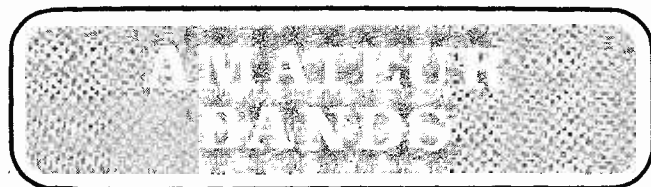

by Eric Dowdeswell G4AR

The business of listening on the amateur bands ought to be more than just a matter of entering long lists of stations in the log. After some months it will become apparent that there is a definite pattern to the times at which stations in different parts of the world appear on the various bands.

I have mentioned this before as a means of understanding the mechanics of the propagation of radio signals in connection with the 11-year sunspot cycle. However there is another aspect which should not be overlooked. Since none of us have unlimited time to spare listening or working on the air, it is essential that the time we do have available is well-spent.

The newly-licensed amateur whether a G4 or a G8 is going to waste an awful lot of time if the optimum band or mode is not chosen as a result of experience gained as a listener. The tyro may call CQ for hours without a reply on a dead band or use the wrong mode for a particular part of a band.

On the h.f. bands a note should be kept of prefixes and when they are heard, at what time and which band, to build up a picture over a year or so. If a band is found to be dead then note it and check all bands if possible, whenever sitting down to listen.

For the listener who is able to copy c.w., check the c.w. end of each band as it is strange how often there is activity there when the s.s.b. part is comparatively dead. In contest work the listener and the transmitting amateur can perform much more efficiently by choosing the right band to work on at any given time. In days gone by I would always watch the bands for a couple of weeks before a big international contest just to get the feel of them, noting when the more elusive countries and prefixes were coming in well, band by band.

Then an operating schedule was compiled of bands against time for 24 hours thus giving two "windows" for working a particular DX station in a 48 hour contest, all aimed at reducing unnecessary operating to a minimum. This resulted on one occasion in being able to work 99 countries on c.w. in a weekend contest using all bands from 3.5 to 28MHz.

It will be noted that occasionally signals from the west coast of the US and from VK are audible in the early morning and late afternoon due to short and long path propagation, thus doubling the possible openings for working or copying stations in these areas.

On the Bands

In spite of our most welcome Indian summer the change to winter conditions has gone on apace on the h.f. bands, exemplified by reports from readers such as **Ian Marquis** A9140 of Leigh-on-Sea, Essex, who copied CT2, EA6, EA8, JA, VP2 and 9K2 on 80m s.s.b. Ian's FRG-7 and long wire also found the extremely rare Willis Island in the form of VK9ZM on 20m, in the DX Net on 14 265kHz. 15m revealed another new country in KV4KV/D on Deception Island, plus W0DX/D on c.w. on 10m, part of the same set-up there.

Richard Smith in Porthcawl, S. Wales, has forsaken his old and trusty t.r.f. set for a KW77 and is particularly glad to find it incorporates a crystal calibrator. He plans to put a 2m converter in front to get the feel of the v.h.f. world before he takes his RAE in the not too distant future. Richard found a 5Y3 and 7X2 on 80m so let's hope this is a sign of more good stuff to come from that direction. African activity has always been low on the l.f. bands due to the high level of static experienced there. It's something that has to be experienced to be believed!

SSTV has captured the imagination of **Simon Robinson** in Stocksfield, Northumberland, and now G8POO. Using an MK Electronics monitor he has seen DL, OZ, I, EA and OK stations, using a 10in diagonal c.r.t. The only call of interest on 10m s.s.b. was JW7FD on Bear Island.

Rod Hunt (Darlington) sticks with his t.r.f. rig and to date has logged over 80 countries on it, mainly on 21 and 28MHz. The latter band has come up with DX such as JW7, ZP5, with 21 producing EA0, HP0, ZB2DV (G4EMR on holiday!), ZL1, 3D6 and 9J2. Rod has started his own RAE course and is not neglecting to get some practice in on the key, while a G3 "on the other side of the hill" is giving advice and assistance.

Loft aerials for **Bob Bell** in Blyth, Northumberland, means sloping tubular ones with coils to load to a particular band but due to the awkwardness of the set-up it's all likely to finish up in the garden very soon! Bob found PY0EG on 20m s.s.b. and an early morning session provided VK 7, not heard too often, ZL4 and VK5.

Not a very exciting month for **Bill Rendell** of Truro but KG4KG in Guantanamo Bay is a rare bird on 20m s.s.b., with KC6GF a good find. Bill also intends dumping his attic aerials and getting something up outside. **Allan Stevens** is still plugging on with his *PW* direct conversion set plus PR40 preselector and has notched up 81 countries so far including excellent find VR6TC on Pitcairn, a real rarity.

In Oswestry, Salop, 14-year-old **David Wyatt** has moved to the amateur bands with his home-brew 4-transistor superhet plus audio amp and b.f.o. Prefixes like HH and HP and another KG4 aren't bad on 20m but an AR88 is in the pipeline. **John and Steven Goodier** have been struggling over the rig trying to decide on BC or amateur bands and I'm glad to report that the latter has won the day! Reports to follow regularly now, I gather. They've been looking for LU3ZY on South Sandwich but no-one seems to have heard them yet. J and S have an FRG-7 and 30ft wire so it can't be the rig.

With the Clubs

Barking Radio & Electronics Society is on a recruitment drive and meets, wait for it, **FOUR** nights a week, Monday to Thursday. Morse classes Tuesdays and main club night Thursdays, all at 1930. Stations G3XBF and G8GPK are active on h.f. and v.h.f. but club activity tends to favour v.h.f. at the moment, hopefully to be redressed very soon! So pop along to the Westbury Recreation Centre, Westbury School, Ripple Road, Barking, Essex some time or contact Sec Nick Dowsett G8PUY, 44 St Ann's, Barking, Essex.

Every Tuesday sees the **Bury RS** hard at work at Mosses Centre, Cecil Street at 1930 onwards with RAE classes at nearby College of FE. 9 Jan has G2BTO on TVI and the Amateur, with G4CLF holding forth on the SL600 series of i.c.s on 13 Feb. The subject on 13 March is v.h.f. linear amps with G8NOF covering Orbiting Satellites on 10 April so there's plenty to look forward to at Bury RS. Write to Eric Thirkell G4FQE, 59 Oulder Hill Drive, Rochdale.

It's all go, down with the Wessex AR Group with a proposal to revert to the old title of the Bournemouth ARS, similar to the society that was first formed there in 1922. As an outsider I heartily approve! Don't like changes that cause a group to lose its identity! Meetings are held at the Dolphin Hotel, Holdenhurst Road, Bournemouth at 1930 hours. Friday 19 Jan sees G2YH talking and demonstrating miniature v.h.f. transmitting devices while 2 February is devoted to "Planning and Preparation for HF and VHF Contests". Note new QTH of Sec/Editor Geoff Cole G4EMN 3A Cavendish Road, Bournemouth or ring 20027.

Log Extracts

R. Bell:—20m PY0EG 20m VK7AZ 15m JR3IIR

S. & J. Goodier:—20m CE0AE HK0QA (San Andres) KG6SW KJ6BZ VK2AGT (L. Howe Is) VK9ZM (Willis Is) VK9ZR (Mellish Reef) VP2EEK VP2GVI VP5BD VR6TC ZK1CV

D. Wyatt:—80m VO1FG 20m CT2CB HH2SD HP1XDN KG4EP

A. Stevens:—20m JW7FD (Svalbard) VE8RCS VK7AZ VR6TC WA4YUG/VQ9 (Diego Garcia)

W. Rendell:—20m CT2BQ HR1JAG KC6GF KG4KG VK7AE VP2AW 15m C5ABK HV3SJ KZ5BA ZB2DV 10m CT2SH HK4DF


I. Marquis:—80m CT2QN EA8CR JA6BSM VP2SD 9K2IX 20m PJ8CO VK9ZM VP2VER 15m EA9EO JW7FD KV4KV/D (Deception Is) TA1DF 10m EP2SL FG0EID/FS VS6FE W0DX/D (Deception Is) YJ8KM

R. Smith:—80m 5Y3GT 7X2DG 40m EA8CR 20m CT3AC S79MC VP8PF 15m AP2KS 10m EL2AG

S. Robinson:—SSTV 20m DL6HP OZ2ARD I2II EA2JO OL7VI 10m JW7FD

R. Hunt:—15m EA0NS HP0ED ZB2DV 3D6BP 10m JW7FD ZP5AO 9K2DR

All s.s.b. unless indicated otherwise.

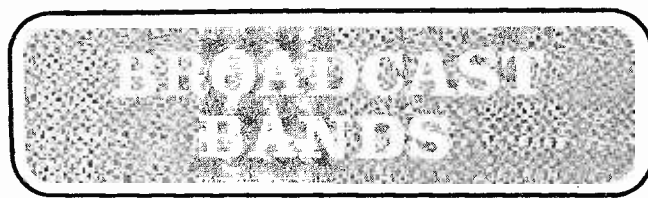

MEDIUM WAVE DX

by **Charles Molloy G8BUS**

This is the time of year to listen to North America on the medium waves. Although reception is possible at any time of year it is in the winter when the nights are long that one can pick up a few local broadcasts from across the Atlantic before going to bed. Listen between 2300 and midnight, as European interference begins to subside for CKVO in Clarendville, Newfoundland on 710kHz, CJYQ in St John's, Newfoundland on 930, WINS in New York City on 1010 and WNEW also in New York on 1130. These are but a few of the many North Americans that can be picked up in the UK when conditions are favourable but be careful. All transatlantic signals are subject to slow fading and it is very easy to pass over quite a strong signal that is temporarily in the minimum of a fading cycle. So tune carefully and slowly. The path is not always open and fadeouts do occur at times so if you are unsuccessful at first then try again a few nights later.

North American Medium Wave Stations

There should be no problem identifying North American DX, for nearly all broadcasts are in English and all, without exception, are issued with callsigns which the stations are obliged to use when they identify themselves. In the United States the callsigns are either of four or three letters which begin with a W or a K. For example, WINS is the call of the station on 1010kHz located in New York while KDKA on 1020 is in Pittsburg. Similarly in Canada where the prefix is C, or V in the case of a few outlets in Newfoundland.

The station separation in North America is 10kHz instead of the 9kHz we have in Europe and each channel is also a multiple of 10kHz which means that the band is divided up into 107 "channels" starting at 540kHz and ending at 1600kHz. It is a lot easier to use kHz instead of metres when dealing with North Americans and receivers in that part of the world are often marked from 54 to 160, i.e., with channels 54 to 160.

North Americans are usually good verifiers, that is of course if you send them an accurate reception report. The time to gather material for the report is just before the hour and the half hour when commercials (jingles),

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segers Lane, Southport, PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BR515744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

weather reports, news items and station identification takes place. The reports themselves should be sent to the chief engineer of the station and the address should include the call letters of the station and the town or city mentioned in the announcement. For example, The Chief Engineer, WNEW Radio, New York City, NY, USA will certainly find the station on 1130kHz.

Loops and Aerials

Although the standard 40in box loop has a single turn for the coupling winding it is worth experimenting a bit to find out what suits your particular receiver best. This point is highlighted by **Harold Emblem** (Mirfield) who tried the effect of using two turns instead of one with a Lafayette HA63 receiver a few years ago. The two turns gave much better results with this receiver. Harold thinks it is worthwhile trying a second turn to see if there is any significant improvement and also the adjustment of the position of the two turns is worthwhile.

Shortwave DXer **J. F. Porter** of Belfast would like to listen to some medium wave DX and he wonders if a ferrite rod aerial could be used as a substitute for a loop. The pick-up of a ferrite rod aerial is really too small for serious DXing. I have played about with ferrite rods (see July 1978 *PW*) and they can be useful for semi-DX but this is really the field for someone who likes experimenting rather than hearing DX. There is nothing wrong with an FRG-7 plus Joystick or 100ft long wire for m.w. DXing and if you want a substitute for a full size loop then try Bob Bell's half size loop (Nov. 1978 *PW*).

Beacons

Although the medium waves are supposed to be used exclusively for broadcasting there are a small number of navigation beacons that operate inside the band at the low frequency end. In answer to **E. C. Adams**, this is probably what you are hearing around 460 metres. Navigation beacons have call signs which are repeated in Morse and the majority of them operate on the long waves on frequencies between the long and medium wave broadcasting bands. The third harmonics of some of these beacons occasionally appear on the medium waves to cause QRM with broadcasting stations and to mystify the DXer. Sometimes these harmonics can travel a considerable distance, much farther than the fundamental. For a number of years, using several different receivers, I have picked up the call SW (... ---) on approx 930kHz while listening to CJON (now CJYQ). There is an SW on 310kHz situated at the Cabo de Santa Marta Grande lighthouse on the north-west coast of Brazil which transmits with a power of 0.5kW (fundamental) and it is interesting to speculate whether it really is the tiny third harmonic of this beacon that we hear as QRM on CJYQ.

Readers' Letters


A number of interesting loggings of stations in the USSR come from **Bob Bell** in Blyth who uses an FRG-7 receiver and a mini (half-sized) loop. These are Kharkov on 836 (837), Stavropol 881, Arkhangelsk 908, Tallin 1034 (1035), Yoshkar Ola 1061 (1062), Baku on 1295 and an unidentified station on 1525. The frequencies are pre-Geneva Plan and those in brackets are the new ones where known. The station on 1525kHz may in fact be in China even though the language was Russian and there is often jamming to be heard on this unauthorised channel. Bob is willing to supply information and to advise anyone who is genuinely interested in his half-size loop. Letters

should go direct to Bob at 5 Byron Avenue, Blyth, Northumberland NE24 5RN with, I would hope, a stamped addressed envelope for a reply.

News of Manx Radio comes from **Douglas Gibb** (Selkirk) who heard their test transmission on 1368kHz last September. This local station is now full-time on the new frequency and the 219 Times gives details of their broadcasts. It is available from Manx Radio, Broadcasting House, Douglas, IOM which is also the address for reception reports. Manx Radio will QSL by return.

Some countries are easier to hear on the medium or long waves than on the short waves and this has been noted by **David Wyatt** of Oswestry who logged Radio Andorra on 710kHz. He received a QSL in three weeks in answer to a report made out in French. On the long waves he picked up Radio Algeria in English on 251kHz at 2025, another country he had not been able to hear. The receiver in use is a 1947 Kolster Brande BR20 and a 90ft long wire. These older domestic sets often perform very well on the medium waves especially when used with a loop. Why not try this before looking for another receiver; it is possible to use low impedance phones in place of the loudspeaker. Be careful though to keep away from the chassis which may be live.

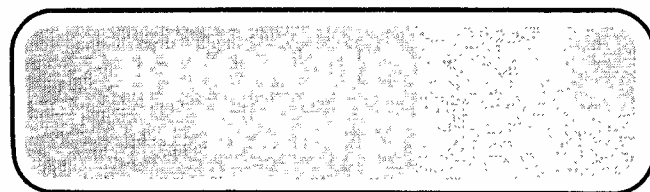Sweden Calling DXers is now on a second frequency on the medium waves as the transmitter at Gothenburg on 991kHz has been allocated to the foreign service during the evening according to a station announcement. A final item from **Ian Rennison** (Horsham) who has logged Radio Paradise, St Kitts on 1265kHz at 0014, details of receiver, etc., not given.



SHORT-WAVE BROADCASTS

by Charles Molloy G8BUS

The majority of short-wave receivers tune from 6MHz to 18MHz, a range which includes six international broadcast bands. These are the 49 metre band (6MHz), 41m (7MHz), 31m (9MHz), 25m (11MHz), 19m (15MHz) and 16m (18MHz). There are also the 13 metre band (21MHz), the 11m band (26MHz) and the 75m band (4MHz) which are within the range of some receivers. It is traditional to quote a band by its wavelength in metres and the individual station within the band by its frequency in kilohertz (kHz) but there is a trend these days to refer to a band by the frequency in megahertz (MHz) and this is the figure shown in brackets. The 49m band for example can also be referred to as the 6MHz band. The relationship between MHz and kHz is quite simple. 1MHz is the same as 1000kHz. Radio Nederland is on 6020kHz in the 49m band but it may appear on 6.02MHz on some receivers.

Short-wave reception is entirely by means of the sky wave, which is reflected by the ionosphere many miles above the surface of the earth. The sky wave is influenced by the amount of daylight between transmitter and

receiver. The more daylight the higher the frequency that may be used. DX is possible on the highest frequencies during the day and on lower frequencies after dark. Short range reception is on lower frequencies by day and either 75m or the medium waves by night. In general, the frequency in use over any particular path will be higher during the day than after dark. In order to help beginners to find their way about the different bands it might be useful to have a look at each one in turn to see what sort of DX can be found there, starting this month with 25m.

25 Metre band

The 25m band has official limits of 11 700kHz to 11 975kHz, though in practice stations are to be found between 11 600kHz and 12 100kHz. There is something to be heard on 25m at any time of the day or night or during any season of the year and for that reason it is a good place for the newcomer. Last autumn the Radio Japan relay in Sines Portugal could be heard on 11 825kHz from 2200 to 2230, but after sign-off the much weaker Voice of Free China in Taiwan could be heard in English in its place, so always investigate weak signals.

During the day, look for distant broadcasts from Radio Pakistan on 11 640kHz, Radio Australia 11 760 and 11 900, Madagascar 11 730, Bonaire 11 790, Kuwait 12 085. Medium range stations that can be heard are Vatican Radio 11 740, Finland 11 755, Spain 11 815, Austria 11 855, Norway 11 865, Budapest 11 910, Greece 11 925 and Bucharest on 11 940. Latin America appears on 25m during the evening. Look for Radio Guaiba on 11 785, Radio Globo 11 805, Pernambuco on 11 865, all of them being in Brazil, and Radio Habana Cuba on 11 760. Other DX that may be heard at this time are WFYR Family Radio USA on 11 805, ELWA Liberia 11 835, Canary Islands 11 880, Radio Bamako in Mali on 11 960 and Radio Abidjan Ivory Coast on 11 920. Broadcasters on the short waves often move around and some of the frequencies mentioned may change but the list is typical of what a DXer may hope to hear without too much difficulty on the 25m band.

Readers' Letters

Sean Stray of Market Harborough (details of receiver and aerial not mentioned) reports some useful DX heard during his recent half term holiday. Radio Japan is a regular on 21 535kHz in the 13m band between 0800 and 0830. The signal is weak but clear of interference but a curious echo effect was observed, probably the result of propagation along different paths through the ionosphere. Radio Nacional Argentina was logged on 11 715 in the 25m band at 2320 and the address for reception reports is RAE Ayacucho 1556, 1000 Buenos Aires, Argentina. Riyadh in Saudi Arabia was picked up at fair strength at 1930 the address to write to being Ministry of P and T, Riyadh, Saudi Arabia. An unidentified with the call Radio Tinian (not Tirana) was heard on the 25m band at 2145. Has anyone any ideas on this?

A signal like a short burst of machine-gun fire is reported by **T. M. Headley** of Seaford in Sussex who has started listening on the short waves again after an absence of many years. This is over-the-horizon radar which can be heard all over the short waves and was the subject of international complaints to the USSR a year or two ago. A Sanyo RP8700 portable communications receiver which was a present from USA is in use by 13-year-old **Paul Cox**

of Twickenham. When used with a 70ft long wire this rig pulled in Delhi on 11 740 at 2125 SIO 544, Radio Kuwait 12 085 at 1940 SIO 544 and Radio Japan on 17 820 at 0715 SIO 344. From Walsall comes another report of reception of R. Japan on 17 820 from **Craig Kelly** who used a t.r.f. receiver and 75ft long wire. Craig asks for identification of a station playing guitar music but he forgot to mention the frequency or band concerned. Requests for identification should contain as much detail as possible including the frequency, date, time and station announcement and the language used.

Tropical Bands

From Blyth in Northumberland comes an interesting log compiled by **Bob Bell** using his FRG-7 and home-made vertical antenna. On the 60m band he heard USSR (unid) on 4775kHz at 0255, Radio Lara Venezuela on 4800 at 0300, Radio Luz y Vida in Ecuador on 4800 at 0405, plus Radio Nacional Canaries on 11 880 in the 25m band at 1400. A Vega 206 plus 20ft outdoor aerial are in use by **Bill Stevenson** who heard Radio Yaounde Cameroon in French on 4850 at 0430 SIO 333, Radio N'Djamena Chad also in French on 4905 at 0430 sign-on SIO 333 and Radio Nigeria in English on 4990 at 0430 SIO 333, all on 60m. Bill has built an r.f. pre-amp for use with his receiver but it does not give good results. The symptoms are of overloading. Bill would be interested to hear from other Vega 206 users. Replies direct to him at 10 Crompton St, Swinton, Lancs.

Reception Reports

A DX Press Release from Radio Finland makes disturbing reading for the DXer. This station has stopped using QSL cards. In their place there will be audience cards with a different card for each month of the year. The new cards will not confirm the date, time or frequency and will therefore only be an acknowledgment of the listener's letter.

The reasons for the change are interesting. Radio Finland gets about 300 reception reports a week and to quote the press release "you could say we were keener to receive programme comments". Of course, if they stop issuing QSLs then they may not get any reports at all and a better policy surely would be to restrict QSLs to reports that are of real value to the station. None-the-less the point of view expressed by Radio Finland is a valid one. A short-wave station transmits a programme for its audience to listen to rather than a signal for DXers to pick up and DXers should bear this in mind when writing to a station. Perhaps if DXers were to include comment on the programme heard and how it compares with other stations, which apparently is what Radio Finland wants, in addition of course to the reception reports, then everyone would be satisfied. The "powers that be" at Radio Sweden, according to a recent broadcast from that station, feel they have few listeners but many DXers for an audience and this might be a prelude to another attempt to cut back the popular Sweden Calling DXers. Radio RSA has reduced its English transmission and cancelled its DX Corner, so abruptly that the editor Gerry Wood did not even have the chance to say goodbye. The future for DXers does not look too good at the moment. On a lighter note. A DXer who recently sent a report to a Middle East country received the reply "Don't you have radio in your country, why you listen to ours?"

MK14-the only low-cost keyboard-addressable microcomputer!

The new Science of Cambridge MK14 Microcomputer kit

The MK14 National Semiconductor Scamp based Microcomputer Kit gives you the power and performance of a professional keyboard-addressable unit - for less than half the normal price. It has a specification that makes it perfect for the engineer who needs to keep up to date with digital systems or for use in school science departments. It's ideal for hobbyists and amateur electronics enthusiasts, too.

But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

MK14 Specification

- ★ Hexadecimal keyboard
- ★ 8-digit, 7-segment LED display
- ★ 512 x 8 Prom, containing monitor program and interface instructions
- ★ 256 bytes of RAM
- ★ 4MHz crystal
- ★ 5V stabiliser
- ★ Single 6V power supply
- ★ Space available for extra 256 byte RAM and 16 port I/O
- ★ Edge connector access to all data lines and I/O ports

Free Manual

Every MK14 Microcomputer kit includes a free Training Manual. It contains



Just
£39.95
(+ £3.20 VAT, and p&p)

operational instructions and examples for training applications, and numerous programs including math routines (square root, etc) digital alarm clock, single-step music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings. Further software packages, including serial interface to TTY and cassette, are available, and are regularly supplemented.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

Tomorrow's technology - today!

"It is not unreasonable to assume that within the next five years... there will be hardly any companies engaged in electronics that are not using micro-processors in one area or another."

Phil Pittman, Wireless World, Nov. 1977.

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, even purely mechanical forms of control systems.

The Science of Cambridge MK14 Standard Microcomputer Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microcomputer in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade,
Cambridge,
Cambs., CB2 1SN.

Telephone: Cambridge (0223) 311488

Regd No. 213817088.

To: Science of Cambridge Ltd,
6 Kings Parade, Cambridge,
Cambs., CB2 1SN.

Please send me an MK14 Standard
Microcomputer Kit. I enclose cheque/
Money order/PO for £43.55 (£39.95
+ 8% VAT and 40p p&p).
Allow 21 days for delivery.

Name _____

Address (please print) _____

Science of Cambridge

PW2

by Ron Ham BRS15744

What more could we v.h.f. addicts ask for than a new amateur satellite to play with, the 10m band alive with signals from all parts of the world, a tropospheric opening which sent the amateur and broadcast bands haywire, and all between mid-October and 18 November?

The 10 Metre Band

How often the new recruits to amateur radio must have heard the old hands reminiscing about the great 10m openings of the past. Well, hopefully, those good times are here again, but now, thanks to the RSGB, we have the International Beacon Project going well and it is almost a daily occurrence to hear strong signals from the beacons in Bahrain A9XC, Bermuda VP9BA, Cyprus 5B4CY, Florida N4RD and Germany DL0IGI indicating the best DX path to use.

Like many other clubs and individuals throughout the world, the Mid-Sussex Amateur Radio Society entered the CQ World Wide contest on 28/29 October from their club shack in Burgess Hill. During the event the operators, G3JMB, WPO, WYN, ZYE, G4GNX and HHB, worked almost 500 stations and more than half of these were on 10m. Afterwards, G4GNX said that conditions were so good that around 1800 on the 28th they worked 60 Ws in 45 minutes, and at 0730 on the 29th they had 16 contacts with JAs in about 20 minutes. Throughout the contest good signal reports were exchanged with stations all around the world, and N. Clarke BRS 34306, Knottingley, Yorks, logged all W call areas within one hour.

While John Branegan GM8OXQ, Saline, Fife, N. Clarke and myself kept a daily watch on the IBP signals and found that A9XC was the most consistent, closely followed by 5B4CY, DL0IGI, N4RD and VP9BA. Graham Lay, West Chilton, Alan Baker G4GNX, Newhaven and Ian Rennison, Horsham, all in Sussex, listened to the world-wide DX on 28MHz. Ian also mentioned the very strong American CB signals he heard in the 27MHz band, especially on 21 October.

Solar Activity

Although the sun has been "quiet" at 136MHz compared with the same period in 1977, a few small bursts of solar radio noise were recorded on 6, 7, 8, 11 and 13 November by John Branegan, Cmdr Henry Hatfield, Sevenoaks, John Smith, Rudgwick, Sussex and myself and, on 6 and 13 Nov., Henry saw several filaments on the sun's disc with his spectrohelioscope.

Satellites

John Branegan has completed a 6-month survey of 70cm propagation from space, based on the signals from OSCAR-8J and says "Not only is OSCAR-8J affected by propagation disturbances both in, and way above, the normal E and F regions, all 70cm satellites are affected. Attenuations of up to 20dB (not due to polarisation rotation) seem to occur regularly in two regions of the world. The most noticeable are the Denmark Strait between Iceland

and Greenland (i.e. between us and the magnetic pole) and over the equator in the South Atlantic". So far he cannot correlate these effects with solar disturbances but there is, writes John, "A positive correlation with time of day, the equatorial disturbance being most marked in the evenings".

For about 20 minutes at 1258, on 27 October, John heard the Russian amateur radio satellite, RS-1, come up over North America, heading east, and pass between his QTH and the pole. The satellite appeared again at 1502 and John accessed it on 145.890MHz (Down link 29.370MHz), called CQ and immediately a c.w. station answered, so excited that he sent John's call sign six times and forgot his own! The next pass was at 1708 when John had a good five-minute QSO with G3IOR. On the 28th he had his first transatlantic QSO via the new bird with W2BXA in New Jersey, followed by contacts with DC9II and DC9ZP. During the same orbit 5 GMs were in QSO with European stations and, that afternoon, a delighted GM8PSM made his first contact outside the UK via RS-1.

Microwaves

The two Ern, G8BDJ and G8GKV assisted Mitch Tribe G8PMT, Worthing, a newcomer to 10GHz activity, to contact four QRA locator squares on Sunday morning, 12 November. While Mitch set up his equipment, with a 60cm dish aerial, on Chanctonbury Ring, a high spot on the South Downs, G8GKV, accompanied by Matthew Walton a keen SWL and student of microwave activity, took his gear to other high spots in squares AK, AL and ZL. G8BDJ made the QSO with Mitch in ZK. Conditions were good and all contacts were 59. During the morning both G8BDJ and G8PMT heard the Isle of Wight beacon, GB3IOW on 3cm, and were later joined by G3JHM to make arrangements for future tests on the band.

Tropospheric

On 18 October, the atmospheric pressure rose rapidly from 30.0in to 30.4in, and with a few fluctuations it remained high until 12 November when it dropped back to 30.1in. This high pressure, coupled with mild and fine weather, frequently upset the v.h.f.s between 27 October and 12 November and as usual, our readers were both active and observant. At 2237 on 27 October, Alan Baker worked G8FRB/P near Derby on 2m s.s.b. and during the evening of the 28th, Belgian stations were working through the Dover repeater GB3KR, R4. While continental broadcast stations were audible in Band II on 28, 29 and 30 October, I frequently received strong pictures from the IBA transmitter at Lichfield, 189MHz, with a dipole aerial. Between 1900 and 2000 on 5 November, Dermot Cronin G4GRO, Royal Sovereign Light, heard 2m s.s.b. signals from DM, HG, OE and OK and at 2057 Ken Smith, Horsham reported patterns on u.h.f. TV. On the 9th both Ken and Ian Rennison heard continental stations in Band II and Alan Baker heard DL3HB and worked F6EVL on 2m c.w. At 0044 on the 10th, Alan, behind 400ft of chalk had a QSO with G8FUE in Somerset on 2m s.s.b.

Although conditions were generally very good for v.h.f. and u.h.f. DX throughout the 10th, 11th and part of the 12th, some strange things also happened. For instance, during the morning of the 10th, Brian Houghton G4BCO, Hastings, worked a station in Luton on f.m. running 1 watt from a hand-held set and Brian Fenwick G8BTC, Brighton, was listening to G8BDJ in nearby Southwick on 2m f.m., when suddenly his strong signals were obliterated by a station in Birmingham.

At 0843 on the 10th, I received strong pictures plus co-channel interference from Lichfield, and with patterning

on some u.h.f. TV channels I was not surprised when I heard signals from the 70cm beacons at Emley Moor GB3EM and Sutton Coldfield GB3SUT, using only a dipole aerial. Around 1800 **John Keegan**, Steyning, Sussex saw German TV signals, complete with adverts in Band V. Later the same evening, **Peter Beer**, near Saffron Walden, Essex, using a loft aerial, received pictures from French u.h.f. television.

Mitch Tribe was delighted with his achievements on the 10th because, using his Multi-800D rig from his stationary car, he worked several PD0 (Dutch Novices' call sign) on 2m f.m. and at 1300 G4GNX/M, situated on Beachy Head, worked PA0 and DJ via the Brugge repeater ON0VW, R2. Between 2145 and 2230 Ian Rennison received Belgian, Dutch and French stations in Band II, using a dipole aerial into his AIWA 5080 stereo system. At 0054 on the 11th, **John Cooper** G8NGO, Cowfold, heard an OZ on 2m s.s.b., and periodically between 0900 and 1400 both Ian Rennison and myself received pictures from a Dutch station on Channel E4.

Amateur Co-operation

While in contact with PA0OOM at 0036 on the 11th, G4GNX learnt that the Dutch station had been trying for two years to work a station in QRA square ZK, so he called G8NGO who lives in ZK who was very soon in touch. Later, PA0OOM told G4GNX that he was going QRT, a very happy man.

During the opening, several amateurs and u.h.f. televiewers complained about total loss of signals and a good example was a local QSO in Hastings between G3JSF and G8PUW on 2m, only about three miles apart, who suddenly completely lost contact with each other. More fading was reported by **Guy Stanbury**, Chelmsford, who became aware of the disturbance when he saw patterning on Band V pictures on the 10th, and from about 1900 received f.m. signals, some in full stereo, from stations in West Germany and the Low Countries. Throughout the evening he noticed that signals would appear for a while and then fade away, and very soon the space would be taken by another. Guy also remarked about the extensive fluctuations in signal strengths and writes "I am sure you will agree that this type of opening is as fascinating when it deteriorates as when it starts".

New VHF Repeater

The first QSO through the Brighton repeater GB3SR, which commenced operation on R3 at 1900 on 15 October, was between G8ETL/M, Brighton, and G3WPO, Worthing, who was using a home-brew, hand-held transceiver. The Sussex Repeater Group, who are responsible for the station, are delighted with its initial performance despite the fact that they are using temporary filters.

From our Overseas readers

Congratulations to **Anthony Mann**, Applecross, Western Australia, who sent us the exciting report that he had received Ch.B1 BBC TV sound, 41.5MHz, down-under, on 13, 14, 16 and 19 October, the vision, 45 MHz, on the 13th and Ch.F2 French sound, 41.25MHz, on the 16th. Anthony also received strong f.m. signals from the Korean Broadcasting Service, 44.3 and 44.9MHz, on each of these days and Russian signals on 41, 42 and 43MHz on the 19th. Also on the 19th he heard signals from Japanese amateurs on 52MHz, and Chinese and Malaysian TV signals on Channels R1 and E3 respectively.

"You might realise that any v.h.f. from the north is DX long before it arrives" writes **Ian Roberts**, Pretoria, South Africa, who also says that 19 October was remarkable because he was receiving Ch. R1 vision at 0900 and the Cyprus beacon, 50.5MHz, just above the noise. Also on the 19th, Ian heard the second harmonic of the French (Issoudun, 500kW) programme at 43.16MHz S5, while the fundamental at 21.58MHz was S9.

Oddleiv Tungland, Trondheim, Norway, is now licensed as LA3GW and is operating from LA1K, the club station of the students in Trondheim. Oddleiv is also interested in DX TV, and in recent years has received signals from about 10 European countries using a dipole aerial in Band I.

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS

BINDERS FOR PW

Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

(Overseas orders please add 60p).

15-240 Watts!

HY5

Preamplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7k Ω at 1kHz.
OUTPUTS: Tape 100mV; Main output 500mV R.M.S.
ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.
DISTORTION: 0.1% at 1kHz. Signal/Noise Ratio 68dB.
OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.
Price £6.27 + 78p VAT P&P free.

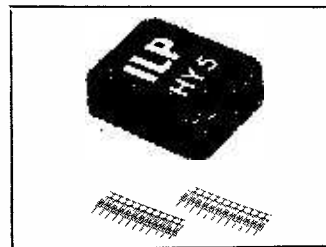

HY30

15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.


FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0.1% at 1.5W.
INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.
SUPPLY VOLTAGE \pm 18V.

Price £6.27 + 78p VAT P&P free.

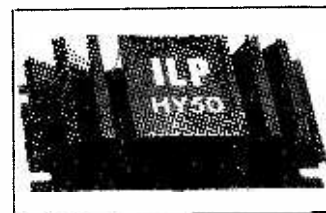

HY50

25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.


FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS:

INPUT SENSITIVITY 500mV
OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 25W at 1kHz
SIGNAL/NOISE RATIO 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.
SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm

Price £8.18 + £1.02 VAT P&P free

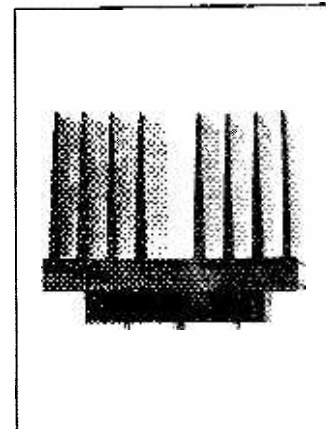

HY120

60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and Organ

SPECIFICATIONS:

INPUT SENSITIVITY 500mV
OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 60W at 1kHz
SIGNAL/NOISE RATIO 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 25V
SIZE 114 50 85mm

Price £19.01 + £1.52 VAT P&P free.

HY200

120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS:

INPUT SENSITIVITY 500mV
OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.05% at 100W at 1kHz
SIGNAL/NOISE RATIO 96dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 25V
SIZE 114 50 85mm

Price £27.99 + £2.24 VAT P&P free.

HY400

240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.


FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.1% at 240W at 1kHz
SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 45V
INPUT SENSITIVITY 500mV **SIZE** 114 100 85mm

Price £38.61 + £3.09 VAT P&P free.

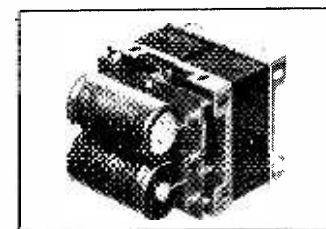

POWER SUPPLIES

PSU36 suitable for two HY30's £6.44 plus 81p VAT, P/P free.
PSU50 suitable for two HY50's £8.18 plus £1.02 VAT, P/P free.
PSU70 suitable for two HY120's £14.58 plus £1.17 VAT, P/P free.
PSU90 suitable for one HY200 £15.19 plus £1.21 VAT, P/P free.
PSU180 £25.42 + £2.03 VAT.
B1 £0.48 + £0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,

CROSSLAND HOUSE, NACKINGTON,
CANTERBURY, KENT, CT4 7AD.

Tel: (0227) 64723.

Regd No. 1032630.

Please Supply _____

Total Purchase Price _____

I Enclose Cheque ☐ Postal Orders ☐ Money Order ☐

Please debit my Access account ☐ Barclaycard account ☐

Account number _____

Name and Address _____

Signature _____

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escheutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200 250V. PRICE £16.00, P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k. (suitable for use with mic. or guitar etc.). Input 3 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escheutcheon. For ac mains operation 200/240V. Size approx. 12 1/2" w. \times 5 1/2" h. \times 7 1/4" d. Special introductory Price £28.00 - £2.50 carr. & pkg.


"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each - p. & p. (one 90p, two £1.10). Now available in either 8" round version or 4 1/2" \times 8 1/2" rectangular. 10 watts RMS 60Hz-20KHz. £5.25 - P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" \times 2 1/2" \times 5 1/2" H. £2.60 - 20p P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm, £3.50 per matched pair - 50p P. & P.

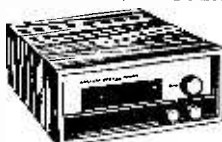MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains Operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz. VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/4" w. \times 4 1/4" h. \times 9 1/4" d approx.

LIMITED NUMBER ONLY at £28.00 - £1.50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good life and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY £15.50, P. & P. £1.40. Also available ready built and tested £20.00, P. & P. £1.40.

STEREO DECODER

SIZE 2" \times 3" \times 1 1/2" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p. P. & P. Stereo beacon light if required 40p extra.

SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette. Size 7 1/2" H. 9 1/2" W. 1 1/2" D. Approx. fully guaranteed. Bargain price of only £10.00 - £1.30 p. & p.

MODEL FL4

Few only similar to above, but battery operation only and fitted with twin speakers. Four wave bands, MW, FM and two VHF bands for reception of aircraft and some public services. ONLY £9.50 - 1.30 p. & p.

MODEL MULTI 5

Specification as Model FL4 but with additional SW band. Fitted with twin speakers. ONLY £11.00 - £1.30 p. & p.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any Speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked. Smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V. at 1.0 amp. Overall Size 12" w. \times 8" d. 2 1/4" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. AMPLIFIER 2218 15p. £14.50 P. & P. 80p (Magnetic input components 35p extra)

POWER PACK KIT

£6.00 P. & P. 95p

CABINET

£6.00 P. & P. 95p

SPECIAL OFFER—only £25.00 if all 3 items

ordered at one time plus £1.25 p. & p.

Also avail. ready built and tested £31.25, P. & P. £1.50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/4" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escheutcheon (to allow the panel to be mounted horizontally or vertically) at only £10.00 plus 50p P. & P. Mains transformer with an output of 17V ac at 500mA can be supplied at £2.00 - 40p P. & P. if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSON SURPLUS CO. LTD. (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.

TTLS BY TEXAS										TRANSISTORS										DIODES									
7400	13p	7497	180p	7421	160p	741S192	140p	74C157	250p	4C127/8	20p	BFY51/2	22p	TIP41C	78p	2N3866	90p	0A47	12p										
7401	14p	74100	130p	74259	140p	741S193	140p	74C160	155p	AD149	70p	BFY56	33p	TIP42C	82p	2N3903/4	18p	0A81	15p										
7402	14p	74104	65p	74260	30p	741S194	140p	74C161	155p	AD161/2	45p	BFY90	90p	TIP295	78p	2N3905/6	20p	0A85	15p										
7403	14p	74105	65p	74270	30p	741S195	140p	74C162	155p	BC107/8	11p	BLY83	700p	TIP305	70p	2N4001/2	18p	0A80	15p										
7404	17p	74107	34p	74271	30p	741S196	140p	74C163	155p	BC109	11p	BRY39	45p	TIP305	70p	2N4001/2	18p	0A81	15p										
7405	16p	74109	55p	74283	190p	741S197	140p	74C170	120p	BC147/8	9p	BSX19/20	20p	TIS93	30p	2N4001/2	18p	0A85	9p										
7406	32p	74110	55p	74284	400p	741S198	140p	74C171	120p	BC147/8	9p	BU105	190p	TIX708	12p	2N4123/4	22p	0A85	9p										
7407	32p	74111	70p	74285	400p	741S199	140p	74C172	120p	BC157/8	10p	BU108	250p	TZX300	13p	2N4125/6	22p	0A200	9p										
7408	19p	74116	200p	74286	400p	741S200	140p	74C173	120p	BC159	11p	BU205	220p	TZX502	18p	2N4089	20p	0A202	10p										
7409	19p	74118	200p	74287	400p	741S201	140p	74C174	120p	BC169C	12p	BU208	240p	TZX502	18p	2N4401/3	20p	0A203	10p										
7410	15p	74119	210p	74288	400p	741S202	140p	74C194	220p	BC172	12p	BU406	45p	TZX504	30p	2N4427	90p	0N186	7p										
7411	24p	74120	110p	74289	200p	741S203	140p	74C195	220p	BC177/8	12p	MJ481	175p	2N4574	250p	2N4871	60p	0N1418	4p										
7412	20p	74121	28p	74290	150p	741S204	140p	74C221	175p	BC179	18p	MJ491	200p	2N696	35p	2N5087	27p	1N4001/2	5p										
7413	30p	74122	48p	74291	150p	741S205	140p	4000 SERIES		BC182/3	10p	MJ2501	225p	2N697	25p	2N5089	27p	1N4003/4	5p										
7414	60p	74123	55p	74292	150p	741S206	140p	CA3130S	150p	BC184	11p	MJ2555	180p	2N697	45p	2N5172	27p	1N4006/7	7p										
7415	27p	74124	55p	74293	150p	741S207	140p	CA3140S	75p	BC187	30p	MJ3001	225p	2N708A	20p	2N5179	27p	1N4006/7	7p										
7416	27p	74125	55p	74294	150p	741S208	140p	CA3160S	75p	BC212/3	11p	MJE340	65p	2N708A	20p	2N5191	30p	1N5401/3	14p										
7417	27p	74126	55p	74295	150p	741S209	140p	FX209	750p	BC214	12p	MJE355	100p	2N918	45p	2N5194	90p	1N5404/7	13p										
7418	27p	74127	55p	74296	150p	741S210	140p	ICL7106	925p	BC214	12p	MJE355	100p	2N930	18p	2N5245	40p	ZENERS											
7419	27p	74128	55p	74297	150p	741S211	140p	LMC8038	340p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	2N4-33V	50p										
7420	27p	74129	55p	74298	150p	741S212	140p	LM301A	36p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	400 mW	9p										
7421	40p	74130	75p	74299	150p	741S213	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	1 V	15p										
7422	22p	74131	75p	74300	30p	741S214	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	SPECIAL											
7423	34p	74132	75p	74301	30p	741S215	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	OFFERS											
7424	34p	74133	75p	74302	30p	741S216	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 741											
7425	34p	74134	75p	74303	30p	741S217	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	£16											
7426	40p	74135	90p	74304	30p	741S218	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7427	34p	74136	90p	74305	30p	741S219	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	£20											
7428	36p	74137	90p	74306	30p	741S220	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+											
7429	36p	74138	90p	74307	30p	741S221	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	RCA 2N3055											
7430	36p	74139	90p	74308	30p	741S222	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	236											
7431	36p	74140	90p	74309	30p	741S223	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	BRIDGE											
7432	36p	74141	90p	74310	30p	741S224	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7433	40p	74142	90p	74311	30p	741S225	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7434	35p	74143	90p	74312	30p	741S226	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7435	35p	74144	90p	74313	30p	741S227	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7436	35p	74145	90p	74314	30p	741S228	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7437	35p	74146	90p	74315	30p	741S229	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7438	35p	74147	90p	74316	30p	741S230	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7439	35p	74148	90p	74317	30p	741S231	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7440	17p	74149	90p	74318	30p	741S232	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7441	70p	74150	90p	74319	30p	741S233	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7442	80p	74151	90p	74320	30p	741S234	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7443	112p	74152	90p	74321	30p	741S235	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7444	112p	74153	90p	74322	30p	741S236	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7445	100p	74154	90p	74323	30p	741S237	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7446	93p	74155	90p	74324	30p	741S238	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7447	93p	74156	90p	74325	30p	741S239	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7448	93p	74157	90p	74326	30p	741S240	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7449	93p	74158	90p	74327	30p	741S241	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7450	17p	74160	140p	74328	30p	741S242	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7451	17p	74161	140p	74329	30p	741S243	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7452	17p	74162	140p	74330	30p	741S244	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7453	17p	74163	140p	74331	30p	741S245	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7454	17p	74164	140p	74332	30p	741S246	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7455	17p	74165	140p	74333	30p	741S247	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7456	17p	74166	140p	74334	30p	741S248	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7457	17p	74167	140p	74335	30p	741S249	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7458	17p	74168	140p	74336	30p	741S250	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7459	17p	74169	140p	74337	30p	741S251	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7460	17p	74170	140p	74338	30p	741S252	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7461	17p	74171	140p	74339	30p	741S253	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7462	17p	74172	140p	74340	30p	741S254	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7463	17p	74173	140p	74341	30p	741S255	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7464	17p	74174	140p	74342	30p	741S256	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7465	17p	74175	140p	74343	30p	741S257	140p	LM318	150p	BC214	12p	MJ3001	225p	2N930	18p	2N5245	40p	100+ 555											
7466</																													

silicon chip of the 3089 device. The use of an external load resistor in the CA3189E enables any noise at pin 10 to be decoupled by a $10\mu\text{F}$ capacitor to ground; in addition, the value of the load resistor can be selected as desired so as to vary the audio output level, which increases with the value of the load resistor. The value of the de-emphasis capacitor from the output to ground must be chosen according to the value of the load resistor used so that the produce of the values of these two components is about $50\mu\text{s}$.

There is no connection to pin 16 of the 3089 devices, but in the CA3189E this pin is used to feed the controlling voltage for the a.g.c. threshold into the device. This controlling voltage may be obtained using the voltage at pin 13 as shown in Fig. 15, in which case the onset of a.g.c. action will vary from about $200\mu\text{V}$ up to 200mV at pin 1 according to the setting of VR1. When the a.g.c. voltage is plotted against the input voltage a curve with an extremely sharp "knee" is obtained, so the onset of a.g.c. action is very rapid. When the a.g.c. voltage from the CA3189E is fed to one of the gate electrodes of a MOSFET in a front-end unit, a range of 40dB in the gain is easily obtained.

FM/AM Devices

The f.m. i.f. devices we have discussed process only an f.m. signal, but many new devices are now coming onto the market which will not only handle the f.m. i.f. signal, but which will also process an a.m. signal. When an f.m. front-end unit is coupled to such a device together with an audio amplifier, all the devices (except possibly one or two diodes or transistors) which are required in a receiver to cover both a.m. and f.m. bands are then available. Devices in this class include the Fairchild μA721 , the A.E.G.-Telefunken TDA1083, the Mullard TBA570 and their new TDA5700 and the SGS-Ates TDA1220 device.

One of the problems of using these devices in a home constructed receiver is the complexity of the circuitry around a single integrated circuit. Many constructors therefore prefer to keep the a.m. and f.m. sections of their receivers quite separate. However, in car radio receivers and in small portable receivers where space can be at a premium, these new combined a.m./f.m. devices are very attractive, especially to the receiver manufacturers.

The μA721

The Fairchild μA721 device is encapsulated in a standard 16 pin dual-in-line plastic package (available from Arrow Electronics Ltd.). It contains the semiconductor devices required for the a.m. r.f. stage, oscillator, mixer and i.f. stage together with an f.m. limiter and quadrature demodulator circuit. Although all of this circuitry has been compressed onto a single chip, the total quiescent current required is only some 20mA. The device operates from a supply of about 9V.

The f.m. section input has a limiting sensitivity of about $500\mu\text{V}$ and provides an audio output signal of about 520mV r.m.s. at a typical total harmonic distortion of some 0.9% (maximum for any μA721 device is 2%). The signal-to-noise ratio is typically 75dB with a minimum value of 60dB. The rejection of a.m. signals is some 46dB (as opposed to about 60dB in the case of the CA3189E).

So You Want to Pass the RAE?

A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint will cost 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:—

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street, London
SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME.....
(BLOCK LETTERS)

ADDRESS.....
(BLOCK LETTERS)

.....

.....

.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

_____ Cut round dotted line _____

READERS PCB SERVICES


BOX 11, FLEET HOUSE — WELBECK STREET
WHITWELL — Nr. WORKSOP — NOTTS
Tel: (0909) 720695 TELEX: 547616 FLEET G

PW PRINTED CIRCUIT BOARDS

Dec 75	Sound-to-light display	DN0798	1.35+15	<input type="checkbox"/>
Dec 75	Disco System Amp (2 req'd) each	AM0421	4.90+25	<input type="checkbox"/>
Mar 76	CMOS Crystal Callibrator	AM0438	1.25+15	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	6.50+25	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3.50+15	<input type="checkbox"/>
July 77	Radio 2 Tuner	A035	1.68+12	<input type="checkbox"/>
July 77	Digital Clock Timer	A036	3.28+12	<input type="checkbox"/>
Aug 77	Atomic Time Receiver	D036	2.65+15	<input type="checkbox"/>
Aug 77	Morse Code Tutor Cards (SRBP)	A037	4.75+15	<input type="checkbox"/>
Oct 77	Audio Level Indicator	D039	0.98+12	<input type="checkbox"/>
Nov 77	Laboratory Power Supply	A039	3.50+12	<input type="checkbox"/>
Jan 78	Direct Conversion Receiver	D043	1.85+15	<input type="checkbox"/>
Mar 78	Audio/Visual Logic Probe	R001	1.40+15	<input type="checkbox"/>
May 78	DX'ers Audio Filter	D001	2.35+15	<input type="checkbox"/>
June 78	Audio Distortion Meter (set)	R007/8/9/10	6.75+25	<input type="checkbox"/>
June 78	Darkroom Timer	R011	1.55+15	<input type="checkbox"/>
July 78	Avon Transmitter	R015/16/19/20	5.10+40	<input type="checkbox"/>
July 78	Digital Lock	D002	1.25+15	<input type="checkbox"/>
July 78	Morse Tutor	R014	2.35+15	<input type="checkbox"/>
Aug 78	Point Motor C.D. Supply	D005	1.25+15	<input type="checkbox"/>
Oct 78	Gillingham SW Receiver	R025/6	4.80+20	<input type="checkbox"/>
Nov 78	Sarum	R030	3.30+20	<input type="checkbox"/>
Nov 78	STD Charge Timer	AD212	3.00+15	<input type="checkbox"/>
Nov 78	Auto Outside Light	AD225	0.60+12	<input type="checkbox"/>
Nov 78	Porch Light	AD232	0.60+12	<input type="checkbox"/>
Dec 78	Digital Door Chimes	R017	4.20+12	<input type="checkbox"/>

SPECIAL OFFERS

A.	Induction balance metal detector	9.50+50	<input type="checkbox"/>
B.	12 or 24hr L.E.D. alarm clock, large display	9.90+75	<input type="checkbox"/>
C.	Vega Selina 8 w.b. radio, 5 s/w, l/w, m/w, and FM with AFC	32.95+1.75	<input type="checkbox"/>
D.	3 w/B.L.E.D. Clock radio alarm, l/w, m/w, FM	19.50+1.50	<input type="checkbox"/>
E.	12 or 24hr Car clock in tachometer case, blue L.E.D. display, 3" x 2 1/2" x 3 1/2" deep	14.95+50	<input type="checkbox"/>
F.	Vega 6" mains/battery portable T.V.	59.40+1.75	<input type="checkbox"/>

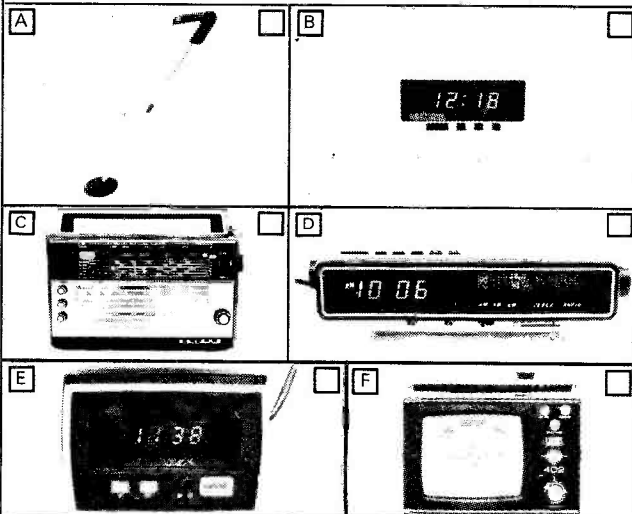

WATCH BATTERIES ALWAYS AVAILABLE—ANY TYPE 49p each

Post and packing is for one board or set of boards or one item. Prices include VAT. Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

I enclose Postal Order/Cheque ACCESS welcome.
Send card number only.

No.....

for £..... made payable to READERS PCB SERVICES LTD.
Box 11, Fleet House, Welbeck St., Whitwell, Nr. Worksop, Notts.

NAME

ADDRESS

Post Code



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMAN'S • I.M.F. • ISOPHON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • SHACKMAN • STAG • TANGENT • TANNOY • VIDEOTONE • WHARFEDALE • YAMAHA

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

THE BRIDGE BETWEEN MANUFACTURERS & USERS OF MICROELECTRONICS

MICROSYSTEMS '79

West Centre Hotel,
Lillie Road, Fulham,
London, SW6
January 31 to
February 2
09.30-16.00 hrs each day

Now in its second great year, Microsystems is a combined conference and exhibition aimed at alerting industrialists and businessmen to the meaning of the microelectronic revolution.

The Exhibition is free. The Conference costs £55 + VAT for each of the first two, professional days (£95 + VAT for a two-day ticket), and £7 + VAT for the final, personal computing, day.

Microsystems is sponsored by 'Computer Weekly'.

'Microprocessors', 'Data Processing', 'Electronics Weekly', 'Systems International', 'Electron', 'Electrical Times', 'Electrical Review' and 'Wireless World' and is organised for them by Iliffe Promotions Ltd, Dorset House, Stamford Street, London, SE1 9LU.

USE THIS COUPON TO BOOK FOR MICROSYSTEMS

PW

To: Microsystems, Room 821, Dorset House, Stamford Street, London, SE1 9LU.


Please send me: ☐ Conference details and registration forms
☐ A free exhibition ticket (Tick as required)

Name

Address

FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY

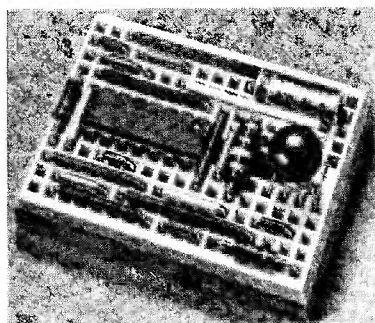Super Strip accepts *all DIP's*—as many as nine 14-pin at a time—and/or TO-5's and discrete components. With interconnections of any solid wire up to 20 AWG. *And no soldering.* Super Strip has 840 contact points, combining a power/signal distribution system with a matrix of 640 contacts in groups of 5. Distribution system has 8 bus-bars, each with 25 contact points.




**Best Buy
2-8**

The modular, solderless system! Breadboards that link together for any size, any configuration. With pitch of 0.1" to accept all IC's. Just take each component, choose its hole and push it in.

BREADBOARDS			BUS STRIPS	
<i>Model</i>	<i>Contacts</i>	<i>Price, each</i>	<i>Model</i>	<i>Price</i>
264L	640	£8.32	121R	£1.78
248L	480	£6.65	209R	£1.62
234L	340	£5.75	206R	£1.45
217L	170	£3.25		

(All prices include p & p and VAT)

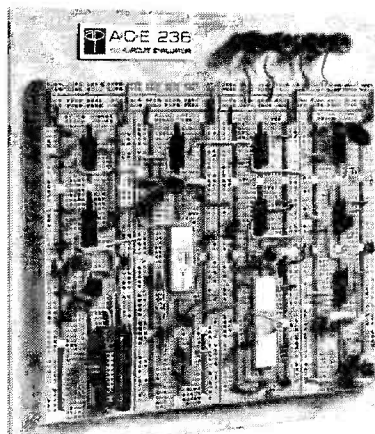

Best Buy
9-15

Just plug in components and make connections with ordinary 22-gauge solid wire. No soldering. Build any working project *complete* as fast as you could lay out a circuit diagram before.

ACE 200-K (728 contacts: £12.53) and ACE 201K (1,032 contacts: £16.75) come in kit form.

LEKTROKIT

PW4

Practical Wireless, February 1979

Transistors			Transistors			Transistors			TTL		
A143	1+	25+ 100+	A143	1+	25+ 100+	A143	1+	25+ 100+	A143	1+	25+ 100+
AD143	.90	82 .69	TP13C	.38	35 .29	2N6809	.58	58	7400	.20	18 .15
AD149	.95	88 .72	TP132	.35	32 .27	2N6810	.80	54 .46	7403	.40	36 .30
AU106	2.16	1.96 1.65	TP132A/B	.35	32 .27	40366	.40	36 .30	7495	.23	21 .18
AU110	2.08	1.89 1.59	TP132C	.38	35 .29	40406	.41	37 .32	7496	.34	31 .26
BC107/A/B	2.08	1.89 1.59	TP141/A	.51	46 .38	40407	.41	37 .32	7497	1.02	94 .76
BC108/A/B	.12	.11 .095	TP142/A/B	.53	48 .40	40411	.88	86 .68	74100/A	.71	65 .56
BC108C	.13	.115 .10	TP142C	.57	52 .44	40594	1.18	106 .90	74100/B	.86	78 .66
BC109/A/B	.12	.11 .095	TP147	1.45	1.32 1.11				74101	.42	38 .32
BC109C	.13	.115 .10	TP148	1.54	1.39 1.17				74111/16	.27	25 .21
BC142	.28	.24 .20	TP111	1.05	95 .80	TTL			74118	.89	81 .68
BC143	.28	.28	TP112	1.02	92 .77	7400	.16	.15 .13	74119/20	.60	54 .46
BC182A/B	.07	.06 .055	TP112	1.02	92 .77	7401	.19	.17 .14	74121	.39	35 .30
BC182L	.10	.09 .075	TP115	1.02	92 .76	7401	.21	.19 .16	74122	.44	40 .34
BC184B/C	.07	.06 .055	TP116	1.07	96 .81	7401	.16	.15 .13	74123	.45	40 .34
BC184B/C	.07	.06 .055	TP117	1.24	1.13 .95	7403	.19	.17 .14	74128	.45	40 .34
BC184C	.10	.09 .075	TP120	1.03	93 .78	7404	.16	.15 .13	74132	.60	55 .46
BC121A/B	.07	.065 .055	TP121	1.05	95 .80	7405	.20	.18 .15	74136	.24	22 .18
BC121C	.10	.09 .075	TP122	1.05	92 .78	7406	.27	.24 .21	74137	.25	23 .19
BC123A/B	.07	.065 .05	TP123	1.07	96 .81	7408	.16	.15 .13	74141	.24	22 .18
BC124B/C	.07	.065 .05	TP127	1.24	1.13 .95	7409	.20	.18 .15	74142	.18	15 .12
BC214L	.10	.09 .075	TP2955	.62	57 .48	7410	.16	.15 .13	74145	.36	33 .27
BC300/1/3	.25	.23 .20	TP3055	.62	57 .48	7412	.20	.18 .16	74147	.71	65 .55
BC337	.09	.08 .065	2N1132	.26	23 .20	74121A	.20	.17 .14	74148	.74	67 .57
BC441	.27	.27 .22	2N2122	.38	33 .28	7413	.32	.29 .25	74150	.45	40 .34
BC461	.30	.27 .23	2N2121A	.24	21 .18	7408	.24	.23 .19	74151/3	.29	26 .22
BC548B/8/7	.07	.06 .055	2N2121A/A	.24	21 .18	7420	.16	.15 .13	74154	.69	63 .55
BC550B/6/7	.07	.065 .055	2N2221A	.17	.16 .13	7422/3	.20	.18 .15	74155	.26	25 .21
BC558B/9/80	.07	.065 .055	2N2222A	.15	.14 .12	7425B/7/8	.21	.19 .16	74156	.36	33 .27
BCY70	.18	.16 .135	2N2846	.41	37 .31	7430	.16	.15 .13	74157	.29	26 .22
BCY71	.36	.36 .30	2N2905	.25	21 .18	7432	.18	.16 .14	74159	.27	25 .20
BD132	.40	.37 .31	2N2904A/5A	.25	.22 .19	7433	.23	.21 .19	74180/1	.36	33 .27
BD142	.88	.80 .67	2N2906/7	.15	.14 .12	7437B	.20	.18 .16	74181	.40	36 .31
BD201	.45	.40 .34	2N2907A	.16	.1						

TTL 74H20 74S10	1+	25+	100+	Triacs, TO220				1+	25+	100+	LM301A					
		28	26	22	2A 100V	.45	41	35	2A 200V	.45	42	35	NE555	1.35	1.22	1.03
		31	28	24	2A 400V	.50	45	38	6A 100V	.51	46	38	NE568	.28	.25	.21
					6A 200V	.52	47	40	6A 400V	.56	51	43	SN7603	2.20	2.00	1.88
CMOS 4001A 4001A 4011/12A 4013B 4014A 4017A 4018B 4021/22A 4023A 4024B 4025A 4027B 4028B 4029A 4030A 4040A 4042B 4049A/44B 4049A 4050B 4051B 4068/69B 4071B 4098B 4160/1/2 4175B 4194B 4409P 4450P 4455P 4501CP 4501PA 4508B	.19	.175	.15	10A 100V	.82	74	63	10A 200V	.84	76	64	SN76023	2.20	2.00	1.88	
	.19	.175	.15	10A 400V	.91	82	69	10A 400V	.91	82	69	UA709C	.38	.35	.29	
	.19	.175	.15	Thyristors, TO220				3A 100V	.37	34	28	UA741CP	.28	.25	.21	
	.19	.175	.15	5A 400V	.41	37	31	5A 100V	.37	34	28	UA748C	.68	.61	.52	
	.19	.175	.15	5A 200V	.37	34	28	5A 600V	.50	45	38	TAA570	2.14	1.94	1.84	
	.19	.175	.15	7A 400V	.56	51	43	7A 200V	.47	42	36	TBA120SU	.91	.82	.69	
	.19	.175	.15	10A 200V	.62	56	48	10A 400V	.59	54	45	TBA520D	2.04	1.85	1.56	
	.19	.175	.15	Bridge Rect				3A 50V	.38	35	29	TBA5300	1.79	1.62	1.36	
	.19	.175	.15	2A 50V	.38	35	29	2A 100V	.42	38	32	TBA5400	1.92	1.73	1.46	
	.19	.175	.15	2A 200V	.47	42	36	2A 400V	.59	54	45	TBA5600C	2.36	2.13	1.80	
	.19	.175	.15	LEDS				2A 50V	.38	35	29	TBA5600C	2.36	2.13	1.80	
	.19	.175	.15	TTL209	.17	.155	.13	TTL212	.21	.19	.16	TBA7500	1.79	1.62	1.36	
DIL Sockets 8 pin 14 pin 16 pin 18 pin 20 pin 22 pin 24 pin 26 pin 40 pin	.13	.115	.095	TTL216	.21	.19	.16	TTL220	.16	.14	.12	TBA8200	2.42	2.19	1.84	
	.14	.125	.105	TTL228	.23	.21	.175	TTL234	.23	.21	.175	TBA8200	2.42	2.19	1.84	
	.16	.16	.16	TTL232	.21	.19	.16	Diodes				TBA950	2.29	2.08	1.75	
	.18	.15	.165	IN314	.03	.015	.013	IN316	.03	.016	.014	TBA990D	2.04	1.85	1.56	
	.20	.21	.18	IN4001	.045	.04	.035	IN4002	.05	.04	.035	TCA2700	1.79	1.62	1.36	
	.22	.25	.22	IN4003	.055	.05	.04	IN4004	.055	.05	.04	TC4800	2.82	2.55	2.15	
	.24	.26	.235	IN4005	.055	.05	.045	IN4006	.06	.05	.045	Disc Ceramics				
	.26	.31	.26	IN4148	.065	.055	.05	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.34	.44	.37	IN4149	.03	.015	.013	IN4149	.03	.015	.013	0.022				
	.49	.44	.44	BYZ88C	.07	.055	.047	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
				Linear ICs				IN4149	.03	.015	.013	1W	.08	.07	.06	
				555	.30	.27	.22	IN4149	.03	.015	.013	Resistors 1W				
				709	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
			710	.42	.38	.32	IN4149	.03	.015	.013	3GV	1+ 25+ 100+				
			741	.24	.21	.18	IN4149	.03	.015	.013	0.022					
			747	.40	.37	.31	IN4149	.03	.015	.013	.1uF	.06	.05	.045		
			748	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06		
			CA3130E	.95	.86	.72	IN4149	.03	.015	.013	Resistors 1W					
			CA3130T	.95	.86	.72	IN4149	.03	.015	.013	Disc Ceramics					
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	1W	.08	.07	.06	
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	0.022				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06	
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	Disc Ceramics				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	1W	.08	.07	.06	
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	0.022				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06	
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	Disc Ceramics				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	1W	.08	.07	.06	
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	0.022				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06	
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	Disc Ceramics				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	1W	.08	.07	.06	
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	0.022				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06	
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	Disc Ceramics				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	1W	.08	.07	.06	
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	Disc Ceramics				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	0.022				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	555	.30	.27	.22	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	709	.42	.38	.32	IN4149	.03	.015	.013	1W	.08	.07	.06	
	.78	.71	.60	710	.42	.38	.32	IN4149	.03	.015	.013	Resistors 1W				
	.78	.71	.60	741	.24	.21	.18	IN4149	.03	.015	.013	Disc Ceramics				
Voltage Regs 7805 7812 7805 7812	.78	.71	.60	747	.40	.37	.31	IN4149	.03	.015	.013	3GV	1+ 25+ 100+			
	.78	.71	.60	748	.42	.38	.32	IN4149	.03	.015	.013	0.022				
	.78	.71	.60	CA3130E	.95	.86	.72	IN4149	.03	.015	.013	.1uF	.06	.05	.045	
	.78	.71	.60	CA3130T	.95	.86	.72	IN4149	.03	.015	.013	1W				

TELEPHONE: 0822 5439 TELEX 45263

Callers Welcome. All components new and to full spec. Send SAE for full list

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

ELECTROVALUE Buying Guide

IMPORTANT ANNOUNCEMENT

With completion of our series of itemised advertisements we announce release of our newest catalogue, CATALOGUE No. 9—completely revised, enlarged and best yet.

SEND FOR YOUR FREE COPY NOW TO DEPT. PW29

HARDWARE/SOLDER TOOLS

SOLDER TOOLS

ORYX50	
Temp controlled	£9.75N
Spare element	£3.50N
Bits (11 types)	ea. £1.00N
ORYX Super 30	£4.45N
Spare element	£3.00N
Bits as for ORYX50	
ISO-TIP Quick Charge cordless	
iron	£20.50N
Bits micro 7566	£2.30N
fine 7545	£2.30N
std 7546	£2.30N
Std 7535	£2.30N
PC drill attachment	
6500	£10.60N
Spare bulb	35pN

ERSA Sprint	
Solder gun	£8.62N
Spare element	£5.00N
Bit No 862VN	40pN
ERSA solder station	
Temp controlled iron with stand	£59.00N
GREENWOOD PYROMETER	£25.00N

DESOLDER TOOL	
SR3A	£6.50N
Spare nozzle, PTFE SR3AN	70pN
ANTEX C-240V 15W	£3.60N
Spare element	£1.60N
Nickel plated bits	46pN
No 2 -094"; No 4 -187"; No 6 -047"	
Iron coated bits	46pN
No. 102, 104, 106	

ANTEX CCN-240V	£3.80N
(low capacitance) 15W	
Spare element	£1.90N
Iron coated bits	46pN
1100 -094"; 1101 -225"; 1102 -187"	

ANTEX CX 240V	£3.60N
Spare element	£1.60N
Bits for CCN above	
ANTEX X25-240V 25W	£3.60N
Spare element	£1.60N
Iron coated bits	50pN
50 -094"; 51 -125"; 52 -187"	

ANTEX STAND ST3.	£1.50N
No 666 Sponge	6pN

SOLDERSTAT RANGE	
HMS 240V 16W	£4.75N
HMS 240V 24W	£4.75N
HMS 110V 16W	£4.75N
HMS 110V 24W	£4.75N
Spare elements	£2.35N

Nickel plated bits	
2037 3-2mm	80pN
2038 2-4mm	80pN
2003 2mm stub	80pN

Iron plated	
2032 4-5mm	£1.90N
2033 6-5mm	£1.90N
IC desolder head for HMS	
Irons	
14-way	£5.70N
18-way	£5.70N

HMS 240V Solder Kit in presentation box	£8.90N
HMS 12V Solder Kit in wallet	£7.60N

POT CORES	
FERRITES	
BOOKS	

Latest price list of all ranges free on request.	
--	--

PRINTED CIRCUIT MATERIALS	
COPPER CLAD BOARD	
300 x 150mm	
Single sided	
SRBP 85p; Fibreglass	£1.85
Double sided SRBP	£1.00

UNCLAD SRBP	
300 x 150mm	56p
FERRIC CHLORIDE	
Lab grade 100gm pack	47p
500gm jar	£2.30

POSITIVE-20 Aerosol 75cc	
with instructions	£1.30
ETCH RESIST PEN	
Decon with spare tip	85p
73-00 63-00	

SILVER CONDUCTIVE PAINT	
3gm vial	
Elecolit 340	£2.20

VERO PRODUCTS	
VEROBOARD	
0.1" matrix copper clad	
3.75" x 2.5"	46p
5" x 2.5"	55p
5" x 3.75"	55p
8.45" x 1.5"	57p
DIP-BOARD	£2.78
VQ Dip-Board	£1.11
24-way plug-in	£2.20
32-way	£2.40
EURO Dip-Board	£3.57

0.1" matrix unclad	
3.75" x 2.5" 31p 5" x 3.75"	56p
3.75" x 2.5" 44p 5" x 2.5"	53p
74p 8.45" x 1.5" 57p	
0.2" matrix, copper clad	
5" x 3.4"	TO CLEAR 30p

PIN INSERTION TOOLS	
No PIT1 for 0.040" pins	
No PIT5 for 0.052" pins	£1.27
(0.15" matrix)	£1.27

SPOT FACE CUTTER	
Suitable for any matrix	89p

TERMINAL PINS	
(Not made by Vero)	
0.040" dia for 0.1" matrix per 100	35p
0.052" dia for 0.15" matrix per 100	40p
(Both types double ended)	

VEROBOK STANDARD BOXES	
High impact polystyrene light grey top, dark grey bottom section.	
Type L W H	
2514F 100 50 25	£1.64
2516G 100 50 40	£1.86
2518H 120 65 40	£2.07
2520J 150 80 50	£2.45
2522K 188 110 60	£3.13

VEROBOK CASES	
Constructed from ABS material light grey top & dark grey bottom section. Anodised all, front and rear panels. Internal guides for PC boards.	
Type L H D	
1237J 154 40 85	£2.56
1238D 154 60 85	£2.82
1239K 154 80 85	£3.38
1410J 205 40 140	£3.53
1411D 205 75 140	£3.96
1412K 205 110 140	£5.12

SLOPING FRONT PLASTIC CASES	
The 1798K has white top and grey bottom section, the 2523E has light grey top and dark grey bottom section.	
Both have anodised aluminium panels.	
Type W H1 H2 D	
1798K 171 38 75 121	£4.19
2523E 220 52 100 156	£6.36

19" CARD/FRAME CASE SYSTEM	
accepts plug-in modules and standard European size circuit boards.	
Light blue with natural anodised aluminium end plates.	
Can be rack mounted.	
Type Item	Price
3841L Case	£20.71N
3842F End plate angles (pr.)	83pN
3843A 8" Module	£4.00N
3844G 4" Module	£3.05N
2845B 2" Front panel	£1.02N
2846B 1" Front panel	97pN
3979K Board for module	£1.39
1034E Veroboard, clad	£1.42
1041J DIP-board	£3.59
0267H 31-way plug	97pN
0258C 31-way socket	£1.06N

EUROCARD CONNECTORS	
2876D 64-way plug	£2.47N
2874C 64-way socket	£4.48N

SWITCHES	
ERG Dual in Line	
One pole change over SDC1 42p	
Two-SDC2, 78p 3-SDC3 £1.08	
On/Off 2 pole SDC2 42p 4 pole	
SDS4 75p, 6p SDS6 £1.08, 8p	
SDS8 £1.32.	
Multiple—1P/8 way DS16A1 8	
99p. 2P/4V DS 16A2 4 £1.08.	

ROTARY MAINS	
Lorlin MS 4 amp	48p
WAVECHANCE	
Lorlin CK series MBB contacts	
1 pole 12W 37p; 2 pole 6W 37p;	
3 pole 4W 37p; 4 pole 3W 37p.	

ROTARY SWITCH KIT	
Type RA 6 wafers	60p
RA Wafers MBB	
1P 1W or 2P 5W	66p
RA Wafers BMM	
1P 12W, 2P 6W.	
3P 4W, 4P 3W.	
6P 2W	66p
RA Shorting wafer, MBB	
Rotating open-circuit	66p

PUSH BUTTONS	
Standard Size	
SSP10, 250V 3A a.c.	
push on, push off	
panel hole 0.5"	67p
SSP11, as SSP10	
push to make	56p
Sub-Minature 250V 0.5A a.c.	
8531 push to make	62p
8533 push to break	62p
(Panel hole 0.25"). Buttons in choice of black or red.	

CASTELCO RANGE 250V 1A a.c.	
0.375" hole with long white fixing ring unless otherwise ordered	
No. 2644 SP make	18p
No. 3244 DP make	34p
No. 2648 SP break	18p
No. 3248 DP break	34p
No. 2634 SP on/off	17p
No. 3234 DP on/off	30p
No. 4434 as 3234 but switch sections reversed	30p
No. 4444 as 3244 but switch sections reversed	34p
Spare rings in black, red, yellow, green, blue, white or pink	each 2p

TOGGLE 250V 1.5A a.c.	
Chrome finish	
1011C SPST	56p
1016C SPDT	61p
1019C SPDT	
centre-off	64p
409 DPDT	77p
Sub-Minature 250V 2A a.c.	
Panel hole 0.25"	
S7101 SPDT	63p
S7201 DPDT	84p
S7203 DPDT	
centre-off	84p
S7205 DPDT biased	
each side	£1.20
S7207 DPDT biased	
one side	£1.20
S7211 SP 3-way	£1.20
S7301 3PDT	£1.42
S7401 4PDT	£1.80

MICROSWITCHES SPDT	
SSU01 button	85p
TIME SWITCHES (Smith's)	
For electrical use. 13A rating	
IMERSSET	
for wired-in installations. 2 on & 2 off actions per day	£13.75N

WE ARE NATIONAL DISTRIBUTORS FOR NASCOM 1 MICROCOMPUTER KITS FOR DELIVERY FROM STOCK NET PRICES FROM £197.50 + V.A.T. QUANTITY DISCOUNTS — TRADE ENQUIRIES INVITED MOTOROLA Microprocessor Evaluation Kit, net £175.87 + V.A.T.

TRANSFORMERS

All mains transformer primaries suitable for 240V input except for 50TS2A.

GP302 30V 2A	tapped at 12, 15, 20, 24V	£4.60
GP501 50V 1A	tapped 19, 25, 33, 40V	£4.30
GP502 50V 2A	tapped 19, 25, 33, 40V	£6.30
GP601 60V 1A	tapped 24, 30, 40, 48V	£4.60
GP602 60V 2A	tapped 24, 30, 40, 48V	£6.70
50TS2 50V 2A	tapped 25, 45V	

GP501 50V 1A	tapped 19, 25, 33, 40V	£4.30
GP502 50V 2A	tapped 19, 25, 33, 40V	£6.30
GP601 60V 1A	tapped 24, 30, 40, 48V	£4.60
GP602 60V 2A	tapped 24, 30, 40, 48V	£6.70
50TS2 50V 2A	tapped 25, 45V	

GP501 50V 1A	tapped 19, 25, 33, 40V	£4.30
GP502 50V 2A	tapped 19, 25, 33, 40V	£6.30
GP601 60V 1A	tapped 24, 30, 40, 48V	£4.60
GP602 60V 2A	tapped 24, 30, 40, 48V	£6.70
50TS2 50V 2A	tapped 25, 45V	

GP501 50V 1A	tapped 19, 25, 33, 40V	£4.30
GP502 50V 2A	tapped 19, 25, 33, 40V	£6.30
GP601 60V 1A	tapped 24, 30, 40, 48V	£4.60
GP602 60V 2A	tapped 24, 30, 40, 48V	£6.70
50TS2 50V 2A	tapped 25, 45V	

GP501 50V 1A	tapped 19, 25, 33, 40V	£4.30
GP502 50V 2A	tapped 19, 25, 33, 40V	£6.30
GP601 60V 1A	tapped 19, 25, 33, 40V	£4.30
GP602 60V 2A	tapped 19, 25, 33, 40V	£6.30
GP701 70V 1A	tapped 19, 25, 33, 40V	£4.30
GP702 70V 2A	tapped 19, 25, 33, 40V	£6.30
GP801 80V 1A	tapped 19, 25, 33, 40V	£4.30
GP802 80V 2A	tapped 19, 25, 33, 40V	£6.30
GP901 90V 1A	tapped 19, 25, 33, 40V	£4.30
GP902 90V 2A	tapped 19, 25, 33, 40V	£6.30
GP1001 100V 1A	tapped 19, 25, 33, 40V	£4.30
GP1002 100V 2A	tapped 19, 25, 33, 40V	£6.30

MAINS INTERCOM

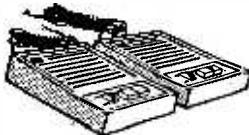

NO
BATTERIES
NO WIRES
ONLY
£32.99
PER PAIR
+ VAT £4.12

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystals clear communications from room to room. Range 1-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom between office and warehouse in surgery and in homes. P. & P. 99p.

4 STATION INTERCOM



£22.95
+ V.A.T. £1.85

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. P. & P. 99p.

NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER




ONLY
£16.95
+ VAT £1.36

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £19.95 + VAT £1.60. P. & P. 89p.

10-day price refund guarantee on all items.
WEST LONDON DIRECT SUPPLIES (PW2)
189 KENSINGTON HIGH STREET, LONDON, W8
01-837 5548

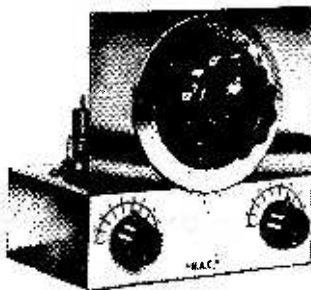H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



"H.A.C." well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.
£10.50 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.
NEW T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £12.50 this receiver is outstanding value, and will give you hours of interest and entertainment.
Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15 Ω as app.
Guarantees:
TITAN 5 years
FANE LIFETIME
OTHERS 1 year
ALL PRICES INC. VAT
Prices correct at 11.12.78

HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" A.F. Model 80 Dual Cone	Sp. Price	£5.95
8" A.F. Model 83 Dual Cone	Sp. Price	£6.95
FANE 8" 808T Dual Cone	Sp. Price	£3.95
WHITDALE L-TON 3XP kit Pr.	£50.70	£41.95
10" DENTON 2XP KIT Pair	£39.15	£26.95
10" GLENDALE 3XP KIT	£82.44	£58.95
A.F. FRI 8" SPKR KIT	Sp. Price Pair	£14.95
8" FANE MODE ONE KIT	Sp. Price Pair	£19.99
10" ELAC Model 10RM 10-15w	Sp. Price	£22.50

CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Model I or FRI Kits and Models 80, 83 or 808T Spkrs.
Limited Number **£6.95** ea.

GROUP/DISCO TYPES

PLEASE STATE IMPEDANCE

12" TITAN T12/45R	£15.00	£12.95
12" TITAN T12/60P	£22.50	£14.95
12" TITAN T12/100A 100w	£30.00	£19.95
12" CELESTION G12M	£18.60	£11.95
12" CELESTION G12H 30w	£22.00	£14.95
12" CELESTION G12/50 50w	£25.75	£18.95
12" GOODMANS 12 PD	Sp. Price	£21.95
12" GOODMANS 12 PG	Sp. Price	£18.95
12" FANE 'SPECIALIST' P.A. 80	£29.95	£19.95
12" " DISCO 80	£29.95	£19.95
12" " DISCO 100	£31.95	£21.95
12" " GUITAR 80L	£28.95	£18.95
12" " GUITAR 100L	£31.95	£19.95
12" " GUITAR 80B	£29.95	£18.95
12" CRESCENDO 80	£44.95	£34.95
12" " 80LT	£49.95	£39.95
12" FANE CRESCENDO 12A	£64.45	£41.95
12" " 12L	£67.67	£39.95
12" " 12 BASS	£63.95	£39.95
15" TITAN T15/60 60w	£26.00	£17.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£29.95
15" FANE 'SPECIALIST' BASS 85	£41.95	£29.95
15" " BASS 100	£44.50	£31.50
15" GOODMANS 15P	Sp. Price	£23.95
15" FANE CRESCENDO/15	£51.95	£51.95
15" " BASS	£85.95	£51.95
15" " 15/100LT	£74.89	£51.95
15" " 15/160 160w	£72.23	£72.95
15" " COLOSSUS 200w	£121.91	£72.95
18" TITAN T18/100 100w	£51.00	£39.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18C	£53.00	£41.5
18" FANE CRESCENDO 18A	£114.97	£72.95
18" " BASS	£101.86	£59.95
18" " COLOSSUS 200w	£129.81	£76.00

HORN UNITS

(Carr. 85p)

CELESTION MH1000 25w	£17.00	£13.75
FANE 910 MK 11 50w	£17.75	£10.99
" 920 100w	£62.00	£44.50
" 144 30-50w	£7.95	£4.95
" 173 50w	£11.75	£7.95
" 1104 50-70w	£16.95	£10.95

HIGH POWER 'CROSS-OVERS'

FANE HPX1R or HPX2R Carr. 35p **£3.65** **£2.25**

ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on' Carr. £1	£41.95	£35.95
TITAN T1H 70w Carr. £1	£33.00	£23.95
TITAN TS2H 100w Carr. £1	£39.00	£23.95
TITAN T2H Carr. £1	£39.00	£26.95

EXTRA SPECIAL MAIL ORDER OFFER TITAN TA 50A 50w AMPLIFIER



High sensitivity
Multi purpose
three ind.
controlled inputs.
Controls Bass,
Treble, presence.
Robust, well styled compact cabinet. Black Vynidie covered. Attractive Black/Silver Fascia.
12 months Guarantee. Carr £1

£39.95

Also for personal shoppers only
**AMPS, T'TABLES, JINGLE MACHINES,
DISCO CONSOLES, LIGHTING, CABINETS,
CREDIT TERMS AVAILABLE** orders **£20** over

Phone orders accepted from Access & Barclay card holders.

403 SAUCHIEHALL STREET **GLASGOW**
Tel: 041 332 0700

Mail Orders/Export enquiries only... to 24 Newgate Shopping Centre, NEWCASTLE. Add £1 carr. on Hi-Fi spkrs. or kits. Otherwise add £1.25 (12" Spkr), £1.50 (15") £2.50 (18")

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
6.3V 1.5A £2.45; 3A £3.00; 6A £3.50; 12V 1.5A £3.00; 3A CT £5.30; 6A CT £6.85; 15V 0.5A £2.50; 18V 1.5A CT £5.30; 24V 1.5A CT £5.30; 3A CT £6.85; 5A CT £14.00; 8A CT £23.00; 12A CT £30; 40V 3A CT £10.00
TWIN SEC TRANSFORMERS: Prim 240V ac.
6V 0.5A + 6V 0.5A; 9V 0.4A + 9V 0.4A; 12V 0.25A + 12V 0.25A; 20V 0.15A + 20V 0.15A; all at £3.50 each; 15V 0.75A + 15V 0.75A £4.85; 15V 1.5A + 15V 1.5A £7.00; 18V 1A + 18V 1A £6.50; 18V 1.5A + 18V 1.5A £7.50; 20V 1.5A + 20V 1.5A £7.50; 12V 4A + 12V 4A £8.50; 25V 2A + 25V 2A £8.50.

MIDGIST RECTIFIER TRANSFORMERS: 240V ac.
6.3V 1.5A; 9V 0.5V 1A £2.50 each; 12-0-12V 1A or 20-0-20V 0.75A £3.00 each; 9.0-0-9.0 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A £2.50 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
0-10-12-14-16-18V 2A £5.00; 4A £7.00; 0-12-15-20-24-30V 2A £5.75; 4A £9.00; 0-5-20-30-60V 1A £7.00; 2A £8.50; 0-40-50-60-80-100-110V 1A £210.00.

MAINS TRANSFORMERS SPECIAL OFFER:

Prim 240V ac.
250-0-250V 60Ma 6.3V 1A £1.75; 250V 100Ma 6.3V 2A £2.50; 9V 3A £2.50; 20V Auto. 110/240V £1.75. 25V .3A **LOUDSPEAKERS** £1.00.
2 1/2in 8 Ω , 2 1/2in 8 or 25 Ω , 2 1/2in 8 Ω , 3in 35 Ω , 3 1/2in 3A, 26 or 80 Ω , all at £1.25 each; 5 x 3 1/2 x 8, 15 or 25 Ω , £1.50; 7 x 4 1/2 x 8, 16, 25 or 80 Ω , £1.75; 8 x 5 1/2 x 8, 25 Ω , £3.00; 8in 8 Ω , £2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER

Instant erasure of cassettes and tape spools, any diameter, demagnetises tape heads. 200/240V ac, £5.50.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.

New, British manufacture, smoothed d.c. output 20V 1.5A, plus stabilised output of 15V 100ma, plus 12V ac 0.5A output, complete with diagram, £3.25.

EDGEWILE LEVEL METER FSD 200uA

Size 19 x 18 x 20mm 800 Ω , £1.10.

CHARGING METERS 1 1/2in diameter.

2A or 3A £1.25 each; 5A or 10A £1.50 each.

SYNCHRONOUS GEARED MOTORS, 240V ac.

Brand new, built in gearbox, 1 or 20 RPH, at £1.20 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS

P.P. sec tapped 3-8-15, A-A 6K 30W, £11.50; A-A 3K 50W, £17.00; 100W (EL31, KT88, etc), £22.00.

E.C. MANUAL OF POWER AMPLIFIERS

Covers valve amplifiers 30W to 400W, 75p.

MULTIWAY SCREENED CABLE, PVC COVERED

36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way individually screened 25p per metre; fig 8 twin stereo do screened 15p.

MAINS CABLE

4 way 30p 3A; 3 core mini cable ideal for speakers; intercoms; telephones etc; £4.50 100 M.

CONDENSERS

Electrolytic, 400/400V 75p; 2000/30V 30p; 1200/75V 50p; 2200/40V 40p; 3900/100V £1.25; Paper tubular, W/E, 4/160V, 6/160V, 2/150V, each 25p, 0-1/2000V 30p.

CARRIAGE EXTRA ON ALL ORDERS

ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. enquiries, lists

46 Kenilworth Road, Edgware, Middx.

HA8 8YG. Tel: 01-958 9314

THE SINCLAIR PDM35 Digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

D.C. VOLTS 1mv-1000v (1% — 1 count)
10m Ω input

A.C. VOLTS 1v-500v.
40Hz-5kHz (1% + 2 counts)

D.C. CURRENT
1 nA-200mA (1% count)

RESISTANCE 1 Ω -20m Ω (1.5% + 1 count) **£29.80** C.W.O.

or £30.95 company or govt. purchase order
Adaptor £3.20 Padded case £3.20 30kV probe £18.92

New DM 350 3 1/2 digit multimeter at £71.28

New DM 450 @ £96 SAE for details

THE SINCLAIR MICROVISION

The amazing pocket T.V. that will pick up programs throughout the world complete with rechargeable batteries, international model

£149.95 inc VAT

UK model £99 inc VAT:

Adaptors £6.00. Battery £1.16.

Sae (for detailed Brochure ex-stock)

SINCLAIR DM 235

Portable 3 1/2 digit 6 function Multimeter

DC volts 1mv to 1000V

AC volts 1mv to 250V

AC & DC current 1uA to 1A

Resistance 1 Ω to 20m Ω

Diode test 0.1uA to 1mA

10m Ω input. DC acc 1.0% AC acc 1.5% 30Hz 10kHz

SINCLAIR ENTERPRISE

79 step programmable calculator

(Trigonometric functions, logs etc.) has seven independent memories which can be used under program control forward or backward stepping facility for examining the store programme and conditional branching under program control. We have thrown in case, mains adaptor alkaline battery and a three volume software library containing 316 programs and an instruction manual.

£23.95 + 88p postage. Rech Batts. £8.95

KRAMER & CO

We will match any lower advertised price on a cash with order basis if competitor has goods in stock

9 October Place, Holders Hill Road, London NW14 1EJ

Telex 888941 Attn. Kramer K7 Tel. 01-203 241

Mail order only. SAE for data sheets. Export enquiries welcome.



SAVBIT

handy solder dispenser
Contains 2.3 metres approx. of 1.2mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 58p inc. VAT

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71mm solder for fine wires, small components and printed circuits.
69p inc. VAT

Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.2mm solder.
Size 19A 63p inc. VAT

Handy size reels and dispensers

of the world's finest cored solder to do a professional job at home



Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

handy size reels of

SAVBIT, 40/60, 60/40 and ALU-SOL solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hinson Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. (mm)	Length metres approx.	Use	Price inc. VAT
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2.16
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.46
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2.38
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2.29



SOLDERING FLUX PASTES

'ERSIN' A non-corrosive, rosin based flux for general and electrical soldering in conjunction with 'Ersin' Multicore solders.

Ref AF14 48p inc. VAT

'ARAX' For general metal joining in conjunction with 'Arax' Multicore solders.

Ref RF10 48p inc. VAT

BIB WIRE STRIPPER and CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Model 8B 97p inc. VAT
Pat. No. 144913



EMERGENCY SOLDER

Self-fluxing, tin/lead solder tape that melts with a match. For electrical and non-electrical applications.

Size ES36 39p inc. VAT



MULTICORE DESOLDERING WICK

Absorbs solder instantly from tags, printed circuits, etc. Only needs 40-50 watt soldering iron. Quick and easy to use. Non-corrosive. **Size AB10 97p inc. VAT**

ECONOPAK

A reel of 1.2mm 'Ersin' Multicore solder for general electrical use. **Size 13A £2.59 inc. VAT**

A reel of 3mm 'Arax' Multicore solder for general non electrical use.

Size 16A £2.59 inc. VAT



Sole U.K. Sales Concessionaires
Bib Hi-Fi Accessories Limited,
Kelsey House, Wood Lane Carl
Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail price. VAT.
From electrical and hardware shops. In difficult to send direct, plus 20p P & P. Prices and specifications subject to change without notice.

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

OA2 1-20	6AMS4 -70	6F25 1-00	7R7 2-00	1487 1-00	50CD6G 4-00
OB2 40	6AN8 -78	6F26 -45	7V7 2-00	18 1-25	50EHS 2-50
OC2 50	6AQ5 -75	6F28 -55	7Y4 -80	19AQ5 -85	50L6G1 0-00
OD4 55	6A28 -40	6F32 1-00	7Z4 -80	19BG6G 1-00	66KU 1-00
LA3 80	6AR5 1-05	6GG6 1-00	8D2 -50	1906 6-50	72 -40
1A5GT 55	6AS7G 1-50	6GH8A -80	8D8 -52	1906 6-50	72 -40
1A7GT 1-00	6AT6 -60	6GK5 -75	9BW6 -90	19H1 4-00	77 -45
1B3GT 65	6AU6 -62	6GK6 2-00	9D7 -70	19Y3 -40	85A2 1-40
1C2 1-00	6AV6 -95	6GJ7 -70	9E8 -45	20J4 -70	8906 1-40
1D5 1-00	6AWSA1-15	6H9GT -60	10C2 -70	20D4 2-50	90C1 1-50
1G6GT 1-00	6AX4 -75	6J5GT -65	10C4 -60	20F2 -85	108C1 -40
1H5GT 1-00	6B8G -75	6J6 -35	10D1 1-00	20L1 1-20	150C2 1-20
1L4 -25	6BA6 -65	6J7G -50	10DE7 -80	20P1 1-00	2158G 1-00
1LD5 -70	6BC8 -90	6J7M -65	10FL12 -75	23T5G -60	5765 -35
1L6 70	6BQ6 -48	6L12 -50	10F13 -80	23Z4G -50	6057 2-00
1N5GT 1-00	6BGG6 1-00	6K7G -50	10F18 -65	20P5 1-50	1625 2-50
1R5 -50	6BH6 1-10	6K8G -50	10L14 -50	25A6G 1-00	1821 2-00
184 -40	6BJ6 -75	6K8GT -55	10LD11 -75	25L6G 1-00	5687 2-00
186 -35	6BK7A -85	6L1 -2-50	10LD12 -45	25Y5 -50	5702 1-20
1T4 -30	6BN8 1-50	6L7 1-50	10PL12 -75	23T5G -60	5765 -35
1U4 -70	6BX6 -40	6L12 -50	10P13 -80	23Z4G -50	6057 2-00
1U5 -35	6BQ7A 1-40	6L18 -2-00	10P14 2-50	26Z5 -75	6060 2-00
2K5 -75	6BR7 1-00	6L19 2-00	12A6 1-00	25Z6G 1-00	5687 2-00
2X2 -70	6BR8 1-25	6LD12 -48	12AC6 6-00	28D7 2-00	6146 4-70
3A4 -55	6BW6 3-75	6LD20 -80	12AD6 -60	30A5 -75	6211 2-00
3B7 -55	6BW7 -65	6N7GT -70	12AE6 -60	30C1 -80	6463 2-00
3D6 -40	6BX6 -40	6PL12 -60	12AT6 -45	30C15 1-00	6550A 6-75
3Q4 -80	6BY7 -45	6P15 -48	12AT7 -52	30C17 -90	7025 2-00
3Q4SGT 1-00	6BZ6 1-50	6Q7G -75	12AU6 -50	30C18 2-25	7193 -80
384 -60	6C4 -50	6Q7GT -75	12AU7 -62	30P4 -90	7475 1-20
3V4 1-00	6C6 -45	6Q7(M) -75	12AV6 -60	30PL2 2-25	9002 -55
4CB6 -75	6C9 2-00	6R7G -70	12AX7 -62	30L3 -35	9204 1-50
4GK5 -75	6CB8A -65	6S7GT -60	12B6 -50	30L15 -75	A3042 6-00
5CG8 -75	6C12 -55	6SG7 -75	12B6E -85	30L17 -70	ACPFN3 3-00
5R4GY 1-00	6CD6G 4-00	6SH7 -70	12B7H -68	30P4MR -98	AC2PFN 1-20
5T4 2-00	6C4 -50	6Q7GT -75	12E1 3-50	30P12 -74	AC2PFN 1-20
6U4G 1-00	6CG8A -90	6S17 -70	12J5GT -40	30P19 -90	DD 1-00
6V4G 1-00	6CL6 -75	6SK7 1-00	12J7GT -70	30P15 -50	AC6PBN 1-00
6Y3GT 65	6CL8A -85	6SK7GT -70	12K7GT -60	30P18 -50	AC6PBN 1-00
6Z3 1-40	6CM7 1-00	6S17 -70	12K8 -75	30PL1 2-20	AC/PA 1-50
6Z4G 75	6C6 -75	6S7GT -75	12Q7GT -50	30PL12 -62	ACTH11 0-00
6Z4GT 1-00	6D3 -75	6G4GT 1-00	12S47 -75	30PL131-30	AL60 1-50
6Z8G 1-40	6DE7 -90	6U7G -55	12S5C -50	30PL141-50	ARF3 -80
6A7 70	6DT6A -85	6U8 -50	12S7 -55	30PL151-80	ATP4 -50
6A8G 35	6E5 -1-00	6X4 -85	12S87 -50	30AZ1 1-00	AZ1 -50
6A97 -70	6F1 -80	6X5GT -50	12S87 -50	30B35 -80	AZ41 -50
6A96 -70	6F6G -70	6Y6G -95	12S87GT -50	35L6GT -80	B36 2-00
6A95 -70	6F12 -70	6Y7G 1-25	12S87GT -50	35Z4 -55	B719 -50
6A98 -55	6F14 -70	7A7 1-00	12S87GT -50	35W3 -80	B729 -50
6A95 -45	6F15 -75	7B6 1-00	12S87GT -50	35Z4GT -70	BL33 2-00
6A98 -45	6F18 -80	7B7 1-00	12S87GT -50	35Z5GT -60	CL33 2-00
6A95 -45	6F19 -80	7D6 2-00	12S87GT -50	35Z6GT -60	CV6 -60
6A95 -25	6F23 -80	7F8 2-00	12S87GT -50	35Z7 -60	CV63 -60
6A96 -70	6F24 -80	7H7 1-00	12S87GT -50	35Z8 -70	CV988 -25

CY1C 1-00	HBC90 -60	EF95 -45	HN309 1-70	PEN25 1-00	UCH81 -60	2N3703 -23	BF153 -21
CY31 1-00	EDC91 -65	EF97 -40	HVR2 1-00	PEN45 1-00	UCL82 -75	2N3709 -23	BF159 -30
D1 -50	EFB80 1-00	EF98 -90	HVR2A1 0-00	PEN45DD 1-00	UCL83 1-00	AA119 -18	BF163 -23
D63 -50	EFB83 -45	EF183 -50	KT2 -90	PEN46 1-00	UF1 -00	AA120 -18	BF173 -44
DAC32 1-00	EFB89 -40	EF184 -65	KT8 3-00	PEN45DD 1-00	UF80 -50	AA129 -18	BF180 -35
DAP91 -35	RBL21 2-00	EF804 6-25	KT32 1-00	PEN45DD 1-00	UF86 -50	AZ13 -21	BF181 -47
DAP96 1-00	EC52 1-00	EBH90 -75	KT41 1-00	PENDD 1-00	UF98 -52	AC107 -18	BF185 -47
D90 70	EC53 1-00	EL30 -70	KT44 1-00	PENDD 1-00	UL41 -90	AC113 -30	BFY50 -26
DD4 -80	EC64 1-00	EL34 -48	KT44 1-00	PENDD 1-00	UL41 -90	AC126 -14	BFY51 -23
DF33 1-00	EC68 -84	EL34 2-50	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF91 -30	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF92 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF93 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF94 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF95 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF96 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF97 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF98 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF99 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF100 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF101 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF102 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF103 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF104 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF105 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF106 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF107 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF108 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF109 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF110 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF111 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF112 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF113 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF114 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF115 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF116 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF117 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF118 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF119 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF120 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF121 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF122 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF123 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF124 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF125 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF126 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF127 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF128 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF129 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF130 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF131 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF132 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF133 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF134 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF135 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23
DF136 -25	EC68 -84	EL37 3-00	KT44 1-00	PENDD 1-00	UL41 -90	AC127 -20	BFY52 -23



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V. 0.47, 1.0, 2.2, 4.7 & 10 mds.—5p, 22, 47—5p, (50V)—6p, 100—7p, (50V)—8p, 220—8p, (50V)—10p, 470—11p, (50V)—15p, 1000/15V—15p, 1000/25V—18p, 1000/40V—35p.

Subminiature bead tantalum electrolytics. 0.1, 0.22, 0.47, 1.0 at 35V, 4.7 at 6.3V—8p, 2.2/35V & 4.7/25V—9p, 10/25V, 15/16V—12p, 22/16V, 33/10V, 47/6V, 68 & 100 at 3V—14p.

Mullard Miniature Ceramic E12 Series 63V 2%. 10 pf. to 47 pf.—3p, 56 pf. to 330 pf.—4p.

Vertical Mounting Ceramic Plate Caps. 50V, E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p.

Polystyrene E12 Series 63V, Hor. Mounting. 10 pf. to 1000 pf.—3p, 1200 pf. to 10000 pf.—4p.

Mullard Polyester 250V Vert. Mtg. E6 Series. .01 to .1—4p, .15, .22—5p, .33, .47—8p, .68—11p, 1.0—14p, 1.5—20p, 2.2—24p.

Mylar (Polyester) Film 100V, Vertical Mtg. .001, .002, .005—3p, .01, .02—4p, .04, .05—5p.

Miniature Film Resistors Highstab. E12 5%.
0.125 watt 10Ω to 2MΩ..... 1p
0.250 watt 1Ω to 10MΩ (10% over 1M)..... 1p
0.500 watt 10Ω to 2MΩ..... 1p
1.000 watt 10Ω to 10MΩ..... 1p

IN4148—3p, IN4002—5p, IN4006—7p, IN4007—8p, BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—3p.

20mm, circuits 15, 25, .5, 1.0, 2.0, 3.0 & 5A—3p. Printed Circuit Holders for 20mm, fuses—8p.

Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

CRYSTALS brand-new .002% precision HC18/U wire leads. £2.95 each, U.K. post paid, No V.A.T.: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7, 18.0, 20.0, 48.0, 100.0 MHz. Also 100 kHz/HC13 and 1.0 MHz .005%, wires or pins, £3.25, 455 kHz/HC6 £3.95. Any freq. 2.5—180 MHz, made six weeks, £3.65. Also AM/CW/SSB COMMUNICATION RECEIVER low-cost modules and kits. New range being prepared. Send S.A.E. for details when ready. P. R. GOLLEGE ELECTRONICS, Merriott, Somerset. TA16 5NS. Tel: 0460 73718.

VALVES

Radio—T.V.—Industrial—Transmitting Projector Lamps and Semiconductors
We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 30p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers are not liable for clerical or printers' errors or their consequences.

THE VINTAGE WIRELESS COMPANY

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.A.E. with enquiries and for monthly newsletter.
THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

D.Y.M. THERMOMETER KIT



Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB, ICL7106, and all components and instructions to make a 0-200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (PP3 battery) ONLY £21.99

TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions.

NEW! TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. £8.99
—Extension kit for TD300K permits operation from another location, two-way switching, etc. £1.50


TS300K—TOUCHSWITCH-DIMMER—One a ternate ON/OFF action. Small knob for presetting lamp brightness. £8.50

TS300K—ON/OFF TOUCHSWITCH. Two touch plates £4.30

TSA300K—AUTOMATIC TOUCHSWITCH. Time delay variable 2 secs to 3 1/2 mins. £4.30

LD300K—300W LIGHTDIMMER KIT £3.00

24 HR. CLOCK/APPLIANCE TIMER KIT

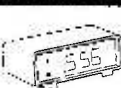

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer I.C., 0.6" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions. £14.90

White box 56 x 131 x 71mm with red Acrylic window £2.20

White box as above ready drilled for kit £2.50

Ready built in box, incl. mains cable £22.50

400V PLASTIC TRIACS, OPTO COMPONENTS

400V PLASTIC TRIACS	OPTO	COMPONENTS
3A 58p	0.2" dia LEDs	555 28p (4 @ £1)
4A 74p	Red 12p (E1/10)	741 22p (5 @ £1)
5A 84p	Green 20p	LM3911
6A 105p	Yellow 20p	Temperature control IC £1.00
7A 165p	DL727 £1.50	ZN1034E £1.80
8A 190p	LCD 0.5" £8.10	ICL7106 £9.25
9A with trigger 80p	LDR sm 50p	TIC106D SCR 30p
10A isolated tab 80p	ORP12 50p	Diac 20p
	Neon 8p	2N6027 34p
		AY-5-1230 £4.50

QUANTITY DISCOUNTS ON REQUEST
ADD 8% VAT + 25p P&P. Callers by appointment only.
T. K. ELECTRONICS
106 STUDLEY GRANGE ROAD, LONDON W7 2LX

Electronic timer unit 240V a.c./6-12V d.c. 43p	Chrome telescopic aerial 6.3in. to 35.5in. 85p
Small reed switch 10p	Micro switches, coin operated 45p
Large reed switch 15p	DPDT 25p, TIL209
Key switch and key £1.25	Green LEDs 25p, TIL209
Type recorder motor, 9V d.c. 14in. x 2in "REG" 75p	Red 15p, Clips 3p
BC107/8/9 12p	Enamelled copper wire 32, 34, 36, 38, 40 SWG 1p ft.
ORP12 75p	

Resistors 2p each. Prices inc. VAT. Add 18p post.
GRIMSBY ELECTRONICS
95 Lambert Road, Grimsby, S. Humberside
100's of bargains at our shop. List 10p.

ATTENTION SWL'S & DXers. HIGH QUALITY, LOW COST equipment. ATU's, Preselectors etc., covering medium & short wave. S.A.E. details. AMTEST, 55 Vauxhall Street, Worcester WR3 8PA.

CODESPEED

Electronic Mail Order

T03 HEAT SINKS !!! Two types of heat sink. Ex-equipment, but condition as new. Most still contain a power transistor (condition unknown). Christmas tree type, 92 x 66 x 35 mm 20p each. Rectangular type 130 x 63 x 32 mm 30p each. Please add 25p per heat sink post and packing.

PACK M1 2 Calculator keyboards. Each has 17 keys and two switches. Only £1.00.

PACK M2 1 x 2102, a 1024 bit static RAM. The most popular of all RAM's in professional or amateur electronics. With data sheet £1.25.

PACK M3 Build your own calculator! MM5725 calculator chip and data book. (Not compatible with Pack M1) £1.00.

CALCULATOR PACK M4 Contains a production line reject calculator. Either fix them (not much wrong with some we checked) or strip them for spares (which ever part is defective the rest must be good value for money—case/key/board/display/chip/PCB). We include all the info. we can find on repairing calculators. What a bargain at £2.50.

PACK C1 10 x 12 pin Hybrid circuits each containing 16 resistors/capacitors Useful values. Ideal for semiconductor circuits and PCB miniaturisation. With data, 10 hybrid circuits for 50p.

PACK P1 An MM5330 Digital Voltmeter I.C. Now build your own digital multimeter or panel meter using this versatile chip. With data and circuit diagram £3.95.

PACK T3 1 x MM5316 Digital Alarm Clock I.C. 12 or 24 hour Will drive LED, LCD or fluorescent displays. With full instructions £2.75.

PACK T4 1 x 0.8" giant multiplexed red LED Clock Display. Common cathode, 3 1/2 digit with am/pm in diator. An excellent display for your digital clock project at only £3.95.

PACK E2 An 8 digit calculator style Liquid Crystal display, 0.33" high digits with right hand decimal points and overflow indicator. With data. £2.95.

PACK E3 Same as Pack E2 but with 0.5" high digits. £4.25.

PACK E6 Contains a brand new 6 digit Texas Instruments LED display. Multiplexed with built-in bubble magnifiers. 0.1" high digits. Common cathode. £1.00.

PACK E8 A miniature 5 digit, 7 segment 0.9" common cathode LED display. Mounted on 16 pin dual-in-line I.C. package. Terrific value at only 75p.

Satisfaction guaranteed or return complete pack for replacement or refund.

Postage and Packing please add 25p (Overseas orders add 60p)

For free catalogue send stamped addressed envelope

CODESPEED, P.O. Box 23, 34 Seaford Road, Copnor, Portsmouth, Hants. PO3 5BJ

TUNBRIDGE WELLS COMPONENTS. BALLARD'S.
108 Camden Road, Tunbridge Wells. Tel: 31803. No Lists. Enquiries S.A.E.

Record Accessories

STYLI for Hi-Fi. Music Centres. III. List free for S.A.E. also cartridges, leads, accessories. Details—FELSTEAD ELECTRONICS (PW), Longley Lane, Gatley, Cheshire. SK8 4EE.

Tapes

Tapes. Low noise cassettes. Free library cases. Delighted or money back. C60 six or more 29p each. Sample 32p. No more to pay. A. W. & J. M. West, 56 Frankwell Drive, Coventry CV2 2FB.

Service Sheets

SERVICE SHEETS—COLOUR TV SERVICE MANUALS

REG OFFICE REAR 14B QUEENS PARADE, NORTH EALING W5 3HU
Service Sheets for Mono TV Radios, Record Players and Tape Recorders £1. Please send large Stamped Addressed Envelope. We can supply manuals for most makes of Colour Television Receivers by return of post
B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON
H.M.V. MARCONI AND MANY MORE
Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court S.A.E. for details. MAIL ONLY TO

G. T. TECHNICAL INFORMATION SERVICE
10 Dryden Chambers, 119 Oxford St., London W1R 1PA

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc., £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p. and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford RM7 0XU (Tel. Romford 66841).

TELEVISION TRAINING

18 MONTHS full-time course for beginners to include all the undermentioned subjects. Short courses, combining one or more subjects, for applicants with suitable education and electronics background such as C & G, HND BSc etc.

13 WEEKS TECHNICAL MATHEMATICS & ENGLISH

13 WEEKS ELECTRONICS & RADIO

13 WEEKS MONOCHROME TELEVISION

13 WEEKS COLOUR TELEVISION

13 WEEKS VIDEO SYSTEMS (CCTV, VCR, Teletext, etc.)

The training incorporates a high percentage of practical work.

Next session starts on April 23rd

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. PWB2, 20 Penryn Road, London SW5 9SU. Tel. 01-373 8721

Courses

COURSES-RADIO AMATEURS EXAMINATION. City & Guilds. Pass this important examination and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, professional examinations etc) write or phone—THE RAPID RESULTS COLLEGE, Dept JX1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or for prospectus requests ring 01-946 1102 (24hr Recordcall).

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order.

C. CARANNA
71, Beaufort Park, London, NW11 6BX
01-458 4882

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p. plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

Books and Publications

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set £5.00 with circuit (if requested). Free catalogue unique TV/other publications. AUSE (PW), 76 Church Street, Larkhall, Lanarkshire ML9 1HE.

Build your own P.A., GROUP & DISCO SPEAKERS by R.F.C. Stephens

Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE DALESFORD SPEAKER BOOK by R.F.C. Stephens. This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING,
5 SWAN STREET, WILMSLOW, CHESHIRE.

For Sale

RAINBOW RIBBON CABLE at silly prices. S.A.E. for details. TRADING POST, 4 Castle Street, Hastings, Sussex.

42 COPIES of PRACTICAL WIRELESS between June 1972 and Sept. 1977 Includes every issue from November 1973 to June 1976. First reasonable offer. Buyer collects. Tel. Preston 43335.

DISCOUNT BOXES, INSTRUMENT CASES, COMPONENTS



Boxes from 48p. LM-741c 8 pin diol I.C.S. only 22p. Discounts up to 20%

Send stamped self addressed envelope for pamphlet to

HARRISON BROS. P.O. Box 55, Milton Road, Westcliff-on-Sea, Essex SSO 7LQ.

NEW BACK ISSUES of "PRACTICAL WIRELESS" available 70p each, post free. Open P.O./Cheque returned if not in stock—BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

PRACTICAL WIRELESS January 1954 to December 1978. Offers. White, 14 Oxford Road, Farmoor, Oxford.

SEEN WHISTONS CAT? 5,000 odds and ends. Mechanical/Electrical Cat Free. WHISTON (Dept. PW). New Mills, Stockport.

Ladders

LADDERS varnished 22' extd. £30. Carriage £2.80. Leaflet. Also Alloy ext. up to 62'ft. LADDER CENTRE (WLS3), Halesfield (1), Telford. Tel: 586644.

Equipment Wanted



Tempting prices paid for

Oscilloscopes-Signal Generators
DVM's-Small Computers
Receivers-Teletypes-VDU's etc.

Electronic Brokers Ltd
49/53 Pancras Road
London NW1 2QB
Telephone 01-837 7781

Miscellaneous

DART STATIONERY

Presents For the Amateur

QSL CARDS. Personalised to your own choice, also LOG BOOKS. Loose leaf binder plus 100 printed log sheets £2.50, extra packets of 100 sheets £1.50. Catalogues available containing complete range of radio stationery, price 45p.

For the D'Xer

RECEPTION REPORT LETTERS. Professionally styled letters printed in two colours and supplied in pads of 100 letters.

1 pad £1.80
2+ pads £1.60 each

EVERY ORDER CARRIES A MONEY BACK ASSURANCE IF NOT COMPLETELY SATISFIED

Please send cheques or P.O. payable to:

DART STATIONERY
20 Bromley Road, LONDON E17 4PS

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept. No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA 6LT.

BELLS AND SIRENS

CARTERS SIREN £5.53
INDUSTRIAL SIX INCH
BELL £8.27
PRICES INCLUSIVE

BARGAIN OFFER

6 to 12v D.C. 12v D.C.
The incredible value of this self-contained smoke detector/fire alarm, similar unit of which normally sell for between £30-50, is enough to warrant special note. The Dormalarm uses the professional ionisation chamber principle with a radio active source of less than one microcurie of Americium 241, which detects the products of combustion at the very earliest stage. It is powered by a single 9V Mallory Duracell MN 1604 battery (supplied) which will last greater than one year. The built-in sounder is very loud (85dB at 3 metres). When the battery is running low, the Dormalarm will give periodic beeps, reminding you to change the battery. As there is no wiring, installation is simplicity itself—just 3 screws. The whole unit is contained in an attractive circular white ABS moulded case, size 175mm diameter x 37mm. PRICE—AN INCREDIBLE £18.95 INCLUSIVE. Trade Enquiries Welcome. Send Cheque, P.O. to:

CWAS ALARM
11 Denbrook Walk, Bradford BD4 0QS.
SAE for full Price List of Professional Burglar Alarm Equipment

ALFAC etch resist transfer and other p.c. board drawing materials available from stock. S.A.E. details. RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford upon Avon CV37 9NF.

PW October issue 2m MOSFET CONVERTER units from the author GACFY. Kit of parts for complete PCB £7.80. Ready built and aligned units boxed £17.00. Parts available separately. 38-6667 Mhz Xtal £2.75. PCB £1.85. 1750 Tone Burst Board, Tested and Aligned 1.4in sq. £3.50.

SPECTRUM COMMUNICATIONS

12 Weatherbury Way, Dorchester, Dorset DT1 2EF.
Prices inclusive of P. & P.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns
ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14 & 16	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited.

AERIAL BOOSTERS Improve weak VHF Radio and Television reception, price £5.00 S.A.E. for Leaflets.
ELECTRONIC MAILORDER LTD., Ramsbottom, Bury, Lancashire BL0 9AG.

GUITAR/PA/MUSIC AMPLIFIERS

100 watt with superb treble bass overdrive, 12 months guarantee. Unbeatable at £40; 60 watt £35; 200 watt £56; Twin channel sep treble/bass per channel £52; 60 watt £46; 200 watt £68; 100 watt four channel sep treble/bass per channel £66; 200 watt £79; Slaves 100 watt £32; 200 watt £48; Fuzz boxes great sound £7.90; Bass fuzz £8.50; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £36; Twin channel £95; Bass Combo £95; Speakers 12in. 100 watt £22.50; 60 watt £14.50; Shure mic unidyn B £26.

Send Cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave, Dukinfield, Cheshire.
Tel. 061-344 5007

BUILD your own 771B type metal detector, details S.A.E. 117 Horton Road, Brighton BN1 7EG.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1.13, SUB C £1.47, HP 11 (C) £2.15, HP 2 (D) £3.27, PP3 £4.09 (PP3 not suitable for fast charge). PP3 charger £5.31. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec, and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc... 1.2 amp hr. 6v. £4.40 6 amp hr. 6v £5.65.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to: **SOLID STATE SECURITY DEPT PW.**, 10, Bradshaw Lane, Parbold, Wigan, Lancs. 0257-4726.



TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit
- Send stamped, addressed envelope for leaflet

Complete £15.95 Built & tested £20.95
KH Post £1.20 + £1.57 VAT Post £1.20 + £1.77 VAT

MINIKITS ELECTRONICS
1a CLEVELAND ROAD,
LONDON, E16 2AN

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation.
Morse by light systems available. Morse Key and Buzzer Unit for sending practice.
Prices each Cassette (including booklets) £4.50. Morse Key and Buzzer £4.50.
Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

LOSING DX?

TOO MUCH QRM? Dig RARE DX from tiring whistles and cw with a Tunable Audio Notch Filter, 350-5000 Hz, speaker amplifier, £8.90.

AR887 STILL NO RADIO 4? 200 KHz to Medium Wave Converter £9.70.

V.L.F. 7 10-150 KHz Receiver only £10.70.

MISSING RARE DX? Get on their frequency with a Crystal Calibrator, switched 1 MHz, 100, 25 KHz equal level markers to vhf, £13.80.

TIME? MSF 60 KHz RECEIVER £13.70 or with sequential YEAR, MONTH, DATE, DAY, HOURS, MINUTES, SECONDS display parts (no case or pcb) £24.40.

HOW LOW CAN YOU GO? 100-600 KHz to 4.1-4.6 MHz Converter only £9.90.

Europe add 40p. Each easy assembly kit includes all parts, printed circuit, case, postage etc, (UK) money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (PP) Old School Lane, Milton, Cambridge

SINGLES HOLIDAYS/Houseparties. Friendship introductions. Free details—Christian Friendship Fellowship, Dept B89, Edenthorpe, Doncaster (S.A.E.).

Aerials

G2DYM ANTI-TVI TRAP DIPOLES

NEW MODELS with Improved Design, Components and Materials

S.W.Ling OR Tx-ing at 250W P.E.P. £41.00; 500W P.E.P. Tx-ing OR "Hi-Q" for S.W.Ling £47.95; 10-160 metres Aerial Matching Unit 500 & S.W.Ling £18.25.
Inc. VAT and P & P. Send 10" x 7" 16p S.A.E. and 3 x 9p stamps for full details, aerial article, test reports and testimonials.

G2DYM Designed and Custom built by:

H. F. TELECOMMUNICATIONS (UK) LTD.
Uplowman, Tiverton, Devon

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS**

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME

ADDRESS

Send to: Classified Advertisement Manager

PRACTICAL WIRELESS,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5848

Rate
22p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS				
Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
18	2	1	3.51	0.78
70	3	1.5	4.03	0.96
108	4	2	5.35	0.96
72	10	5	7.42	1.14
116	20	10	8.99	1.32
117	30	15	10.72	1.32
175	60	30	13.98	2.08
187	60	30	17.05	2.08
226	60	30	36.74	OA

50 VOLT RANGE Pri 220/240V Sec 0-20-25-33-40-50V Volt- ages available 5, 7, 8, 10, 12, 15, 17, 20, 33, 40 or 20V-0-20V & 25V-0-25V.				
Ref	12V	24V	£	P & P
102	0.5	0.25	3.41	0.78
103	1.0	0.5	4.57	0.96
104	2.0	1.0	7.16	1.14
105	3.0	1.5	8.56	1.32
106	4.0	2.0	11.41	1.50
107	6.0	3.0	15.06	1.64
118	8.0	4.0	20.26	2.08
119	10.0	5.0	24.98	OA

MAINS ISOLATING (SCREENED) Pri 120/240V SEC 120/240V CT				
Ref	VA (Watts)	£	P & P	
*07	20	4.40	0.79	
149	60	6.70	0.96	
150	100	7.61	1.14	
151	200	11.16	1.50	
152	250	13.28	1.84	
153	350	16.43	1.84	
154	500	20.47	2.15	
155	750	29.66	OA	
156	1000	37.20	OA	
157	1500	51.38	OA	
158	2000	61.81	OA	
159	3000	86.66	OA	

HIGH VOLTAGE ISOLATOR Pri 200/220V or 450/440V Sec 110/120V CT or 200/240CT				
VA	Ref	£	P & P	
60	243	6.70	1.32	
350	247	16.43	1.84	
1000	250	37.10	OA	
2000	252	61.81	OA	

SEND 15p FOR CATALOGUE

30VOLT RANGE Pri 220/240V Sec 0-12-15-20-24-30V Volt- ages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V & 15V-0-15V.				
Ref	12V	24V	£	P & P
112	0.5	0.25	2.64	0.78
79	1.0	0.5	3.57	0.96
3	2.0	1.0	5.77	0.96
20	3.0	1.5	6.20	1.14
21	4.0	2.0	7.99	1.14
51	5.0	2.5	9.87	1.32
117	6.0	3.0	11.17	1.45
88	8.0	4.0	14.95	1.64
89	10.0	5.0	17.25	1.84

60 VOLT RANGE Pri 220/240V Sec 0-24-30-40-48-60V Volt- ages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V, or 30V-0-30V.				
Ref	12V	24V	£	P & P
124	0.5	0.25	3.88	0.96
126	1.0	0.5	5.91	0.96
127	2.0	1.0	7.60	1.14
128	3.0	1.5	11.00	1.32
123	4.0	2.0	12.52	1.84
40	5.0	2.5	15.84	1.64
120	6.0	3.0	18.06	1.84
121	8.0	4.0	25.56	OA
122	10.0	5.0	29.55	OA
189	12.0	6.0	34.06	OA

AUTO TRANSFORMERS Ref VA (Watts) £ P & P				
113	15 0-115-210-240	2.48	0.71	
64	75 0-115-210-240	4.01	0.96	
4	150 0-115-200-220-240	5.35	0.96	
67	500 0-115-200-220-240	10.99	1.64	
84	1000 0-115-200-220-240	18.78	2.08	
93	1500 0-115-200-220-240	23.36	OA	
95	2000 0-115-200-220-240	34.82	OA	
73	3000 0-115-200-220-240	59.21	OA	
80s	4000 0-115-200-220-240	76.86	OA	
57s	5000 0-115-200-220-240	89.50	OA	

CASED AUTO TRANSFORMERS 240V cable in 115V USA flat pin outlet				
VA	Ref	£	P & P	
15	4	4.96	0.96	113W
75	7	7.73	1.14	64W
150	10	10.01	1.14	4W
200	9	9.92	1.45	69W
250	10	10.49	1.45	69W
500	19	17.17	1.64	67W
750	23	23.41	1.76	83W
1000	27	27.88	OA	84W
1500	26	26.02	OA	93W
2000	49	49.97	OA	95W

Prices correct 21-11-78. Please add VAT after P & P.

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.57	0.55
212	1A, 1A	0-6, 0-6	2.85	0.78
13	100	9-0-9	2.14	0.38
235	300, 330	0-9, 0-9	1.99	0.38
207	500, 500	0-8-9, 0-8-9	2.77	0.71
208	1A, 1A	0-8-9, 0-8-9	3.53	0.78
236	200, 200	0-15, 0-15	1.99	0.38
214	300, 300	0-20, 0-20	2.80	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.63	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	6.04	0.96
239	50	12-0-12	2.57	0.38

MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res-150kΩ 1000Ω/V Bargain £6.45. VAT 8% P & P 62p.

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V DC current to 250mA. Resistance to 3 Mohms. 5" x 3 1/2" x 1 1/2". £14.36. VAT 8%. P & P £1.05.

TEST METERS		
AVO 8 MK5	£81.70	Megger BM7 battery
AVO 71	£33.50	U4315 Budget meter
AVO 73	£44.20	20kΩ/VDC2K/VAC
AVO MM5	£28.66	1000V AC/DC 2.5A
Wee Megger	£66.90	AC/500K res. in
EM272	£53.70	robust steel case
DA116 digital	£102.00	and leads
AVO TT169 in circuit	£34.75	Transistor Tester

NEW RANGE TRANSFORMER
Pri 120V or 220/240V Sec 0-36-48 twice to give 36-0-36V 48-0-48V 72V or 92V.

Ref	Price	P & P
3A	14.70	1.48
4A	18.77	1.84
5A	26.64	2.15

PANEL METERS			
41 x 41mm		82 x 82mm	
0-50μA	£5.50	0-50μA	£6.70
0-500μA	£5.50	0-500μA	£6.70
0-1mA	£5.50	0-1mA	£8.40
0-30V	£5.50	0-30V	£8.40

VU Ind. Panel 90mm 250mA
VU Ind. Edge 54 x 14mm 250μA FSD
65p Carriage 8% VAT.

Special Offer—Quality low noise cassette tapes. C60 30p, C90 42p. P & P 15p. VAT 8%.

TMK 500
30K/V Mirror scale meter, AC 0-2-5-10-25-100-250-500-1000V DC 0-25-1-2-5-10-25-100-250-1000V. Resistance 0-6K-60K-6M-60M. auto a/load protection £23.30. P & P £1.05. VAT 8%.

COMPONENT PACKS

65 High Quality Metal Oxide
5% 1/2 + 1/2 W resistors.
150 Mixed Value Capacitors.
10 Reed Switches.
50 Wire Wound Resistors
10 3000μF 30V Caps.
25 Assorted presets.
50 3 tag terminal strips.
Hardware pack nuts, bolts, washers, insulators
200 Mixed Resistors
70p ea. P & P 40p. VAT 12 1/2%

BRIDGE RECTIFIERS

100V	100A*	£2.10
200V	2A	£0.45
400V	4A	£0.85
400V	6A	£1.25
500V PM7A6	12A	£2.55*

VAT 12 1/2% 15p P & P *VAT 8%

AMPLIFIER MODULES

10W	(AL30)	£3.75
25W	(AL60)	£4.57
35W	(AL80)	£7.15
125W	(AL250)	£17.25
Power Supply PS12		£1.30
Power Supply SPM80		£4.25

VAT 12 1/2% P & P 35p.

250VA ISOLATOR

0-200-220-240V
0-240V centre tap.
250VA £5.20 P & P 96p Ref. 62.

Aluminium Boxes—with 1/2" lip lid & screws.

B1	5 1/2"	2 1/2"	1 1/2"	62p
B2	4"	2"	1"	62p
B3	4"	2"	1"	62p

P & P 29p. VAT 8%.

S-DECS

Solderless bread boarding
S Dec 70 contacts £3.10
T Dec 208 contacts £4.35
U Dec "A" for I.C.s etc £4.50
U Dec "B" for I.C.s etc £6.99
VAT 8% P & P 40p

ANTEX SOLDERING IRONS

15W £3.75
25W £3.95 Stand £1.52 +
VAT 8% P & P 46p VAT 12 1/2%

Electronic Construction Kit

Home electronic teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. £8.29 + 96p p & p VAT 8%.

ABS PLASTIC BOXES

inset brass nuts, slots to take P.C. cards flush fitting lid.
PB1 180mm x 62 x 40 65p
PB2 100mm x 75 x 40 73p
PB3 120mm x 100 x 45 87p
PB4 215mm x 130 x 85 £2.54
P & P 66p VAT 8%

Miniature Transformers

Ref	Price	PP
171 500 ma	2.09	.45
172 1A	2.96	.78
173 2A	3.59	.78
174 3A	3.75	.86
175 4A	5.73	.96

P.W. Purbeck oscilloscope transformer in silk 250-0-250 6.3V, 12.9V

£6.20 p & p 90p

BE3 100V Line to 4n 7/10W £2.05

p & p 66p

BE4 0-120V x 2 (120V or 240V)

Screen Sec. 9-0-9V

1 amp £2.40 p & p

71p

BE5 15W matching trans. sec 150V suit

EL89 £1.50 p & p

30p

BE6 Pn 0-220V sec

4500V 10ma £4.50

p & p £1.00

BE7 0-110-120-220V Pn 240V sec

20V 1 amp £1.50

p & p 30p

BE8 0-240 15-0-15V

2A £1.50 p & p 70p


Ref 30-240-240 Iso-

lators 200VA £4.29

p & p 96p

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

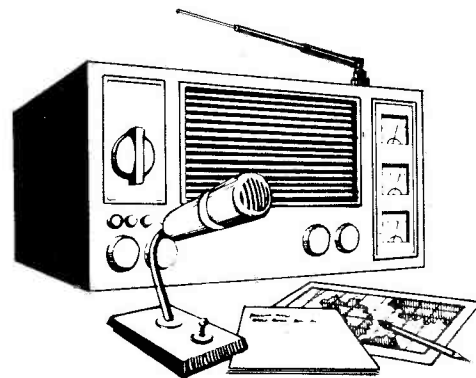

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WC279

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT	0-65	6AX4GTB	1-00	6CY5	1-00	12AT6	0-60	ECF200	0-90	EM84	0-60	PCL81	0-65	PY82	0-55	UCC84	0-75
1R5	0-50	6AX5GT	1-30	6CY7	1-00	12AT7	0-50	ECF201	0-90	EM87	1-00	PCL82	0-80	PY83	0-70	UCC85	0-55
1X2B	1-20	6BA6	0-45	6D09B	1-45	12AU6	0-65	ECF801	0-95	EY81	0-50	PCL84	0-75	PY88	0-75	UCF80	0-75
5AT8	0-80	6BE6	0-48	6DT6	0-80	12AU7	0-47	ECF802	0-95	EY87	0-50	PCL86	0-85	PY500A	1-30	UCH42	0-90
5T4	0-75	6BF6	0-85	6DT8	0-80	12AV6	0-85	ECF802	1-10	EY88	0-55	PCL805	0-75	TT21	7-80	UCH81	0-65
5U4G	0-60	6BF6	0-75	6DW4	0-90	12AV7	1-00	ECF802	0-55	EY500A	1-50	PCL805	0-75	TT22	7-80	UCH81	0-70
5U8	0-75	6BG6G	0-30	6ES5	1-00	12AX7	0-55	ECF802	0-80	EZ80	0-50	PCL805	0-75	TT22	7-80	UCH81	0-70
5V4G	0-60	6BH6	0-85	6EV5	1-50	12AY7	0-85	ECL80	0-75	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
5X4G	0-80	6BJ8	1-20	6EW6	0-80	12BA6	0-67	ECL81	0-75	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
5X8	0-90	6BJ7	0-65	6GCH8A	0-80	12BF6	0-75	ECL82	0-75	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
5Y3GT	0-65	6BK4B	1-40	6GK5	0-70	12BH7A	0-75	ECL83	1-15	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
5Z4GT	0-65	6BN4A	0-90	6GK8	0-90	12BL6	0-70	ECL84	0-70	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AB7	0-60	6BN6	0-80	6J4	1-20	12B08	0-90	ECL85	0-65	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AC7	0-80	6B07A	0-65	6J5GT	0-80	12BY7A	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AD8	0-60	6BR8A	1-20	6J6	0-55	12CJ6	0-90	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AF4A	0-60	6BS7	2-30	6J7	0-80	19A05	0-75	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AG5	0-85	6BU8	0-85	6K5GT	0-75	19B06G	0-50	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AG7	0-85	6BW7	1-00	6K6GT	0-85	35A3	0-70	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AH6	0-95	6BZ6	0-65	6L6GT	0-85	35B5	0-65	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AJ5	0-65	6BZ7	0-70	6N7GT	0-85	35C5	0-70	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AK5	0-55	6C4	0-55	6D7	0-90	50C5	1-00	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AK6	0-75	6C5GT	0-60	6SA7	0-80	50EH5	0-85	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AK7	0-85	6C6	0-50	6SG7	0-80	DAF98	0-60	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AL5	0-40	6C8G	0-60	6SK7	0-80	DF96	0-70	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AM6	0-70	6C8B	0-55	6SL7GT	0-70	DK92	1-00	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AM8	0-70	6C8T	0-70	6SN7GT	0-70	DL96	0-60	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AN5	2-50	6C8A	0-75	6S07	0-80	ECC84	0-60	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AN6	0-85	6CM7	0-60	6SR7	0-80	ECC85	0-48	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6A05	0-85	6CN7	1-20	6V6GT	0-65	ECC86	1-25	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AS6	1-00	6CQ8	0-75	6X4	0-60	ECC88	0-75	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AS7G	1-20	6CS7	0-85	6X5GT	0-60	ECC89	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AT6	0-75	6CU5	1-00	6X8	0-80	ECC189	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AU6	0-60	6CUG	1-00	12AB	0-60	ECC189	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AV6	0-75	6CW4	3-75	12AL5	0-65	ECC189	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70
6AW8A	0-75	6CX8	1-00	12AQ5	0-60	ECC189	0-80	ECL86	0-85	EY501	0-90	PCL805	0-75	TT22	7-80	UCH81	0-70

OSCILLOSCOPE TUBES

current production. Made in USSR

One inch Tube Type 3L011. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00***. Three-inch tube Type 3BP1. This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50**. 14-pin base for the above **£0.80**.

VAT is not included. Please add 12½% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR **£0.30**

NEW! BUILD-IT-YOURSELF TEST GEAR KIT

BASIC SERVICING
INSTRUMENTS WITH
EASY STAGE BY STAGE BUILDING
INSTRUCTIONS—IDEAL FOR THE AMATEUR

MULTI RANGE TEST METER

A general purpose meter covering all usual
ranges of A.C. and D.C. volts current and
resistance measurements

AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz
and variable output. Distortion less than
0.01% Ideal for HIFI Testing.

OSCILLOSCOPE

A basic 3" general purpose cathode ray
oscilloscope for simple testing and
servicing work. Sensitivity 0.3 volts/cm

SEND NOW FOR FREE DETAILS

To LERNAKITS, P.O. Box 156, Jersey.

W0279

Name

Address

SEMICONDUCTORS	BC351	0-10	8T106	1-10	IN4001/2	0-05	*TBA120A	0-80	
*A117/9	0-67	*BC547/8/9	0-10	*BU205	1-50	IN4004/5	0-08	*TBA120S	0-80
AC178	0-19	BC557	0-12	*BU208	1-60	IN4006/7	0-07	*TBA1750	1-60
AC187	0-19	BCY70/1/2	0-15	*BU208A	1-75	*IS44	0-04	*TBA800	0-80
*AC187	0-19	BD115	0-43	*BY127	0-10	*IS920	0-06	*TBA810S	1-05
*ACY20	0-34	BD131/2/5	0-34	C1060	0-44	*IS941	0-04	W/W RESISTORS	
AD161/2	0-35	BC136/7	0-35	MJE340	0-43	2N930	0-16	2.5W, 15W	0-10
AS566	0-86	BD138/9	0-36	MJE520	0-43	2N3053	0-20	5W, 10W	0-09
*BB105A	0-27	BD140	0-36	MJE2955	1-05	2N3055	0-50	ANTEX SOLDERING	
*BB105B	0-30	BD695A	0-85	MJE3055	0-80	*2N3702/3	0-08	IRON	
BAX13	0-05	BD698A	0-65	*0A47	0-10	*2N3704/5	0-08	C-240V 15W	£3-60
BC107/8/9	0-08	BF115	0-18	*0A200	0-08	*2N3819	0-21	BARGAIN PAKS	
*BC117	0-14	*BF167	0-23	OC28	0-88	2N4443	0-80	*PAK 1	
*BC132	0-14	BF173	0-20	OC35	0-78	LINEAR IC's	100 gen. purpose		
*BC147/8	0-08	BF180/1/4	0-28	OC101	0-72	7418P	0-19	transistors including	
*BC147/8	0-08	BF185	0-26	*R2008B	0-10	5558P	0-27	BC149, 2N3703, etc.	£5-00
*BC157/8	0-09	*BF194/5	0-09	*R2010B	1-70	*IM301	0-35		
*BC159	0-09	*BF197	0-10	*TIP29	0-40	*IM380N	0-95	PAK 3	
*BC182/L	0-09	*BF198	0-16	TIP31A	0-39	LM1303N	1-50	100 mixed W/W	
*BC183/L	0-09	BF200	0-28	TIP32A	0-46	LM3900	0-60	resistors including	
*BC184/L	0-09	BF257/8/9	0-26	TIP32B	0-85	*MC1310P	1-20	2.5W, 5W, 10W, etc.	
*BC207B	0-11	BF324	0-26	TIP33B	0-88	*76003N	1-70		£3-50
*BC212/L	0-09	BF336	0-32	TIP34B	0-88	*76013N	1-30	PAK 4	
*BC213/L	0-09	*BF337	0-28	TIP41A	0-61	*76023N	1-30	100 off 74 series	
*BC214/L	0-09	*BF800	0-23	TIP42A	0-62	*76023ND	1-20	with preformed pins	
BC301/3	0-27	BFY50/2	0-18	*TZT212/B	0-16	*76033N	1-76	including 74110	
BC348	0-10	BSX19/20	0-16	*TZT302	0-11	*TA6821AXI	1-95	7430, etc.	£4-00

Discounts: 25+ 10% (on any one type). Min. Order £2.00 P&P 30p. VAT please add 8% except those marked * which are 12.5% SAE for lists Export, wholesale and industrial enquiries welcome.

K & A DISTRIBUTORS, 52 Barkway Road, Siston, Leicester, LE7 8AF Tel 0533 609391

Discounts: 25+ 10% (of any one type). Min. Order £2.00 P&P 30p. VAT please add 8% except those marked * which are 12.5% SAE for lists. Export, wholesale and industrial enquiries welcome.
K & A DISTRIBUTORS, 52 Barkby Road, Syston, Leicestershire, LE7 8AF. Tel. 0533 609391

STERNWAY ELECTRICAL LIMITED

ANNOUNCE THEIR NEW ELECTRONIC COMPONENTS
SHOP AT 3 BRIDE COURT, LONDON EC4 2AB (OFF
FLEET STREET)

SPECIAL OPENING OFFERS INCLUDE:


DENSHI BEGINNER'S CONSTRUCTION KITS

SR1A 16 Projects including Radio Receivers, Morse Code Trainer,
Warning devices, etc. **£5.95 (Post & Pkg. 85p)**

Resistance substitute boxes provide close tolerances substitution for 36
preferred values from 5Ω to 1 meg Ω with leads and clips **£3.95** post
paid.

All Component enquiries welcome on 01-353 8530 or by post. Most popular
TTL CMOS Linear Transistors in stock at keen prices.

Model TCSU1 Soldering Station

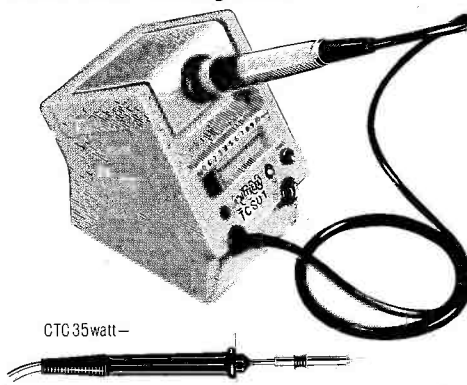

The TCSU1 soldering station with either the XTC 50 watt — 24/26 volt soldering iron or the CTC 35 watt — soldering iron for pin point precision and exceptionally fast recovery time. We have put at least twice as much power into irons which are already well known for good recovery time. The temperature control stops them from over-heating; the "fail-safe" electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station £38.10 XTC and CTC irons £14.85 inclusive of VAT and P & P.

Model CX - 17 watts



A miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak free. Only 7 1/2" long. Fitted with a 3/32" bit. £4.37 inclusive of VAT and P & P. Range of 5 other bits available from 1/8" down to 3/64".

Model X25 - 25 watts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at £4.37 inclusive of VAT and P & P. Range of 4 other bits available.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at £6.21 inclusive of VAT and P & P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.


Model SK4 Kit



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at £6.21 inclusive of VAT and P & P.


Model SK1 Kit

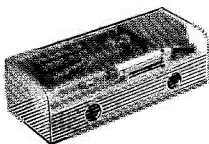This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet 'How to solder'. Priced at £6.48 inclusive of VAT and P & P.



Model MLX Kit

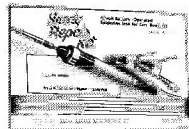
The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price £4.83 inclusive of VAT and P & P.



Now heat to any level

between 145° - 400°c

(with accuracy of 2%)

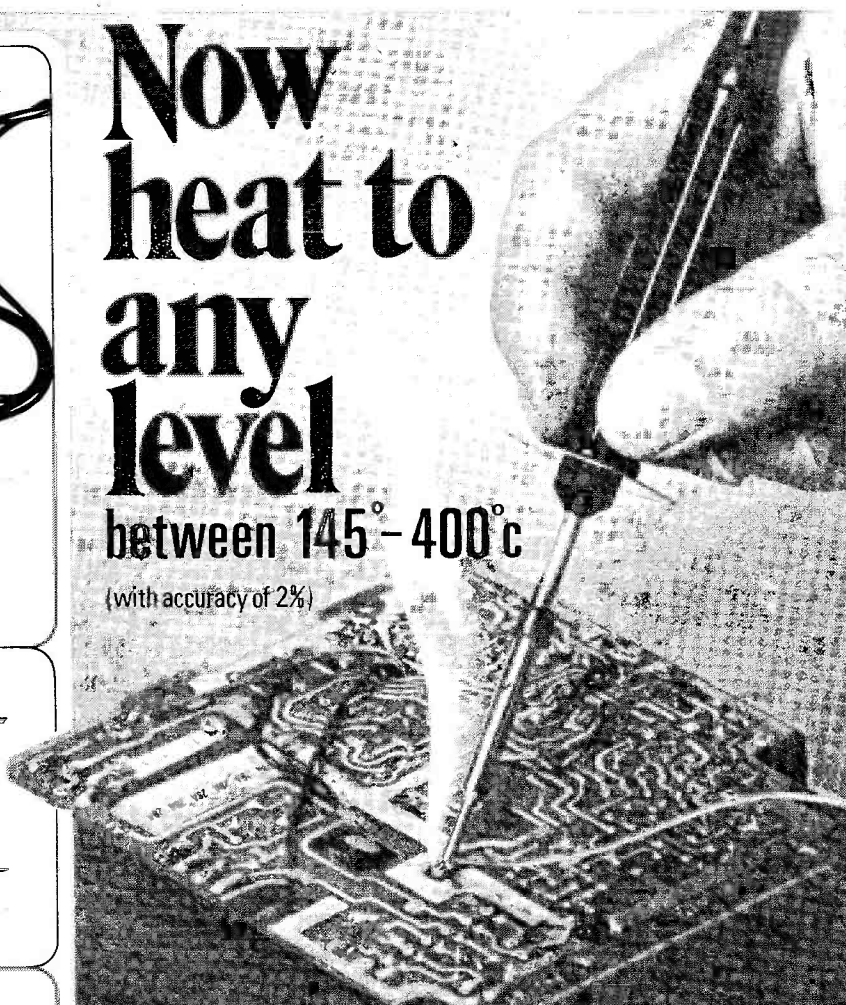

With the Antex TCSU1 Soldering Station

All Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft, giving maximum heat transference; this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are slit to make them easily interchangeable.

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,
Plymouth, Devon
Tel: 0752 67377/8
Telex: 45296

Please send me the Antex colour brochure ☐ I enclose cheque/P.O. / Giro No. 258 1000 ☐

Please send the following

Name _____ Address _____

Antex Ltd, Freeport, Plymouth PL1 1BR Tel: 0752 67377

PW2



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road,
Westcliff-on-Sea, Essex.
(Closed on Monday).

Telephone: Southend (0702) 554155.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue—send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____

PW27B

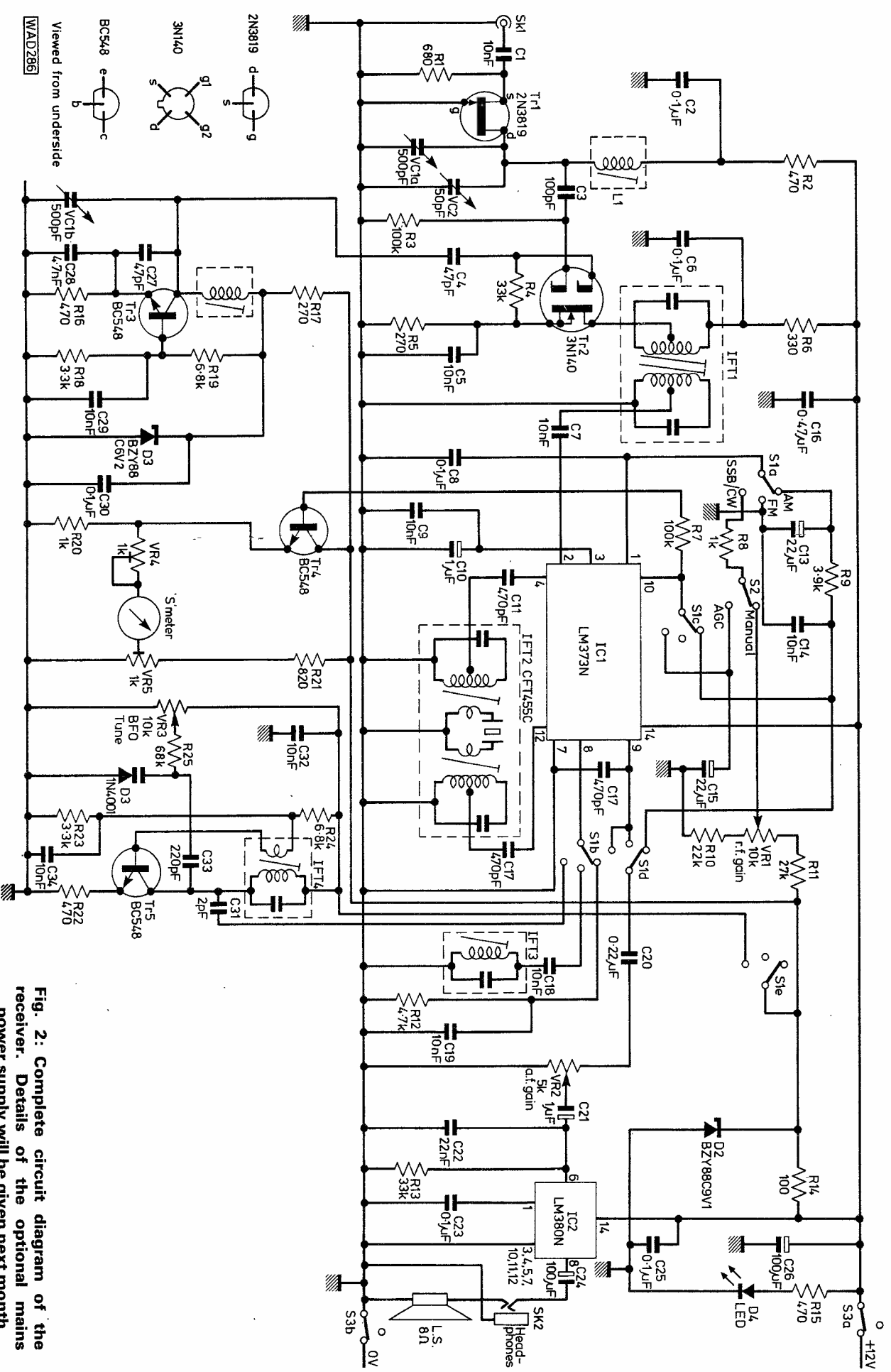


Fig. 2: Complete circuit diagram of the receiver. Details of the optional mains power supply will be given next month

practical **WIRELESS**

PULL-OUT

INDEX TO
Volume 54
MAY TO DECEMBER 1978

Note: This volume consists of eight issues only to permit Volume 55 to begin with the January 1979 issue.

Beginning with this volume the page numbering starts at 1 with each issue. Contents are indicated by page number and month of issue.

IPC Magazines Ltd
Westover House
West Quay Road
POOLE
Dorset BH15 1JG

INDEX

Volume 54

May to December 1978

EDITORIAL

A Professional Finish	20	Sept
Caveat Emptor	20	Oct
Chaos Reigns	20	Nov
Chicken and Egg	18	Aug
Crystal Gazing	18	June
Happenings	20	Dec
Standards	20	July
The British Connection	18	May

CONSTRUCTIONAL—Receiving

Aerial Tuner by F. G. Rayer	61	Oct
Car Radio Long Wave Converter by M. J. Hutchinson	37	Dec
'Dorchester' All-Band Tuner by W. S. Poel Part 1	26	Dec
DXer's Audio Filter by R. A. Penfold	52	May
'Gillingham' Frequency Readout by D. S. Coutts	44	Oct
Kindly Note	50	Dec
Image Rejection Filter by R. A. Penfold	58	Aug
'Wimborne' Music-Centre by N. B. Matthey Part 1	44	Sept
Part 2	30	Oct
Part 3	25	Nov
Part 4	46	Dec
2m MOSFET Converter by A. J. Nailer	22	Oct

CONSTRUCTIONAL—General

Battery Power Supply for PW Economy Timing Strobe by G. Gould	55	Aug
'Bovington' Tank Battle Game by D. Coutts	38	June
Kindly Note	60	July
'Burley' Stabilised Power Supply by W. S. Poel	38	Nov
Darkroom Timer by A. P. Donleavy	49	June
Digital Door Chimes by J. B. Harvey	54	Dec

Digital Lock by P. J. Wheeler	56	July
Electronic Fish Feeder by G. F. Smith	36	Sept
'Experimenter' 3-Way Power Supply Supplement		Dec
Gadgets Around the House	47	Nov
Slot Car Brake Lights, Porch Light Timer, STD Charge Timer, Door Bell Changeover Unit, Automatic Outside Light, Battery Indicator		
Kindly Note	50	Dec
μ -DeCnology by D. Gibson 3. Simple 741 Receiver	37	May
4. Fuzz Box	61	July
5. Mains Cable Detector	26	Aug
6. Audio Oscillator	36	Oct
Micro-power Pilot Light by R. A. Penfold ..	45	Dec
Model Railway Point Motor Supply by R. A. Ganderton	42	Aug
Kindly Note	59	Nov
ZL Special 2m Beam by F. C. Judd	22	Nov
Kindly Note	50	Dec

CONSTRUCTIONAL—Test Equipment

Audio Distortion Meter by E. A. Rule Part 1	40	May
Part 2	20	June
Phase-locked Calibrator by C. H. Luck	22	July
'Purbeck' Oscilloscope by I. Hickman Part 2	24	May
Part 3	27	June
Part 4	32	July
Part 5	20	Aug
Part 6	54	Sept
'Sarum' Q-Meter by M. Tooley	60	Nov
Simple High Resistance Voltmeter by C. Attenborough	52	Sept
Kindly Note	59	Nov
Wideband Calibrated Attenuator by M. Tooley	22	Sept
2m VSWR Bridge by M. Tooley & D. Whitfield	20	May

CONSTRUCTIONAL—Transmitting

'Avon' 2m Transmitter by B. L. Phillips

Part 1	44	July
Part 2	49	Aug
Digital Display by R. Ganderton	Part 3	28 Sept
Power Supply by N. Foot	Part 4	28 Sept
Kindly Note	59	Nov

IC of the MONTH by B. Dance

No. 69 Thompson CSF ESM532 Power Amplifier.....	41	July
No. 70 RCA TBA120 IF/Limiter/De-mod IC.....	24	Sept
No. 71 CA3189E FM/IF IC.....	55	Nov
No. 72 LM3909N LF Oscillator.....	64	Dec

KINDLY NOTE

Points arising from articles in previous volumes

Active Tone Control March 1978.....	51	Sept
Experimenter's Corner—LED Light Display Apr 1978.....	19	June
IC of the Month March 1978.....	19	June
'Jubilee' Organ—Follow up.....	59 July, 51 Sept	
Morse Tutor August 1977—Follow up.....	52	July
Multi-range Test Meters March 1978.....	19	June
Portable PA Amplifier December 1977.....	57	Aug
Radio 2 Tuner July 1977.....	19	June
'Shoot' August 1977.....	19	June

MISCELLANY—Technical

Amateur SSTV by P. Barker.....	29	Oct
AM Receivers—Devices and Circuits by M. J. Darby.....	Part 1 33 Aug	
	Part 2 54 Oct	
Kindly Note	51	Sept
Calculator Jargon by J. A. C. Beattie.....	60	Dec
Economical VMOS Power Devices by B. Dance.....	51	Oct
Experimental Broadcast Satellite for Japan.....	46	Aug
Hotlines by Ginsberg (recent developments in electronics) 23 May, 26 June, 53 July, 48 Aug, 65 Sept, 38 Oct, 51 Dec		
Ideas Department		
Stereo Headphone Blender by R. N. Soar.....	55	July
Electronic Switch by A. P. Cooper.....	55	July
Short Pulse Gate by T. Austin.....	44	Dec

Introduction to Logic by S. A. Money

Part 1	29	July
Part 2	28	Aug
Part 3	32	Sept
Part 4	41	Nov
Part 5	31	Dec
Landsat System Scans the Earth.....	60	Oct
LW/MW Frequency Changes.....	52	Dec
Making it Work by I. Hickman.....	50	July
Modernising a Valved Receiver by R. Brett-Knowles.....	60	Sept
Phase-locked Loops by C. Budd.....	30	May
Receiver Add-on Accessories by E. Dowdeswell.....	22	Dec
So You Want to Pass The RAE by J. Thornton-Lawrence and K. McCoy		
No. 9 Receivers—Propagation.....	44	May
No. 10 Aerials—Interference—The Examination.....	52	June
New Scheme—new format RAE 1979	40	Sept
Correction to No. 6 February 1978.....	51	May
Reprint of series.....	64	Oct
	35	Nov
Special Product Report		
Home Radio—Electronic Workshop.....	42	Sept
Mega Electronics—Photolab Kit.....	34	Nov
SES—Electronic Ignition Kit.....	24	July
'Stray Signals' by 'Point Contact'.....	28	July
The Norton Amplifier by S. H. Davies.....	39	Oct
Using Transistor Pads.....	26	Oct
Why Programmable? (Calculators).....	37	Nov

ON THE AIR

Amateur Bands by E. Dowdeswell, 66 May, 61 June, 65 July, 61 Aug, 66 Sept, 65 Oct, 69 Nov, 66 Dec		
Choosing a Receiver by E. Dowdeswell....	66	May
SW Broadcast Bands by C. Molloy, 58 May, 64 June, 69 July, 63 Aug, 70 Sept, 69 Oct, 74 Nov, 69 Dec		
MW Broadcast Bands by C. Molloy, 61 May, 66 June, 66 July, 62 Aug, 69 Sept, 66 Oct, 70 Nov, 67 Dec		
VHF Bands by R. Ham, 62 May, 62 June, 70 July, 64 Aug, 71 Sept, 70 Oct, 76 Nov, 70 Dec		
VHF Personalities by R. Ham		
John Branegan GM8OXQ.....	72	July
Anthony Mann.....	74	Sept
Frank Luman.....	72	Oct
What do the VHF's Have To Offer by R. Ham.....	Part 1 63 June	
	Part 2 79 Nov	

PRODUCTION LINES by Alan Martin

Abrasive Tools—Hacksaw Files.....	50	Oct
Ambit International—Ambitune LW Converter.....	47	Dec

AVO—Digital Multimeter DA116.....	43	May
Boss—Desoldering Tools.....	50	Sept
Clement-Clark—Airlite 62 Headset.....	43	Dec
Erg—Keyboard Switches.....	54	July
Kelgray Products—Rechargeable Iron.....	48	June
Loctite—Adhesives.....	43	Dec
Lowe Electronics—TR922 Linear Amplifier.....	50	Oct
Mega Electronics—Photolab Kit.....	56	Aug
Monitel—Telephone Charge Clock.....	56	Aug
National Panasonic—Receivers RF2200 & RF4800.....	54	July
OK Machine Tool—Wire Cutters.....	50	Oct
Pelltech—Alfac Electro Transfers.....	56	Aug
PIL—Pantech Minor Multimeter.....	50	Sept
Rastra Electronics—Timer XR2242.....	43	May
R & TVC—Package Modules.....	50	Sept
Spectrum Marketing—Chess Challenger.....	50	Sept
Tempus—LCD Alarm Clock.....	48	June
Tempus—Casio Calculators.....	43	Dec
Texas—Teleview Module VDP11.....	56	Aug
Vero—AB Boxes.....	48	June
Vero—Catalogue.....	43	May
WKF Electronics—Watches.....	48	June
WKF Electronics—Digital Car Clock.....	50	Oct
3M—Cassette Editing & Repair Kit.....	43	May

SHOW REPORTS

Hi-Fi SERT Seminar by G. C. Arnold.....	64	Sept
IEA/Electrex—Wireless Show—Energy Show by E. Parratt.....	38	July
Paris Show by D. Gibson.....	44	Aug

NEW BOOKS

A Practical Introduction to Electronic Circuits by M. H. Jones.....	50	Dec
The Secret War by Brian Johnson.....	52	July

MISCELLANEOUS

Cover Price Increase.....	20	Nov
News, News, News.....	19 May, 19 June, 21 July, 19 Aug, 21 Sept, 21 Oct, 21 Nov, 21 Dec	

PW Personality		
Geoffrey C. Arnold.....	20	Sept
Ted Parratt.....	20	Oct
Rob Mackie.....	20	Nov
Sylvia Barrett.....	20	Dec
PW Subscription Service.....	62	July
PW Subscription Form.....	41	Dec
QSL by C. Molloy.....	40	Aug
Readers' Letters.....	56 May, 57 Aug, 39 Sept, 42 Dec	
Readers' PCB Service.....	57 May, 68 June, 27 July, 47 Aug	
Enlargement of PCB Service.....	18 Aug, 59 Sept	
Special Subscription Offer.....	58	Nov
Stateside Calling by J. Kasser.....	32	June
The Start of Empire Broadcasting by R. Ham.....	25	July

SUPPLEMENT etc

'Breadboards' Survey of Systems.....	Dec
Gifts —General Purpose Tweezers.....	May
Transistor Pads.....	Oct
Index —Volume 53 May 1977–April 1978.....	June
Special Feature —Gadgets Around the House.....	Nov
Special Offer —Commodore PR100 Programmable Calculator.....	68 Nov

LIST OF AUTHORS

Arnold G. C. T.Eng (CEI)	Hickman I.
FSERT	Hutchinson M. J.
Attenborough C.	Judd F. C. G2BCX
Austin T.	Kasser J. G3ZCZ/W3
Barker P.	Martin A.
Brett-Knowles R.	Mattey N. B.
Budd C.	McCoy K. GW8CMY
Beattie J. A. C. MSc	Molloy C. G8BUS
MInstP	Nailer A. J. G4CFY
Coutts D. S.	Parratt E. BA
Cooper A. P.	Penfold R. A.
Dance B. MSc	Phillips B. L. G8FWM
Darby M. J.	Poel W. S.
Davies S. H.	Rayer F. G. G3OGR
Donleavy A. P.	Rule E. A.
Dowdeswell A. E. G4AR	Smith G. F. BSc MSc
Foot N. G8MCQ	Soar R. N.
Ganderton R. A. C.Eng,	Thornton-Lawrence J.
MIERE	T.Eng(CEI) FSERT
Gibson D. G3JDG	MIERE GW3JGA
Gould G.	Tooley M. H. BA G8CKT
Ham R. BRS15744	Wheeler P. J.
Harvey J. B.	Whitfield D. BA G8FTB

practical WIRELESS

FEBRUARY 1979
VOLUME 55
NUMBER 2
ISSUE 864

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUESTIONS

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on troubleshooting to our designs, nor on our equipment, TV or electronic appliances. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and including a stamped self-addressed envelope. Only one request per letter please. Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.00 per annum, from "Practical Wireless" Subscription Department, Orchard House, Farningham Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

United stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available from £2.00 in U.K. addresses or £3.45 overseas, including post and packing each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavendon House, 88 Lavendon Street, London SE1 6PP.

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are accurate. We cannot however guarantee it and we cannot accept legal responsibility for it. Please be aware of this as we go to press.

NEWS & VIEWS

- 30 Editorial
Our Role
- 30 *PW* Personality
Alan Martin
- 21 News . . . News . . . News . . .
- 32 Special Product Report
Spectra DM235 Digital Multimeter
- 40 Medicine Strategy
Recent developments in electronics
- 47, 88 Production Lines
Information on the latest products Alan Martin
- 61 New Books
Comments on recent books in the electronics field
- 71 RAE Reprint Announcement

FOR OUR CONSTRUCTORS

- 32 12V Fluorescent Light
An economical emergency light source
- 36 Follow-up to the Wide-range Capacitance Meter Ian McMan
- 41 Extending the range of measurement to 30,000pF
- 41 *PW* "Hythe" Marine Band Receiver—3 M. Tooley & D. Whitfield
A simple multi-mode receiver
- 60 *PW* "Dorchester" AUS Band Tuner—3 W. S. Pool
Mechanical details and alternative applications

GENERAL INTEREST

- 26 Digital Audio Amplification Gordon J. King
A look at pulse-width-modulation amplifiers
- 34 FM Receivers—Devices & Circuits—2 M. J. Darby
The L1 stage
- 48 IC of the Month Brian Deane
The LM331N—80 audio power driver
- 62 Introduction to Logic—7 S. A. Massey
LSI and microprocessors
- 63 On the Air
Amateur Bands Eric Dunderwood
QRP Broadcast Bands Charles Massey
SSTV Broadcast Bands Charles Massey
VHF Bands Ron Hogg

EXTRA

Index to Volume 54
Contents of our Month dated May—December 1978

Our March issue will be published on 2 February
(for details see page 33)