

RF design

engineering principles and practices

May 1991



Featured Technology
Test and Measurement
Crystal Oscillators
Quadrature Detectors

Wavecom SP2T coaxial switches

The most choices. The largest line.

Wavecom offers the largest line of SP2T switches in the business. What's more you can get exactly the specs you want – at commercial prices and with products that are manufactured to Wavecom standards of space age reliability.

That's because we designed our basic switches to accommodate an almost infinite variety of spec combinations.

Frequency range: DC through 26.5 GHz.

RF connectors can be SMA, TNC, N, BNC, SC or PC board mount.

Actuation can be failsafe, latching, or normally open. Make-before-break available for hot switching applications.

Options can include 50 ohm terminations, indicator circuitry, TTL logic, BCD TTL decoder, self de-energizing circuitry, and manual operation.

We also offer a complete line of multi-position (SP3T to SP12T) and transfer switches – all available with the same variety of spec combinations as SP2T switches.

All switches can be manufactured to meet any spec requirements, whether commercial, mil-spec or deep space probes.

For more information or a free catalog, call or write Loral Microwave-Wavecom, 9036 Winnetka Avenue, Northridge, CA 91324. Tel: (818) 882-3010. Fax: (818) 709-8204.


Specifications – Wavecom SP2T coaxial switches

Frequency Range (GHz)	DC - 3	3 - 8	8 - 12.4	12.4 - 18	18 - 26.5
VSWR (Max)	1.2:1	1.3:1	1.4:1	1.5:1	1.6:1
Insertion Loss (Max dB)	0.2	0.3	0.4	0.5	0.6
Isolation (Min dB)	80	70	60	60	50



LORAL
Microwave-Wavecom

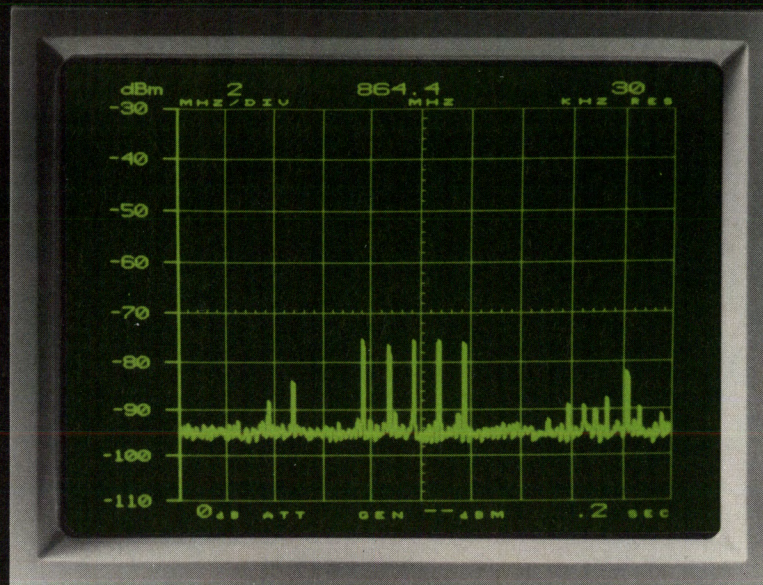If you're not using a spectrum analyzer...




Spectrum analyzer display of cellular telephone transmissions.


maybe it's time to take a closer look.



Spectrum Analyzers

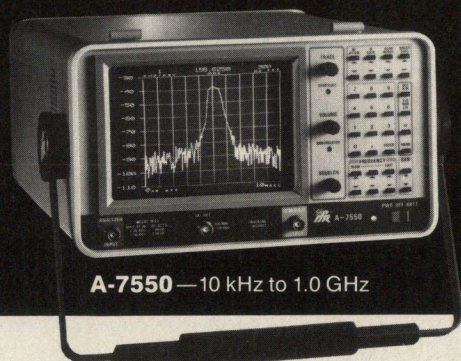

A-7550 — 10 kHz to 1.0 GHz

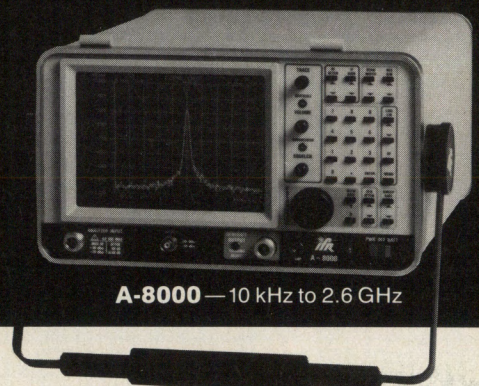

A-8000 — 10 kHz to 2.6 GHz

You can't hear them or see them, but there are probably thousands of electromagnetic signals being transmitted through the air around you at this very moment.

Many of these signals originate from radio and television transmission. However, many other signals are emitted from computers, CRT display terminals, and other electrical devices.

Each of these signals can be a potential source of harmful interference to sensitive electrical equipment or critical systems you are operating.

The IFR A-7550 and A-8000 Spectrum Analyzers provide a full set of features to speed the identification and measurement of signals over a wide frequency range.

Optional built-in features including a rechargeable battery, tracking generator, sensitive AM/FM/SSB receiver, IEEE-488 interface, RS-232 interface, and quasi-peak detector allow either instrument to be configured to your unique testing requirements at a surprisingly affordable price.

For more information or a demonstration of the A-7550 or the A-8000, contact your local IFR representative or call IFR at (316) 522-4981.



IFR SYSTEMS, INC.

10200 West York Street
Wichita, Kansas 67215-8935 U.S.A.
FAX 316 / 524-2623

GaAs Pains?



Call DAICO!

SELECTION CHART

Part No.	Type	Freq/MHz	IL/dB*	Iso/dB*	Sw. Speed/ nSec**	Package	Control
DS0841	SPST	10-200	1.7	70	7.0	14 Pin DIP	TTL
DS0699	SPST	5-1500	1.0	48	23.0	TO-8	TTL
DS0990	SPST	10-2000	1.5	62	25.0	14 Pin DIP	TTL
DS0850	SP2T	DC-2000	0.4	47	5.0	TO-5	0/-7
DS0813	SP2T	DC-2000	0.7	40	140.0	TO-5	TTL
DS0812	SP2T	10-1000	0.5	54	50.0	TO-8	TTL
DS0860	SP2T	10-1000	0.5	47	50.0	.380 sq	TTL
DS0602	SP2T	5-9000	1.3	65	26.0	14 Pin DIP	TTL
DS0842	SP2T	5-1500	1.0	75	50.0	14 Pin DIP	TTL
DS0864	SP4T	5-2000	1.3	49	28.0	16 Pin DIP	TTL
DS0874	SP4T	DC-2000	2.2	60	55.0	14 Pin DIP	TTL
DS0838	SP8T	5-1000	2.2	40	40.0	24 Pin DIP	TTL
DS0918	SP16T	DC-4000	3.8	30	150	58 Pin DIP	TTL

*Typical performance measured mid-band.

**50% TTL to 10%/90% RF.

Does your switch supplier give you GaAs pains?...Call DAICO.

DAICO remedies GaAs pains fast with 20 high performance GaAs switches available directly from stock. In fact, we have a total of 64 different models of GaAs switches, digital attenuators and VCA's in stock guaranteed to alleviate your GaAs pains.

So get rid of your GaAs pains fast...call DAICO for technical assistance and our 1991 Catalog at (213) 631-1143.



DAICO INDUSTRIES, INC.

2453 East Del Amo Blvd., Compton, CA 90220
Telephone (213) 631-1143 • FAX (213) 631-8078

featured technology

26 A Channel Sounder for Indoor Communication Systems

The authors describe a test transmitter and receiver for characterizing indoor radio propagation at L-band. Path performance measurements are required if reliability of factory or other radio systems is to be assured.

— Fernando Casadevall and Xavier Barba

40 High Power Bi-Directional Coupler for Space Applications

Control and protection of high reliability circuits such as spaceborne power amplifiers is critical. This article describes a high power coupler designed to meet specific coupling and directivity requirements.

— Pascal R. Goux

emc corner

56 Surge and Transient Considerations

A review of the causes and nature of surges and transients on power utility and common carrier signal lines, plus notes on protection of electronic equipment from their effects.

— Gary A. Breed

design awards

58 A Simple Clock and PSK Carrier Recovery Circuit

This month's featured contest entry is a simple circuit that simultaneously recovers clock and data information from a PSK modulated signal.

— Francois Methot

61 VHF and UHF Crystal Oscillators — Part II

Another note from *RF Design's* Consulting Editor on his experiments with some remarkably simple high frequency fundamental and overtone oscillator circuits.

— Andrzej B. Przedpelski

68 Design of Quadrature Detectors


A review and analysis of the quadrature detector, typically the lowest cost option for demodulation of frequency and phase modulated information.

— Edward A. Richley

73 CAD of Single and Tandem Lange Couplers

The authors show how two Lange couplers connected in tandem can solve the problem of small dimensions at microwave frequencies. They provide a computer program for design of both single and tandem couplers.

— Timothy O'Connell and Patrick Murphy

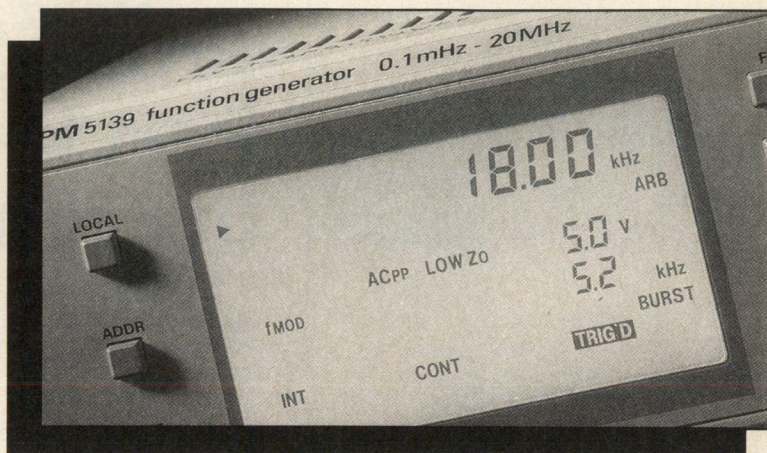

departments

- 6 Editorial
- 12 Letters
- 14 Calendar
- 16 Courses
- 19 News
- 24 Industry Insight
- 48 New Products
- 77 Product Report
- 78 New Software
- 79 New Literature
- 82 Advertiser Index
- 83 Reader Survey
- 86 Info/Card

Our cover, provided by John Fluke Mfg. Co., represents our emphasis on engineering test and measurement. More information on this product can be found on page 48.

R.F. DESIGN (ISSN: 0163-321X USPS: 453-490) is published monthly plus one extra issue in September. May 1991. Vol. 14, No. 5. Copyright 1991 by Cardiff Publishing Company, a subsidiary of Argus Press Holdings, Inc., 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111 (303) 220-0600. Contents may not be reproduced in any form without written permission. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: *RF Design*, 5615 W. Cermak Rd., Cicero, IL 60650. Domestic subscriptions are sent free to qualified individuals responsible for the design and development of communications equipment. Other subscriptions are: \$38 per year in the United States; \$48 per year in Canada and Mexico; \$52 (surface mail) per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700.

SUBSCRIPTION INQUIRIES: (312) 762-2193.

POSTMASTER & SUBSCRIBERS: Please send address changes to R.F. Design, 5615 W. Cermak Rd., Cicero, IL 60650.

HIGH POWER COMBINER



FEATURES:

- LOW LOSS
- HIGH ISOLATION
- EXTERNAL TERMINATIONS

4 WAY COMBINER MODEL

D2650	54-88 MHz
D2685	88-108 MHz
D2655	174-216 MHz

TYPICAL SPECIFICATIONS

INS. LOSS	0.15db
ISOLATION	25db
VSWR	1.2:1
POWER	2Kw
Connectors	
input	N
output	1-5/8 EIA

WERLATONE has an extensive line of 2 and 4 way combiners covering the TV and FM bands

1965 - 1990
25 years in business




decades ahead

WERLATONE, INC.
P.O. Box 47
Brewster, NY 10509
Tel: (914) 279-6187
FAX: (914) 279-7404

RF editorial

Engineering Productivity Part II — Test Instruments

By Gary A. Breed
Editor

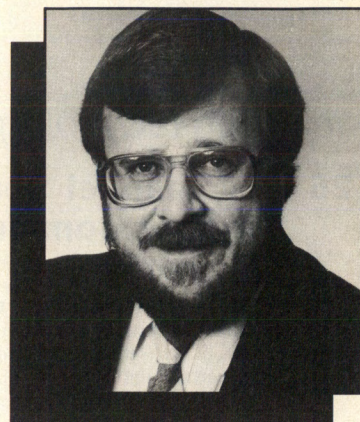

Last month, I noted some of the organizational changes that are occurring in the U.S. electronics industry. To effectively improve efficiency, these changes require that companies get the maximum results from their employees' efforts. For RF companies, this is an especially difficult assignment, since experienced RF designers are in relatively short supply and many are already extremely busy.

One method of improving an RF engineer's productivity is to provide support that allows him more time for creative engineering. Recent developments in the world of test and measurement certainly fit this description, with instruments that not only offer improved performance, but have operating features that minimize setup time.

The principal enhancement in newer test instruments is the incorporation of computing power. This allows the user to store standard setups, eliminating all the knob-twisting that used to be needed. Errors in those dial settings are eliminated, too. Computations based on the measured data can be performed as part of the pre-programmed test procedure. For example, a spectrum analyzer can list the harmonic levels relative to the fundamental, or identify spurious signal levels and frequencies.

All this power can be utilized in a multi-unit test setup. A modulated signal generator, spectrum analyzer, power supply and DC multimeter could be connected into a power amplifier test system, controlled by a host computer. A little extra time to program the system eliminates lengthy and tedious manually-operated measurements. You might not need a computer, either. The controller might be inside one of these instruments, since a few already have a keyboard option that is all they need to

be stand-alone PCs!

Performance features improve the accuracy and reliability of measurements, especially in high performance testing. Improved measurement confidence reduces the need to repeat a test "just to make sure." Lower noise synthesizers in signal generators, spectrum analyzers and network analyzers have increased the dynamic range of these instruments' measurements. Direct digital synthesis and digital modulation allows generation of complex waveforms that previously required combinations of several sources. Baseband FFT analysis in spectrum analyzers dramatically increases the precision of their measurements. Internal calibration routines make sure that these powerful functions are operating as intended when you need them.

These advantages are not limited to the designer's bench — production line testing may receive an even bigger benefit. Faster, more accurate measurements are exactly what the production test manager wants! Pre-programmed setup takes most of the human error out of the instrument operation and data collection process. To meet the needs of manufacturing, a new generation of instruments with "practical" rather than "ultimate" performance specifications is beginning to show up.

So, the next time you find yourself wishing for some new test equipment, take the time to evaluate how much time you spend preparing for tests, running them by hand, and manually tabulating the results. If you are under pressure to deliver your designs on increasingly shorter timetables, this information might be all that is needed to justify the investment. Your company will get more out of your talents, and you'll get greater satisfaction doing it.

NOISE/COM

"NOISE IS OUR ONLY BUSINESS"


Broad Band Noise Sources

For Space, Military and Commercial Applications

DC-50 GHz

Broad Band Precision, Calibrated Waveguide

W/R-22,-28,-42

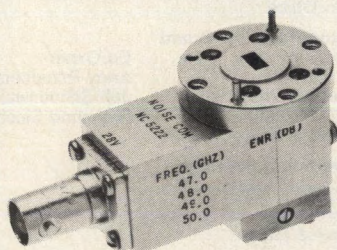

TYPICAL STANDARD MODELS

NC 5100 Series	up to 50 GHz 15.5 dB ENR, noise figure meter compatible
NC 5200 Series	up to 50 GHz 21-25 dB ENR, high noise output
NC 5300 Series	up to 50 GHz 21-25 dB ENR, high noise output

**For More
Information
And Quick
Response Call:
GARY SIMONYAN
at 201-261-8797**

Broad Band Instruments

115V or 230V Standard
Bench Type or Rack Mounted
MANUALLY CONTROLLED
+ 10 dBm Output




TYPICAL STANDARD MODELS

NC 6101	up to 20 kHz
NC 6107	up to 100 MHz
NC 6108	up to 500 MHz
NC 6109	up to 1 GHz
NC 6110	up to 1.5 GHz
NC 6111	up to 2 GHz
NC 6218	up to 18 GHz

Other standard models available
MOST ARE IN STOCK

PROGRAMMABLE

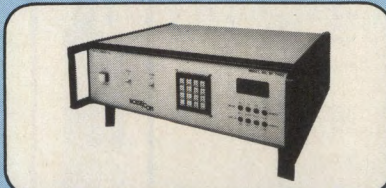IEEE-488 (GPIB), MATE (CII)
RS232, etc. + 10 dBm Output



TYPICAL STANDARD MODELS


NC 7101	up to 20 kHz
NC 7107	up to 100 MHz
NC 7108	up to 500 MHz
NC 7109	up to 1 GHz
NC 7110	up to 1.5 GHz
NC 7111	up to 2 GHz
NC 7218	up to 18 GHz

OPTIONAL: Remote variable
filters, signal input combiner,
75 ohms output, marker input.
Other standard models available
MOST ARE IN STOCK

Custom & Hi Rel Products


**HYBRID FOR SPACE QUALIFIED
AMPLIFIED MODULES**

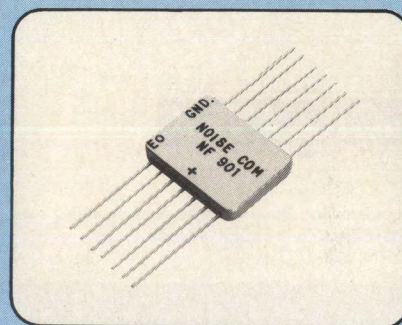10 Hz to 10 MHz, 7 GHz, 9 GHz,
14 GHz etc. Small size and weight



DC COUPLED AMPLIFIED MODULES

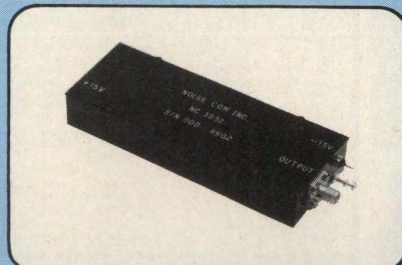- 1 volt output into 50 ohms
- DC-100 kHz
- Low offset voltage
- Compact
- DC-4 MHz



NOISE/COM

"NOISE IS OUR ONLY BUSINESS"

NOISE COM, INC.
E. 49 Midland Ave.
Paramus, NJ 07652

PHONE (201) 261-8797

FAX (201) 261-8339

TWX 910-380-8198

TCXO's in DIP packages

ALL Logic Families
available in 4- or 14-pin
DIP .5"x.8"x.375"

SPECIFICATIONS

Voltage stability: $V_{cc} \pm 5\%$, ΔF
< 1PPM

$V_{cc} \pm 10\%$, ΔF
< 12PM

Aging: 5 PPM first year; 2PPM per year
thereafter


Frequency Adj.: Control voltage in
range of 9 to 5V (variable capacitor
optional)

OSCILLATEK

A DOVER TECHNOLOGIES COMPANY

620 N. Lindenwood Drive • Olathe, Kansas 66062
FAX: (913) 829-3505 • TELEX: 437045
Phone: (913) 829-1777

OSCILLATEK
M84 SERIES

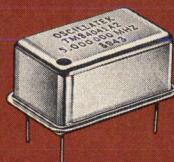

ACTUAL SIZE

TEMPERATURE RANGE/ STABILITY	FREQUENCIES AVAILABLE
0° - + 50°C, ± 2 PPM	TTL = 1KHz to 32MHz
0° - + 50°C, ± 5 PPM	*CMOS = 1KHz to 10MHz
0° - + 70°C, ± 5 PPM	ECL = 4MHz to 32MHz
-30° - + 70°C, ± 10 PPM	SINE = 4MHz to
-30° - + 85°C, ± 15 PPM	

INFO/CARD 6

LOWEST PRICED, HIGHEST QUALITY ATTENUATORS - BNC \$15.00 1-9 EA., SMA \$15.00 1-9 EA.
AND TERMINATIONS - BNC \$5.60 10 EA., SMA \$5.60 10 EA. MIL. HI-REL. NETWORKS

Model Number (2)	Impedance Ohms (Power W)	Frequency Range	BNC	UNIT PRICE (4) EFFECTIVE, 1-15-88	TNC	SMA	UHF	SMB	PC
Fixed Attenuators, 1 to 20 dB:									
AT-50 (3)	50 (1.5W)	DC-1.5GHz	17.50	29.00	22.00	20.00	-	-	-
AT-51	50 (1.5W)	DC-1.5GHz	15.00	26.00	19.50	17.50	-	-	12.00
AT-52	50 (11W)	DC-1.5GHz	20.50	29.00	26.00	22.00	-	-	-
AT-53	50 (.25W)	DC-3.0GHz	20.50	26.00	-	15.00	-	18.00	-
AT-54	50 (.25W)	DC-4.2GHz	-	-	-	20.00	-	-	-
AT-55	50 (.25W)	DC-4.2GHz	-	-	-	19.20 (10P)	-	-	-
AT-75 or AT-90	75 or 93 (.5W)	DC-1.5GHz	17.50	26.00	45.50	19.50	-	-	-
Detector, Mixer, Zero Bias Schottky:									
CD-51, 75	50, 75	01-4.2GHz	64.00	-	-	64.00	-	-	-
DM-51	50	01-4.2GHz	-	-	-	64.00	-	-	-
Resistive Impedance Transformers, Minimum Loss Pads:									
RT-50/75	50 to 75	DC-1.5GHz	17.50	26.00	45.50	17.50	-	-	-
RT-50/93	50 to 93	DC-1.0GHz	17.50	26.00	45.50	17.50	-	-	-
Terminations:									
CT-50 (3)	50 (1.5W)	DC-4.2GHz	11.50	15.00	15.00	17.50	-	-	-
CT-51	50 (1.5W)	DC-4.2GHz	9.50	12.00	14.00	9.50	-	9.00	-
CT-52	50 (11W)	DC-2.5GHz	10.50	15.00	15.00	13.00	15.50	-	-
CT-53M	50 (.5W)	DC-4.2GHz	-	5.60 (10P)	-	5.60 (10P)	-	-	-
CT-54	50 (.2W)	DC-2.0GHz	14.00	15.00	15.00	17.50	-	-	-
CT-75	75 (.25W)	DC-2.5GHz	10.50	15.00	15.00	13.00	15.50	-	-
CT-93	93 (.25W)	DC-2.5GHz	13.00	15.00	-	15.00	15.50	-	-
Mismatched Terminations, 1:05:1 to 3:1, Open Circuit, Short Circuit:									
MT-51	50	DC-3.0GHz	45.50	45.50	45.50	45.50	-	-	-
MT-75	75	DC-1.0GHz	-	-	45.50	-	-	-	-
Feed thru Terminations, shunt resistor:									
FT-50	50	DC-1.0GHz	17.50	26.00	19.50	17.50	-	-	-
FT-75	75	DC-500MHz	17.50	26.00	45.50	17.50	-	-	-
FT-90	93	DC-150MHz	17.50	26.00	45.50	17.50	-	-	-
Directional Coupler, 30dB:									
DC-500	50	250-500MHz	60.00	-	84.00	84.00	-	-	-
Resistive Decoupler, series resistor or Capacitive Coupler, series capacitor:									
RD or CC-1000	1000 (1000PF)	DC-1.5GHz	17.50	26.00	19.50	17.50	-	-	-
Adapters:									
CA-50 (N to SMA)	50	DC-4.2GHz	17.50	26.00	19.50	17.50	-	-	-
Inductive Decouplers, series inductor, Bias T:									
LD-R15	0.17uH	DC-500MHz	17.50	26.00	19.50	17.50	-	-	-
LD-R68	6.8uH	DC-55MHz	17.50	26.00	19.50	17.50	-	-	-
BT-50	1.8uH	15-500MHz	84.00	84.00	94.00	84.00	-	-	-
Fixed Attenuator Sets, 3, 6, 10 and 20 dB, in plastic case:									
AT-50-SET (3)	50	DC-1.5GHz	76.00	120.00	92.00	84.00	-	-	-
AT-51-SET	50	DC-1.5GHz	64.00	108.00	82.00	74.00	-	-	-
Reactive Multicouplers, 2 and 4 output ports:									
TC-125-2	50	1.5-125MHz	84.00	-	94.00	84.00	-	-	-
TC-125-4	50	1.5-125MHz	94.00	-	104.00	94.00	-	-	-
Resistive Power Dividers, 3, 4 and 9 ports:									
RC-3-50	50	DC-2.0GHz	84.00	84.00	94.00	84.00	-	-	-
RC-4-50	50	DC-500MHz	84.00	84.00	94.00	84.00	-	-	-
RC-9-50	50	DC-500MHz	-	-	-	104.00	-	-	-
RC-3-75, 4-75	75	DC-500MHz	84.00	84.00	-	84.00	-	-	-
Double Balanced Mixers:									
DBM-1000	50	5-1000MHz	61.00	-	71.00	61.00	-	-	34.00
DBM-500PC	50	2-500MHz	-	-	-	-	-	-	34.00
RF Fuse, 1/8 Amp., and 1/16 Amp.:									
FL-50	50	DC-1.5GHz	17.50	26.00	45.50	17.50	-	-	-
FL-75	75	DC-1.5GHz	17.50	26.00	-	17.50	-	-	-

NOTE: 1) Critical parameters fully tested and guaranteed. Fabricated from MIL-Spec. High-Rel. resistors, Schottky diodes, MIL-Spec. plated parts, and connectors in nickel, silver, and gold. 2) See catalog for complete Model Number. Specify connector series. Specials available. 3) Calibration marked on label of unit. 4) Price subject to change without notice. Shipping \$5.00 Domestic or \$25 Foreign on Prepaid Orders. Minimum Order \$50. Delivery in stock to 30 days APO.

Send for Free Catalog on your Letterhead

Elcom SYSTEMS INC. TEL. 407-994-1774 FAX. 407-994-1770
932 CLINT MOORE ROAD, BOCA RATON, FL 33487



RFdesign

a Cardiff publication

Established 1978

Main Office:

6300 S. Syracuse Way, Suite 650
Englewood, CO 80111 • (303) 220-0600
Fax: (303) 773-9716

Publisher

Kathryn Walsh

Editor

Gary A. Breed

Associate Editor

Liane Pomfret

Consulting Editor

Andy Przedpelski

Associate Sales Manager

Bill Pettit

Account Executive

Maryanne Averill

Main Office

Account Executive

Cindy Wieland

Main Office

Editorial Review Board

Alex Burwasser

Doug DeMaw

Dave Krautheimer

James W. Mize, Jr.

Robert J. Zavrel, Jr.

Ed Oxner

Andy Przedpelski

Jeff Schoenwald

Raymond Sicotte

Advertising Services

Tisha Bobers Schmidt Hill

Secretary

Theresa Maier

Convention Manager

Kristin Hohn

Registration Coordinator

Barb Binge

Customer Service Representative

LeAnn Nowacki

Associate Production Managers

Matt Park

Maurice Lydick

Artists

Kim Austin

Joyce Fields

Brad Fuller

Paul Rivera

Sheri Ryder

Composition

Mike C. Moore

Marcie Tichenor

Creative Director

Bob Stewart

Published by

CARDIFF
PUBLISHING COMPANY, INC.

BPA

President

Robert A. Searle

Vice President — Production

Cherryl Greenman

Vice President — Convention Management

Kathy Kriner

Treasurer

Jennifer Burger

Circulation Director

Patricia Shapiro

Credit Manager

Patti McManness

Please address subscription inquiries to:
RF Design

5615 W. Cermak Rd., Cicero, IL 60650

Postmaster: send form 3579

to the above address.

May 1991



For Most People, It Was Just Another Warm September Day.

For design engineers, it was the day mixed analog/digital design came of age.

The event was the mixed-signal design demonstration at the IEEE Bipolar Circuits and Technology Meeting (BCTM). The goal was to give credence to mixed-signal simulation and to benchmark companies in the marketplace. The results were conclusive.

Viewlogic came up with the right answer first.

But more to the point, what we did at BCTM in September, we can do for you now. We're the only company with a proven technology and a three year track record of success. The only one that integrates design capture, simulation and analysis.

But that's just the beginning.

Performance and Flexibility available nowhere else.


With VIEWsim/SD, you'll get the choices you need. You'll be able to mix behavioral models with gates and SPICE primitives. Choose from leading analog simulators like PSPICE and HSPICE. Include physical hardware models for devices when software models are not available. Use the most popu-

Full Hierarchical Design

Automatic Design Partitioning

Mixed-Signal Simulation With Behavioral, Device, Hardware Models


Integrated Mixed Signal Analysis

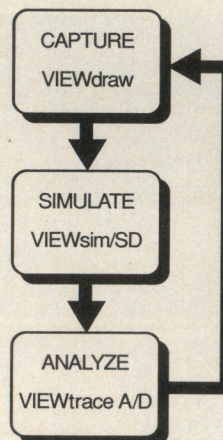

lar platforms from SUN, DEC and IBM.

Our white paper "Mixed-Signal Simulation Benchmark Report"

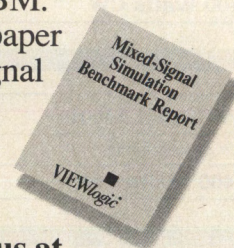proves the point. Call us at **1-800-422-4660, Ext. 103.** You'll like the climate we're creating for mixed-signal design.



VIEWlogic®

The CAE Company

Viewlogic Systems, Inc.
293 Boston Post Road West
Marlboro, MA 01752
508-480-0881
508-480-0882 FAX

PSPICE and HSPICE are trademarks of their respective companies.

LA SERIES

Smart

RF POWER AMPLIFIERS

MODEL LA100H	MODEL LA100F	MODEL LA100U	MODEL LA100UE	MODEL LA100UF
.3 - 100MHz	100-250MHz	200-400MHz	200-500MHz	100-500MHz
100 Watts CW	100 Watts CW	100 Watts CW	100 Watts CW	100 Watts CW

MODEL LA200H	MODEL LA200F	MODEL LA200U	MODEL LA200UE	MODEL LP300H
.5 - 100MHz	100-250MHz	200-400MHz	250-500MHz	.3 - 100MHz
200 Watts CW	200 Watts CW	200 Watts CW	200 Watts CW	300 Watts Pulse

MODEL LA400U	MODEL LA500H	MODEL LA500V	MODEL LA500U	MODEL LA1000H
200-400MHz	.5-50MHz	10-100MHz	200-400MHz	2-32MHz
400 Watts CW	500 Watts CW	500 Watts CW	500 Watts CW	1000 Watts CW

MODEL LA1000V	MODEL LA2000H1	MODEL LA3000HS	MODEL LP4000HV2	MODEL LP12000HV
10-100MHz	2-30MHz	5-45MHz	2-50MHz	2-50MHz
1000 Watts CW	2000W pk, 1000W CW	3000 Watts CW	4000 Watts pk. pulse	12KW peak pulse

KALMUS EUROPEAN SALES AND SERVICE CENTERS

FRANCE: KMP Electronics PHONE: 1-46-45-09-45
FAX: 1-46-45-24-03

GERMANY: Telemeter Electr GMBH PHONE: (0906) 4091
FAX: (0906) 21706

ENGLAND: EATON, Ltd. PHONE: 734-730900
FAX: 734-328335


ITALY: Vianello Strumentazione PHONE: 02-89200162
FAX: 02-89200382



21820 87th SE, Woodinville, WA 98072 (206) 485-9000 FAX 206-486-9657

100W to 12KW ALL MOS-FET RF POWER AMPLIFIERS

LA 100/200

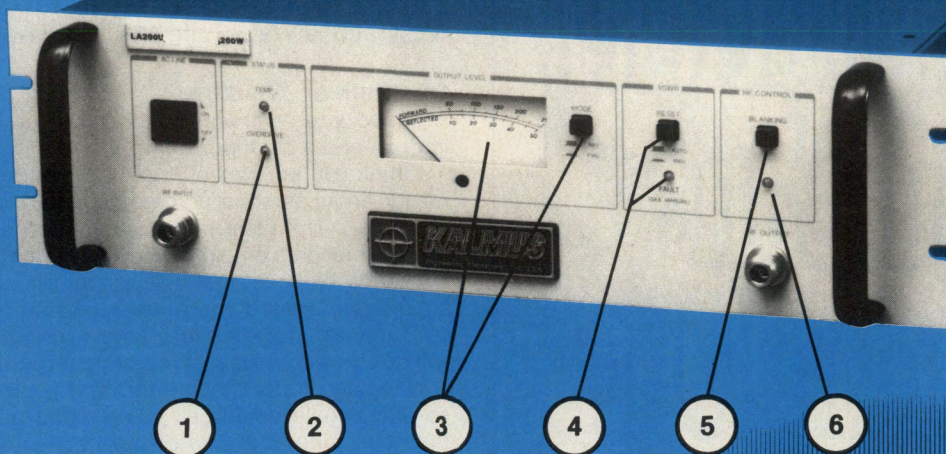


- All MOS-FET class AB linear RF POWER AMPLIFIERS.
- Bicolored LED indicators.
- Automatic Limiting Control (Overdrive protection). **(1)**
- Remote and Local Forward and Reflected monitoring. **(3)**
- Remote and Local temperature status. **(2)**
- Dual Temperature Protection. **(2)**
- Remote and Local Overdrive and Over ALC status. **(1)**
- Remote and Local VSWR status. **(4)**
- Remote and Local Blanking status. **(6)**

- Remote Automatic Levelling Control.
- Remote and Local Gain control.
- Remote and Local Blanking. **(5)**
- Infinite VSWR compatibility, without shut down in AUTO mode. **(4)**
- 47-440Hz AC power capability from 97 to 265VAC.
- Single AC Phase and three AC Phase, user selectable on most models.
- Forced-air cooled.
- Functionally designed and competitively priced high-tech RF Power equipment.

LA 3000 AND 12000HV
(12KW OUTPUT)




LA 500/600/1000
AND 4000HV

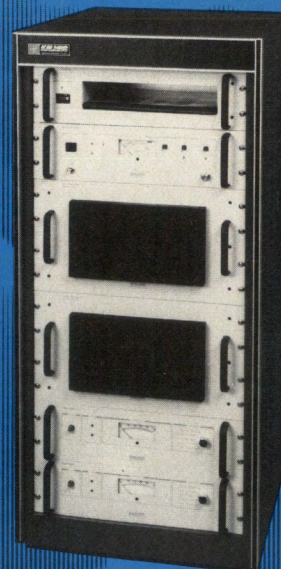

LA 2000



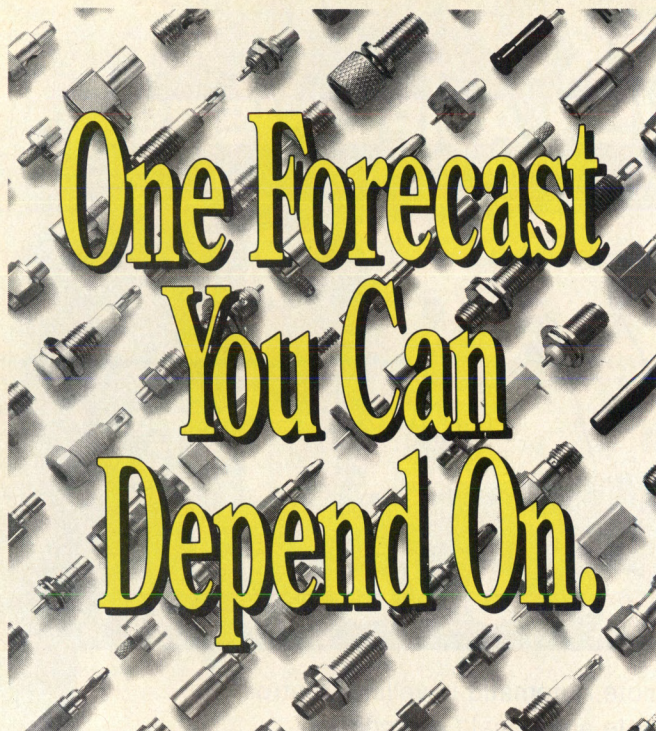

For more than 60 years, we've been making high-performance electronic components to meet the most demanding applications. For the E.F. Johnson distributor nearest you, call 1-800-247-8256. Demand the best. Specify E.F. **E.F. JOHNSON®**

©1991, E.F. Johnson

INFO/CARD 10

RF letters

Letters should be addressed to: Editor, *RF Design*, 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111.

Obsolete or Absolute?

I read your editorial on obsolete technologies with much interest and a bit of puzzlement.

I think you are way off base, 180 degrees out of phase with reality, about personal communications making "inconvenience obsolete." The plain truth is that such a system would make inconvenience *complete*. If you doubt this point of view, I challenge you to make a simple test. Just give all the secretaries around you a week off and for one week, answer your phone yourself every time it rings. And, of course, you will do this with no lessening of your regular work output.



Hanging one of those infernal machines around your neck so that people could call you up and talk about a subject of their choosing at a time of their choosing, with absolutely no thought for your convenience would be — well, the inner circle of hell! The phone is getting to be an invasion of privacy already, but what would it be like if there were nowhere you could go to get away from it?

Add this to your list of pet peeves, and contemplate that we now have the technology to bring all of them to pass.

C.A. Chrestien
Sunnyvale, CA

Short cycle your circuits.

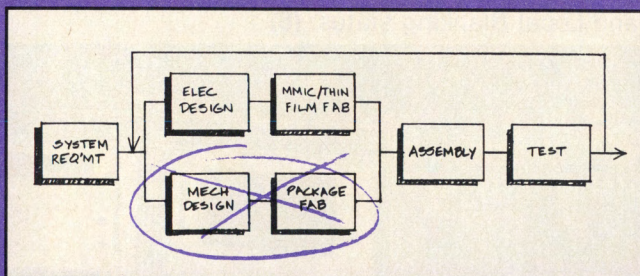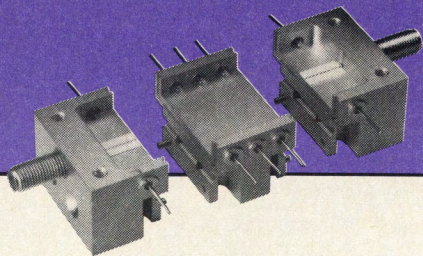If you need a faster way to get your designs to market, try the new HP 83040 Series Microcircuit Package. Compared to custom packaging and test fixtures, it can cut weeks off your design time. And thousands of dollars off your development costs.



Pre-designed and off-the-shelf, the HP 83040 is ready for prototype and IC testing. Its modular format is compatible with CAE systems and network analyzer calibration techniques. Call your local HP sales office or circle the inquiry number below.

There is a better way.




©1990 Hewlett-Packard Co. TMMTA038

QUAD COMPARATORS

8ns, 18mW—ONLY \$1.50*

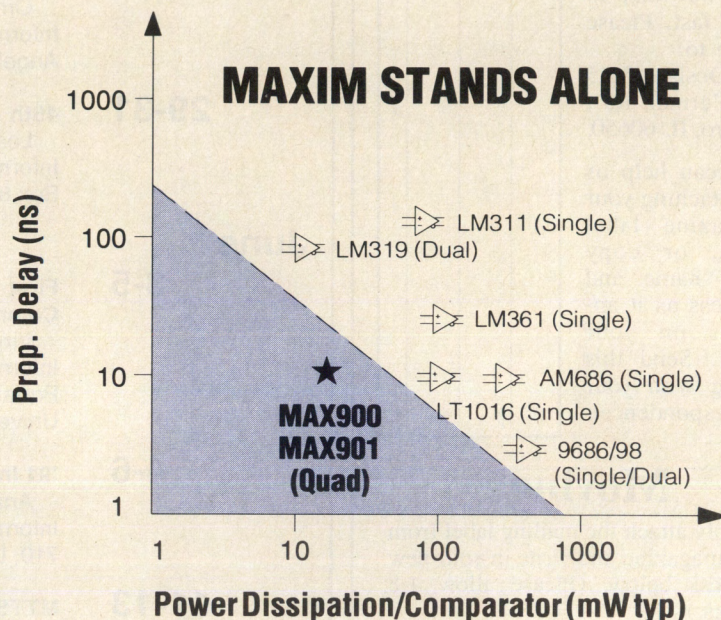- ◆ **+5V Operation Cuts Power Drain and Heat Dissipation**
- ◆ **Input Range Includes Ground and Eliminates Need For Negative Supply**
- ◆ **Four Comparators in One Package Saves Board Space and Reduces Cost**
- ◆ **Separate AGND and DGND Minimizes Noise, Improves System Performance**
- ◆ **Dual Supply $\pm 5V$ Capability Allows Bipolar Input Range**



One Stop Shopping For High Speed/Low Power

Maxim's new MAX900 and MAX901 quad comparators can deliver both high speed *and* low power at a price that compares favorably to high speed single or dual equivalents. MAX900/MAX901 offer you propagation delays of only 8ns with a 5mV overdrive, power dissipation of 18mW per comparator (when powered from a +5V supply) and space saving 0.3" DIP or small outline (SO) packages - for only \$1.50 per comparator.

Maxim's High Speed Comparator Family

Part Number	# Comps	Logic	Delay (typ)	Latch	Package	Price†
MAX900	4	TTL	8.0ns	Yes	DIP, SO	\$7.01
MAX901	4	TTL	8.0ns	No	DIP, SO	\$5.98
MAX9685	1	ECL	1.3ns	Yes	DIP, SO, Can	\$3.38
MAX9686	1	TTL	6.0ns	Yes	DIP, SO, Can	\$2.31
MAX9687	2	ECL	1.4ns	Yes	DIP, SO	\$5.12
MAX9690	1	ECL	1.3ns	No	DIP, SO	\$3.29
MAX9698	2	TTL	6.0ns	Yes	DIP, SO	\$3.92

* MAX901, 1000-up F.O.B. USA price per comparator † 1000-up F.O.B. USA

Call your Maxim representative or distributor today for applications information, datasheets and samples. Or, write Maxim Integrated Products, 120 San Gabriel Drive, Sunnyvale, CA 94086, (408) 737-7600, FAX (408) 737-7194.

MAXIM

Distributed by Arrow, Bell/Graham, Elmo, Hall-Mark, Nu Horizons, Pioneer, and Wyle. Authorized Maxim Representatives: Alabama, (205) 830-0498; Arizona, (602) 730-8093; California, (408) 248-5300, (619) 278-8021, (714) 261-2123, (818) 704-1655; Colorado, (303) 799-3435; Connecticut, (203) 384-1112; Delaware, (609) 778-5353; Florida, (305) 426-4601, (407) 830-8444; Georgia, (404) 447-6124; Idaho, (503) 292-8840; Illinois, (708) 358-6622; Indiana, (317) 844-8462; Iowa, (319) 393-2232; Kansas, (816) 436-6445; Louisiana, (214) 238-7500; Maryland, (301) 644-5700; Massachusetts, (617) 329-3454; Michigan, (313) 583-1500; Minnesota, (612) 944-8545; Mississippi, (205) 830-0498; Missouri, (314) 839-0033, (816) 436-6445; Montana, (503) 292-8840; Nebraska, (816) 436-6445; Nevada, (408) 248-5300; New Hampshire, (617) 329-3454; New Jersey, (201) 428-0600, (609) 778-5353; New Mexico, (602) 730-8093; New York, (201) 428-0600, (607) 754-2171; N. Carolina, (919) 851-0010; Ohio, (216) 659-9224, (513) 278-0714, (614) 895-1447; Oklahoma, (214) 238-7500; Oregon, (503) 292-8840; E. Pennsylvania, (609) 778-5353; W. Pennsylvania, (614) 895-1447; S. Carolina, (919) 851-0010; Tennessee, (404) 447-6124; Texas, (214) 238-7500, (512) 835-5822, (713) 789-2426; Utah, (801) 561-5099; Virginia, (301) 644-5700; Washington, (206) 823-9535; W. Virginia, (513) 278-0714; Canada, (416) 238-0366, (613) 225-5161, (604) 276-8735, (514) 337-7540.

Maxim is a registered trademark of Maxim Integrated Products. © 1991 Maxim Integrated Products.

Have a problem with your subscription?

We want to solve it to your complete satisfaction, and we want to do it fast. Please write to:

RF Design, 5615
W. Cermak Rd.,
Cicero, IL 60650.

You can help us by attaching your magazine label here, or copy your name and address as it appears on your label. Send this along with your correspondence.

Name	Address	City	State	Zip

Moving?

Simply attach the mailing label from this magazine and write in your new address below. (Please allow 4-8 weeks.)

Your New Address Goes Here

Name _____

Address _____ Apt. # _____

City _____

State _____ Zip _____

Subscription Rate:

12 issues \$38. Add \$14 a year for foreign orders.

☐ Renewal ☐ New Order

For Fast Service...

...it is better to write us concerning your problem and include the magazine label. Also, address changes are handled more efficiently by mail. However, should you need to reach us quickly the following number is available:

1-708-656-8266

RFdesign

5615 W. Cermak Rd. • Cicero, IL 60650

RF calendar

May

14-16

IEEE Instrumentation and Measurement Technology Conference

Omni Hotel, Atlanta, GA
Information: Robert Myers, 3685 Motor Avenue, Ste. 240, Los Angeles, Ca 90034. Tel: (213)-1463. Fax (213) 287-1851.

29-31

45th Annual Symposium on Frequency Control

Los Angeles Airport Marriott, Los Angeles, CA
Information: Annual Symposium on Frequency Control, PO Box 826, Belmar, NJ 07719.

June

3-5

First Virginia Tech Symposium on Wireless Personal Communications

Virginia Tech, Blacksburg, VA
Information: Prof. Theodore S. Rappaport, Director, Mobile & Portable Radio Research Group, Virginia Polytechnic & State University, Blacksburg, VA 24061 -0111.

4-6

'91 International Communications Association Expo

Anaheim Convention Center, Anaheim, CA
Information: Angela Gallagher, ICA, 12750 Merit Drive, Suite 710, LB-89, Dallas, Texas, 75251. Tel: (214) 716-4124.

11-13

MTTS International Microwave Symposium and Expo

Boston, MA
Information: Tel: (617) 769-9750.

13-14

ARFTG

Boston, MA
Information: ARFTG, c/o Henry Burger, 1061 E. Frost Drive, Tempe, AZ 85282. Tel: (602) 839-6933.

24-27

Test Engineering Conference

Georgia World Congress Center, Atlanta, GA
Information: Miller Freeman Expositions. Tel: (800) 223-7126 or (617) 232-3976.

25-27

EMC Expo '91

Walt Disney World Resort, Orlando, FL
Information: Ellen Lunsford, Registration. Tel: (703) 347-0030.

July

15-18

Communication Networks West '91

Moscone Center, San Francisco, CA
Information: Conference Sales, Tel: (800) 225-4698.

22-24

Fifth International Conference on HF Radio: Systems and Techniques

Edinburgh Conference Centre, Edinburgh UK
Information: Secretariat, Conference Services, IEE, Savoy Place, London WC2R 0BL, United Kingdom. Tel: 071 240 1871 ext. 222.

August

13-15

IEEE 1991 International Symposium on Electromagnetic Compatibility


Cherry Hill, NJ
Information: IEEE International Symposium on EMC, PO Box 609, Lincroft, NJ 07738. Tel: (201) 386-2378.

8×8 VIDEO CROSSPOINT SWITCH WITH BUFFERS -ONLY \$2.50*/CHANNEL

Connects Any Input to Any Output

Maxim's new **MAX456** is the **first** monolithic 8×8 video crosspoint switch that routes standard video signals (NTSC, PAL, SECAM). With a digitally controlled 8×8 switch matrix, control logic, and eight 35MHz output buffers together in a 40-pin DIP or 44-pin PLCC, the MAX456 significantly reduces component count, board space and cost over discrete designs. Applications include video surveillance, imaging, visual automation, and video editing.

MAX456 Eliminates Over 20 Components

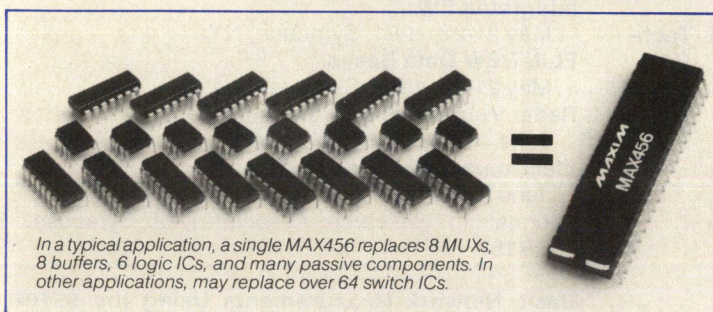


- Reduces Board Space up to 5X
- Reduces Cost 5X Compared to Discrete Designs
- Reduces Design and Layout Time
- Reduces Stray Capacitances
- Improves Reliability

Build Larger Crosspoint Arrays

Each MAX456 buffer output can be disabled under logic control. With three-state outputs, multiple MAX456s can be paralleled to form larger switch networks.

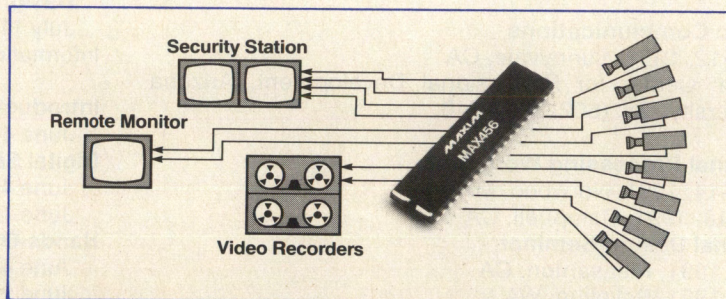- **Eight Internal Buffers**
250V/ μ s Slew Rate
35MHz Bandwidth
Buffer Disable Saves Power
- ± 5 V Power Supplies
- 80dB Off Isolation at 5MHz
- 70dB Crosstalk at 5MHz
- Serial or Parallel μ P Interface



MAX456 and MAX457s Drive 75 Ω Loads

Maxim also offers the MAX457, a dual 70MHz unity gain stable video amplifier. The MAX456 teams up with the MAX457 to drive 75 Ω loads efficiently. Special pricing is available for MAX456/MAX457 combination purchases.

Call your Maxim representative or distributor today for applications information, data sheets, and free samples. Or, contact Maxim Integrated Products, 120 San Gabriel Drive, Sunnyvale, CA 94086, (408) 737-7600, FAX (408) 737-7194

* MAX456CPL, \$19.98 1000-up
F.O.B. U.S.A. price.



Distributed by Arrow, Bell/Graham, Elmo, Hall-Mark, Nu Horizons, Pioneer, and Wyle. Authorized Maxim Representatives: Alabama, (205) 830-0498; Arizona, (602) 730-8093; California, (408) 248-5300, (619) 278-8021, (714) 261-2123, (818) 704-1655; Colorado, (303) 799-3435; Connecticut, (203) 384-1112; Delaware, (609) 778-5353; Florida, (305) 426-4601, (407) 830-8444; Georgia, (404) 447-6124; Idaho, (503) 292-8840; Illinois, (708) 358-6622; Indiana, (317) 844-8462; Iowa, (319) 393-2232; Kansas, (816) 436-6445; Louisiana, (214) 238-7500; Maryland, (301) 644-5700; Massachusetts, (617) 329-3454; Michigan, (313) 583-1500; Minnesota, (612) 944-8545; Mississippi, (205) 830-0498; Missouri, (314) 839-0033, (816) 436-6445; Montana, (503) 292-8840; Nebraska, (816) 436-6445; Nevada, (408) 248-5300; New Hampshire, (617) 329-3454; New Jersey, (201) 428-0600, (609) 778-5353; New Mexico, (602) 730-8093; New York, (201) 428-0600, (607) 754-2171; N. Carolina, (919) 851-0010; Ohio, (216) 659-9224, (513) 278-0714, (614) 895-1447; Oklahoma, (214) 238-7500; Oregon, (503) 292-8840; E. Pennsylvania, (609) 778-5353; W. Pennsylvania, (614) 895-1447; S. Carolina, (919) 851-0010; Tennessee, (404) 447-6124; Texas, (214) 238-7500, (512) 835-5822, (713) 789-2426; Utah, (801) 561-5099; Virginia, (301) 644-5700; Washington, (206) 823-9535; W. Virginia, (513) 278-0714; Canada, (416) 238-0366, (613) 225-5161, (604) 276-8735, (514) 337-7540.

Maxim is a registered trademark of Maxim Integrated Products. © 1991 Maxim Integrated Products.

RF courses

Fundamentals of Radar Cross Section

May 20-24, 1991, San Diego, CA
Information: Kelly Brown, SCEEE, Tel: (407) 892-6146.

Microwave/Millimeter Wave Monolithic Integrated Circuits

June 4-7, 1991, Los Angeles, CA

Radiation Hardening of Electronic Systems

June 10-14, 1991, Los Angeles, CA
Information: UCLA Short Course Program Office. Tel: (213) 825-3344. Fax: (213) 206-2815.

Frequency Hopping Signals and Systems

May 20-22, 1991, Washington, DC

Principles of High Frequency Radio Communications: Applications for Operators and Managers

May 20-23, 1991, Washington, DC

New HF Communications Technology: Advanced Techniques

June 3-7, 1991, Washington, DC

Spread Spectrum Communications Systems

June 10-14, 1991, Washington, DC

Introduction to Modern Radar Technology

June 26-28, 1991, Washington, DC

Ionospheric Radio Propagation for System Planners

July 8-11, 1991, Washington, DC

Radio Frequency Spectrum Management

July 8-12, 1991, Washington, DC

Synchronization in Spread-Spectrum Systems

July 15-19, 1991, Washington, DC

Information: The George Washington University, Continuing Engineering Education, Merril A. Ferber. Tel: (202) 994-8522 or (800) 424-9773.

Fiber Optic Communications

June 10-12, 1991, Sunnyvale, CA

Information: Center for Professional Development, Arizona State University. Tel: (602) 965-1740.

Digital Signal Processing Workshop

June 12-14, 1991, Norwood, MA

July 16-18, 1991, Campbell, CA

Mixed Signal Design Seminar

May 15, 1991, Pleasanton, CA

May 16, 1991, Bellevue, WA

May 17, 1991, Beaverton, OR

May 20, 1991, Woburn, MA

May 21, 1991, Montreal, Canada

May 22, 1991, Bloomington, MN

May 23, 1991, Houston, TX

May 24, 1991, Dallas, TX

May 28, 1991, Phoenix, AZ

May 29, 1991, Denver, CO

May 30, 1991, Arlington, Heights, IL

May 31, 1991, Rochester, NY

Information: Analog Devices, DSP Applications Department, Maria Butler. Tel: (617) 461-3672.

Touchstone/Academy

June 3-7, 1991, Gilching, Germany

Libra/Academy

June 17-21, 1991, Baltimore, MD

June 17-21, 1991, Gilching, Germany

Information: EEsof. Tel: (818) 991-7530. Fax: (818) 991-7109.

Frequency-Time and Spatial-Time Signal Processing

June 10-14, 1991, United Kingdom

Information: CEI-Europe/Elsevier, Mrs. Tina Persson, Box 910, S-612 01 Finspong, Sweden. Tel: 46 (0) 122-17570. Fax: 46 (0) 122-14347.

Modern Power Conversion Design Techniques

May 20-21, 1991, San Rafael, CA

July 15-19, 1991, Chicago, IL

Information: e/j Bloom Associates, Joy Bloom. Tel: (415) 492-8443. Fax: (415) 492-1239.

ELINT Interception

May 14-16, 1991, Syracuse, NY

ELINT/EW Applications of Digital Signal Processing

May 14-16, 1991, Syracuse, NY

Integrated EW

May 21-22, 1991, Syracuse, NY

ELINT/EW Data Bases

May 21-23, 1991, Syracuse, NY

Radar Vulnerability to Jamming

June 4-5, 1991, Syracuse, NY

Electromagnetic Propagation

June 4-6, 1991, Syracuse, NY

Information: Research Associates of Syracuse. Tel: (315) 455-7157.

Basic Network Measurements Using the 8510B Network Analyzer

May 29-31, 1991, Los Angeles, CA

June 11-13, 1991, San Francisco, CA

June 18-20, 1991, Atlanta, GA

June 25-27, 1991, Los Angeles, CA

Designing for EMC

July 11-12, 1991, Atlanta, GA

Information: Hewlett-Packard Company. Tel: (714) 999-6700.

Introduction to Fiber Optic Communications

June 4-7, 1991, San Francisco, CA

Digital Signal Processing: Techniques & Applications

June 4-7, 1991, San Francisco, CA

June 18-21, 1991, Washington, DC

Hands-On Datacomm Troubleshooting

June 4-7, 1991, Washington, DC

June 25-28, 1991, San Francisco, CA

Introduction to Telecommunications

June 11-14, 1991, Los Angeles, CA

June 25-28, 1991, Washington, DC

Information: Learning Tree International. Tel: (800) 421-8166, (703) 893-3555, (203) 417-8888.

Introduction to EMI/RFI/EMC

May 21-23, 1991, Washington, DC

June 24-25, 28, 1991, Orlando, FL

EMI Control Methodology and Procedures

May 21-24, 1991, Philadelphia, PA

Practical EMI Fixes

June 3-7, 1991, Las Vegas, NV


Grounding and Shielding

June 24, 27, 28, 1991, Orlando, FL

System Integration and Design for EMC

June 24, 25, 28, 1991, Orlando, FL

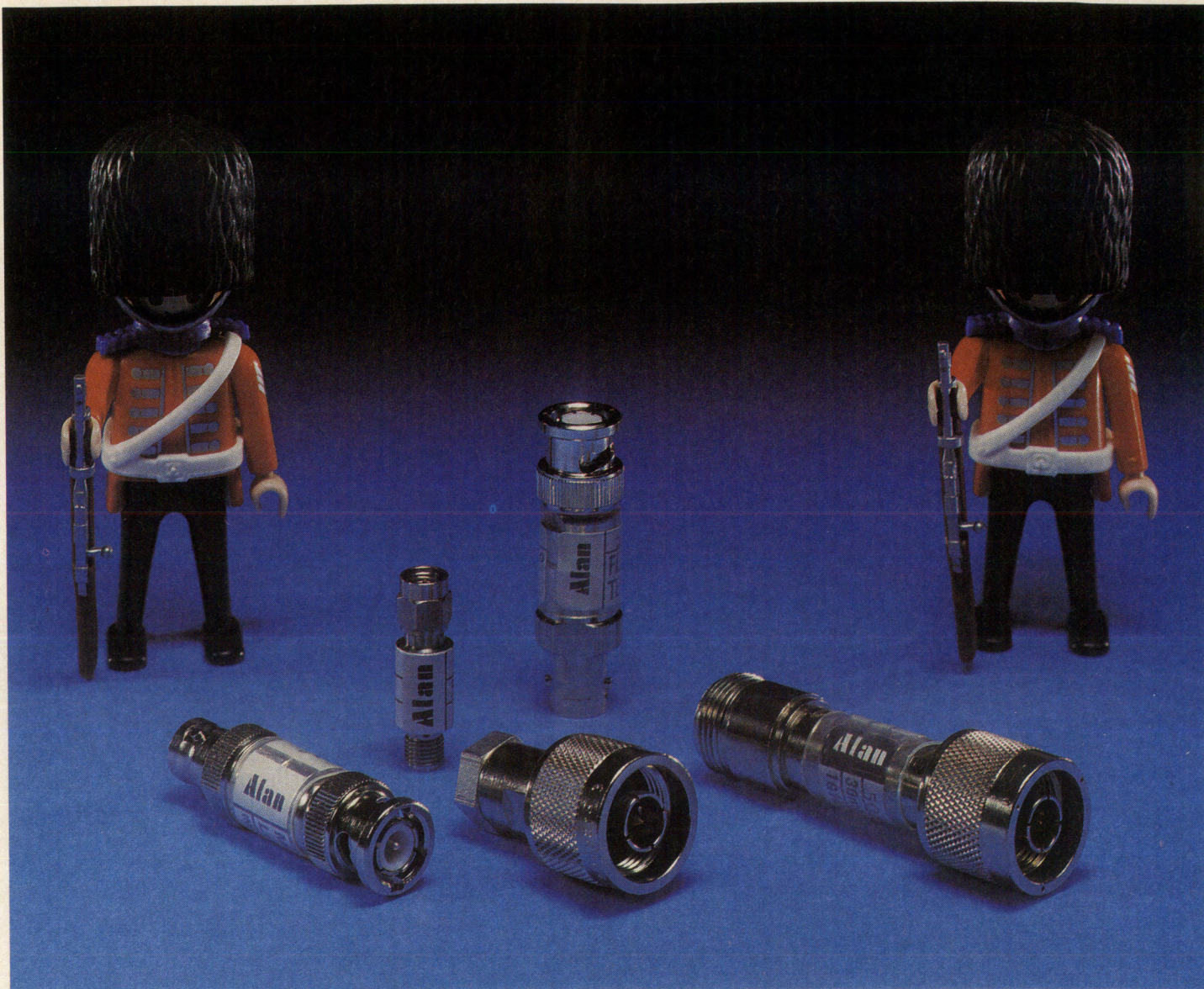Information: Interference Control Technologies, Registrar. Tel: (703) 347-0030.



Fixed Sentries

Alan precision SP and MP fixed attenuators handle 2 watts average power and up to 750 watts peak power. These accurate, quiet components offer low VSWR and operate over -55 to $+125^{\circ}\text{C}$. Select from a wide choice of attenuation values, broadband frequency coverage, connector options and

MIL-Qualified models. Key accessories include Z Series impedance matching pads and F and T Series terminations.

For more information on how our products can help guard your equipment call us today, toll free.

Alan Industries, Inc.

745 Greenway Drive, P.O. Box 1203, Columbus, Indiana 47202

Phone: 812-372-8869 **CALL TOLL FREE: 800-423-5190**

FAX: 812-372-5909

Alan


Manufacturers of...

Attenuators: Programmable • Rotary • Manual Switch • Fixed • Continuously Variable
Accessories: Loads • Dividers • Terminations • RF Fuses • Bridges

Two Bits.


FIELD
TESTED
AND
IMPROVED!

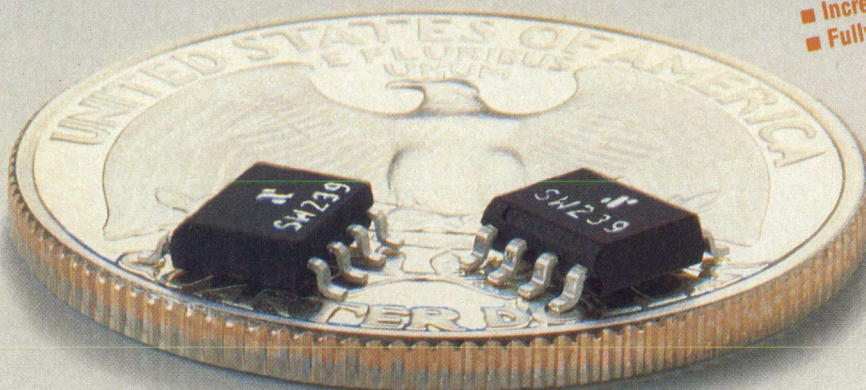- Improved Frequency Performance
- Increased Operating Temperature Range
- Fully Passivated Die



ANZAC Does It Again!

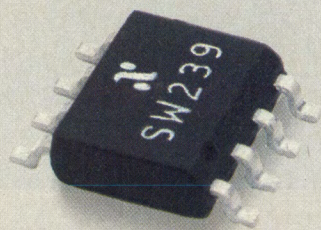ANZAC offers yet another GaAs Monolithic alternative to pin diode switch technology.



The SW-239 SPDT RF switch features nanosecond speed with only microwatts of DC power.

Utilizing an 8-Lead SOIC package these units come ready for full automatic insertion.

Tomorrow's GaAs MMIC technology can be yours today for just a handful of quarters. (40 to be exact.)

Contact your local ANZAC distributor or representative today.

\$10.00

STOCK
DELIVERY



MODEL SW-239 Performance Characteristics	
Frequency Range	DC-2000 MHz
Operating Temperature	-40°C to +85°C
Insertion Loss	0.5 dB
VSWR	1.1:1
Isolation	50 dB
1 dB Compression	+27 dB
Switching Speed	4 nsec TYP
Package	8 Lead SOIC (3.8mm x 4.8mm)

ANZAC
A **MACOM** COMPANY

80 Cambridge Street Burlington, MA 01803 (617) 273-3333 FAX: (617) 273-1921

INFO/CARD 16

Bell Atlantic to Expand Microcell Technology

— Bell Atlantic Mobile has announced that it will expand its use of microcellular technology to enhance cellular reception indoors in public locations. The first location will be Amtrak's Union Station in Washington, DC. Microcell technology utilizes the cellular concept on a smaller scale than the traditional car usage. It will use extremely low-power cell sites in heavily trafficked areas. A cell site, housing computer-controlled transmitters and receivers, is a key piece of the cellular system, serving as a gateway to the traditional telephone network. In Union Station, a suitcase-sized transmitter and antenna will be placed in the Amtrak passenger waiting area. The initial equipment was developed by NovAtel Communications, Inc. Regardless of what network equipment is in use at a given time, customers will be able to make calls on their cellular phones while within the microcell's coverage area. Initially, the microcell will not be connected to the outside "macrocellular" system. Later this year, the two will be interconnected and customers will be able to make and receive calls, as well as hand-off calls as they leave the station.

Tektronix Announces Equipment Grant

— Tektronix Inc. recently presented a grant to the University of Minnesota's Institute of Technology School totaling approximately \$130,000 in the form of state-of-the-art engineering equipment. The contribution is comprised of test and measurement equipment manufactured by Tektronix and includes such instruments as digital oscilloscopes, spectrum analyzers, digital voltmeters, function and pulse generators, and color plotters. The equipment is dedicated for use at the newly-constructed senior design lab at the school.

USSR Air Traffic Control Modernization

— AT&T, Westinghouse, IBM, C. Itoh and Daimler-Benz have committed themselves to an approximately \$10 billion modernization of the Soviet air traffic control system. The plan is slated for completion by the year 2005. The plan calls for merging of Soviet national airspace plans with air traffic control plans of the United States, Canada, Europe and Asia.

Researchers Develop New Class of Antenna

— Engineers at the Georgia Tech Research Institute have

developed a new class of microstrip antenna that combines the broad-band performance typical of spiral and sinusoidal antennas with the surface mount capabilities, efficiency and low cost of microstrip antennas. The new antenna design was developed through a research program supported by the U.S. Air Force's Wright Research & Development Center. Though designed for mili-

tary use, the new antenna could have widespread commercial applications such as cellular telephones, identification, satellite communications, inter and intra-building communications and the tracking of ground shipments. The antenna uses existing technology and therefore could be mass-produced at a low-cost.

The antenna was developed using



Need A New Way To Tune Your Filter?

Why Not Consider The New ATC STA-TUNE™ Adjustable Multilayer Capacitor?

STA-TUNE™ Capacitors, which brought you all the advantages of trimmers and multilayer capacitors in one 1/8 inch surface mount package, are now available in kit form. STA-TUNE is built with an external electrode employing a unique four-pad design, which allows incremental capacitance increases. In-circuit value adjustment is accomplished by connecting one of six (6) different capacitance combinations. The Kit includes a conductive epoxy pen for attachment. Kit Number ATC ST2001 is available from stock through ATC's QUIK-PICK 48 HOUR SYSTEM™. ATC ST2001 contains 3 pieces each of 22 capacitance values from 1.0 to 68 pF.

Call our APPLICATIONS HOTLINE
(516) 547-5708

SEE US AT MTT-S '91, BOOTH NO. 608



american technical ceramics corp.
one norden lane, huntington station, n.y. 11746-2102 usa
phone 516-547-5700 • telex 825707 • fax 516-547-5748



INFO/CARD 17

See
M/A-COM's
Latest Technology
at MTT-S #1005

Stripline Solutions

Couplers, Power Dividers, Hybrids

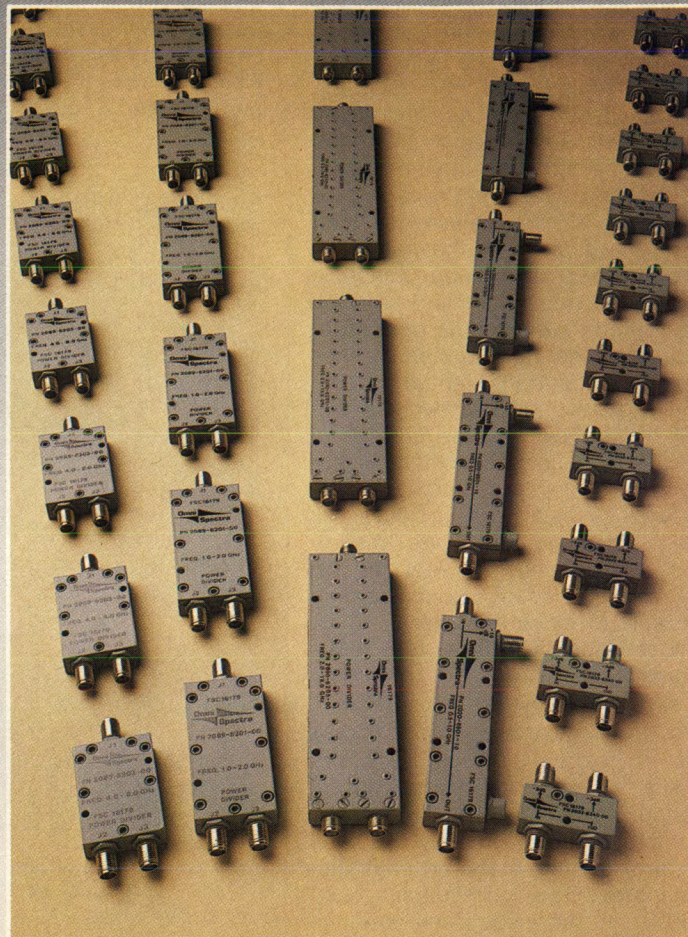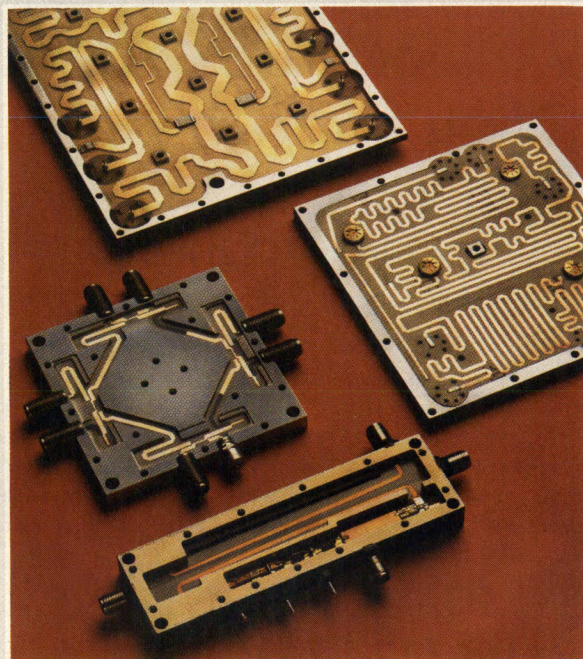- 0.5 to 50 GHz, Octave and Multi-Octave Bandwidths
- Rugged Stripline Construction
- Small Lightweight Designs
- Meet MIL-E-5400 and MIL-E-16400 Environments, Operation from -65° to $+125^{\circ}$ C
- Power Handling to 100 Watts CW
- 3, 6, 10, 20 and 30 dB Couplers In Stock
- 2-, 3-, 4- and 8-Way Power Dividers In Stock
- Mil-Spec Equivalents In Stock
- 90° , 180° , Magic "T", Crossover, Non-Crossover Hybrids In Stock



- Phase and Amplitude Matched Units
- Customized and Multi-Function Designs
- Space Qualified Units

M/A-COM Control Components Division offers the industry's broadest line of standard and custom Couplers, Power Dividers and Hybrids.

Find your Stripline Solution. Call or write today for our NEW Passive Component Catalog.

M/A-COM Control Components Division
21 Continental Blvd., Merrimack, NH 03054
Tel: 603-424-4111 Fax: 603-424-6580

two different antenna technologies: the broad-band spiral technology and the microstrip technology. While most microstrip antennas offer a bandwidth of just 10 percent, the new design offers bandwidths as high as 500 to 600 percent.

Direct Conversion Technique Relocates — Direct Conversion Technique (DCT) recently announced the opening of its new headquarters facility in Des Plaines, Illinois. Their new address is 1245 Forest Avenue, #12, Des Plaines, IL 60016. Tel: (708) 827-2282. Fax: (708) 827-2280.

MIC Technology Acquires Thin Film Coating and Patterning Business — MIC Technology has acquired the U.S. portion of the thin film coating and patterning business of Materials Research Corporation's Hybrid Products Division. MIC will operate this business as the Thin Film Division of MIC Technology. Materials Research Corporation will retain its European based Hybrid Products Division and continue to service the European market.

EEsof Users' Group to Meet at 1991 IEEE MTT Symposium — EEsof Inc. will sponsor the MTT-S meeting of its Users' Group, June 11 from 5:00 p.m. to 7:30 p.m. in room 311 at the Hynes Convention Center, Boston, MA. The EEsof Users' Group invites both members and non-members to attend the meeting. Technical papers will be presented investigating the use of CAE/CAD software applications in microwave and RF circuitry design. Proceedings will be available at the meeting.

Magnavox to Provide Pilot Automatic Vehicle Location System — Magnavox/Nav-Com has won a contract to provide the Swedish Road Administration with a pilot Automatic Vehicle Location System (AVLS), which will be used to track the location and movements of vehicles at a central facility. The vehicle navigation system uses a small multi-channel GPS receiver, which determines the vehicle's location from signals broadcast from the satellite based Global Positioning System. The Swedish Road Administration will provide the data link for the vehicles, based on the established Mobitex radio data communications network. The vehicles will be equipped with Volvo VTS

MC100 data terminals, which will be interfaced with the Magnavox navigation system, and will transmit AVLS messages to the central facility. There, using Magnavox-developed software, the vehicle positions are displayed on a 19 inch color graphics monitor.

IITS Purchases Dash, Straus & Goodhue — Inchcape Inspection and

Testing Services recently announced the purchase of Dash, Straus & Goodhue (DS&G). DS&G is involved with compliance testing for electrical and electronic products, particularly in the area of electromagnetic compatibility, including testing for electromagnetic interference and radio frequency interference. DS&G will become a member of IITS's Manufactured Goods Testing Group.



CAN WE TALK A BIT?

Looking for a better alternative to expensive telephone line data transmission?

THINK LINKS!

"LINKS"

Neulink's line of superior telemetry products offers "quick as a links" industry standard Telemetry Transmitters, Receivers, Transceivers and Full Duplex Panels.

- Speech, Data, AFSK, and RS 232 Compatible Interfaces.
- 2-4 Wire Hybrid, Duplexers, RF Bypassed Connectors and Radio Control Links.
- Each piece environmentally tested for temperature stability.
- Adjustable RF Power Output Control
- Low Current Drain



RF NEULINK

Unlimited Lifetime Warranty

(National) 800-233-1728 (FAX) 619-587-0049 (TELEX) 499-3540 LSV 10040 Mesa Rim Road, San Diego, CA 92121

Microwave Hybrid Circuits Call For Papers

— A call for papers has been issued for the 1991 Microwave Hybrid Circuits Conference. The conference will be held October 13-16 in Sedona, Arizona. The conference theme is "Designing for Production — Issues in the Transition from the Drawing Board to the Factory Floor." Papers describing new work will be considered on the

following subjects: innovative MIC and MMIC design; MIC processing and quality issues; advancement in MIC materials; MIC materials testing; MMIC packaging techniques; unsolved problems in MIC design or implementation; and Taguchi methods and design centering techniques. Abstracts are due June 1, 1991. Abstracts should be sent to: MHCC, c/o Toshikazu Tsukii, Pro-

gram Chairman Raytheon ESD, 6380 Hollister Avenue, Goleta, CA 93117. Tel: (805) 967-5511. Fax: (805) 964-0470.

New Report on Future of Broadcast Transmission Systems

— A new report issued by Elsevier Advanced Technology discusses the future of broadcast transmission systems to the year 1995 and beyond. The report, "The World Market for Broadcast Transmission Systems to 1995," discusses the effects of slow economic growth on the market, the changing political climate, increased competition and long term trends. Areas of special interest include the continuing expansion of alternative broadcasting technologies such as satellite and cable used for broadcasting transmission. The report predicts a doubling of the number of households who receive satellite or cable within a few years. Direct broadcasting by satellite is also expected to increase rapidly. The falling demand for LF and HF transmissions is also discussed and the subsequent changes in companies who will serve that market. On the brighter side, the growth of FM and TV transmission systems are expected to show significant growth especially in less developed countries. Problems are expected though in areas such as southern Europe where stricter spectrum management policies will be put into place.

Federal Rules on Antennas Should Supersede Local Rules

— The NAB has called for broader federal authority over local zoning restrictions on satellite dishes and other types of radio and TV antennas. The NAB made these comments to the Federal Communications Commission because many of the nation's municipal rules on radio and TV antennas are "undefined and unreasonable." These requests were made as a result of a Deerfield, New York zoning ordinance on satellite dishes.

Arlon Announces Plant Expansion

— Arlon, Microwave Materials Division has announced a 75,000 square foot building addition and equipment acquisition. The new facility will contain production, quality control, and testing laboratories for the company's PTFE laminated substrate materials. The addition is expected to be completed in February 1992 and will complement the company's existing 60,000 square foot facility.

Good Sines & Bad Signs

Looking for a low-noise, fast-switching signal source?

Good Sines

Whether it's automatic test equipment, satellite uplinks, EW communications or imaging systems, **Programmed Test Sources** has a frequency synthesizer to fit your needs. GE MRI units, Teradyne Testers, Varian Spectrometers... all use **PTS** synthesizers.

Bad Signs \$\$\$

And while other manufacturers have big dollar signs, PTS synthesizers start as low as \$1,950.

PTS manufactures a complete line of precision synthesizers covering the 100 KHz to 1 GHz frequency range with switching times as fast as 1μ second for our **direct digital** models. And plenty of other options as well, like resolution down to .1 hertz (millihertz available as special order), GPIB and digital phase rotation.

Just as important, along with every **PTS** synthesizer comes our "absolutely everything covered" **2-year warranty**. At the end of two years comes our flat \$350 service charge for any repair up to the year 2001! **PTS** has a commitment to quality you won't find anywhere else.

Find out how **PTS** synthesizers used the world over can help you in for your application today. Call for our complete catalog, or to talk to an applications engineer.

Call (508) 486-3008 Fax (508) 486-4495

PTS

PROGRAMMED TEST SOURCES, Inc.
9 Beaver Brook Road, P.O. Box 517, Littleton, MA 01460



RF Technologies Announces Opening

— A new company has opened who will provide high power and super high power waveguide and coax networks, as well as transmission systems and components. The company, RF Technologies Corporation, will also offer a line of RF instrumentation and control equipment. Their address is 482 Congress Street, Suite 101, Portland, Maine 04101. Tel: (207) 773-7778 or (800) 634-4075.

Motorola and Northern Telecom to Develop Open Cellular System Standards

— Motorola and Northern Telecom recently announced an agreement to develop major enhancements to their existing cellular products for global markets, based on new open system standards. The two companies intend to jointly specify, develop and implement, in connection with the appropriate standards bodies, open cellular system interface standards which will permit operators to purchase cellular system components from a number of vendors. The standards will be based

on existing international switching and cellular standards, such as CCS7, GSM, ISO and ISDN.

New Cellular Network Antenna

— CAL Corporation and Bell Cellular recently introduced a new cellular antenna to improve network performance for cellular users. The low profile sector-beam cellular antenna was developed through a joint venture. The antenna tilt, used to adjust antenna frequency and scope, can be controlled remotely and adjustments no longer need to be done manually.

Antenna Specialists Relocates

— Antenna Specialists Company have announced the moving of its Site Management Products Research and Development Group to new facilities in Reno, Nevada. The new facility, with 50 percent more space, will include additional test equipment and environmental test chambers.

Varian Completes Restructuring

— Varian Associates recently com-

pleted the initial phase of its financial turnaround with the sale of its last remaining non-core business, a broadcast transmitter operation in England, to the Harris Corporation. The sale of this unit and four other non-core businesses and six product lines have generated combined proceeds in excess of \$60 million. The funds will be used for various purposes, including the second phase of Varian's turnaround which involves achieving operational excellence in each of its core businesses — electron devices, analytical instruments, medical equipment and semiconductor equipment.

S.T. Research Receives HPI Receiver System Contract

— S.T. research has been awarded a contract for the development and product of the High Probability of Intercept (HPI) Receiver System from the Naval Sea Systems Command. The contract, depending upon options exercised and ancillary system and support, will exceed \$50 million.

WBE

Celebrating Our 20th Anniversary Year 1971 - 1991

HYBRID POWER DIVIDER/COMBINERS

Models A66 and A67 are hybrid splitter/combiners with exceptional bandwidth and performance for instrumentation and communications. Applications include signal splitting, combining, mixing, and phasing. Due to the high port-to-port isolation, effects of impedance changes, shunts, or disconnections at one or more ports have a minimum effect on the insertion loss or impedance match through the other ports. This high isolation also minimizes intermodulation problems caused by mixing between signal sources.

Each Model A66 or A67 is individually tuned for optimum performance.

Connector options are available. 3-Way, N-Way, and Special Couplers are available. Quantity and O.E.M. pricing.



Model	N-Way	Freq. Range MHz	VSWR (max)	Loss (max) back-back dB	Isolation (with matched input termination) dB	Response Flatness dB	Max Power to Input	Max Power to Output
A66	2	1-500	1.5:1	.7	20	±.25	.5 Watts	.25 Watts
		2.5-300	1.1:1	.30	35	±.1		
A66GA	2	1-500	1.5:1	.7	20	±.25		
		2.5-400	1.1:1	.5	40	±.15		
A66L	2	.3-100	1.5:1	.5	35	±.2		
		1-50	1.1:1	.2	40	±.06		
A66U	2	5-1000	1.2:1	1.0	30	±.3		
A67	4	1-500	1.5:1	1.0	20	±.25		
		2.5-300	1.2:1	.5	30	±.1		

WIDE BAND ENGINEERING COMPANY, INC.

P.O. BOX 21652, PHOENIX, AZ 85036

TELEPHONE: (602) 254-1570

HDTV: The World is Waiting


By Gary A. Breed
Editor

High definition television (HDTV) has clearly reached critical mass in its development. Regular developmental broadcasts are taking place in Europe and Japan, studio video equipment is readily available (although expensive), and component manufacturers are actively developing products for HDTV receivers and monitors.

The components industry is nearly ready for high-volume HDTV manufacturing, although production will wait until the market requires it. Thomson-ICS, Sawtek, and other SAW device houses have announced HDTV IF bandpass filters. Video amplifier and switching components from Maxim, National Semiconductor, Comlinear, Elantec, Burr-Brown and Analog Devices are capable of handling the required bandwidths. Direct satellite broadcast of HDTV is attractive to GaAs front-end suppliers such as Pacific Monolithics, Triquint and Anadigics.

Also required are high performance analog and digital signal processing components. A-to-D and D-to-A converters with at least 10-bit resolution must accurately handle greater than 25 MHz video bandwidth. Digital signal processing circuits have the same constraints. To put the required performance in perspective, current NTSC studio video requires 6 to 10 MHz bandwidths, depending on the ultimate quality level desired, while HDTV requires 25 to 50 MHz.

Studio equipment is already in place, and manufacturers are clamoring to supply networks, stations and video production houses with new systems. Test equipment, cameras, recorders, graphics and special effects, signal routing equipment, signal processing systems, and monitor makers are waiting for the doors to open on a huge market. However, the list of current suppliers is a Who's Who of Japanese electronics. NHK, the Japanese broadcasting agency, sponsored an HDTV "open house" at the recent National Association of Broadcasters convention, and the list of participating companies included 20 major firms such as Sony, Canon, NEC, Panasonic, and Toshiba.

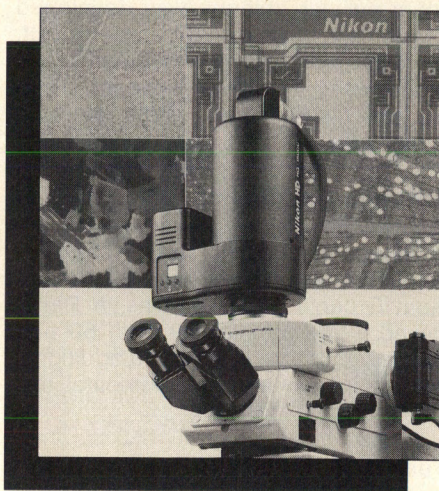

Nikon offers HDTV imaging for microscopic observation.

Non-broadcast applications are helping keep enthusiasm high while broadcast standards evolve. Medical imaging, industrial monitoring and inspection, photo archives, and military display systems are but a few of the more promising applications. For example, Nikon is promoting high resolution imaging systems for microscopy in medical, metallurgical and microelectronic applications. Although alternative high resolution display technologies are available now, many potential applications will not become widespread until the large quantity manufacturing for consumer HDTV receivers brings prices down.

Terrestrial Broadcast

The selection of a method to bring HDTV to homes in the U.S. is the single major problem area at this time. FCC testing of the five applicants for consideration as the broadcast standard has been delayed again, this time due to delivery problems with a standards converter being built by Tektronix. Final development of this complex unit has required hand-picked A to D converters because standard components cause visible defects in the picture.

The goal of the FCC is to complete on-the-air testing by Spring 1992, in order to have evaluation ready for

Commission consideration by September of that year. Selection of a standard is currently planned for early 1993. Many industry and government observers believe that this is the latest possible date that is acceptable, and any further delay will certainly jeopardize the U.S. market position in the world HDTV market.

One industry participant, choosing to remain anonymous, muses, "Why are terrestrial standards holding things up when DBS and fiber are perfectly capable of delivering HDTV?" The strength of the broadcast lobby is one part of the answer to his question, but the situation is not quite that simple. First, neither fiber nor DBS is in widespread use in North America, and the time required to bring those technologies to "universal" status is unknown, perhaps longer than that required for a changeover to a broadcast system that at least approaches the quality available with HDTV.

With HDTV VCRs already developed, and given the current popularity of rented video programming, it will be extremely interesting to see how the average consumer reacts to broadcast television that has somewhat lesser picture quality than taped programming. Currently, the opposite is true.

Which leads us to the biggest question — will the consumer accept HDTV at all? The quality difference is analogous to that of the compact audio disc versus vinyl records, and CDs are enormously successful. However, the improvement offered by stereo AM broadcasting and quadraphonic FM has been generally ignored. Even stereo television sound has been under-utilized.

Will reruns of Gilligan's Island become more interesting on HDTV, or will program producers react to the quality of the medium and produce higher quality programs? The answer to this question is probably the key to HDTV's future, not the technical standards or hardware capabilities.

RF

For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600; ask for the Circulation Department.

Coilcraft Designer's Kits

**First they save you time.
Then they save you money.**

These kits make it easier than ever to pick the right coils, chokes and other magnetics for your project.

Why waste hours calling around

for samples or trying to wind them yourself. Coilcraft's low-cost kits put dozens of values right at your fingertips!

You not only save time on engineering. You also save money when you go into production

because we stock just about all the parts in our kits at low off-the-shelf prices.

Call in today, and you can have your kit tomorrow!

To order, phone **800/322-COIL**.

"Unicoil" 7/10 mm Tuneable Inductors

.0435 μ H - 1.5 μ H
49 shielded, 49 unshielded (2 of each)
Kit M102 \$60

"Slot Ten" 10 mm Tuneable Inductors

0.7 μ H - 1143 μ H
18 shielded, 18 unshielded (3 of each)
Kit M100 \$60

Surface Mount Inductors

4 nH - 33 μ H
48 values (10 of each)
Kit C100 \$125

Axial Lead Chokes

0.1 μ H - 1000 μ H
25 values (5 of each)
Kit F101 \$50

Horizontal Mount Inductors

Tuneable and fixed
Inductance: 31.5 - 720 nH
33 Values (6 of each)
Kit M104 \$60

Common Mode Data Line Filters

Attenuation bandwidth: 15 dBm, 1.5-30 MHz
DC current capacity: 100 mA
2, 3, 4 and 8 line styles (4 of each)
Kit D101 \$65

Common Mode Line Chokes

Current: .25 - 9 amps RMS
Inductance: 508 μ H - 10.5 mH
8 styles (2 of each)
Kit P202 \$100

Current Sensors

Sensing range: 0.5-35 amps
Freq. resp.: 1 - 100 kHz, 50 - 400 Hz
Transformer and sensor-only versions
8 styles (15 total pieces)
Kit P203 \$50

Base/Gate Driver Transformers

Inductance: 1.5 mH Min.
Frequency: 10 - 250 kHz
2 single, 2 double section (2 of each)
Kit P204 \$50

Mag Amp Toroids

Current: 1, 5 amps
Volt-time product: 42 - 372 V- μ sec
6 styles (2 of each)
Kit P206 \$100

Power Filter Chokes

Current: 3, 5, 10 amps
Inductance: 5 - 300 μ H
18 styles (48 total pieces)
Kit P205 \$75

Axial Lead Power Chokes

Current: .03-4.3 amps
Inductance: 3.9 μ H - 100 mH
60 styles (2 of each)
Kit P209 \$150





Coilcraft

CEM/electronic engineers master See our catalog in Vol. A, Section 1800

1102 Silver Lake Rd., Cary IL 60013 800/322-COIL Fax 708/639-1469

Now we should be your 1st source!

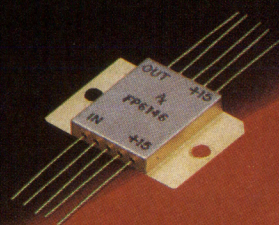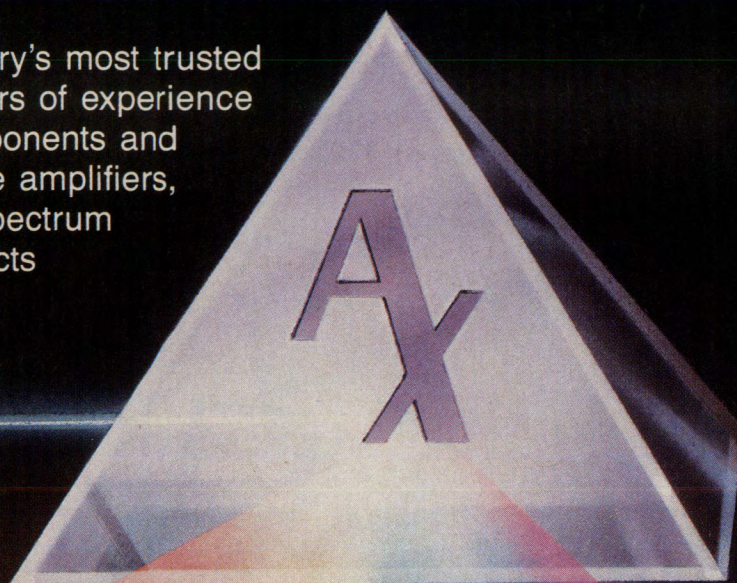Amplifonix is one of the industry's most trusted 2nd sources. With over 10 years of experience in producing high-quality components and thousands of high-performance amplifiers, Amplifonix can deliver a full spectrum of standard and custom products designed to meet your exact specifications.



SWITCHES

GaAs MMIC


Frequency	DC to 2000 MHz
Ins. Loss	0.6 to 2.5 dB
Isolation	35* to 70 dB ⁽¹⁾
Sw. Spd. (Typ.)	7 to 50 μ sec
*1500 MHz to 3,000 GHz (1) DC to 1500 MHz	



AMPLIFIERS

BiPolar/GaAs FET

Frequency	5-2500 MHz
Gain	8 to 40 dB
Noise	1.2 to 9.5 dB
Pwr Out	Up to +27 dBm

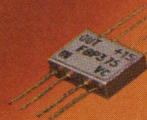


STEP ATTENUATORS

Frequency	10 to 500 MHz
Attenuation Steps	0.1 to 32 dB
Switching Characteristics	1 μ sec to 10 μ sec
Sections	1 to 8 bits



VCOs


Frequency	70 to 2500 MHz
Output Power	+7 to +20 dBm
Phase Noise 10 kHz to 100 kHz	-85 to -125 dBc/Hz
Tuning Voltage Sensitivity	2.25 to 12.0 mHz/V
Supply Voltage	+8 to +20

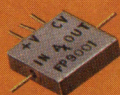

Write or call for complete information.



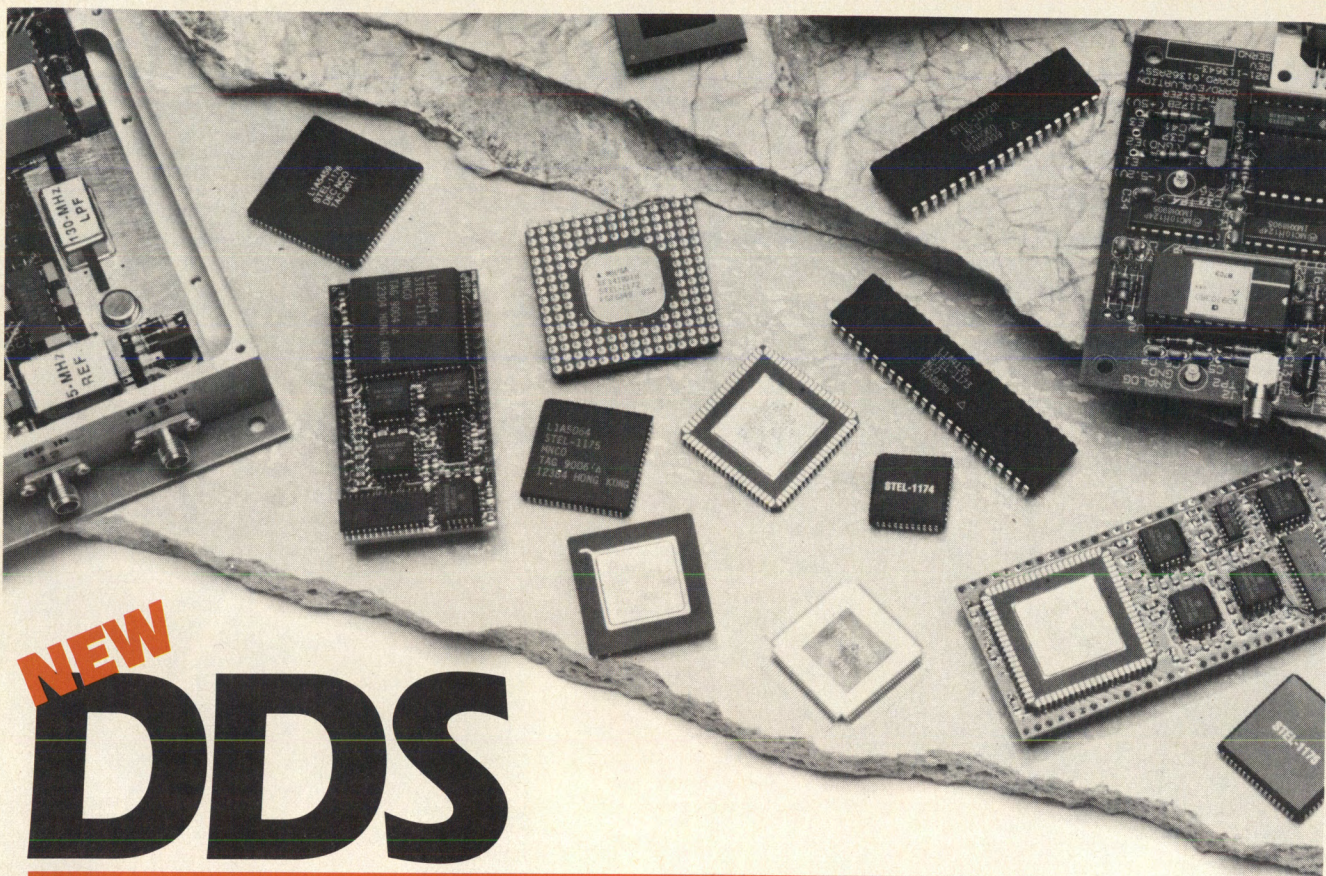2707 Black Lake Place • Philadelphia, PA 19154
PHONE: 215-464-4000 • FAX: 215-464-4001



NEW DDS

PRODUCTS AND PRICES

Stanford Telecom . . . continues to lead the way in providing the highest performance at the lowest cost.

These are but a few of the many outstanding products and prices available today and offered by Stanford Telecom for frequency synthesis and digital communications. For the highest performance and most cost effective solutions in integrated digital communications products, Stanford Telecom continues to stand out as the industry leader.

Call today to discuss how Stanford Telecom might become a member of your team. New prices also available for Stanford Telecom's entire line of Digital Communication ASICs.

**STANFORD
TELECOM®**

ASIC
Custom
Products
Group

2421 Mission College Boulevard
Santa Clara, California 95056-0968
TEL: (408) 980-5684 FAX: (408) 727-1482

STEL-1178 Dual 50MHz NCO **Only \$25***

(Check for compatibility and price savings over other dual NCO's available!)

STEL-2373 750 MHz GaAs Synthesizer **Single Package**

(NCO, DAC, converters, etc. all within a single 70-pin package!)

STEL-1174 50 MHz NCO **Less Than \$20***

(Cost, area, power & spurs are all held to a minimum with this outstanding, low cost performer)

STEL-1176 80 MHz BCD NCO **Only \$50***

(For BCD interface & resolution characteristics, this NCO is not only distinguished, but unmatched in architecture, performance & cost effectiveness)

*1,000 piece quantity

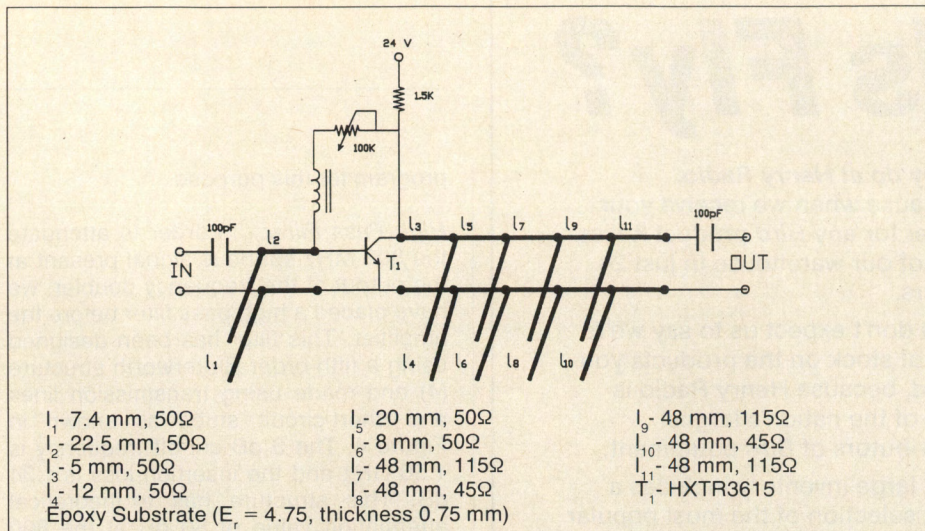


Figure 3. Frequency doubler.

spurious signals around 800 MHz that appear at the frequency doubler output. The output amplifier increases the useful signal level up to 20 dBm. Finally, the low pass filter attenuates the level of the harmonics present in the output signal.

In the paragraphs below we describe the most relevant aspects of each part.

Synthesizer - The synthesizer is built around the integrated circuit NJ8820 from Plessey. This circuit contains a reference oscillator, an 11 bit programmable reference divider, two phase comparators: one digital and one sample and hold type, two programmable dividers: one, called A, that counts down to zero from the programmed input, with a 7 bit length, and the other, called M, that counts up from zero to the programmed input and with a 10 bit length, and finally the necessary control and latch circuitry for accepting and latching the input data. By means of an external dual modulus counter ($N/N+1$), the synthesizer is able to program a total division ratio given by $NM+A$, where A is between 0 and 127, M is always greater than or equal to A and the minimum division ratio is N^2-N . However, the value of N must also be large

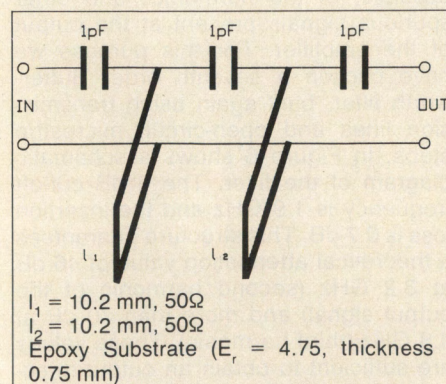


Figure 4. High pass filter.

enough to guarantee that the output frequency from the dual modulus counter not exceed the maximum input frequency of the integrated circuit.

The frequency synthesizer is completed by an active loop filter and a VCO, as shown in Figure 2.

For each synthesized frequency, the NJ8820 circuit reads eight 4 bit words from an external memory. The timing signals needed are provided by the same integrated circuit. With this structure the synthesizer can produce a carrier frequency that ranges from 800 MHz to 850 MHz, with a frequency step of 25 KHz and whose level is around -5 dBm.

Frequency Doubler - The schematic of the frequency doubler is shown in Figure 3. It uses an HXTR3615 transistor as active device. The input matching network is composed of an open circuit microstrip stub and a transmission line, whereas the output matching network uses two open circuit microstrip stubs with two sections of transmission line between them (3). In this case the stub lengths are designed in order to present a $1/4$ length at the second and the third harmonic of the output signal, respectively. In this way the network not only matches the output impedance but also introduces a selective effect to the undesired signals. A band stop filter, tuned at 800 MHz, is placed behind the output matching network. This filter is built using two open circuit microstrip stubs and three transmission line sections. Obviously this filter also eliminates the undesired signals placed around the third, fifth and seventh harmonics of the input signal.

It is important to emphasize that this circuit, and everything described below, have been designed using computer aided design (CAD) techniques. In particular, we used the SuperCompact

Coaxial Switches Delivered in 24 HOURS!

Subject to Stock-on-Hand

Miniature SPDTs

28 VDC
SMA Connectors

DC-22 GHz Failsafe
DC-22 GHz Failsafe with indicators
DC-22 GHz Latching with Indicators

Miniature Transfers

28 VDC
SMA Connectors

DC-18 GHz Failsafe
DC-18 GHz Failsafe with indicators
DC-18 GHz Latching
DC-18 GHz Latching with Indicators

Miniature Multi-Throws


28 VDC
SMA Connectors

DC-18 GHz 1P3T Failsafe
DC-18 GHz 1P4T Failsafe with indicators
DC-18 GHz 1P6T Failsafe
DC-18 GHz 1P6T Failsafe with indicators




TELEDYNE MICROWAVE

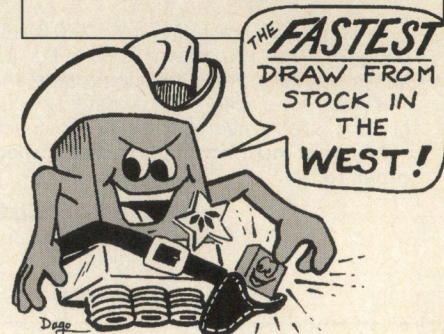1290 Terra Bella Ave.
Mountain View, CA 94043
Phone: 415-960-8610
Fax: 415-966-1521



Do Birds Fly?

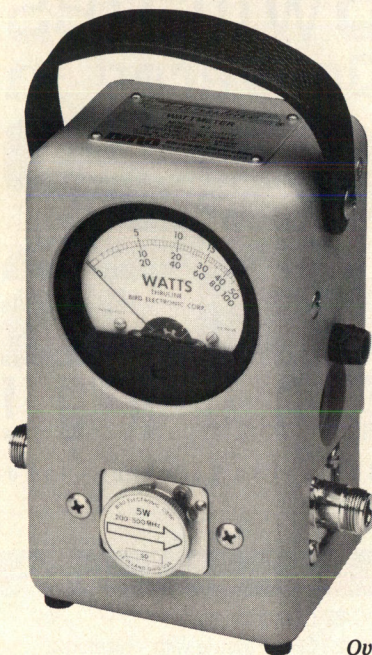

They do at Henry Radio.

Because when we receive your order for any *Bird* product it flies out of our warehouse in just 24 hours.

And don't expect us to say we're out of stock on the products you need, because Henry Radio is one of the nation's largest distributors of *Bird* equipment.

Our large inventory includes a vast selection of the most popular *Bird* equipment, including wattmeters, elements, loads and accessories. So if you're looking for a hard-to-find *Bird* product, call Henry Radio.

HENRY RADIO

Over a half-century of reliability in communications.

2050 S. Bundy Drive, Los Angeles, CA 90025;
TOLL FREE: 1-800-877-7979; FAX: 1-213-826-7790

INFO/CARD 26

RF Design Software Service

Computer programs from *RF Design*, provided on disk for your convenience. All disks are MS-DOS/PC-DOS compatible, unless otherwise noted.

Disk RFD-0591: May 1991

"CAD of Single and Tandem Lange Couplers," by T. O'Connell and P. Murphy. Computes design parameters of Lange couplers, with output in tabular form or in a Touchstone® file format. (Fortran, compiled version and source code listing.

Disk RFD-0391: March 1991

This disk contains "NOVA" by Robert Stanton, a nodal circuit analysis program for AC, time domain, and S-parameter analysis. Numerous models are included, and operating instructions are included in a README file. This is offered by the author as shareware; a co-processor version, additional documentation, and future updates are provided to users who wish to pay for registration.

Disk RFD-0291: February 1991

"Cable Equalizer Design," by Frederick Radler of Trilithic. For the design of equalizers to flatten frequency response of cable runs. (Compiled, executable)

Send for a complete listing of available programs, or circle Info/Card below.

Disks are \$9.00 each (5¼ in.) or \$10.00 (3½ in.). Outside U.S. and Canada, add \$8.00 per order. Foreign checks must be in U.S. funds, and must be payable through the U.S. banking system. Prices include postage and handling.

Annual subscriptions are available, providing 13 disks for \$90.00 (5¼ in.) or \$100.00 (3½ in.). Specify starting date. For subscribers outside the U.S. and Canada: add \$50.00.

Payment must accompany order...specify disks wanted...send check or money order to:

RF Design Software Service

P.O. Box 3702
Littleton, Colorado 80161-3702

Questions and comments should be directed to *RF Design* magazine.

INFO/CARD 100

program for this purpose.

High Pass Filter - In order to attenuate the 800 MHz spurious signal present at the output of the frequency doubler, we have placed a high pass filter before the amplifier. This filter has been designed using a fifth order Butterworth structure (4) and made using transmission lines and short-circuit stubs as shown in Figure 4. The 3 dB cut-off frequency is 1.56 GHz and the insertion loss is 1.34 dB. This structure has a theoretical attenuation value of 50 dB at the 800 MHz band and it guarantees sufficient attenuation of the spurious signals.


Amplifier - The signal level at the output of the frequency doubler is -5 dBm. Therefore, in order to obtain an useful signal of 20 dBm at the transmitter output, the amplifier gain must be approximately 25 dB. This amplifier has three stages with power gains of 10, 10 and 5 dB respectively. The first two stages make use of a HXTR3102 transistor as an active device whereas the output stage uses a BFG34 transistor able to produce the required output level. The matching network between stages is built by means of transmission lines and microstrip stubs in open and short circuit.

In Figure 5 we show the schematic diagram the amplifier. The last two microstrip stubs, placed at the output of the amplifier, are designed in order to attenuate the second and third harmonic respectively. It is important to emphasize that we have chosen for the second stage a short-circuit microstrip stub to diminish the low frequency gain of the amplifier and consequently to increase its stability.


Low Pass Filter - The low pass filter is devoted to attenuation, as much as possible, of the harmonics and other spurious signals present at the output of the amplifier. For this purpose we have chosen a seventh order Butterworth filter, built again using transmission lines and open-circuit microstrip stubs. In Figure 6 shows a schematic diagram of the filter. The 3 dB cut-off frequency is 1.9 GHz and the insertion loss is 0.7 dB. This structure guarantees a theoretical attenuation value of 46 dB at 3.2 GHz (second harmonic of the output signal) and more than 70 dB at 4.8 GHz (third harmonic). These values are sufficient to obtain an output rejection to harmonics and spurious signals greater than 60 dB with respect to the

Trilithic Family Album

From our industry leading surface mount filters to our time-proven rotary and fixed pad attenuators, Trilithic is your source for a complete family of RF and microwave components. Our strict quality assurance standards apply to all product lines, whether your application is for high reliability military or field-tough commercial items. In addition, Trilithic's high stock volume ensures competitive pricing and availability, so call us toll-free at 800-344-2412, and get acquainted with our family.

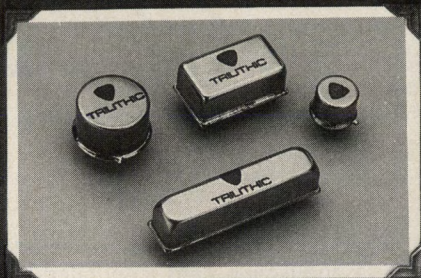


Miniature filters

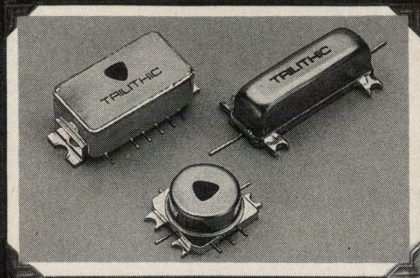


Surface mount filters



Tubular filters

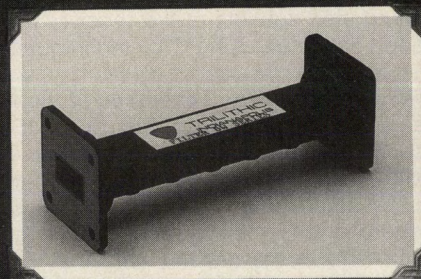


Waveguide filters

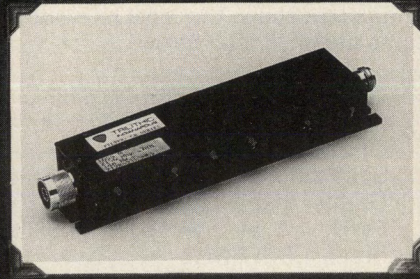

Cavity filters




Tunable filters

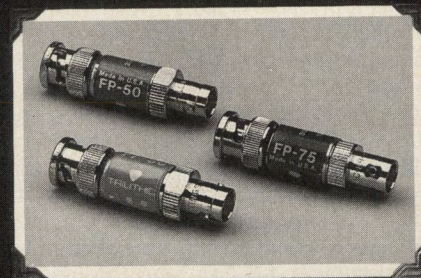


Coaxial attenuators




Pushbutton attenuators

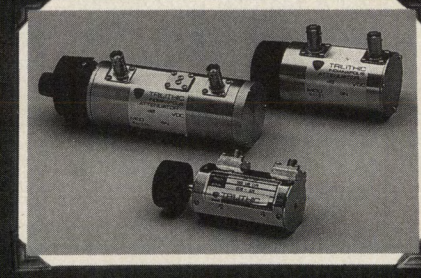


Rotary step attenuators

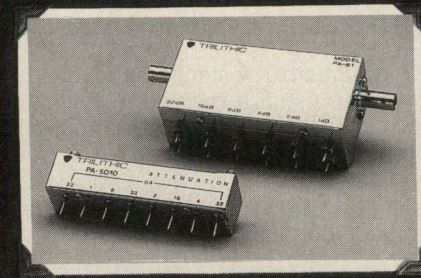

Programmable step attenuators

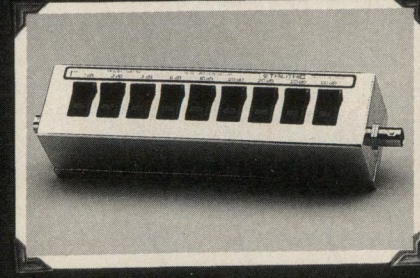

Switch attenuators

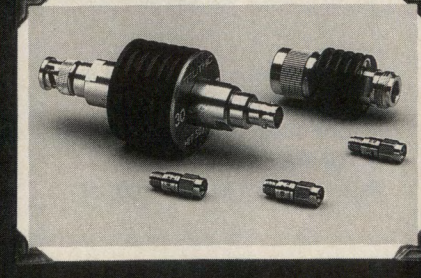

Microwave coaxial attenuators



9202 East 33rd Street • Indianapolis, IN 46236
Phone: 317-895-3600 1-800-344-2412 FAX: 317-895-3613

25 WATTS RF POWER 1-500 MHZ.



NEW, ALL SOLID STATE AMPLIFIER WORKS INTO ANY LOAD IMPEDANCE.

The 525LA is an extraordinarily versatile source of power that will find wide application in virtually all RF labs. Covering the frequency range of 1 to 500 MHz, with a flat 50 dB of gain, the 525LA is driven to its full Class A linear output by any signal or sweep generator.

Like all ENI amplifiers, the 525LA features unconditional stability, absolute protection from overloads, and it will work into any load impedance. So if you need a rugged source of RF power for RFI/EMI, RF transmission, component testing, NMR or transmitter design, the 525LA amplifier could just be the most useful tool in your laboratory.

For more information, or a full-line catalog, contact us at:

ENI
A Division of Astec America, Inc.
100 Highpower Road,
Rochester, NY 14623-3498
(716) 427-8300
Telefax: (716) 427-7839

ENI

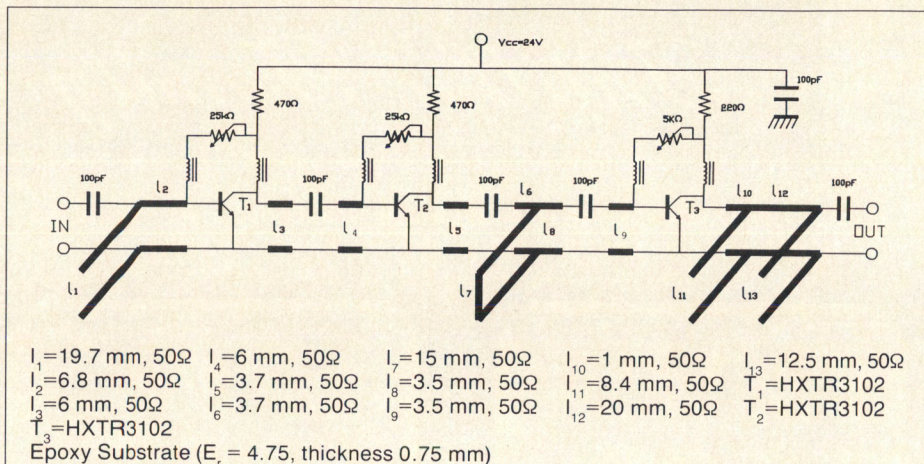


Figure 5. RF amplifier.

useful signal.

Transmitter Performance - Once the transmitter was made, a complete set of measurements was taken for its characterization. The most relevant features are described below:

- Output level: 18.5 dBm - 0.5 dB
- Frequency Range: 1.6 GHz to 1.7 GHz, with 50 kHz steps
- Spurious and harmonic rejection: Greater than 60 dBC
- SWR: 1.5 at 1.65 GHz, <1.85 between 1.6-1.7 GHz

Receiver

The schematic drawing of the CW receiver is shown in Figure 7. We can distinguish six different parts: an RF amplifier that increases the level of the weak signal present at the antenna output; an RF attenuator that generates an appropriate level at the input of the mixer; the mentioned mixer that produces a frequency translation of the received signal to a new carrier frequency of 70 MHz; the local oscillator associated with the mixer; an IF amplifier, and finally a logarithmic amplifier that produces an output signal proportional to the received power at the

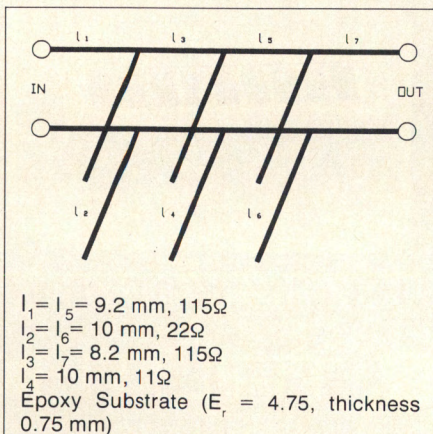


Figure 6. Low pass filter.

antenna port. This signal is delivered to a data acquisition card, controlled by a personal computer (PC), in order to be processed properly.

As with the transmitter, all the above mentioned subsets of the receiver have been designed using CAD techniques.

RF Amplifier - The schematic of the RF amplifier is shown in Figure 8. It is composed of two amplifier stages and a high pass filter. The first amplifier stage is designed to optimize the noise figure whereas the linearity aspects are emphasized in the second amplifier. Both use common emitter structure with transmission lines and open circuit microstrip stubs for the matching circuits. The transistor HXTR3615 from Hewlett-Packard is used as an active device. The power gains are 12.5 dB for the first stage and 13.5 dB for the second, and the 3 dB bands are 1.5-2 GHz and 1.5-1.9 GHz respectively. A high pass filter is placed between both stages which eliminates the noise and all the spurious signals below 1 GHz that could appear in the antenna port. The cut-off frequency is 1.3 GHz and the insertion loss is 0.3 dB. This high pass filter is placed after the first amplifier in order to optimize the noise figure of the receiver.

RF Attenuator - A simple attenuator can be made using a resistive pi structure. If the resistor values are controlled properly this circuit is capable of giving variable attenuation over a wide bandwidth and provide matched impedances in both ports. On the other hand, for

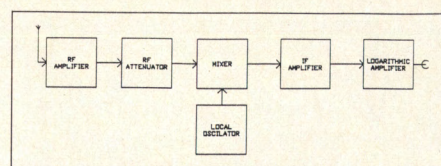


Figure 7. Schematic drawing of the CW receiver.

When Selecting a Spectrum Analyzer, Go by the Numbers.


CATV • EMC/EMI • Mobile Radio • Satellite Communications • Radar • Production test • Broadcast • R&D

from \$12,900 from \$5,995



R3261/3361 Series

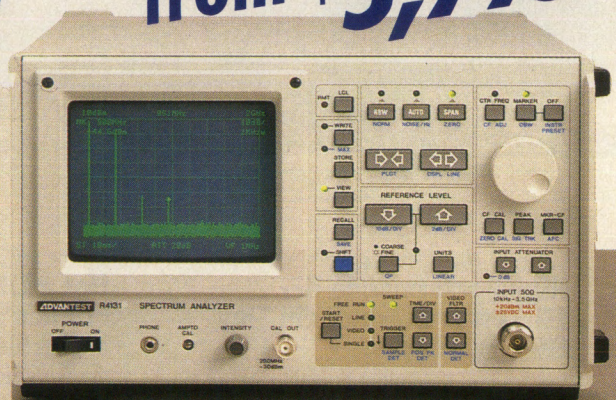- 9kHz to 2.6GHz frequency range for R3261A/3361A
- 9kHz to 3.6GHz frequency range for R3261B/3361B
- 1Hz resolution setting and measurements with synthesis technique
- Also featured are a built-in tracking generator, IC memory card, controller function, preselector and GPIB



R4131C/4131D Series

- 10kHz to 3.5GHz frequency range
- 22lb(10kg) weight for portability
- -80dBc skirt characteristics
- Also featured are built-in quasi-peak measurement and saving/recalling measurement conditions, including waveforms and GPIB

New visions in test instrumentation

ADVANTEST®

Advantest America, Inc. 300 Knightsbridge Parkway, Lincolnshire, IL 60069, U.S.A. (708)634-2552 FAX (708)634-2872

AVANTEK MMICs NATURE, AT A NATURAL PRICE



High Performance RF/ Microwave Circuits in Tiny SMD Packages


Fresh idea. A growing family of DC to 5.0 GHz amplifiers, active mixers, and other high performance monolithic microwave ICs (MMICs), at design conscious prices—as low as \$0.95 each in 10,000 piece quantities. Avantek's new ISOSAT™ process yields a harvest of silicon MMICs in plastic SMD packages for portable, handheld, and low-power high-volume designs, where size and cost are as critical as RF performance.

Cellular, Spread Spectrum, Fiber Optics, GPS—Any RF/ Microwave Application


Avantek, the pioneer of commercial and defense RF/microwave solid-state, offers the ISOSAT family of plastic MMICs in bulk, tape and reel. High-volume, low-cost circuits that meet your highest requirements for low power consumption, bandwidth, low noise (as low as 1.7dB), high gain, stability and cascadeability. ISOSAT products make your linear design goals easy and efficient.

Get a Little Help from Your Friends

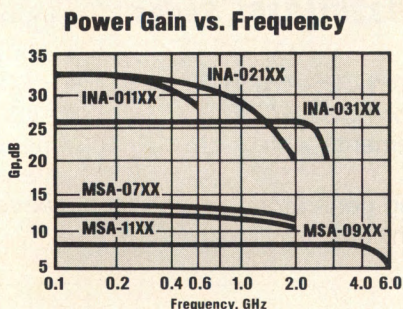
Avantek has over 50 field specialists around the world to assist in developing your RF/microwave designs. And, Avantek ISOSAT amplifier product data is available for use in all major CAE libraries, such as EEsof Touchstone™.



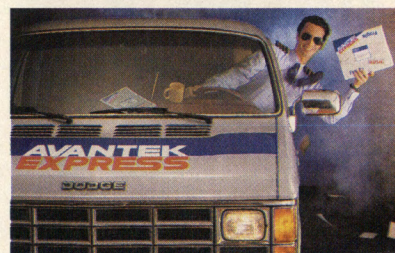With over 20 major stocking locations, and a worldwide trans-shipment operation, Avantek has the largest RF/microwave semiconductor distribution network in the world. We meet the demands of the most demanding JIT programs, or supply critical prototypes with the same matchless service and support.



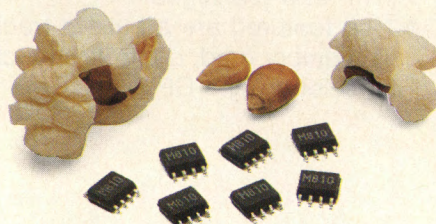**Call Your Local Distributor or
1-(800) AVANTEK for Fast
Delivery**



*Putting Microwave
Technology to Work for You*

AVANTEK

NO WAITING AVANTEK DELIVERS TODAY

North America Distributors

Northeast
Nu Horizons
(617) 246-4442 MA
Sickles Distribution Sales
(617) 862-5100 MA

East Central
Applied Specialties, Inc.
(301) 595-5395 MD
Nu Horizons
(301) 995-6330 MD
(201) 882-8300 NJ
(516) 226-6000 NY
(716) 248-5980 NY
(215) 557-6450 PA
Penstock East
(800) 842-4035 NJ
(516) 368-2773 NY
(215) 383-9536 PA

Southeast
Component Distributors,
Inc.
(800) 558-2351 FL
Nu Horizons
(305) 735-2555 FL

North Central
Penstock Midwest
(708) 934-3700 IL
(317) 784-3870 IN

South Central
Insight Electronics, Inc.
(800) 677-7716 TX
Thorson Distributing Co.
(214) 233-5744 TX

Northwest
Insight Electronics, Inc.
(800) 677-7716

Penstock, Inc.
(800) PENSTOCK
(206) 454-2371 WA

Southwest/Rocky Mountain
Insight Electronics
(800) 677-7716
Sertek, Inc.
(800) 334-7127

Canada
Sertek, Inc.
(800) 548-0409

International Distributors

Europe
Italy
BFI-Ibexsa SpA
(39) 2-331-005-35 Milan
(39) 6-8088191 Rome
Germany
BFI-Ibexsa Elektronik GmbH
(49) 89-3195135
France
Scie Dimes
(33) 1-69-41-8282
Sweden
BFI-Ibexsa Nordic AB
(46-8) 626-99-00
U.K.
BFI-Ibexsa Electronics LTD.
(44) 62-288-2467

Asia and Far East
Japan
Yamada Corporation
(81) 03-3475-1121



**Putting Microwave
Technology to Work for You**

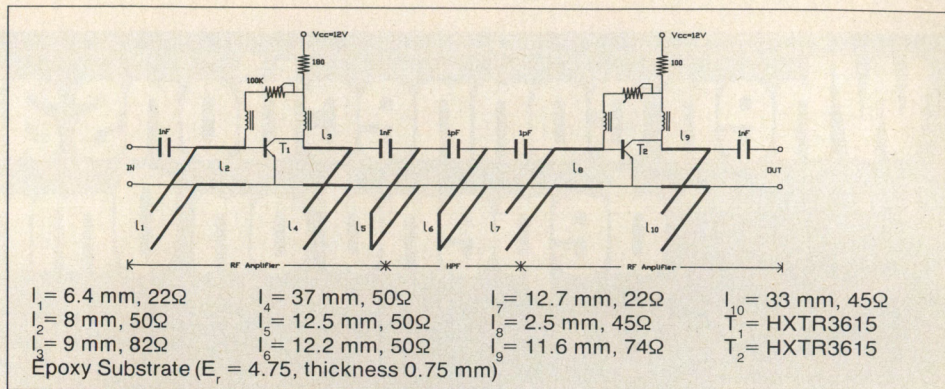


Figure 8. Receiver part: RF amplifier.

small signals at RF frequencies, the PIN diode, when it is conducting, appears essentially as a pure resistor whose value is roughly inversely proportional to the bias current. Moreover, the quality of this resistor, i.e. its linearity and lack of distortion products, can be very good if the diode is used under the right conditions. So, for these reasons the RF attenuator has been made using a PIN diode attenuator, as shown in Figure 9, where the series and parallel bias currents are properly controlled by means of a single control voltage (5). The insertion losses are 1.5 dB, the attenuation reaches up to 18 dB and the SWR ratio is lower than 2 dB in the full range of the attenuation values.

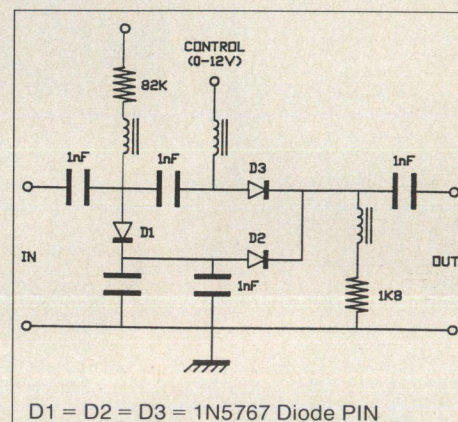


Figure 9. Receiver part: RF attenuator.

Mixer - This circuit is built around the SRA-2000 double balanced mixer from Mini-Circuits. In order to guarantee that the RF port and the IF port have 50 ohms at any frequency, special matching networks have been used (6), as shown in Figure 10. The input network is composed of an impedance transformer, made by means of a transmission line, and a short circuit microstrip stub in series with a 50 ohm resistor. At

the working frequency the stub appears as an open circuit. Then, the impedance transformer changes the output impedance of the RF amplifier (50 ohms) to the nominal mixer impedance of 200 ohms. At lower frequencies the stub appears as a very small inductive impedance. A 50 ohm resistor is placed at the input of the impedance transformer regardless of the source impedance value. Really, at these frequencies, the 10 pF capaci-

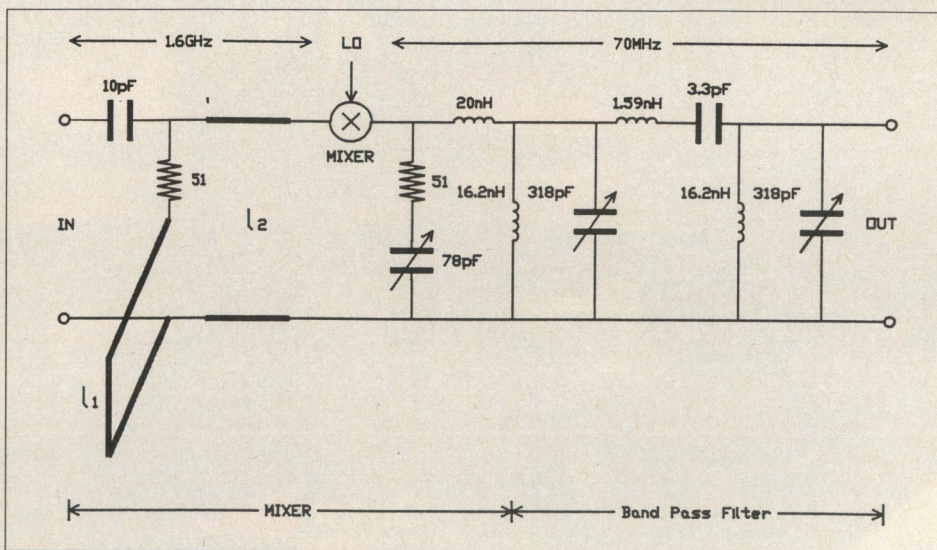


Figure 10. Receiver part: mixer.

When connections are critical, depend on Omni Spectra.

When you need subminiature connectors, depend on the company who makes more of them than anyone else. More people buy SMA's from Omni Spectra because we don't compromise on quality.

Our totally integrated capabilities, coupled with state-of-the-art SPC, assure the highest degree of quality. We control the critical processes of machining, plating, brazing and glass sealing in-house.

When you really need to get small, think big. Depend on Omni Spectra.

For more information, call or write:

M/A-COM Omni Spectra, Inc.

140 Fourth Avenue. Waltham, MA 02254

Tel: USA (617)890-4750

UK (0734)580833

Japan 03(226)1671



See
M/A-COM's
Latest
Technology
at MTT-S #1005

Omni
Spectra

A **M/A-COM** COMPANY
INFO/CARD 31

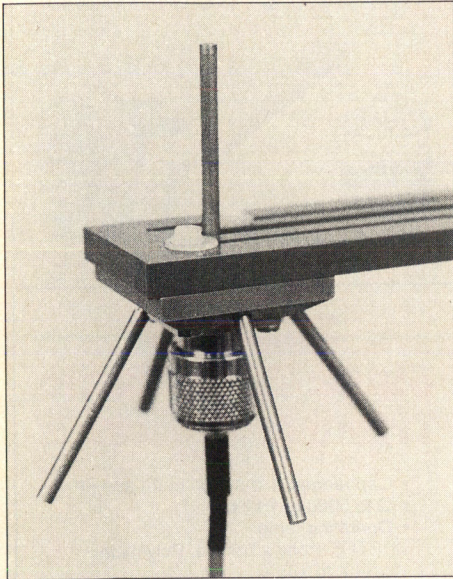


Figure 14. Photograph of the antenna.

is around 12 dB whereas for the SL623B it is 24 dB. The former provides a logarithmic characteristic over a 10 dB range and the later over 20 dB. As the integrated circuits provide a current whose level is proportional to the logarithm of input signal (with maximum level equal to 2.1 mA), the common base transistor and the operational amplifier

act as a current-voltage transformer with appropriate gain and DC offset.

The input signal must range between $0.2 \text{ mV}_{\text{RMS}}$ and 1 V_{RMS} for an accurate behavior of the logarithmic amplifier, but it could withstand input voltages up to $1.8 \text{ V}_{\text{RMS}}$ without damage. Within the input range, the dynamic error of the logarithmic characteristic is lower than 0.5 dB and the DC output signal ranges between 0 to 5 Volts.

Receiver Performance - Once the receiver was built, we obtained a complete set of measured characteristics, whose most relevant aspects are described below:

- Sensitivity: -97 dBm
- Maximum input level: 0 dBm
- IF Bandwidth: 10 MHz
- Logarithmic amplifier output: $0\text{-}5 \text{ Volts}$
- CAG: 18 dB manually controlled
- SWR: 1.9 at 1.65 GHz , <2.2 between $1.6\text{-}1.7 \text{ GHz}$

Antennas

In order to complete the channel sounder, two monopole antennas with ground planes were constructed. We used a $1/4$ monopole with four bars inclined 45 degrees to simulate the ground plane. The measured SWR at the antenna port is lower than 1.2 in the

$1.6\text{-}1.7 \text{ GHz}$ working band. A photograph of the antenna is shown in Figure 14.

Preliminary Measurements and Conclusion

Using the above described channel sounder, some preliminary measurements of the propagation conditions inside buildings were done. We recorded the received signal during 20 minute periods and using 20 samples/sec. In Figure 15 a typical example of the recorded measurements of the received signal amplitude in two standard cases is shown. The first case is line of sight between the transmitter and receiver and the second when obstructed. In both cases we can see large fluctuations (fading) in the received signal voltage. As was explained in the introduction, these fluctuations are due to the changing phasor sum of the signal components arriving at the receiver antenna via different paths. Presently a complete set of measurements is in process in order to characterize the transition channel in different buildings constructed using different materials.

In conclusion, a simple narrow-band channel sounder, appropriate for characterizing narrow band indoor communications channels, has been described.

-150 dBc Phase Noise...

Acknowledgements

This work has been supported by CICYT (Spain) under Grant TIC880543.

RF

References

1. R. Bultitude, "Measurement, Characterization and Modeling of Indoor 800/900 MHz Radio Channels for Digital Communications," *IEEE Communications Magazine*, Vol.25, pp.5-12, June 1987.
2. T. Rappaport, "Indoor Radio Communications for Factories of the Future", *IEEE Communications Magazine*, Vol.27, pp.15-24, May 1989.
3. K.C. Gupta and alt., *Microstrip Lines*

and Slotline, Artech House, New-York, 1970.

4. A. Zverev, *Handbook of Filter Synthesis*, John Wiley and Sons Inc. New York, 1970.

5. Hewlett-Packard, "An Attenuator Design Using PIN Diodes," Application Note 912.

6. J. Kestler, "Matching Circuits for Schottky Ring Mixers," *VHF Communications*, Vol.1, pp. 13-18, 1976.

7. M. Birch, "Logarithmic Receivers," *Advanced Signal Processing* (edited by D.J. Creasey), IEE Telecommunications Series. Peter Peregrinus Ltd. London 1985.

About the Authors

Fernando Casadevall received his Engineer of Telecommunications and PhD degrees from the Catalunya Polytechnic University in Spain. He has been an Associate Professor there since 1983. Xavier Barba received his Engineer of Telecommunications degree from Catalunya Polytechnic University in 1990. He is currently doing research on mobile communications. They may be reached at Dpto. Teoria del Senyal i Comunicacions, Universitat Politècnica de Catalunya, Apdo. 30.002, 08080-Barcelona, Spain. Tel: 34-3-4016781. Fax: 34-3-4016901.

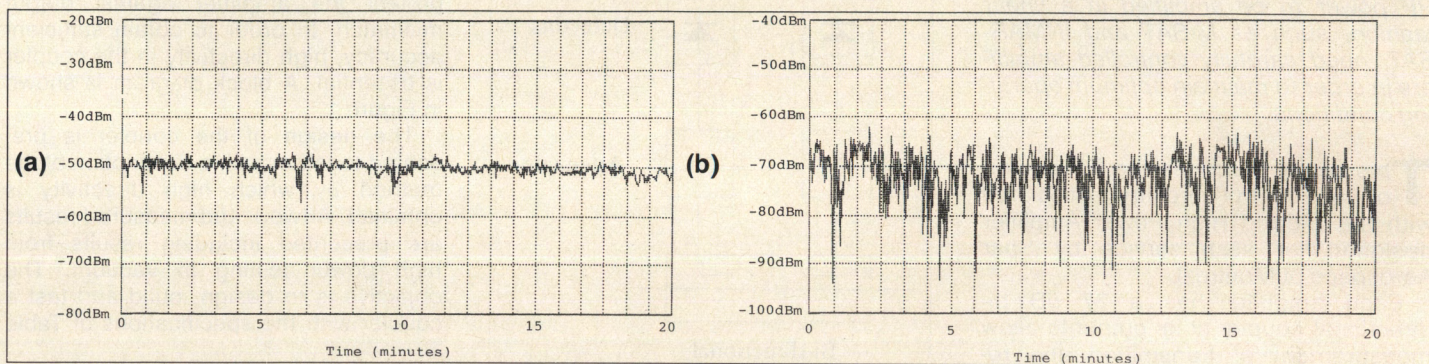


Figure 15. Signal level at the antenna port versus the time, (a) line of sight, (b) obstructed.

Your Design Deserves It.

You work hard to design a quiet synthesizer. Shouldn't you have a PLL to match?

With QUALCOMM's new Q3036 single-chip PLL, you can have a PLL noise floor of <-150dBc at 100 Hz.

You can input VCO frequencies from DC to 1.6 GHz using the built-in prescaler while selecting division ratios as wide as 2 to 1295.

Choose reference input frequencies from DC to 100 MHz with division ratios of 1-16.

The quiet Q3036 PLL, named a Top New Product of 1990 by the editors of *Microwaves & RF* magazine.

Now it's your turn to give what you and your synthesizer deserve. Peace and Quiet.

To learn more, please call or FAX:

QUALCOMM
"the elegant solution"

VLSI Products Division
10555 Sorrento Valley Road San Diego, CA 92121 USA
TEL: 619-597-5005 • FAX: 619-452-9096

Satellites requiring their transmitted RF power to be amplified in a linear fashion, such as M-SAT and INMAR-SAT, need carefully controlled amplifiers in order to maintain optimum operating conditions.

Each amplifier has a 27 dB bi-directional coupler at its output to allow measurement of transmitted and reflected signal power levels. The resulting detector signals are used to limit output power, hence power consump-



The design of the coupler is presented together with a description of the method by which high directivity is obtained. Artwork and measured results are presented including results from high power testing in vacuum. The objective is to design, build and test a coupler with the specifications of Table 1.

In order to be compatible with the rest of the circuitry making up the amplifier, the coupler must be fabricated using microstrip techniques on metallized alu-



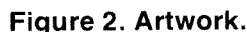


Table 1. Design specifications.

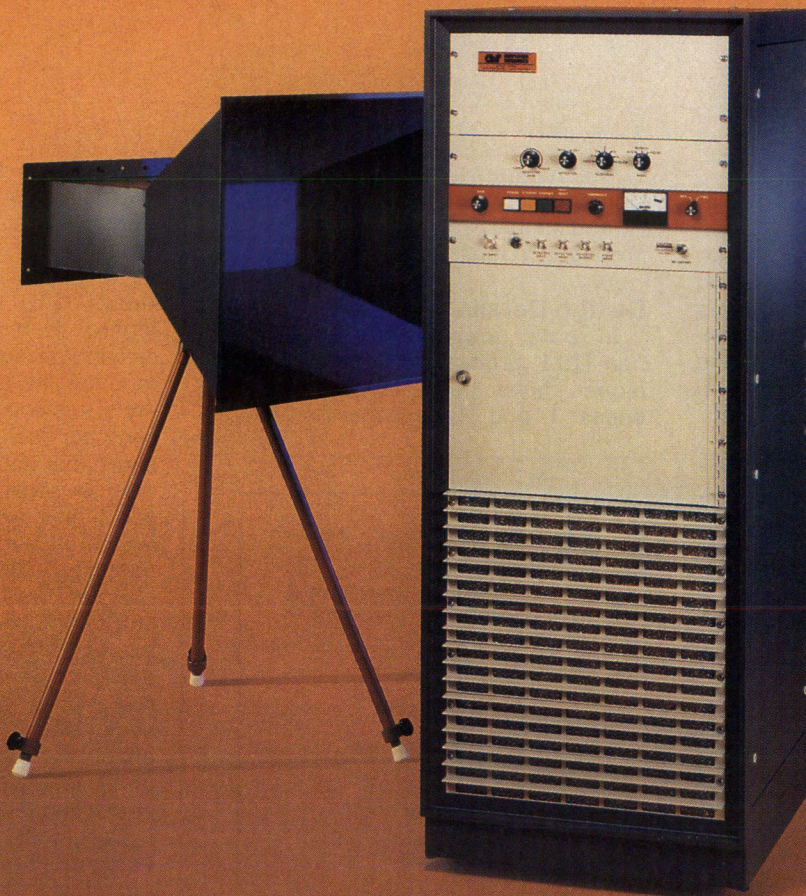

Testing for rf susceptibility to 200 volts/meter? You need the power to do it.

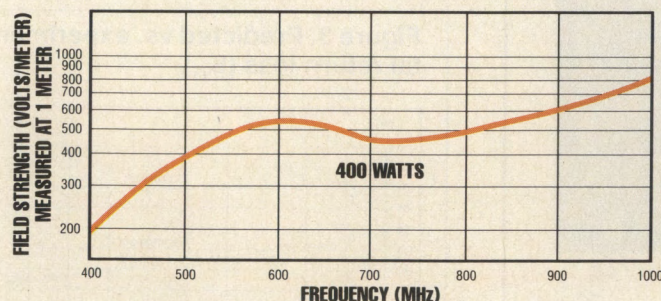If you're lining your shielded room with anechoic material to avoid multipath reflections, you already know you need an amplifier with infinite-VSWR tolerance. But you also



need an amplifier/antenna marriage made in heaven.

Here is one of our many matched systems specifically designed to assure you reliable field levels as high as 1,000 V/m.

Our new Model 400HB power amplifier delivers a *minimum* of 400 watts through a bandwidth of 400 to 1,000 MHz. And our Model AT4001 horn antenna dis-

plays the happy faculty of putting out more V/m as the frequencies rise.

Other matched systems of AR amplifiers and antennas cover the frequency spectrum from 10 kHz to 1 GHz with reliable power from one to 2,000 watts. Systems that give you the reserve power you're bound to need sooner than you may think. Systems that let you sweep clean through the band of interest without the headache and delay of changing antennas.

Why not chat—on our nickel—with one of our applications engineers about *your* rf susceptibility-testing situation? He'll answer the phone himself when you dial

1-800-933-8181

AR **AMPLIFIER
RESEARCH**

160 School House Road, Souderton, PA 18964-9990 USA
215-723-8181 • TWX 510-661-6094 • FAX 215-723-5688

mina substrate (0.050" thick, $\epsilon_r = 9.9$).

The problem of designing a high directivity coupler in this medium, (compared to an ideal TEM design), is due to the inhomogeneity of the dielectric structure. The isolation of the coupler is the most difficult characteristic to control, requiring wave cancellation and equal phase velocities for the even and odd modes of propagation.

The quarter-wave edge coupled design approach is chosen for its symmetry and simplicity, however the non-TEM propagation must be compensated.

Design Details

In order to solve the problem of non-TEM propagation, various techniques have been proposed. References 1 and 2 describe the Wiggly

coupled line but the available design information and mathematical relationships are not well suited for loose coupling. The electromagnetic field analysis is quite complex and none of the known CAD tools are helpful in this regard. References 3-5 describe the dielectric overlay coupler, but show poor repeatability due to the overlay boundary's position affecting matching, coupling and isolation. This solution is also somewhat cumbersome to produce and may be sensitive to high temperatures and high power levels. A configuration that is simple, repeatable and requires no tuning would be preferable.

References 6-10 present the design of an edge coupler with lumped capacitors at each end to compensate for the unequal phase velocities of even and odd modes at the isolated port. In the even mode, the capacitors have no effect, but they increase the odd mode phase length (transit time, ϵ_{reff} odd), thus equalizing the waves.

Due to the small value of the capacitance required, it can be realized as an interdigital structure (ICAP) formed on the same microstrip substrate as the coupler. From a mathematical approach, a capacitor at each end of the coupled

NEW MULTIPOINT SWITCH

NEW PRODUCT



MULTIPOINT N303 SERIES SMA SWITCHES

- Excellent insertion loss repeatability
- Epoxy sealed cases
- Low power actuator
- DC - 18 GHz operation
- Convenient packaging
- Competitive pricing
- 12 & 28 volt actuator; 6,5,4 & 3 ports are options



ARROWSMITH

SHELBURNE, INC.

A KDT COMPANY

2085 SHELBURNE ROAD, SHELBURNE, VERMONT 05482
TEL 802-985-8621 FAX 802-985-2070

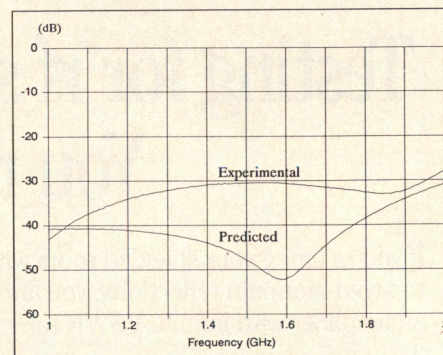


Figure 3. Predicted vs. experimental return loss (S_{11}).


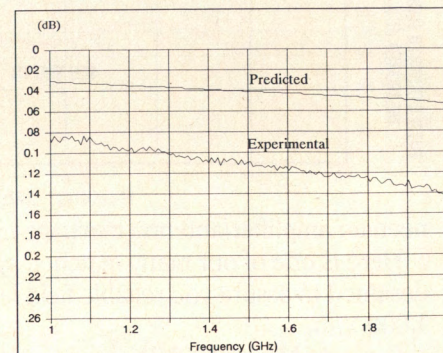


Figure 4. Predicted vs. experimental insertion loss (S_{21}).

Because you're
thinking fast...

Our new high-performance quads compress space and cost.

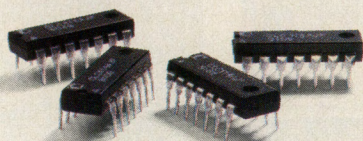Multi-channel designs have you in a corner? Want to cut cost and space? Then take a look at Comlinear's four new high-speed quad amplifiers.




Fast op amps for multi-channels.

For high-speed designs such as multi-stage active filters and video, consider these quads. The 90MHz CLC414 offers high speed and low power with a $1000\text{V}/\mu\text{s}$ slew rate at just 2mA per channel. And our 160MHz CLC415 combines excellent video specs with a fast $1500\text{V}/\mu\text{s}$ slew rate at only 5mA per channel. INFO/CARD 37

Buffers for video and more.

For multi-channel buffering, the 200MHz CLC114 features a $450\text{V}/\mu\text{s}$ slew rate at 3mA per channel. It's ideal for driving high density crosspoint switches. And our 350MHz (5V_{pp}) CLC115 delivers a $2700\text{V}/\mu\text{s}$ slew rate for large-signal designs. Plus 0.03%/0.03° diff. gain/phase with the ability to drive up to six video loads per channel.

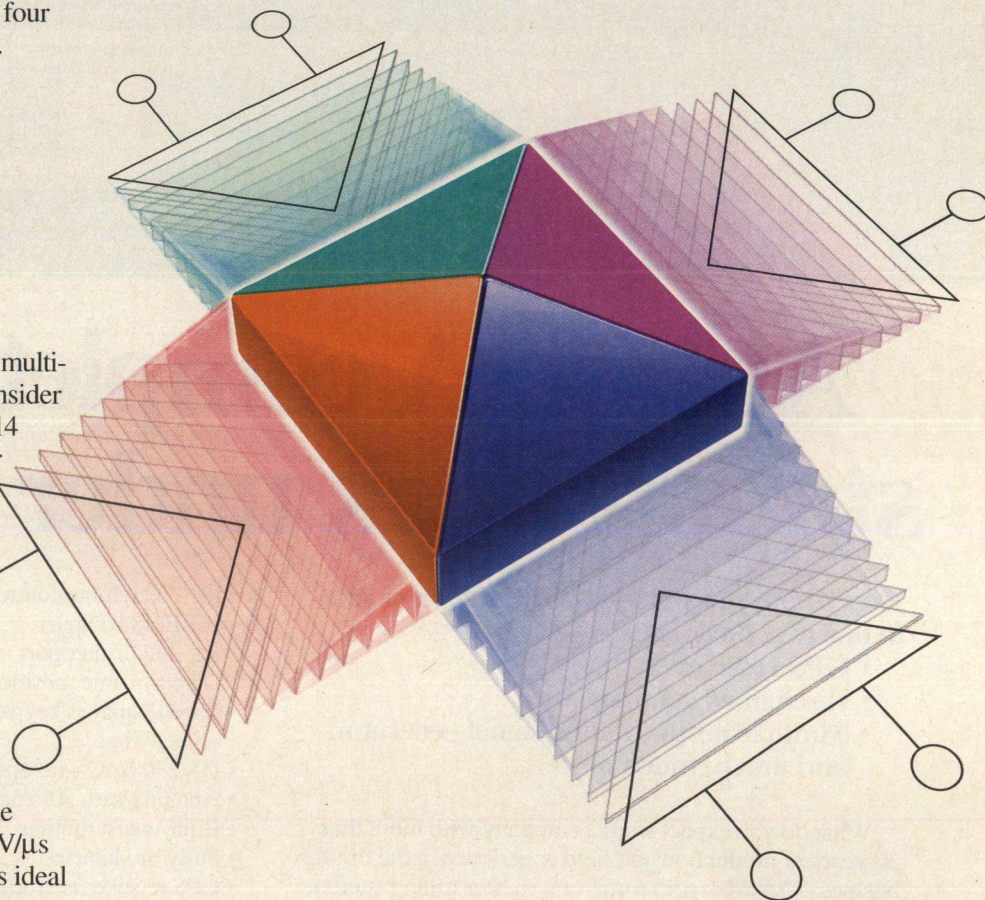
Call today for details. And start cutting down on space and cost. INFO/CARD 38



Comlinear
Corporation

Solutions with speed

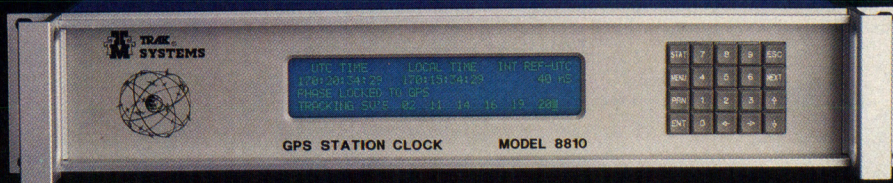4800 Wheaton Drive
Fort Collins, CO 80525
(303) 226-0500
1-800-776-0500 (USA)



At last: A complete GPS station clock under \$10,000

Everything you want in a GPS station clock, in one neat box:

- GPS receiver
- Disciplined standard
- Multiple output timing signal generator, and much, much more.

What do you expect from a company with more than 30 years of production and field experience in the timing business? You'd expect a one-unit master timing station, capable of tracking six satellites simultaneously — even while moving at 1,000 miles per hour — all inside a 3½ inch rack-mount chassis.

That's the **Model 8810** — a mature product, value-engineered and time-tested, just like the ones we've been providing to NASA and DoD for decades. And there's so much built into this unit, it's hard to describe. Just review the features listed below:

- Automatically determines geographical coordinates — no need to enter position anywhere on earth
- Automatic multi-satellite acquisition
- Time accuracy maintained with platform velocities to over 1,000 mph
- Outputs position data whether stationary or moving
- Multiple time code and rate output options
- User friendly, menu-prompted setup
- 20-key keypad and 4-line, 40 character display allows complete operation, checkout, and status acquisition without ancillary equipment
- Nonvolatile memory stores setup and data indefinitely
- Accurate to within 100 ns worldwide, 24 hours a day

- RS-232 remote control and time output (optional IEEE-488 output)
- RS-232 printer port
- Displays time, position, and REF-UTC/GPS
- Time display is keypad-selectable to UTC, GPS, or local time
- 115/230 VAC with optional 24 VDC backup
- Antenna with 50' coax cable included
- Built-in test routines
- Fully modularized
- GPS receiver is drop-in replaceable
- Workmanship standards to MIL-STD-454
- Three-year limited warranty
- Plus, a host of desirable options

That's the **Model 8810**, from TRAK Systems. And at this price, there's nothing else like it on the market. So why pay more, and install boxes of equipment, when you can have it all in one neat unit?

For free literature, or more information, contact us at:

TRAK SYSTEMS DIVISION
4726 Eisenhower Blvd.
Tampa, Florida 33634-6391
Phone: (813) 884-1411, extension 248
TLX: 52-827
FAX: (813) 886-2794



TRAK SYSTEMS
DIVISION OF **TRAK MICROWAVE CORP.**

line is used, (they must be separated by a quarter-wave length in order not to generate scattered waves to all ports). As mentioned in Reference 11, the capacitor at either end is satisfactory, but in order to have a good return loss, the capacitor should be located in the middle of the coupler to preserve the double symmetry of the circuit. The possibility of using just one capacitor located in the middle of the coupler was then investigated.

With this configuration, some characteristics tend to conflict and it is theoretically impossible to obtain both coupling flatness and optimum isolation. The selection of the capacitor requires evaluating the major performance parameters in terms of the intended service. In our case, the slope in frequency response of the coupled port can be conveniently equalized with a capacitor in the middle of the double-pi attenuator. Note that if the ICAP varies, the slope does not change, only the level changes. The design therefore is made for maximum isolation and the capacitor value is calculated to be 0.11 pF. The model of the ICAP was derived from Reference 12. It is important to note that the ICAP has a significant shunt component that can affect the even mode. In order to reduce this undesired shunt capacitance, the ground plane below the ICAP is removed. Figure 2 details the artwork and layout of the coupler, attenuators and detectors. Note the ICAP and compensating capacitors (C1) in the attenuators (AT1 and AT2).

The coupling value was chosen for the best tradeoff between low insertion loss (loose coupling) and high directivity (tight coupling because of fixed isolation). Optimum power levels and slope for the Schottky diode detectors (D2) is then adjusted with the appropriate attenuator. The computed prediction and experimental results are shown in Figures 3-6.

Results

Due to the double symmetry of the coupler (verified experimentally), only four parameters are shown: the return loss (S_{11}) in Figure 3, the insertion loss (S_{21}) in Figure 4, the coupling (S_{31}) in Figure 5 and the isolation (S_{41}) in Figure 6. Comparing these experimental results and computer predictions, we can see some small explainable differences.

In Figure 3, we see that the predicted return loss is better than the one obtained experimentally. This is attributed to the connector-to-microstrip dis-

continuities.


In Figure 4, we see that the experimental insertion loss is more than expected. This is due to the coax-microstrip transition which was not included in the simulation.

In Figure 5, we see a small difference in the slope and level of the coupling. The slope difference is due to the presence of the capacitor between the

two coupled lines in the coupled region resulting in an incomplete confining of the fringing field through the dielectric. The level difference is due to the ICAP stray capacitance to ground.

In Figure 6, we see that the isolation is as expected, the small difference being due to a 0.1 pF over-etching of the ICAP. This could be fixed with a dielectric slab to increase the serial ICAP

DC-3GHz

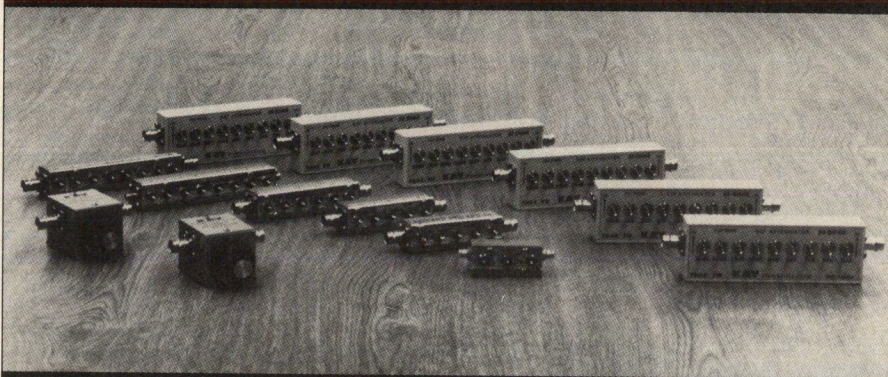

Kay Dependable Attenuators

Kay Elemetrics Corp. offers a complete line of **Programmable, In-Line and Continuously Variable Attenuators**. We can supply you with the right model to fit your application. We have both 50Ω and 75Ω models from DC-3GHz.

Model No.	Impedance	Freq. Range	Atten. Range	Steps
839	50Ω	DC-3GHz	0-101dB	1dB
1/839	50Ω	DC-1GHz	0-22.1dB	1dB
847	75Ω	DC-1GHz	0-102.5dB	1dB
870	75Ω	DC-1GHz	0-132dB	1dB
4440	50Ω	DC-1.5GHz	0-130dB	10dB
4450	50Ω	DC-1.5GHz	0-127dB	1dB
1/4450	50Ω	DC-1GHz	0-16.5dB	.1dB
4467	75Ω	DC-1GHz	0-31dB	1dB
0/400	50Ω	DC-500MHz	1-13dB	—
0/410	75Ω	DC-400-MHz	2-14dB	—

For more information or to place an order call **Kay's Product Specialist at (201) 227-2000**.

KAY

Kay Elemetrics Corp.
12 Maple Avenue • Pine Brook, NJ 07058 USA
Tel. (201) 227-2000 • TWX: 710-734-4347
FAX: (201) 227-7760

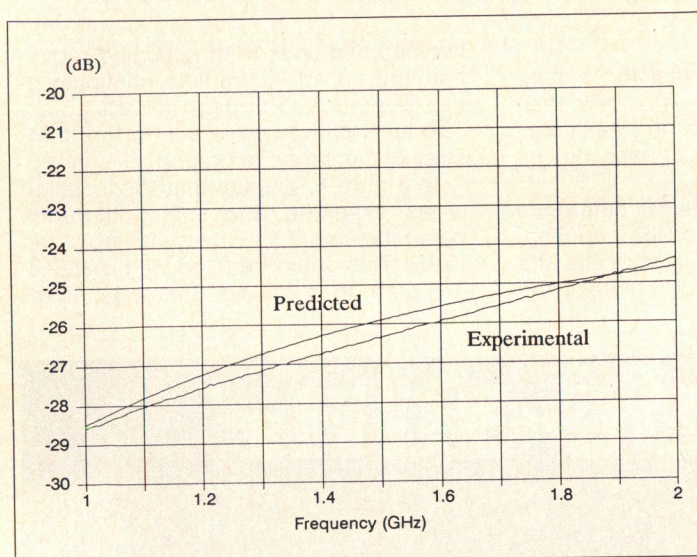


Figure 5. Predicted vs. experimental coupling (S_{31}).

value (note that all results are without tuning).

space as an RF/Microwave engineer.

Acknowledgement

This paper was written while the author was employed by Spar Aero-

References

1. A. Podell, "A High Directivity Microstrip Coupler Technique," *International Microwave Symposium*, IEEE MTT 1970, pp. 33-36.
2. F.C. de Ronde, "Wideband High Directivity

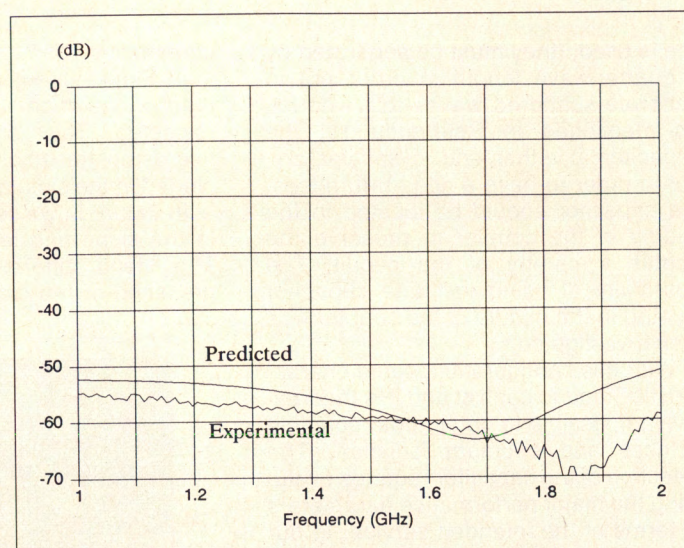


Figure 6. Predicted vs. experimental isolation (S_{41}).

in MIC Proximity Couplers by Planar Means," *International Microwave Symposium*, IEEE MTT 1980, pp. 480-482.

3. B. Sheleg and B.E. Spielman, "Broadband Directional Couplers Using Microstrip With Dielectric Overlays," *IEEE MTT* 1974, pp. 1216-1220.
4. D.D. Paolino, "MIC Overlay Coupler Design Using Spectral Domain Techniques," *IEEE MTT* 1978, pp. 646-649.
5. B. Majkic and C.E. Smith, "Analysis of Two-Conductor Microstrip Transmission Lines With Dielectric Overlay," *IEEE Southeastcon '82 Conference Proceedings*, April 1982, Paper 4.2, pp. 84-87.
6. G. Schaller, "Directivity Improvement of Microstrip $\phi/4$ Directional Couplers," *AEU* 26, 1972, pp. 508-509.
7. G. Schaller, "Optimization of Microstrip Directional Couplers With Lumped Capacitors," *AEU* 31, 1977, pp. 301-307.
8. H.J. Herzog, "Microstrip Couplers With Improved Directivity," *Electronic Letters*, Vol. 14, Feb. 1978, pp. 50-51.
9. D. Kajfez, "Raise Coupler Directivity With Lumped Compensation," *Microwaves*, Vol. 17, March 1978, pp. 64-70.
10. S.L. March, "Phase Velocity Compensation in Parallel-Coupled Microstrip," *IEEE MTT Symposium Digest*, 1982, pp. 107.1-107.3.
11. L.F. Franti and G.M. Paganuzzi, "Wideband High Directivity Microstrip Couplers for Microwave Integrated Circuits," *European Microwave Conference*, 1980, pp. 377-381.
12. J.I. Smith, "The Even- and Odd-Mode Capacitance Parameters for Coupled Lines in Suspended Substrate," *IEEE MTT* 1971, pp. 32-38.

About the Author

Pascal Goux is currently an EMI/EMC engineer working as a consultant for Ancom Electromagnetics Ltd. He may be reached at 9665 Cote de Liesse, Dorval, Quebec, H9P 1A3. Tel: (514) 633-9679. Fax: (514) 633-9681.

- Crystals
- Crystal Oscillators
- Crystal Filters
- Ceramic Resonators

WHEN IT COMES TO OSCILLATORS, ONLY RALTRON HAS IT ALL.

RALTRON manufactures one of the industry's most complete lines of high quality oscillators. Call us for all your oscillator needs from clock to temperature compensated, oven or voltage controlled. Or call us for our 28 page catalogue.

WORLD'S SMALLEST OCKO - ROXO 210A

- Frequency Range: 1.0 MHz-20.0 MHz
- Temperature Stability: $\pm 2 \times 10^{-7}$ (-20°C to $+65^{\circ}\text{C}$)
- Long Term Stability: $\pm 2 \times 10^{-7}$ per year
- Phase Noise: 145 dbc (10 KHz offset)
- Power consumption (stabilized): 2.0 W
- Size: 35.3 x 27 x 25.4 mm (1.40" x 1.06" x 1.0")

MINIATURE TCXO - RTX0-065-X

- Frequency Range: 1.0 MHz-20.0 MHz
- Frequency Stability: ± 1.0 ppm (-40°C to $+85^{\circ}\text{C}$)
- Aging: ± 1.0 ppm per year
- Size: DIL 16 Pin (.980" x .520" x 0.4")
- MIL - 0-55310 if required

The Products. The Prices. The People. Only RALTRON has it all.

RALTRON ELECTRONICS CORP.





















2315 NW 107th Avenue, Miami, Florida 33172
FAX (305) 594-3973 TELEX 441588 RALSENU
(305) 593-6033

Meet our new division.

VISIT US AT
MTS BOOTH
1208

Frequency Dividers

NEC

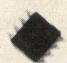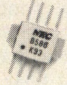$\div 2$  UPG502 UPB565 UPG504 UPB581 UPB558 UPB584	$\div 4$  UPG501 UPB565 UPG503 UPB582 UPB585	$\div 8$  UPG506 UPB565 UPB567	$\div 2/4/8 \div 8/9$  UPB555 UPB587	$\div 10/11$  UPB551 UPB552 UPB554
$\div 16/17$  UPB553 UPB556 UPB555 UPB571	$\div 20/21$  UPB572	$\div 20/22$  UPB551 UPB552 UPB554	$\div 32/33$  UPB555 UPB569 UPB571	$\div 40/41$  UPB572
$\div 40/44$  UPB551 UPB552 UPB554	$\div 64$  UPB564 UPB565	$\div 64/65$  UPB566 UPB569 UPB571	$\div 64/68$  UPB562 UPB568	$\div 80/81$  UPB572
$\div 128 \div 128/129$  UPB564 UPB566	$\div 128/64$  UPB588	$\div 128/136$  UPB562 UPB568	$\div 256$  UPB564	$\div 256/512$  UPB586

Our low cost prescalers help you divide and conquer just about any design problem you face, including delivery.

Need wide band-width? Low power dissipation? Performance to 14 GHz?

Start here and save money.

We have both Silicon and GaAs ICs—in chips and a variety of packages from auto-insertable to

MIL screened.

And the price is right.

So if frequency division has been multiplying your design costs, give us a call. We'll send you a *Product Summary and Selection Guide*, and arrange for samples and applications assistance.

NEC quality and CEL support. It's a combination that'll *work* for you.

NEC®

California Eastern Laboratories

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 Santa Clara, CA (408) 988-7846 □ Los Angeles, CA (213) 645-0985
 Bellevue, WA (206) 455-1101 □ Scottsdale, AZ (602) 945-1381 □ Richardson, TX (214) 437-5487 □ Shawnee, KS (913) 962-2161 □ Woodridge, IL (708) 241-3040 □ Cockeysville, MD (301) 667-1310
 Peabody, MA (508) 535-2885 □ Hackensack, NJ (201) 487-1155 or 487-1160 □ Palm Bay, FL (407) 727-8045 □ Nepean, Ontario, Canada (613) 726-0626

20 MHz General Purpose/Arbitrary Function Generator

John Fluke Mfg. Co. introduces the PM 5139 from Philips Test and Measurement, a 0.1 MHz to 20 MHz function generator combining ten general purpose test waveforms with arbitrary function capability. Sonar, mechanical testing, brain and heart waves, and baseband video or RF signals are just a few examples of arbitrary waveform applications. Using WaveCAD, a waveform generator and editing software package available from Fluke, the PM 5139's memory can be loaded with up to six arbitrary waveforms. Also, a real signal can be captured with a Philips digital storage oscilloscope, edited in software, and downloaded to the PM 5139.


Standard waveforms include sine, triangular and square waves, positive and negative rectangular pulses, positive and negative sawtooth waves, haversine, half-period sine, and triangular pulses. Modulation modes avail-

able are: AM, FM, gating, bursts, PSK, and linear or logarithmic sweeps. Frequency accuracy is within ± 2 ppm over the entire range, with low jitter and phase noise, and very flat amplitude response. In the low frequency range, five of the standard waveforms can be varied in duty cycle from 1 to 99 percent with 0.1 percent accuracy. All manual settings can be performed remotely using an IEEE-488 bus interface.

The panel has a single rotary knob for numerical setting of parameters, with a logical array of parameter selection and control keys. Each key activates the rotary knob for dialing in the desired setting. A large central backlit LCD display shows all instrument settings at a glance.

The price of the PM 5139 is \$4190, or \$4690 with the IEEE-488/GPIB interface.

John Fluke Mfg. Co., Inc.
INFO/CARD #230

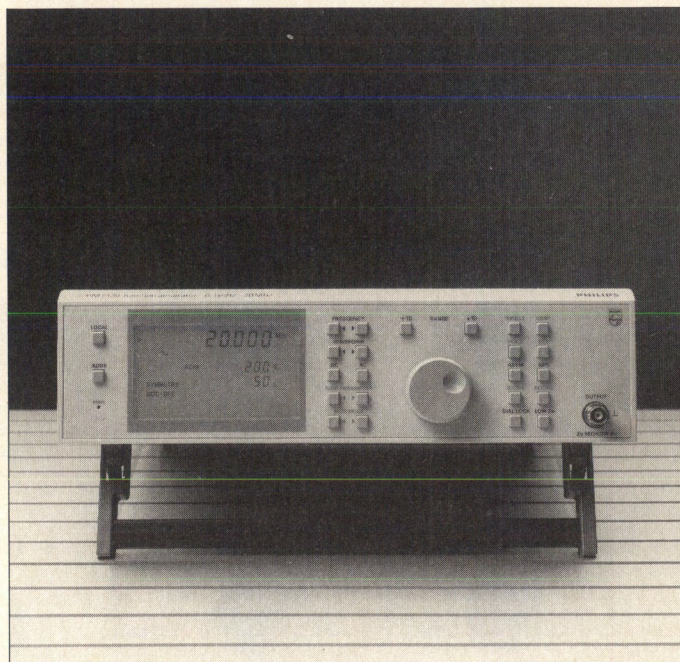

Six-Octave Bandpass Filter

Optoelectronics announces a new receiver bandpass filter that separates closely spaced radio signals. The Model APS-204 has a constant 4 MHz bandwidth, tunable over a 20 MHz to 1000 MHz frequency range.

The unit is an active circuit with no loss and very small size ($4 \times 1 \frac{1}{2} \times 7$ inches). At the heart of the circuit is a 4 MHz bandwidth, 4-pole resonant cavity filter with a Q of 325. A unique double-heterodyne technique currently being patented routes the signal to the filter and back to the operating frequency.


Noise figure is specified at 10 dB, and the third-order intercept is 15 dBm, typical. Power requirements are 12 VDC with 6 watts consumption. Price of the APS-204 is \$995.

Optoelectronics Inc.
INFO/CARD #229



RF Modem for Wireless Networking

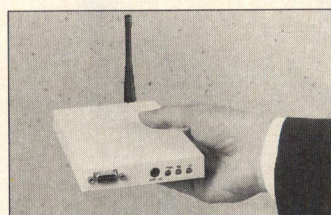The RF Modem, using uncoded spread spectrum tech-



niques defined by FCC Part 15, has been introduced by Proxim. Applications include hospital bedside monitors, point-of-sale devices, portable data recorders, traffic management, and security systems.

Usable for distances up to 500 feet, the RF Modem interfaces to a computer using a standard RS-232 or RS-485 port. Packages and unpackaged versions are available.

Two unpackaged versions are available for designing into OEM products. One operates at 121 kbps, while the other operates at 242 kbps.

Proxim, Inc.
INFO/CARD #228

Farnell Instruments Now Available in U.S.

Wayne Kerr announces the introduction of the Farnell line of RF test instruments to the U.S. and Canadian markets. Farnell equipment has previously been marketed in the U.K. and the rest of Europe.

The product line includes the following signal generator products: The PSG1000 Synthesized Signal Generator (pictured below) covering 10 kHz to 1 GHz, the ESG Signal Generator which also covers 10 kHz to 1 GHz, the 100 kHz to 2 GHz SSG2000 Signal Generator. Other current product models include the 352C Spectrum Analyzer, covering 300 kHz to 1 GHz, and the AMM2000 Modulation Meter with 250 kHz to 2.4 GHz coverage.

Wayne Kerr Inc.
INFO/CARD #227




Lightning Protector for Cellular Radios

Huber+Suhner has introduced a 1/4-wave shorted stub specifically designed for cellular radio base stations, with an operating frequency range of 797-1016 MHz. Features include lower residual pulse than other protection methods and no inter-modulation effects. The unit is offered with either type N or 7/16 connectors.


Mechanically, the lightning protector features zinc diecast construction, waterproof design for outdoor installation, and easy mounting with standard plumbing brackets or clamps.

Huber+Suhner AG
INFO/CARD #224

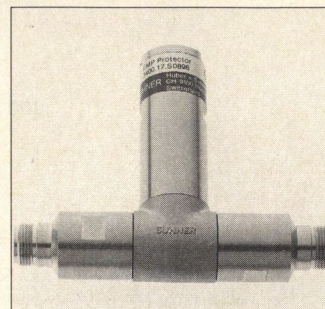

Common Problem:
SPECS CALL FOR CUSTOM DESIGN –
DEADLINES CALL FOR OFF-THE-SHELF

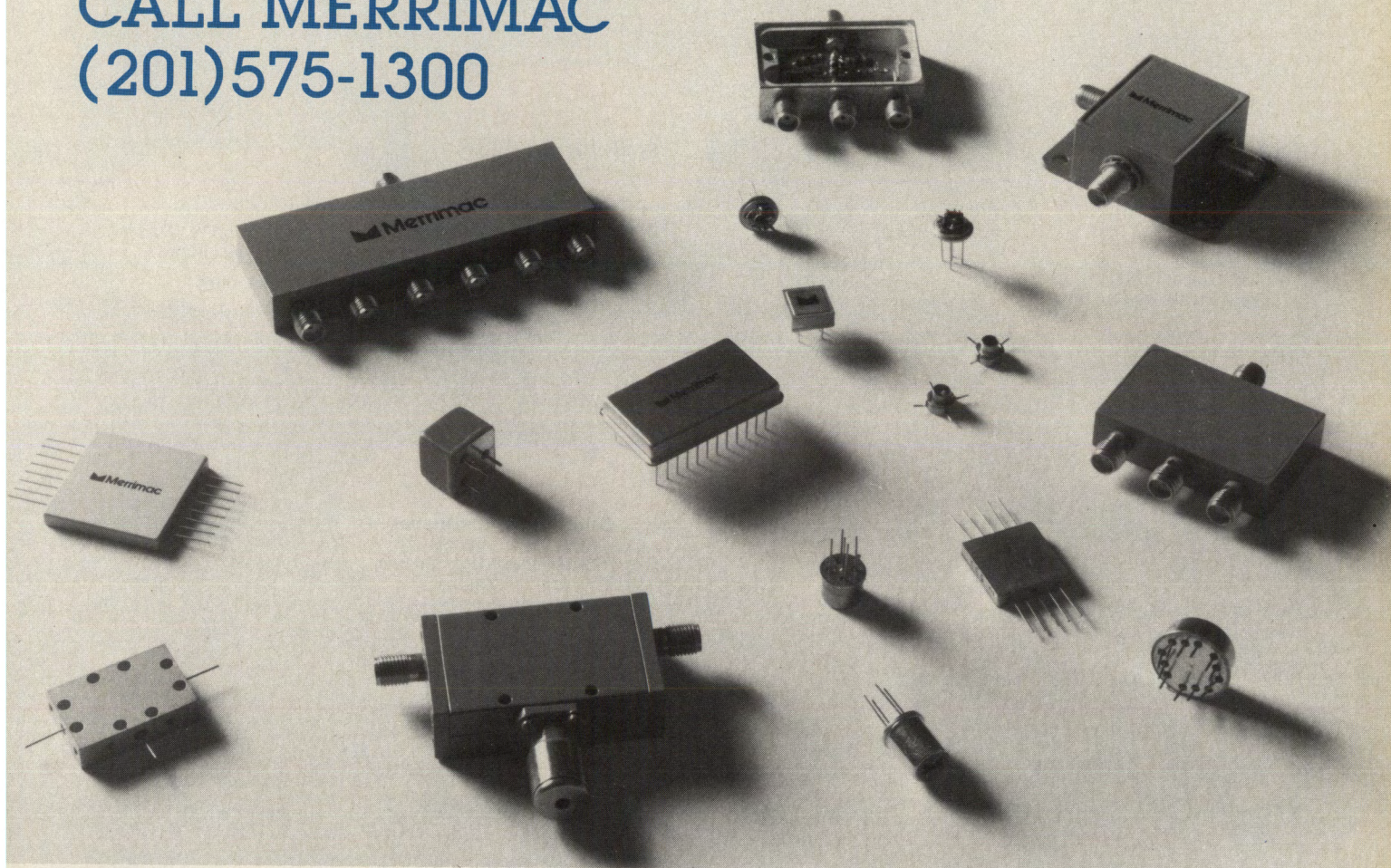Simple Solution:
CALL MERRIMAC
(201)575-1300



Our Stock is Anything but Common!

Double Balanced Mixers
Image Reject Mixers
Biphase Modulators
Frequency Doublers
Quadrature Modulators
Vector Modulators
Single Sideband Modulators
Phase Modulators
I & Q Phase Detectors
Frequency Discriminators
Phase Comparators

Analog Phase Shifters
Digital Phase Shifters
Precision Phase Resolvers
0° Power Dividers
2, 3, 4, 5, 6, 8 & 12 ways
90° Power Dividers
Quadrature Hybrids

180° Power Dividers
Hybrid Junctions
Quadrature Couplers
Filmbrid Couplers
Directional Couplers
Bidirectional Couplers
Complex Phasing Networks
Digital Attenuators
Analog Attenuators
Balanced Switches
Amplifiers & Isolators


 **Merrimac**

41 Fairfield Place, West Caldwell, NJ 07006
Tel: (201) 575-1300 / Fax: (201) 575-0531

Software

Eagleware
Formerly Circuit Busters

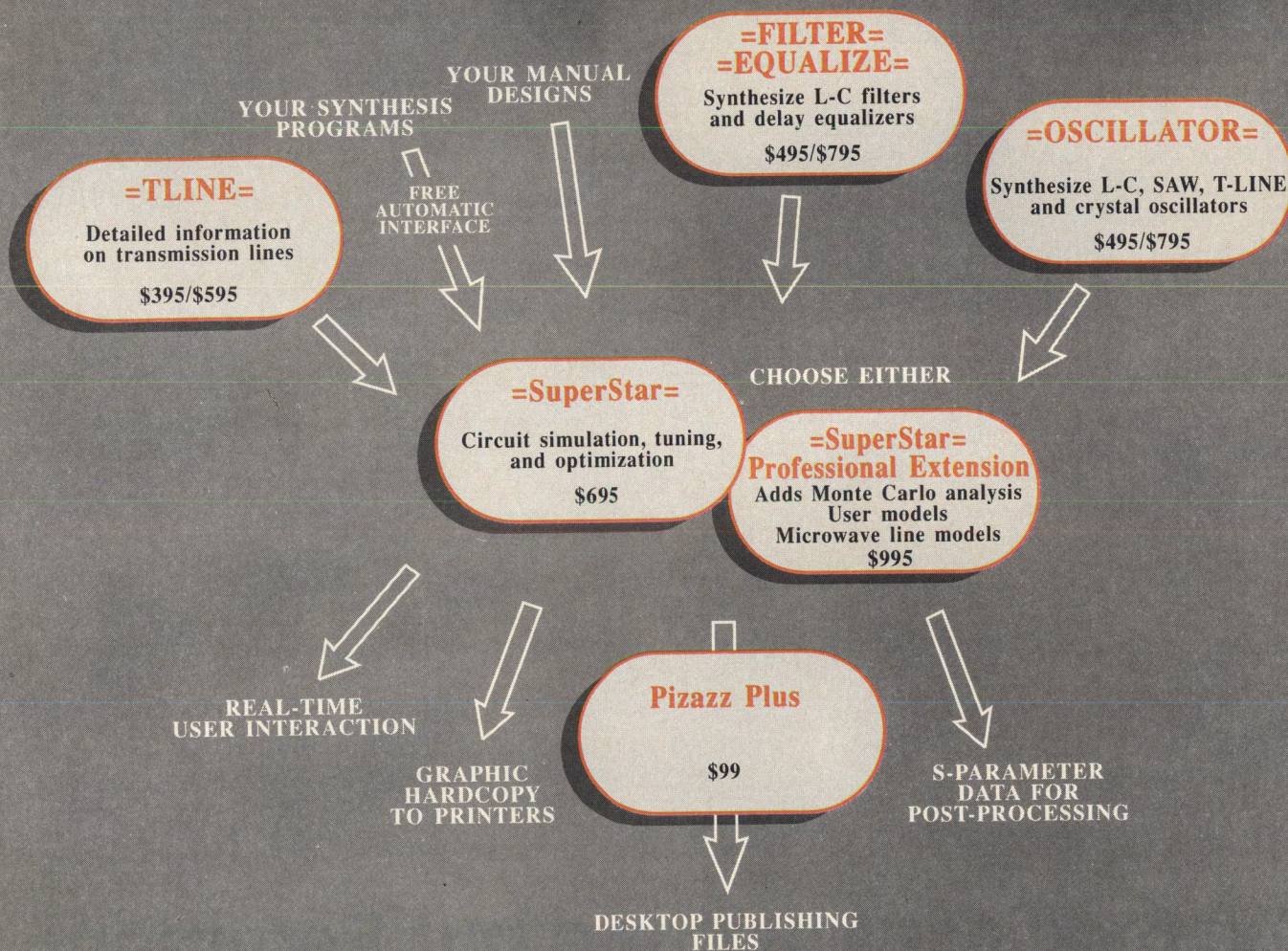Eagleware software integrates network synthesis for the initial design with the flexibility and power of high-speed simulation, tuning and optimization.



- One easy-to-learn environment
- Unmatched performance/price ratios
- Fast execution on standard IBM PCs/compatibles

- Quick and responsive support
- No annual maintenance fees
- 30 day satisfaction guarantee



Eagleware
Formerly Circuit Busters

For more information or for immediate shipment, telephone Eagleware.

1750 Mountain Glen
Stone Mountain, GA 30087 USA

Tel (404) 939-0156
FAX (404) 939-0157

Smaller SMT DIP Package

Signetics announces the first two integrated circuit products in their new SSOP small-footprint SMT package. The package is small enough to replace chip-and-wire assembly in some applications. The NE/SA575DK Comparator and the NE/SA605DK FM IF System are available in the $1.5 \times 4.5 \times 6.75$ mm SSOP. In 100s, these device are priced at \$2.04 and \$3.54, respectively.

Signetics Company
INFO/CARD #226

GPS Precise Positioning Module

Stanford Telecommunications has received National Security Agency endorsement of its STEL-9300 Precise Positioning Service - Security Module (PPS-SM), allowing authorized users to realize the most accurate capabilities of GPS. Anti-Spoof and Selective Availability techniques deny access to the Precise Positioning Service (PPS) to unauthorized users. With this capability, GPS equipment can provide access to PPS for authorized users without making the equipment classified.

Stanford Telecommunications
INFO/CARD #225

Standard Power Amplifier Line

Alpha Industries announces the new CMA Series of Standard Power Amplifiers for terrestrial and satellite microwave communications systems. Models cover 5.9-6.4 GHz with 60 dB linear gain (minimum) and power outputs ranging from 40 to 44 dBm (minimum), utilizing +12 or +15 volt power supplies.

Alpha Industries, Inc.
INFO/CARD #224

Power Measurement Upgrade

High speed CW power measurement capabilities have been added to the 8003 Precision Scalar Analyzer from Wavetek Microwave. These new measurement modes provide power readings at greater than 100 per second over GPIB. The upgrade provides a 10 to 100 times improvement in speed over thermocouple CW power meters. This speed is particularly attractive in automated measurement systems.

Wavetek Microwave, Inc.
INFO/CARD #223

1000 Watt Amplifier


Model BHE4819-1000 from Power Systems Technology offers 1000 watts CW power output in AB linear service over 400-1000 MHz. RF input is 0 dBm, in CW, AM, Pulse, FM, or phase modulation. Protective circuits prevent damage from excessive VSWR, and the unit offers graceful degradation in the event of transistor failure. Applications include EMI testing, EW and ECM, troposcatter, television broadcasting, and laboratory amplification.

Power Systems Technology Inc.

INFO/CARD #222

Video Brickwall Filters

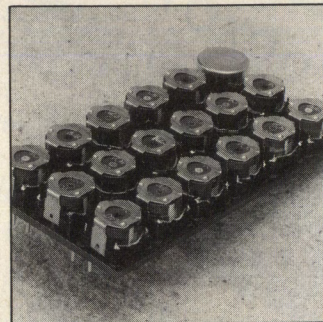Miniature filters for NTSC and PAL video systems are available from Allen Avionics, offering cut-



off frequencies from 2 to 8.4 MHz. P.C. board or packaged versions are available. The typical ABW-4P20-P has passband flatness of 0.15 dB to 4.2 MHz, less than ± 10 nsec delay distortion, and 1.066 stopband ratio. These filters reduce interference from high frequency subcarriers and other out-of-band signals.

Allen Avionics, Inc.
INFO/CARD #221

ECL Oscillators With Enable/Disable

MF Electronics announces the M1900 ECL oscillators for graphics and other high speed circuits requiring clocks of 10 to 225 MHz. A unique feature is a "tristate" enable/disable feature which effectively disconnect the output. System test, selectable clock frequencies, and noise reduction by shutoff of unused sources are all benefits of this feature.

MF Electronics Corp.
INFO/CARD #220

The Leader in Quality

We offer a full array of custom capabilities based on extensive library of existing designs and in-depth subsystem experience


Locus Converter and Modulator/Demodulator Subsystems

Unique solutions for unique requirements

- Ultra-High Dynamic Range IF to Baseband Converters and Tuners
- Single and Independent-Sideband Modulators
- FSK Modulators
- Coherent and Non-Coherent Demodulators
- Modulation Recognizers
- I-Q Detectors

We're problem solvers. CALL for information or with your questions.
(814) 466-6275

See the Locus Difference

 **LOCUS, Inc.**

KAMAN

P.O. Box 740
State College, PA
16804

814-466-6275

FAX 814-466-3341

INFO/CARD 47

Are You Designing for the Following Applications?

- GPS
- Wireless LAN
- Spread Spectrum
- Wireless Key
- Wireless ID
- Wireless P.O.S.

Penstock has the largest inventory of RF/Microwave Semiconductors & Components. Application Assistance is just a phone call away

- Datasheets/Technical Assistance
- Overnight Delivery/No minimums
- FREE Product Selection Guide

CALL
1-800 PENSTOCK

Multipath and Fading Simulator

The new HP 11757B multipath-fading simulator/signature test set features an internal printer, firmware and error counters to produce permanent records of M-curves. These signatures are used in installation and maintenance of digital radio systems. The HP 11757B is \$19,000,

and an upgrade to the earlier HP 11757A is \$4000.
Hewlett-Packard Co.
INFO/CARD #219

MIL-STD-2000 Capability

Bliley Electric announces that it is qualified and certified to design and manufacture soldered electrical and electronic assem-

blies to meet all requirements of MIL-STD-2000. This capability is used in custom-designed crystal oscillators, and is also available for contract assembly.

Bliley Electric Co.
INFO/CARD #218

Feedthrough Terminations

Coaxial feedthrough termina-

tions designed to terminate inputs to oscilloscopes, frequency counters, RF voltmeters, etc., have been introduced by Elcom Systems. They are available in 50, 75 and 93 ohms, with BNC, TNC, type N or SMA connectors. Prices start at \$17.50 in small quantities.

Elcom Systems, Inc.
INFO/CARD #217

KVG products-

to solve your frequency control problems with crystals:

Crystal Oscillators

VCXO

VCXO from 0,1 Hz to 140 MHz

KVG-crystal oscillators are especially qualified by: large pullability from ± 50 ppm to ± 200 ppm depending on frequency and pulling voltage. Standard temperature range 0/ + 70 dc; - 20/ + 70 dc



OCXO - TCXO - XO

OCXO from 5 MHz to 20 MHz
 TCXO from 0,1 Hz to 40 MHz
 XO from 0,1 Hz to 140 MHz

KVG-crystal oscillators are especially qualified by: high temperature stability, for ex. $\pm 1 \times 10^{-9}/^{\circ}\text{C}$ - 25/ + 70 dc (OCXO)
 $\pm 1 \times 10^{-6}$ - 40/ + 80 cs (TCXO)
 high reliability and smallest dimensions





Kristall-Verarbeitung Neckarbischofsheim GmbH
 P.O. Box 61 · D-6924 Neckarbischofsheim
 Federal Republic of Germany
 Phone 72 63/648-0 · Telex 782335 kvgn d
 FAX 72 63/61 96 · Teletex 726312

KVG NORTH AMERICA INC. - 7300 West Camino Real
 Suite 109 • USA • Boca Raton, FL 33433 • Phone (407) 393-7548 • FAX (407) 393-7439

Hybrid Amplifiers

Two new 10 MHz - 1.2 GHz high linearity amplifiers have been introduced by Motorola RF Devices. Models CA5900 and CA5915 are designed for operation in 50 ohm linear systems, offering 28 or 15 volt supply, 15 dB gain, and 1 watt power output at 1 dB compression. Packaging is in the CATV style case 714P-01, and they are also available with a low profile heat sink package. Pricing is \$91.30 (U.S. delivery, 100s).

Motorola RF Devices
INFO/CARD #216


3-Way Divider

New three-way power dividers/combiners are available from RLC Electronics. Featuring 5 watt dissipation and either pin or SMA connector configurations, standard units are offered in octave or narrow band ranges from 500 MHz to 12 GHz. Amplitude balance is ± 0.5 dB, phase balance is ± 3 degrees, and isolation is 18 dB minimum. Prices start at \$225.

RLC Electronics, Inc.
INFO/CARD #215

EMI Measuring System

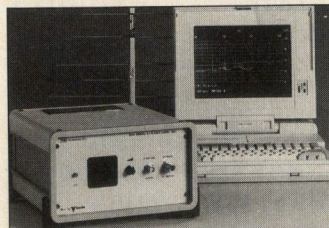The Vianello PMM-8030 from IBEX Group is a complete emission measurement and monitoring system in the 30 to 1000 MHz band, meeting CISPR, VDE, FCC and EN specifications. External PC control offers ease of use and



flexibility. A complete package is available, including receiver, antennas, computer and software.
IBEX Group Inc.
INFO/CARD #214

SMT RF Chokes

Vanguard Electronics is offering surface-mount RF chokes designed and built to MIL-C-15305 or MIL-T-27. The chokes are fully encapsulated; suitable for various soldering techniques. Products are available for the 1 to 500 MHz frequency range with impedances up to 10 kohms. 1000-

piece pricing ranges from \$3.50 to \$4.50 each.

Vanguard Electronics Co.
INFO/CARD #213

EMC/TEMPEST Antennas

Two new models from Antenna Research Associates are designed for shield room testing requirements of MIL-STD 285 and NSA 65-6. Each antenna is a 12-inch tuned loop operating from 1 kHz to 30 MHz. The PLA-130/A is a two-band transmit/receive antenna capable of handling 1 kW input power, and the Model ALA-130/A is a receive antenna containing a low noise preamplifier. Each is individually calibrated.

Antenna Research Assoc., Inc.
INFO/CARD #212

New SMT Filters

Trilithic has introduced two new surface mount filter packages, which extend center frequencies to the 10-2000 MHz range and increase ultimate rejection to 70 dB. Designs available include Chebyshev, Butterworth, Linear Phase, Bessel, Gaussian and Elliptic with -3 dB bandwidths from 2 to 150 percent.

Trilithic, Inc.
INFO/CARD #211

Crystal Products

New products from KS Electronics include a 70.0 MHz VCXO with pullability of over ± 1500 ppm and +10 dBm output. Higher frequencies are also available. Also announced are 70.0 MHz crystal filters with 1.0 MHz bandwidth, with other frequencies available. The company has the capability of manufacturing crystal filters with third order intercept of +30 dBm.


KS Electronics
INFO/CARD #210

Matrix Switch


Watkins-Johnson introduces a series of Matrix Switch Distribution Systems offering high performance and reliability. Technology used varies with the frequency range, and may be reed relay, FET or PIN switching. Designs are available for audio (DC-20 kHz), video (DC-20 MHz), HF (1-30 MHz), VHF (20-500 MHz), V/UHF (20-1000 MHz) and IF (narrow bands 80-200 MHz). Control is via front panel, RS-232

RF SHIELD PROTOTYPE KIT!

No tooling costs with standard shields!

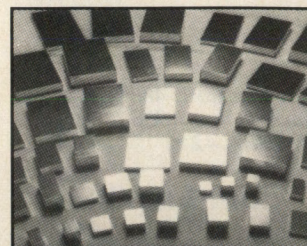

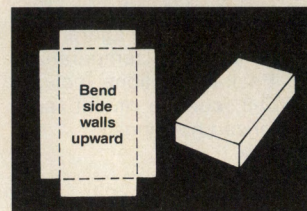27 prototype rf shields to choose from (range: .5" x .5" to 2.5" x 5.0"). Selectable side-wall heights (.25", .50", .75"). 54 potential combinations in all. All on two flat 12" x 17" sheets. Shields fold into boxes easily by hand. You get 90° corners every time. All shields are made from .016 brass. They're tin-plated for solderability.



Immediate Delivery!

For your production, you can order any *one* of the 54 sizes in our kit by-the-sheet in large or small quantities. We supply 12" x 18" sheets of .016 thick brass shields with tin plating.

Introductory price only \$145⁰⁰

Just call, fax or mail your purchase order to:




Fotofabrication Corp.
3758 Belmont • Chicago, IL 60618
Tel.: (312) 463-6211 • Fax: (312) 463-3387
Specify UPS or FEDX
Questions? Call Barry at (312) 463-6211

FOTOFABRICATION corp.

INFO/CARD 30

MOBILE RADIO LOW LOSS SAW FILTERS

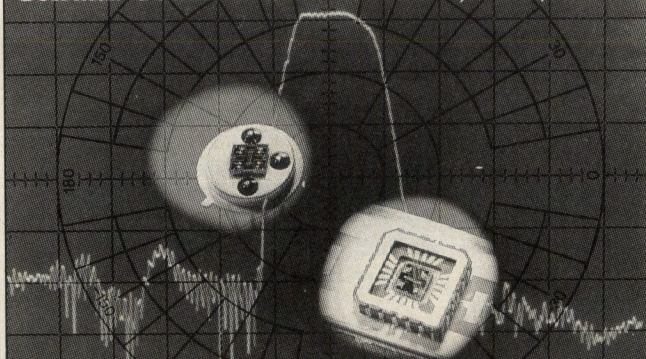Cellular Communications : GSM, PCN, LAN...



Commercial, Military or Space Quality Levels

Center Frequency :	40 to 1500 MHz
Fractional Bandwidth :	0.2 to 10 %
Insertion Loss :	< 10 dB

THOMSON-ICS CORPORATION in the U.S. & Canada
P.O. Box 1088 - Southwick MA 01077, Phone (413) 569 0575, Fax (413) 569 0529
THOMSON SINTRA ACTIVITES SOUS-MARINES elsewhere
DTAS Département des Techniques Acoustiques Spécialisées
BP 138 - 06561 Valbonne Cdx France. Phone (33) 92 96 31 79, Fax (33) 92 96 31 90

SAW BAW AO IO
Devices and Subsystems

THOMSON-CSF

INFO/CARD 51

interface, or IEEE-488 bus.
Watkins-Johnson Co.
INFO/CARD #210

+17 dBm Amplifier

Model TM5150 from Amplifonix offers 19 dB gain, +17 dBm power output at 1 dB compression, and 3.5 dB noise figure over the -55C to +85C temperature range. Package options include 4-pin TO-8, surface mount, and connectorized housings.

Amplifonix
INFO/CARD #209


SPDT Switches

Teledyne Microwave announces type CS-53 coaxial switches with faster switching times; 20 msec for failsafe and 10 msec for latching designs. DC to 6 GHz performance specifications include: 1.25:1 maximum VSWR, 0.4 dB maximum insertion loss and minimum 70 dB isolation. To 18 GHz, these specifications are 1.5:1, 0.5 dB and 60 dB, respectively, and from 18-26.5 GHz, they are 1.8:1, 0.7 dB and 50 dB.

Teledyne Microwave
INFO/CARD #208

Grounding Contacts

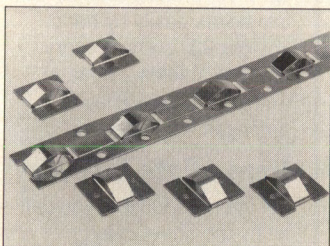The Omni Grounding Series provides a simple means of mounting grounding contacts individually or in series, using pressure sensitive tape or mechanical fasteners. Made from beryl-



lium copper, they compress to 80 percent of their height and allow sliding contact from either end.

Tech-Etch, Inc.
INFO/CARD #207

ESM Antenna

RF Microsystems has added

the model 216 antenna to their line, a shaped biconical design with a very broad bandwidth, omnidirectional azimuth coverage and vertical polarization. The antenna operates over 0.5 to 18 GHz with a maximum VSWR of 2.5:1 in a 50 ohm system. Weight is one pound, and the size is approximately 5 inch diameter by 5.25 inch height, plus mounting flange.

RF Microsystems Inc.
INFO/CARD #206

2 GHz Power FETs

ST5000 and ST5001 from Semetex provide 0.5 and 1.0 watts of class A power with 11.5 and 10 dB gain, respectively, at 2 GHz. Applications include broadband multi carrier, low noise, high intercept amplifiers, medium gain power amplifiers, high level VCOs and high performance receiver front ends. 1-99 unit pricing is \$45.00 for the ST5000 and \$52.00 for the ST5001.

Semetex Corp.
INFO/CARD #205

SMT Connectors

Surface mount connectors in SMA and SMB types are available from Applied Engineering Products. Accurate solder seating with no-hole mounting shortens assembly time. Parts tested withstood straight pull of 24 lb., side loads to 40 lb., and radial torque to 16 in -lb.

Applied Engineering Products
INFO/CARD #204


Switched Filter Modules

Integrated Microwave offers two, three and four channel modules for frequencies up to 3 GHz. GaAs switching offers 150 ns speed and typical switch loss of 4 dB. Highpass, lowpass, bandpass and band-reject responses are available.

Integrated Microwave
INFO/CARD #203

GSM/PCN SAWs

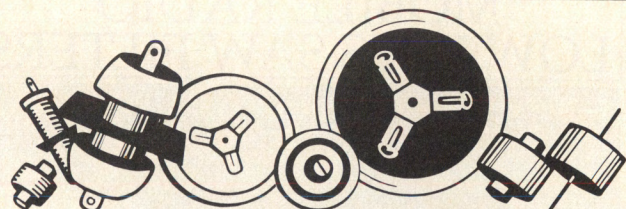Sawtek has applied low-loss filter techniques for IF filtering requirements of GSM/PCN equip-



POWER CAPACITORS


...for high power density applications

Plate, barrel and feed-through capacitors for a wide range of applications such as solid state RF generators, RF suppression and HF transmitters.

Capacitance: 1.5-10,000 pF • Voltage: 2-30 kVp
 Power: 2-150 kVA • Current: 5-50 Arms.

Manufactured by Draloric GmbH. Call now for information including special design assistance.

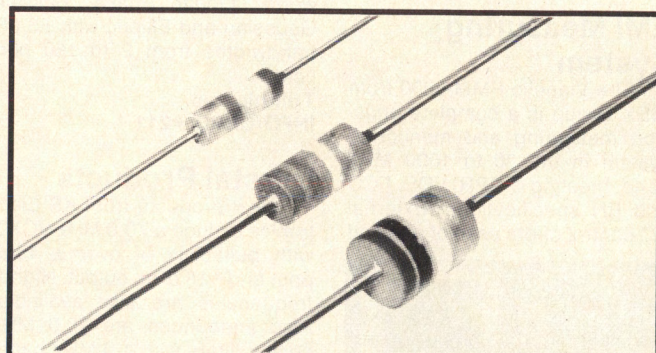109 Alfred Street, Biddeford, ME 04005-2526 • Phone: (207) 284-5695



Ceramic fixed value capacitors are ideal for communication applications requiring high quality, low values at competitive prices.

For over 40 years Quality Components Inc. has been a major supplier of high quality fixed value capacitors to the OEM electronic communication industry.

Engineers prefer the broad range of low values, close tolerances ($\pm 5\%$) and values ranging from .1pf to 4.7 pf with increments of .1 pf between each value.

Quality Components' capacitors are ideal for applications such as RF filters, coupling capacitors, bypasses, wave shapers and tuned circuits, requiring high reliability at a competitive price.

For detailed information or sample kit contact:



Quality Components Inc.
 P.O. Box 113, St. Mary's, PA 15857
 TEL. (814) 834-2817 • FAX (814) 834-9141

ment. Center frequencies between 70 and 250 MHz have been demonstrated, with insertion loss of approx. 6 dB. Group delay variation is an excellent 150 nsec. A simple fabrication technique reduces manufacturing costs.

Sawtek, Inc.
INFO/CARD #202

Multitone Generator

Systematix offers a multitone generator for intermodulation testing, with up to four carriers available, tuned as close as 100 kHz at frequencies of 800-900 MHz or higher. Internal intermod spurs are better than -80 dBc at 45 dBm output. All four tones are independent and front-panel tunable. Modulation and automatic control are optional. Price of the unit is \$19,500.

Systematix
INFO/CARD #201

BNC Crimp Connectors

Alpha Wire announces their new BNC Crimp Connector, a

nickel plated connector with Delrin dielectric and gold-plated center pin. Rapid assembly time and reliable electrical and mechanical contact are major features. The connector is provided in standard 50 ohm impedance.

Alpha Wire Corp.
INFO/CARD #200

Cell Site Antenna


Model ASP-2892 is a 13 dB gain log periodic array for 60-degree sectorized cell sites. The design covers a bandwidth of 800-960 MHz with only a 15 degree vertical beamwidth. Five degrees of beam tilt is built in, with additional tilt available by adjustment of the mounting clamp. Power rating is 500 W and wind velocity rating is 130 MPH.

The Antenna Specialists Co.
INFO/CARD #199

Solderable Flexible Laminates

Foil-film laminates are offered by Chomerics, to serve as flexible circuits in commercial and mili-

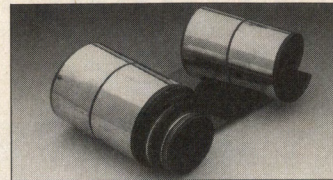tary equipment. The laminates can be copper or solder-coated copper, bonded to a variety of dielectric films in continuous rolls



or die-cut pieces. These products are also suitable for grounding and shielding applications.

Chomerics, Inc.
INFO/CARD #198

Package Seam Welder

The Venus II Parallel Seam Sealer from Polaris adjusts to variations in carrier configurations in electronic packages and package placement. Square or rectangular package up to 6 inches are sealed by resistance welding or solder reflow.

Polaris Electronics Corp.
INFO/CARD #197

Coaxial Resonator Oscillators

T and M Microwave offers the CR 1000 series of coaxial resonator oscillators covering the frequency range of 300 MHz to 4.5 GHz. Nominal power output is +13 dBm, harmonics and spurious are specified at -20 dBc and -80 dBc, respectively, and phase noise at 10 kHz offset is -115 dBc. Size for a typical 840 MHz unit is .475 x 1.0 x 1.5 inches.

T and M Microwave, Inc.
INFO/CARD #196

Arbitrary Waveform Generator

The HI-2009A by Hitronetic has been introduced in the U.S. by Kersaint Associates. The unit synthesizes analog signals with a time resolution of 2.2 nsec per point, two megabytes of signal memory, programming flexibility, and a 450 Mpts/sec sample rate. The price starts at \$40,000.

Kersaint Associates
INFO/CARD #195

RF expo

PROCEEDINGS

Design Ideas From the Best RF Engineers in the Business

Successful engineers like yourself rely on the latest engineering information to stay on top of your profession. Every RF Expo Proceedings has hundreds of pages of outstanding RF reference material covering advanced RF design and analysis, practical design techniques, product applications, and basic tutorials.

Give yourself the designing edge...
order your copies of the
RF EXPO PROCEEDINGS today!

Hurry, supplies are limited.

Save 20% Take all 10 for \$1,160 A savings of \$290

Please send me the following Proceedings:

- ☐ RF Technology Expo 91
- ☐ RF Technology Expo 90
- ☐ RF Technology Expo 89
- ☐ RF Technology Expo 88
- ☐ RF Technology Expo 87
- ☐ RF Technology Expo 86
- ☐ RF Expo East 90
- ☐ RF Expo East 89
- ☐ RF Expo East 87
- ☐ RF Expo East 86

Price:

\$145 each — outside U.S. add \$30.00 to total order for shipping charges.

Payment: (Payment must accompany order)

- ☐ Check enclosed ☐ Bill my: ☐ VI ☐ AE ☐ MC

Name _____
Title _____ Phone _____
Company Name _____
Address _____
Bldg. No. _____ M/S _____
City _____ State _____ ZIP _____
Country _____ Postal Code _____
Card # _____ Exp. _____
Signature _____ Date _____

SEND TO: RF EXPO PROCEEDINGS

6300 S. Syracuse Way, Suite 650
Englewood, CO 80111
(303) 220-0600

Surge and Transient Considerations

By Gary A. Breed
Editor


Surges and transients on power and signal lines are major EMC problems in electronic equipment of all types. It is common to see these events occur at magnitudes of thousands of volts, with a considerable amount of total energy. The problem is a particular nuisance at radio frequencies, where even small amounts of energy can interfere with the reception of desired signals. Eliminating, or at least limiting the effects of this unwanted energy usually requires a combination of several standard protection components and circuits.

Surges

Surges are by common definition a low frequency phenomenon, whether they occur on power distribution circuits or signal lines. Intuitively, they can be considered as low frequency modulation of the desired electric or electronic energy normally found on the line. Most signal line surges can be traced to lightning, while power lines are also subject to the inductive kick of machinery or sudden changes in load.

Lightning surges (not direct hits) are usually the result of the discharge path being inductively coupled to a power or telecommunications line. Rural locations are particularly susceptible, since there are long, uninterrupted stretches of distribution lines available for coupling. This type of surge can be very substantial, but is largely dissipated by a combination of spark-gap discharge units and metal-oxide varistors (MOVs). However, equipment must be designed to withstand surges that are below the protection threshold of these devices.

Inductive kick and distribution circuit load changes are somewhat more predictable. Unless they are accompanied by switching transients, they tend to be smooth changes in voltage, with a damped swing of voltage on the line. Their effects are almost always limited to power supply variations. Linear power supplies must be designed to have an adequate raw DC voltage and capacitive storage to remain above the regulator's dropout threshold. Switching supplies

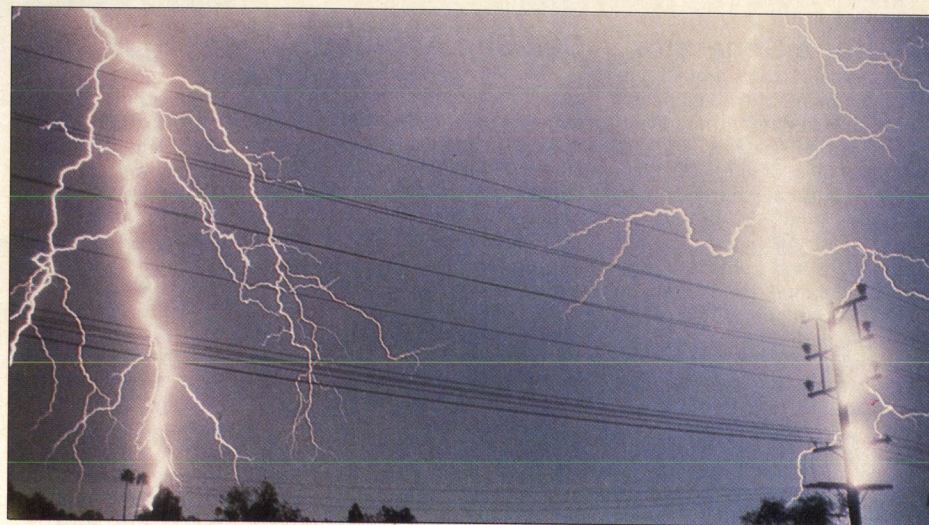

react much like they would to a change in load. If the supply is near its maximum current output capability, the voltage swing of the surge can modulate the regulated output.

Transients and Noise

Variations with very short time duration or with repetitive spikes are called transients, and they come from a large number of sources. In power distribution, they occur when circuits are switched in and out of the power grid, or when nearby lightning results in energy from close coupling or by direct contact of charged ions to the lines. Physical damage causing arcing or shorts contribute to the problem, as well. On signal lines, the potential effects due to lightning are the same as on power lines. AC line filters will remove most of the RF noise conducted by the lines, but

radiation from nearby wiring will still be present, unless shielded by conduit.

AC or DC potentials on signal lines can be another source of trouble. DC and ringing voltages are present on telephone circuits, and DC power is present on CATV distribution coaxial cable, as well the RF signals. If a leakage path is present, or if balanced lines become unbalanced with respect to ground, the resulting currents can cause problems with hum pickup from longitudinal currents coupled from AC power distribution circuits. These currents are normally suppressed by the balanced nature of the signal lines.

Outside sources of trouble are common on signal lines. Failed distribution equipment, faulty customer equipment and physical damage are relatively common. The result may not be restricted to disturbances in the desired signals

Metallic Surge (across wires):	100 A, 800 V, 10 x 560 msec rise/fall
Longitudinal Surge (common mode):	200A, 1500 V, 10 x 160 msec
Surge Protection Devices:	Breakdown voltage greater than 250 V
Leakage Current (tip or ring to ground):	10 mA, 1000 VRMS
On-Hook Impedance (tip or ring to ground):	100 kohms
Signal-to-Noise Ratio (voice grade):	greater than 30 dB, typical
Signal-to-Noise Ratio (digital loops):	depends on data rate
Longitudinal-to-Metallic Balance:	60 dB minimum

Table 1. Some telephone circuit performance specifications.

and voltages. A broken shield on a coaxial line or unbalance due to inadvertent grounding of one side of a telephone line increases susceptibility to RFI from nearby transmitters. Illegal telephone and CATV connections are notorious culprits for increased RFI because they create mismatch, unbalance or compromise shielding integrity.

Noise in the user's equipment is the result of all the above effects, and more. Other sources of impairment on signal lines include crosstalk, distortion and excess attenuation. Line balance, its physical condition, and the status of transmission equipment all affect overall signal transmission performance. Table 1 shows some key performance specifications for telephone line performance, including surge and overvoltage protection standards, as well as signal path performance.

Protection and Prevention

Transients and noise are insidious problems. They often result in intermittent problems that are extremely difficult to diagnose. Methods of dealing with

voltage-current surges and transients include filtering techniques to minimize high-frequency components of the disturbances, along with fuses, spark gap, varistor and zener protection against more dramatic spikes.

Standard practices in the construction of these facilities include separation of signal and power distribution conductors whenever possible, metallic sheathing on telephone trunk lines, periodic grounding to minimize the accumulation of a potential on the shield, and static discharge wires on certain power lines. CATV systems, with a completely shielded system, usually include a ground block with a spark-gap arrestor at the entrance to the customer's location. Telephone lines have fuses in both tip and ring circuits, which may be at a distribution pedestal or at the customer service entrance.

Noise, hum, distortion and interference that appear along with the desired signal require different techniques. Most areas of noise performance are dependent on the condition of the transmission equipment and the transmission me-

dium. Designers of user equipment must be certain that they are compatible with the wire or coax system they utilize, and must allow sufficient design margin to be sure that the transmission medium is the weakest link in the system. Minimizing noise and distortion requires control of signal levels to maintain exactly what is specified for the system used.

Above all, familiarity with system requirements, and the nature of surges, transients and noise helps make a good relationship with the power, telephone and CATV companies. The best service always seems to be given to knowledgeable customers.

RF

See the RF Design Awards winners in the July issue!

TRIMMER CAPACITOR PROTOTYPING KITS



- GIGA-TRIM®
- CERA-TRIM®
- PHASE-TRIM®
- AIR DIELECTRIC
- CERAMIC TRIMMER
- MICROWAVE TUNING ELEMENT
- THIN-TRIM®
- SEAL-TRIM®

Johanson

MANUFACTURING CORPORATION
Rockaway Valley Road
Boonton, N.J. 07005
(201) 334-2676 FAX: 201-334-2954

FILTERS THAT DELIVER WHEN YOU NEED THEM



**Custom designs, Fast prototypes,
Quantities in stock, Specifications guaranteed.**

- Lowpass ■ Highpass ■ Bandpass ■ Band reject
- NTSC & PAL video ■ Medium cut-off ■ Sharp cut-off
- Delay equalized ■ Delay equalized, sharp cut-off
- Linear phase ■ Tempest ■ Anti-Aliasing
- Tubular ■ TO-8 ■ Low profile ■ Subminiature

Call or write for Application Brochures
from Allen Avionics and BAL.

ALLEN AVIONICS, INC.

224 East Second Street, Mineola, NY 11501
Tel: 516-248-8080 Fax: 516-747-6724



A Simple Clock and PSK Carrier Recovery Circuit

By Francois Methot
RadioSysteme, Inc.

Today, analog designers have to interface with the digital world by recovering the clock from their modem (electric or optic) for high speed data transmission.

The interface between analog and digital is critical, especially when it must be done at a low cost. I propose a different approach to obtain PSK demodulator and clock recovery with the same kind of circuit.

The circuit is based on a PLL with a "D" flip-flop as the phase comparator, coupled with a VCXO to avoid locking on undesired frequencies.

The carrier and/or clock is recovered by using the positive edge of the incoming PSK signal or data stream to sample the carrier or clock and create a DC voltage to control the VCXO. Figure 1 depicts the interconnection between the "D" flip-flop and the VCXO.

However, there is a compromise to be made in using this design. The phase detector does not have a linear transfer

function versus phase error. The gain of the phase detector ($K\phi$) in frequency is low but $K\phi$ for the phase is very high. Figure 2 shows an example of the transfer function of this design.

In the absence of data, the output of the "D" flip-flop can be at a logical "0" or "1" depending where the data did the last sampling in the clock, so the VCXO can be at the maximum or the minimum frequency. When the PLL begins the search for the frequency, it requires many samples to converge on the correct frequency, but the search for the phase is very fast.

For a low bit rate, I recommend the use of a CMOS "D" flip-flop because it has the same threshold for a logical "1" or logical "0". Most of the time a passive filter will do, when it is connected on the Q or Q output, depending if it is the positive edge or negative edge that is required at the center of the data bit.

For a high bit rate, an ECL "D" flip-flop must be used because it has only 1 nsec of propagation delay. However, an active filter (integrator) must be implemented to increase the range on the diode varicap in the VCXO circuit.

This circuit can be implemented to demodulate a PSK signal with some compromise. The carrier must be an exact multiple of the bit rate. Moreover, the phase transition of the carrier must be synchronized with the data. These requirements are cost efficient and easily implemented on the demodulator.

When feasible or when given the choice of IF frequency, the carrier to be modulated must be an exact multiple of

the data clock to be transmitted. A simple PLL can multiply the clock synchronously and form the carrier to be modulated. Figure 3 shows an example of a simple PSK modulator. Now the PSK carrier can be seen as a data stream of "1", "0", "1" ..., with one extra "0" or one extra "1" at each transition of the data. Refer to Figure 4 for the timing diagram.

A carrier can be regenerated at twice the PSK carrier frequency with the same circuit for the clock recovery and later, by dividing the carrier by two. A simple exclusive "or" can demodulate the PSK signal. Because of the use of the divider, there exists a phase ambiguity of 180 degrees. By using a differential code or NRZI encoding, the demodulated data will always be the same polarity.

In Figure 5, one ECL IC is used for limiting the PSK signal, another IC has the phase comparator and the frequency divider, and a final IC to demodulate the PSK signal and produce the VCXO. An NRZI to NRZ must be added after the low pass filter. This technique, compared to the conventional approach, requires no treatment on the signal (X^2) to rebuild the carrier information.

The component values of the integrator were calculated using Communica-

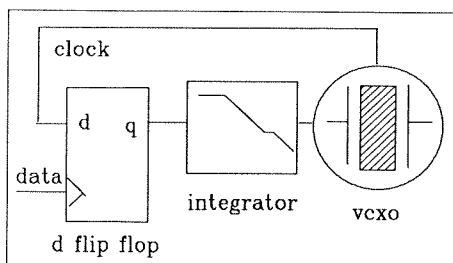


Figure 1. Interconnection between "D" flip-flop and VCXO.

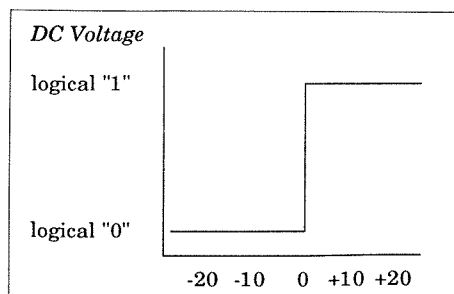


Figure 2. Transfer function from design in Figure 1.

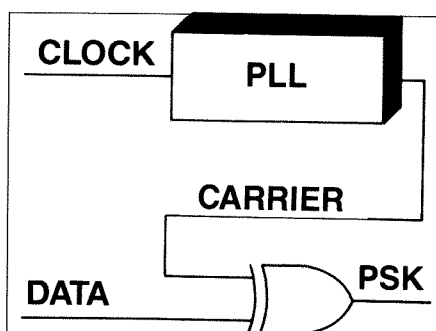


Figure 3. A simple PSK modulator.


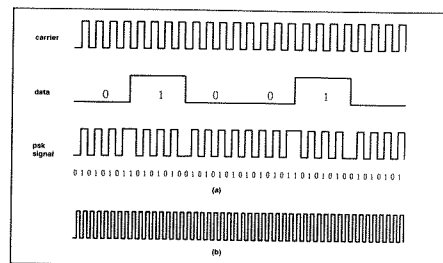


Figure 4. Timing diagram (a) the PSK signal can be seen as a data stream of 1, 0, 1, ... with one extra 0 or 1 at each transition of the data, (b) a carrier can be regenerated at twice the PSK carrier with a simple clock recovery and when it is divided by two, can demodulate the PSK signal.


At last, an affordable PIN DIODE TUNED HOPPING FILTER!

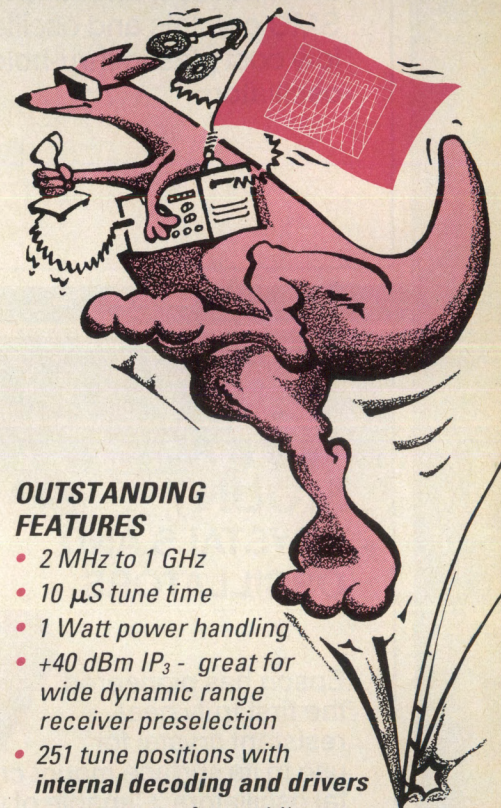Useful whenever you need a tunable narrowband filter...
Or when you just need a filter you can set to a particular frequency...
For testing, breadboards, or as a system component.



OUTSTANDING FEATURES

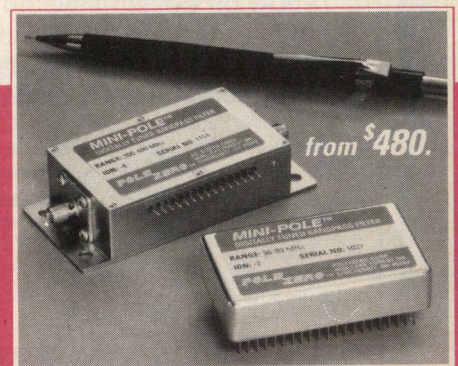- 2 MHz to 1 GHz
- 10 μ S tune time
- 1 Watt power handling
- +40 dBm IP_3 - great for wide dynamic range receiver preselection
- 251 tune positions with internal decoding and drivers
- Less than 2 in³ - world's smallest digitally tuned RF filters



from \$480.

**POLE
ZERO**
CORPORATION

4480 LAKE FOREST DRIVE
CINCINNATI, OHIO 45242
PHONE/513 563-1133
INFOCARD 55

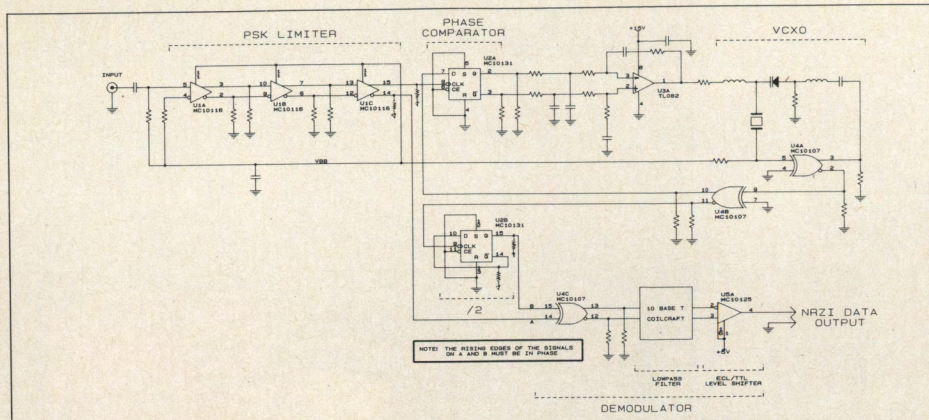


Figure 5. PSK demodulator circuit.

tions Consultation Corporation's (now Compact Software) PLL Design Kit.

Figure 6 shows my RF Design Contest entry: clock recovery based on "D" flip-flop phase detector. Figures 7 and 8 show the performance of the circuit's clock and data recovery.

Conclusion

The circuit shown in Figure 6 uses only one IC to both perform the phase comparator and sample the data. The VCXO was made with a crystal in fundamental at 139.264 MHz to eliminate frequency multiplication and achieve a larger range. A ΔF of 50 kHz was obtained with ± 15 kHz of capture range. The data stream comes from the optical detector from a source at -25

dBm. The clock recover still locks up to -31 dBm even if the data is at 10^{-2} of error rate. For the PLL, the parameters are: $W_n = 10$ kHz, $K_{VCO} = 1$ kHz/volt, $K_o = 10$ volts/radian, $\xi = 0.7$. **RF**

About the Author

Francois Methot is President of RadioSysteme Inc., and has 15 years experience in CATV, digital telephony, radio communications and fiber optic networks. He can be reached at (514) 426-0773.

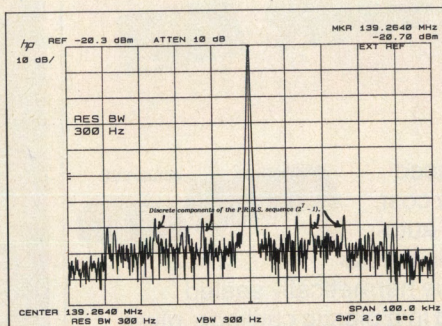
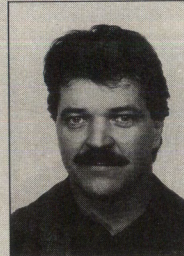


Figure 7. Spectrum analyzer display of the recovered clock signal.

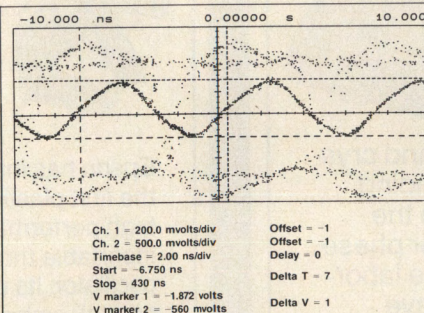


Figure 8. Digital oscilloscope display of clock and recovered data.

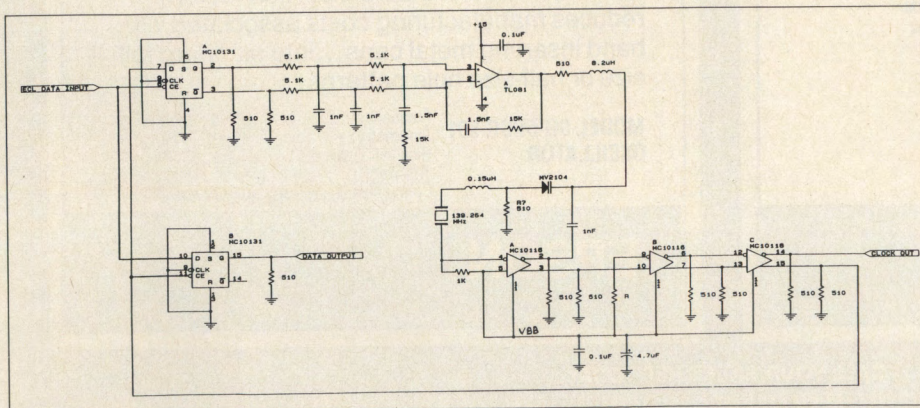



Figure 6. Clock recovery based on "D" flip-flop phase detector.

EPSON



THE CRYSTALMASTER™

leads new
crystal oscillator
technologies into
the 90's with...

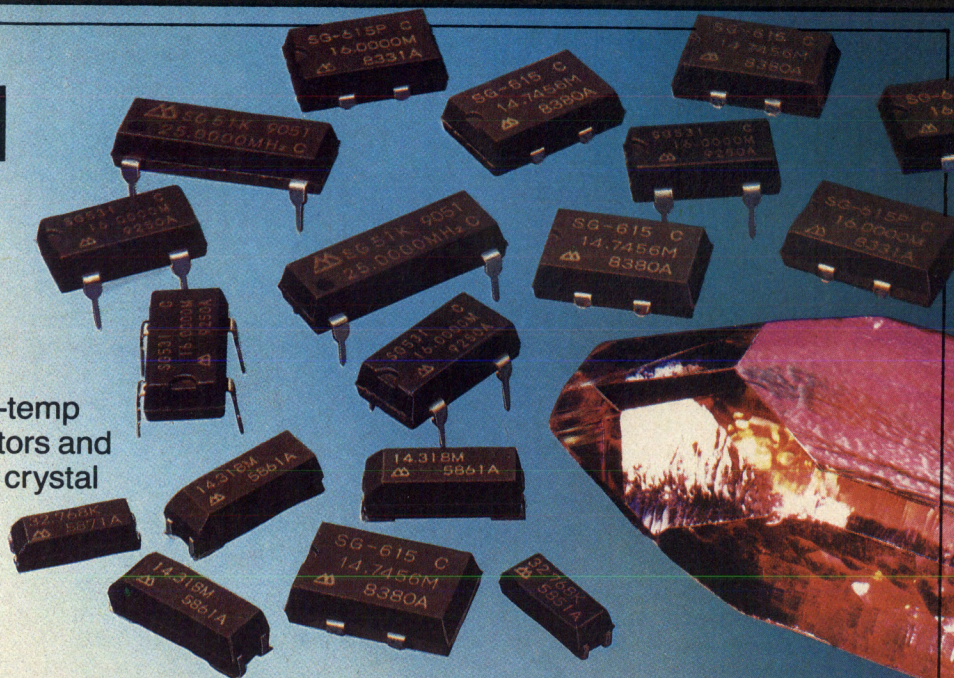the most cost effective hi-temp
SMD crystals and oscillators and
low cost plastic thru-hole crystal
oscillators.



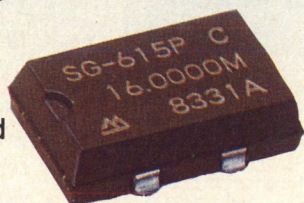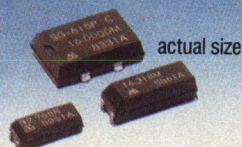EPSON SURFACE MOUNT CRYSTALS AND OSCILLATORS




Epson has pioneered the first truly heat resistant crystal for use in its surface mount crystals and crystal oscillators. Capable of withstanding 260°C for 20 seconds... far above the demands of standard IR and vapor phase reflow processing systems... these labor-saving high-temp SMD crystals have become the accepted standard for surface mount crystal and oscillator components.

MODEL SG-615 OSCILLATOR
Frequency: 1.5 to 66.7 MHz
Symmetry: 45/55 (TYP)
Rise/Fall Time: 5 nsec (TYP)
Tristate: Available
Compatible
Technology: CMOS and TTL
Op. Temp. Range: -40°C to 85°C


MODEL MA 505/506 CRYSTAL
Frequency: 4.00 to 66.7 MHz
MODEL MC-405 CRYSTAL
Frequency: 32.768 KHz

EPSON®
EPSON AMERICA, INC.
Component Sales Department Telephone: 213/787-6300

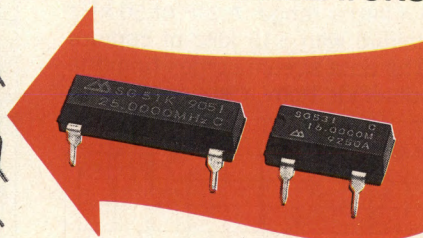EPSON THRU-HOLE OSCILLATORS REPLACE METAL CAN OSCILLATORS



Epson has introduced the first plastic low cost, high performance auto-insertable thru-hole crystal oscillator. Its unique hermetically sealed crystal, embedded in a plastic package, gives the same EMI protection and higher performance than metal can oscillators... at a much lower cost. And, the auto-insertion feature reduces manufacturing costs associated with hand inserting metal cans... into standard full-size or half-size hole patterns.

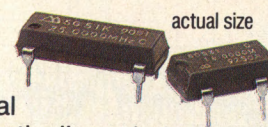

**MODEL SG-51/SG-531
OSCILLATOR**

Frequency: 1.5 to 66.7 MHz
Symmetry: 45/55 (TYP)
Rise/Fall Time: 5 nsec (TYP)
Tristate: Available
Compatible Technology: CMOS and TTL

EPSON®
EPSON AMERICA, INC.
Component Sales Department Telephone: 213/787-6300

CALL YOUR SALES REP TODAY

EPSON Sales Representatives: **AL-GA-TN** Concord Components 205/772-8883 • **AZ-NM** Fred Board Assoc. 602/994-9388 • **CA-No.** Costar 408/446-9339 • **CA-So.** Bager Electronics 714/957-3367 • **CO-UT** Wn. Region Mktg. 303/428-8088 • **FL** Dyne-A-Mark 407/831-2822 • **IL-WI** LTD Technologies 708/773-2900 • **IN-KY** C C Electro 317/921-5000 • **KS-MO-IA** Microtronics 913/262-1444 • **MA-NH-CT** Rosen Assoc. 617/449-4700 • **MD-VA** Tech Sales Assoc. 301/461-7802 • **MN** Electro Mark 612/944-5850 • **NC-SC** WLA Assoc. 919/231-9939 • **NJ** JMR Sales 201/525-8000 • **NY** Elcom Sales 716/385-1400 • **Metro, NY** Niktronix 516/929-4671 • **OH-MI** J. D. Babb Assoc. 216/934-4454 • **OR-WA** Matrex 503/245-8080 • **PA** Omega Sales 215/244-4000 • **TX-OK** Component Tech. 214/783-8831 9101

VHF and UHF Crystal Oscillators — Part II

By Andrzej B. Przedpelski
A.R.F. Products, Inc.

This note contains some theory, more circuits, some suggestions and further considerations of 5th, 7th, and 9th overtone crystal oscillators (up to 630 MHz) using simple easy to build circuits.

I should have started Part I, July of 1990 (1), with some applicable theory, but I got carried away by the ease of constructing and adjusting these high frequency crystal oscillators and their reliable performance. To rectify this omission let's consider the requirements for an oscillator. Barkhausen tells us that for a circuit to oscillate, two conditions have to exist.

- the open loop gain $A(\omega) \times \beta(\omega)$ of Figure 2) has to be more than unity, and
- the phase of this gain has to be $360n$, where n is an integer (including 0).

In the circuits described, the gain, $A(\omega)$ is supplied by the MMIC amplifier and the feedback, $\beta(\omega)$ consists of the crystal, in series with a length of transmission line, and the capacitor(s). Using an ideal non-inverting amplifier (such as Figure 1a) (1), the feedback can have 0 degrees phase shift and no phase shifting network is thus necessary. The crystal can, theoretically, operate in series resonance (presenting only a resistance in the feedback path) and becomes an attenuator in conjunction with the 50 ohm input impedance of the MMIC amplifier. If this attenuation is

lower than the gain of the amplifier, the circuit will oscillate. The oscillations start slowly (relatively speaking) by amplifying circuit noise at the resonant frequency until the amplifier saturates (gain of the amplifier becomes equal to the feedback attenuation).

In the inverting amplifier configuration (such as Figure 1b) (1), the feedback has to provide the (theoretically) required 180 degree phase shift to allow oscillations to take place.

In practice, of course, the non-inverting amplifier has some phase shift at the operating frequency, and the inverting amplifier phase shift is usually somewhat less than 180 degrees. Thus, the feedback circuit has to compensate for these small phase shift discrepancies.

The inverting amplifier oscillator configurations are generally preferred, since they have less tendency to oscillate at undesired frequencies. Any "simple" undesired feedback usually does not have the required 180 degree phase shift.

To provide the needed feedback phase shift, different methods can be used. The crystal itself can provide some phase shift. However, it is better to use it in a series resonance mode to reduce losses through the crystal. Thus, a phase shifting network providing almost 180 degree phase shift has to be used. At lower frequencies, a pi or tee phase shifter can be used. However, at the higher frequencies, accurate inductors

are difficult to construct, and spurious reactances cause additional uncontrolled phase shifts. To overcome this, and to provide very simple implementation of reliable circuits, a transmission line can be used to provide the main required feedback phase shift. This approach is feasible at the higher frequencies and provides easily reproducible phase shifts. To demonstrate this, the circuit shown in Figure 3 was built. While feasible and very simple it was not considered very practical since the length of the transmission line was difficult to optimize. A more feasible method using variable capacitors to fine-adjust the feedback phase shift was used in the more practical circuits. This method had the additional advantage of allowing some "pulling" of the oscillator frequency.

Now back to some more circuits

Circuit # 1 (350 MHz fifth overtone)

The circuits presented in Part I used hybrid type RF amplifiers. To reduce size still more and allow the use of surface mounted components, monolithic RF amplifiers were then tried. A typical inverting type was used (Avantek MSA-0735). Two possible circuit configurations were tried (Figures 4 and 5). Both gave an output of 6-8 dBm with either a 3.6 inch or 6 inch length of transmission line. The capacitors had to be retuned, of course. The circuit of Figure 5 seemed to have lower harmonic content (35-40 dB below fundamental for second and third harmonics). While monolithic amplifiers usually have the disadvantage of requiring input and output capacitors, one capacitor can be omitted, since the crystal provides DC isolation. These amplifiers also require a biasing resistor. In the case of the circuits shown, this was actually taken advantage of to provide a circuit which worked reliably directly from an airborne power source of 22-30 VDC. This was accomplished by the use of the high value (1000 ohm) biasing resistor.

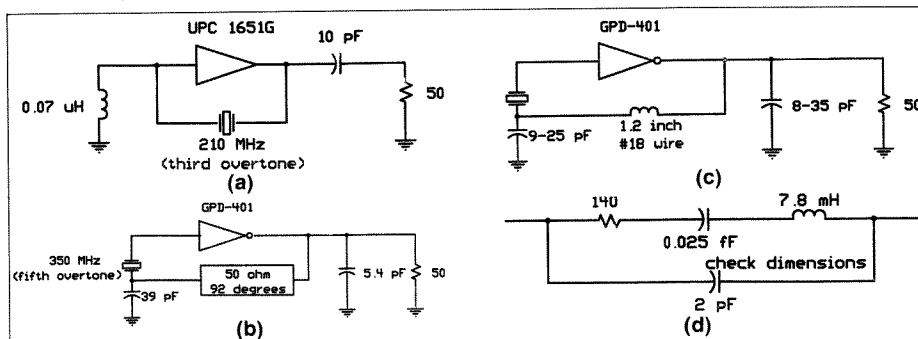


Figure 1. Figures from Part I: (a) third overtone circuit, (b) 350 MHz fifth overtone, (c) overtone oscillator with L/C phase shift, (d) approximate crystal equivalent circuit at fifth overtone.

Circuit # 2 (490 MHz seventh overtone)

The basic circuit of Figure 5 could be easily modified to provide reliable operation on the seventh overtone of the crystal. The same crystal was used with an 8.2 or 7.2 inch length of transmission line, as shown in Figure 6. An output of 6-8 dBm was obtained, but the harmonic content was high (-10 to -15 dB).

Otherwise, the circuit performed reliably.

Comments

Output was always observed on a spectrum analyzer to ensure that the proper overtone operation was obtained. Power output was measured at the desired output frequency.

All circuits were checked to ensure

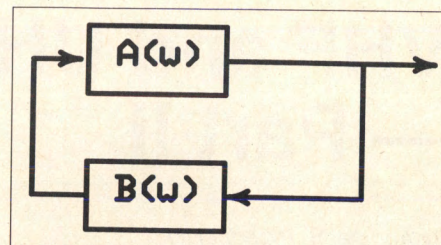


Figure 2. Oscillator equivalent circuit.

that no mode switching could be induced. DC power was turned on instantaneously or was brought up gradually while output was observed on the spectrum analyzer. The oscillators always started at the desired frequency.

50 ohm coaxial transmission lines were used, since they are readily available and easily changed. Once the circuit is finalized, the transmission line can be part of the PC board. There is no apparent reason why other impedances cannot be used. However, only 50 ohm coax cables were used.

An amplifier gain of about 12 dB at the desired frequency seems adequate. Higher gain amplifiers would allow a higher loss in the feedback circuit. This could reduce the crystal drive and improve stability. However, too much gain may make the circuit more susceptible to oscillations at undesired frequencies.

The phase shift in the amplifier changes with frequency. The typical inverting amplifier actually becomes non-inverting at higher frequencies. This occurs at about 4.5 GHz for the MSA-0735 used in the tests. The amplifier still has gain at this frequency, however, and this should be considered.

The crystal resistance does not seem to be critical. The crystal used had a resistance of about 140 ohms at the fifth harmonic (Figure 10). Higher resistance crystals can be used, if the amplifier gain is adequate.

The feedback path loss has to be less than the amplifier gain to sustain oscillations. The input impedance to the feedback path should be higher than 50 ohms to allow most of the amplifier power output to appear as useful power in the load. This is not unreasonable, since the feedback path can have appreciable insertion loss.

A quick temperature check was made using the circuit of Figure 5. The frequency vs. temperature curve was smooth and no mode jumping was observed.

The circuits were very reproducible.

Precision Under Pressure

In the cockpit of a jet fighter there is no room for doubt. The pilot must trust his life to complex navigational and communications systems.


You can trust EG&G Frequency Products to provide you with high quality AT and SC Cut precision quartz crystals and oscillators that will perform in such critical applications.

EG&G's high reliability standards include compliance with WS6536E. Our continuous quality assurance from raw quartz to finished product

Precision quartz crystals in solder seal, resistance weld, and coldweld configurations and oscillators with low aging and low phase noise characteristics.

helps maintain that level of excellence. Computerized production control enables us to provide you with shortened lead time delivery.

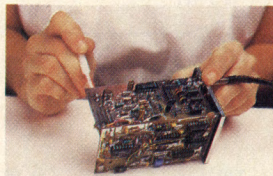EG&G also supplies custom-designed high performance crystal and LC filters, discriminators, modules and atomic frequency standards making us a *single qualified source* for all your frequency control needs. Call or write today for more information on precision products that perform under pressure.




In-house experts working in state-of-the-art facilities produce highly stable TCXOs, VCXOs and OCXOs for precise control of frequency.

EG&G FREQUENCY PRODUCTS, INC.

EG&G Frequency Products, Inc. 4914 Gray Road, Cincinnati, Ohio 45232
FAX 513-542-5146, PHONE 513-542-5555

INFO/CARD 57

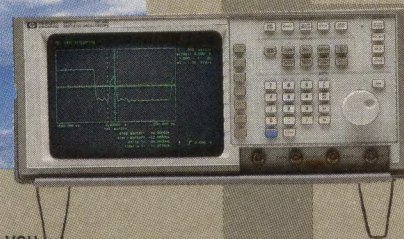Imagine A Single Source For Every Frequency Control Need...




Now Imagine What That Source Can Do For You.

With CTS, you can specify from one of the broadest lines of frequency control products available anywhere—crystals, clock oscillators, VCXO's, TCXO's and ovenized oscillators. If a standard product won't do, our engineers will design one that meets the requirements of your application. But there are more reasons for making CTS your single source for frequency control products.

Our cutting-edge technology assures you of the most advanced frequency control products. The in-house production of crystals, precision designs and strict quality control give you an added margin of reliability. Additionally, our technical support teams provide a problem solving capability that can be a real asset for your design and engineering teams.

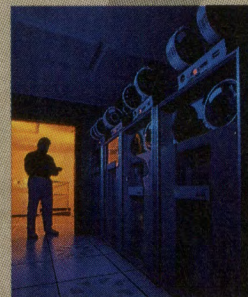Get the product your application requires, plus technical services and reliability proven in the most demanding military, instrumentation, telecommunication and data processing applications. All from a single source. Call now for the name of your CTS Sales Representative.



CTS
CORPORATION

*Around The World,
Your Single Source For ExcellenceSM*



CTS Frequency Control Division,
400 Reimann Ave., Sandwich, IL 60548, Tel: 815/786-8411, Fax: 815/786-9743

INFO/CARD 58

THE INDUSTRY'S

MOST WANTED

TCXO

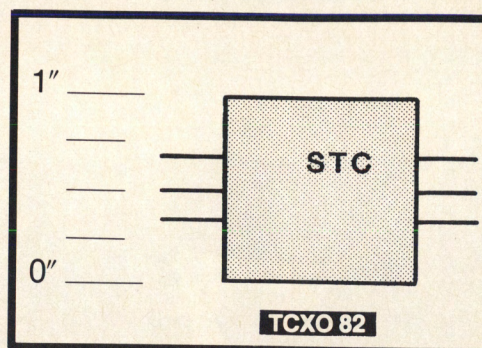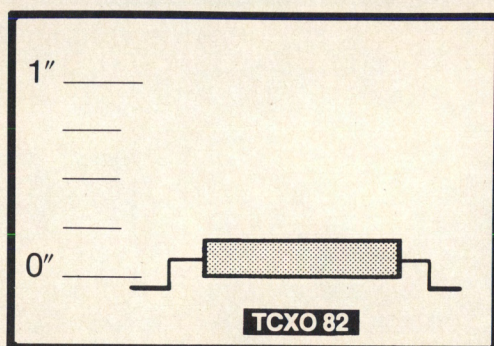

The latest TCXO from STC

DESCRIPTION:

- 0.2 cubic inches
1" x 1" x 0.2" high
- Mil grade available
- Surface mountable
- Custom configurable leads

MODE OF OPERATION:

- Low phase noise
- Frequencies up to 350 mhz
- Low power consumption
- Highly stable, precision performance

Analog Chip Temperature Compensation Technology

Buy one or borrow one.

Call us for technical literature and complete details
on our unique offer.

STC COMPONENTS, INC., 636 REMINGTON ROAD, SCHAUMBURG, IL 60173
1.800.624.6491 • 708.490.7150 • FAX 708.490.9707 • CANADA: 1.800.624.6494
UK: 0279.626626

INFO/CARD 59



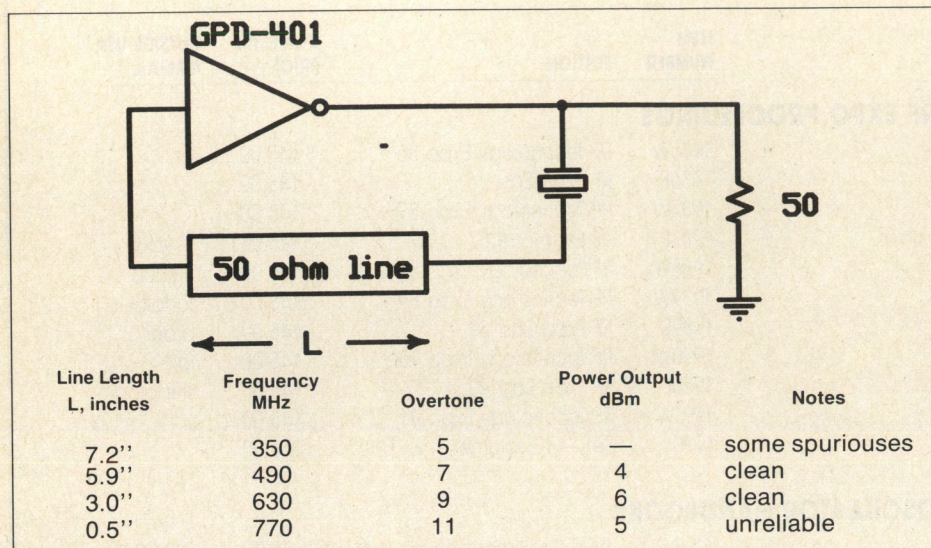


Figure 3. The simplest circuit.

The same circuit was built using direct interconnections (no chassis), using a ground plane or a PC board with all surface mount components. The performance was essentially the same.

Increasing feedback loss (reducing drive to the amplifier) reduces harmonic content (as expected). This reduces power output somewhat. For a power output reduction of 1-2 dB, the harmonic content can be reduced by 15-25 dB.

The initial tuning procedure is quite simple. Using a spectrum analyzer (to make sure that the right overtone operation is achieved) set one capacitor and tune the other (if two are used). If proper operation is not obtained, retune the first capacitor and repeat tuning with the other. Once the proper frequency is obtained, the output can be maximized using both capacitors.

The crystal can oscillate at the fundamental or an odd overtone. Circuit #10 (Figure 1c) (1), for instance could be made to oscillate at the third, fifth and seventh overtone by retuning the two capacitors. At these different frequen-

cies, the phase shift through the amplifier is different. While at very low frequencies it is the theoretical 180 degrees, it decreases with frequency. The crystal also looks different at these frequencies. Mr. David Smith of Innovative Frequency Control Products, Inc. kindly supplied typical equivalent circuit values for the crystal used (see Figure 1d) (1). Series R is about the same for the overtones, but is about 1/6 this value for the fundamental operation. The motional inductance (series L) is about the same for the fundamental and overtones. The motional capacitance varies to provide the proper series resonance.

While operation only up to the 9th overtone (630 MHz) was confirmed, there were indications that the 11th overtone was also feasible. The transmission line length became very short and was difficult to optimize. However sporadic operation at 730 MHz was obtained using the Figure 3 circuit and a transmission length of about 0.5 inch. As results of Figure 3 indicate, there is some spurious phase shift caused by

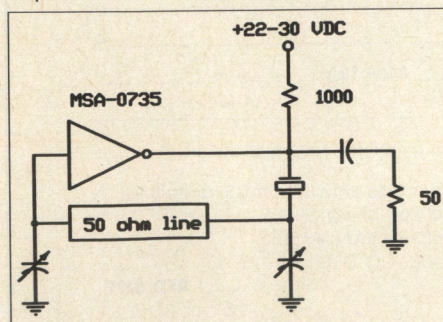


Figure 4. 350 MHz fifth overtone oscillator.


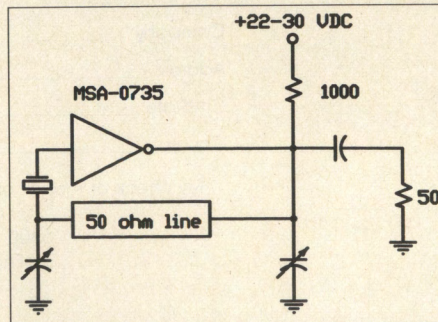


Figure 5. 350 MHz fifth overtone oscillator.

NEW NAME!
The Block Diagram Simulator you knew as **TESS** is now:

TESLA

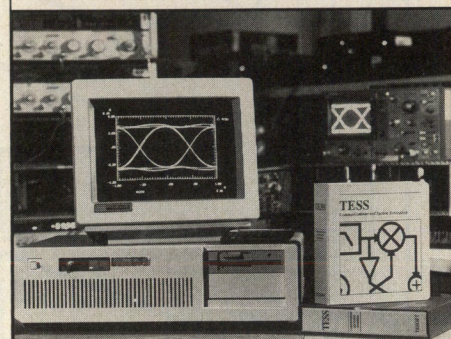

TESLA has all of the great features that classic **TESS** had like:

- **Fast RF Time Simulation**
 - **Mixed Analog & Digital**
 - **Spectrum Analysis**
 - **Input with OrCAD & PCAD**
 - **Free support & BBS (1yr)**
- Plus TESLA** has the powerful new goodies added in version 1.1:

- **24 new filters**
- **Amp and mixer models with intercept specs**
- **Hi-res graphics output to lasers, plotters, printers and wordprocessors**
- **Quantizer, Integ&Dump, Laplace and resp models**
- **Lots more space for user-added models—fill it up from the free BBS.**
- **Run OrCAD and PCAD without leaving TESLA**
- **Many new power-features**

STILL ONLY \$695!

30-day Moneyback Guarantee!
CALL FOR DEMO DISK

TESOFT

PO Box 305 Roswell GA 30077
404-751-9785 FAX 404-664-5817

INFO/CARD 60

THE SWEET'S LIBRARY

ITEM NUMBER	EDITION	DOMESTIC PRICE	OUTSIDE USA AIRMAIL
----------------	---------	-------------------	------------------------

RF EXPO PROCEEDINGS

1986W	RF Technology Expo 86	\$ 145.00	
1986E	RF Expo East 86	145.00	
1987W	RF Technology Expo 87	145.00	
1987E	RF Expo East 87	145.00	* Add
1988W	RF Technology Expo 88	145.00	\$30.00
1989W	RF Technology Expo 89	145.00	to total
1989E	RF Expo East 89	145.00	order
1990W	RF Technology Expo 90	145.00	for
1990E	RF Expo East 90	145.00	shipping
1991W	RF Technology Expo 91	145.00	
1900	Set — 10 volume	1160.00	

OSCILLATOR HANDBOOKS

3190	1990 Oscillator Design	\$ 28.00	\$31.00
------	------------------------	----------	---------

FILTER HANDBOOKS

3211	1991 Filter Applications Vol. 1	\$ 28.00	\$31.00
3212	1991 Filter Design Vol. 2	28.00	31.00
3200	Set — 2 volume	50.00	55.00

TO ORDER: Fill out order form, indicating item number, quantity desired and price. Shipping charges are included.
PAYMENT MUST ACCOMPANY ORDER.

ITEM	QUANTITY	PRICE
------	----------	-------

_____	_____	\$ _____
_____	_____	_____
_____	_____	_____
TOTAL ENCLOSED		\$ _____

☐ Payment enclosed (check or money order)
☐ Charge my order to: ☐ Visa ☐ MasterCard ☐ American Exp

Account Number _____

Signature _____
(as it appears on card)

Expiration date _____ / _____
Mo / yr

Name _____

Title _____

Company _____

Address _____ Mail Stop _____

City/State _____

County _____ Zip/Mail Code _____

My check or money order is made payable in U.S. dollars to:
 Cardiff Publishing
 6300 S. Syracuse Way, #650
 Englewood, CO 80111

RFD 5/91

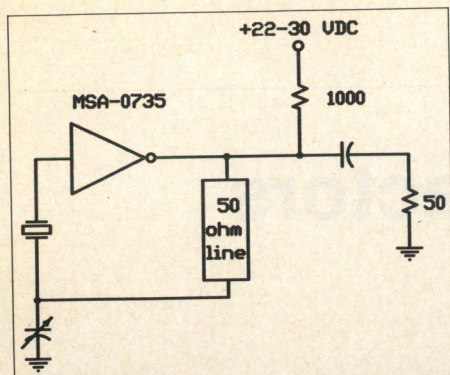


Figure 6. 490 MHz seventh overtone oscillator.

the stray inductances and capacitances in the circuit. With the breadboard used it was also somewhat difficult to accommodate the very short transmission line lengths. A better layout may make the 11th overtone operation quite feasible.

Another problem at the higher overtones is the stray pin-to-pin crystal capacity. While small (about 2 pF) its reactance at the higher frequencies becomes comparable or smaller than the crystal resistance. It may then provide the necessary feedback path to sustain oscillation at the wrong frequency. No effort was made to "tune-out" this reactance, as is sometimes done at lower frequencies to obtain true

series resonant operation and to reduce the risk of spurious oscillations.

While the above treatment of UHF crystal oscillators is by no means complete, the main effort was directed toward the simplest low cost reproducible designs using non-critical components. It was also meant as a starting point for further investigations using this general overall approach. The non-inverting amplifier circuits were also not adequately explored. One reason was that only one device was available at the time of the test; several manufacturers make suitable low cost inverting types.

RF

References


1. Andrej B. Przedpelski, "VHF and UHF Crystal Oscillators," *RF Design*, July 1990, pp. 63-65.

About the Author

Andrej B. Przedpelski is the consulting editor for *RF Design* and vice president of development for A.R.F. Products, Inc., 7260 Terrace Place, Boulder, CO 80303. Tel: (303) 443-4844.

HIGH ENERGY CORP

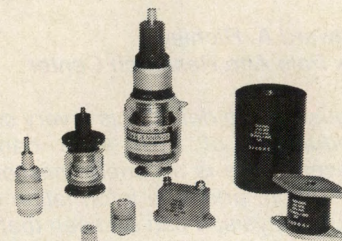CERAMIC RF CAPACITORS
C-D/SANGAMO
MICA RF CAPACITORS



JENNINGS
A LEAR SIEGLER COMPANY

VACUUM CAPACITORS
VACUUM RELAYS

SURCOM ASSOCIATES, INC.

2215 Faraday Avenue, Suite A
Carlsbad, California 92008
TEL (619) 438-4420
FAX (619) 438-4759

INFO/CARD 61

FREE CATALOG

OCXO

HIGH REL CRYSTAL OSCILLATORS
CUSTOM DESIGNS, BLILEY QUALITY.


Bliley...Your Prime Oscillator Option

Bliley

BLILEY ELECTRIC COMPANY

2545 West Grandview Blvd., P.O. Box 3428, Erie, PA 16508
(814) 838-3571 FAX 814-833-2712

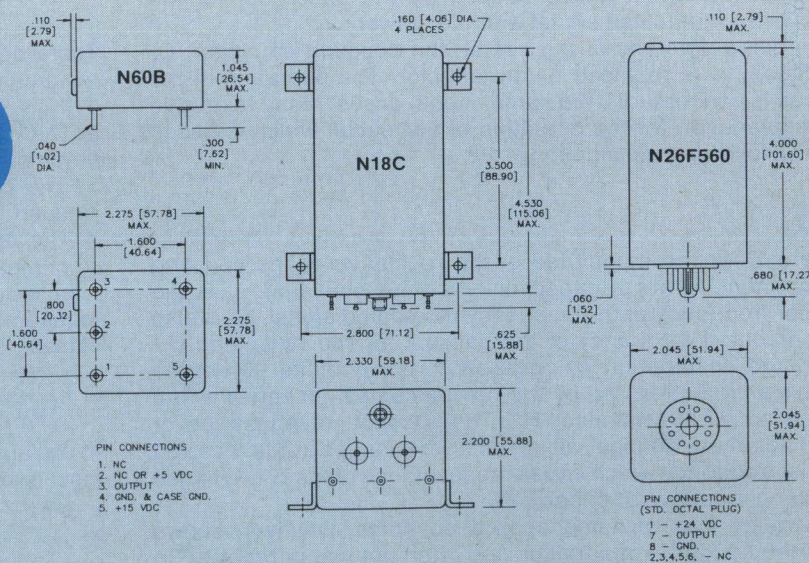Standard:
Sine Wave; +15 Vdc/N60B & +24 Vdc/N18C & N26F power supply; mechanical adjustment/N60B & N26F
Options:
TTL & HCMOS; electrical tuning/N26F; mechanical tuning/N18C; +12 Vdc to +28 Vdc/N60B & +12 Vdc to +30 Vdc/N26F (fixed value) power supply



	N60B	N18C	N26F560
FREQUENCY:	5 MHz or 10 MHz standard 5 MHz to 15 MHz available	5 MHz or 10 MHz	10 MHz standard; 5 MHz to 10 MHz available
FREQUENCY STABILITY:	$\pm 5 \times 10^{-9}$ to $+50^\circ\text{C}$ standard; $\pm 1 \times 10^{-8}$ to -20°C to $+70^\circ\text{C}$ optional	$\pm 1 \times 10^{-9}$ to $+55^\circ\text{C}$	$\pm 5 \times 10^{-9}$ to $+50^\circ\text{C}$ standard; $\pm 1 \times 10^{-8}$ to -20°C to $+60^\circ\text{C}$ optional
AGING:	1×10^{-9} /day; 5×10^{-10} /day optional	1×10^{-10} /day after 30 days	1×10^{-9} /day
SINGLE SIDEBAND PHASE NOISE (SINE WAVE)	-155 dB/Hz at 10 KHz; -160 dB/Hz noise floor	-135 dB/Hz at 10 KHz; -140 dB/Hz noise floor	-150 dB/Hz at 10 KHz; -160 dB/Hz noise floor

BLILEY ELECTRIC COMPANY IS CERTIFIED FOR MIL-STD-2000 ON SOLDERED ELECTRICAL AND ELECTRONIC ASSEMBLIES

INFO/CARD 62

Design of Quadrature Detectors

by Edward A. Richley
Xerox Palo Alto Research Center

The quadrature detector is a very common circuit used for the demodulation of both wide band and narrowband FM. However, there is a general misconception about its method of operation, and little information on its proper design. After careful analysis, it can be seen that the engineering trade-offs involved in the design of a quadrature network are easy to understand and very interesting. This article will describe such an analysis, and will show the important considerations for proper design.

The basic single-tuned quadrature detector network is shown in Figure 1. This network is typically used with FM receiver ICs such as the Motorola MC3357 (and related parts), Signetics NE604, or the RCA CA3189. The network has one input and one output. The input generally comes from the output of a limiting IF strip. This input, V_{IN} , and the output of the network, V_{OUT} , are connected to the inputs of an analog multiplier.

The basic purpose of the quadrature network is to produce two signals which have a nominal phase difference of 90 degrees (hence the term "quadrature detector"), but with a variation in phase which depends on instantaneous frequency. The multiplier then serves as a phase detector, and can detect the lead or lag in phase caused by the interaction of the frequency modulated signal with the network.

In some versions of the circuit, the coupling capacitor, C_1 of Figure 1, is replaced by an inductor. The operation of the circuit is conceptually the same in both cases. Many texts give an explanation for the operation of this circuit which is based on the following assumption (1,2):

$$X_1(\omega_0) \gg R_L \quad (1)$$

where X_1 is the magnitude of the reactance of the coupling component, either a capacitor or an inductor, and ω_0 is the center frequency of the frequency modulated signal. ω_0 is also the resonant frequency of the network formed by L_L and C_L . With the assumption of equation 1, the nominal 90 degree phase shift is provided by the reactance of X_1 in series with a much smaller resistance, R_L . The subsequent phase lag or lead about the nominal will result from changes in the received signal frequency which cause the reactance of the R-L-C circuit to swing inductive or capacitive.

A quick look at some application notes, however, shows that the condition of equation 1 is often not met in practice. In fact, it is often strongly violated (3,4). Thus, the question arises as to how the nominal 90 degree phase shift is provided, and how the phase shift varies with frequency. In order to address this point of confusion, the network of Figure 1 must be examined more closely.

It is instructive to look at the network of Figure 1 in an alternate form. The dashed portion of Figure 2 can be transformed into a Norton equivalent, as shown in Figure 3. The resultant parallel capacitors combine as a single element of value $(C_1 + C_L)$. From Figure 3, it is evident that the nominal 90 degree phase shift can be guaranteed at the frequency ω_0 by simply making the combination of L_L and $C_L + C_1$ resonant

at ω_0 . Thus, the condition of equation 1 is not necessary. The size of C_1 relative to C_L does not affect the phase characteristics of the circuit at all, since the two capacitors are effectively in parallel. Their relative sizes only affect the amplitude of the output, and, as shall be seen later, the input impedance of the network. Thus, the condition of equation 1 is not necessary at all.

The Transfer Function

The circuit of Figure 1 has a transfer function, $H(j\omega)$, defined as the ratio of the output voltage to the input voltage, when both are expressed in phasor notation:

$$H(j\omega) = \frac{V_{OUT}(j\omega)}{V_{IN}(j\omega)} \quad (2)$$

From the equivalent circuit of Figure 3, it is easy to show that $H(j\omega)$ is determined by the impedance of the R-L-C circuit, and is given by:

$$H(j\omega) = - \frac{\omega^2 C_1 L_L R_L}{R_L(1 - \omega^2 L_L(C_1 + C_L)) + j\omega L_L} \quad (3)$$

There are four main concerns regarding the design of the quadrature network. These are as follows:

1. $|H(j\omega_0)|$ should be as large as possible.
2. The variation in $|H(j\omega)|$ over the desired range of frequency deviation should be as low as possible.
3. The phase variation in $H(j\omega)$ over the desired range of frequency deviation should be as linear as possible.
4. The input impedance of the network must be sufficient so as to not load the driving circuit.

In order to simplify the investigation of each of these requirements, it is useful to define some quantities. The first of these is the loaded Q of the network:

$$Q = \frac{R_L}{\omega_0 L_L} \quad (4)$$

In this analysis, any load resistance due to the phase detector input is lumped into the resistance R_L .

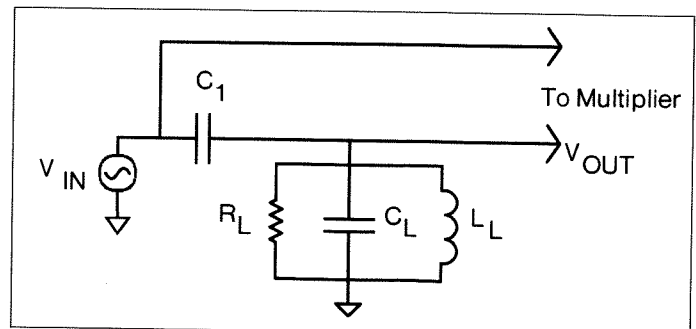


Figure 1. Basic single tuned quadrature detector network.

Another useful quantity is the center frequency, ω_0 . As described earlier, component values are chosen for resonance at ω_0 , so that:

$$\omega_0^2 = \frac{1}{L_L(C_1 + C_L)} \quad (5)$$

Finally, the frequency, ω , can be normalized to ω_0 by defining a new quantity, γ , as follows:

$$\gamma = \frac{\omega}{\omega_0} \quad (6)$$

In terms of these quantities, the transfer function is given by:

$$H(j\omega) = - \frac{C_1}{C_1 + C_L} \frac{\gamma^2 Q}{(1 - \gamma^2)Q + j\gamma} \quad (7)$$

From equation 7 it follows that the magnitude of the transfer function at the center frequency ($\gamma = 1$) is given by:

$$|H(j\omega_0)| = \frac{C_1 Q}{C_1 + C_L} \quad (8)$$

From equation 8 it is clear that for greatest magnitude of $H(j\omega_0)$, both Q and C_1 should be as large as possible. However, once C_1 is made comparable to C_L there is not much to be gained from increasing it further.

It is also useful to define the normalized frequency, γ , in terms of the deviation, ξ :

$$\gamma = 1 + \xi \quad (9)$$

In terms of ξ , the transfer function is :

$$H(j\omega) = - \frac{C_1}{C_1 + C_L} Q \frac{(1 + \xi)^2}{(-\xi(2 + \xi))Q + j(1 + \xi)} \quad (10)$$

The Amplitude Response

In order to examine the flatness of the amplitude response with frequency, it is helpful to look at the magnitude squared of the transfer function:

$$|H(j\omega)|^2 = \left(\frac{C_1}{C_1 + C_L} \right)^2 Q^2 \frac{(1 + \xi)^4}{Q^2 \xi^2 (2 + \xi)^2 + (1 + \xi)^2} \quad (11)$$

This expression can be expanded in terms of ξ about the center frequency, $\xi = 0$:

$$|H(j\omega)|^2 = \left(\frac{C_1}{C_1 + C_L} \right)^2 Q^2 (1 + 2\xi + (1 - 4Q^2)\xi^2 + \dots) \quad (12)$$

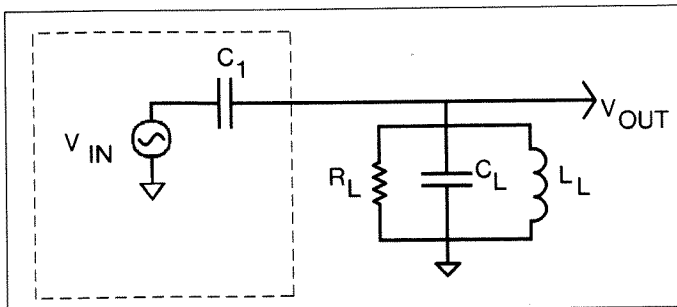


Figure 2. The quadrature network redrawn.

From equation 12 it is clear that in order to prevent AM distortion from becoming induced on the detector, it is necessary that:

$$|\xi| \ll \frac{1}{2} \quad (13)$$

and that:

$$4Q^2|\xi|^2 \ll 1 \quad (14)$$

In general, $|\gamma|$ is quite small (0.01 is typical) so that both of these requirements will be met for modest values of Q .

The Phase Response

The phase response can be examined in a similar manner. Equation 10 leads to the following expression for ϕ , the phase of the transfer function, $H(j\omega)$:

$$\phi = \arctan \left(\frac{(1 + \xi)}{\xi(2 + \xi)Q} \right) \quad (15)$$

Since the nominal value of ϕ is known to be 90 degrees ($\pi/2$), it is most useful to look at the deviation in ϕ about this mean. This deviation, θ , is given by:

$$\theta = \phi - \frac{\pi}{2} = - \arctan \left(\frac{\xi(2 + \xi)Q}{(1 + \xi)} \right) \quad (16)$$

The linearity of the phase response of the network can be evaluated by looking at the quantity $\partial\theta/\partial\xi$. From equation 16, it follows that:

$$\frac{\partial\theta}{\partial\xi} = -Q \frac{2 + 2\xi + \xi^2}{1 + 2\xi + (4Q^2 + 1)\xi^2 + 4Q^2\xi^3 + Q^2\xi^4} \quad (17)$$

This expression can be expanded in terms of ξ to give:

$$\frac{\partial\theta}{\partial\xi} = -2Q(1 - \xi + \frac{1}{2}(3 - 8Q^2)\xi^2 + \dots) \quad (18)$$

In order to maintain a linear phase response, it is important for the constant term in equation 18 to be the dominant term. Thus, the requirement for phase linearity can be expressed as follows:

$$|\xi| \ll 1 \quad (19)$$

and

$$4Q^2|\xi|^2 \ll 1 \quad (20)$$

These requirements can be seen to be almost identical to the requirements of equations 13 and 14.

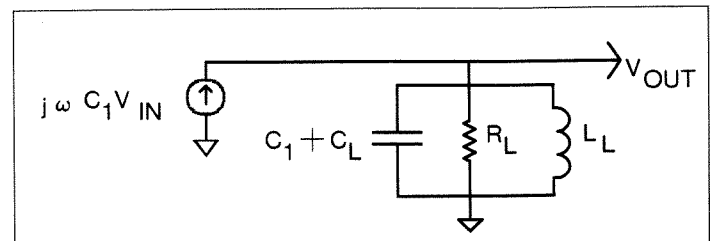


Figure 3. Norton equivalent of the quadrature network.

The Input Impedance

The remaining requirement has to do with the input impedance of the network. The magnitude of the impedance of the network of Figure 1, at the center frequency, ω_0 , as seen by V_{IN} , is:

$$|Z_{IN}(\omega_0)| = \omega_0 L_L \frac{\sqrt{Q^2 + \left(\frac{C_1 + C_L}{C_1}\right)^2}}{1 + Q^2 \left(\frac{C_1}{C_1 + C_L}\right)^2} \quad (21)$$

For even modest values of Q , and for values of C_1 which approach C_L (which is encouraged from equation 8), $|Z_{IN}(\omega_0)|$ approaches the following form:

$$|Z_{IN}(\omega_0)| \rightarrow \frac{\omega_0 L_L}{Q} \quad (22)$$

Clearly, a large enough value of Q and a small enough value of L_L could lead to an input impedance which is too low to be driven from the IF output. This consideration places a limit on the size of Q or the size of C_1 relative to C_L .

Design Procedure

Consideration of all of these constraints leads to a reasonable approach to the design of these single tuned quadrature networks. As with most engineering problems, there are trade-offs to be made. In general, the following procedure should suffice:

1. Choose frequency deviation or center frequency such that $|\xi| \ll 1/2$.
2. Choose Q as large as possible, without violating the requirement: $4Q^2 |\xi|^2 \ll 1$.
3. Choose the largest value for L_L which can be obtained within the limits of physical size, self-resonance, and the effects of its unloaded quality factor on Q .
4. If $(\omega_0 L_L / Q)$ is an acceptable value for input impedance, choose a value for C_1 which about is half the capacitance needed for resonance with L_L at ω_0 . Let C_L be the remaining capacitance needed for resonance.
5. If $(\omega_0 L_L / Q)$ is not acceptable, choose a value for C_1 which provides an acceptable value for $|Z_{IN}(\omega_0)|$, from equation 21. Choose a value for C_L which completes the requirement for resonance with L_L at ω_0 (equation 5).

This procedure should work well for most designs. It will provide the largest possible output level without sacrificing other parameters. Equations 8, 9, 12, 18, and 21 provide some quantitative insight into the behavior of signal tuned quadrature detectors. Although this analysis has been carried out for

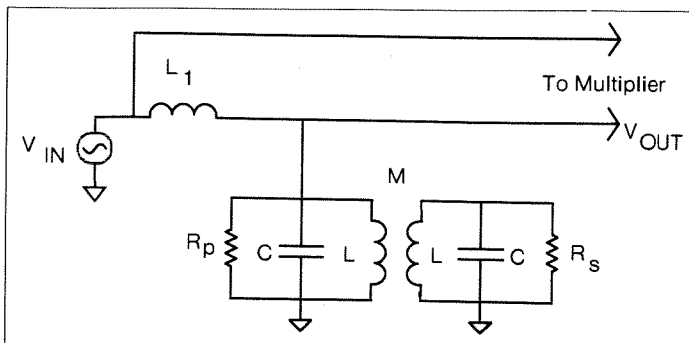


Figure 4. The double tuned quadrature network.

capacitive coupling, it must be emphasized that a similar exercise could be performed for a circuit using an inductor in place of C_1 .

The Double Tuned Quadrature Detector

There is a higher performance version of the quadrature network which is often described in application notes (4,5). This is the double-tuned network which is shown in Figure 4. Much better linearity is claimed for this network.

This network uses a weakly coupled transformer having a tuned primary and a tuned secondary. In most implementations, both windings are identical. In Figure 4, both windings are shown to have an inductance, L . The amount of mutual inductance, M , is always a fraction of L . Thus:

$$M = kL, \quad k < 1 \quad (23)$$

where k is known as the coupling coefficient.

Instructions in various application notes indicate that the coupling coefficient, k , should be at least 70 percent of critical coupling, k_{cr} , where k_{cr} is defined in terms of the primary Q , Q_p , and the secondary Q , Q_s , as follows:

$$k_{cr} = \frac{1}{\sqrt{Q_p Q_s}} \quad (24)$$

Instructions also indicate that the primary is to be tuned for maximum signal, while the secondary is to be tuned for maximum linearity.

An analysis of the double tuned network will now be presented. This analysis will focus on the phase response of the network, as that is the important advantage of a double tuned network when compared with the single tuned network. An analysis of the amplitude response and the input impedance can be derived easily from this phase response analysis, and so will not be presented.

Some Approximations

The double tuned network is significantly more complicated and difficult to analyze than the single tuned network. Consequently, some assumptions and approximations will be used. These approximations are extremely plausible and serve to greatly enhance the understanding of the analysis. In fact, the analysis of the single tuned network would be greatly simplified by these approximations and would yield exactly the same result as equation 20.

The first assumption is simply that the maximum frequency deviation is very small. Thus, it is assumed that:

$$|\xi| \ll 1 \quad (25)$$

In comparison with terms of order 1, ξ can be ignored. Of course, one must be very careful to not ignore ξ when subtraction of large numbers will result in a term of the order ξ .

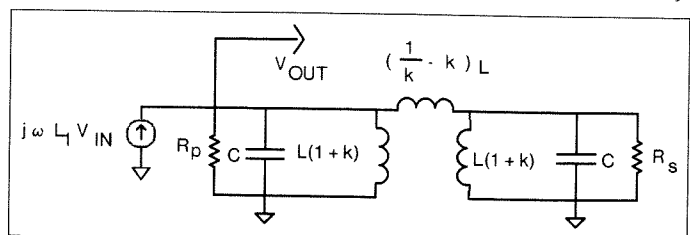


Figure 5. Equivalent of the double tuned quadrature network.

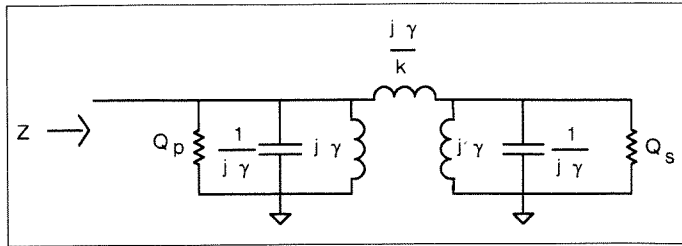


Figure 6. Approximation of the double tuned quadrature network.

Furthermore, it is assumed that the Q of both primary and secondary are large:

$$Q_s \gg 1, \quad Q_p \gg 1 \quad (26)$$

From these assumptions, and the definition of k_{cr} , it is clear that:

$$k \ll 1 \quad (27)$$

Equivalent Circuit

An equivalent circuit can be made for the double tuned network of Figure 4. This is shown in Figure 5. This equivalent will yield exactly the same output as the original circuit. The transfer function is determined once again by the input impedance of this network.

Only an analysis of the phase response of the double tuned network will be given here. Clearly the variation in the phase of the transfer function, about the 90 degree point, is given by the phase of the input impedance of the network. Just as with the single tuned network, the coupling element provides the initial 90 degrees of phase shift while the tuned network provides the deviation. Thus, the phase of interest is simply the phase of the input impedance.

Figure 6 shows this input impedance as Z , with the impedance of all elements normalized to $\omega_0 L$. Simplification is provided by the use of equation 27. This simplified approximate network clearly consists of two networks in parallel. Figure 7 shows these two networks distinctly. Clearly, the admittance of the combined network Y , is simply the sum of the two admittances, Y_1 and Y_2 . The admittance, Y , is just as useful for determining the phase response of the network as the impedance, Z , because Y and Z are reciprocals of each other. Thus, the variation component of phase response is simply the negative of the phase of Y .

Using equation 25, it is easy to show that, to a very good approximation sufficiently close to the center frequency, the admittance, Y_1 , is given by:

$$Y_1 = \frac{1}{Q_p} + 2j\xi \quad (28)$$

Similarly, the admittance, Y_2 , can be well approximated by:

$$Y_2 = k \frac{1 + 2jQ_s\xi}{Q_s(k - 2\xi) + j} \quad (29)$$

These forms for the admittances, Y_1 and Y_2 , assume that the tuned circuits of Figure 7 are tuned for resonance at $\xi = 0$. This is not necessarily the case. In fact, some degree of mistuning will yield the desired results. This mistuning can be represented by replacing ξ with $(\xi - \xi_1)$ in equation 28 and $(\xi - \xi_2)$ in equation 29. Thus, the total admittance, Y , is given by:

$$Y = \frac{1}{Q_p} + 2j(\xi - \xi_1) + k \frac{1 + 2jQ_s(\xi - \xi_2)}{Q_s(k - 2(\xi - \xi_2)) + j} \quad (30)$$

This detuning accounts for several effects. Slight differences in winding inductance, the loading effects of the coupling

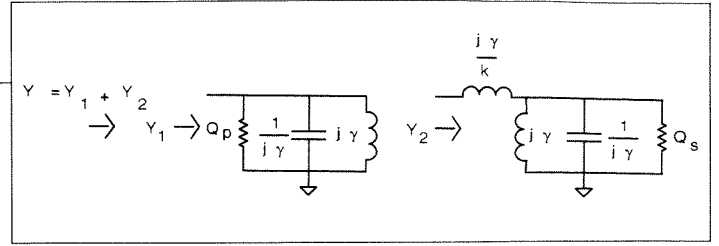


Figure 7. Simplified double tuned quadrature network.

element, L_1 , and the approximation made by replacing $L(1 + k)$ if Figure 5 with L in Figure 6 are a few of these effects. In general, the quantities ξ_1 and ξ_2 allow two more degrees of freedom for optimizing the transfer function.

The Phase Response

The trouble with the single tuned network is that once it has been tuned for nominal 90 degree phase shift, the transfer function is completely determined. Basically, the phase shift in a single tuned network is determined to be $\arctan(2Q\xi)$. There is no such limitation in the double tuned network. If the argument of the $\arctan()$ function could be made to more closely resemble the $\tan()$ function, a more linear phase relationship would be possible. This is exactly what the double tuned circuit allows. In order to see this more clearly, it is important to look at the Taylor expansion of the function $\tan(ax)$:

$$\tan(ax) = ax + \frac{a^3x^3}{3} + \frac{2a^5x^5}{15} + \dots \quad (31)$$

where a is some constant. For the purpose of this analysis, it is clearly desirable to have:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = \tan(a\xi) \quad (32)$$

In practice, the best that can be obtained is an approximation to equation 32 for some range of ξ . If this relation can be approximated, the \arctan function performed by the phase detector would more closely reflect a linear relation with input frequency. Several requirements on Y are immediately clear:

$\text{Im}(Y)$ must vanish as ξ goes to zero. The ratio $\text{Im}(Y)/\text{Re}(Y)$ must have no even order terms. The coefficients of $(a\xi)$ should match those in the expansion of equation 31 through as many terms as possible.

The first two of the above requirements can be met by proper choice of ξ_1 and ξ_2 . Although not easy to derive, it is easy to verify that the choice of $\xi_1 = \xi_2 = -k/2$ satisfies both. Inserting this condition into equation 30 leads to:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = 2\xi Q_p \left(\frac{(1 - k^2 Q_s^2)}{(1 + k^2 Q_s Q_p)} \right) \left(\frac{(1 + \frac{4Q_s^2}{1 - k^2 Q_s^2} \xi^2)}{(1 + \frac{4Q_s^2}{1 + k^2 Q_s Q_p} \xi^2)} \right) \quad (33)$$

This expression clearly has no terms in even powers of ξ . It also goes to zero as $\xi \rightarrow 0$. The polynomial quotient can be expanded to give the complete power series:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = 2\xi Q_p \frac{(1 - k^2 Q_s^2)}{(1 + k^2 Q_s Q_p)} \left[1 + 4Q_s^2 \frac{k^2 Q_s (Q_s + Q_p)}{1 + k^2 Q_s (Q_p - Q_s) - k^4 Q_s^3 Q_p} \xi^2 + \dots \right] \quad (34)$$

The coefficient of the third order term in the Taylor expansion of $\tan(ax)$ can be matched by making:

$$\frac{1}{3} 4Q_p^2 \frac{(1 - k^2 Q_s^2)^2}{(1 + k^2 Q_s Q_p)^2} = 4Q_s^2 \frac{k^2 Q_s (Q_s + Q_p)}{1 + k^2 Q_s (Q_p - Q_s) - k^4 Q_s^3 Q_p} \quad (35)$$

This defines a relation between k , Q_s , and Q_p . For example, if $Q_s = Q_p = Q$, the requirement of equation 35 can be found to be simply that $kQ = 0.327$. For $Q_s \neq Q_p$, the opportunity to make more terms in the expansion coincide, at least approximately, is available.

The data sheet for the RCA CA3189 (4) indicates that a preferred circuit uses $Q_s = 20$, $Q_p = 55$, and k is at least 70 percent of k_{cr} . Application of equation 35 leads to a value of 0.0229 for k . This is roughly 76 percent of k_{cr} , precisely as indicated by the data sheet. Although this choice does not give a good match for the term in ξ^5 , it gives a much better coefficient for that term than could be obtained from the choice of $Q_s = Q_p = Q$.

In general, for quadrature network design, the phase response, amplitude response, and input impedance are the important considerations. Of these quantities, the one most often overlooked is input impedance. It is clear from this analysis that as the output impedance of the limiting IF is lowered, its drive capability is increased. With proper design, a greater output signal from the quadrature network can be provided. Finally, the double tuned network can be used to greatly improve the linearity of the demodulator. Proper design of the double tuned network can be a bit tedious, as several

terms in the power expansion of equation 34 should be carefully evaluated. However, it is fairly easy to get a good match through the third order term.

Although the quadrature detector is a very popular device for the demodulation of FM, the literature contains very little information on its operation or design. This analysis provides the fundamental relations needed for the proper design of quadrature networks. The relations derived here provide the RF engineer with a means for optimizing the design of quadrature detectors.

RF

References

1. Henry Stark and Franz B. Tuteur, *Modern Electrical Communications*, Prentice-Hall, 1979.
2. William Gosling, *Radio Receivers*, Peter Peregrinus, Ltd., 1986.
3. Motorola, Inc., *Motorola Linear/Interface Devices*, 1988.
4. RCA Corporation, *RCA Integrated Circuits for Linear Applications*, 1986.
5. Sprague Electric Company, Semiconductor Division, *Integrated Circuits Data Book*, 1982.


About the Author

Edward Richley works in the Computer Science Laboratory at Xerox Corporation. He may be reached at Xerox Corp., Palo Alto Research Center, 3333 Coyote Hill Road, Palo Alto, CA 94304. Tel: (415) 494-4410.

RSG-10 SIGNAL GENERATOR

The \$2495 profit generator.

**NOW
SHIPPING!**

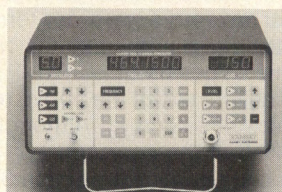

Quality crafted In the USA



Finally, a synthesized signal generator that's designed to help you generate more than just signals. The Ramsey RSG-10, is the signal generator you can afford, the signal generator that's designed to do what a signal generator is meant to do—provide a very stable, accurate, easy to control signal from 100 KHz to 1.0 Ghz.

For the price, you wouldn't expect any more. But, there is more to the

RSG-10. An intelligent micro-processor controlled/programmable memory, for example, can store up to 20 of your most commonly used test set-ups. And unlike other units, just one touch of the memory exchange button is all it takes to quickly shift from one test set-up to another. You get more work done, easier and faster.

At \$2495, the Ramsey RSG-10 is your profit generator.

RAMSEY

RAMSEY ELECTRONICS
793 CANNING PARKWAY, VICTOR, NY 14564
FAX: (716) 924-4555
TELEX: 466735 RAMSEY CI




ORDER DIRECT—CALL 716-924-4560

Why engineers have relied on TTE filters for over 35 years

- Over 1,239,580 standard filters
- Custom designs at stock filter prices
- 10 day shipment guaranteed
- 72 hour prototype service is available
- Unconditional factory guarantee

Got a problem? Call our Engineering Hotline.

(213) 445-2796

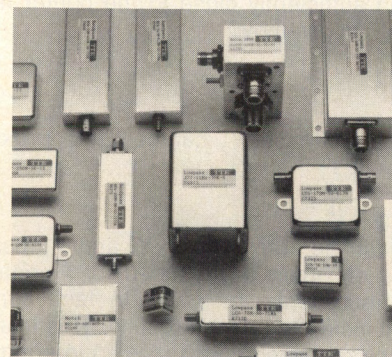

TTE®

America's Filter Specialist

T T E, Inc.
West Los Angeles, CA

(213) 478-8224
FAX: 1-800-473-2791
or (213) 445-2791

CAD of Single and Tandem Lange Couplers

Timothy O'Connell and Patrick Murphy
University College Cork, Ireland

In recent times the 90 degree hybrid has become one of the most important passive elements to be used in microwave integrated circuits (MICs), because of its important function in balanced mixers, balanced amplifiers, and other circuits. Although there are many types of hybrids available that provide equal power division with 90 degree phase shift, the Lange coupler has been the most widely used because of its superior broadband performance. This article describes a CAD program which calculates the design parameters of Lange couplers. Since the main disadvantage of Lange couplers is their difficulty in fabrication due to the very small dimensions of the interdigitated fingers, the concept of combining couplers in tandem is presented, and this option is incorporated into the CAD program.

Since its introduction by Julius Lange in 1966 the Lange coupler (1) has been the most widely used 90 degree hybrid at microwave frequencies because of its very wideband -3 dB coupling over octave bandwidths. The structure of the device, shown in Figure 1 is relatively simple, with alternate interdigitated fingers coupled together using bond wires. For this structure:

S is the spacing between interdigitated fingers.

W is the width of the interdigitated fingers.

L is the width of the coupler; $1/4$ wavelength at the center frequency.

h is the substrate thickness of the microstrip.

To date, the accepted design approaches are those reported by Presser (2) and Osmani (3), which are similar in nature and are suitable for CAD implementation. Their design approach may be summarized as follows:

The interdigitated directional coupler may be viewed as a multiconductor transmission line of K (K even) elements, not including the ground plane. However, coupling between non-adjacent sections may be neglected with little error. Using

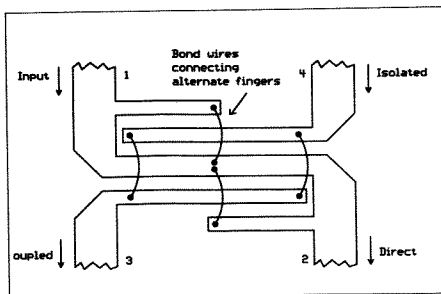


Figure 1. Diagram of a Lange coupler.

this simplification, Ou (4) derived the following set of equations for the even and odd mode impedances for such an array of parallel coupled lines.

$$Z_{oo} = Z_o \left(\frac{1 - C}{1 + C} \right)^{1/2} \frac{(K - 1)(1 + q)}{(C + q) + (K - 1)(1 - C)} \quad (1)$$

$$Z_{oe} = Z_{oo} \frac{C + q}{(K - 1)(1 - C)} \quad (2)$$

where,

K = even number of strips

Z_o = terminating impedance (usually 50 ohms)

C = voltage coupling coefficient

$$q = [C^2 + (1 - C^2)(K - 1)^2]^{1/2}$$

Next, the shape ratios are calculated from the synthesis equations of Akhtarzadm et al (5):

$$S/h = \frac{2}{\pi} \cosh^{-1} \left[\frac{\cosh\left(\frac{\pi}{2}(W/h)_{se}\right) + \cosh\left(\frac{\pi}{2}(W/h)'_{so}\right) - 2}{\cosh\left(\frac{\pi}{2}(W/h)'_{so}\right) - \cosh\left(\frac{\pi}{2}(W/h)_{se}\right)} \right] \quad (3)$$

$$W/h = \frac{1}{\pi} \cosh^{-1} \left[\frac{g + 1}{2} \cosh\left(\frac{(W/h)_{se}}{2}\right) + \frac{g - 1}{2} \right] - \frac{S}{2h} \quad (4)$$

where,

$$(W/h)'_{so} = 0.78(W/h)_{so} + 0.1(W/h)_{se} \quad (5)$$

and $(W/h)_{se,so}$ are given by Wheeler's equations for wide and narrow microstrip lines:

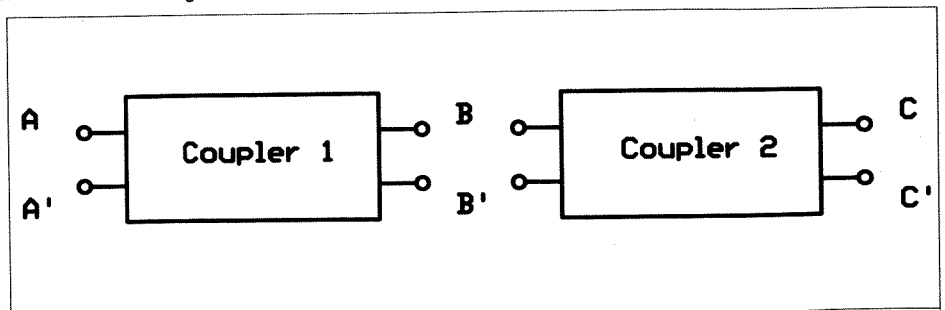


Figure 2. Couplers connected in tandem.

$$(W/h)_{se,so} = \frac{8}{p} \left[\frac{p(7 + 4/\epsilon_r)}{11.0} + \frac{11/\epsilon_r}{0.81} \right]^{1/2} \quad (6)$$

$$p = \left[e^{\left(\frac{Z_{00.06}}{84.8} \sqrt{\epsilon_r + 1} \right)} - 1 \right] \quad (7)$$

Tandem Lange Couplers

Although the design of Lange couplers is relatively straightforward using the above equations, their main disadvantage lies in the fact that the dimensions of the finger width (W) and spacing (S) are often so small that fabrication of the circuit is difficult. Typical dimensions for Lange couplers are of the order of 10 μm , and this can pose difficulties unless the fabrication process has very good tolerances. A novel solution is to combine two Lange couplers in tandem, so that the overall coupling coefficient is higher than the individual coupling coefficients. Therefore, since the dimensions are inversely related to the value of the coupling coefficients, the etching constraints are greatly reduced.

Consider two couplers connected in tandem as shown in Figure 2. Assuming the signal level at input A is 1, and is 0 and A', and that the coupling coefficient of each section is k, the signal level at the other ports are:

$$B = k \quad (8)$$

$$B' = j \sqrt{1 - k^2} \quad (9)$$

$$C = k^2 - (1 - k^2) \quad (10)$$

$$C' = j2k \sqrt{1 - k^2} \quad (11)$$

Here we can see that the 90 degree phase shift between C and C' is still preserved. Now for -3 dB power division, signals at C and C' must be equal. Therefore,

$$K^2 - (1 - k^2) = 2k \sqrt{1 - k^2} \quad (12)$$

Defining $l = k^2$ yields:

$$8l^2 - 8l + 1 = 0 \quad (13)$$

By solving this equation and discarding one of the solutions, we get $k = -8.34$ dB. Thus, to achieve an overall coupling factor of -3 dB, each of the two couplers connected in tandem

must have a coupling factor of -8.34 dB.

Therefore, two Lange couplers with coupling factors of -8.34 dB can be combined to make a -3 dB coupler with the same overall characteristics as a single coupler. The more loosely coupled individual sections will relax the etching constraints by increasing the dimensions of the coupled fingers. Figure 3 shows two Lange couplers connected in tandem.

The CAD Program

A FORTRAN CAD program has been written which enables the user to design Lange couplers using the equations above. Single or tandem configurations can be selected, depending on the dimensions obtained and the quality of the etching process available. Figure 4 shows the simulated Touchstone® response of the single and tandem couplers. While the response of the single coupler is marginally better, in some applications this slight deviation is much less than the discrepancy in results (with a single coupler) due to the etching tolerances of the process available.

Finally, the CAD program gives the user the option of producing an output file directly in the format of a Touchstone input file. This allows great flexibility in incorporating the Lange coupler into a larger circuit, or allows the mask of the circuit to be generated directly from software such as MICAD® or GAS-STATION®.

The operation of the program TLANG is described by the flowchart in Figure 5. First, the design parameters are entered; substrate dielectric constant, substrate thickness, center frequency, and overall coupling coefficient. If a tandem arrangement is selected, the program then calculates the coupling coefficient of each section. Next, the dimensions of the Lange coupler are calculated using the Osmani/Presser method, and finally, the results are produced either directly to the screen, or in the format of a Touchstone input file. Figure 6 shows a typical output of the TLANG program. Here a six finger tandem Lange coupler with a center frequency of 4 GHz has been designed on 5880 RT-Duroid® (0.79 mm substrate thickness).

The program is available from the RF Design Software Service, including a compiled version and source code listing. See page 30 for more information. **RF**

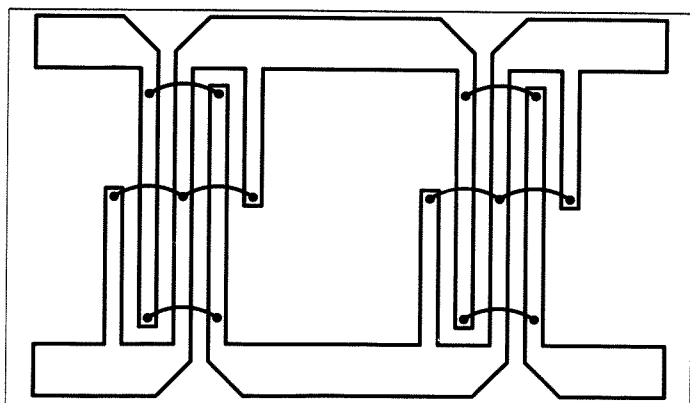


Figure 3. Tandem Lange coupler arrangement.

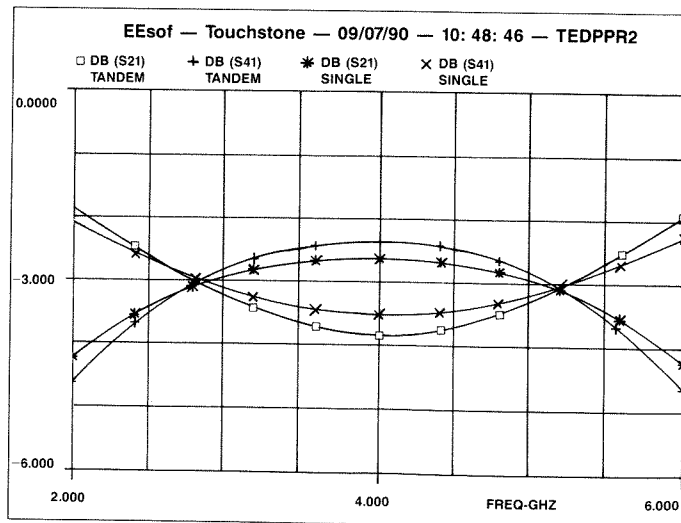


Figure 4. Simulated results of a single and tandem Lange coupler.

References

1. J. Lange, "Interdigitated Stripline Quadrature Hybrid," *IEEE Trans. on MTT*, December 1969, pp. 1150-1151.
2. A. Presser, "Interdigitated Microstrip Coupler Design," *IEEE Trans. on MTT*, October 1978, pp. 801-805.
3. R.M. Osmani, "Synthesis of Lange Couplers," *IEEE Trans. on MTT*, February 1981, pp. 168-170.
4. W.P. Ou, "Design Equations for an Interdigitated Directional Coupler," *IEEE Trans. on MTT*, February 1975, pp. 253-255.
5. S. Akhtarzed, et al, "The Design of Coupled Microstrip Lines," *IEEE Trans. on MTT*, June 1975, pp. 486-492.

About the Authors

Timothy O'Connell is currently working towards a Ph.D. in the area of "Microwave Components for Digital/Cellular Radio" at The Microwave Laboratory, University College Cork, Ireland. He completed his M.Eng.Sc. in 1989 and a B.E. with first class Honours in 1987. Dr. Patrick J. Murphy is Director of the Microwave Laboratory, University College Cork, Ireland. Both authors can be reached at telephone no. +353 21 276871 ext. 2214.

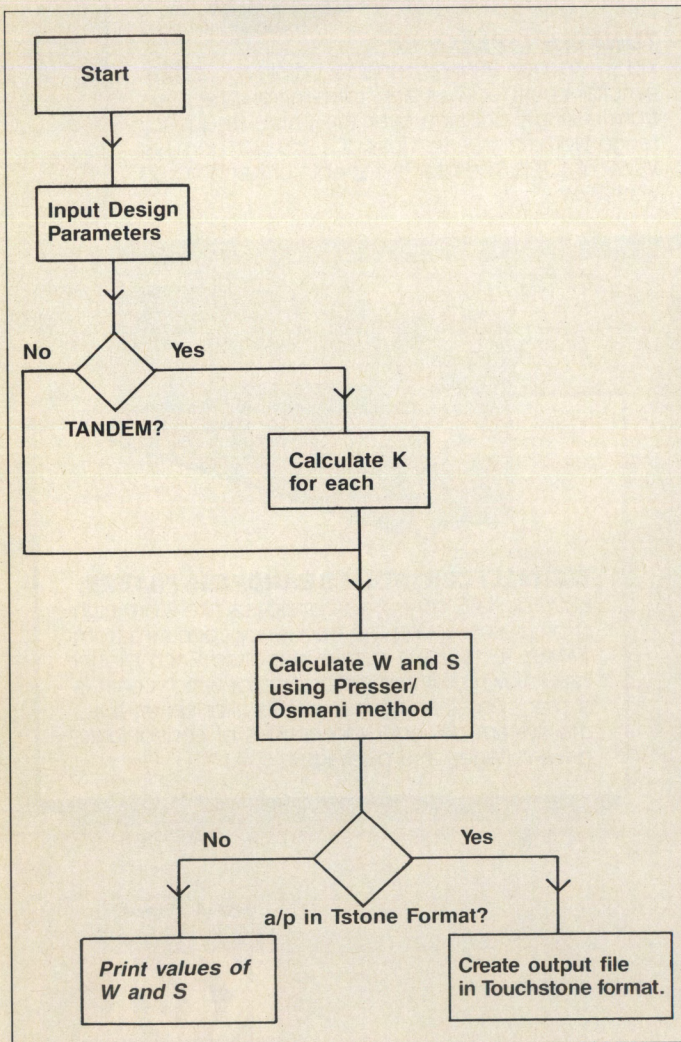


Figure 5. Flowchart of the TLANGE program.

```

DIM
FREQ GHZ
RES OH
IND NH
CAP PF
LNG MM
TIME PS
COND /OH
ANG DEG
  
```

```

CKT
MSUB ER= 2.20 H=0.79 T=.005 RHO=1 RGH=0
MLANG6 1 2 3 4 W=.253 S=.406 L=13.500
MLANG6 2 6 4 7 W=.253 S=.406 L=13.500
DEF4P 1 6 3 7 LNGE
  
```

```

OUT
LNGE DB[S21] GR1
LNGE DB[S41] GR1
  
```

```

FREQ
SWEEP 2.5 4.0 5.5
  
```

```

GRID
RANGE 2.5 4.0 5.5
GR1 0 -20 2
  
```

Figure 6. Touchstone file output from the TLANGE program.

Need Clock Oscillators or Crystals?

Think 800-333-9825

Quartz Crystals

50 KHz to 200 Mhz

TTL Clock Oscillators

250 KHz to 70 Mhz

HCMOS Clock Oscillators

3.50 Mhz to 50 Mhz

TTL and HCMOS Half Size and Surface Mount also available on request

**Fast Service -
3 weeks or less**


**Special frequencies
our speciality**

CAL CRYSTAL LAB, INC. • COMCLOK, INC.

1142 No. Gilbert, Anaheim, CA 92801 • FAX 714-491-9825

Tunable Filters

FROM K&L

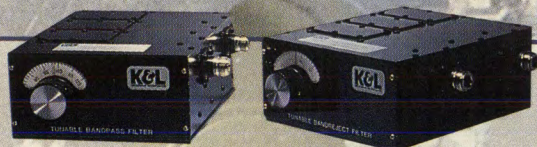

BANDPASS & BANDREJECT FILTERS:


With K&L's bandpass filters you can tune any center frequency over the 3-3,000MHz frequency range (1 octave per filter). These filters are available in either 3 or 5 sections, a VSWR of 1.5:1, and a low insertion loss of < 1 dB in the 5% 3dB bandwidth model.

Bandreject or "notch" filters have a 25-1,000MHz (1 octave per filter) frequency range, VSWR of < 1.2:1 and is capable of eliminating undesirable signals by greater than 50dB rejection.



HIGH Q BANDPASS FILTERS:

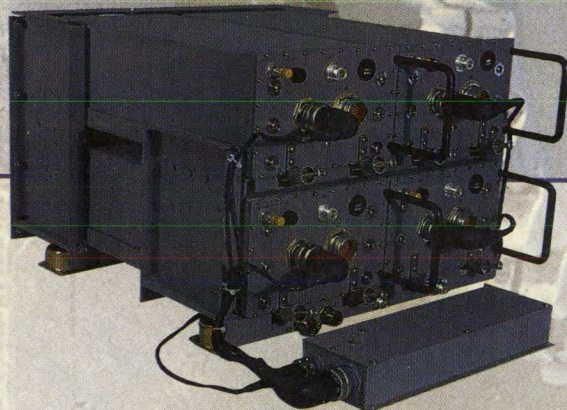Provides the answer to noise and interference signals found on co-located communication links. These filters feature 225-400MHz UHF or 100-163 MHz VHF frequency range capability. High selectivity of > 70dB, narrow 3dB bandwidth < 600KHz, VSWR < 1.5:1 and a typical tuning speed of 10 seconds.




MULTICOUPLERS:

Standard units cover the 225-400MHz UHF and 100-160MHz VHF frequency ranges. Both manually and digitally tuned models are available. Ground based or airborne modules of up to four units each.




TUNABLE DIPLEXERS:

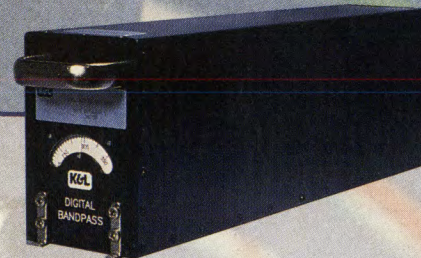K&L's 30 to 88MHz tunable diplexer allows simultaneous receiver and transmitter operation from a single antenna over the entire frequency range. Nominal insertion loss of 2.5dB with nominal VSWR of 1.75:1. The filter is capable of handling 50 watts C.W.



DIGITALLY CONTROLLED BANDPASS FILTERS:

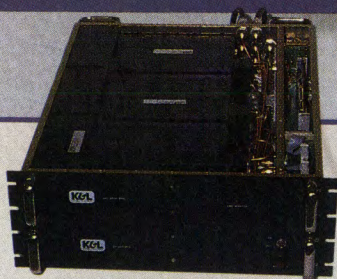K&L's digitally controlled bandpass filters are high Q devices covering the frequency spectrum from 24MHz to 18GHz, 1 octave per filter. Each model has its own built-in microprocessor which controls a precision stepping motor. This filter series gives the system designer the options of control logic, drive voltages and packages.



DIGITAL TRACKING FILTER NETWORKS:

K&L's digitally controlled tunable bandpass network has a 20-1500MHz frequency range, using a single controller. The network has a tuning accuracy of $\pm .25\%$ of tuned center frequency, a 5 section Chebychev response with 3 to 30dB shape factor of 2.2:1 and 3 to 50dB shape factor of 3.5:1 and RF/EMI moisture-sealed racks with 100dB isolation.

For A Partner...



A DOVER TECHNOLOGIES COMPANY

408 Coles Circle Salisbury, Md. 21801 • PHONE: 301-749-2424 • FAX: 301-749-5725 • TWX: 710-864-9683

A Clear Signal for RF Filters


By Liane G. Pomfret
Associate Editor

The market for RF filters is stable and growing with minor variations that can be linked to the current recession. As usual, the commercial market is enjoying greater success than the military market. Despite a worldwide economic slump, some of the best business is being generated internationally and has buoyed relatively flat domestic sales. Surface mount technology is also contributing to continued profits. With a host of new applications and new technology, there's little to stand in the way of a successful future for RF filters.

It comes as no great surprise that the military market for RF filters has suffered because of congressional cutbacks. While the cutbacks have not been disastrous, they have been noticeable and companies involved in military have felt the pinch. For companies who focus on the commercial market, business is much better. The recent explosion of commercial RF applications has opened up new business opportunities. The list of applications — wireless communications, PCNs, mobile and land mobile, data transfer, medical systems, and satellites — continues to grow. While much of this technology was developed for the military, it has found success within the commercial arena, making it doubly profitable for the manufacturers.

Not all of the technology evolved from military contracts. Some developments came from the commercial sector. Surface mount and miniaturization of RF filters are the results of requests for smaller commercial devices — the 2 pound cellular phone as opposed to the 7 pound cellular phone. Like much of the RF industry, surface mount technology is now working its way into the filter industry. Yet the military still lags behind. Arie Verhagen, Vice President of Marketing for Murata-Erie comments, "The industry as a whole, has to do their homework to bring surface mount to the military's attention." Qualifying new technology for military specifications is a long, expensive process and the industry is reluctant to invest time and money without assurances that the technology will be accepted.

In the commercial sector, suppliers

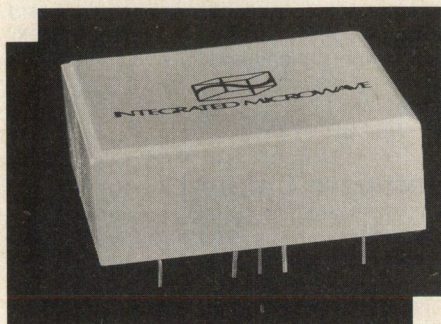

A switched filter module from Integrated Microwave.

have been reducing their prices while maintaining or improving quality. As a result, manufacturers have more latitude to experiment with manufacturing techniques and materials. Steve Sodaro, Vice President of Marketing and Sales at TTE notes, "Components now are not as costly. It affords us the opportunity to do miniaturization. We're always trying to miniaturize without sacrificing performance." However, while a large firm has the resources to experiment with technologies such as surface mount, smaller companies are often restricted because of the lack of available packaging technology within their company. Packaging technology is available from outside vendors but cost and availability are a stumbling block to in-house development.

The communications industry offers a large number of uses for filters. Voice communications, data transfer and acquisition, LANs, and voice over data are all demanding more sophisticated filtering techniques. "The applications for filters in general are increasing, mainly due to enhancements in telecommunications, LANs, and various radio systems including cellular and land mobile beyond the classic military market," says Dave Distler, Director of Sales and Marketing for Trilithic. Manufacturers are demanding extremely sophisticated filters capable of high reliability, high performance filtering.

Every company has its own area of specialty and responses will vary regarding the active areas for filter products. However, the general consensus is that communications equipment is the hot area right now. Randy Rhea, President of Eagleware notes, "We see a definite

increase in interest in filters for data communications systems and that often results in a greater emphasis in the delay characteristics of filters." Al Lowenstein, National Sales Manager, for Motorola's RF filter products components division, sees interest for their products in other areas as well. "The new activity is in the 915 MHz range, especially spread spectrum, new generation portable telephones, and remote data acquisition, meter reading and things along that line." He adds, "The other thing that is taking off is GPS and the satellite industry in general." Wavetek's focus has been high reliability communications such as those found in avionics communications systems. Even with the slowdown in the domestic military market, Sara Mussman, Components Business Unit Manager for Wavetek comments, "I see a significant amount of business out there."

A lot of this business is coming from the international sector. Mussman notes, "Any country that is aggressively pursuing an upgrade will be a good source of business." For George Szentirmai, President of DGS, business has been fairly flat. "The only thing is that our international sales are pretty strong especially in Europe." His company has had a great deal of interest from eastern European countries, but since there's no money available, there's been no sales. Werner Mueller, Vice President of KVG, North America comments, "I would hope that due to the reunification of Europe and due to the communication lack in eastern Europe, that there will be an increase in the European market." Toyocom's market situation is different. They currently hold less than 10 percent of the U.S. market and are looking to expand within the United States according to Dennis Reifel, Marketing Manager at Toyocom.

With the majority of the RF filter business on the upswing, the outlook for the future is optimistic. The advent of surface mount technology and constant improvements in price and performance make filters an excellent prospect for profit in the coming year. **RF**

For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600; ask for the Circulation Department.

RF software

SPICE Transistor Library

A comprehensive library of RF transistor SPICE models is available from Intusoft. Models include 36 popular bipolar and JFET transistors, usable with any Berkeley SPICE compatible simulator. The models use a subcircuit approach that accounts for package parasitics, and matches published S-parameter magnitude and phase data up to 5 GHz. The library is priced at \$99, and is available in PC and Macintosh formats.

Intusoft
INFO/CARD #233

Dielectric Resonators

Two programs with easy data input are available for analyzing dielectric resonators. The program DRESV3 computes the resonant frequency and the Q factor of the TE_{01d} mode. Program FOAM3 estimates the resonant frequencies of sixteen higher-order modes. Diskettes for the IBM PC or compatibles are priced at \$25.

Kajfez Consulting
INFO/CARD #235

Version 3.0 Introduced

EEsof announces the new Version 3.0 product suite, upgrading their line of high-frequency software tools. Version 3.0 links all

of EEsof's simulators under a single design environment; linear and nonlinear frequency domain, nonlinear transient SPICE analysis, and system/subsystem analysis. Its graphical design environment provides block diagram and schematic entry, multi-simulator control, documentation, and optional IC and board layout capability. Version 3.0 runs on UNIX-based workstations and PCs using the OS/2 operating system.

EEsof, Inc.
INFO/CARD #234

Software Catalog

A new eight page catalog presents simulation and synthesis CAE tools from Webb Laboratories. Included are the SysCad and Receiver Advantage system simulators, FilSolv and TransCad for filter and transmission line structure synthesis, and SANA for microwave network signal and noise analysis and optimization.

Webb Laboratories
INFO/CARD #232

Graphics-Based Analysis

DADISP is a visually-oriented graphics software package designed for scientific and technical applications. Among the 200 data processing functions are signal arithmetic and editing, waveform generation, FFTs, and

peak-finding. Extended memory support is an option, as is an IEEE-488 bus driver and an software module to interface with popular data acquisition boards. Versions are available for a wide range of PCs, workstations and larger computers.

DSP Development Corp.
INFO/CARD #231

SPICE Library for Linear ICs

SPICE macromodels are now available for nearly every Burr-Brown op amp, difference amp, and instrumentation amplifier. Two levels are offered: PSpice® Parts™ and Enhance Parts™ macromodels. A 5 1/4 inch diskette with more than 75 models is free from Burr-Brown.


Burr-Brown
INFO/CARD #230

Thermal Analysis

Version 1.33 of SAUNA, a 3-D thermal annalysis package has been released by Tatum Labs. Larger models are possible; up to 700 nodes and 2750 thermal resistors. Reduced air density due to altitude is also accoutned for. SAUNA runs on IBM PC compatible and Macintosh II and SE/30 computers.

Tatum Labs, Inc.
INFO/CARD #229

RF Circuit Designers

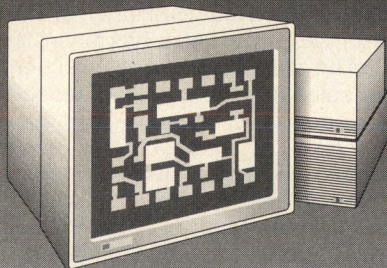

Mask Software CAD Translators

Reduce turnaround time and cut mask costs when you use our software postprocessors to directly photoplot board artwork. Stop cutting and peeling Rubylith®. Our postprocessors convert AutoCAD, EGS, Generic CADD, or Calma drawings into Gerber photoplotter code.

PHOTOPLOTTERS

ACS 500	DXF to Gerber
ACS 600	GDSII to Gerber
ACS 700	HP EGS to Gerber

TRANSLATORS

ACS 800	EGS to AutoCAD DXF
ACS 1000	MiCAD to AutoCAD
ACS 3500	AutoCAD to GDSII
ACS 3600	EGS to GDSII

Call or write for our application notes describing how to photoplot hybrid circuits directly from your CAD database.

ARTWORK CONVERSION SOFTWARE, INC.
1320 Mission St. #5, Santa Cruz, CA 95060
408/ 426-6163 Fax: 408/ 426-2824

INFO/CARD 67

RFdesign

REPRINTS
REPRINTS
REPRINTS
REPRINTS
REPRINTS
REPRINTS

RF Design reprints are available for printing in quantities of 500 or more.

For further information contact:

Reprint Department
RF Design
6300 S. Syracuse Way, Ste. 650
Englewood, CO 80111
(303) 220-0600

CRYSTAL FILTERS

• MONOLITHIC • DISCRETE •

TEMEX ELECTRONICS is a manufacturer of Crystal Filters, Discriminators, L/C Filters and Crystals. TEMEX designs to custom specifications as well as the 10.7 MHz and 21.4 MHz standards. We take pride in fast response and the support of our customers. • PHONE • FAX • MAIL •

TEMEX ELECTRONICS, INC.

5021 N. 55th Ave. #10 Glendale, Az. 85301

(Tel) 602-842-0159

(Fax) 602-939-6830

INFO/CARD 78

RF/Microwave Product Guide

Avantek offers a 48-page Product Selection Guide to give engineers a quick overview of the company's standard products. Summary specifications are provided for transistors, integrated circuits, amplifiers, signal processing and control products, LNAs, uplink amplifiers, cellular base amplifiers, and YIG oscillators. Most items are in stock at Avantek distributors.

Avantek, Inc.
INFO/CARD #250

Ceramic Filter Catalog

Murata Erie announces a design manual and catalog for their line of ceramic filters for communications. Single and multiple element filters are listed, covering standard frequencies such as 455 kHz, 3.58 MHz, 4.5 MHz and 10.7 MHz. Ceramic discriminators and signal detectors are also included, as are surface mount filters. Application information includes theory of operation and circuit design considerations.

Murata Erie North America
INFO/CARD #249

Frequency Control Products

Comprehensive data on products available from Piezo Technology, Inc. is included in a new 96-page handbook. Monolithic and discrete crystal filters, LC filters, cavity band-pass filters, combline filters, interdigital filters, crystal and non-crystal oscillators, precision crystal resonators, RF subassemblies, and custom hybrid circuits are listed.

Piezo Technology, Inc.
INFO/CARD #248

RF Data Book

Motorola's RF Products Division has released their new RF Data Book, DL110/D Rev. 4, a two-volume edition covering power FETs, power bipolar and small-signal transistors, plus RF power modules. 84 new products have been included since the previous version, along with new applications information.

Motorola, Inc.
INFO/CARD #247

Coaxial Switches

A new Standard Products Brochure is available from Dow-Key Microwave, listing standard electromechanical coaxial switches and relays in configurations from SPDT to SP12T. Transfer switches, bypass switches and low cost RF relays are also included. Photographs, specifications and schematic diagrams are provided for these products.

Dow-Key Microwave Corp.
INFO/CARD #246

1991 Test Instruments

Tektronix' 1991 customer catalog is now available, highlighting more than 3000 products in three broad areas: electronic test and

measurement instruments, professional broadcast equipment, and computer peripherals. New products include communication signal analyzers, VXIbus products, high resolution display monitors, HDTV test equipment and low cost broadcast spectrum analyzers.

Tektronix, Inc.
INFO/CARD #245

Coatings Brochure

A line of coating and ink systems is described in a new brochure from Emerson & Cuming. One and two-component systems are presented, used in making membrane switches, molded and flexible circuits, polymer thick film circuitry, and for modifying circuit boards. The coatings provide protection against electrical contact during component assembly.

Emerson & Cuming, Inc.
INFO/CARD #244

Frequency Chart Update

The RF Products and Linear Integrated Circuits Divisions of Motorola have published a new U.S. frequency allocation chart covering the RF spectrum up to 4000 MHz. Added to the previous version's allocation categories is a segment for Part 15 unlicensed devices. The chart is free, and is suitable for convenient wall mounting.

Motorola, Inc.
INFO/CARD #243

SAW Filter Note

A new Application Note discussing SAW coupled-resonator (CR) filters is available from RF Monolithics. SAW CR filters are suitable for many narrow-band applications from 70 MHz to 1500 MHz, and can be built with fractional bandwidths from 0.03 to 0.5 percent. The filters exhibit low loss (3 dB typical) under matched conditions. The note covers theory, operational performance limits, and a comparison with other filter technologies.

RF Monolithics, Inc.
INFO/CARD #242

Reconditioned Equipment

A catalog featuring reconditioned Philips/Fluke test and measurement equipment is announced by Rubytron. Oscilloscopes, synthesizers, frequency counters/timers, sweepers, function generators and pulse generators are among the equipment types available. All instruments are calibrated and warranted.

Rubytron Instruments
INFO/CARD #241

Distributor Catalog

Tektronix 1991 Distributor Products Catalog contains data on analog and digital oscilloscopes, frequency counters, digital multimeters and function generators. These products are offered through authorized distributors.

RAG Electronics, Inc.
INFO/CARD #240

No matter how you look at it...we've got the right GPS time and frequency receiver for you


- ✎ Event Time Logging Module provides precise time-tagging for power line fault locating systems
- ✎ Power line Voltage Phase Angle Module provides precise time-tagged 60-cycle phase angle measurement
- ✎ Network synchronization configurations support telecommunications master clock applications
- ✎ Integrated antenna/downconverter supports long cable feeds

Contact us **today** for complete literature and information. Find out how you can benefit from GPS and get with the leading edge of today's most sophisticated technology.


FTS / AUSTRON

Datum companies working together to meet your needs...

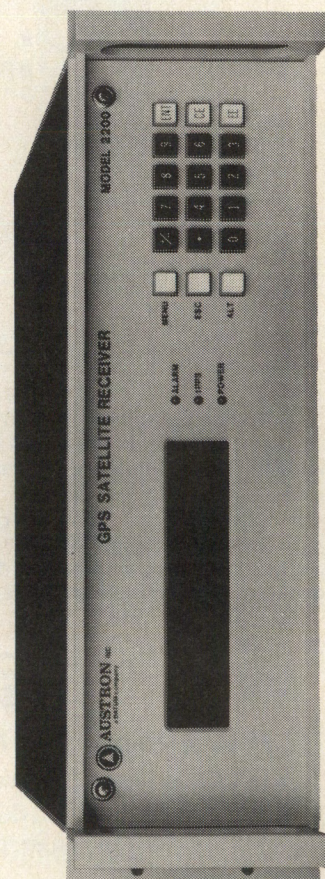P. O. BOX 14766 AUSTIN, TX 78761 ■ TEL (512) 251-2313 ■ FAX (512) 251-9685



JFW Rotary Attenuators

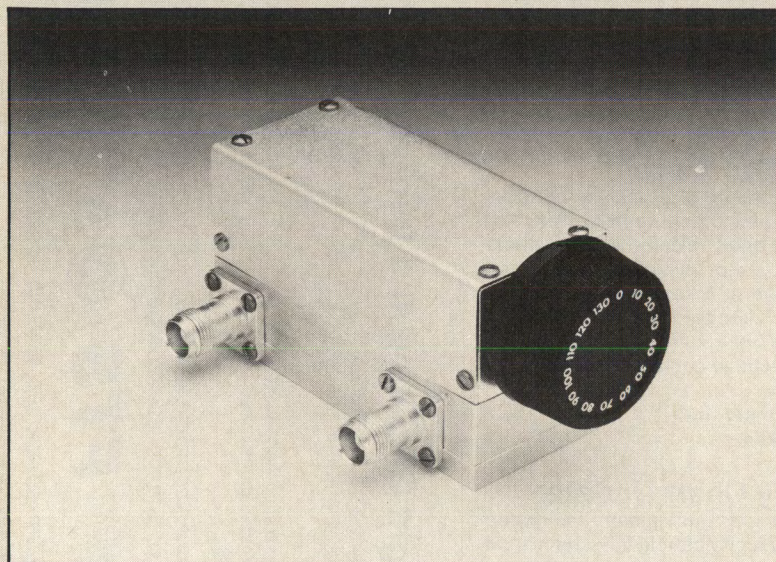


50R-002

Frequency Range: DC-1000 MHz
Attenuation Range: 0-130 in 10 dB steps
Connectors: BNC, N, TNC or SMA

50BR-008

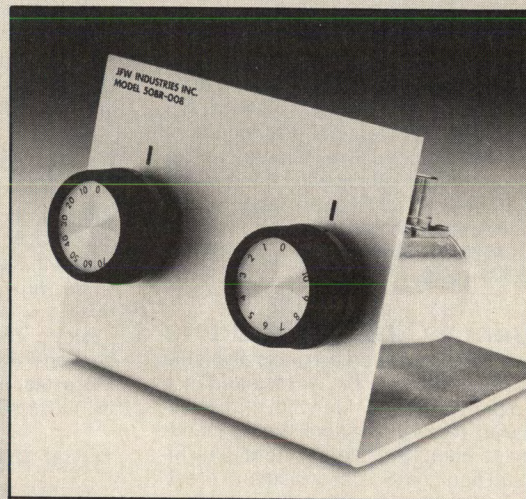Frequency Range: DC-2000 MHz
Attenuation Range: 0-80 dB in 1 dB steps
Connectors: BNC female (standard) SMA and N available upon request



50R-029 (left)

Frequency Range: DC-2000 MHz
Attenuation Range: 0-70 dB in 10 dB steps
Connectors: SMA female (standard) BNC available upon request

50R-019 (right)


Frequency Range: DC-2000 MHz
Attenuation Range: 0-10 dB in 1 dB steps
Connectors: SMA female (standard) BNC available upon request

50R-079 (left)
Frequency Range: DC-1000 MHz
Attenuation Range: 0-120 dB
Connectors: BNC female or "N" female

50R-080 (right)
Frequency Range: DC-1000 MHz
Attenuation Range: 0-12 dB
Connectors: BNC female or "N" female



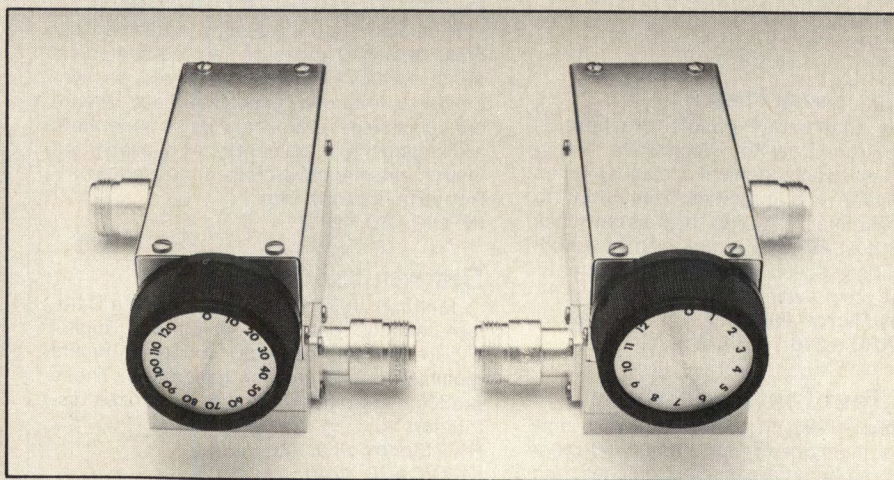JFW Industries, Inc.
5134 Commerce Square Dr.
Indianapolis, Indiana 46237
(317) 887-1340



Advertising Index

A&A Engineering	82	Kay Elemetrics Corp.	45
Adams Russell Electronics—		KVG	52
Anzac Division	18	Locus, Inc.	51
Advantest America, Inc.	33	Loral Microwave—Wavecom	2
Alan Industries, Inc.	17	M/A-Com Control	
Allen Avionics, Inc.	57	Components Division	20
American Technical Ceramics Corp.	19	M/A-Com Omni Spectra, Inc.	36
Amplifier Research	41	Maxim	13, 15
Amplifonix	27	Merrimac	49
Andersen Laboratories	88	Noise/Com, Inc.	7
Applied Specialties, Inc.	87	Oscillatek	8
Arrowsmith Shelburne, Inc.	42	Penstock Engineering, Inc.	51
Artwork Conversion Software, Inc.	78	Pole Zero Corporation	59
Avantek	34-35	Programmed Test Sources	22
Axon Corporation	82	QUALCOMM, Inc.	38-39
Bliley Electric Company	67	Quality Components, Inc.	54
Cal Crystal Lab, Inc.	75	Ramsey Electronics	72
California Eastern Laboratories	47	RF Design Software Service	30
CIR-Q-TEL Microwave	82	RF Neulink	21
Coilcraft	25	RF Prototype Systems	82
Comlinear Corporation	43	Somersoft	82
CTS Corp.	63	Sprague-Goodman	37
DAICO Industries, Inc.	4	Stanford Telecommunications	28
Dale Electronics	54	STC Components	64
Eagleware	50	Surcom Associates, Inc.	67
E.F. Johnson, Inc.	12	Teledyne Microwave	29
EG&G Frequency Products, Inc.	62	Temex Electronics, Inc.	78
Elcom Systems	8	Tesoft	65
ENI	32	Thomson—CSF	53
Epson America, Inc.	60	Time & Frequency, Ltd.	46
Fotofabrication Corp.	53	Trak Microwave Corporation	44
Frequency & Time Systems/Austron	79	Trilithic	31
Henry Radio	30	TTE, Inc.	72
Hewlett-Packard	12	Viewlogic Systems, Inc.	9
IFR Systems, Inc.	3	Voltronics Corporation	83-84
JFW Industries, Inc.	80	Wavecom	2
Johanson Manufacturing Corp.	57	Werlatone, Inc.	6
K&L Microwave	76	Wide Band Engineering	
Kalmus Engineering International, Ltd.	10-11	Company, Inc.	23

RF engineering opportunities

RF ENGINEERS

GEO-CENTERS, INC., a high technology, growth-oriented research and development company specializing in engineering and high-tech services for the U.S. Department of Defense, has the following immediate, full-time openings at our central New Jersey location:

Senior RF Engineer — to perform R&D on high stability frequency standards and clocks, including oscillator design and specifications; and resonator and oscillator testing. A PhD in EE or a related field and CAD/ATE experience are desirable. Must be a self-starter who is capable of independent and creative work in an R&D environment.

RF Engineer — to perform R&D on high stability frequency standards and clocks, including oscillator design, fabrication and specification; and resonator and oscillator testing. A BS in EE or a related field and CAD/ATE experience are desirable. Experience in data analysis, modern computational methods and good oral and written communication skills are necessary.

GEO-CENTERS, INC. offers competitive salaries, an outstanding benefits package and unlimited growth potential. To explore these positions, please forward your resume with salary requirements to: GEO-CENTERS, INC., Human Resources Dept. - RF, 762 Rt. 15 South, Lake Hopatcong, NJ 07849. An Equal Opportunity/Affirmative Action Employer. U.S. citizenship or permanent residency required.

YOU HAVE AS MUCH POTENTIAL AS WE DO— UNLIMITED. RADIO FREQUENCY ENGINEERS

When you're creating the world's most advanced cellular network, you need the most advanced Radio Frequency Engineers.

Among your varying responsibilities, you will evaluate subscriber traffic, present and future RF coverage and growth data to forecast system expansion and to provide optimal service for our customers. You will design the frequency plan, conduct testing on potential installation areas, assist the real estate group on potential cell and enhancer locations, and remain current on new technology and industry advancements.

The individuals we're seeking will have a Bachelor's degree in Electrical Engineering and two or more years of experience in the cellular or radio design industry.

Located in the Southern California community of Irvine, near recreational parks and the ocean, you'll enjoy many of the benefits that come from a progressive company, including a competitive salary, company wide bonus plan and an extensive benefits package. For immediate, confidential consideration, please send your resume with salary history to: PacTel Cellular, Dept. CR-RF/D, P.O. Box 19707, Irvine, CA 92713-9707. An Equal Opportunity Employer. Principals only, please.

PAC TEL.
Cellular

A Pacific Telesis Company

RFdesign

MARKETPLACE

WHEN YOU ARE READY TO BUY-SELL-TRADE CALL RF DESIGN MARKETPLACE
Increase your REVENUES with **RF Design Marketplace** advertising! Over 40,000 prospects read and buy from this section each month. To reach this sophisticated, targeted market call today **(303) 220-0600**.



450 MHz SPECTRUM ANALYZER
Adapted from Nov. 85 QST article
by Al Hellrick K2BLA

Complete Kit Only \$459.95
Assembled & Tested ... \$799.95

FEATURES: Three digit LED center frequency digital readout. 12 position calibrated scan width 1KHz to 50MHz. switchable bandwidth, wide = 300KHz, narrow = 10KHz. Use your low frequency scope for the display portion. Switchable 10KHz video filter. Variable IF attenuator, LOG output calibrated in 10 db steps.
CA residents add 6 1/2% sales tax. S&H \$6.50 (insured). Foreign orders add 15%.
For more info or price list send large SASE (\$2*) to:



A&A Engineering



2521 W. LaPalma #K • Anaheim, CA 92801 • 714-952-2114

INFO/CARD 70

For All Your RF / Microwave Prototyping Needs



RF PROTOTYPE SYSTEMS

QUICK BOARDS™ for:
PLL's, synthesizers, Avantek devices
Breadboarding • Evaluation

Free brochure! Call now

1-800-874-8037 (outside Calif.)

(619) 689-9715 FAX (619) 689-9733



INFO/CARD 71

CIR-Q-TEL
MICROWAVE

FILTERS OFF THE SHELF AND BY DESIGN

- BANDPASS, LOWPASS, HIGHPASS
NOTCH FILTERS TO 26.5 GHZ
- MINIATURES, CAVITIES, COMBINES
INTERDIGITALS AND TUBULAR
- MIL-STANDARD 2000

CIR-Q-TEL MICROWAVE

6600 VIRGINIA MANOR ROAD
BELTSVILLE, MD. 20705
(301) 470-2900 FAX # (301) 776-3882

INFO/CARD 72

SPREAD SPECTRUM COMMERCIAL DESIGNS

- Specialize in High Volume,
Low Parts Costing
- Long/Short Range
- 900 MHz / 2.4 GHz
- Complete RF Lab Facilities
- Patented, FCC Approved
Designs

AXONN CORPORATION

101 W. Robert E. Lee Blvd.,
2nd Floor
New Orleans, Louisiana 70124
(504) 282-8119

INFO/CARD 73

**BUY-SELL-TRADE
FOR ONLY
\$175/Mo.**

Call
Today

303-220-0600

RF SYNTHESIS SOFTWARE

Smithsoft Plus by Somersoft

PC Software for Every RF Engineer

INTERACTIVE SMITH CHART

Data are entered directly onto the chart by using the mouse, keyboard, or by loading a disk file. Component arcs, including parasitic effects, are drawn on the chart by making component selections from the top menu bar. A schematic is automatically generated and displayed as components are selected. Once a circuit is entered, the circuit editor allows you to randomly tune, cut, copy or paste any component. This makes it very easy to experiment with many different kinds of circuit topologies in order to achieve the best design. This also makes the software very educational for those who are just learning the Smith chart.


... PARTIAL LIST OF FEATURES ...

Network Analyzer Z-Theta Chart
H, S, Y, Z, ABCD Conversions
Common B ↔ Common E ↔ Common C
Simultaneous Multiple File Analysis
Operating and Available Power Gain Circles
Unilateral Power Gain Circles
Noise Circles Stability Circles
S-Parameter Stack for Recursive Operations
Data Tables on Screen or Dump to Printer
Internal Graphic Screen Dump

\$259.00, Somersoft, (707) 829-0164

INFO/CARD 74

The Betta Better Bender

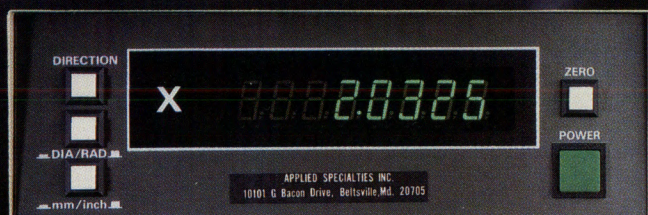

Model 04
\$5995^{US}
10 Day Delivery

- ▶ **Simple**
- ▶ **Economical**
- ▶ **No Programming**
- ▶ **.086 to .250 Dia.**
- ▶ **3 Day Free Trial**


Distributed exclusively by:



**RF & Microwave
Supermarket**

APPLIED SPECIALTIES INC.

Beltsville, MD 20705	(301) 595-5395	Toll Free (800) 950-8555
Baltimore, MD	(800) 950-8555	FAX 24 Hr. (301) 595-0050
Largo, FLA 33541	(813) 530-7309	Toll Free (800) 722-4599
Campbell, CA 95008	(408) 370-2644	FAX 24 Hr. (408) 370-0380

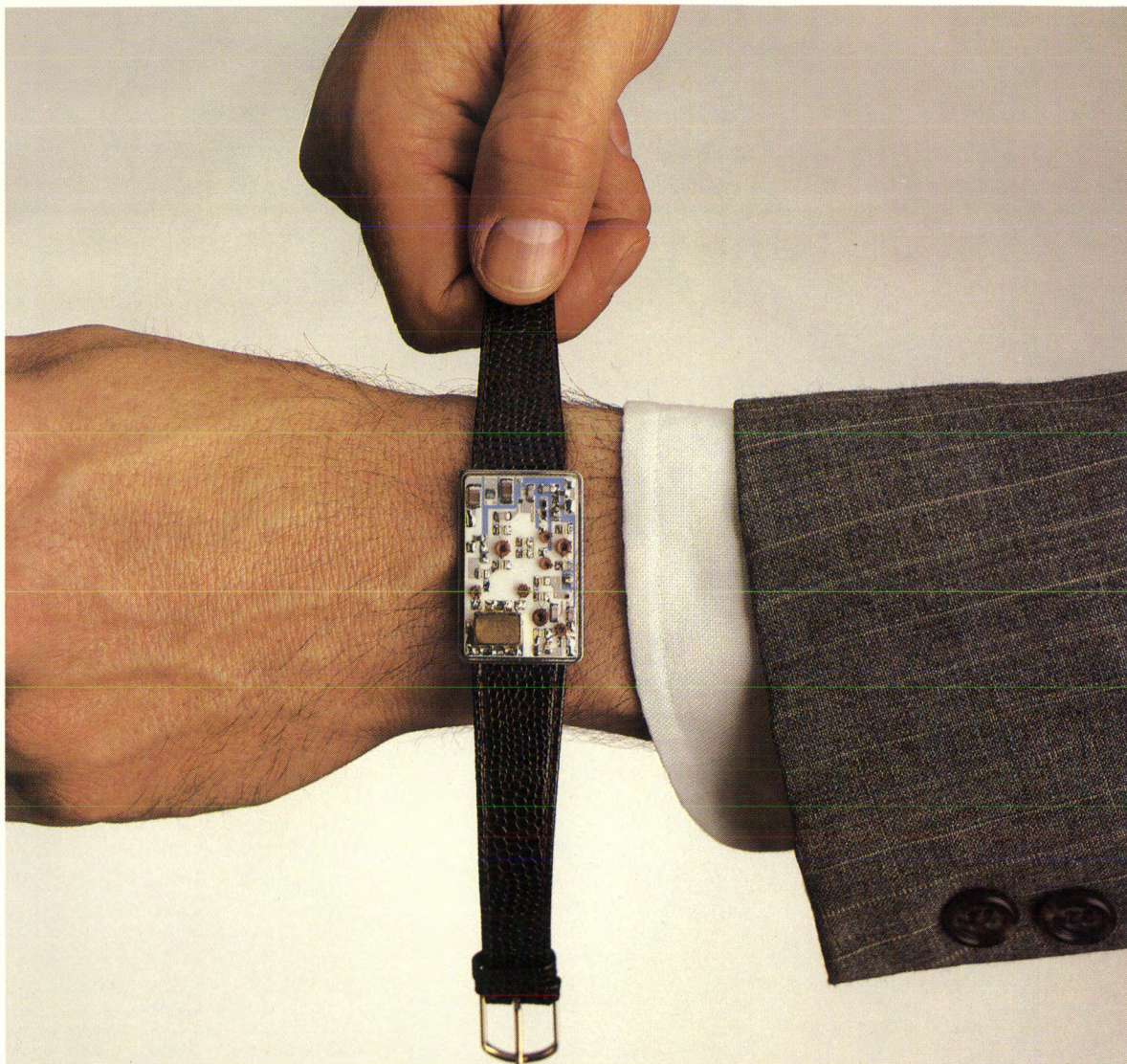

**You can't buy
a better precision
timepiece for
under 2.4 GHz.**

If you're operating in a frequency range from 100 MHz to 2.4 GHz, you can't buy a better oscillator than an Andersen VCO. It gives you the highest spectral purity with the lowest spurious ($> -60\text{dB}$). And typical single sideband phase noise of $> -119\text{dBC @1 KHz offset}$.

It's compact. It's rugged. It operates in temperatures up to 100°C . It can be tuned up to 1.5 MHz or phase-locked to a reference. Plus, its low mass and low profile make it ideal for surface-mount technology, DILS or flatpaks.

Isn't it about time you discovered the precision, the versatility and simplicity of designing with Andersen oscillators? Contact Andersen Laboratories, 45 Old Iron Ore Road, Bloomfield, CT 06002. Telephone (203) 286-9090/FAX 203-242-4472.

 **ANDERSEN LABORATORIES**