

RF design

engineering principles and practices

January 1993



Cover Story
**New Oscillators Reach
for Lower Noise**

Featured Technology
Computer Modeling Applications

A lot more than a varactor company


FSI semiconductors mean buying made easy.

Just about every microwave or RF semiconductor you need to manufacture commercial or military components or sub-systems is now available from FSI.

Not just tuning varactors, but PIN and NIP diodes, limiters, multipliers, SRD's, MNS capacitors and spiral inductors. In any of a dozen or more packages including chip, beam lead, glass, ceramic and surface mount configurations.

As an added benefit, every product is available off the shelf or it's in process of replenishment. So we can give you a hard-and-fast shipping date.

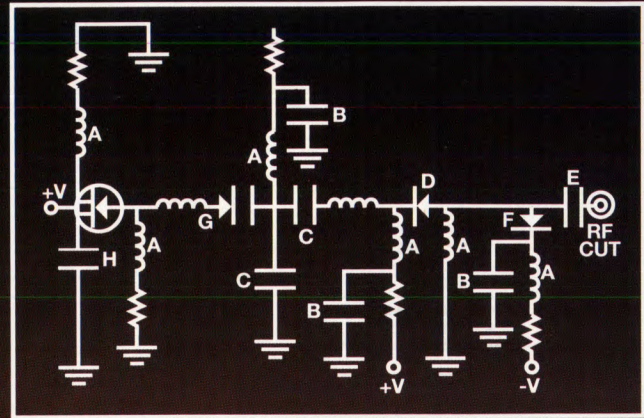Beyond that, we've been providing this kind of quality service for more than 20 years.



Typical switch with FSI semiconductors. (A) GC9002 Spiral Inductor; (B) GC84020 MNS Chip Capacitor; (C) GC86001 MNS Chip Capacitor; (D) GC4901 Beam Lead; (E) GC84030 MNS Chip Capacitor; (F) GC4221 PIN Diode; (G) GC15004 Linear Tuning Varactor; (H) GC84001 MNS Chip Capacitor.

Sample requests filled promptly.

Comprehensive, 120-page catalog free on request. For more information,

call or write Donna Langan,
Semiconductor Sales Manager,

Loral Microwave-FSI,

16 Maple Road,

Chelmsford, MA 01824.

Tel: (508) 256-4113.


Fax: (508) 937-3748.

INFO/CARD 1

LORAL

Microwave - FSI

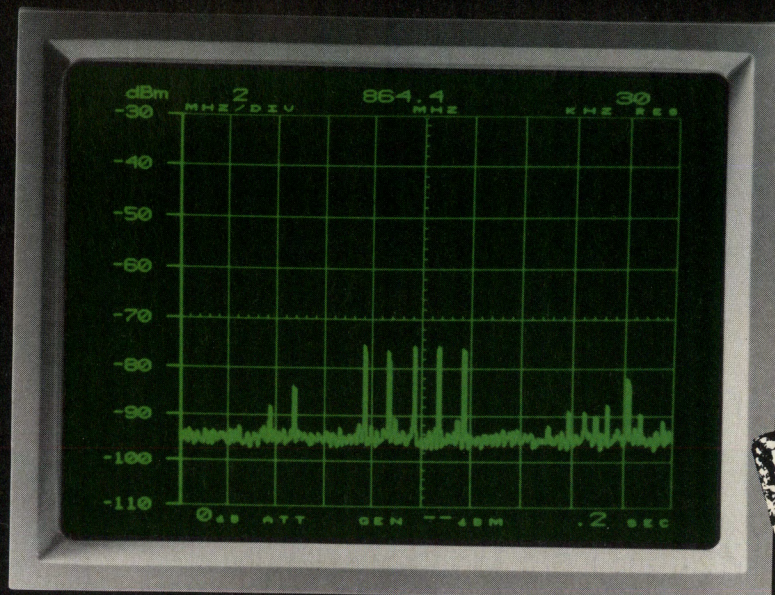
If you're not using a spectrum analyzer...



Spectrum analyzer display of cellular telephone transmissions.


**RENT directly
from IFR.
Call 316/522-4981,
Ext. 207 for details.**

maybe it's time to take a closer look.

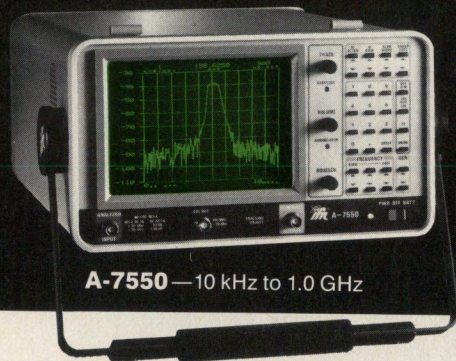

A-7550 — 10 kHz to 1.0 GHz

IFR
**Spectrum
Analyzers**

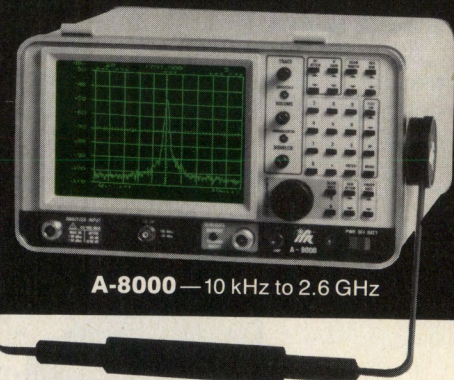

A-8000 — 10 kHz to 2.6 GHz

You can't hear them or see them, but there are probably thousands of electromagnetic signals being transmitted through the air around you at this very moment.

Many of these signals originate from radio and television transmission. However, many other signals are emitted from computers, CRT display terminals, and other electrical devices.

Each of these signals can be a potential source of harmful interference to sensitive electrical equipment or critical systems you are operating.

The IFR A-7550 and A-8000 Spectrum Analyzers provide a full set of features to speed the identification and measurement of signals over a wide frequency range.

Optional built-in features including a rechargeable battery, tracking generator, sensitive AM/FM/SSB receiver, IEEE-488 interface, RS-232 interface, and quasi-peak detector allow either instrument to be configured to your unique testing requirements at a surprisingly affordable price.

For more information or a demonstration of the A-7550 or the A-8000, contact your local IFR representative or call IFR at (316) 522-4981.



IFR SYSTEMS, INC.

10200 West York Street
Wichita, Kansas 67215-8935 U.S.A.
FAX 316/524-2623

INFO/CARD 2

**CRAFTED WITH PRIDE IN
USA**


POWER SPLITTERS/ COMBINERS

the world's largest selection
2KHz to 10GHz from \$2⁹⁵

With over 300 standard models, from 2-way to 48-way, 0°, 90° and 180°, 50- and 75-ohms, covering 2KHz to 10GHz, Mini-Circuits offers the world's largest selection of off-the-shelf power splitter/combiners. And, with rapid turnaround time, we'll also supply "special" needs, such as wider bandwidth, higher isolation, lower insertion loss and phase matched ports.

Available for use in military and commercial requirements, models include plug-in, flat-pack, surface-mount, connectorized standard and custom designs. New ultra-miniature surface mount units provide excellent solutions in cellular communications, GPS receivers, Satcom receivers, wireless communications, and cable systems.

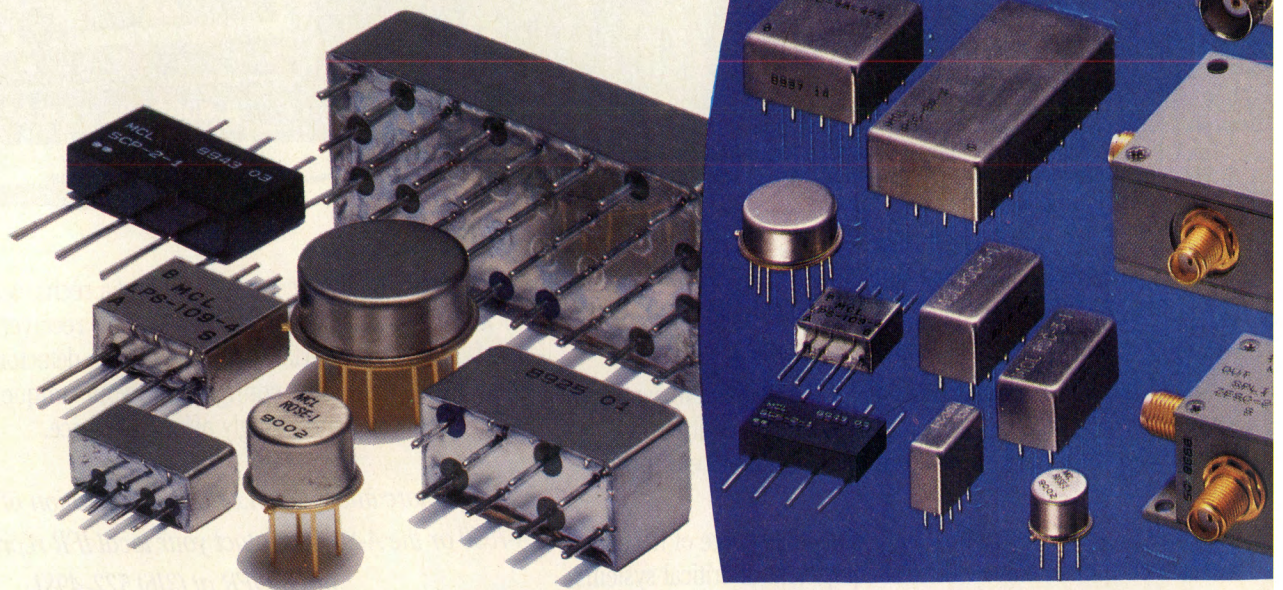All units come with a one-year guarantee and unprecedented "skinny" sigma unit-to-unit and production run-to-production run repeatability. All catalog models guaranteed to ship in one week. Mini-Circuits...dedicated to exceed our customers' expectations.




finding new ways ...
setting higher standards

 **Mini-Circuits**TM


WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

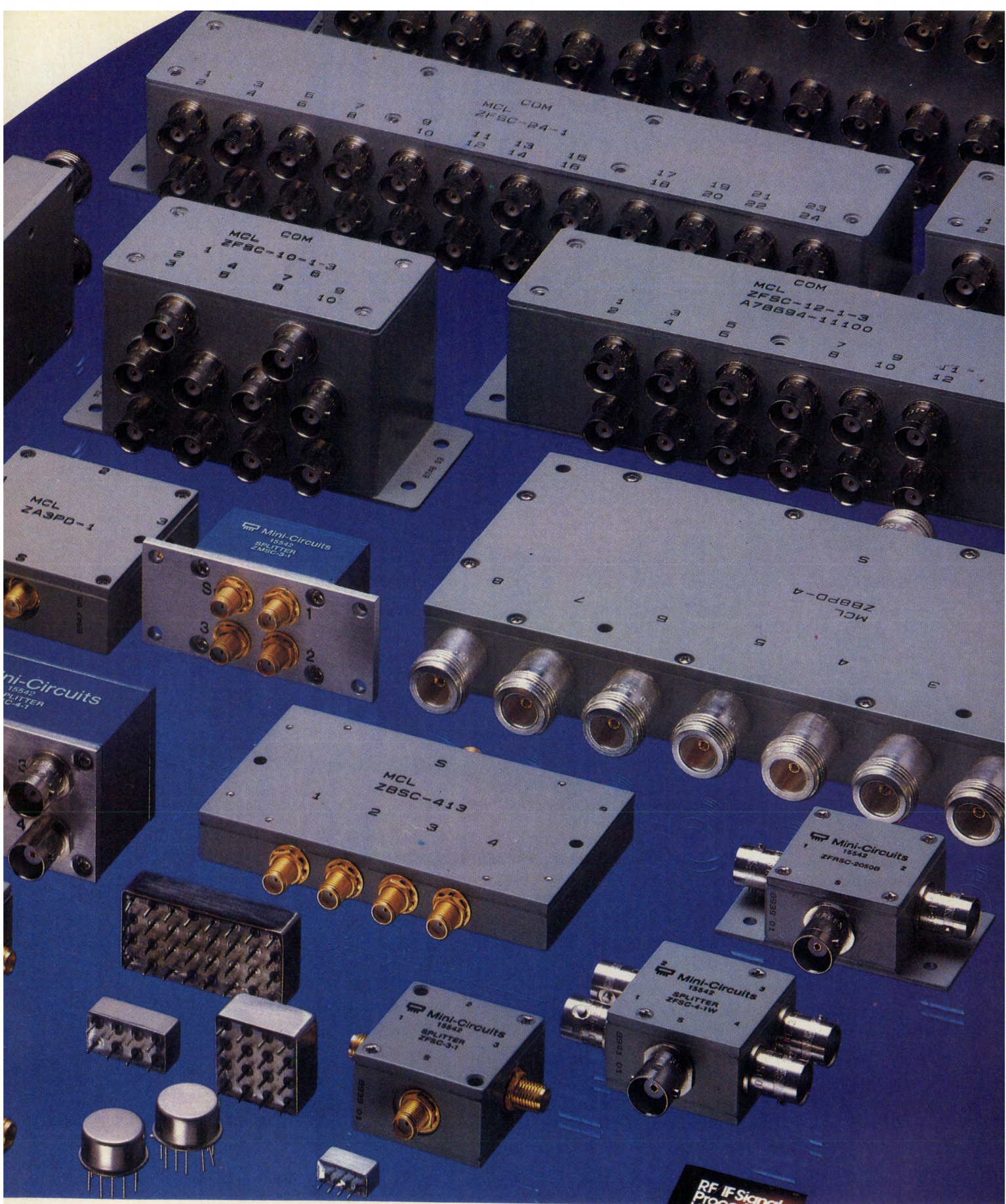
Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010



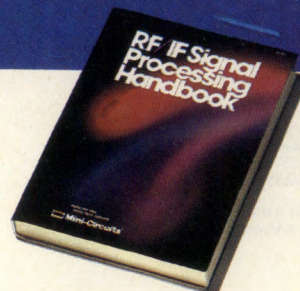For detailed specs on all Mini-Circuits products refer to
 • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY
 • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.



R2600

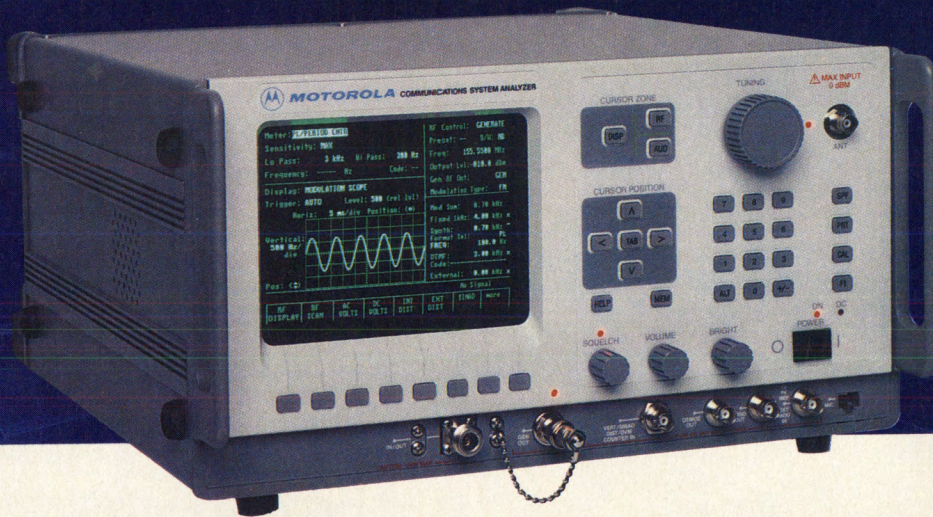

All that test equipment you've been using, with its endless cabling and "we mean business" knobs and switches, has served you well over the years. But someday you're going to need to replace it. That someday is today!

Digital testing is a reality; Cellular testing is big business; Software-driven testing is the future, and it's all available now in one box... the R2600 from Motorola.

The R2600 can provide:

- 1GHz Signal Generator
- Sweep Generator
- Duplex Offset Generator
- AC/DC Voltmeter
- Sensitive Off-the-Air Receiver
- Audio Generators
- AF & RF Counters
- Full Screen Spectrum Analyzer with Audio
- SINAD & Distortion Meters
- Terminated Wattmeter
- Signalling Simulator & Decoder
- Signal Strength Meter
- Full Screen Digital Oscilloscope
- 50 MHz Tracking Generator Option
- Cable Fault Option
- Subscriber Unit & Cellular Base Station Test Options

The R2600 features: 30 Test Set-Up Memories; Built-in Self Calibration; RS-232 Remote Control; Operator Selectable Special Functions; Help Screens; and a Color Monitor Port. Easy to use, easy to setup, transportable, intuitive to operate, economical, and upgradeable.

Call **1-800-235-9590**
or call (602) 441-8676, or write:
P.O. Box 2606 - M/D H3170 - Scottsdale, AZ 85252

Ⓜ MOTOROLA is a trademark of Motorola Inc.
© Copyright 1992 Motorola Inc.



featured technology

- 25 Simulating Lossy Transmission Lines with PSpice**
A lossy transmission line model has been added to PSpice's model library. This article describes the parameters used in that model and how to extract those parameters from manufacturer's data to improve analysis accuracy.
— *Walter Banzhaf, P.E.*

- 30 MIMP Analyzes Impedance Matching Networks**
Motorola's Impedance Matching Program (MIMP) allows power amplifier designers to match the input or output impedances of a user specified device or one of the power transistors contained in a device library. A distributed capacitance element provides accurate transmission line matching, and a unique Smith Chart plotting routine provides intuitive impedance graphing.
— *Dan Moline*

- 44 Microstrip Antenna Modeling**
Microstrip transmission-line and patch antenna models are presented which can be implemented in most major CAD packages.
— *Andre Boulouard, Michel Le Rouzic and Jean Paul Castelletto*

cover story


- 51 New Oscillators Advance the Art of Low Noise Performance**
Low drive levels and low noise circuitry are combined to provide an oscillator with an extremely low noise floor and extremely low close-in phase noise.
— *Charles Wenzel*

tutorial

- 58 Switching Speed: Definition and Measurement**
A precise definition is required for meaningful measurement of switching speed. Practical definitions and measurement techniques are presented.
— *Ra'anan Sover*

design awards

- 65 The Design of Constant Phase Difference Networks**
This article, an entry in the 1992 RF Design Awards contest, presents a unified method for calculating the pole frequencies and element values for a variety of constant phase difference network configurations.
— *Robert J. Dehoney*
- 68 A Logic-Compatible Mixer**
More digital communications means more mixers are being driven with logic level signals. This contest entry is a mixer which can be directly driven with TTL or ECL signals and is incorporated in a direct sequence spread spectrum modulator.
— *Thomas P. Hack*

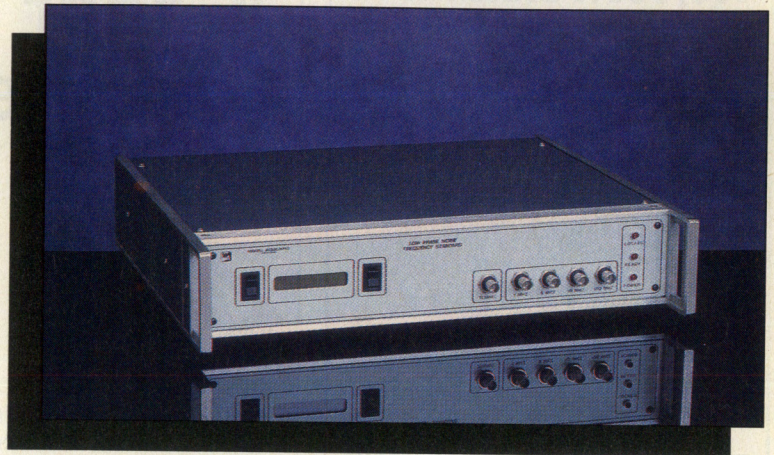

departments

- 8 Editorial
- 13 Calendar
- 14 Courses
- 16 News
- 22 Industry Insight
- 53 New Products
- 74 Product Report
- 75 New Software
- 76 New Literature
- 78 Marketplace
- 79 Info/Card
- 81 Reader Survey

R.F. DESIGN (ISSN:0163-321X USPS: 453-490) is published monthly plus one extra issue in summer. January 1993. Vol.16, No. 1. Copyright 1993 by Cardiff Publishing Company, a subsidiary of Argus Press Holdings, Inc., 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111 (303) 220-0600. Contents may not be reproduced in any form without written permission. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: *RF Design*, P.O. Box 1077, Skokie, IL 60076. Subscriptions are: \$39 per year in the United States; \$49 per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700.

SUBSCRIPTION INQUIRIES: (708) 647-0756.

POSTMASTER & SUBSCRIBERS: Please send address changes to R.F. Design, P.O. Box 1077, Skokie, IL 60076.

HIGH POWER COUPLER

100,000:1 BANDWIDTH



TYPICAL SPECIFICATIONS

MODEL C2630

FREQUENCY RANGE01-1000MHz
COUPLING40db
FLATNESS ± 0.6 db
DIRECTIVITY20db MIN
VSWR (ML)1.3:1
POWER100 W.CW.

NEED MORE POWER? We cover the same frequency range at 1 KW with just two 50db couplers.


**MODEL C1460 .01-250 MHz
MODEL C2675 200-1000 MHz**

**our products employ...
WERLATONE WIDEBAND
TECHNOLOGY for no
compromise high power
multi-octave performance.**

**WERLATONE, INC.
DECADES AHEAD
P.O. Box 47 Brewster, N.Y. 10509
TEL. (914) 279 6187
FAX. (914) 279 7404**

RF editorial

1993: A Year of Change

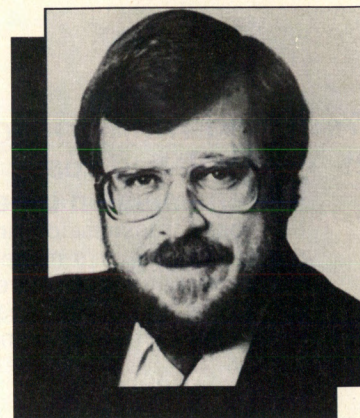

By Gary A. Breed
Editor

Change is the operative term for 1993! A new President will be inaugurated this month and one political party is in firm control of the government. Bill Clinton will be the first President who grew up after World War II, representing the "baby boom" generation that makes up a huge part of U.S. society. For better or worse, there will be change in our Federal government.

In the world of RF, personal communication equipment (PCN, PCS) is ready to take off. Low earth orbit (LEO) systems for paging, voice and data communications could see their first hardware. This could be the year that the FCC approves standards for Advanced Television, with Digital Audio Broadcast standards coming, as well. If that's not enough, most analysts see the cellular boom continuing through 1993.

There has been another major change — a change in thinking about what makes technology exciting. For over 30 years, the term "high tech" has meant pushing the laws of physics, or reaching the limits of engineering understanding. These things will always be exciting, but with a slowing world economy, there is renewed glamour in "making things that work."

Today's emphasis is on practical products that put technology to work in new ways. Engineering creativity now includes more than just translating a function into hardware. Engineers are refining existing theory and reducing complex (and expensive) concepts into inexpensive, reproducible circuitry. They are making products that are not only technically advanced, but elegantly designed to be easy to use, and at the lowest cost.

The roles and attitudes of RF engineers are changing, too. The image of

an engineer stuck in his cubicle designing one perfect circuit is gone. An engineer now needs to know all the RF he or she can, then add knowledge of digital and analog control circuitry, digital signal processing, plus governmental rules and regulations — with a little promotional and marketing attitude thrown in. Instead of being reclusive, top engineers are part of a team; communicating with engineers in other departments, talking to customers, helping purchasing and sales staffs.

Here at *RF Design*, we've seen these changes happening. Over the past two or three years, the number of articles submitted for our consideration has grown rapidly as engineers recognize that exposure to the "outside world" is good for them and their companies. In the companies we talk to, more marketing and customer relations positions are being filled with engineers rather than someone with sales experience. The overall sophistication of the engineering community is advancing rapidly.

Change is not always good for everyone, however. Engineers laid off from defense-oriented companies will have a hard time finding jobs in the new cost-conscious marketplace. To make things worse, many of the RF products in development will not be manufactured in the U.S. Let's hope that today's change leads to a better combination of creative design and efficient manufacturing.

New for Noise Figure Measurement!

NC 346Ka Noise Sources Have Continuous Coverage From 10 MHz To 40 GHz

Noise Com's new NC 346Ka is the only noise figure meter compatible noise source that delivers broadband noise from 10 MHz to 40 GHz. The NC 346Ka is compatible with the HP 8970 and other popular noise figure meters and has low VSWR across the entire operating range. It uses reliable, repeatable K connectors that are electrically and mechanically compatible with SMA and 3.5-mm precision connectors.

The NC 346Ka has a built-in regulator that makes it insensitive to input voltage variations, and each unit is fully calibrated at frequencies throughout its operating range. Every NC 346Ka also comes with a feature found nowhere else: Noise Com's hard-earned reputation for fast delivery and customer support.

For more information about the NC 346Ka, call Gary Simonyan at (201) 261-8797.



NC 346Ka Specifications

Frequency range (GHz)	Output (dB ENR)	VSWR
0.01 to 5	15 to 17	1.25:1
5 to 18	14 to 17	1.30:1
18 to 26.5	13 to 16	1.40:1
26.5 to 40	13 to 16	1.50:1
Connector type	K male, K female optional	
Calibration	Traceable to NIST	
Input power	+28 VDC +/-2 V at 20 mA maximum Built-in regulator	
Noise figure meter compatibility	HP 8970 and most other popular instruments	

NOISE/COM

E. 49 Midland Ave., Paramus, NJ 07652
(201) 261-8797 • FAX (201) 261-8339

HI-POWER RF AMPLIFIERS, TRANSMITTERS AND POWER GENERATORS

MILLIONS OF WATTS SOLD... Henry has delivered for 30 years. We can ship designs in the 2 to 500 MHz range with power ratings to 10,000 watts from stock. If we don't have it we'll design it.



HENRY RADIO

2050 S. Bundy Drive
Los Angeles CA 90025
Toll Free: 1-800-877-7979
Or: 1-310-820-1234
FAX: 1-310-826-7790

APPLICATIONS:

- POWER AMPLIFIERS
- SHORE STATIONS
- CW/AMTOR/TELEX
- BROADCAST
- NUCLEAR MAGNETIC
- LASER EXCITATION
- PLASMA GENERATORS
- SPUTTERING
- MEDICAL



INFO/CARD 7

RF Design Software Service

Programs from RF Design, provided on disk for your convenience.

January Program: RFD-0193

"The Design of Constant Phase Difference Networks" by Robert Dehoney. PHASEDIF program computes poles for networks generating arbitrary phase differences. Component values can be obtained for several passive L-C and active all-pass network configurations. (BASIC, compiled, with source code)

December Program: RFD-1292

"Calculation of Mixer Spurious Responses in Broadband EW Systems" by Ronald Day. This program covers mixer spurs in wideband block-conversion systems. Helps identify problems that a narrowband analysis can miss. Creates spur charts and spur lists. (QuickBasic compiled version and BASIC source code)

Call or write for a listing of all available programs

We Accept VISA, MasterCard, and American Express! When ordering by mail, please include card number, correct name, and expiration date.

Order by telephone! Call (303) 770-4709 to place your credit card order. Occasionally, you may reach an answering machine, but your call will be returned promptly.

Each month's program(s)..... \$ 15.00postpaid, with article reprints and any author's notes. Price includes shipping to U.S. or Canadian addresses. Orders from other countries must add \$8.00 per order for extra shipping and handling. Specify 3 1/2 or 5 1/4 inch disks
Annual subscription..... \$ 130.00 postpaid..(\$170 Foreign, via Air Mail).....get each program ASAP.

Check, money order, VISA, MasterCard or American Express accepted for all orders. Purchase orders from U.S. and Canadian companies accepted for orders of \$100 or more. All foreign orders must be pre-paid, with payment via charge card; or bank draft drawn on a bank located in the U.S.

RF Design Software Service
P.O. Box 3702
Littleton, Colorado 80161-3702 U.S.A.
(303) 770-4709

INFO/CARD 100

RF design

a Cardiff publication Established 1978

Main Office:
6300 S. Syracuse Way, Suite 650
Englewood, CO 80111 • (303) 220-0600
Fax: (303) 773-9716

Vice President – Group Publisher
Kathryn Walsh

Editor
Gary A. Breed

Associate Editor
Liane Pomfret

Technical Editor
Andrew M. Kellett

Consulting Editor
Andy Przedpelski

Associate Sales Manager
Bill Pettit
Main Office

Account Executive
Maryanne Averill
Main Office

Account Executive
Cindy Wieland
Phone and Fax: (602) 955-7115

Editorial Review Board

Alex Burwasser
Doug DeMaw
Dave Krautheimer
James W. Mize, Jr.
Robert J. Zavrel, Jr.

Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Sicotte

Advertising Services
Tisha Bobers Schmidt Hill

Reprints Manager
Vivian Peterson

Secretary
Theresa Maier

Convention Manager
Barb Binge

Registration Coordinator
Rena Fierros

Exhibits Coordinator
Dawn Keith

Trade Show Account Executive
Steffanie Engel

Associate Production Managers
Matt Park Maurice Lydick

Artists
Kim Austin Paul Rivera
Joyce Fields Sheri Culmer
Brad Fuller

Composition
Mike C. Moore Marcie Tichenor

Art Director
Bob Stewart

Published by

CARDIFF
PUBLISHING COMPANY, INC.



President
Robert A. Searle

Vice President — Production
Cherryl Greenman

Vice President — Convention Management
Kathy Kriner

Vice President — Finance
Jennifer Burger

Vice President — Circulation
Patricia Shapiro

Credit Manager
Christine Kloack

Please address subscription inquiries to:
RF Design
P.O. Box 1077, Skokie, IL 60076-9931
Postmaster: send form 3576
to the above address.

I & Q Modulators/Demodulators Drive Out Unwanted Products...

SINGLE SIDEBAND MODULATOR
 RL -4.63 dBm
 ATTN 10 dB
 10.00 dB/DIV

TWO TONE THIRD ORDER INTERMODULATION
 5.0 dBm ATTN 30 dB
 MARKER Δ 500 kHz
 -54.60 dB
 CENTER 2.00 MHz RES BW 30 kHz
 SPAN 2.00 MHz P 2.00 sec
 VBW 100 Hz

Adjustable ϕ & A makes the unwanted Sideband Practically disappear!

High level I & Q can really reduce intermodulation


**Check Merrimac
 For the Very Best I & Q Performance**

Call for Merrimac Catalogue M-92 to see complete range of Mixers, Modulators and Demodulators.

Merrimac
 41 Fairfield Place, West Caldwell, N.J. 07006
 Tel: (201) 575-1300 / FAX: (201) 575-0531

No More Beam Leads!

SurMount Schottky Diodes

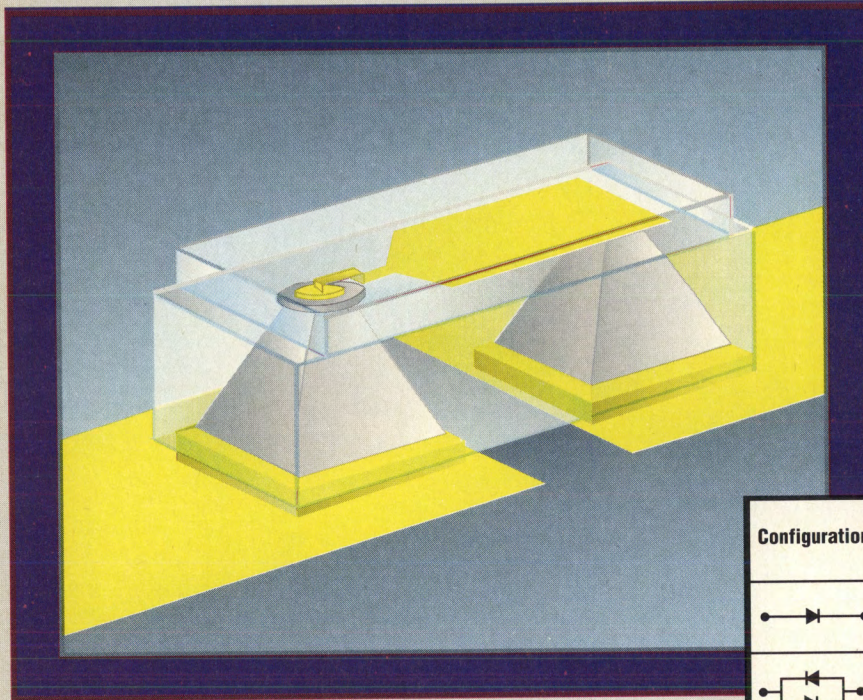

- Surface Mountable Chips
- Multiple Circuit Configurations
- Simple Die Attach
- Low Barrier Diodes

- Robust *HMIC* MMIC Construction
- 100% 300°C 16 hr. Stabilization Bake
- Useful to K Band
- Exceptionally Low Parasitics

For technical assistance contact Rick Cory on ext. 1536.
For more information, call or write:

M/A-COM Semiconductor Products
South Avenue, Burlington, MA 01803
(617) 272-3100 • FAX (617) 272-8861

INFO/CARD 9

Configuration	Model Number	Device Type	Recommended Frequency	Max C_j @ 0 Volts and 1 MHz	Max R_T at 10 mA
	MA4E2502L	Single	Ku Band	.10 pF	16 Ohms
	MA4E2503L		C-X Band	.20 pF	12 Ohms
	MA4E2508L	Anti-Parallel Pair	Ku Band	.10 pF	16 Ohms
	MA4E2509L		C-X Band	.20 pF	12 Ohms
	MA4E2532L	Ring Quad	Ku Band	.10 pF	16 Ohms
	MA4E2533L		C-X Band	.20 pF	12 Ohms
	MA4E2538L	Bridge Quad	Ku Band	.10 pF	16 Ohms
	MA4E2539L		C-X Band	.20 pF	12 Ohms
	MA4E2544L	Cross-Over Ring Quad	Ku Band	.10 pF	16 Ohms
	MA4E2545L		C-X Band	.20 pF	12 Ohms
	MA4E2514L	Series Tee	Ku Band	.10 pF	16 Ohms
	MA4E2515L		C-X Band	.20 pF	12 Ohms
	MA4E2520L	Reverse Tee	Ku Band	.10 pF	16 Ohms
	MA4E2521L		C-X Band	.20 pF	12 Ohms
	MA4E2526L	Common Cathode Tee	Ku Band	.10 pF	16 Ohms
	MA4E2527L		C-X Band	.20 pF	12 Ohms

RF calendar

January

11-14 **Design & Test Expo**
Anaheim, CA
Information: Miller Freeman, Inc., 13760 Noel Road,
Suite 500, Dallas, TX 75240. Tel: (800) 223-7126. Fax:
(214) 419-7915.

19-20 **Portable Intelligence Expo 1993**
San Francisco, CA
Information: PIX 93, Cardiff Publishing, 6300 S.
Syracuse Way, Suite 650, Englewood, CO 80111. Tel:
(303) 220-0600, (800) 525-9154. Fax: (303) 770-0253.

February

7-11 **NEPCON West '93**
Anaheim, CA
Information: Michael Critser, Director of Conferences,
Reed Exhibition Companies, 1350 E. Touhy Ave., Des
Plaines, IL 60018. Tel: (708) 299-9311. Fax: (708) 635
-1571.

March

17-19 **RF Expo West**
San Jose, CA
Information: Barb Binge, Cardiff Publishing Company,
6300 S. Syracuse Way, Suite 650, Englewood, CO 80111.
Tel: (303) 220-0600, (800) 525-9154. Fax: (303) 773
-9716.

30-31 **The 1993 Mid-Lantic Electronics Show**
King of Prussia, PA
Information: Mid-Lantic Electronics Show '93, Judith
Ginsberg, 4113 Barberry Drive, Lafayette Hill, PA
19444. Tel: (215) 828-2271. Fax: (215) 941-6773.

30-2 **8th International Conference on Antennas and
Propagation**
Edinburgh, UK
Information: IEE, Savoy Place, London WC2R 0BL. Tel:
(44) 071 240 1871. Fax: (44) 071 497 3633.


April

18-21 **The 4th IEE Conference on Telecommunications**
Manchester, UK
Information: ICT 93 Secretariat, Conference Services,
IEE, Savoy Place, London, WC2R 0BL, United Kingdom.

18-22 **Symposium on Ceramics for Wireless Communication**
Cincinnati, OH
Information: Henry O'Bryan, AT&T Bell Laboratories.
Tel: (908) 582-6980. Fax: (908) 582-2521.

27-29 **Electro**
Edison, NJ
Information: Electronic Conventions Management, PO Box
92275, Los Angeles, CA 90009-2275. Tel: (800) 877-2668.
Fax: (310) 641-5117.

Sprague-Goodman

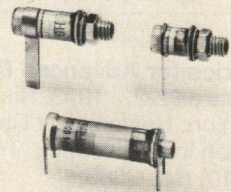

Glass and Quartz Pistoncaps®

- Designed to meet MIL-C-14409D
 - QPL models
 - Extremely stable over temperature, frequency, voltage, etc.
 - Cap ranges: 0.5-3.0 pF to 1.0-120 pF
 - Zero backlash multiturn adjust mechanism
 - Operating temp: -55° to +125°C (models to +200°C)
 - Q to 1500 at 20 MHz
 - Wide variety of configurations for PC and panel mounting
 - Voltage ratings from 500 to 5000 V
- Phone, fax or write today for
Engineering Bulletin SG-205A.

**SPRAGUE
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 10

Sprague-Goodman



Ceramic Dielectric Trimmer Capacitors

Rugged 5 & 7 mm types

Operating temp: -55° to +125°C
Cap ranges: 1.3-2.0 pF to 12-160 pF

Miniature types suitable for hybrids

Operating temp: -25° to +85°C
3 series: 2.0 x 1.2 mm; 3.0 x 1.5 mm;
5.0 x 2.0 mm
Cap ranges: 2.5-10 pF to 5.5-40 pF

Microwave types

Operating temp: -55° to 85°C
Cap ranges: 0.5-2.0 pF; 1-4.0 pF; 2.0-10 pF
Q > 500 at 100 MHz

Plastic encased 4 x 4.5 mm and 5 mm types

Designed for volume applications
Surface mount and printed-thru-hole models
Cap ranges: 1.7-3.0 pF to 10-50 pF

Phone, fax or write today for
Engineering Bulletin SG-305B.

**SPRAGUE
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 11

RF courses

Dielectrics for Advanced Microelectronics

February 22-23, 1993, San Francisco, CA
 Information: University of California-Berkeley, Continuing Education in Engineering. Tel: (510) 642-4151.
 Fax: (510) 643-8683.

Phased-Array Antennas: Theory, Design and Technology

January 26-29, 1993, Atlanta, GA
Antenna Engineering
 February 2-5, 1993, Atlanta, GA
Principles of Pulse Doppler Radar: High, Medium and Low PRF
 February 9-11, 1993, Atlanta, GA

Coherent Radar Performance Estimation

February 17-19, 1993, Atlanta, GA
Radar Signal Processing: Theory, Technology and Applications
 February 22-25, 1993, Atlanta, GA

Radar Cross Section Reduction

March 23-26, 1993, Atlanta, GA
 Information: Georgia Institute of Technology, Continuing Education. Tel: (404) 894-2547.

Antennas: Principles, Design, and Measurements

March 10-13, 1993, St. Cloud, FL
 Information: Southeastern Center for Electrical Engineering Education, Kelly Brown. Tel: (407) 892-6146

RF/Microwave Circuit Design II: Linear/Nonlinear Techniques and Applications

February 1-5, 1993, Los Angeles, CA
High-Resolution Microwave Imaging: Principles and Applications
 February 23-26, 1993, Los Angeles, CA
 Information: UCLA Short Course Program Office. Tel: (310) 825-1047. Fax: (310) 206-2815.

Digital Signal Analysis

February 22-24, 1993, Tempe, AZ

Fiber Optic Communications

March 3-5, 1993, Tempe, AZ


Antenna Analysis, Design, and Measurements

March 8-11, 1993, Tempe, AZ
 Information: Center for Professional Development, College of Engineering and Applied Sciences, Arizona State University. Tel: (602) 965-1740 Fax: (602) 965-8653

EMC Measurement and Regulation



January 18, 1993, St. Petersburg, FL
 January 20, 1993, Albuquerque, NM
 January 22, 1993, Phoenix, AZ
 February 15, 1993, San Francisco, CA
 February 17, 1993, Los Angeles, CA
 February 19, 1993, San Diego, CA
 Information: Tektronix Inc. Tel: (800) 426-2200.

Streamline Crystal Oscillator

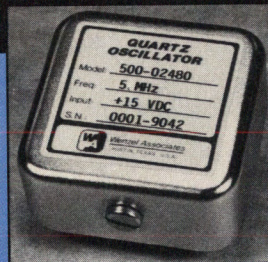

- Small Package
- Low Phase Noise
- Low Power Consumption
- Can be Customized

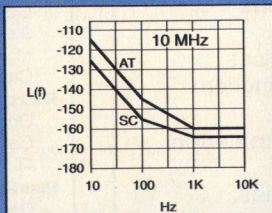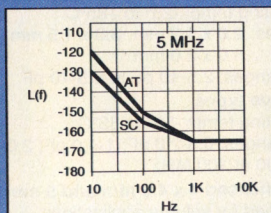Frequency: 1 to 20 MHz Package: 2x2x1"
 Phase Noise:



WA Wenzel Associates
Quietly the best

1005 La Posada Drive, Austin, Texas 78752 • 512-450-1400 • Fax 512-450-1490

INFO/CARD 12

When space is at a premium, choose a high performance



SURFACE MOUNT CRYSTAL PACKAGE

Miniature applications often found in military and commercial, one-way and two-way, mobile and portable radios require crystal controlled accuracy. EG&G's new AT-cut crystal, in a surface mount package, performs excellently under these rugged conditions. Frequencies range from 6.5 to 110 MHz, and standard motional parameters are available. They contain the same high performance features found in our complete line of AT-cut crystals, only smaller.

These surface mount crystals meet MIL-STD-202 method 210, resistance to soldering heat, and are ideal for automated assembly.

So, give us a call at 1-800-424-0266. (U.S. or Canada)
 No matter what size your applications may be...

our crystals are a perfect fit.





EG&G
FREQUENCY PRODUCTS

4914 Gray Road • Cincinnati, Ohio 45232 | In Canada represented by: ELLAM & Assoc. Ltd.
 Phone 513-542-5555 • FAX 513-542-5146 | Phone 613-727-3892 • FAX 613-727-0368

INFO/CARD 13

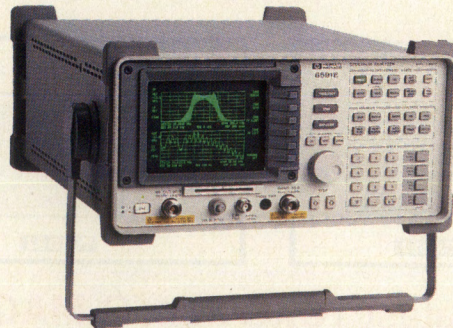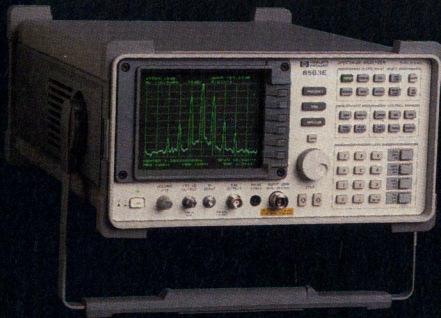Everything you expect from
a powerful new generation of
HP spectrum analyzers.



Except the price.

© 1992 Hewlett-Packard Co. TMSAD250

Introducing the HP 8590 & 8560 E-Series: more performance than anything at their price — less price than anything with their performance.

If advancing technologies and receding budgets make life difficult, it's time to look at HP's new generation of portable spectrum analyzers.

Start with the new HP 8590 E-Series, which offers surprising measurement power at an economical price. Since there are 5 models, you buy *exactly* the frequency range you need. And

get a spectrum analyzer that's easy to use and can be configured for your specific application.

The remarkable HP 8560 E-Series delivers the kind of performance that until now was found only on expensive benchtop models. Yet for its extremely affordable price you get lower phase noise, narrower resolution bandwidths, and improved sensitivity. Clearly, this level of performance doesn't exist in any other spectrum analyzer at this price.

Of course, you'll want more details than we can provide here. So call your local HP office or one of the numbers listed below to get an

ordering guide with detailed product information. Plus one very important thing.

An early start on the next generation of test solutions.

There is a better way.



United Kingdom (0344) 362-867 • Spain (900) 123-123 • France (1-69) 82-65-00 • Italy (02) 95-300-134 • Netherlands (020) 547-6669 • Germany (06172) 16-0 • Singapore (65) 291-8554 • Taiwan (886-2) 714-8740 • Hong Kong (852) 848-7070 • Korea (82-2) 784-2666

GE Sells Aerospace Division to Martin Marietta

In one of the biggest deals in the defense contracting industry, Martin Marietta has agreed to purchase General Electric's aerospace division for \$3 billion. The General Electric division

includes: GE Aerospace, GE Government Services, Knolls Atomic Power Lab and Machinery Apparatus Operation with a 1991 revenue of \$6 billion. General Electric will receive about \$2 billion in cash and another \$1 billion in convertible preferred stock. Martin Marietta is now ranked as the United State's largest defense firm.

Frequency Control Symposium Call for Papers

— The 1993 IEEE Frequency Control Symposium has issued a call for papers for its conference to be held June 2-4, 1993, in Salt Lake City, Utah. Authors are invited to submit papers dealing with recent progress in research, development and applications in the following areas: fundamental properties of piezoelectric crystals, theory and design of piezoelectric resonators, resonator processing techniques, filters, SAW devices, quartz crystal oscillators, microwave and millimeter wave oscillators, synthesizers and other frequency control circuitry, atomic and molecular frequency standards, noise phenomena and aging, frequency and time coordination and distribution, sensors and transducers and applications of frequency control. Two copies of a 500 word summary, with a topic indicated in the upper right hand corner of the first page, together with the author's name, address and telephone number should be sent to: Mr. Jack Kusters, 52U/07, Hewlett-Packard Company, 5301 Stevens Creek Blvd., PO Box 58059, Santa Clara, CA 95052-8059. Tel: (408) 553-2041. Fax: (408) 246- 5925. The deadline for submission of summaries is January 15, 1993.

Republics Join ITU — The International Telecommunications Union has announced that the Republic of Moldova and the Republic of Bosnia and Herzegovina both joined the ITU in October, 1992. Moldova is a former USSR republic and Bosnia Herzegovina was part of Yugoslavia. This brings ITU membership to 174 countries.



Setting Standards for Optical Fibers

— The telecommunications industry has teamed up with NIST's Time and Frequency Division to develop phase noise and synchronization standards for new optical fiber communication systems. Since 1991, the institute has participated in industry-wide meetings to develop standards for the proposed optical fiber network. NIST will continue to work with the industry on synchronization and timing questions, which promise to get more severe as communication data rates increase.

THE INDUSTRY'S

MOST WANTED

TCXO

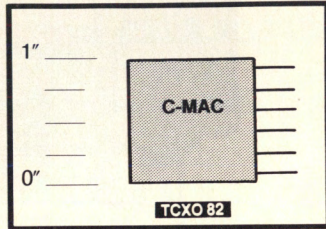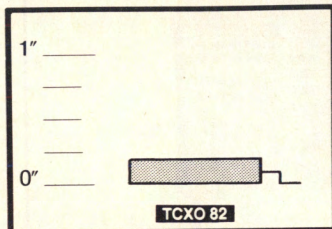

The latest TCXO from C-MAC

DESCRIPTION:

- 0.2 cubic inches
1" x 1" x 0.2" high
- Mil grade available
- Surface mountable
- Custom configurable leads

MODE OF OPERATION:

- Low phase noise
- Frequencies up to 350 mhz
- Low power consumption
- Highly stable, precision performance

Analog Chip Temperature Compensation Technology

Buy one or borrow one.

Call us for technical literature and complete details on our unique offer.




C-MAC QUARTZ CRYSTALS
33 W. HIGGINS ROAD SUITE 3030
SOUTH BARRINGTON, IL 60010
PHONE: 708.428.3800 FAX: 708.428.3803 UK: 0279.626626

BROADBAND

RF AMPLIFIERS

NEW!
Model 6100L
100W
400-1000MHz

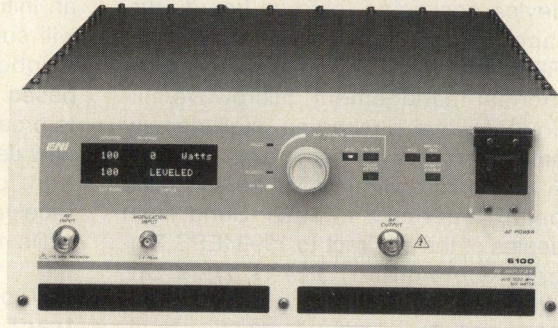

FOR PRIORITY SERVICE

Fax This Ad To Us At
(716) 427-7839

Just fill in your name, address, and fax or phone in the spaces below! For specifications & pricing on specific models, place a ✓ in the first column.

Name: _____
 Title: _____
 Company: _____
 Mail To: _____
 Call : _____
 Fax: _____

Check Here To Receive Complete Catalog In Mail:

RFD 1/93

✓	MODEL	CLASS	FREQ. RANGE	POWER	GAIN
LF/MF					
	1040L	B	10kHz -500kHz	400W	55dB (±1dB)
	1140LA	B	9kHz -250kHz	1100W	55dB (±1dB)
	AP-400B	B	80kHz - 2.7MHz	400W	55dB (±1.5dB)
	240L	A	20kHz -10MHz	40W	50dB (±1.5dB)
	2100L	A	10kHz -12MHz	100W	50dB (±1.5dB)
HF					
	A-150	A	300kHz -35MHz	150W	55dB (±1dB)
	A-300	A	300kHz -35MHz	300W	55dB (±1dB)
	A-500	A	300kHz -35MHz	500W	60dB (±1dB)
	A-1000	A	300kHz -35MHz	1000W	60dB (±1.5dB)
VHF					
	325LA	A	250kHz -150MHz	25W	50dB (±1.5dB)
	3100LA	A	250kHz -150MHz	100W	55dB (±1.5dB)
	3200L	A	250kHz -120MHz	200W	55dB (±1.5dB)
UHF					
	400AP	A	150kHz -300MHz	3W	37dB (±1dB)
	403LA	A	150kHz -300MHz	3W	37dB (±1dB)
	411LA	A	150kHz -300MHz	10W	40dB (±1.5dB)
	525LA	A	1MHz -500MHz	25W	50dB (±1.5dB)
	550L	A	1.5MHz-400MHz	50W	50dB (±1.5dB)
	5100L	A	1.5MHz-400MHz	100W	50dB (±1.5dB)
	603L	A	800kHz -1GHz	3W	40dB (±1.5dB)
	630L	A	400MHz-1GHz	30W	51dB (±2dB)
	6100L	AB	400MHz-1GHz	100W	51dB (±2dB)

PHONE: (716) 292-7440 • **FAX:** (716) 427-7839

ENI
A Division of
Astec America, Inc.
100 Highpower Road
Rochester, NY 14623
USA

WORLDWIDE SALES & SERVICE
Santa Clara, CA • Tel: (408) 727-0993
Welwyn Garden City, UK • Tel: (0707) 371558
Gerlingen, Germany • Tel: (0715) 621095
Tokyo, Japan • Tel: 0425 229011
Osaka, Japan • Tel: 06 367-0823



CUT HERE

NEW!
**CRYSTAL
OSCILLATORS**
FROM **VECTRON!**

**Sinewave
Crystal Oscillators
to 2.6 GHz**



Frequency:	5 MHz to 2.6 GHz
Output:	+7 dBm standard
Stability:	±5 ppm, over 0/+50°C ±50 ppm, over -55/+85°C tighter stabilities avail.
Size:	2" x 2 1/2" x 1/2"

**Low Noise OCXOs
(25-200MHz)**



Type:	CO-724SL2	CO-725SL2
Aging:	2x10 ⁻⁹ /day (5x10 ⁻⁷ /yr)	5x10 ⁻¹⁰ /day (1x10 ⁻⁷ /yr)
Phase Noise	100 Hz: -130 dBc/Hz 1 kHz: -145 dBc/Hz 10 kHz: -155 dBc/Hz	-120 dBc/Hz -135 dBc/Hz -140 dBc/Hz
Size:	2" x 2" x 1"	2" x 2" x 1 1/4"

To order, or for complete
engineering assistance, call:
(203) 853-4433



VECTRON

The Crystal Oscillator Company

VECTRON LABORATORIES, INC.

166 Glover Ave., P.O. Box 5160, Norwalk, CT 06856-5160
Phone: 203/853-4433 Fax: 203/849-1423

Packaging Conference Call for Papers — The International Electronics Packaging Conference to be held September 12-15, 1993 in San Diego, California has issued a call for papers. Abstracts of unpublished work in recent developments in the following areas of electronic packaging are requested: device packaging, chip on board, surface mount, ceramic technology, RF/mixed signal applications, reliability, thermal management, microwave/millimeter wave packaging, high density substrates, interconnects, and materials. A 300 word abstract must be submitted before February 1, 1993. Send eight copies of the abstract to 1993 IEPS Program Committee, 114 N. Hale St., Wheaton, IL 60187-5113. Tel: (708) 260-1044. Fax: (708) 260-0867.

NIST/Industry R&D Agreement — NIST has signed a cooperative research and development agreement with Wiltron to assess the performance of commercial automatic network analyzers (ANAs) used to calibrate microwave system components. ANAs have replaced many manual systems for microwave calibrations throughout government and industry. NIST pioneered the development of six-port ANAs, which enhanced ANA technology. While the six-port device is still available for NIST calibrations, it is costly for the user. NIST wants to determine whether it can achieve calibration integrity by using commercial instruments at a lower cost to customers. During the three-year agreement with Wiltron, NIST will explore the feasibility of using commercial ANAs for NIST calibration services and develop procedures for validating their uses in routine calibrations. For more information, contact Bob Judish, Div. 813.01, NIST, Boulder, CO 80303. Tel: (303) 497-3380.

Stetco Sells Thirty Percent of Stock — Stetco, Inc. recently announced the sale of thirty percent of its corporate stock to Fastron GmbH. Stetco will continue to serve as Fastron's agent in the United States and Mexico, and Fastron Malaysia will represent Stetco's sales interests in Southeast Asia. The two companies will also work closely together in developing new products for the electronic marketplace.

Harris Wins Naval Contract — The U.S. Navy Space and Naval Warfare Systems Command has awarded Harris Corporation RF Communications Division a contract to supply high frequency radio communications systems for the Navy's surface ships. The contract is for \$180 million over a six-year period, with an initial award of \$33.5 million. Harris will supply state-of-the-art, solid-state shipboard communications systems, based on a newly developed approach to broadband HF radio architecture. The new design permits simultaneous operation of multiple transmitters and receivers in a collocated environment while minimizing mutual interference.

BFGoodrich Awarded TCAS Contract — BFGoodrich Flight Systems was recently awarded its first major contract for its Traffic Alert and Collision Avoidance System. Mesa Airlines selected BFGoodrich to provide the TCAS I for all seven divisions of the airline. Terms of the contract were not released.


Imaging Technology Center Receives NSF Grant — The National Science Foundation has awarded a \$1.2 million grant to finance a new technology center for electronic imaging. The Center for Electronic Imaging Systems was established by Harris Corporation and other Rochester, New York based high-tech corporations and universities. The NSF grant is being matched by contributions from New York State and private industry, giving the center a total of \$3.6 million over four years.

Milcom Awarded Amplifier Contract — Milcom International has received a \$200,000 contract from a major Far East electronics manufacturer. The contract is for the development of an 800 MHz, 1000 Watt ultra linear power amplifier for digital cellular telephone applications. Prototypes will be delivered in early 1993 with project completion in the spring of 1993.

Retliff Receives Laboratory Approval — Retliff Testing Laboratories has been granted "Approved Laboratory Status" by Interference Technology International, a United Kingdom-

If A Standard Frequency Control Product Won't Do, Check With CTS.

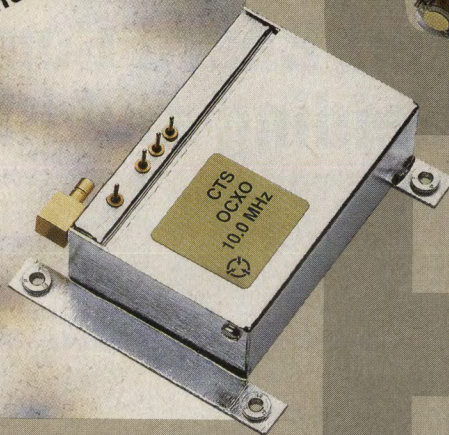- Technical Services
- Crystal Production
- In-House Environmental Testing
- Domestic/European Manufacturing
- Comprehensive Line
- CTS Quality



When it comes to selecting a reliable source for advanced custom crystals and oscillators, CTS should be at the top of your list. Quality products, experienced technical assistance, and a broad line are just a few of the reasons why CTS is the obvious choice.

First, check CTS' vertical integration, including the in-house production of crystals, that results in reduced lead times and stricter quality control. In-house testing gives CTS Knights crystals and oscillators that extra edge of reliability that's so important.

Next, check technical services that are second to none. CTS' worldwide engineering staff offers you advanced problem solving capabilities, and help designing products for your specific applications.

With one of the industry's broadest lines, CTS can provide you with everything from custom crystals to OCXO's, including military/QPL crystals and oscillators.

When it comes to custom crystals and oscillators, check with the industry leader. Call CTS today for more information on our full-line of custom frequency control products.

CTS
CORPORATION

*Around The World,
Your Single Source For ExcellenceSM*

CTS Frequency Controls

400 Reimann Ave., Sandwich, IL 60548, Tel: 815/786-8411, Fax: 815/786-9743

based, European Community-designated Competent Body. To receive the certification, a one week on-site review of Retliff's Quality Assurance, Calibration and Administrative Procedures as well as its Training and Technical Capabilities, was conducted. As a result, Retliff's test data can now be accepted for use in the Technical Construction Files ITI generates to attest to the compliance of

products to the EC EMC Directive.

Education Foundation Endowed by Wayne Kay Estate

— The estate of E. Wayne Kay has endowed \$1.5 million to the Manufacturing Engineering Education Foundation of the Society of Manufacturing Engineers in Kay's memory. The monies will be used exclusively for scholarships provided by the SME

Foundation. For information regarding the SME Foundation and the Wayne Kay Scholarship Fund, contact the SME Foundation, One SME Drive, PO Box 930, Dearborn, MI 48121. Tel: (313) 271-1500, ext. 511 or 512.

Cubic Defense Systems Awarded \$12.8 Million Contract

— Cubic Defense Systems was recently awarded a \$12.8 million contract for their personnel locator systems by the U.S. Army's Communications and Electronics Command. The contract is a follow-on to an existing one and calls for \$9 million with an option for an additional \$3.8 million. Deliveries are scheduled during fiscal years 1993-1995.

Teklogix and Atlet AB Sign Strategic Agreement

— Teklogix International and Atlet AB recently announced the signing of an agreement for the distribution of Teklogix radio frequency data communications (RF/DC) systems in Europe. Atlet and Teklogix already had a business alliance in the United Kingdom and will now distribute Teklogix RF/DC products and systems in Sweden and Holland. Teklogix's new European subsidiary, Teklogix GmbH will take over all of the Atlet Mobile Terminal Systems staff in Germany.


Malaysian Radio System Contract

— The Government of Malaysia has signed an \$81 million contract with Motorola's Land Mobile Products Sector to provide the Royal Malaysian Police with a public safety radio communication system. The contract was awarded in an open tender for the supply, delivery and commissioning of an integrated VHF telecommunication system. Under the terms of the contract, Motorola will provide the Royal Malaysian Police with its Advanced Securenet System™. The system offers communication security through digital voice encryption. The new system will be commissioned by early 1994.

Webb Laboratories Relocates

— Webb Labs has announced its relocation to a new facility. Their new address is 13731 W. Capitol Drive, Suite 260, Brookfield, WI 53005. Their phone and facsimile numbers are unchanged.

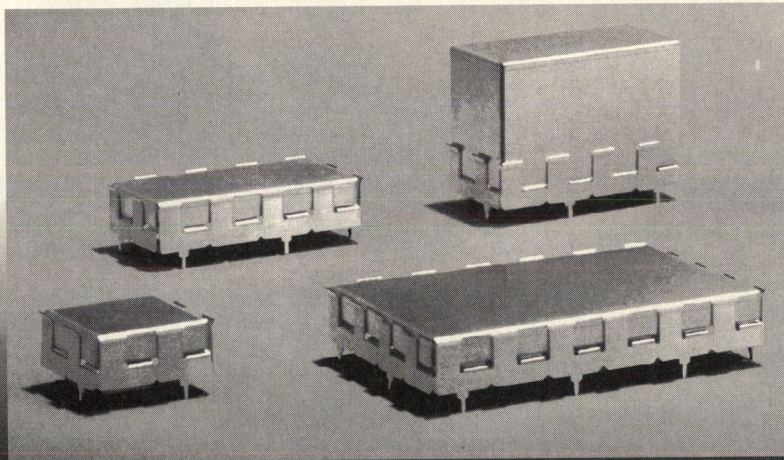NEW! FROM THE LEADING SOURCE OF EMI/RFI SHIELDING
Circuit Board Component Shielding and RF Cans



Leader Tech's new Circuit Board Shielding provides board level protection from EMI. Available in a broad range of sizes the snap-in dimple design provides a positive contact and downward stop while allowing removal of the cover for component accessibility.

- Hundreds of standard sizes and configurations
- No tooling costs
- Rugged design
- Superior shock and vibration resistance
- Leader Tech quality and service

Call or write for technical information and samples



14100 McCormick Drive
Tampa, Florida 33626
(813) 855-6921
FAX (813) 855-3291

ULTRA-BROADBAND RF POWER AMPLIFIER SYSTEMS

From KALMUS ENGINEERING, Of Course!



EMI-EMC-RFI

- AC Operation
- Fully Protected
- Drive Mismatched Loads
- No VSWR Shutdown
- ALC Flat Gain Response
- Remote Functions
- Lowest Prices

ALL SOLID-STATE MOS-FET RF AMPLIFIER SYSTEMS

MODEL	RF OUTPUT	FREQUENCY RANGE	GAIN	SPECIAL USA PRICE
700LC	1.5W CW	.003-1000 MHz	33dB	\$ 1,550
704FC	4W CW	.5-1000 MHz	33dB	\$ 1,995
210LC	10W CW	.008-225 MHz	40dB	\$ 2,295
710FC	10W CW	1-1000 MHz	40dB	\$ 5,895
*727LC	10W CW	.006-1000 MHz	44dB	\$ 6,995
225LC	25W CW	.01-225 MHz	40dB	\$ 2,995
*737LC	25W CW	.01-1000 MHz	45dB	\$ 8,595
712FC	25W CW	200-1000 MHz	45dB	\$ 6,695
250LC	50W CW	.01-225 MHz	47dB	\$ 4,880
715FC	50W CW	200-1000 MHz	47dB	\$ 13,995
707FC	50W CW	400-1000 MHz	50dB	\$ 8,995
*747LC	50W CW	.01-1000 MHz	47dB	\$ 17,550
116FC	100W CW	.01-225 MHz	50dB	\$ 7,995
709FC	100W CW	500-1000 MHz	50dB	\$ 15,550
717FC	100W CW	200-1000 MHz	50dB	\$ 19,500
*757LC	100W CW	.01-1000 MHz	50dB	\$ 24,995
122FC	250W CW	.01-225 MHz	55dB	\$ 13,950
723FC	300W CW	500-1000 MHz	55dB	\$ 27,500
LA500G	500W CW	500-1000 MHz	57dB	\$ 46,500

RUGGED VACUUM TUBE DISTRIBUTED AMPLIFIERS

116C	100W CW	.01-220 MHz	50dB	\$ 8,830
122C	200W CW	.01-220 MHz	53dB	\$ 11,162
134C	500W CW	.01-220 MHz	57dB	\$ 18,810
137C	1000W CW	.01-220 MHz	60dB	\$ 26,172
140C	2000W CW	.01-220 MHz	64dB	\$ 42,740

Warranty: Full 18 months all parts. Vacuum tubes 90 days.

* = Indicates Dual-Band System (coaxial band switching)



1-800-344-3341
(206) 485-9000 fax (206) 486-9657
21820-87th S.E. Woodinville, WA 98072 USA

INFO/CARD 20

The World's Most Complete Line of RF Power Amplifiers

More Than 200 Standard Models
to Choose From

Test Equipment Trends — Processing Power and Automation

By Gary A. Breed
Editor

Recent demonstrations of new test equipment products make two points clear: 1) more power is being put into each box, board or module; and 2) greater access to the units for control and communication is deemed necessary. These enhancements to performance and productivity offer design, test and service personnel greater capabilities, but they require special attention to "human engineering" to avoid making instruments difficult to use due to over-complexity.

Control and Communications

Microprocessor and standard communications buses make test instruments more accessible to the rest of the engineering environment. Extensions to the IEEE-488/GPIB bus have increased its capability, and the continuing growth in VXI bus instrumentation systems is an example of reliance on communications among the various test, analysis and record-keeping functions.

On a smaller scale, local setups can be controlled by the internal processor that may be in one or more of the instruments used. For example, Hewlett-Packard has optional IBASIC controller software, external keyboards, and simplified programming capabilities to eliminate the need for a dedicated controller. Tests can be coordinated among various instruments and collected for network collection or diskette storage.

At the single-box level, screen display interfaces to plotters and printers allow hard-copy communications with greater ease than ever. The IFR 8000 Spectrum Analyzer, for example, has an internal controller that is essentially a PC, allowing standard interfaces to peripheral devices. Preset test sequences let engineers run standard tests without having to set them up each time. Anritsu-Wiltron has also done extensive work in developing test and analysis software for key applications for their 360 network analyzer.

Processing Power

Inside the latest generation of high

performance test instruments is real computing power using both micro-processor and dedicated digital signal processing (DSP) components. Mathematical manipulation of measured data allows quick decisions instead of post-test analysis. Limit lines, frequency and bandwidth computations and searches for predictable harmonic and spurious responses save considerable operator time. Fast Fourier Transform (FFT) analysis in DSP allows precise time- and frequency-domain analysis. The availability of computing power has created fast frequency counters, which measure the period of each cycle of a waveform instead of the conventional many cycles per unit time.

In signal generating equipment, processing power allows for complex modulation that is completely arbitrary (within the limits of the digital architecture used). Spread spectrum signals, complex vector modulation, video, chirp and pulse formats are all available in a single instrument. Multiple tests can be performed under computer control with fewer instruments.

High precision digital processing requires analog circuitry that is better than ever. High dynamic range front ends, low distortion amplification, low noise, fast frequency synthesizers and optimal filtering are all essential in the analog portion of digitally-enhanced test equipment. This combination of technologies has led to rapid advances in the performance of RF test equipment.

A logical follow-on is greater integration of instruments, computers, controllers and accessories. This is especially important in automated test systems, where instruments must be compatible with a common controller. Development of instruments for the VXI bus is primarily aimed at automated test systems. VXI bus products are generally smaller, and can be combined into a compact test package, saving room on the manufacturing floor when used in production testing. Racal-Dana, Hewlett-Packard, EIP Microwave, Gigatronics and others continue to invest in VXI bus products.

PC-based instrumentation is beginning to increase. General purpose instruments such as voltmeters, data acquisition systems and low frequency oscilloscopes have been around for some time, but few RF products have been available until recently. Among the most complex PC-card instruments is the Morrow Technologies 9052 spectrum analyzer that has high performance specifications and plenty of operating features. Inline Components offers an HF receiver card with full programmability for surveillance and other applications. Also offering PC-card products are Pole-Zero with hopping filters, and Guide Technology, which offers fast frequency counters.

Equipment Cost Trends

Competition and customer demand has led to an interesting situation — many features and processing power are being added without increasing the cost over previous models. In some cases, prices are being reduced as performance edges ahead. Some of this new-found value is in response to a slow economy, but it is also partly a result of competition. Economy instruments have improved, closing the gap between themselves and the bottom of the premium instrument lines. At the same time, the state-of-the-art has been advancing for the most critical applications. This overall upward trend in performance is helping instrumentation customers keep their costs under control. The instrumentation industry has been significantly affected by the economic downturn of the past few years. Test equipment is part of a customer's capital budget, which has been cut drastically at most firms. Only by offering more performance at the same or lower cost can instrument makers entice their customers to fight for extra test equipment budget dollars in a tight economy. *RF*

For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600. Ask for the Circulation Department.

The Easiest Test You'll Ever Take

2-1100 MHz Signal Generator

Scalar Network Analyzer with 66 dB Dynamic Range

0.0005% Frequency Accuracy

14" Color VGA Monitor

LCD screen provides status of all instrument settings


A small footprint means more space for you

Marker amplitudes are indicated in trace colors

Marker search functions provide continuous updating

Color limits and Pass/Fail indicators make Go/No Go tests simple

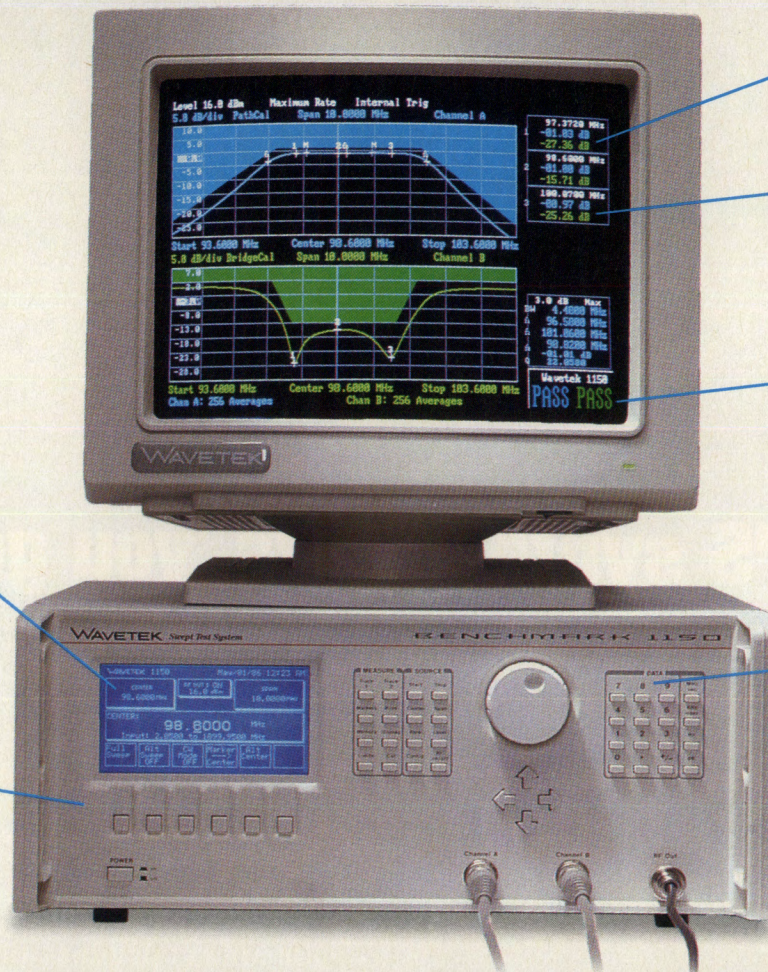All major functions are at your finger tips



The Scalar Analyzer Preferred By Technicians

Small details make a big difference, especially when they involve exacting measurements and long hours of critical daily testing. The Benchmark 1150 Scalar Analyzer is packed with innovative features designed to enhance productivity and accuracy, and is simple to use.

Imagine working with the Benchmark's large 14" high-resolution color display!

Now it's easy to see a small 0.1dB adjustment that could be the difference between a marginal DUT and one that passes with flying colors. Match that display to the industry's smallest analyzer footprint, and you have a unit that leaves ample room for your test fixtures *and* is easy on your eyes.

Most technicians can be productive on the Benchmark in less than one day, with a minimum of retraining.

Highly visible color screens reduce trace and limit confusion, and make most operator functions virtually effortless.

The Benchmark is as easy on your budget as it is on your staff. Put the Benchmark 1150 to the test. You'll be positively impressed with its performance and price. Call your local Wavetek representative for more information or for a product demonstration.

800-622-5515 317-788-5965

You don't always get what you pay for.



With PTS synthesizers, you get more.

Because we're synthesizer specialists, we give you *more for your money* in more ways than one.

From our economy PTS x10, to our space-saving PTS 310, to our top-of-the-line PTS 1000, we have *more models* to cover your source needs from 100 KHz to 1 GHz.

And more options, including:

- OCXO, TCXO or external standard,
- choice of resolution from 100 KHz to 0.1 Hz,
- DDS with phase-continuous switching,
- digital phase rotation,
- BCD or GPIB remote control,

and almost a hundred others to let you specify a synthesizer so well-tailored to your requirements that it's like having one custom made for you.

Our priority in design and manufacturing is to make our synthesizers *more reliable*, and this has led to a demonstrated MTBF of 25,000 hours. That's why we can back them with our all-inclusive 2-year warranty, along with a flat-rate service charge for eight years following the warranty period.

But wait, there's less!

All of our synthesizers feature *low power consumption*, *low spurious output* (as low as -75 dBc), *low phase noise*, and *fast frequency switching* (as fast as 1 μ second).

And all of our models are available, at a lower price, in a remote-only OEM configuration for easy integration into your OEM system.

Our full catalog has all the information you need to specify the most synthesizer for your money.

Call or FAX us for your copy, or for immediate engineering assistance.



PTS

PROGRAMMED TEST SOURCES

P.O. Box 517 Littleton, MA 01460
508/486-3008 FAX 508/486-4495

Simulating Lossy Transmission Lines With PSpice®

By Walter Banzhaf, P.E.
Ward College, University of Hartford

MicroSim Corp. has added a lossy transmission line element to its analog circuit simulator PSpice, allowing attenuation and dispersion to be included in circuit simulations. This now makes PSpice, an established tool for the analog circuit designer, a powerful software package for the RF circuit designer.

The Berkeley SPICE analog circuit simulator, in addition to basic circuit elements (independent and dependent voltage and current sources, resistors, capacitors, inductors and semiconductors) includes a transmission line circuit element which is lossless. While this is a reasonable approximation for physically short lines, such as those that might be found within an integrated circuit or on a small circuit board, for many other applications the transmission line loss and dispersion must be included if circuit behavior is to be predicted accurately. MicroSim Corporation, which developed PSpice, included the capability for describing a lossy transmission line in a recent release (1) (Version 5.1, January 1992).

When a circuit simulation is done, an input file is submitted to SPICE or PSpice which describes all circuit elements and the kind of analysis desired. The location of circuit elements is done by specifying the numbers of the circuit nodes to which it is connected. The type of element is indicated by the first letter of the element name: resistors begin with R, capacitors with C, and transmission lines with T. In order to describe a lossless transmission line to SPICE (or PSpice), an element line must be added to the input file. The element line would look like:

```
T_STUB 5 0 12 26 Z0=72 F=50MEG NL=0.5
T_STUB 5 0 12 26 Z0=72 TD=10E-9
```

The two element lines above are equivalent and describe the same line; the first locates the input of lossless transmission line T_STUB between nodes 5 and 0, the output between nodes 12 and

26, and describes a line with a characteristic impedance of 72 ohms which at 50 MHz has an electrical length of 0.5 wavelength. The second element line expresses the line length by using its delay time of 10 ns.

A transmission line with loss can be described to PSpice in a similar way; however, instead of specifying the characteristic impedance, the primary line constants, R (loss per meter), L (inductance per meter), C (capacitance per meter) and G (conductance per meter) must be given along with the physical (as contrasted with electrical) length of the line. An element line for a lossy transmission line would look like:

```
T_STUB 5 0 12 26 LEN=3.048 R=2 L=.3U
+ G=50U C=120P
```

This line is 3.048 meters (10 feet) long, and has primary line constants of 1.665 ohms, 0.3uH, 50 uS and 120pF per meter. The plus symbol (+) in the second line makes it a continuation of the first line. Notice that the characteristic impedance, attenuation and electrical length are not explicitly stated. The next section will illustrate how to derive primary line constants from transmission line data supplied by manufacturers.

Data about a transmission line obtained from manufacturers' literature (2) often includes the characteristic impedance, the capacitance per foot, and the attenuation in dB per 100 feet. For example, for an RG-58C coaxial cable, Z_0 is 50 ohms, C is 30.8 pF/ft, and at 100 MHz, loss is 4.9 dB/100 ft. In order to describe a lossy transmission line to PSpice, the primary line constants (R, L, G and C) must be extracted from the data above. The first step is to convert C to pF/meter by multiplying by 3.2808, resulting in C = 101 pF/m. Since for high frequencies (3) $Z_0 = \sqrt{L/C}$, L can be found from:

$$L = Z_0^2(C) = 50^2(101 \times 10^{-12}) = 0.2526 \text{ nH/m} \quad (1)$$

The loss of 4.9 dB/100 feet can easily be converted to 0.1608 dB/m (by dividing by 30.48), which in turn is 0.0185 neper/m (1 neper = 8.686 dB). When a transmission line is operated at high frequencies, (valid when $\omega L \gg R$ and $\omega C \gg G$) an approximate expression for transmission line loss, α , in neper/m, is: (4)

$$\alpha \approx R / (2Z_0) + G(Z_0 / 2) \quad (2)$$

In the absence of detailed knowledge about skin effect losses and dielectric losses, one way to convert this loss to the primary line constants R and G involves making an educated guess. Since most of the loss of a coaxial transmission line at high frequencies comes from the resistance of the center conductor (R) (5), as an approximation 90 percent of the loss can be assigned to R. This is reasonable, as the dielectric losses are small compared to the conductor losses for most transmission lines up through microwave frequencies (5). Thus, $0.9(\alpha) \approx R / (2Z_0)$, and R can be found from:

$$R \approx 0.9(\alpha)(2Z_0) \approx 0.9(0.0185)(2)(50) \approx 1.665 \Omega / \text{m} \quad (3)$$

Similarly, if the remaining 10 percent of the loss is assigned to G, $0.1(\alpha) \approx G(Z_0)/2$, and

$$G \approx 0.1(2)(\alpha) / Z_0 \approx 0.1(0.0185)(2) / (50) \approx 74 \mu\text{S} / \text{m} \quad (4)$$

A more analytical method which will give the R and G constants for a transmission line requires that the loss tangent of the dielectric, δ , be known at the operating frequency. For high frequency operation, the relationship between δ and G is (6):

$$G = \omega C \tan \delta \quad (5)$$

For RG-58C, which has a solid polyethylene dielectric, the loss tangent is approximately 0.0002 at 100 MHz (7).

Once δ is known, G can easily be found, and then R can be determined. To illustrate how to use this method, at 100 MHz:

$$G = 2\pi(100 \times 10^6)(101 \times 10^{-12})$$

$$\tan(2 \times 10^{-4}) = 12.7 \mu\text{S/m} \quad (6)$$

Since $\alpha \approx R/(2Z_0) + G(Z_0/2)$, and α was found previously to be 0.0185 neper/m, the equation can be rearranged to give R :

$$R = [\alpha - G(Z_0/2)](2Z_0) = 2Z_0\alpha - GZ_0^2$$

$$R = 2(50)(.0185) - 12.7 \times 10^{-6}(50)^2 \quad (7)$$

$$= 1.82 \Omega / \text{m}$$

The results for R are close for the two methods, while the results for G differ considerably. However, since the effect of the G parameter is quite small compared to the R parameter, often the simpler method where 90 percent of the

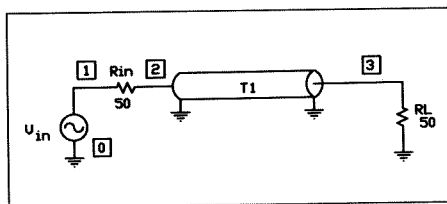


Figure 1a. Matched line fed by AC source.

```

EXAM1.CIR      Lossy RG-58C, Sinusoidal Input
VIN 1 0 AC 2
RIN 1 2 50
*
* Units below are per meter,
* determined from manufacturer's data.
T1 2 0 3 0 LEN=30.48 R=1.665
+ L=.2526U G=74U C=101P
RL 3 0 50
.AC LIN 21 80MEG 120MEG
.PROBE
.END
  
```

Figure 1b. PSpice input file EXAM1.CIR.

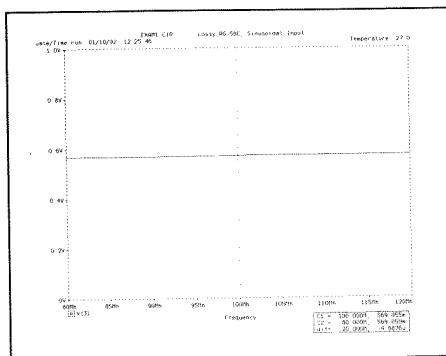


Figure 1c. PSpice analysis results for EXAM1.CIR.

loss is attributed to R and 10 percent is attributed to G gives satisfactory results. Once the primary line constants have been determined, the lossy transmission line, at 100 MHz, can now be described to PSpice. This will be illustrated in Example 1, below, using the parameters obtained with the simpler method.

Example 1: Matched Line At 100 MHz

A 100-foot length of RG-58C will be described to PSpice as a lossy transmission line, terminated by a matched load, connected to a sinusoidal source which is varied from 80 MHz to 120 MHz. Figure 1a is the diagram of the circuit, with node numbers shown. Note that the generator has a 50 ohm output impedance and an open-circuit voltage of 2 V. The input file which describes the circuit is shown in Figure 1b, where the primary line constants (R , L , G and C) are given along with the length (30.48 meters, or 100 feet).

The PSpice analysis results, Figure 1c, show that the load voltage, $V(3)$, is constant at 569 mV as the frequency varies from 80 MHz to 120 MHz. If the line were lossless, the load voltage would be 1 V. The line loss, given by $20(\log(1V/.569V))$, is 4.90 dB, which agrees with the original manufacturer's data at 100 MHz. It should be noted here that the parameters R and G , which determine the loss of the transmission line, are constants to PSpice, whereas in reality they increase with frequency (R varies with the square root of frequency, and G varies linearly with frequency) (8).

Example 2: Pulses On A Matched Line

A 100 MHz pulse train is fed into a ten-foot length of RG-58C which is terminated by a matched load. The circuit is shown in Figure 2a, and Figure 2b is the input file describing this circuit. Notice that the length parameter, LEN , is 3.048 (understood to be in meters), equivalent to ten feet. Figure 2c shows the pulses at the transmission line input on top, and the pulses across the load resistor on the bottom. A ten-foot length of RG-58C has a propagation time of 15.4 ns, which can be seen as the time delay between the first pulse occurring at the input and the output. The output pulses are slightly lower in amplitude than the input pulses, due to line attenuation.

Example 3: Z_{in} of Unmatched Line at 100 MHz

Figure 3a shows a one amp sinusoidal current source feeding a ten-foot lossy RG-58C transmission line which is terminated by a five ohm resistor. A one amp current source is used so that the voltage at the transmission line input is the same as the input impedance of the line. The load has a VSWR of 10:1, which means that as frequency varies the input impedance of the transmission line can vary between a minimum of $5+j0$ ohms and a maximum of $500+j0$ ohms (if the line were lossless). The impedances between $5+j0$ ohms and $500+j0$ ohms will be reactive, with a non-zero imaginary component. The input file describing this circuit is shown in Figure 3b, and specifies that PSpice perform an AC analysis at 201 frequencies linearly spaced between 80 MHz and 120 MHz.

The input impedance is presented two

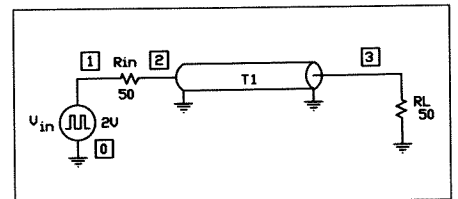


Figure 2a. Matched line fed by pulse source.

```

EXAM2.CIR      Lossy RG-58C, Pulse Input
VIN 1 0 PULSE(0 2 2N .1N .1N 10N)
RIN 1 2 50
*
* Units below are per meter, determined
* from manufacturer's data, at 100 MHz.
T1 2 0 3 0 LEN=3.048 R=1.665
+ L=.2526U G=74U C=101P
RL 3 0 50
.TRAN .1N 30N
.PROBE
.END
  
```

Figure 2b. PSpice input file EXAM2.CIR.


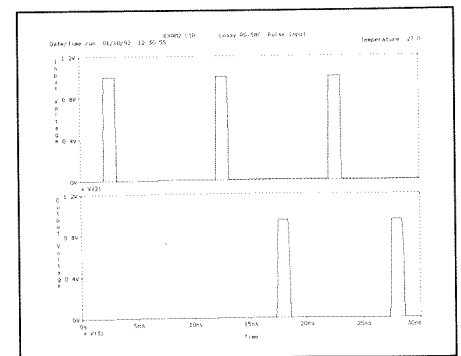


Figure 2c. PSpice analysis results for EXAM2.CIR.

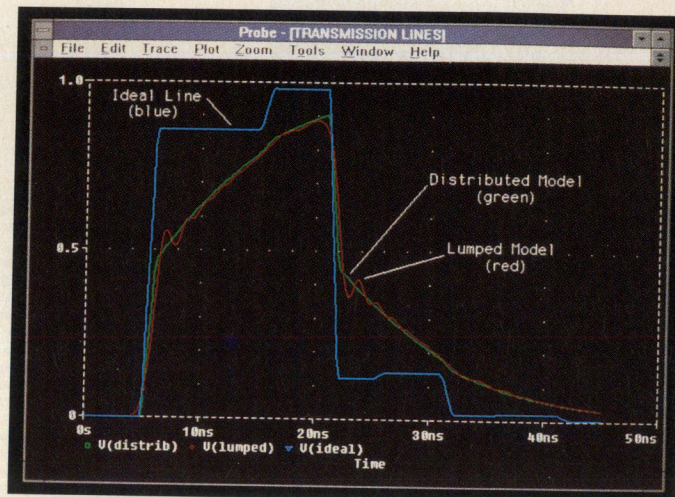Our Lossy Transmission Lines Have the Edge!



Comparison of the ideal and lossy transmission line models

Greater Accuracy and Faster Simulation

That's our lossy transmission line edge. We've extended PSpice's intrinsic T device to model lossy transmission lines using the distributed model rather than the traditional lumped approach. What you get is a smoother approximation of the line's behavior in significantly less time. Here's why.

The Distributed Model Advantage

Our lossy line behavior is modeled in the frequency domain instead of with the commonly used ladder structures associated with lumped models. Using this technique, lossy lines can be easily specified in terms of their electrical length and the resistance, inductance, capacitance, and conductance distributed along the entire length of the line. Frequency dependent phenomena, such as skin effect and dielectric loss, is straightforward to simulate.

Elimination of Spurious Oscillations

Our lossy lines are modeled as continuous lines. Thus, the simulation artifacts (oscillations) observed in lines modeled as a finite set of lumped segments, vanish with the distributed model.


Optimized Simulation Performance

For any given circuit, the continuous lines produced by a distributed model avoid the performance overhead created by the multiple line segments required for accurate results using the lumped model approach. Hence, simulation time can be several times faster with the distributed model.

Model Loss, Dispersion, and Skin Effect with Accuracy and Efficiency

That sums up the PSpice lossy line edge. Discover for yourself why PSpice continues to hold the industry edge on mixed analog and digital circuit simulation.

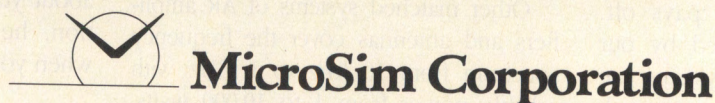For more information on PSpice and the **Design Center**, call MicroSim Corporation toll free at (800) 245-3022 or FAX at (714) 455-0554.




The Standard for Circuit Design

20 Fairbanks • Irvine, CA 92718

THE MAKERS OF PSpICE

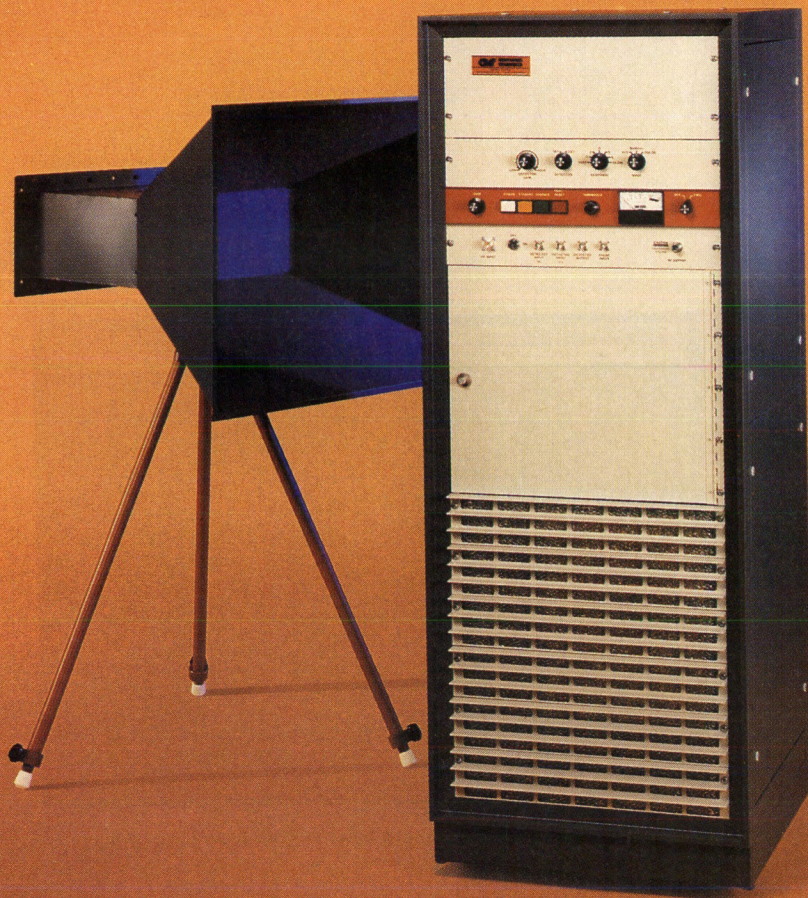PSpice is a registered trademark of MicroSim Corporation



200-V/m susceptibility testing: Your fields shouldn't fade as the frequencies rise.


A broadband amplifier that's operating Class A isn't squandering a good portion of its output power to feed unwanted harmonics. And superior load/VSWR tolerance keeps it pumping its full rated power even under outrageous mismatch conditions.

Let's compare the actual minimum output of our two newest high-power Class A solid-state amplifiers with some well-regarded Class AB amplifiers. You could buy a 1,000-watt Class AB amplifier and wonder why it can't give you more than 450 watts. The reason is its inherent load/VSWR foldback. Think about what that would do to the fields you *think* your kilowatt is generating.

In the band from 400 to 1,000 MHz, Class A performance really pays off. Notice how the fields created by our matched amplifier/antenna systems are maintained and even increase in strength

as the frequencies rise. Conservatively rated, our models 500HB and 1000HB deliver a *minimum* of 500 and 1,000 watts respectively throughout the 400-1,000 MHz frequency range. And our Series AT4000 horn antennas display the happy faculty of maintaining the field level as the frequency sweep goes up. To assure yourself of the 200-volts-per-meter field at every sampling in the test, you need the *team* of amplifiers and antennas that comes only from AR.

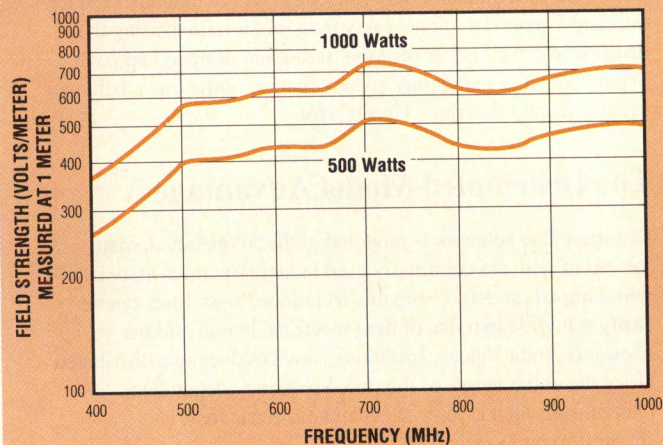Other matched systems of AR amplifiers and antennas cover the frequency spectrum from 10 kHz to 1 GHz with reliable power from 1 to 10,000 watts.



You can get systems for generating fields as low as 20 V/m through that entire five-decade range, up to and beyond the 200-V/m systems shown here.

If you'd like to chat—on our nickel—with one of our applications engineers about your rf susceptibility-testing situation, he'll answer the phone himself when you dial **1-800-933-8181**.



160 School House Road • Souderton, PA 18964-9990 USA • TEL 215-723-8181 • FAX 215-723-5688

For engineering assistance, sales, and service throughout Europe, call EMV • Munich, 89-612-8054 • London, 908-566-556 • Paris, 1-64-61-63-29

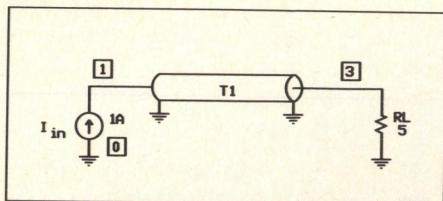


Figure 3a. Mismatched line fed by sinusoidal current source.

```

EXAM3.CIR      Lossy RG-58C, Sinusoidal Input
*             Current Input Gives Zin Directly
* IIN 0 1 AC 1
*             Units below are per meter,
*             determined from manufacturer's data.
T1 1 0 3 0 LEN=3.048 R=1.665
+ L=.2526U G=74U C=101P
RL 3 0 5
.AC LIN 201 80MEG 120MEG
.PROBE
.END

```

Figure 3b. PSpice input file EXAM3.CIR.

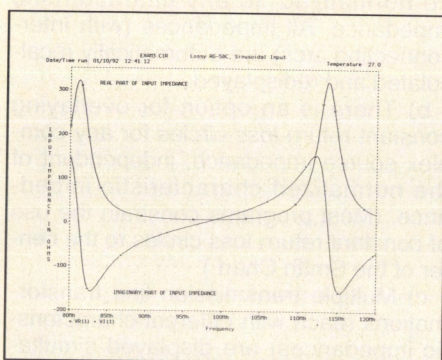


Figure 3c. Real and imaginary input impedance vs. frequency.

different ways: Figure 3c is a graph of the real and imaginary parts of the input impedance of the transmission line versus frequency, while Figure 3d plots the imaginary impedance versus the real impedance. Figure 3c shows that the real part of the input impedance reaches a maximum of 321 ohms at about 81.2 MHz, and a minimum of 7.8 ohms around 100 MHz; at both these frequencies, since the imaginary component is zero, the input impedance is purely real. Due to the attenuation of the transmission line, the maximum input impedance is less than 500 ohms and the minimum is more than 5 ohms. The cyclical nature of the input impedance can be seen also in Figure 3d, whereas frequency varies the plot of the impedance imaginary part versus the impedance real part describes a circle. If the PSpice internal transmission line model allowed loss to increase with frequency, Figure 3d would be a spiral whose radius decreased as frequency increased.

Conclusion

PSpice now has the capability of simulating circuits containing lossy trans-

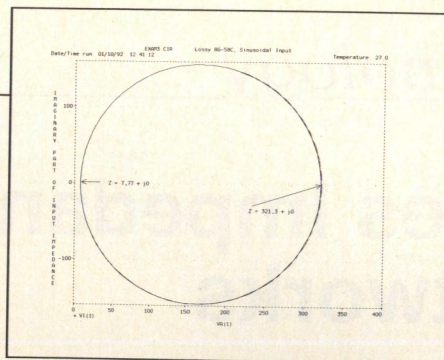


Figure 3d. Imaginary input impedance vs. real input impedance.

mission lines. The transmission line is described to PSpice by its primary line constants (R, L, G and C) and its physical length. The primary line constants for any transmission line can easily be derived from manufacturers' data. Information on PSpice, including an evaluation version, may be obtained from MicroSim Corporation, 20 Fairbanks, Irvine, CA 92718, (714) 770-3022. **RF**

References

1. *Circuit Analysis User's Guide*, Version 5.1, MicroSim Corporation, Irvine, CA., 1992.
2. *RF Transmission Line Catalog and Handbook*, Times Fiber Communications, Inc., 1972, Wallingford, CT.
3. Dennis Roddy, *Microwave Technology*, Reston/Prentice Hall, 1986, pp.13-14.
4. *Reference Data for Radio Engineers*, 4th Ed., International Telephone and Telegraph Corp., 1956, pp. 552-54.
5. C.W. Davidson, *Transmission Lines for Communications*, Halsted Press, 1978, pp. 66-68.
6. Stephen F. Adam, *Microwave Theory and Applications*, Prentice Hall, Inc., 1969, p. 36.
7. *Reference Data for Radio Engineers*, 4th Ed., International Telephone and Telegraph Corp., 1956, p. 66.
8. Stephen F. Adam, *Microwave Theory and Applications*, Prentice Hall, Inc., 1969, p. 41.

About the Author

Walter Banzhaf is professor and department chair at Ward College of Technology, University of Hartford. He has BEE and MEE degrees from RPI, and previously worked on antenna systems at the Naval Underwater Systems Center. He is the author of the Prentice Hall book *Computer-Aided Circuit Analysis Using PSpice*, and can be reached at: U of Hartford, West Hartford, CT 06117, or by telephone at (203) 768-4764.

SC CUT CRYSTALS!

PIEZO CRYSTAL COMPANY... THE WORLD LEADER.

Piezo's SC cut crystals are the secret to optimum precision timekeeping, communications, navigation (GPS), electronic systems, and instrumentation.

You can expect this kind of performance:

- Aging rates of 5×10^{-12} /day
- Warm-up within 1×10^{-9} of final frequency in less than 1½ minutes
- Time domain stability to 1×10^{-12} /second
- Vibrational sensitivity to 2×10^{-10} /g
- Available 3 to 200 MHz

PIEZO CRYSTAL COMPANY is an innovator in quartz crystal design with over 50 years experience in satisfying customer requirements.

Contact an Applications Engineer to discuss *your* requirements.



100 K Street • P. O. Box 619
Carlisle, PA 17013
Phone 717-249-2151
FAX 717-249-7861

MIMP Analyzes Impedance Matching Networks

By Dan Moline
Motorola Semiconductor Products Sector

This is the age of computer aided design. Most engineers have sophisticated tools at their disposal to synthesize, analyze, optimize and help fabricate RF circuits. These programs are typically priced in the thousands of dollars. Their degree of complexity and versatility generally warrants this price. So, what earthly good is a "freeware" program that can only do simple impedance matching?

Motorola's Impedance Matching Program(1) (MIMP, programmed using the Microsoft® C Professional Development System, Version 6.0) is a specialized form of CAD specifically developed for RF power amplifier circuit design. It provides a simple environment for entering and analyzing impedance matching circuitry. Commercially available programs include a multitude of circuit elements and provide numerous analytical capabilities. However, MIMP focuses only on impedance transformations. This type of analysis is more important than others for most RF power amplifier design problems, since data sheets for RF devices present only large signal impedances, representing a single combination of frequency, voltage, power

level and power dissipation. These impedances must generally be transformed to another set of impedances (50 ohms or the input/output impedance of another device). To do this, MIMP includes a standard library of passive circuit elements, including various combinations of capacitors, inductors and transmission lines in both series and shunt configurations. It also contains a unique, distributed capacitance element that models a capacitor distributed along a transmission line.

The real nucleus of MIMP is its computer aided Smith™(2) Chart. It is uncommon for CAD programs to incorporate the benefits of manipulating actual impedance transformations on a Smith Chart. If commercially available programs were used for merely impedance matching, a typical final result of a computer run would be: S11 vs. frequency. To supplement this, many RF designers still keep a Smith Chart, compass, straight edge and pencil handy so they can pictorially represent each circuit component's contribution to the total transformation. MIMP's Smith Chart facility provides this service — electronically. It also displays each circuit element's contribution to the total imped-

ance transformations. Simply stated, it is an electronic form of a standard, printed Smith Chart. Some of the unique features of the Smith Chart display screen include:

- a) The Smith Chart can be instantly 're-normalized' to any characteristic impedance. All impedances (with interconnecting arcs) are automatically recalculated and redisplayed.
- b) There is an option for overlaying constant return loss circles for any complex source impedance, independent of the normalized characteristic impedance. (Most programs constrain the use of constant return loss circles to the center of the Smith Chart.)
- c) Multiple transmission line transformations (each with different characteristic impedances) are displayed simultaneously and in exact graphical relationships to each other, independently of the Smith Chart's normalized impedance. (Drawing transmission line transformations by hand requires an iterative denormalize/renormalize/replot/redraw procedure.)
- d) A tabular impedance display is provided to view the impedance at any 'node'.
- e) Constant Q arcs can be added to

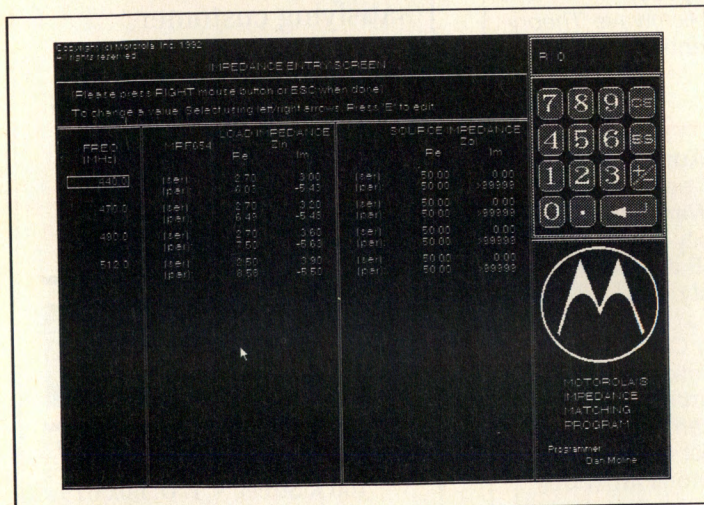


Figure 1. Impedance entry screen.

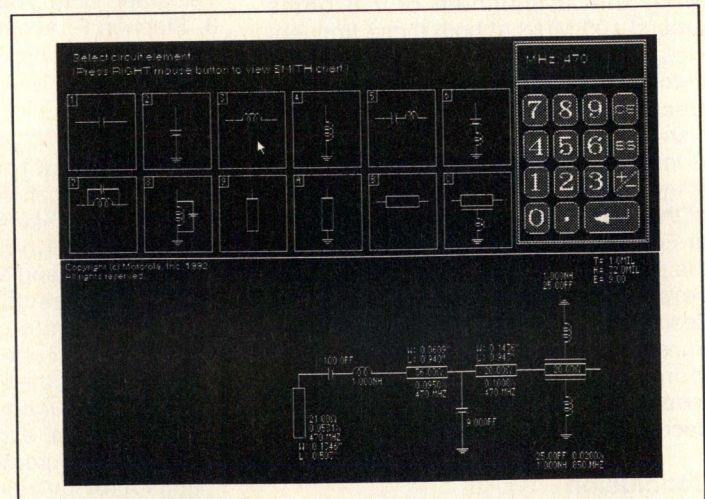


Figure 2. Circuit entry screen.


Need a relay matrix? Come to Matrix.

Since 1969 Matrix Systems has been designing reed relay and solid state switching modules, matrices and complete systems built to rigid specifications for defense contractors, government agencies, the TV industry, ATE and Telecom companies. Matrix Systems has supplied thousands of unique switching systems, with computer interfaces, control panels, status indicators and power supplies.




**AUDIO MATRIX
MODEL 10980**

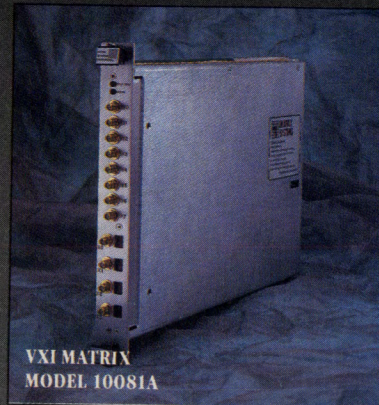- 48 x 48 2-wire non-blocking matrix configuration
- Wide bandwidth: DC to 150kHz
- Both RS-232C and IEEE-488 interfaces are "built-in"
- Solid-state crosspoint design with intelligent control CPU, plus front panel control keypad and LCD display
- Lightweight and compact



**VXI MATRIX
MODEL 10081A**

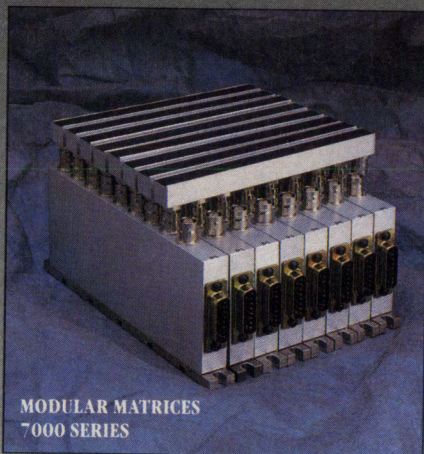- 4 x 8 blocking matrix configuration
- Extremely wide bandwidth: DC to 900MHz
- C-size single wide VXI module
- 50 and 75 ohm versions



**MODULAR MATRICES
7000 SERIES**


- Variable matrix sizes, from 2 x 2
- Rugged modular design
- Field proven, reed relay technology
- Programmable via IEEE-488 and RS-232C



**3-STAGE MATRICES
MODEL 10693**

- 32 x 32 matrix configuration
- Solid-state and reed switch versions
- DC to 100MHz bandwidth (minimum)
- Efficient 3-stage switching architecture
- Remotely and locally programmable with display

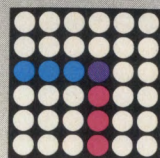So, whether you are switching DC, video, VHF, IF or HF, come to Matrix. Call or fax us for a free catalog.



MATRIX


SYSTEMS CORPORATION

5177 North Douglas Fir Road
Calabasas, California 91302
(818) 222-2301 • Fax (818) 222-2304



RF TRANSFORMERS

Over 80 off-the-shelf models...

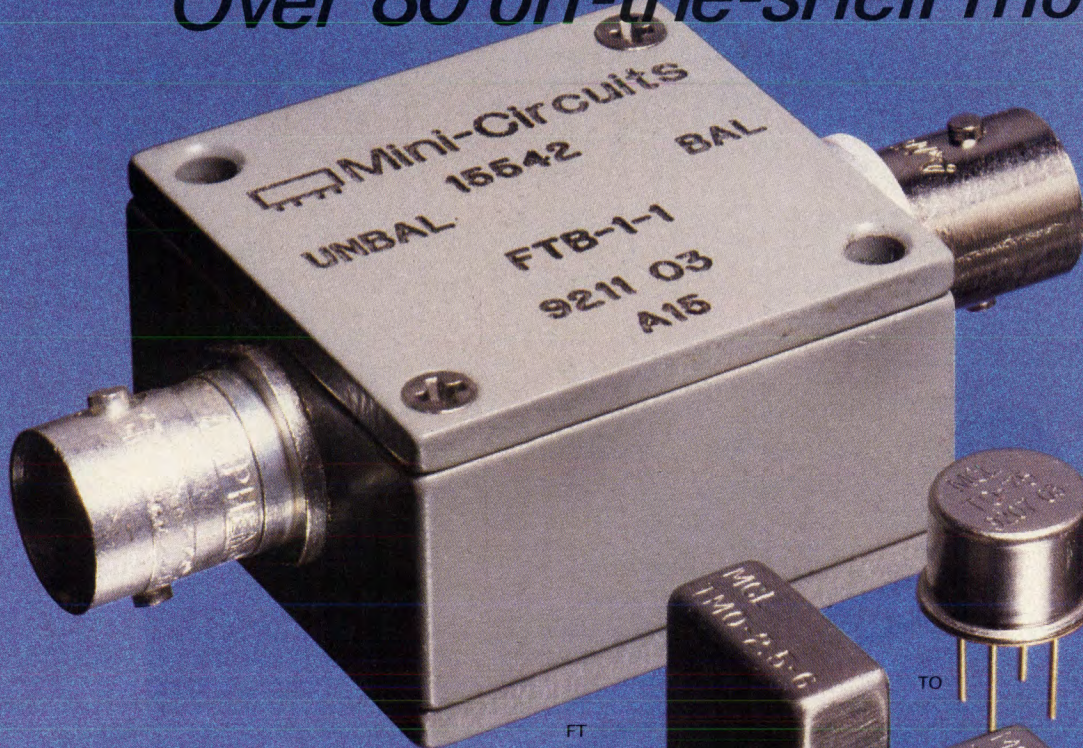


Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specified frequency range?... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, in connector, TO-, flatpack, surface-mount, or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements*). Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard, other types on request.

Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100mA primary current, use the T-H series. Fully detailed data appear in our 740-pg RF/IF Designer's Handbook.

Need units in a hurry?... all models are covered by our exclusive one-week shipment guarantee. Only from Mini-Circuits.

*units are not QPL listed.

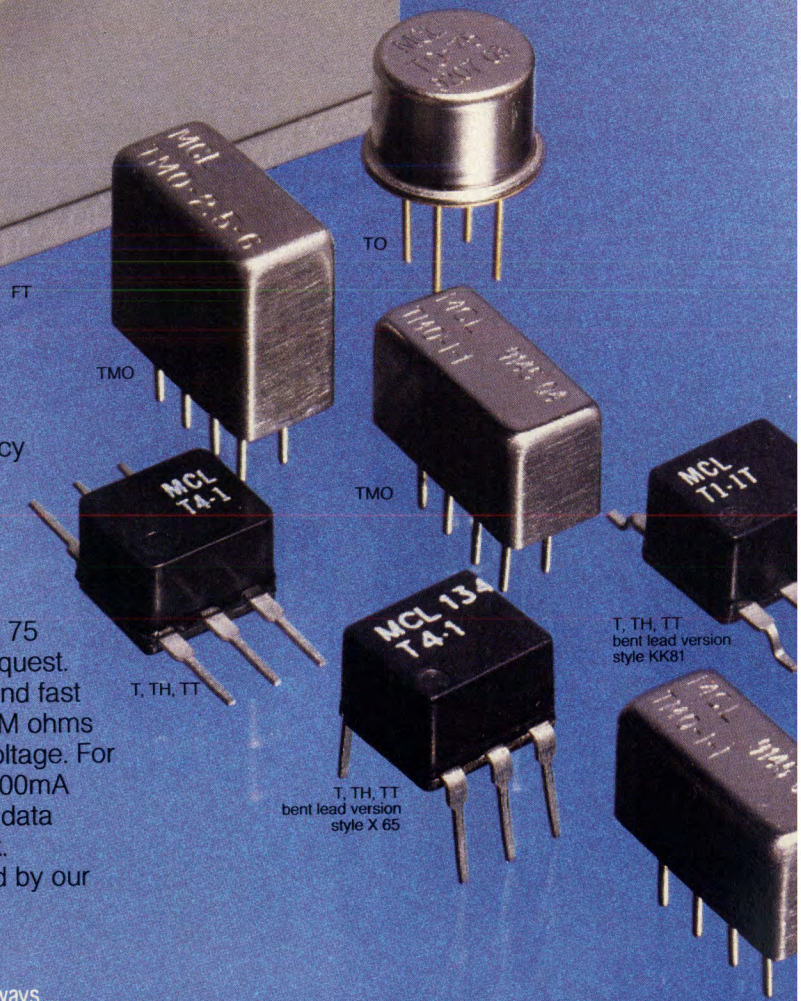

finding new ways...
setting higher standards

Mini-Circuits™

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661







EUROPE 44-252-835094 Fax 44-252-837010

Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-PG HANDBOOK

FORMERS

3KHz-1500MHz from \$195

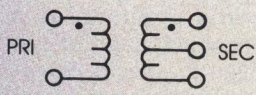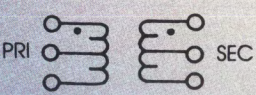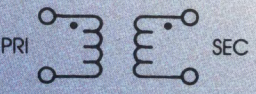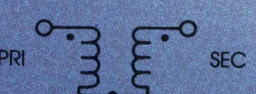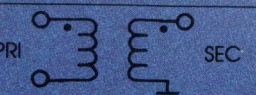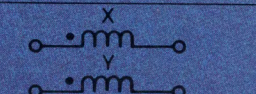	MODEL NO.	Ω RATIO	FREQUENCY MHz	INSERTION LOSS			PRICE \$ Qty. (1-9)		
				3dB MHz	2dB MHz	1dB MHz			
A* 	T	T1-1T	1	.05-200	.05-200	.08-150	2-80	4.45	
		T1-6T	1	.015-300	.015-300	.021-150	.03-50	6.95	
		T2-1T	2	.07-200	.07-200	.1-100	5-50	4.95	
		T2.5-6T	2.5	.01-100	.01-100	.02-50	.50-20	4.95	
		T3-1T	3	.05-250	.05-200	1-200	5-70	4.95	
		T4-1	4	2-350	2-350	35-300	2-100	3.25	
		T4-6T	4	.02-250	.02-250	.05-150	0.1-100	4.45	
		T5-1T	5	3-300	3-300	6-200	5-100	4.95	
		T8-1T	8	0.3-140	0.3-140	0.7-80	1-60	7.95	
		T13-1T	13	3-120	3-120	7-80	5-20	4.95	
		T16-6T	16	0.3-75	0.3-75	0.6-30	1-20	5.65	
		T4-1H	4	10-350	10-350	15-300	25-200	5.95	
		TMO	TMO1-1T	1	.05-200	.05-200	.08-150	2-80	7.95
		TMO2-1T	2	.07-200	.07-200	1-100	5-50	8.45	
		†TMO2.5-6T	2.5	.01-100	.01-100	.02-50	0.5-20	8.45	
		†TMO3-1T	3	.05-250	.05-250	1-200	5-70	7.95	
TMO4-1	4	2-350	2-350	35-300	2-100	6.25			
TMO5-1T	5	3-300	3-300	6-200	5-100	8.45			
TMO13-1T	13	3-120	3-120	7-80	5-20	8.45			
B* 	TT	TT1-6	1	.004-500	.004-500	.02-200	1-50	6.95	
		TT1.5-1	1.5	.075-500	.075-500	2-100	1-50	5.95	
		TT2.5-6	2.5	.01-50	.01-50	.025-25	.05-10	6.45	
		TT4-1	3	.05-200	.05-200	2-50	1-30	5.95	
		TT4-1A	4	0.1-300	0.1-300	0.2-250	0.3-180	6.95	
		TT25-1	25	.02-30	.02-30	.05-20	1-10	9.95	
		TTMO	TTMO25-1	25	.02-30	.02-30	.05-20	1-10	11.95
		TTMO1-1	1	.005-100	.005-100	.01-75	0.5-40	11.45	
		TTMO4-1A	4	0.1-300	0.1-300	0.2-250	0.3-180	13.95	
		C 	T	T1-1	1	.15-400	.15-400	35-200	2-50
T1.18-3	1.18			0.01-250	0.01-250	0.02-200	0.03-50	5.65	
T1-6	1			.01-150	.01-150	.02-100	0.5-50	5.65	
T1.5-1	1.5			1-300	1-300	2-150	5-80	4.45	
T1.5-6	1.5			.02-100	.02-100	.05-50	0.1-25	5.65	
T2.5-6	2.5			.01-100	.01-100	.02-50	0.5-20	4.45	
T4-6	4			.02-200	.02-200	.05-150	1-100	4.45	
T9-1	9			15-200	15-200	3-150	2-40	3.95	
T16-1	16			3-120	3-120	7-80	5-20	4.45	
T36-1	36			0.3-20	0.3-20	0.5-10	1-5	6.95	
TO	TQ-75			1	10-500	—	10-500	40-250	6.95
TH	T1-1H			1	8-300	8-300	10-200	25-100	5.95
T9-1H	9			2-90	2-90	3-75	6-50	6.45	
T16-1H	16			7-85	7-85	10-65	15-40	6.45	
TMO	TMO1-02			1	1-800	1-800	2-500	—	9.45
TMO1-1	1			15-400	15-400	35-200	2-50	6.25	
TMO1.5-1	1.5			1-300	1-300	2-150	5-8	8.45	
†TMO2.5-6	2.5			.01-100	.01-100	.02-50	0.5-20	7.95	
†TMO4-6	4			.02-200	.02-200	.05-150	1-100	7.95	
TMO6-1	6			3-200	3-200	5-150	5-50	7.95	
TMO9-1	9	15-200	15-200	3-150	2-40	7.95			
TMO16-1	16	3-120	3-120	7-80	5-20	7.95			
D 	T	T2-1	2	.050-600	.050-600	1-400	5-200	3.95	
		T3-1	3	5-800	5-800	2-400	—	4.45	
		T4-2	4	2-600	2-600	5-500	2-250	3.95	
		T8-1	8	15-250	15-250	25-200	2-100	3.95	
		T14-1	14	2-150	2-150	5-100	2-50	4.95	
		TMO	TMO2-1	2	.050-600	.050-600	1-400	5-200	7.95
		TMO3-1	3	5-800	5-800	2-400	—	8.45	
		TMO4-2	4	2-600	2-600	5-500	2-250	7.95	
		TMO8-1	8	15-250	15-250	25-200	2-100	7.95	
		TMO14-1	14	2-150	2-150	5-100	2-50	8.45	
FT	FT1.22-1	1.22	.005-100	.005-100	.01-50	.05-25	35.95		
	FT1.5-1	1.5	1-400	1-400	5-200	1-100	35.95		
E 	FTB	FTB-1	1	2-500	2-500	5-300	1-100	36.95	
		FTB1-6	1	0.1-125	0.1-125	0.5-50	1-25	36.95	
		■FTB-1-75	1	5-500	5-500	5-300	10-100	36.95	
F 	T	T-622	1	0.1-200	0.1-200	0.5-100	5-80	3.25	
		T626	1	0.01-10	0.01-10	0.2-5	0.4-2	3.95	
		T2-613.1	1	0.01-10	0.01-10	0.2-5	0.4-2	3.95	

■ Denotes 75 ohm models

* FOR A AND B CONFIGURATIONS
 Typical Amplitude Unbalance
 0.1 dB over 1 dB frequency range
 0.5 dB over entire frequency range
 Typical Phase Unbalance
 1.0° over 1 dB frequency range
 5.0° over entire frequency range

case styles

T, TH, case W 38, X 65 bent lead version, KK81 bent lead version
 TMO, case A 11, + case B 13 FT, FTB, case H 16
 NEW TC SURFACE MOUNT MODELS from 1 MHz to 1500 MHz

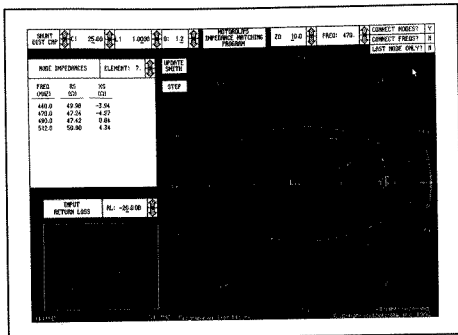


Figure 3. Smith Chart display screen.

the Smith Chart.

f) Real time changes in the impedance transformation are displayed while individual circuit elements are tuned. This utility is provided to perform manual circuit optimization. A scalar display of Input Return Loss is updated simultane-

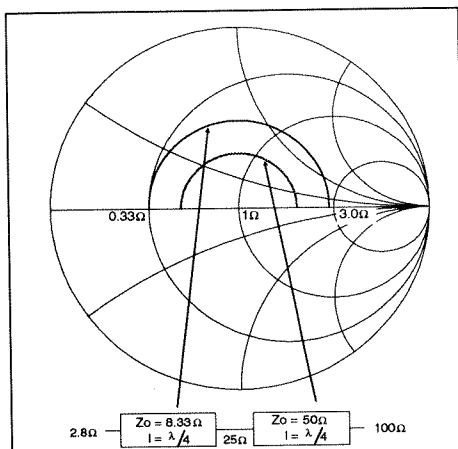


Figure 4. Two different transmission lines normalized and plotted on same Smith Chart.

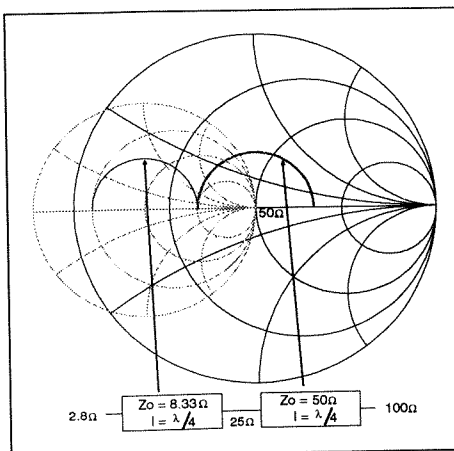


Figure 5. Transmission lines plotted on separately renormalized reflection coefficient planes.

ously as an additional tool for optimization.

RF engineers, who choose to use Motorola's RF Power Transistors in their designs, can access the auxiliary database. Included with MIMP are the input and output impedances for many of the RF power devices contained in Motorola's *RF Data Book*.

Program Description

Motorola's Impedance Matching Program (MIMP) is divided into three screens: the impedance entry screen, the circuit entry screen and the Smith Chart display screen. A mouse is recommended for easy entry and manipulation of data. However, there are keyboard equivalents for most of the mouse functions. Pressing the ESC key or the right mouse button cycles through the impedance entry screen, circuit entry screen and Smith Chart display screen (after minimum data entry has been completed). While in the Smith Chart display screen, pressing both left and right mouse buttons returns the operator immediately to the circuit entry screen.

Hardware requirements are an IBM compatible with 640k, an 80286 or higher and a VGA graphics adapter. A mouse is recommended.

Impedance Entry Screen

To begin the program, change to the directory in which MIMP.EXE resides. This directory must also contain the following three files:

DEVFILE.ASC (This file is a listing of the MRF devices and the location of its associated impedance data in the datafile.) DATAFILE.BIN (This file contains the impedance information for each device included in DEVFILE.ASC.) HELVB.FON (This is a Microsoft C font file.)

The program begins in the impedance entry screen, which is separated into four basic sections: the frequency table, load impedance table, source impedance table and data entry keypad. The first prompt requests the user to specify the number of frequencies at which source and load impedances will be entered. Up to 11 frequencies can be entered. If a standard Motorola device is to be specified, the user is prompted to press ENTER. (MIMP includes a database of input/output impedances for MRF, 2N, JO and TP devices.) Mouse users may enter numeric data by pointing and clicking on the keypad display, or numeric data may be entered from the keyboard.

User Entry

The program first prompts the user for the number of frequencies to be entered. The program will only accept values less than or equal to 11. (If zero is entered, the program advances to a standard device entry sequence; as described later.) After the number of frequencies has been supplied, each frequency should be entered sequentially starting with the lowest value. When the last frequency has been entered, the user is prompted to supply the load impedance data for each frequency. An option to specify 50 ohms is supported by simply pressing ENTER. After all the load impedance data is furnished, the source impedance data is requested. Again, there is an option to specify 50 ohms by pressing ENTER. (Parallel equivalents are calculated and displayed for all impedances.) After the

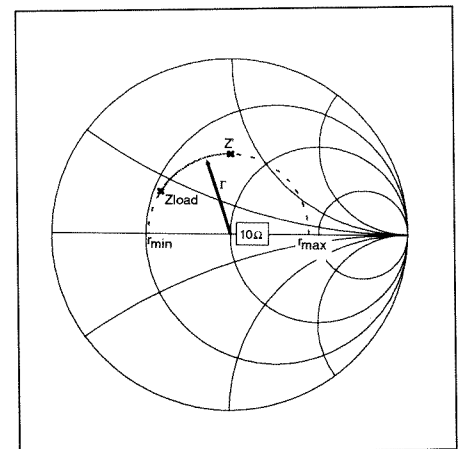


Figure 6. Load and transformed impedances plotted and real axis impedances interpolated.


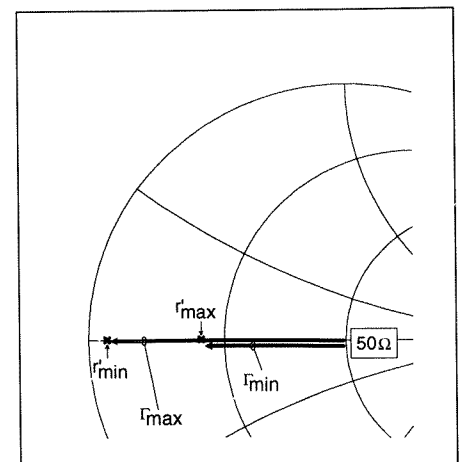


Figure 7. $\Gamma_{\max/\min}$ determined via renormalized $r_{\min/\max}$

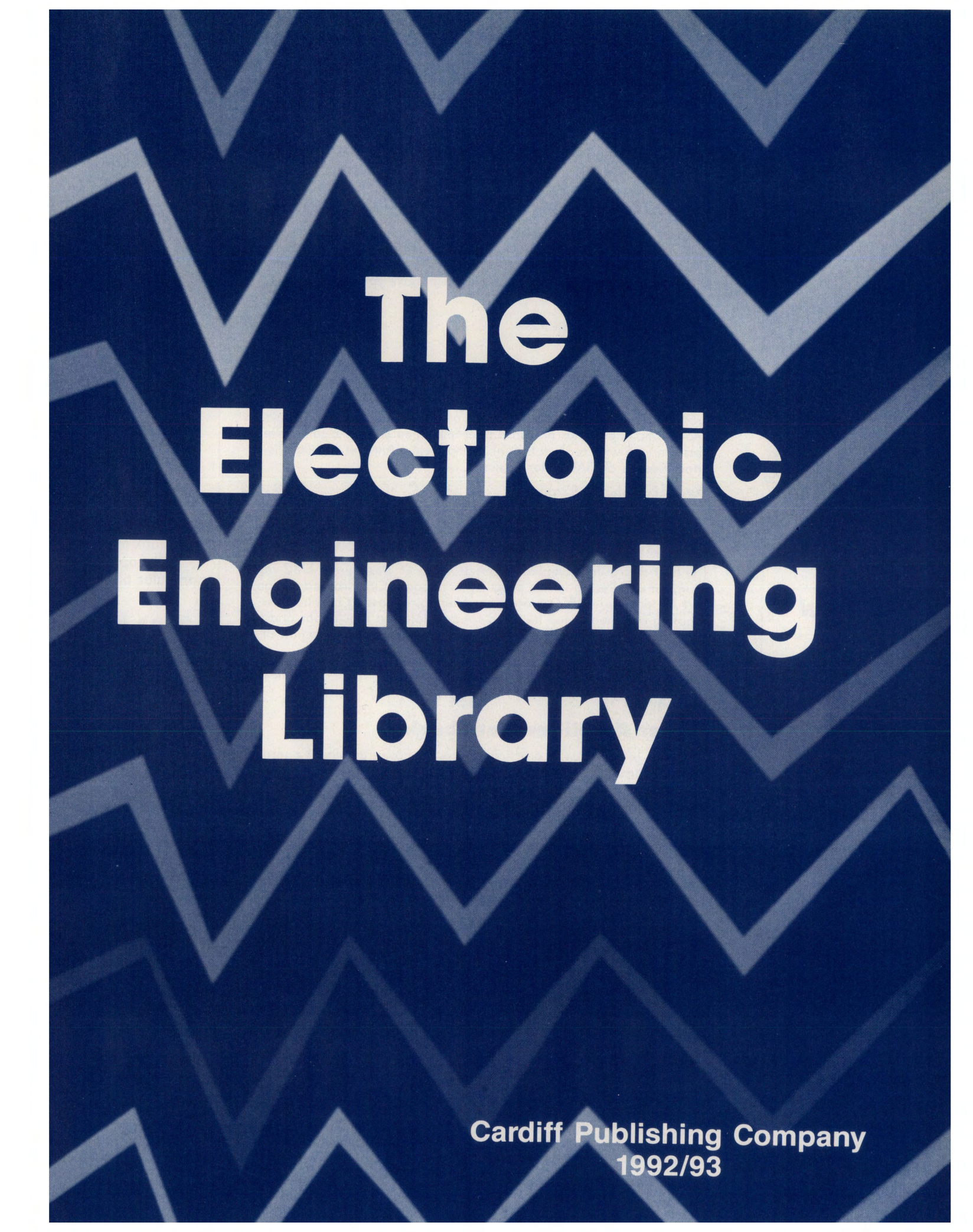

The Electronic Engineering Library

**Cardiff Publishing Company
1992/93**




1. Oscillator Design Handbook

You can benefit from the contributions of more than 20 top RF engineers as they share their expertise on oscillator theory, design and applications. Analytical topics and practical circuits are presented for crystal oscillators, LC circuits and VCOs. Along with traditional designs, this book includes some unique approaches not found anywhere else.

Cardiff Publishing 80 pages

\$25.00

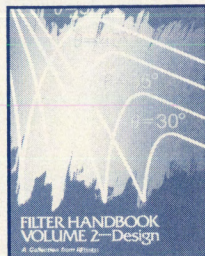


2. Filter Handbook: Volume 1 — Applications

The best practical filter circuits from *RF Design* are collected in this book, allowing you to see how the best engineers solved their design problems. Essential information on active, passive, lumped element, microstrip, helical and SAW filters will help make your filter design tasks easier.

Cardiff Publishing 80 pages

\$25.00

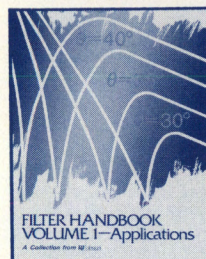

3. Filter Handbook: Volume 2 — Design

Do you need to brush up on filter theory and analysis? This book offers fundamental and advanced material on classic Butterworth, Chebyshev and elliptic filters, plus notes on filter implementation, including filter performance with real, not ideal, components. Another highlight is a tutorial series on SAW filter basics.

Cardiff Publishing 82 pages

\$25.00




4. RFI/EMI/EMC: A Designer's Handbook

The best design-for-compliance articles from *RF Design* and *EMC Test & Design* are collected in this practical handbook. Circuit board design, Part 15 techniques, ESD protection, filtering, bypassing and troubleshooting are among the featured topics. Notes on regulations and test methods are also included, making this a well-rounded collection of EMC and ESD engineering techniques.

Cardiff Publishing 80 pages

\$25.00

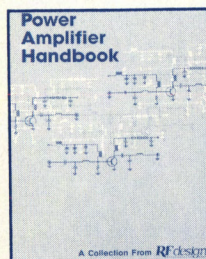


5. Power Amplifier Handbook

This book is loaded with practical circuits for power amplifiers operating from HF through L-band, from a few watts to over a kilowatt, with clear explanations of how these circuits were designed. Articles on high power couplers, combiners, biasing techniques and VSWR protection will help simplify the design of your next power amplifier system.

Cardiff Publishing 80 pages

\$25.00

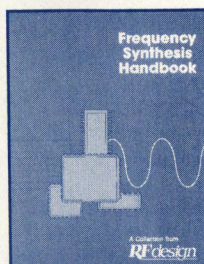


6. Frequency Synthesis Handbook

Phase locked loops and direct digital synthesis are the main focus of this handbook, with articles ranging from Andy Przedpelski's "PLL Primer" series to advanced analytical techniques. Theoretical material is complemented by practical circuits and application notes on some of the latest synthesizer products.

Cardiff Publishing 80 pages

\$25.00

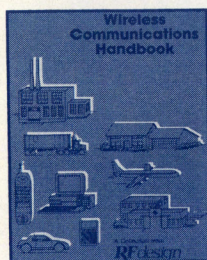

7. Wireless Communications Handbook

Engineering methods for new wireless applications are highlighted in this collection from *RF Design*. Topics include spread spectrum systems, Part 15 devices, digital modulation, demodulation, transmission, reception and signal propagation. A special feature is a repeat of our popular tutorial series on Complex Modulation.

Cardiff Publishing 80 pages

\$25.00

RF HANDBOOK

SPECIAL SET PRICES

TAKE ANY	FOR
4	\$69
5	\$84
6	\$98
7	\$110

Mix and match the RF Handbook titles or order bulk copies of a particular title and . . .


SAVE!!!

8. Transmission Line Transformers, 2nd Edition By Jerry Sevick

This book is becoming widely recognized as the best text on broadband transformers in the HF range. After an introduction that covers the classic Ruthroff and Guanella approaches, the author proceeds to describe and analyze well over a hundred different designs, including detailed construction information and extensive measured frequency response and loss data. It is one of the few technical books that combines rigorous engineering accuracy with down-to-earth practical information.

ISBN 0-87259-296-0 American Radio Relay League

\$20.00

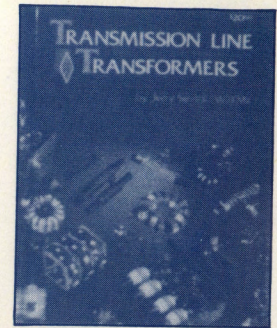


9. RF Circuit Design By Chris Bowick

The author introduces RF circuit design at the most basic level, starting with individual components and proceeding through resonant circuits, transmission lines, filters, the Smith chart, impedance matching, small-signal amplifiers and power amplifiers. It is an excellent teaching text for beginning engineers, and a valuable reference for fundamental RF principles.

ISBN 0-672-21868-2 Sams 176 pages

\$24.00

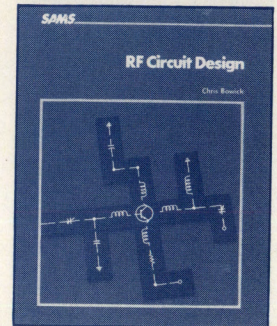


10. Electronic Filter Design Handbook By Arthur B. Williams and Fred J. Taylor

A modern classic for active, passive and digital filter design, this book is an indispensable engineering reference. Basic information is provided on filter types, passband and stopband characteristics, mathematical analysis and various topologies. Extensive tables of filter parameters are included for ease of design, and notes on component selection assist in construction. Completeness is enhanced with chapters on phase shift networks and delay equalizers.

ISBN 0-07-070434-1 McGraw-Hill

\$68.00

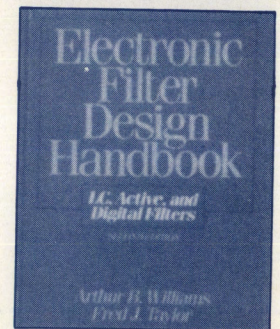


11. Oscillator Design and Computer Simulation By Randall W. Rhea

This unified approach to oscillator design is of particular help to engineers new to these circuits, but serves as an excellent reference for even the most experienced designers. The book covers a wide range of resonator types and active devices, and is applicable to both RF and microwave frequency ranges. Included with the text is a copy of Eagleware's Star 2.0 circuit analysis program, which is intended to reduce the tedium in analyzing oscillator circuits as various parameters are modified.

ISBN 0-13-642513-5 Prentice Hall 260 pages

\$63.00

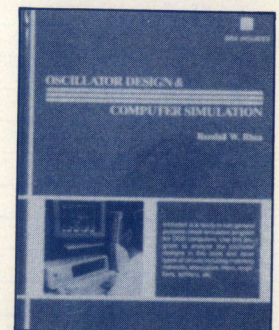


12. MMIC Databook

The 1991 MMIC Databook, written with the help of some of the MMIC Industries' most active players, effectively converts "MMIC know-nothings" into "MMIC gurus," and as rapidly as possible. The Databook contains performance graphs based on manufacturers' typical ratings; charts detailing product availability; key contacts for standard, semi-custom and custom foundry information; and foundry data in both datasheet and summary spreadsheet format.

Berson & Associates

\$295.00



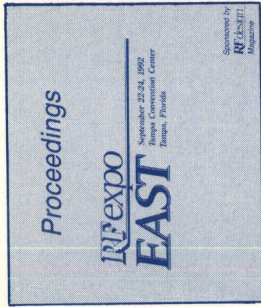

RF Expo Proceedings

Successful engineers like yourself are constantly searching for information to keep them up-to-date on the rapidly changing world of electronic technology. Twice a year, this vital information is presented in the technical sessions and complete tutorial series at the RF Expos. If you were unable to attend the show or particular session — you can now obtain the same information in the RF Expo Proceedings.

- | | |
|---|---|
| 13 <input type="checkbox"/> RF Technology Expo 92 | 19 <input type="checkbox"/> RF Expo East 92 |
| 14 <input type="checkbox"/> RF Technology Expo 91 | 20 <input type="checkbox"/> RF Expo East 91 |
| 15 <input type="checkbox"/> RF Technology Expo 90 | 21 <input type="checkbox"/> RF Expo East 90 |
| 16 <input type="checkbox"/> RF Technology Expo 89 | 22 <input type="checkbox"/> RF Expo East 89 |
| 17 <input type="checkbox"/> RF Technology Expo 88 | 23 <input type="checkbox"/> RF Expo East 88 |
| 18 <input type="checkbox"/> RF Technology Expo 87 | 24 <input type="checkbox"/> RF Expo East 87 |

25. Take all 12 for \$1392 — a savings of \$348

Cardiff Publishing

\$145.00 each

26. EMC/ESD Int'l Conference Proceedings

You'll find papers highlighting extensive coverage of domestic and international EMC and ESD regulatory standards by the industry's leading experts. Additional papers offer excellent practical techniques for dealing with difficult environments, handling surges and transients, analyzing EMC phenomena, controlling ESD, managing EMC through circuit design, and performing EMC and ESD tests and measurements.

Cardiff Publishing 340 pages


\$145.00 each

27. Filters and Matching Networks

A nine-tape video short course with notes for working engineers which covers the topic from baseband to microwaves. The tapes are Fundamentals I & II, CAE Techniques, The Real-World, Matching, Bandpass Filter Symmetry, Group Delay, Direct Coupled Microwave Filters and Field-Coupled Microwave Filters. Important filter concepts are described in easy-to-follow terms. These concepts are then applied to case studies of a variety of filters available for solving practical application problems. Just a few of the hundreds of ideas in these tapes could save you lots of time and effort.

Eagleware

\$895.00 each (NTSC)

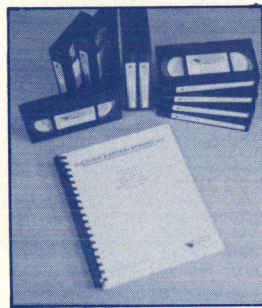

ORDER FORM

No.	Title	Price

Amount Spent	*Shipping Charge
\$0-50.00	\$3.00
\$51.00-100.00	\$5.00
\$101.00-150.00	\$7.00
\$151.00-200.00	\$9.00
\$201.00-250.00	\$11.00
\$251.00++	FREE

Outside US Double Shipping Charges

Subtotal \$	_____
Add Shipping Charges*	_____
Total Payment Enclosed \$	_____

Send Order To:
 Cardiff Publishing Co.
 Attn: Circulation
 6300 S. Syracuse Way, #650
 Englewood, CO 80111

CALL: 1-800-525-9154

FAX: 303-773-9716

Method of Payment:

Payment enclosed \$ _____
 Bill My: MC Visa AE
 Card # _____ Exp _____
 Signature _____

Bill to:

Name _____
 Title _____ Phone _____
 Company _____
 Address _____
 City _____
 State/Zip _____
 Country _____

Ship to: (if different than above)

Name _____
 Title _____ Phone _____
 Company _____
 Address _____
 City _____
 State/Zip _____
 Country _____

data is entered, the user may proceed to the circuit entry screen or edit any of the frequency or impedance data. The ESC key or right mouse button may be pressed at anytime to proceed to the circuit entry screen.

Standard Device Selection

If a standard device is to be selected as the load impedance, the ENTER key is pressed at the prompt for 'Number of frequencies to be entered'. The following selections are provided: 2N, MRF, JO and TP. The user selects the prefix for the device he wishes to use, and the

prefix is immediately displayed in the numeric entry window, allowing the user to complete the device number followed by pressing ENTER. Next the program prompts the user to select either the device's input impedance or output impedance as the load. If the requested device is included in the database, the impedance information is displayed at their corresponding frequencies. The source impedance is entered manually as described above in the user entry section. Editing can be performed on any frequency or impedance before proceeding to the circuit entry screen.

The program will accept only positive numbers for the real portion of the load or source impedances. The ESC key or right mouse button may be pressed at anytime to proceed to the circuit entry screen.


Circuit Entry Screen

The circuit entry screen is separated into three sections: the component library, data entry keypad and circuit display area.

A component is selected by clicking on it with a mouse (using the left mouse button). Keyboard users should press

QUARTZ SCIENTIFIC

K V G - Q U A R T Z A T I T S B E S T

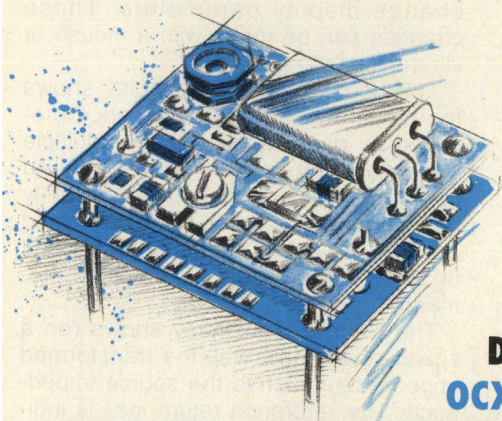

KVG Products. To solve your frequency control problems with crystals!

Quartz crystals. 800 KHz - 300 MHz.

High temperature stability.

Resistance to shock and vibration.

Crystal filters. 400 KHz - 200 MHz.

Discrete and monolithic. Crystal oscillators.

OCXO. $< \pm 5 \times 10^{-8}$; - 25... + 70 °C,


PXO/VCXO. 3 KHz - 300 MHz;

DTCXO. 100 KHz - 17 MHz.

**Low power consumption
in small cases.**

**If crystals are of
interest to you, we will
supply all the informa-
tion you need.**

**KVG - Selected
to be the best.**

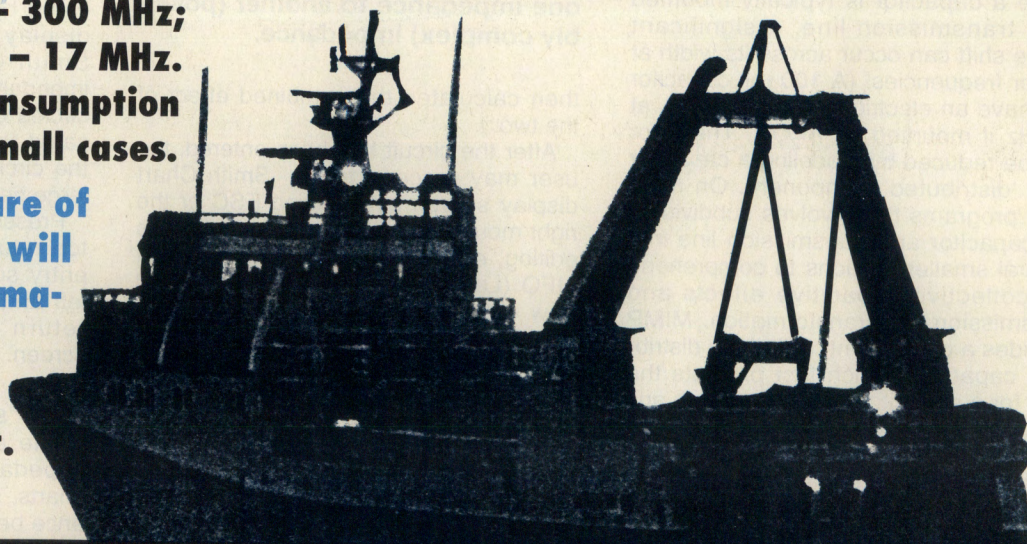

KVG GmbH P.O.-Box 61,
D-6924 Neckarbischofsheim, Federal Republic of Germany
Phone 07263/648-0, Telefax 07263/6196



KVG North America Inc.
2240 Woolbright Rd, Suite 320, Boynton Beach, FL. 33426-6325
Phone (407) 734-9007, Fax (407) 734-9008

the number or letter displayed in the upper left hand corner of the box that outlines the component. Immediately after a component is selected, the numeric keypad is activated and the user is prompted to enter the appropriate component values. Inductors are recognized in nanohenries; capacitors in picofarads. If the user prefers to specify the capacitive/inductive reactance, press ENTER at the prompt. The program then expects a reactance to be provided (in ohms) at a specific frequency.

A transmission line is defined by its characteristic impedance (in ohms) and its electrical length (in fractions of a wavelength). The electrical length needs to be referenced to a specific frequency (in MHz). Transmission lines may also be classified in physical terms. Pressing ENTER at the prompt causes the program to request the conductor's width and length. Whenever the first transmission line is selected (whether it is defined in electrical or physical properties), the following basic microstrip information is also requested: relative dielectric constant, dielectric thickness and conductor thickness (3). This information is assumed to be the same for all subsequent transmission lines and is displayed in the upper right hand corner.

Most CAD programs assume that a capacitor has *no* width; i.e., it contacts the circuit at a single point. As frequencies increase, this assumption introduces a significant error in circuit analysis, particularly at low impedances. Since a capacitor is typically mounted on a transmission line, a significant phase shift can occur across its width at higher frequencies. (A 100 mil capacitor can have an electrical width of 0.02λ at 1 GHz if mounted on Al_2O_3). The error can be reduced by modeling a capacitor as a 'distributed' component. On most CAD programs this involves subdividing the capacitor and transmission line into several smaller sections to comprehend the collective capacitive effects and transmission line transformation. MIMP provides a component, called the distributed capacitor, which first prompts the user for a capacitor value along with any accompanying series lead inductance. Next, it asks for the characteristic impedance of the transmission line, on which the capacitor is mounted. Finally, the transmission line's electrical length (in fractional wavelengths) is entered for that portion of the transmission line on which the capacitor is mounted. MIMP

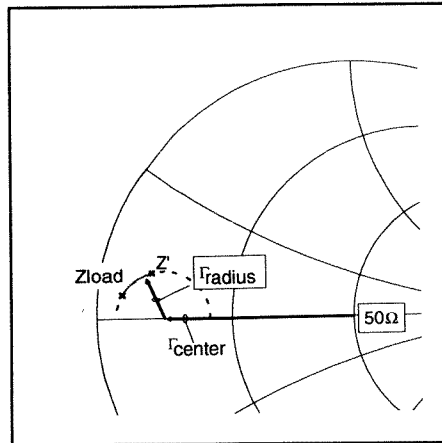


Figure 8. Center and radius of rescaled transmission line impedance.

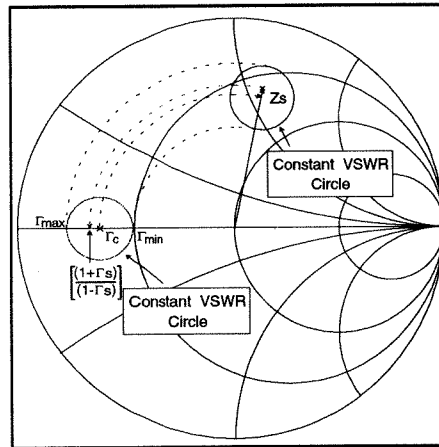


Figure 9. Remapping of constant reflection coefficient circle from one impedance to another (possibly complex) impedance.

then calculates the combined effect of the two.

After the circuit has been entered, the user may proceed to the Smith Chart display screen by pressing ESC or the right mouse button. If the circuit requires editing, elements may be removed in a LIFO (Last In First Out) sequence and new elements may then be entered if desired.

Smith Chart Display Screen

The Smith Chart display screen is separated into four sections: the Smith Chart display, the menu bar, the nodal impedance display and the scalar input return loss graph.

The Smith Chart graphically displays the impedances transformed by each shunt or series element. These impedances

are represented by small X's. Each frequency is depicted by a different color. If there are multiple series or shunt elements, the combined effect of all the elements is lumped together as one element. Upon entry to the Smith Chart display screen, the following default conditions are set:

- The impedances at the lowest frequency are interconnected.
- The conjugate of the source impedance is shown as a yellow X encircled by a -20 dB return loss circle. (The conjugate is the desired transformed impedance.)
- The Smith Chart is initially normalized to 10 ohms.
- The constant Q arcs are set to 0.
- The nodal impedances are listed for the last node.
- The first circuit element is selected for tuning.

The menu bar allows the user to select and fine tune circuit elements and change display parameters. These changes can be made with a mouse or via the keyboard.

The nodal impedance display shows the actual transformed impedance produced by each circuit element. Multiple series or shunt elements are lumped together. (NOTE: These are not really nodal impedances. It is the transformed circuit impedance, starting from the load up to (and including) the selected element.)

The return loss display shows (on a scalar chart) how well the transformed impedance matches the source impedance. The reference return loss is indicated by the yellow line on the scalar display and the yellow circle on the Smith Chart display. If the source impedance is frequency dependent, the circles on the Smith Chart will be relocated for each frequency. To eliminate the circle; change return loss to a very large negative number.

Pressing ESC or the right mouse button returns the user to the impedance entry screen. Mouse users can press left and right buttons simultaneously to return directly to the circuit entry screen.


MIMP's Smith Chart Plotting

The accepted practice, for plotting impedance transformations on Smith charts, requires that each circuit impedance be first normalized to its respective transmission line's characteristic impedance. Once normalized, the impedances can be plotted (and transformed) on a


JFW...The Leader In Programmable Attenuators

50 and 75 Ohms


Model 50P-832
Frequency Range
DC-1000 MHz
Attenuation Range
0-127 dB in 1 dB steps

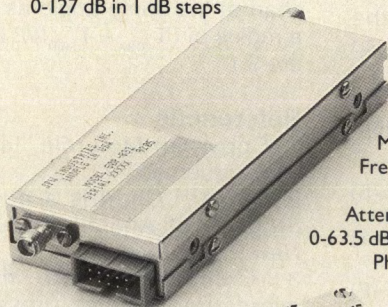



Model 50P-323/D
Frequency Range
20-500 MHz
Attenuation Range
0-63 dB in 1 dB steps
Phase Constant

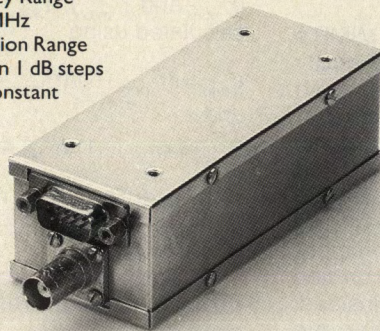


Model 50P-609
Frequency Range
20-1000 MHz
Attenuation Range
0-63.5 dB in .5 dB steps

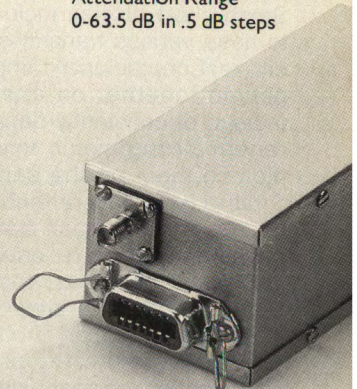


Model 50P-324
Frequency Range
10-300 MHz
Attenuation Range
0-63.5 dB in .5 dB steps
Phase Constant

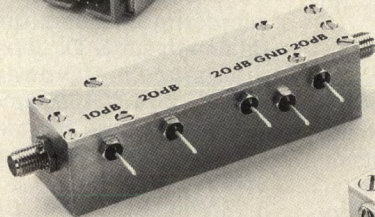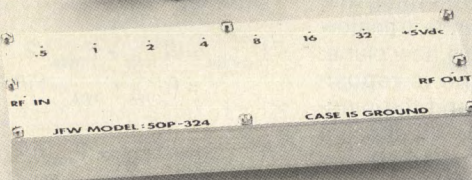

Model 50P-766
Frequency Range
DC-5 GHz
Attenuation Range
0-70 dB in 10 dB steps

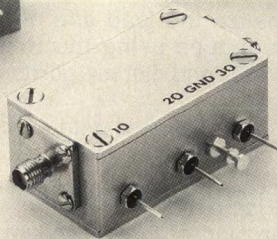

Model 50P-856
Frequency Range
DC-1000 MHz
Attenuation Range
0-60 dB in 10 dB steps

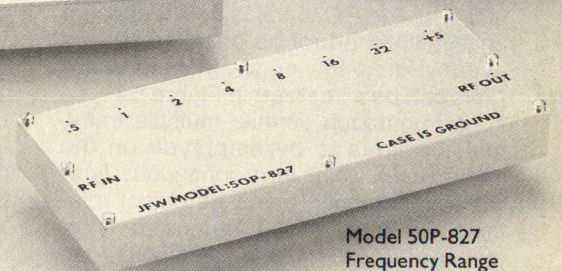

Model 50P-827
Frequency Range
10-600 MHz
Attenuation Range
0-63.5 dB in .5 dB steps
Phase Constant



Model 75AP-012
Frequency Range
20-1000 MHz
Attenuation Range
0 to 25 dB minimum



Model 75AP-008
Frequency Range
20-600 MHz
Attenuation Range
0 to 25 dB minimum



JFW Industries, Inc.

5134 Commerce Square Drive

Indianapolis, Indiana 46237

317-887-1340 Fax: 317-881-6790

INFO/CARD 29

similarly normalized Smith chart. Each time a new transmission line is encountered in the circuit, the impedances must then be denormalized using the old Z_0 and renormalized with the new Z_0 , before additional graphical manipulations can be accomplished. The normalized Smith chart (typically 1 ohm) remains unchanged with each new transmission line transformation. This results in a series of non-contiguous impedance transforms whose visual relationships have little or no value. See Figure 4.

One of the unique features of MIMP's Smith chart display includes the ability to have various transmission lines (with different characteristic impedances) displayed together on one Smith chart. Instead of constantly denormalizing and renormalizing circuit impedances and plotting them on the same normalized Smith chart, the reflection coefficient (RC) plane (for each transmission line transformation) is renormalized instead. The locus of points, representing the transmission line's impedance transformation, is remapped into this new plane. The origin of the RC plane is repositioned along the real axis and the magnitude of the RC is rescaled. In effect, a 2nd Smith chart (of an adjusted size) is overlaid on the original Smith chart. (This can be visualized in Figure 5.)

This approach permits multiple transmission lines to be displayed on the same Smith chart in a contiguous flow, while maintaining exact graphical relationships between the various transformations. Because of the additional calculations, it is obviously more applicable for manipulation on CAD programs than by hand. Once the program is set up to handle these calculations, all impedance transformations maintain their relative positions as the relative characteristic impedance of the Smith chart is changed. (MIMP also allows the user to specify any relative Z_0 for the Smith chart.)

Here is the basic procedure (4,5) used to remap a transmission line transformation (whose Z_0 differs from the Smith chart's relative Z_0):

1) The load and transformed impedances are determined for a particular transmission line. (The load impedance should already be known. The transformed impedance (Z') is calculated based on the transmission line's Z_0 and electrical length.)

2) Next, two hypothetical impedances are calculated (Figure 6). These are the real axis impedances; assuming the

reflection coefficient is extended to 0 degrees and 180 degrees. r_{min} and r_{max} are calculated using:

$$r_{min} = (1 - \Gamma)/(1 + \Gamma) \quad (1)$$

and

$$r_{max} = (1 + \Gamma)/(1 - \Gamma) \quad (2)$$

3) r_{min} and r_{max} are denormalized using the respective transmission line's Z_0 (ZTx) and then renormalized to the relative Z_0 of the Smith chart (Figure 7). Using the new values of r_{min} and r_{max} (r'_{min} and r'_{max}); Γ_{min} and Γ_{max} may be calculated using:

$$\Gamma_{min} = (r'_{max} - 1)/(r'_{max} + 1) \quad (3)$$

and

$$\Gamma_{max} = (r'_{min} - 1)/(r'_{min} + 1) \quad (4)$$

(In Figure 7, the relative Z_0 of the Smith chart changes from 10 ohms to 50 ohms.)

4) The center and radius of the rescaled constant reflection coefficient circle is:

$$\Gamma_{center} = (\Gamma_{min} + \Gamma_{max})/2 \\ = (r'_{min} r'_{max} - 1)/(r'_{min} + 1)(r'_{max} + 1) \quad (5)$$

$$\Gamma_{radius} = (|\Gamma_{max} - \Gamma_{min}|)/2 \\ = (r'_{max} - r'_{min})/(r'_{min} + 1)(r'_{max} + 1) \quad (6)$$

5) Renormalize the load and transformed impedances using the Smith chart's relative Z_0 and plot the points on the Smith chart.

6) Connect the 2 points with a constant reflection coefficient circle whose origin is at Γ_{center} and whose radius is Γ_{radius} . (See Figure 8).

A slight variation of this procedure is also used for plotting a constant reflection coefficient circle for any impedance on the Smith chart. Many programs plot constant RC circles about the center of the Smith chart (when the network's source impedance is also assumed to be in the center of the Smith chart). However, if the source impedance is different from the Smith chart's Z_0 (it can even be complex); its constant reflection coefficient circle can also be remapped to a different location on the Smith chart. When remapping to a new real value source impedance, the procedure is the same as described above. Plotting the constant reflection coefficient circle, for a complex source impedance, requires some additional steps. The center and radius for the newly mapped constant reflection coefficient circle are determined by first translating Γ_{Zs} to either 0

degrees or 180 degrees. From this, R is calculated using:

$$R + (1 + \Gamma_{Zs})/(1 - \Gamma_{Zs}) \quad (7)$$

Followed by calculating r_{min} , r_{max} , Γ_{min} and Γ_{max} .

$$r_{min} = (1 - \Gamma_{VSWR})/(1 + \Gamma_{VSWR}) \cdot R \quad (8)$$

$$r_{max} = (1 + \Gamma_{VSWR})/(1 - \Gamma_{VSWR}) \cdot R \quad (9)$$

$$\Gamma_{min} = (r_{min} - 1)/(r_{min} + 1) \quad (10)$$

and

$$\Gamma_{max} = (r_{max} - 1)/(r_{max} + 1). \quad (11)$$

The constant reflection coefficient circle is then redrawn with its center at $(\Gamma_{max} + \Gamma_{min})/2$ from the origin of Smith chart at the same angle as Γ_{Zs} and with a radius of $(|\Gamma_{max} - \Gamma_{min}|)/2$ (Refer to Figure 9.) **RF**

References

1. Copyright Motorola, Inc. 1992, All rights reserved.
2. Smith™ Chart is a trademark and property of Analog Instruments Co., New Providence, NJ.
3. Calculations are made using microstrip formulas presented by: E. Hammerstadt & O. Jensen, 1980 *IEEE International Microwave Symposium Digest*, pp. 407-409, June 1980.
4. Javid, M. and Brenner, E., *Analysis, Transmission & Filtering of Signals*, pp. 366-370, McGraw Hill Book Co., 1963.
5. Smith, Phillip H., *Electronic Applications of the Smith Chart*, pp. 197-200, Robert E. Kreiger Publishing Co., 1983.

About the Author

Dan Moline is currently the manager of Advanced Packaging in Motorola's RF Integrated Circuit group. He has a BSEE degree from the University of Missouri at Rolla. During his 20 years with Motorola, he has had design responsibilities for both RF power amplifiers and components ranging in frequency from 100 to 1000 MHz. He developed Motorola's Impedance Matching Program during a three year assignment with Motorola's semiconductor facility in Seremban, Malaysia. He can be reached at Maildrop EL610, 2100 E. Elliot Rd., Tempe, AZ 85284, or by phone at (602) 897-4319.

THE Defense LIBRARY

ITEM NUMBER	EDITION	DOMESTIC PRICE	OUTSIDE USA AIRMAIL
-------------	---------	----------------	---------------------

INTERNATIONAL COUNTERMEASURES HANDBOOK

3802	... ICH - 2ND EDITION	\$ 18.50	\$ 33.00
3803	... ICH - 3RD EDITION	18.50	33.00
3804	... ICH - 4TH EDITION	18.50	33.00
3805	... ICH - 5TH EDITION	23.50	38.00
3806	... ICH - 6TH EDITION	28.50	43.00
3807	... ICH - 7TH EDITION	28.50	43.00
3808	... ICH - 8TH EDITION	33.50	48.00
3909	... ICH - 9TH EDITION	33.50	48.00
3810	... ICH - 10TH EDITION	33.50	48.00
3811	... ICH - 11TH EDITION	33.50	48.00
3812	... ICH - 12TH EDITION	33.50	48.00
3813	... ICH - 13TH EDITION	53.50	68.00
3814	... ICH - 14TH EDITION	63.60	78.00
3815	... ICH - 15TH EDITION	78.50	93.00
3816	... ICH - 16TH EDITION	78.50	93.00
3800	... ICH - SET (2ND-16TH)	\$ 390.00	\$ 580.00

COMMAND, CONTROL, COMMUNICATIONS AND INTELLIGENCE HANDBOOK

3901	... C3I - 1ST EDITION 1986	\$ 18.50	\$ 33.00
3902	... C3I - 2ND EDITION 1987	22.50	37.00
3903	... C3I - 3RD EDITION 1988	28.50	43.00
3900	... C3I - SET *SPECIAL PRICE	\$ 50.00	\$ 65.00

MICROWAVE SYSTEM DESIGNERS HANDBOOK

4001	... MSDH - 1ST EDITION 1983	\$ 13.50	\$ 28.00
4004	... MSDH - 4TH EDITION 1986	18.50	33.00
4005	... MSDH - 5TH EDITION 1987	28.50	43.00
4000	... MSDH - SET *SPECIAL PRICE	\$ 45.50	\$ 54.00

TO ORDER: Fill out order form; indicating item number, quantity desired and price. Shipping charges are included.
PAYMENT MUST ACCOMPANY ORDER.

ITEM	QUANTITY	PRICE
_____	_____	\$ _____
_____	_____	_____
_____	_____	_____

TOTAL ENCLOSED \$ _____

- Payment enclosed (check or money order)
 Charge my order to: Visa MasterCard American Exp.

Account Number _____

Signature _____
(as it appears on card)

Expiration date _____ / _____
Mo. yr.

Name _____

Title _____

Company _____

Address _____ Mail Stop _____

City/State _____

County _____ Zip/Mail Code _____

My check or money order is made payable in U.S. dollars to:
 Cardiff Publishing
 6300 S. Syracuse Way, #650
 Englewood, CO 80111
 U.S.A.

Microstrip Antenna Modeling

By Andre Boulouard, Michel Le Rouzic and Jean Paul Castelletto
Centre National d'Etudes Des Télécommunications

Microstrip antennas play an important role in the design of radio communication systems as both feed and array elements. They have found increasing use because they can be fabricated at low cost by lithographic techniques. As the demand for commercial products containing RF antennas continues to grow, the availability of good microstrip antenna models is required. This article describes accurate transmission-line antenna models suited for commercially available CAD packages.

Microstrip antenna design requires good quality models for low and high permittivity substrates. As the need for increased bandwidth leads to thicker substrates, the models used for thin, low dielectric constant substrates must be improved (1). Although analytical models such as the loaded transmission-line resonator (2) and the cavity models (3) involve rather simplified approximations, they provide sufficient information for a first pass design. More rigorous solutions may be obtained by finite difference techniques or moment solutions, although the computational cost is high (4).

The transmission-line model is both accurate and numerically efficient. It can be represented by a transmission line section terminated at both ends by radiation admittances, surface wave loss conductances and coupled current

sources as shown in Figure 1. The radiation conductance is expressed as:

$$G_r = \left[(\omega \int_0^{\omega} \frac{\sin(x)}{x} dx + \sin(\omega) / \omega + \cos(\omega) - 2)(1 - s^2 / 24) + (1 / 3 + \cos(\omega) / \omega^2 - \sin(\omega) / \omega^3) s^2 / 12 \right] / (\eta_0 \pi)$$

where:

$$c_0 = 299,792,500 \text{ m/s}$$

$$\eta_0 = 376.467 \text{ ohms}$$

$$k_0 = 2\pi \text{ frequency}/c_0$$

$$\omega = k_0 W_e$$

$$s = k_0 D_l$$

$$W_e = \text{antenna effective width}$$

$$D_l = \text{open end equivalent line length}$$

The surface wave loss equivalent conductance is obtained from Reference 5 as:

$$L_0 = c_0 / \text{frequency}$$

$$H_s \omega = (H/L_0) \sqrt{(\epsilon_r - 1)}$$

$$E_s \omega = 1 - 3.4 H_s \omega + 1600 (H_s \omega^3 - 100 H_s \omega^5) \epsilon_r^3$$

where:

$$H = \text{substrate height}$$

$$\epsilon_r = \text{substrate dielectric constant}$$

The self susceptance, B_r , is obtained from the open end equivalent transmission line length as:

$$B_r = \tan(k_0 D_l) \sqrt{(\epsilon_r)} / Z_c$$

where:

ϵ_r = transmission line effective dielectric constant

Z_c = transmission line characteristic impedance

The real and imaginary parts of the mutual admittance, Y_m , are expressed as:

$$x = k_0(L + D_l)$$

$$F_g = J_0(x) + s^2 J_2(x) / (24 - s^2)$$

$$N_b = (\pi/2)(Y_0(x) + s^2 Y_2(x) / (24 - s^2))$$

$$F_b = N_b / (\ln(s/2) - 0.9228 + (s^2/12) / (24 - s^2))$$

$$G_m = G_r F_g$$

$$B_m = B_r F_b (1 - \exp(-0.21\omega))$$

$$Y_m = G_m + jB_m$$

where J_0 , J_2 and Y_0 , Y_2 are Bessel functions of the first and second kind respectively.

In order to improve the accuracy of the resonant frequency compared to the results published in Reference 1, the physical antenna length should be corrected as follows:

$$L_c = L + (-0.12 + 0.043\epsilon_r)H$$

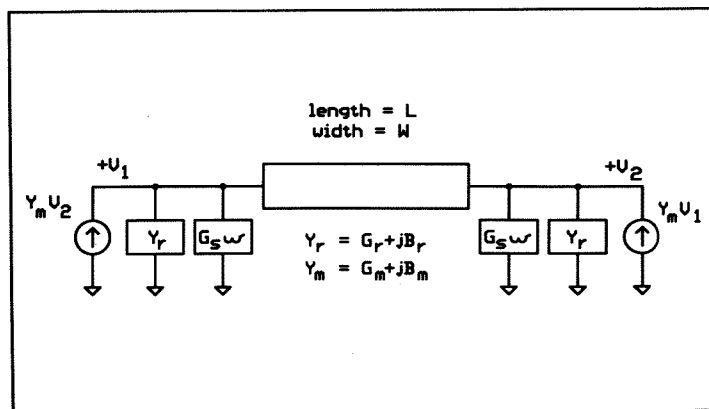


Figure 1. Antenna transmission line model.

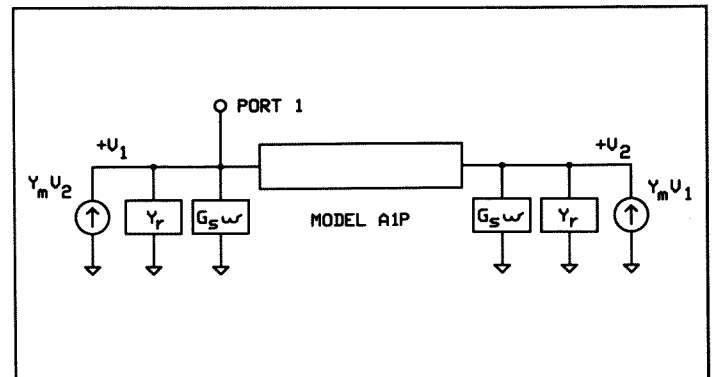


Figure 2. One port antenna fed along a radiating edge.

The 48 cent solution.

Wideband Amplifiers – From \$.48 each

UPC1653 To 1300MHz 18dB G _p	UPC1654 To 1100MHz 19dB G _p	UPC1655 To 900MHz 18dB G _p	UPC1656 To 850MHz 19dB G _p	UPC1658 To 1100MHz 17dB G _p 2.0dB NF	
UPC1659 600MHz to 2300MHz 23dB G _p	UPC1675 To 2100MHz 12dB G _p	UPC1676 To 1300MHz 20dB G _p 4.0dB NF	UPC1677 To 1700MHz 24dB G _p P _{out} = 19.5dBm	UPC1678 Up to 1900MHz 23dB G _p P _{out} = 18dBm	UPC1688 Up to 1000MHz 21dB G _p 4.0dB NF

Prescalers – From \$2.20 each

UPB581 + 2 500MHz to 2.8GHz	UPB582 + 4 500MHz to 2.8GHz	UPB584 + 2 500MHz to 2.5GHz	UPB585 + 4 500MHz to 2.5GHz	UPB586 + 512/256 500MHz to 2.5GHz	UPB587 + 2/4/8 50MHz to 1.0GHz V _{cc} = 2.2 to 3.5V	UPB588 + 64/128 500MHz to 2.5GHz
--	--	--	--	--	--	---

Freq. Convertors – From \$1.58 each

UPC1685 DC to 890MHz 14dB GAIN Double Balanced Mixer Applications	UPC1686 DC to 890MHz 22dB GAIN	UPC1687 DC to 890MHz 28dB GAIN I _{cc} of 38mA
--	---	--

IF Amplifiers – From \$3.50 each

UPC1668 10 to 170MHz G _i = 14.5dB 60dB Isolation	UPC1669 10 to 180MHz G _i = 10.5dB 55dB Isolation	UPC1670 10 to 150MHz IM ₃ of 56dBc 60dB Isolation
---	---	--

Transistor Arrays From \$2.40 each

UPA101 F _T = 9GHz Double Balanced Mixer Applications	UPA102 F _T = 9GHz Differential Amplifier
UPA103 F _T = 9GHz Differential Amplifier	UPA104 F _T = 9GHz OR/NOR Functions

Special Function MMICs From \$1.08 each

UPC1684 LED DRIVER 150mA Drive Current 300 Mbits NRZ	UPC1663 VIDEO AMPLIFIER 170MHz @ A _{volt} = 100 1.6ns Propagation Delay
---	---

Note: MMIC prices based on 25K quantities

NEC[®]

Want to make life simpler? Reduce the parts count in your design with silicon MMICs from NEC. They're the low cost, no-hassle way to achieve your design goals.

But be aware of the side effects!


Reducing your parts count can also make your QC easier. Your overall circuit more reliable. And your assembly, whether manual or automated, faster and more efficient.

NEC MMICs come in chips and a variety of packages, including hermetic, low cost plastic, surface mount and tape and reel. So they're ideal for high volume automated assembly.

And their quality and reliability is proven: With a production rate of *7 million a month*, no one knows MMICs like NEC.

Our Silicon MMIC Product Selection Guide

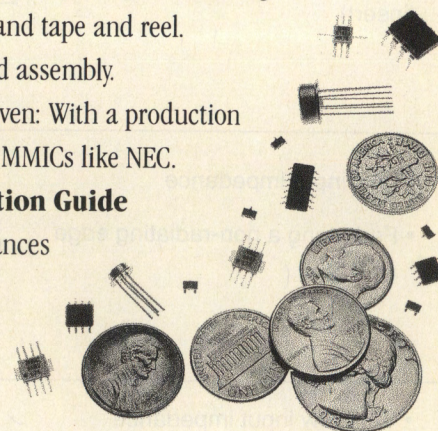lists specifications for dozens of parts. Chances are good it has just what you need. To get a copy, call your nearest CEL Sales Office or circle the number below.



California Eastern Laboratories

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 □ Santa Clara, CA (408) 988-7846 □ Los Angeles, CA (310) 645-0985
San Diego, CA (619) 467-6727 □ Bellevue, WA (206) 455-1101 □ Richardson, TX (214) 437-5487 □ Shawnee, KS (913) 962-2161 □ Woodridge, IL (708) 241-3040 □ Cockeysville, MD (410) 667-1310
Peabody, MA (508) 535-2885 □ Hackensack, NJ (201) 487-1155 or 487-1160 □ Palm Bay, FL (407) 727-8045 □ Snellville, GA (404) 978-4443 □ Nepean, Ontario, Canada (613) 726-0626

© 1992 California Eastern Laboratories

INFO/CARD 31

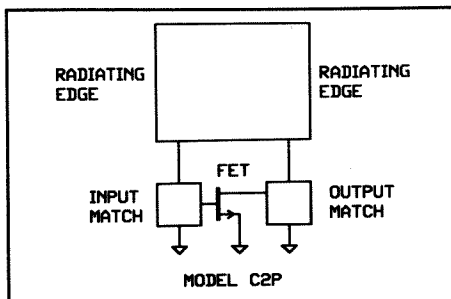


Figure 3. Non-radiating edge fed oscillator-antenna.

Different antenna types have been modeled after this basic theory. They differ by the position(s) of the feeding line(s), relative to the antenna as seen in Table 1. The simplest one port model shown in Figure 2 is obtained when the antenna is fed by a high impedance microstrip transmission line along a radiating edge (model AIP).

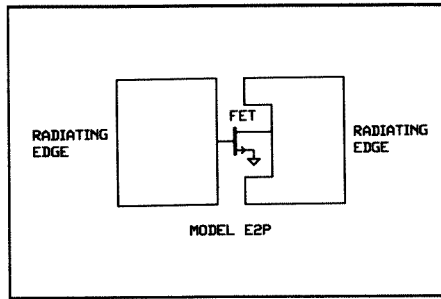


Figure 4. Center fed oscillator-antenna.

As the antenna input impedance is the highest when fed along a radiating edge, a lower impedance is obtained by etching an insert at the center of a radiating edge (model BIP) or by feeding the antenna on a non-radiating edge (model CIP), thus facilitating the matching procedure. Two-port antennas are used to build linear arrays (model A2P) (6) or

active radiating antennas using FETs (models A2P, C2P and E2P) as shown in Figures 3 and 4 (7,8).

Using a commercial CAD software (9), fewer than 100 equations were necessary to define each of these models inside a circuit page. A special Microstrip Antenna Components Library file has been built upon these models and can be made available to interested readers for comparison purposes. Contact the authors at the address given below. **RF**

References

1. D.H. Schaubert, D.M. Pozar and A. Adrian, "Effect of Microstrip Antenna Substrate Thickness and Permittivity: Comparison of Theories with Experiment," *IEEE Trans. Antennas and Propagation*, vol. AP-37, pp. 677-682, June 1989.
2. H. Poes, A. Van de Capelle, "Accurate Transmission-Line Model for the Rectangular Microstrip Antenna," *IEE Proc.*, vol. 131, Pt. H, 1984, pp. 334-340.
3. W.F. Richards, Y.T. Lo and D.D. Harrison, "An Improved Theory for Microstrip Antennas and Applications," *IEEE Trans. Antennas and Propagation*, vol. AP-29, 1981, pp. 38-46.
4. D.M. Pozar, "Microstrip Antennas," *Proceedings of the IEEE*, vol. 80, no. 1, January 1992, pp. 79-91.
5. B. Nauwelaers, A. Van de Capelle, "Surface Wave Losses of Rectangular Microstrip Antennas," *Electron. Lett.*, 1989, vol. 25, pp. 696-697.
6. A.G. Derneryd, "Linearly Polarized Microstrip Antennas," *IEEE Trans. Antennas and Propagation*, vol. AP-22, 1974, pp. 74-78.
7. K. Chang, K.A. Hummer and G.K. Gopalakrishnan, "Active Radiating Element Using FET Source Integrated with Microstrip Patch Antenna," *Electron. Lett.*, 1988, vol. 24, pp. 1347-1348.
8. R.A. York and R.C. Compton, "Quasi-Optical Power Combining Using Mutually Synchronized Oscillator Arrays," *IEEE Trans. Microwave Theory Tech.*, vol. 39, no. 6, June 1991, pp. 1000-1009.
9. Hewlett-Packard Microwave Design System Software, Revision MDS B.03.00, 1991.

Antenna features	One-port	Two-port
<ul style="list-style-type: none"> • High input impedance • Fed along a radiating edge 	<p>Model AIP</p>	<p>Model A2P</p>
<ul style="list-style-type: none"> • Low input impedance • Fed along a radiating edge (insert) 	<p>Model BIP</p>	<p>Model B2P</p>
<ul style="list-style-type: none"> • Low input impedance • Fed along a non-radiating edge 	<p>Model CIP</p>	<p>Model C2P</p>
<ul style="list-style-type: none"> • Very low input impedance • Center fed • Active antenna (oscillator) 	<p>Model E2P</p>	<p>Model E2P</p>

Table 1. Different types of microstrip antennas.

About the Authors

Andre Boulouard is a senior engineer; and Michel Le Rouzic and Jean Paul Castelletto are chief technicians at Centre National d'Etudes des Télécommunications. They are currently involved in MMIC, MIMIC, MIC and subsystem designs for high-speed optical and millimeter-wave communications systems. They can be reached at: CNET/LAB/OCM/MLS, CNET - Route de Tregastel, Lannion, 22301, France. Fax: (33) 96 05 10 08.

For ten years we've been supplying our NE710 customers with the industry's leading FET.

What more could they ask for?

"My needs are simple: A FET that delivers absolutely the best noise performance available. Period."

Introducing the new extra-low noise Pseudomorphic Heterojunction

NEW

NE326	NF	Ga	P1dB	Freq
	0.5	11.5	10.75	12

In chip and low cost ceramic and hermetic packages

"How about a chip that does it all? Good noise figures, good gain, moderate output power, and bandwidth enough for my 6 - 18 GHz amplifiers."

You've got it. Introducing the new Heterojunction version:

NEW

NE332	NF	Ga	P1dB	Freq
	0.8	10.5	12.5	12

In chip and low cost ceramic or hermetic packages

"How about a low cost plastic version? One I can order in volume for applications to 14 GHz."

Our high-yield Ion Implant process produces a consistent, uniform MESFET at a new low cost.

NE760	NF	Ga	P1dB	Freq
	0.8	15.5	14.5	4

In plastic, low cost ceramic and hermetic packages and chips

NOTE:
Noise Figures (NF) in dB
Gain (Ga) in dB
Power Out (P1dB) in dBm
Frequency in GHz

"How about a part with Heterojunction-style performance for my DBS, MMDS and commercial communications applications—at a MESFET price."

Meet the ideal second stage device:

NEW

NE424	NF	Ga	P1dB	Freq
	0.8	11.5	11.0	12

In low cost ceramic packages

"I'm building mixers at 900 MHz and need dual gate MESFETs by the thousands. Can you fix me up—at under 50¢ per part?"

We can—two different ways:

NE251	NF	Ga	P1dB	Freq
	0.8	12.0	12.0	0.9
NE253	NF	Ga	P1dB	Freq
	0.8	12.0	15.0	0.9

In low cost plastic packages


"I need a low noise FET for the LNA in my TVRO system. And, of course, I need it in a high volume, tape and reel package."

How about a 0.6 dB noise figure at 12 GHz?

Introducing the new:

NE324	NF	Ga	P1dB	Freq
	0.6	11.5	11.0	12

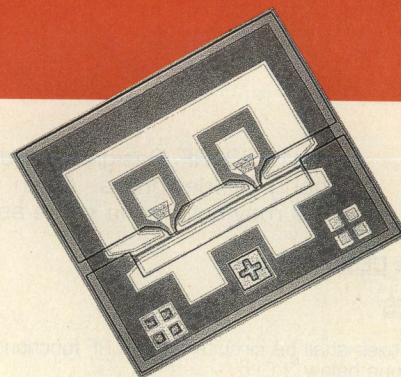In chip and low cost ceramic and hermetic packages



"Don't mess with the original! It's designed into more of my circuits than any other FET. The 710 is a workhorse; solid, consistent—and I still use 'em by the truckload. Don't change!"

Here you go:

NE710	NF	Ga	P1dB	Freq
	0.6	13.0	14.5	4

In chip form



They're here.

They're fully characterized.

And they're ready to ship!

For Data Sheets and a Small Signal FET Product Selection Guide, call your nearest CEL Sales Office, or circle the number below.

NEC[®]

California Eastern Laboratories

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 □ Santa Clara, CA (408) 988-7846 □ Los Angeles, CA (310) 645-0985
San Diego, CA (619) 467-6727 □ Bellevue, WA (206) 455-1101 □ Richardson, TX (214) 437-5487 □ Shawnee, KS (913) 962-2161 □ Woodridge, IL (708) 241-3040 □ Cockeysville, MD (410) 667-1310
Peabody, MA (508) 535-2885 □ Hackensack, NJ (201) 487-1155 or 487-1160 □ Palm Bay, FL (407) 727-8045 □ Snellville, GA (404) 978-4443 □ Nepean, Ontario, Canada (613) 726-0626

CALL FOR ENTRIES

1993 RF Design Awards Contest Official Rules

The 1993 RF Design Awards Contest provides recognition for innovation and engineering excellence among RF designers. Again this year, there are two separate entry categories. Please note that the rules may not be the same as previous years' contests.

I. The DESIGN Contest

RULES

- 1) Entries shall be circuits with an RF function, operating in the frequency range below 3 GHz.
- 2) Circuits entered shall have a complexity equivalent to that of a circuit using 8-10 discrete active devices, or 6-8 integrated circuits. This rule is for ease of judging, to have all entries be of a similar scope. The entry can be a portion of a larger system.
- 3) Entries may represent design or test methods. Design method entries should include an example circuit. Test method entries should include a description of the device or system under test.
- 4) The entries shall be the original work of the entrant, not previously published. If developed as part of the entrant's employment, entries must have the employer's approval for submission.
- 5) Only one entry per person is permitted. An entry may have two or more co-authors.
- 6) Submission of an entry implies permission for publication by *RF Design*. All prize-winning entries will be published, plus additional entries of merit.
- 7) Winners are responsible for any taxes, duties, or other assessments which result from the receipt of their prizes.
- 8) Entries must be postmarked by March 19, 1993 and received no later than March 26, 1993.
- 9) All entries will remain confidential until the publication of the July 1993 issue of *RF Design*.

JUDGING CRITERIA

Originality — Each design will be evaluated for similarity to work by others, and other judgements of its unique contributions.

Engineering — Entries should clearly identify how the entry was created in response to a need.

Documentation — A complete description of the circuit or technique is required, including sufficient theoretical background, description of circuit operation, and performance data.

II. The PC SOFTWARE Contest

RULES

- 1) Each entry shall be a computer program which assists in the design, test, or control of RF circuits or systems.
- 2) Programs must operate on computers compatible with MS-DOS/PC-DOS or Apple Macintosh operating systems. Any special hardware requirements should be noted (memory, graphics, etc.).
- 3) Programs should be provided in a form that can be run without special support software; programs should be provided in compiled, directly executable form. Programs using the BASICA or GWBASIC interpreters are acceptable. Programs that require spreadsheet or mathematics software packages cannot be accepted.
- 4) Programs entered must be submitted on disk. Supporting documentation on theory of operation, references, and operating instructions must be supplied in printed form. Source code must be supplied, either on disk or in printed form.
- 5) The entries shall be the original work of the entrant, not previously published or distributed (including public BBS or shareware). If developed as part of the entrant's employment, entries must have the employer's approval for submission.
- 6) Only one entry per person is permitted. An entry may have two or more co-authors.
- 7) Submission of an entry implies permission for publication by *RF Design* and distribution by the RF Design Software Service. All prize-winning entries will be published, plus additional entries of merit. Some restrictions on publication and distribution of source code may be acceptable.
- 8) Winners are responsible for any taxes, duties, or other assessments which result from the receipt of their prizes.
- 9) Entries must be postmarked by March 19, 1993 and received no later than March 26, 1993.
- 10) All entries will remain confidential until the publication of the July 1993 issue of *RF Design*.

JUDGING CRITERIA

Technical Merit — Computer programs will be compared to accepted standards for accuracy, and will be judged for their achievement in translating RF theory into software tools.

Usefulness — The value of the software to the RF engineering community will be evaluated. Both the nature of the computations performed and ease of operation of the program will be considered.

**DEADLINE FOR ENTRIES:
POSTMARKED BY MARCH 19, 1993 — RECEIVED BY MARCH 26, 1993**

Send entries to:

**RF Design Awards Contest
RF Design magazine
6300 S. Syracuse Way, Suite 650
Englewood, CO 80111**

GRAND PRIZE ANNOUNCEMENT

Continuing our tradition of offering prizes valued in the tens of thousands of dollars, here are the Grand Prizes to be awarded to the winners of the Circuit Design and PC Software categories of the 1993 RF Design Awards Contest —

THE DESIGN GRAND PRIZE



The NOISE COM model UFX-BER Noise Generator for Bit Error Rate Testing

This instrument offers advanced testing using calibrated injection of White Gaussian noise into the IF or RF of a transmission system. It displays the actual E_b/N_0 or $(C+N)/N$ for testing of satellite communications or digital radio systems. Center frequencies are available for all common IFs, to be selected by the winner. A powerful test solution for today's communications!

provided by

NOISE/COM


EEsof's new Windows-based software — Libra®, Touchstone® and LineCalc®

Version 3.5 software offers advanced circuit simulation in the PC environment under the Microsoft Windows operating system. Linear analysis is provided by Touchstone for classic amplifier, filter and other linear circuits. Libra offers nonlinear analysis for such circuits as power amplifiers, oscillators and mixers. LineCalc adds the capability for physical design of transmission line circuits to the package. The highly visual Windows operating system allows flexibility in graphical and physical representations.

provided by

EEsof

THE PC SOFTWARE GRAND PRIZE

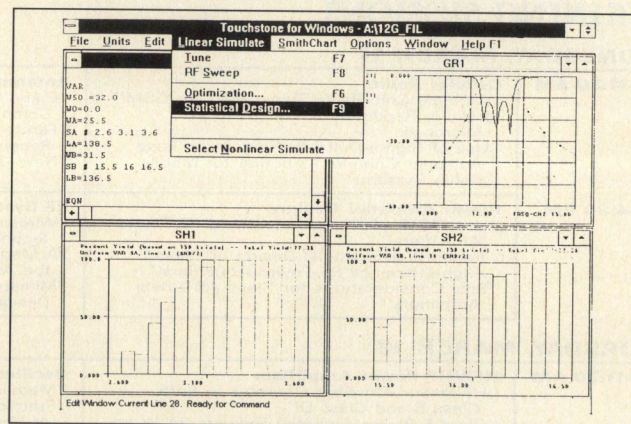

**Watch for more prizes in the next issue
of RF Design!**

YOUR BEST TRAINING INVESTMENT FOR 1993

An unequaled selection of training sessions and exhibits organized by *RF Design* magazine.

Ninth Annual

RF expo WEST

March 17-19, 1993
San Jose Convention Center
Silicon Valley, California

ON DISPLAY:

CAD/CAE SOFTWARE SYSTEMS

Software
Systems — Hardware

COMPONENTS

Capacitors
Crystals
Diodes
Inductors
Integrated Circuits
Resistors
Transformers
Transistors
Vacuum Tubes

EMC PRODUCTS

Absorbers
AC Line Filters
Anechoic Chambers
ESD Control Devices
Gaskets/Finger Stock
Shielded Enclosures
Shielding
Surge & Transient Protectors
Test Equipment & Systems

MATERIALS & HARDWARE

Cabinets and Enclosures
Ceramics
Component/Hybrid Packages

Crystal Blanks
Electronic Hardware
Equipment Racks
Ferrites, Other Magnetics
Heat Sinks
Insulating Materials
PC Boards
Sockets
Substrates

MODULES & HYBRIDS

Amplifiers
Detectors
Filters
Frequency Multipliers
Limiters
Mixers
Modulators
Noise Sources
Oscillators
Resonators

SERVICES

Antenna Measurement
Circuit Assembly
Consultants
Custom Hybrids
Custom ICs and ASICs
EMC Testing
Equipment Calibration

Instrument Rental/Leasing
PC Layout/Fabrication
Plating/Coating
Software Development
Training/Education

SYSTEM BLOCKS & SUBASSEMBLIES

Amplifiers
Frequency Converters
Frequency Synthesizers
Motion/Proximity Sensors
Receivers
RF Modems
Tone Encoders/Decoders
Transmitters

TEST EQUIPMENT

Amplifiers (Lab)
Antenna Measurement Systems
Calibrators/Standards
Dummy Loads
Field Intensity Meters
Frequency Counters
Modulation Meters
Network Analyzers
Noise Figure Meters
Noise Generators
Oscilloscopes
Power Meters
Probes

Pulse Generators
RLC/Impedance Bridges
Signal Level Meters
Signal/Sweep Generators
Spectrum Analyzers
SWR Meters
Test Fixtures
Wave/Distortion Analyzers

TRANSMISSION

COMPONENTS

Antenna Positioners
Antennas
Attenuators
Coaxial Cable
Directional Couplers
Equalizers
Filters
Isolators/Circulators
Loads
Multicouplers
Multiplexers/Diplexers
Phase Shifters
Power Dividers/Combiners
Relays
RF Connectors
Switches
Terminations
Tuners

TRAINING SESSIONS

WEDNESDAY, MARCH 17

Exhibits Open 10 am-6 pm

8:30-11:30 AM	Cellular Radio "A Single Chip Radio Transceiver for GSM" "Cellular Repeaters and/or Cellular Microcells" "Use of Sigma-Delta Technology to Ease Adjacent Channel Rejection for Mobile Radio Systems"	Antennas and Transmission Lines "E and H Field Radiator for Personal Communications Systems/Networks (PCN)" "Ferrite Rod Antennas for AM Broadcast Receivers" "New Generation of RF Transmission Line"	Circuit Analysis Tutorial — Part I "Driving Point Impedance Circuit Analysis Techniques"
1:30-4:30 PM	Power Amplifier Design "Use EMTP (ATP) to Understand RF Power Amplifiers" "Tradeoffs in Practical Design of Class E High-Efficiency RF Power Amplifiers" "Bias Considerations for Class AB Linear Amplifiers"	RF Systems "Wireless Transmission Using Inferred Techniques" "A Medical Radio Frequency Network for the Aged" "Miniaturization Techniques in Receiver Design"	Circuit Analysis Tutorial — Part II "Driving Point Impedance Circuit Analysis Techniques" (continued)

THURSDAY, MARCH 18

Exhibits Open 10 am-6 pm

8:30-11:30 AM	HF/VHF Power Amplifiers "HF Power Amplifier Operates in Both Class B and Class D" "Class-E Power Amplifier Delivers 24 W at 27 MHz at 89.92% Efficiency, Using One \$1.05 Transistor" "A New Method of Input/Output Impedance Measurement for Class C/D Amplifiers Using a Spectrum Analyzer"	Oscillators "Modulating SAW Oscillators" "Practical Methods of Computer Simulation of Very High Q Oscillators Using SPICE and LIBRA"	Electromagnetic Modeling "Circuit Radiation Modeling Based on S-parameters" "Electromagnetic Simulation of RF Discontinuities"
1:30-3:30 PM	UHF and L-Band Power Amplifiers "Transistors for High Power Linear Amplifiers in the 1.5-2.0 GHz" "100-400 MHz 250 Watt Power Amplifier" "3 Stage, 2 Way 50 Watt Linear L-Band Amplifier"	Digital Transmission Systems "The Development of X-Band SSPAs and QPSK Modulators for Remote Sensing Satellite Applications" "Simulating Common Impairments Found in RF Digital Communications Systems"	Components Applications "RF Circuits — The ASIC Way" "Tiny Transceiver, Wireless Microphone, and Superhet Receiver"

FRIDAY, MARCH 19

Exhibits Open 10am-1pm

8:30-11:30 AM	Personal Communications "A Fully Integrated Modulator/Demodulator for DECT" "Vector Modulator IC's for use in Wireless Communication" "A 2.4 GHz Communication System"	Frequency Synthesis "FM Modulation Scheme For A DDS: Digital-PLL Signal Source" "Operating Principle and Applications of a Frequency Independent Phase Tracking Circuit"	Computer Methods "Knowledge Systems: The Fast Track to RF Design and Testing Solutions" "The Design of Software for Automated RF Testing"
---------------	--	---	--

Call or fax now for complete program and registration information:

(303) 220-0600 * (800) 525-9154 * FAX: (303) 770-0253

New Oscillators Advance the Art of Low Noise Performance


By Charles Wenzel
Wenzel Associates

Over the last two decades, tremendous improvements in telecommunications, radar systems, and instrumentation have driven phase noise specifications from near obscurity to prime importance. Quartz crystal reference oscillators are especially crucial since oscillator noise often limits the channel capacity of communication systems, degrades the resolution of radar and timing instruments, gives synthesizers wide skirts and restricts the resolution of spectrum analyzers.

Wenzel Associates has developed new low noise oscillators with significant improvements in phase noise. In addition to a line of component VHF oscillators, a high stability frequency standard is available that employs phase locking to achieve excellent noise and long term aging. The phase noise performance of three, 100 MHz oscillators is shown in Figure 1.

Noise floor measurements near -180 dBc/Hz push the limits of ordinary phase noise measurement systems, so a phase noise calibration was requested of Fred Walls at the National Institute of Standards and Technology (NIST). His system uses a cross correlation technique to greatly reduce the system noise floor for measuring the higher Fourier frequencies. [This measurement technique will be described in the March 1993 issue of RF Design — Editor] Fourier frequencies below 20 Hz were made using a multiplied 5 MHz reference. Each oscillator's noise data was fit to a mathematical model included in Figure 1. Overall measurement accuracy was stated to be ± 1 dB between 1 Hz and 50 kHz.

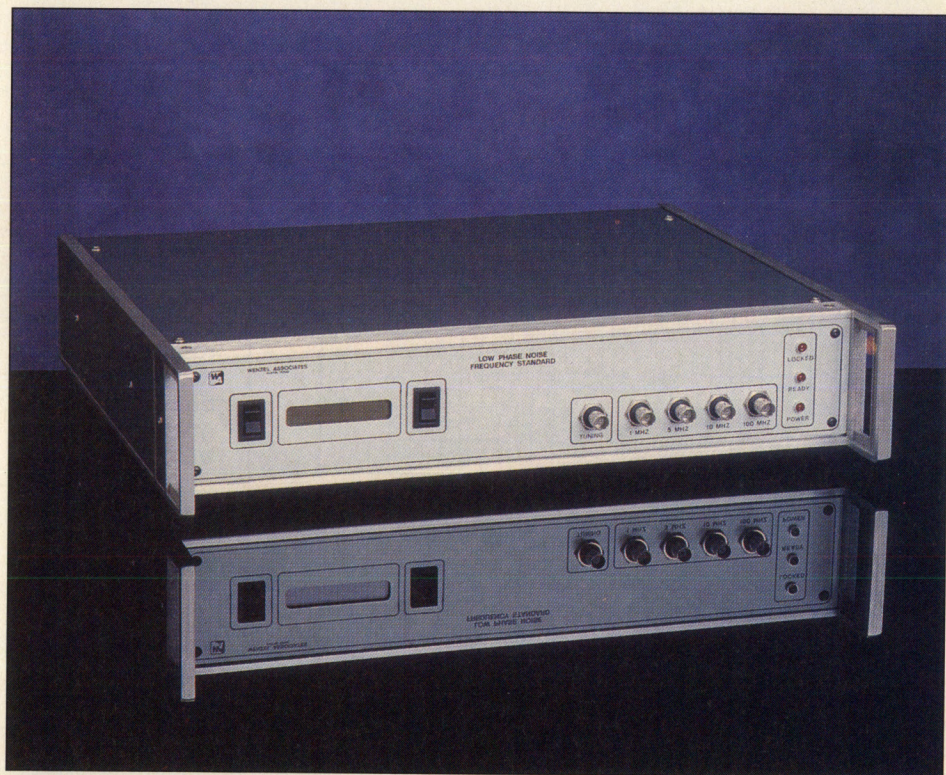Previous attempts to achieve low noise floors have employed drive levels reaching 50 mW in a brute force signal to noise battle with a corresponding



Wenzel Associates' new reference standard offers extremely low phase noise performance.

degradation in close-in noise and aging. The unusual combination of a -180 dBc/Hz noise floor with a -77 dBc/Hz flicker frequency level is achieved by using low crystal dissipation (1 mw) in specially designed low noise circuitry. Careful attention was paid to voltage regulator noise and to oven current noise, two common sources of degraded performance. The oscillators' output level is set to 1 VRMS so the sideband noise at the floor is about 1.4 nanovolts/ $\sqrt{\text{Hz}}$ or about as much noise as exhibited by a 120 ohm resistor. Taking full advantage of such low noise levels poses a significant challenge to the sys-

tems engineer.

The model 500-03475 low phase noise frequency standard combines this new VHF oscillator with a similarly improved 5 MHz reference in a phase locked configuration. Figure 2 shows the phase noise for the standard's various output frequencies. The 5 MHz oscillator noise drops below -150 dBc/Hz 10 Hz away from the carrier and continues down to a floor of -180 dBc/Hz. The bandwidth of the internal phase locked loop is set to about 300 Hz where the 100 MHz oscillator begins to out perform the multiplied 5 MHz reference. The model 500-03475 employs a shielded

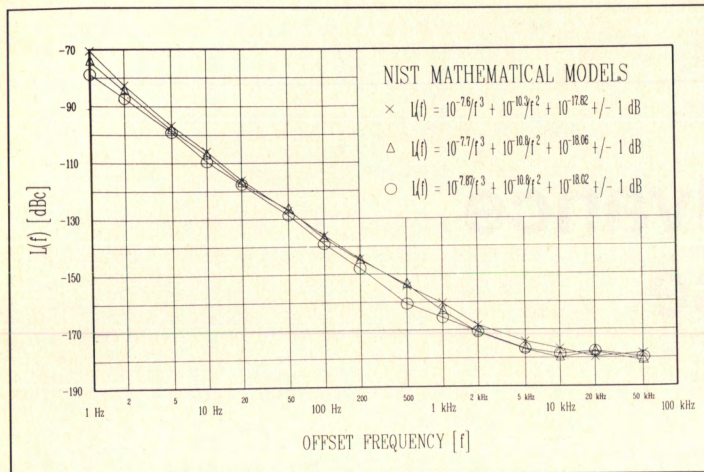


Figure 1. The phase noise of three oscillators measured by NIST.

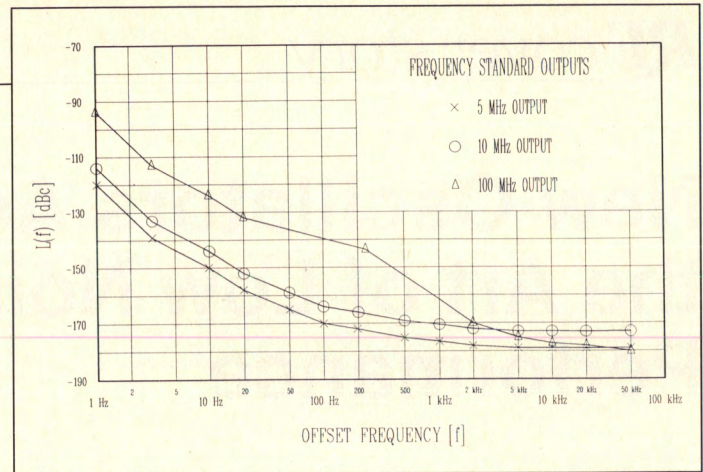


Figure 2. Phase noise performance of the 500-03475 Frequency Standard.

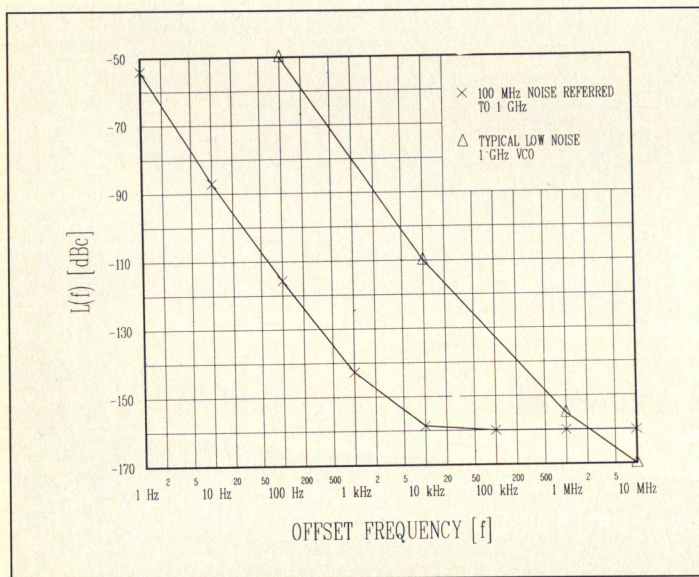


Figure 3. Comparison of a low noise VCO at 1 GHz to the multiplied 100 MHz oscillator.

line transformer to reduce line related noise in addition to a 10 hour rechargeable battery. Other features include digital monitoring of output levels and battery condition and digital control of tuning and aging rate.

High Performance Applications

Crystal oscillators with significantly improved phase noise can enhance a variety of systems. Microwave systems are particularly susceptible to reference oscillator phase noise because the process of frequency multiplication increases the power in the sidebands by the square of the multiplication factor. Phase locked loops or filters are often used to clean up the multiplied reference. In a typical system the filtering bandwidth is set near the point where the microwave oscillator's flicker noise drops below the reference oscillator's noise floor. With a reference noise floor

of -180 dBc at 100 MHz an ideal x10 frequency multiplier would exhibit a noise floor of -160 dBc at 1 GHz, which rivals the noise floor of many microwave sources. Even after multiplication to 10 GHz the resulting -140 dBc floor would remain below the flicker noise of most VCOs out to several MHz. In some applications the VCO might be replaced by a simple filter to remove the subharmonics without any phase noise penalty. Figure 3 compares the new oscillator's noise, after multiplication, to an "ultra low noise" cavity oscillator operating at 1 GHz.

The combination of low flicker and low noise floor improves the bit error rate of a digital communication system for a given modulation scheme since the BER increases with the area under the phase noise curve. This small integrated noise or phase jitter similarly improves the resolution and probability of detection of radars and enhances the accuracy of distance measuring devices.

Modern spectrum analyzers using low noise synthesized local oscillators have improved sufficiently to allow for the direct observation of sideband noise of fairly good sources. A higher performance reference would lower the local oscillator noise even further, making smaller measurement bandwidths feasible for direct measurement of all but the

best sources.

The electronics in these new oscillators is beginning to approach theoretical limits so future improvements will concentrate on the crystal resonators with a goal of lowering the flicker frequency level. Of course, improvements in temperature stability, aging, and other critical parameters will receive continued attention.

For more information on these low noise oscillators and frequency standard, contact the author at the address below, or circle Info/Card #160. **RF**

References

1. Fred L. Walls, "Calibration of 100 MHz crystal oscillators Model 500-02268B Serial #s 0578-9041 and 2110-9220 for Wenzel Associates," report by the National Measurement Laboratory, National Institute of Standards and Technology, Boulder, Colorado, 25 September 1992.
2. Addendum to above report, 6 November 1992.
3. Warren F. Walls, "Cross-Correlation Phase Noise Measurements," 46th Annual Symposium on Frequency Control, Hershey, PA, 1992.

About the Author


Charles Wenzel is president and founder of Wenzel Associates, a manufacturer of high performance frequency standards and oscillator modules since 1978. He is a graduate of the University of Texas at Austin, and a past Grand Prize winner in the RF Design Award Contest. He can be reached at Wenzel Associates, 14050 Summit Drive, Austin, TX 78728; telephone (512) 244-7741.

Communications Link Laser

Ortel has introduced its Model 1541A, a 10 GHz microwave distributed feedback (DFB) laser, designed for transmission distances longer than 5 to 10 km. The single-mode spectrum of DFB lasers offer dramatic improvements over multi-mode lasers in long fiber-path transmission performance. The DFB laser incorporates an optical isolator mounted with the laser diode on the thermo-electric cooler to stabilize the temperature for a more stable optical output over wide operating temperature ranges. Benefits of the new laser and iso-


lator include: higher spur free dynamic range of 115 dB/Hz^{2/3}, transmission distances of 30 to 40 km and reduced link loss of 25 to 30 dB. RF parameters of the model 1541A include: frequency range of 0.1 to 10 GHz, input impedance of 50 ohms and EIN at 2 GHz of less than -125 dBm/Hz. With a guaranteed frequency range of 10 GHz, the laser can be used with C-band satellite up-links, military satellite communications and airborne radar bands.

Ortel Corporation
INFO/CARD #250

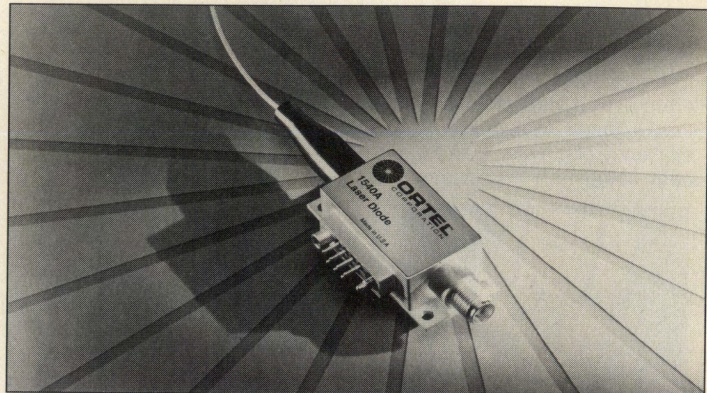

Landline/Wireless Modem Chipset

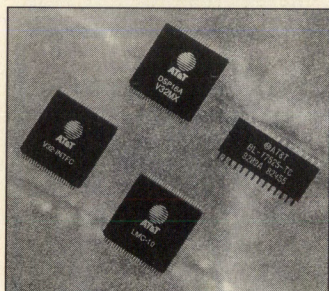AT&T Microelectronics plans to incorporate the MOBITEK two-way wireless data-transmission architecture in its V.32bis and V.17 Complete Modem Chipset, making these modem chips the first to support both high-speed landline and wireless communi-




cations. AT&T's DSP-based modem technology uses the AT&T DSP16A digital-signal processor for transmission and signal recovery of the GMSK-encoded baseband signal used in RAM Mobile Data's Mobitex networks. The DSP16A works with the T7572 codec, the V32INTFC interface device and the LMC10 modem controller. The V32MX Complete Modem Chipset achieves a 8000 bit/s data rate over the air and interfaces directly to third party radio transceivers. The chip set can be sampled in early 1993 and will be in full production by mid 1993. In quantities of 10,000, the chips will be priced at \$109, packaged in plastic quad flat packs. In small-outline QFPs suitable for use in the PCMCIA form factor, the chips will be priced at \$129.

AT&T Microelectronics
INFO/CARD #249

Spectrum/Vector Network Analyzer

Hewlett-Packard has introduced the HP 4396A, a 1.8 GHz combination spectrum and vector network analyzer with an optional built-in instrument controller (Option 1C2). The HP 4396A combines dual measurement and control functions in one instrument, allowing engineers to test a wide variety of RF devices or circuits on one test station. A stepped FFT provides fast spectrum analysis, while excellent noise performance and narrow filter-shape factors improve close-in and small-signal spectrum analysis results. An optional time-gated spectrum analysis capability allows measurement of repetitive signals. Full S-parameter measurements with full error correction can be made within the

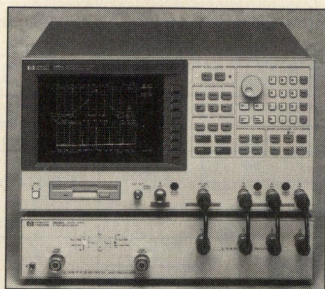


vector network mode. Fast sweep times allow operators to see real-time gain and phase-trace updates. Option 1C2 consists of an instrument-controller and HP Instrument BASIC (IBASIC). Base price for the HP 4396A network/spectrum analyzer is \$33,900 with delivery at four weeks ARO.

Hewlett-Packard Company
INFO/CARD #248

EMC Pre-qualification Equipment

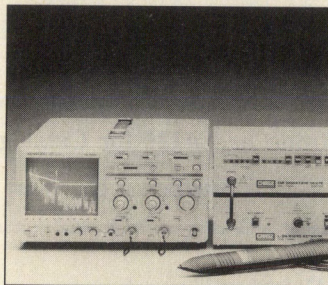The Chase ESS7500 displays the spectral signature of an item under test and can compare this signature to either limit lines or against previously stored signa-




tures. The ESS7500 works with any oscilloscope having a bandwidth of 30 MHz or more. The flicker-free display can show either the complete frequency range (from 3 kHz to 30 MHz) or can inspect smaller ranges individually for a more detailed display. Up to 15 pre-programmed limit-lines (for international or in-house standards) can be stored in ROM. Two non-volatile signature memories are available. Before/after comparisons are possible with this feature, as are comparisons between "golden samples" and production samples. A magnetic near-field probe (MFP9150) and an electric near-field probe (EFP9152) are available for radiated emissions testing, and a 6 Amp mains network (CLN2060) is available for measurement of conducted emissions. The ESS7500 is priced at \$4500, with delivery in two weeks.

ibex Group, Inc.
INFO/CARD #247

Current Feedback Amplifier

National Semiconductor Corporation has introduced a current feedback amplifier, the LM6181, offering a combination of bandwidth (100 MHz), slew-rate (2000 V/us) and output current (100 mA) which makes it ideal for video and other high-speed amplifier applications. Because the LM6181 is a current feedback amplifier, bandwidth is relatively independent of closed loop gain. The amplifier has differential gain of 0.05 percent and a differential phase of 0.04 degrees, key parameters in video applications. The high power output stage enables

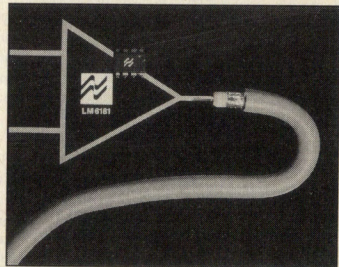


the LM6181 to directly drive a 10 V signal into 50 ohm or 75 ohm back terminated coaxial cable systems over the full industrial temperature range. A free LM6181 evaluation kit, including a fully assembled evaluation board and SPICE micromodel, is available. The LM6181 is fully characterized and specified at both ± 5 V and ± 15 V. Available in both 8-pin plastic DIP and 16-pin SO packages, The LM6181's suggested 1000-piece resale pricing is \$2.45 for both package styles.

National Semiconductor
INFO/CARD #246

Product Spotlight: Transistors

Power MOSFETs

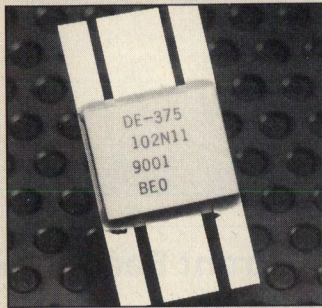The DE-Series from Directed Energy makes it feasible to generate over a kilowatt of power in the HF band, with a conversion efficiency of greater than 85 percent using only two devices in




push pull configuration. Designs based on these devices, at less than \$0.50/watt, are a fraction of the cost of conventional bipolar and low voltage MOSFET approaches.

Directed Energy, Inc.
INFO/CARD #245

Microwave Power Transistors

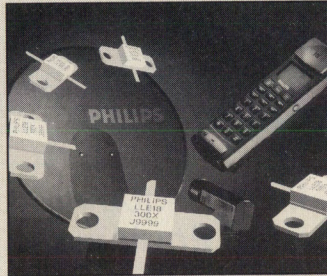New NPN silicon microwave power transistors from Philips Semiconductors reduce the number of components required



in class AB output stages for transmitters operating in the 1.5 to 2 GHz band. The LLE18100X and LLE18300X deliver respectively 10 and 30 W and are opti-

mized for operation in the 1.7 to 2.0 GHz range. LLE16120X and LLE16350X deliver 12 and 35 W, respectively, and are optimized for the 1.5 to 1.7 GHz band.

Philips Semiconductors
INFO/CARD #244


SMT Small Signal Transistors

Motorola has introduced its lowest noise small signal amplifier transistors in a miniature surface-mount package. The MRF947 and MRF957 small signal transistors are state-of-the-art low noise NPN bipolar devices with the same die as Motorola's MRF941 and MRF951 transistors, mounted in the SC-70 surface mount package. In quantities less than 1000, the MRF947 and MRF957 are priced at \$0.43 and \$0.49, respectively.

Motorola Semiconductor
INFO/CARD #243

SMT Military Transistors

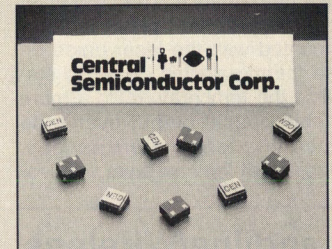Central Semiconductor offer four device types in the new CERSOT-23 case: CHT918, a NPN RF oscillator; CHT2222A, a NPN amplifier/switch; CHT-2369A, a NPN saturated/switch; CHT2907A, a PNP amplifier/switch. The CERSOT-23 case is



a hermetically sealed, leadless chip carrier which mounts on SOT-23 pads. JANTXV construction includes pre-cap visual inspection.

Central Semiconductor Corp.
INFO/CARD #242

WBE

Circle Info/Card #125 for Catalog and Price List.


DIRECTIONAL COUPLERS

A73 Series Directional Couplers are of reciprocal hybrid ferrite circuitry, featuring broad bandwidth with outstanding directivity and flatness.

Some general applications for the A73 Series are:

- Line Monitoring:** Power split from the line is -20 dB down for sampling without altering line characteristics, for level measuring, VSWR alarms, etc..
- Power Measurements:** Insertion in the line allows level measurements with simple lower level detectors or field strength meters and power measuring equipment. By reversing the coupler in the line or using the A73D types, an indication of impedance match and/or reflected power can be measured by comparing the forward to reflected power levels.
- Load Source Isolator:** Using a directional coupler in the line, a signal can be taken from the source to the tap with high attenuation (directivity) between the tap and the load.

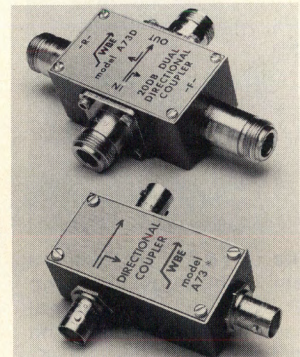This chart is just a sampling of couplers available. Connector options available. Consult factory for specials and OEM applications.



Model	Freq Range MHz	Coupling Level dB	Coupler Type	In Line Power	Minimum Directivity (dB)		In Line Loss (dB)	Flatness of Coupled Port (dB)	VSWR	Price 50 ohm with BNC conns.
					1-500 MHz	5-300 MHz				
A73-20	1-500	20	single	5W cw (10W cw 5-300 MHz)	20	30	.4 max .2 typical	±.1 5-300 MHz ±.25 1-500 MHz	1.05:1	\$68.00
A73-20GA					30	40			5-500 MHz	\$131.00
A73-20GB					40	45			1-500 MHz	\$242.00
A73-20P	1-100	20	single	50W cw (75 ohm limited to 10W cw)	35 dB min 40 dB min typical		.15 .3	±.1	1.1:1 max	91.00
A73D-20P			dual		.15	150.00				
A73-20PAX	10-200	20	single	50W cw (75 ohm limited to 10W cw)	45 dB min		.15 .3	±.1	1.04:1 typical	310.00
A73D-20PAX			dual		.3	300.00				
A73-20GAU	1-1000	20	single	2W cw	30 dB min 40 dB typical		1 max .3 typical	±.25	1.1:1 10-1000 MHz	425.00
A73-20GBU			single		40 dB min 45 dB typical				1.5:1 1-10 MHz	312.00
A73-30P2	1-100	30	single	200W cw 50 ohm	30 dB		.05	±.15	1.05:1 max	312.00

WIDE BAND ENGINEERING COMPANY, INC

P. O. Box 21652, Phoenix, AZ 85036


Phone: (602) 254-1570

Fax: (602) 254-1570

INFO/CARD 125

Broadband, N-Channel MOS-FETs

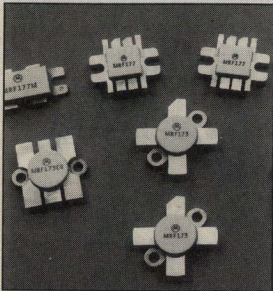Two transistors from Motorola feature high gain



and high power capabilities, along with broadband operation. The MRF173 is designed for broadband commercial and military applications in the 2 to 200 MHz range. At 150 MHz and 28 V, the MRF173 has 11 dB gain and an output power of 80 W. The MRF177 is designed for broadband applications in the 2 to 400 MHz range. At 400 MHz and 28 V, the MRF177 has 12 dB gain and an output power of 100 W.

Motorola Semiconductor
INFO/CARD #241

HJ FET

The NE32684A from CEL is a pseudomorphic HJ FET designed for low noise figure requirements in the 0.5 to 30.0 GHz range. Noise figure is 0.5 dB typ. with gain of 11.5 dB typ. at 12 GHz. Gate length is less than 0.2 microns. The NE-32684A is in an epoxy sealed metal/ceramic package and is available on tape and reel.

California Eastern Laboratories, Inc.
INFO/CARD #240

AMPLIFIERS

Gain Adjustable Amplifier

MITEQ introduces a new series of ultra-wideband, low-noise

amplifiers with variable gain option. Designated as AVG6-00102100-8, the amplifier covers the 100 MHz to 21 GHz frequency range with 24 dB gain. Gain can be continuously adjusted for 0-15 dB attenuation. The amplifier input/output ports are matched to 10 dB min. return loss.

MITEQ
INFO/CARD #239

Low Distortion Amplifiers

Phoenix Microwave announces a new class of low distortion power hybrid amplifiers for the communications industry. Model PA996 offers linear output power of 20 dBm over the 50 to 500 MHz frequency range with typical third and second order intercepts of 35 and 64 dB, respectively. The unit is offered in a hermetic dual in-line or flatpack package configuration. Availability is stock to 45 days.

Phoenix Microwave Corporation
INFO/CARD #238

100 W, UHF Amplifier

Model 400-220-100-35A UHF power amplifier has an output power level of 100 W CW from 220 to 440 MHz or can be customized to deliver that power over the 400 to 500 MHz band. The amplifier has over 45 percent efficiency with 35 dB of gain and operates from a 28 V supply. This model is available as a module (measuring 4.84 x 2 x 1 inches) or as a rack-mountable system with power and cooling.

LCF Enterprises
INFO/CARD #237

Integrated Power Amplifiers

Modularized, integrated designs are employed in amplifiers producing RF output powers to 10 kW for select frequency bands between 2 and 135 MHz. Efficient RF designs, coupled with switching regulator and power factor correction pre-regulation modules, result in minimum AC line current with low distortion. Typical ratio of RF power output to AC line VA input is 0.50.

Brounley Engineering
INFO/CARD #236

Take Control.

When frequency control is critical, call us for quick response, technical assistance, and precision production and testing of quartz crystals.

JAN Crystals

DESIGN • PROTOTYPING
MANUFACTURING

CALL TOLL FREE: 1-800-JAN-XTAL



Post Office Box 06017
Fort Myers, Florida 33906




INFO/CARD 34

CERAMIC RF CAPACITORS

C-D/SANGAMO

MICA RF CAPACITORS

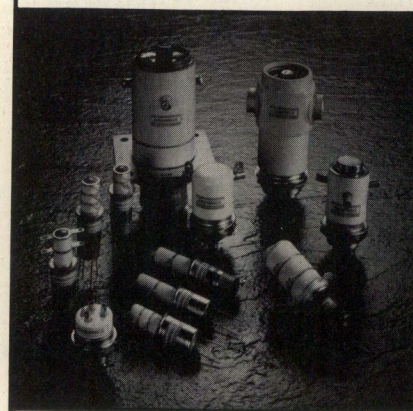

JENNINGS

VACUUM CAPACITORS
VACUUM RELAYS

SURCOM ASSOCIATES, INC.

2215 Faraday Avenue, Suite A
Carlsbad, California 92008
TEL (619) 438-4420
FAX (619) 438-4759

CRYSTALS
70KHz-200MHz

OSCILLATORS
70KHz-200MHz

TCXO, VCXO, TCVCXO
4 MHz-125MHz

**Alignment Oscillators
Crystal and Oscillator
Accessories**

Call or fax TOLL FREE for information

INTERNATIONAL CRYSTAL MFG. CO., INC.
P. O. Box 26330 • 729 W. Sheridan • Oklahoma City, OK 73126-0330 • (405) 236-3741
FAX (405) 235-1904 • Toll Free Phone 1-800 426-9825 • 24 Hour Toll Free Fax 1-800 322-9426

INFO/CARD 35

RF and Microwave Power Semiconductors

Design, Production or Maintenance

- Cellular
- GPS
- Telemetry
- PCN
- GSM
- SATCOM
- Avionics
- Wireless LAN
- Wireless ID
- Land Mobile
- Broadcast
- Industrial



RF PRODUCTS, inc.



Power Components Inc.

Available: Data Sheets, Technical Assistance, Cross References, Value Added Services Include: DC Matching (BiPolar) and GFS Matching (FETs) and Same Day Shipment

We Speak RF.

In the U.S. 1-800-RF POWER (1-800-797-6937),

Canadian office: 1-800-348-5580,

International inquiries 708-208-2200



Richardson Electronics, Ltd.

Corporate Headquarters
40W267 Kesling Road
LaFox, IL 60147-0393

INFO/CARD 36

RF products *continued*

SEMI-CONDUCTORS

12-bit DAC for DDS

Burr Brown's DAC600 is a 12-bit, monolithic D/A converter featuring the best harmonic distortion and DC linearity in its speed range. The DAC600 has a 256 MHz clock rate, 5 ns 12-bit settling time, 900 mW power dissipation and 74 dB SFDR ($f_{clk}=100$ MHz, $f_0=10$ MHz). It is ECL compatible and priced from \$79 each in quantities in the 100's. Delivery is from stock.

Burr-Brown Corp.
INFO/CARD #235

Feedback-less Differential Amplifier

Maxim announces the new MAX435/MAX436 wideband (275 MHz) transconductance amplifiers with a unique architecture that provides extremely high common mode rejection (53 dB @ 10 MHz) and accurate gain (± 2.5 percent) without feedback. The commercial, plastic DIP and SO versions of the MAX435 and MAX436 are priced at \$2.75 in quantities of 1000.

Maxim Integrated Products
INFO/CARD #234

Low Cost GaAs VCO

The ADC20010, by Anadigics is a GaAs VCO chip costing only \$7 in quantities of 100. The VCO has output power of 5 dBm and phase noise of -70 dBc/Hz at 10 kHz offset. Tuning range is 1430 to 2600 MHz with a control voltage from 1 to 20 V. The chip comes in a surface mount package with power dissipation typically less than 65 mW. Small quantities are available from stock; larger quantities can be shipped in six to eight weeks.

Anadigics, Inc.
INFO/CARD #233

High Speed RSSI IF System

The NE/SA624/625/627 FM IF system ICs from Philips Semiconductors feature received signal strength indicators (RSSIs) which

respond up to eight times faster than those in previously available devices. The 624 incorporates two limiting IF amplifiers, a quadrature detector, muting circuit, logarithmic RSSI and a voltage regulator. The 625 adds a mixer oscillator, and the 627 adds a mixer oscillator and an additional limiter amplifier.

Philips Semiconductor
INFO/CARD #232

50 MHz, 80 dB RSSI

Designed as a demodulating logarithmic amplifier for received signal strength indicator (RSSI) functions in mobile phones and receivers, Analog Devices' AD606 is also effective as a high performance limiting amplifier in FM demodulators and wireless LAN equipment. As a log amp, overall dynamic range is -75 to $+5$ dBm. As a limiter, it provides a hard-limited signal output as a differential current of ± 1.2 mA from open-collector outputs.

Analog Devices, Inc.
INFO/CARD #231

LNA MMIC

TriQuint has announced the TQ9121N, a surface mount, low noise amplifier (LNA) for GPS and other narrow band applications in the 1.2 to 1.6 GHz. The TQ9121N supplies typically 16 dB gain at the GPS frequency band. The device has a 1.25 dB noise figure and third order intercept point, with respect to the output, of $+11$ dBm. It operates from a $+5$ V supply. The TQ9121N is \$5.40 in quantities of 500 to 999.

TriQuint Semiconductor
INFO/CARD #230

CABLES & CONNECTORS

Phase-Matched Cables

Available on a quick delivery basis from MAST Microwave is a full line of custom phase-matched microwave cable assembly sets. Both flexible and semi-rigid cables are offered in a wide variety of cable and connector combinations. The MAST line covers frequencies from DC to 26.5 GHz. Typically, the cable assembly sets hold absolute phase

deviation within ± 5 degrees.
MAST Microwave
INFO/CARD #229

SIGNAL SOURCES

Miniature Phase Locked Sources

EM Research Engineering has introduced a line of miniature phase locked signal sources covering 100 to 2500 MHz. S packages come as small as 1.5 x 1.5 x 0.75 inches and are PC mountable. The A package is a stand-alone 2 x 2 x 0.75 inch aluminum housing with standard SMA female connectors. These sources can be internally or externally referenced.

EM Research Engineering, Inc.
INFO/CARD #228

TCXO

Piezo Technology has developed a new temperature com-

pensated crystal oscillator. Model XO3010C offers a standard ± 0.3 ppm stability over the temperature range of 0 to +70 degrees C. The standard frequency is 10.0 MHz, with optional frequencies between 8.0 and 15.0 MHz. Output is 7 ± 2 dBm sinewave into 50 ohms with a supply of +12 V.
Piezo Technology, Inc.
INFO/CARD #227

Low Profile OCXO

Model TK802, hybrid ovenized oscillator, operates over 50 to 100 MHz with temperature stabilities of ± 0.05 ppm over -20 to +70 degrees C. With warm-ups less than five minutes, the OCXO achieves 5×10^{-8} stability with +28 V at 250 mA heater current. Phase noise is -135 dBc/Hz at 1 kHz and -155 dBc/Hz at 10 kHz. The package measures 2 x 2 x 0.75 inches. Price is \$790 in quantities less than 10.

ST Microsonics Corp.
INFO/CARD #226

Half-Size AC MOS

M-tron's MAH series oscillators offer a state-of-the-art, TTL and CMOS compatible, high frequency clock oscillator. The MAH oscillator is available in the 70-135 MHz range. Its leads are on 0.300 x 0.300 inch centers (8-pin DIP compatible), and the overall dimensions are 0.520 x 0.520 inches maximum. Surface mount and extended temperature and stability options are available.

M-tron Industries, Inc.
INFO/CARD #225

TEST EQUIPMENT

HF Channel Simulator

Signatron's model S-251A Real-Time HF Channel Simulator permits comprehensive modem testing over a very wide range of HF channel conditions. The simulator comprises a card to be

installed in an IBM compatible computer and software. The simulator operates on a 4 kHz bandwidth channel and allows the user to independently vary the delay, Doppler shift, Doppler spread and amplitude for up to six multipath components.
Signatron Corp.
INFO/CARD #224

Analog Network Analyzer

The model 102A Analog Network Analyzer plots magnitude and phase versus frequency in the 0.01 Hz to 15 MHz range. The analyzer has 100 dB dynamic range, 0.01 dB magnitude resolution and 0.1 degree of phase resolution. The analyzer uses an IBM compatible PC to provide the graphical interface and to host the analyzer's DSP board. The model 102A Analog Network Analyzer has a price of \$3795 including probes.

AP Instruments
INFO/CARD #223

RF design


REPRINTS
REPRINTS
REPRINTS
REPRINTS

RF Design reprints are available for printing in quantities of 500 or more.

For further information contact:

Reprint Department
RF Design
6300 S. Syracuse Way, Suite 650, Englewood, CO 80111
(303) 220-0600

Radio Links

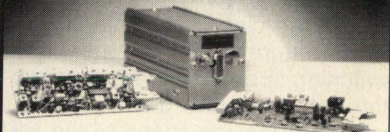

- ▶ Eliminate leaseline and wireline costs
- ▶ Aggressively priced with quantity discounts available
- ▶ Transmitter and receiver links in VHF, UHF and 900 MHz are designed specifically for high-performance data transmission
- ▶ Utility data system accommodates audio inputs (modem tones) or TTL-level digital inputs
- ▶ RS-232 radio modems available in VHF, UHF and spread-spectrum (unlicensed) frequencies
- ▶ A two-way radio manufacturer for more than 30 years

Repro Aerotron-Repro Sales, Inc.
1-800-950-5633

2400 Sand Lake Road
Orlando, Florida 32809

Dealer Inquiries Invited

INFO/CARD 37

Switching Speed: Definition and Measurement

By Ra'anan Sover
Microkim Ltd.

RF switches have been around for quite some time. Whether they are electro-mechanical or solid state, switching speed is still one of the most important characteristics. A general comparison of different types of switches and their performance has already been conducted, see References 1 and 2. Even so, there are several different definitions and methods of measurement of the switching speed (3,4,5,6,7,8). In this paper, we will take a closer look at the definition of switching speed and several methods of measurement.

The exact definition of switching speed must be related to the specific switch being tested and the system requirements. Since most "off-the-shelf" switch vendors do not know where their switch will end up, a more common definition is required. This definition is what we call the classic switching speed definition (Figure 1). It can be seen that the switching speed is made up of two basic time intervals: the driving circuit delay and the transition speed of the RF components. In some cases, the transition time (rise/fall time) is mistaken for the switching speed. The switching speed is the total time interval between the cross-

ing of the 50 percent level of the control signal and the 10 percent or 90 percent level of the RF signal. The 100 percent level corresponds to the steady state insertion loss and the zero percent corresponds to the ideal isolation state. A true zero percent RF (infinite dB isolation) is not physically achievable. We must then relate the 10 percent and 90 percent RF level to the insertion loss level. Therefore, the 90 percent RF level can be seen as the insertion loss level less 0.45 dB, and the 10 percent RF would be the insertion loss level less 10 dB. Since most of the RF switches have an isolation much greater than 10 dB, the classic definition takes into consideration only a small part of the isolation. This may be a good enough definition for general switching speed measurement, but it leaves a lot of uncertainty about what happens at higher isolation levels.

For example, let us look at two solid state PIN diode switches (Figure 2). Both switches were designed to give at least 80 dB isolation within the 2 to 6 GHz region. One was designed using only series PIN diodes while the other uses both series and shunt PIN diodes. Using a test set-up, which will be

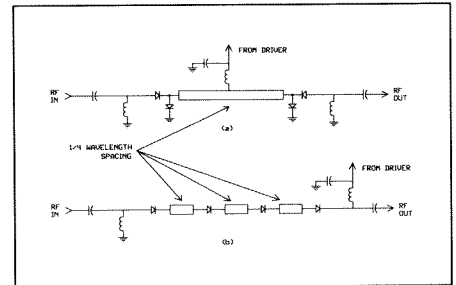


Figure 2. Tested switches' circuit diagrams, a) Series/shunt PIN diode switch, b) All series PIN diode switch.

described later, and a suitable driver, the switching behavior can be seen in Figure 3. The switch with the series/shunt diodes reaches full isolation fairly quickly. The switch with all series diodes initially starts to "turn off" quickly but then decays slowly to the full isolation state after a much longer period of time. This behavior is due to the fact that the diodes are in series and the stored charge in the I-layer of the diodes must recombine through the other diodes while the stored charge of the series/shunt diodes can recombine directly through the driver. Using the

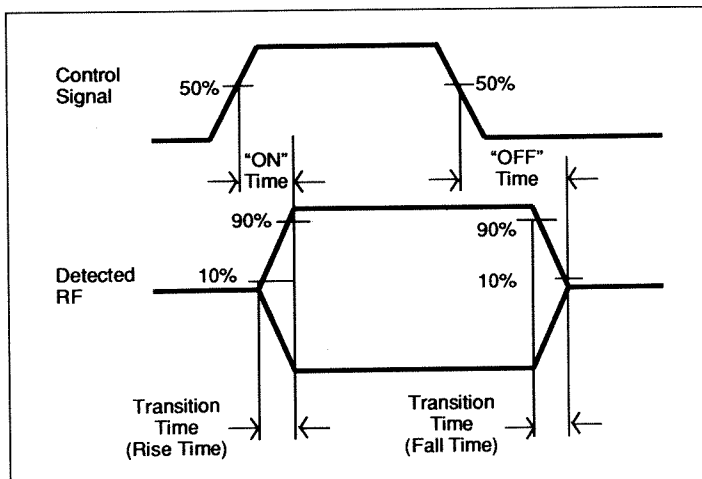


Figure 1. The classic switching speed definition.


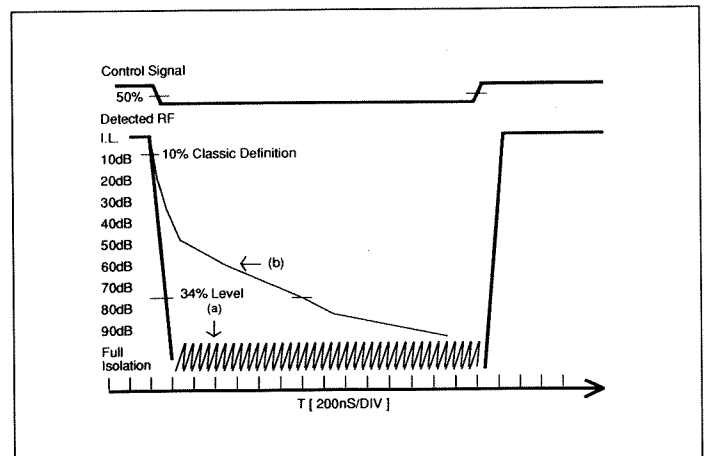


Figure 3. Switching behavior of the two switches, a) Series/shunt switch, b) Series only switch.

incredible!

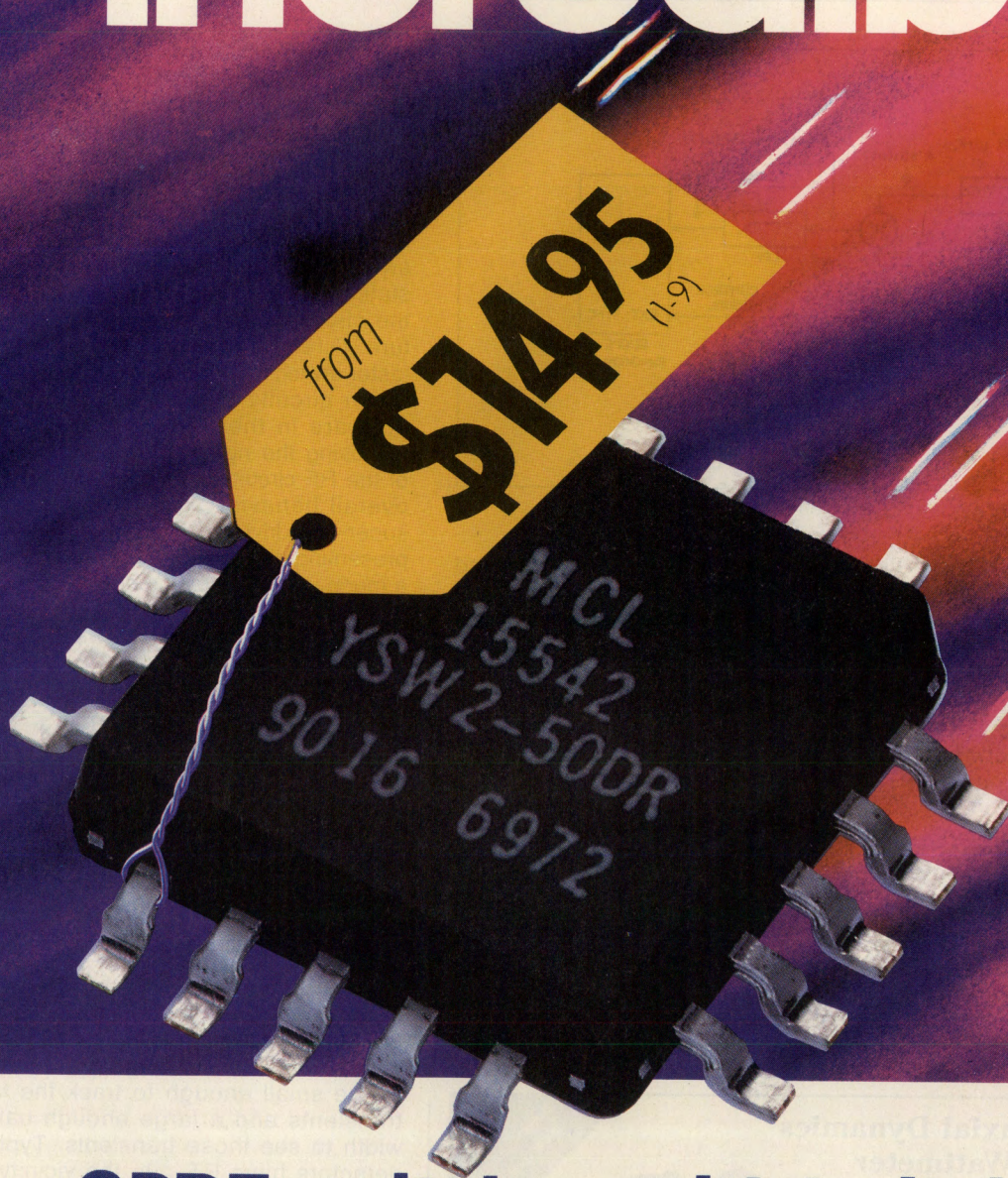


SPDT switches with built-in driver

ABSORPTIVE or REFLECTIVE dc to 5GHz

Truly incredible... superfast 3nsec GaAs SPDT reflective or absorptive switches with built-in driver, available in pc plug-in or SMA connector models, from only \$14.95. So why bother designing and building a driver interface to further complicate your subsystem and take added space when you can specify Mini-Circuits' latest innovative integrated components?

Check the outstanding performance of these units... high isolation, excellent return loss (even in the "off" state for absorptive models) and 3-sigma guaranteed unit-to-unit repeatability for insertion loss. These rugged devices operate over a -55° to +100°C span. Plug-in models are housed in a tiny plastic case and are available in tape-and-reel format (1500 units max, 24mm). All models are available for immediate delivery with a one-year guarantee.

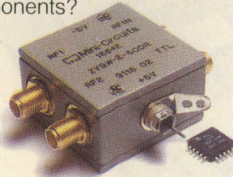

finding new ways ...
setting higher standards

SPECIFICATIONS (typ)

	Absorptive SPDT			Reflective SPDT		
	YSWA-2-50DR	YSWA-2-50DR	ZYSWA-2-50DR	YSW-2-50DR	YSW-2-50DR	ZYSW-2-50DR
Frequency (MHz)	dc-500	500-2000	2000-5000	dc-500	500-2000	2000-5000
Ins. Loss (dB)	1.1	1.4	1.9	0.9	1.3	1.4
Isolation (dB)	42	31	20	50	40	28
1dB Comp. (dBm)	18	20	22.5	20	20	24
RF Input (max dBm)	—	20	—	22	22	26
VSWR "on"	1.25	1.35	1.5	1.4	1.4	1.4
Video Bkthru (mV,p/p)	30	30	30	30	30	30
Sw. Spd. (nsec)	3	3	3	3	3	3
Price, \$ (1-9 qty)	YSWA-2-50DR (pin) 23.95 ZYSWA-2-50DR (SMA) 69.95			YSW-2-50DR (pin) \$14.95 ZYSW-2-50DR (SMA) 59.95		

Mini-Circuits™

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK INFO/CARD 43

F141 REV. D

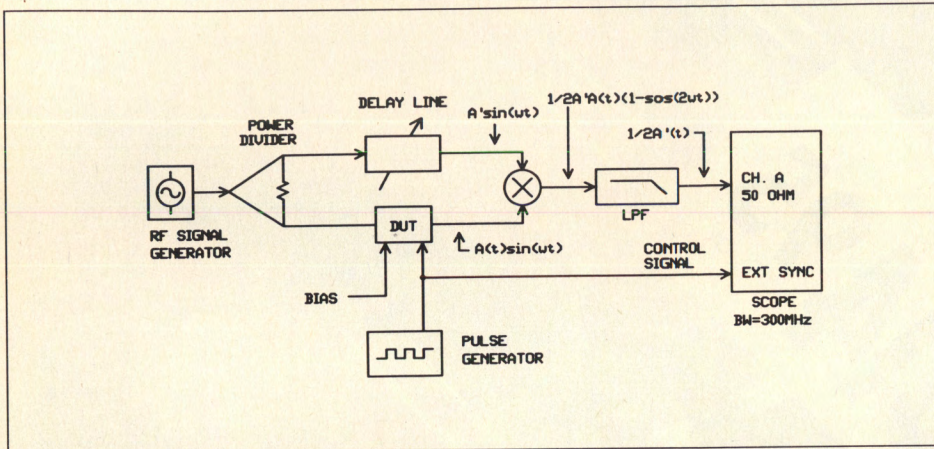


Figure 4. Test set-up using mixer.

classic definition, both these switches have about the same switching speed even though only one reaches full isolation within a short period of time. Similar examples can even be seen from vendors' advertisements and photographs of switching times. One only has to take a closer look at the photographs of the switching behavior to see a slight ringing effect or sloping-off at the trailing edge of the RF envelope. They may seem slight, but the dynamic range of the scope is only 20 to 40 dB, so those "bumps" can be as high 20 to 30 dB.

These examples show that the classic definition of switching speed is sometimes incomplete. To get a more precise definition we have to transform the classic 10 percent RF level to a much lower

level within the range of the required isolation. If, for instance, the required isolation of the switch is at least 80 dB then we can define the "off time" as the time the RF level reaches a level within 5 dB of the required isolation (75 dB, 3×10^{-6} percent) or any other criterion as required. This will then give us a true picture of how the switch behaves. This new criterion ultimately changes the definition of the transition time as well. Therefore, it would be measured now from the crossing of the 0.5 dB from insertion loss level (90 percent) to the crossing of the 75 dB isolation level and vice versa.

Until now we have dealt with RF component delays. However, the driving circuit also has a large effect on the overall

switching speed due to the internal delay of the circuit itself. A large number of drivers comprise some sort of TTL/ECL input circuit which has a propagation delay of several nanoseconds (depending on the technology) and an analog driving circuit with a delay of several nanoseconds to milliseconds. High switching speed hybrid drivers switch states within 6 to 12 ns depending on the circuit load and ambient temperature. Direct driving circuits have even faster switching speeds. Most monolithic driver circuits are somewhat slower; they are in the 50 to 200 ns range. Choosing the right driver to fit the load of the RF circuit can also determine the overall behavior. You can connect a super fast driver to a switching element presenting a heavy load and end up with a much longer switching speed than you expected; whereas a slower driver capable of driving the heavy switch would yield better results.

Methods of Measurement

There are several methods of measuring the switching speed of an RF switch. They can range from very simple to very complex as we shall see. Perhaps the most common and simplest is the method using an AM detector circuit (Schottky or tunnel diode) to convert the RF peak voltage into a DC level, which can then be seen on a scope. An example of such a test set-up can be seen in Reference 9. The scope should have a low input impedance (50 ohms) in order that the time constant of the AM detector be small enough to track the fast transients and a large enough bandwidth to see those transients. Typical detectors have PT_{SS} in the vicinity of -40 dBm and a dynamic range of 40 dB. Since the detected voltage follows the square law of the input power, it is very difficult to see the entire dynamic range on the scope at a specific V/div setting. Using an attenuator, one can see and calibrate at least a 20 dB dynamic range (in most cases). If one uses the classic definition, where at least 10 dB dynamic range is required, this method of measurement is quite satisfactory. Most of the detectors of this type have a high VSWR at the input, therefore it is recommended that an isolator be placed between the DUT and the detector in order to prevent ringing due to mismatching.

Another method of measurement is the down conversion method whereby the modulated RF signal is downconverted to DC with the help of a mixer

Measure Up With Coaxial Dynamics Model 83550 Digital Wattmeter

The "Generation Gap" is filled with the "new" EXPEDITOR, the microprocessor based R.F. AnaDigit System. The EXPEDITOR power computer... you make the demands, it fills the requirements.

- Programmable forward AND reflected power ranges.
- Can be used with the elements you now have.
- Compatible with all Coaxial Dynamics line sizes and power ranges.
- 18 scales from 100 mV to 50 kW.

Contact us for your nearest authorized Coaxial Dynamics representative or distributor in our world-wide sales network.

- **PEAK POWER CAPABILITY NOW AVAILABLE**



COAXIAL DYNAMICS, INC.

15210 Industrial Parkway
Cleveland, Ohio 44135
216-267-2233 1-800-COAXIAL
Fax: 216-267-3142

Service and Dependability... A Part of Every Product



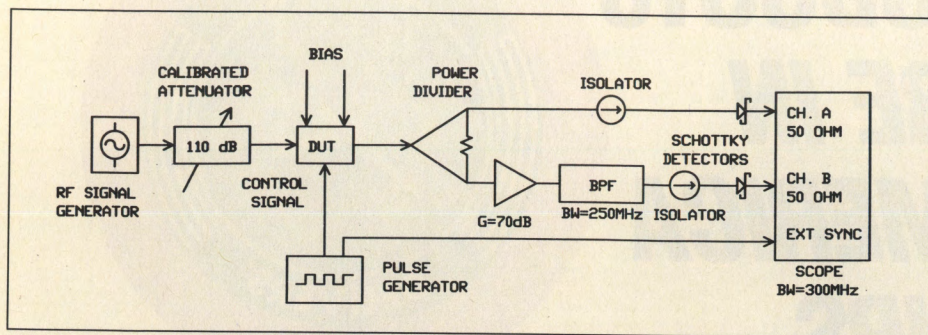


Figure 5. Test set-up measuring the first and last 20 dB of the switch dynamic range.

(Figure 4). A CW RF signal is passed through the DUT which modulates the signal. This signal is mixed with the original CW RF signal to produce two new byproducts, one at twice the original frequency of the RF signal and one at DC. This signal at DC is actually the RF envelope of the modulated RF signal from which the switching signal can be obtained. A low pass filter is used to remove the high frequency components and the phase shifter is used to obtain a maximum RF envelope amplitude from the mixer by multiplying the modulated signal and the CW RF signal in phase. The RF envelope can be seen on an oscilloscope as described earlier, but this method lacks dynamic range due to the limitations of the oscilloscope.


With present sampling oscilloscopes, the DUT can be directly connected to the scope and the RF signal envelope seen on the display. This method of measurement also lacks dynamic range as does the previous method because, here too, a specific V/div is usually set, which limits the range one can observe. In some cases, the size and resolution of the display is enough to see a 40 dB dynamic range (200mV/2mV ratio) making this method slightly better than the previous one. Again, this method is quite satisfactory when using the classic definition. The only disadvantage of this method is the extremely high price of very high bandwidth sampling oscilloscopes.

As we have noted, the problem is: how can we observe the full dynamic range at one time? A possible solution would be to use a device called a DLVA detector (Detector Log Video Amplifier) or SDLA (Successive Detector Log Amplifier) (10,11) which consists of three basic components: 1) an AM detector of the RF signal 2) a wide band RF/video amplifier and 3) performance of LOG of the detected and amplified signal. These enable the detection of

weak signals since the PT_{SS} of these devices is between -40 dBm and -70 dBm with a dynamic range from 40 dB to 70 dB. The output signal voltage is presented in a dB scale (mV/dBm) enabling us to see simultaneously a much larger dynamic range on the oscilloscope. This would seem to have solved our problems, but some of the other characteristics of these devices prevent us from using them to measure fast switches (sub-microsecond switching speeds). First, these devices have a propagation delay of their own, which may be within the same time range as the switching speed of the DUT. Secondly, the rise and fall times are limited by the slew rate of the video amplifier and could be mistaken as the rise/fall time of the DUT. And lastly, they usually have a very long recovery time which may be interpreted as part of the "off time" of the DUT.

Since it is impossible to see a dynamic range of 60 to 100 dB on one oscilloscope display, let us look at the two extremes: the first 20 dB measured from the insertion loss level and the last 20 dB measured to the isolation state. Using the test set-up in Figure 4, the first and last 20 dB can be seen simultaneously on the scope. The RF signal from the switch is split into two paths: channel A displays the first 20 dB since the input power is high enough to be detected directly by the detector, and channel B displays the last 20 dB since the extremely low power near the isolation is amplified to a level high enough for the detector. Each channel complements the other, what can not be seen at a specific time on one channel can be clearly seen on the other. For example, during insertion loss the detector of channel B is "blinded" by the saturation of the amplifier, but the detector of channel A detects the signal properly. Care should be taken when choosing the amplifier: 1) the gain should be in the

SOLID STATE SWITCHES AND ...

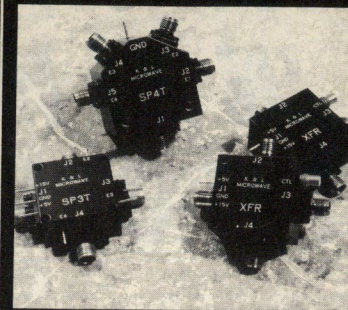

Type	Freq. GHz	I.L. ref./non-ref.
SP1T with Driver	.5-1.0	1.2
	1-2.0	1.2
	2-8.0	2.0
	8-18.0	2.5
SP2T with Driver	.5-4.0	1.8
	4-12.4	2.2
	12.4-20	2.5
SP4T with Driver	.5-4.0	2.5
	4-12.4	2.8
	12.4-18	3.5

Type	VSWR	ISO dB	S.S. nS
SP1T with Driver	1.6:1	45	20
	1.6:1	70	20
	1.7:1	85	20
	1.8:1	80	20
SP2T with Driver	1.8:1	75	250
	1.9:1	60	250
	2.0:1	50	250
SP4T with Driver	1.8:1	60	250
	1.9:1	60	250
	1.9:1	55	250

Request detailed data sheet for mechanical/electrical specifications.

NEW FROM

K&L
MICROWAVE INCORPORATED

DOVER TECHNOLOGIES COMPANY

408 Coles Circle
Salisbury MD 21801
Phone: 410-749-1144
FAX: 410-749-4592

ANZAC PRODUCTS *ANYWHERE IN NORTH AMERICA IN 24 HOURS* THROUGH **PENSTOCK**



M/A-COM ANZAC products are world leaders in a wide range of RF signal processing components including amplifiers, control devices, couplers, mixers and power dividers for commercial, industrial and military applications. The M/A-COM ANZAC product line includes conventional discrete component devices as well as their market-leading line of GaAs control devices.

For a free catalog, to place an order or for technical/application assistance call the Penstock office nearest you . . .

Penstock Northwest
 Tel (800) 736-7862

Penstock Midwest (Illinois)
 Tel (800) 736-7862

Penstock New England
 Tel (800) 736-7862

Penstock Northern California
 (Headquarters)
 Tel (408) 730-0300 or (800) 736-7862

Penstock Midwest (Indiana)
 Tel (800) 736-7862

Penstock East (Long Island)
 Tel (800) 736-7862

Penstock Southern California
 Tel (800) 736-7862

Penstock East (Pennsylvania)
 Tel (800) 736-7862

Penstock Rocky Mountain
 Tel (800) 736-7862

Penstock East (New Jersey)
 Tel (800) 736-7862


Penstock Texas
 Tel (800) 736-7862

Penstock Mid-Atlantic
 Tel (800) 736-7862

Penstock Midwest (Kansas)
 Tel (800) 736-7862

Penstock South
 Tel (800) 736-7862

Penstock Florida
 Tel (800) 736-7862

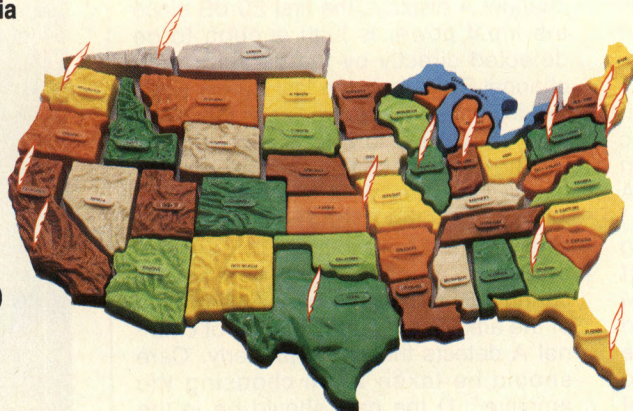

vicinity of the isolation of the DUT 2) an amp with a very short delay should be chosen 3) the amp saturation recovery time should be very fast and 4) the output saturated power must be low so as to not burn out the detector. With the use of a step attenuator, one is able to find the -0.5 dB level on channel A and the 5 dB from isolation (for example) on channel B. The filter is used to remove any spurs produced by the amplifier due to the RF switching. This method ensures that no unwanted behavior occurs in the entire dynamic range of the switch being tested. As described earlier, the slow decay of the series switch would be immediately observed since the switch will settle in the full isolation state only after a long period of time.

This method can be used for any dynamic range required. So if the switch being tested has an isolation of 60 dB, one only has to choose an amp with approximately 50 dB gain and calibrate using the step attenuator to the -55 dB level. In all cases one must be careful with the construction of the switching speed test set-up. Cable lengths must be taken into account. Isolator, filter and amplifier propagation delays must be compensated. In some cases the delays of the above components are within the same time range of the switching speed being tested. These propagation delays become very important when measuring very fast switches. A 10 ns propagation delay due to a test set-up is negligible when measuring a switching speed in the millisecond range, but it gives 100 percent error for a device switching in about 10 ns.

Summary

We now know that the classic switching speed definition may still be valid for general switching speed measurement. Although it does not always give us a complete picture of the behavior of the switch being tested. In those cases where high isolation is required, one has to use a different definition and perhaps a different test set-up with which to measure it. One of the most common errors of definition is equating transition time with switching speed. In most cases the transition time is much shorter than the overall switching speed. **RF**


Acknowledgement

The author would like to thank Microkim Ltd. for their support, and Rami Perry for performing the testing and debugging of the test set-up.

References

1. W. Reed, "Compact Electromagnetic Switches Meet Aerospace Performance Demands", *Microwave System News*, June 1989, pp. 50-56.
2. E. Blair, K. Farrington, K. Tubbs, "Selecting the Right RF Switch", *Microwave Journal*, June 1989, pp. 161-167.
3. J.F. White, *Microwave Semiconductor Engineering*, Van Nostrand Reinhold, 1982, pp. 125-127.
4. "GaAs MMIC Products", Alpha Industries, Inc., Publication no. 50090299 pp. 11.8-11.12, 11.18.
5. "GaAs FET MMIC Control Products", M/A-COM, 1989, pp. 260-261.
6. S.J. Algeri, G.R. Hicks, "Microwave Switch Selection Techniques", *RF and Microwave Components Designers Handbook*, Watkins-Johnson Co., 1990-1991, pp. 784-790.
7. "Fast Switching PIN Diodes", Hewlett Packard, Inc., Application Note 929.
8. "RF & Microwave Signal Processing Components", Anzac-RHG, Adams-Russell Electronics Co., Inc., Publication 1-87-28M, pp. 88-92.
9. F. Lefrak, "Gauge Component Parameters with Simple Test Setups", *Microwaves & RF*, February 1992, pp. 99-110.
10. R.S. Hughes, "RF Detector Logarithmic Video Amplifier", *Microwave Journal*, August 1989, pp. 137-148.
11. D. Johnson, E. Gertel, R. Kopski, M. Kumar, "Consider Options When Selecting Log Amplifiers", *Microwaves & RF*, March 1990, pp. 107-114.

About the Author

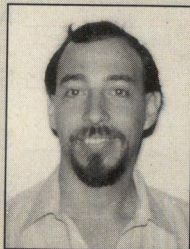


Ra'anán Sover received his BSEE degree from the Technion in Haifa, Israel in 1988. He is a project manager at Microkim Ltd. where he has

been employed for five years. He specializes in microwave control devices. His interests also include RF and microwave antennas and electrooptics. He is also a member of the IEEE. He can be reached at Microkim Ltd., P.O. Box 1797, Haifa, Israel or by phone at 972-4-551211 or FAX at 972-4-551218.

SOLID STATE RF MATRICES.

WE GO TOGETHER.

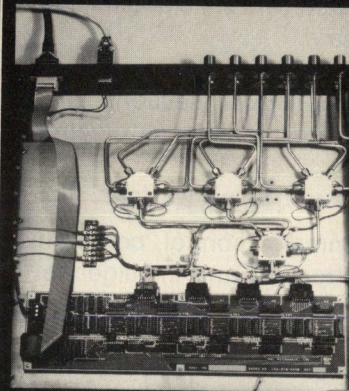

Specifications:

- 1 X 12 switch configuration
- Insertion Loss : 7dB
- Frequency range: 3.6 to 12.8GHz
- Isolation: >60dB
- VSWR: <2.0:1
- 3.5" rack mounted system

Optional Model 115 Controller

- 1.75" rack mounted system
- Front panel manual control
- IEEE-488 or RS232 interface
- 110/220 VAC supply

GET THE SOLID CHOICE



408 Coles Circle
Salisbury MD 21801
Phone: 410-749-1144
FAX: 410-749-4592

INTRODUCING . . .

1992 Edition


THE INTERNATIONAL DEFENSE ELECTRONICS SYSTEMS HANDBOOK

(incorporating The International Countermeasures Handbook)

The First Edition of the International Defense Electronics Systems Handbook (IDESH) is a concise, yet comprehensive guide to the electronics systems deployed worldwide in the full-spectrum of applications — from submarine to satellite-based systems. Split into twelve system-specific sections, the Handbook also includes a Foreword by renowned authority, Dr. Robert Costello, on the current state and the possible future of the defense electronics industry.

The individual sections of the Handbook cover the following categories of defense electronic systems:

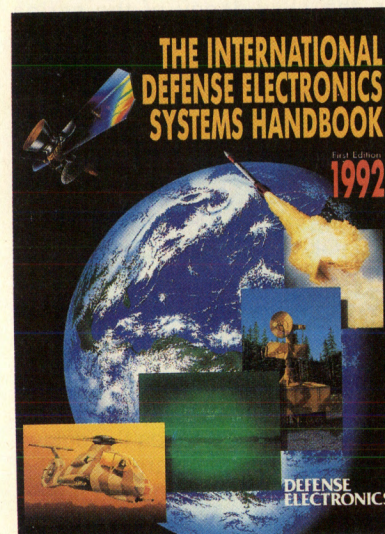- antisubmarine warfare
- command control, communications, computers and intelligence
- imagine and night vision
- navigation and identification
- radar/sonar
- simulation/training
- unmanned vehicles
- space-based systems
- field/flight line test equipment
- computers and peripherals
- electronic warfare



THE INTERNATIONAL DEFENSE ELECTRONICS SYSTEMS HANDBOOK — 1992

YES! Please send me _____ copies of the IDESH 1992 edition at \$195 each.

Bill my company (PO enclosed) _____ Number of Copies
 Payment enclosed _____ \$ 3.00 ea. U.S. postage)
 Charge my: MC Visa AE _____ \$18.00 ea. Int'l Air Mail
Card No. _____ EXP _____ \$ _____ Total Enclosed
Signature _____

Name: _____
Title: _____ Phone: _____
Address: _____
City: _____ State: _____ Zip: _____
Country: _____

The Design of Constant Phase Difference Networks

By Robert J. Dehoney
Consultant

This article presents a unified method for calculating the pole frequencies and element values for a variety of constant phase difference network configurations. The accompanying BASIC program, PHASEDIF, implements the equations.

Phase difference networks are linear circuits with one input and two outputs. With a constant input amplitude, the two output amplitudes are constant with frequency, but their phases shift in such a way as to keep their phase difference constant over some bandwidth. When the phase difference is 90 degrees, the circuits are useful for single sideband generation, antenna pattern and polarization control, signal processing, FSK systems, CRT display generators, and solid state power module combining. With 60 or 120 degree shift, three-phase power amplifier combining is possible. This allows cancellation of odd order harmonics as push-pull does for even order harmonics.

The design of constant phase difference networks has been the subject of many papers and articles since Darlington's classic work in 1950 (1). In spite of this wealth of information, the practicing engineer still cannot find a simple straightforward method of designing phase difference networks of any bandwidth, any number of poles, even or odd, and any phase difference. In addition, there is no unified method of calculating the element values for the various possible all-pass circuits. This article starts to fill this need. It is based on the work of Darlington, Beaugard (2), and Lloyd (3).

In contrast to some other papers, no attempt is made here to summarize the theory; it is well covered in the literature and is too complicated to be easily described. The interested reader can consult the references included at the end of this article.

The basic configuration consists of two all-pass networks, driven in parallel, which shift the phase by different amounts. The difference in the phases

of the two networks remains constant within some prescribed error over the design bandwidth.

Required is knowledge of the highest and lowest frequencies between which the phase difference is to be controlled. Given these frequency limits and the desired phase difference, a table of phase error vs. number of poles, N, can be calculated, enabling the engineer to decide on the configuration. With N known, the pole frequencies can be calculated, and after the network types are chosen, the circuit component values can be determined.

The formulas used in PHASEDIF are presented here in algebraic form. We proceed as follows:

- Enter the lowest frequency f_l and the highest frequency f_h .
- Calculate r and f_0 .

$$r = \frac{f_l}{f_h} \quad (1)$$

$$f_0 = \sqrt{f_l f_h} \quad (2)$$

- Using the iterative procedure from Lloyd's program, calculate y , then q .

$$y(j) = \frac{r^2}{j} \left(j - \frac{5}{4} \right) (1 + y(j+1)) \quad (3)$$

$j = 12, 11, \dots, 1$

$$h = -\frac{y(1)}{4 + 2y(1)} \quad (4)$$

If $h > 10^{-6}$ then $q1 = h + 2h^5 + 15h^9 + 150h^{13}$ (5)

If $h < 10^{-6}$ then $q1 = h$ (6)

$$q = \exp \left(\frac{\pi^2}{\ln(q1)} \right) \quad (7)$$

- Enter the desired phase difference d , degrees.
- Convert d to radians.
- Calculate phase error vs. number of poles.

$$e = 4q^n \sin(d) \text{ for } n = 1, 2, \dots, P \quad (8)$$

(d in radians)

PHASEDIF.BAS limits P to 20 by a DIM statement in line 10.

- Display e in degrees vs. n for errors greater than, say, 0.1 degrees.
- If the networks are to be used for sideband canceling, calculate sideband suppression = $20 \log\{\tan(e/2)\}$, dB.
- Enter number of poles needed, N
- Find normalized pole frequencies $p(k)$ from $p(1)$ to $p(N)$.

If N is even, then

$$x = \frac{(k-1)\pi - \frac{d}{2}}{N} \quad (9)$$

If N is odd, then

$$x = \frac{(k-1)\pi - \frac{\pi-d}{2}}{N} \quad (10)$$

$$p1(k) = \cos x + q^2 \cos 3x + \dots + q^{(m^2-m)} \cos((2m-1)x) \quad (11)$$

$$p2(k) = \sin x - q^2 \sin 3x + \dots + (-1)^m q^{(m^2-m)} \sin((2m-1)x) \quad (12)$$

Finally, $p(k) = \frac{p1(k)}{p2(k)}$ (13)

- To get actual pole frequencies, de-normalize.

$$p1 = p(1)f_0 \quad (14)$$

$$p2 = p(2)f_0, \text{ etc.} \quad (15)$$

When all the pole frequencies have been obtained, it will be seen that some are negative and the rest are positive. If N is even, there will be N/2 of each. The positive poles pertain to the A network and the negative poles to the B network.

Performance

At this point, the performance of the system can be calculated. Each pole contributes a phase shift, thus the total phase difference is simply the sum of all the individual shifts.

$$\frac{A}{2} = \tan^{-1}\left(\frac{f}{p_1}\right) + \tan^{-1}\left(\frac{f}{p_2}\right) + \dots + \tan^{-1}\left(\frac{f}{p_N}\right) \quad (16)$$

If this calculation is made, it will be seen that, from f_1 to f_n , the phase difference will be as chosen with equal positive and negative error, e.

Circuit Values

Circuit files and schematics are provided in file "PHASEDIF.BAS"; the schematics are seen in Figure 1. The simplest implementation is to provide as many single pole circuits as there are poles. We will consider balanced and unbalanced RC and LC circuits and active RC circuits. In what follows, ω_k represents $2\pi p_k$, a pole frequency in radians with the sign ignored.

RC Lattice — For design, choose either R or C and either R1 or R2.

$$RC = \frac{1}{\omega_k} \quad (17a)$$

$$R1 \cdot R2 = R^2 \quad (17b)$$

Isolation is required between stages since the input impedance is not

constant.

$$\frac{E_{out}}{E_{in}} = \frac{1}{\left(\frac{R}{R^2 + 1}\right)^2} \quad (17c)$$

$$\text{Phase Shift} = -2 \tan^{-1}(\omega RC) \quad (17d)$$

LC Lattice — Choose R. Then,

$$C = \frac{1}{R\omega_k}, \quad L = \frac{R}{\omega_k} \quad (18a,b)$$

Isolation is not required between stages since the input impedance is constant and equal to R.

$$\text{Phase Shift} = -2 \tan^{-1}(\omega RC) \quad (18c)$$

LC Tee — Choose R. Then,

$$C = \frac{2}{R\omega_k}, \quad L = \frac{R}{2\omega_k} \quad (19a,b)$$

$$M = L \text{ (very tight coupling)} \quad (19c)$$

This is a difficult circuit to realize, because of the unavoidable stray capacitance between primary and secondary of the transformer and the high degree of coupling that is required.

$$\text{Phase Shift} = -2 \tan^{-1}(\omega\sqrt{LC}) \quad (19d)$$

Active RC — For design, choose either R or C

$$RC = \frac{1}{\omega_k} \quad (20a)$$

$$\text{Phase Shift} = -2 \tan^{-1}(\omega RC) \quad (20b)$$

Two Pole Circuits

These circuits generate a phase shift equivalent to two single pole circuits in tandem. Designed with the same pole frequencies, they will produce the same phase shift vs. frequency. We will consider RC active and LC passive types. Information on RC passive multipole networks can be found in References 4-6.

For these circuits, the two pole frequencies are p_j and p_k or in radians, ω_j and ω_k . Then:

$$\omega_0 = \sqrt{\omega_j \omega_k} \quad (21)$$

$$S = \frac{(\omega_j + \omega_k)}{\omega_0} \quad (22)$$

$$x = \frac{\omega}{\omega_0} \quad (23)$$

$$\text{Phase Shift} = -2 \tan^{-1}\left(\frac{Sx}{1-x^2}\right) \quad (24)$$

Wien Bridge Active All Pass Type 1 and Type 2 — These circuits have been extensively analyzed, but usually with restrictions on the relations between $R1C1$ and $R2C2$ or $R1C2$ and $R2C1$. See References 7-9. Here, we relax the restrictions and allow the designer to select $C1$ and $C2$. Since 1 percent resistors are cheaper and more common than 1 percent capacitors, this seems like a sensible scheme. As a result, the design equations are as follows:

Choose $C1$ and $C2$. Two sets of values for $R1$, $R2$ and M will result:

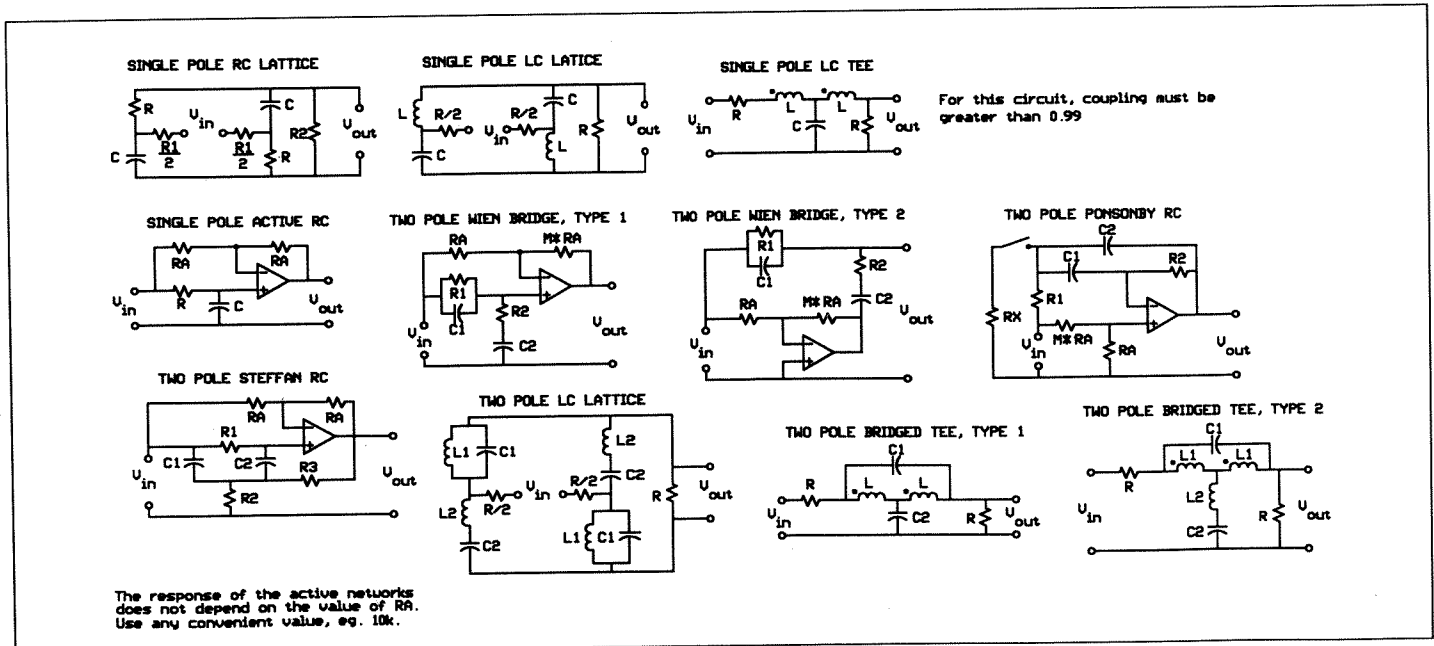


Figure 1. Constant phase difference networks.

$$R1 = \frac{S + \sqrt{S^2 - 4(C1 + C2)}}{2\omega_0(C1 + C2)} \quad (25a)$$

$$R2 = (\omega_0^2 \cdot C1 \cdot C2 \cdot R1)^{-1} \quad (25b)$$

$$M = \frac{2S - \omega_0 R1 \cdot C2}{\omega_0 R1 \cdot C2} \quad (25c)$$

and

$$R1 = \frac{S - \sqrt{S^2 - 4(C1 + C2)}}{2\omega_0(C1 + C2)} \quad (25d)$$

$$R2 = (\omega_0^2 \cdot C1 \cdot C2 \cdot R1)^{-1} \quad (25e)$$

$$M = \frac{2S - \omega_0 R1 \cdot C2}{\omega_0 R1 \cdot C2} \quad (25f)$$

Obviously, not all values of C1 and C2 will provide real values of R1, but the calculation is so trivial on a programmable calculator or computer that satisfactory values can quickly be found.

Ponsonby Active RC All Pass — This two pole circuit has the interesting feature that the phase shift can be disabled by switching in a resistor. See References 10 and 11. As with the Wien Bridge types, the circuit values can be derived in a number of ways, depending on the initial assumptions, but as before, we will assume values for C1 and C2. First, calculate K,

$$K = \frac{C2 + C1}{C2 \cdot S} \quad (26a)$$

Then,

$$R1 = (C2 \cdot \omega_0 K)^{-1} \quad (26b)$$

$$R2 = (\omega_0^2 \cdot C1 \cdot C2 \cdot R1)^{-1} \quad (26c)$$

$$M = \frac{2S}{K}, \quad Rx = \frac{R1}{M} \quad (26d,e)$$

This circuit does not have unity gain, as do the others. Its gain magnitude is:

$$G = \frac{1}{1 + M} \quad (26f)$$

As the C1/C2 ratio increases, the gain approaches unity.

Steffan Two Pole RC — Enter C1 and C2

$$CP = \frac{C1 \cdot C2}{(C1 + C2)} \quad (27a)$$

$$R1 = \frac{S + \sqrt{S^2 + 4C2}}{2C2\omega_0} \quad (27b)$$

$$RP = (\omega_0^2 \cdot R1 \cdot C1 \cdot C2)^{-1} \quad (27c)$$

$$K = \frac{RP \cdot C1}{R1 \cdot CP} \quad (27d)$$

$$R2 = (S\omega_0 C1)^{-1}, \quad R3 = \frac{RP}{K} \quad (27e,f)$$

LC Two Pole Lattice — Choose R. Then:

$$C1 = (R\omega_0 S)^{-1}, \quad L1 = \frac{SR}{\omega_0} \quad (28a,b)$$

$$L2 = \frac{R}{\omega_0 S}, \quad C2 = \frac{S}{\omega_0 R} \quad (28c,d)$$

As with the single pole lattice, the input impedance is R, so isolation is not required between stages.

Bridged Tee, Type 1 — First, solve for K, the coefficient of coupling:

$$K = \frac{S^2 - 1}{S^2 + 1} \quad (29a)$$

Choose R. Then:

$$L1 = \frac{S \cdot R}{\omega_0(1 + K)} \quad (29b)$$

$$C1 = (2\omega_0 RS)^{-1}, \quad C2 = \frac{2S}{\omega_0 R} \quad (29c,d)$$

This circuit is seldom used since it requires a specific coefficient of coupling K. The next circuit helps this problem.

Bridged Tee, Type 2 — Solve for K_{min} :

$$K_{min} = \frac{S^2 - 1}{S^2 + 1} \quad (30a)$$

Choose a value of K ($>K_{min}$) appropriate to the transformer construction technique. Choose R. Then:

$$L1 = \frac{S \cdot R}{\omega_0(1 + K)} \quad (30b)$$

$$L2 = \frac{R}{2\omega_0 S} - L1 \cdot \frac{1 - K}{2} \quad (30c)$$

$$C1 = (2R\omega_0 S)^{-1}, \quad C2 = \frac{2S}{\omega_0 R} \quad (30d,e)$$

Adjust L2 to compensate for errors coupling.

This article has presented, in one place, the equations used in the design of several types of constant phase difference networks. While specific operating instructions for PHASEDIF were not given here, the program follows the design procedure outlined in this article.

PHASEDIF is available on disk from the RF Design Software Service. Please see page 10 for ordering information. RF

References

1. S. Darlington, "Realization of a Constant Phase Difference," *Bell System Technical Journal*, January 1950, pp. 94-104.
2. W.G. Beauregard, "Phase Difference Networks," *1991 RF Design Directory*, pp. 89-92.
3. Allan G. Lloyd, "90 Degree Phase-Difference Networks," *Electronic Design*, September 13, 1976, pp. 90-94.
4. W.J. Albersheimand, F.R. Shirley, "Computation Methods for Broad-Band 90 Deg Phase-Difference Networks," *IEEE Trans. Circuit Theory*, May 1969, pp. 189-196.
5. P. Allemandou, "RC All-Pass," *Proc IEEE*, October 1967, pp. 1752-1753.
6. S.C. Dutta Roy, "R-C Active All-Pass Networks using a Differential-Input Operational Amplifier," *Proc IEEE*, November 1969, pp. 2055-2056.
7. R. Genin, "Realization of an All-Pass Transfer Function Using Operational Amplifiers," *Proc IEEE*, October 1968, pp. 1746-1747.
8. U.S. Ganguly, "An Inductorless All-Pass Phase Shifter," *Proc IEEE*, October 1966, pp. 1462-1463.
9. R. Khera, "Another Realization of an All-Pass Transfer Function Using an Operational Amplifier," *Proc IEEE*, July 1969, pp. 1337-1338.
10. D.H. Schoonaert and J. Kretschmar, "Realization of Operational Amplifier All-Pass Networks," *Proc IEEE*, June 1970, pp. 953-955.
11. J.E.B. Ponsonby, "Active All-Pass Filter Using a Differential Operational Amplifier," *Electron. Letters*, April 1966, pp. 134-135.
12. C.R. Hoffman, "Develop Your Own Delay-Distortion Equalizer," *EDN*, April 5, 1977, pp. 74-77.
13. Allan G. Lloyd, "Allpass Networks," *RF Design*, April 1989, pp. 47-53.
14. Thomas A. Keely, "Design of Constant Phase Difference Networks," *RF Design*, April 1989.

About the Author



Robert Dehoney received his BSEE from MIT in 1950. After graduation, he worked for the Allen B. DuMont Labs designing RF equipment for UHF TV. He retired from Fairchild Weston in 1987 as a Technical Director in ECM. He is now a private consultant. He can be reached at 4602 Palm Blvd., Isle of Palms, SC, 29451, or by phone at (803) 886-5785.

A Logic-Compatible Mixer

By Thomas P. Hack
Comlinear Corp.

RF circuit designers increasingly must drive analog mixers and modulators with inherently digital signals. Digital circuits form the bulk of frequency division and fractional-N circuitry in frequency synthesizers. BPSK and QPSK modulators (by definition) work with digital signals. Direct-sequence spread-spectrum systems use digitally-produced spreading codes. In all of these examples the signal that eventually makes it to the mixer or modulator starts with conventional logic levels. A mixer/modulator that works with existing logic levels (TTL, ECL, ect.) could simplify all of these designs. A unique circuit based on a high frequency multiplexer will be described which does just that.

Besides working with TTL and ECL signals, the circuit has a number of other advantages. It is small in size and uses only eight parts. It can provide lower conversion loss (with proper transformer selection) than passive approaches. All ports are well isolated from one another. DC to VHF operation is possible on all three ports by adding one high frequency op amp and two resistors to the basic design.

Circuit Operation

Although this circuit actually uses a high-speed two-input multiplexer, operation is conceptually the same as a conventional passive double-balanced mixer. With the proper local oscillator applied (large enough to provide good diode switching action) a positive LO signal makes D2 and D4 conduct, connecting the lower half of T2's secondary (Figure 1a). D1 and D3 are reverse biased. The RF signal is coupled to the IF port with an in-phase relationship to the RF port. A negative LO excursion makes D1 and D3 conduct (D2 and D4 are off) and an out-of-phase RF signal shows up at the IF port (Figure 1b).

Compare this with an active mixer based on a multiplexer (Figure 1c). T1 acts as a phase splitter and the LO port once again determines whether the RF signal is routed to the IF port in an in-phase or out-of-phase relationship. The multiplexer replaces the diodes in routing the RF signal to the IF port.

Although conceptually the same, the

circuit differences between the two approaches make for a number of interesting performance differences. The active approach has good isolation. LO to RF isolation is good since the inputs of the multiplexer are buffered. LO to IF isolation is also very good in the active approach because only one transformer and the multiplexer determine mixer balance. The multiplexer has high channel-to-channel matching (because in part it is a monolithic device and the two signal paths are laid out for high channel-to-channel matching). Compare this with a passive mixer which must match four diodes and have two well balanced transformers in order to get reasonable isolation.

When it comes to distortion the active mixer is extremely good at low frequencies, but the passive approach is better at high frequencies. The active mixer's distortion performance is less affected by improper IF port terminations (such as those caused by IF filters).

A Complete Circuit

Figure 2 is the complete schematic for the mixer. T1, a 1:4 impedance ratio transformer delivers anti-phase voltages to input A (pin 2) and input B (pin 4) of multiplexer U1. With select (pin 7) high, channel A is routed to the output (pin 11) of the multiplexer. With select low, channel B is routed to the output. C2 and C3 provide active circuit compensation. C1 and C4 are power supply bypasses. R1 in conjunction with T1 sets the RF port input impedance. R2 sets the output impedance. Pin 7 is a logic-compatible LO port. The circuit as shown (with pin 6 open) works with ECL logic levels. Connecting pin 6 to Vcc makes pin 7 TTL compatible.

Mixer Test Results

Figure 3 shows the block diagram of the test setup used in evaluating the performance in a low frequency mixer application. An HP 3326A synthesizer provides an 8 MHz RF signal and a HP 8662A synthesizer provides a 29.45 MHz LO signal. Low pass filters are used after each synthesizer to remove harmonics which might otherwise corrupt the measurement. In addition, a squaring circuit based on an MC10114

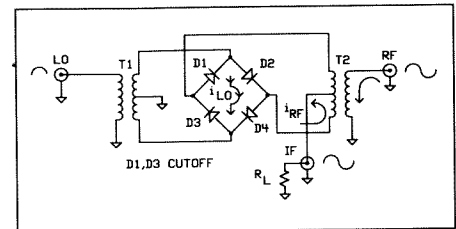


Figure 1a. Passive double-balanced mixer, positive-going LO.

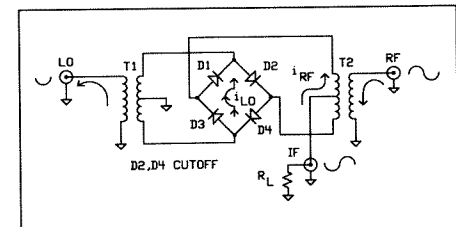


Figure 1b. Passive double balanced mixer, negative going LO.

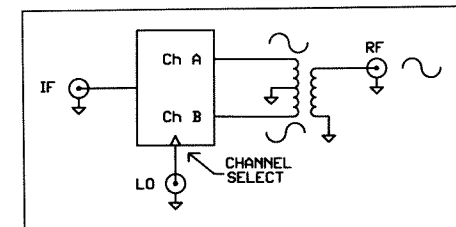


Figure 1c. Active double-balanced mixer.

is used to convert the LO to ECL logic levels. At this point you might be asking "Why filter the LO signal when it is only going to be squared up?" The answer is that the LO filter's primary purpose is to remove even order harmonics. The squaring circuit will not generate significant even-order terms if set up properly.

With the signals fed to the mixer, the mixer not only produces the desired IF (which in this case is at approximately 21.45 MHz) but undesired signals due to feedthrough, higher-order mixing, and so on. A HP 3588A spectrum analyzer measures all of these products (up to 150 MHz).

The frequency references for the synthesizers and the spectrum analyzer are locked together eliminating any relative frequency errors between them. This means that we can precisely predict

TOUGH ALL-WELDED MIXERS



SURFACE-MOUNT or PLUG-IN FROM **\$395** (10 qty)


Expose Mini-Circuits' TUF-mixers to 250°C for five minutes, or to the extreme shock and vibration stresses of MIL-STD-28837, or to 200 cycles of thermal shock from -55° to +100°C... they'll survive without any change in specs. They are mighty tough mixers!

Available with LO drive levels from +7 to +17dBm, performance features include very low conversion loss flat over the entire band, high isolation (L-R, L-I), and well-matched VSWR at all ports.

All-welded internal and external construction is used to assemble and package the TUF-unit in its tiny 0.5 by 0.2 by 0.25 in. metal case, for plug-in or surface-mount* assembly.

TUF-Ultra-Rel™ mixers are guaranteed for five years and boast unprecedented "skinny" sigma (δ) unit-to-unit repeatability as shown in the Table.

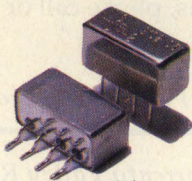Tough, tiny, and with tight repeatability... Mini-Circuits' Ultra-Rel™ TUF-mixers with a five-year guarantee, priced from \$3.95... available only from Mini-Circuits.



actual size

ULTRA-REL™ MIXERS

5-YR. GUARANTEE

with extra long life due to unique HP monolithic diode construction, 300°C high temp. storage, 1000 cycles thermal shock, vibration, acceleration, and mechanical shock exceeding MIL requirements.

finding new ways...
setting higher standards

SPECIFICATIONS

Model	LO Power (dBm)	Freq. LO/RF (MHz)	Conv. Loss (dB)		Isol. L-R (dB)	Price, \$ Ea.
			\bar{X}	δ		
TUF-3	7	0.15-400	4.98	0.34	46	5.95
TUF-3LH	10		4.8	0.37	51	7.95
TUF-3MH	13		5.0	0.33	46	8.95
TUF-3H	17		5.0	0.33	50	10.95
TUF-1	7	2-600	5.82	0.19	42	3.95
TUF-1LH	10		6.0	0.17	50	5.95
TUF-1MH	13		6.3	0.12	50	6.95
TUF-1H	17		5.9	0.18	50	8.95
TUF-2	7	50-1000	5.73	0.30	47	4.95
TUF-2LH	10		5.2	0.3	44	6.95
TUF-2MH	13		6.0	0.25	47	7.95
TUF-2H	17		6.2	0.22	47	9.95
TUF-5	7	20-1500	6.58	0.40	42	8.95
TUF-5LH	10		6.9	0.27	42	10.95
TUF-5MH	13		7.0	0.25	41	11.95
TUF-5H	17		7.5	0.17	50	13.95
TUF-860	7	860-1050	6.2	0.37	35	8.95
TUF-860LH	10		6.3	0.27	35	10.95
TUF-860MH	13		6.8	0.32	35	11.95
TUF-860H	17		6.8	0.31	38	13.95
TUF-11A	7	1400-1900	6.83	0.30	33	14.95
TUF-11ALH	10		7.0	0.20	36	16.95
TUF-11AMH	13		7.4	0.20	33	17.95
TUF-11AH	17		7.3	0.28	35	19.95

*To specify surface-mount models, add SM after P/N shown.

■ \bar{X} = Average conversion loss at upper end of midband ($f_u/2$)
 δ = Sigma or standard deviation

Mini-Circuits™

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661
WE ACCEPT AMERICAN EXPRESS AND VISA


Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.

INFO/CARD 38

F 145 REV. F

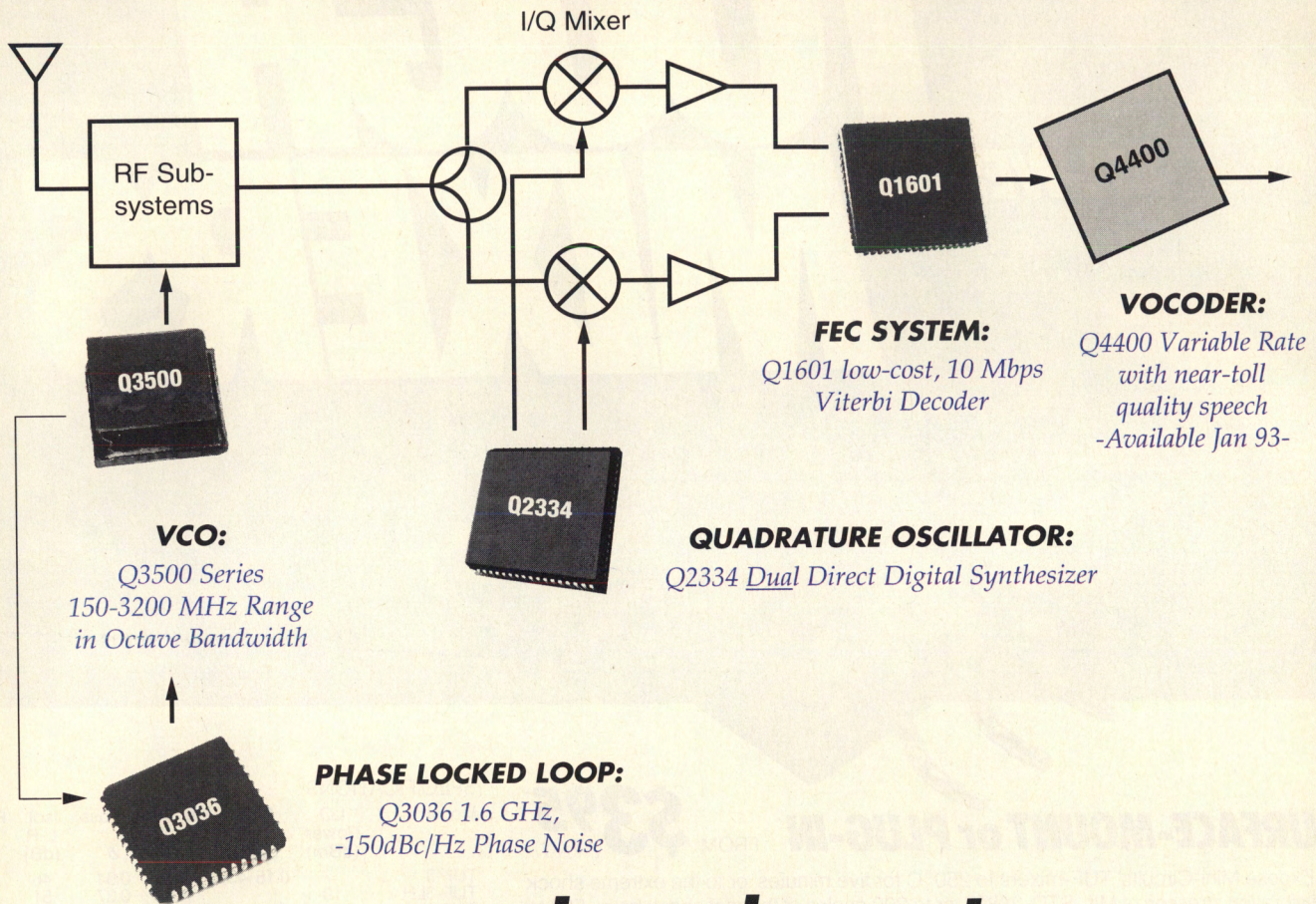You Know What Your Wireless Communication System Needs to Succeed...



...and so do we!

Today's *wireless* communication systems require high performance, low power, small size, quick time-to-market, and affordable pricing.

QUALCOMM answers your tough needs with complete VLSI sub-systems on a single chip.

With QUALCOMM, your communications design can take advantage of the world's most advanced VLSI devices including: Viterbi and Trellis Codec Systems, Variable Rate Vocoder, Voltage Controlled Oscillators (VCO), Phase-Locked Loop (PLL) and Direct Digital (DDS) frequency synthesizers.

And, you can expect complete applications engineering and system-level support from the engineers behind the **QUALITY COMM**unications name.

To learn how your design can succeed with QUALCOMM's VLSI solutions, please call or FAX:

QUALCOMM
VLSI Products Division

10555 Sorrento Valley Road
San Diego, CA 92121 USA
TEL# 619-597-5005
FAX# 619-452-9096

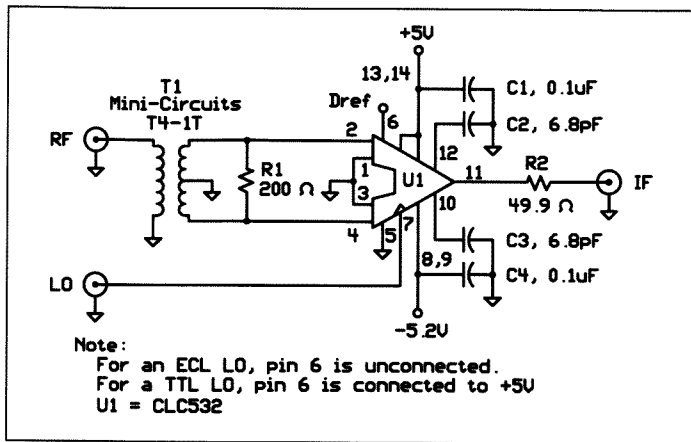


Figure 2. The logic compatible active double-balanced mixer.

**Mixer harmonic intermodulation
(in dBc to desired IF)**

RF order	0	1	2	3	4
0	—	-48.3	-36.8	-61.8	-35.3
1	-45.7	0.0	-42.3	-9.2	-39.0
2	-52.6	-49.5	-50.4	-48.5	-48.2
3	-62.4	-39.5	-59.9	-39.4	-58.1
4	-63.5	-64.8	-61.8	-64.4	-61.2

Harmonic LO order

LO = 29.45 MHz, 4dBm
RF = 8.00 MHz, -4dBm

Figure 4. Mixer test results

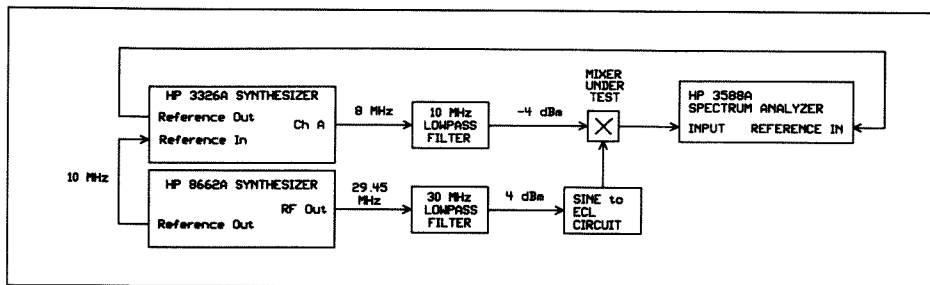


Figure 3. Mixer test block diagram

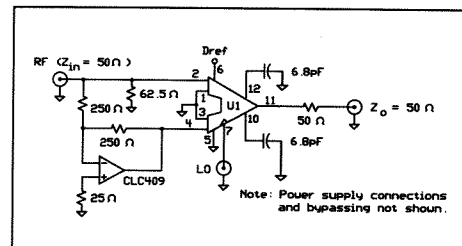


Figure 5. A fully DC-coupled mixer.

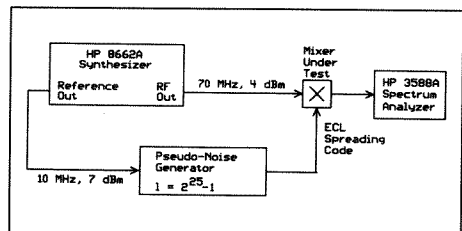


Figure 6. BPSK and direct-sequence spread-spectrum test circuit.

where any given mixer product will show up on the spectrum analyzer. The spectrum analyzer can use a zero frequency span setting and still provide accurate measurements. Zero frequency span was used producing very fast sweeps. A 10 sweep video average was used to reduce measurement uncertainty.

The results are given in Figure 4. At these frequencies the mixer is roughly comparable to a standard, type-1 (+7 dBm LO), passive double-balanced mixer. At lower frequencies it does even better. With a 1:4 impedance ratio transformer for T1, single sideband conversion loss is approximately -9 dB. Substituting a 1:16 transformer should drop the conversion loss to approximately -3 dB.

A DC-Coupled Mixer

We have seen that this part makes a reasonable low-frequency mixer. Higher-order mixer products are reasonable and the LO and IF ports are DC coupled. The RF port can be DC coupled by removing the transformer and substituting an active phase splitter (Figure 5). Now all ports are DC coupled — something not found in most mixers. This might be useful in products such as low frequency spectrum analyzers.

Modulators

Probably the best application of this circuit is in BPSK, QPSK, and direct

sequence spread spectrum modulators. To test the circuit, a 10 Mchips/sec (suitable for the 915 MHz ISM band) linear maximal PN spreading code was applied to the LO port and a 70 MHz pure tone was applied to the RF port of the circuit, (Figure 6). A long spreading code ($2^{25}-1$) was used so that the spreading code itself did not degrade the observed carrier suppression (The frequency of occurrence of ones and zeros in a linear maximal sequence is slightly imbalanced but gets better as the sequence length is increased.) ECLinPS logic was used to generate the PN signal (Figure 7) because this logic family has excellent edge rates (giving the best possible code balance). For most consistent performance, the ECL device that drives the modulator and the modulator should share the same -5.2 V supply.

Carrier balance is very good in this application (no visible spike at the center frequency, Figure 8). The results shown are without any adjustments. Code balance is imperfect (spikes are visible in the nulls in the spectrum) but can be improved with tweaking.

Phase Detector Tests

In addition to modulator and mixer applications, this circuit also can be used as a phase detector. To test the circuit in phase detector applications, two squarewaves, one at 1 MHz and another at 1.0001 MHz were applied to

the circuit (Figure 9). The phase detector produces an output proportional to the difference in instantaneous phase between the two signals (the difference product) as well as a "sum" product which is filtered before the mixer output is sent to a digitizing oscilloscope. The difference frequency is 100 Hz so the instantaneous phase between the two input signals slips 2π radians every 10 milliseconds. With a two volt p-p RF input signal, the phase detector output amplitude is 0.8 Vpp with a double terminated output (Figure 10). This corresponds to a phase detector constant of 0.25 V/radian. Phase detector linearity is very high with no obvious flat spots or other problem areas.


Summary

A digitally compatible mixer has been described with a number of desirable attributes:

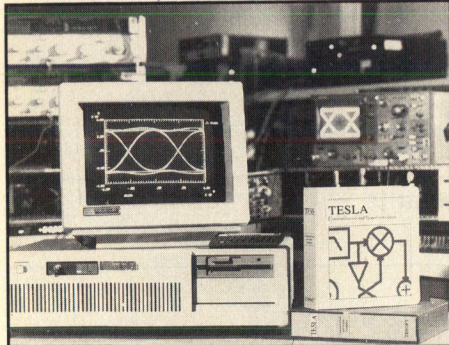
- 1) The LO port is ECL and TTL compati-

Easy TESLA Block Diagram Simulation Runs on Your PC

- Nonlinear time simulation with built-in spectrum analysis lets you test with noise, multipath and adjacent channels
- Use TESLA to simulate modems, radios, cellular, GPS, spread spec, DSP, HDTV, radar, controls, audio & more!
- Over 60 analog & digital blocks: Filters, VCO, Mixer, RFamp, Laplace, A/D & D/A Converters, BER tester, Noise, S&H, Integ&dump, 5-Function Generator, Phase meter, & more!
- Add new blocks with MODGEN option—BBS user library
- Use OrCAD® to input block diagrams—runs under TESLA



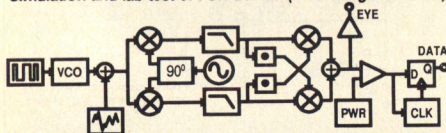Simulation and lab test of FSK demod (block diagram below)




FREE APPLICATION NOTE

TESOFT Inc, PO Box 305
Roswell GA 30077
Phone 404-751-9785
FAX 404-664-5817

CALL FOR WORKING DEMO DISK
TESLA Simulator \$695
MODGEN Model Generator \$495
Symbols for OrCAD/SDT® \$195

INFO/CARD 45

U.S. MADE

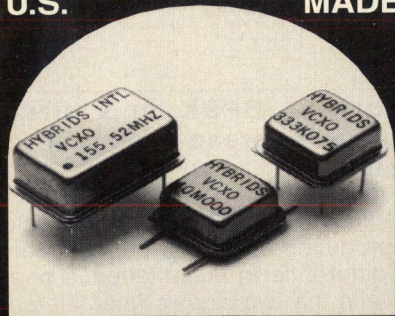

VCXO's CRYSTAL CLOCK OSCILLATORS

CMOS, ECL, TTL
FREQUENCY RANGE
TO 300 MHz

OPTIONS:

- Pullability
- Control Voltage
- Linearity
- Accuracy and Temp. Stability
- S.M.D. and Other Packages

HYBRIDS
INTERNATIONAL, LTD.

311 N. LINDENWOOD DRIVE/OLATHE, KS 66062
PHONE: (913) 764-6400 • FAX (913) 764-6409

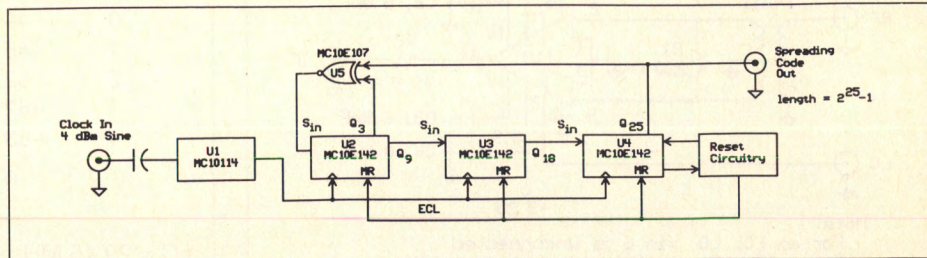


Figure 7. Pseudo noise generator, simplified diagram.

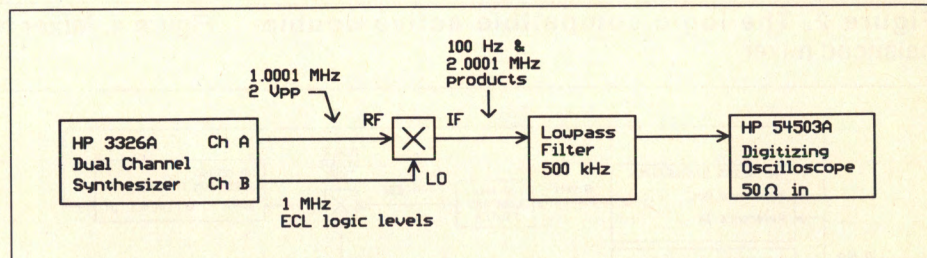


Figure 9. Phase detector test circuit.

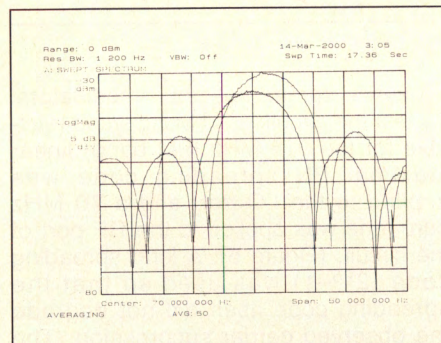


Figure 8. A 70 MHz carrier with 10 Mch/sec pseudo noise modulation. An offset trace is also shown to display null spikes.

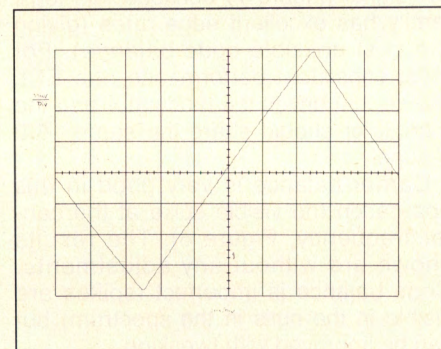


Figure 10. Phase detector output.

ble making it suitable for digital modulators, phase detectors, and spread spectrum applications.

2) All three ports can be DC coupled. This may be useful in low frequency

spectrum analyzers.

3) It can have lower conversion loss than passive double-balanced approaches.

4) Performance is high at low frequencies.


This circuit provides another alternative in several thorny mixer applications. **RF**

References

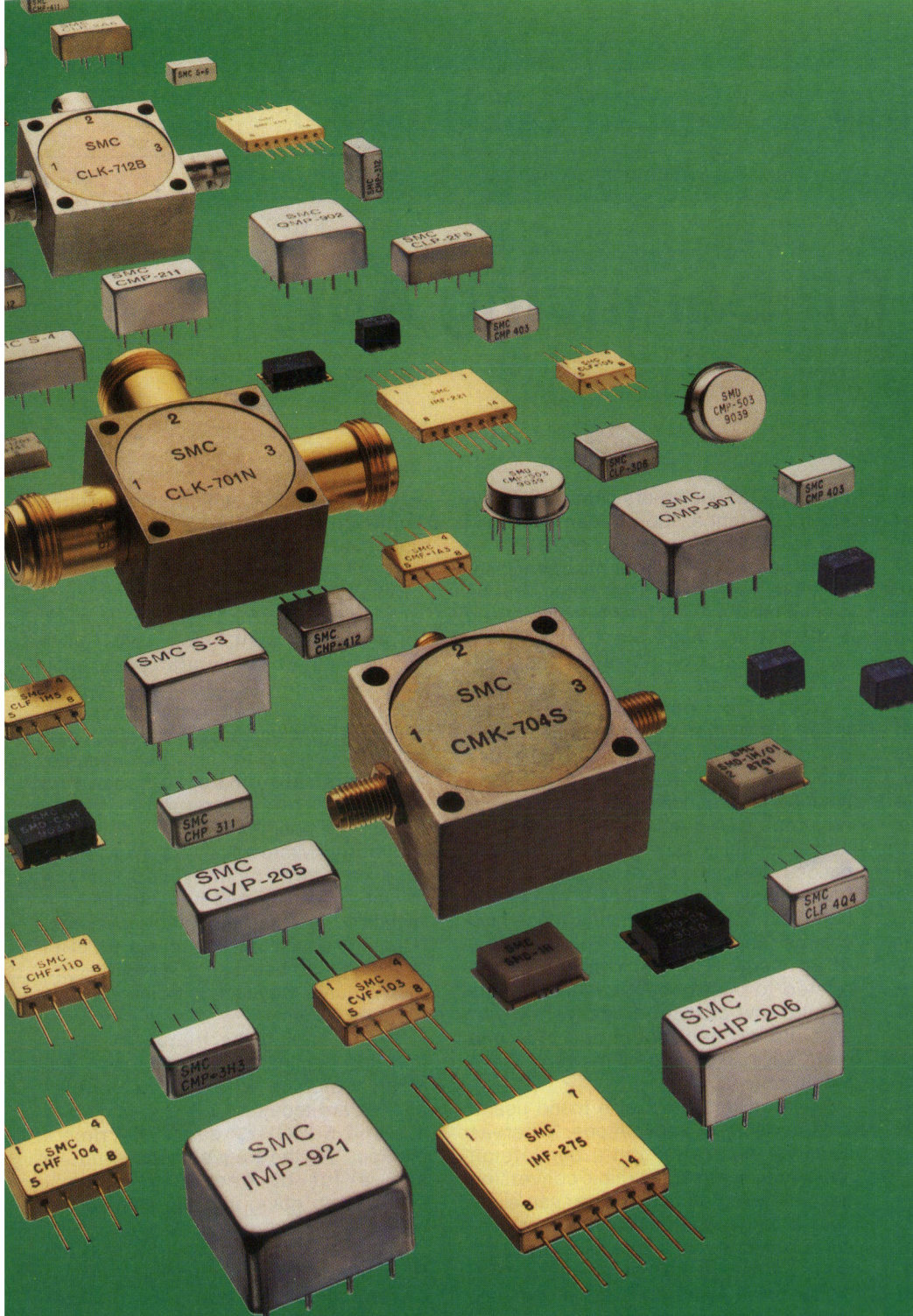1. Dixon, Robert C., *Spread Spectrum Systems*, 2nd. ed., John Wiley & Sons, NY, 1984.
2. *RF/IF Signal Processing Handbook*, Volumes 1 and 2, Mini-Circuits.

About the Author

Until recently, Tom Hack was an applications engineer at Comlinear Corporation. He received his BSEE from Cooper Union, his MSEE from Rensselaer Polytechnic Institute and his MBA from the University of Colorado. Questions regarding the CLC532 should be addressed to Comlinear Corp. at 4800 Wheaton Dr., Ft. Collins, Co. 80525. Other questions should be directed to Mr. Hack at (303)229-0601.



MIXERS

S Synergy offers the largest catalog selection of mixers in the industry ... for commercial and military applications, including double balanced, quadrature IF and Image reject, housed in a variety of package styles ... all very competitively priced. Most models meet or exceed MIL-M-28837 requirements and applicable tests of MIL-STD-202.

Harmonic and starved L.O. drive models are also available.
 The experience of the Synergy Applications Engineering Team is ready to answer technical questions and help with your custom designs.
 For a copy of our new catalog, contact: SYNERGY MICROWAVE CORPORATION, 483 McLean Boulevard, Paterson, NJ 07504. (201) 881-8800. FAX: (201) 881-8361



Mixers: An RF Balancing Act

By Andy Kellett
Technical Editor

It is hard to find a block diagram for an RF communications system that doesn't contain a mixer. Up conversion, down conversion, product detection, IQ modulation, phase locked loops, all these functions are implemented with mixers. As a result, mixer use is expanding with the RF market.

Mostly found at the front end of communications systems, mixers have the difficult task of taking a weak signal and translating it in frequency, an inherently non-linear function. In the process, spurious products must be kept small while the resulting signal is kept out of the noise. It is no wonder that designers look to mixer manufacturers for what might seem to be an easy module to homebrew.

Some of the key specifications for mixers (apart from price, size, reliability and other such generic qualities) are isolation, intercept point (third order and others), conversion gain, LO power and dynamic range. These qualities are all linked; improving one can improve others — and degrade yet others. So what specifications are manufacturers working to improve? The answer depends on the application the mixer will go into.

High signal purity is the most important quality in some systems. For these, mixers with high third order intercept point and high isolation are required. The mixer most commonly used to meet these requirements is the double balanced diode ring mixer. Standard lines of these mixers are available from a number of companies: Synergy Microwave, Tele-Tech, RF Prime, Lorch Vernitron and Mini-Circuits, among others, but very high performance requirements more often lead to custom orders.

"We have a catalog which represents what we are capable of doing, but we make a number of custom mixers for different people. That's how we've been able to grow — by supplying the market with special mixers," says Shankar Joshi, engineering manager for Synergy Microwave Corp. Similarly, Lorch Vernitron offers custom high performance

mixers, "Our customers come to us saying for instance, 'Lorch, can you build me something that instead of 12 dB isolation has 40?'; I tell our mixer engineer to make something 5 dB better and he comes back a week later with something 6 dB better," says Mark McWhorter, Lorch's director of marketing and product development.

While signal performance is still an issue for higher volume applications, power consumption and cost are also important considerations. The much ballyhooed emergence of wireless communications has made battery operation and affordability new goals in communications designs. "Local oscillator power has become more important with all the handheld applications, so for these high volume [applications] LO power is more of an issue. That, of course, is then related to cost because high volumes require low cost, and finally, low cost ties into surface mount and tape and reel," says RF Prime's President, Steve Markoe Sr.

Active mixers have also found use in cost conscious applications. Whereas passive mixers exhibit a conversion loss, active mixers exhibit conversion gain, meaning an active mixer can eliminate a stage of amplification after conversion. However, active mixers pay for their gain with narrower bandwidth, higher noise figure and smaller dynamic range than passives.

Discrete active mixers can be implemented with just a FET, however, according to the President of Tele-Tech Corp., John Duncan, "I don't think there's as big a market for active mixers because the people who use them build them themselves." Active mixers as integrated circuits might be used by a larger market says Gary LaBelle, Product Marketing Manager for Hewlett-Packard Company's Wireless Component Division, "Really, it's the digital cellular and cordless stuff that's pushing active mixers, because they are much more complex. Instead of just having a simple modulator in a system, now you need a

vector modulator, which also requires some phase shifting and maybe an upconversion. The demand is to integrate all this into one package."

What things are mixer manufacturers working on? "I think packaging is going to be the big push," says Tele-Tech's Duncan, "there really aren't any good surface mount packages for mixers." According to Duncan, conventional gull-wing SMT packages have too much parasitic inductance for high performance, and substrate-on-board packaging results in poor production yields because of poor bonding.

Synergy Microwave has also recognized a need for improved surface mount packaging and has introduced a metalized, surface mountable package, "Ordinary plastic packages lack EMI/RFI shielding, and because of a lack of common ground, they lack in isolation," says Synergy's Joshi.

"We're seeing the frequency move from the dominant area which was 900 MHz, which is where your cellular phones are today, to 1.8, 2.4, and up to 4.8 and 5.2 GHz," says RF Prime's Markoe, "As the frequency goes up we see a lot of people in military microwaves going into the commercial sector.

The use of mixers will grow with the RF market. Balancing customer's electrical specifications and price requirements has been and will be the task that mixer manufacturers face. Says Mini-Circuits' President and CEO, Harvey Kaylie, "When I got into the mixer market it was small and it required a much smaller investment than it does today, so it represented a good opportunity, and fortunately we gave the customers what they wanted." Though the mixer market today is large, making mixers that meet customers' individual needs still seems to be the way to succeed. **RF**

For reprints of this report call Cardiff Publishing Company at (303) 220-0600. Ask for the Circulation Department.

Antenna Pattern Distortion

The effect of a tower on an omnidirectional antenna can be calculated with software from SoftWright Limited Liability Co. Using a mathematical model developed by Antenna Specialists Co., SoftWright's Antenna Pattern Module calculates, tabulates and plots antenna patterns for mounted antennas. The module can be run independently or as part of SoftWright's Terrain Analysis Package. **SoftWright Limited Liability Co.**
INFO/CARD #190

Engineering Environment

Innovation First has released Object Engineering, a new approach to producing custom engineering applications in Windows 3.1. The Object Engineering program can be used to produce applications without programming, and the object oriented framework can be extended in C++. Full source code is included. It comes with a conditional 30-day money back guarantee at the introductory price of \$499. **Innovation First**
INFO/CARD #189

Modulation Spectra and BER

A single Microsoft Excel worksheet calculates both the power spectra and bit-error rate (BER) curves for several different types of dig-

ital modulation schemes. Modulations covered are: ASK, FSK, BPSK, QPSK and MSK. BER calculations include BPSK, QPS, non-coherent DPSK and FSK, coherent FSK and non-coherent orthogonal M=4 and M=8 schemes. An Apple Macintosh or IBM with Microsoft Excel 2.X or greater is required. Cost is \$50.

Engineering Solutions
INFO/CARD #188

Class D Simulation

HB-SIM from Design Automation helps engineers to design half-bridge (Class D) power amplifiers or power converters. The program simulates steady-state, periodic, time-domain waveforms 100 to 1000 times faster than SPICE and takes into account the AC and DC parasitic resistances of all components. HB-SIM runs on IBMs and compatibles. North American price is \$495.

Design Automation, Inc.
INFO/CARD #187

MMIC Design

MMIC_plan, from MMIC_CAD, calculates the inductance, capacitance, frequency dependant resistance and microstrip characteristics of any number of signal paths in a MMIC layout. In addition, MMIC_plan also includes a frequency and time domain simulator, and layout editor. MMIC_plan is currently available for

the price of \$1995 plus shipping and handling. **MMIC_CAD, Inc.**
INFO/CARD #186

Radio Modem Operating System

Monior Electronics announces a new operating system for use in radio modem networks. TurboLink 2.0 is a highly optimized implementation of the CCITT X.3 protocol as it applies to radio LANs. TurboLink 2.0 has idle times of 10 ms per keystroke, is interrupt driven, supports multi-drop operation and includes a number of new commands. Price is \$40 per radio transceiver in the field, plus a labor charge for upgrades performed by the factory. **Monior Electronic Corp.**
INFO/CARD #185

DSP Development

array Microsystems announces the full production release of the a66523 FDaP™ Development System for the IBM-PC Host (arraysofftSM), v. 1.0. The a66523 arraysofft software supports the a66 family of products and includes a code generator for the DaSP™/PaC™ chipset. The a66523 FDaP Development System is priced at \$99. **array Microsystems, Inc.**
INFO/CARD #184



NOW OFFERING: Microprocessor crystals at competitive pricing!

QUARTZ CRYSTALS

- | | |
|--------------------------|-----------------------|
| ■ Communication Crystals | ■ Baseplated Blanks |
| ■ Custom Crystals | ■ Finished Blanks |
| ■ QPL/Mil-Spec Crystals | ■ Rough Lapped Blanks |

"Not just another crystal company"

ELECTRO DYNAMICS CRYSTAL CORPORATION

9075 Cody • Overland Park, KS 66214

PH (800) EDC-XTAL ■ FAX (913) 888-1260

INFO/CARD 47

RF expo
WEST

March 17-19, 1993
San Jose, California

Plan Now to Attend!

For information call:
800-525-9154

SURPLUS SALES OF NEBRASKA

Looking For INTEGRATED CIRCUITS?

We have a 50 page catalog which lists ICs currently in our inventory including rare and "Hard-To-Find" part numbers.
• Send US\$4 for your copy •

Looking For TRANSISTORS/DIODES?

We have a 30 page catalog which lists transistors and diodes currently in our inventory including rare and "Hard-To-Find" part numbers.
• Send US\$2 for your copy •

Looking For MS Circular Connectors?

Over 10,000 in stock. Send US\$2 for list.


NOW AVAILABLE FLYER 6A

16 BIG pages of components....
TEST EQUIPMENT • FINGER STOCK • DUMMY LOADS,
ATTENUATORS • VACUUM RELAYS & CAPACITORS •
TRANSMITTING COMPONENTS • TUBES • FEED-
THRU • MICROWAVE COPPER CLAD • WAVE GUIDE
Send a postcard asking for your copy!

Do you have surplus parts or equipment on hand? Fax or mail your list for a prompt bid.

SURPLUS SALES OF NEBRASKA
1502 Jones St. • Omaha, NE 68102
402-346-4750 • fax: 402-346-2939

INFO/CARD 48

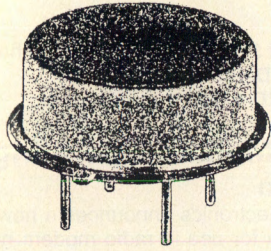

TO-8 Filters

\$25.00 each

(quantity: 100 and up)

- 10 MHz to 2,500 MHz.
- 3 sections
- 3 dB bandwidths: 5% to 20%
- Stopband rejection: 50 dBc.
- Temperature: -25 to +50 °C
- Shock: to 15 G
- Vibration: to 5 G
- Relative humidity: to 90%

Special models are also available in the TC series, with up to 6 sections, frequency ranges to 6,000 MHz, 3 dB bandwidths from 3% to 100% of the center frequency, and increased environmental capabilities. Other Lark Engineering Company TO-8 package filter models include lowpass and highpass configurations, and also models that can be qualified to MIL-SPEC environmentals.

**Call, Write, or Bingo for
our new 100 page Catalog!**
714-240-1233



Lark Engineering Company
A Division of Baier & Baier, Inc.
27151 Calle Delgado
San Juan Capistrano, CA 92675
FAX: 714-240-7910

INFO/CARD 49

RF literature

Circuit Board Material

Rogers Corp. offers a data sheet on TMM® temperature stable microwave material for high reliability stripline and microstrip circuit boards. TMM laminates, based on a ceramic/thermoset polymer composite, offer many of the benefits of both ceramic and traditional PTFE microwave circuit materials. Electrical, mechanical and thermal data is included.

Rogers Corporation
INFO/CARD #180

Reduced BW Digital Data Transmission

"Designing a Multirate ADPCM System with SPW", a 12-page application note available free of charge from Comdisco Systems describes the design of a multirate adaptive differential pulse code modulation (ADPCM) system that can reduce the bandwidth required to transmit digitized speech, video, modem data and other information.

Comdisco Systems, Inc.
INFO/CARD #179

Product Selection Guide

Harris Semiconductor's new Product Selection Guide provides shortform reference for all of the company's standard and discrete products as well as ASIC services. The eight sections include a guide to new products and publications, as well as an alphanumeric part numbering index. The analog section covers amplifiers, intelligent power ICs and specialty analog circuits.

Harris Semiconductor
INFO/CARD #178

Capacitor Characterization

Microelectronics Ltd.'s publication, "Introduction to Capacitors for Microwave Applications", is a five-page article describing the design requirements of capacitors at frequencies above 300 MHz. The significance of Q and the problems involved in measuring Q at high frequencies are discussed. The use of ceramic dielectrics in microwave capacitors is supported by parametric data.

Microelectronics Ltd.
INFO/CARD #1177

Quartz Crystals and Oscillators

Piezo Crystal Co. announces the availability of a new-product brochure, covering quartz crystals and quartz crystal oscillators. The brochure includes detailed technical information on Piezo's low cost, high performance OXCO (2920139), which is designed for the test equipment, cellular and VSAT industries.

Piezo Crystal Co.
INFO/CARD #176

Hopping Filter Catalog

A 14-page catalog from Pole Zero contains information on their expanded MINI-POLE™ and MAXI-POLE™ hopping filter product line.

Additionally, it covers their new digitally tuned high frequency (HF) filters and PC/AT RF Pre/Postselectors for personal computers.

Pole Zero Corp.
INFO/CARD #175

Microwave Printed Circuits

Poly Circuits announces the release of a new technical guideline for fabrication of high frequency circuit boards and passive microwave frequency components. Technologies such as SMT to flat pad topography, integrating high frequencies with low frequencies and heat sinking for high power applications are discussed.

Poly Circuits, Inc.
INFO/CARD #174

EMI Shielding Products

Tecknit's new EMI shielding-products catalog includes knitted wire mesh, metal fibers, screens, oriented wires in elastomers, conductive elastomers, shielding windows, vent panels, conductive adhesives, epoxies, coatings, and low closure force gaskets such as silver nylon thread knitted over foam and Beryllium copper fingerstock. The 156-page catalog is divided into nine clearly tabulated product sections.

Tecknit
INFO/CARD #173

VCO Specification Guide

M/A-COM Semiconductor Division offers a selection guide for specifying their voltage controlled oscillators. The VCOs are available in TO-8 packages and in frequency bands between 1 and 10 GHz, with bandwidths from 5 to 40 percent.

M/A-COM Semiconductor Division
INFO/CARD #172

RFI/EMI Shielding Products

A four-color brochure from Tech-Etch describes their line of RFI/EMI shielding products. The fold-out brochure contains a product selection matrix, displaying products across the top and parameters and descriptions going down the page. Among the products are finger stock, knitted wire mesh strips, flat gaskets, shield-wrap, and vent and filter shields.

Tech-Etch, Inc.
INFO/CARD #171

EMI Groove Gasket Mounting Guidelines

A designer's guide from Spira discusses five different ways to employ their high shielding, long wearing EMI gaskets. One of the groove designs highlighted is the new "pinch boss" groove which offers a very inexpensive, reliable solution for high volume commercial applications. The pros and cons of each method are examined, including: shielding benefits, cost considerations, and manufacturability.

Spira Mfg. Corp.
INFO/CARD #170


MARKETPLACE

WHEN YOU ARE READY TO BUY-SELL-TRADE CALL RF DESIGN MARKETPLACE

Increase your REVENUES with *RF Design Marketplace* advertising! Over 40,000 prospects read and buy from this section each month. To reach this sophisticated, targeted market call today (303) 220-0600.

Advertising Index

Advertiser	Page No.
Amplifier Research	28
Analog & RF Models	77
Andersen Laboratories	84
California Eastern Laboratories	45, 47
C-MAC Quartz Crystals	16
Coastel Cable Tools, Inc.	79-80
Coaxial Dynamics, Inc.	60
Coilcraft	83
CTS Corp.	19
EG&G Frequency Products	14
Electro Dynamics Crystal Corp.	75
ENI	17
Henry Radio	10
Hewlett-Packard	15
Hybrids International Ltd.	72
IFR Systems, Inc.	3
International Crystal Manufacturing Co., Inc.	56
JAN Crystals	55
JFW Industries, Inc.	41
K & L Microwave	61, 63
Kalmus Engineering Int'l. Ltd.	21
KVG North America	39
Lark Engineering Co.	76
Leader Tech	20
Loral Microwave — FSI	2
M/A-Com Semiconductor Products Operation	12
Matrix Systems, Inc.	31
Merrimac	11
MicroSim Corp.	27
Mini-Circuits	4-5, 32-33, 59, 69
Motorola - GEG	6
Noise/Com, Inc.	9
Nova RF Systems, Inc.	77
Penstock, Inc.	62
Piezo Crystal Co.	29
Programmed Test Sources, Inc.	24
QUALCOMM, Inc.	70
Repco	57
RF Design Software Service	10
Richardson Electronics Ltd.	56
SCITEQ Electronics, Inc.	78
Sprague Goodman	13
Surcom Associates, Inc.	55
Surplus Sales of Nebraska	75
Synergy Microwave Corp.	73
Tesoft, Inc.	72
Vectron Laboratories, Inc.	18
Wavetek	23
Wenzel Associates	14
Werlatone, Inc.	8
Wide Band Engineering Co., Inc.	54

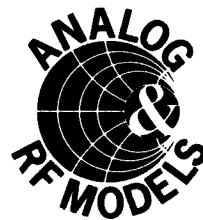

RF SPICE MODELS


- BIPOLAR, FET, DIODE
- NON-LINEAR MODELS
- CLASS C POWER
- OPTO, LOGIC, OPAMPS
- MEASUREMENTS IN-HOUSE

6987 N. Oracle Rd., Tucson, AZ 85704
PHONE (602) 575-5323 FAX (602) 297-5160

INFO/CARD 53

NOVA RF Systems, Inc.

The Complete RF/Microwave Solution

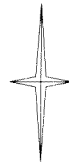

- RF/Microwave Systems
- Custom Design/Consulting
- Simulation Software
- Synthesizers (PLL/DDS)
- Complete Lab/Machine Shop
- TDMA/CDMA/Spread Spectrum

1740 Pine Valley Dr. • Vienna, Virginia 22182
(703) 255-2353

INFO/CARD 54



- Promote your company...
- Trade used equipment...
- Sell your products...

Every month for only \$395

CALL 303-220-0600 TODAY!



FREQUENCY SYNTHESIS

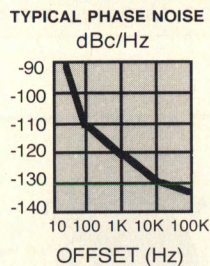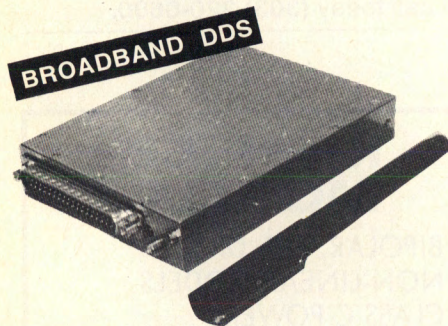Bandwidth 1 to 400 MHz
 Step size <1 Hz
 Frequency control 30-bits, parallel
 Spurs <-45 dBc typ
 Size 3.75" x 4.78" x 0.89"
Output **Quadrature**



ADS-431
ADVANCED DDS

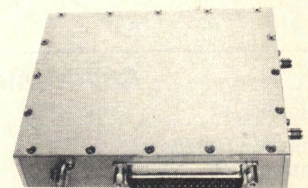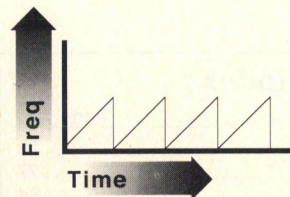Bandwidth 1 to 230 MHz
 Step size <30 Hz granularity
 Phase control 12-bit
 Switching 2 nanosecond update
 Spurs -55 dBc typical (CW)
 5.25" chassis or 5" x 7" x 1.125" module



DCP-1
GaAs DDS

This **LOW COST** module is perfect for ATE, simulation, EW, and all other applications where speed and phase continuity are important.



The VDS-6030 is a low cost C-band solution, with excellent phase noise and low power dissipation. It's also available in L-band.

SCITEQ
 specializes in advanced technology
frequency synthesis,
 using direct digital, phase-locked-loop,
 Arithmetically Locked Loop, and mix/filter
 designs, plus unique combination
 architectures that combine the advantages of
 multiple underlying technologies.

For Synthetic Aperture Radar and other systems requiring state of the art LINEAR FM. Sciteq's DCP-1 provides extended bandwidth, high linearity, phase control, and excellent spectral purity.


This one square inch waveform generator includes digital phase, frequency, and amplitude control, yet it only dissipates 1.5W at f_{ck} max.

VDS-6030
ARITHMETICALLY
LOCKED LOOP

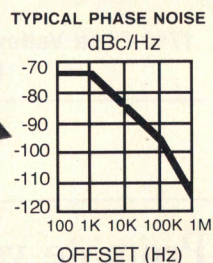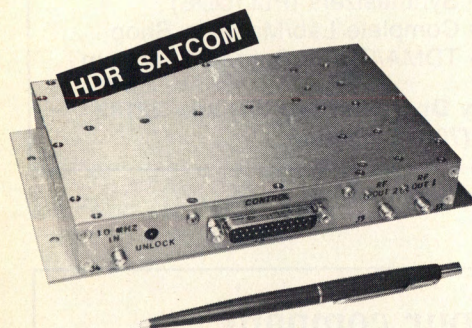

Bandwidth 4.65 to 5.25 GHz
 Step size 2.5 MHz
 Outputs 2-channels @ +17 dBm
Total power <5W
 BIT TTL lock indicator
 Spurs -60 dBc
 Reference 10 MHz, ext (internal optional)

DDS-1
SYNTHESIZER &
MODULATOR

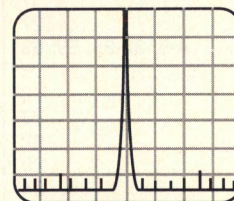

TYPICAL SPURS



Maximum clock up to 25 MHz
 Frequency control 32-bit
 Switching speed <1 μsec
 Output SINE, 1 VP-P
 Phase noise per the clock
 Gating >>100 dB ON/OFF, 1-bit toggle
Modulation digital amplitude, φ, FSK



Make your common mode EMI disappear into this black hole.

This tiny toroid inside every Coilcraft EMI filter provides over 15 dB of *true* common mode noise suppression.

By using a single magnetic structure to filter multiple lines, Coilcraft data line filters give you differential *and* common mode noise suppression, something simple ferrite beads just can't do.


You get >15 dB attenuation from 30 to 300 MHz. Or up to 40 dB just by adding capacitors!

They're small and easy to install. And they're far less expensive than filtered connectors.

Order our D103 Designers Kit (\$75) containing 16 samples of our surface mount and DIP filters. Or for more information call 800/322-2645.



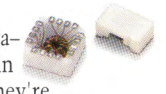
Surface Mount Filters Our ultra-miniature surface mount filters come in 10, 8, 4, 3 and 2 line configurations. They're packaged in a flat top ceramic case and are available in tape and reel format for auto insertion.




DIP Filters These filters reduce conducted noise by a factor of 32 from nearly 1 MHz to 300 MHz while passing frequencies below 100 kHz without attenuation. They come in 8, 4, 3 and 2 line versions



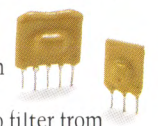SIP LC Filters With capacitors on each line, these filters achieve up to 40 dB attenuation. We offer versions to filter from 1 to 8 lines.



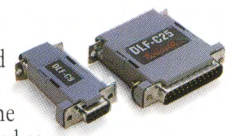Cable Filters Plug one of these modules into a cable and its common mode magnetics will filter all lines including the frame ground. EMI is attenuated as much as 19 dB while leaving data signals undisturbed. Choose DB-9, 15, 25 or IEEE 488 versions



Tip and Ring Filters These low cost filters help telecom designers meet FCC Part 15 and 68 requirements. Available in 2 and 4 wire versions, they provide 20 dB attenuation of common mode noise over a 30 to 250 MHz range; 15 dB out to 300 MHz.



Phone Line Filters Fix noisy phone lines with these plug-in filter modules. They come in 2 and 4 line versions, in RJ-11, RJ-14 and RJ-45 configurations.



Coilcraft

1102 Silver Lake Rd., Cary IL 60013
800/322-2645 Fax 708/639-1469
INFO/CARD 51



**You can't buy
a better precision
timepiece for
under 2.4 GHz.**

If you're operating in a frequency range from 100 MHz to 2.4 GHz, you can't buy a better oscillator than an Andersen VCO. It gives you the highest spectral purity with the lowest spurious ($> -60\text{dB}$). And typical single sideband phase noise of $> -119\text{dBC @1 KHz offset}$.

It's compact. It's rugged. It operates in temperatures up to 100°C . It can be tuned up to 1.5 MHz or phase-locked to a reference. Plus, its low mass and low profile make it ideal for surface-mount technology, DILS or flatpaks.

Isn't it about time you discovered the precision, the versatility and simplicity of designing with Andersen oscillators? Contact Andersen Laboratories, 45 Old Iron Ore Road, Bloomfield, CT 06002. Telephone (203) 286-9090/FAX 203-242-4472.

 **ANDERSEN LABORATORIES**