

RF design™

engineering principles and practices

July 1993



**1993 RF Design Awards
Contest Winners!
Terry Hock and Ray Page**

New radiation monitor from narda

Any signal environment. Any type of modulation.

The new Series 8700 is the most capable, accurate, expandable system ever developed. And it's available only from Narda.

With it, you get a test set that combines automatic zeroing with true RMS average results. It measures any signal environment, even pulsed RF, and any type of modulation. Isotropic detecting, magnetic field probes are virtually immune to the out-of-band responses that in the past compromised the integrity of field surveys below 300 MHz.

Field probes are available in a wide selection of measurement levels and frequency ranges including ultra-broadband 300 KHz to 40 GHz, with FLAT or ANSI-shaped responses.

Only from Narda.



Field probes that measure magnetic or electric fields with multiple emitters. They display readings directly as a percentage of the new IEEE C95.1-1991 standard.

For more information, or a free catalog, call or write Loral Microwave-Narda, 435 Moreland Road, Hauppauge, NY 11788. Tel: (516) 231-1700. Fax: (516) 231-1711. TWX: 510-221-1867. Cable: NARDACORP HAUPPAUGE, NEW YORK.




LORAL
Microwave-Narda

Time domain composite video wave form

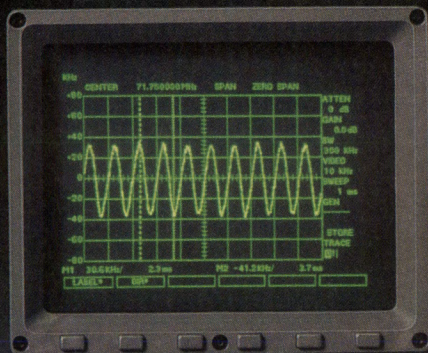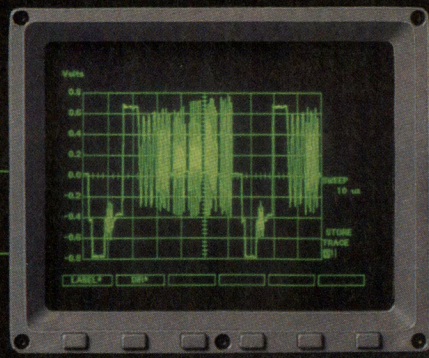

Demodulated FM carrier

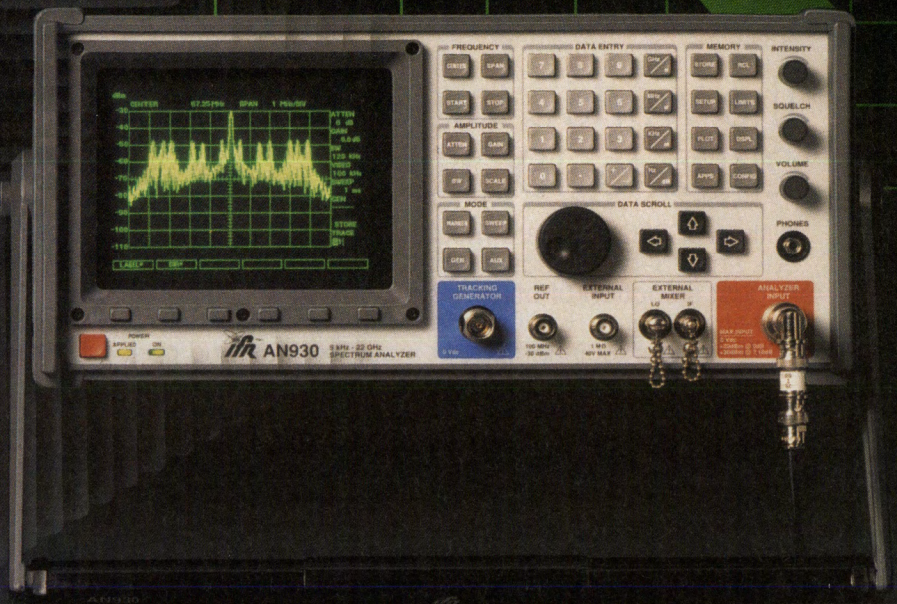

GET THE TOTAL PICTURE WITH AN IFR SPECTRUM ANALYZER

In addition to being a full-featured 22 GHz spectrum analyzer, the AN930 is a powerful measurement tool that can perform frequency or time domain analysis on the complex signals found in many modern communications systems.

A 30 MHz resolution bandwidth filter combined with a powerful set of time domain measurement functions provides the AN930 with a unique ability to capture and analyze pulsed and digital transmissions that previously has been unavailable in any other spectrum analyzer.

A built-in, sensitive FM/AM receiver with modulation measurement scales enables direct measurements of FM deviation or AM percent modulation. The accompanying high-quality audio output aids in identification of unknown or interfering signals.

Other standard AN930 features include an automatic limits test function for unattended detection of random or intermittent signals, a built-in frequency counter for precise frequency measurements, RS-232 and IEEE-488 interfaces, and operation from DC power sources.

Optional features including a built-in 2.9 GHz tracking generator, quasi-peak detector, high stability time base, and a rechargeable battery pack add even greater flexibility for solving your unique measurement requirements.

Contact IFR or your local IFR representative for more information or to arrange for a demonstration of the AN930.



IFR SYSTEMS, INC.

RENT DIRECTLY FROM IFR
Call 316/522-4981, Ext. 207 for details

CRAFTED WITH PRIDE IN
USA

10200 West York Street / Wichita, Kansas 67215-8935 U.S.A.
Phone 316/522-4981 / TWX 910-741-6952 / FAX 316/522-1360

INFO/CARD 2


POWER SPLITTERS/ COMBINERS

the world's largest selection
2KHz to 10GHz from \$2⁹⁵

With over 300 standard models, from 2-way to 48-way, 0°, 90° and 180°, 50- and 75-ohms, covering 2KHz to 10GHz, Mini-Circuits offers the world's largest selection of off-the-shelf power splitter/combiners. And, with rapid turnaround time, we'll also supply "special" needs, such as wider bandwidth, higher isolation, lower insertion loss and phase matched ports.

Available for use in military and commercial requirements, models include plug-in, flat-pack, surface-mount, connectorized standard and custom designs. New ultra-miniature surface mount units provide excellent solutions in cellular communications, GPS receivers, Satcom receivers, wireless communications, and cable systems.

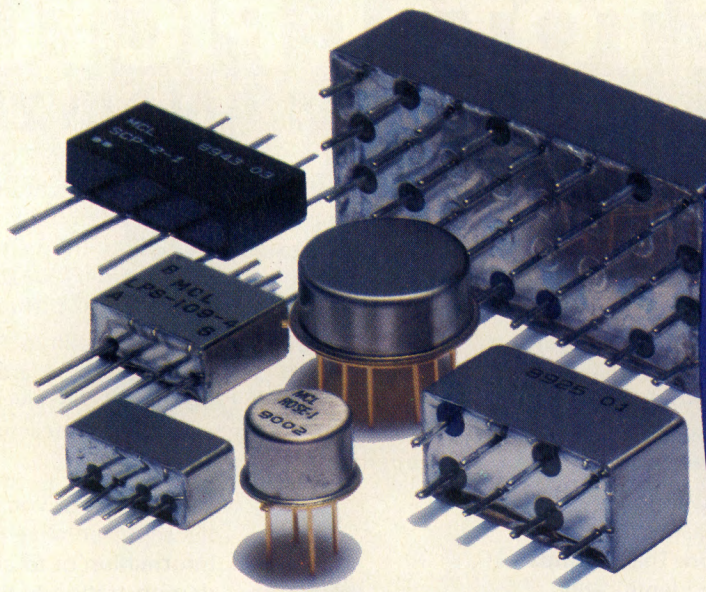All units come with a one-year guarantee and unprecedented "skinny" sigma unit-to-unit and production run-to-production run repeatability. All catalog models guaranteed to ship in one week. Mini-Circuits...dedicated to exceed our customers' expectations.



finding new ways ...
setting higher standards


Mini-CircuitsTM

WE ACCEPT AMERICAN EXPRESS AND VISA


Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010



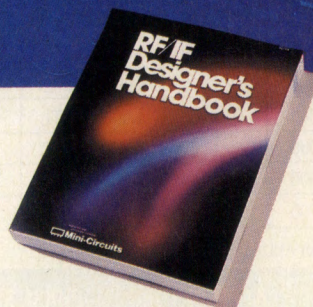For detailed specs on all Mini-Circuits products refer to
 • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY
 • EEM • MINI-CIRCUITS' 740-PG HANDBOOK.



WE'RE IN CONTROL.

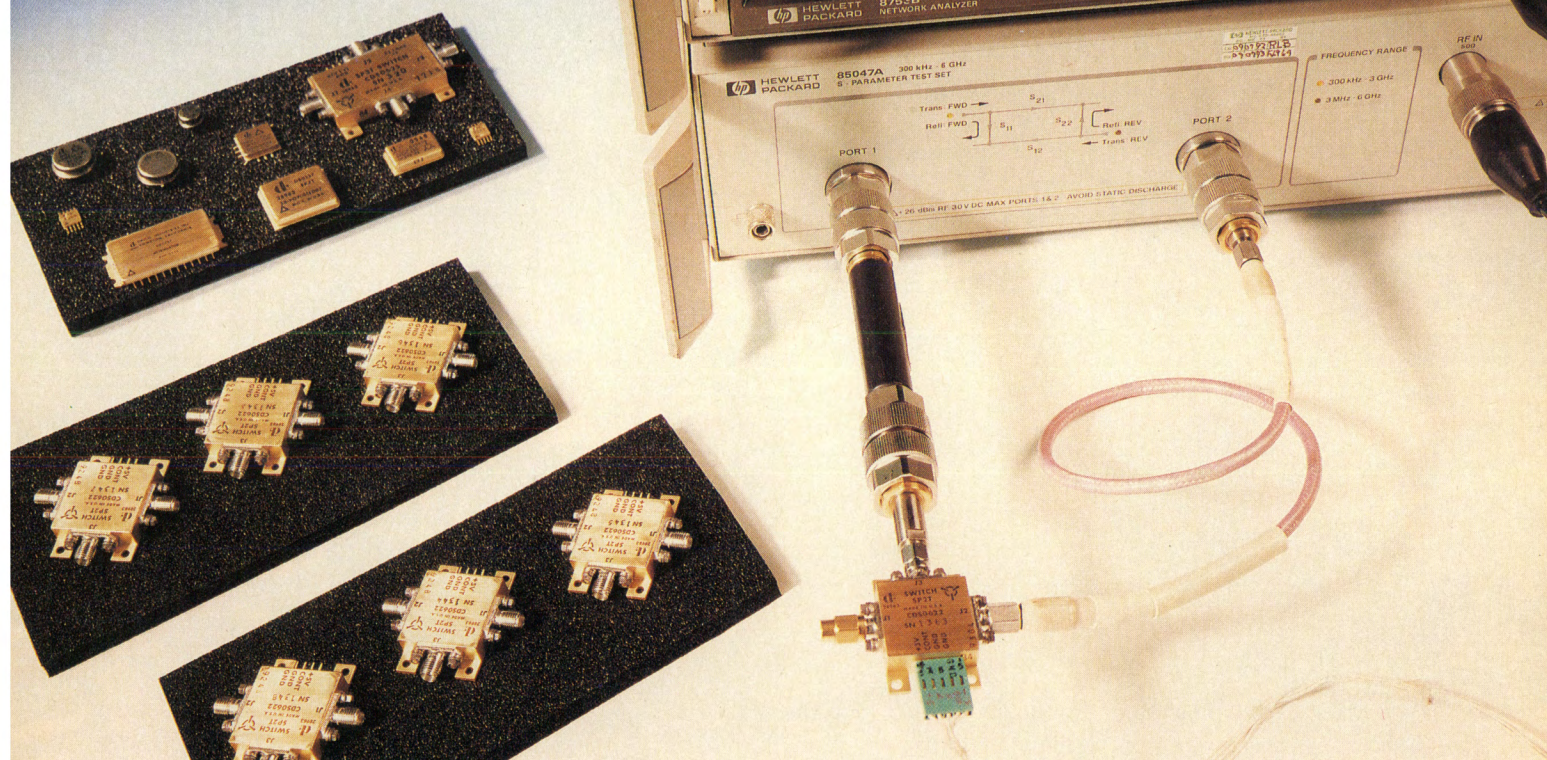

We've been the leader for 26 years and keep getting better. Whether its small quantities direct from stock or all encompassing blanket agreements... We have creative solutions to meet your price, quality and delivery objectives. We're in control and we're there for you.

Stock Switches

Con-fig	Freq MHz	IL dB	Iso dB	Switch Speed μ SEC Max	Control	Package	Part No.
SP2T	20-2000	0.7	85	3.000	TTL	SMA	CDSO622
SP2T	5-4000	1.0	79	0.035	TTL	SMA	CDSO882
SP4T	20-2000	0.9	72	3.000	TTL	SMA	CDSO624
SP2T	10-2000	0.60	82	1.000	TTL	14 Pin DIP	DSO052
SPST	10-2000	1.8	67	0.035	TTL	14 Pin SMP	DSO790
SP2T	DC-2000	0.7	50	0.200	TTL	TO-5	DSO813-T
SP4T	DC-2000	1.7	70	0.075	TTL	14 Pin DIP	DSO874

WE ACCEPT VISA AND MASTERCARD

Stock Digital Attenuators

# Of Sections	Freq MHz	LSB Range dB	IL dB	Switch Speed μ SEC/Max	Control	Package	Part No.
4	10-1000	1-15	1.9	0.030	TTL	SMP	DAO784-1
6	10-1000	1-63	4.2	0.050	TTL	24 Pin DIP	DAO886
7	DC-1000	0.5-63.5	7.1	0.100	TTL	38 Pin DIP	DAO897
7	10-1000	0.5-63.5	6.4	0.035	TTL	SMA	CDAO867



DAICO INDUSTRIES, INC.

2453 E. Del Amo Blvd., Rancho Dominguez, CA 90220
Telephone 310/631-1143 • FAX 310/631-8078

SWITCHES

ATTENUATORS

PHASE SHIFTERS

MMICS

BIT DETECTORS

INFO/CARD 4

COUPLERS

MODULATORS

AMPLIFIERS

design awards

31 **A Low Power RF ID Transponder**

This circuit, the design Grand Prize Winner of the 1993 RF Design Awards Contest, is a passive transponder intended for automated railcar tracking. Illuminating this low parts-count device with low power 915 MHz energy yields a modulated return signal at 1830 MHz.

— Raymond Page

37 **Synthesizer Design With Detailed Noise Analysis**

The winning software entry in the 1993 RF Design Awards Contest will help analyze and design phase locked loop synthesizers. The program provides a thorough model for all contributions to phase noise within the loop and predicts spur levels. Changes to loop response parameters result in an immediate change in the on-screen response graphs.

— Terrence F. Hock

cover story

49 **Contest Winners Demonstrate Innovation and Hard Work**

Now that judging is complete for the 1993 RF Design Awards Contest, the winners of this year's contest are formally announced. Brief descriptions of some of the "best of the rest" entries provide a preview of some of the designs to be seen in coming months.

tutorial

64 **RF Component Modeling for CAD/CAE**

This tutorial presents lumped passive models for RLC components, including parasitic effects and losses. For simplicity, only first order resonances are considered, although second order effects are discussed. — Les Besser



departments


8	Editorial
15	Letters
17	Calendar
18	Courses
21	News
28	Industry Insight
59	New Products
70	Marketplace
72	Product Report
73	New Software
74	New Literature
75	Info/Card
77	Reader Survey

R.F. DESIGN (ISSN:0163-321X USPS: 453-490) is published monthly and semi-monthly in August, July 1993. Vol.16, No. 7. Copyright 1993 by Cardiff Publishing Company, a division of Argus Press Holdings Inc., 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111 (303) 220-0600. Printed in USA. Contents may not be reproduced in any form without written permission. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: RF Design, P.O. Box 1077, Skokie, IL 60076. Subscriptions are: \$39 per year in the United States; \$49 per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700.

SUBSCRIPTION INQUIRIES: (708) 647-0756.

POSTMASTER & SUBSCRIBERS: Please send address changes to R.F. Design, P.O. Box 1077, Skokie, IL 60076.

HIGH POWER QUADRATURE HYBRIDS

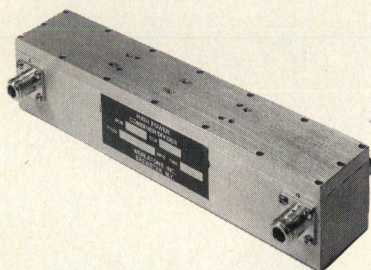

**FREQ. RANGE 100-1000 MHz
POWER 250 WATTS CW**

TYPICAL SPECIFICATIONS

**MODEL QH3198 100-300 MHZ
MODEL QH3199 300-1000 MHZ**

LOSS0.5db. max.
AMP.BAL..... ± 0.3 db max.
ISOLATION20db typ.
PHASE..... 90 ± 2 deg.
VSWR1.3:1 max.
CONNECTORSN

WERLATONE offers a full line of quadrature hybrids covering the 2-1000MHz frequency range at power levels to 1000 watts.

BROADBAND HIGH POWER
• DIRECTIONAL COUPLERS
• POWER COMBINERS
• HYBRID JUNCTIONS

WERLATONE INC.
DECADES AHEAD
P.O. Box 47
Brewster, NY 10509
Tel. (914) 279 6187
FAX. (914) 279 7404

RF editorial

Put the "R" Back Into R&D

*By Gary A. Breed
Editor*

Here in the U.S. we have a remarkable history of making scientific discoveries and engineering breakthroughs. We take pride in putting men on the moon, developing super computers, and creating world-wide communications systems.

But many American innovations have become commercial successes for foreign companies. Business practices in other countries often emphasize manufacturing rather than research. In the name of competitiveness, we're seeing U.S. industry being pushed to do the same; putting all of its effort into development. We may be over-reacting, with the danger of short-changing research.

The computer industry is giving us a look at the cost of a one-sided approach. Many companies that were riding on the PC boom are now in trouble as growth slows in the one technology they have been exploiting. Even big computer companies seem uncertain about the next step they should take. Maybe they don't have enough new ideas fermenting in their labs.

It's not time to panic, but the pendulum needs to start swinging back toward center. Fortunately, the timing of new RF growth opportunities puts them in the development stage and the current attitude is not yet a problem. But before we get caught unprepared for the next generation of opportunities, let's be sure that new ideas are being explored.

Some of these new ideas have been explored by engineers seeking recognition in this year's RF Design Awards contest. Ray Page's winning RFID transponder scheme is a good example of engineering research and develop-

ment, while Terry Hock's championship PLL design and analysis program demonstrates how engineers create tools to support their R&D work.


Our contest has been around for eight years now, and I took some time to reflect on past winners. At least 75 percent of the time, the winning engineers had significant, direct support from their employers. This support ranged from giving complete freedom to develop the project, to providing access to test equipment and time for writing. Yet, of the 11 Grand Prize winning entries, only three were the result of regular job assignments. There's a message here that shouldn't be missed — creative ideas are developed in an environment that supports creativity. If those companies had limited our past winners to only "productive" work, we would not have seen their great ideas.

To sum things up, it is essential that the U.S. electronics industry learn better ways to bring products to market. However, this should be a *new* capability, not a replacement for our proven record of innovation and creative research. We should be careful to encourage our best people to be creative, to maintain a constant and generous flow of new concepts and discoveries to fuel those newly-developed manufacturing skills.



No compromise necessary.

Murata Erie's new ASIC-based DCXO

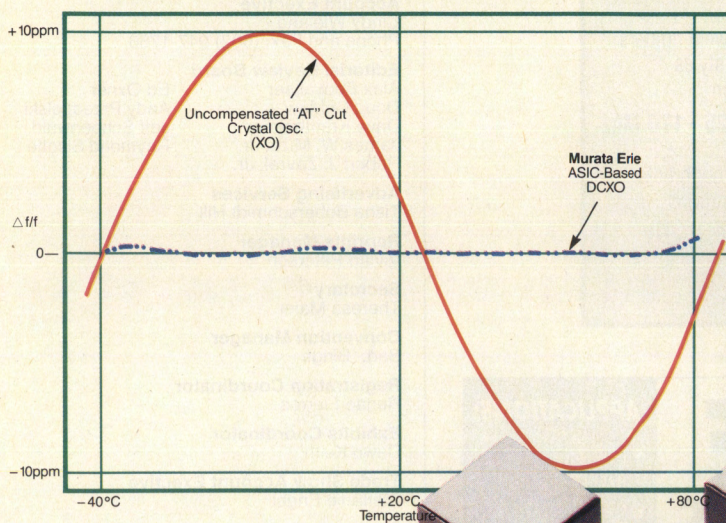


Excellent frequency stability has been a fact of life with crystal oscillators for years. So has small size (a relative term), low cost and flexibility. **But**, did you ever try to get everything that you needed in a single oscillator/package? No way. One, maybe two desirable characteristics but certainly not all. You had to compromise.

Now, compromise no more.

Murata Erie has the solution...our new ASIC-based, digitally compensated crystal oscillator is exceptionally stable, truly tiny, low in cost and extremely flexible. It is basically everything that you always wanted in a crystal oscillator but always had to compromise to get.

Check some of these features and specifications:

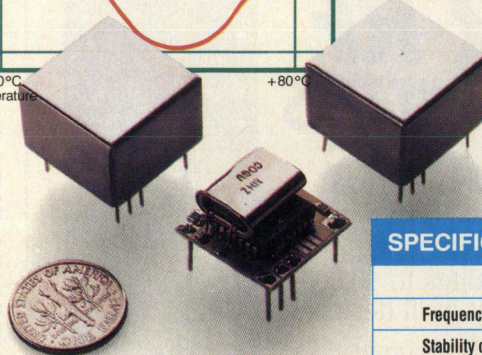- To ± 0.25 ppm stability
- Less than 5.0 cubic centimeters volume
- 100 mW max power
- Built-in interface for reconfiguration capability and software
- Single +5VDC power supply



SPECIFICATIONS

	DC2210 AH
Frequency Range	10MHz to 25MHz
Stability over -40°C to $+85^{\circ}\text{C}$	± 0.5 ppm
Output	"HC" CMOS
Power Dissipation	+5V @ 15mA
Short Term Stability	1×10^{-9} @ $T=1$ sec.
Package Size	$0.79" \times 0.79" \times 0.45"$, PC PINS

Find out more about how you can take the compromise out of your crystal oscillator specifications. Write for complete details on Murata Erie's new ASIC-based DCXO or call 1-800-831-9172, FAX: 1-404-684-1541.



MURATA ERIE NORTH AMERICA
Marketing Communications
2200 Lake Park Drive
Smyrna, GA 30080
Delivering Technology WorldwideSM

LAP-TECH INC.

FREQUENCY CONTROL PRODUCTS

LAP-TECH INC.
230 SIMPSON AVE.
BOWMANVILLE, ONTARIO
CANADA L1C 2J3

TEL: 416-623-4101
FAX: 416-623-3886

- **QUARTZ CRYSTALS 2 - 250 Mhz**
Precision glass encapsulation
Cold Weld and Resistance weld holders
Leaded and surface mount styles
Standard and custom design
- **CLOCK OSCILLATORS 0.25 - 170 Mhz**
TTL, HCMOS AND ECL
Hermetic packages with through hole
and surface mount configurations
- **EMERGENCY SERVICE DELIVERY**
- **QUALITY**
ISO 9002 pending

INFO/CARD 7

HI-POWER RF AMPLIFIERS, TRANSMITTERS AND POWER GENERATORS

MILLIONS OF WATTS SOLD... Henry has delivered for 30 years. We can ship designs in the 2 to 500 MHz range with power ratings to 10,000 watts from stock. If we don't have it we'll design it.



**HENRY
RADIO**

2050 S. Bundy Drive
Los Angeles CA 90025
Toll Free: 1-800-877-7979
Or: 1-310-820-1234
FAX: 1-310-826-7790

APPLICATIONS:

- POWER AMPLIFIERS
- SHORE STATIONS
- CW/AMTOR/TELEX
- BROADCAST
- NUCLEAR MAGNETIC
- LASER EXCITATION
- PLASMA GENERATORS
- SPUTTERING
- MEDICAL



INFO/CARD 8

RF design

a Cardiff publication

Established 1978

Main Office:

6300 S. Syracuse Way, Suite 650
Englewood, CO 80111 • (303) 220-0600
Fax: (303) 773-9716

Vice President -- Group Publisher
Kathryn Walsh

Editor

Gary A. Breed

Associate Editor

Liane Pomfret

Technical Editor

Andrew M. Kellett

Consulting Editor

Andy Przedpelski

National Sales Manager

Bill Pettit
Main Office

Account Executive

Maryanne Averill
Main Office

Account Executive

Cindy Wieland
Phone and Fax: (602) 947-1786

Editorial Review Board

Alex Burwasser
Doug DeMaw
Dave Krauthimer
James W. Mize, Jr.
Robert J. Zavrel, Jr.

Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Sciotte

Advertising Services

Tisha Bobersmidt Hill

Reprints Manager

Vivian Peterson

Secretary

Theresa Maier

Convention Manager

Barb Binge

Registration Coordinator

Rena Fierros

Exhibits Coordinator

Dawn Keith

Trade Show Account Executive

Steffanie Engel

Associate Production Managers

Matt Park

Maurice Lydick

Artists

Kim Austin
Joyce Fields
Brad Fuller

Paul Rivera
Sheri Culmer

Composition

Mike C. Moore

Art Director

Bob Stewart

President

Robert A. Searle

Vice President — Production

Cherryl Greenman

Vice President — Convention Management

Kathy Kriner

Vice President — Finance

Jennifer Burger

Vice President — Circulation

Patricia Shapiro

Credit Manager

Christine Kloack

Please address subscription inquiries to:

RF Design

P.O. Box 1077, Skokie, IL 60076-9931

Postmaster: send form 3576
to the above address.


CARDIFF
PUBLISHING COMPANY, INC.

BPA


A Division of Argus Press Holdings Inc.

**ARGUS
PRESS
GROUP**


WHAT DO THESE FILTERS HAVE IN COMMON?

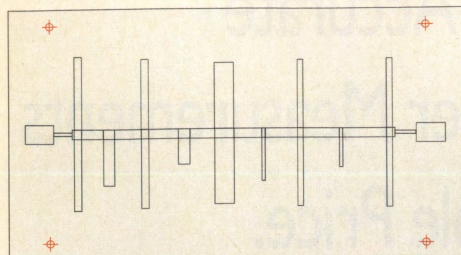

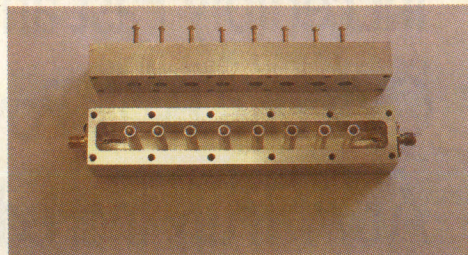
5.6 GHz Elliptic Bandpass on Teflon Board




1.27 GHz Machined Combine Bandpass

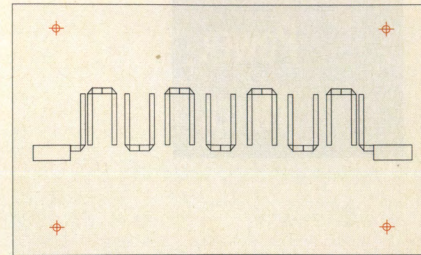


2.2 GHz Hairpin Bandpass on Teflon

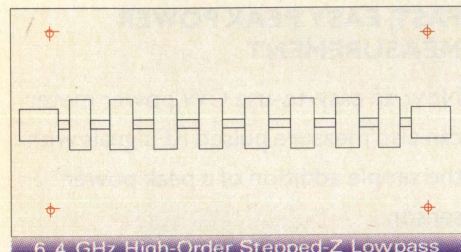

6.4 GHz High-Order Stepped-Z Lowpass

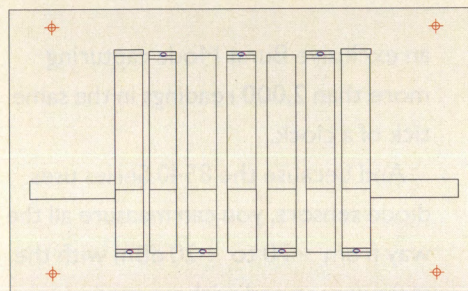


10 GHz Wideband Interdigital BP

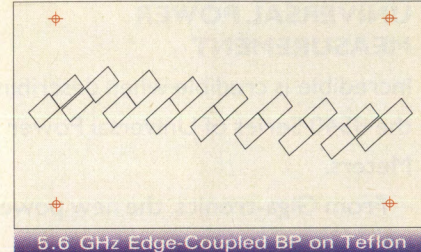


5.6 GHz Edge-Coupled BP on Teflon



5.6 GHz Hairpin Bandpass on Teflon

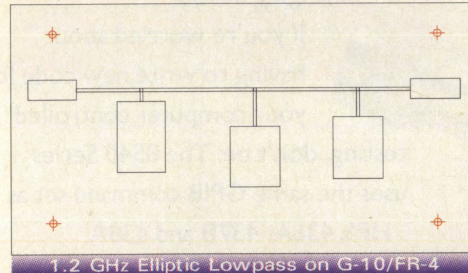

1.2 GHz Elliptic Lowpass on G-10/FR-4

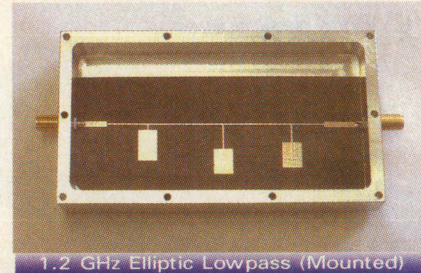

1.2 GHz Elliptic Lowpass (Mounted)

THEY WERE DESIGNED WITH THE NEW =M/FILTER=

COMPLETE SET OF DISTRIBUTED STRUCTURES

- ★ Lowpass, bandpass, highpass & bandstop
- ★ Microstrip, stripline, coax & slabline (machined)
- ★ Edge coupled, end coupled, direct coupled
- ★ Hairpin, combine, interdigital, elliptic, stepped-Z

START TO ART


- ★ Complete design including synthesis & simulation
- ★ Output layout to plotters & laser printers
- ★ HPG and DXF files ready for board suppliers

STATE-OF-THE-ART ALGORITHMS

- ★ Automatic end, bend, tee and cross absorption
- ★ Corrects dispersion & differential phase velocity
- ★ Accurate design bandwidth
- ★ N-coupled line models



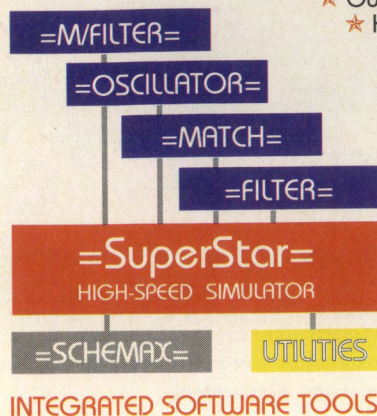★ Design began at 11AM on four microstrip filters and HPG files were ready for board suppliers by 1 PM. Using T-Tech's Quick Circuit milling platform, boards were ready for test by 5PM. =M/FILTER= files were tested by several board suppliers to insure compatibility.



SAME PRICES INTERNATIONALLY
DIRECT SALES & USER SUPPORT
BY FAX, PHONE OR LETTER

EAGLEWARE

Eagleware Corporation ★ 1750 Mountain Glen ★ Stone Mtn, GA 30087 ★ USA
TEL (404) 939-0156 ★ FAX (404) 939-0157

GIGA-TRONICS
8540
UNIVERSAL
POWER
METER

Incredibly Fast and Accurate CW and Peak Power Measurements At A Truly Incredible Price.

UNIVERSAL POWER MEASUREMENT

Incredible is credible when describing the 8540 Series of Universal Power Meters.

From Giga-tronics, the new power in power meters.

For the very first time, you can make CW and peak power

an exclusive Burst Mode capturing more than 2,000 readings in the same tick of a clock.

And because the 8540 Series uses diode sensors, you can measure all the way from -70 to $+20$ dBm with the same sensor, and without range

changing delays.

If you're worried about having to write new code for your computer controlled testing, don't be: The 8540 Series uses the same GPIB command set as HP's 436A, 437B and 438A.

Think about what all this will do for your ATE productivity as well as for your company's bottom line.

FAST, EASY PEAK POWER MEASUREMENT

Now, an easy-to-use CW power meter can also measure pulsed RF signals with the simple addition of a peak power sensor.

There are no time-consuming, unreliable duty cycle corrections, and you'll get the same accuracy and speed you'd get with a much-more-expensive dedicated peak power meter.

View the pulsed signal's amplitude profile on a scope and see the exact power measurement point on the pulse. Measure the overshoot. Measure the droop.




The two-line display also lets you set the desired resolution and select either Lin or Log readout for each line.

measurements quickly and accurately with a single meter—a Universal Power Meter.

And all for about the same price you'd pay for the competitor's CW only power meter.

POWER MEASUREMENTS INSTANTLY

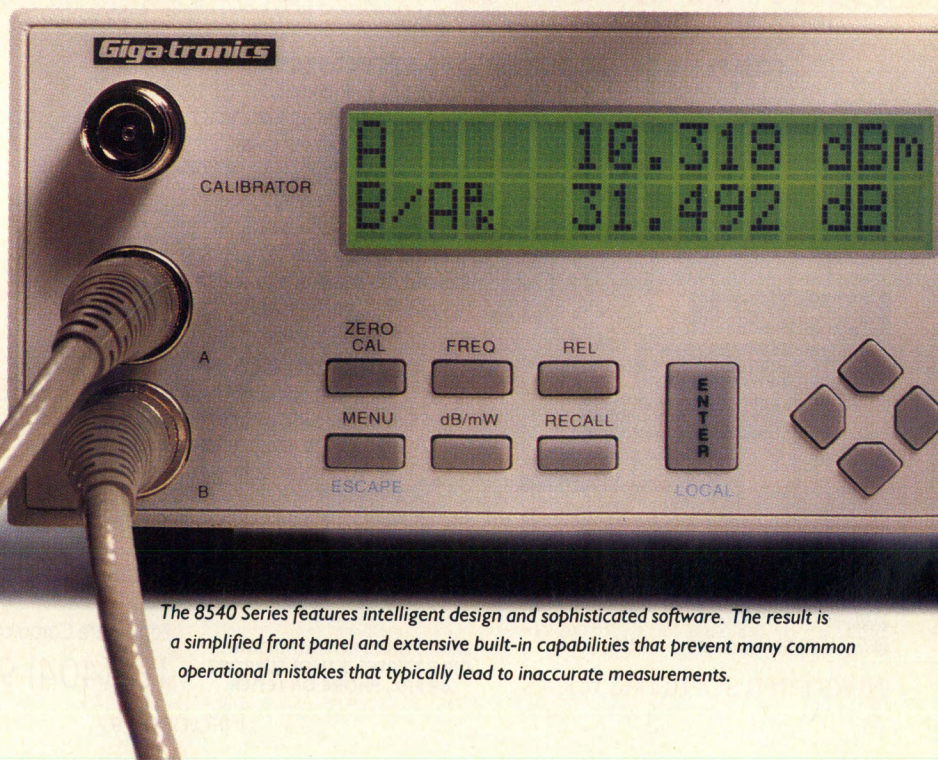Imagine seeing display updates instantly: measurement speeds over the GPIB exceeding 200 readings per second and




The 8540 Series features intelligent design and sophisticated software. The result is a simplified front panel and extensive built-in capabilities that prevent many common operational mistakes that typically lead to inaccurate measurements.

The Secret Is The Sensors.

Surface Mount technology
assures greater sensor
accuracy and reliability.

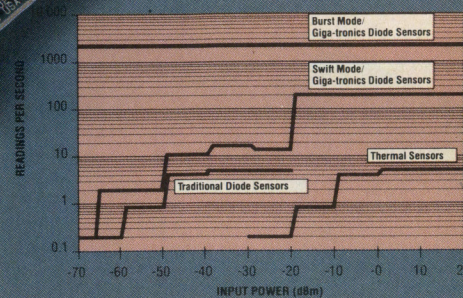Just look
at the incred-
ible improvement
in speed you'll get with
Giga-tronics' diode sensors.



You'll be confident of your peak power readings, and still have all the benefits of an incredibly fast CW power meter.

ONE OR TRUE TWO CHANNEL OPERATION

If a single-channel meter is what you need, the Model 8541 is the meter for you. But if you need two-channel capability, the Model 8542 lets you see readings from both channels *simultaneously*.

SIMPLE, INTELLIGENT OPERATION

The 8540 Series has only half as many controls as other power meters, but don't let that fool you. Intelligent design and sophisticated software give you easy

access to extensive built-in capabilities.


For example, you use the same key to zero and calibrate the power sensors. The meter automatically determines the function you want by detecting whether a sensor is connected to the calibrator.

Imagine all this power and performance. But why just imagine? Get the truly incredible Giga-tronics 8540 Series Universal Power Meter, and start measuring CW and peak power in a fraction of the time.


The Giga-tronics 8540 Series delivers incredible performance by taking full advantage of the speed and dynamic range of diode sensors.

What's more, Giga-tronics has solved the challenge that previously limited diode sensors to the "square law" region—below -20 dBm—by utilizing a built-in power sweep calibration system. So you get speed and a full 90 dB dynamic range without sacrificing accuracy.

8542 Power Meter

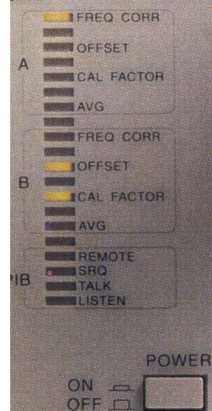

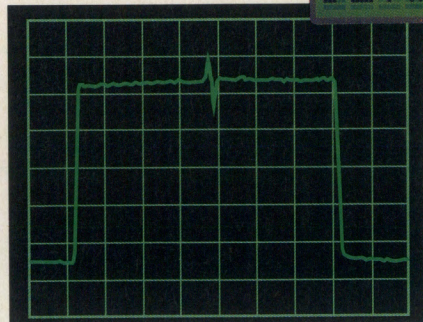A two-line back lit LCD display provides you more data in less time.



The peak sensor adds a marker on a monitor output for setting an exact measurement point on pulsed signals.

A -14.375 dBm
DLVA 122.010 US

Call us toll-free at
1 800 726 GIGA.
Outside the U.S.
call your local
Giga-tronics
representative, or

call 001 408 734 5780. We'll send you more information or arrange for an incredible hands-on demonstration.


Giga-tronics

Giga-tronics Incorporated
488 Tasman Drive
Sunnyvale, California 94089
Telefax: 408 747 1265

Merrimac


LUMPED ELEMENT CAPABILITIES

MIXERS, MODULATORS & BIPHASE MODULATORS

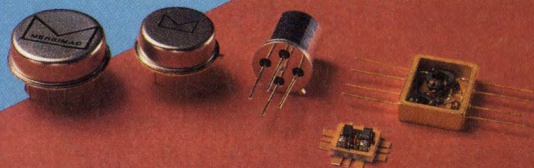


- ☐ Double and triple Balanced Mixers from 2 kHz to 18 GHz
- ☐ Class III Mixers with high intercept, low intermodulation
- ☐ TTL/ECL Biphasic Modulators to 5 GHz
- ☐ Hi-Rel/QPL Models for space and airborne applications

PHASE SHIFTERS AND TRIMMERS TO 3 GHz

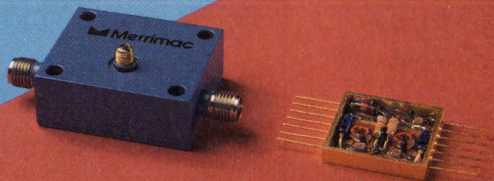


- ☐ Multi-turn 90°, 180° & 360° models for High Resolution
- ☐ TTL/ECL, D/A models for guaranteed phase monotonicity
- ☐ Miniature mechanical Phase Shifters and Trimmers to 3 GHz
- ☐ Linearized Wideband Phase Modulators and Shifters to 2.5 GHz

MECHANICAL AND ELECTRONIC ATTENUATORS

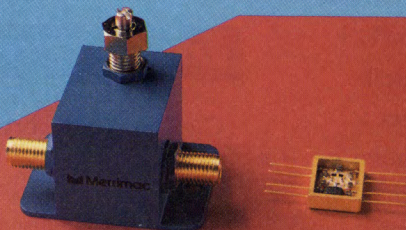


- ☐ Mechanical multi-turn attenuators to 500 MHz
- ☐ Digital 4 and 5 bit, PC mount and SMA models
- ☐ Guaranteed monotonic, D/A version, 8 bit, to 1 GHz
- ☐ Constant phase, variable attenuators to 500 MHz

OFF-THE-SHELF I & Q PHASE DETECTORS

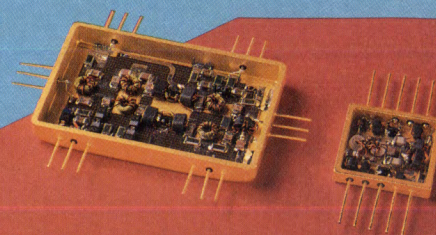

- ☐ Close tolerance I & Q for precision QPSK Demodulation
- ☐ Models with Integrated Video Amplifiers, TTL/ECL Drivers
- ☐ Ultrawide I & Q Networks for 1-100 & 30-1000 MHz
- ☐ Versions to 8 GHz in flatpack or connectorized packages

I & Q COMPLEX MODULATORS & DEMODULATORS

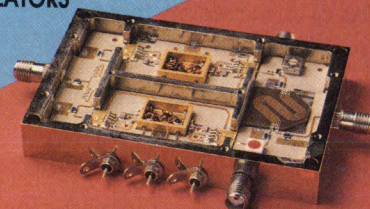

- ☐ Image Reject Mixers, with Phase and Amplitude Optimization
- ☐ Single Sideband Modulators, stable with Temperature
- ☐ Complex Vector, MSK, $\pi/4$ DQPSK Modulators
- ☐ 0° to 360° High Accuracy Phase Comparators

0°, 90° & 180° POWER DIVIDERS/ COMBINERS



- ☐ 2,3,4,5,6,8 & 12 way models in hermetic pin & SMD packages
- ☐ 2,3,4,6 & 8 way models with in-line SMA, & N-connectors
- ☐ 90° Power Dividers, Quadrature Hybrids, bandwidths to 23:1
- ☐ 180° Hybrid Junctions, 3 and 4 port, bandwidths to 80:1

Merrimac continues to lead the way in the design and manufacture of miniature lumped element circuits. Merrimac packages are now smaller, have a lower profile, contain more elements and outperform the competition in all important specifications

Merrimac

41 Fairfield Place, West Caldwell, New Jersey 07006
Tel: (201) 575-1300 • FAX: (201) 575-0531

RF letters

Letters should be addressed to: Editor, *RF Design*, 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111. Published letters may be edited for length or clarity.

Proposed Signalling Technique Comes Under Fire

Editor:

The system described by Greg Magin ("A Robust Signalling Technique for Part 15 Control Network Applications", *RF Design*, April 1993) has virtually zero processing gain because the spread signal is amplitude limited prior to the despreading operation. In order to gain most of the potential benefits from spread spectrum, it is necessary that the received signal be despread and passed through a filter having the desired despread bandwidth PRIOR to any limiting operations. ...

John MacConnell
Itron/Enscan
Eden Prairie, MN

Editor:

... Assume for a moment that the jammer power level was 1 dB above the power level of the desired signal. Since the system is hard limited, the output of the limiter would be the squared up jammer containing none of the information from the desired signal other than zero crossing timing jitter. ... The important point to understand here is that once the jammer signal level is increased by 1 dB over the desired signal level, the hard limiting of the system is going to erode ALL of the process gain. ... As Mr. Magin points out, the FCC is interested in the ability of the receiver to accept (put up with) and reject interference. The described architecture cannot reject any interference if it is stronger than the signal of interest.

John Kesterson
Mitsubishi Electronics America
Nevada City, CA

Mr. Magin responds:

... Most of the concern seems to focus on the use of post limiting despreading and signal processing. The architecture described in the article is but one possible implementation of the signalling technique. ... The post limiting architecture was chosen for low cost receivers because of the many real advantages including: reduced component count and cost, reduced power consumption

and elimination of AGC issues.

The major concern seems to be that when the jammer power equals the signal power, the limiter is captured and all information is lost. Our system produces very acceptable performance when the jammer power is equal to the signal power. Complete message packets are typically received with an 80 percent success rate. This corresponds to a BER of 3.4×10^{-3} which is more than 10 dB better than that achieved by a coherent BPSK system under similar conditions. It is interesting to note that the limiter-based Intellon system performed on par with classical direct sequence pre-detection despreading systems during jammer testing performed by the EIA CEBus RF committee. Pre-detection despreading systems must achieve and maintain accurate carrier lock in the presence of interference. This typically adds a lot of overhead in terms of synchronization preamble time and proves to be the weak link in many implementations.

To prevent loss of information when the level of the jammer exceeds the level of the desired signal, the CEBus RF system transmits the desired information on two identical sidebands which are separated by 10.5 MHz. When CRC errors are detected on one sideband, the receiver automatically tries the other sideband. For this reason, an interferer may be many orders of magnitude stronger than the desired signal without affecting link performance. The merit of a low cost communication link should be based on overall system performance and cost. We believe that our system achieves an extremely high performance to cost ratio.

Greg Magin
Intellon Corp.
Ocala, FL


Correction

In Andrzej Przedpelski's May 1993 tutorial, "A Comparison of Simple Software Methods for RF Calculations", equation three should be:

$$\begin{aligned} & [(42 + j2\pi f \cdot 0.01 + (j2\pi f \cdot 0.342 \times 10^{-15})^{-1} \\ & + j2\pi f \cdot 2 \times 10^{-12})^{-1} \end{aligned} \quad (3)$$

RF Expo East
Oct. 18-21
Tampa, FL

Sprague-Goodman

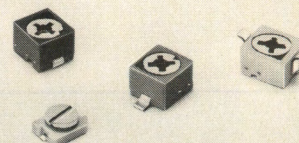

Surftrim® Surface Mount Trimmer Capacitors

- 2 sizes:
3.2 x 4.5 x 1.6 mm
4.0 x 4.5 x 2.7 mm (sealed)
- 4 mounting configurations
- Carrier and reel, or bulk pack
- 1.7 to 50 pF in 7 cap ranges
- Operates to 85°C


Phone, fax or write today for
Engineering Bulletin SG-305B.

**SPRAGUE
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 12

Sprague-Goodman

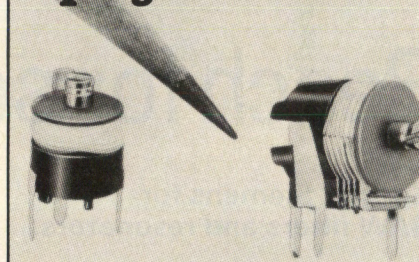

Filmtrim® Single Turn Plastic Trimmer Capacitors

- Cap ranges: 1.0-5.0 pF to 25-500 pF
- Q to 5000 at 1 MHz
- Operating temp:
PTFE, Polycarbonate, Polyimide: -40° to +85°C
Polypropylene: -40° to +70°C
High temp PTFE: -40° to +125°C
- 6 sizes from 5 mm to 16 mm
- More stable with temperature than other single turn trimmers


Phone, fax or write today for
Engineering Bulletin SG-402E.

**SPRAGUE
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 13

SIEMENS

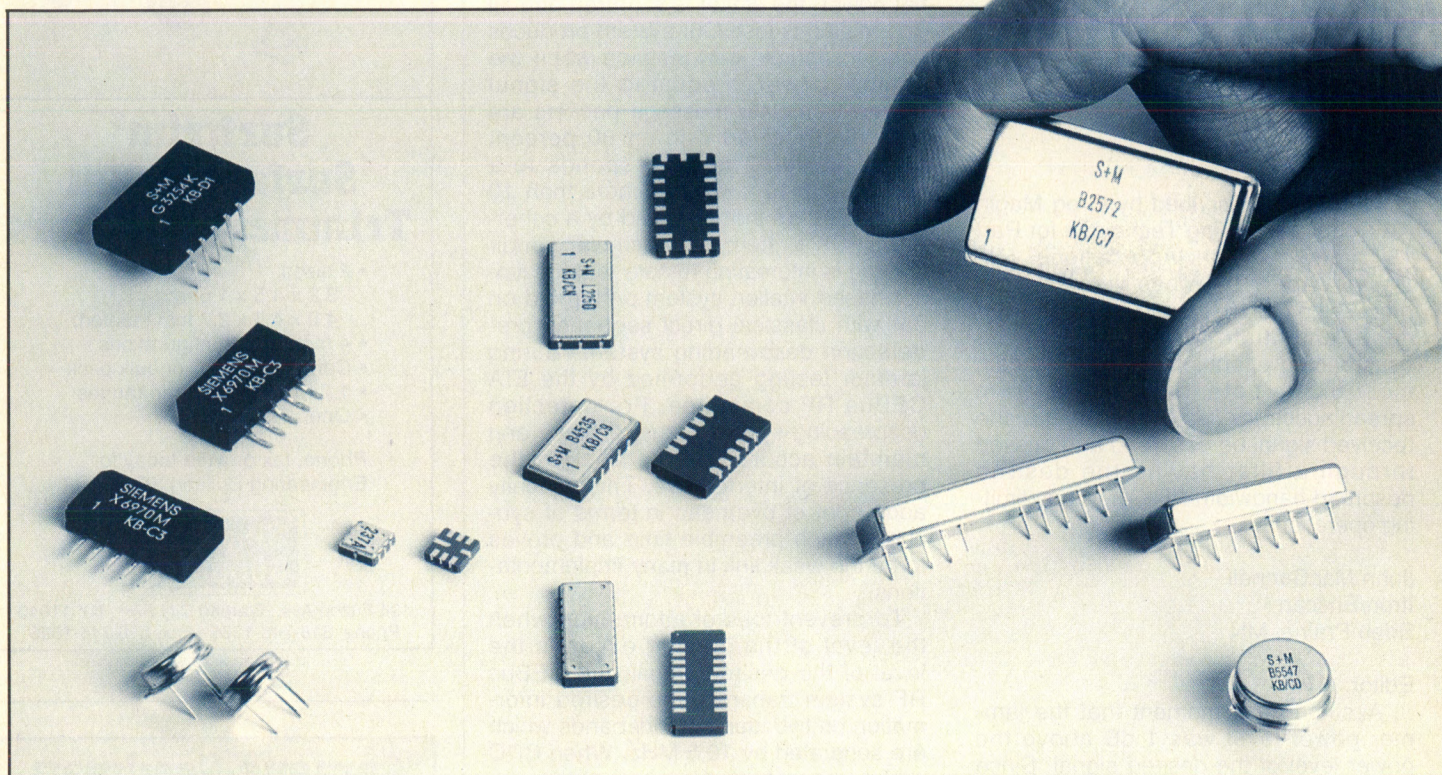

Reach for selection in SAW devices.


Specify Siemens for SAW filters and resonators.

Specify Siemens for a wide selection of SAW filters and resonators from 30MHz to several GHz. Siemens standard and custom SAW devices offer these key advantages:

- Wide package selection: plastic, metal, and surface mount.
- Low insertion loss.
- Precise amplitude and phase characteristics.
- Low temperature drift.
- Excellent reliability and high-volume reproducibility.

For your most demanding applications, select from a broad Siemens line that includes:

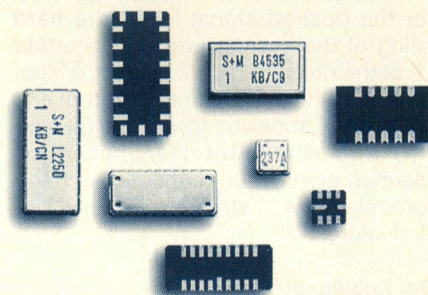- RF and IF Filters for mobile and cordless phones.
- Single and Dual Bandpass Filters for satellite receivers.
- Spectrum Shaping and Clock Recovery Filters for digital communication.
- Vestigial Sideband Filters for CATV equipment.
- Resonators for keyless entry and security systems.
- Inter-carrier and Split Sound Filters for TVs.



Siemens has produced 200 million SAW devices – your assurance of product consistency and delivery for high volume applications.

Call: Siemens Components, Inc.
for literature or technical assistance: 1-800-888-7729

RF calendar

August

2-5 International Microwave Conference
Sao Paulo, Brazil
Information: Paulina Cardoso, IMT-Escola de Engenharia Maus, Estrada das Lagrimas, 2035, 09580 S. Caetano do Sul - SP, Brazil.

9-13 IEEE International Symposium on Electromagnetic Compatibility
Dallas, TX
Information: Dr. Frederick M. Tesche, c/o International Compliance Corporation, 1911 E. Jeter Rd., Argyle, TX. Tel: (817) 491-3696. Fax: (817) 491-3699.

17-20 Sixth Workshop on Technical and Scientific Aspects of MST/ST Radar
Chung-Li, Taiwan
Information: Professor Shin-Yi Su, Chairman, Local Committee, NSC Chung-Li Instrument Center, National Central University, Chung-Li, Taiwan, R.O.C. Tel: (886) 3-4227151 ext 5750. Fax: (886) 3-4255535 and (886) 3-4224394.

18-21 IEEE 1993 International Geoscience and Remote Sensing Symposium (IGARSS '93)
Tokyo, Japan
Information: Mr. Natsuhiko Motomura, Remote Sensing Technology Center of Japan, 7-15-17 Roppongi, Minato-ku, Tokyo 106, Japan. Tel: +81-3-3403-1761. Fax: +81-3-3403-1766.

18-21 International Symposium of Radio Propagation (ISRP '93)
Beijing, P.R. China
Information: Prof. Zong Sha, China Research Institute of Radiowave Propagation, P.O. Box 138/93, Xinxiang, Henan 453003, China.

24-26 Advanced Microelectronic Qualification/Reliability Workshop
Denver, CO
Information: Dorothy Kelly, GTS, Inc., 3100 Route 138, Wall, NJ 07719. Tel: (908) 544-3231. Fax: (908) 389-3992.


25-2 XXIV General Assembly of the International Union of Radio Science (URSI)
Kyoto, Japan
Information: Prof I. Kimura c/o Osaka Office, Business Center for Academic Societies of Japan, 10th Tabuchi Bldg, 6-3 Matsugaecho, Kita-ku, Osaka 530, Japan. Tel: (81) 6-356-6041. Fax: (81) 6-356-6190.

30-3 European Conference on Circuit Theory and Design
Davos, Switzerland
Information: Prof. J. Neiryneck or Mrs. Renate Agotai. Tel: (41) 1-256-51-93. Fax: (41) 1-262-08-23.

September

6-9 23rd European Microwave Conference and Exhibition
Madrid, Spain
Information: Microwave Exhibitions and Publishers, 90 Calverley Road, Tunbridge Wells, Kent TN1 1BR, England.

25 WATTS RF POWER 1-500 MHZ.

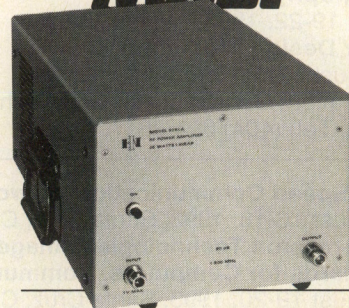

**NEW, ALL SOLID STATE
AMPLIFIER WORKS INTO
ANY LOAD IMPEDANCE.**

The 525LA is an extraordinarily versatile source of power that will find wide application in virtually all RF labs. Covering the frequency range of 1 to 500 MHz, with a flat 50 dB of gain, the 525LA is driven to its full Class A linear output by any signal or sweep generator.

Like all ENI amplifiers, the 525LA features unconditional stability, absolute protection from overloads, and it will work into any load impedance. So if you need a rugged source of RF power for RFI/EMI, RF transmission, component testing, NMR or transmitter design, the 525LA amplifier could just be the most useful tool in your laboratory.

For more information, or a full-line catalog, contact us at:

ENI
A Division of Astec America, Inc.
**100 Highpower Road,
Rochester, NY 14623-3498
(716) 427-8300
Telefax: (716) 427-7839**

ENI

RF courses

Basic Radar

July 13-15, 1993, Atlanta, GA

Near-Field Antenna Measurements and Microwave Holography

July 19-22, 1993, Atlanta, GA

Radar Design Workshop

August 17-19, 1993, Atlanta, GA

Information: Georgia Institute of Technology, Continuing Education. Tel: (404) 894-2547.

High-Speed Communication Networks

August 16-18, 1993, Santa Cruz, CA

Compression Technologies: Image, Video & Associated Standards for Computers, Communications & Consumers

August 19-20, 1993, Santa Cruz, CA

Information: University of California Extension, Santa Cruz, Tel: (408) 427- 6600. Fax: (408) 427-6608.

RF Circuit Components: Measurements, Models and Data Extraction

July 12-16, 1993, Oxford, UK

August 16-20, 1993, Los Angeles, CA

RF Circuit Design: Passive and Active Linear Networks

August 24-27, 1993, Los Altos, CA

RF Design: Nonlinear Circuits and Devices

August 30-Sept 2, 1993, Los Altos, CA

Information: Besser Associates, Tel: (415) 949-3300. Fax: (415) 949-4400.

Finite Element and Finite Difference Time Domain Methods for Solving Electromagnetic Engineering Problems

July 19-21, 1993, Worcester, MA

Electromagnetic Compatibility and Interference

September 14-17, 1993, San Diego, CA

Information: Southeastern Center for Electrical Engineering Education, Kelly Brown - Registrar. Tel: (407) 892-6146. Fax: (407) 957-4535.

Inherently Conductive Polymers: An Emerging Technology

September 8-10, 1993, Boston, MA

Information: Advanced Polymer Courses, Dr. M. Aldissi. Tel: (802) 655-2121. Fax: (802) 655- 2025.

Wavelet Transform: Techniques and Applications

August 9-11, 1993, Los Angeles, CA

Data, Speech, Image and Video Compression: Principles, Applications and Standards

August 9-13, 1993, Los Angeles, CA

Active and Passive RF Components: Measurements, Models, and Data Extraction

August 16-20, 1993, Los Angeles, CA

RF and High Speed Digital Circuit Components: Measurements, Models and Data Extraction

August 16-20, 1993, Los Angeles, CA

Wireless Personal Communications Services

September 15-17, 1993, Los Angeles, CA

Information: UCLA Short Course Program Office. Tel: (310) 825- 1047. FAX: (310) 206-2815.

WBE

Circle INFO/CARD #125 FOR CATALOG AND PRICE LIST

IMPEDANCE CONVERTERS

The A65 Series uses a specially designed, individually tuned broadband transformer for converting 50 ohms to 75 ohms or 75 ohms to 50 ohms with virtually no loss (.15 dB typical).


This device replaces the conventional MLP (minimum loss pad) where extra padding is unnecessary. Model A65 is frequently attached directly to a 50 ohm test instrument for use in a system requiring a 75 ohm impedance. The unit is also valuable when attached to both ports of a device under test of opposite impedance than the measuring system. When the A65 series is substituted for two resistive MLPs on each end of a two port device or on both generator and detector, a gain of approximately 11 dB is added to the circuit.

MINIMUM LOSS PADS

MLP Series is a resistive minimum loss pad (MLP) for converting 50 and 75 ohm equipment. This is essential for direct connection to the "device under test" for critical impedance mismatch isolation. It provides accurate and repeatable through loss and gain measurements. Available as standard value of 5.7 dB or other values such as 6.3 dB for RF Bridge Suppression.

ATTENUATOR PADS

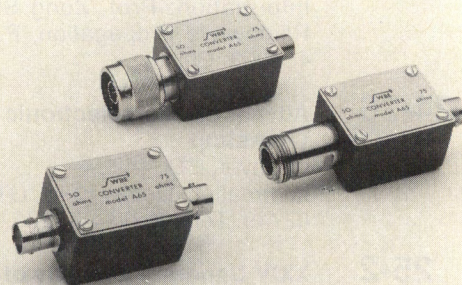Matching attenuator pads are available by special order for any value from 0-40 dB.



Model	Freq. Range MHz	VSWR	Loss dB	Power	Price (BNC conns.)
A65	1-500	1.2:1 max. 1-500 MHz 1.05:1 max. 2-500 MHz	.25 max. .8-500 MHz .16 max. 5-500 MHz	5 W cw	\$50.00
A65GA	1-500	1.2:1 max. 1-500 MHz 1.03:1 max. 5-500 MHz	.25 max. 1-500 MHz .16 max. 5-500 MHz	5 W cw	63.00
A65L	.05-200	1.2:1 max. .05-250 MHz 1.05:1 max. .1-200 MHz	.35 max. .020-200 MHz .15 max. .05-100 MHz	5 W cw	63.00
A65U	1-900	1.1:1 max. 2-900 MHz 1.05:1 typical 10-900 MHz	.5 max. 1-900 MHz	5 W cw	75.00

Model	Freq. Range MHz	VSWR (Return Loss)	Loss (dB)	Loss Flatness	Power	Price (BNC conns.)
MLPV	0-500	1.05:1 max. (32 dB min)	5.7 nominal	±.1 dB max.	.25 W cw	\$45.00
MLPU	0-900	1.05:1 max. (32 dB min)	5.7 nominal	±.2 dB max.	.25 W cw	75.00

WIDE BAND ENGINEERING COMPANY, INC.

P.O. BOX 21652, PHOENIX, AZ 85036

TELEPHONE/FAX: (602) 254-1570

Bit-Error Rate Tests With Variable E_b/N_o

High data rates and high reliability are of utmost importance in modern digital communication systems. BER versus E_b/N_o or BER versus $(C_o + N_o)/N_o$ is used as a quantitative quality factor when evaluating products, testing data links to determine if they will sustain higher data rates, and in verifying performance of digital communication systems on-site or in production.

BER versus E_b/N_o curves can be generated easily with a precision noise generating instrument and a BER tester that is often built into digital communication equipment.

The E_b/N_o of an RF, microwave, or fiber-optic digital communication system can be adjusted either before or after downconversion to an intermediate frequency. The procedures using Noise Com's UFX-BER Series noise test sets are outlined below.

The total power level is adjusted to the level specified by the receiver manufacturer and maintained at this level with a 1 dB (or 0.1 dB) step attenuator. The signal carrier power can be kept constant by passing the signal through a linear automatic gain controlled (AGC) amplifier. The amplifier must be fast enough to compensate for the fading encountered in RF and microwave links. The carrier power level is then set with the instrument's built-in precision step attenuator.

A precise calibrated amount of White Gaussian noise is injected at an IF, RF, or microwave frequency in the receiver or communications channel. The injected noise power level is adjusted only when necessary to maintain constant total power.

The instrument's built-in power meter assists in setting the carrier and the total power levels as well as performing a test of the noise level and attenuator settings.

The signal plus injected noise is now fed into the receiver's RF or IF input, and the BER is measured at 1 different settings of E_b/N_o with the total power level kept constant. The E_b/N_o is a function of the bit rate, carrier power, and noise level as shown in the following equation:

$$E_b/N_o(\text{in dB}) = C(\text{in dBm}) - N_o(\text{in dBm/Hz}) - 10\log(f_b)$$

where:

f_b is the transmission bit rate
 N_o is the noise spectral density
 E_b is the bit energy
 C is the carrier power

A correction factor for the noise level must be applied when the added noise level approaches the noise floor of the receiver:

$$E_b/N_o(\text{in dB}) = C(\text{in dBm}) - 10\log(N_i) - 10(f_b) - 10\log(1 + F \times k \times T/N_i)$$

where:

N_i is the injected noise spectral density generated by the noise test set (in mW/Hz)
 T is the room temperature (in degrees K)
 F is the noise factor at the injection point of the receiver
 k is Boltzmann's constant = 1.380×10^{-23} J/K

If this correction is not added, the BER will be larger, a worst case value, than the result of a corrected measurement.

$(C_o + N_o)/N_o$ is related to E_b/N_o as follows:

$$(C_o + N_o)/N_o(\text{in dB}) = 10\log[(10^{(E_b/N_o + 3)/10}) + 1]$$

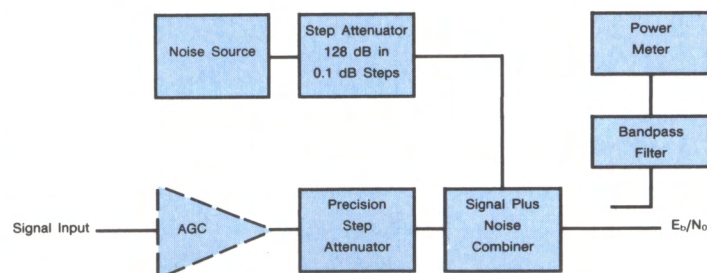


Figure 1. IF Noise Test Set for BER Vs E_b/N_o Measurements.

Noise Com's UFX-BER Series will automatically make this correction and display the actual E_b/N_o or $(C_o + N_o)/N_o$ once the transmission bit rate, f_b , room temperature (T), and receiver noise figure, $NF = 10\log(F)$, have been entered.

Turn the page for related products . . .

E_b/N_o Noise-generating Instruments for Bit Error Rate Testing

UFX-BER Series

General Specifications

Carrier Path

Attenuation	0 to 60 dB, automatically programmed
Range of carrier input power (C_{in})	-45 to +15 dBm
Flatness	± 0.20 dB for 70 MHz (± 20 MHz) ± 0.30 dB for 140 MHz (± 40 MHz)
Group delay	0.20 ns or less

Output Path

Range of carrier output power	-45 dBm to carrier input level
Range of noise output power (N)	-45 dBm to +5 dBm
Noise flatness	± 0.50 dB or less from 100 kHz to 200 MHz
Accuracy of C/N	See graph
Third-order intercept point	+29 dBm typical
Crest factor (peak to average noise voltage)	14 dB or more

Features:

- Direct display of E_b/N_o or C/N
- Accuracy of 0.21 dB RSS
- 75 ohm impedance BNC connectors
- Variable output power

The UFX-BER Series of noise-generating instruments display the actual E_b/N_o or C/N for testing of satellite communications or digital radio equipment. The UFX-BER generates and measures E_b/N_o for IF back-to-back or loop-back testing with extreme precision over a broad range of input or output power, steps, increments, decrements, and desired E_b/N_o values can be entered directly in dB in 0.25 dB increments from the front panel or by IEEE-488 bus.

Settings are stored in non-volatile memory and the user can create up to eight test routines (including delay time and loops) that will run automatically under program control. The instrument measures 5 1/4 in. high, 17 in. wide, and 20 in. deep and comes with brackets for 19-in. rack mounting.


Options:

1. Automatic gain control amplifier to maintain constant carrier power level
2. Other custom configurations
3. 50-ohm input and output impedance instead of standard 75-ohm impedance
4. RS-232C, RS-422, or RS-423 interface in addition to IEEE-488 interface
5. 220 VAC, 50 Hz, instead of standard 110 VAC, 60 Hz
6. Interferor input
7. Switched filter bank with up to six customer-specified filters



UFX-BER SERIES

MODEL	CENTER FREQUENCY	BANDWIDTHS
UFX-BER-455	455 kHz	Filters are customer specified
UFX-BER-10	10.7 MHz	
UFX-BER-21	21.4 MHz	Maximum bandwidth 200 MHz
UFX-BER-45	45 MHz	
UFX-BER-70	70 MHz	
UFX-BER-140	140 MHz	
UFX-BER-IF1	70 MHz, 140 MHz	
UFX-BER-___	User Specified	

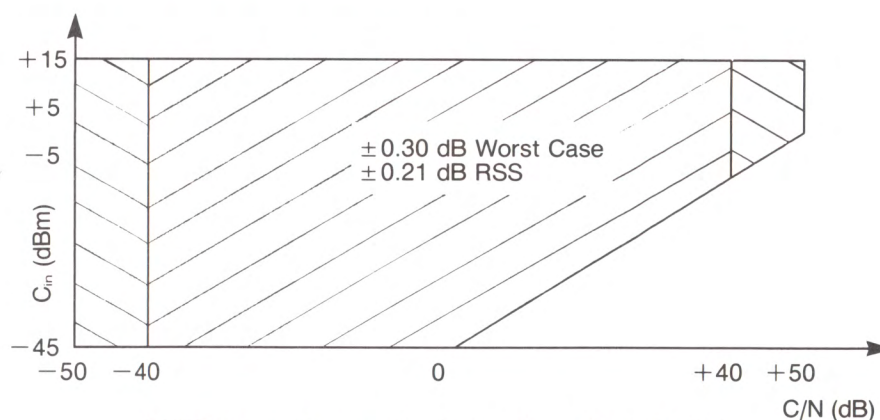

C/N Accuracy Versus Carrier Input Level at $23 \pm 3^\circ\text{C}$

NOISE/COM

E. 49 Midland Avenue, Paramus, New Jersey 07652
(201) 261-8797 • FAX (201) 261-8339

Canada Establishes Digital Radio

The Canadian Broadcasting Corporation (CBC) and the Canadian Association of Broadcasters (CAB) recently announced the formation of a new corporation, Digital Radio Research Inc. (DRRI) which will launch experimental digital radio service in Canada by late 1993. The DRRI will build and operate a number of transmitting installations to be used for digital radio research and development, and commission and publish research studies on digital radio broadcasting technology. The initial sites of the prototype stations will be in Montreal and Toronto. They will operate on the 1.5 GHz band (L-band) and begin broadcasting before the end of the year by using new or existing programming from the CBC and private broadcasters and converting it to digital form.

U.S. and Japanese Engineer Exchange Program — The U.S. Commerce department has announced a program to place U.S. engineers in Japanese manufacturing firms for up to one year. The goal of the Manufacturing Technology Fellowship project is to help U.S. engineers learn more about — and then use — Japanese manufacturing practices and to promote long-term professional exchanges with the Japanese. Fellowships will last about 15 months, including three months of intensive Japanese language and culture training in the United States. That will be followed by up to 12 months of hands-on manufacturing experience in Japan. U.S. participants will learn about Kanban, Just-In-Time manufacturing, Total Quality Control and other Japanese-inspired techniques as they are used in Japan.

Candidates must be U.S. citizens or permanent residents currently employed in manufacturing at an American company. They must have at least two years of manufacturing experience and long-term goals in manufacturing. For more information about the program or to receive an application, potential candidates should contact: The U.S. Japan Manufacturing Technology Fellowship Program, c/o Japan Technology Program, Room 4817, U.S. Department of Commerce, 14th St. and Constitution Ave., N.W., Washington, DC 20230. Tel: (202) 482-0356. Fax requests are encouraged at (202) 482-4826. Applications are due no later than July 16, 1993.

NIST Publication Available — A new NIST publication, *Measurements for Competitiveness in Electronics* (NISTIR 4583), identifies those currently unmet measurement needs most critical for the U.S. electronics industry to compete successfully worldwide. Nine fields of electronics are covered: semiconductors, magnetics, superconductors, microwaves, lasers, optical-fiber communi-

cations, optical-fiber sensors, video and electromagnetic compatibility. Each field's section contains a technology review, an overview of economic importance to the world market, a look at U.S. industry goals for competing internationally and a discussion of measurements needed to meet those goals. NISTIR 4583 is available for \$52 (print) and \$19.50 (microfiche) prepaid from the

While Others Make Noise About Their RF Amps, We Quietly Prove Our Quality

Q-bit quality means:

- guaranteed gain windows, • guaranteed 2nds and 3rds.
- guaranteed performance for every operating parameter over a full temperature range.


Q-bit's proven designs and our patented Power Feedback™ technology yield low VSWR, flat gain response, high reverse isolation and unconditional stability. These thirteen Q-bit Corporation amplifiers are direct replacements* for more than sixty standard catalog amplifiers of five competitors.

Guaranteed -55°C to +85°C Performance

Model Number	Frequency Range (MHz)	Gain (dB)	1dB Compression (dBm)	Noise Figure (dB)	Reverse Isolation (dB)	Output Intercept 3rd/2nd (dBm)	Power (V/mA)	Price For Quantity
QBH-101	5-500	13.0	6.0	3.0	24.0	18/25	15/19	\$75
QBH-102	5-500	12.3	21.0	7.5	22.0	32/48	15/95	\$85
QBH-107	5-550	14.8	-1.0	2.8	25.0	8/12	15/10	\$85
QBH-110	5-500	15.0	9.0	3.5	25.0	22/32	15/31	\$90
QBH-119	5-500	15.0	11.0	3.3	25.0	24/33	15/34	\$95
QBH-120	5-500	14.5	1.0	2.3	26.0	13/17	15/11	\$95
QBH-122	10-500	17.0	19.0	4.6	22.0	24/32	15/65	\$110
QBH-126	5-500	15.0	15.0	4.2	24.0	28/34	15/54	\$95
QBH-155	5-300	15.0	21.0	6.4	28.0	36/48	15/95	\$65
QBH-183	5-1100	10.3	14.0	6.5	12.0	27/38	15/72	\$80
QBH-184	5-1000	14.8	10.0	5.0	17.0	24/33	15/31	\$85
QBH-815	5-1000	11.4	20.5	8.0	12.5	30/45	15/98	\$95
QBH-822	10-2000	20.0	10.0	6.0	24.0	23/34	15/60	\$162

*Meets or exceeds published specifications

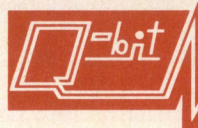Call us for a catalog available on a PC compatible data disk.



Q-bit Corporation

2575 PACIFIC AVENUE NE, PALM BAY, FL 32905

TELEPHONE (407) 727-1838

TWX (510) 959-6257 • FAX (407) 727-3729

INFO/CARD 17

National Technical Information Service, Springfield, VA 22161. Tel: (703) 487-4650. Order by PB 93-160588.

Russian Company Enters Western Market — Svetlana Electron Devices Manufacturing Corporation has announced that they will market their power grid and modulator electron tubes in the United States and other Western

countries. Svetlana power grid tubes will be sold through Svetlana Electron Devices, Inc. Svetlana is Russia's largest power grid and modulator tube manufacturer. They will introduce tube types widely used in Russia but new to Western equipment designers and will also provide exact replacement, plug-compatible Western tube types. For more information contact Svetlana Electron De-

vices, Inc., 3000 Alpine Road, Portola Valley, CA 94028. Tel: (415) 233-0429.


Potential Standard for Wireless LANs

— National Semiconductor recently proposed an open standard for Wireless LANs to foster interoperability between equipment offered by a wide variety of vendors. There are currently several Media Access Control (MAC) submissions before the IEEE 802.11 wireless LAN committee. One leading submission is a "Reservation-Based" MAC protocol based on a repetitive constant length frame which can support "isochronous" LAN traffic for voice and video. Another submission is the "Hybrid" Carrier Sense Multiple Access with collision Avoidance (CSMA/CA) protocol. The Unified MAC submission from National Semiconductor is based on major elements of both protocols. They are proposing a simple physical layer interface (PHY) description that partitions the synchronization, timing, and control functions on the MAC side of the service interface. This provides for a simple command set for the control of the radio side of the PHY to drive down both cost and power consumption.

Call For Papers — The Technical Program Committee of the Third International Conference on Multichip Modules, scheduled for March 29-31, 1994 in Denver, Colorado has issued a call for papers. The conference and exhibition is organized and sponsored by the International Electronics Packaging Society and the International Society of Hybrid Microelectronics. Topics being sought include: international and domestic applications, design and test, assembly and interconnections, materials, yield and reliability, processing MCM design and implementation, MCM/PCB interface, structure type, management and cost strategies, memory management, electrical and thermal performance, changes and change technology, telephone and cellular applications. Six copies of a 150 word abstract should be sent by November 1, 1993 to ISHM, 1861 Wiehle Ave., Suite 260, Reston, VA 22090.

"Clipper Chip" Developed for Communications Security

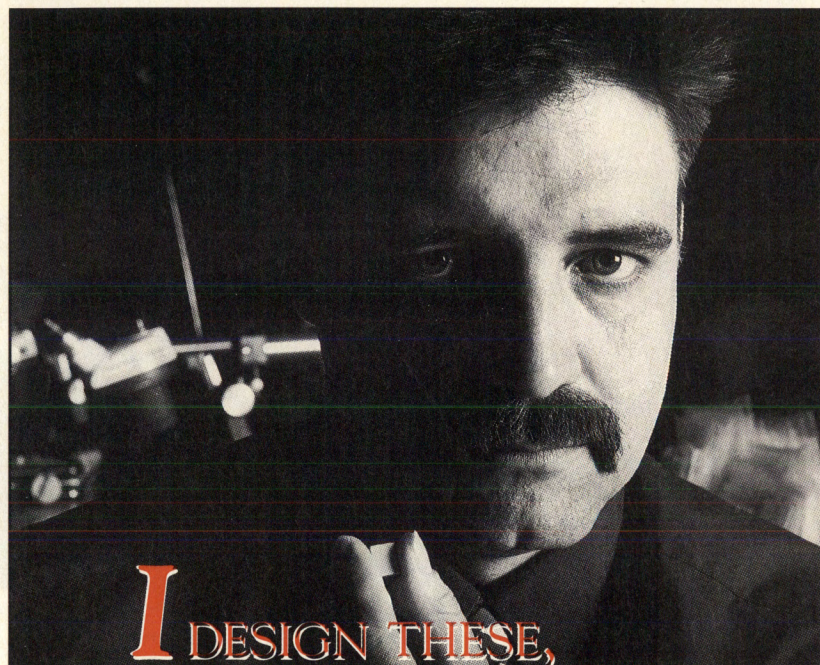— The National Security Agency with NIST assistance has developed the state-of-the-art "Clipper Chip" which can be used in new, relatively inexpensive encryption devices that can be attached to telephones. The microcircuit scrambles communications using a power encryp-



and **I** make sure they're built right. If anything goes wrong I take it **very** personally. A while back I decided that we were having more long term failures than we should. No more than anybody else in the business, but still... it wasn't right. So, I developed a new test that gets us fewer long-term failures than anyone around, under four per million device hours.

I'm convinced we're the better supplier for your porcelain chips, so I've put together a package with our new test data that will convince you too. Don't take my word, call and check it out for yourself.



Ultra Hi Q

You need more information, or have a problem - talk to me! I'm sitting right next to the production line so I can get you the answer you need, fast. Like I said, I take this **very** personally.

Ask for me, Mark, 315-655-8710, and I'll send you our test data and sample kit.

The best quality control is the right attitude.



**dielectric
laboratories
inc.**

Cazenovia, NY 13035
Tel: 315-655-8710
FAX: 315-655-8719



If you think the best RF Power Modules come from Japan, we'd like to re-orient you.

A lot of good things come from the "land of the rising sun"—like VCRs, hi-fi audio equipment and sushi. But when it comes to RF devices, specifically small amplifier assemblies called "modules" for use in cellular radios, the best source is right here in the good'ol USA. You got your first power modules for analog cellular radio from Motorola—now get your first power modules for digital cellular radio from the same source!

Motorola is proud to announce the first linear power modules, **MHW926** and **MHW927A/B**, for use in the United States Digital Cellular (USDC) radio system. Each module supplies 6 watts of average power, operates from 12.5 volts, and has the standard features of 50 ohm input and output impedance, stability, ruggedness, low harmonics and wide dynamic range in output control. The MHW927A/B require only 1 mW of RF input power, while the MHW926 requires 65 mW. Linearity is indicated by a 3rd order intermodulation distortion (IM3) specification of -29 dBc. A bias voltage of 9.5 volts is required for both the MHW926 and MHW927A, while the MHW927B requires a bias voltage of 8.0 volts.

Pioneers Then and Now!

Motorola was the first company to offer modules for mobile and cellular radios, having introduced modules for the 900 MHz cellular systems in the USA (AMPS) and in Europe (NMT) in the early 1980s. Last year we announced a complete line of linear

Check Out These Features:

- Frequency—824-849 MHz
- Output Power—6 W Avg.
- Input/Output Impedances of 50 ohms
- Supply Voltage—12.5 Vdc
- Bias Voltage—9.5 Vdc—MHW926 & MHW927A
8.0 Vdc—MHW927B
- Input Power—18 dBm Max. for MHW926
0 dBm Max. for MHW927A/B
- Harmonics—-30 dBc Max for 2Fo
- Package—301AB-01 for MHW926
301AA-01 for MHW927A/B

modules for the digital cellular system in Europe (GSM). With the introduction of these linear UHF silicon bipolar modules, along with our recently introduced UHF GaAs FET power modules, we're proud to say we're continuing to take giant steps in cellular technology.

Whether you need tens, hundreds or thousands of modules, Motorola offers you repeatable performance from unit to unit. Plus quality, delivery and service you can depend on. So why go all the way to Japan for the Power Modules you need? Reorient yourself to an American pioneer in mobile and cellular radio technology—Motorola.

For more information on Motorola's **MHW926** and **MHW927A/B** power modules, request RF Products Data Sheet MHW926/D and Selector Guide SG46/D by calling 1-800-441-2447, by sending the coupon below, or by writing Motorola Semiconductor Products, P.O. Box 20912, Phoenix, AZ 85036.



MOTOROLA

Motorola and (M) are registered trademarks of Motorola Inc.

To: Motorola Semiconductor Products, Inc., P.O. Box 20912, Phoenix, AZ 85036

Please send me the RF Products Data Sheet MHW926/D and Selector Guide SG46/D.



Name 595RFD070093

Title

Company

Address

City State Zip

Call Me ()

tion algorithm. Each device containing the chip will have two unique "keys" that must both be used to decode messages. "Key escrow" agents will retain the keys and provide access only to government officials with legal authorization to conduct a wiretap. Companies and individuals will gain protection for proprietary and private information, while law enforcement agencies will still be able to lawfully intercept the phone conversations of criminals. NIST is working on a standard to facilitate federal government procurement and use of the "Clipper Chip."

British Association for Low Power Radio Devices — The Low Power Radio Association is a British group that was "formed to promote the responsible use of low power radio equipment and to act as a channel of communication between the Radiocommunications Agency and LPRA members." Their primary focus is on devices that operate at short range and with less than 500 mW power. Application areas include RF data communications,


telemetry, video/audio, telecommand, wireless local area networks, alarms, RFID, telemonitoring, radio microphones and teleapproach. For more information about the association contact: LPRA Secretariat, The Old Vicarage, Haley Hill, Halifax, HX3 6DR, United Kingdom. Tel: (44) 0422 359161. Fax: (44) 0422 355604.

Electrical Engineering Scholarship Established — Telecommunications Techniques Corporation has established the Joseph A. Sciulli Memorial Scholarship to be awarded to a student majoring in electrical engineering entering the University of Maryland at College Park. The scholarship will be awarded to a Maryland resident entering the Engineering Department based on financial need, scholastic excellence in math and science, leadership, and work ethics. The scholarship program, including the selection process, will be administered by the University of Maryland's College of Engineering. An optional summer internship at TTC will enable the student to get hands-on experience.

Epitronics Awarded Contracts — Epitronics recently announced they were awarded an ARPA SBIR Phase I contract to investigate Indium Phosphide based device structures for microwave and millimeter wave monolithic integrated circuits and a subcontract with Ware Technical Services, Inc. to deposit strain-free epitaxial layers on indium gallium arsenide substrates.

New RF Tags Unique to Industry — Lanex Corporation recently announced the availability of an active RF tag that is unique to the industry because of its long range, low cost and ability to read multiple tags in a designated field of reception. The Locator, using state-of-the-art technology is detectable from 40 to 50 feet away from the reader and sells for \$32 in small quantities. The tag system can be used for security management, inventory and process control solutions and is compatible with most host systems or can be used in a stand alone version. The Locator contains a receiver and transmitter that are powered by a miniature lithium

CRYSTAL FILTERS

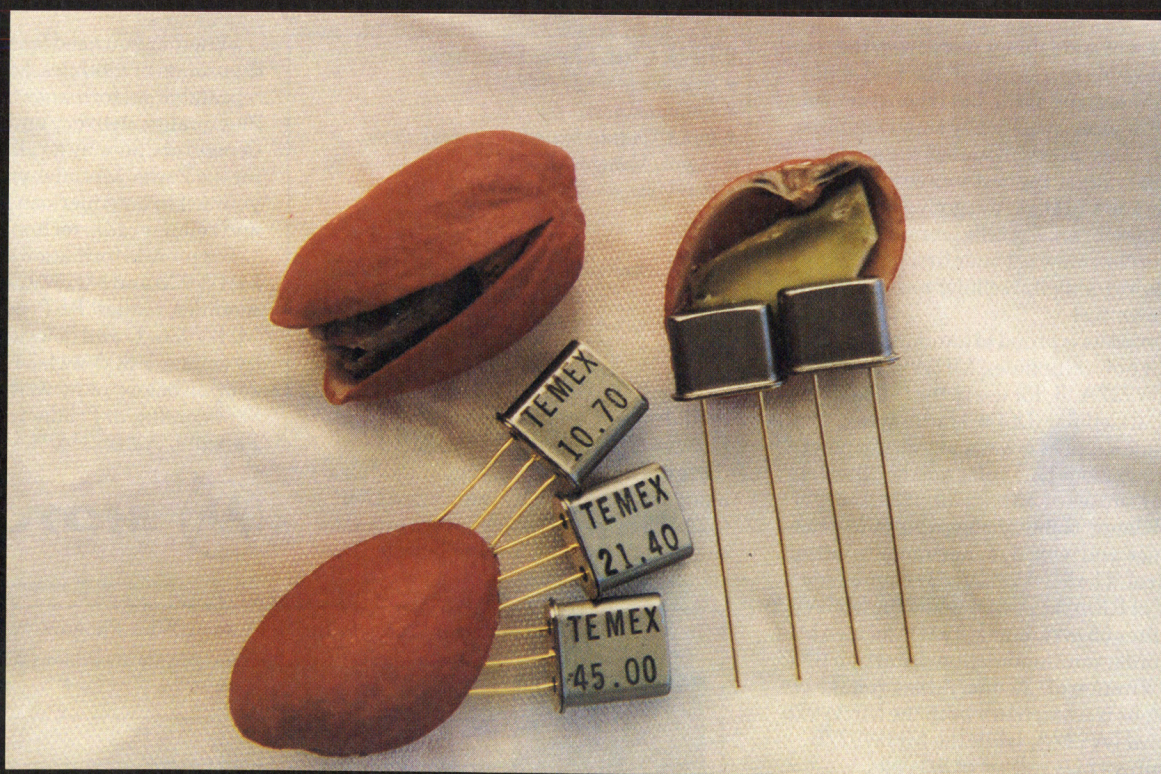

TEMEX ELECTRONICS

3030 W. Deer Valley Road Phoenix, AZ 85027 (602) 780-1995 FAX: (602) 780-2431

ANY KIT

\$99⁰⁰

OR LESS



CALL: 1-800-PENSTOCK (408) 730-0300
FOR OVERNIGHT DELIVERY ON TOKO PROTOTYPING KITS

Fixed Inductors \$99⁰⁰ LL Chip Inductors \$49⁰⁰
Surface Mount Inductors \$99⁰⁰ 5MM Surface Mount Coils \$99⁰⁰
5MM Coils \$59⁰⁰ 7MM Coils \$59⁰⁰ 10MM Coils \$59⁰⁰ Molded Coils \$59⁰⁰



TOKO

PENSTOCK
 RF/MICROWAVE DISTRIBUTION

battery with a life expectancy of 10 years. Communications are achieved by the reader transmitting a low frequency signal and receiving a high frequency one.

Garbage Collection Goes High-Tech

— The city of Edmond, Oklahoma recently began replacing garbage cans with new 105 gallon waste bins, each of which is equipped with a small radio frequency transponder from Texas Instrument TIRIS™ division. Each passive transponder contains a unique identification code, which allows electronic readers to accurately identify the bin's owner. Fully-automatic trucks lift the plastic household waste bins, identify the owner, weigh and empty the garbage, place the bin back on the sidewalk and later download the information, allowing the owner to be billed based on the garbage's weight.

Aviel Electronics Relocates

— Aviel Electronics has announced its new address. They are now located at: Aviel Electronics, 5530 South Valley View,

Suite 103, Las Vegas, NV 89118. Tel: (702) 739-8155, 8157. Fax: (702) 739-8161.

HK Microwave Changes Name and Relocates

— HK Microwave recently announced that it has changed its name to Dynatech Spectrum, Inc. and has relocated the company from Santa Clara to Milpitas, California. The decision on the name change was made to give a closer association with the company's product lines and their markets. Their address is now 100 S. Milpitas Blvd., Milpitas, CA 95035. Tel: (408) 956-9570. Fax: (408) 956- 9595.

EEsof Forms Strategic Alliance

— EEsof, Inc. has announced the formation of a long-term strategic alliance with STEP Electronics to exclusively distribute and support EEsof products throughout the Pacific Rim and other parts of the world. STEP employees are currently undergoing extensive training in the sale and support of the full range of EEsof products for workstations and PCs.



General Microwave Awarded Contract

— General Microwave Corporation recently announced that it was awarded a \$2.2 million contract by BMY Combat Systems for the development of a microwave Terrain Mapping Sensor. The sensor will be integrated into an Automatic Depth Control system for a tank-mounted mine clearing blade. General Microwave will use its patented short range radar technology to develop a system that provides data describing the terrain ahead of the vehicle with a high degree of accuracy.

Stanford Awarded Receiver Assembly Contract

— The ASIC & Custom Products Division of Stanford Telecommunications, Inc. has announced that it has entered into an agreement with Harris Corporation's Information Systems Division to develop a specialized receiver board assembly for use in weather satellite reception. Harris plans to deploy the receiver module in a system which will receive, process, and display real-time weather satellite data.

ROTARY ATTENUATORS

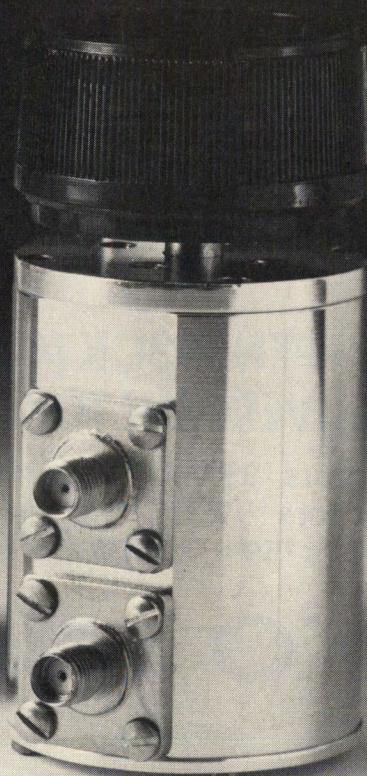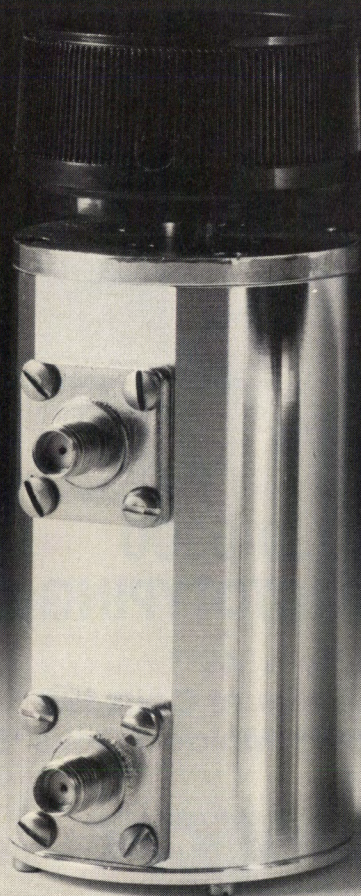

50R-028
DC-1 GHz
0-1 dB in .1 dB Steps

50R-019
DC-2 GHz
0-10 dB in 1 dB Steps

50R-029
DC-2 GHz
0-70 dB in 10 dB Steps

50R-043
DC-1 GHz
0-100 dB in 10 dB Steps

Available in SMA, BNC or TNC Connectors

75 Ohm Rotary Attenuators available



JFW Industries, Inc.
5134 Commerce Square Dr.
Indianapolis, Indiana 46237
317-887-1340
INFO/CARD 22

ULTRA-BROADBAND RF POWER AMPLIFIER SYSTEMS

From KALMUS ENGINEERING, Of Course!



EMI-EMC-RFI

- AC Operation
- Fully Protected
- Drive Mismatched Loads
- No VSWR Shutdown
- ALC Flat Gain Response
- Remote Functions
- Lowest Prices

ALL SOLID-STATE MOS-FET RF AMPLIFIER SYSTEMS

	MODEL	RF OUTPUT	FREQUENCY RANGE	GAIN	USA PRICE
	700LC	1.5W CW	.003-1000 MHz	33dB	\$ 1,695
	704FC	4W CW	.5-1000 MHz	33dB	\$ 2,195
	210LC	10W CW	.008-225 MHz	40dB	\$ 2,495
	710FC	10W CW	1-1000 MHz	40dB	\$ 6,695
	*727LC	10W CW	.006-1000 MHz	44dB	\$ 7,750
NEW	713FC	15W CW	10-1000 MHz	42dB	\$ 4,250
	225LC	25W CW	.01-225 MHz	40dB	\$ 3,295
	*737LC	25W CW	.01-1000 MHz	45dB	\$ 9,995
	712FC	25W CW	200-1000 MHz	45dB	\$ 6,950
NEW	714FC	30W CW	10-1000 MHz	45dB	\$ 9,950
	250LC	50W CW	.01-225 MHz	47dB	\$ 5,250
	715FC	50W CW	200-1000 MHz	47dB	\$ 16,990
	707FC	50W CW	400-1000 MHz	50dB	\$ 9,990
NEW	716FC	50W CW	10-1000 MHz	47dB	\$ 17,950
	*747LC	50W CW	.01-1000 MHz	47dB	\$ 19,500
	116FC	100W CW	.01-225 MHz	50dB	\$ 8,800
	709FC	100W CW	500-1000 MHz	50dB	\$ 16,990
	717FC	100W CW	200-1000 MHz	50dB	\$ 19,500
NEW	718FC	100W CW	10-1000 MHz	50dB	\$ 26,950
	*757LC	100W CW	.01-1000 MHz	50dB	\$ 29,950
	122FC	250W CW	.01-225 MHz	55dB	\$ 14,650
	723FC	300W CW	500-1000 MHz	55dB	\$ 29,995
	LA500G	500W CW	500-1000 MHz	57dB	\$ 53,500

RUGGED VACUUM TUBE DISTRIBUTED AMPLIFIERS

	116C	100W CW	.01-220 MHz	50dB	\$ 9,295
	122C	200W CW	.01-220 MHz	53dB	\$ 11,750
	134C	500W CW	.01-220 MHz	57dB	\$ 19,800
	137C	1000W CW	.01-220 MHz	60dB	\$ 27,550
	140C	2000W CW	.01-220 MHz	64dB	\$ 44,990

Warranty: Full 18 months all parts. Vacuum tubes 90 days.

* Indicates Dual-Band System (coaxial band switching)



1-800-344-3341
(206) 485-9000 fax (206) 486-9657
21820-87th S.E. Woodinville, WA 98072 USA
INFO/CARD 23

**The World's Most Complete
Line of RF Power Amplifiers**

**More Than 200 Standard Models
to Choose From**

A Diverse Market for RF Amplifiers

By Gary Breed
Editor


Companies making medium- and high-power RF amplifiers continue to direct their efforts toward device, design and manufacturing improvements. Current applications include new wireless communications systems in the 900 MHz-2.5 GHz range, but these applications are by no means the sole force driving amplifier development.

The observations of companies manufacturing and selling RF amplifier products suggest that the market is extremely diverse. Each company seems to have identified a specific niche that is providing a good market for its products. Rebuilding commercial communications equipment in the 400 MHz range to handle digital information was identified as a strong market by David London, Director of Marketing for Trontech. "Digital technology is coming on stream rapidly because it is the most efficient way to transfer information," he explains. On a different course is Milcom International, which recently introduced a wideband distributed amplifier providing 50 watts of linear power from 1 to 512 MHz. Among potential customers, Milcom expects this product to reach power semiconductor manufacturers who need improved test system capabilities.

The positive side of this diversity is that the overall market is not subject to the fate of a single large application. However, the negative side is that the market is hard to predict. It is difficult to decide exactly which smaller applications to target, making it hard to anticipate customers' needs. One effect is to shift amplifier sales efforts from specific products to "company capabilities." Rather than speculate on an amplifier line for a specific 1.8 GHz Personal Communications System (PCS) application, an amplifier manufacturer may choose to promote its ability to quickly design and produce amplifiers for a wide range of applications. Response to customers is more important than a catalog full of stock products.

Medium-Power Applications

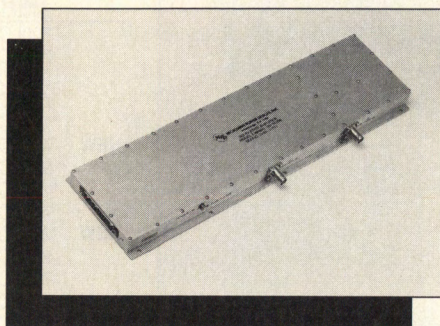Power capabilities in the 0.1 to 10 watt range are rapidly increasing in importance. Formerly reserved for drivers in



New applications include cellular micro-cells, the intended use for this MicroWave Power Devices amplifier.

higher power systems or as final amplifiers in handheld equipment, medium power amplifiers are doing a lot more, especially in receiver applications.

Dynamic range is the problem solved by using a power amplifier in a receiving system. Cellular systems, repeater sites and PCS all require receivers to perform properly in the presence of co-located transmitters. To avoid intermodulation distortion (IMD), the front-end receiver preamplifier must be capable of handling signals varying from the microwatts of received signal from a handheld cellular phone user to watts of power as the cell site transmits another conversation on a nearby channel. The transistors used must also have a low noise figure, to maintain good receiver performance. Companies like Locus, Inc., Trontech, Mini-Circuits and TIW Systems are pursuing this market area, along with several others.

Modular amplifiers for medium power are more common than they were just a few years ago. Q-Bit, Avantek, Cougar Components and Watkins-Johnson are among numerous suppliers of TO-8, connectorized, and flatpack amplifiers. The availability of these amplifiers makes it possible to speed a product's development cycle by using off-the-shelf parts to avoid the time and cost of circuits designed and built from scratch in-house.

New Devices

The search for higher efficiency, low

voltage operation, lower cost and better performance (linearity, noise, etc.) has kept transistor manufacturers busy. Class A efficiency at 1 GHz, for example has improved by over 5 percent over the last few years, and class C amplifiers have seen improvements of 10 to 30 percent, depending on the frequency. Bipolar transistors, silicon FETs and GaAs FETs have all been the subject of research efforts. New buzzwords in power devices are HFET (heterostructure FET), HBT (heterojunction bipolar transistor) and PHEMT (power pseudomorphic HEMT). These technologies represent the current efforts at improving amplifier performance.


Internal matching of RF power transistors has been used extensively at microwave frequencies, but it is now seen at HF and VHF/UHF. One recent addition to this group are two product families from MicroWave Technology. Their SLAM devices (basically, these are power JFETs) include internal resistors to make 50-ohm matched, self-biased class A push-pull power amplifiers with minimal external circuitry. At higher frequencies, their new self-biased GaAs FETs provide 4 to 10 watts in the 500-2000 MHz range. They can be dropped into 50 ohm systems, making them truly amplifiers rather than transistors.

Summary

The technology and applications of RF amplifiers are, unfortunately, much too broad for a short report. This brief look has identified a few trends in amplifier markets and some of the developments in amplifier products. The key word to remember is *diversity*. The market for amplifiers is becoming one of many different specific requirements, with customers requiring a particular set of performance features rather than adapting a standard amplifier to their application.

RF

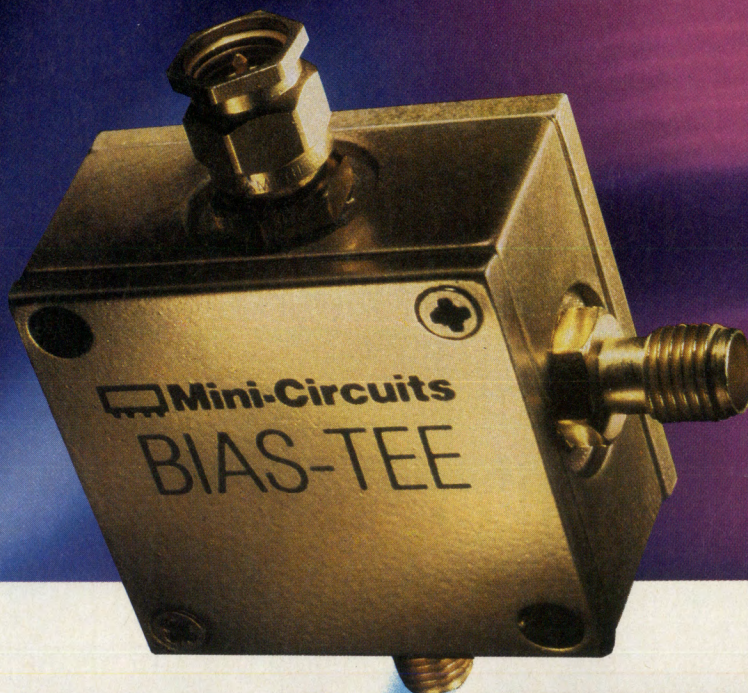For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600. Ask for the Circulation Department.



BIAS TEES

From **\$59⁹⁵**

RF —||— RF+DC

Easily combines RF+DC signals
for your modulation or
test requirements.



Now up to 200mA DC current 100KHz-6GHz

Now you can DC connect to the RF port of an active device, and modulate a laser over a very broad frequency range. Using statistical process control and a patent-applied for technique of combining magnetics and microstrip, large DC currents may pass through the Bias-Tee without saturation and degradation of performance. At 1/3 to 1/4 the price of competitive units, these new Bias-Tees are packaged in an aluminum case, available with SMA connectors. So why wait, solve your connection problems with Mini-Circuits' Bias-Tees. Available from stock.

Model	Freq MHz	Insertion Loss, dB Typ.	Isolation dB (RF)-(DC) (RF+DC)-(DC) Typ.	VSWR Typ.	Price \$ ea.	Qty
	f_l f_u	L M U	L M U			1-9
ZFBT-4R2G	10-4200	0.15 0.6 0.6	32 40 50	1.3:1	\$59.95	
ZFBT-6G	10-6000	0.15 0.6 1.0	32 40 30	1.3:1	79.95	
ZFBT-4R2GW	0.1-4200	0.15 0.6 0.6	25 40 50	1.3:1	79.95	
ZFBT-6GW	0.1-6000	0.15 0.6 1.0	25 40 30	1.3:1	89.95	

L = low range M = mid range U = upper range

finding new ways ...
setting higher standards

Mini-Circuits®

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661
EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.

CUSTOM PRODUCT NEEDS... **Let Our Experience Work For You.**

F164 REV.ORG.

INFO/CARD 24

You don't always get what you pay for.



With PTS synthesizers, you get more.

Because we're synthesizer specialists, we give you *more for your money* in more ways than one.

From our economy PTS x10, to our space-saving PTS 310, to our top-of-the-line PTS 1000, we have *more models* to cover your source needs from 100 KHz to 1 GHz.

And more options, including:

- OCXO, TCXO or external standard,
- choice of resolution from 100 KHz to 0.1 Hz,
- DDS with phase-continuous switching,
- digital phase rotation,
- BCD or GPIB remote control,

and almost a hundred others to let you specify a synthesizer so well-tailored to your requirements that it's like having one custom made for you.

Our priority in design and manufacturing is to make our synthesizers *more reliable*, and this has led to a demonstrated MTBF of 25,000 hours. That's why we can back them with our all-inclusive 2-year warranty, along with a flat-rate service charge for eight years following the warranty period.

But wait, there's less!

All of our synthesizers feature *low power* consumption, *low spurious output* (as low as -75 dBc), *low phase noise*, and fast frequency switching (as fast as 1 μ second).

And all of our models are available, at a lower price, in a remote-only OEM configuration for easy integration into your OEM system.

Our full catalog has all the information you need to specify the most synthesizer for your money.

Call or FAX us for your copy, or for immediate engineering assistance.



PTS

PROGRAMMED TEST SOURCES

P.O. Box 517 Littleton, MA 01460
508/486-3008 FAX 508/486-4495

INFO/CARD 25

A Low Power RF ID Transponder

By Raymond Page
Wenzel Associates

This is the Grand Prize winner in the design category of the 1993 RF Design Awards Contest. This entry exhibited both innovative use of RF technology and an elegant implementation of that technology. The author was awarded a NOISE COM model UFX-BER noise generator for bit error rate testing.

For some time railroad companies have been wrestling with the problem of tracking rail cars. This has traditionally required manual log entry of identification numbers displayed on the cars as they pass through the switching yard. Some years ago, an effort was undertaken to use an optically scanned ID system. Dirt and optical registration problems led to its demise, forcing railroad companies to revert to the manual system. RF engineers have come up with a solution, using transponders mounted on the side of the cars which are read by interrogating transceivers positioned along the track.

Design Considerations

A practical transponder design must include minimal maintenance, a rugged low profile and low cost. The most elusive of these has been low cost. Presented here is a design which meets these requirements along with a brief discussion on the current state-of-the-art in passive RF identification transponders.

An important design constraint is that the transponder require little or no maintenance. Since no power is available from the rail car, the only conventional options are batteries or solar cells that maintain rechargeable batteries. The non-rechargeable batteries require periodic replacement, and the solar cell option would be both expensive and vulnerable to the environment. A passive design eliminates the need for batteries by rectifying energy from the interrogating RF field to power the circuitry.

The harsh environment presented to an RF device mounted on the side of a rail car is a challenging problem. Minimum clearance requirements, dirt, weather, vibration and an extremely large chunk of ferro-magnetic material near the antenna have to be considered. Additionally, the unit should be encapsu-

lated. Microstrip patch antennas have come to the rescue. They afford a low profile and can be made with an ordinary double-sided printed circuit board. The patch antenna is on the top and a ground plane is on the bottom, thereby eliminating the effects of the steel mounting surface.

A Low Cost Transponder

An unusually simple method of converting the interrogating RF field into a data-modulated signal which can be transmitted back to the reader contributes to the low manufacturing cost of this transponder design. The circuit uses only one inexpensive microwave semiconductor (a diode) and allows all parts to be mounted on an FR-4 printed circuit board with the patch antennas (Figure 1). By contrast, other approaches use expensive microwave parts, including SAW devices, oscillators, mixers, filters and amplifiers. Designs involving more RF circuitry tend to be power hungry, requiring increased RF interrogation fields.

Figure 2 shows the block diagram of the low power transponder. A 915 MHz receive antenna powers the rectifier/frequency doubler/AM modulator. It provides a rectified DC source to the MCU which returns data to be AM modulated onto the doubled frequency. An 1830 MHz antenna transmits the modulated

carrier.

A reader, incorporating an unmodulated 915 MHz interrogation transmitter with low (< -60 dBc) second harmonic distortion and an 1830 MHz AM receiver, is placed a relatively short distance away from where the transponder will pass (Figure 3). The amount of transmitted RF interrogation power needed to make the system function properly at a given distance can be estimated by equation 1:

$$P_r = P_t G_t G_r \lambda^2 / (4\pi R)^2 \quad (1)$$

Where P_r is the received power, and P_t is the transmitted power radiated by an antenna of gain G_t . G_r is the gain of the receive antenna, λ is the free space wavelength and R is the distance between transmitters. G_t and G_r are the gains over an isotropic radiator. A sufficient second harmonic return path signal will occur for any combination of power gain and distance capable of energizing the MCU.

One watt of power transmitted with an antenna gain of 31.6 (16 dB) and received with an antenna gain of 2 (3 dB) allows the transponder to function from as far as 20 feet away. This suggests that just over 1 mW is adequate to energize the transponder.

The transponder's surprisingly low

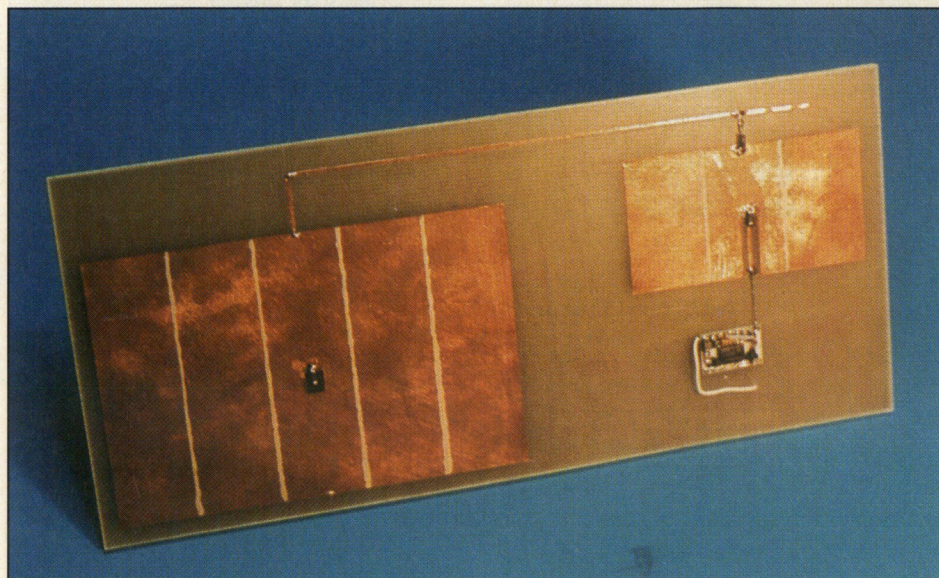


Figure 1. The complete transponder, with the 74AC00 test oscillator.

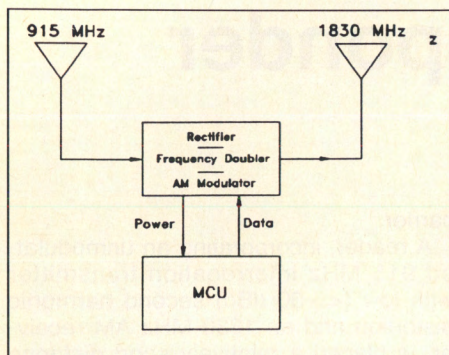


Figure 2. Block diagram of the passive transponder.

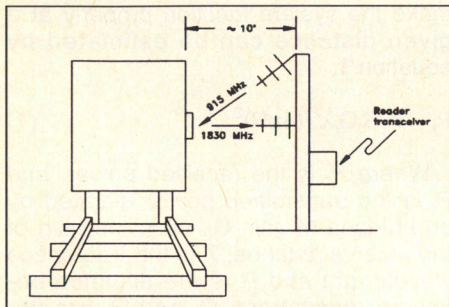


Figure 3. RF ID reader and transponder with rail car.

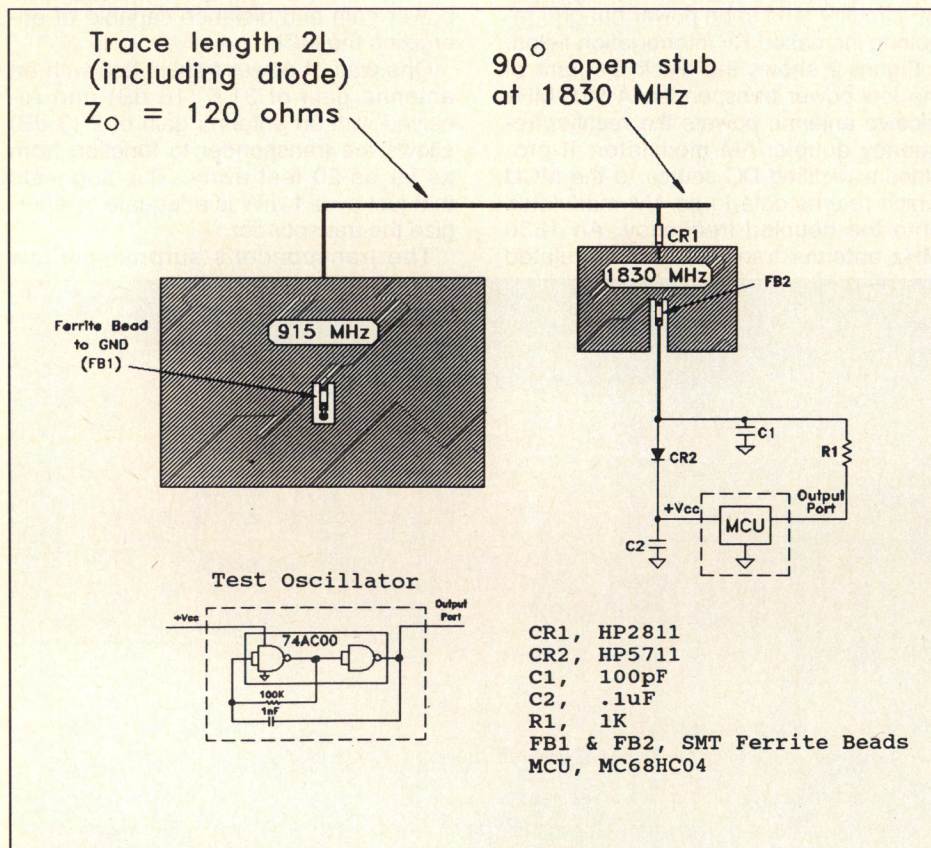


Figure 4. Hybrid schematic of transponder circuit.

power requirement is due to its efficient means of rectification, frequency doubling and modulation. All of these functions are accomplished by a single microwave diode. A hybrid schematic in Figure 4 details the circuit. The 915 MHz patch antenna has two connections, a DC return path connected at the zero impedance point and a transmission line matched to the 120 ohm impedance at the edge of the antenna. The transmission line routes the signal to CR1 for rectification. A DC tap on the 1830 MHz antenna provides the power connection for the MCU. (See side bar on microstrip patch antennas.)

Careful placement of CR1 along the transmission line is crucial in creating the proper AC impedances for efficient frequency doubling. The 1830 MHz antenna becomes a 90 degree open stub at 915 MHz at the cathode of CR1, effectively giving the 915 MHz signal a low impedance trap to work against (Figure 5). Since the transmission line does not provide a similar low impedance on the anode side of CR1, a 90 degree open stub at 1830 MHz must be added.

Less than 100 uA are required to power the MCU (Figure 6). Consequently, little second harmonic is produced by

CR1, leaving plenty of modulation headroom. Increased frequency multiplication occurs when the output port of the MCU goes low providing a path to ground for rectified current via the 1 kohm resistor, R1. Varying the value of R1 controls the modulation depth. CR2 and C2 work together to maintain sufficient voltage to the MCU while the voltage at C1 is being pulled down by the modulation action.

Performance

As previously noted, the system can operate up to 20 feet away. However, performance is measured at the 10-foot separation required during normal operation (Figure 7). For test purposes, a spectrum analyzer functions as the receiver. A 74AC00 gate oscillator in Figure 4 is substituted for the MCU to simulate load and logic level conditions. The oscillator simplifies confirmation of the concept. Three kHz modulation is used for easy detection by the analyzer.

The transponder transmits data at 94 percent AM modulation. Figure 8 is the detected 3 kHz square wave. Measurements of the rectified voltage (2.7 VDC) and current (1.45 mA DC) give 3.9 mW total power which correlates nicely with the received power (5.3 mW) predicted

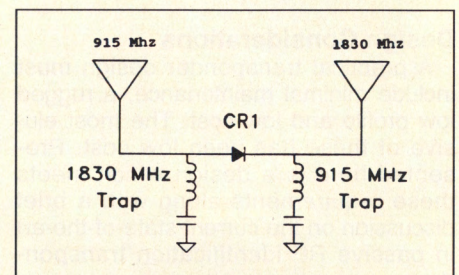


Figure 5. Equivalent AC circuit of transponder showing RF traps.

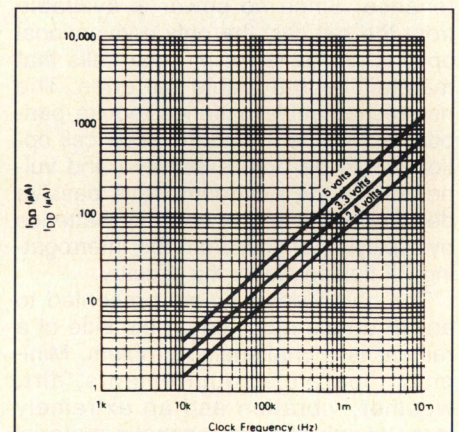


Figure 6. Current vs. clock frequency for a typical 68HC04 MCU.



There's Strength in Numbers.

Backed by the Strength and Stability of Hewlett-Packard, the New Avantek is Committed to Serving its Customers in a Whole New Way.

It's a new world out there. A world shaped by change. A world of new alliances, new borders, and new commitments.

Avantek, as part of the Hewlett-Packard family, is committed to meeting these changes by bringing new capabilities and long-term stability to our customers. A commitment expressed

in the form of major new investments in our GaAs Fab, manufacturing systems, and information systems.

The Strength of Avantek Technology.

For 28 years, Avantek has proudly served the RF and Microwave electronics needs of the defense and aerospace industries with focus, determination, and unmatched technological leadership. Today, with HP's support, we are investing in the next generation of our core GaAs and thin-film technologies. The result: no other company can offer you the technology,

expertise, and product breadth of the new Avantek.

The Strength of HP Support.

HP brings to Avantek a long-term commitment to quality in its products, service and support. Building on these strengths, Avantek has installed its own tough standards, systems, and infrastructure to ensure you receive a superior product delivered on time and to your specifications. At the new Avantek, customer satisfaction is our top priority.

A Strong Commitment to Your Success.

Your success depends on finding the right business and technology partners. Avantek is committed to heading up your list of trusted, dependable suppliers. Whatever it takes. Strong words, but we have never been better prepared to back them up.

Call **1(800)227-1817 ext. 7432** to find out more about Avantek. In Europe, FAX to **31 2979-8 41 83**. You'll find there's strength in our numbers.



AVANTEK
A Subsidiary of Hewlett-Packard

In Canada call: 1(800) 387-3867 Dept. 7432

INFO/CARD 26

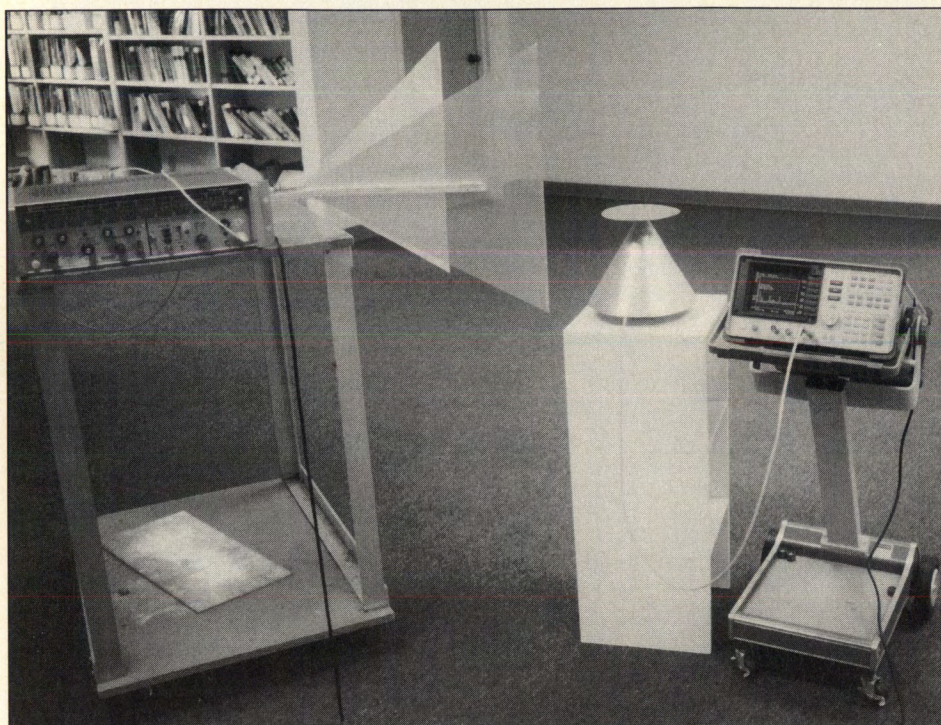


Figure 7. Test setup for transponder operating at a distance of 10 feet.

by equation 1 at a distance of 10 feet.

Improvements

Inherent compatibility with spread spectrum is provided by this design

since the returned signal frequency is derived directly from the interrogation signal. Frequency spreading is limited only by the bandwidth of the patch antennas. With the simple addition of a

Rectangular Microstrip Patch Antenna

The rectangular patch antenna is essentially a resonant microstrip with an electrical length of $1/2$ the wavelength of the frequency to be transmitted or received. Microstrip patch antennas work well for applications requiring a low profile, offering a height equal to the thickness of the printed circuit board from which they are made. PTFE substrates are normally used to minimize dielectric losses which affect the efficiency of patch antennas. However, FR-4 is a cost effective alternative for low power applications at frequencies below 2 GHz.

Microstrip antennas come in all sizes and shapes. A rectangular patch is chosen for its simple geometry and linear polarization when fed from the center of an edge. The input impedance varies as a function of feed location. The edge of a $1/2$ wavelength antenna has an input impedance of approximately 120 ohms which drops to zero ohms as the feed point is moved inboard to the center of the antenna. This allows easy impedance matching and provides a convenient means of DC tapping the antenna as seen in the transponder design.

For simplicity, the dimensions of the microstrip patch antennas in Figure 9 are in terms of L , which is equal to $1/2$ the electrical wavelength of the receive antenna (915 MHz). L can be determined by equation 2:

$$L = 0.49(\lambda/\epsilon_r) \quad (2)$$

where λ is the free-space wavelength and ϵ_r is the relative permittivity of the printed circuit board.

Bandwidth is determined by the substrate thickness and can be approximated for an SWR of less than 2 by equation 3:

$$BW = 128f^2t \quad (3)$$

BW is in MHz, f is the operating frequency in GHz, and t is the substrate thickness in inches.

Applying equations 1 and 2 to the transponder design using 0.125 inch FR-4 substrate material with an effective permittivity of 4.7 results in a value of 2.92 inches for L and a bandwidth of 13.4 MHz at 915 MHz.

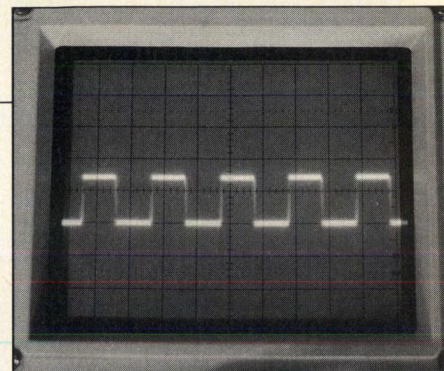


Figure 8. Detected 3 kHz square wave.

micro-power line receiver and the associated communications software, the transponder can be upgraded for two-way information applications. Size reduction can be accomplished by increasing operating frequency at the expense of costlier substrate material. Borrowing technology from missile and aircraft radar technology the transponder could be made a part of the "skin" of its host.

Summary


This paper has described the design, operation and application of a low-power RF identification transponder. The simple design is spectrum friendly, requiring

Our Design Contest Winner

Raymond Page is a design engineer for Wenzel Associates, a manufacturer of high performance crystal oscillators and frequency standards. Ray specializes in low noise designs for devices including oscillators,



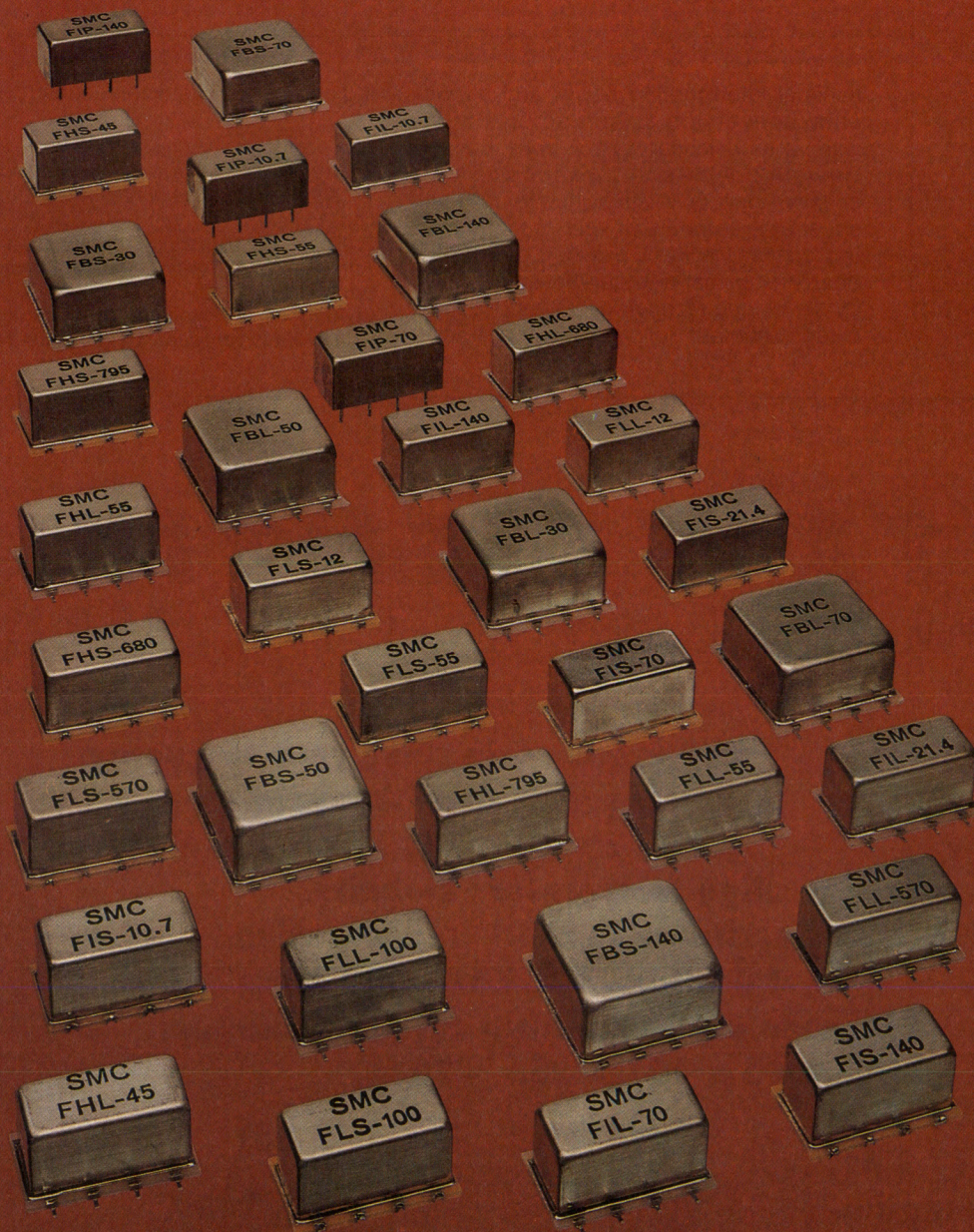phase locked frequency sources, multipliers and dividers. In addition to having fun with electronics, he enjoys outdoor sports and music. He can be reached at Wenzel Associates, 1005 La Posada Drive, Austin, Texas 78752, or by telephone at (512) 450-1400.



Synergy has introduced a selection of high performance, low cost standard catalog and custom highpass, lowpass and bandpass filters covering passbands within the DC to 2000 MHz range. These filters are readily available in standard pin packages as well as the newest Synergy patented metal surface mount package with either leaded or flush mounting configurations.

Most importantly, when you specify Synergy, you benefit from our Sales and Applications team to assist you in the wide choices of available filters.

For a copy of our latest catalog, contact:
SYNERGY MICROWAVE CORPORATION,
 483 McLean Boulevard,
 Paterson, NJ 07504.
 Phone (201) 881-8800 or
 FAX (201) 881-8361.

SYNERGY
 MICROWAVE CORPORATION
 INFO/CARD 27

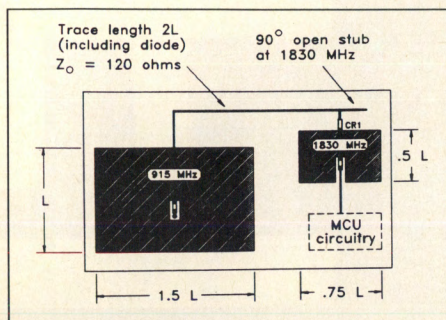


Figure 9. Dimensions for patch antennas.

minimal interrogation power and allows easy conversion to spread spectrum without modification to the transponder. Designed with one inexpensive microwave part on a single piece of FR-4 substrate, component and manufacturing costs are kept down, potentially opening up markets served exclusively by bar coding technology. Other uses include automatic tolling, inventory track-

ing and military vehicle security.


RF

References

1. Howard W. Sams & Co., *Reference Data for Radio Engineers*, Chapter 27, Sixth Edition, 1977.
2. Robert E. Munson, "Conformal Microstrip Antennas," *Microwave Journal*, March 1988, pp. 91-109.
3. Alan Tam, "Principles of Microstrip Design," *RF Design*, June 1988, pp. 29-34.

QUARTZ SCIENTIFIC

K V G - Q U A R T Z A T I T S B E S T

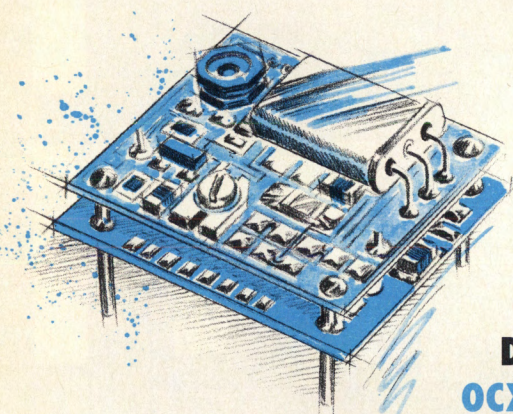

KVG Products. To solve your frequency control problems with crystals!

Quartz crystals. 800 KHz - 300 MHz.

High temperature stability.

Resistance to shock and vibration.

Crystal filters. 400 KHz - 200 MHz.

Discrete and monolithic. Crystal oscillators.

OCXO. $< \pm 5 \times 10^{-8}$; $-25... +70^\circ\text{C}$,


PXO/VCXO. 3 KHz - 300 MHz;

DTCXO. 100 KHz - 17 MHz.

**Low power consumption
in small cases.**

**If crystals are of
interest to you, we will
supply all the informa-
tion you need.**

**KVG - Selected
to be the best.**

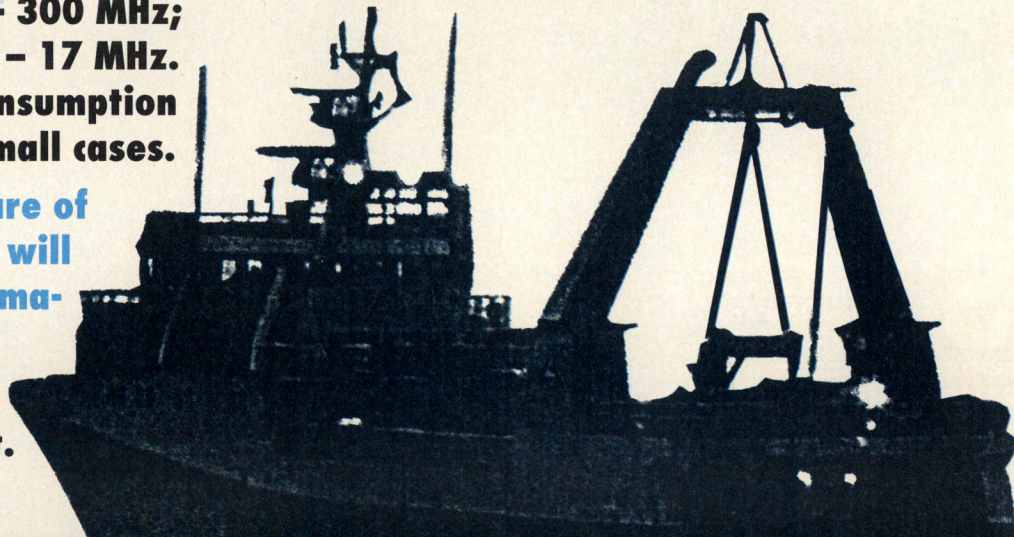

KVG GmbH P.O.-Box 61,
D-6924 Neckarbischofsheim, Federal Republic of Germany
Phone 07263/648-0, Telefax 07263/6196



KVG North America Inc.
2240 Woolbright Rd, Suite 320, Boynton Beach, FL 33426-6325
Phone (407) 734-9007, Fax (407) 734-9008

Synthesizer Design With Detailed Noise Analysis

By Terrence F. Hock
National Center for Atmospheric Research

Here is the winning software entry in the 1993 RF Design Awards Contest. The author has been awarded a software package provided by EEsof, Inc. which includes the Touchstone linear circuit analysis program for Windows and the LineCalc transmission line analysis program.

This program is designed to aid in the design of PLL synthesizers, taking into account all the noise sources present in the circuit. The program will analyze and design the loop filter and calculate the loop steady state responses, with results in both tabular and graphical form. It will also compute the reference spur levels for a digital phase/frequency detector with a differential output and can optionally add an active low pass filter to reduce the spur level. The program was written to simplify designs using commercial synthesizer integrated circuits. It operates on a DOS machine and requires a minimum of VGA graphics.

The total phase noise of the synthesizer is determined by several noise sources in the loop such as the reference oscillator, voltage controlled oscillator (VCO), phase detector and operational amplifier loop filter. Typically, the op amp noise is considered a second or third order effect when a good low noise op amp is used, but in reality the op amp may be the limiting noise factor in a synthesizer.

Program Overview

When designing a synthesizer, there

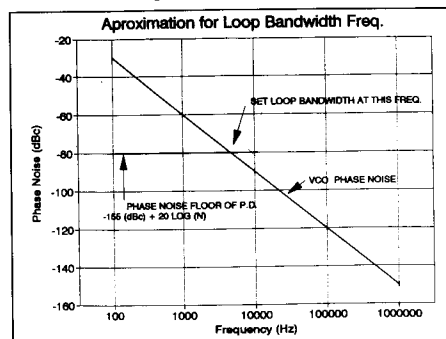


Figure 1. Method for selecting loop bandwidth.

are several performance criteria that must be considered: phase noise, switching speed, reference spur levels, etc. Optimizing one parameter usually gives less than adequate performance in another area. Thus, the performance of a single loop synthesizer is a compromise of all design goals.

In the past when designing synthesizers, several design tools have been used: spread sheets, small Basic programs and Spice simulators. This program was developed to combine all synthesizer design criteria into a single program which allows a design to be completed in a minimal amount of time. One parameter can be varied while the effect is observed in all other performance areas. Prior to developing this program, an adequate model for the phase noise of the synthesizer was not available.

The program calculates the noise contribution from the individual stages to obtain the total phase noise of the synthesizer. The loop bandwidth can easily be changed while observing the phase noise, which allows for easy optimization. The program displays the integrated phase jitter, providing an aid in choosing the loop bandwidth for lowest overall phase noise. The loop filter model incorporates the performance of a real op amp for the calculations of op amp filter noise, reference spur levels and steady state loop responses. The Johnson noise of the resistors is also incorporated into the op amp noise calculation.

All calculations use linear control theory in the frequency domain for both the

steady state responses and phase noise calculations. A wideband synthesizer (loop bandwidth greater than 20 percent of the reference frequency) analyzed with linear analysis will introduce errors. A better approach would be to use discrete time analysis or Z-transforms for analysis. However, if wide loop bandwidths are desirable for fast switching speeds, the reference spurs may be at undesirably high levels when using the digital phase/frequency detector in a low cost synthesizer IC.

To improve the accuracy of the calculations, the user has the option of adding a delay term to the steady state loop calculations. There has been considerable discussion in past issues of *RF Design* as to what the delay value should be (1). The value of this delay term is dependent upon the type of phase detector used in the synthesizer (digital phase/frequency, sample and hold), and the location of the first pole. There is not a clear consensus on what the sampling delay should be for all cases, so its value is left for the user to choose.

Currently the program does not calculate the switching speed of the synthesizer, but uses a simple approximation for a rough estimate of the switching speed. Gavin has demonstrated how a Spice simulator can be used to estimate the switching speed incorporating all delay terms for accurate switching speed analysis (2).

Phase Noise

When designing a synthesizer for low-


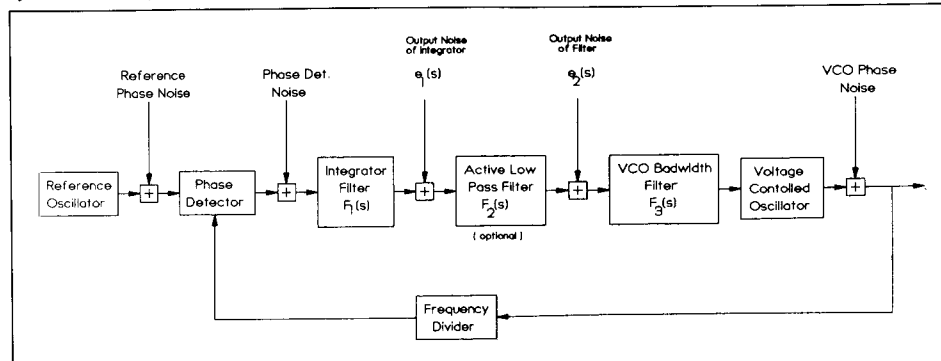


Figure 2. Noise sources in a synthesizer.

**SPECS
UPDATED!
NEW!**

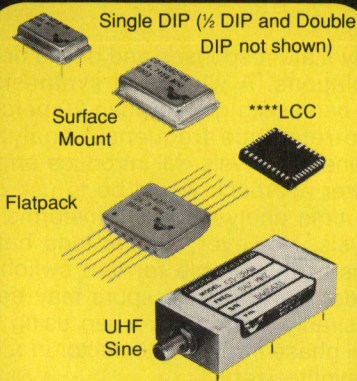Clock and Sinewave Crystal Oscillators (1 Hz thru 2600 MHz)



	TTL	CMOS	*HCMOS	**ECL	SINE
Frequency	16KHz-100MHz	1 Hz-15 MHz	1 Hz-175 MHz	***5-700 MHz	***50 Hz-2.6 GHz
Input:	5V	5V or 8-15V	5V	***5.2V or -4.5V	12-24V
Accuracy: (25°C):	Five options: ±50 ppm, ±25 ppm, ±15 ppm, ±10 ppm and in some models externally settable to ±1 ppm				
Stability:	Standard: ±25 ppm over 0°C to +70°C Option: ±50 ppm over -55°C to +125°C Option: ±5 ppm over 0°C to +50°C				

Improved accuracy/stability available on some models

Logic Oscillators available OPL (TTL: M55310/16; CMOS: M55310/18; HCMOS: M55310/26; ECL: M55310/25)

* Tri-state available 4 MHz to 175 MHz
** 10K, 10KH, MECLIII, 100K, or ECLnPs
*** ECL > 625 MHz and sine > 500 MHz are non-hybrid designs
**** LCC limited to TTL (1-60 MHz) and HCMOS (12.5-50 MHz)

To order a Free catalog, or for engineering assistance, call:

(203) 853-4433

Fax: (203) 849-1423

VECTRON

The Crystal Oscillator Company

VECTRON LABORATORIES, INC.

166 Glover Ave., P.O. Box 5160, Norwalk, CT 06856-5160

A DOVER TECHNOLOGIES COMPANY

INFO/CARD 29

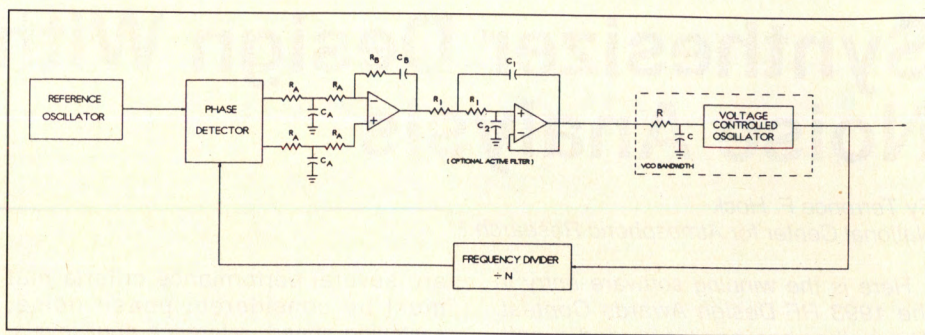


Figure 3. Synthesizer topology analyzed by the program.

est phase noise, optimum selection of the loop bandwidth is critical. Typically only the VCO noise and phase detector noise floor are considered in determining the final phase noise of the synthesizer. The phase noise inside the loop bandwidth is usually approximated by equation 1:

phase noise
= 20 log (N) + phase det. noise floor (1)

where N is the total division ratio of the VCO frequency to the reference frequency and the phase detector noise floor might be -155 dBc. The phase detector noise floor varies with the type of technology used, such as CMOS, ECL

and GaAs. CMOS has the lowest noise floor of the three. For optimum phase noise performance, the loop bandwidth would be chosen where the noise floor from equation (1) intersects the phase noise of the VCO. This simplified analysis is shown in Figure 1. As a quick evaluation of where to place the loop bandwidth, this procedure is quite valid. However this method excludes the true loop behavior or closed loop response and error loop response since they modify the VCO phase noise and the phase detector noise floor.

A more detailed analysis is required to predict the actual value of the phase noise in the synthesizer. As the architecture of the synthesizer changes from

$$\text{REF OSC PHASE NOISE} = \frac{\text{Kpd Kvc} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{1 + \frac{\text{Kvc} \text{Kpd} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{sN}} \cdot \theta_{\text{Ref}}(s)$$

$$\text{PHASE DET. PHASE NOISE} = \frac{\text{Kvc} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{1 + \frac{\text{Kvc} \text{Kpd} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{sN}} \cdot \theta_{\text{PD}}(s)$$


$$\text{VCO PHASE NOISE} = \frac{1}{1 + \frac{\text{Kvc} \text{Kpd} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{sN}} \cdot \theta_{\text{VCO}}(s)$$

$$\text{OP-AMP INTEGRATOR NOISE} = \frac{\text{Kvc} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{1 + \frac{\text{Kvc} \text{Kpd} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{sN}} \cdot E_1(s)$$

$$\text{OP-AMP LOW PASS FILTER NOISE} = \frac{\text{Kvc} \frac{F_3(s)}{s}}{1 + \frac{\text{Kvc} \text{Kpd} \frac{F_1(s)}{s} \frac{F_2(s)}{s} \frac{F_3(s)}{s}}{sN}} \cdot E_2(s)$$

Table 1. Phase noise system equations.

THE SMART CHOICE

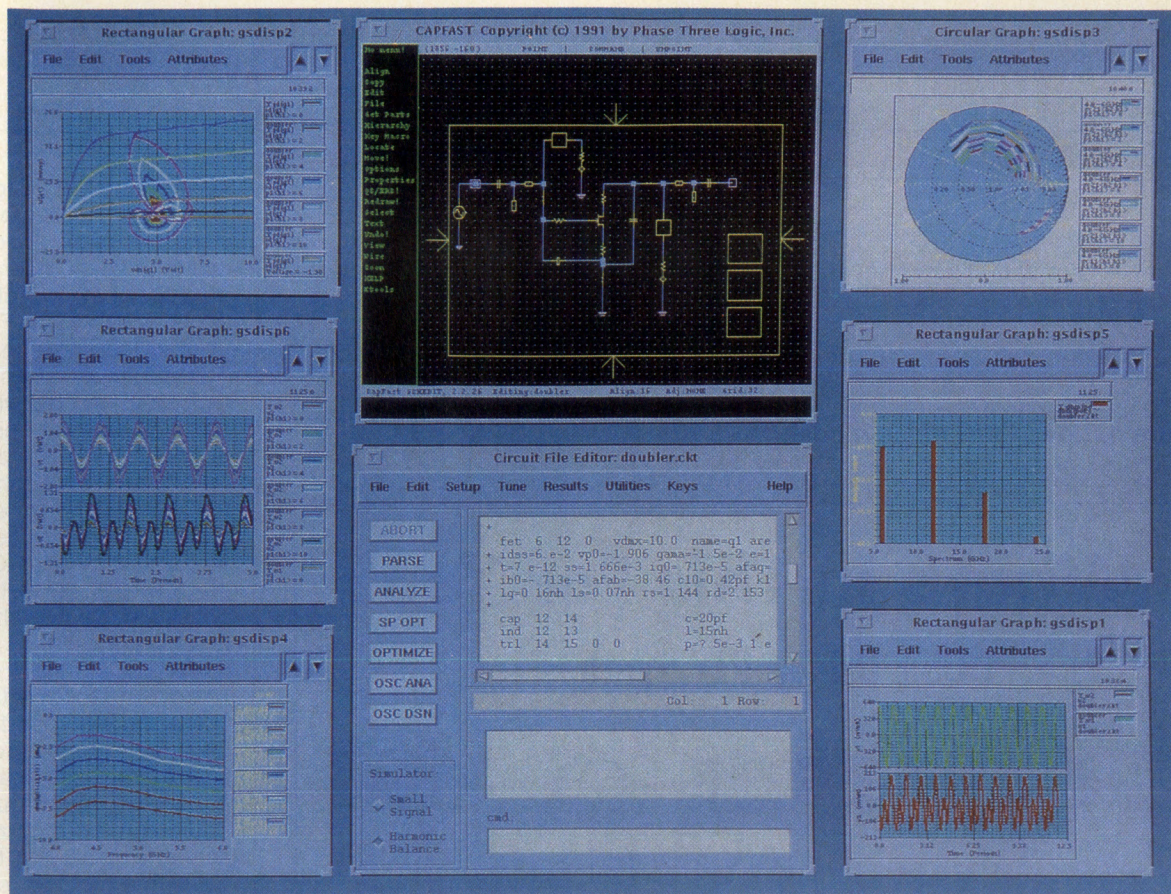

Compact Software *again* leads the **ANALOG DESIGN AUTOMATION** field with its new EASi™ Interface.

The exciting EASi Interface makes it even simpler to use our circuit simulators, Super-Compact and Microwave Harmonica.

EASi (Environment for Analog Simulation) provides you with the most advanced user interface tools available today for workstation CAD. Using X-Windows and Motif standards, EASi presents you with a uniform environment - a "look and feel" with clear menus, fill-forms, and editor windows that take you quickly through analysis, tuning, optimization,

statistical analysis and more. EASi interfaces with our linear and nonlinear engines, including our new Super-Spice, as well as our electromagnetic simulator, Explorer, providing

highly-acclaimed accuracy and efficiency of computations. You switch from one engine to another with the mere "click" of a mouse button and when the simulations are complete, EASi guides you through the

almost limitless possibilities of tabular and graphical outputs. And it's network compatible too!

As EASi as



WELCOME to a new world of high-productivity using Compact's EASi Interface.

**Compact
Software**
The Leader In CAD Software

483 McLean Boulevard, Paterson, NJ 07504 USA
TEL: (201) 881-1200 or FAX: (201) 881-8361

In Europe, contact the European Support Center
TEL: (49) 7309-5075 or FAX: (49) 7309-3275


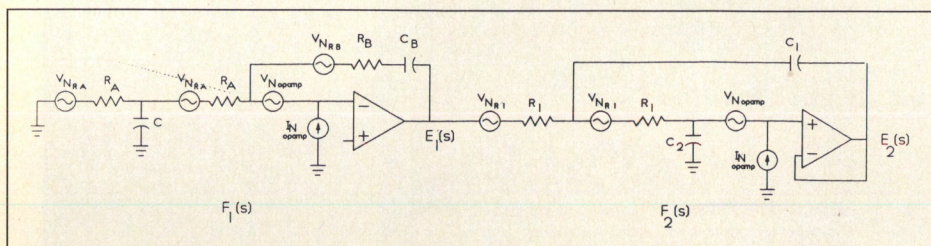


Figure 4. Loop filter noise model.

What's In This For You?

DDS - Driven PLL Synthesizer

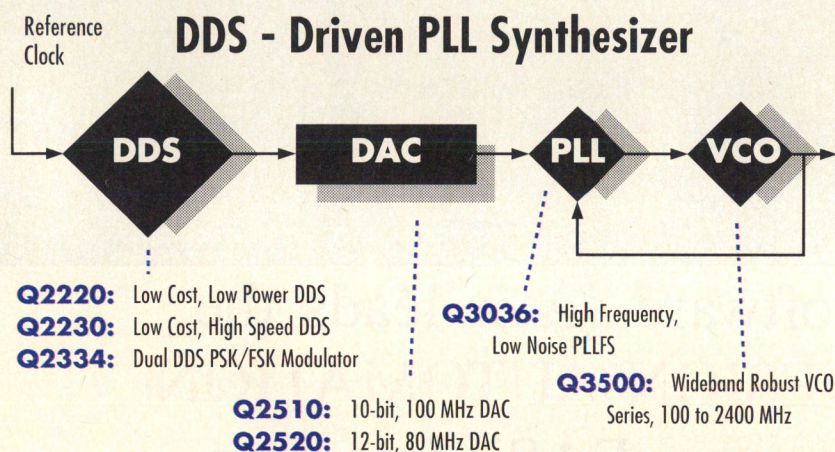

DDS-driven PLL technology provides the high frequency output, wide frequency range, and fine frequency resolution you need. QUALCOMM provides *all* the major components your synthesizer system requires:

- Direct Digital Synthesizers
- Digital to Analog Converters
- Phase Locked Loop Frequency Synthesizers
- Voltage Controlled Oscillators.

Explore the benefits of DDS/PLL technology with our Q0710 DDS/PLL demo circuit, or send for our **free** "DDS/PLL Hybrid" Application Note and discover *what's in this for you!*

QUALCOMM
VLSI Products

**10555 Sorrento Valley Road
San Diego, CA 92121-1617 USA
Tel: (619) 597-5005
Fax: (619) 452-9096**

synthesizer
"...the elegant solution"

large values of N to high VCO phase noise, this simple model will have significant errors in predicting the phase noise. A block diagram of all the noise sources that contribute to the phase noise is shown in Figure 2. Equations used in the noise analysis are shown in Table 1. The op amp noise source is typically neglected when high quality low noise op amps are used in the loop filter integrator circuit. Yet, in certain cases the op amp will be the major contributor to the phase noise, even when very low noise op amps are used. This is typically the case when a VCO with a high tuning sensitivity of 25 MHz/V or greater and phase detectors with low gain (1 V/rad or less) are used.

Program Description

The program has four major sections: Design, Analysis, VCO Phase Noise and Synthesizer Phase Noise. The program assumes the user is familiar with designing synthesizers. Figure 3 is a schematic showing the circuit topology which the program evaluates. The synthesizer is a type II fifth order including the VCO bandwidth as a pole and first pole in an op amp. If an active filter is used to reduce the reference spurs, the synthesizer is a type II seventh order control system.

Design — The synthesizer design rou-

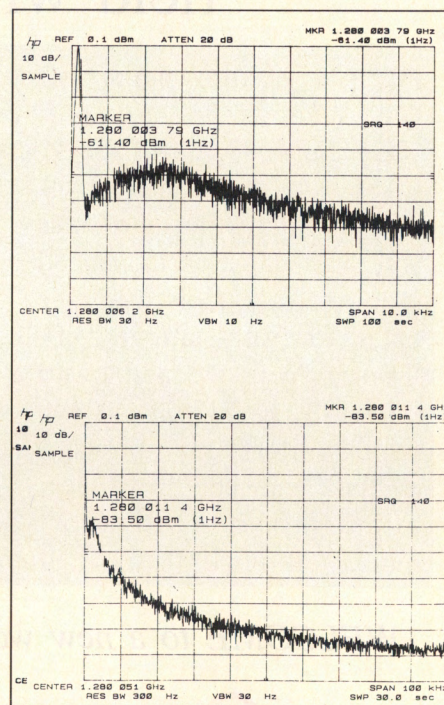


Figure 5. Measured phase noise of example synthesizer at 10 kHz and 100 kHz maximum span.

Frequency (Hz)	FILTER (dBc)	VCO (dBc)	REF (dBc)	Phase Det. (dBc)	Total (dBc)	
10.0	-80.1	-84.3	-64.7	-80.8	-64.4	
17.8	-80.1	-81.8	-69.6	-80.8	-68.7	Fcco: 1200.00 MHz
31.6	-80.1	-79.3	-74.4	-80.8	-71.8	
56.2	-80.1	-76.8	-79.0	-80.8	-72.9	Fref: 250.00 kHz
100.0	-80.0	-74.3	-83.4	-80.8	-72.2	
177.8	-79.8	-71.8	-87.3	-80.7	-70.6	Kuco: 23.0 MHz/v
316.2	-79.1	-69.5	-90.6	-80.5	-68.7	
562.3	-77.7	-67.3	-92.9	-79.9	-66.7	Kpd: 0.796 u/rad
1000.0	-75.6	-65.6	-93.9	-78.8	-65.0	
1778.3	-73.4	-64.8	-94.0	-77.4	-64.1	
3162.3	-73.5	-66.6	-95.6	-78.1	-65.6	
5623.4	-80.6	-75.1	-104.3	-86.2	-73.8	
10000.0	-89.8	-84.8	-116.1	-97.6	-83.4	Phase jitter over
17782.8	-98.8	-92.9	-128.9	-110.2	-91.8	100 Hz to 1 MHz
31622.8	-108.1	-100.1	-142.8	-124.0	-99.5	2.897 deg.
56234.1	-117.8	-106.9	-157.4	-138.5	-106.5	
100000.0	-127.7	-113.3	-172.3	-153.4	-113.1	
177827.9	-137.7	-119.3	-187.3	-168.4	-119.2	
316227.8	-147.7	-125.0	-202.6	-183.7	-125.0	
562341.3	-157.7	-130.5	-218.4	-199.5	-130.5	
1000000.0	-167.7	-135.8	-235.2	-216.2	-135.8	

Figure 6. Program analysis of the example synthesizer (tabular form).

tine prompts the user for the common synthesizer design parameters such as VCO tuning sensitivity, phase detector gain, reference frequency, loop bandwidth, etc. The component values of the loop filter are calculated based on the equations from reference (3). The program allows the user to easily change the component values for practical sizes in the loop filter without having to re-enter the initial design data. The new values are immediately updated on the screen. The program will next compute the values of the reference spurs at the VCO output. The spur calculation is only valid for a digital phase/frequency detector using differential phase detector outputs. This type of phase detector is used in the spur calculation since it has lower spur levels than the single ended output from a digital phase/frequency detector as long as the loop filter is an op amp integrator. The program then provides the option to add a 2-pole active low pass filter to reduce the spur level. The program prompts for the bandwidth and damping coefficient of the filter. The filter component values are easily changed for practical values.

The design routine will also compute and display the steady state responses of the synthesizer in table and graph form. The steady state responses computed are closed loop gain, open loop gain, error loop gain and phase margin. The open loop gain and phase margin are the most critical parameters for evaluating the loop stability. The phase margin at 0 dB open loop gain frequency

PHASE NOISE COMPARISON

FREQUENCY MEASURED CALCULATED

kHz	dBc	dBc
1	-66.9	-65.0
3	-61.4	-65.6
10	-83.5	-83.4
50	-106	-106.0

SWITCHING SPEED

MEASURED	1.2 msec
CALCULATED	1.54 msec

Figure 7. Comparison of measured and computed results.

should typically be 40 to 60 degrees for a well behaved loop.

Usually, a synthesizer is designed to operate at several (or many) different frequencies. In a single loop synthesizer the output frequency may vary 25 percent or more, which requires changing the divider value, which varies the loop gain. The loop should be evaluated at several operating conditions for stability and bandwidth.

Typically the tuning sensitivity of the VCO changes at different control voltages. Both the tuning sensitivity and divider values can be evaluated quickly by entering either K or F followed by new values. The output frequency is changed in lieu of changing the actual divider ratio. The loop switching speed is also calculated based on a simple approximation of $t=4/\text{loop BW}$.

Analysis — The synthesizer analysis routine is very similar to the design routine except actual component values of the loop integrator and active low pass filter are entered. The steady state responses of the loop are calculated along with reference spur level. The steady state responses, open, closed and error loop are calculated in table and graphic form. The switching speed is not calculated since the analysis routine does not directly compute the loop bandwidth. The analysis routine is very valuable for analyzing current designs and to evaluate component sensitivity in the loop filter versus performance variations. The output frequency and the VCO gain can both be easily changed for different operating frequencies and VCO gain varia-

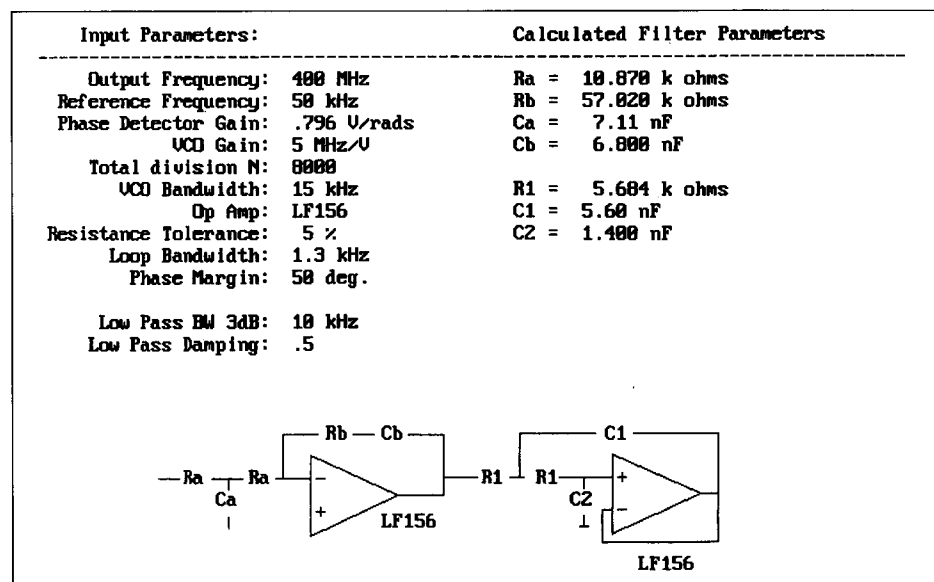


Figure 8. Input screen display.

FREQUENCY (Hz)	OPEN LOOP GAIN Gain (dB)	Angle (deg)	CLOSED LOOP Gain (dB)	ERROR LOOP Gain (dB)	50.0 kHz REFERENCE SPUR ANALYSIS
10.0	74.6	1.2	78.1	-74.6	
17.0	64.6	2.1	78.1	-64.6	Spur level with only Op-Amp
31.6	54.6	3.7	78.1	-54.6	integrator [Ra,Rb,Ca,Cb].
56.2	44.7	6.5	78.1	-44.6	INITIAL LEVEL: -44.2 dBc
100.0	34.8	11.3	78.2	-34.7	
177.8	25.3	19.2	78.5	-24.9	
316.2	16.6	30.2	79.2	-15.4	Attenuation
562.3	9.1	40.7	80.3	-6.8	@ 50.0kHz @ 1.3kHz
1000.0	2.8	44.4	81.2	0.3	(dB) (deg)
1778.3	-3.1	36.4	79.3	4.4	
3162.3	-9.4	13.7	72.0	3.4	VCO BW: 18.8
5623.4	-16.8	-28.1	62.5	1.2	ACTIVE LPF: 27.8
10000.0	-27.7	-103.8	50.3	-0.1	TOTAL 30.6 -12.5
17782.8	-48.4	-178.9	29.6	-0.8	Final Reference Spur Level:
31622.8	-72.4	141.0	5.6	-0.8	-82.8 dBc @ 50.0 kHz
56234.1	-97.1	118.5	-19.0	-0.8	
100000.0	-122.0	105.3	-43.9	-0.8	
177827.9	-146.9	97.2	-68.9	0.0	
316227.8	-171.9	91.6	-93.9	0.0	
562341.3	-196.9	86.5	-118.9	0.0	Approximate switching speed:
1000000.0	-222.1	80.4	-144.0	0.0	3.00 asec

Figure 9. Display of steady-state responses, spur and switching speed calculation.

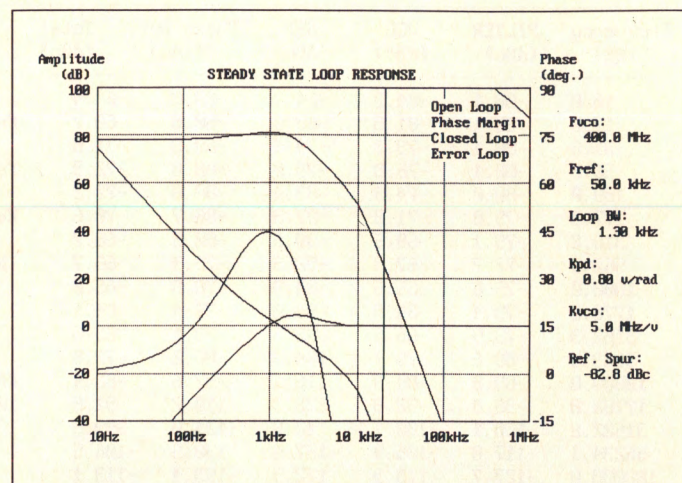


Figure 10. Graph of steady-state responses.

tions.


VCO Phase Noise — The VCO routine uses Leeson's equation for calculating the phase noise of an oscillator (4). The two dominant parameters that set the phase noise are the loaded Q of the resonator and the operating frequency

or the ratio of operating frequency to Q. The output power and flicker frequency are also required in the VCO phase noise calculation. The varactor diode is also a major noise source in a voltage controlled oscillator, since it has an effective thermal noise resistance. This re-

sistance generates a noise voltage given by Nyquist's equation which modulates the varactor diode. This noise source typically dominates the phase noise of the VCO in wide frequency tuning oscillators.


The VCO routine prompts the user for

Streamline Crystal Oscillator

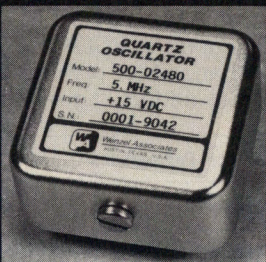

- Small Package
- Low Phase Noise
- Low Power Consumption
- Can be Customized

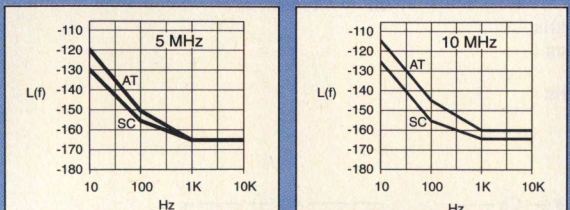Frequency: 1 to 20 MHz Package: 2x2x1"
Phase Noise:



Wenzel Associates
Quietly the best

1005 La Posada Drive, Austin, Texas 78752 • 512-450-1400 • Fax 512-450-1490

INFO/CARD 32

Choose from a world of high performance crystal packages designed for: MICROWAVE APPLICATIONS



From miniature Surface Mount to "World Class" crystals, EG&G's complete line of AT-cut crystals are ideal for a variety of microwave, telemetry and satellite communications applications.

When you need ULTRA-LOW aging, high performance under rugged conditions or have applications requiring precision timing, EG&G's engineering staff is available to fill your needs and solve your problems.

So, give us a call at 1-800-424-0266. (U.S. or Canada)
No matter what size your applications may be...
our crystals are a perfect fit.



EG&G
FREQUENCY PRODUCTS

4914 Gray Road • Cincinnati, Ohio 45232 | In Canada represented by: ELLAM & Assoc. Ltd.
Phone 513-542-5555 • FAX 513-542-5146 | Phone 613-727-3892 • FAX 613-727-0368

INFO/CARD 33

The Best Selection of Surface Mount Tuning Varactors in the Industry!

Three Families of Silicon

Abrupt:



Featuring higher Q

Hyperabrupt:

Low cost and general tuning

Wide-band Hyperabrupt:

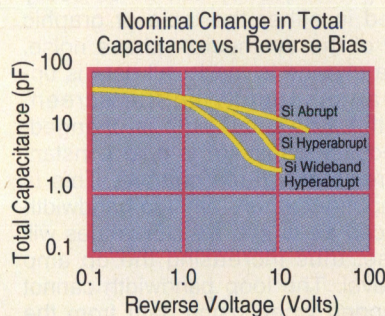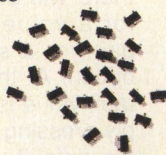Large capacitance change at low voltages for battery applications



M/A-COM will meet your Surface Mount Tuning Varactor needs. For more information and technical assistance contact (617) 272-3100 FAX (617) 272-8861.

Our Surface Mount Tuning Varactors are also in stock at Richardson Electronics 1-800 348-5580 and Nu Horizons (516) 226-6000.

M/A-COM, Inc.
Burlington Semiconductor Operations
43 South Avenue
Burlington, MA 01803

Four Families of Gallium Arsenide

Abrupt

Highest Q

Hyperabrupt (Gamma 0.75)


Improved Linear Tuning

Hyperabrupt (Gamma 1.25)

Higher Q, moderate tuning rate

Hyperabrupt (Gamma 1.5)

Wide bandwidth tuning

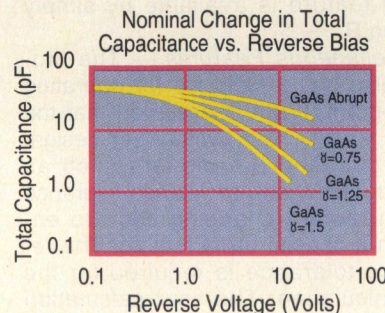

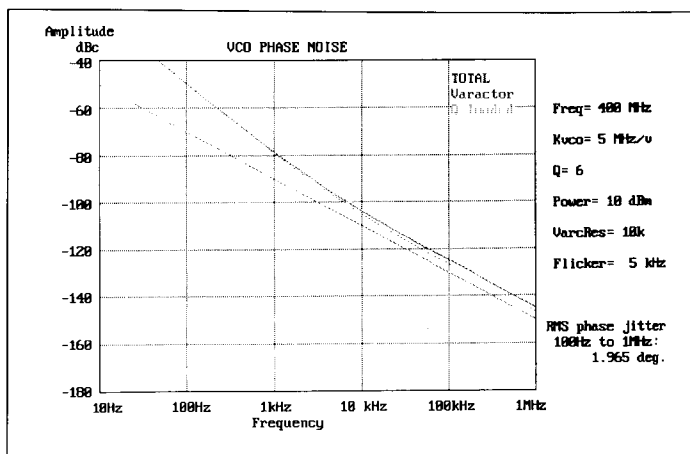


Figure 11. Graph of VCO performance.

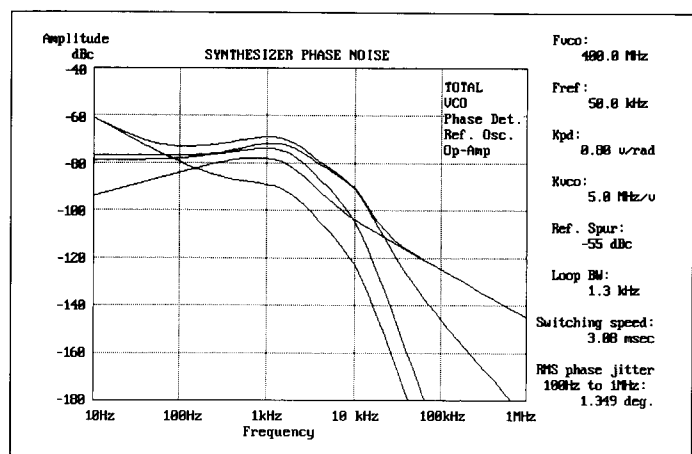


Figure 12. Graph of synthesizer phase noise.

operating frequency, loaded resonator Q, output power, flicker frequency, effective noise resistance of varactor diode and tuning sensitivity. The VCO phase noise analysis separately calculates the phase noise due to the varactor diode, Leeson's equation and the total phase noise. The performance of the VCO is easily evaluated, with the results in table and graph form.

The resonator Q and tuning sensitivity can easily be changed in 5 percent increments up or down. This feature is useful for adjusting the phase noise performance to match that of a commercial VCO. When the Q and tuning sensitivity are changed, the results are updated immediately on the screen. The phase noise from this routine will be used in the synthesizer phase noise calculations. When designing VCO's this routine is very useful for estimating the phase noise performance of an oscillator.

Synthesizer Phase Noise — The synthesizer phase noise routine is the most useful feature of the program. It computes the individual terms from each noise source in the loop and simultaneously displays the level of the reference spur, switching speed and integrated phase jitter. All design parameters are displayed on one screen while the user easily changes the loop bandwidth, observing the phase noise, spur level, switching speed, etc. The output frequency and VCO tuning sensitivity can also be changed to account for the different operating conditions as the synthesizer is set to different frequencies.

The synthesizer phase noise calculation uses data from either the Design or Analysis routine for the loop filter and data from the VCO phase noise routine. Phase noise is computed for the op amp

filter, reference oscillator, VCO, phase detector and the sum of these noise sources. The op amp noise model also includes the active low pass filter if it is chosen in either the analysis or design routines. The model includes the thermal noise of all the resistors in the filters. The phase jitter is also computed by integrating the total phase noise from 100 Hz to 1 MHz. The phase jitter is useful when adjusting the loop bandwidth for lowest phase noise.

The loop bandwidth, tuning sensitivity and output frequency can all be easily changed in either the table or graphic display of the synthesizer phase noise. When a change is made, all data is updated automatically on the screen. When the loop bandwidth is changed, the feedback capacitor is held constant so all resistor values change. This is very important when the loop bandwidth is reduced as all the resistor values will increase, thus increasing the op amp noise level. The loop bandwidth cannot be changed when using data from the analysis routine. The phase noise plot has five parameters plotted simultaneously, so when a parameter like VCO gain is changed several times the graph becomes cumbersome to evaluate. A redraw feature is available by simply pressing R.

Miscellaneous Features — The program also has a Help file for operating the program, but it is assumed that the user is familiar with synthesizer design. A few common parameters such as sampling delay and resistance tolerance seldom require changing and are entered in a special utility routine. The resistance tolerance is required for the spur calculation. The spur calculation computes the common mode rejection of the op amp integrator from the op

amp data and resistor values. The op amp data is in a separate ASCII file that contains the individual parameters for each op amp. This ASCII data file can easily be changed with any text editor to add, delete, or modify the op amp data file. The READ.ME file provides the format for the ASCII op amp data file. A second ASCII data file is required which stores all synthesizer data parameters as the default values when the program is terminated. These parameters will then be recalled when the program is run again. The op amp and PLL data files must reside in the same directory when the program is executed for proper operation.

General Operation

The program is designed to be very easy to use and operate with a minimal number of key strokes. At each prompt there will be a question which will ask for a value, such as phase detector gain, or a single letter designating an option. At the end of a prompt, the default value is shown in brackets. By simply pressing return, the program accepts the default value. When only one parameter has to be changed, this feature quickly allows the user to go through the input parameters without having to re-type every value. An option selection will have different letters in brackets; pressing the letter will execute that command.

Printing — The results on the screen can easily be dumped to a printer using the PrintScreen key. A hard copy of the graphs can also be printed by running the DOS utility GRAPHICS.COM prior to running the program, and pressing [Shift] and [Print Screen] simultaneously. If a Laser printer is being used, be sure to add the appropriate extension to the graphics command given in a DOS

The 48 cent solution.

Wideband Amplifiers – From \$.48 each

UPC1653 To 1300MHz 18dB G _p	UPC1654 To 1100MHz 19dB G _p	UPC1655 To 900MHz 18dB G _p	UPC1656 To 850MHz 19dB G _p	UPC1658 To 1100MHz 17dB G _p 2.0dB NF	
UPC1659 600MHz to 2300MHz 23dB G _p	UPC1675 To 2100MHz 12dB G _p	UPC1676 To 1300MHz 20dB G _p 4.0dB NF	UPC1677 To 1700MHz 24dB G _p P _{out} = 19.5dBm	UPC1678 Up to 1900MHz 23dB G _p P _{out} = 18dBm	UPC1688 Up to 1000MHz 21dB G _p 4.0dB NF

Prescalers – From \$2.20 each

UPB581 ÷ 2 500MHz to 2.8GHz	UPB582 ÷ 4 500MHz to 2.8GHz	UPB584 ÷ 2 500MHz to 2.5GHz	UPB585 ÷ 4 500MHz to 2.5GHz	UPB586 ÷ 512/256 500MHz to 2.5GHz	UPB587 ÷ 2/4/8 50MHz to 1.0GHz V _{cc} = 2.2 to 3.5V	UPB588 ÷ 64/128 500MHz to 2.5GHz
--	--	--	--	--	--	---

Freq. Convertors – From \$1.58 each

UPC1685 DC to 890MHz 14dB GAIN Double Balanced Mixer Applications	UPC1686 DC to 890MHz 22dB GAIN	UPC1687 DC to 890MHz 28dB GAIN I _{cc} of 38mA
--	---	--

IF Amplifiers – From \$3.50 each

UPC1668 10 to 170MHz G _L = 14.5dB 60dB Isolation	UPC1669 10 to 180MHz G _L = 10.5dB 55dB Isolation	UPC1670 10 to 150MHz IM ₃ of 56dBc 60dB Isolation
---	---	--

Transistor Arrays From \$2.40 each

UPA101 F _T = 9GHz Double Balanced Mixer Applications	UPA102 F _T = 9GHz Differential Amplifier
UPA103 F _T = 9GHz Differential Amplifier	UPA104 F _T = 9GHz OR/NOR Functions

Special Function MMICs From \$1.08 each

UPC1684 LED DRIVER 150mA Drive Current 300 Mbits NRZ	UPC1663 VIDEO AMPLIFIER 170MHz @ A _{vol} = 100 1.6ns Propagation Delay
---	--

Note: MMIC prices based on 25K quantities

NEC[®]

Want to make life simpler? Reduce the parts count in your design with silicon MMICs from NEC. They're the low cost, no-hassle way to achieve your design goals.


But be aware of the side effects!

Reducing your parts count can also make your QC easier. Your overall circuit more reliable. And your assembly, whether manual or automated, faster and more efficient.

NEC MMICs come in chips and a variety of packages, including hermetic, low cost plastic, surface mount and tape and reel. So they're ideal for high volume automated assembly.

And their quality and reliability is proven: With a production rate of *7 million a month*, no one knows MMICs like NEC.

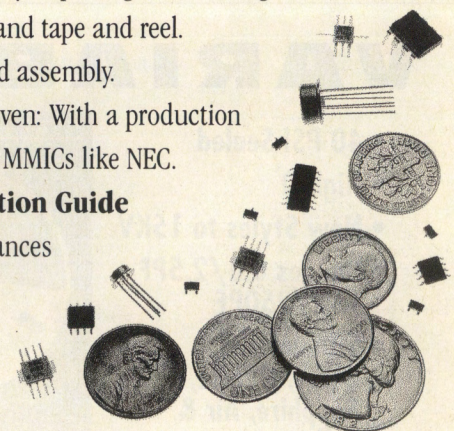Our **Silicon MMIC Product Selection Guide** lists specifications for dozens of parts. Chances are good it has just what you need. To get a copy, call your nearest CEL Sales Office or circle the number below.



California Eastern Laboratories

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 □ Santa Clara, CA (408) 988-7846 □ Los Angeles, CA (310) 645-0985
San Diego, CA (619) 467-6727 □ Bellevue, WA (206) 455-1101 □ Richardson, TX (214) 437-5487 □ Shawnee, KS (913) 962-2161 □ Woodridge, IL (708) 241-3040 □ Cockeysville, MD (410) 667-1310
Peabody, MA (508) 535-2885 □ Hackensack, NJ (201) 487-1155 □ Palm Bay, FL (407) 727-8045 □ Snellville, GA (404) 978-4443 □ Nepean, Ontario, Canada (613) 726-0626

© 1992, California Eastern Laboratories

INFO/CARD 35

manual.

Phase Noise Model — Several assumptions are made in the computation of the phase noise. The steady state equations used for the analysis and design routine are used for the phase noise calculations in modifying the appropriate noise source in the loop. The Z-transform would be the better choice for improved accuracy in wide loop bandwidth designed synthesizers. However for small loop bandwidths relative to the reference frequency, linear equations provide excellent results. The most unique feature of the program is that it incorporates all noise contributions from the loop's integrator and active low pass filter.

A block diagram of the noise sources considered in this program are shown in Figure 4. The noise sources $E_1(s)$ and $E_2(s)$ are lumped together into the op amp noise source when displayed on the screen. $E_1(s)$ represents the output noise of the integrator circuit including the thermal noise of all the resistors. $E_2(s)$ represents the output noise of the active low pass filter including the thermal noise of the resistors. The noise from the low pass filter is only considered if selected in the design or analysis routines.

Since most synthesizers use CMOS technology, the final frequency division of the VCO is with CMOS technology. CMOS has the lowest phase noise of all technologies available. Therefore the frequency divider phase noise was omitted from the analysis. However, the reference oscillator noise floor and divider

noise are equivalent in the system equations. The phase noise of the reference oscillator is based upon Leeson's equation with a very high Q representative of a crystal oscillator. The reference oscillator usually dominates the total phase noise below 100 Hz in designs with high divider values.

An accurate model of the phase detector noise floor is not available for the various types of technologies and types of phase detectors so a constant value is entered by the user. Even though the phase noise density of the phase detector is not constant versus frequency, the noise floor will dominate the total phase noise typically at only one frequency range. The value entered should correlate to this frequency region.

The noise model of the loop filter accounts for the internal noise generated by the op amps (input noise current density and input noise voltage density) and the thermal noise of the resistors. Figure 4 shows the noise sources considered in the filter noise model used by the program. Only the Johnson or thermal noise of the resistors is considered. Contact or popcorn noise in the resistor is not considered, as this noise is very dependent on the type of resistor used and is not well defined. Metal film resistors are a good choice in the integrator filter for low noise since they have minimal contact noise. The output noise of each filter stage is computed for the calculation of the phase noise. The flicker frequency noise of the op amps, typically DC to 100 Hz is not considered in the calculation of the op amp noise. Since

the phase noise of the synthesizer is typically dominated by the reference oscillator at these low frequencies, it would add little to program accuracy.

The op amp noise is minimized by keeping the input resistors of the integrator circuit small. The input noise current is effectively magnified by the size of the input resistors. Also the Johnson noise from the input resistors can become excessive if the resistors are large. If the low pass active filter is implemented, it does contribute noise to the overall loop filter and is added to the op amp noise display.

The program requests a VCO bandwidth which is used in the steady state analysis and synthesizer phase noise calculations. This is an additional pole in the loop. The VCO bandwidth in the analysis is represented as a single RC low pass filter. The VCO bandwidth can be either the actual bandwidth of the VCO or an RC low pass filter located at the input of the VCO. This additional pole filters the noise generated in the op amp circuits which can improve the phase noise performance when op amp noise is high.

Example


It is very easy to determine the dominating noise source at a given offset frequency from the carrier in a synthesizer. In loops with high division values, the phase noise inside the loop bandwidth is typically dominated by the phase detector noise floor and the loop filter (op amp noise). If a VCO with poor phase noise is used, it still will contribute significant

VARIABLE CAPACITORS

- 40 PSI Sealed
- High Q
- New Styles to 15KV
- Ranges 0.4/2.5PF to 2/250PF
- 5 Dielectrics; Glass, Quartz, Sapphire, Air & Teflon



MULTI-TURN

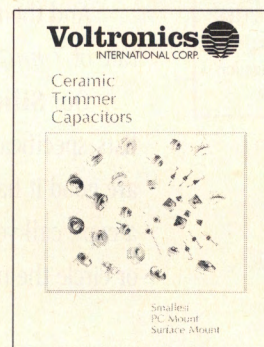



ONE-TURN

- Smallest Available
- PC & Surface Mount
- Up to 40 PF
- LOW COST for Commerical Applications
- Large Choice of Styles

Voltronics
CORPORATION

WRITE, CALL OR FAX FOR CATALOGS
100-10 FORD ROAD • DENVER, NEW JERSEY 07834
PHONE: (201) 586-8585 • FAX: (201) 586-3404

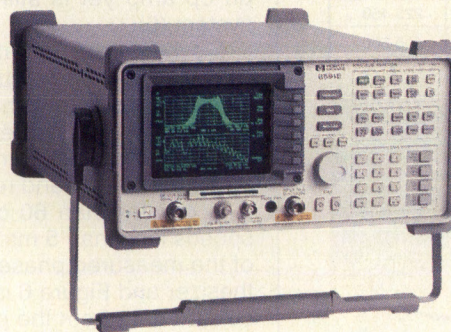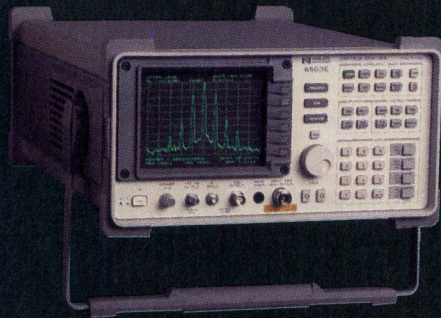Everything you expect from
a powerful new generation of
HP spectrum analyzers.



Except the price.

© 1992 Hewlett-Packard Co. TMSAD250

Introducing the HP 8590 & 8560 E-Series: more performance than anything at their price — less price than anything with their performance.

If advancing technologies and receding budgets make life difficult, it's time to look at HP's new generation of portable spectrum analyzers.

Start with the new HP 8590 E-Series, which offers an economical way to get surprising measurement power. Since there are 5 models, you buy *exactly* the frequency range you need. And

get a spectrum analyzer that's easy to use and can be configured for your specific application. All at a starting price of only \$11,500.

The remarkable HP 8560 E-Series delivers the kind of performance that until now was found only on expensive benchtop models. Yet the HP 8560 E-Series starts at only \$26,000 — and you get lower phase noise, narrower resolution bandwidths, and improved sensitivity. Clearly, this level of performance doesn't exist in any other spectrum analyzer at this price.

Of course, you'll want more details than we can provide here. So call

1-800-452-4844. Ask for Ext. 7149 and we'll give you an ordering guide and detailed product information. Plus one very important thing.

An early start on the next generation of test solutions.


There is a better way.



In Canada call 1-800-387-3867, Dept. 460.
U. S. list prices.


DESIGN SOLUTIONS FOR THE RF INDUSTRY

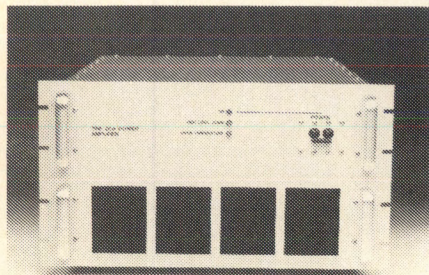The best of RF technology, quality, and design comes from Silicon Valley Power Amplifiers, a leading manufacturer of high-performance amplifiers and components.



AMPLIFIERS

Part Number	Power Output Watts	Gain dB	Frequency Range MHz
V-1000	1000	60	100-200
U-1000	1000	60	225-450
C-500	500	60	100-500

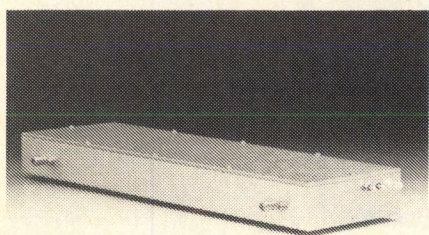

MODULES

Part Number	Power Output Watts	Gain dB	Frequency Range MHz
10-150-4	4	36	10-150
10-100-25	25	40	10-100
10-100-100	100	40	10-100
80-220-300A	300	60	80-220
220-500-300A	300	60	220-550
100-500-25	25	30	100-500
100-500-100	100	40	100-500
100-500-150	150	10	100-500

This high-quality hardware is backed by:

- Excellent service
- Customized design
- Fast response
- Expert technical support
- In-stock delivery
- Standard/special parts

For a free catalogue describing our complete range of power amplifiers and modules,
call 408.986.9700 today!



1530 O'Brien Drive Δ Menlo Park, CA 94025
408.986.9700 Δ Fax 408.986.1438

INFO/CARD 38

noise inside the loop bandwidth as there is not enough loop gain to reduce the VCO noise. The phase noise is dominated again by the op amp noise and VCO noise outside the loop bandwidth. It becomes clear that for low phase detector gains and large VCO tuning sensitivities the loop filter is a major noise contribution to the overall performance.

The op amp noise can be minimized by using a VCO which has a lower tuning sensitivity or a phase detector with higher gain. A sample and hold phase detector with high gain of 10 V/rad or more may significantly improve the overall phase noise by minimizing the op amp noise. A second approach would be to use a phase detector with a current driver output that does not require an op amp yet is still a type II control system (5).

A synthesizer operating at 1280 MHz with a reference frequency of 250 kHz was designed and analyzed using this program. The main design goal was for low phase noise using a commercial VCO, good sideband reference suppression greater than 60 dB, and switching speeds less than 5 ms. Figure 5 is a plot of the measured phase noise of the synthesizer and Figure 6 is a plot of the calculated data from the program. Note the small noise peak at an offset of 3 kHz in the measured data, this agrees with the program's prediction. The noise peak may be mistaken for a marginally stable loop with a low damping coefficient but the frequency step response shows that the loop is well behaved. There is quite good agreement between the measured data and calculated data. A comparison of results is shown in Figure 7, along with measured switching speed for a 200 MHz change. The simple switching speed approximation in the program gives a good first order approximation.

Figures 8 through 12 show a second design example of a synthesizer, to illustrate the operation of the program and the graphical outputs.

Conclusion

Using this program, it is easy to evaluate which component in a synthesizer is the dominating noise source at a given offset frequency from the carrier. The engineer can quickly evaluate several different synthesizer architectures for best performance without prototyping. In today's competitive market, an accurate synthesizer model is extremely valuable in minimizing development time. This program has been shown to have good agreement with measured data taken

from an actual synthesizer.

I would especially like to thank Mitch Randall and Tom Thomas for their valuable feedback in evaluating the program as it was developed. **RF**


This program is available on disk from the RF Design Software Service. See page 73 for ordering information.

References

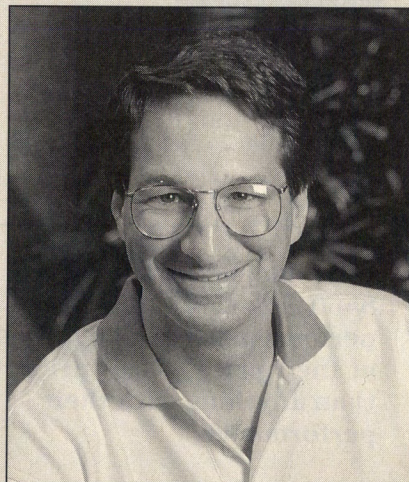1. William Egan, "Sampling Delay - Is It Real?," *RF Design*, February 1991.
2. Dan T. Gavin, "Phase Locked Loop Synthesizer Switching Speed Optimization and Measurement Techniques," *Proceedings*, RF Technology Expo, 1989, pp. 355-372.
3. Andrzej B. Przepelski, "PLL Primer — Part III," *RF Design*, July/August 1983.
4. W.P. Robins, *Phase Noise in Signal Sources: Theory and Applications*, Peter Peregrinus Ltd., 1982.
5. William C. Beam, Phillip J. Rezin, "Design Considerations for Fast Switching PLL Synthesizers," Watkins-Johnson Co. *Tech Note*, Vol. 18, No. 2, March/April 1991.

Our Software Contest Winner

Terry Hock is a Senior RF Engineer in the Atmospheric Technology Division of the National Center for Atmospheric Research, where he has worked since 1982. He has BSEE and MSEE degrees from the University of Colorado-Boulder. His experi-



ence is primarily in the design of many types of communications systems. Recently, Terry was responsible for setup and support of a group of advanced weather stations, part of a multi-national research effort studying the El Niño phenomenon in the South Pacific. He can be reached at NCAR, P.O. Box 3000, Boulder, CO 80307, or at (303) 497-8767.

Contest Winners Demonstrate Innovation and Hard Work

The 1993 RF Design Awards contest is over and two RF engineers have been awarded Grand Prizes. Terry Hock is the winner of the Software Contest with a PLL analysis program, and Ray Page picks up the top prize in the Design Contest for his passive RF transponder circuit.

This year's contest, the eighth running of the RF Design Awards, was the most difficult to judge. Last year's winners, Tom Hack (design) and Don Miller (software) joined RF Design's Consulting Editor Andy Przedpelski and Editor Gary Breed on the judging team.

In the Design Contest, the judges' challenge was to compare very dissimilar entries. Different entries emphasized design methods or circuit construction, covering the RF spectrum from low frequencies to microwaves. Within this mix of applications, finding the best combination of an innovative idea, a proper engineering problem-solving approach, and good documentation was a daunting task.

Judging the Software Contest was even more difficult. The entries had to be judged on both engineering merit and implementation in a computer program. The team had to examine the philosophic issue of which aspect is most important — difficulty of the engineering problem, technical accuracy of the computations, power and easy use of the program, and overall usefulness to the RF engineering community. Finding the right balance required more than just engineering expertise.

The Software Contest

At the top of software heap is Terry Hock, an RF design engineer at the National Center for Atmospheric Research. He is awarded the Version 3.5 software package from EEsos, Inc. Terry's program covers important phase-locked loop design and analysis factors using equations from linear control theory. Noise analysis received special treatment in his program, using Leeson's equation to calculate VCO phase noise, and adding the effects of the reference, phase detector and op amp loop filter. Steady-state response, switching speed estimation, and extensive plots of PLL

parameters are other major features. His complete write-up can be found on page 37 of this issue.

Terry notes that the program had an interesting period of development. Most of it was written during a research trip that included stays on various South Pacific islands, part of an international group studying the El Niño phenomenon that affects global weather patterns. Apparently, there was plenty of time available to write computer code after beachcombing and admiring the tropical flora and fauna!

Several other entries were also of extremely high quality, making judging very difficult. Among the best of the rest was a symbolic circuit analysis program by Henry Yiu of Beckman Instruments, which calculates AC or DC transfer functions in an interactive format. Henry's program is an excellent tool for obtaining a mathematical analysis of circuits.

Another software entry of note is the Tiny Electromagnetics Simulator by Jonathon Cheah of Hughes Network Systems. His program uses the Transmission Line Model to solve and plot the time domain response of a transmission line structure.

Other entries of note include a set of ECM analysis tools by Ronald Day of ITT Avionics, an S-parameter-based amplifier design aid by Dale Henkes of Philips Consumer Electronics, and a mixer analysis program by Richard Yaeger of AEL Defense Corp. These and other entries of merit will be published in RF Design over the next several months.

The Design Contest


Ray Page receives the Grand Prize of a Noise Com UFX-BER noise-based communications test instrument. Ray is an engineer at Wenzel Associates, and entered a design for a remotely-powered RFID transponder. His design recovers energy from an illuminating RF source to power a digital circuit. Meanwhile, the illuminating source is multiplied by two, and the resulting second harmonic is modulated to send data back to the interrogating unit.

Ray's circuit represents a mix of RF techniques: low-power digital circuit con-

siderations, patch antenna design, multiplier and filtering techniques, and extensive work in the test setup to illuminate the unit and detect the re-transmitted signal. With much work in the engineering community on short-range, low-power RF systems, this design should generate plenty of interest. The design is described in Ray's article on page 31.



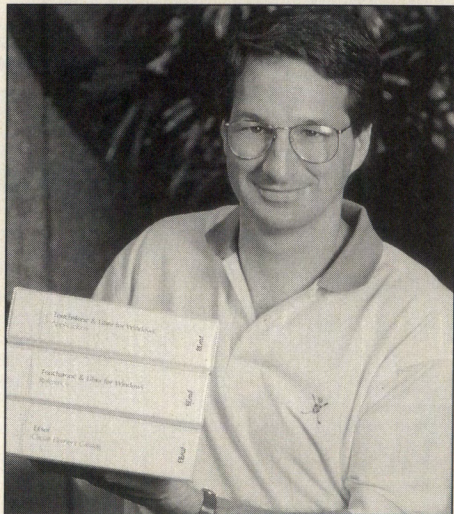Design winner Ray Page admires his new UFX-BER test set from Noise Com.



Terry Hock's software victory was rewarded with an EEsos Version 3.5 package.

A few other designs deserve special mention. Pavlo Bobrek of Loral Data Systems entered a high speed, high voltage isolated line receiver that was developed to minimize the effects of lightning-induced currents. Thomas McDermott and Roy Keeney of Toshiba America MRI described the design of a programmable gain amplifier with constant phase shift, and Paul Shuch of Pennsylvania College of Technology entered a novel circuit for testing radar detector sensitivity. You will be able to examine these circuit design entries, along with several others, in the coming months.

Conclusion


Once again, RF engineers have shown us that creativity and hard work go together. But, these winning entries are only a hint of the quality and depth of work that goes on in RF engineering labs around the world. Congratulations to the winners, to all those who entered, and to every other RF engineer — you all deserve recognition for your fine efforts.

RF

The Grand Prizes!

Software Contest — Version 3.5 for Windows from EEsof, Inc.

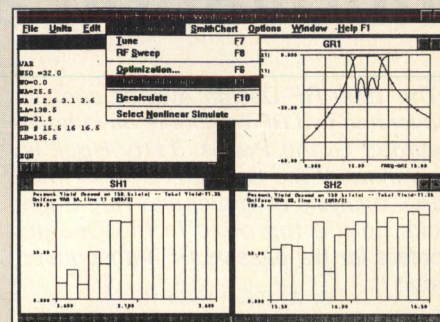Winner Terry Hock receives a complete design software package for the PC, operating under Windows 3.1. Version 3.5 from EEsof includes Touchstone linear analysis, Libra nonlinear simulation, and LineCalc transmission line design. This package uses the highly visual Windows environment for flexibility in graphical and physical circuit representation.





Design Contest — UFX-BER Test Instrument from Noise Com

Ray Page takes home the UFX-BER Noise Generator for bit error rate testing. Most new RF communications and control systems transmit digital information, and this instrument offers advanced testing of these systems by injecting White Gaussian noise into the IF or RF of the system. The unit displays the actual E_o/N_o or $(C+N)/N$.



Programmable Attenuators

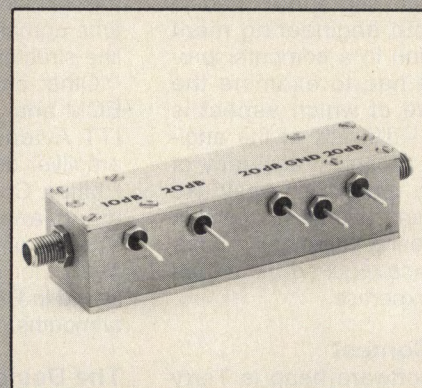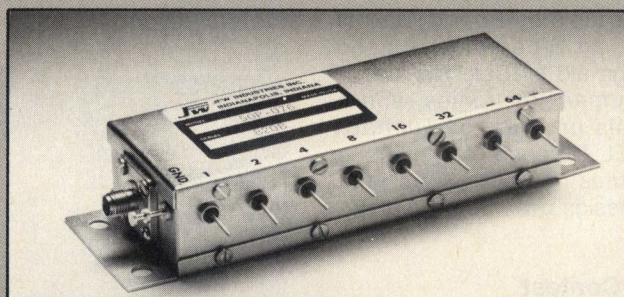50P-076
Frequency Range
DC-1000 MHz
Attenuation Range
0-127 dB in 1 dB steps



50P-766
Frequency Range
DC-5 GHz
Attenuation Range
0-70 dB in 10 dB steps

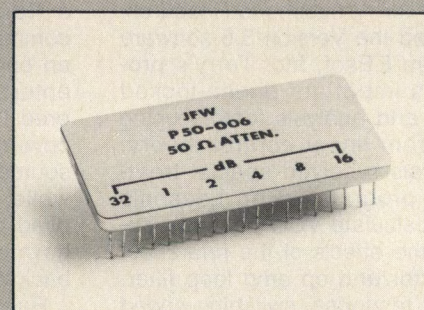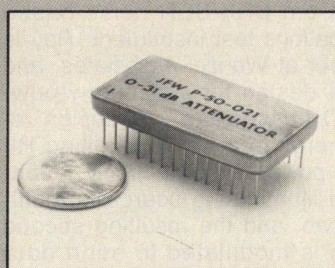P-50-021
Frequency Range
50-250 MHz
Attenuation Range
0-31 dB in 1 dB steps




P50-006
Frequency Range
10-600 MHz
Attenuation Range
0-63 dB in 1 dB steps



JFW Industries, Inc.
5134 Commerce Square Drive
Indianapolis, Indiana 46237
317-887-1340 Fax: 317-881-6790

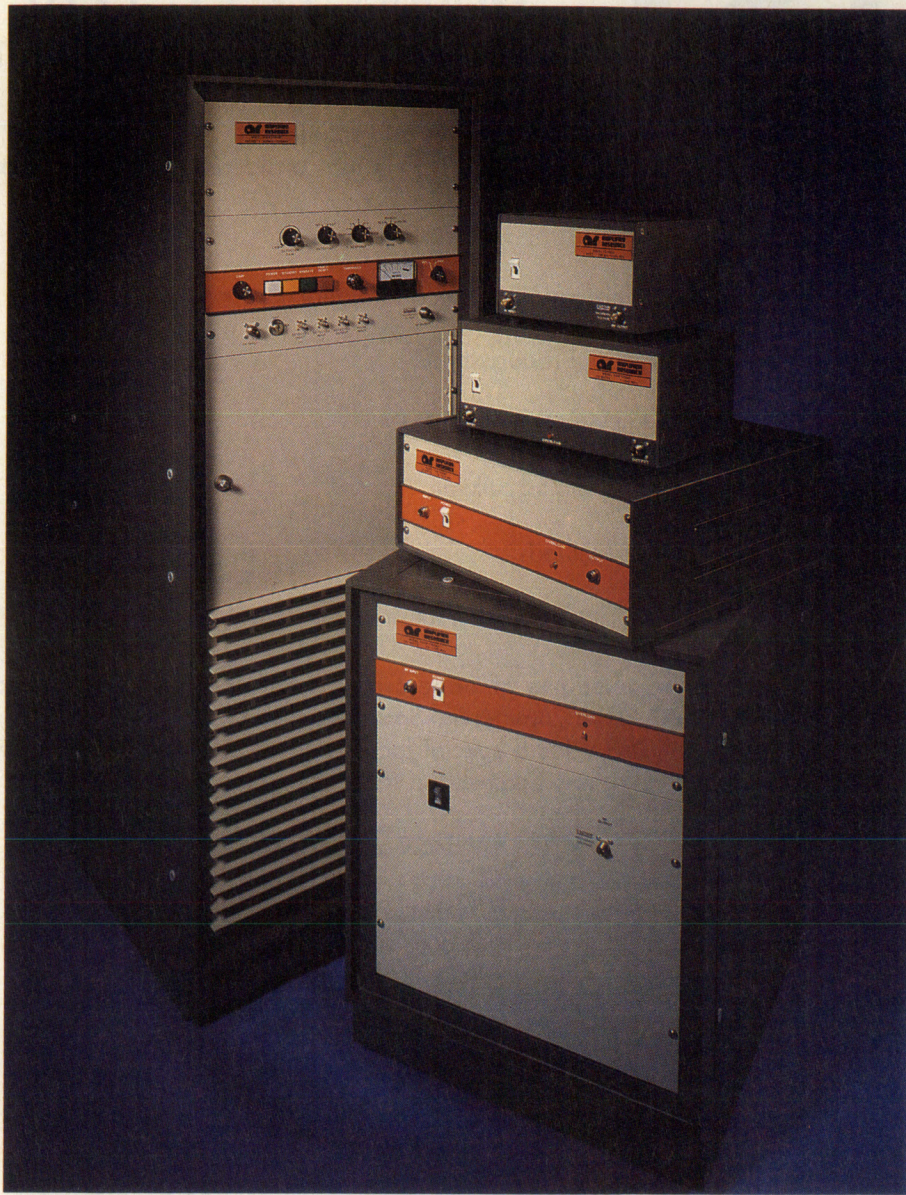When it gets lonely out there at 1 GHz, you'll be glad you have all this power.




The only amplifier that can deliver 500 watts through that balky decade from 100 to 1,000 MHz is our new Model 500W1000M7. That's the majestic one on the left, with the front-panel bi-directional power meter, ALC, and a bagful of other controls that will let you actually *enjoy* automatic sweep testing in your lab.

The 500W1000M7 presently heads our well-known "W" Series of all-solid-state linear amplifiers that cover four crucial decades of bandwidth from 100 kHz to 1 GHz. Today, you may need only 1 watt (the little portable on the top), or 5, or 10, or 25, or 50, or even 100 or 200 watts *minimum*—all with that fantastic bandwidth instantly available without tuning or bandswitching—a combination of power and bandwidth that's comforting when you work the outer reaches of the rf spectrum. Whenever your power requirements are today, they're sure to go up. And one of these days you're going to want a 500W1000M7.

The "W" Series is part of a complete line of AR amplifiers offering rf power up to 10 kilowatts for rf susceptibility testing, nmr spectroscopy, plasma/fusion research, and a host of other test situations that demand rf power of unconditional stability—immunity to even the worst-case load mismatch, shorted or open cable, wild swings of VSWR—with no fear of oscillation, fold-back, or system shutdown.

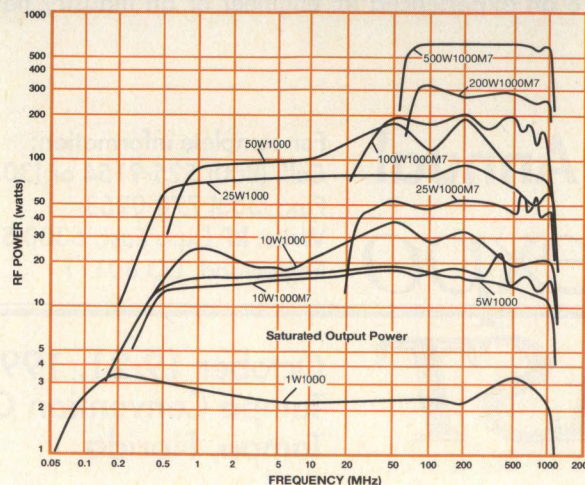You might learn a lot from our free booklet, "Guide to Broadband Power Amplifiers." Send for a copy. Or call our toll-free number (800-933-8181), which will connect you directly to one of our applications engineers.



AR AMPLIFIER RESEARCH

160 School House Road
Souderton, PA 18964-9990 USA
TEL 215-723-8181 • FAX 215-723-5688

For engineering assistance, sales, and service throughout Europe, call EMV:
Munich, 89-612-8054 • London, 908-566-556 • Paris, 1-64-61-63-29

INFO/CARD 40

RF expo **EAST**

October 19-21, 1993
Tampa Convention Center

RF Expo East showcases real-world engineering problems and solutions.

Here is a sample of the wide-range of topics in papers now being considered for this fall's show:

- Personal Communications
DECT, CT-2, PHP, PCS, PCN, Microcell
- Data Communications and DSP
Wireless networks, RF digital signal processing, analog to digital conversions
- Specialized Design Techniques
Medical, Automotive, Scientific, Military, Broadcast
- New Wireless Applications
Part 15, Spread Spectrum, RF-ID, Factory Automation
- Cellular and Mobile Radio
Circuit Design, components, antennas, digital cellular
- Test, Measurement and Analysis
Test Methods, CAD/CAE, Analytical Methods
- Essential RF Circuits
Oscillators, Amplifiers, RF Power, Mixers, Filters, Synthesizers

In addition to the complete course schedules of papers and tutorials, RF Design is proud to announce the introduction of RF EXPO PLUS: Commercial Space Applications.

With this program, RF Expo East 1993 adds a special focus area to our already comprehensive technical program! Included will be a three-day engineering track targeting Commercial Space Applications, with such topics as:

- LEO Systems
- INMARSAT
- IRIDIUM
- GLOBECOM
- GPS/NAVSTAR
- Video Compression
- Direct Satellite Broadcast
- Satellite Paging
- Space-Qualified Performance
- Remote Sensing and Imaging

In addition, you'll see the latest in RF technology.

As more than 100 exhibiting companies bring their top engineering and marketing people to talk to you about: components, test equipment, system components, transmission line components, systems EMC/EMI products, packaging, and RF design-related services.

Whether you are an experienced RF engineer or an industry newcomer, RF Expo East has something for you.

Eighth Annual
RF expo
EAST

For complete information:

Call: (800) 525-9154 or (303) 220-0600

Fax: (303) 770-0253

**Write: RF Expo East, 6300 S. Syracuse Way, #650,
Englewood, CO 80111**

October 19-21, 1993
Tampa Convention Center
Tampa, Florida


Sponsored by *RF Design* magazine

High Power Hybrid Couplers

A new family of high power ninety degree hybrid couplers which cover the 400-1000 MHz range has been introduced by RF Power Components. Designed for power combining and dividing, these models feature backward wave stripline designs with custom dielectrics. This technology allows for use in high power applications. These high power couplers are provided in three models — models RFP401-102-90-200, RFP401-102-90-400 and RFP401-102-90-800 offer 200, 400 and 800 W CW power handling, respectively. The 400 to 1000 MHz frequency range is unique to the industry since similar competitive models typically

cover the 500 to 1000 MHz range and only offer power capabilities up to 400 watts. High isolation, low insertion loss and good phase balance are additional features provided in all three devices. The couplers are available in non-magnetic drop-in versions which are ideal for medical equipment applications. Connectorized versions are also available, with SMA connectors provided in the 200 W model and type "N" connectors in the 400 and 800 W models. Sizes range from 1.35 × 0.50 × 0.12 inches for the 200 W device to 2.65 × 2.65 × 0.35 inches for the 800 W device.

RF Power Components, Inc.
INFO/CARD #250

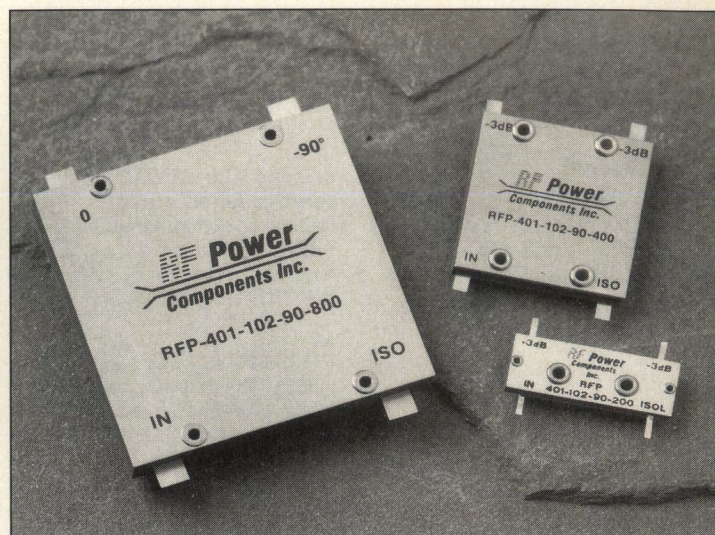

Power Grid Tubes

Svetlana Electron Devices of St. Petersburg, Russia and Huntsville, Alabama has announced a line of power grid tubes. The tubes, many of which have broadcasting applications, are exact, plug-compatible replacements for tubes currently




manufactured in the United States, Great Britain and elsewhere. The initial line of Western-style, plug-compatible tubes includes the Svetlana 4X150A, 4CX250B, 4CX250BC, 4CX350A, 4CX350AC, 4CX15000A, 4CX15000J, 5CX1500A and 5CX1500B. In addition to the plug-compatible tube types, Svetlana offers several tubes new to the Western market, including the 4CX800A and 4CX1600A, which are well suited for SSB linear amplification at 750 PEP and 1500 W CW key down.

Svetlana Electron Devices, Inc.
INFO/CARD #249

Wireless System Modules

Sciteq announces a new line of modular solutions for wireless. This new series of aggressive Sciteq products for wireless now includes an upconverter, downconverter, AGC amplifier, power module, and a wideband synthesizer. The synthesizer, the VDS-9001, is a low-cost, DRO-based synthesizer that covers all PCS bands up to 1 GHz, and supports all the common PCS step sizes of 25, 30, 50 and 100 kHz. Phase noise is excellent at -70 dBc. The interface is simple, the unit in-

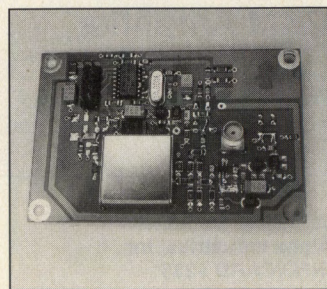


cludes an onboard crystal reference, and the complete synthesizer draws only 30 mA at +5 VDC. Price of the VDS-9001 is under \$100, even in modest quantities, and availability ranges from stock to 12 weeks depending upon quantity and band selected.

Sciteq Electronics, Inc.
INFO/CARD #248

Planar Electromagnetic Simulator

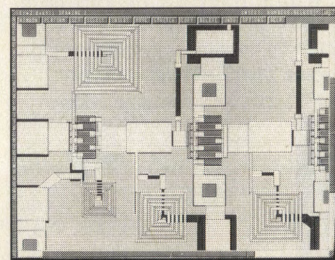Momentum from Hewlett-Packard computes the S-, Y-, or Z- parameters of arbitrary multi-layer planar patterns. Patterns such as matching networks, filters, transmission-line discontinuities and other passive circuitry



found on a PC board, hybrid or MMIC design are efficiently and accurately solved with this new product. Momentum uses the method of moments for fast simulation, and its computer-generated grid composed of arbitrarily sized rectangular and triangular cells allows accurate simulation of arbitrarily shaped planar structures. Momentum allows open-boundary simulations, letting it account for radiation losses without requiring a box or enclosure. The simulator is available both as part of the HP RF or Microwave Design Systems, or as a stand-alone program with links to EEsof and Compact circuit simulators.

Hewlett-Packard Co.
INFO/CARD #247

DACs Designed for DDS

Qualcomm has introduced the Q2500 series of digital-to-analog converters (DACs). The series is well suited for use with high-speed direct digital synthesis (DDS) and other high speed applications. The Q2510 and Q2520 devices offer excellent spectral purity performance and 10-bit or 12-bit digital inputs, respectively. The 10-bit Q2510 is TTL-interface compatible and boasts update speeds to 100 Msps. The device offers fast settling time (4.5 ns to $\pm 1/2$ LSB), low power consumption (1.2 W), and low glitch impulse (1.5 pV-s). The 12-bit Q2520 updates to 80 Msps,




settles to $\pm 1/2$ LSB in 27 ns, consumes only 800 mW, and has glitch impulse of 28 pV-s. Both devices are available in 28-pin PDIP and COIC packages, operating over the -25 to +85 degree C temperature range. Prices for the Q2510 start as low as \$38.10 (qty. 1000); the Q2520 starts at \$34.50 (qty. 1000).

Qualcomm, Inc., VLSI Products Group
INFO/CARD #246

Product Spotlight: ICs

Receiver Front End

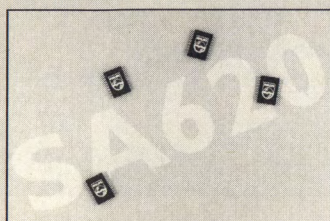Philips Semiconductor announces the first integration of a low-noise amplifier, mixer and



voltage controlled oscillator in a single 3 V device. The SA620 is a complete 3 V front end solution targeted for portable cellular phones, cordless telephones, RF data links, UHF frequency conversion and spread spectrum receivers. The LNA exhibits a 1.6 dB noise figure and 12 dB power gain at 900 MHz. The active mixer supplies 6 dB power gain with an 8 dB noise figure. The SA620 consumes 8.8 mA at 3 V and is enclosed in the SSOP 20 package. The device is available now and is priced at \$5.22 in quantities of 1000.

Philips Semiconductor
INFO/CARD #245

Viterbi Decoder ASIC

Stanford Telecom's ASIC and Custom Products Division announces the STEL-2060, a Viterbi decoder operating at data rates up to 45 Mbps. The STEL-

2060 operates at constraint length $K=7$, has multiple coding rates, internal depuncturing capability, differential decoding, an invert G2 descrambler, and an internal BER monitor and counter. The STEL-2060 is currently available and is priced less than \$20 in commercial volume quantities.

Stanford Telecom
INFO/CARD #244


Front-End Circuit

GEC Plessey has released its latest 1 GHz radio receiver front-end circuit, the SL6444. The device integrates a low-noise amplifier and double balanced mixer in a single 14-pin small outline package. The function blocks may be used independently. The SL6444 operates from 2.7 V supplies, consumes only 2 mA, has 19 dB gain, 3 dB noise figure and third order intercept point of -12 dBm. It is available in a 14-pin small outline package and is priced at \$3.18 in 1000s.

GEC Plessey Semiconductors
INFO/CARD #243

Low Noise Op Amp

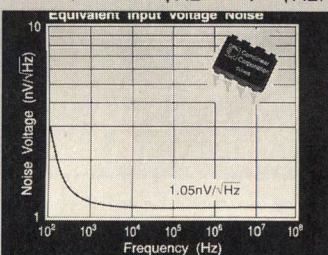Comlinear's CLC425 combines a wide-gain bandwidth (1.7 GHz) with an ultra-low input noise ($1.05 \text{ nV}/\sqrt{\text{Hz}}$, $1.6 \text{ pA}/\sqrt{\text{Hz}}$)



and excellent DC characteristics (100 uV v.o.s. , 2 uV/degree C drift). The CLC425 employs a traditional voltage-feedback topology and operates from a $\pm 5 \text{ V}$ supply.

Comlinear Corp.
INFO/CARD #242

Prescalers

Motorola has introduced seven new prescaler products offering toggle frequency ranges of 1.1, 2.0 and 2.8 GHz, a variety of divide by ratios, low power consumption and supply voltages of 2.7 to 5.0 VDC or 4.5 to 5.5 VDC. Many devices are available in both 8-pin DIP and SOIC packages. Suggested resale pricing ranges from \$4.03 to \$6.52 in 1000-piece quantities.

Motorola Semiconductor
INFO/CARD #241

DC-Restored Video Amp

The EL4089C is an 8-pin DC-restored monolithic amp subsystem that includes a high quality video amplifier and a DC nulling sample-and-hold amplifier that will stabilize video performance. The device has a 70 MHz bandwidth, 0.02 percent differential gain and 0.1 degree differential phase. The EL4089C is available in an 8-pin P-DIP and 8-lead small outline packages at \$5.75 and \$5.85 respectively in 100-unit quantities.

Elantec, Inc.
INFO/CARD #240

GSM Amplifier

The GSM Low Noise Amplifier from AT&T Microelectronics is a thin film, balanced amplifier design. It operates in the 890 to

915 MHz frequency range and exhibits exceptionally low noise (1.3 dB max.) and high third order intercept (38 dBm). While tailored for the GSM band, it provides similar performance in the 824 to 849 MHz AMPS band.

AT&T Microelectronics
INFO/CARD #239

Transfer Switch


Mini-Circuits has introduced the model MSWT-4-20 GaAs transfer switch. The surface mount device offers repeatability (typically 4.5 sigma from mean), wide bandwidth (DC-2000 MHz), low video leakage to 50 ohm ports (typ. 15 mVpp at 500 MHz video BW), and very fast switching (4 ns typ.). Pricing for the MSWT-4-20 is just \$5.75 each for quantities of 1 to 9 units.

Mini-Circuits
INFO/CARD #238

Video Op Amps

Linear Technology offers the LT1252/53/54 family of low cost, 100 MHz video amplifiers. The LT1252 is a single amplifier for \$1.75; the LT1253 is a dual for \$2.49, and the LT1254 is a quad for \$4.49. These current feedback amplifiers operate over supply voltages from single 5 V to $\pm 12 \text{ V}$.

Linear Technology Corp.
INFO/CARD #237

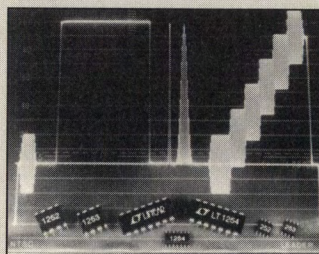

SEMI-CONDUCTORS

Power Modules

Microwave Technology is expanding its "SLAM" line of ultra-linear, class A power modules operating in the HF band. The SLAM-0122 is a self-biased, push-pull device that operates at 50 W with 14 dB typical gain. The SLAM-0133 is a single-ended device with 10 W power output and 13.5 gain.

Microwave Technology, Inc.
INFO/CARD #236

Face Bondable Diode

Alpha Industries introduces its new Metal Electrode Leadless Face Bondable (MELF) diode. The rectangular surface mount package lends itself to high volume manufacture and has no wire bonding internally. The device is capable of three times greater power handling than round MELFS with tungsten plug

vs. copper domet.
Alpha Industries, Inc.
INFO/CARD #235


Broadband Detectors

Metelics introduces a line of detectors that offer high sensitivity and low VSWR. The detectors are available in a number of packages. Depending on the model, the frequency range is 2 to 8 GHz or 8 to 18 GHz.


Metelics Corp.
INFO/CARD #234

Power FETs

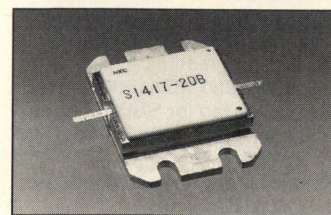Available from California Eastern Labs are high efficiency, L-band, S-band and UHF power FETs. The 20 W NES1417-20B



MIXERS UNPRECEDENTED IN VALUE.

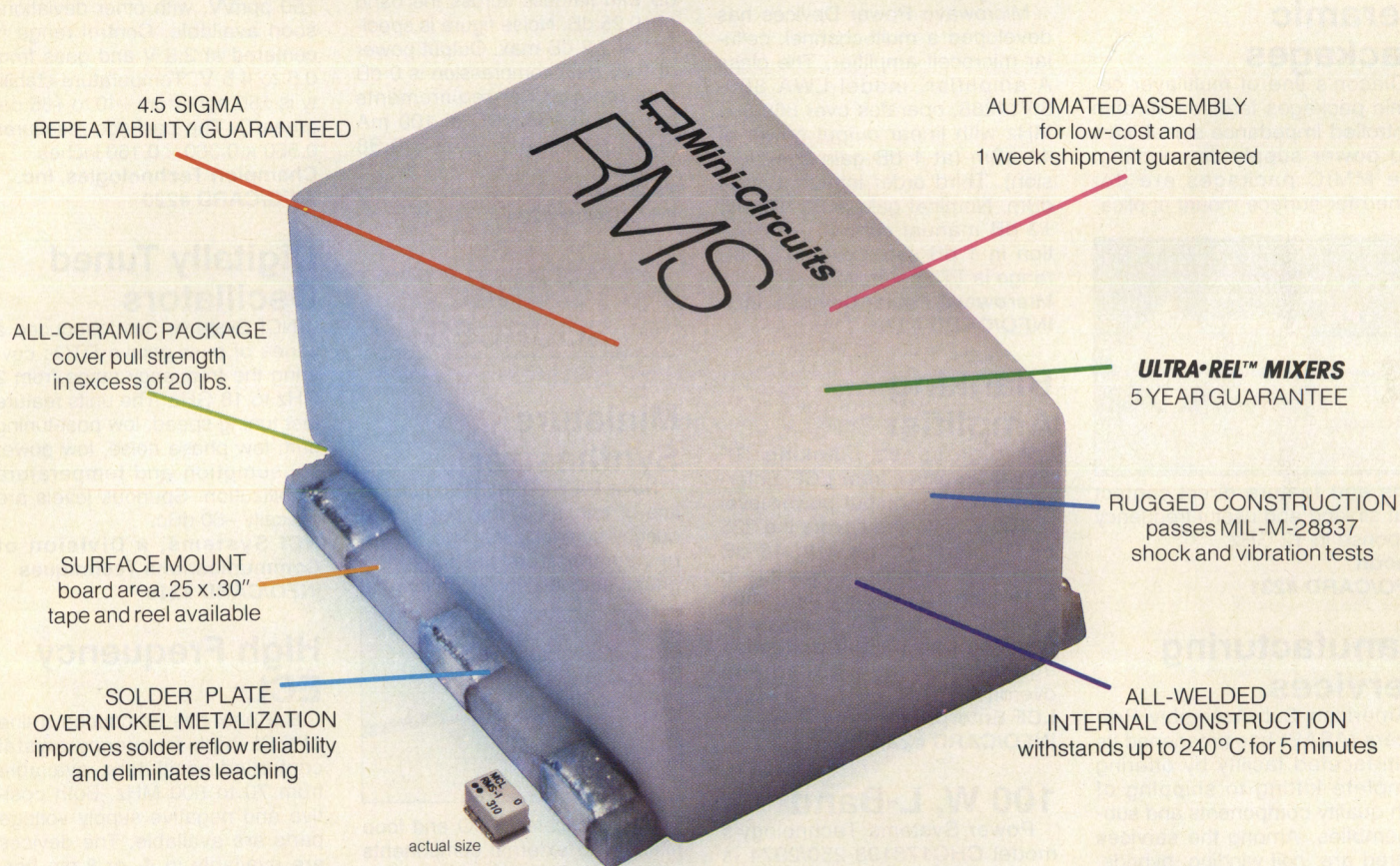

ALL-CERAMIC 5 to 3000MHz **\$395**
from (10-49 qty)

Now you can buy very low-cost, high-performance commercial mixers with the ruggedness and reliability required for military applications. That's value!
... Only from Mini-Circuits.

Model	LO (dBm)	Freq. (MHz) LO,RF	IF	Midband, dB			\$ ea. (10-49)
				Conv. Loss	Isol L-R	L-I	
RMS-11X	+7	5-1900	5-1000	7.1	29	31	3.95
RMS-11F	+7	350-2000	DC-400	5.5	31	30	4.95
RMS-30	+7	200-3000	DC-1000	6.5	26	22	6.95
RMS-25MH	+13	5-2500	5-1500	7.5	32	32	7.95

finding new ways ...
setting higher standards



Mini-Circuits®

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.

CUSTOM PRODUCT NEEDS... Let Our Experience Work For You.

F166 REV. ORIG.

INFO/CARD 41


covers the 1.4 to 1.7 GHz range; the 20 W NES1818-20B covers 1.7 to 1.95 GHz applications; the 10 W NE345L-10B covers L- and S-band and UHF frequencies.

California Eastern Laboratories, Inc.
INFO/CARD #233

TOOLS, MATERIALS AND MANUFACTURING

Ceramic Packages

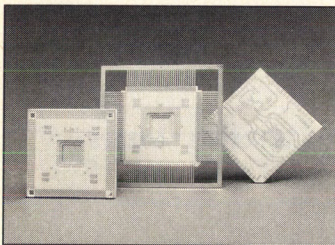Diacon's line of multilayer ceramic packages features 50 ohm controlled impedance signal lines and power supply de-coupling. The MMIC packages are designed for surface mount applica-



tions and feature direct contact heat sinking and useful frequency response to 12 GHz.

Diacon
INFO/CARD #231

Manufacturing Services

American Sub-Assembly Producers (ASAP) has broadened its multi-faceted facility by offering complete kitting to shipping of high quality components and sub-assemblies. Among the services offered are: coil winding, hybrids, mechanical/electro-mechanical assembly and RF testing. ASAP is completely compliant with MIL Spec. 45208 and thoroughly ESD protected. All manufacturing personnel are certified to MIL Class C assembly requirements.

American Sub-Assembly Producers
INFO/CARD #230

Tuning Wrench

Coilcraft's Trituner™ tuning wrench is a unique 3-in-1 tool for adjusting variable components. The non-magnetic tool has one end stepped with a hex tip for

1/428 cores and a smaller hex tip for 10-32 cores. The other end has a molded-in ceramic straight tip for 6-32 slotted cores. Trituners cost \$1.39 each in a pack of 12 dozen.

Coilcraft
INFO/CARD #229

AMPLIFIERS

Cellular Microcell Amplifiers

Microwave Power Devices has developed a multi-channel, cellular microcell amplifier. The class A amplifier, model LWA 880-30/14288, operates over 869-894 MHz with linear output power of 44 dBm (at 1 dB gain compression). Third order intercept is 54 dBm. Nominal gain is 30 dB with ± 3 dB manual control. Attenuation in 1 dB steps over a 30 dB range is TTL controlled.

Microwave Power Devices, Inc.
INFO/CARD #228

Blanking Amplifier

A high-speed blanking RF power amplifier from LCF Enterprises has an output power level of 100 W CW and covers the 225 to 400 MHz range with 40 dB gain. The amplifier is available in a 19 inch rack-mount air-cooled system for \$3950 each, with blanking and built-in protection against thermal overload and overdrive.

LCF Enterprises
INFO/CARD #227

100 W, L-Band

Power Systems Technology's model CHC178198-250/2974 is designed and packaged for mounting on the external structure of a satellite earth station antenna. Covering 1750 to 1850 MHz, the amplifier offers 250 W min. class C output power. Input VSWR is 1.3:1 and the output is circulator protected to infinity for any phase.

Power Systems Technology, Inc.
INFO/CARD #226

Compact Amplifiers

Microwave Solutions introduces broadband amplifiers with

a 120 VAC power supply. Model MSH-3494201-PS operates from 0.1 to 3.0 GHz. Typical output power is +10 dBm and gain is 26 dB, with other gain and power options available. With power supply, this amplifier measures $5.4 \times 3.0 \times 1.9$ inches.

Microwave Solutions, Inc.
INFO/CARD #225

Low Noise


A low noise amplifier, model ANR 17835, operates over the cellular frequency range of 825 to 845 MHz and gain of 17 dB ± 1.0 dB with flatness across the band of ± 0.25 dB. Noise figure is specified at 2.2 dB max. Output power at 1 dB gain compression is 0 dB min. Input power requirements are +15 to +30 VDC at 100 mA max. Size is $0.5 \times 0.9 \times 0.38$ inches.

TRM, Inc.
INFO/CARD #224

SIGNAL SOURCES

Miniature Synthesizer

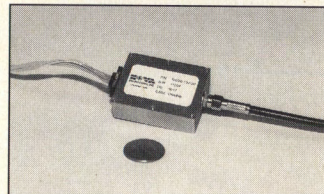Nova Engineering introduces a line of miniature, low power frequency synthesizers. The NS-series synthesizers are fully integrated modules, including internal



TCXO, prescaler, VCO and loop filter — no external components are required. The series covers 100 to 1100 MHz, with any model tuning in a 1.5:1 range in 20 or 25 kHz steps. All models in the series share a common $2.00 \times 1.50 \times 0.625$ inch enclosure.

Nova Engineering, Inc.
INFO/CARD #223

Low Noise Crystal Source

Techtrol Cyclonetics' 2000A-SC series ovenized crystal source features low phase noise and small size. The unit is available at frequencies between 40 and 125 MHz, meeting frequency

stabilities up to $\pm 1 \times 10^{-7}$. The oscillator meets an improved phase noise level of -152 dBc at 1 kHz and a floor of -169 dBc at 100 kHz offset. Harmonics are down at -26 dBc. The unit is housed in a circuit board mountable $2.0 \times 2.0 \times 1.0$ inch package.

Techtrol Cyclonetics, Inc.
INFO/CARD #221

SMT VCXO

The K1526 series of surface mount VCXOs is available within the frequency range of 2.0 to 33.0 MHz. Deviation sensitivity is ± 50 ppm/V, with other deviations soon available. Control range is centered at 2.5 V and goes from 0.5 to 4.5 V. Temperature stability is ± 50 ppm from -40 to $+85$ degrees C. The package measures $0.560 \times 0.360 \times 0.160$ inches.

Champion Technologies, Inc.
INFO/CARD #220

Digitally Tuned Oscillators

NCI Systems has introduced a series of multi-octave DTOs covering the frequency range from 2 GHz to 18 GHz. The units feature fast tuning speed, low post-tuning drift, low phase noise, low power consumption and temperature stabilization. Spurious levels are typically -60 dBc.

NCI Systems, a Division of Communications Techniques
INFO/CARD #219

High Frequency ECL

SaRonix has introduced a line of ECL high frequency crystal controlled oscillators, available from 70 to 600 MHz. Both positive and negative supply voltage parts are available. The devices are available in 4- or 8-pin hermetically sealed 14-pin DIP compatible metal cases.

SaRonix
INFO/CARD #218

DISCRETE COMPONENTS

Chip Inductors

Toko America has expanded its LL2012F series of ceramic multi-layer chip inductors, adding four new values. Inductors with values of 3.3, 2.7, 2.2 and 1.8 nH were added. Members of the se-

ries have a footprint of 2.0×1.2 mm and a height of less than 1 mm. Typical Qs are over 40 at 600 MHz, with self resonant frequencies of up to 6 GHz.

Toko America, Inc.
INFO/CARD #217

Non-Magnetic Trim Cap

A line of non-magnetic, high-Q variable capacitors have a diameter of 0.275 inches while maintaining a high voltage rating. The capacitance spans 1 to 35 pF with a 2 kV peak test voltage.

Polyflon Co.
INFO/CARD #216


Quartz Crystals

Mercury United Electronics is introducing the UM-1, UM-5 and UM-4 series of quartz crystals. The UM-1 is 8 mm high, the UM-5 6 mm high, and the UM-4 is 4.7 mm high. The UM-1 SLIM is 2.6 mm thick versus the UM-1's 3.2 mm thickness. All crystals cover frequency from 10 MHz fundamental mode to 160 MHz 5th overtone. Frequency stability is ± 10 ppm over -10 to $+60$ degrees C.

Mercury United Electronics, Inc.
INFO/CARD #214

Miniature Trimmers

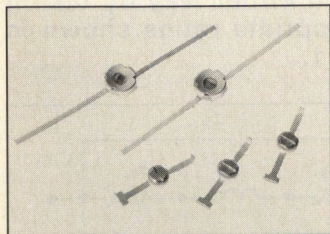Voltronics is producing the RP 0.094 inch and RD 0.14 inch diameter one-half turn ceramic trimmers. These designs are stable because of a compact inter-



nally supported structure. The RP tunes from 5.5 to 20 pF and the RD tunes from 5 to 25 pF. Costs are \$0.58 and \$0.50 in quantities of 1000 and \$0.44 and \$0.34 in quantities of 10,000.

Voltronics Corp.
INFO/CARD #213

Small Trim Caps

AVX/Kyocera's CTZ2 and CTZ3 trimmer capacitors have

maximum dimensions of 3.0 mm and 4.5 mm, respectively. Both trimmer capacitors feature high capacitance in a small size and low profile. The trimmers are usable with reflow soldering and are washable.

AVX Corp
INFO/CARD #212

TEST EQUIPMENT

Electrooptic Spectrum Analyzer

Photonic Systems now offers two Bragg-cell-based spectrum analyzers. The AOS-1000 has 1 GHz instantaneous bandwidth and 1000 frequency channels. The AOS-1000X4 has 4 GHz instantaneous bandwidth and 4000 frequency channels. Both instruments have 1 MHz channel bandwidth.

Photonic Systems, Inc.
INFO/CARD #211

RF Exposure Probes

Narda has introduced two probes shaped in accordance with the new IEEE C95.1-1991 standard for human exposure to RF/microwave energy. Models 8722B and 8732 monitor electric and magnetic fields, respectively, and have a detection sensitivity that mirrors the new standard.


Loral Microwave - Narda
INFO/CARD #210

Antenna/Transmission Line Testing

Using one of Direct Conversion Technique's scalar network analyzers and their newly introduced DI-8 data interface, frequency swept measurements such as return loss can be quickly made on site and stored to disk. In addition, FFT capability allows sweep information to be shown in the time domain, yielding distance-to-fault information.

Direct Conversion Technique, Inc.
INFO/CARD #209

Radio Links

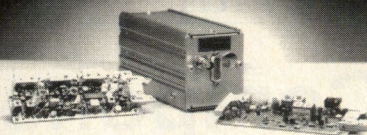

- ▶ Eliminate leaseline and wireline costs
- ▶ Aggressively priced with quantity discounts available
- ▶ Transmitter and receiver links in VHF, UHF and 900 MHz are designed specifically for high-performance data transmission
- ▶ Utility data system accommodates audio inputs (modem tones) or TTL-level digital inputs
- ▶ RS-232 radio modems available in VHF, UHF and spread-spectrum (unlicensed) frequencies
- ▶ A two-way radio manufacturer for more than 30 years

Repcor Aerotron-Repcor Sales, Inc.
1-800-950-5633

2400 Sand Lake Road
Orlando, Florida 32809

Dealer Inquiries Invited

INFO/CARD 42



CRYSTALS

70KHz-200MHz

OSCILLATORS

70KHz-200MHz

TCXO, VCXO, TCVCXO

4 MHz-125MHz

**Alignment Oscillators
Crystal and Oscillator
Accessories**

Call or fax TOLL FREE for information



INTERNATIONAL CRYSTAL MFG. CO., INC.

P.O. Box 26330 • 729 W. Sheridan • Oklahoma City, OK 73126-0330 • (405) 236-3741
FAX (405) 235-1904 • Toll Free Phone 1-800 725-1426 • 24 Hour Toll Free Fax 1-800 322-9426

INFO/CARD 43

RF Component Modeling for CAD/CAE

By Les Besser
Besser Associates

This article offers a tutorial review of lumped passive RLC component models, including parasitic effects and losses. For simplicity, only first order resonances are considered, although second-order effects are also discussed. Most of the material presented here is taken from a one-week long continuing education course entitled "RF/High Speed Circuit Components: Measurements, Models and Data Extraction" (1).

During the 1970s and 80s defense-supported R&D created significant progress in the modeling of active microwave devices and various forms of physical transmission lines. At the same time, RF passive component models attracted little attention. Researchers felt that passive lumped components were very "simple" and their modeling would pose little challenge. As a result, RF components were represented by their ideal forms in early CAE programs. Recent cutbacks in military microwave spending prompted the CAE industry to pay attention to lumped-element components for commercial RF products. While we are still far from having libraries with dependable lumped models, RF component modeling is becoming an increasingly important effort and should play a more significant part in modern CAE.

Q of Physical Inductors and Capacitors

Before looking at equivalent circuits, let's define an important circuit parameter. The quality (Q) factor of a reactive component is defined by the ratio of stored energy over dissipated energy that can be expressed in series or parallel form:

$$Q = Q_S = \frac{X_S}{R_{SE}} = Q_P = \frac{R_{PE}}{X_P} \quad (1)$$

where:

X_S is the equivalent series reactance of the series equivalent circuit.

X_P is the equivalent parallel reactance of the parallel equivalent circuit.

R_{SE} is the total equivalent series resistance of the series equivalent circuit.

R_{PE} is the total equivalent parallel resistance of the parallel equivalent circuit.

The parallel and series circuits shown in Figure 1 represent a series/parallel conversion at a specified frequency, maintaining the input Q.

RLC Component Models

Up to 1 GHz, relatively simple lumped equivalent circuits may be used to accurately describe the behavior of RLC components in chip and discrete forms. Above that frequency, depending on the size of the components, modeling may require more detailed circuits and distributed (transmission line) elements. However, most surface mount components can be adequately described by the lumped models, even up to 2 GHz.

Resistors — Figure 2 illustrates the equivalent circuit of a typical resistor, using lumped circuit elements, assuming that parasitic self-inductance and capacitance may be combined into single components L_S and C_P . Depending on the physical form of the resistor, the nominal resistance, R_N , may or may not be frequency dependent. For example, if the thickness of the resist layer does not exceed skin depth, the resistance is virtually independent of frequency. The second resistor of the model R_S represents the lead and contact resistances; they may need to be separated from the nominal resistance due to different temperature and frequency dependencies.

For low value resistors the series inductance is the prime parasitic, meaning that the total impedance of the part increases with frequency. At some point the parallel capacitance creates a low-Q parallel resonance with the inductance of the series branch, from that frequency the terminal impedance of the part declines. Below the resonant frequency the physical resistor behaves inductively while above resonance it looks like a lossy capacitor. If the nominal resistance is relatively high (several hundred ohms), the series inductance may be

neglected and the parallel capacitor represents the prime parasitic. In this case the impedance declines as the frequency increases; approximating the behavior of a parallel RC (see Figure 3). While the parallel capacitance may be relatively small, i.e. a fraction of a picofarad, its effect may need to be considered. For example, if the resistor is used as a collector-to-base DC bias resistor, even a small parallel capacitance forms a significant feedback path at RF.

Inductors — Figure 4 shows the first order approximation of an RF inductor equivalent circuit. In this model the series resistance R_S represents frequency dependent ohmic self-resistance of the inductor which forms a relatively high Q series equivalent circuit with the nominal inductance. The parallel capacitor represents the inter-winding and terminal capacitances lumped together into a single

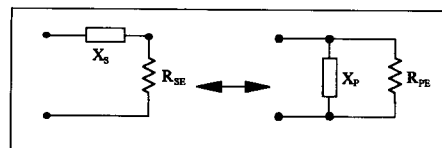


Figure 1. Lossy reactive elements may be represented by these equivalent circuits. Q may be computed either way by taking the appropriate ratios shown in equation 1.

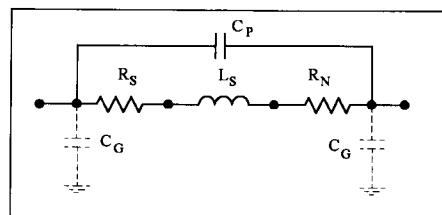


Figure 2. Lumped RF equivalent circuit of a resistor. R_S and R_N may both be frequency dependent. L_S represents the total parasitic self-inductance and C_P the self-capacitance. If the resistor is realized above a ground-plane, the additional stray capacitances C_G also exist.


DC-2000 MHz AMPLIFIERS

In plastic and ceramic packages, for low-cost solutions to dozens of application requirements, select Mini-Circuits' flatpack or surface-mount wideband monolithic amplifiers. For example, cascade three MAR-2 monolithic amplifiers and end up with a 25dB gain, 0.3 to 2000MHz amplifier for less than \$4.50. Design values and circuit board layout available on request.

It's just as easy to create an amplifier that meets other specific needs, whether it be low noise, high gain, or medium power. Select from Mini-Circuits' wide assortment of models (see Chart), sketch a simple interconnect layout, and the design is done. Each model is characterized with S parameter data included in our 740-page RF/IF Designers' Handbook.

All Mini-Circuits' amplifiers feature tight unit-to-unit repeatability, high reliability, a one-year guarantee, tape and reel packaging, off-the-shelf availability, with prices starting at 99 cents.

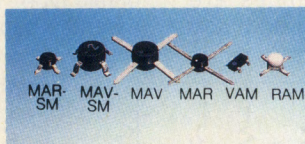Mini-Circuits' monolithic amplifiers...for innovative do-it-yourself problem solvers.



Models above shown actual size

from **99¢** Unit price \$ (25 qty)

PLASTIC SURFACE-MOUNT

add suffix SM to model no. (ex. MAR-ISM)

CERAMIC SURFACE-MOUNT

PLASTIC FLAT-PACK

	MAR-1	MAR-2	MAR-3	MAR-4	MAR-6	MAR-7	MAR-8	MAV-11
1.04	1.40	1.50	1.60	1.34	1.80	1.75		
1.15	1.45	1.55	1.65					2.15
4.95	4.95	4.95	4.95	4.95	4.95	4.95	4.95	
1.10	1.40	1.50	1.60					2.10
0.99	1.35	1.45	1.55	1.29	1.75	1.70		
1000	2000	2000	1000	2000	2000	1000	1000	
18.5	12.5	12.5	8.3	20	13.5	32.5	12.7	
1.5	4.5	10.0	12.5	2.0	5.5	12.5	17.5	
5.5	6.5	6.0	6.5	3.0	5.0	3.3	3.6	

Notes: + Frequency range DC-1500MHz

++ Gain 1/2 dB less than shown

designer's amplifier kits

DAK-2: 5 of each MAR-model (35 pcs), only \$59.95

DAK-2SM: 5 of each MAR-SM model (35 pcs) only \$61.95

DAK-3: 3 of each MAR, MAR-SM, MAV-11, MAV-11SM (48 pcs) \$74.95


designer's chip capacitor kit

KCAP-1: 50 of 17 values, 10pf to 0.1µf (850 pc), \$99.95

chip coupling capacitors at .12¢ each (50 min.)

Size (mils)	Value
80 x 50	10, 22, 47, 68, 100, 220, 470, 680 pf
80 x 50	1000, 2200, 4700, 6800, 10,000 pf
120 x 60	.022, .047, .068, .1µf

Typical Circuit Arrangement

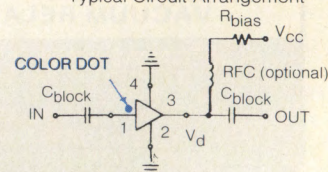

finding new ways ...
setting higher standards

Mini-Circuits™

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK. F154 REV. A

INFO/CARD 44

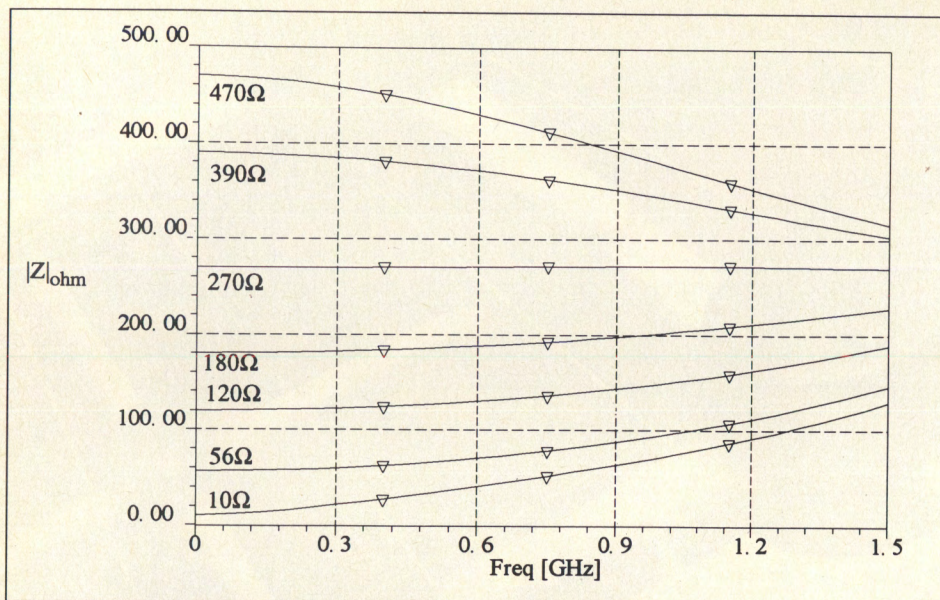


Figure 3. Impedance changes of various nominal resistors, assuming constant parasitics for all resistor values. Although the 270 ohm resistor seems to be the least frequency dependent when the magnitude of Z is plotted, the picture may be deceiving. A better way is to look at the $RE(Z)$ vs. frequency.

part — something that is acceptable as long as the physical length of the inductor is much less than the wave length of the applicable frequency. As in the resistor model, the shunt capacitor causes

parallel resonance, except the resonance is now a relatively high-Q kind (see Figure 5 for various inductor values).

The parallel resistor, R_p , of the inductor model represents the frequency dependent core losses for magnetic core type of inductors. Since permeability is a complex quantity, the frequency behavior of this resistor needs to be described very carefully, often requiring the use of piece-wise approximation or curve-fitting techniques.

The physical inductor behaves inductively until resonance; above that it is dominated by the parallel capacitor. However, in multi-layer inductors the situation is more complicated since each layer has individual equivalent circuits. In such a case, after a particular layer's parallel resonance, that layer behaves as a capacitor and eventually series resonates with another layer that still acts as an inductance, forming series resonance. Then the next layer goes through parallel resonance and so on. These parallel and series resonances are called secondary resonances and vary

the terminal impedance of the inductor between high and low values, instead of just a parallel resonance and capacitive behavior of the single layer coil. If such inductor is used as a choke, assuming constant high impedance behavior, the overall circuit response might be quite different than expected.

At resonance, the inductor behaves like a parallel RLC network. The two reactances cancel each other, leaving only the resistor. To find the value of the resistor R_{PE} , the series RL branch must first be transformed to parallel form changing R_S to a high value parallel resistance R_{SP} that is equal to

$$R_{SP} = (Q_{RL}^2 + 1)R_S \quad (2)$$

where Q_{RL} is the Quality factor of the series RL branch,

$$Q_{RL} = \frac{2\pi f L_N}{R_S} \quad (3)$$

Combining R_p and R_{SP} provides the total equivalent parallel resistance R_{PE} . After the transformation the new inductor value

$$L_{SP} = \left(\frac{1}{Q_{RL}^2} + 1 \right) L_N \quad (4)$$

Note that for high-Q inductors $R_{SP} \approx Q_{RL} R_S$ and $L_{SP} \approx L_N$.

For example, an inductor without a magnetic core ($R_p = \infty$), having Q of 100 and series RF resistance of 1 ohm, the transformed parallel resistance at resonance is about 10 kohm. (When a magnetic core is not used, the parallel loss term R_p equals to infinity, so $R_{SP} = R_{PE}$ is the total parallel resistance.)

Capacitors — Just like the magnetic-core inductor, the capacitor also has two different types of losses, but here one is dielectric loss and the other one is ohmic type. The former is generally represented by a frequency-dependent par-


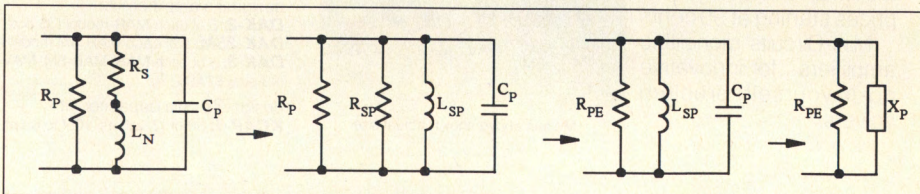


Figure 4. Four different representations of the lumped inductor model. L_N is the nominal low-frequency inductance, R_p and R_s are the frequency dependent losses (combined into R_{PE}), C_p is the self-capacitance. For Q calculation at any single frequency the basic model may be transformed to a simpler equivalent circuit shown at right.

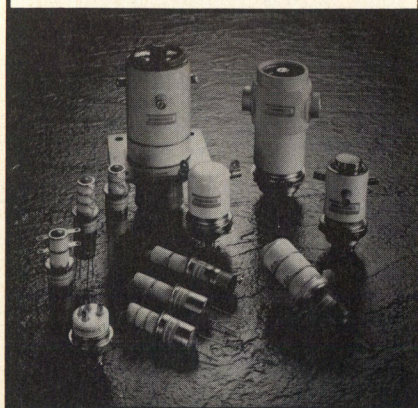CERAMIC RF CAPACITORS C-D/SANGAMO MICA RF CAPACITORS



JENNINGS VACUUM CAPACITORS VACUUM RELAYS

SURCOM ASSOCIATES, INC.

2215 Faraday Avenue, Suite A
Carlsbad, California 92008
TEL (619) 438-4420
FAX (619) 438-4759

INFO/CARD 45

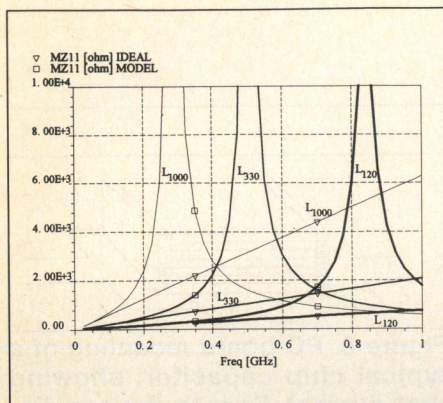


Figure 5. Impedance changes of three different physical inductors ranging from 120 nH to 1000 nH, assuming constant parasitics for all values. Straight lines correspond to ideal and curves to physical inductors.

allel resistor across the capacitance, while the ohmic losses are shown as frequency dependent series type. For maximum accuracy the ohmic losses of different origins (contact, fingers, leads, etc.) should also be separated since their frequency and temperature dependencies may differ.

The equivalent circuit shown in Figure 6 represents the first order approximation of the capacitor model. The parallel RC (representing the dielectric portion) may be converted to a frequency-dependent series form to show the series (first order) resonance of the capacitor. In this case, the converted capacitor C_{PS} resonates with the self-inductance to form a low-impedance series resonance, at which point only the combined resistance R_S plus R_{PS} exists in the circuit (see Figure 7). The sum of these two resistors is often referred to as ESR (effective series resistance), a frequency dependent term. Although ESR represents quite a low value, typically in the order of the few hundred to few tenths of an ohm, it must not be ignored in many

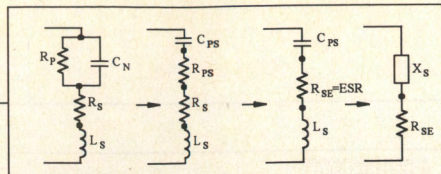


Figure 6. Lumped equivalent circuits of a capacitor. The dielectric and ohmic losses (R_P and R_S) may be combined at any frequency to a single resistor $R_{SE}=ESR$.

cases. In tuned circuits and high-power applications even such low resistance have significant effects. The series-to-parallel transformation changes the R_P and C_N to new values

$$R_{PS} = \frac{R_P}{1 + Q_{RC}^2} \quad (5)$$

$$\text{and } C_{PS} = \left(\frac{Q_{RC}^2}{1 + Q_{RC}^2} \right) C_N \quad (6)$$


$$\text{where } Q_{RC} = 2\pi f C_N R_P \quad (7)$$

The self-inductance of the contacts between the parallel fingers cause additional resonances, but these are parallel kinds, leading to high impedances. Depending on the way the capacitor is attached to the PC board these secondary resonances can be pushed to higher frequencies by the proper orientation of the chip (see Figure 8). Unfortunately, the form factors of the most commonly available parts are not appropriate to take advantage of the optimum mounting orientation. Some of the capacitor makers recognize this problem and produce "cube-like" forms to minimize the secondary resonance effects.

Parasitic Effects on Apparent Component Values

The effects of parasitic self-inductance and self-capacitance are frequently misjudged, even by those experienced in RF circuitry. For example, most designers feel that series self-inductance of a

NEW!

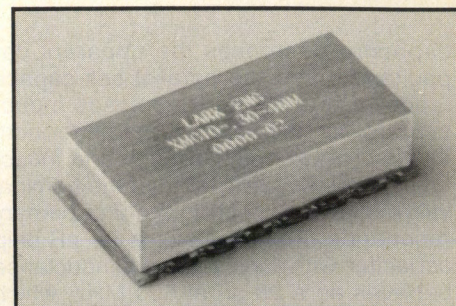

Surface Mount Filters

for the same low price

\$25⁰⁰

each in quantities of 100

- 10 to 1600 MHz
- Three Sections
- 3 dB BW : 5% to 20%
- 50 dBc Stopband Rejection
- -25° to +50°C Operation

Special models are also available with as many as eight sections, 3-dB bandwidths from 3 to 100%, and increased lowpass and highpass configurations.

Call, Write, or Bingo for our new 100-page Catalog!
(714) 240-1233



Lark Engineering Company
A Division of Baier & Baier, Inc.
27151 Calle Delgado
San Juan Capistrano, CA 92675
FAX: 714-240-7910

INFO/CARD 47

HF LINEAR AMPLIFIERS - BROADBAND TRANSFORMERS

HF AMPLIFIERS per MOTOROLA BULLETINS

Complete Parts List for HF Amplifiers Described in the MOTOROLA R.F. Device Data

AN758 300W \$154.15	EB63 140W \$ 89.65
AN762 140W \$ 95.15	EB27A 300W \$136.80
AN791L 20W \$ 83.79	EB104 600W \$371.65
AN779H 20W \$ 93.20	AR305 300W \$346.82
AR313 300W \$366.00	

NEW!! 1K WATT 2-50 MHz Amplifier
MOTOROLA AR347 \$1,100.95

POWER SPLITTERS and COMBINERS

2-30MHz	
600 Watt PEP 2-Port	\$ 69.95
1000 Watt PEP 2-Port	\$ 79.95
1200 Watt PEP 4-Port	\$ 89.95

100 WATT 420-450 MHz PUSH-PULL LINEAR

AMPLIFIER — SSB-FM-ATV

KEB67-PK (Kit)	\$159.95
KEB67-PCB (PC Board)	\$ 18.00
KEB67-I (Manual)	\$ 5.00

We also stock Hard-to-Find parts


CHIP CAPS—Kemet/ATC	
METALCLAD MICA CAPS—Unelco/Semco	
RF POWER TRANSISTORS	
MINI-CIRCUIT MIXERS	
SBL-1 (1-500Mz)	\$ 6.50
SBL-1X (10-1000Mz)	\$ 7.95

ARCO TRIMMER CAPACITORS

VK200-204B RF Choke	\$ 1.20
56-590-65-3B Ferrite Bead	\$ 20

Broadband HF Transformers

Add \$4.00 for shipping and handling.

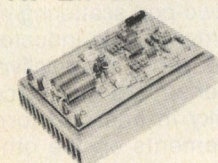

2 METER VHF AMPLIFIERS

35 Watt Model 335A	\$ 79.95 Kit
75 Watt Model 875A	\$119.95 Kit

Available in kit or wired/tested

For detailed information and prices, call or write for our free catalog.

WE SHIP
WORLDWIDE



CCI Communication Concepts Inc.

508 Millstone Drive • Beavercreek, OH 45434-5840 • (513) 426-8600
FAX (513) 429-3811



WE SHIP
WORLDWIDE

INFO/CARD 46

capacitor decreases the apparent capacitance, and the parallel self-capacitance of an inductor decreases inductance, while the opposite is true for both cases. The true capacitance and inductance is *always* greater than the nominal value, all the way up to the first primary resonance. For example, a 22 pF chip capacitor with 1 nH total self-inductance behaves as a 28 pF at 500 MHz, which is a 28 percent increase from the nominal value. The same is true for inductors; a 0.33 μ H inductor with 0.3 pF stray parallel capacitance acts like a 1.58 μ H inductor at 450 MHz, or about 380 percent increase above the nominal value.

The effects of self parasitics may be compensated by choosing *smaller* nominal values than specified. However, compensation is only possible for narrow (± 5 percent) bandwidths, or even less as the frequency approaches self-resonance. In broadband applications several smaller nominal values are needed instead of a single component. A careful simulation is always recommended to prevent painful surprises. As a rule-of-thumb, the ideal and physical components behave alike until 10-15 percent of the resonant frequency. Significant changes may take place at frequencies higher than 25-30 percent of resonance.

Parasitic Effect on Q

The presence of inductive or capacitive parasitics *always* decrease the component Q, even if parasitic elements were completely lossless. To explain the reason, let's look at two cases; one for inductors and one for capacitors.

Self-inductance of a capacitor — Once we accept that self-inductance always increases the apparent capacitor value (by reducing capacitive reactance), it is easy to see that in a series RC circuit the reactance is decreased, the Q also decreases ($Q = X_S/R_{SE}$).

To illustrate this point, let's look at the 22 pF capacitor mentioned above with a 1 nH self inductance (for simplicity assume that this self-inductance comes in an ideal lossless form). We showed that the series inductance increases the true capacitance increases to 28 pF at 1 GHz, which leads to a 28 percent reduction of series reactance and Q. This situation gets much worse as we approach resonance where the effective component Q, as we define it, goes to zero.

Self-capacitance of an inductor — Since the parasitic capacitor acts as a parallel element, its effect is viewed in

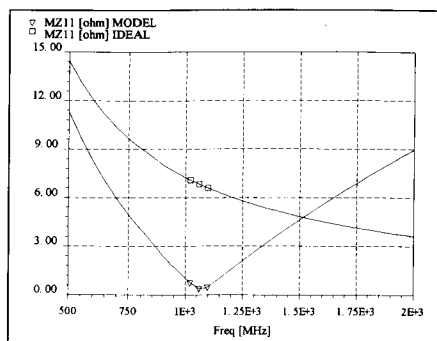


Figure 7. Impedance plot of ideal and physical 22 pF capacitors. The physical component has 1 nH self-inductance that causes a primary series resonance at 1074 MHz.

the parallel form. When the inductor is reduced to a parallel RLC equivalent circuit it was said that the presence of the parasitic capacitance *increases* inductive reactance. Parallel Q is expressed as parallel resistance over parallel reactance, therefore when reactance increases, the Q decreases.

Q Behavior of Physical Capacitors and Inductors

Even though the capacitor and inductor models contain both series and parallel circuit combinations, at a given frequency these sections may always be reduced to a single series or parallel form of one resistor and one reactive element as shown in Figure 1. Q is then computed by taking the appropriate ratio of these elements.

The frequency dependent Q behavior of inductors and capacitors are quite different. Physical capacitors have extremely high Q at low frequencies since the equivalent series reactance is very large and the series resistance (loss) is very low. As the frequency increases, the effective series resistance (ESR) increases while the series capacitive reactance decreases, resulting in a rapidly decreasing Q versus frequency.

Inductor Qs, on the other hand, behave quite differently. At low frequency the series reactance is very low, therefore Q is low. Series reactance increases with frequency, also increasing Q linearly. As the skin-effect becomes noticeable, the equivalent series ohmic resistance increases with the square-root of frequency, thereby the Q-slope changes from linear to a square-root increase. Next, the self capacitance comes into the picture, further decreasing the Q. At this point the Q levels off

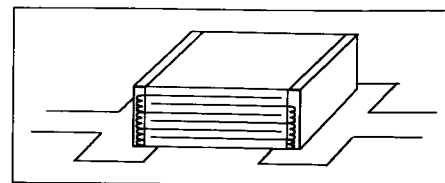


Figure 8. PC board mounting of a typical chip capacitor, showing that current flow to the top fingers must pass through additional inductance resulting in secondary resonances. These resonances may be "pushed" to higher frequencies by mounting the chip rotated 90 degrees so that the shaded surfaces contact the circuit board.

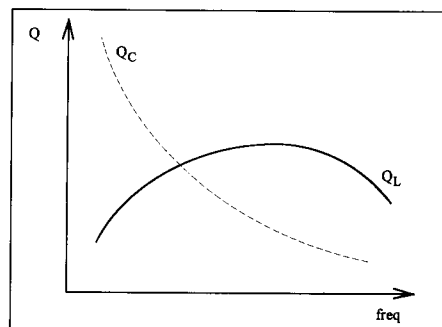



Figure 9. Inductor Q increases linearly at low frequencies, but adversely affected by skin-effect, self-capacitance, core and dielectric losses. Capacitor Q always decreases with frequency since losses increase and series reactance decreases.

with frequency, and when wire insulation and/or core losses make the picture worse, the Q begins to decline. Figure 9 compares the Q changes of inductors and capacitors.

Component Measurements

RLC components may be modeled based on one- or two-port scattering parameter measurements. For inductors and capacitors, measuring the relatively small equivalent series loss resistances may be quite tricky in one-port form. Two-port measurements on the other hand provide the necessary loss information with much higher resolution, although system impedance sometimes needs to be transformed by addition of small series capacitors.

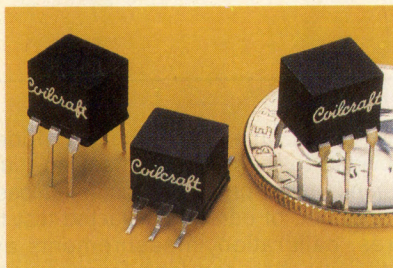In most cases, the components to be measured cannot be attached directly to the calibrated network analyzer; they must be placed into test fixtures. There-



Coilcraft offers low-cost wideband RF transformers

Coilcraft offers a family of low-cost wideband RF transformers that cover the frequency range from .005 to 600 MHz, with impedance ratios from 1:1 to 4:1.

The transformers are offered in tapped or untapped configurations and are packaged in a low-profile DIP-style plastic case. All parts are available in either a through-hole or surface mount version.

Applications include impedance matching, voltage or current transformation, DC isolation, balanced/unbalanced mixing, matching, power splitting, coupling, and signal inversion.

For more information, contact **Coilcraft**, 1102 Silver Lake Road, Cary IL 60013. 708/639-6400.

INFO/CARD 59




Precision test fixtures for surface mount devices

Coilcraft offers a series of test fixtures that assure faster, more accurate measurements of surface mount components. They're especially well-suited for testing tight-tolerance, low value passive components at frequencies from 1 to 1000 MHz.

The fixtures accommodate body sizes 0805 to 1812 and have exceptionally low stray capacitance and residual inductance. Several versions are offered for use with network analyzers, spectrum analyzers, and RF impedance analyzers such as the Hewlett Packard 4191A. Prices range from \$425 to \$498 depending on configuration.

For more information, contact **Coilcraft**, 1102 Silver Lake Road, Cary IL 60013. 708/639-6400.

INFO/CARD 60

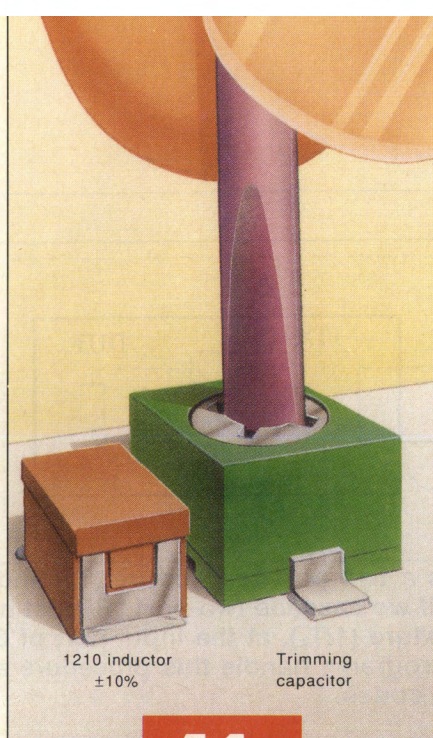


1210 inductor
±10%

Trimming
capacitor

41¢

PLUS TUNING

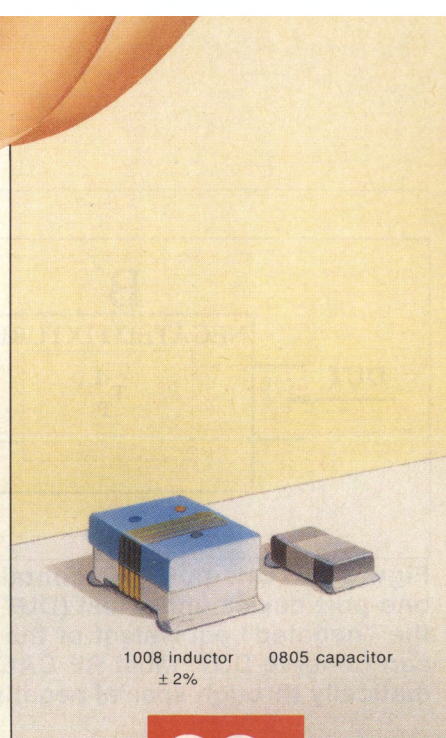

1008 inductor
±2%

0805 capacitor

22¢

Why your tuned circuits ought to be fixed.

Maybe it's time to rethink the way you design high frequency RF circuits.

Instead of costly tuneable components, why not switch to a fixed LC approach using Coilcraft's tight tolerance chip inductors.

You'll save up to 50% on component costs. Eliminate the time and expense of tuning. Cut board space from 60 to 70%.

And you'll end up with a circuit that's more precise and stable.

We've broken the high price barrier on tight tolerance chip inductors by

using a ceramic instead of a ferrite core. Besides having a much higher SRF, ceramic is electrically neutral. So we can turn out a steady supply of 2% parts and sell them at an amazingly low price.

Our 2% inductors come in 1008 (56 nH - 1 µH) and 0805 (56 - 220 nH) sizes. For non-critical applications, our 5 and 10% parts offer maximum savings.

For data sheets or to order one of our Designer's Kits with prototyping samples, call 800/322-2645.

Coilcraft

CEM/electronic engineers master
See our catalog in Vol. A, Section 1800

1102 Silver Lake Road, Cary IL 60013
800/322-2645 Fax 708/639-1469

INFO/CARD 48

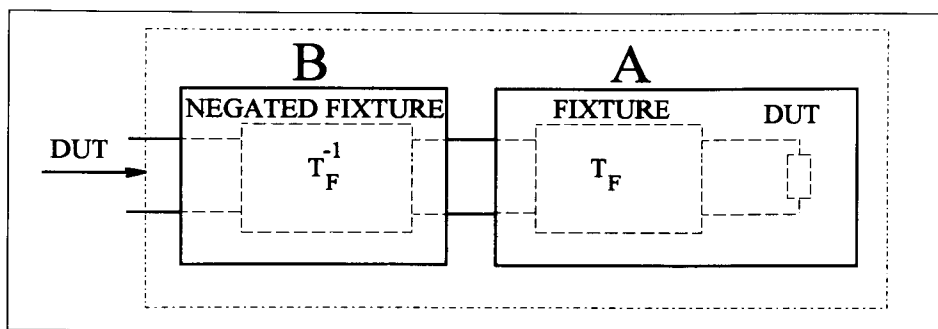


Figure 10. One-port "A" contains a two-port test fixture (T_F) and the one-port device under test (DUT). If we cascade two-port "B" that holds the "negated" equivalent of the fixture ($1/T_F$), at the input port of B we can observe DUT. Most RF CAE programs handle this procedure automatically through special negating codes.

fore, the measured data includes the parameters of the fixture and the device under test. By careful characterization, the test fixture parameters (or equivalent circuit) may be established and later de-embedded from the measured data, leaving the net parameters of the device under test. The final data then can be used for model optimization to obtain values of the component equivalent cir-

cuit. This process is illustrated in Figure 10.

Summary

With greater availability of computer simulators, it is possible to predict the behavior of RLC circuits, minimizing costly and time consuming prototype cycles. Unfortunately, circuit simulators can only predict the outcome of the cir-

cuit based on the component models provided to them. The old saying, "junk in, junk out" strongly applies in this case. Proper use of carefully selected test fixtures, calibration, measurements and data extraction can lead to appropriate models to behavior of circuits throughout the RF range. **RF**

References

1. L. Besser, "RF/High Speed Circuit Components: Measurements, Models and Data Extraction," Besser Associates, 1993.

About the Author

Les Besser is President of Besser Associates, 4600 El Camino Real, Suite 210, Los Altos, CA 94022. Les holds a BSEE, an MSEE and a Ph.D.E.E. degree. He has extensive experience in CAE software development (author of the Compact program) and RF product design, and has taught RF/microwave design courses worldwide. He can be reached at (415) 949-3300.

RF engineering opportunities

... YOUR CAREER

Cellular Engineers: Design/develop RF and analog circuits for high capacity cellular systems. Requires minimum of 2 years experience in any of the following: DSP, ASIC Design, CAE Development, Digital Modulation, Digital Mobile Communications, Channel Equalizers, Transmitter-Receiver-Synthesizer or Audio Design, Digital Signal Processing.

RF Design Manager: To establish and direct an RF product center. Will lead a small team in a design effort to develop functional modular products for the wireless communications market. Will come up with new product concepts and specifications for modules (basic idea is to replace portions of RF circuit with smaller, cheaper functional modules). Target end markets are cordless phone, cellular, RF Data Units and RF LAN. BSEE, MSEE preferred. Minimum 10 years experience with indepth knowledge complete RF circuit design. 2GHz-Audio. Experience with spread spectrum technology. Familiar with current SST components. Experience with low cost high volume design for consumer applications. Proven products development experience. Good technical writing skills.

VSAT Sr. Staff Engineer: Familiarity with equipment and systems utilized by broadcast organizations for the distribution of analog and digital audio programming via satellite. Experience with communications systems design, data communications receiver design and satellite link budget calculations. BSEE.

SATCOM Systems Engineers: Opportunities for satellite communications systems engineers. Responsibilities include satellite calculations, block diagram designs, equipment definitions, and specification for proposals and programs. Requirements include a BSEE, MSEE preferred, and a minimum of 5 years of applicable experience. This must include the design, proposal and implementation of medium-to-large aperture (4.5 to 21 meters) earth stations for commercial satellite computer spreadsheets is a must.

RF Design Engineer: Responsible for design of analog and RF systems and circuits for consumer and commercial digital wireless products. Five to ten years experience in RF systems analysis and design. Experience with low-cost design techniques for frequency synthesizers, power amplifiers, up/down converters and baseband circuits for digital communications systems. Must be able to derive RF systems and module requirements to meet overall performance and cost goals. Familiarity with time division duplex or CDMA a plus.

Staff/Principal Engineer: This individual will be responsible for the design/development of UHF/VHF amplifiers. Will be required to control the design on a stand-alone basis while meeting cost and schedule requirements with the support from junior engineers and experienced technicians. Hands-on engineer will also be required to lead IR&D efforts in UHF/VHF RF Power Amplifier design to enhance transmitter technology position. BSEE/MSEE.

RFIC Design: MS or PhD in Electrical Engineering with minimum 5 years related experience is preferred. The candidate should have a good knowledge and experience in Linear Bipolar High Frequency IC design and measurement techniques to design IC's like Amplifiers, Mixers, Oscillators, VCO's, Prescalers, Synthesizers, Limiting Amplifiers, etc. operating up to 2 GHz in Bipolar or BiCMOS technologies.

MMIC Design Engineer: Develop L/S band GaAs MMIC power amplifiers for commercial wireless communications. Requires M.S. or BSEE, +2 years experience with GaAs MMIC design, simulation, packaging and test.

Design Engineer: Responsible for the design and development of 900 MHz wireless consumer electronic products. Designed and developed AM/FM/FSK transmitters/receivers in 902-928 MHz frequency range. Hands-on experience on HF/VHF/UHF systems and subsystems which includes LNAs, medium power amplifiers, down converters, saw and coaxial resonator oscillators, VCOs, AM/FM IF systems, RF modulators/demodulators, PLLs and audio video circuits.

MICRO

COMMUNICATIONS
EXECUTIVE SEARCH

871 Turnpike St. • North Andover, MA 08145

We specialize in the placement of communications professionals both nationally and internationally.

CALL COLLECT: TEL: 508-685-2272 FAX: 508-794-5627

RF/MICROWAVE ENGINEERS

M/A-COM PHI is a state-of-the-art designer and manufacturer of RF and microwave transistors and amplifiers utilizing bipolar and MOSFET technology. Currently, we are looking for creative and technically qualified circuit design engineers with 3+ years experience in microwave circuit/component design and applications, with a BSEE or advanced degree. Microwave power bipolar and MOSFET familiarity is desirable. Our team based, concurrent engineering culture requires excellent communications skills.

In addition to a Southern California beach lifestyle (we provide relocation assistance), our company offers an excellent compensation and benefits package. Above all, M/A-COM PHI offers growth opportunities within a TQM/continuous improvement environment. Please submit your resume and salary history in confidence to the Director of Human Resource:


M/A-COM PHI
1742 Crenshaw Blvd.
Torrance, CA 90501
(310) 320-6160

Equal Opportunity Employer M/F/H/V

RF design MARKETPLACE

WHEN YOU ARE READY TO BUY-SELL-TRADE CALL *RF DESIGN* MARKETPLACE

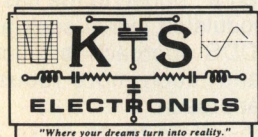Increase your **REVENUES** with *RF Design Marketplace* advertising! Over 40,000 prospects read and buy from this section each month. To reach this sophisticated, targeted market call today **(303) 220-0600**.



- STD. 5 AND 10 MHZ OCXO
- TCXO • VCXO • TC-VCXO
- VCO's • CLOCK OSCILLATORS
- CUSTOMIZED CRYSTAL FILTERS
- STD. 10.7 MHZ, 21.4 MHZ and 45 MHZ
- L/C FILTERS

Call or Fax your requirements.

**16406 N. Cave Creek Rd. #5
Phoenix, AZ 85032-2919
Phone & Fax (602) 971-3301**

INFO/CARD 54

CAL CRYSTAL LAB., INC. • COMCLOK, INC.

Need Clock Oscillators or Crystals? Call 1-800-333-9825 • 714-991-1580

Quartz Crystals 50Khz to 200Mhz

TTL Clock Oscillators 250Khz to 70Mhz

HCMOS Clock Oscillators 3.5Mhz to 50Mhz

Tri-State, Half Size and Surface Mount also available on request

Fast Service - 3 weeks or less

Special frequencies our speciality

1142 N. Gilbert, Anaheim, CA 92801 • FAX 714-491-9825

INFO/CARD 55

- Promote your company...
 - Trade used equipment...
 - Sell your products...
- Every month for only \$395
CALL 303-220-0600 TODAY!

NOVA RF Systems, Inc.

The Complete RF/Microwave Solution



- RF/Microwave Systems
- Custom Design/Consulting
- Simulation Software
- Synthesizers (PLL/DDS)
- Complete Lab/Machine Shop
- TDMA/CDMA/Spread Spectrum

**1740 Pine Valley Dr. • Vienna, Virginia 22182
(703) 255-2353**

INFO/CARD 56

Advertising Index

Advertiser	Page No.
Amplifier Research	51
Andersen Laboratories	80
Avantek/Subsidiary of Hewlett-Packard	33
Cal Crystal Lab, Inc.	71
California Eastern Laboratories	45
Coilcraft	69
Communication Concepts, Inc.	67
Compact Software	39
DAICO Industries, Inc.	6
Dielectric Laboratories	22
Eagleware	11
EG&G Frequency Products	42
ENI	17
Giga-tronics, Inc.	12-13
Henry Radio	10
Hewlett-Packard	47

IFR Systems, Inc.	3
International Crystal Mfg. Co., Inc.	63
JFW Industries, Inc.	26,50
Kalmus Engineering, Inc.	27
KS Electronics	71
KVG North America	36
Lap-Tech, Inc.	10
Lark Engineering Co.	67
Loral Microwave-Narda	2
M/A-Com Semiconductor Products Division	43
Merrimac	14
Mini-Circuits	4-5,29,61,65
Motorola Semiconductor Products, Inc.	23
Murata Erie North America	9
Narda	2
Noise/Com, Inc.	19-20
Nova RF Systems, Inc.	71
Penstock, Inc.	25

Programmed Test Sources, Inc.	30
Q-bit Corp.	21
QUALCOMM, Inc.	40
Repco	63
Richardson Electronics Ltd.	79
SCITEQ Electronics, Inc.	74
Siemens Components, Inc.	16
Silicon Valley Power Amplifiers	48
Sprague Goodman	15
Surcom Associates, Inc.	66
Synergy Microwave Corp.	35
Temex Electronics, Inc.	24
Tesoft, Inc.	73
TIP Co.	73
Vectron Laboratories, Inc.	38
Voltronics Corp.	46
Wenzel Associates	42
Werlatone, Inc.	8
Wide Band Engineering Co., Inc.	18

Data Converters Meet RF Needs Bit by Bit

By Andy Kellett
Technical Editor

The advantages of moving RF data between the analog and digital domains have probably been obvious since the first Analog to Digital Converters (ADCs) and Digital to Analog Converters (DACs) were made. However, the implementation of such systems has been anything but obvious. It has been a slow evolution from expensive converters operating at audio frequencies to relatively inexpensive devices operating at tens of megahertz.

Analog to Digital

The number of applications where analog to digital conversion makes engineering sense has increased as cost has come down and performance has gone up. ADCs are being used more and more in document scanners, camcorders and medical imaging devices. Once limited to cost insensitive military systems, direct IF sampling is now becoming more cost effective than traditional analog signal processing in some applications. "Cost is really the thing that's going to make data conversion attractive," says David Duff, Product Manager for High Speed Converter products at Analog Devices. According to Duff, both parts and labor can be reduced when digitized IF signals are demodulated and processed in digital signal processing (DSP) devices.

Sampling speed and resolution are traditionally the two most looked at figures of merit for ADCs. Both of these figures have increased, but it is still necessary to trade one for the other. According to Pat Kirk, Product Manager for High Speed Products at Burr-Brown Corporation, some speeds and bit resolutions representative of higher end devices are 16 bits at 1 Mega-sample per second (Ms/s), 14 bits at 10 Ms/s, 12 bits at 25 Ms/s and 10 bits at 100 Ms/s.

While the number of bits is certainly an indication of the resolution possible with an ADC, the effective resolution depends on several other factors. "The Effective Number of Bits (ENOB) is always less than the theoretical resolution," notes Analog's Duff, "at high analog input frequencies, ENOB is dominated less by quantization noise than by ADC

AC non-linearities." An ADC's application determines what type of noise is most undesirable. According to Comlinear's Data Conversion Product Line Manager, Alan Hansford, applications that convert sampled data into the frequency domain are concerned with harmonics. For those applications that keep sampled data in the time domain, such as video applications, signal to noise ratio and differential non-linearity are most important.

Sample speed, resolution and noise are all balanced when an ADC's architecture is selected. Flash converters are the fastest, but are only used in ADCs of eight bits or less. Most high speed, high resolution ADCs today use subranging or pipelined architectures. To reduce non-linearities caused by mis-sampling an AC signal, many ADCs use sample-and-hold or track-and-hold amplifiers to give the ADC a DC value to convert.

One more concern of ADC users is power consumption. For portable applications, this concern is obvious, but even some stationary applications such as ultrasound imagers are also concerned with power consumption. "For an ultrasound machine with hundreds of channels to be digitized, it's literally a function of the current that can be pulled out of the wall socket," notes Burr-Brown's Kirk.

Digital to Analog

DACs at RF frequencies are almost exclusively used in direct digital synthesis (DDS). "DDS is an enabler, not just a more elegant way to do something, but a way to do something you couldn't do before," says Bill Woodruff, Director of Marketing at the DCSP Division of TriQuint Semiconductor. Qualcomm is currently releasing a line of DACs to go specifically with their DDS chips. "We would like to offer a complete system solution," noted Steve Anderson, a Technical Product Manager for Qualcomm, "in the past you didn't know what the spurious response of a DDS/DAC combination was until you breadboarded it." Just as with ADCs, DACs often reduce part counts because of their ability, in conjunction with a numerically con-

trolled oscillator (NCO), to directly produce a modulated IF signal. In the case of a complex modulated signal such as 64 QPSK, the DDS approach is much less complex and much more robust than an analog approach.

While ADC designers try to strike a balance between speed and resolution, DAC designers struggle to balance speed and spurious free dynamic range. "The higher a DAC's output frequency, the more spurs you will get from the AC non-linearities in the DAC," says Burr Brown's Kirk. The same signals that are the forte of DDS, broadband and frequency agile signals, also make the design of filters to attenuate spurs exceedingly difficult. The problem of designing fast moving filters for frequency agile applications can be eliminated if the spur free dynamic range is large enough to ensure that all significant spurs will fall well outside the channel bandwidth.

Trends

ADCs and DACs are becoming less expensive, in part, because more and more of the devices are monolithic. High performance ADCs and DACs have traditionally been hybrid devices. Hybrid construction allows designers to use the optimum technology for each part of the system. Designers of monolithic converters have to compromise the performance of each sub-system to get an acceptable total system performance. The disadvantage of hybrid construction is its cost. "In high volume applications the cost of hybrids can only come down so much. But monolithically, that's when you can really reduce the cost," says Richard Mintle, Director of Marketing for Signal Processing Technology.

"The converter capacities and RF requirements are beginning to go hand-in-hand," says Don Travers, Product Marketing Manager at Analogic. It has been a long haul from concept to implementation, but RF data conversion has gained a foothold in RF designs. **RF**

For reprints of this report contact Cardiff Publishing at (303) 220-0600. Ask for the Circulation Department.

RF software

DSP Software

The Athena Group now offers the Monarch series of DSP software. The series is comprised of four packages. The Digital Filters package (\$99) offers FIR and IIR filter design methods. SIGLAB (\$99) is a comprehensive interpretive DSP language. The Adaptive Filters package (\$399) offers different algorithms and architectures for both single- and multi-dimensional signals. Code Generators (\$99) for DSP microprocessors completes the series.

The Athena Group, Inc.
INFO/CARD #195

Bulletin Board

Decibel Products has activated a 24-hour bulletin board where inquiries and messages can be exchanged with Decibel staff. Product information can also be accessed. The phone number is (214) 819-4254, the modem format is 300/1200/2400/9600/14400 - N81.

Decibel Products
INFO/CARD #194

Design Tool Integration

The EEsof Mentor Graphics Integration Module makes it easy to interchange information between high-frequency simulation tools available in EEsof's Series IV Project Design

Environment (PDE) and Mentor's Falcon Framework (v. 8.2) design environment. Schematics, layouts and documentation can all be seamlessly exchanged between both design environments.

EEsof, Inc.
INFO/CARD #193

Mathematical Software

A general mathematics package, a differential equation solver, an equation evaluator and plotter, and a revised data smoothing program are all now offered by Dynacomp. Electrical engineering and electromagnetics applications packs are available for the equation evaluation and plotting program.

Dynacomp, Inc.
INFO/CARD #192

EMI Tools

Kimmel Gerke Associates offers the EMI-Toolkit™, a collection of over thirty EMI formulas, graphs and tables. The Windows based program costs \$100 for a single user license and \$500 for single-site/single-network license.

Kimmel Gerke Associates, Ltd.
INFO/CARD #191

RF Design Software Service

Programs from RF Design, provided on disk for your convenience.

July Program: RFD-0793 — Contest Grand Prize Winner!

"Synthesizer Design With Detailed Noise Analysis" by Terry Hock. This program was written to simplify the design of PLLs using commercial synthesizer ICs. It includes loop analysis, including effects of the reference, phase detector, loop filter and VCO. Noise analysis includes application of Leeson's equation for VCO noise performance, and uses data for specific op amps in the loop filter. (Requires VGA)

June Program: RFD-0693

"A Generic GPIB/RS-232 Controller" by Kevin Cordle. This program allows the user to control instruments using both IEEE-488 bus (GPIB) and RS-232 serial data. Includes a graphical on-screen editor for creation of control sequence macros. Requires PC-based GPIB controller card with appropriate device drivers. (Turbo Pascal, interface uses Turbo Vision)

Call or write for a listing of all available programs

Each month's program(s)..... \$ 15.00postpaid, with article reprints and any author's notes.

Price includes shipping to U.S. or Canadian addresses. Orders from other countries must add \$8.00 per order for extra shipping and handling. Specify 3 1/2 or 5 1/4 inch disks

Annual subscription.. \$130.00 postpaid.. (\$170 Foreign, via Air Mail).. get each program ASAP.

We Accept VISA, MasterCard, and American Express! When ordering by mail, please include card number, correct name, and expiration date.

Order by telephone! Call (303) 770-4709 to place your credit card order. Occasionally, you may reach an answering machine, but your call will be returned as soon as possible.

RF Design Software Service
P.O. Box 3702
Littleton, Colorado 80161-3702
U.S.A.
(303) 770-4709

INFO/CARD 100

PROTO PC BOARDS - 3 DAYS - DOUBLE SIDED & MULTI

POLYESTER GLASS & FR-4

POLYESTER OFFERS:

- Low Dielectric Constant
- fast digital & RF circuits
- Temperature Stability
- over -50F to +200F
- High Tracking Index
- high density Circuits
- UL 94 VO Approved
- FR-4 PRICES - or LOWER

TIP Co.

P.O. Box 255

Lake Peekskill, NY 10537


TEL: 914-528-3774

FAX: 914-526-3558


INFO/CARD 49

Easy TESLA Block Diagram Simulation Runs on Your PC

- Nonlinear time simulation with built-in spectrum analysis lets you test with noise, multipath and adjacent channels
- Use TESLA to simulate modems, radios, cellular, GPS, spread spec, DSP, HDTV, radar, controls, audio & more!
- Over 60 analog & digital blocks: Filters, VCO, Mixer, RFamp, Laplace, A/D & D/A Converters, BER tester, Noise, S&H, Integ&dump, 5-Function Generator, Phase meter, & more!
- Add new blocks with MODGEN option—BBS user library
- Use OrCAD® to input block diagrams—runs under TESLA

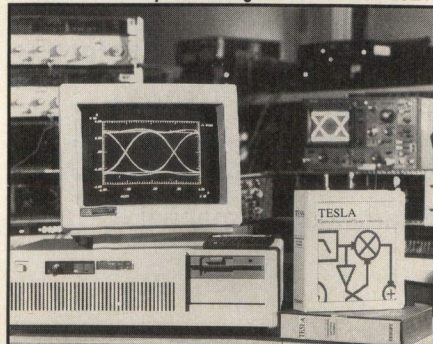

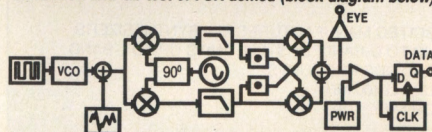Simulation and lab test of FSK demod (block diagram below)



FREE APPLICATION NOTE

TESOFT Inc, PO Box 305	CALL FOR WORKING DEMO DISK
Roswell GA 30077	TESLA Simulator \$695
Phone 404-751-9785	MODGEN Model Generator \$495
FAX 404-664-5817	Symbols for OrCAD/SDT® \$195

INFO/CARD 50

FREQUENCY SYNTHESIS

HERE'S
A.L.L.*
YOU
ASKED
FOR...



Frequency Synthesis... the *next* generation!

- 20 dB better phase noise than PLL
- Single ALL = double PLL
- Adds DSP in the feedback loop
- The simplest solution for wireless

Order your ALL technology
evaluation kit TODAY!
(619) 292-1650

Board + disk + manual = \$189

*Arithmetically Locked Loop

SCITEQ MANUFACTURES PLL SYNTHESIZERS
UP TO C-BAND, DDS+PLL UNITS UP TO L-BAND
AND DDS PRODUCTS
UP TO 400 MHz
OR MIL.

SCITEQ Electronics, Inc.
4775 Viewridge Avenue
San Diego, CA 92123
(619) 292-0500
(619) 292-9120



RF literature

Silicon MMICs

An eight-page Silicon MMIC Product Selection Guide is now available from California Eastern Labs. It covers NEC's wide range of silicon IC products, including: wideband amplifiers up to 3.0 GHz, prescalers up to 2.8 GHz, transistor arrays, frequency converters and other devices.

California Eastern Laboratories
INFO/CARD #189

RF Amplifiers

ENI's six-page color catalog, "Solid State Amplifiers", includes 20 primary specifications for 28 different broadband RF amplifiers covering milliwatts to kilowatts and 9 kHz to 1 GHz. Also featured are pulse amplifiers for use with MRI and NMR-spectroscopy.

ENI
INFO/CARD #188

Short Form Catalog

Amplifonix announces their new 16-page short form catalog. The catalog specifies a complete line of amplifiers, voltage variable attenuators, GaAs MMIC and PIN diode switches, digital attenuators, and voltage controlled oscillators.

Amplifonix, Inc.
INFO/CARD #187

Spectrum Analyzer

A 20-page color brochure on Anritsu's MS2702A and MS2802A spectrum analyzers has been released by Anritsu Wiltron Sales Company. The brochure also contains information on creating a specialized measurement system using Anritsu's Personal Test Automation (PTA), and optimal system construction.

Anritsu Wiltron Sales Co.
INFO/CARD #186

Implementation Guides

Two new guides are now available from the NAB: the 1993 *Guide to HDTV Implementation Costs* and *Ghost Canceling: An Implementation Guide*. The HDTV guide analyzes the costs associated with completing a successful transition to a terrestrial HDTV broadcast service. The other guide presents guidelines on implementing ghost canceling technology and what levels of performance can be expected from it when in place.

National Association of Broadcasters
INFO/CARD #185

RF Manufacturing

Hybrid-Tek now offers a brochure which describes the company's capabilities in design, print, fire, and assembly of microelectronic circuits using thick film technology. Hybrid-Tek now also manufactures RF components, including GaAs switches, PIN switches and PIN diode attenuators.

Hybrid-Tek, Inc.
INFO/CARD #184

Spectrum Analyzer Measurements

Tektronix announces the availability of several new application notes and technical briefs. The new titles are: "Spurious-Free Signal Range in Spectrum Analysis", "2782 Spectrum Analyzer Mathematics Signal Computation Functions", "The 2782 Spectrum Analyzer Detector Function Applications", and "Sideband Noise Measurement with the Tektronix 2782 Spectrum Analyzer".

Tektronix, Inc.
INFO/CARD #183

Communications Products

The 1993 data book covering Silicon Systems' communications products ICs is now available. This year's book, approximately 900 pages long, covers analog signaling, LAN, programmable filter, modem, modem support, interface and PCM standard ICs.

Silicon Systems
INFO/CARD #182

Rad Hard Products

The 1993 *Radiation Hardened Product Databook* from Harris is now available. The 2300-page databook contains information on more than 500 ICs and transistors and includes design and manufacturing sections dealing with rad hard environments.

Harris Semiconductor
INFO/CARD #181

RF Coverage

SoftWright has released its new catalog of software products detailing its fourteen different interactive modules of RF engineering software. Also available is digitized topography for all fifty states, Puerto Rico and the Virgin Islands.

SoftWright Limited Liability Co.
INFO/CARD #180

Operational Amplifiers

The new second edition of *Operational Amplifiers* by Jiri Dostal is now available from Butterworth-Heinemann publishers. The book presents the reader with the practical knowledge necessary to select and use operational amplifier devices. The 360-page hardcover book sells for \$49.95.

Butterworth-Heinemann
INFO/CARD #179

VXIbus Downconverter

A four-page brochure for EIP's model 1313A, VXIbus microwave downconverter, is now available on request. The downconverter offers operation from 1 to 20 GHz with a 500 MHz IF bandwidth and a 3 dB typical conversion loss.

EIP Microwave, Inc.
INFO/CARD #178

No One Supports Motorola's RF Products Better Than Richardson Electronics.



- Inventory
- Technical Assistance
- Delivery
- Design Help

You're Supported by:

- An extensive inventory and off-the-shelf availability of Motorola RF power FETs, power Bipolar, small-signal transistors and power modules.
- A toll-free hotline in the U.S.—**1-800-RF POWER**—to call for technical assistance and design help.

Call **Richardson** today and let us take any RF concerns off your shoulders.

U.S. (800) RF POWER Canada (800) 348-5580




MOTOROLA
INFO/CARD 52



**Richardson
Electronics, Ltd.**

Motorola's Largest RF Distributor

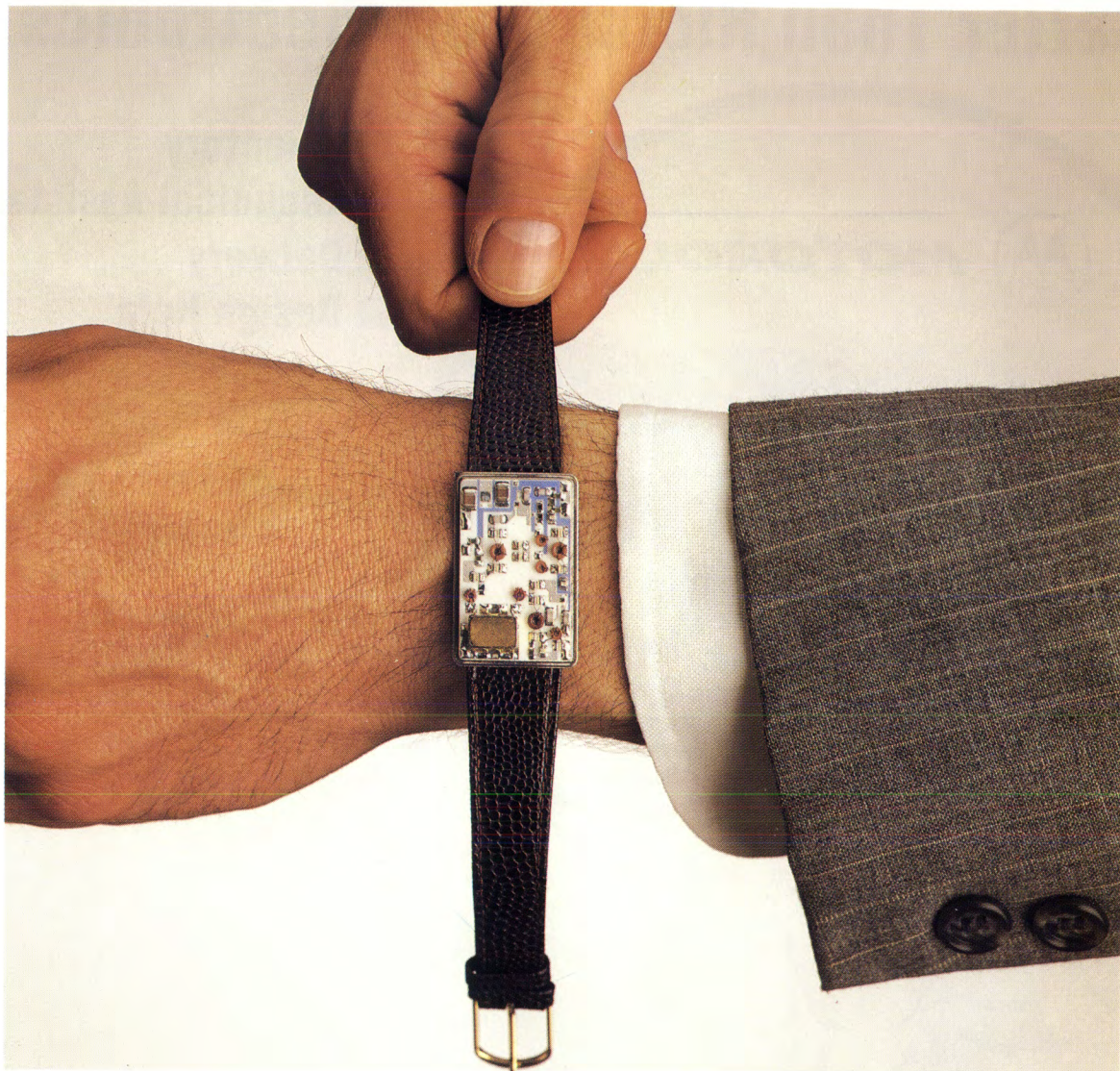

**You can't buy
a better precision
timepiece for
under 2.4 GHz.**

If you're operating in a frequency range from 100 MHz to 2.4 GHz, you can't buy a better oscillator than an Andersen VCO. It gives you the highest spectral purity with the lowest spurious ($> -60\text{dB}$). And typical single sideband phase noise of $> -119\text{dBC @1 KHz offset}$.

It's compact. It's rugged. It operates in temperatures up to 100°C . It can be tuned up to 1.5 MHz or phase-locked to a reference. Plus, its low mass and low profile make it ideal for surface-mount technology, DILS or flatpaks.

Isn't it about time you discovered the precision, the versatility and simplicity of designing with Andersen oscillators? Contact Andersen Laboratories, 45 Old Iron Ore Road, Bloomfield, CT 06002. Telephone (203) 286-9090/FAX 203-242-4472.

 **ANDERSEN LABORATORIES**