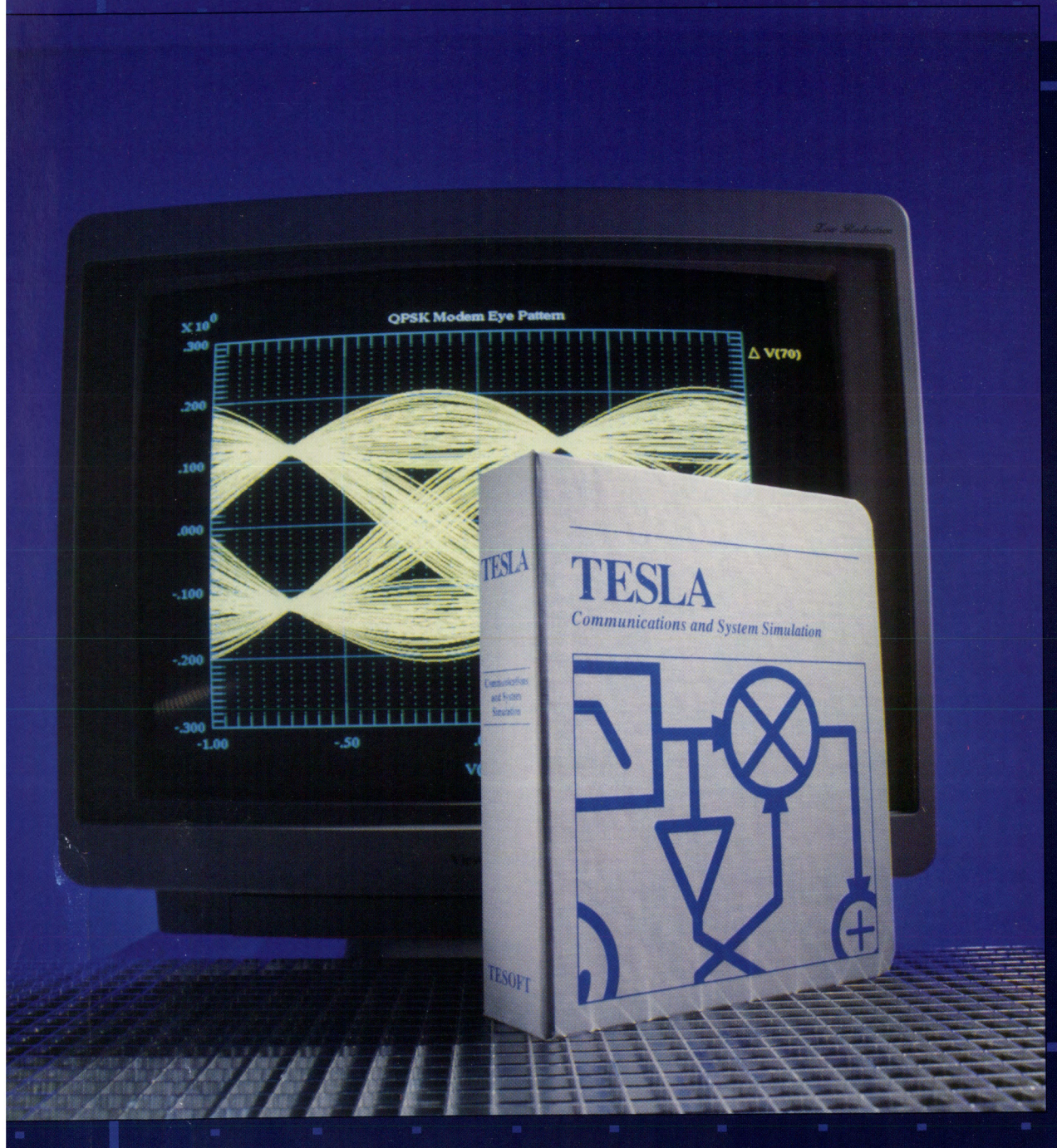


# RF design™

engineering principles and practices

February 1994




*Featured Story*  
**CAD/CAE Methods**  
*Inside —*  
**RF Expo West Preview**



■ LARGEST SELECTION

■ INDUSTRY PIONEER

# SURFACE MOUNT

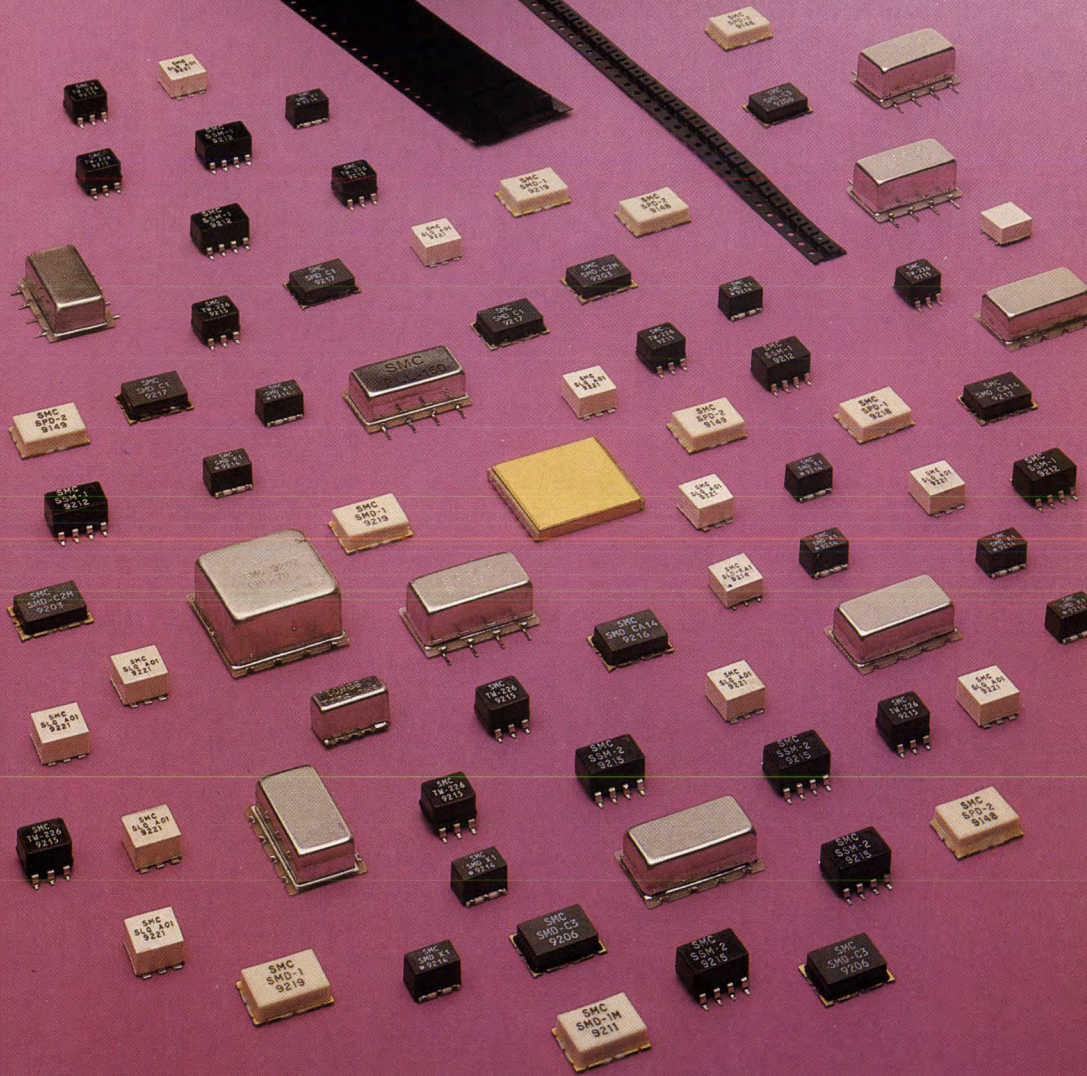



MIXERS • POWER DIVIDERS • COUPLERS • FILTERS  
I/Q MOD. & DEMOD. • PHASE DETECTORS • PHASE SHIFTERS  
ATTENUATORS • VECTOR MODULATORS and more...




483 McLean Boulevard • Paterson, New Jersey 07504 • (201) 881-8800 • Fax: (201) 881-8361



Time domain composite video wave form

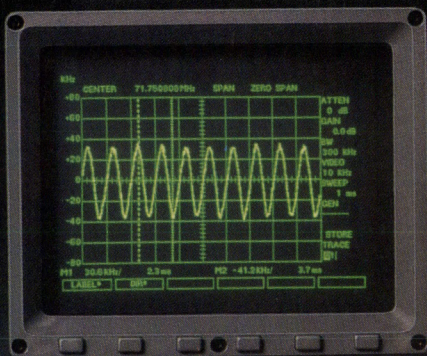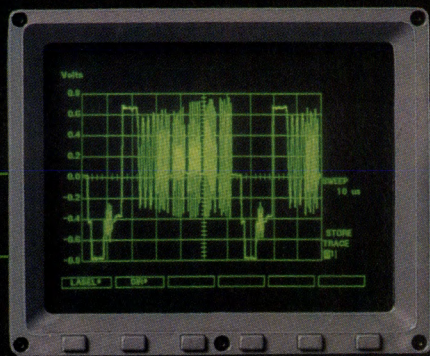

Demodulated FM carrier

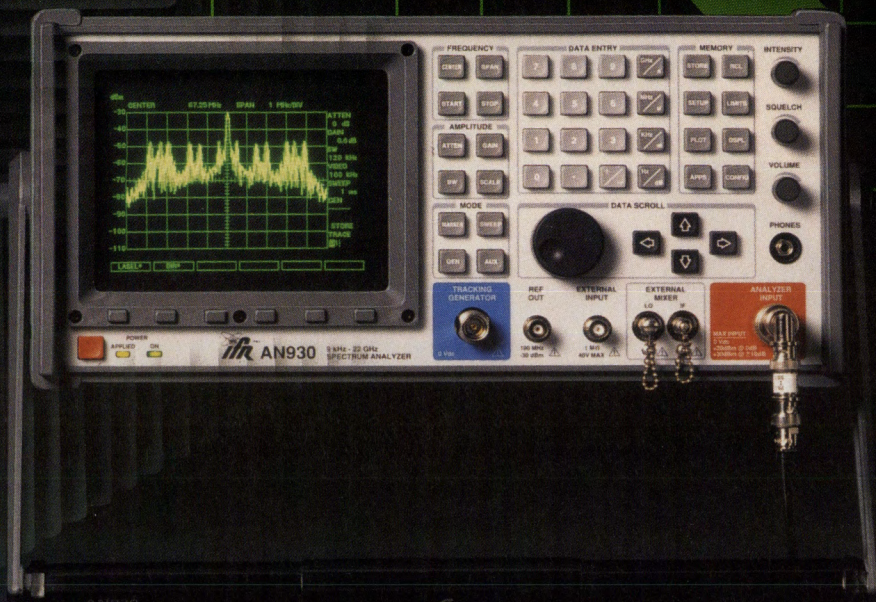

# GET THE TOTAL PICTURE WITH AN IFR SPECTRUM ANALYZER

In addition to being a full-featured 22 GHz spectrum analyzer, the AN930 is a powerful measurement tool that can perform frequency or time domain analysis on the complex signals found in many modern communications systems.

A 30 MHz resolution bandwidth filter combined with a powerful set of time domain measurement functions provides the AN930 with a unique ability to capture and analyze pulsed and digital transmissions that previously has been unavailable in any other spectrum analyzer.

A built-in, sensitive FM/AM receiver with modulation measurement scales enables direct measurements of FM deviation or AM percent modulation. The accompanying high-quality audio output aids in identification of unknown or interfering signals.

Other standard AN930 features include an automatic limits test function for unattended detection of random or intermittent signals, a built-in frequency counter for precise frequency measurements, RS-232 and IEEE-488 interfaces, and operation from DC power sources.

Optional features including a built-in 2.9 GHz tracking generator, quasi-peak detector, high stability time base, and a rechargeable battery pack add even greater flexibility for solving your unique measurement requirements.

Contact IFR or your local IFR representative for more information or to arrange for a demonstration of the AN930.



**IFR SYSTEMS, INC.**


**RENT DIRECTLY FROM IFR**  
Call 316/522-4981, Ext. 207 for details



10200 West York Street / Wichita, Kansas 67215-8935 U.S.A.  
Phone 316/522-4981 / TWX 910-741-6952 / FAX 316/522-1360



# ***I&Q MODULATORS***

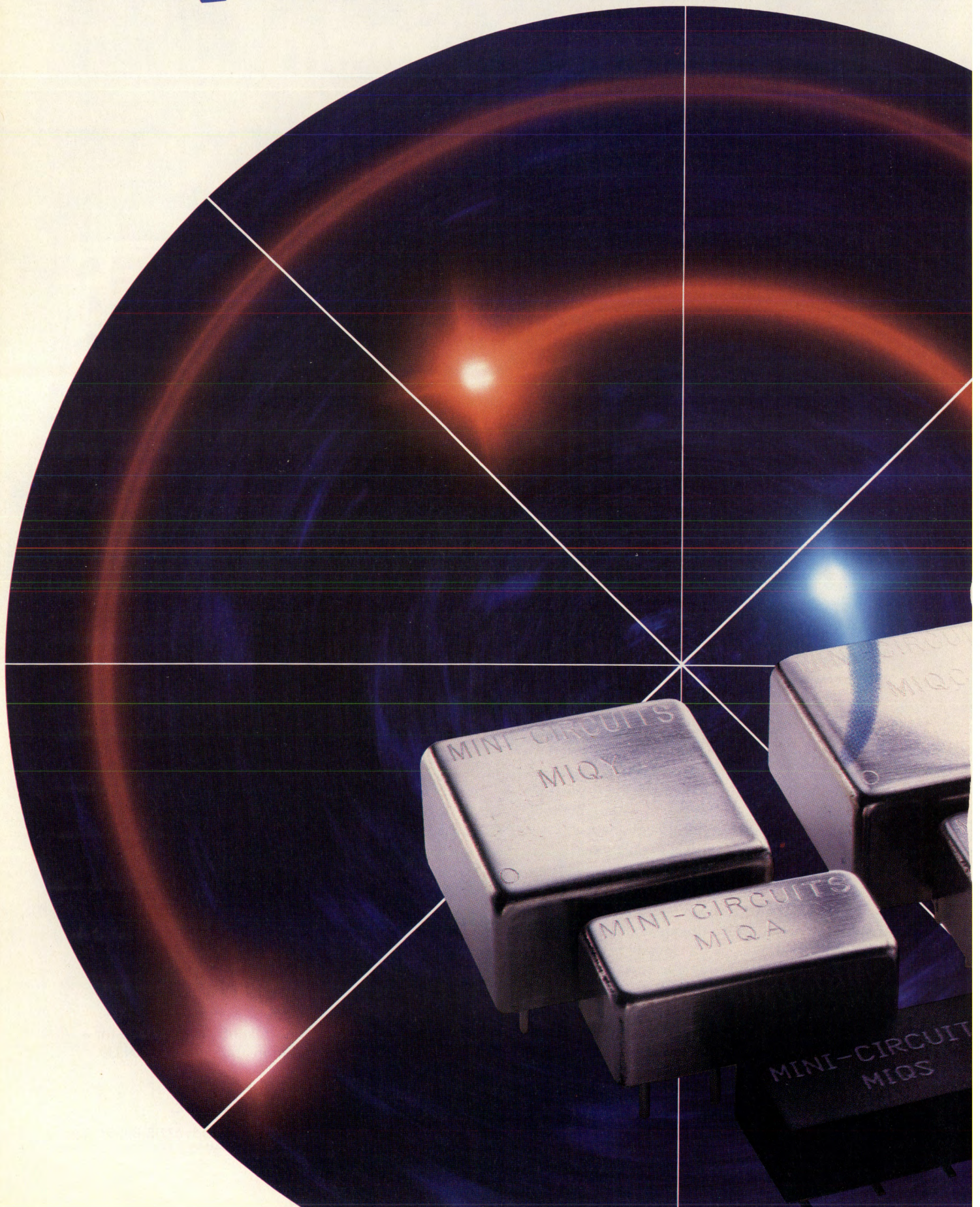



# DEMODULATORS

1.15MHz to 1880MHz from **\$19.95**


I&Q Modulators and Demodulators...another smart offering from Mini-Circuits that's pushing industry standards to new heights (and prices to new lows)!

Infuse your cellular, radar and communication system project with the powerful new I&Q Modulator and Demodulator, surface mount and plug-in units. Units so reliable, the specified statistical data on performance holds up with rock-solid repeatability unit-to-unit.


For high speed assembly operations, I&Q Modulators and Demodulators are available in tape and reel format, so you can bank on consistent assembly performance for production efficiency time after time...and with prices starting at just \$19.95, these powerful and compact units truly are the next generation of value on the market today.

So, call your Mini-Circuits distribution-center at a number listed below for guaranteed one week shipment or, turn to our applications department with your special specs for custom units at catalogue prices.

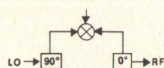*We're redefining what VALUE is all about!*



MODEL NO.	FREQ. (MHz)		CONV. LOSS (dB)		CARRIER REJ. (dBc)	SIDE BAND REJ. (dBc)	HARM. SUPPRESS (dBc) Typ.		PRICE \$ QTY (1-9)
	$f_L$	$f_U$	$x$	$\sigma$	Typ.	Typ.	3xl/Q	5xl/Q	
<b>I/Q MODULATORS</b>									
MIQA-10M	9	11	5.8	0.20	41	40	58	68	49.95
MIQA-21M	20	23	6.2	0.14	50	40	48	65	39.95
MIQA-70M	66	73	6.2	0.10	38	38	48	58	39.95
MIQA-70ML	66	73	5.7	0.10	38	38	48	58	49.95
MIQA-91M	86	95	5.5	0.10	38	38	48	58	49.95
MIQA-100M	95	105	5.5	0.10	38	38	48	58	49.95
MIQA-108M	103	113	5.5	0.10	38	38	48	58	49.95
MIQA-195M	185	205	5.6	0.10	38	38	48	58	49.95
MIQC-88M	52	88	5.7	0.10	41	34	52	66	49.95
MIQC-176M	104	176	5.5	0.10	38	36	47	70	54.95
MIQC-895M	868	895	8.0	0.10	40	40	52	58	99.95
MIQC-1785M	1710	1785	9.0	0.30	35	35	40	65	99.95
MIQC-1880M	1805	1880	9.0	0.30	35	35	40	65	99.95
MIQY-70M	67	73	5.8	0.20	40	36	47	60	19.95
MIQY-140M	137	143	5.8	0.20	34	36	45	60	19.95

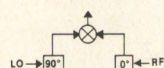

MODEL NO.	FREQ. (MHz)		CONV. LOSS (dB)		AMP. UNBAL. (dB)	PHASE UNBAL. (Deg.)	HARM. SUPPRESS (dBc) Typ.		PRICE \$ QTY (1-9)
	$f_L$	$f_U$	$x$	$\sigma$	Typ.	Typ.	3xl/Q	5xl/Q	
<b>I/Q DEMODULATORS</b>									
MIQA-10D	9	11	6.0	0.10	0.15	1.0	50	65	49.95
MIQA-21D	20	23	6.1	0.15	0.15	0.7	64	67	49.95
MIQC-895D	868	895	8.0	0.20	0.15	1.5	40	55	99.95
MIQY-125D	1.15	1.35	5.0	0.10	0.15	1.0	59	67	29.95
MIQY-70D	67	73	5.5	0.25	0.10	0.5	52	66	19.95
MIQY-140D	137	143	5.5	0.25	0.10	0.5	47	70	19.95

- ☐ NON-HERMETICALLY SEALED  
MIQA case 4 x .8 x .4 in.  
MIQY case 8 x .8 x .4 in.  
MIQC case 8 x .8 x .4 in.  
MIQS case 8 x .4 x .2 in.

INFO/CARD 3

**Mini-Circuits®**


P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.


CUSTOM PRODUCT NEEDS... **Let Our Experience Work For You.**




# WHAT DO THESE FILTERS HAVE IN COMMON?

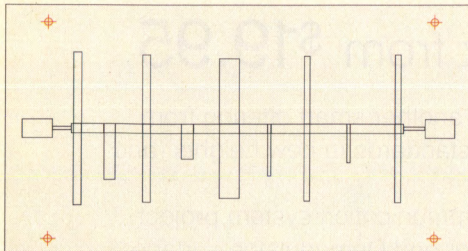

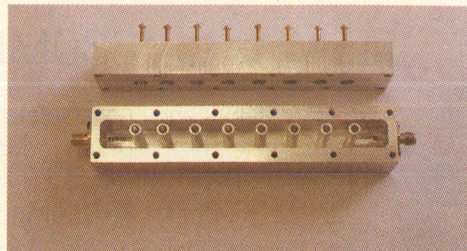
5.6 GHz Elliptic Bandpass on Teflon Board




1.27 GHz Machined Combline Bandpass

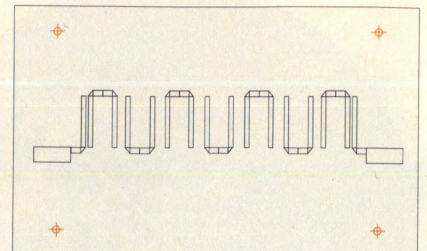


2.2 GHz Hairpin Bandpass on Teflon

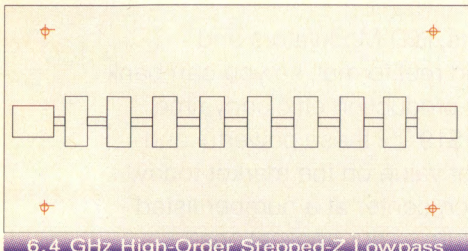


6.4 GHz High-Order Stepped-Z Lowpass

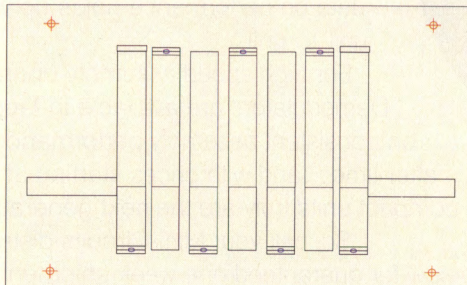


10 GHz Wideband Interdigital BP

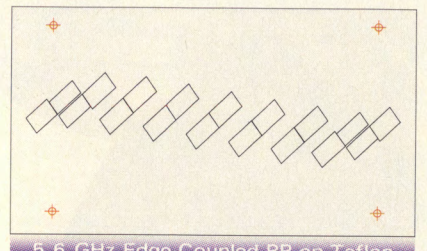


5.6 GHz Edge-Coupled BP on Teflon

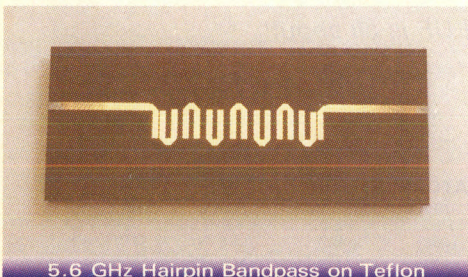

5.6 GHz Hairpin Bandpass on Teflon

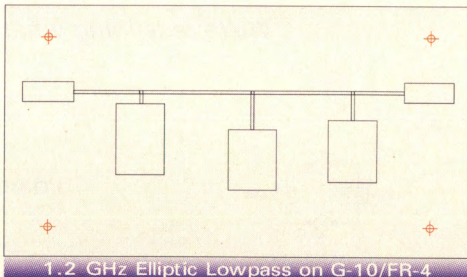

1.2 GHz Elliptic Lowpass on G-10/FR-4

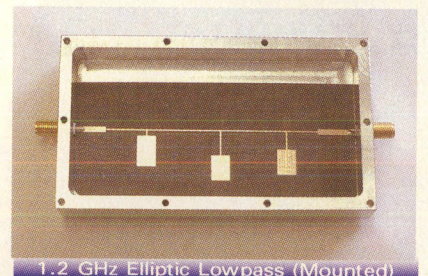

1.2 GHz Elliptic Lowpass (Mounted)

## THEY WERE DESIGNED WITH THE NEW =M/FILTER=

### COMPLETE SET OF DISTRIBUTED STRUCTURES

- ★ Lowpass, bandpass, highpass & bandstop
- ★ Microstrip, stripline, coax & slabline (machined)
- ★ Edge coupled, end coupled, direct coupled
- ★ Hairpin, combline, interdigital, elliptic, stepped-Z

### START TO ART


- ★ Complete design including synthesis & simulation
- ★ Output layout to plotters & laser printers
- ★ HPG and DXF files ready for board suppliers
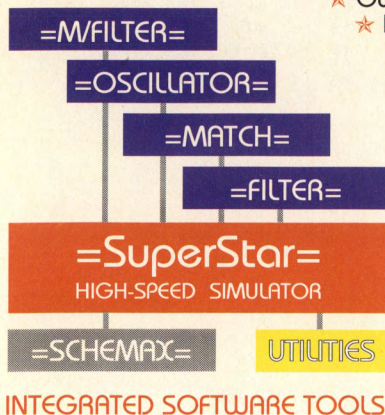
### STATE-OF-THE-ART ALGORITHMS

- ★ Automatic end, bend, tee and cross absorption
- ★ Corrects dispersion & differential phase velocity
- ★ Accurate design bandwidth
- ★ N-coupled line models



★ Design began at 11AM on four microstrip filters and HPG files were ready for board suppliers by 1 PM. Using T-Tech's Quick Circuit milling platform, boards were ready for test by 5PM. =M/FILTER= files were tested by several board suppliers to insure compatibility.



SAME PRICES INTERNATIONALLY  
DIRECT SALES & USER SUPPORT  
BY FAX, PHONE OR LETTER

## EAGLEWARE

Eagleware Corporation ★ 1750 Mountain Glen ★ Stone Mtn, GA 30087 ★ USA

TEL (404) 939-0156 ★ FAX (404) 939-0157




### featured technology

#### 24 **Medium Power Bipolar Design Using the NE46134 Nonlinear Model**

Once out of the small-signal regime, determining a transistor's input and output impedances becomes difficult. In this article, a nonlinear transistor model is used to determine the input and output impedances of the NE46134. The results of the non-linear modeling are compared to impedances derived with other theoretical models and with the performance of an operating, "hand tuned" amplifier.

— Lynne Olsen and Brian Kirk

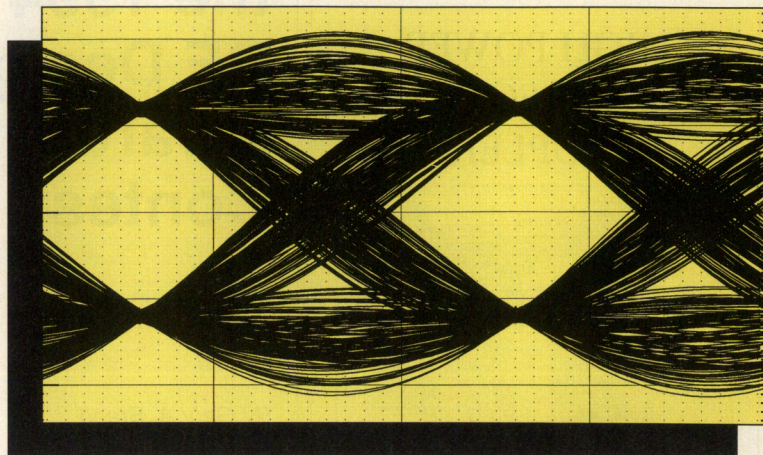

### cover story

#### 34 **Simulating a QPSK Modem**

This article demonstrates the use of TESLA, a block-level simulator, to perform fast, accurate evaluation of a QPSK modem design. Intersymbol interference, bit error rate and even occupied bandwidth can be evaluated.

— Don Miller

### tutorial

#### 48 **Receiver Basics — Part 1: Performance Parameters**

The first part of this receiver tutorial presents the parameters that are used to specify and characterize receiver performance.

— Gary A. Breed

### design awards

#### 60 **Software for Lumped Element Design**

This software entry to the 1993 RF Design Awards contest designs lumped-element circuits for VHF frequencies and below. Routines for designing power dividers, matching networks, bandpass filters and attenuators are among the those incorporated into this program.

— M. Saroja

#### 62 **Broadband Transmission Line Transformer Family Matches a Wide Range of Impedances**

The family of broadband transmission line transformers introduced here achieves impedance matching flexibility that is not possible with existing designs, such as the well-known Guanella devices.

— Donald A. McClure

#### 67 **RF Expo West Program and Short Courses Schedule**

Presented here are the courses and sessions offered at the *tenth* RF Expo West. Courses start on March 21, while technical sessions and company exhibits begin on March 22.

### departments

- 8 Editorial
- 12 Courses
- 17 Calendar
- 18 News
- 22 Industry Insight
- 40 New Products
- 69 Product Report
- 70 Marketplace
- 70 Advertiser Index
- 73 New Software
- 74 Company Index
- 75 Info/Card

RF DESIGN (ISSN:0163-321X USPS: 453-490) is published monthly and semi-monthly in August, February 1994, Vol.17, No. 2. *RF Design* is a registered trademark of Argus Inc. Copyright 1994 by Argus Business, a division of Argus Inc., 6151 Powers Ferry Road, NW, Atlanta, GA 30339, (404) 955-2500; Scott Smith, President; Wayne Otterbourg, C.P.A., Vice President, Finance; Arthur E. Sweum, Senior Vice President; Dennis Corcoran, President, Argus Trade Shows. Editorial and advertising offices at 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111, (303) 220-0600. Printed in USA. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: *RF Design*, P.O. Box 1077, Skokie, IL 60076. Subscriptions are: \$39 per year in the United States; \$49 per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700. Authorization to photocopy items for personal use is granted by *RF Design*, provided the base fee of \$3 is paid directly to Copyright Clearance Center, 222 Rosewood Drive, Danvers, MA 01923 and provided the number of copies is fewer than 100. For authorization, contact the Copyright Clearance Center at (508) 750-8400. The Transactional Reporting Service fee code is: 0163-321X/94/\$3.00. For those seeking 100 or more copies, please contact the magazine directly at (303) 220-0600.

SUBSCRIPTION INQUIRIES: (708) 647-0756.



# WERLATONE

DECADES AHEAD

## HIGH POWER DUAL DIRECTIONAL COUPLERS



### MULTI-OCTAVE BANDWIDTH

### TYPICAL SPECIFICATIONS

FREQ. RANGE ..... 80-1000 MHz  
INS. LOSS ..... 0.1 db  
FLATNESS ..... +/-0.5db  
DIRECTIVITY ..... 20 db min.  
VSWR ML ..... 1.2:1max.

#### MODEL C3240

COUPLING ..... 40db nom.  
POWER CW ..... 200 watts

#### MODEL C3271

COUPLING ..... 50 db nom.  
POWER CW ..... 1500 watts

### BROADBAND HIGH POWER

- DIRECTIONAL COUPLERS
- POWER COMBINERS
- HYBRID JUNCTIONS

P.O. BOX 47 • ROUTE 22 • BREWSTER, N.Y. 10509  
914-279-6187 • FAX 914-279-7404

## RF editorial

# Announcing the 1994 RF Design Awards Contest

By Gary A. Breed  
Editor

Get ready for the new, improved and updated 1994 RF Design Awards Contest!

We are ready once again to recognize the innovation and hard work that results in new ideas and better ways for RF engineers to get the job done.

We have held the RF Design Awards Contest every year since 1986. In that time, the Grand Prizes have gone from a \$500 programmable calculator to \$20,000+ instruments and software packages! In 1991, we expanded the contest into two separate contests, one for circuit design and one for design software. Also, each year the winners have been presented to the RF engineering community in the July issue. After examination of past contests and consideration of all the factors surrounding them, we have made a few adjustments.

The only major change is a return to a single contest — we decided that judging one contest, and determining one Grand Prize winner is enough! However, the single contest will allow either circuit design or design software entries. The entry rules for each type of entry are very similar to past years' contests (see page 25), but we are implementing some new judging criteria.

The primary goal of the judging is to determine which entry makes the biggest contribution to the art and science of RF engineering. This might be "the greatest good for the greatest number," or a more specialized development that advances the state of the art. We want to recognize the efforts of an RF engineer whose work has the greatest significance for the profession.



This year, the Grand Prize is once again, well, grand! Hewlett-Packard's CAE group will present the winner with a Touchstone/Libra for Windows package from their EEsof operation. This has a value well over \$20,000, something to really shoot for!

To encourage all types of entries, we completing a line-up of the best-ever collection of second and third place prizes, plus honorable mention prizes. There is no excuse to hold back your entry because "it can't win." Lots of entries will be winners!


The other significant change is in our timing. The Grand Prize winner will be featured on the cover of our November issue, and will be presented with his or her prize in person at RF Expo East in Orlando. The prize presentation will be followed by presentation of the winning entry at a special awards session.

The deadline for entries is July 29. Entries must be postmarked by this date, and received no later than August 5. So, read the rules and look over the prizes on page 25, then get to work — you've got less than seven months to perfect that idea!


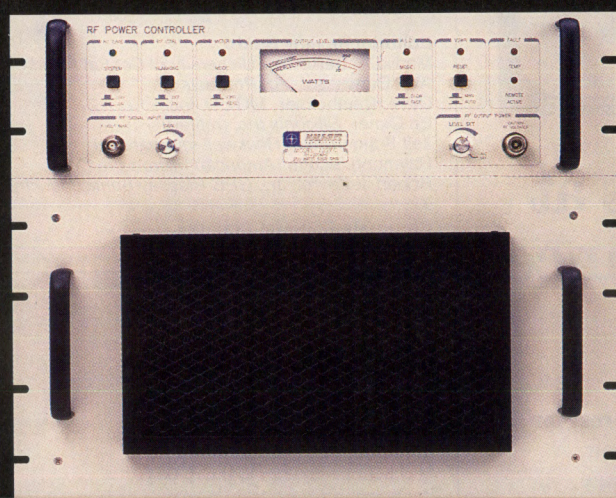
# *WHAT YOU'VE BEEN WAITING FOR!*


**Technology of the Future  
Available Today**



***250 Watts CW  
.01 - 220 MHz***
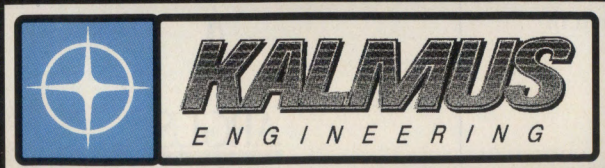
## **WORLD'S FIRST 14 Octave 250W SOLID-STATE RF Amplifier MODEL 122FC**

- Instantaneous bandwidth, no warm-up
- Fully protected
- No VSWR shutdown, drives mismatched loads
- ALC gain leveling & power limit set
- All front panel controls available via remote connector
- IEEE488 / RS232 interface capability
- 19" rack mountable, weight 50 kg
- US \$19,950.00




**1-800-344-3341**  
**(206) 485-9000** **fax (206) 486-9657**  
**21820-87th S.E. • Woodinville, WA 98072 • USA**  
**Paris, France**  
**phone 1-4645-0945** **INFO/CARD 6** **fax 1-4645-2403**

***The World's Most Complete  
Line of RF Power Amplifiers***

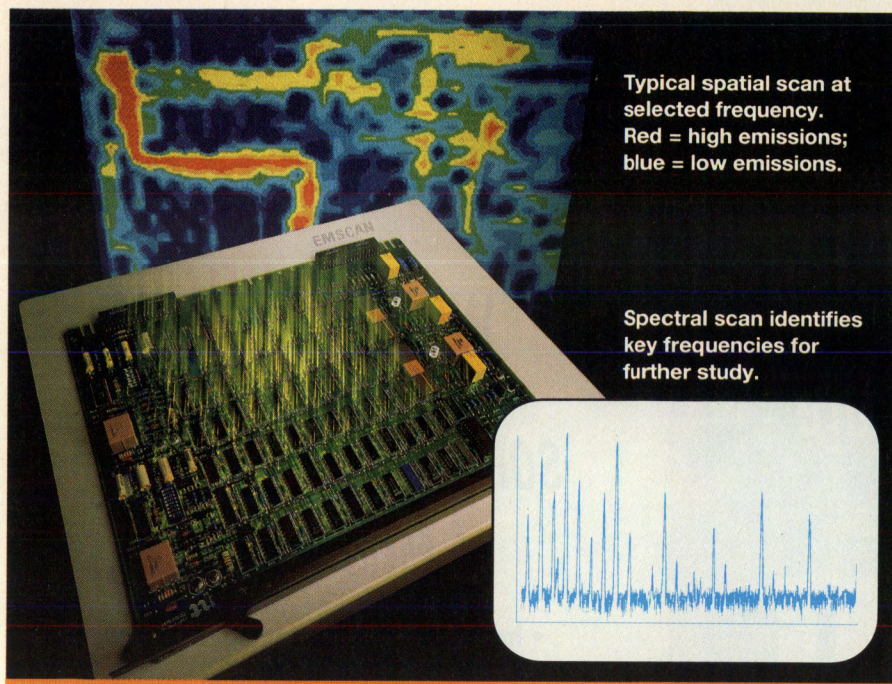***More Than 200 Standard Models  
to Choose From***





## Catch emissions problems at board level, where compliance fixes are least costly.

**N**ow you can quickly get a color image of the electromagnetic performance of your printed-circuit board or subassembly *before* final compliance testing. Spatial and spectral displays generated by the EMSCAN PCB emissions scanner show you which frequencies and which areas of the board under test are guilty. These scans are stored for later comparison after design alterations, to check whether offending emissions are now down to acceptable levels.

Just plug your receiver or spectrum analyzer, and your computer with IEEE-488 interface, into the EMSCAN scanner, and a matrix of 1280 H-field probes maps the area of your test board (up to 9" x 12") for high, medium, and low-emissions spots within the 10-to-750-MHz frequency range. Or you can see a spectral display showing the overall condition of the board across the spectrum. You may then choose a

frequency of particular interest for intensive spatial examination.

After the development stage, you can use EMSCAN as a quality-control tool, checking completed boards against a "good" scan before they go into assembly. This is the point where production compliance becomes virtually assured.

The software operates under "Windows" to make early diagnosis easy, even for those who are new to compliance testing. It can run on several PCs and workstations, and is readily ported to other environments for analysis.

You should learn all about this qualitative and quantitative measure of emissions for use during product development—where design corrections are least costly. To start, call toll-free (1-800-933-8181) to speak with an applications engineer and arrange to see a demonstration in your office or plant.



160 School House Road  
Souderton, PA 18964-9990 USA  
215-723-8181 • Fax 215-723-5688

For engineering assistance, sales, and service throughout Europe, call  
EMV • Munich, 89-612-8054 • London, 908-566-556 • Paris, 1-64-61-63-29

INFO/CARD 7

# RFdesign

Established 1978

**President — Argus Business**  
Jerrold France

**Editorial and Advertising Offices**  
6300 S. Syracuse Way, Suite 650  
Englewood, CO 80111  
(303) 220-0600 Fax: (303) 773-9716

**Vice President and Group Publisher**  
David Premo (303) 220-0600

**Editor**  
Gary A. Breed (303) 220-0600

**Technical Editor**  
Andrew M. Kellett (303) 220-0600

**Assistant Editor**  
Ann M. Trudeau (303) 220-0600

**Consulting Editor**  
Andy Przedpelski, *The Shedd Group*

**Editorial Review Board**  
Madjid A. Belkaid, *University of Central Florida*  
Alex Burwasser, *RF Products*  
Dave Krautheimer, *MITEQ, Inc.*  
Ed Oxner, *Siliconix Inc. (retired)*  
Jeff Schoenwald, *Rockwell International*  
Raymond Sicotte, *American Microwave Corp.*  
Robert J. Zavrel, Jr., *GEC Plessey Semiconductors*

**Corporate Editorial Director**  
Robin Sherman (404) 618-0267

**Account Executives**  
Jessica Caid (303) 220-0600  
Mike Henry (703) 257-1202  
Tisha Hill (303) 220-0600  
Brian Noto (303) 220-0600  
Jeff Peck (303) 220-0600  
Cindy Solomonson (303) 220-0600

**Classified Advertising Manager**  
Michael Applegate (404) 618-0217

**Vice President — Production and Promotion**  
Cherryl Greenman (404) 618-0302

**Production Manager**  
Jenny Tague (404) 618-0401

**Reprints Manager**  
Vivian Peterson (303) 220-0600

**Creative Director**  
Brian Buxton (404) 618-0108

**Art Director**  
David Alden (404) 618-0188

**Circulation Manager**  
Shawn DeMario (404) 618-0259

**List Rental Manager**  
Etta Davis (404) 618-0266


**Argus Business Corporate Offices**  
6151 Powers Ferry Rd., N.W.  
Atlanta, GA 30339-2941  
Tel: (404) 955-2500



Subscription inquiries: (708) 647-0756


February 1994



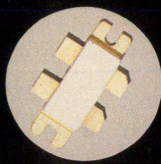
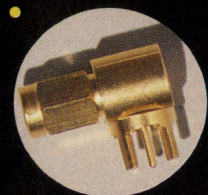
# Richardson Electronics is Your Global Partner in RF Technology

Offering solutions to customer problems for more than 40 years, Richardson Electronics, Ltd. has grown into one of the world's premier suppliers of RF devices.




Philips Components

## This Month's Feature . . .



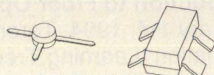
# PHILIPS

Quality RF & Microwave Semiconductors and Modules




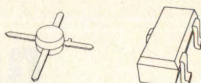
### Discrete Semiconductors

- Wideband Transistors
- Video Transistors
- RF Power Transistors
- Microwave Transistors


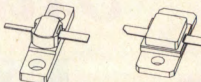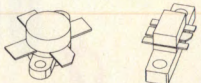
### Modules

- Wideband Amplifiers
- Video Amplifiers
- CATV Amplifiers
- RF Power Amplifiers




### Application Information

- Wideband Transistors
- Video Transistors
- RF Power Amplifiers
- Microwave Amplifiers



**Design Support • Extensive Inventory •  
Market Knowledge**

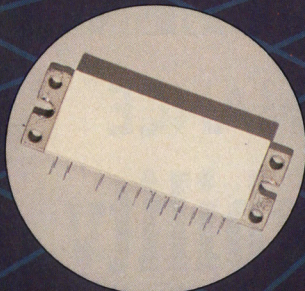- Technical Expertise
- Experience
- Inventory
- Market Knowledge
- Supplier Literature



Richardson Electronics, Ltd. has available from stock the wide range of RF & Microwave semiconductors and modules from Philips components. Richardson is your source for Philips quality products from stock. Call Richardson with all your Philips RF needs today.

**Our industry-leading RF suppliers . . .**



MOTOROLA



SGS-THOMSON

**Amphenol®**

**MACOM**



RF JOHNSON



PHILIPS



RF PRODUCTS

**AMERICAN  
MICROWAVE  
TECHNOLOGY**




**PINEAPPLE  
TECHNOLOGY**

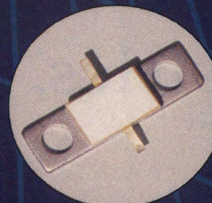**Committed to the RF Market—**



**Richardson  
Electronics, Ltd.**

40W267 Keslinger Road  
LaFox, Illinois 60147  
(708) 208-2200



U.S. (800) RF POWER  
CANADA (800) 348-5580  
U.K. (0522) 542631  
FRANCE (1) 34-26-4000  
ITALY (055) 420-10-30  
SPAIN (1) 528-37-00  
GERMANY (089) 80-02-13-1  
JAPAN (3) 3874-9933  
SINGAPORE (65) 298-4974

Latin America and other international inquiries, contact Corporate Headquarters at (708) 208-2200



# RF courses

## **Principles of Pulse Doppler Radar: High, Medium, and Low PRF**

February 15-17, 1994, Atlanta, GA

## **Phased-Array Radar System Design**

April 19-22, 1994, Atlanta, GA

## **Principles of Electronic Counter-Countermeasures**

April 26-28, 1994, Atlanta, GA

Information: Georgia Institute of Technology, Continuing Education Tel: (404) 894-2547.

## **RF & Microwave Measurements & Applications**

March 7-10, 1994, San Diego, CA

## **Navstar/GPS: Design Applications**

August 1-3, 1994, Washington, DC

## **High Speed & Microwave Devices & Applications**

October 24-27, 1994, Boston, MA

Information: University Consortium for Continuing Education, 16161 Ventura Boulevard, M/S C-752, Encino, CA 91436.

Tel: (818) 995-6335. Fax: (818) 995-2932.

## **Satellite Communication Systems**

April 18-22, 1994, Cambridge, UK

## **VSAT Networks**

April 20-21, 1994, Cambridge, UK

## **Mobile Cellular and Microcellular Telecommunications**

April 20-22, 1994, Cambridge, UK

Information: CEI-Europe/Elsevier, Mrs. Tina Persson. Tel: (46) 122-175-70. Fax: (46) 122-143-47.

## **Antennas: Principles, Design, and Measurements**

March 9-12, 1994, St. Cloud, FL

Information: Northeast Consortium for Engineering Education, Central Florida Facility - Management Office, 1101 Massachusetts Ave, St. Cloud, FL 34769, Kelly Brown - Registrar. Tel: (407) 892-6146. Fax: (407) 957-4535.

## **DSP Without Tears**

February 2-4, 1994, Albuquerque, NM

February 9-11, 1994, Falls Church, VA

April 6-8, 1994, Chicago, IL

May 11-13, 1994, Richardson, TX

May 18-20, 1994, San Jose, CA

Information: Z Domain Technologies, Inc., 325 Pine Isle Court, Alpharetta, GA 30202. Tel: (800) 967-5034, (404) 664-6738.

Fax: (404) 442-1210.

## **Introduction to Fiber Optic Communications**

February 1-4, 1994, Toronto, Canada

Information: Learning Tree International. Tel: (800) 421-8166, (703) 893-3555, (203) 417-8888.



- *Fixed Attenuators*
- *Terminations*
- *Rotary Attenuators*
- *Programmable Attenuators*
- *Switches*
- *Matrix Switches*

**QUALITY**  
*Innovation*  
**EXCELLENCE**  
**PERFORMANCE**  
**Reliability**

## **JFW Industries, Inc.**

5134 Commerce Square Drive

Indianapolis, Indiana 46237

Tel. 317-887-1340

Fax 317-881-6790

INFO/CARD 9

*JFW celebrates  
15 years as  
the innovative force  
in the industry!*



# **No One** Stocks More

## **RF & Microwave Transistors, Semiconductors and Modules**



 **Richardson  
Electronics, Ltd.**

**1-800-RF POWER (U.S.A.)**

**40W267 Keslinger Road  
LaFox, Illinois 60147  
(708) 208-2200**

INFO/CARD 10

<b>CANADA</b>	<b>(800) 348-5580</b>
<b>U.K.</b>	<b>(0522) 542631</b>
<b>FRANCE</b>	<b>(1) 34.26.4000</b>
<b>ITALY</b>	<b>(055) 420.10.30</b>
<b>SPAIN</b>	<b>(1) 528 37 00</b>
<b>GERMANY</b>	<b>(089) 80 02 13 1</b>
<b>JAPAN</b>	<b>(3) 3874-9933</b>
<b>SINGAPORE</b>	<b>(65) 298-4974</b>



**GIGA-TRONICS**  
**6080A & 6082A**  
**SYNTHESIZED**  
**RF SIGNAL**  
**GENERATORS**

# Giga-tronics Presents The Alternative To \$30,000 And \$40,000 RF Synthesizers.

Hewlett-Packard makes a couple of very good RF synthesizers. And if you can afford the luxury of paying \$30,000 or \$40,000 for the name, by all means, call HP right now. They'll be happy to take your order, and your money.

However, if you're looking for an RF synthesizer with outstanding performance and proven reliability for about half the price, you'd better call Giga-tronics.

Here's why:

## Performance.

Check the charts. In virtually every category, the Giga-tronics 6080A and 6082A RF Synthesizers meet or exceed the specs of the HP machines. And they use the same GPIB command set, for direct replacement without expensive new software.

## Experience.

Granted, Hewlett-Packard has been around a long time. But, Giga-tronics


is no Johnny-come-lately.

Giga-tronics has a 13-year history of building test and measurement gear for the most demanding requirements. We've shipped thousands of instruments for use in the testing of radar, EW and communications systems.

## Reliability.

Making reliable RF synthesizers is usually no fluke.

However, in this case, it is.

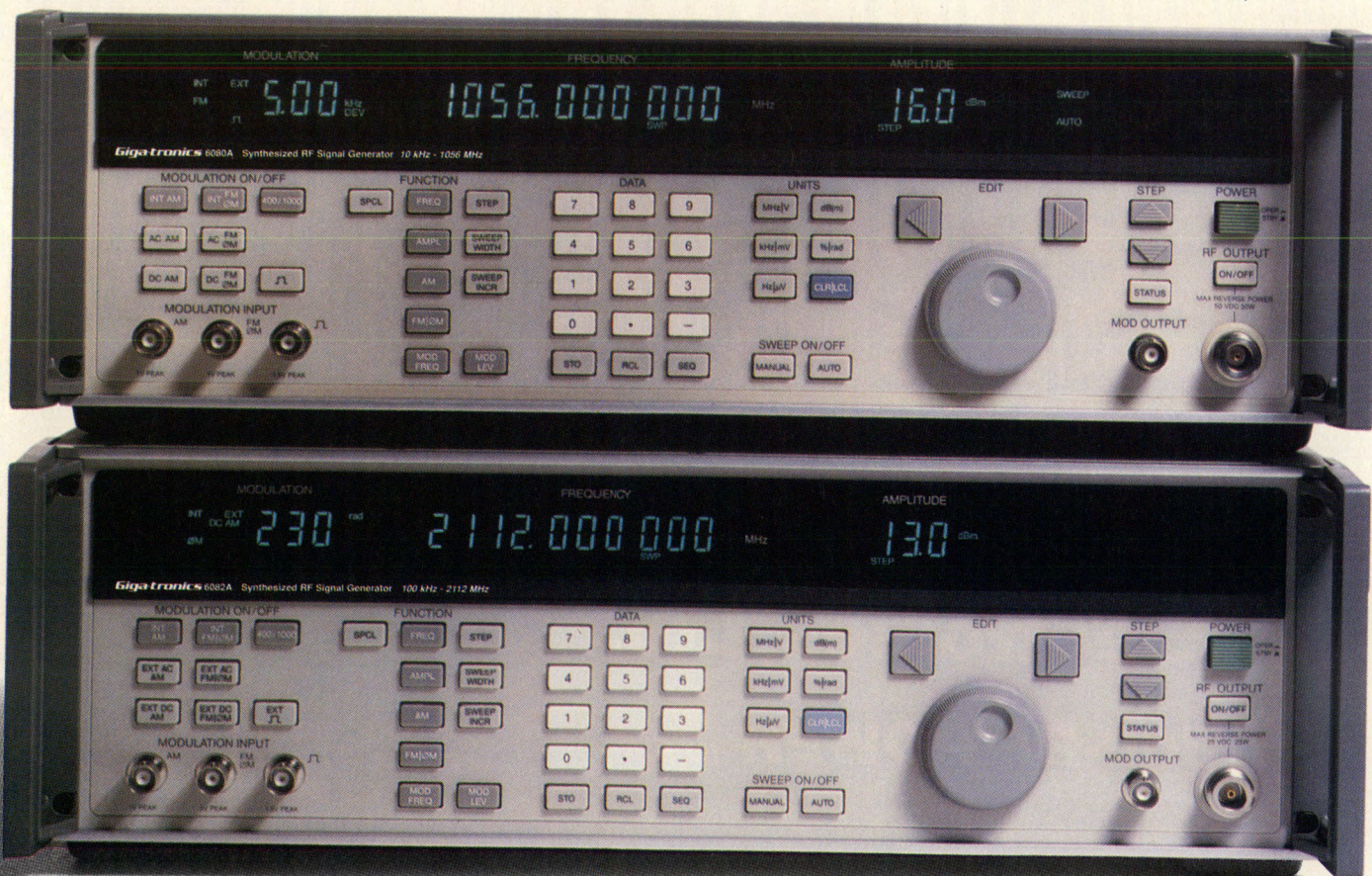

*The Giga-tronics 6080A and 6082A RF Synthesizers give you great performance and proven reliability for a lot less money.*



Both the 6080A and 6082A were originally introduced in 1990 by John Fluke Manufacturing Company. To date, thousands have performed flawlessly in the field.

For added confidence, the instruments incorporate self-testing, internal diagnostics and modular design for easy fault isolation and repair.

#### Service.

If a problem occurs, Giga-tronics technical support staff can often help you find and fix the problem over the phone.

If you need to return an instrument for repair, we can service it at our factory in California, or at one of our worldwide sales and service centers.

But at Giga-tronics, customer service starts even before you become a customer.

Whether you're looking to buy one unit or one hundred, you'll get the same assistance, including a demonstration at your facility.

#### Price.

Considering all this, the real question is not why Giga-tronics is so much less, but rather, why Hewlett-Packard wants so much more?

Specifications	Hewlett-Packard HP 8642A	Giga-tronics 6080A	Hewlett-Packard HP 8642B	Giga-tronics 6082A
Frequency Range	.1 to 1057 MHz	.01 to 1056 MHz	.1 to 2115 MHz	.1 to 2112 MHz
Switching speed	<85 ms	<100 ms	<85 ms	<100 ms
Spectral Purity*				
Spurious	<-100 dBc	<-100 dBc	<-94 dBc	<-94 dBc
Subharmonics	None	None	<-45 dBc	<-45 dBc
Phase Noise*				
@ 20 kHz offset	<-134 dBc/Hz	<-131 dBc/Hz	<-125 dBc/Hz	<-125 dBc/Hz
Residual FM*				
(.3 to 3 kHz BW)	<2 Hz	<1.5 Hz	<5 Hz	<3 Hz
Output Range*	+16 to -140 dBm	+17 to -140 dBm	+16 to -140 dBm	+13 to -140 dBm
Accuracy	±1 dB >-127 dBm	±1 dB >-127 dBm	±1 dB >-127 dBm	±1 dB >-127 dBm
Reverse Power Protection	50 Watts/50 Vdc	50 Watts/50 Vdc	25 Watts/25 Vdc	25 Watts/25 Vdc
Amplitude Modulation				
Depth	0-99.9%	0-99.9%	0-99.9%	0-99.9%
Distortion @ 30%	<2%	<1.5%	<2%	<1.5%
Frequency Modulation				
Max. Deviation*	3 MHz	4 MHz	3 MHz	8 MHz
Distortion	<2%	<1% @ 50% Dev.	<2%	<1% @ 50% Dev.
Phase Modulation				
Max. Deviation*	100 Rad.	40/400 Rad.	200 Rad.	80/800 Rad.
Pulse Modulation				
On/off	>40 dB	>40/60 dB	>40/80 dB	>80 dB
Rise/fall time	<400 ns	<15 ns (Typ 7.5 ns)	<400 ns	<15 ns (Typ 7.5 ns)
Minimum Pulse Width	<2 µs	<30 ns	<2 µs	<30 ns
Internal Modulation Source	20 Hz to 100 kHz	0.1 Hz to 200 kHz	20 Hz to 100 kHz	0.1 Hz to 200 kHz
Level Range	0 to 3 Vpk	0 to 4 Vpk	0 to 3 Vpk	0 to 4 Vpk
Waveforms	Sine	Sine/Sq/Tri/Pulse	Sine	Sine/Sq/Tri/Pulse
Programmable	Yes	Yes	Yes	Yes
Memory Locations (NVM)	51 Full Function	50 Full Function	51 Full Function	50 Full Function
U.S. List Price	\$30,340	\$16,950	\$41,680	\$22,950

The question is not why Giga-tronics is so much less,

but rather, why Hewlett-Packard wants so much more.

\*Specifications for both the 6080A and the HP 8642A are at 1 GHz. Specifications for both the 6082A and the HP 8642B are at 2 GHz. Prices and specifications for the HP 8642A and HP 8642B are from the Hewlett-Packard 1993 catalog. Prices for the Giga-tronics 6080A and 6082A are U.S. list prices.

So, if you're interested in paying a lot less for great performance and proven reliability, backed by a worldwide network of service and support, call us toll free at **800 726 GIGA (4442)**. We'll send you more information and arrange for a demonstration.

**Giga-tronics**

Giga-tronics Incorporated  
2495 Estand Way  
Pleasant Hill, California 94523  
Telephone 800 726 4442  
Telefax 510 680 7736  
INFO/CARD 11




# TRANSMITTERS

**\$ 1,248.00 each** (\$978.00 each at 100 units)

45-Day Delivery for the First Unit of our Standard 2-Watt, Single Frequency, AC Coupled Transmitter in any of the following configurations:

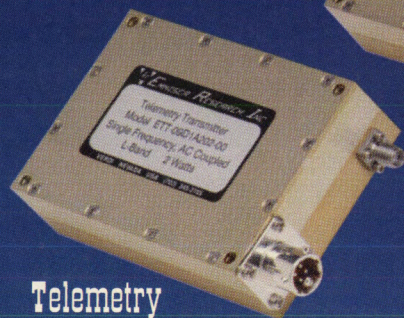Telemetry, Video, or Digital  
L, L/S, or S Band  
SMA, N, or TNC  
RF Connector



Telemetry



Video



Digital

## OTHER PRODUCTS:

Receivers • Beacon Transmitters  
Command Encoders & Decoders  
Amplifiers • VCOs  
(Rack Mount Available)

## OTHER TRANSMITTERS AVAILABLE IN ANY COMBINATION OF THE FOLLOWING FEATURES:

- Telemetry, Video, or Digital
- 2, 5, or 10 Watts
- Single Frequency or Channelized
- Frequency Bands:
  - D1 = 1435 to 1540 MHz (L Band)
  - D2 = 1710 to 1850 MHz (L/S Band)
  - E1 = 2200 to 2299 MHz (Lower S Band)
  - E2 = 2300 to 2400 MHz (Upper S Band)
- AC or DC Coupled
- SMA, N, or TNC RF Connector
- 9 Cubic Inch (3.5" x 2.5" x 1.0") or  
11 Cubic Inch (3.5" x 2.5" x 1.3")

## Call for Price and Delivery

Starting from Single Piece Price of

**\$ 1,783.00 each**

*Call our engineers with your specific requirements*

- **Options:** Pre-Emphasis, Subcarrier(s),  
Extended Temperature, Multiple Bit Rate,  
Other Special Requirements



**EMHISER RESEARCH, INC.**

2705 Old Highway 40 West  
P.O. Box 189  
Verdi, Nevada 89439-0189 USA  
INFO/CARD 12

TEL: (702) 345-2705  
FAX: (702) 345-2484

Since 1978





# RF calendar

## March

**14-17 The Second International Symposium on Digital Audio Broadcasting**  
Toronto, Canada  
Information: DAB Symposium '94, 126 York Street, #401, Ottawa, Ontario, Canada, K1N 5T5. Tel: (613) 594-8226. Fax: (613) 565-2173.

**20-24 National Association of Broadcasters '94**  
Las Vegas, NV  
Information: NAB '94 Convention, 1771 N Street, NW, Washington, DC 20036-2891. Tel: (800) 342-2460. (202) 342-4972. Fax: (202) 775-2146.

**22-24 RF Expo West**  
San Jose, CA  
Information: RF Expo West, Registration Coordinator, 6151 Powers Ferry Rd. NW, Atlanta, GA 30339. Tel: (800) 828-0420. Fax: (404) 618-0441.

**29-30 IEEE SCV EMC '94**  
Santa Clara, CA  
Information: David Hanttula, Chairman Santa Clara Valley EMC '94, P.O. Box 2102, Cupertino, CA 95015-2102. Tel: (415) 390-1071.

## April

**5-7 Second International Conference on Ultra-Wideband, Short-Pulse Electromagnetics**  
New York, NY  
Information: Lawrence Carin, Weber Research Institute, Polytechnic University, Six MetroTech Center, Brooklyn, NY 11201. Tel: (718) 260-3876. Fax: (718) 260-3906.

**12-14 Second International Conference on Computation in Electromagnetics**  
Nottingham, UK  
Information: CEM 94 Secretariat, IEE Conference Services, Savoy Place, London WC2R 0BL, UK. Tel: (071) 344-5478 or 5477. Fax: (071) 497-3663.


**12-15 EMC/ESD International**  
Anaheim, CA  
Information: EMC/ESD International, Registration Coordinator, 6151 Powers Ferry Rd. NW, Atlanta, GA 30339. Tel: (800) 828-0420. Fax: (404) 618-0441.

## May

**23-24 Microwave & Millimeter-Wave Monolithic Circuits Symposium**  
San Diego, CA  
Information: Richard B. Gold, Pacific Monolithics, 245 Santa Ana Court, Sunnyvale, CA 94086-4512. Tel: (408) 732-8000. Fax: (408) 732-3413.

**23-26 IEEE MTT-S International Microwave Symposium**  
San Diego, CA  
Information: MTT-S Symposium 1994, c/o LRW Associates, 1218 Balfour Drive, Arnold, MD 21012

## Sprague-Goodman

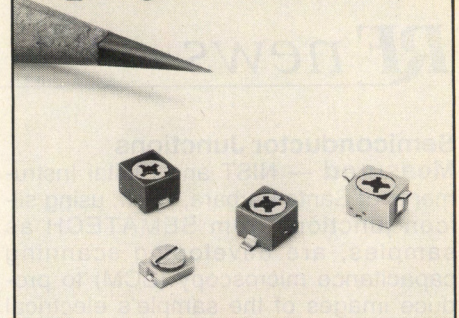

### Surftrim® Surface Mount Trimmer Capacitors

- 2 sizes:  
3.2 x 4.5 x 1.6 mm  
4.0 x 4.5 x 2.7 mm (sealed)
- 4 mounting configurations
- Carrier and reel, or bulk pack
- 1.7 to 50 pF in 7 cap ranges
- Operates to 85°C

Phone, fax or write today for  
Engineering Bulletin SG-305B.


**SPRAGUE  
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040  
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 13

Please see us at RF Expo West '94, booth 718

## Sprague-Goodman

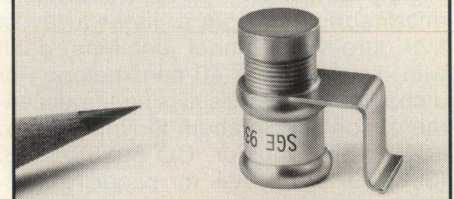

### Airtrim® Air Dielectric Multiturn Trimmers

- Q (min): 5000 at 100 MHz
  - Nine mounting styles including surface mount
  - Designed to meet MIL-C-14409D
  - Operating temp: -65°C to +125°C
  - Standard cap ranges: 0.35 to 3.5 pF, 0.6 to 6 pF, and 0.8 to 10 pF
  - Multiturn resolution
  - Extremely stable over temperature, frequency, voltage, etc.
  - Rated voltage: 250 VDC
  - Self-resonant frequency: >5 GHz
  - Insulation resistance: >10<sup>8</sup> MΩ
- Phone, fax or write today for  
Engineering Bulletin SG-660.

**SPRAGUE  
GOODMAN**

134 Fulton Ave., Garden City Park, NY 11040  
Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 14

Please see us at RF Expo West '94, booth 718



## Semiconductor Junctions

**Measured** — NIST and Digital Instruments of Santa Barbara, Calif., using silicon junctions from SEMATECH as samples, are developing scanning capacitance microscopy (SCM) to produce images of the sample's electrical character. The Semiconductor Industry Association's Technology Roadmap identifies nanoscale junction profiling as essential metrology for the development of integrated circuits. Theoretical SCM modeling research is being coupled with the practical measurement and calibration techniques possible with an atomic force microscope. This technology is expected to affect the semiconductor industry by giving developers a critical tool for improving integrated circuits. For technological information, contact Joseph J. Kopanski, A305 Technology Bldg., NIST, Gaithersburg, MD 20899-0001. (301) 975-2089.

## Capacitance Standard In Development

— NIST has developed a new standard of capacitance based on counting electrons as they charge the capacitor at 0.1 Kelvin. Metrological applications require errors lower than 1 ppm and NIST has demonstrated an electron pump that operates with errors slightly lower than 1 ppm. The device is microfabricated from a linear array of five ultra-small tunnel junctions, each with dimensions of 40 nanometers. For a copy of a paper discussing the experiment, contact Sarabeth Moynihan, Div. 104, NIST, Boulder, CO 80303-3328. (303) 497-7765. Ask for paper No. 43-93.

**Cellular Interface Standard** — The Telecommunications Industry Association's (TIA) TR 45.4 subcommittee has the task of defining and developing a standard interface between cellular Base Station Subsystems (BSS) and Mobile Telephone Switching Offices (MTSO), to be used throughout Pan America. The Interface Specification submitted by Motorola will support RF interfaces for AMPS (IS-533), NAMPS (IS-88), USDC (IS-54), CDMA (IS-95) and other functions including Intersystems Operations (IS-41). The proposed interface, developed by Motorola and other cellular equipment suppliers, would enable any vendor's base station to work with any cellular switch.

**World Communications Development** — In November of 1993 the World Telecommunication Advisory

Council (WTAC) recommended to the ITU to proceed with the feasibility phase on WorldTel—a funding and development organization to promote worldwide telecommunication expansion. The study, expected to be conducted in early 1994, will focus on the establishment of a commercially run organization whose goal is to cut the widening gap between the information-rich industrialized countries and the information-poor developing countries. WTAC reported that the prospects for reducing the gap without an international effort are very slim. WorldTel is to act as a multinational (not purely intergovernmental) organization and will have no institutional linkage to the ITU. However, the study is expected to be undertaken under the auspices of ITU with the support of the WorldTel Working Group of WTAC. It will be financed by contributions from interested sponsors who will be provided with the opportunity of reviewing the study at the draft stage.

## Voluntary Standards Seminar

— The Federal Interagency Committee on Standards Policy, chaired by Stanley I. Warshaw, director of NIST's Office of Standards Services, will hold a one-day seminar on the Oct. 1993 revisions to the Office of Management and Budget Circular No. A-119. This meeting is for private-sector and public interests to discuss the revisions' affect on the standards' community. The seminar is Feb. 23, 1994, 9 a.m. in the auditorium of the Department of Commerce, 14th Street and Constitution Avenue, N.W.; Washington, DC 20230. Contact: Office of Standards Services, A603 Administration Bldg., NIST, Gaithersburg, MD 20899-0001. Phone: (301) 975-4000. FAX: (301) 963-2871.

## BBS has SPICE Models and Application Notes

— Intusoft has setup a SPICE Bulletin Board on CompuServe Information Service. The BBS also contains software utilities and demonstration software and is under the CADD/CAM/CAE Vendor forum an on-line electronic service. On CompuServe type "Go CADDVEN" at any prompt and select the "All CADD/CAM/CAE" section. The Intusoft CompuServe address for e-mail is 71564,3147. Internet users can send Intusoft e-mail via: "71564.3147@compuserve.com".

## FM Data Broadcasting Proposals

— The NAB and the Electronic Industries Association (EIA) sponsor the

National Radio Systems Committee (NRSC) which sets technical standards for broadcasters and manufacturers. Proposals are being sought by the High-Speed FM Subcarrier Subcommittee of NRSC for the new standard that would allow the 6,000 FM radio stations to provide high-speed data broadcasting to fixed and mobile receivers. Cars, for example, would have real-time access to traffic information with data broadcast receivers.

## NSI Awards Diamond Depositions Contract

— Applied Science and Technology, Inc. was awarded a Phase II contract from NSF for microwave plasma diamond depositions at high growth rates. ASTeX will concentrate on gas phase chemistry changes at high power densities, techniques to control film morphology and increasing the growth rates, all of which will lead to higher deposition rates. This will make diamond coatings more cost effective per carat for use as heat sinks for thermal management, coatings for cutting tools, and free standing thick infrared optics.

## Johnstech Moves Headquarters

— A producer of test sockets Johnstech International's new address for their corporate and manufacturing headquarters is: 1210 New Brighton Blvd., Minneapolis, MN 55413-1614. Phone: (612) 378-2020. FAX: (612) 378-2030.

## RF Power Components New Address

— RF Power Components, Inc. has moved to 125 Wilbur Pl., Bohemia, NY 11716. Phone: (516) 563-5050. FAX: (516) 563-4747.

## Harris Farinon Canada Moves

— As of Jan. 3, 1994, Harris Farinon will have moved 10 km west of their original location to 3 Hotel de Ville, Dollard-des-Ormeaux; Quebec, Canada H9B 3G4. The new numbers are: (514) 421-8400. FAX: (514) 421-4222. Telex: 05-821893. Customer Service: 1 (800) 465-4654.

## Geleco RF Business Acquired by LBA Technology

— The RF systems of Geleco Electronics, Limited of Toronto, Canada has been purchased by LBA Technology, Inc. of Greenville, North Carolina, supplier of medium wave broadcasting antenna systems. Geleco, producers of antenna tuning units and RF equipment for radio broadcasting, will have their assets and inventory relocated to the expanded LBA Greenville manufacturing facility.



# \$9900

**OR LESS\***



## ANY DESIGN KIT

Type	Price, Each Kit
5mm Variable Coil .....	\$99.00
SMD Variable Coil .....	\$99.00
7mm Variable Coil .....	\$59.00
10mm Variable Coil .....	\$59.00
SMD Chip Inductors .....	\$99.00
Molded Coil .....	\$59.00
Leaded Fixed Inductors .....	\$59.00
Multilayer Chip Inductors .....	\$69.00
SMD Spring Coil .....	\$49.00

**TOKO**

**PENSTOCK**  
WORLD'S LARGEST RF/MICROWAVE DISTRIBUTOR

**CALL: 800-PENSTOCK or 408-730-0300, Canada 613-592-6088**  
**FOR OVERNIGHT DELIVERY ON TOKO PROTOTYPING KITS**



**Telecommunication Chip Sets** — Analog Devices, Inc. and Aware, Inc. have formed a development partnership to design and build chip sets that will support the emerging standard for asymmetric digital subscriber line, ADSL. This is a new ANSI-standard technology which increases the usable bandwidth of telephone lines to bring video-rate services into the home.

These services would include distance learning, video on demand, remote healthcare consultation, and telecommuting. The products will be available in mid-1994 to telecom OEMs. Data rates of 1.5-20 megabits per second can be achieved. Three companies have agreed to use the Analog/Aware chip sets in ADSL products: AT&T Network Systems, Morristown, NJ; Westell, Inc.,

Oswego, IL.; and Newbridge Networks, Kanata; Ontario, Canada.

**Cadence Sells Automated Systems Division** — This sale will allow Cadence Design Systems, Inc., San Jose, CA, to focus on software that automates and enhances the design of ICs and electronic systems. Cadence sold its Automated Systems Inc. (ASI) Division, at the end of 1993, to a corporation formed by certain ASI management personnel. ASI manufacturers and provides design services for complex PCBs and is headquartered in Brookfield, Wis.

**Small Business Research Contract** — Superconductor Technologies Inc. (NASDAQ: SCON), which supplies high-temperature superconductor (HTS) products and services, received a \$742,000 Small Business Innovative Research contract to build superconducting switches for electronic warfare (EW) subsystems. The new contract allows STI to integrate cryogenic switches with super conductor filters.



**Synthesizer Symphony**


DDS DAC  
PLL VCO

**All your synthesizer functions working in unison and perfect harmony from the Synthesizer Maestro...**

**QUALCOMM**  
VLSI Products

10555 Sorrento Valley Road  
San Diego, CA 92121 USA  
TEL: 619-597-5005  
FAX: 619-452-9096

## Radio Links

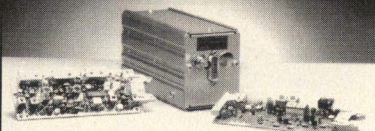

- ▶ Eliminate lease line and wireline costs
- ▶ Aggressively priced with quantity discounts available
- ▶ Transmitter and receiver links in VHF, UHF and 900 MHz are designed specifically for high-performance data transmission
- ▶ Utility data system accommodates audio inputs (modem tones) or TTL-level digital inputs
- ▶ RS-232 radio modems available in VHF, UHF and spread-spectrum (unlicensed) frequencies
- ▶ A two-way radio manufacturer for more than 30 years

**Repcor** Aerotron-Repcor Sales, Inc.  
1-800-950-5633

2400 Sand Lake Road  
Orlando, Florida 32809

**Dealer Inquiries Invited**

INFO/CARD 17



MHz

log MAG


1: 550.000 MHz

hp


SCALE

2 dB/div

# Seeing is Believing

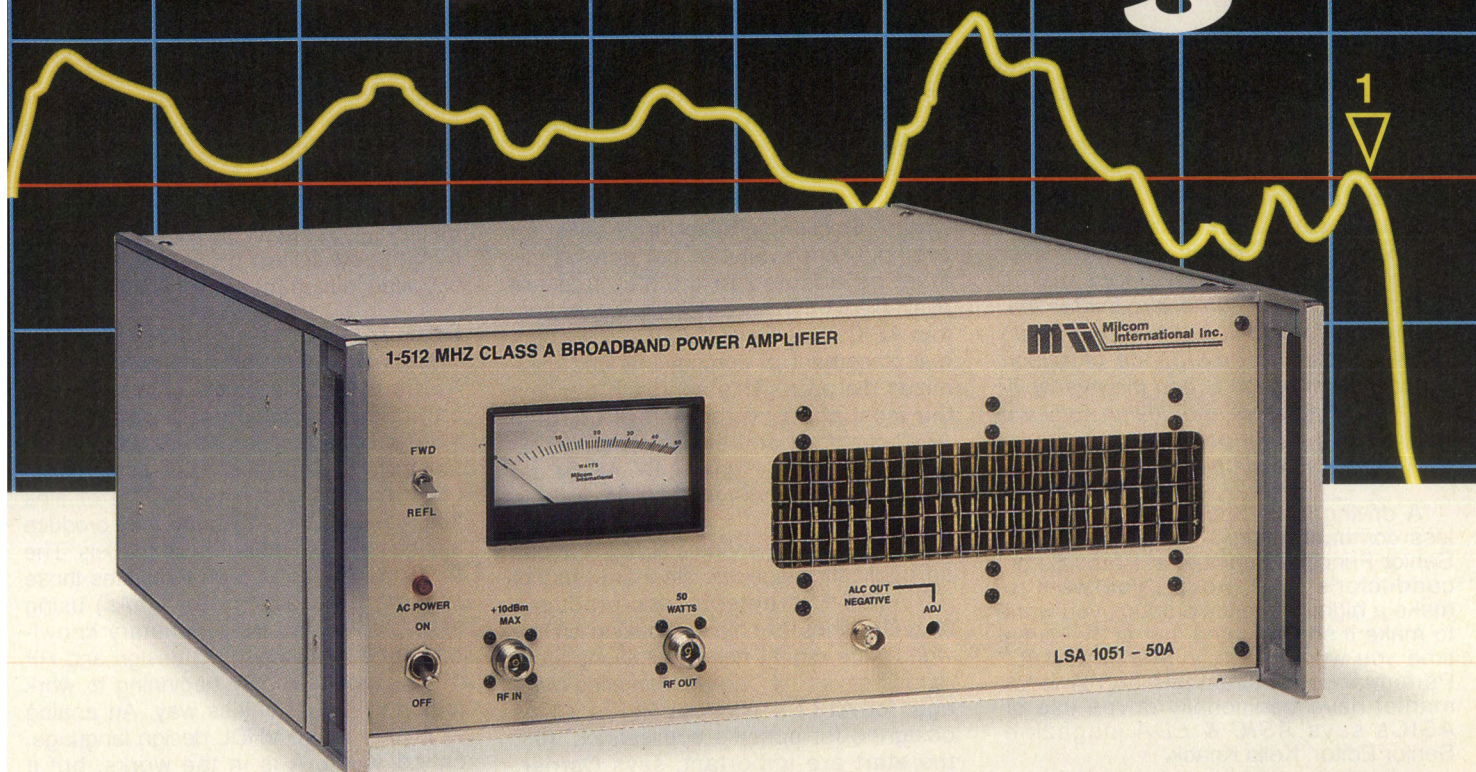
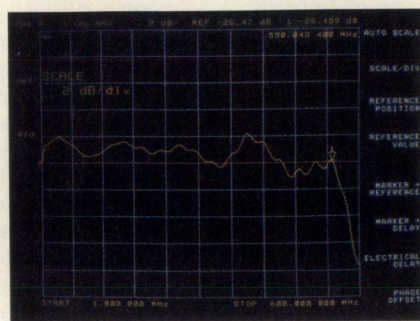
## Milcom's Newest RF Power MOSFET Distributed Amplifier 1-512 MHz, 50 Watts Class "A" Design



The newest introduction in amplifiers is not for the narrow-minded. For a range of 1 - 512 MHz, you won't find another 50 watt amp offering such

a wide range and exclusive versatility. You might say it blows the market wide open.

In fact, nothing beats it as an instrument for semi-conductor, passive component, E.M.I. development or production testing. It even produces exceptional results in fields as diverse as laser modulation and medical research.

And it's no wonder. Excellent output VSWR provides constant power into any load. And with features like a built-in power meter, external ALC output,

and totally enclosed RF modules for low E.M.I., this 50 watt amplifier sets a new standard for the industry.

So before making your next amplifier purchase, take a good look at the new 50 watt wide band amp from Milcom International. Because seeing really is believing. Give us a call at (714) 554-1710 for more details.

**Milcom International Inc.**  
We Design and Manufacture RF Power Amplifiers

INFO/CARD 18

17500 Gillette Avenue, Irvine, California 92713 • 714-554-1710 • FAX 714-554-3090



# Fast Si, New Design Tools and Portability Demands Bring ASICs to RF

By Andy Kellett  
Technical Editor

**F**ew RF designers would have even thought of implementing a new design on a single semiconductor chip a decade ago. It would have been possible to implement a complete design, after several expensive design iterations, on a single chip, (or two), of very expensive GaAs. But the need to do so just wasn't there. Today, RF Application Specific ICs (ASICs) have appeared at the confluence of three circumstances: the need for small but complex radio transceivers, the emergence of silicon processes with high  $f_t$ , and the availability of fast computers and design software which can reliably predict the behavior of RF integrated circuits.

"A driving force behind ASICs is wireless communications," says Moji Chian, Senior Principal Engineer at Harris Semiconductor's CAD group, "you want to make a high-frequency product, you want to make it sophisticated, but at the same time you want it to fit in a shirt pocket." Performance requirements and time-to-market have traditionally driven use of ASICs says *ASIC & EDA* magazine Senior Editor, Kella Knack.

Integration provides several benefits for RF applications besides reduced size, says Jack Guedj, Marketing Manager and Applications Engineer for Raytheon's high speed communications products. Among them are better performance, lower power consumption, easier board design and better reliability. There are several ways to arrive at integration: transistor array ASICs, standard cell ASICs, custom design ASICs and application specific standard products. Strictly speaking, an ASIC is any IC designed to perform most or all of the functions for a single end-use. However, when most people think of ASICs they think of one of the species of ASIC that are at least partly designed by the customer.

Picking a type of ASIC requires a balance of design effort and performance. Transistor and tile arrays allow designers to connect individual transistors and passive components, and because the customer only specifies the metalization layers, development time is fast. However, the placement of components is not opti-

mal. Standard cells reduce both die size and interconnects by providing pre-designed function blocks. Not only are the number of interconnections reduced, but so is the risk associated with creating a custom design from scratch says Guedj. Normally a few versions of any type of function (a mixer or amplifier for example) are available, but designs still must be adapted to the tiles that are available. A third approach is a fully custom ASIC. This type of ASIC allows optimal placement of components and minimizes die area. This approach requires the most effort on the part of both the ASIC customer and manufacturer, but as Chian points out, "Typical RF ASICs are small, so transistor-level design is not a far stretch."

Another way to shrink a circuit is to use an application-specific standard-product IC. AT&T Microelectronics produces standard lines of chips, "focusing on the world-wide digital communications standards," says Phil Carrier, Marketing Manager for AT&T's Wireless RFICs. Chips designed for specific applications from the start are important, says Carrier, because, "In subscriber, hand-portable terminals every mA counts." Other manufacturers acknowledge that ASICs are not the best choice in every instance. "In general, if there's a good chip-set that does the job ASICs don't compete," says Bill Dennehy, Director of Marketing for ASICs at Harris Semiconductor.

Some companies are both producers and users of ASICs. While Stanford Telecom does offer standard products, their ability to produce their own ASICs helps them to sell items at the system level, says Charles Frank, Managing Director of ASICs and custom products. "We are unique in being able to combine digital communications expertise with ASIC implementation expertise."

### Fast Silicon

Integrating complex RF circuits could only be dreamed about until a few years ago says Dr. Charles Leung, President of Bipolarics. New processes have pushed silicon's  $f_t$  above 10 GHz. "Small is the key for fast silicon devices," says Leung

"RFIC processes have features as complex as the most advanced DRAM. In addition, we deal with the subtleties involved with RF transistor design," says Dr. Leung. Several companies have developed high-frequency silicon processes and offer them for ASIC manufacture. Despite all the attention given to high-speed silicon processes, GaAs is still used in high-frequency ASICs.

### Design Tools

Another key to the emergence of RF ASICs is the availability of design tools capable of accurately predicting an ASIC's behavior before it is fabricated. Most of the time, the ASIC customer is given models of the transistors or tiles that make up the ASIC and they produce a schematic based on those models. The ASIC manufacturer then translates those schematics to silicon (or GaAs) using their own tools and proprietary knowledge of their process. IC design and RF design tools are only beginning to work together in a seamless way. An analog extension to the VHDL design language, called VHDL-A is in the works, but it mostly addresses low-speed analog and mixed-signal designs. Another developing high-level language for IC design is tailored for RF IC design and is called MMIC Hardware Development Language, (MHDL).

Harris Semiconductor has already managed to incorporate RF tools into an IC design system. Called Fastrack, Harris' new system uses Cadence Design Systems' IC design framework and incorporates a number of RF tools such as S-parameter analysis, noise analysis and large-signal distortion analysis. The combination of RF and IC design makes for some new measurements says Chian, "for instance, measurements of the statistical distribution of third order intercept point." Harris takes a "hard line" on making sure ASIC designs are manufacturable says Harris' Dennehy.

The tools, processes and demand for monolithic RF systems are just now converging. The extent to which future RF designs will be done on a single piece of semiconductor remains to be seen. **RF**






# TESLA



## PC Block Diagram Simulator

## Powerful Communications Simulation

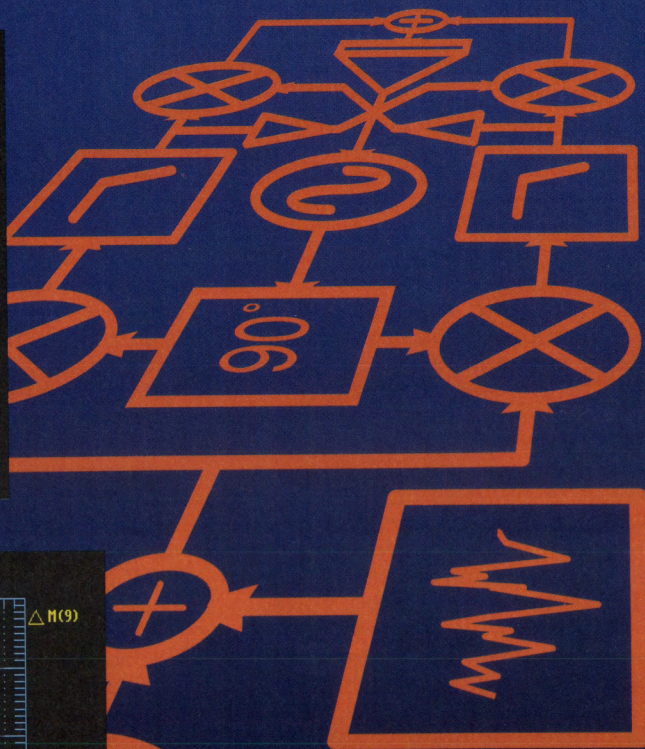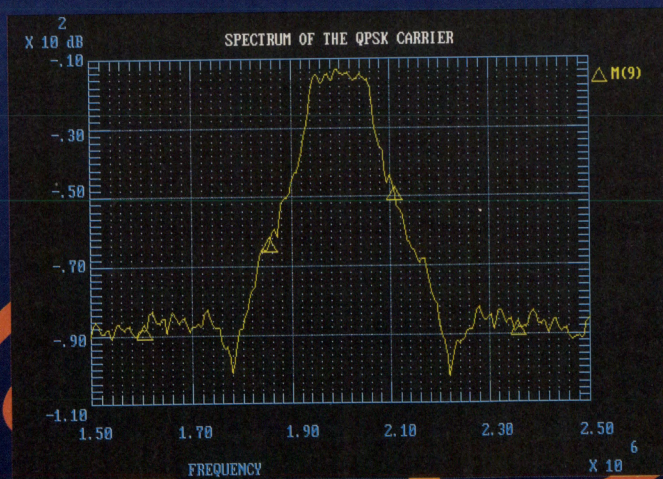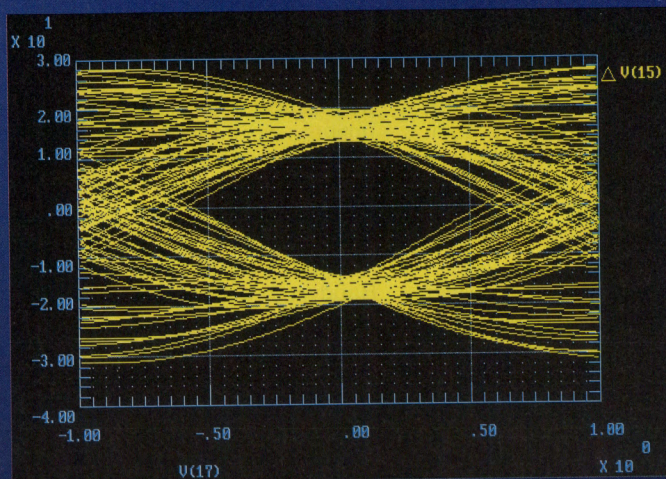

"We were doing threshold noise tests on an instantaneous frequency measuring device...TESLA was on-target—the closest of all our techniques of analysis. It impressed a lot of folks." — B.G. Goleta, CA

TESLA is the easiest way to get fast answers to design problems. It does full nonlinear, mixed analog & digital simulation. Built-in spectrum analysis shows you the results. TESLA has the power to handle multiple modulated carriers, complex demods, and any kind of modulation. You can test spread spectrum with multipath, noise-loaded Costas loop

acquisition, IM from multiple mixers and amplifiers, PLLs with complicated loop filters and digital phase detectors—virtually anything you can do in the lab! But the most important thing is that it's easy to use. You build your system in OrCAD from our intuitive library of blocks like filters, mixers, and vco's. TESLA gives you great graphics output

from the frequency or time domains. We guarantee results. You get the best tech support in the business and a 30-day trial. At \$695 it's a steal! Ask about TESLA's powerful options.

**Call today for a demo package:**

### 800-631-1113

U.S. and Canada

Intl: 404-751-9785 Fax 404-664-5817  
TESOFT Inc. PO Box 305, Roswell GA 30077



## Medium Power Bipolar Design Using the NE46134 Nonlinear Model

By Lynne Olsen and Brian Kirk  
California Eastern Labs

This article presents a method for determining the source and load impedances of a medium power amplifier using a nonlinear simulator and optimizer. The amplifier is designed to produce 27.5 dBm output power at the 1 dB gain compression point (P1dB) while conjugately matching the input for maximum power gain. This method is compared to two other methods: using measured load pull data, and calculating the optimum load impedance from small signal S-parameters [4]. The nonlinear model was developed by California Eastern Laboratories for the NEC NE46134 medium power bipolar junction transistor (BJT) using the nonlinear simulators LIBRA and XTRACT, both developed by EESof™.

The benefits of using a nonlinear simulator [8] to evaluate output power, intermodulation distortion, harmonic distortion, time-domain wave forms, and other nonlinear responses have always been apparent. However, only in the last decade have nonlinear simulators become computationally efficient and cost effective enough to be used for power design. This advance is due pri-

marily to: 1) the implementation of harmonic balance algorithms, 2) the drastic price reduction in computer hardware with an accompanying increase in computing power, and 3) the availability of nonlinear models that are robust enough to accurately predict the nonlinear responses required. However, power modeling is still in its infancy.

Narrowband, medium power amplifier design consists of determining the optimum load impedance,  $\Gamma_L(\text{opt})$ , that will provide the maximum output power. Next, the device is terminated with this load impedance and the source is conjugately matched to provide maximum gain. In this article, the impedances are represented as reflection coefficients.  $\Gamma_L(\text{opt})$  can be determined using one of several methods. The easiest is for the circuit designer to use measured load-pull data, (if it is available from the device manufacturer). If load-pull data is not available, a second method developed and documented in 1983 by S.C. Cripps [2,4,5] can be used. Cripps' method not only determines  $\Gamma_L(\text{opt})$ , but also can be used to generate approximate power contours. This method uses small-signal S parameters, which are fairly easy to measure, to approximate the large-signal output impedance of the device. The third method detailed in this article uses a non-

linear model and a nonlinear simulator and optimizer. The optimizer is used to perturb the source and load impedances until the desired power and gain specifications are achieved.

The amplifier design specifications are:  
P1dB = 27.5 dBm  
G1dB = 7 dB  
Frequency = 900 MHz  
Bandwidth = 40 MHz

The NEC NE46134 was chosen because of its useful bias range, excellent dynamic range and high output power. This device is available in a low cost surface mount package (the NEC 34), as well as in chip form. The NEC 34 package is similar to the industry standard SOT-89 package style.

For this design, the critical specification is to achieve 27.5 dBm output power at 1 dB gain compression [6]. The NEC NE46134 is biased at 12.5 V, 100 mA to provide best linearity at 27.5 dBm output power.

### Measured Load-Pull Data

Load pull-data, also referred to as large signal impedance data, can sometimes be obtained from the manufacturer. The load-pull data provides load impedances that correspond to different output power levels. For any output

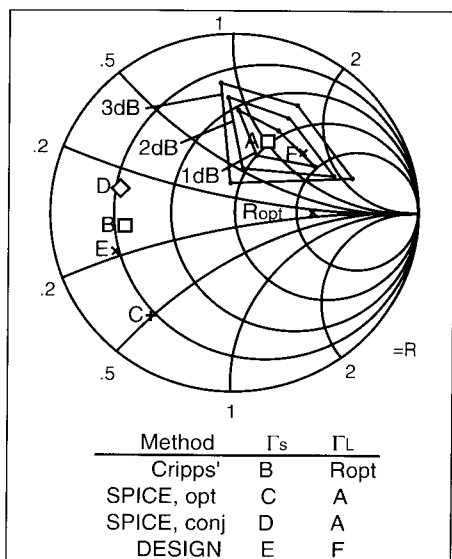


Figure 1. Power contours and impedances on the Smith Chart.

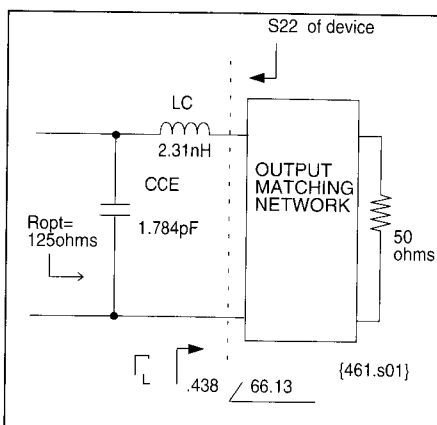


Figure 2. Load impedance derived using Cripps approximation at 12.5 V, 100 mA, 900 MHz.

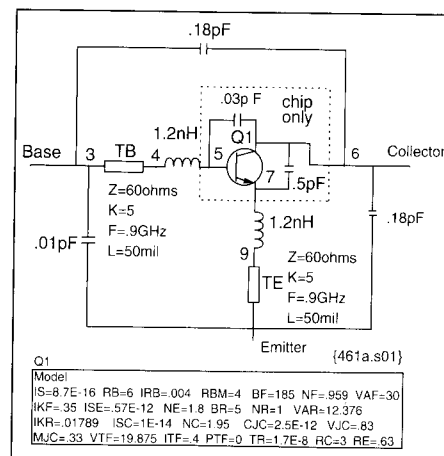


Figure 3. Schematic of the NE46134 nonlinear model.



## RF Design Awards Contest

### GRAND PRIZE! Touchstone/Libra for Windows

This PC-based major linear and nonlinear analysis software is provided by the CAE group at Hewlett-Packard Company.

### Official Rules

1. Entries shall represent RF functions operating at frequencies from tens of kHz to 3 GHz.
2. Entries may be circuits, circuit design methods, test procedures, or design software programs.
3. If the entry is a circuit, it shall have a complexity equivalent to that of a circuit using 8-10 discrete active devices or 6-8 integrated circuits. The circuit may be a portion of a larger system.
4. If the entry is a design method, it must include an example of a circuit designed using the method described.
5. If the entry is a test method, it must include actual results of the measurement described.
6. If the entry is a computer program, it must operate on either an MS-DOS or Apple Macintosh system. It must be provided in a form that can be operated directly, without additional software (e.g., compiled). Programs must be submitted on disk, with supporting documentation provided in printed form.
7. Entries shall be the original work of the entrant, not previously published or publicly distributed. If developed as part of the entrant's employment, entries must have the approval of the entrant's employer.
8. Only one entry per person is permitted. An entry may have two or more co-authors.
9. Submission of an entry implies permission for publication in *RF Design*, and distribution of software submissions by the RF Design Software Service.
10. Winners are responsible for any taxes, duties, or other assessments which result from the receipt of their prizes.
11. Entries must be postmarked no later than July 29, 1994 and received no later than August 8, 1994.
12. All entries will remain confidential until publication of contest results in the November 1994 issue of *RF Design*.

### Judging Criteria

The single objective of the judging is to determine which entry makes the most significant contribution to the advancement of the art and science of RF engineering. Specific judging criteria include:

- *Engineering* — identifying a problem and developing a solution
- *Documentation* — completeness of the entry submission
- *Usefulness* — practicality or wide applicability
- *Technical Merit* — difficulty or magnitude of the work
- Other criteria as deemed appropriate

Send entries to: RF Design Awards Contest  
RF Design magazine  
6300 S. Syracuse Way, Suite 650  
Englewood, Colorado 80111

*We've synthesized*

THE MOST IMPRESSIVE  
PERFORMANCE  
CHARACTERISTICS ON THE  
MARKET WITH AFFORDABLE  
COST


*in our*

ULTRA WIDEBAND  
FREQUENCY SYNTHESIZER  
FROM .5 TO 18 GHz IN ONE  
COMPACT UNIT

The specs speak for themselves:

Output power	+13dBm +/-3dB
Frequency resolution	100kHz in standard
Phase noise	-85dBc/Hz at 10kHz from carrier -115dBc/Hz at 100kHz from carrier
Spurious signals	60dB below output
Compact size	180x150x90mm. (7.1"x6.2"x3.5")
Now look at the options:	
Frequency range	2-9 GHz (standard) 0.5-18 GHz
Frequency resolution	10kHz & 50kHz
Amplitude modulation	

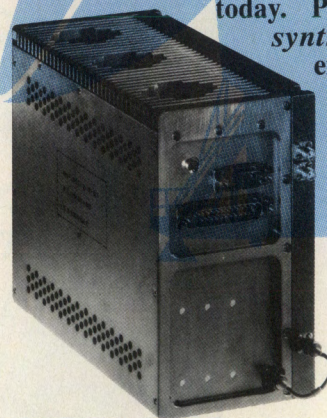Ask **elisra** for more information  
today. Put our  
synthesizer  
expertise  
to work  
for you.



**elisra** electronic  
systems ltd.

Chile, Gallyas S.A.(02)2259001; Denmark, Ole B. Skipper (042)995959; England, Marlow Electronics Ltd. (0628)890552; France, Informate 1-43072888; Germany, Telemeter GmbH (0906)706930; India, KLB Instruments Ltd. (011)735899; Italy, DSPM (02)48009748; Hong Kong, Brayway Ltd. (852)3854244; Korea, Dong Hyun Int'l (02)8863983; Singapore, Precision Technologies Ltd. 2734573; Spain, Anatron S.A. (91)5424455; Switzerland, Telemeter AG (054) 219525; Taiwan, Channel Link Inc. (02)2184986; USA, (212)9477077, (603)8891119, (703)7681660; Israel, Elisra Microwave Division (03)7545655




# If you're going to win the wire. be sure you've got an expert c

## HP RF components. We've got what it takes to win.

The wireless race is on. Lead times are getting shorter. Product specifications are more demanding. Market windows are moving so fast, only those with an edge can meet them.

As a leading supplier of RF components for wireless transmitter and receiver applications, the HP team has what you need to win. Whether your applications include cellular phones, cordless phones, LANs, TV delivery, Satcom, GPS, or mobile data receivers.

In fact, since HP offers the industry's

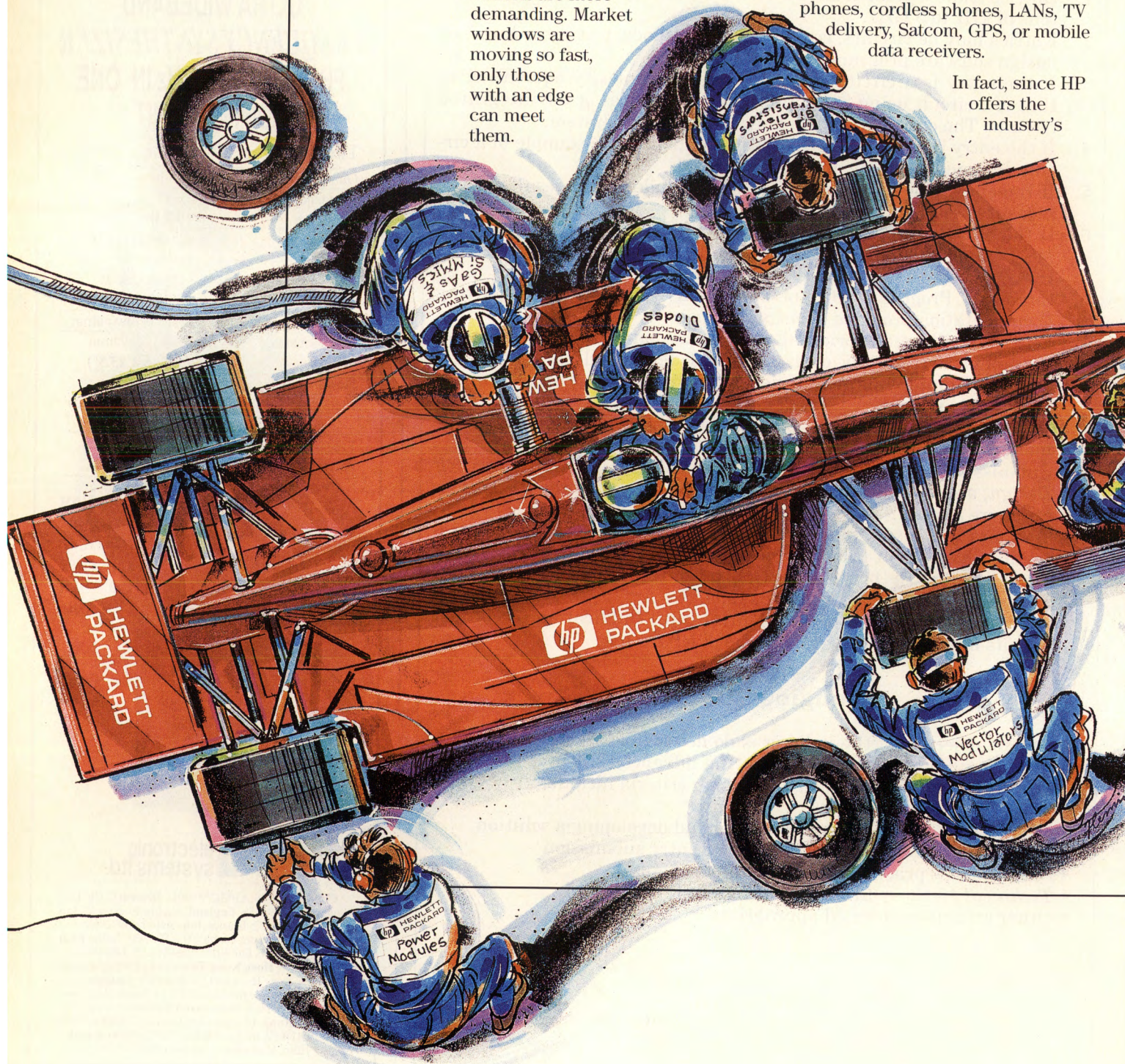




# ess race, ew.

broadest range of RF component solutions—from discrete diodes, transistors and MMICs to RFICs—designers have the distinct advantage of working with a single, reliable, world leader.
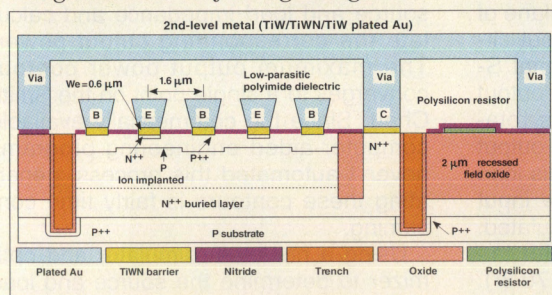
## Race-tuned technologies deliver the winner's edge.

In racing, performance is everything. Which is why designers greet



Si Bipolar ISOSAT II process.

HP's finely-tuned engines with enthusiasm. RF devices deliver 15 GHz  $f_T$  and 35 GHz  $f_{MAX}$ , enabling unequalled receiver/transmitter performance at frequencies up to 5 GHz and beyond. HP's Si Bipolar highly integrated, low-power consumption MMICs

HP puts you in the pole position with its high-volume, low-cost products:

- AT-41511—Si Transistor
- ATF-10236—GaAs FET
- HSMS-2802—Schottky
- HSMS-2822—Schottky
- HSMP-3890—PIN
- IAM-81008—Active Mixer
- INA-03184—Gain Block
- INA-10386—Gain Block
- MSA-0611—Gain Block
- MSA-0886—Gain Block


provide longer battery life and increased talk time. Further, HP GaAs technology provides low-noise PHEMT FETs as well as GaAs MMICs—switches and gain blocks.

## Hot off the line: HP's newest team of RF leaders.

The benefits of our new ISOSAT II manufacturing process are well summed up by

our newest crew members. HP's HPMX-2003 and 2005 vector modulators provide

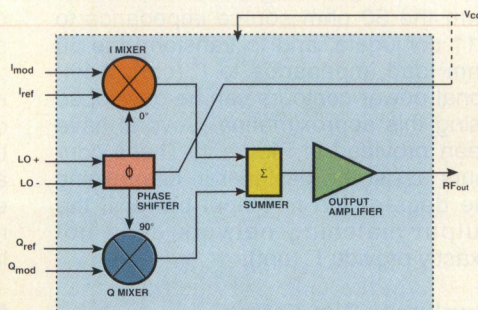precision building blocks for the next generation of digital radios. The new AT-3 series transistors offer 13 dB gain and 1.0 dB NF at 1 GHz while biased at 2.7V and 1 mA. And all are available in small surface mount packages.



HP's Silicon RFIC Vector Modulator.

Also new, our MGA-86576 PHEMT amplifier MMIC delivering 22 dB gain and 2.0 dB NF from 1.5 to 8 GHz. And, HP will soon release power modules for NADC and GSM applications.

## HP integration: your fast track to the future.

HP will push the limits with its next releases, including an RF LSI

circuit with over 1500 NPNs, 50 PNP's, 50 Cs and Ls, and 1800 resistors for cellular

telephone applications.

HP's 2-chip (RF & IF)

DECT chipset puts

you on a clear path to higher levels of RF component integration. The benefits are clear: design becomes easier, saving you time and costs.

## The industry's most responsive support crew.

HP's components sales force and worldwide distributor network provide all the tools you need to stay ahead of the pack. Our strategic market focus, broad product line, competitive pricing, and wide range of advanced technologies make HP the ideal RF design partner. For more information, call 1 (800) 537-7715, x7906. But do it now, because the race is on!

HP RF components.


Winning the wireless race.

**hp HEWLETT®  
PACKARD**

INFO/CARD 21

In Canada, call 1 (800) 387-3867, x7906.  
In Europe, fax to 31 2503 52977.



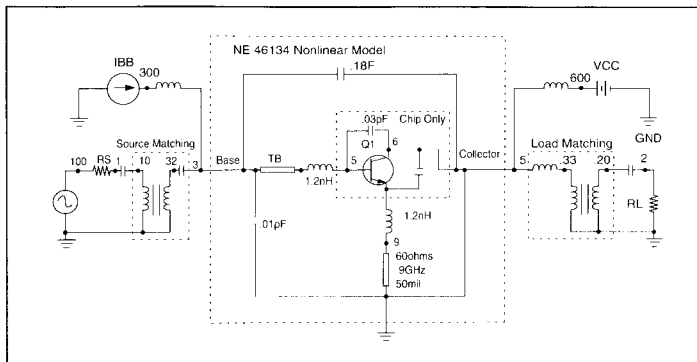

**Figure 4. SPICE optimization to determine source and load terminations.**

power less than maximum, there is a locus of impedance values that form a closed contour on the output impedance plane. For maximum output power, the contour converges to a single point.

Once the load pull contours are obtained, the designer notes the source and load reflection coefficients corresponding to the desired output power level and gain specifications. Then the input and output matching networks are developed and the circuit is built and tested. No load-pull data was available from NEC at the time of this writing.

### Cripps Approximation

A widely used approximation method documented by Steven Cripps uses small-signal S-parameters to determine  $\Gamma_L(\text{opt})$ . Although Cripps' technique was developed to obtain power contours for GaAs FETs, we have found the technique works well with bipolar junction transistors also. The key to successfully implementing the approximation is to develop an accurate model for the output of the device over the frequency range and bias of interest, as demonstrated in California Eastern Laboratories' application note AN-PF-1007 [10].


This method entails calculating the optimum load impedance for the maxi-

mum output power. At 12.5 V, 100 mA, the optimum load resistance,  $R_{\text{opt}} = 12.5 \text{ V}/100 \text{ mA} = 125 \text{ ohms}$  as shown in Figure 1. This impedance point is then rotated to the output impedance plane of the package. The equivalent output circuit is generated from small-signal S-parameters. Figure 2 shows the output impedance that results from this rotation,  $\Gamma_L(\text{opt}) = 0.438/66.13^\circ$ . The output of the device is terminated with this load reflection coefficient and the new input reflection coefficient,  $S_{11}'$ , is calculated. The input is then terminated with the conjugate of  $S_{11}'$  ( $S_{11}' = 0.63/-170.3^\circ$ ). Power, gain, and intermodulation distortion using these terminations are simulated as shown in Table 3. P1dB is 27.1 dBm with an associated gain of 9.5 dB.

The design task then becomes an impedance matching exercise to transform the 50 ohm source impedance to  $S_{11}$  conjugate, and to transform the 50 ohm load impedance to  $\Gamma_L(\text{opt})$ . Additional power contours can be developed using this approximation. Several have been provided in Figure 1. These contours assist the designer in determining the degradation in output power if the output matching network does not exactly provide  $\Gamma_L(\text{opt})$ .

### Nonlinear Simulation

Before delving into nonlinear simulation, a brief review of small-signal amplifier design is provided to note the similarities between small-signal linear amplifier design and large-signal nonlinear power design. For small signal design, the S-parameters are used in the well known power gain equations [2]. These power gain equations characterize the bilateral, linear relationships of the device and are implemented in many linear simulators. The simulators automate the task of calculating and plotting constant gain circles. Constant gain circles are very similar to load-pull contours. Both consist of impedance values plotted on the Smith Chart. The difference is that gain circles are circles of constant gain and the power contours

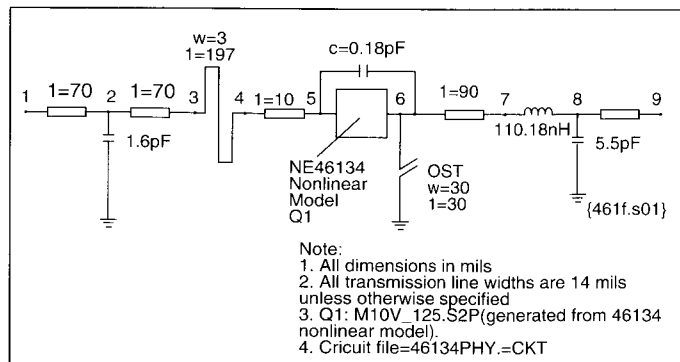

**Figure 7. Final schematic including matching networks and layout parasitics.**

are contours of constant power. Theoretically, a nonlinear simulator could be used to generate power contours, since the nonlinear simulator can vary the source and load impedance and calculate the corresponding output power. The maximum output power contour converges to a single point on the Smith Chart. Since the commercially available computer-aided engineering programs haven't automated this process, generating these contours is fairly time consuming.


Using a nonlinear simulator and optimizer to determine the source and load impedances for this design problem at a single frequency and bias range is straightforward. All we have to do is input the nonlinear model parameters and design goals, and have the optimizer vary the source and load impedances until our design goals are achieved. The next step is to design the input and output matching networks using actual fabrication technology, re-simulate the circuit with expected layout parasitics and then, build the circuit. If your measured and simulated results differ, then re-evaluate the device and component models and add any overlooked layout/fabrication parasitics.

### Nonlinear Model

The nonlinear model for the NE46134 [1] is shown in Figure 3 and is used to predict the behavior of the device under various power conditions. The nonlinear model consists of the nonlinear chip model using Gummel-Poon [3] parameters embedded in the NEC 34 package model.

### Simulation and Optimization

The circuit description consists of the nonlinear model, the DC biasing circuitry, the AC input, and the optimizable terminations indicated as "source matching" and "load matching" in Figure 4. The DC biasing circuitry provides  $V_{ce} = 12.5 \text{ V}$  and  $I_c = 100 \text{ mA}$ . The AC input provides a 900 MHz signal with a power sweep from 0 to 30 dBm in 5 dBm steps.

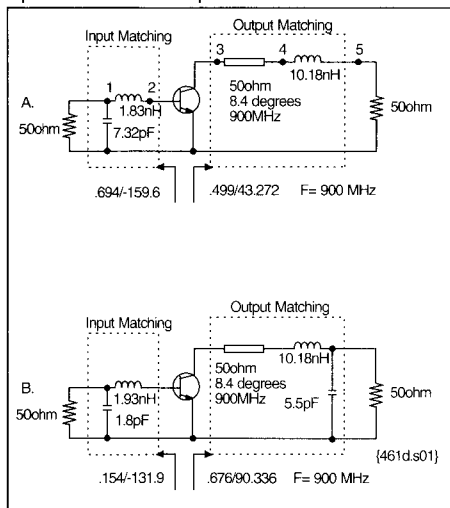

**Figure 5. Matching networks.**



# Is this what BIPOLAR TECHNOLOGY has finally come DOWN TO?

## 12 GHz $f_T$ Bipolars: one third the size of a SOT-23!


Need performance, but short on real estate?

Our new bipolars from NEC deliver up to 9 dB Gain and 1.5 dB Noise Figure at 1.9 GHz — in an ultra-super mini mold "19" package that's just 1.6 X 0.8 mm!

These bipolars operate below 3V and at low current to reduce battery size and increase battery life for your wireless applications.

Want the performance, but not quite ready for the miniature package? They're also available in traditional SOT-23, 323, and 143 style packages — and a new high performance 4 pin "18" package that delivers MAG of 13.0 dB at 1 V, 1 mA, 900 MHz.

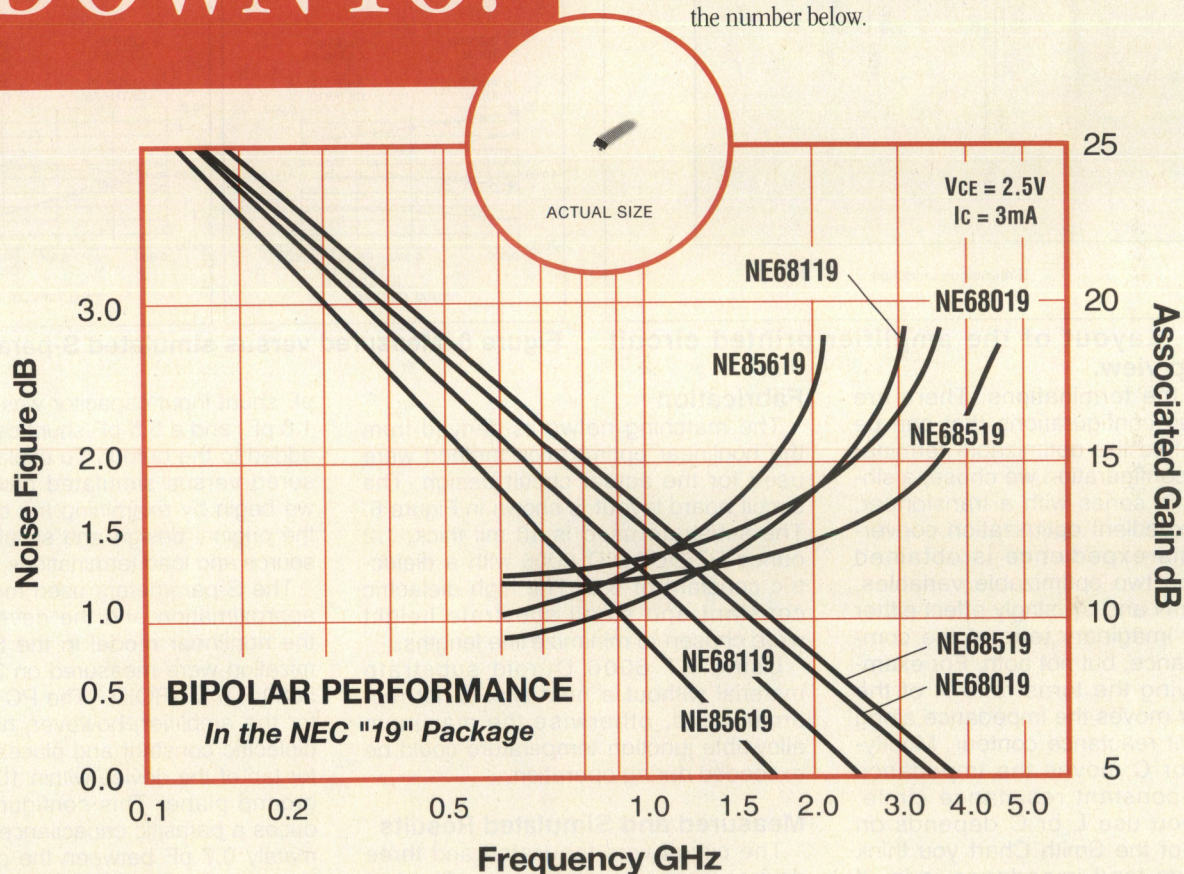They're available now, on tape and reel, and priced to meet your needs. For Data Sheets and a copy of *Automated Assembly of Miniature Parts*, call your nearest CEL Sales Office or circle the number below.



**NEC**

NEC Bipolars are available  
in these packages  
(shown approx. 2X size)



NEC "19" Pkg  
Ultra Super  
Mini Mold



NEC "18" Pkg  
4 Pin Super  
Mini Mold



NEC "30" Pkg  
SOT-323 Style



NEC "33" Pkg  
SOT-23 Style




NEC "39" Pkg  
SOT-143 Style

**California Eastern Laboratories**

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 □ Santa Clara, (408) 988-7846 □ Los Angeles, CA (310) 645-0985  
San Diego, CA (619) 450-4395 □ Bellevue, WA (206) 455-1101 □ Richardson, TX (214) 437-5487 □ Olathe, KS (913) 780-1380 □ Woodridge, IL (708) 241-3040 □ Cockeysville, MD (410) 667-1310  
Peabody, MA (508) 535-2885 □ Hackensack, NJ (201) 487-1155 □ Palm Bay, FL (407) 727-8045 □ Snellville, GA (404) 978-4443 □ Nepean, Ontario, Canada (613) 726-0626



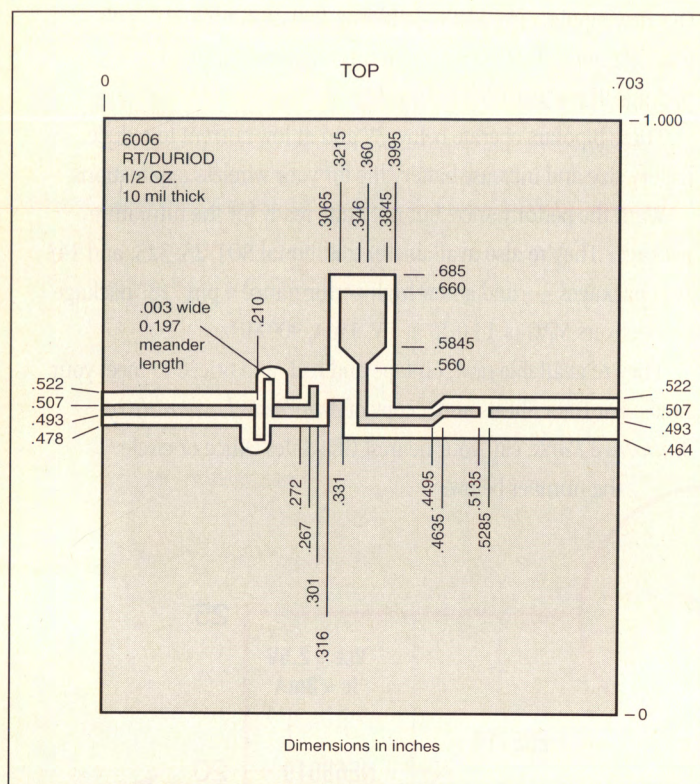

**Figure 6. Layout of the amplifier printed circuit board, top view.**

Now for the terminations. There are many circuit configurations that can be used to define the optimizable terminations. The configuration we chose, a single L or C in series with a transformer, provides expedient optimization convergence. This expedience is obtained because the two optimizable variables, N and L (or N and C), singly effect either the real or imaginary term of the complex impedance, but not both. For example, modifying the turns ratio N of the transformer moves the impedance along the constant reactance contour. Modifying the L or C moves the impedance along the constant resistance circle. Whether you use L or C depends on which half of the Smith Chart you think the optimum load impedance is in. If you're not sure whether to use an L or C, both can be used (a series L, C or shunt L, C) at the expense of increased optimization time.

After you define the topology for the terminations, optimize the source and load impedances simultaneously until the design specifications are achieved. The resulting source and load reflection coefficients are used to develop the input and output matching networks. The initial matching networks and final matching networks after bench tuning are shown in Figure 5.


### Fabrication

The matching networks derived from the nonlinear optimization method were used for the actual circuit design. The circuit board layout is shown in Figure 6. The substrate used is 10 mil thick, 1/2 ounce RT/DUROID 6006 with a dielectric constant of 6.0. The high dielectric constant and small substrate height were chosen to minimize line lengths.

Using RT 6006 Duroid substrate material without a heat sink is not recommended, otherwise the maximum allowable junction temperature could be exceeded during operation.

### Measured and Simulated Results

The circuit was fabricated and three devices were secured in the amplifier test circuit and measured. The initial test results were compared to the design specifications. At 900 MHz, the small-signal gain was higher than the expected 8 dB (8.54, 8.81 and 9.26), the output power was lower than the expected 27.5dBm (25.9, 25.82, 26.35), and the input return loss wasn't very good considering the input was designed to be conjugately matched. Tuning on the bench [7] to achieve 27.5 dBm output power resulted in modifications to the input and output matching circuits as indicated in the schematic of Figure 5. The original 7.32

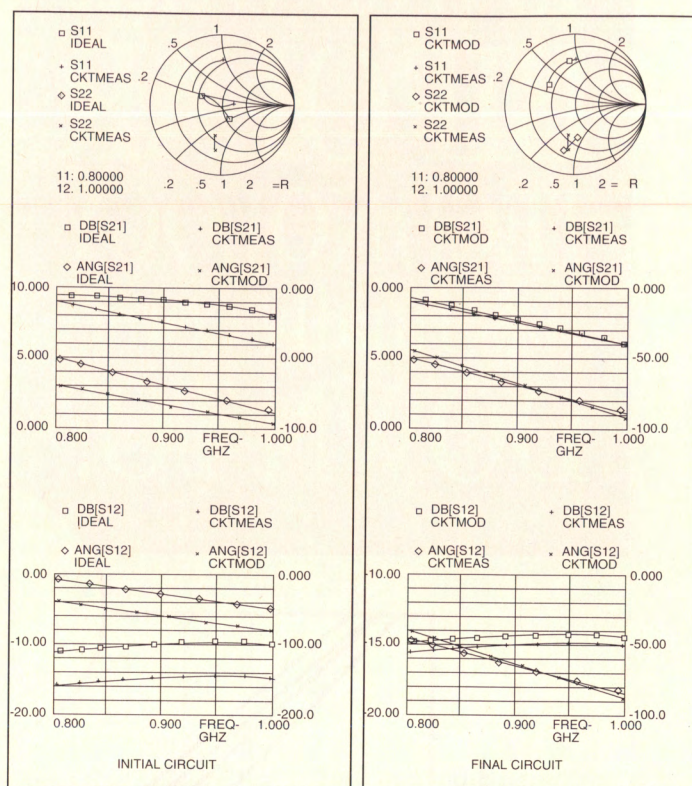

**Figure 8. Measured versus simulated S-parameters.**

pF shunt input capacitor was changed to 1.8 pF, and a 5.5 pF shunt capacitor was added to the output. To explain the measured versus simulated discrepancies, we begin by examining the data used in the original design and simulation of the source and load terminations.

The S-parameters used for the Cripps approximation and the development of the nonlinear model in the SPICE optimization were measured on 30 mil thick, 5880 RT/ DUROID. The PC board used for the amplifier, however, has a higher dielectric constant and places the collector tab of the device within 10 mils of the ground plane. This configuration introduces a parasitic capacitance of approximately 0.7 pF between the collector tab and ground. This parasitic capacitance and other layout parasitics were added to the simulation file. Figure 7 is a schematic representation of the complete amplifier, including pertinent layout parasitics. Figure 8 shows the measured versus simulated S-parameters for the initial circuit design shown in Figure 5, and the measured versus simulated S-parameters after adding layout parasitics as shown in the schematic of Figure 7.

For additional comparison, the nonlinear model and optimizer were used to obtain the load impedances for maximum output power, instead of using an



S-parameter file as in Cripps approximation. The input was then terminated with the resulting conjugate of the large signal S11.

All of the preceding discussed source ( $\Gamma_s$ ) and load ( $\Gamma_L$ ) reflection coefficients are included in Table 1. The different techniques referred to in Tables 1 through 7 are:

1. *Cripps* - use small signal S-parameters to determine the load impedance and match the input to the small signal S11 conjugate.

2. *SPICE,opt* - SPICE optimization of the source and load simultaneously.

3. *SPICE,conj* - nonlinear optimization of the load for maximum power and match the input to the large signal S11 conjugate.

4. *DESIGN* - matching networks used for the initial amplifier layout are the terminations.

5. *DESIGN,final* - Simulation including matching networks and layout parasitics, final simulation.

Also included in the tables are the 2nd and 3rd order intermodulation distortion products.

The formulas used for comparing magnitude and phase differences are:

$$\text{Mag. difference} = \frac{= (\text{Cripps} - \text{SPICE}) / \text{SPICE}}{\quad} \quad (1)$$

$$\text{Phase Diff.} = \frac{= \frac{(180 - |\text{Cripps}|) + (180 - |\text{SPICE}|)}{\text{SPICE}}}{\quad} \quad (2)$$

Using the preceding formulas, we find the load impedances for Cripps and SPICE,opt differ by only 3% in magnitude and 7% in phase. The source impedances for Cripps and SPICE,conj are fairly close as expected, differing by 3% in magnitude and 12% in phase. The source impedances obtained by simultaneously optimizing the source and load (SPICE,opt) differ from those obtained using Cripps' method by 19% in magnitude and 51% in phase. The large difference between these two methods is the result of differing constraints. Gain at P1dB is constrained to 7.0 dB in the method that simultaneously optimizes source and load imped-

ances, while Cripps' and the SPICE,conj method terminate the input with S11's conjugate to maximize gain at P1dB.

The source impedances of the DESIGN and SPICE,conj designs differ by 6% in magnitude and 18% in phase. The differences in load magnitude and phase are 9% and 30%, respectively. Power simulations are included in Tables 2 through 6.

A comparison of the measured, simulated, and data sheet P1dB and G1dB are included in Table 7. The simulated 1 dB compression power levels are very close to the measured and data sheet values (27.2 dBm to 27.5 dBm). G1dB, however, varies from 7.0 dB to 9.6 dB. As is to be expected, the three methods which conjugately match the input yield the higher gains of 9.5 dB (Cripps), 8.8 dB (SPICE,conj) and 9.6 dB (DESIGN). The G1dB from the SPICE optimization (7 dB) and the measurement (7.2 dB) are very close to the NEC data sheet specification of 7.0 dB. The entire amplifier G1dB simulation including matching networks and layout parasitics is 7.8 dB, 8% higher than the measured value of

## STEWARD FERRITES...When It Comes To EMI Suppression, We've Got It.

Standard EIA size Surface Mount Chips as well as MLC for high current suppression applications.

Steward  
FERRITES  
EMI Suppressor Kit  
(Part No. 28B0000-KIT)

Steward  
EMI Suppressor  
P.O. Box 510  
Chattanooga, TN 37401  
Phone: 615-867-4100 FAX: 615-867-4102

● Wide selection of standard parts for boards, interfaces and cable applications.

● World class quality.

● Competitive pricing.

● Approved by most major hardware producers.

● Standard materials cover wide frequency range.

● Available evaluation kits.

Steward

**Dial 1-800-634-2673**  
for the location of our nearest distributor.

EAST 36TH STREET  
P.O. BOX 510  
CHATTANOOGA, TN 37401  
U.S.A.  
PHONE: 615-867-4100  
FAX: 615-867-4102



7.2 dB. This difference is because the amplifier parasitics were optimized to produce the lowest comprehensive error (including all S parameters, not just gain) over a 40 MHz band (880 MHz to 920 MHz) instead of at a single frequency of 900 MHz. The parasitics were optimized to achieve 7.2 dB gain at 1 dB power compression at 900 MHz at a slight sacrifice to the overall error. The final amplifier measurement and simulations cover

the 800 MHz to 1000 MHz band.

Using a nonlinear model and simulator/optimizer took about four hours total to arrive at the source and load impedances. Two of the hours were used to input the circuit and optimization criteria; another two hours were used for the optimizer to converge using a 386/33 MHz computer with a co-processor. This technique is valid only if the nonlinear model is accurate for the operating con-

Technique	$\Gamma_s$ (mag, ang)	$\Gamma_l$ (mag, ang)
CRIPPs	0.63, -170.3	0.438, 66.13
SPICE, opt	0.75, -125.8	0.453, 61.4
SPICE, conj	0.646, 168.8	0.453, 61.4
DESIGN	0.69, -159.6	0.499, 43.27
DESIGN, final	0.165, -176.7	0.59, 83

Table 1.

Pin (dBm)	Pout (dBm)	Gain (dB)	2nd IMD	3rd IMD
-5	3	8	-46.4	-94
0	8	8	-36.5	-79
5	13	8	-26.6	-64
10	18	8	-16.5	-48.5
20	27.1	7.1	0.4	-6.9
20.3	27.3	7	2.3	-6.5
25	27.6	2.6	8.2	-3

Table 2.

Pin (dBm)	Pout (dBm)	Gain (dB)	2nd IMD	3rd IMD
-5	5.53	10.53	-42.2	-86.4
0	10.53	10.53	-32.3	-71.6
5	15.52	10.52	-22.2	-56.1
10	20.5	10.5	-12.3	-40.3
15	25.4	10.4	-3.5	-19.3
17.6	27.1	9.54	3.6	-6.4
20	27.5	7.5	10.2	4.6
24	27.9	3.9	8.4	5.6
25	28.1	3.1	8.7	4.9

Table 3.

Pin (dBm)	Pout (dBm)	Gain (dB)	2nd IMD	3rd IMD
-5	4.8	9.8	-44	-89.5
0	9.8	9.8	-34.1	-74.9
5	14.8	9.8	-24	-59.5
10	19.8	9.8	-14.1	-44.3
18.5	27.3	8.8	2.6	0.3
20	27.5	7.5	5.4	-1.3

Table 4.

ditions being simulated.


Cripps' technique took about four hours to determine the output equivalent circuit from manufacturer supplied S-parameter data, set up the linear circuit file and rotate  $R_{opt}$  to the final load impedance value.

## Production Results

A production amplifier using the NEC NE46134 was built and tested by M/A-COM. The amplifier exhibited excellent thermal performance and high linearity using a 25 mil aluminum nitride substrate mounted on a carrier. The dielectric constant was 8.8. M/A-COM was able to fit 70 circuits on a 2.0 inch by 2.0 inch substrate. Mask costs were less than \$150.00 and the substrate costs less than \$ 1.00 for each amplifier in small quantities. Since linearity was the key design specification, the device was biased at 12.5 V, 100 mA with the input power reduced to achieve an output power somewhat less than 0.5 watts.

## Conclusions

1) Both techniques, Cripps approxima-

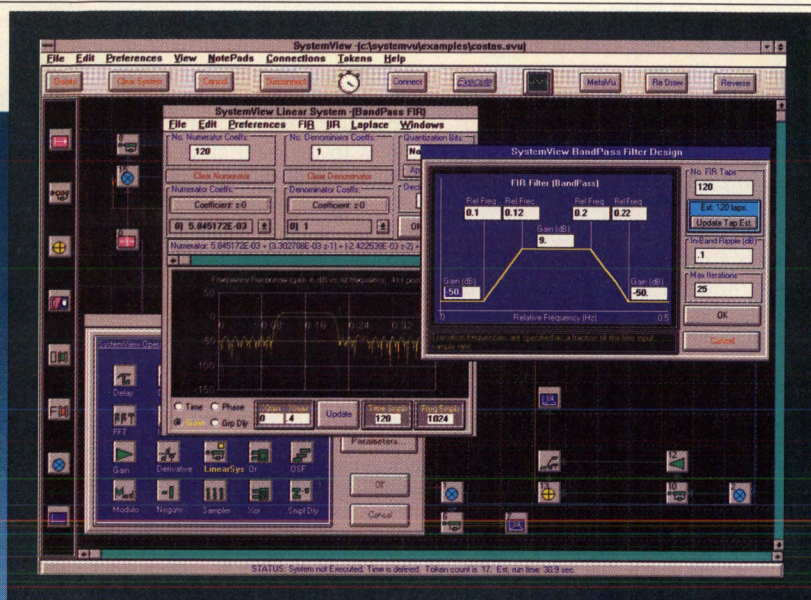

Workstation power on your PC. Performs in the familiar Microsoft Windows environment.

# SystemView

BY ELANIX

**PERSONAL DYNAMIC SYSTEM SIMULATOR:**  
Powerful. Portable. And instantly productive.

Introducing workstation-level design, simulation and analysis tools for your PC. Intuitive, powerful and dynamic, SystemView thinks like you do. And there's no code to learn! It provides application development tools for DSPs, signal processing, communication and control system applications, plus mathematical system modeling. For more information or to place an order, call ELANIX now.

**\$985**

Quantity discounts available

**1-800-535-2649**

5655 Lindero Canyon Rd., Suite 304 • Westlake Village, CA 91362 • (818) 597-1414 • Fax (818) 597-1427  
© ELANIX, Inc. 1993. SystemView by ELANIX is a registered trademark of ELANIX, Inc.

INFO/CARD 24



# BROADBAND DDS

Pin (dBm)	Pout (dBm)	Gain (dB)	2nd Harm	3rd Harm
-5	5.64	10.64	-41.3	-87.4
0	10.64	10.64	-31.3	-72.7
5	15.63	10.63	-21.2	-57.4
10	20.6	10.6	-11.3	-42.1
15	25.5	10.5	-1.8	-23.1
17.6	27.2	9.6	-12.5	0.9
20	27.5	7.5	-2.9	4.2
25	27.9	2.9	-1.6	-1.5

**Table 5.**

Pin (dBm)	Pout (dBm)	Pout (dBm)	Pout 3rd (dBm)
	(17, #1)	(01QS)	(18, #2)
0	8.15	7.82	8.12
5	12.95	12.63	12.90
10	17.90	17.53	17.87
20	—	27.04	—
20.3	27.50	—	—
20.37	—	—	27.5
20.93	—	27.7	—
26	29.58	29.75	29.75

**Table 6.**

	P1dB (dBm)	G1dB (dB)	Simulation conditions
NEC data sheet	27.5	7.0	1 GHz sim.
SPICE, opt	27.3	7.0	900 MHz opt.
CRIPPs	27.2	9.5	900 MHz meas. S-parameters
SPICE, conj	27.3	8.8	900 MHz optimization
DESIGN	27.2	9.6	
DESIGN, FINAL	27.5	7.7	
Measured L/N 17	27.5	7.2	

**Table 7.**

tion and nonlinear optimization, yield similar results.

2) Using a SPICE optimizer allows the circuit, and changes to the circuit, to be better understood and evaluated. For example, changing the substrate for thermal considerations can effect the small signal gain and power compression characteristics of the device. A properly modeled device and circuit can predict the effects of these changes.

3) With the introduction of more efficient nonlinear simulators in the last decade, power amplifiers, and their layout parasitics, can be simulated prior to fabrication. The accuracy of the simulation depends mainly on the accuracy of the nonlinear device model and the designer's ability to properly model the overall circuit being built, including fabrication parasitics.

4) After fabricating the initial circuit, it became apparent that the computer simulation and measured data were very different. The circuit was tuned on the bench until the measured data agreed with the design specifications and simulated results. The differences between measured and designed quantities are attributed to omission of the layout parasitics in the initial design. If

the layout parasitics had been included when determining the source and load reflection coefficients, the initial measured data would have more closely agreed with the simulation.

5) SPICE simulators permit the designer to predict linear as well as nonlinear behavior such as power compression curves and third order intermodulation prior to circuit layout.

## Acknowledgement

Our many thanks to Steven Cripps for his review and discussion of the methods presented here.

RF


## References

1. Olsen, L. and Kirk, B., "Nonlinear Model Verification for a Medium Power Bipolar Transistor", *RF Design*, March 1992, pp. 41-66.
2. Gonzales, Guillermo, *Microwave Transistor Amplifiers, Analysis and Design*, 1984, Prentice-Hall, ISBN 0-13-581646-7, pg. 92.
3. I.E. Getreu, CAD of Electronic Circuits 1, *Modeling the Bipolar Transistor*, Tektronix, Inc., Beaverton, Oregon, 1976.
4. Cripps, S.C., "A Theory for the Prediction of GaAs FET Load-pull Power Contours," *IEEE/MTT-S DIGEST*, 1983, pp. 221-223.
5. Cripps, Steve C., "GaAs FET Power Amplifier Design," Matcom, Inc., Technical Note 3.2.
6. Sechi, Franco N., "Design Procedure for High-Efficiency Linear Microwave Power Amplifiers," *IEEE MTT-28*, No. 11, Nov. 80, pp. 1157-1163.
7. Hall, L.C. and Trew, R.J., "Maximum Efficiency Tuning of Microwave Amplifiers," *IEEE/MTT-S DIGEST*, 1991 pp. 123-126.
8. Nagel, L.W. and Pederson, D.O., "Simulation Program With Integrated Circuit Emphasis (SPICE), " *16th Midwest Symposium on Circuit Theory*, Waterloo, Ontario, April 12, 1973. Available as Electronics Research Laboratory Report No. ERL-M383, University of California, Berkeley, April 12, 1973. A detailed description of SPICE is also available in Nagel, L.W., "SPICE2: A Computer Program to Simulate Semiconductor Circuits," Electronics Research Laboratory Report No. ERL M520, University of California, Berkeley, May 9, 1975.
9. H.K. Gummel and H.C. Poon, "An Integral Charge Control Model of Bipolar Transistors," *Bell System Technical Journal*, No. 49, 1970.
10. California Eastern Laboratories, "Designing High Power GaAs FET Amplifiers Using Single Cell FET Parameters", Application Note AN-PF-1007, 11/88.

## About the Authors


Brian Kirk is an Applications Engineer with California Eastern Laboratories. Brian has an MSEE and nine years experience with RF and microwave power amplifier design. Brian can be reached at (408) 988-3500, ext. 232. Lynne Olsen is an engineering consultant for California Eastern Laboratories, specializing in RF and microwave circuit design and component modeling. Lynne can be reached at (406) 587-0334.

## ADS-431 Low Cost!!!

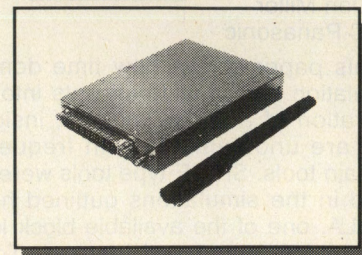

BW ..... up to 400 MHz  
Step size ..... < 1 Hz  
Spurs ..... <-45 dBc typical  
Output ..... quadrature, -4 dBm  
Control ..... Parallel  
Power ..... <6 W  
Switching ..... <50 nsec  
                                φ continuous

## ADS-432 Integrated!!!

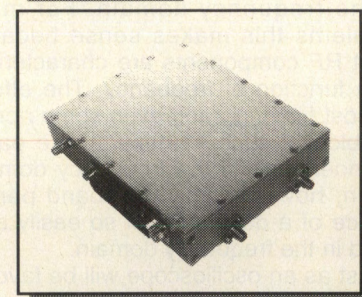

ADS-432 is similar, with power conditioning, reference generator, output amplifier, etc.

- Self-contained
- 1ppm internal clock, or external
- +6 dBm output power

SCITEQ'S standard products include advanced-technology DDS, PLL, direct-analog, and combination synthesizers. Formats include chips, boards, modules, and chassis. Custom designs combine proven modules to minimize risk, cost and time.

SCITEQ Electronics, Inc.  
4775 Viewridge Ave.  
San Diego, CA. 92123  
(619) 292-0500  
Fax (619) 292-9120





## Simulating a QPSK Modem

By Don Miller  
MCC Panasonic

This paper shows how time domain simulation can provide insights into the operation of a QPSK modem, insights that are unobtainable with frequency domain tools. SPICE-type tools were not used in the simulations outlined here. TESLA, one of the available block level simulators, was used instead. Tools such as these animate the behavior of all the system blocks in parallel. The blocks interact just as they would in the lab. This is much faster than circuit simulation, which solves large matrices of circuit equations. Unlike steady-state nonlinear simulators, a tool like TESLA easily handles complex digital logic and long sequences of data.

**R**F Engineers are comfortable analyzing the performance of their designs in the frequency domain. For many problems this makes sense because most RF components are characterized as a function of frequency. The effects of most filtering, (and even some nonlinear blocks, such as mixers), are easier to understand in the frequency domain. Often, however, the baseband performance of a design is not so easily analyzed in the frequency domain.

Just as an oscilloscope will be favored over a spectrum analyzer for observing some aspects of system behavior in the lab, alternative software tools will be better suited for simulating some aspects of a design. If a system is linear and time invariant, then linear simulation will be the tool of choice. Nonlinear sys-

tems that need be analyzed only in the steady-state case are good candidates for harmonic balance analysis. Time domain simulation is a tool that is useful for simulating systems where transient behavior must be studied or where frequency domain analysis provides little intuitive insight. For example, spectral analysis may show distortion, but a time plot shows the actual clip point of a waveform. However, employing a time simulation tool does not prevent us from looking at frequency domain behavior. This is provided for by the Fast Fourier Transform.

### Modulator

The block diagram of a QPSK RF modem is shown in Figures 1 and 2. Figure 1 details the modulator section. Data and clock signals from the random bit generator go to a data stream splitter. It separates each pair of bits into two parallel data streams, each running at half the input data rate. Encoding is applied to the bit streams to determine the mapping of the bit pairs to the output carrier phase state. The resulting bit pairs, which define the current "symbol", are filtered with low pass filters having carefully controlled time responses. The resulting analog waveforms are applied to a quadrature modulator to generate the QPSK signal.

### Demodulator

The demodulator circuit in Figure 2 operates almost like a modulator in

reverse. The quadrature demodulator drives filters which can be identical to the ones in the modulator. The filtered signals are sliced with a comparator, decoded, and serialized into the same data stream as was transmitted. If only it were that easy! In reality the demodulator is much more complicated than the modulator. Carrier recovery is the problem. The local oscillator signal used in the quadrature demodulation process needs to be synchronized with the incoming carrier frequency (which is suppressed). Often, the demodulator is part of a special phase-locked loop, called a Costas loop, that recovers the carrier. The mixers in the demodulator are part of the phase detector, so the input signal level affects the phase detector sensitivity, ( $K_F$ ). This means AGC is required! After the data is decoded, we must provide a bit rate clock to the device that is using the data we are delivering. This is yet another PLL! Luckily, we can "ship" clock and carrier to the demod from the modulator during our simulations until we are ready to add the carrier and clock recovery circuitry. This enables us to keep things simple at first and then add complexity as we are satisfied with the basics. Our ability to pick and choose between the real and ideal worlds enables us to simulate only as much of the system as we care or need to. The simulations here will carefully ignore clock recovery and AGC, while illustrating how filter effects and carrier recovery may be analyzed.

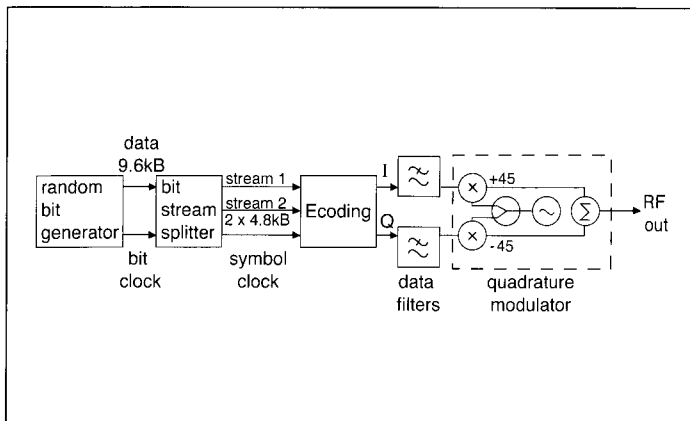


Figure 1. Block diagram of a QPSK modulator.

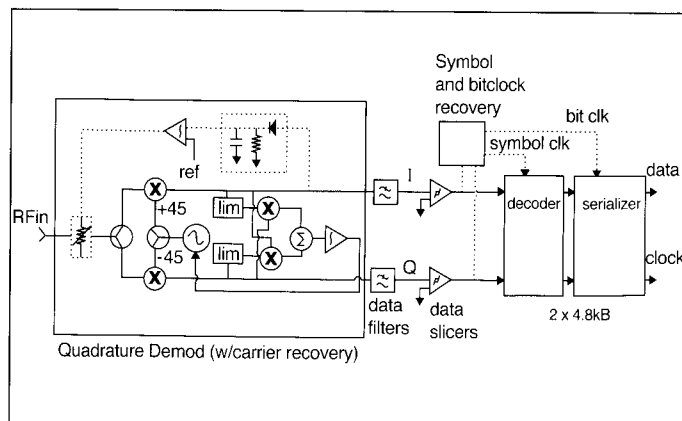
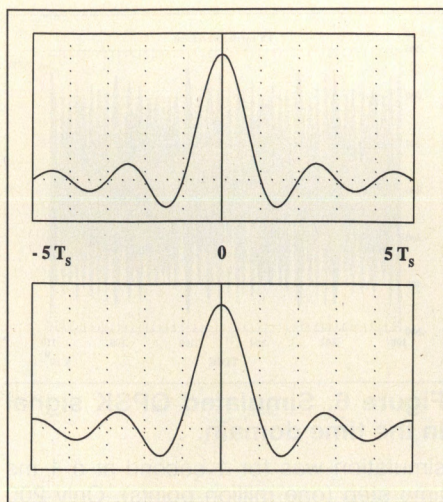


Figure 2. Block diagram of a QPSK demodulator.

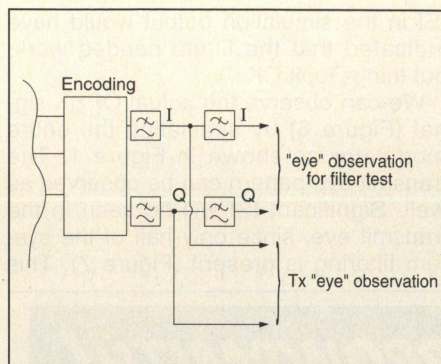




**Figure 3. Impulse responses of filters with and without inter-symbol interference.**


#### Filter Performance

After confirming that the data stream splitter and coder operate properly, the first real analysis task on the modulator side will be to confirm proper operation



**Figure 4. Simulation block diagram**

of the low pass data filters. If the filtering in a data link is optimum, the intersymbol interference (ISI) will be zero. Any ringing from the previous symbols or precursors from future symbols will pass through zero at each sample point. Figure 3 shows the impulse response for the filtering in a system with zero ISI, and one with significant ISI. Note that for the filter with zero-ISI, the zero crossings of the impulse response coincide with the sampling points. If our filters have significant ISI, then the nonzero

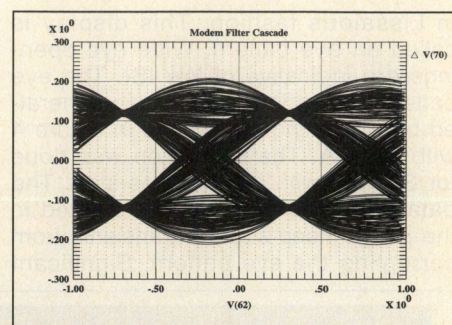

**Figure 5. Eye diagram of system in Figure 4.**

residual time response of the previous symbol will add to the pulse resulting from the next symbol. This interference adds to the uncertainty in interpreting the state of a particular symbol.

We can check the filtering in our simulated modem by doing a simulation with the baseband output of the transmit low-pass filters cascaded into the receive filters. A block diagram of this simulation is shown in Figure 4. The output of the receive I or Q channel filter can be observed using a symbol rate timebase

**MORE  
NEW  
LOWER**  
S/Filsyn™ Filter  
Design Software

**FEATURES  
MANUAL  
PRICE!**  
**50% Off!**

#### NEW FEATURES!

- Design lattice & ladder wave digital filters
- Design rectangular and round rods
- Plot from the optimizing pre-processor
- GUI simplifies operation
- Easier to use manual complete with many designs
- Users Guide for PC users

Call our **NEW** telephone number and ask about the 50% off discount!

**415-325-4373**

**DGS ASSOCIATES, INC. FAX 415-325-7278**

**1,239,580  
Filters**

**America's Filter Specialist  
since 1956**

0.1 Hz to 3000 MHz -

1,239,580 standard filter types ☐ Miniature and subminiature sizes ☐ Passive and active types ☐ Stock filters ☐ Gaussian, Butterworth, Chebyshev designs ☐ Call or write for free catalog today.

**TTE®**

TTE, Inc.  
2251 Barry Avenue  
Los Angeles, CA 90064  
Fax (800) 473-2791  
Tel (800) 776-7614

**1,239,580  
STANDARD  
FILTER  
DESIGNS**

**FREE CATALOG**




in Lissajous fashion. This display is called an eye pattern. Wide eye openings are indicative of low ISI. The eye pattern shown in Figure 5 was generated by simulating the system in Figure 4 with TESLA. The simulation was done for 300 ms with a 1 ms time-step. The data from 0 to 100 ms was omitted in the plot to keep start-up transients from corrupting the eye pattern. Significant

ISI in the simulation output would have indicated that the filters needed work, but things look OK.

We can observe the actual QPSK signal (Figure 6) by simulating the entire modulator as shown in Figure 1. The transmit eye pattern can be observed as well. Significant ISI will be seen in the transmit eye, since only half of the system filtering is present (Figure 7). This

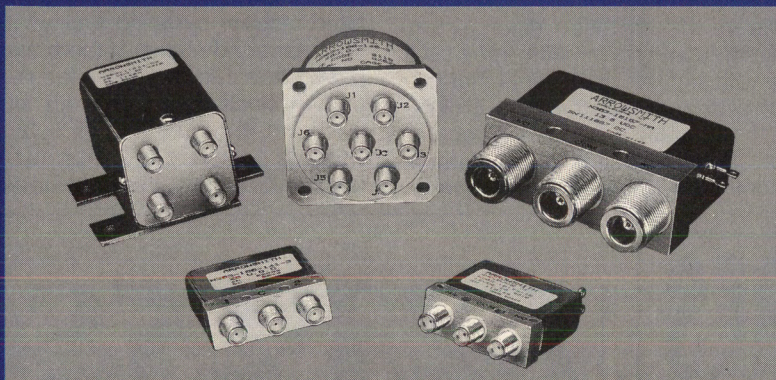
## SWITCH TO ARROWSMITH!

For All Your Microwave Switch Needs –  
The N-Series Microwave Switches from  
Arrowsmith Shelburne




**DESIGN IN HIGH QUALITY AND  
SUPERIOR PERFORMANCE AT A  
REASONABLE COST**

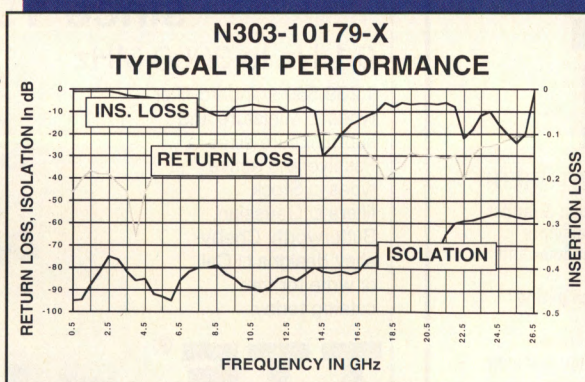The N series switches are available with 50 or 75 ohm impedance SMA, SMB, BNC, TNC, F, and N type connectors. Custom voltages are available. Other options include TTL compatibility, self de-energizing, indicator circuitry and suppression diodes. Please contact a sales representative for price and availability today.



**ARROWSMITH**  
Shelburne, Inc.

2085 Shelburne Road • Shelburne, Vermont 05482  
802-985-8621 • FAX: 802-985-1042

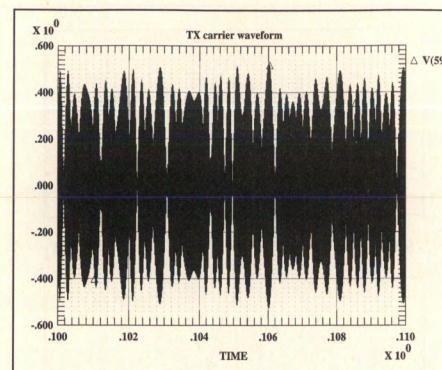


**Figure 6. Simulated QPSK signal in the time domain.**

simulation was for 1 second at a 1 ms time step (one million points). Only 200 ms of the data was plotted. The full second of simulation was necessary so that ample RF output simulation data could be stored to disk for the upcoming system bit error rate tests.

The quadrature demodulator can be tested quickly by using an imported local oscillator from the modulator in lieu of the carrier recovery system in Figure 2. If the I and Q channels are displayed in an XY fashion, the phase and amplitude trajectory of the QPSK signal will result. Once the operation of the quadrature demod is confirmed, the carrier recovery circuitry (Costas loop) can be added and debugged.

### Carrier Recovery Performance

This system is a second order phase locked loop, and the same methods as used on frequency synthesizers can be applied. The designer must be aware that the phase modulation on the carrier has spectral components that go quite low in frequency, so the bandwidth of the loop must be quite small. In a real system, switched time constants and/or sweep acquisition circuitry may be necessary for acceptable lock times. These types of systems can be simulated with TESLA, but the fast acquisition problem will be ignored here. The system simula-

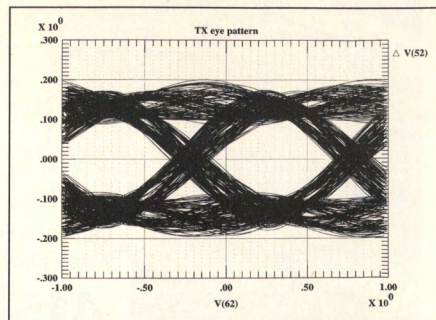


**Figure 7. Transmitter eye diagram.**

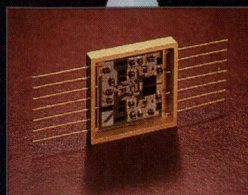

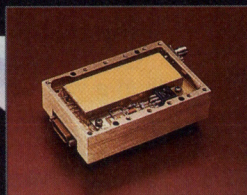
# THE VANGUARD


SPDT GaAs Switch with TTL Driver  
2 nSec Rise Time  
INFO/CARD 29




Digital Frequency Discriminator  
500 KHz Frequency Accuracy  
INFO/CARD 28



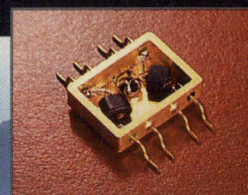Starved LO Mixer  
+7 dB Conversion Loss  
INFO/CARD 30



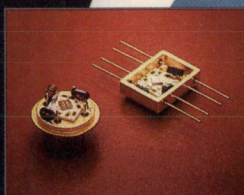RF Limiting Amplifier  
Gain Flatness  $\pm 1.0$  dB  
to 1 GHz  
INFO/CARD 27



Packageless  
Power Dividers  
O.D. as small as  
0.25" x 0.25"  
INFO/CARD 31



**T**HE STAR IS SYNONYMOUS WITH ACHIEVEMENT, QUALITY, AND REPRESENTATIVE OF THE ONE WHO LEADS THE REST. WHETHER IT'S OUR CUSTOM MANUFACTURING CAPABILITIES OR THE HUNDREDS OF IN-STOCK PRODUCTS, ST OLEKTRON IS AND WILL ALWAYS BE A LEADER IN THE RF COMPONENTS MARKET.

THESE FIVE COMPONENTS ARE JUST THE VANGUARD OF OUR GALAXY OF PRODUCTS. CIRCLE THE INDIVIDUAL READER NUMBER, CALL US AT 508-922-0019, X614, OR WRITE US AT ST OLEKTRON, 28 TOZER ROAD, BEVERLY MA 01915, AND WE'LL MAIL OR FAX YOU DATA SHEETS TODAY!



**ST**  
**OLEKTRON CORP.**  
a subsidiary of Signal Technology Corporation



28 Tozer Road • Beverly, MA 01915-5579 • Tel. 508.922.0019 • Fax 508.927.9328



tor will let us set initial conditions so that we can simulate only the locked case, or just the time period immediately surrounding the lock instant. Figure 8 is a composite of four TESLA plots showing the receive constellation in the unlocked state approximately one second before acquisition, nearing the correct frequency as the constellation spins slower a few tenths of a second later, the constellation on frequency just before phase lock, and finally the locked constellation.

### Bit Error Rate Performance

The real gauge of modem performance is the bit error rate (BER) in the presence of noise. The simulator has a BER tester model that can be used to this end. It is important to simulate the system at the highest error rate possible in order to keep the simulations short. In the case of QPSK, the variation of BER versus the signal to noise ratio (usually expressed as the energy per bit divided by the noise in a one hertz bandwidth,  $E_b/N_0$ ) is published and generally available. The BER of our demod with an input  $E_b/N_0$  of 5.7 dB is about  $10^{-2}$  (Figure 9). The difference in  $E_b/N_0$  (for a given BER) for a real modem and an ideal one is referred to as the implementation margin. An ideal QPSK modem will have a BER of  $10^{-2}$  with an input  $E_b/N_0$  of 4.3 dB. Our radio therefore has an implementation margin of 1.4 dB. This degradation in performance could be due to the small amount of ISI resulting from the system filters, the nonzero bandwidth of the Costas loop, or a characteristic of the coding scheme. The coding scheme used here was differential QPSK. The phase of each symbol is interpreted

based on that of the previous one. Unfortunately, this means that any error more or less automatically causes an error in the next symbol. This doubles our bit error rate. Without this degradation, the  $E_b/N_0$  would have been 5.2 dB. This leaves only 0.5 dB error that must be accounted for elsewhere (I feel better about my filters already!).

### Occupied Bandwidth

The tools at our disposal have been valuable for looking at things in the time domain, but sometimes we really need a frequency domain tool. For example, if we need to look at the transmitter occupied bandwidth, an oscilloscope type display just would not do much for us. The simulator's FFT facility gives us the tool we need for the task. Figure 10 shows the results of TESLA's FFT com-

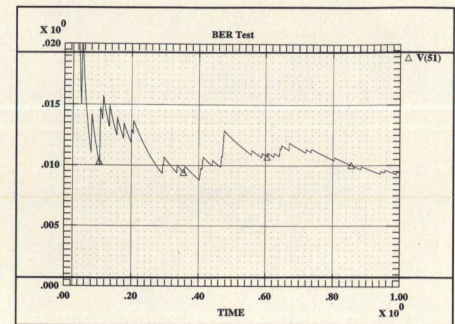


Figure 9. Simulated bit error rate for the modem.

putation on the transmitter output time data. The result is the spectral output of the transmitter.

### Conclusions

Outlined here is the sum of well less than a week of total engineering time. A


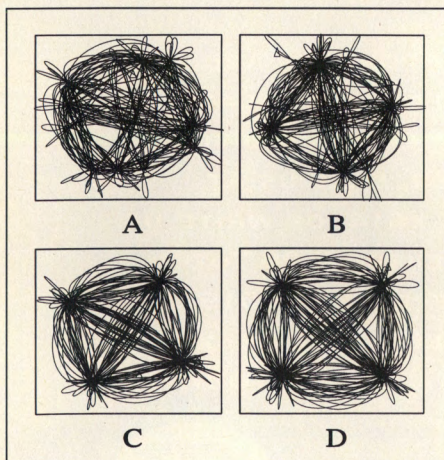


Figure 8. Receive constellation at various stages of signal acquisition and locking.

## On the Cover

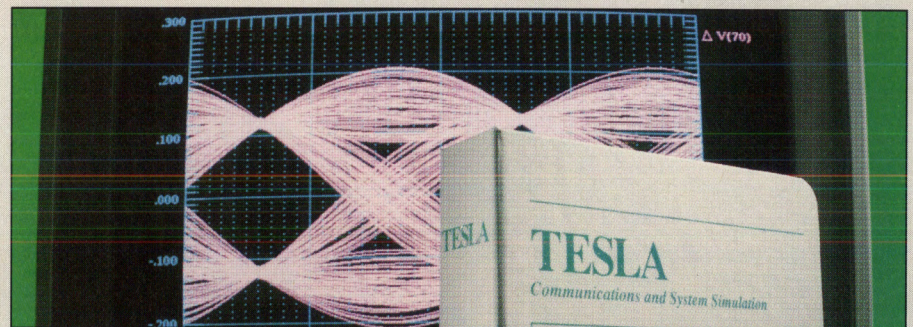

TESOFT's TESLA system simulator let's an engineer "build" an RF system in block diagram form and perform a time-domain simulation to analyze its performance. FFTs up to 4096 points are available to observe results in the frequency domain.

TESLA has over fifty circuit element models, including amplifiers, filters of all major types, VCOs, mixers, detectors, multiplexers and modulators. Standard digital logic functions and interface functions (A/D and D/A converters, comparators, delay lines, etc.) are available to make a complete system encompassing much more than simply the RF functions.

Software "test and measurement equipment" includes a bit error rate tester, sweep and coherent signal generators, metering in RMS, linear or dB, noise generators, pulse generators, and more.

With a wide selection of models for the system, signal sources and test points, a complex communications system can readily be modeled. Up to 800

circuit blocks with 1000 nodes can be modeled to more than 16 million time points. Data at 100 nodes can be stored for analysis.

Speed is a feature designed into TESLA. Speed in computation is achieved with dedicated models and good software development practices. Speed in usage comes from interactive commands that let the user edit schematics, tweak parameters or plot results from within TESLA.

Development speed comes from schematic capture libraries for the popular OrCAD and P-CAD programs. And, the MODGEN model generator allows custom models to be added to the simulator.

With pressures of time-to-market higher than ever, fast and accurate RF system simulation will help speed the development of new communications products.

For more information, contact TESOFT at 205 Crossing Creek Ct., Roswell, GA 30076, (404) 751-9785, or circle Info/Card #180.



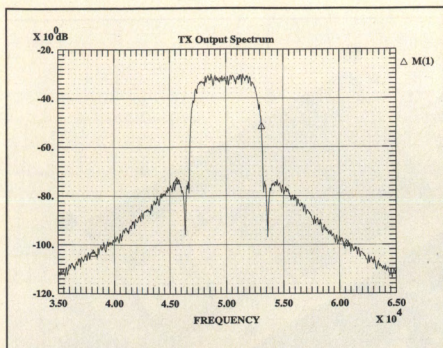


Figure 10. QPSK spectrum.

simple QPSK modem was designed, and several aspects of the design were evaluated. Without touching a single electronic component, we have some idea of the BER performance we can reasonably expect and how long it would take to "lockup" with the loop filter chosen. If modifications need to be made to meet the requirements, we can do it on the simulation before we start burning up time in the lab.

Time domain simulation can be used as a valuable tool to study the effects of design decisions well before the hardware prototyping stage. The skeleton of a system can be simulated using ideal components to test concept, and then models of the real world components can be substituted to study the overall effects on the system. With the cost of computer horsepower plummeting, and the cost of lab time (and time to market) shooting through the roof, many designs can benefit from the initial substitution of keyboard for oscilloscope and spectrum analyzer.

RF

#### References

1. D.R. Smith, *Digital Transmission Systems*, Van Nostrand Reinhold, New York, 1985.
2. V. Manassewitsch, *Frequency Synthesizers Theory and Design*, Wiley, New York, 1976.
3. J.J. Poklemba, "Pole-zero Approximations for the Raised Cosine Filter Family," *Comsat Technical Review*, Vol. 17, No. 1, Spring 1987, pp. 127-157.
4. J.J. Spilker, Jr., *Digital Communications by Satellite*, Prentice-Hall, Englewood Cliffs, NJ, 1977, pp. 302-312.

#### About the Author

Donald J. Miller is a staff engineer at Panasonic/Matsushita Communication Industrial Corp. He has a BSEE from Georgia Tech, and has worked at Panasonic for three years. His most recent projects have included cellular transmitter circuits and UHF VCOs. He can be reached at MCC Panasonic, 2001 Westside Parkway, Bldg. 200, Suite 260, Alpharetta, GA 30201.

# High Power RF Amplifiers and Power Generators

Our specialty is producing quality high power RF amplifiers, power generators and transmitters in the frequency range of 1 MHz to 200 MHz and at power levels up to 5000 watts.

We can deliver amplifiers from stock, custom build your design or design a product to your specifications.

Whether you need one or OEM quantities, you'll get the lowest prices and the fastest delivery in the industry.



By starting with raw sheet metal and copper clad boards and by using modern CAD tools and CNC machinery, we manufacture from start to finish.

You don't pay expensive middle man profits, you get quicker turnaround and better quality control.


For more information, call toll-free 800-647-1801 today and ask for Steven Pan. Be prepared to be amazed at our low prices and all that we can do for you.

**600 Watt FET Linear Amplifier Module, AL-4150, \$849.** Operates to VHF.

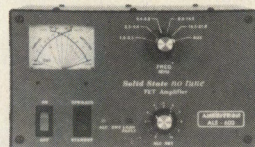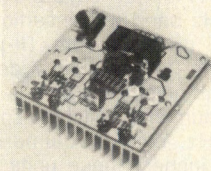Can be combined to produce several kilowatts. Ready-to-use. Assembled and tested with four MRF-150 FETs mounted on heat sink with solid copper heat spreader. Evaluate one today!



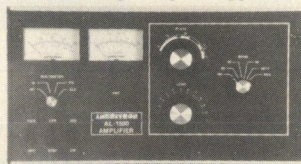This FET linear amplifier covers VLF to VHF with 200 watts continuous power output or 1500 watts output in pulse applications.



The rugged 3CX1500A7 tube in this HF amplifier delivers over 750 watts of continuous power or up to 4 KW of pulsed output power.

Write or call Steven Pan... 800-647-1801  
**Free Information**

**AMERITRON®**

... the high power RF specialists

921 Louisville Road • Starkville, MS 39759

(601) 323-8211 • FAX: (601) 323-6551

For more information call: 800-647-1800

8 a.m. - 4:30 p.m. CST, Monday-Friday


Prices and Specifications subject to change © 1993 Ameritron, Inc.

INFO/CARD 32

Now you can get the high Q of an air core inductor. Plus the convenience and cost savings of a true surface mount component.

Coilcraft springs come in values from 2.5 to 43 nH with Qs at high frequencies that reach 200 and higher.
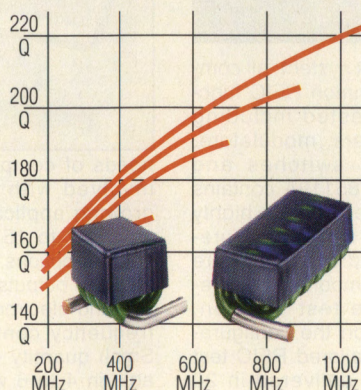
## Need more Q? Try our new surface mount spring inductors.



Our 2% tolerance versions can help you eliminate circuit tuning altogether!

They're tape and reel packaged and have a jacket with a flat top for auto insertion. We even tin the leads for reliable soldering.

Order our \$60 C102 Designer's Kit with 10 spring values. Or call us for our complete RF and surface mount product catalogs.

**Coilcraft**

1102 Silver Lake Road, Cary IL 60013  
800/322-2645 FAX 708/639-1469

INFO/CARD 33




## Bi-Phase Modulators

The Components and Subsystems division of Alpha Industries introduces the MX1016 and MX1017 Bi-phase Modulator Series. The MX1016 series covers the 0.5 to 2 GHz band with 4 dB minimum insertion loss. The MX1017 series covers the 2 to 18 GHz band with insertion loss of 5.5 dB maximum. Bi-phase error is 0.75 dB and 7 degrees for both units. Rise time is 10 ns, maximum and switching speed is 10 MHz. With a volume of 0.5 cubic inches, these units utilize carefully matched diodes and proprietary microstrip baluns to


yield broad band performance superior to quadrature-hybrid-based methods. Integrated MMIC drivers are available for either TTL or ECL inputs. The drive waveform is shaped to give -60 dBm switching spurious in the RF band for the MX1016 and -70 dBm for the MX1017. Units without drivers are also available. Power requirements are +5 V and -15 V at 40 mA each. Dimensions are 1.00 x 1.00 x 0.50 inches, without the field-replacable SMA connectors.

**Alpha Industries**  
INFO/CARD #250

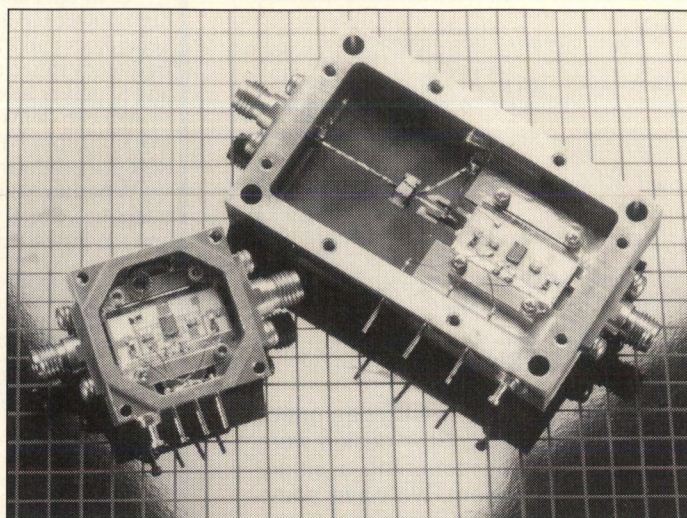
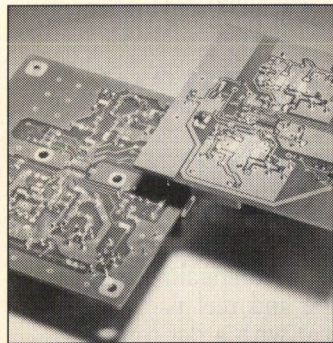
## Dual-Frequency Synthesizers

Three new synthesizers from Philips Semiconductor feature two independent frequency loops, direct drive to a voltage controlled oscillator, operation at supply voltages as low as 2.7 V, plus an auxiliary output port or DAC to control other handset functions. Current consumption is typically only 10 mA. Operating over 400 to 1100 MHz, the UMA1015M's two RF dividers and phase comparators share a common reference divider, which operates up




to 35 MHz. The UMA1018M has two completely independent synthesizers, one operating up to 1.2 GHz, the other, to 300 MHz. The UMA1020M is a 2.4 GHz version of the UMA1018M, and can operate at that frequency on a 2.7 V supply rail. All three synthesizers are controlled via a high-speed 3-wire serial interface. All are supplied in 20-pin, SSOP surface mount packages.

**Philips Semiconductor**  
INFO/CARD #249
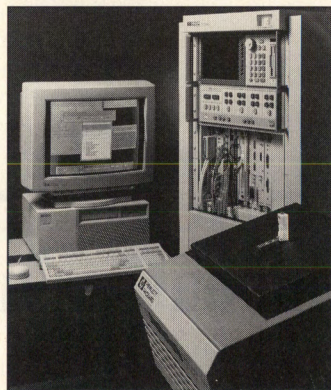
## RFIC Test System

Hewlett-Packard has announced an RF Integrated Circuit (RFIC) test system that provides complete, single-insertion 0.5- to 5-second test times for RFICs used in wireless communications. The HP 85119A RFIC test system gives semiconductor manufacturers test throughput up to ten times that of rack-and-stack R&D equipment, according to



HP. With the test system, all combinations of common RFIC functions can be tested including amplifiers, mixers, modulators, demodulators, switches and VCOs. The HP 85119A contains a high-speed receiver, a highly repeatable test set, a measurement director and other hardware and software components to create a complete test solution. Price is based on the configuration desired, a tailored RFIC test system can be delivered in 20 weeks.

**Hewlett-Packard Co.**  
INFO/CARD #248

## Compact, High Performance OCXO

Oak Frequency Control Group's 4840 OCXO is designed to provide performance and versatility in a compact, two-inch square by 0.75 inch package. The 4840's temperature stability is excellent at  $\pm 6 \times 10^{-9}$  from -20 to +70 °C, and aging is only  $\pm 7 \times 10^{-10}$  per day. Output level is 10 dBm, and power consumption is 3 W at 25 °C. Output is within 0.010 ppm of final frequency in 5 minutes. Designed to meet the




needs of component engineers involved with today's fastest growing applications, the 4840 covers 7 to 15 MHz and offers multiple options, including Sine or HCMOS outputs, 12 or 15 V supply, and electronic or mechanical frequency control adjustment. Small quantity orders are available in 4 to 6 weeks, and large quantities in 10 to 12 weeks.

**Oak Frequency Control Group**  
INFO/CARD #247
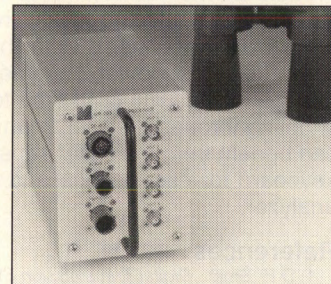
## Surveillance Receiver

The MR-203 receiver from Maxim Signal Products features 10 Hz tuning resolution, 1 ppm internal synthesized frequency accuracy and third-order intercept point of +5 dBm, typical. A high-performance tracking preselector operates over the HF/VHF/UHF



frequency range, giving the MR-203 a typical performance of 90 dB image and IF rejection with spurious signals at less than -110 dBm. In addition to an 8 MHz wide IF output, six other IF bandwidths, ranging from 500 Hz to 200 kHz, are standard. Detection modes include AM, FM, CW, SSB, and Log. Manual, spectrum search, band sweep and channel scan operation are all controllable via a serial interface. In the standard configuration, the receiver draws less than 5 W. An optional low-power model draws only 2 W. The MR-203 operates from 9 to 32 VDC over temperature ranges of -20 to +50 °C, in 100% condensing humidity.


**Delfin Systems, Maxim Signal Products Div.**  
INFO/CARD #246



## Product Spotlight: Switches
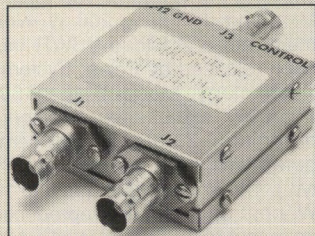
### 75 Ohm Switches

JFW Industries announces an addition to their RF switch line. Model 75S-134 is a solid state, 75 ohm 1P2T switch with an operating frequency range of 0.3 to 600 MHz. Minimum isolation is 80 dB, and switch-



ing speed is 60 MUs. The device requires +12 VDC (100 mA). RF input power is rated at +13 dBm (operating), +27 dBm (non-destructive).

**JFW Industries, Inc.**  
INFO/CARD #245

### Cellular Switches

A series of electromechanical switches developed for cellular frequency band applications is offered by Narda. These products include SPDT, multi-throw, and transfer switches. Examples of members of this family are model 020-A0-A1D-0C0, a SPDT unit for switching redundant components in cell and microcell equipment, model 042-B347-A1D-0C2, a latching SP4T unit with TTL-control for switching operating systems at the cell site, and model 063-D1234-D2B-0C1, a TTL-controlled, normally open SP6T unit with type-N connectors and indicator circuits for system ATE.

**Loral Microwave - Narda**  
INFO/CARD #244

### High Power Reflective Switch


A SP2T reflective, high power switch for the 1.02 to 1.1 GHz frequency range is offered by Norsal Industries. The switch handles 4 kW pulses at 0.15% duty cycle with 35 dB minimum isolation. It is switched by a +12 V control signal, and draws 400 mA nom-

inally. The switch's PIN diodes are field replaceable with no soldering required. The switch is qualified to MIL-STD-202 and is sealed against moisture.

**Norsal Industries, Inc.**  
INFO/CARD #243
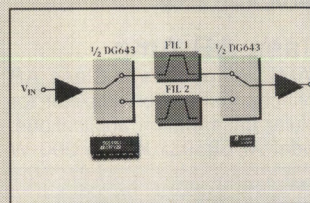
### SPDT RF/Video Switch

The DG643, a dual single-pole, double-throw switch, offers typical on-resistance of only 8 ohms and very low on-state capacitance of 10 pF. The switch from Siliconix offers a -3



dB bandwidth of 500 MHz and has a 75 mA current capability. In 1000-piece quantities, the device is priced at \$1.80 for a 16-pin plastic DIP and \$1.96 for a SO-16 package.

**Siliconix**  
INFO/CARD #242

### Electromechanical Switch Line

KW Microwave has added a coaxial electromechanical switch line to its family of products. The typical frequency range for the switches is DC to 26.5 GHz. These multi-throw switches are available in up to six throw positions, with latch, fail-safe, indicator and TTL options.

**KW Microwave Corp.**  
INFO/CARD #241


### SP10T Switch

Model DSO820 from Daico Industries is a SP10T PIN diode non-reflective switch that features an operating frequency of 10 to 1500 MHz. The switch requires 15 mA at +5 V. Its insertion loss is 0.95 dB from 10 to 500 MHz, and 1.6 dB from 500 MHz to 1500 MHz. Switching speed is 3.0 MUs (50% control to 10%/90% RF). Isolation is 46 dB to 1000 MHz and 42 dB from 1000 MHz to 1500 MHz, with VSWR of 1.3:1. The TTL-controlled switch comes in a 38 pin DIP package.

**Daico Industries, Inc.**  
INFO/CARD #240

# For RF, Use EF... E.F. Johnson
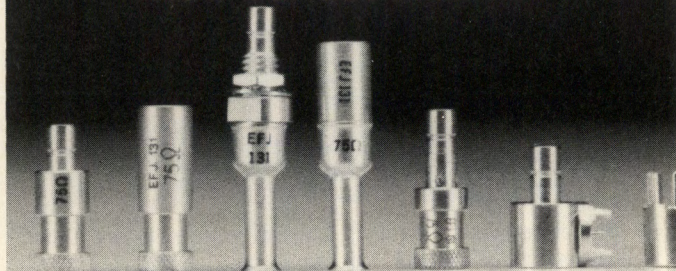
## RF Subminiature Connectors SMA, SMB & SMC New Surface Mounts




**EFJohnson**  
COMPONENTS

299 Johnson Ave., Waseca, MN 56093

**1-800-247-8256**

INFO/CARD 34

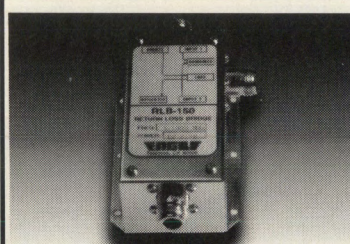

### Features

- Directivity: >50 dB typical
- Internal reference
- RF reflected port
- High power rating: 5 watts
- Swept measurements
- Rugged construction
- .04 Mhz to 3.0 GHz

## Return Loss Bridges

Return Loss Bridges are a low cost solution for swept SWR measurements. These bridges can be used with a spectrum analyzer/tracking generator or service monitor. Being a self contained unit, no external attenuators, amplifiers, comparators or detectors required. Five watt power rating, unmatched in the industry, protects YOUR bridge from power coming down the feedline during antenna measurements at crowded sites. Rugged nickel plated brass enclosures assure excellent durability and shielding.

**FREE** application note, "High Performance VSWR Measurements", call and ask for it!

Application note covers the uses of return loss bridges such as: tuning antennas, receivers, cavities, duplexers, isolators, and pre-amps. The relationship of VSWR, return loss and reflection coefficient is also discussed.

Model	Freq Range MHz	Directivity	Price
RLB150B1	.040 to 150	45 dB	\$259.00
RLB150N3A	5 to 1000	35 dB	\$329.00
RLB150N3B	5 to 1000	45 dB	\$389.00
RLB150N3C	5 to 1300	45 dB	\$425.00
RLB150N5A	5 to 3000	40 dB	\$579.00
RFT050NM2	DC-3000 reference load	40 dB	\$125.00
CCS050-NN5	Coaxial cable set 3 ft	NA	\$31.00

**EAGLE**

Phone: Voice: (316) 265-2050  
FAX: (316) 265-2255  
P.O. Box 9446 Wichita, KS 67277



## THE VCXO WITH PULLABILITY FROM RALTRON.



### VC 7025

Raltron manufactures its compact VC 7025 Voltage Controlled Crystal Oscillator to meet your Phase Locked Loop specifications, delivering deviation sensitivity or pullability of up to  $\pm 100$  PPM/V. Big performance in a small package. At a price you've been looking for.

Raltron manufactures a complete line of the highest quality VCXO's to both standard and custom specifications.

Call or fax your specs to Sandy Cohen.

**RALTRON**

**ELECTRONICS CORP.**

2315 NW 107 AVENUE  
MIAMI, FLORIDA 33172 U.S.A.  
FAX (305) 594-3973  
TELEX 441588 RALSEN  
(305) 593-6033

### ONLY RALTRON HAS IT ALL

Crystals / Crystal Oscillators  
Crystal Filters / Ceramic Resonators

INFO/CARD 36

## RF products *continued*

### AMPLIFIERS

#### Multi-Channel Cellular Amplifier

A multi-channel, solid-state, linear class-A amplifier module from Microwave Power Devices is designed for low intermodulation, multi-carrier operation. Model LWA880-50 operates over 869 to 894 MHz with linear output of 47 dBm (at 1 dB gain compression). Third order intercept is 54 dBm. A built-in digital attenuator provides 30 dB of control via TTL lines.

**Microwave Power Devices, Inc.**  
INFO/CARD #239

#### Class AB Amp

AML announces a Class AB multi-channel power amplifier for cellular base station applications. Model APB8596200 is a 200 W



PEP amplifier with 25 MHz instantaneous bandwidths from 850 MHz to 960 MHz. Intermodulation products measured in a two-tone environment at 50 W per tone are  $-30$  dBc min. The amplifier operates at +26 VDC. A power supply is optional, and the amplifier is offered in 19-inch, 24-inch and compact chassis configurations.

**AML, Inc.**  
INFO/CARD #238


#### Booster Amplifier

An AB linear booster amplifier covering the range of 100 to 500 MHz and delivering 200 W minimum into a 2:1 load VSWR has been released by Power Systems Technology. Model BME 1858-200/2997 exhibits low harmonic distortion ( $-23$  dBc typical) combined with high efficiency (23% typ.). The amplifier accepts 5 to 10 W input and faithfully reproduces an output at the 200 W level, while operating from conditioned vehicular power of +26.5 to +30 VDC.

**Power Systems  
Technology, Inc.**  
INFO/CARD #237

**TEMEX**  
**ELECTRONICS, INC.**  
3030 W. DEER VALLEY RD. PHOENIX, AZ 85027  
(602) 780-1995 FAX (602) 780-9699

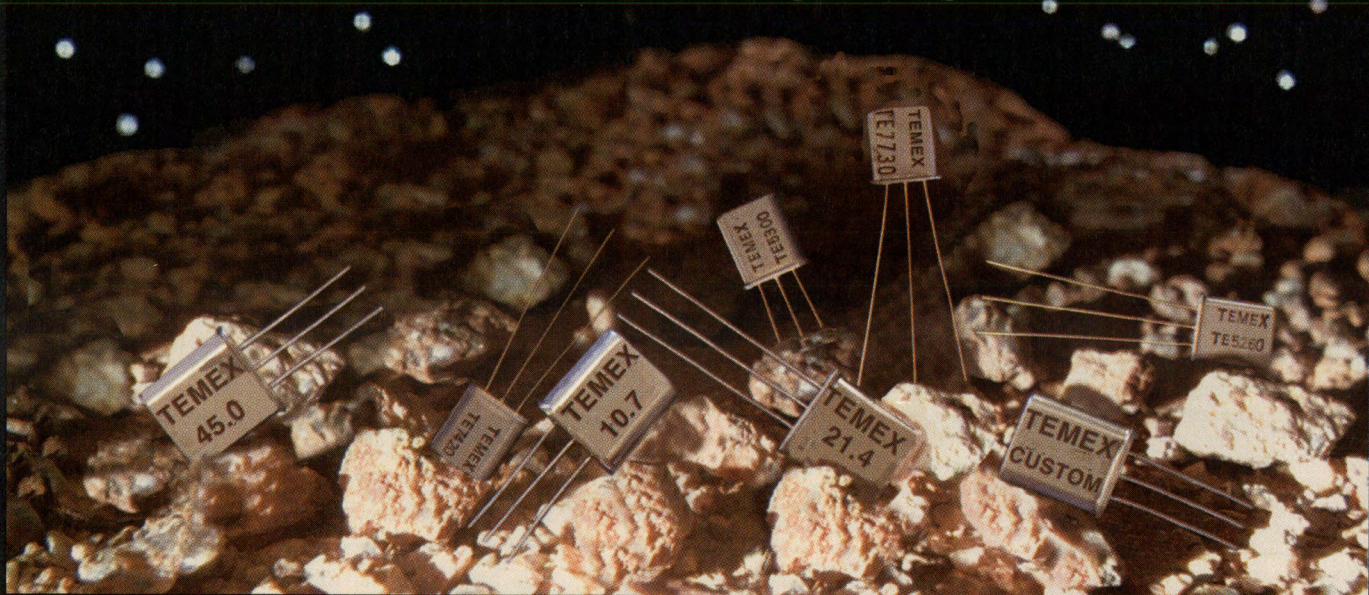CRYSTALS  
CRYSTAL FILTERS  
LC FILTERS  
FRONT END FILTERS  
DISCRIMINATORS



INFO/CARD 37



## TEST EQUIPMENT


### Pulse Modulator

Marconi Instruments has introduced a pulse modulator for testing civilian and military radar. The 6145 adds pulse modulation capability to the integral synthesized signal generator of the company's 6200 series Microwave Test Sets, as well as any other microwave source. The modulator covers 70 MHz to 20 GHz and has 5 dB of insertion gain. On/off ratio is greater than 70 dB, and rise/fall times are less than 5 ns. Price of the 6145 is \$6185.

**Marconi Instruments, Inc.**  
INFO/CARD #236
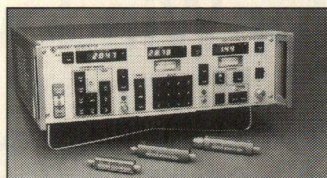
### Noise Figure Meters

Maury Microwave announces the availability of the MT2075C and MT2075C06 noise gain analyzers. The MT2075C has uncertainty better than  $\pm 0.05$  dB and the capability of accepting signals in the range from 10 to 2047 MHz.



Option 06 adds a high-speed processor that reduces measurement time by a factor of more than four.

**Maury Microwave Corp.**  
INFO/CARD #235

## SIGNAL PROCESSING COMPONENTS

### Voltage Variable Attenuator

A voltage variable attenuator covering 30 to 1000 MHz has been added to Hybrid-Tek's product line. The HTAA102 features a high third order intercept point of +40 dBm, while maintaining a dynamic range of 15 dB. The




## 948 Years Experience!

When reliability and accuracy count, call us. 948 years of combined employee crystal experience and 43 years of service to businesses like yours translates into our dedication to the quality products and customer satisfaction that you deserve.

- ENGINEERING AND DESIGN SUPPORT
- EXPERIENCED SALES STAFF

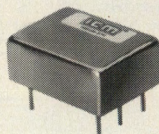- CRYSTAL ANALYSIS
- EXPEDITE SERVICE
- CUSTOM CRYSTALS TO YOUR SPECS
- MICRO-BALANCED/LAB CRYSTALS
- SOON TO BE ISO 9001 CERTIFIED
- LIFETIME CRYSTAL GUARANTEE



*Call or FAX for more information about Crystals, Elements, Oscillators and Accessories.*


## WHEN QUALITY COUNTS...

**INTERNATIONAL CRYSTAL MANUFACTURING CO., INC.**

PHONE 24-HOUR FAX  
**1-800-725-1426 • 1-800-322-9426**  
P.O. BOX 26330 • OKLAHOMA CITY, OK 73126

INFO/CARD 38

# High Performance Attenuators

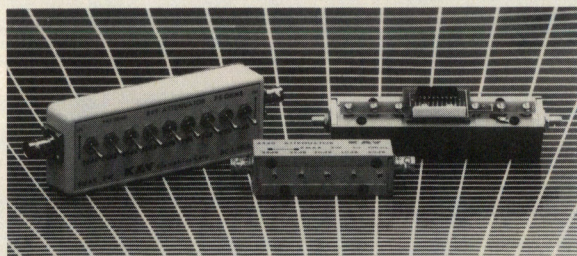

- New Low Prices
- History of Durability
- Impressive Accuracy
- Quick Delivery
- Long Operational Life

For price list and FREE catalog, contact:

**KAY** Kay Elemetrics Corp.  
12 Maple Avenue, PO Box 2025  
Pine Brook, NJ 07058-2025 USA  
TEL: (201) 227-2000  
FAX: (201) 227-7760

### Manual Step Attenuators

837	50Ω	DC-1500MHz	0-102.5dB	.5dB Steps
839	50Ω	DC-2000MHz	0-101dB	1dB Steps
1/839	50Ω	DC-1000MHz	0-22.1dB	.1dB Steps
847	75Ω	DC-1000MHz	0-102.5dB	.5dB Steps
849	75Ω	DC-1500MHz	0-101dB	1dB Steps
1/849	75Ω	DC-500MHz	0-22.1dB	.1dB Steps
860	50Ω	DC-1500MHz	0-132dB	1dB Steps
865	600Ω	DC-1MHz	0-132dB	1dB Steps
870	75Ω	DC-1000MHz	0-132dB	1dB Steps

### Programmable Attenuators

4440	50Ω	DC-1500MHz	0-130dB	10dB Steps
4450	50Ω	DC-1500MHz	0-127dB	1dB Steps
1/4450	50Ω	DC-1000MHz	0-16.5dB	.1dB Steps
4460	50Ω	DC-1500MHz	0-31dB	1dB Steps
4480	50Ω	DC-1500MHz	0-63dB	1dB Steps
4540	50Ω	DC-500MHz	0-130dB	10dB Steps
4550	50Ω	DC-500MHz	0-127dB	1dB Steps
1/4550	50Ω	DC-500MHz	0-16.5dB	.1dB Steps
4560	50Ω	DC-500MHz	0-31dB	1dB Steps
4580	50Ω	DC-500MHz	0-63dB	1dB Steps

INFO/CARD 39




ENHANCED  
TUNE MODE

VERSION 6.0
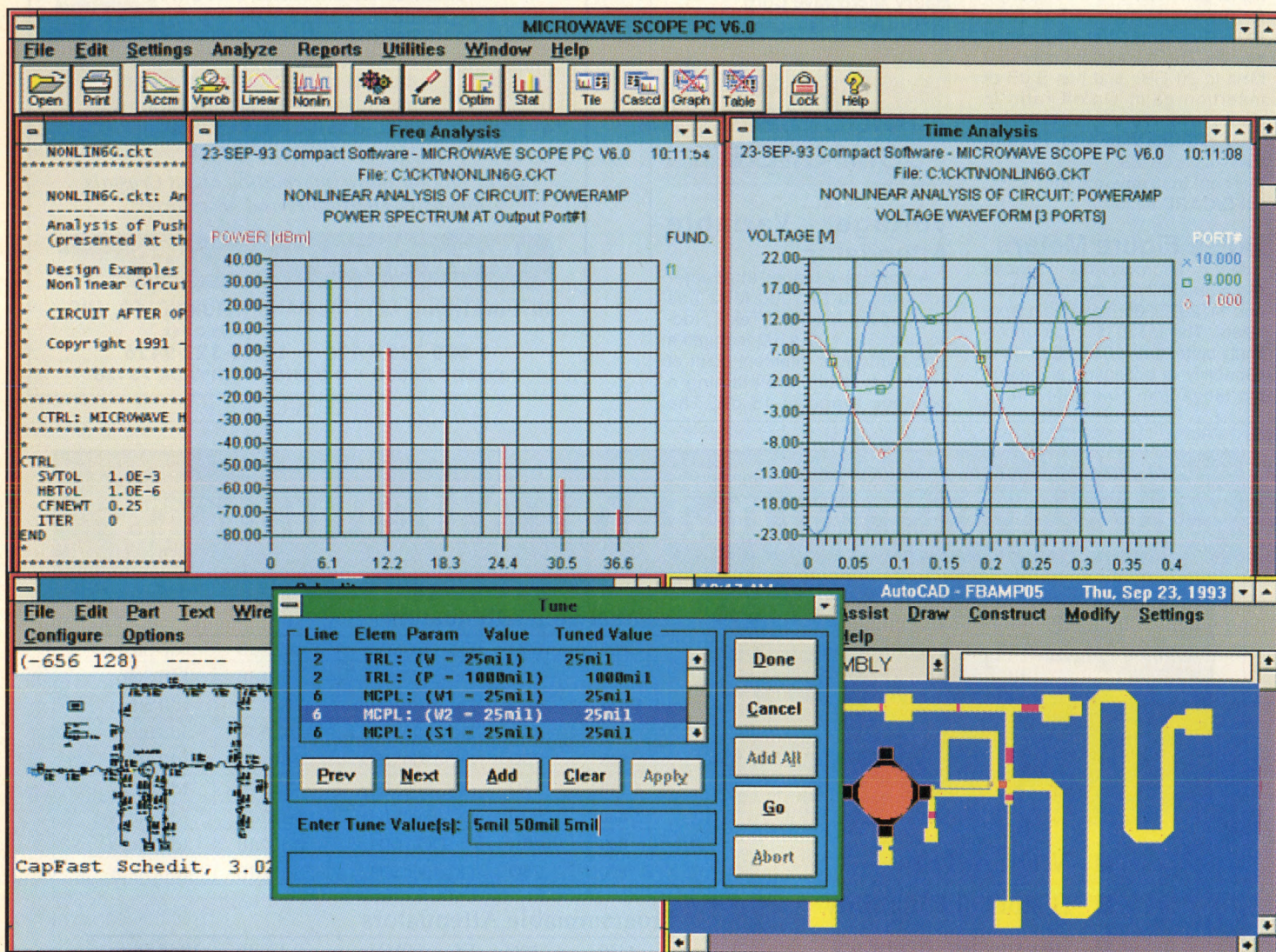
# Serenade<sup>®</sup> PC for Windows<sup>™</sup>

Super-Compact<sup>®</sup>, Microwave Harmonica<sup>®</sup>, and Microwave Scope<sup>®</sup>  
RF, Microwave, and Lightwave Circuit Simulators  
Integrated with Schematic and Layout Editors



# Compact Software<sup>®</sup>

201 McLean Boulevard  
Paterson, NJ 07504  
Tel: (201) 881-1200  
FAX: (201) 881-8361

INFO/CARD 40


**Super-Compact<sup>®</sup>**  
Linear Circuit Simulator

**Microwave Harmonica<sup>®</sup>**  
Nonlinear Circuit Simulator

**Microwave Scope<sup>®</sup>**  
Lightwave Circuit Simulator



# Serenade® PC for Windows™

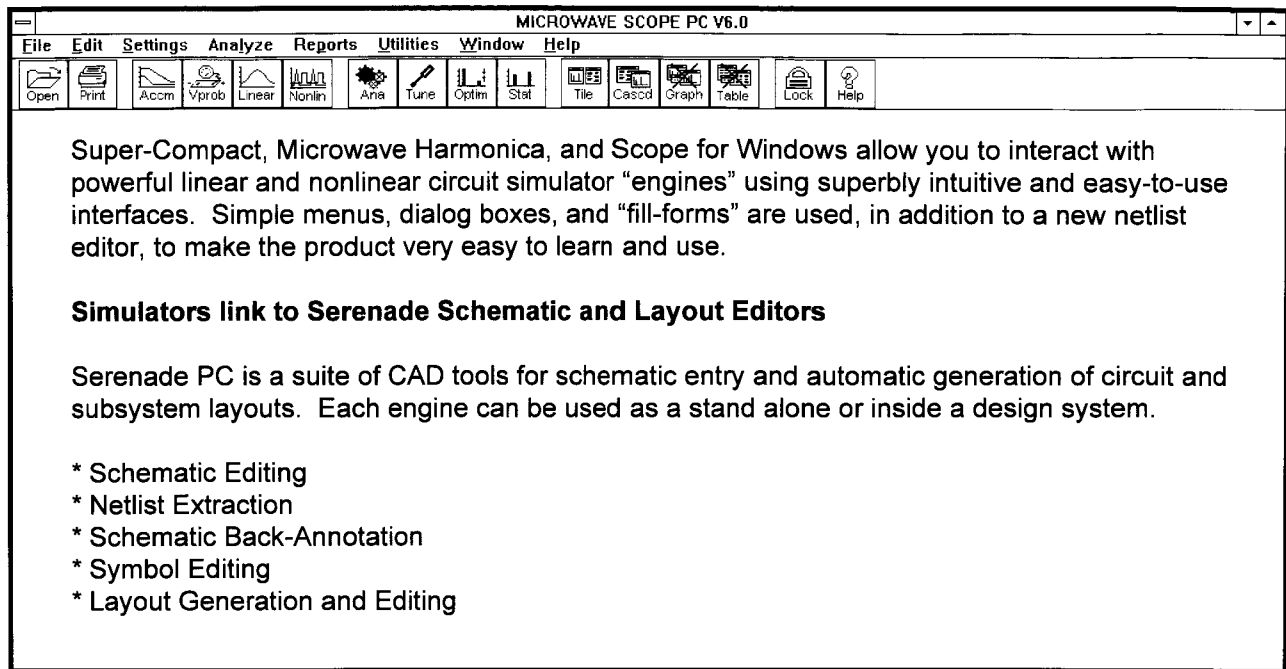

*In order to receive complete literature and a **free demo software kit**, please fax or send this page to Compact Software, or to the representative in your country.*

European Support Center  
Austria, Denmark, Finland, France, Germany, Italy, Luxembourg,  
Norway, Portugal, Spain, Sweden, Switzerland  
Technical Software Service (Germany)  
FAX: 49-7309-3275 - PHONE: 49-7309-5075

**Belgium** – See The Netherlands

**Ireland** – See United Kingdom

**Israel**  
U.S.I.E. Ltd.  
FAX: 972-3-93-02558 - PHONE: 972-3-93-45979

**Japan**  
Seki Technotron Corp.  
FAX: 81-3-3820-1433 - PHONE: 81-3-3820-1714

**The Netherlands**  
BFI Ibexsa Electronics, S.A.  
FAX: 31-20-65-31-353 – PHONE: 31-20-65-350

**South Africa**  
Microwave & Electronic Technology  
FAX: 27-12-663-2978 - PHONE: 27-12-663-2975

**Taiwan**  
Evergo Corporation  
FAX: 886-2-712-2466 - PHONE: 886-2-715-0283

**Turkey**  
Momentum Projects & Consulting  
FAX: 90-1-257-7663 - PHONE: 90-1-257-7170

**United Kingdom**  
BFI Ibexsa Electronics, S.A.  
FAX: 44-622-882469 - PHONE: 44-622-882467

Name: \_\_\_\_\_  
Title: \_\_\_\_\_  
Company: \_\_\_\_\_  
Address: \_\_\_\_\_  
\_\_\_\_\_  
Fax #: \_\_\_\_\_  
Phone #: \_\_\_\_\_  
Interested in:  
\_\_\_\_ Super-Compact  
\_\_\_\_ Microwave Harmonica  
\_\_\_\_ Microwave Scope  
\_\_\_\_ Serenade Schematic Editor  
\_\_\_\_ Serenade Layout Editor  
Platform: \_\_\_\_ Workstation \_\_\_\_ PC

CSBQ001F

**Compact Software®**  
201 McLean Boulevard • Paterson, NJ 07504  
Tel: (201) 881-1200 • FAX: (201) 881-8361



attenuator has control voltage range of 0 to +10 V and draws only 20 mA. The HTAA102 is available in TO-8 and surface mount flat pack packaging, and in 50 ohm versions.

**Hybrid-Tek, Inc.**  
INFO/CARD #234

## Cellular Filter

K&L's dielectric resonator filter is centered at 882 MHz. The 3 dB bandwidth is 26 MHz. The filter is capacitively coupled and inductively loaded to provide more than 80 dB rejection at 740 MHz and 1024 MHz. Insertion loss is 2.2 dB maximum at mid-band.



The unit is protected in a solid housing measuring  $1.6 \times 0.83 \times 0.6$  inches, with a drop-on laser sealed cover.

**K&L Microwave, Inc.**  
INFO/CARD #233

## Wideband Mixer

The RMS-30 mixer covers the 200 to 3000 MHz frequency band, and has IF response down to DC. The RMS-30's surface mount package is all ceramic and measures  $0.25 \times 0.31 \times 0.275$  inches. The mixers have all-welded internal construction and can withstand temperatures from  $-55$  to  $100^\circ$  C. The RMS-30 is offered for off-the-shelf delivery at \$6.95 in qty. of 10 to 49, and includes a 5-year guarantee.

**Mini-Circuits**  
INFO/CARD #232

## Step Attenuator

The 3200 series programmable step attenuators are designed for use in automatic test equipment and OEM systems operating in the DC to 2 GHz range. This series is available in four stan-

dard attenuation ranges and cell configurations. Power rating is 1 W avg., 50 W peak. Standard connectors are SMA female, and SWR is 1.25 from DC to 1 GHz, and 1.35 from 1 to 2 GHz.

**Lucas Weinschel**  
INFO/CARD #231

## SAW Filters

Two new SAW, coupled-resonator filters, the RF1210 and the RF1211, operate at 303.875 and 315 MHz, respectively. Both filters have 1.2 dB insertion loss, a 3 dB BW of 600 kHz and selective nulls placed 10.7 and 21.4 MHz below their center frequencies. The RF1210 and RF1211 are available now, and cost \$2.71 each the 1000's.

**RF Monolithics, Inc.**  
INFO/CARD #230

## SEMI-CONDUCTORS

### Capacitive-Load Op Amps

Linear Technology's CLOAD™

high speed op amps are based on a new topology that prevents oscillation with capacitive loads. In addition, this topology results in very high slew rate with lower supply currents, lower noise, lower input bias current, lower input offset voltage and less drift than previous circuits. The first members of this family are available with gain bandwidths of 12, 25, 50 and 70 MHz, and in single-, dual- and quad-op amp versions.

**Linear Technology Corp.**  
INFO/CARD #229


### Class AB, 1 GHz, 5W MOSFET

The WRLS0945 provides 5 W of class AB output power with 10.0 dB of gain from a 12.5 V supply. This device will withstand a 30:1 mismatch at rated power output at 925 MHz. The transistor is packaged in a high-dissipation, ceramic SO-8 surface mount package. Pricing at 100 pieces is \$27, with delivery from stock.

**RF Products, Inc.**  
INFO/CARD #228

## HF POWER AMPLIFIERS

*High Reliability, Commercial Quality*

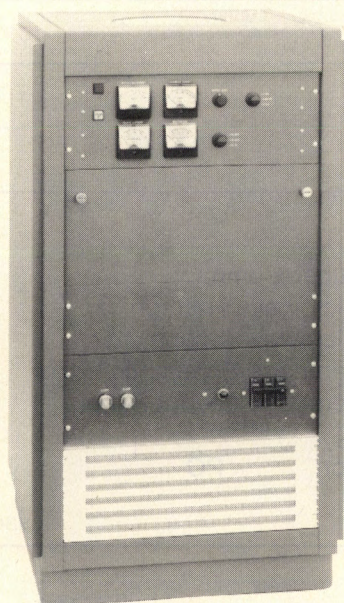

◆ 1.8 to 30 MHz  
◆ 1500 to 10,000 Watts

HENRY HF Power Amplifiers have been the reliability standard for 30 years. Thousands are in use at commercial, government, and military installations around the world.

If you require trouble-free, 24-hour-per-day, year-round operation, call or write today for prices and specifications.

TOLL-FREE (800) 877-7979

**HENRY RADIO**



2050 South Bundy Drive  
Los Angeles, CA 90025

Phone (310) 820-1234  
FAX 310-826-7790

PREVIOUSLY OWNED

**TOP QUALITY  
MICROWAVE  
TEST EQUIPMENT  
AND HARDWARE**

**WHY PAY  
TOP DOLLAR  
FOR THE BEST...  
WHEN YOU CAN  
BUY AT A  
DISCOUNT FROM**

*Accutest  
Instruments*

P.O. BOX 130/Route 526,  
Clarksburg, NJ 08510

**CALL TODAY  
1-800-524-0747**

(CATALOG AVAILABLE)



# Designing telecommunications equipment? Here's how to put your world on a string.

Quite simply, tap into the proper sources. Because, while in one sense the world's a lot smaller, it can seem pretty big when the support you need is on the other side of it.



It needn't be that way in passive components. Because Murata's always nearby. Whether you're building Global Positioning Systems in Singapore, RF modems in Milan, or telephone systems in Thailand.

And we're there in a big way. With the technical expertise that ensures speed and flexibility in meeting new design requirements. With the high-volume manufacturing and distribution resources that—in getting parts where and when you need them—shrink the world to “neighborhood” size. And, of course, with undisputed Murata quality, backed by our unique 1.0 QRS (100% quality, reliability, service) program.

Oh, yes—product line breadth. You'll find our line, the largest, from chip caps to piezoelectric gyroscope systems, can make a world of difference in calculating the economic rewards of vendor reduction efforts.

Call or write for details: Murata Electronics North America, Marketing Communications, 2200 Lake Park

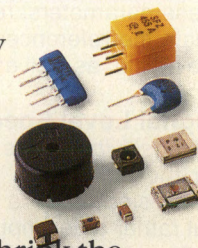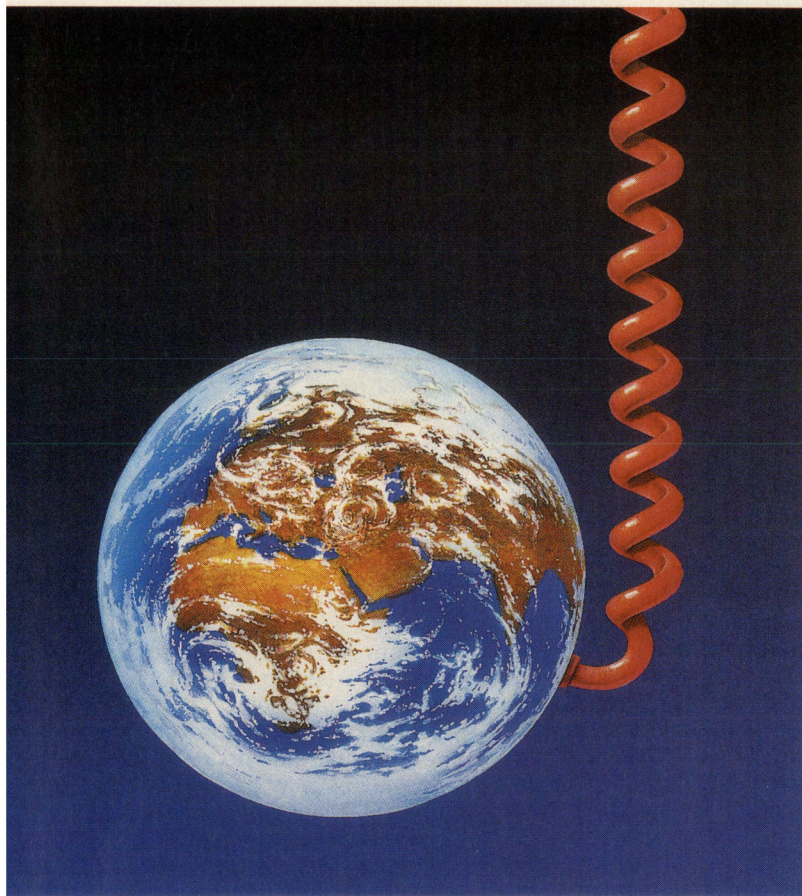Drive, Smyrna, GA 30080; 1-800-831-9172, Fax: 1-404-684-1541. Because, if it's the telecommunications world you're after, you'll want to string along with us.



MURATA ELECTRONICS NORTH AMERICA, INC.  
INFO/CARD 43



## Receiver Basics — Part 1: Performance Parameters

By Gary A. Breed  
Editor

*Receiver designs range from the simplest TRF remote control units to ultra-high performance communications and surveillance receivers. This tutorial, the first of two parts, introduces the fundamental performance concepts that receiver designers must understand.*

**P**erformance drives the design of receivers. Once the basic functions of frequency range and modulation types have been defined, the design of a receiver will be determined by the requirements for sensitivity, distortion, noise, dynamic range, and other performance parameters. These fundamental parameters are identified and presented here. For detailed information on any of these parameters, readers should investigate the references given at the end of the article, as well as other sources.

### Signal Level Specifications

**Sensitivity** — This is the “generic” term for the ability of a receiver to pick out weak signals. It is not a specification, but rather a descriptive term.

**Signal-to-Noise Ratio (S/N)** — S/N is the ratio of the level of the signal to the level of the noise. Many specifications are written for Signal-Plus-Noise to Noise ratio (S+N)/N, the level by which the signal exceeds the noise level, since (S+N)/N is readily measured.

**Noise Figure (NF)** — A figure of merit which is simply the ratio (in dB) of the S/N of the output versus the S/N of the input of a circuit or system. Accurate measurement of NF requires a calibrated noise source (a known noise level).

**Minimum Discernible Signal (MDS)** — This is one specific measure of sensitivity, which includes the bandwidth of the system. The accepted method of measuring MDS is with any automatic gain control functions disabled. A signal is applied and the generator is adjusted until the signal-plus-noise is 3 dB above the no-signal noise level. At this point, the applied signal power is equal to the no-signal noise power, since their sum is two times the latter. Noise power is proportional to the square root of band-

width, so an MDS measurement will be different at differing bandwidths, even in the same receiver. Therefore, MDS performance specifications must include the measurement bandwidth.

**Desensitization Level** — Where MDS was a weak signal, desensitization is a strong-signal specification. Typically, a desensing of 1 dB is specified, the level of a strong signal which reduces a nearby weak signal by 1 dB. Usually, this means that the strong signal has begun to saturate the mixer diodes or an amplifier transistor.

**Third Order Intercept Point** — This specification is a figure of merit for intermodulation distortion (IMD). Nonlinearities are measured by introducing two signals that are close together in frequency, then increasing their levels and observing the level of the two close-in third order distortion products (2F1–F2 and 2F2–F1). Square-law behavior is predominant, so the slope of desired versus third-order signals is 3:1 (in dB); for each 1 dB increase in the test signals, the IMD increases by 3 dB. With this kind of slope, at some point, the IMD would equal the test signal. This is physically impossible, since the circuit will go into compression before this point is reached, but if the levels are plotted in the square-law region, the lines can be extended to the imaginary intersection, which is the intercept point. As the intercept point increases, so does the range of signals that do not create high IMD levels. Specifications must note whether they are referenced to signal levels at the input or the output of the circuit or device.

**Dynamic Range** — This defines the range of signals that a receiver can handle with a specified performance. This may be the range from MDS to 1 dB compression, or blocking dynamic range. It may also be the range from MDS to the point where third order IMD equals MDS, which is spurious-free dynamic range (SFDR). In some cases, it may be specified as the difference between MDS and a level with specified IMD (e.g. –40 dBc).

### Unwanted Signal Specifications

**Image Rejection** — The first mixer stage responds to be either the sum or difference of the desired signal and the local oscillator. The signal that represents the opposite case is undesired, and must be kept from reaching the mixer by filtering. The measure of the filter's performance is image rejection, with measurement usually made by applying an image signal at the input and increasing its level until it is detectable. A test signal within the desired receiver passband is then applied and its level adjusted until it is the same as the earlier image signal. The difference in amplitude of these two test signals is the image rejection.

**IF Rejection** — A signal that is within the IF passband may find a path past the filters and mixers and be coupled into the IF circuitry. IF rejection is the measure of attenuation between the receiver input and the IF circuit. Measurement is the same as image rejection, except that an IF signal is applied as the first test signal.


**Spurious Rejection** — Signals at any other frequency than those noted above are considered spurious. They are identified by sweeping a test signal across a band at least as wide as the receiver's intended tuning range, while tuning the receiver through its entire range. Exhaustive testing is needed to find all possible frequency combinations, but sweeps made a several different frequencies within the receiver tuning range will usually identify any significant problems. Measurement is done in the same manner as image and IF rejection.

**Internally-Generated Spurious Signals** — With the antenna input terminated, the receiver is tuned through its entire range. Any internally-generated signals will be detected as if they were weak CW signals. Typical specification of internally generated spurious signals is a maximum level, equivalent to a specified external signal level.

**Unwanted Modulation Rejection** — AM rejection in an FM receiver is a common application of this specification, as



# MIXERS UNPRECEDENTED IN VALUE.

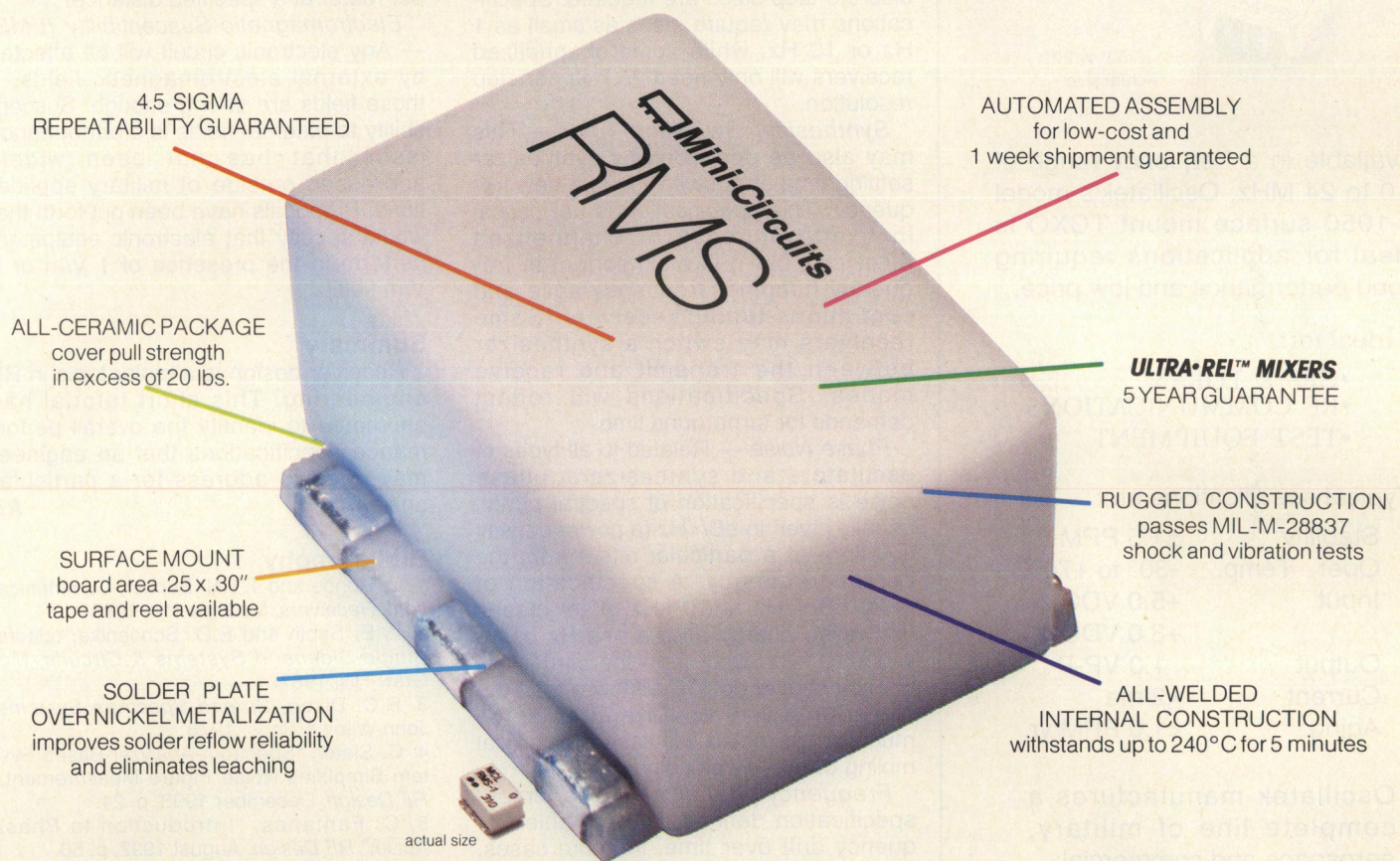

**ALL-CERAMIC 5 to 3000MHz \$395**  
from (10-49 qty)

Now you can buy very low-cost, high-performance commercial mixers with the ruggedness and reliability required for military applications. That's value!  
... Only from Mini-Circuits.

Model	LO (dBm)	Freq. (MHz) LO, RF	IF	Midband, dB			\$ea. (10-49)
				Conv. Loss	Isol L-R	L-I	
RMS-11X	+7	5-1900	5-1000	7.1	29	31	3.95
RMS-11F	+7	350-2000	DC-400	5.5	31	30	4.95
RMS-30	+7	200-3000	DC-1000	6.5	26	22	6.95
RMS-25MH	+13	5-2500	5-1500	7.5	32	32	7.95

finding new ways ...  
setting higher standards

**Mini-Circuits®**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

**Distribution Centers** / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.


CUSTOM PRODUCT NEEDS... Let Our Experience Work For You.

F166 REV. ORIG.

INFO/CARD 44



# SURFACE MOUNT TCXO's

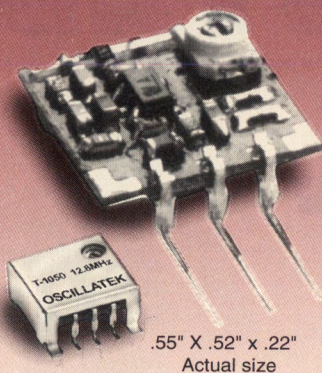

Available in a frequency range of 8.0 to 24 MHz, Oscillatek's model T-1050 surface mount TCXO is ideal for applications requiring good performance and low price.

Ideal for:

- GPS & LORAN
- RF COMMUNICATIONS
- TEST EQUIPMENT

Typical specifications are:

Stability	±1.5 PPM
Oper. Temp.	-30° to +70°C
Input	+5.0 VDC or +3.0 VDC
Output	1.0 VP-P
Current	<2 ma
Aging	<1.0 PPM/yr.

Oscillatek manufactures a complete line of military, aerospace and commercial:

OCXO's & OVCXO's  
TCXO's & VCXO's  
HYBRID CLOCKS  
QPL CLOCKS

## OSCILLATEK

A DOVER TECHNOLOGIES COMPANY

620 NORTH LINDENWOOD  
OLATHE, KS 66062  
FAX (913)829-3505  
PH. (913)829-1777  
INFO/CARD 45

well as AM carrier feedthrough in a SSB receiver. Measurement is made by the equivalent level method noted above.

### Overall Performance

**System Gain** — The overall gain must be sufficient to provide an output at a usable level when the input is the MDS. For example, with an MDS of -120 dBm to drive an audio output of 0.1 watt (20 dBm), the power gain must be 140 dB.

**Synthesizer Resolution** — How fine must the tuning steps be? In analog-tuned receivers, coverage was continuous, but with digital frequency synthesis, discrete step sizes are required. Specifications may require steps as small as 1 Hz or 10 Hz, while some channelized receivers will only need 25 kHz per step resolution.

**Synthesizer Switching Time** — This may also be described as synthesizer settling time after switching to a new frequency. This specification is not critical in fixed-frequency or channelized receivers, but it is all-important in frequency-hopping, frequency-agile and continuous-tuning receivers. Some receivers may switch a synthesizer between the transmit and receive modes. Specifications will reflect demands for turnaround time.

**Phase Noise** — Related to all types of oscillators and synthesizers, phase noise is specification of spectral purity, usually given in dBc/Hz (a power density function) at a particular offset from the center frequency. A specification of -120 dBc/Hz at 10 kHz offset means that noise energy at in a one Hz bandwidth 10 kHz away from the carrier frequency should be 120 dB lower than the carrier. In a very sensitive receiver, too much phase noise will cause reciprocal mixing or mask weak signals.

**Frequency Stability** — This simple specification defines the allowable frequency drift over time. In some cases, the specification follows regulations for the radio service being received. In other cases, the modulation type and bandwidth usually dictate stability requirements. Spread spectrum systems and some very narrow band modes typically require the greatest stability.

**Demodulation Linearity** — Accuracy of demodulation may include harmonic and intermodulation distortion specifications for audio signals or differential phase and gain requirements for video signals. Digital signal demodulation is usually not separated from full-system performance, which is measured in terms of bit error rate (BER).

### Electromagnetic Interference (EMI) —

Ideally, electronic equipment only performs its intended function, no more, no less. In practice, however, most electronic equipment will generate electromagnetic energy at more than one frequency. A receiver's oscillators can be a source of unwanted radiation, with a maximum level given as part of the receiver specification. Part 15 of the FCC Rules and Regulations includes limits on radiation from electronic equipment, and is the most common specification in the U.S. Specifications are typically given in field intensity (mV or  $\mu$ V per meter at a specified distance).

### Electromagnetic Susceptibility (EMS)

— Any electronic circuit will be affected by external electromagnetic fields, if those fields are strong enough. Susceptibility to external fields is a performance issue that has not been widely addressed outside of military applications. Proposals have been put forth that would specify that electronic equipment perform in the presence of 1 V/m or 3 V/m fields.

### Summary

Receiver design is a major topic in RF engineering. This short tutorial has attempted to identify the overall performance specifications that an engineer may need to address for a particular design.

RF

### Bibliography

1. U. Rohde and T.T.N. Bucher, *Communications Receivers*, McGraw-Hill, 1988.
2. W.E. Sabin and E.O. Schoenike, editors, *Single-Sideband Systems & Circuits*, McGraw-Hill, 1987.
3. R.C. Dixon, *Spread Spectrum Systems*, John Wiley & Sons, 1976.
4. C. Slater, "Spectrum-Analyzer-Based System Simplifies Noise Figure Measurement," *RF Design*, December 1993, p. 24.
5. C. Fantanas, "Introduction to Phase Noise," *RF Design*, August 1992, p. 50.
6. J. Donohue, "A Program for the Design and Analysis of Receivers," *RF Design*, October 1993, p. 101.
7. G.A. Myers, "User-Friendly Error Curves for Digital Radios," *RF Design*, April 1992, p. 39.
8. M. Bartz, "Designing Effective Two-Tone Intermodulation Distortion Test Systems," *RF Design*, November 1987, p. 59.
9. B. Kasmir, "Fundamentals of Receiver Design for Part 15 Applications," *RF Design*, September 1992, p. 35.
10. R. Hawkins, "Combining Gain, Noise Figure, and Intercept Point for Cascaded Circuit Elements," *RF Design*, March 1990, p.77.
11. N. Ayrandjian, "Simple Computation of Spurious-Free Dynamic Range," *RF Design*, January 1987, p. 65.



# TOUGH ALL-WELDED MIXERS



## SURFACE-MOUNT or PLUG-IN

FROM **\$3<sup>95</sup>** (10 qty)


Expose Mini-Circuits' TUF-mixers to 250°C for five minutes, or to the extreme shock and vibration stresses of MIL-M-28837, or to 200 cycles of thermal shock from -55° to +100°C...they'll survive without any change in specs. They are mighty tough mixers!

Available with LO drive levels from +7 to +17dBm, performance features include very low conversion loss flat over the entire band, high isolation (L-R, L-I), and well-matched VSWR at all ports.

All-welded internal and external construction is used to assemble and package the TUF-unit in its tiny 0.5 by 0.2 by 0.25 in. metal case, for plug-in or surface-mount\* assembly.

TUF-Ultra-Rel™ mixers are guaranteed for five years and boast unprecedented "skinny" sigma ( $\delta$ ) unit-to-unit repeatability as shown in the Table.

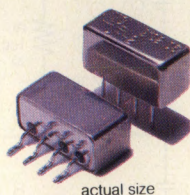Tough, tiny, and with tight repeatability...Mini-Circuits' Ultra-Rel™ TUF-mixers with a five-year guarantee, priced from \$3.95...available only from Mini-Circuits.



## ULTRA-REL™ MIXERS

5-YR. GUARANTEE

with extra long life due to unique HP monolithic diode construction, 300°C high temp. storage, 1000 cycles thermal shock, vibration, acceleration, and mechanical shock exceeding MIL requirements.

## SPECIFICATIONS

Model	LO Power (dBm)	Freq. LO/RF (MHz)	Conv. Loss (dB)		Isol. L-R (dB)	Price,\$ Ea. 10 qty
			$\bar{X}$	$\delta$		
TUF-3	7	0.15-400	4.98	0.34	46	5.95
TUF-3LH	10		4.8	0.37	51	7.95
TUF-3MH	13		5.0	0.33	46	8.95
TUF-3H	17		5.0	0.33	50	10.95
TUF-1	7	2-600	5.82	0.19	42	3.95
TUF-1LH	10		6.0	0.17	50	5.95
TUF-1MH	13		6.3	0.12	50	6.95
TUF-1H	17		5.9	0.18	50	8.95
TUF-2	7	50-1000	5.73	0.30	47	4.95
TUF-2LH	10		5.2	0.3	44	6.95
TUF-2MH	13		6.0	0.25	47	7.95
TUF-2H	17		6.2	0.22	47	9.95
TUF-5	7	20-1500	6.58	0.40	42	8.95
TUF-5LH	10		6.9	0.27	42	10.95
TUF-5MH	13		7.0	0.25	41	11.95
TUF-5H	17		7.5	0.17	50	13.95
TUF-860	7	860-1050	6.2	0.37	35	8.95
TUF-860LH	10		6.3	0.27	35	10.95
TUF-860MH	13		6.8	0.32	35	11.95
TUF-860H	17		6.8	0.31	38	13.95
TUF-11A	7	1400-1900	6.83	0.30	33	14.95
TUF-11ALH	10		7.0	0.20	36	16.95
TUF-11AMH	13		7.4	0.20	33	17.95
TUF-11AH	17		7.3	0.28	35	19.95

\*To specify surface-mount models, add SM after P/N shown.

■  $\bar{X}$  = Average conversion loss at upper end of midband ( $f_u/2$ )

$\delta$  = Sigma or standard deviation

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers/NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.



## Software for Lumped Element Design

M. Saroja  
ISRO Satellite Centre

This 1993 Software Contest entry is a package of routines for the design of lumped element circuits, including power dividers, matching networks, bandpass filters, attenuators, etc. The package, dubbed RFDSK (RF Designers Software Kit) by the author, is written in GWBASIC and will run on any IBM or compatible PC.

At RF and lower microwave frequencies, transmission line methods (e.g. microstrip) are too large to be practical, and lumped element design is used. References 1-4 were used as the basis for this program, which is intended to help designers construct various passive circuits in this frequency range. As long as the Q of the components used is high enough, circuit performance should approach that of well-made distributed designs.

### Power Divider Example

It is best to illustrate program usage with an example. Let us design a 2-way power divider with the following specifications:

Source impedance: 50 ohms  
Load impedance: 50 ohms  
Frequency range: 9-11 MHz

When the program is run, it first gives an introduction, then displays the Main Menu. Selection 1 is for a power divider. Input values are then entered, or default values (in brackets) can be selected by just pressing ENTER. For example,

source and load defaults are 50 ohms. Now, the program calculates preliminary parameters such as center frequency and bandwidth, then it asks the user to validate the information. If the bandwidth is more than 20 percent, a warning is given. Input parameters can be changed at this stage, if desired.

The program uses the tank capacitance value as the basis for calculation. After entering a value or selecting the default value, the tank inductance is calculated and the design proceeds. If the coupling capacitors are too small, as in the case of very narrow band, high frequency designs, the design procedure can be repeated until a realizable value is achieved.

The choice of either maximally flat or Chebyshev response can be selected by entering a ripple value — zero for maximally flat, or the chosen value for Chebyshev response. Once the value has been entered, the program calculates the individual component values for the corresponding circuits. The program also calculates midband insertion loss based on the unloaded Q of the coil, VSWR, bandwidth, etc.

RFDSK gives element values for both tank and pi type sections with performance and input parameters listed for reference, as shown in Figure 1. The circuit of the prototype power divider is given in Figure 2.

### Conclusion

This program has been used to design lumped element N-way power dividers,

impedance matching networks, Butterworth and Chebyshev filters, and attenuators. Simple data entry allows anyone to use the program, yet it provides sufficient latitude in selected component values to generate realizable designs. The program has been used in the successful design of circuits for HF and VHF radar systems — including RF and IF amplifier matching networks and filters.

This program is available from the RF Design Software Service; see page 73 for ordering information.

### Acknowledgments

The author would like to thank Sri. S. Balasubramanian and Sri. K.V. Janardhanan for their guidance and help.

### References

1. E.J. Wilkinson, "An N-Way Hybrid Power Divider," IRE Trans. Microwave Theory and Tech., Vol. MTT-8, pp. 116-118, Jan. 1960.
2. J.J. Taub and B. Fitzgerald, "A Note on N-Way Hybrid Power Dividers," IEEE Trans. Microwave Theory and Tech., Vol. MTT-12, pp. 260-261, Mar. 1964.
3. J.J. Taub and G.P. Kurpis, "A More General N-Way Hybrid Power Divider," IEEE Trans. Microwave Theory and Tech., Vol. MTT-17, pp. 406-408, Jul. 1969.
4. G.L. Matthei, L. Young and E.M.T. Jones, Microwave Filters, Impedance Matching Networks and Coupling Structures, McGraw-Hill, 1964.

### About the Author

M. Saroja is an engineer in the Payload Checkout Facility Division of the ISRO Satellite Centre, ISRO, Bangalore, PIN : 560017, India.

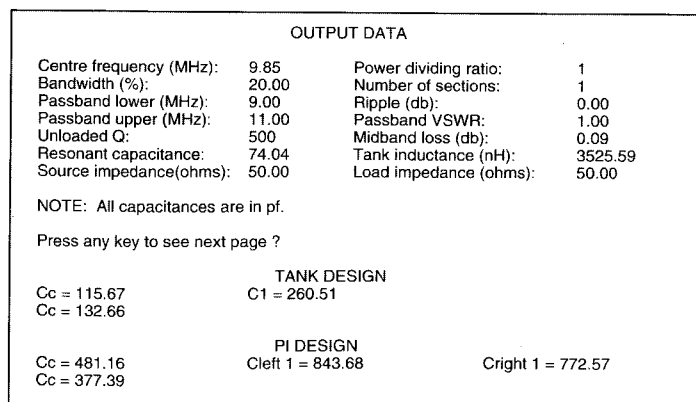


Figure 1. Power divider output screen.

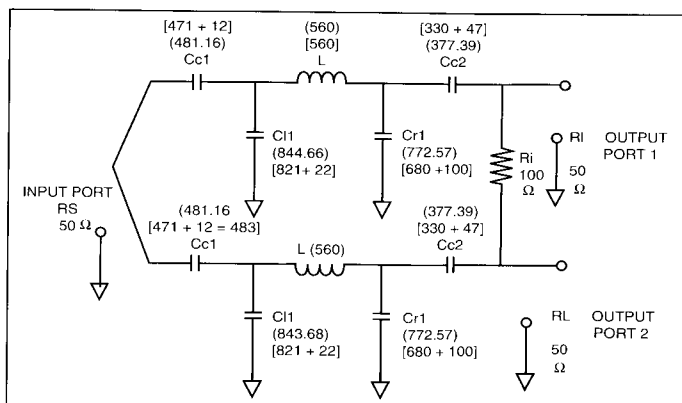


Figure 2. Circuit diagram of power divider example.



# Mini-Spur<sup>TM</sup> 1.0

turns your PC into a Spectrum Analyzer\*



**Spot Spurious Signals Easily...**  
choose the best mixer for your design problems

**\$49<sup>95</sup>**



Introducing Mini-Spur<sup>TM</sup>, the software simulation program for analysis of system spurious responses. Using actual data on Mini-Circuits mixers, spurious signal levels are calculated and then displayed.

Operation is simple. The user defines the input frequency and power level, the program then graphically displays the various outputs including all the spurs (up to  $10 \times LO \pm 10 \times RF$ ) falling within the user-defined IF filter bandwidth. As the user tunes the frequency, the output spectrum scrolls across the screen just like that of a sophisticated spectrum analyzer.

Required hardware; IBM AT or compatible with 640k memory, and EGA or VGA display. Optional, dot matrix, laser printer or plotter.

So maximize design efficiency... use Mini-Spur<sup>TM</sup> only from Mini-Circuits.

\* PC simulates measured results. Does not become a measuring instrument.

**Mini-Circuits<sup>®</sup>**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.

CUSTOM PRODUCT NEEDS... **Let Our Experience Work For You.**

INFO/CARD 47

F-167-Rev. B



## Broadband Transmission Line Transformer Family Matches a Wide Range of Impedances

By Donald A. McClure

The family of broadband transmission line transformers introduced here achieves impedance matching flexibility that is not possible with existing designs, such as the well-known Guanella devices [1]. In 1972, the author prepared a patent disclosure document [2] describing this method, but a patent application was not filed and the information was not made public. After more than twenty years, and with his personal retirement, the author now presents this transmission line transformer family for industry-wide dissemination.

To begin, we should review the example of a typical Guanella transformer shown in Figure 1. A number of transmission lines of equal length and characteristic impedance are all connected in parallel at one end and all in series at the other. These connections provide voltage transformation ratios that are equal to the number of lines used, and impedance transformations that are the squares of those simple integers. The impedance ratios are thus restricted to 4, 9, 16, 25 and so forth, or their inverses. These ratios may be useful, but it is often frustrating that other ratios can not be attained without cascading Guanella structures.

We shall see that Guanella devices constitute a special case of a more general connection scheme that can provide voltage ratios of any rational number without the need to cascade two or more transformers. Rational numbers are defined to be of the form  $m/n$ , where  $m$  and  $n$  are integers. For lack of a better name, it is convenient to term these  $m/n$  devices as RAVOR transmission line transformers — the name being an acronym of RAtional VOltaGe Ratio. In the same vein, devices made in the Guanella connections could be called IVOR transformers for Integer VOltaGe Ratio. The IVOR devices are clearly a special case of the RAVOR family in which either the  $m$  or  $n$  integer is 1. The

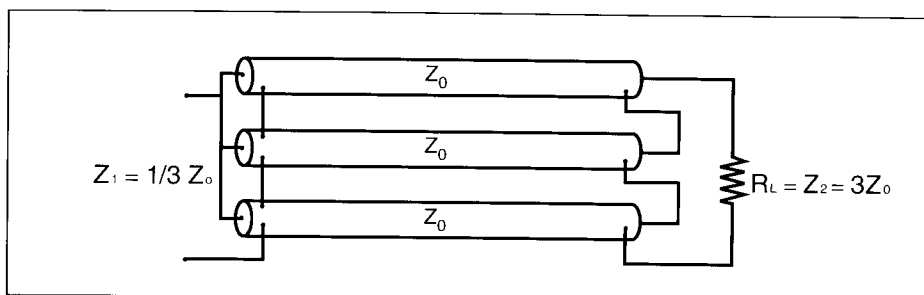


Figure 1. A simple 1/3 voltage ratio Guanella transformer as an example of prior art.

existence of the RAVOR family has generally been overlooked except for a rather recent article [3] in which some connections were derived in an entirely different manner from the method described here.

### Transmission Line Connections

If a group of equal-length transmission lines of equal characteristic impedance are connected at one end in arbitrary combinations of parallel and series, how should the lines be connected at the other end to obtain frequency-independent behavior of the input and output impedances? Calculations of input impedance based upon equality of input and output powers, or simply physical experimentation, will quickly show that the connections at the output end cannot be arbitrary with respect to the input end without the producing mismatches and frequency-selective behavior. With some possible trivial exceptions, broadband behavior can be achieved in only two ways:

1) Output connections are exactly the same as the input connections. This arrangement results in no voltage or impedance transformation and does not constitute a transformer, but it can be useful to achieve a composite cable of some  $Z_0$  other than that of the constituent cables.

2) Output connections are exactly the opposite of the input connections. That is to say, that any transmission lines or

groups of transmission lines which are connected in parallel at one end of the transformer must be connected in series at the other end, and vice versa.

This second method of interconnection describes the family of RAVOR transformers. Figure 2 shows an example of the RAVOR devices, a transformer with a voltage ratio of 5/2, constructed to provide transformation from 50 to 8 ohms. This transformer will operate over decades of frequency with low loss and low standing wave ratio (SWR).

### The General Principle

The series-parallel interchange interconnection of transmission lines having equal length and equal characteristic impedance,  $Z_0$ , causes the driving port and load port impedances,  $Z_1$  and  $Z_2$ , respectively to be related in the following manner (neglecting time delay):

$$Z_1 = KZ_0$$

$$Z_2 = \frac{1}{K} Z_0 = R_{\text{Load}}; \text{ it follows that:}$$

$$Z_1 Z_2 = KZ_0 \frac{1}{K} Z_0 = Z_0^2; \text{ and:}$$

$$Z_0 = \sqrt{Z_1 Z_2}$$

The characteristic impedance of the lines is the geometric mean of the input and load impedances. The coefficient  $K$  is the quotient of two integers, the values of which are determined by the way in which the transmission lines are con-



*Over 80 off-the-shelf models...  
3KHz-1500MHz from **\$1<sup>95</sup>***

**3KHz-1500MHz from \$1<sup>95</sup>**



INFO/CARD 49



TMC

T, TH, TT  
bent lead version  
style KK81

T, TH, T  
bent leaf  
version style X 6

TC

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

CUSTOM PRODUCT NEEDS... ***Let Our Experience Work For You.***



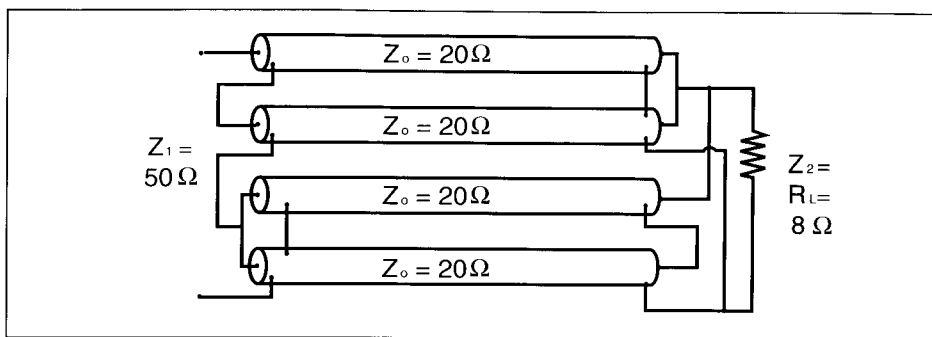


Figure 2. RAVOR transformer providing 50 to 8 ohm transformation.

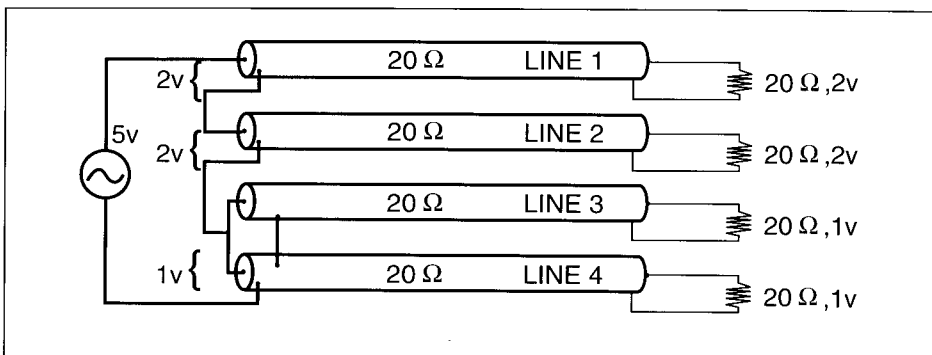


Figure 3. Input connection of Figure 2, with each line terminated in  $Z_o$ , showing voltage distribution.

nected. It is also the voltage transformation ratio of the transformer.

The coefficient  $K$  can always be expressed in the form  $m/n$ , where  $m$  and  $n$  are integers, and is thus a rational number.

### Current-Voltage Duality

A current-voltage duality exists between the two ends of the transformer, resulting from the series-parallel interchange of connections between one end and the other. One way of expressing the duality is that the input current loop equations and the output voltage nodal equations have exactly the same form and coefficients, shown as follows:

$$\text{Input Loop equation: } V_1 - I_1 K Z_o = 0$$

$$\text{Output Nodal equation: } I_2 - V_2 K Y_o = 0$$

$$\text{where: } \begin{aligned} I_1 &= \text{Input current} \\ I_2 &= \text{Load current} \\ Y_o &= 1/Z_o \end{aligned}$$

Similar equations apply to a lossless, conventional transformer of turns ratio  $K$ , which would also exhibit duality.

The duality relationship causes the voltages and currents to be distributed among the termination ends of the lines so that each line operates as though it

were terminated in its characteristic impedance. Thus, the transformers can operate over extreme bandwidths, limited at the high frequencies only by the stray inductances of the end connections. The low frequency limit is determined by the amount of inductive reactance that can be attained along each conductor so that the input and output ends are effectively isolated from one another and common-mode currents are nil.

To illustrate how the series-parallel interchange results in properly terminated lines, Figure 3 depicts the same input connection as in Figure 2, but with the output of each line terminated in a resistance equal to the  $Z_o$  of the line. Five volts of RF is applied to the input. Because lines 1 and 2 each present 2 volts to their respective loads, the loads may be paralleled to yield a composite load of 10 ohms with no effect at the driving end. The currents in the loads of lines 3 and 4 are the same, hence the loads and lines may be respectively series connected to obtain 2 volts across 40 ohms. Now, the 3 and 4 series combination provides 2 volts, as does each of lines 1 and 2. Therefore, the series 3-4 combination may be paralleled with lines 1 and 2 to give a total output of 2 volts. The 40 ohm load of the

3-4 combination acts in parallel with the 10 ohm load of the 1-2 combination to yield a composite load impedance of 8 ohms.

It is apparent from the above discussion that the individual 20 ohm resistors of Figure 3 can be replaced by a single 8 ohm load if the lines are connected as in Figure 2. No change will occur in the input voltage distribution or impedance when the substitution of a single load is made, provided that there is sufficient inductive reactance along each conductor to isolate the voltages at the load end from those at the input end.

### End-to-End Isolation

If 5 volts were applied to the input of the transformer of Figure 2, 2 volts will appear at the output, leaving a 3 Volt drop along the center-conductor of the upper-most cable, which could cause a large, unwanted current to flow. Such currents are reduced to insignificant values by making each conductor have a high inductive reactance throughout the intended frequency range. The low-frequency reactance can be enhanced by winding the lines into individual coils, or by winding them on, or surrounding them by, high permeability materials such as ferrite. For the 2 MHz to 100 MHz range, winding each coaxial cable on a ferrite toroid having an initial permeability of about 125 works well. For proper operation, there should be no magnetic or electric coupling between the transmission lines.

### Impedance Calculations

With confidence that the lines making up the transformers are properly terminated, the driving point impedance may be written by inspection of the input connections. In the case of the connection in Figure 2, writing in general form:

$$Z_1 = 2Z_o + \frac{Z_o}{2} = \frac{5}{2} Z_o ; \text{ therefore:}$$

$$K = \frac{5}{2}$$

The above example illustrates the way in which the ratio  $K = m/n = V_1/V_2$  appears in the impedance equations. A similar inspection of the output end yields:


$$Z_2 = \frac{\frac{Z_o}{2} \cdot 2Z_o}{\frac{Z_o}{2} + 2Z_o} = \frac{Z_o^2}{\frac{5}{2} Z_o}$$




$$= \frac{2}{5} Z_0 = \frac{1}{K} Z_0$$
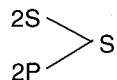
### Connection Notations

There are so many possible transformer configurations that it is convenient to use a system of shorthand notation to describe the connections without sketching the cables and wiring. The device of Figure 2 is fully described, except for impedance levels, by the symbology:



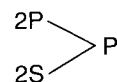which means: two lines are connected in series to form a group; two other lines are paralleled to form a group; then the two groups are connected in series. The opposite end of the transformer is connected in the opposite fashion and need not be described. In this case it is denoted by:



The transformer connections are completely defined by either the input or output end notations above.

Table 1 lists voltage ratios and corresponding connection schemes for values of K with a denominator up to 9. Equivalent ratios (e.g. 2/3 and 4/6) are not duplicated. The author has determined connections for ratios up to a denominator of 13, a total of 57 different voltage ratios. Of these, only 12 can be achieved by a single-stage Guanella transformer, which means the RAVOR principle provides 45 additional ratios to choose from!

Also, all of the transformers of the RAVOR family, including the Guanella types, may be used as baluns (BALanced to UNbalanced converters) because of the necessary isolation from input to output.


While all ratios of the form m/n are theoretically realizable with this class of transformer, there are obviously practical limits to the number of transmission lines that can be used. As of this writing, the author has conducted a systematic search for all the connection possibilities up to and including six lines. Some ratios resulting from the use of more lines have also been found for the purpose of knowing the simplest connection for all of the ratios shown in Table 1. Using six lines, there are 53 different

Voltage Ratio K	Connections	Minimum No. Lines	Voltage Ratio K	Connections	Minimum No. Lines
$\frac{1}{2}$	2P*	2	$\frac{5}{7}$		5
$\frac{1}{3}$	3P*	3	$\frac{6}{7}$		5
$\frac{2}{3}$		3	$\frac{1}{8}$	8P*	8
$\frac{1}{4}$	4P*	4	$\frac{3}{8}$		5
$\frac{3}{4}$		4	$\frac{5}{8}$		5
$\frac{1}{5}$	5P*	5	$\frac{7}{8}$		7
$\frac{2}{5}$		4	$\frac{1}{9}$	9P*	9
$\frac{3}{5}$		4	$\frac{2}{9}$		6
$\frac{4}{5}$		5	$\frac{4}{9}$		6
$\frac{1}{6}$	6P*	6	$\frac{5}{9}$		6
$\frac{5}{6}$		5	$\frac{7}{9}$		6
$\frac{1}{7}$	7P*	7	$\frac{8}{9}$		7
$\frac{2}{7}$		5			
$\frac{3}{7}$		5			
$\frac{4}{7}$		5			


\*Guanella (integer) ratios

**Table 1. Voltage ratio and connection data for RAVOR transformers with fractional ratios through a denominator of 9.**



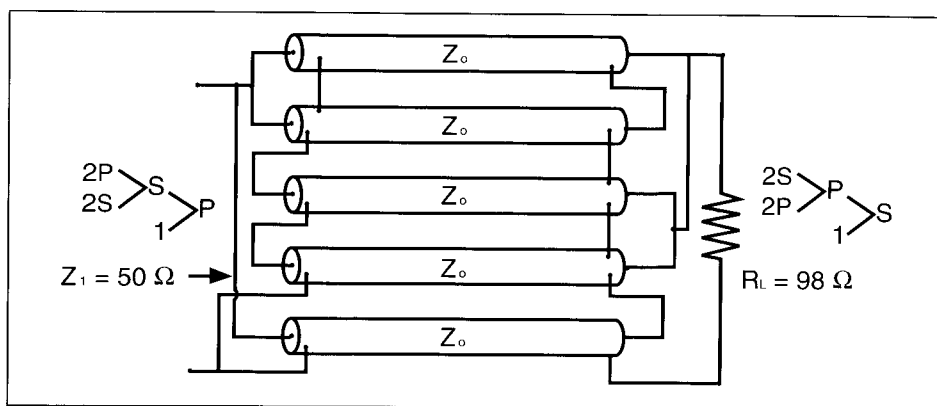

**Figure 4. 5/7 ratio RAVOR configuration approximating a 1:2 impedance transformation ( $Z_0 = 70$  ohms).**

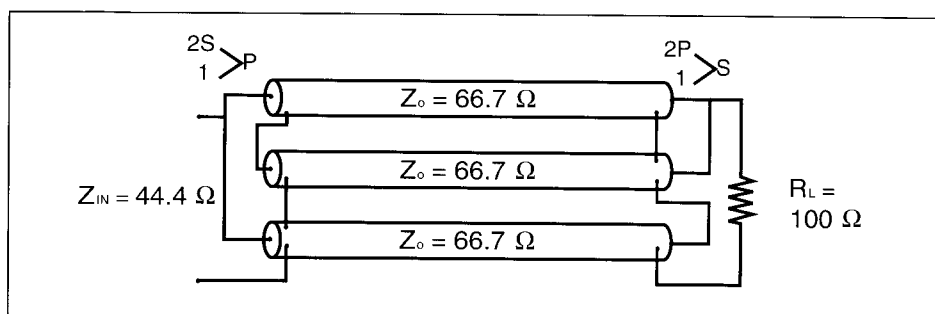

**Figure 5. The 2/3 ratio RAVOR is a simpler but less accurate way to approximate a 1:2 transformation.**

combinations that can be made, not all of them useful. Using seven and eight lines, there are hundreds of connections and corresponding ratios, but to use such a large number of lines and ferrite cores is to reach beyond the limits of practicality.

### Configuration Selection

As an example of the use of Table 1, postulate that it is desired to make a transformer that will provide a 50 ohm to 100 ohm conversion. The voltage ratio,  $K$ , is found to be  $\sqrt{50/100} = 0.707$ . Look through Table 1 to find a ratio that approximates 0.707. The ratio 5/7, which in decimal form is 0.7143, differs from 0.707 by only about 1 percent and is thus an excellent approximation.

Because 5/7 is a ratio of two prime numbers, it is already in its lowest form. Table 1 indicates the connections for the low impedance end of the transformer and five transmission lines are required. The configuration is sketched in Figure 4. The  $Z_0$  of the lines is chosen to be 70 ohms, the geometric mean between 98 and 50 ohms.

A test transformer using the configuration of Figure 4 was constructed using five equal lengths of 50 Ohm cable (RG-

196), each wound on a ferrite toroidal core of Indiana General type Q1 material which has an initial permeability of about 125. The frequency response of the test transformer was essentially flat from 3 to 300 MHz, and the voltage transformation ratio was 5/7, as expected.

For some purposes, a less accurate approximation to a 1/2 impedance ratio than that provided by the five-line configuration of Figure 4 would suffice. Returning to Table 1, it is seen that the simplest structure to approximate the 0.707 voltage ratio is the three-line device which yields a  $K$  of 2/3, or 0.667. The connection is sketched in Figure 5.

If the transformer of Figure 5 were loaded with 100 ohms at the output as shown, and the line  $Z_0$  were chosen to be 66.67 ohms, also as shown, impedance at the input (left) end would be 44.44 ohms. In a 50 ohm system, the transformer would thus introduce an SWR of 1.125:1, which may be a tolerable number.

### Summary

The article describes the theoretical basis for, and the general principles of, a class of broadband RF transmission-

line transformers having voltage transformation ratios of rational form,  $m/n$ , where  $m$  and  $n$  are integers. The described configurations overcome the simple integer transformation ratio limitations of the older Guanella designs which represent a special case of these principles. The theoretical basis of operation is viewed in the light of current-voltage duality due to the series-parallel, parallel-series interchange of connections between the ends.

Design tools are provided in the form of a configuration selection procedure, and a table of ratios and the corresponding connections. These aids enable the reader to determine quickly the required number of transmission lines and the connection scheme to obtain the desired transformation. The table lists 19 rational ratios and their connections, in addition to 8 Guanella integer ratios and connections. Two examples of configuration selection are included.

With regard to synthesis of a transformer configuration, it can be shown that the connections for any ratio can be determined by using a continued fraction expansion, but sometimes connections requiring fewer lines can be found by the use of partial fraction expansions.

*Future articles are planned, covering synthesis, construction and measured performance of RAVOR transformers.*

### Acknowledgement

Many thanks to Dr. Jerry Sevick of Basking Ridge, NJ for his encouragement and useful suggestions. **RF**

### References

1. G. Gaunella, New Method of Impedance Matching in Radio Frequency Circuits, the *Brown Boveri Review*, September 1944, pp. 327-329.
2. Donald A. McClure, "A Family of Broadband Transformers," RCA Corporation patent disclosure document, April 28, 1972, RCA Docket no. 66148. Note: the RCA Patent Operations office decided not to seek patents for the many transformer configurations disclosed.
3. Daniel Myer, "Equal Delay Networks Match Impedances of Wide Bandwidths," *Microwaves & RF*, April 1990, pp. 179-188.

### About the Author

Don McClure is an engineer retired from RCA. He can be reached at 12 W. Azalea Lane, Mt. Laurel, NJ 08054; tel. (609) 778-7328.



## RF Expo West Program and Short Courses Schedule

**Tuesday, March 22**  
**8:30-11:30 a.m.**

**Session A-1:**  
**RF Data Communications I**

*FQPSK, A Modulation that Outperforms Pi/4 DQPSK in Both Radiation Effects and Battery Power Dissipation While Maintaining Equal Capacity*

Hussein Mehdi  
University of California, Davis

*Theory and Development of a Digital Amplitude Modulator*

Timothy P. Hulick  
Acrodyne Industries

*An I-Q Demodulator IC for Compressed Video Applications*

Eric Bausback  
California Eastern Laboratories

**Session A-2: Power Amplifiers I**

*Low Cost Antenna Interface RFIC for Wireless Applications*

Peter S. Bachert  
RF Micro Devices, Inc.

*HF and VHF Linear Power Amplifiers Using SSTs and SLAMs*

Adrian I. Cogan, Kenneth Sooknunan, Lee Max,  
Microwave Technology, Inc.

*Comparative Study of Four Broadband Microwave Amplifier Concepts*

Samuel R. Lauretti, Rui Souza  
CPQD-Telebras/NEC

**Session A-3: Filter Design**

*Dielectric Filter Design*

Tsang-Fu Chang  
Kaimei Electronic Corp.

*Microstrip Techniques and Filter Design*

Raymond S. Pengelly, Raytheon

**Tuesday, March 22**  
**1:30-4:30 p.m.**

**Session B-1: Oscillators**

*SAW Resonator Oscillator Design Utilizing Linear RF Simulation*

Alan R. Northam  
RF Monolithics, Inc.

*Injection Lock*

Mike Black, Texas Instruments

*Oscillator Design for Lowest Phase Noise*

Ulrich L. Rohde, Compact Software

**Session B-2:**  
**Product Design and Manufacturing**

*Fundamentals of Design for Manufacturability*

Radha Setty and Harvey Kaylie  
Mini-Circuits

*Improving Product Design/Development by Identifying Key Customer Values and Product Features*

Bruce A. Murray  
Erbtec Engineering, Inc.

*High Frequency High Bandwidth IF Crystal Filter Designed for Manufacturing*

Jose Miguel Fernandez Gomez  
Tiempo Frecuencia y Electronica, S.A.

**Session B-3: RF Materials**

*A High Power RF Package Using Aluminum Nitride Ceramic*

Dr. Gerald Miller  
Carborundum Microelectronics

*Microwave Based Measurements of a Layered Dielectric Medium*

Dr. Rick Keam  
Industrial Research Ltd.

*Realisation of Microwave Circuit, Components & Antennas Using a New Transmission Medium of Conducting Liquids such as Mercury & Salt Solutions*

Kosta Yogeshwar Prasad  
ISRO Space Applications Centre

**Wednesday, March 23**  
**8:30-11:30 a.m.**

**Session C-1: Data Communications II**

*IF Amplifiers and Quadrature Demodulators for Digital Communication Receivers*

Bill Pratt, RF Micro Devices, Inc.

*An FSK Modulation Data Receiver for 900 MHz Using a Low Cost Silicon Monolithic Integrated Circuit Chip Set*

Harry Swanson, Motorola

### Five Short Courses Offer Formal Training

**Digital Communications and Spread Spectrum** — Dr. Kamilo Feher, instructor. An advanced class for engineers working on wireless personal communications applications. Monday, March 21, 8:00 a.m. to 5:00 p.m.

**Introduction to RF Circuit Design Part I: Fundamental Concepts** — Drs. David Hertling and Robert Feeney, instructors. This entry-level class assumes a BSEE, but little experience. Part I emphasizes passive circuits, transmission line and matching principles. Monday, March 21, 8:00 a.m. to 5:00 p.m.

**Introduction to RF Circuit Design Part II: Active Circuit Design** — Drs. Feeney and Hertling continue with basic design principles. Small-signal and

large-signal amplifier design is the major emphasis. Part I or II may taken alone or together as a two-part course. Tuesday, March 22, 8:00 a.m. to 5:00 p.m.


**RF Filter Design: LC and Distributed Circuits** — HF to Microwaves — Randy Rhea, instructor. Beginner to intermediate class covering all major filter types and methods. Lumped element and microstrip implementation are covered extensively. Wednesday, March 23, 8:00 a.m. to 5:00 p.m.

**Oscillator Design Principles** — Randy Rhea, instructor. Another beginner to intermediate level class, covering the design of oscillator circuits. The instructor's unified approach removes the mystery from oscillator design. Thursday, March 24, 8:00 a.m. to 4:00 p.m.



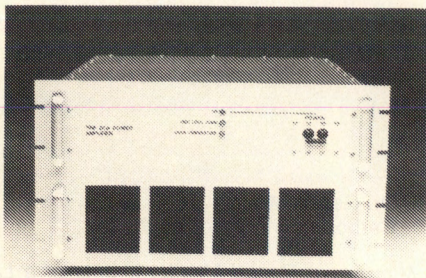
# DESIGN SOLUTIONS FOR THE RF INDUSTRY

The best of RF technology, quality, and design comes from Silicon Valley Power Amplifiers, a leading manufacturer of high-performance amplifiers and components.



## AMPLIFIERS

Part Number	Power Output Watts	Gain dB	Frequency Range MHz
V-1000	1000	60	100-200
U-1000	1000	60	225-450
C-500	500	60	100-500

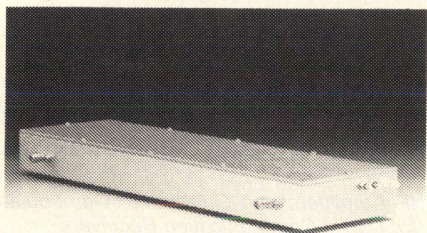

## MODULES

Part Number	Power Output Watts	Gain dB	Frequency Range MHz
10-150-4	4	36	10-150
10-100-25	25	40	10-100
10-100-100	100	40	10-100
80-220-300A	300	60	80-220
220-500-300A	300	60	220-550
100-500-25	25	30	100-500
100-500-100	100	40	100-500
100-500-150	150	10	100-500

This high-quality hardware is backed by:

- Excellent service
- Customized design
- Fast response
- Expert technical support
- In-stock delivery
- Standard/special parts

For a free catalogue describing our complete range of power amplifiers and modules, call 408.986.9700 today!



**Silicon Valley  
POWER  
AMPLIFIERS**

1530 O'Brien Drive Δ Menlo Park, CA 94025  
408.986.9700 Δ Fax 408.986.1438  
INFO/CARD 51

*A Low Power Spread Spectrum CMOS RFIC for Radio Identification Applications*  
John R. Tuttle  
Micron Communications Inc.

### Session C-2: RF Power II

*Linearisation Techniques for RF Amplifiers*  
Dr. P.B. Kenington  
University of Bristol

*Some Improvements on the Feedforward Technique*  
Mauro De Lima Coimbra  
CPQD-Telebras

*Considerations of Using Collector Amplitude Modulation in Class E Power Amplifier With Finite DC-Feed Inductance*  
Mihai Albulet, Sergiu Radu  
Technical University IASI

### Session C-3: RF Components

*RF Circuit Components: Measurements, De-embedding and Equivalent Circuits*  
Les Besser, Besser Associates

*Numerical Simulation of Silicon Hyperabrupt Diodes for VCO and Filter Applications*  
Ricardo Borges, M/A Com

## Wednesday, March 23 1:30-4:30 p.m.

### Session D-1: Wireless Communications

*The Design of UHF and VHF Loop Antennas*  
Dr. Ian J. Dilworth, University of Essex

*Techniques for Open Loop Modulation of a Wideband VCO for DECT*  
Daniel E. Fague  
National Semiconductor Corp.

*A Covert Video Communications System*  
Roger Bracht, Tom Kuckertz  
Los Alamos National Laboratory

### Session D-2: Synthesizers

*Frequency Synthesizer Technology in the Nineties*  
Uri Yaniv, CTI

*NCO - The Next Generation Oscillators*  
T.J. Apren, ISRO-VSSC

### Session D-3: Communications Systems

*LINK 16: Tactical Advantage in the 21st Century*  
Lester E. Polisky, Sentel Inc.

*A Simple Technique for Assessing HF Automatic Link Establishment Radio Interoperability*  
David Wortendyke  
U.S. Department of Commerce

*The Art of CW Rejection in ESM Receivers*  
Sherman R. Vincent, Raytheon

## Thursday, March 24 8:30-11:30 a.m.

### Session E-1: Data Communications III

*Multi-Mode Radio Transceiver Design*  
Dr. A. Bateman, University of Bristol

*Design an Infrared Data Link Using an Integrated FSK Transceiver*  
Gaylene Phetteplace, Motorola

*Data Communications by Means of Reflective Transmission*  
Claude A. Sharpe, Texas Instruments

### Session E-2: Circuit Design Methods

*Ground Current Control in RF and High Speed Digital Circuits*  
Earl McCune  
RF Communications Consulting

*Design Microstrip Components With a Dielectric Cover Without Buying Additional Software*  
Denis Jaisson, S.A.T.

*Circuit Theory Approach Versus Field Theory Approach in Shielding Evaluation*  
Sergiu Radu, Mihai Albulet  
Technical University IASI

### Session E-3: Integrated Circuit Solutions

*Digital Processor Performance and Integration*  
Mark Gill, Analog Devices

*RF/IF Processes and Circuits for Wireless Communications*  
Bob Clark, Analog Devices

*Digital Receivers and DDS for Base Stations*  
Scott Berhorst, Analog Devices

**To register for RF Expo West,  
or, to get more information, call:  
800-828-0420.**



# The RF Coupler: A 20th Century Workhorse

By Ann Marie Trudeau  
Assistant Editor

RF couplers are considered a mature product, so RF designers probably haven't expected any modifications for what is now considered a basic tool. Nearly everything that could have been done to a coupler has been done. But now, designers are having to look at this taken-for-granted item. The reason for this turnaround is that the marketplace is being inundated by cable TV, cellular, the future personal communication network, and the magnetic resonance imaging (MRI) industries. RF designers have had to take another look at couplers to see what can be changed so that the industry can respond to the market demands for smaller, more consistent and cheaper couplers.

### Cellular Market

The cellular industry affects companies which in turn have changed their manufacturing techniques to meet the customer's need for low cost products. Automatic testing of base stations is a focus of the RF industry and companies are responding in various ways.

Arthur Butts of RLC Electronics said that the worldwide market for RF couplers could easily be \$50 million. Presently their clients want high end applications for the cellular industry, primarily for the systems which involve cellular base stations. Butts said that at least one company selected RLC directional couplers because of their maximally flat 32 dB coupling response in processing the signal.

Mini-Circuits' Director of Engineering Radha Setty said that customers can't afford to tune components during high-speed volume production and this has led to their innovative approach of putting what would normally be considered a customized coupler on the shelf as a standard part. The savings are passed on to the customer.

"That means that we have to produce components that are surface mount, smaller, and provide very repeatable performances," he said. Setty felt that the cellular RF coupler market will lend itself more to surface mount, high per-

formance couplers.

They have also responded to higher power in a smaller size by designing the coupler so it didn't have to dissipate any heat. Setty said that Mini-Circuits is researching RF magnetics to get more accurately repeatable performances.

Jerry Moore, director of marketing for Sage Laboratories, said that Sage manufactures caseless hybrids called Wireline™ and Wirepac™ for the cellular industry. He's aware that surface mounts do reduce cost but he had some reservations. "There are some applications where surface mounts don't give you the best trade off," Moore said.

### MRI Use Grows

But, to show that companies are diversifying their coupler markets Sage Laboratories also uses Wireline couplers in Magnetic Resonating Imagery (MRI). The MRI creates detailed images of the human body, requiring very high magnetic fields to do so. This creates problems for the RF connector because most low frequency couplers have ferrites, or magnetic material, in them. "So they came to us and we made a coupler that they can use that does not have any ferrite material in it," Moore said. "It solves their problem because it can be used in these high magnetic fields. This is an interesting aspect of our product. The coupler is 70" long, but because it looks like a piece of cable we coil it tightly so that it takes up only six to eight inches of space," he said.

Another company totally agrees with the effect of MRI on the trade. "Up and coming are the devices for these scanner machines," Bob Wells, lead engineer of Lorch Electronics, said. "That's a major chunk of a new market."

Wells said that they had to go to packaging that was essentially non-magnetic except for the pin contacts and they are brass plated so that there wasn't a magnetic contact.

### A Need

No single testing measuring or instrument can fit all applications, so there will

always be a need for RF couplers. According to John Yochum, contract manager for Bird Electronics, "I think there is always going to be a market place for RF couplers, the reason being that until suppliers like us can produce products that would meet everybody's needs then there wouldn't be a need for an RF coupler." Bird, well known throughout the industry, produces the couplers that are used in their wattmeters.

### Interesting Applications

Lossy coax is used in tunnels and subways in Europe and is made with slots in it so it radiates a little bit, according to Glenn Werlau of Werlatone Inc. Used on ships or in confined spaces where a radio signal can't radiate or be piped around using an extremely wide bandwidth. Werlatone sells RF couplers that split off the power to different compartments or levels.

A company that has original coupler patents from the 1950s certainly has seen changes from those days. Tony Ramsden, Vice-President of Marketing says that Merrimac Industries responds to a stronger market because more signals are monitored in radar systems, communication's transmitters and automatic test systems. "We got a large corner of that market and it's used in the automatic measurement of chips which are still in the wafer form," he said.

Also, the military still has requirements that have to be met and John Duncan of Tele-Tech said that military radio applications are the company's biggest RF coupler demand but sees that the only advancement for RF couplers would be an improvement in materials for stripline couplers. "A coupler is as old as a dinosaur," Duncan said.

### RF Summary

However, unlike the dinosaur the RF coupler is not extinct but has turned into a modern day workhorse. Plodding, steady, unseen for the most part, but doing its job because the industry is counting on it. **RF**



# RF design MARKETPLACE

**WHEN YOU ARE READY TO BUY-SELL-TRADE CALL RF DESIGN MARKETPLACE**  
Increase your REVENUES with RF Design Marketplace advertising! Over 40,000 prospects read and buy from this section each month. To reach this sophisticated, targeted market call Michael Applegate at (404) 618-0217 today.

## RF career opportunities

**RF/MICROWAVE**  **MIDWEST** **WIRELESS**  
WORK WITH AN RF-ENGINEER IN YOUR MOVE TO THE MIDWEST!

My clients need top-notch RF Design Engineers and Managers, 3 to 10+ years experience, HF to 3.0 GHz, Receivers, Transmitters, Power Amplifiers, Synthesizers, Spread Spectrum, ASIC/MMIC Design, Modems, Communications DSP.

**DON GALLAGHER MSEE**

Phone: 319-895-8042 Fax: 319-895-6455  
1145 LINN RIDGE RD. MT. VERNON, IA 52314

10 YEARS OF RF-ENGINEERING, MANAGEMENT, AND PLACEMENT OF ENGINEERS

INFO/CARD 60

**RF DESIGN MARKETPLACE**  
**Get In • It Works**  
**404-618-0217**

### SUNBELT OPPORTUNITIES

Several of our growing commercial major electronic companies located in the southeast have asked us to identify candidates in the mid-level experience range.

- 1) BSEE - to design analog/RF circuitry for receiver/transmitters in 300-900 MHTZ - PSpice
- 2) BSEE - RF Test Engineer - 50 MHTZ to 1 GHTZ. Spectrum analyzers, net work analyzers; HP Basic
- 3) BSEE - High power amplifier design engineer - Class AB 100-200 watts; 800-900 MHTZ
- 4) BSEE - Power supply design engineer - switch mode; power factor correction
- 5) MSEE - To design high efficiency power MMICS for military systems. L-Band thru KU Band (2-18 GHz). Knowledge of non-linear modeling.

**Fortune**

**PERSONNEL CONSULTANTS OF RALEIGH, INC.**  
P.O. Box 98388R • Raleigh, NC 27624-8388  
Phone: 919-848-9929 • Fax: 919-848-1062  
**Stan Deckelbaum**

INFO/CARD 61

**...YOUR CAREER**

**Cellular Engineers:** Design/develop RF and analog circuits for high capacity cellular systems. Requires minimum of 2 years experience in any of the following: DSP, ASIC Design, Cae Development, Digital Modulation, Digital Mobile Communications, Channel Equalizers, Transmitter-Receiver Synthesizer or Audio Design, Digital Signal Processing.

**Regional Sales Manager:** Responsible for sales, promotion and technical support within a specified geographical region with the support of field sales representatives. Identifies new opportunities and coordinates efforts to secure contracts. Responsible for ensuring that field sales representatives are satisfying the customer's needs and providing technical training. This position requires a BS degree in electrical engineering with 1-3 years experience in the RF components industry. This person could be a design engineer with a desire to begin a sales career.

**Product Marketing Manager:** Our client, a well known microwave firm, seeks an experienced professional to perform classical marketing functions for a product line: i.e., develop short and long term business plan, determine marketplace, etc. Excellent compensation package along with executive benefits.

**Consumer Electronics Engineer:** Design and development of microwave common waveguide horn antennas, X and Ka-band Gunn Diode oscillators, mixers, VCO's filters/receiver front ends. BSEE

**Filter Design Engineer:** B.S. (prefer M.S. or Ph.D.). Minimum 3 years experience in the filter design and development of Broad Band, comb-line, strip line, interdigital, low pass and high pass filters, multiplexers, diode switches, (phase shifters), attenuators and microwave sub-systems desirable.

**RFIC Design:** MS or PhD in Electrical Engineering with minimum 5 years related experience preferred. The candidate should have a good knowledge and experience in Linear Bipolar High Frequency IC design and measurement techniques in design IC's like Amplifiers, Mixers, Oscillators, VCO's, Prescalers, Synthesizers, Limiting Amplifiers, etc. operating up to 2 GHz in Bipolar or BiCMOS technologies.

**MMIC Design Engineer:** Develop L/S band GaAs MMIC power amplifiers for commercial wireless communications. Requires: M.S. or BSEE, +2 years experience with GaAs MMIC design, simulation, packaging and test.

**Design Engineer:** Responsible for the design and development of 900 MHz wireless consumer electronic products. Designed and developed AM/FM/FSK transmitters/receivers in 902-925 MHz frequency range. Hands-on experience on HF/VHF/UHF systems and sub-systems which includes LNAs, medium power amplifiers, down converters, saw and coaxial resonator oscillators, VCOs, AM/FM IF systems, RF modulators/demodulators, PLLs & Audio video circuits.

**MICRO COMMUNICATIONS EXECUTIVE SEARCH**  
871 Turnpike St. • North Andover, MA 08145  
We specialize in the placement of communications both nationally and internationally.  
FOR THESE AND OTHER OPENINGS  
CALL COLLECT: TEL: 508-685-2272 FAX: 508-794-5627

INFO/CARD 62

## Advertiser Index

ADVERTISER	PAGE #	ADVERTISER	PAGE #
Accutest Instruments	46	Kalmus Engineering	9
Ameritron/MFJ Enterprises	39	Kay Elemetrics Corp.	43
Amplifier Research	10	Locus, Inc.	71
Analog & RF Models	71	M/A COM	78
Axonon Corp.	71	Micro Communications Executive Search	70
Arrowsmith Shelburne, Inc.	36	Milcom International	21
Cal Crystal Lab, Inc.	71	Mini-Circuits	4-5, 49, 59, 61, 63
California Eastern Labs	29	Murata Electronics North America, Inc.	47
Coilcraft	39	Nova RF Systems, Inc.	71
Compact Software	44-45	Oscillatek	50
Comtronix Ssystems, Inc.	71	Penstock, Inc.	19
DGS Associates, Inc.	35	Philips Semiconductors	72
Eagle	41	Power Systems Technology, Inc.	77
Eagleware	6	QUALCOMM, Inc.	20
E.F. Johnson Components	41	Raltron Electronics Corp.	42
Elanix, Inc.	32	Ramsey Electronics	72
Electro Dynamics Crystal Corp.	73	Repco, Inc.	20
Elisra Electronics Systems	25	Richardson Electronics Corp.	11, 13
Emhiser Research	16	Sciteq	33
Fortune	70	Silicon Valley Power Amplifiers	68
Gallagher & Associates	70	Sprague Goodman Electronics, Inc.	17
Giga-tronics, Inc.	14-15	ST Olektron Corp.	37
Henry Radio	46	Steward Manufacturing Co.	31
Hewlett-Packard/Sig. Ana. Div.	26-27	Synergy Microwave Corp.	2
IFR Systems, Inc.	3	Temex Electronics	42
International Crystal Mfg. Co., Inc.	43	Tesoft, Inc.	23
JFW Industries, Inc.	12	TTE, Inc.	35
K.S. Electronics	72	Werlatone, Inc.	8



# RF career opportunities



**AXONN CORP.** is the leading supplier of high performance, low cost, embedded spread spectrum technology. Axonn's Fortune 500 customers integrate our SW and HW designs into an impressive array of innovative, very high volume applications. Our designers work

hand-in-hand with engineers worldwide to create future product lines. Axonn continually researches new, patentable RF communication techniques. If you want challenge, variety, design creativity and the growth available in a smaller company, call or FAX your resume.

## SENIOR & STAFF RF DESIGN ENGINEERS

Hands-on design experience required with frequency synthesizers, receiver design, transmitter design and 900 to 2400 MHz. Must be proficient with RF modeling software such as Touchstone or Eagleware and familiar with surface mount. 5 to 10 years experience required for Senior position.

Phone: (504) 282-8119 Fax: (504) 282-0999

INFO/CARD 63

## Interested in placing an ad in RF DESIGN MARKETPLACE?

### Contact:

Michael Applegate  
6151 Powers Ferry Rd. N.W.  
Atlanta, GA 30339  
Phone: (404) 618-0217  
Fax: (404) 618-0342

## RF products

### ANALOG & RF MODELS

SPICE models from DC to 10 GHz  
Full non-linear models including:  
RF pin diodes, class C, opto, & logic.  
We also do measurements and consulting.  
Give us a call at (602) 575-5323

INFO/CARD 64

## RF products & services

### O.E.M. Electronic Products

- Computerized • RF Systems
- Spread Spectrum Communications
- Custom, RF/Digital ASICs • 14 Year History
- Harris and Hitachi Authorized Design Center
- Complete, Fulltime Professional Staff

by: **LOCUS, Inc**

1842 Hoffman St., Madison, WI 53704  
TEL 608/244-0500 FAX 608/244-0528

INFO/CARD 65

### COMTRONIX SYSTEMS, INC.

#### CUSTOMIZED

SOLID STATE • HIGH POWERED • VHF/UHF

## AMPLIFIERS

DESIGNED AND BUILT TO YOUR SPECIFICATIONS

UP TO 200 WATTS  
HIGHEST QUALITY/BEST PRICES

CALL OR SEND FOR INFORMATION TEL 413/785-1313 FAX 413/739-1352

INFO/CARD 66

### NOVA RF Systems, Inc.

#### The Complete RF/Microwave Solution



- RF/Microwave Systems
- Custom Design/Consulting
- Simulation Software
- Synthesizers (PLL/DDS)
- Complete Lab/Machine Shop
- TDMA/CDMA/Spread Spectrum

**International Inquiries Welcome**  
1740 Pine Valley Dr. Vienna, VA 22182  
(703) 255-2352

INFO/CARD 67

### CAL CRYSTAL LAB, INC. • COMCLOCK, INC.

Need Clock Oscillators or Crystals? Call 1-800-333-9825 • 714-991-1580

Quartz Crystals 50Khz to 200Mhz

TTL Clock Oscillators 250Khz to 70Mhz

HCMOS Clock Oscillators 3.5Mhz to 50Mhz


Tri-State, Half Size and Surface Mount also available on request

**Fast Service - 3 weeks or less**  
**Special frequencies our specialty**

1142 N. Gilbert, Anaheim, CA 92801 • FAX 714-491-9825

INFO/CARD 68



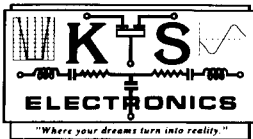

- STD. 5 AND 10 MHZ OCXO
- TCXO • VCXO • TC-VCXO
- VCO's • CLOCK OSCILLATORS
- CUSTOMIZED CRYSTAL FILTERS  
STD. 10.7 MHZ, 21.4 MHZ and 45 MHZ
- L/C FILTERS


Call or Fax requirements.

16406 N. Cave Creek Rd. #5  
Phoenix, AZ 85032-2919  
Phone & Fax (602) 971-3301

INFO/CARD 69
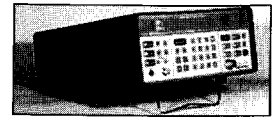
## RSG-10 SIGNAL GENERATOR

The \$2495 profit generator  
Quality crafted in the USA



Finally, a synthesized signal generator that's designed to help you generate more than just signals. The Ramsey RSG-10, is the signal generator you can afford, the signal generator that's designed to do what a signal generator is meant to do- provide a very stable, accurate, easy to control signal from 100 KHz to 1.0 Ghz. For the price, you wouldn't expect any more. But, there is more to the RSG-10. An intelligent microprocessor controlled/programmable memory, for example, can store up to 20 of your most commonly used test set-ups. And unlike other units, just one touch of the memory exchange button is all it takes to quickly shift from one test set-up to another. You get more work done, easier and faster.

At \$2495, the Ramsey RSG-10 is your profit generator.



**RAMSEY ELECTRONICS**  
793 CANNING PARKWAY, VICTOR, NY 14584  
Fax: (716) 924-4555  
TELEX: 466735 RAMSEY CI



ORDER DIRECT—CALL 1-800-446-2295

INFO/CARD 70

## RF Design Industry Marketplace

### Get In • It Works

# 404-618-0217

## WHERE COMMUNICATION MEETS INNOVATION

It's right here at Philips Semiconductors. Our RF and Data Communications products are truly cutting-edge, and we have the resources and dedication to keep the innovations right on schedule—which is to say, ahead of their time. The ideas generated here are truly improving people's lives, from cellular telephone breakthroughs to the latest networking advancements. So if you're looking for an exciting environment where communication meets innovation, join Philips Semiconductors in one of the following opportunities.

### SENIOR RF CIRCUIT DESIGN ENGINEERS

Primary responsibilities include product definition, circuit design and production release of integrated circuits for the RF communications market. In addition to a MS/PhD in EE, your skill set should include knowledge in linear bipolar high frequency IC design and measurement techniques and excellent communication and project leadership skills.

### SENIOR TEST ENGINEERS

You will define and develop test plans and strategies for mixed signal products, generate and develop ATE hardware/software, debug new silicon, and work closely with the new product introduction team. A background with RF and SynchroMaster is a plus.

### RF BASEBAND/MODEM ENGINEER

Design and debugging of baseband modulator/demodulator and radio control circuitry on board level wireless data products is your primary focus. This will involve implementation of wireless data modem circuits using Philips IC technology and integration of a complete solution in a team environment. Experience in modem and digital modulator/demodulator design is essential; knowledge of cellular or wireless LANs is a plus.

### PRODUCT ENGINEER

Responsibilities include characterization and yield analysis for new RF products and sustaining products released in full production to include cost reduction activities. RF expertise is highly desirable.

### RF DESIGNER

Primary responsibility will include RF systems and circuit design and debugging on board level wireless data products to include implementation of transmitter and receiver circuits using Philips RF IC technology. You need experience in UHF/Microwave circuit design. Knowledge of cellular or wireless LAN design and FCC type acceptance is a plus.

*Unless otherwise indicated, the above positions require a BS/MSEE or equivalent and a minimum of 3-5 years of related experience.*

Philips Semiconductors offers competitive compensation and a comprehensive benefits package. Please send your resume to: Philips Semiconductors, Staffing Department RFD, MS 07, 811 East Arques Ave., Sunnyvale, CA 94088-3409, or fax to (408) 991-2656. We believe in maintaining a safe work environment for all employees and require pre-employment drug and alcohol testing. Philips Semiconductors is a division of Philips Electronics North America Corporation, and an Equal Opportunity Employer. Principals only, no phone calls, please.

**Philips  
Semiconductors**



# PHILIPS

INFO/CARD 71



# RF software

## Spectrum Sharing Software

Comsearch introduces the third generation of their spectrum sharing software. The UNIX®-based software allows potential bidders on PCS spectrum to select a PCS technology, define a range of PCS technical parameters and thus identify areas in any market where spectrum is limited. The software incorporates both demographic analysis and databases containing data on every type of antenna and radio used in the 1.9 and 2.1 GHz bands today.

**Comsearch**  
**INFO/CARD #196**

## Radio Modem OS

An operating system for radio modems features an Adaptive Dynamic Access Protocol (ADAP), and a novel power conservation feature. TurboLink 2.2 from Monicor Electronic Group extends portable modem battery charge by as much as 65%. Its ADAP drops inactive nodes from the network poll cycle, increasing data throughput and access time. In addition, TurboLink 2.2 extends the maximum number of portable network modems from 49 up to 99. Price is quoted at \$40 per portable unit plus a nominal labor charge for upgrades performed by the factory.

**Monicor Electronic Corp.**  
**INFO/CARD #197**

## New SPICE Models

Comlinear's latest library of SPICE models includes their CLC522 wideband variable-gain amplifier, the CLC532 high-speed 2:1 analog multiplier, and the new ultra-low noise, wideband op amp, the CLC425. Software release MMD.04 is supplied without charge on a 5.25 inch IBM PC-compatible disk.

**Comlinear Corp.**  
**INFO/CARD #198**

## Power Meter Calibration

System IIA from Lucas Weinschel allows a user to perform automatic calibration and transfer of calibration factors for the most commonly used power sensors and power meters. Both analog and digital power meters can be calibrated with or without the IEEE-488 bus options. Typically, a 10 MHz to 18 GHz power sensor can be calibrated at all standard NIST calibration frequencies in less than five minutes. The software runs on both the HP-9000 Measurement Controller and IBM compatibles with IEEE-488 bus interface.

**Lucas Weinschel**  
**INFO/CARD #199**

## Expanded Design Family

Release 6.0 of MicroSim's Design Center family of products includes an analog, small-circuit simulator, which runs in extended DOS memory. The program simulates approximately 100 transistors, and requires a minimum of 1 Mb of extended memory. Cost is \$1495 and includes "Probe", a mid-analysis waveform analysis tool.

**MicroSim Corp.**  
**INFO/CARD #200**

# RF Design Software Service

Programs from RF Design, provided on disk for your convenience

## This Month's Program — Disk RFD-0294

"Software for Lumped Element Design" by M. Saroja. This program helps design power dividers for equal or unequal impedance loads, impedance matching networks, bandpass filters and attenuators, all using lumped elements (resistors, capacitors, inductors). (The program is written in GWBASIC (not compiled), and will run on virtually any MS-DOS compatible computer).

## January programs — Disk RFD-0194

"Programs Help Design Vacuum Tube Amplifier Output Circuits" by Thomas Crawford. Programs in this set are designed to compute the output matching network component values for Class AB1, AB2, B and C power amplifiers. L, Pi and Pi-L network programs are included. (Written in GW Basic, compiled versions and source code included)

## SPECIAL OFFER!

### RF Design Editorial Index: 1978-1993

A listing of all articles published in the 15-year history of RF Design, sorted by topic, including title, author, issue and page number. This special package includes a hard-copy listing, plus a text file on disk, ready to be loaded into your favorite word processing program for sorting and browsing — provided in IBM or Macintosh format (specify). Postpaid — shipment by First Class or Air Mail.

**All at a special price of just \$12.00! (\$15.00 Foreign)**  
**Order #RFD-INDEX**

Each month's disk of programs.....\$15.00 each.....postpaid to U.S. and Canada  
(other foreign add \$8.00 per order)

Order by mail or by telephone at (303) 770-4709. You may reach an answering machine, but your call will be returned as soon as possible.

Payment may be by check, money order, VISA, Master Card or American Express. All orders under \$100 and all foreign orders (outside U.S. and Canada) must be prepaid. Foreign payment must be either by charge or by a check drawn on a bank located in the U.S.

**RF Design Software Service**  
**P.O. Box 3702**  
**Littleton, Colorado 80161-3702**  
**303-770-4709**

All prices and terms subject to change without notice



## FREQUENCY PRODUCTS

### ELECTRO DYNAMICS CRYSTAL CORP.

#### Crystals

- Microprocessor
- Military Spec/QPL
- Communication
- Custom Crystals

#### Oscillators

- Hybrid Clock
- TCXO
- VCXO
- Custom Oscillators

**9075 Cody Overland Park KS 66214**  
**Phone (800) EDC-XTAL Fax (913) 888-1260**



ENGINEERING  
PROJECT & DESIGN ENGINEERS

## Exciting Developments In Broadband Technologies.

GENERAL INSTRUMENT, INC. is known for excellence in the design and development of broadband technologies for the Cable Television industry...and for the creativity, hard work and foresight of our employees. We are looking for skilled Engineers interested in developing the next generation of two way, digital cable systems, interactive video, television/telephony interface and a variety of other new and exciting products.

### SENIOR PROJECT ENGINEER

We seek an individual with 10 years of experience in project management and a BS Degree or the equivalent. A Master's Degree would be helpful. You will work in the area of signal processing to include RF and DSP, therefore exposure to microprocessors and CATV would be desirable.

### SENIOR DESIGN ENGINEER

We seek someone with experience in broadband RF circuit design who possesses a familiarity with low noise, linear RF amplifier and passive filter design with circuit techniques up to 1 GHz.

If creating innovative cable television and broadband products excites you, consider joining us. We offer a competitive compensation package and a full range of benefits. Please forward your resume, specifying position applying for, to: Ed Zakrzewski, Employment Manager, Dept. RFD, General Instrument Corp., P.O. Box 668, Hatboro, PA 19040. An Equal Opportunity Employer M/F/D/V

**GI General Instrument**

*Where Innovation Is A Tradition*  
INFO/CARD 53

## RF companies

### Companies and institutions mentioned in this issue's editorial pages


Alpha Industries	40	Georgia Inst. of Technology	12	Motorola	18
AML Inc.	42	Harris Farinon	18	National Association of Broadcasters	17, 18
Analog Devices	20	Harris Semiconductor	22	National Inst. of Standards and Tech.	18
Applied Science and Technology	18	Hewlett-Packard Co.	40	NEC	24
ASIC & EDA	22	Hybrid-Tek	46	Newbridge Networks	20
AT&T Microelectronics	22	IEE Conference Services	17	Northeast Consortium for Engr. Ed.	12
AT&T Network Systems	20	IEEE EMC Santa Clara Valley	17	Norsal Industries	41
Automated Systems Inc.	20	Intenational Telecommunicaitons Union	18	Oak Frequency Control Group	40
Aware, Inc.	20	Intusoft	18	Philips Semiconductors	40, 42
Bipolarics	22	JFW Industries	41	Polytechnic University	17
Bird Electronics	69	Johnstech	18	Power Systems Technology	43
Cadence Design Systems	20, 22	K&L Microwave	46	Raytheon	22
California Eastern Laboratories	24	KW Microwave	41	RF Power Components	18
CEI-Europe/Elsevier	12	LBA Technology	18	RLC Electronics	69
Comlinear Corp.	73	Learning Tree International	12	Sage Laboratories	69
Comsearch	73	Loral Microwave - Narda	41	SEMATECH	18
DAB Symposium '94	17	Lorch Electronics	69	Siliconix	41
Daico Industries	41	Lucas Weinschel	46, 73	Stanford Telecom	22
Delfin Systems, Maxim Signal Prod. Div.	40	M/A-COM	33	Superconductor Technologies	20
EEsof (Hewlett-Packard)	8, 24	Marconi Instruments	43	Telecommunications Industry Assoc.	18
Electronics Industry Association	18	Maury Microwave	43	Tele-Tech	69
Filtronetics	46	MCC Panasonic	34	TESOFT	34
Geleco Electronics	18	Merrimac Industries	69	University Consortium for Continuing Ed.	12
		MicroSim	73	Werlatone	69
		Microwave Power Devices	42	Westell, Inc.	20
		Mini-Circuits	46, 69	Western Microwave	46
		Monicor Electronic Corp.	73	Z Domain Technologies	12


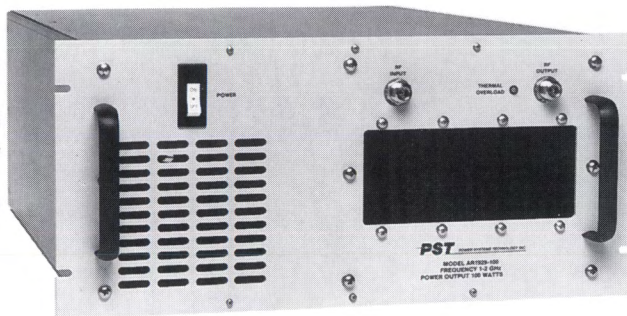
# 100 WATTS 1-2 GHz BANDWIDTH

**Class A Linear Power Amplifiers For Advanced Performance  
Plus Super Solid State Reliability: 30,000 Hrs. MTBF**

- Modular Maintainability
  - Reduced Spares Inventory
  - IEEE 488 Bus (option)



- Automatic Circuit Protection
- Built-In Thermal Protection

These new generation Series AR rack-mount instruments are truly the state-of-the-art in Class A linear power amplifiers for RF/microwave applications. The Model AR1929-100, for example, delivers 100 watts over an instantaneous bandwidth of 1-2GHz. Design and performance features include excellent linearity, wide dynamic range and a 50dB gain rating. Other AR models offer power outputs from 2 to 100 watts and frequency ranges from 1-500MHz to 1-2GHz. All models include a built-in power supply, forced-air cooling, and completely modularized design for maximum maintainability – common, pre-aligned spare modules allow easy field replacement plus reduced spares inventory. They are ideal TWT replacements, for applications such as EMI/RFI susceptibility testing, frequency-agile multi-carrier ECM/EW jammers, fast rise time pulse amplifiers, and broadband sweep generator boosters.

Write or call for complete tech information – ask for Product Data 1010B – or to inquire about any of our other product areas: Class AB, C, narrow band and pulsed; powers up to 10KW; frequencies up to 4,000MHz.

# PST

A SUBSIDIARY OF COMTECH  
TELECOMMUNICATIONS CORP.

**POWER SYSTEMS TECHNOLOGY INC.**

105 BAYLIS ROAD, MELVILLE, NY 11747  
TEL. 516-777-8900 • FAX 516-777-8877



# When you're out in front, chances are you'll get there first.



Unique  
HMIC™  
silicon  
process.

From cellular base stations to automotive sensors, from the global positioning system to pen-based computers, you'll find M/A-COM's components, subsystems and systems wherever you find today's most advanced RF and microwave technology.

Since we combine technological expertise with high-volume, low-cost manufacturing capabilities, M/A-COM is the partner of choice for the world's most competitive companies.

## **We cover the spectrum.**

Our semiconductor-based design, manufacturing and packaging technologies offer customers unequalled advantages.

We use predictive, physics-based, computer-integrated modeling and design methods to reduce development risk and expense. And link on-wafer testing with continuous flow manufacturing to cut production costs and enhance performance.

As a result, our products surpass both market and budget requirements.

## **We speak digital.**


We are creating the seamless communications and transportation networks of tomorrow.

As applications for wireless technology increase, the interface


M/A-COM's GaAs technology  
sets the industry standard.

INFO/CARD 55

between microwave and digital technology becomes increasingly important. Our high-speed digital signal processing capabilities transparently link microwave technology to the digital world. Our expertise in areas such as miniaturization, voice and data compression, and end-to-end systems modeling and simulation is creating the integrated, multifunction solutions which will be the standards of the wireless industry.

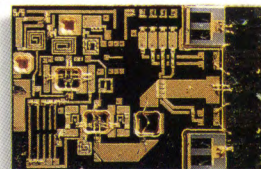

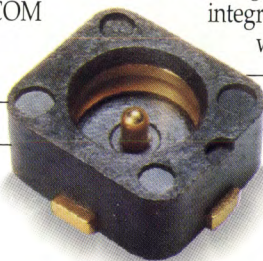Switch,  
Limiter  
and LNA  
integrated  
into a  
common  
medium.



Microwave coaxial  
surface mount connector.

## **Choose your partner.**

The most important technological choices are made in the earliest stages of the product development process, and demand an understanding and awareness of each system and its technological needs. This is when M/A-COM's strengths and experience are of greatest benefit. Our expertise, our ability to adapt to the changing

needs of both commercial and government industries, and our commitment to our customers make us your best choice as a technology partner. A partner you can count on to help you get to your destination first.

To learn more, call us at 1-800-366-2266. In Europe, +44 (0344) 869 595. In Asia, +81 (03) 3226-1671.

HMIC is a trademark of M/A-COM, Inc.

