

# WHATEVER HAPPENED TO AM RADIO?

# EL Radio Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

## BUILD THIS LEAD-VOCAL ZAPPER




Remove the vocal tracks  
from stereo recordings

## BUILD R-E's DIGITAL DASHBOARD

Add a high-tech look to any car

## DATA DISKS

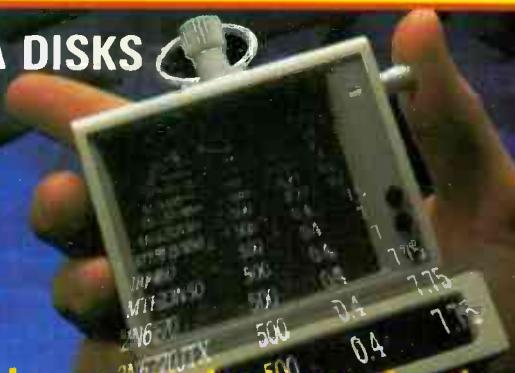

Speed up your device selection  
in the 90's — often for free!



0 9

\$2.50 U.S.  
\$2.95 CAN

A  
GERNSBACK  
PUBLICATION

SEPTEMBER 1990

## BUILD THE LAWN RANGER

Let a robot take the work  
out of cutting your lawn!

## TAKE CONTROL OF YOUR PHONE!



Our Telephone Line Controller  
lets you restrict incoming and  
outgoing calls, and lots more!

## MICROWAVE TECHNOLOGY

Early attempts at  
microwave generation

XXXXXXXXXXXX 5-DIGIT 60506  
390736DHMD997G093 09 47  
MR. ROBERT DAHM JAN 91  
997 GRAND AV RE  
AURORA, IL 60506

FLUKE



PHILIPS



The new Fluke 80 Series  
shown actual size

The new 80 Series  
is a digital meter,  
an analog meter,  
a frequency counter,  
a recorder,  
a capacitance tester,  
and a lot more.

It's the first multimeter that can truly be called "multi" ... not only standard features, but special functions usually limited to dedicated instruments.

Plus, innovations only Fluke can bring you. Like duty cycle measurements. Or recording the minimum, maximum *and* average value of a signal. Or the audible MIN MAX Alert™ that beeps for new highs or lows.

There's even Fluke's exclusive Input Alert™, that warns you of incorrect input connections. And a unique Flex-Stand™ and protective holster, so you can use the 80 Series almost anywhere.

Make sure your next multimeter is truly multi. Call today at **1-800-44-FLUKE, ext 33.**

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS.



#### FLUKE 83

Volts, ohms, amps, diode test, audible continuity, frequency and duty cycle, capacitance, Touch Hold™, Relative, protective holster with Flex Stand™.

\$199*	\$239*	\$289*
0.3% basic dc accuracy	0.1% basic dc accuracy	0.1% basic dc accuracy
5 kHz acV	20 kHz acV	20 kHz acV
Analog bargraph & zoom	Analog bargraph & zoom	High resolution analog pointer
Three year warranty	Three year warranty	True rms ac
		1 ms PEAK MIN MAX
		4½ digit mode
		Back lit display
		Three year warranty

\*Suggested U.S. list price

#### FLUKE 85

Volts, ohms, amps, diode test, audible continuity, frequency and duty cycle, capacitance, Touch Hold™, Relative, protective holster with Flex Stand™.

\$199*	\$239*	\$289*
0.3% basic dc accuracy	0.1% basic dc accuracy	0.1% basic dc accuracy
5 kHz acV	20 kHz acV	20 kHz acV
Analog bargraph & zoom	Analog bargraph & zoom	High resolution analog pointer
Three year warranty	Three year warranty	True rms ac
		1 ms PEAK MIN MAX
		4½ digit mode
		Back lit display
		Three year warranty

#### FLUKE 87

Volts, ohms, amps, diode test, audible continuity, frequency and duty cycle, capacitance, Touch Hold™, Relative, protective holster with Flex Stand™.

\$199*	\$239*	\$289*
0.3% basic dc accuracy	0.1% basic dc accuracy	0.1% basic dc accuracy
5 kHz acV	20 kHz acV	20 kHz acV
Analog bargraph & zoom	Analog bargraph & zoom	High resolution analog pointer
Three year warranty	Three year warranty	True rms ac
		1 ms PEAK MIN MAX
		4½ digit mode
		Back lit display
		Three year warranty

FLUKE

# September 1990

**Radio**  
**Electronics**®

Vol. 61 No. 9

## BUILD THIS

### 33 R-E'S VOCAL STRIPPER

Filter out the lead vocals from your favorite recordings, and dub in your own voice!

**Terry L. Weeder**

### 37 TELEPHONE LINE CONTROLLER

Block out unwanted incoming and outgoing calls, and more!

**Mordechai Saad**

### 53 THE LAWN RANGER: PART 4

It's time to get the lawn mowed!

**Raymond Rafaels**

### 61 R-E'S DIGITAL DASHBOARD

Build an array of digital gauges for your car.

**Ross Ortman**

## TECHNOLOGY

### 47 DATA DISK: HIGH-SPEED DEVICE SELECTION FOR THE '90'S

Electronic data processing makes it easy to find the right components for your applications.

**Ed Prestwood**

### 68 INTRODUCTION TO MICROWAVE TECHNOLOGY

The focus is on early RF oscillators.

**Joseph J. Carr**

### 71 AM RADIO

What does the future hold for the AM band?

**Gerry L. Dexter**

## COMPUTERS

### 88 COMPUTER CONNECTIONS

Windows 3.0 and ToolBook

**Jeff Holtzman**

## DEPARTMENTS

### 6 VIDEO NEWS

What's new in video.

**David Lachenbruch**

### 16 EQUIPMENT REPORTS

Hewlett-Packard's 48SX scientific calculator.

### 83 DRAWING BOARD

Let's start on control circuitry.

**Robert Grossblatt**

### DATA DISKS: HIGH SPEED DEVICE SELECTION FOR THE '90'S



Finding the right component for a particular application is easier than ever with the help of today's data disks.

ED PRESTWOOD

# ON THE COVER

WHATEVER HAPPENED TO AM RADIO?



If there's a common thread that runs through the three seemingly disparate stories highlighted on this month's cover, it would have to be the notion of control—whether at home, at work, or at play. Our Telephone Line Controller (see page 37) is an obvious example, allowing you to block out any calls, either incoming or outgoing, that you deem undesirable. If your work (or your hobby) involves electronic design, the article on data disks that replace bulky, inconvenient cross-reference books will show you how to take better control of your valuable time. Turn to page 47 to find out how to speed up the device-selection process. And, just for fun, our Lead-Vocal Zapper (see page 33) gives you some control over your stereo records, by letting you replace the lead vocal with your own voice.

## COMING NEXT MONTH

### THE OCTOBER ISSUE GOES ON SALE SEPTEMBER 4.

#### BUILD A ROCKET ALTIMETER

Get a second-by-second playback of the flight of model rockets.

#### LASER-JET MEMORY CARD

Add memory to HP's LaserJet printer, for a fraction of HP's price.

#### SOME TV SETS CROSS THE BENCH

Case histories in TV service have some lessons to teach.

#### MICROWAVES: PART III

A look at magnetron tubes.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS (ISSN 0033-7862) September 1990. Published monthly by Gernsback Publications, Inc., 500-B Bixby County Boulevard, Farmingdale, NY 11735. Second-Class Postage paid at Farmingdale, NY, and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$17.97, Canada \$23.97, all other countries \$26.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$2.50. © 1990 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

# Radio Electronics®

Hugo Gernsback (1884-1967) founder  
M. Harvey Gernsback,  
editor-in-chief, emeritus

**Larry Steckler, EHF, CET,**  
editor-in-chief and publisher

#### EDITORIAL DEPARTMENT

**Brian C. Fenton, editor**  
**Marc Spiwak, associate editor**

**Daniel Goodman, technical editor**  
**Kim Dunleavy,**  
assistant technical editor

**Teri Scaduto, assistant editor**

**Jeffrey K. Holtzman**  
computer editor

**Robert Grossblatt, circuits editor**

**Larry Klein, audio editor**

**David Lachenbruch**  
contributing editor

**Don Lancaster**  
contributing editor

**Richard D. Fitch**  
contributing editor

**Kathy Campbell, editorial assistant**

#### ART DEPARTMENT

**Andre Duzant, art director**  
**Injae Lee, illustrator**

**Russell C. Truelson, illustrator**

#### PRODUCTION DEPARTMENT

**Ruby M. Yee, production director**

**Janice Box,**  
editorial production

**Karen S. Tucker**  
advertising production

**Marcella Amoroso**  
production assistant

#### CIRCULATION DEPARTMENT

**Jacqueline P. Cheeseboro**

circulation director

**Wendy Alanko**

circulation analyst

**Theresa Lombardo**  
circulation assistant

**Michele Torrillo, reprint bookstore**

Typography by Mates Graphics

Cover photo by Diversified Photo Services

**Radio-Electronics** is indexed in  
*Applied Science & Technology Index*  
and *Readers Guide to Periodical Literature*.


Microfilm & Microfiche editions are available. Contact circulation department for details.

**Advertising Sales Offices listed on page 96.**


Radio-Electronics Executive and  
Administrative Offices:  
**1-516-293-3000.**

Subscriber Customer Service:  
**1-800-288-0652.**

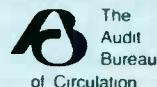Order Entry for New Subscribers:  
**1-800-999-7139.**


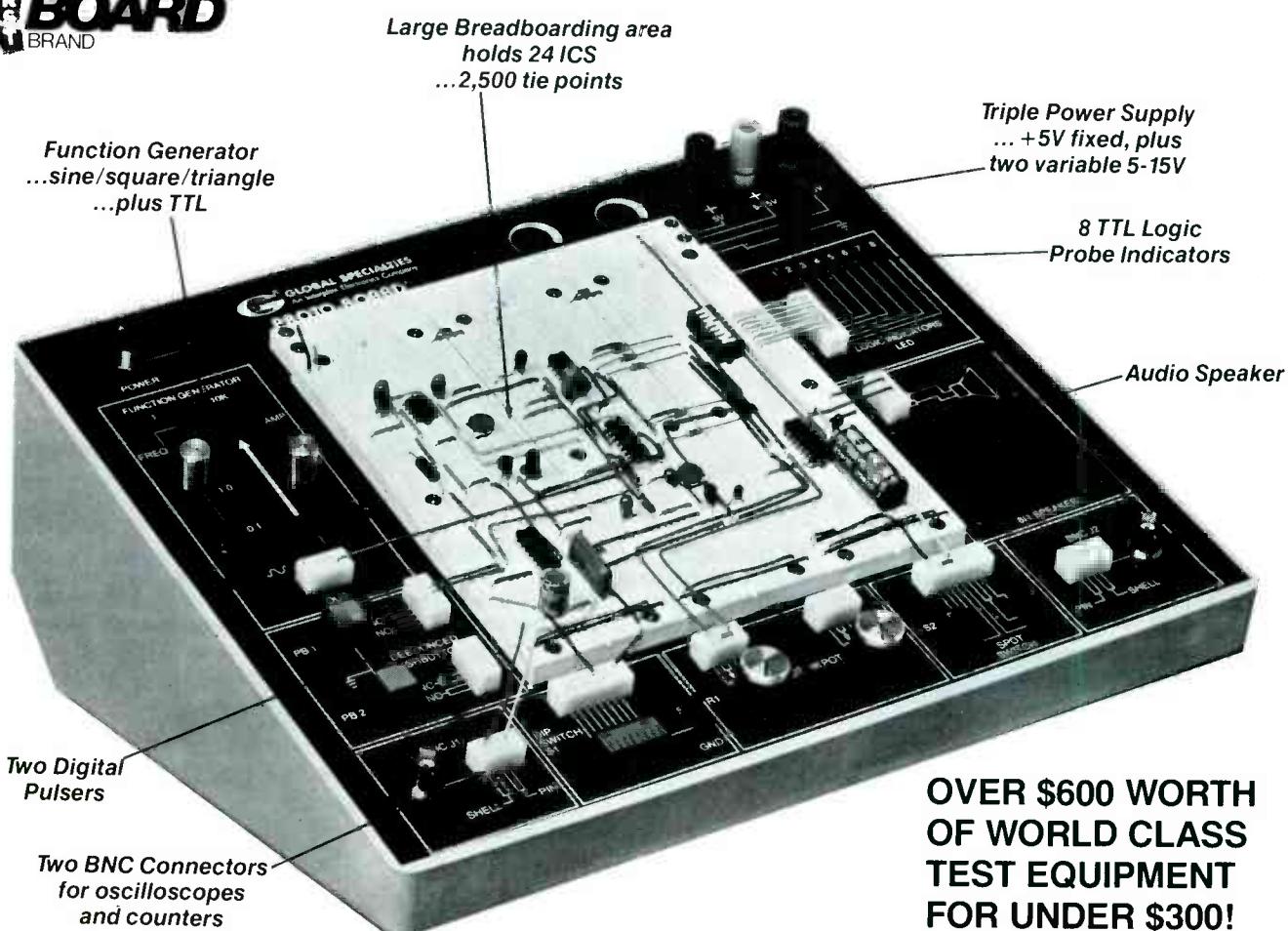
# AT \$299.95, NO OTHER DESIGN WORKSTATION GIVES YOU SO MUCH FOR SO LITTLE.



OVER \$600 WORTH  
OF WORLD CLASS  
TEST EQUIPMENT  
FOR UNDER \$300!

Here's PB-503, the total design workstation. It has everything! **Instrumentation**, including a function generator with continuously variable sine/square/triangle wave forms—plus TTL pulses. **Breadboards** with 8 logic probe circuits.

And a **Triple Power Supply** with fixed 5VDC, plus two variable outputs (+ 5 to 15VDC and - 5 to 15VDC). Throw-in 8 TTL compatible LED indicators, switches, pulsers,

potentiometers, audio experimentation speaker...plus a lifetime guarantee on all breadboarding sockets! You have everything you need right there in front of you! PB-503—one super test station for under \$300! Order yours today!!



Call toll-free for details  
1-800-572-1028



**GLOBAL  
SPECIALTIES**

CIRCLE 189 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

A016

an  
Interplex  
Industries  
company

Global Specialties  
70 Fulton Terrace, New Haven, CT 06512.  
Telephone: (203) 624-3103. © Interplex Electronics, 1990.  
All Global Specialties breadboarding products made in USA.  
ProtoBoard is a registered trademark of Global Specialties.

# WHAT'S NEWS


*A review of the latest happenings in electronics.*
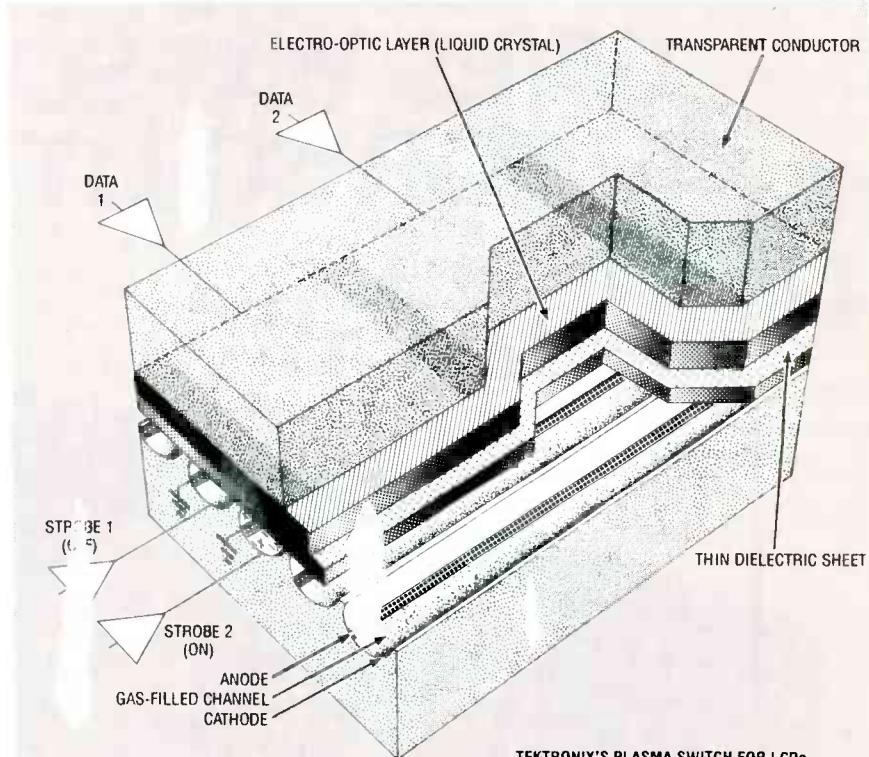
## Ultra-pure silicon crystal

Scientists at the Westinghouse Science & Technology Center (Pittsburgh, PA) have produced a silicon crystal that is four times purer and significantly larger than any previously reported silicon material. Impurities comprise only a few parts in 100 trillion, compared to more than 10 parts in 100 trillion previously reported for one-inch diameter silicon crystals. The 22-pound cylindrical structure—called a boule—is more than a yard long and has a diameter of just over 3 inches. Its larger size makes it more practical for use in microelectronics circuits and devices. Crystal boules are sliced into wafers on which microelectronic circuits and power semiconductor devices are fabricated. The Westinghouse crystal, which its developers believe to be the purest silicon crystal ever made, is expected to play an important role in the manufacture of infrared detectors for space, defense, and environmental applications. The ultrapure silicon crystal was grown in Westinghouse's float-zone crystal-growth facility, the largest float-zone furnace in the U.S.,



**WESTINGHOUSE TECHNICIAN** Don Nebel holds a single-crystal boule of silicon, believed to be the purest and largest ever produced.



TEKTRONIX'S PLASMA SWITCH FOR LCDs

**IN TEKTRONIX'S PLASMA-ADDRESSING PROCESS**, the liquid-crystal material and a protective dielectric layer are sandwiched between two sheets of glass; the upper sheet contains the data electrodes patterned from the transparent indium-tin-oxide conductors and the bottom sheet provides channels that contain the plasma gas with two electrodes per channel.

which can be adapted to produce boules up to four feet long and five inches in diameter.

## Plasma-addressing approach for high-resolution LCD's

Tektronix researchers in Beaverton, Oregon, are developing a new plasma technique using a plasma switch to address the active matrix of a liquid-crystal display. Intended as an alternative to silicon thin-film transistors (TFT's), which are successful in small, full-color displays but are difficult to manufacture in a large array to address more than a million elements, the new technique could significantly reduce the number of row drivers and make the displays easier to manufacture.

The plasma technique uses gas-filled channels to address a variety of

twisted-nematic and polymer-dispersed liquid crystals. Confined ionized gas acts as an electrical switch: It conducts in an ionized state and becomes nonconductive when de-ionized. The degree of conductivity is determined by the number and mobility of the carriers in the gas. Tektronix says that the conductivity range of the gas (between conducting and nonconducting states) can be ten orders of magnitude. They have developed a plasma switch to take advantage of that property.

The plasma switch is a three-terminal structure that uses a probe electrode on one terminal to alter the conductivity between the other two. A single switch can replace a whole row of silicon-based TFT's.


Results of the initial demonstrations have been promising. **R-E**



# Select 5 Books for only \$4.95


## when you join The Computer Book Club<sup>SM</sup>

(Values to \$139.75)

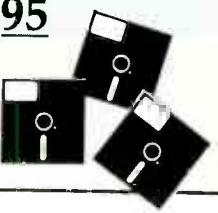


Counts as 2

3570P \$22.95

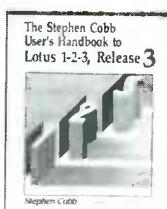


3417P \$24.95

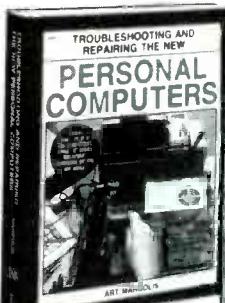

2809 \$29.95

Counts as 2

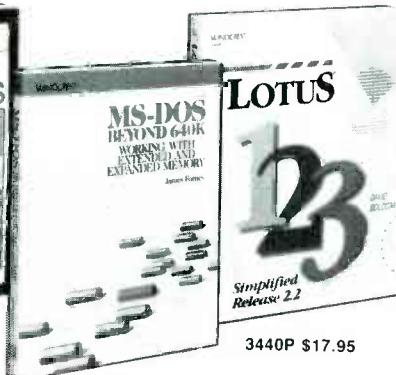

3440P \$17.95


LOTUS

1-2-3  
Simplified Release 2.2

3239 \$29.95




3382P \$29.95

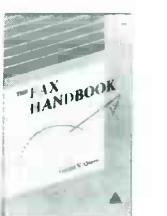


3563P \$22.95

Counts as 2

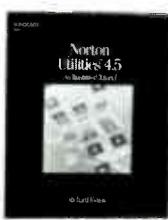


3359P \$16.95

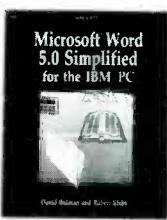


3318P \$19.95

Counts as 2

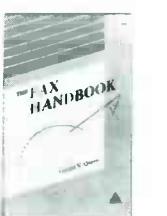


3341 \$16.95

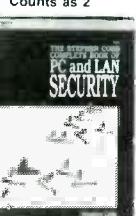

3280 \$31.95

Counts as 2

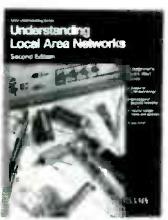


9335P \$19.95

Counts as 2



3616 \$27.95

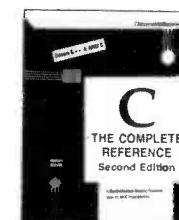

9309P \$28.95

Counts as 2




3578P \$16.95




9262 \$39.95

Counts as 2

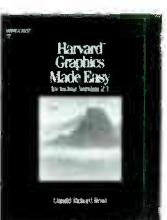

3401P \$17.95

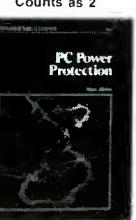

9250P \$19.95




3278 \$34.95

Counts as 2



3176P \$16.95

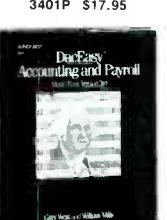


3204P \$21.95



3146P \$17.95




3131 \$26.95

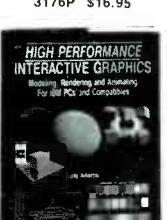

2879P \$22.95

Counts as 2

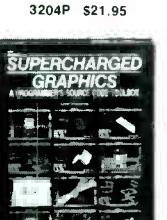

2959 \$29.95

Counts as 2



3101P \$19.95




3006P \$29.95

Counts as 2




2870P \$16.95

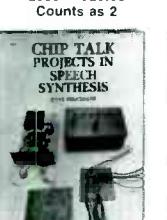

2812P \$14.95

Counts as 2

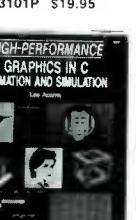

3049 \$37.95

Counts as 2

All books are hardcover unless number is followed by a "P" for paperback.

**Membership Benefits** • **Big Savings.** In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' prices. • **Bonus Books.** Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. • **Club News Bulletins.** 15 times per year you will receive the Book Club News, describing all the current selections—main, alternates, extras—plus bonus offers and special sales, with scores of titles to choose from. • **Automatic Order.** If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. You will have at least 10 days to decide. As a member, you agree to purchase at least 3 books within the next 2 years and may resign at any time thereafter. • **Ironclad No-Risk Guarantee.** If not satisfied with your books, return them within 10 days without obligation! • **Exceptional Quality.** All books are quality publishers' editions especially selected by our Editorial Board.

(Publishers' Prices Shown)

**The Computer Book Club<sup>SM</sup>**  
Blue Ridge Summit, PA 17294-0820

Please accept my membership in The Computer Book Club and send the 5 volumes listed below, billing me \$4.95. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase at least 3 books at regular Club prices during the next 2 years and may resign any time thereafter. A shipping/handling charge and sales tax will be added to all orders.

--	--	--	--	--

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Phone \_\_\_\_\_ Signature \_\_\_\_\_

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by The Computer Book Club.

RPI990

# VIDEO NEWS

*What's new in the fast-changing video industry.*

DAVID LACHENBRUCH

• **More 8mm converts.** The 8-millimeter camcorder format is gaining adherents in the United States at the expense of the full-size VHS and VHS-C (for compact) versions. Last month I reported the addition of an 8mm camcorder to Zenith's line (**Radio-Electronics**, August 1990). The latest brands to add 8mm are even more significant. RCA, owned by France's Thomson Consumer Electronics, has added four 8mm camcorders to its line, and—perhaps even more telling—Hitachi entered the 8mm field with three camcorders. Hitachi's entry is particularly significant since it is a member of the original Japanese VHS group and the first to break ranks and market an 8mm product under its own name. In addition to fielding 8mm camcorders under its own brand name, Hitachi is manufacturing the camcorders for RCA's line.

The VHS-C camp is replying with significant artillery. JVC has introduced several VHS-C recorders that rival 8mm in compactness and light weight with excellent picture quality. Panasonic, Quasar, and Magnavox have added tiny, palm-size VHS-C models built by Matsushita. The VHS-C group says it will mount a major promotion campaign for the VHS-C format.

Neither Zenith, Hitachi, nor Thomson is abandoning VHS-C. All three will also have the compact semi-compatible format as well. Zenith introduced several VHS-C models made by JVC, while Hitachi added a fold-up VHS-C camcorder for easy storage, and Thomson said its GE brand will have a model similar to Panasonic's Palmcorder. Although VHS-C is fighting back, 8mm is definitely gaining ground in the camcorder wars.

## • **TVRO's climbing again.**

After a major setback when signal scrambling started, home satellite dishes are on the upswing, according to the Satellite Broadcasting & Communications Association (SCBA). It puts the home-dish population at 3,000,000 and estimates that sales

are now running at 30,000 monthly, with total new installations expected to hit 400,000 this year, up from 240,000 when the scrambling-induces slump began.

• **CDTV.** That stands for "Commodore Dynamic Total Vision," a new interactive system combining audio and video scheduled for introduction this fall. Developed by Nolan Bushnell, who originated the video game when he headed Atari, CDTV can play standard compact discs, the new Compact Discs + Graphics, or special CD-ROM interactive audio-visual programs. Included in the initial 100 programs, to be sold for \$30 to \$100, will be a world atlas, a cookbook, encyclopedias, and games for both adults and children. The system uses the basic chips of the Commodore Amiga computer—in fact, it's convertible to a computer with the addition of a keyboard.

The basic system, to be priced at "less than \$1,000" initially, is operated by a wireless remote control, which lets users pan, zoom, and control a cursor, among other things. It permits full motion on half the screen, or 15 frames per second for full-screen scenes, but Commodore says it is an "open architecture" system that can be converted to a full-screen, full-motion medium when a standard is approved by the International Standards Organization.

Philips and American Interactive Media previously announced that they will market their full-screen Compact Disc-Interactive (CD-I) system in 1991. A Philips official expressed disappointment that the CDTV system was introduced before a standard was set. Consumer confusion could be the result.

• **Laserdiscs grow up.** More than a decade after its introduction, the laserdisc is beginning to approach mass-market status. Sales of discs exceeded 3,500,000 last year, and by midyear at least 16 brands were offering combination CD-laserdisc players or had announced their

intentions to do so. Players are now, or will soon be, available under these brands: Denon, Fisher, Funai, Kenwood, Magnavox, Marantz, Mitsubishi, NEC, Panasonic, Philips, Pioneer, Quasar, RCA, Sharp, Sony, and Yamaha.

• **Video vignettes.** After lagging for three years, sales of projection-TV receivers in the first quarter of 1990 were up 25% from the same period in 1989, and there were forecasts that 1990 would be the first record year for projection TV since 1986.

The picture-tube shortage that plagued the TV industry for the last few years seems to have ended, and an overcapacity of 3,000,000 to 4,000,000 tubes is being forecast for 1992. Companies that have expanded, built, or announced new color-tube plants in the United States since 1988 include Hitachi, Matsushita (Panasonic), Philips, Sony, Thomson (RCA and GE), and Toshiba.

• **Digital VHS audio.** JVC, the leader of Japan's VHS group, has developed a compatible digital soundtrack for VHS recordings. Although the system is at least a year from the market, the company has released specifications, presumably to encourage other VHS manufacturers to go along. The system uses "depth multiplex" recording, which permits video and audio signals to be recorded on different layers of the tape's magnetic coating.

The recorded digital signal doesn't disturb the other soundtracks on the VHS tape—longitudinal mono and AFM stereo. The PCM audio signal uses a 48-kHz sampling frequency and 16-bit quantization, according to JVC. It will be used only on Super VHS recordings; if the technique were used on standard VHS it would overlap the luminance signal and cause interference, said JVC. The signal may be split into four channels for multilingual recording or other purposes.

R-E

# ASK R-E

Write to Ask-RE, Radio-Electronics, 500-B Bi-County Blvd., Farmingdale, NY 11735

## XT TO AT UPGRADE

**I recently upgraded my computer from an XT to an AT clone, and there seems to be some sort of problem with the disk drives. Whenever I try to read a disk from the AT on my XT, I get one of two kinds of errors. The most common one is that lots of read errors show up, but occasionally I can't read the disk at all. I can't even get a directory to show up on the screen. What's going on?—F. Scher, Amsterdam, NJ**

You haven't given me all the particulars of your computers, but I can make a good guess as to the source of the problem. The chances are that you got your AT with a 1.2-MB 5½ inch drive and your XT has a 360K drive. The two drives look very much alike on the outside, but there's a big difference internally. In order to understand what's causing your first problem, let's talk a bit about the basic difference between the drives.

The original 360K floppies have two sides with 40 tracks each, and each track has nine sectors. The 1.2-MB disks were organized a bit differently to get the increased amount of storage. The high-density disks have 80 tracks on two sides, and each track is divided into 15 sectors. Since you've got twice as many tracks and 60% more sectors, you can store more data on the disk. If you do the arithmetic, you'll see that the numbers work out correctly.

It makes sense that something had to be done to the original drives to allow them to hold so much more information. And it's what was done to the drives that's causing both of your problems.

Disk drives are essentially the same as tape recorders. They have a read/write head, and they record information on magnetic media (the disk surface). When the number of tracks was doubled, the distance between tracks was halved (makes sense), and doing that increased the chances of crosstalk between the tracks.

The problem was solved by reducing the write current on high-density drives. Since the signal was much lower, the unwanted noise from nearby tracks was reduced. In order to read the desired tracks, however, the read gain was also increased. The system worked well (and still does), but it was necessary to change the composition of the recording medium in order to make the system reliable. There's a real, physical difference between 360K and 1.2-MB disks, and each can only be used for its intended purpose.

If you want to use a 1.2-MB drive to write to a 360K disk, you have to use a disk made for 360K operation. Both the number of tracks and the number of sectors can be changed in software. When you issue the command FORMAT A:/4, you're telling the software to make the head put forty tracks and nine sectors on the disk—you'll be formatting a 360K floppy disk.

What's causing your problem is that while the software can force the drive to do the correct number of tracks and sectors, it can't do anything about the write current—that's an internal adjustment on the drive and the software can't do a thing about it.

When you write a 360K disk on a high-density drive, the information is going to be correctly organized on the disk but the recorded level will be very low. Since the 360K drive has its read gain set for a higher recorded level, the drive often has trouble reading the disk and that's the first problem you're having.

The second problem you're having—not being able to read the disk at all—is probably because you're trying to read a 1.2-MB floppy in the 360K drive. That can't be done at all.


The solution to your problems is through hardware, and the cheapest way to do it is to add a 360K drive to the AT. Adding a 1.2-MB to your XT will undoubtedly mean you'd need a new disk controller as well, and there's no reason to spend the extra cash.

## COMMON-CATHODE DRIVERS

**I'm building a circuit that uses a 4511 to drive a seven-segment LED display. Everything is fine but the chip is designed to drive only common-cathode displays and I have a box of common-anode displays. Is there any way I can use these instead of having to go out and buy a bunch of common-cathode displays? I asked the person in the store about this and he said there was no way it could be done. You're my last hope.—N. Rofe, New Brunswick, NJ**

Although you're not supposed to do it, there's always a way to do that kind of thing. The person in the store who told you that it was impossible has, in kind words, a very limited imagination.

The 4511 is designed to directly drive a common-cathode display, but using it to drive a common-anode display means that you'll have to add a transistor as shown in Fig. 1. The transistor is working as a simple inverter, and just about any small signal PNP transistor should be able to handle the amount of current you'll need. Re-

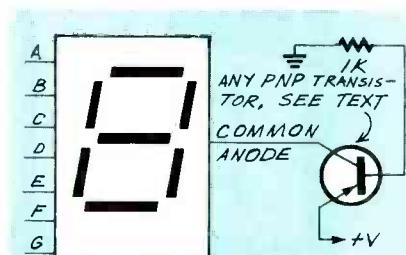

**FIG. 1—THE 4511 IS DESIGNED to directly drive a common-cathode display but, by adding a transistor as shown here, you can use it to drive a common-anode display.**

member the rule: Better to underrate parts than to overrate them.

You may find the schematic shown in Fig. 2 to be useful as well. Even though the 4511 can directly drive a common-cathode display, it has (as do all display drivers) a maximum current that it can deliver at the outputs.

That causes a problem when you try to drive really big displays or even incandescent bulbs.

Putting a transistor at the output switches the burden of powering the display from the chip to the transistor. If you need more current just add a

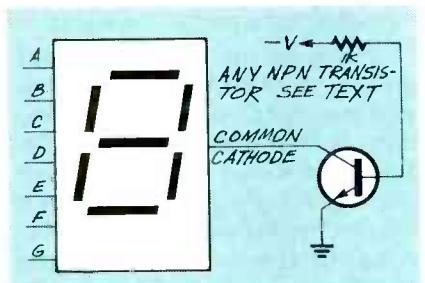


FIG. 2—EVEN THOUGH THE 4511 can directly drive a common-cathode display, you may have to add a transistor to the output. That allows you to drive really big displays or even incandescent bulbs.

chunkier transistor. The solution is really that simple.

Of course you have to keep in mind that the 4511 is a CMOS part and it can't be expected to deliver enough current to trigger heavy-duty transistors. If you ever want to do something like that, you'll have to build an

intermediate transistor stage to bring the output of the 4511 up to the level of the output transistor. But, for driving standard common-anode displays that typically want a maximum of about 20 mA per segment, that circuit should solve the problem without any difficulty.

## DIGITAL AMPLIFICATION

I've built a circuit to accept data from a temperature sensor but the input signal is a bit too low to go through my A-to-D converter. I don't want to have to add analog circuitry to the design so is there any easy way to amplify the incoming signal with digital IC's?—A. Dolan, Belmar, N.J.

Once upon a time there was no way to do that, but your problem can be solved with the addition of a couple of CMOS inverters. You may have to add an IC to the board but, if you've got three spare inverters around, you can use them.

The 4049 is a good choice for this application since it can handle higher power levels and is perfect to use if you've got to do any sort of voltage

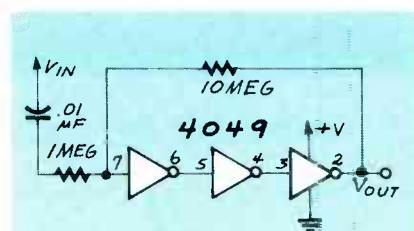


FIG. 3—The 4049 CAN HANDLE high power levels and is perfect for any sort of voltage translation. The amplifier will give you a gain of 10 with an input impedance of over a megohm.

translation. As shown in Fig. 3, the amplifier will give you a gain of 10 with an input impedance of over a megohm. It doesn't require any kind of special layouts and should work without a problem. If you add a 4049 remember to do something with the unused inverter inputs.

Although you can easily build the circuit, and it will do the job, I don't understand why you don't build a small single-transistor amp to do the same job. I don't know what the characteristics of your input signal are but I'm sure you could easily design a simple transistor amp to provide the gain you need. **R-E**

R-E



**With The Market Proven VA62A Universal Video Analyzer™**

Are you finding it tough to service today's hi-tech VCR and TV circuits? Successful video servicers have told us that, to them, the new technology meant lost profit and troubleshooting grief until they tried the VA62A's time tested, functional analyzing methods. *"The VA62A cuts servicing time and increases profits . . ."*

\*Based on a nationwide survey of users who reported an average time savings of 54% compared to their previous test equipment.

You can prove it to yourself, in your shop, absolutely risk free—and share in the profits successful video servicing can bring. Call **1-800-SENCORE (736-2673)** and ask about our exclusive VA62A instrument evaluation program. Tech-Tape Video Preview and FREE full line color catalog are also available.

**SENCORE**®  
3200 Sencore Drive, Sioux Falls, SD 57107  
100% American Made

CIRCLE 180 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Discover Your Career Potential In The Fast Growing Field Of High-Tech Electronics!

CIE Gives You The Training You Need to Succeed...  
At Your Own Pace...& In Your Own Home!

If you're anxious to get ahead...and build a *real* career...you owe it to yourself to find out about the Cleveland Institute of Electronics!

CIE can help you discover your career potential in the fast growing field of high-tech electronics. A career that will challenge and excite you every day...reward you with a powerful feeling of personal accomplishment...and deliver a level of financial security you may have only dreamed of before!

As the leading school in home-study electronics, CIE has helped over 150,000 students in the U.S.A. and over 70 foreign countries get started in this exciting field. To find out how CIE could be helping you...read on...then send for a CIE catalog TODAY!


## A Growing Need For Trained Professionals!

The career opportunities shown here are only a few of the challenging, high-paying careers you could enjoy as an electronics technician.

You could be the "brains" behind the scenes of an exciting TV broadcast...trouble-shoot life-saving medical equipment...design exotic new aeronautics systems...CIE's job-oriented programs offer you the quickest possible path to the career of your dreams! And CIE also features military and union re-training, to build on what you already know.
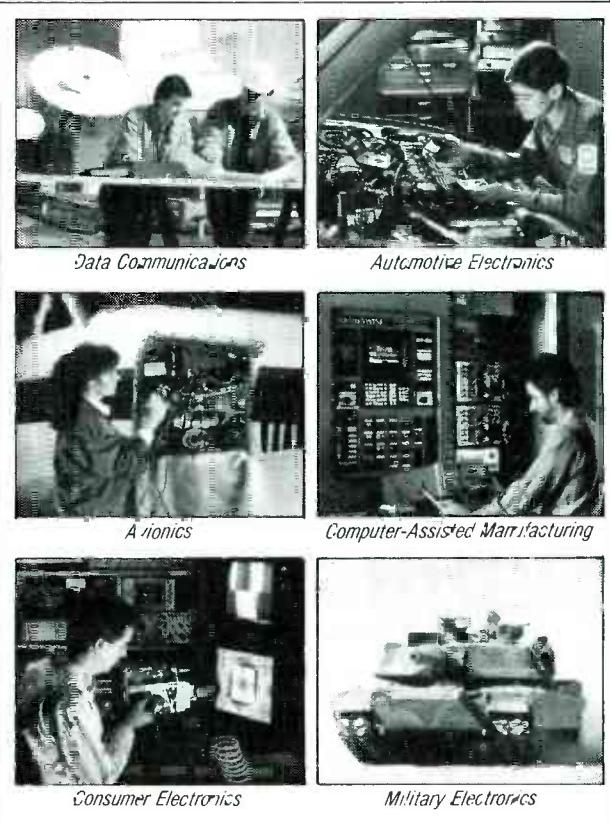
## Dozens Of Fascinating Careers To Choose From!

Even if you aren't sure which career is best for you, CIE can get you started with core lessons applicable to *all* areas of electronics. As you advance, CIE makes job opportunities available to you through the bimonthly school paper, *The Electron*.



## Practical Training... At Your Own Pace.

Through CIE, you can train for your new career while you keep your present job. Each course allows a generous completion time, and there are no limitations on how fast you can study. Should you already have some electronics experience, CIE offers several courses which start at the intermediate level.

## "State-Of-The-Art" Facilities & Equipment.

In 1969, CIE pioneered the first electronics laboratory course, and in 1984, the first Microprocessor Laboratory. Today, no other home study school can match CIE's state-of-the-art equipment. And all your laboratory equipment is included in your tuition cost. There is no extra charge—it's yours to use while you study at home and on the job after you complete your course!

## Earn Your Degree To Become A Professional In Electronics!

Every CIE course you take earns you credit towards the completion of your Associate in Applied Science Degree, so you can work towards your degree in stages. And CIE is the only school that awards you for fast study, which can save you thousands of dollars in obtaining the same electronics education found in four-year Bachelor's Degree programs! Write for details today!

## Personal Training From A Renowned Faculty.

Unlike the impersonal approach of large classroom study, CIE offers you one-on-one instructional help 6 days a week, toll-free. Each CIE lesson is authored by an independent specialist, backed by CIE instructors who work directly with you to answer your questions and provide technical assistance when you need it.

## Send For Your Catalog Today!



### CIE World Headquarters

Cleveland Institute of Electronics, Inc.  
1776 East 17th St., Cleveland, Ohio 44114

ARE-174

**YES!** Please send me your independent study catalog (For your convenience, CIE will have a representative contact you—there is no obligation.)

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt # \_\_\_\_\_


City/State/Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_

Check box for G.I. Bill bulletin on educational benefits:  Veteran  Active Duty

## Mail This Coupon Today!

ARE-174

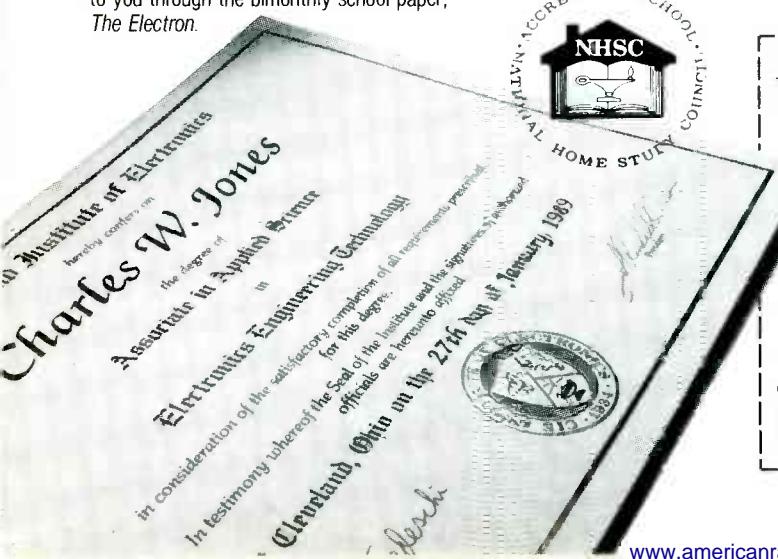

SEPTEMBER 1990

# LETTERS

Write to Letters, Radio-Electronics, 500-B Bi-County Blvd., Farmingdale, NY 11735

## DESOLDERING DEVICES

I'm writing in response to Mr. Perdue's letter that appeared in the May 1990 issue of **Radio-Electronics**. (He was responding to a previously published letter that concerned IC removal.) I take extreme exception to his general statement that the use of desoldering braid is "the only one approved by government organizations." I work for a government organization that regards the use of desoldering braid as a last resort! As a matter of fact, the U.S. government approves several methods of both soldering and desoldering components on printed-circuit boards.

One of the approved methods of desoldering IC's is to use a motorized vacuum device, such as a "Pace Kit." Of course, that method requires specialized training, and the cost of such a device would be prohibitive to the average home technician. Next on the list is the mechanical vacuum device, commonly known as the "solder sucker." That item is available at most electronics parts stores. To use it, simply cock it and then heat the joint to be desoldered with a low-wattage iron. As soon as the solder begins to flow, place the tip of the solder-sucker vacuum over, and in physical contact with, the joint, and press the trigger button. When the solder sucker has tripped, remove both the iron and the vacuum immediately. Check the joint to make sure that all the solder was removed. If not, simply repeat the procedure.

A few words of caution: First, use a low-wattage (10-25 watts) soldering iron at all times, to prevent overheating the IC and causing internal damage. A temperature-controlled iron is even better. Next, when working with IC's—particularly CMOS types—always use a ground strap (a metal wrist strap with a detachable ground wire) and connect its wire to ground. That will prevent the dreaded static discharge from destroying your IC or other components on the circuit board. If you don't have a ground strap, discharge yourself on a cold-water pipe or some other type of

ground before starting work. Finally, use a small-diameter pointed or wedge tip on your soldering iron. That helps to heat only the area intended to be heated, and will prevent circuit-board runs from being lifted.

As a last resort, Mr. Perdue's desoldering braid method, as described in his letter, will work. Using either the solder-sucker or the solder-wick method will take some practice, and I, too, would recommend that the novice practice on a junk circuit board to get a feel for either method. That lessens the chance of accidentally destroying a good circuit board or its components.

STEVEN E. SWENTON  
Glen Burnie, MD

## I/O CARD INPUT

I was intrigued by Mark Hanslip's article, "Build This Experimenter's I/O Card" (**Radio-Electronics**, June 1990). I find it amazing that the 8255 PPI, an LSI IC introduced about a decade and a half ago for 8080

systems, is still being used in new designs.

I disagree with the author's statement about Port B when Port A is initialized for mode 2 operation: "Port B is not used at all." Although Port B cannot be initialized for mode 2 operation, it is far from useless. Port B, independent of Port A's mode of operation, can still be used in either mode 0 or 1.

One last thing: The pins of Port C that are not commandeered for use by Ports A and B (when operating in modes 1 and/or 2 for handshaking) are available for use as input or output lines.

JAMES KOVAR  
Lincoln, NE

Fig. 1 goes here

Mr. Kovar has a point. The chart that he provided (Fig. 1) leaves a blank where Port B would be located in relation to mode 2. As I have never needed to use mode 2, the situation has never come up. Thanks, Mr. Kovar, for clearing up that anomaly.

Mode Definition Summary

	MODE 0		MODE 1		MODE 2	
	IN	OUT	IN	OUT	GROUP A ONLY	
PA <sub>0</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>1</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>2</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>3</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>4</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>5</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>6</sub>	IN	OUT	IN	OUT	↔	↔
PA <sub>7</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>0</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>1</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>2</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>3</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>4</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>5</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>6</sub>	IN	OUT	IN	OUT	↔	↔
PB <sub>7</sub>	IN	OUT	IN	OUT	↔	↔
PC <sub>0</sub>	IN	OUT	INTR <sub>B</sub>	INTR <sub>B</sub>	I/O	I/O
PC <sub>1</sub>	IN	OUT	IBF <sub>B</sub>	OBF <sub>B</sub>	I/O	I/O
PC <sub>2</sub>	IN	OUT	STB <sub>B</sub>	ACK	I/O	I/O
PC <sub>3</sub>	IN	OUT	INTR <sub>A</sub>	INTR <sub>A</sub>	I/O	I/O
PC <sub>4</sub>	IN	OUT	STB <sub>A</sub>	I/O	ACK <sub>A</sub>	ACK <sub>A</sub>
PC <sub>5</sub>	IN	OUT	IBF <sub>A</sub>	I/O	OBF <sub>A</sub>	OBF <sub>A</sub>
PC <sub>6</sub>	IN	OUT	I/O	I/O		
PC <sub>7</sub>	IN	OUT	I/O	I/O		

The 8255 is truly a great device. It allows for software-configurable hardware. In the past, I have designed interfaces using the 8255 for Apple, Radio Shack, Timex, Decision Mate V, and S-100 computers.

MARK HANSLIP

### TUBE TALK

While browsing through some old issues of **Radio-Electronics** I came across several letters in the December 1988 issue that dealt with tubes from Russia being imported into this country, and it brought to mind an experience I once had.

At a government auction (where I purchased a couple of pallets of test gear), a well-dressed fellow was bidding on items that I considered to be just so much junk. (After all, they were all full of tubes.) He was picking the stuff up by the ton, while hardly anyone else there showed any interest in it.

When I asked him about his purchases, he told me that he and two other ex-Air-Force pilots had formed their own business. He went around the country to all the government auctions and routed his purchases to a port, where they were loaded onto a ship and sent to Taiwan. One of his partners headed a group there that dismantled all the gear, "even salvaging the pan-head screws." The tubes, considered "choice" items, were rerouted to Europe where they commanded a very high price. (The third ex-pilot handled the European end.)

When I saw those letters about Russian tubes, I couldn't help but wonder: "Does it seem likely that a lot of our own tubes are coming back at us—re-labeled?"

RUSSELL RIESBERG  
Weimar, CA

### ALL ABOUT THX SOUND

In Josef Bernard's June 1990 article, "All About Surround Sound," he gives the mistaken impression that "THX" is "... just quality control for movie sound ..." The THX Sound System was developed by Tom Holman for the main sound-mixing theater at Lucasfilm. It consisted of particular speakers mounted in a special construction behind the screen along with a crossover designed with those elements in mind. Its sound was amazing. Since the vast majority of sound systems in cinemas were outdated, and few could

## LEARN VCR CLEANING/MAINTENANCE/REPAIR

EARN UP TO \$1000 A WEEK, WORKING PART TIME FROM YOUR OWN HOME!



EARN UP TO \$60  
AN HOUR AND  
MORE!

### THE MONEY MAKING OPPORTUNITY OF THE 1990'S

IF you are able to work with common small hand tools, and are familiar with basic electronics (i.e. able to use voltmeter, understand DC electronics). . . . IF you possess average mechanical ability, and have a VCR on which to practice and learn. . . . then we can teach **YOU** VCR maintenance and repair!

**FACT:** up to 90% of ALL VCR malfunctions are due to simple MECHANICAL or ELECTRO-MECHANICAL breakdowns!

**FACT:** over 77 million VCRs in use today nationwide! Average VCR needs service or repair every 12 to 18 months!

Viejo's **400 PAGE TRAINING MANUAL** (over 500 photos and illustrations) and **AWARD-WINNING VIDEO TRAINING TAPE** reveals the **SECRETS** of VCR maintenance and repair—"real world" information that is **NOT** available elsewhere!

Also includes all the info you'll need regarding the **BUSINESS-SIDE** of running a successful service operation!

FREE INFORMATION  
CALL TOLL-FREE 1-800-537-0589  
Or write to: Viejo Publications Inc.  
3540 Wilshire BL, STE. 310  
Los Angeles, CA 90010 Dept. RE

CIRCLE 178 ON FREE INFORMATION CARD

## SUPER LONG PLAY TAPE RECORDERS

12 Hour Model —  
USES D-120 TAPE  
\$119.00\*

Modified Panasonic Slimline,  
high quality AC-DC provide 6  
continuous hours of quality  
recording & playback on each  
side of cassette for 12 hours  
total. Includes • Voice level  
control • Digital counter,  
etc. TDK D-120 Cassette  
Furnished



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid  
state connects to your telephone  
jack and tape recorder. Starts  
recording when phone is lifted. \$28.50\*  
FCC APPROVED

VOX VOICE ACTIVATED CONTROL SWITCH  
Solid state. Self contained. Adjustable  
sensitivity. Voices or other  
sounds automatically activate and  
control recorder. Uses either re-  
corder or remote mike. \$28.50\*

\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea.  
Recorders \$4.00 ea. Cal. Res. add tax. Mail order. VISA,  
MC, COD's OK. Money Back Guarantee. Free data. ©  
AMC SALES INC. Dept. A 9335 Lubec St.  
Box 928, Downey, CA. 90241.  
Phone (213) 869-8519  
FAX (213) 923-1478

CIRCLE 108 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# It's no fluke.



Made in the U.S.A.

Building the best DMM for the money is no accident. The new RMS225 was carefully designed to give you what you wanted at a price you could afford. Visit your local distributor today and you'll agree the choice is obvious.

Fluke Model 77	Beckman Industrial RMS225
3-1/2 Digits	4 Digits
3,200 Counts	10,000 Counts
0.3% Accuracy	0.25% Accuracy
Touch Hold®	Probe Hold™
31 Segment Analog Bar Graph	41 Segment Analog Bar Graph
2,000 Hour Battery Life	1,000 Hour Battery Life
10A Range (Fused)	10A Range (Unfused)
Protective Holster	Protective Holster
3 Yr. Warranty	3 Yr. Warranty
—	True RMS
—	Auto Min Max™
—	Relative Mode
—	Self-Resetting Fuse (40mA Input)
\$159*	\$149

® Touch Hold is a registered trademark of the John Fluke Mfg. Co., Inc. \*1990 Fluke and Philips Catalog

**Beckman Industrial™**

An Affiliate of Emerson Electric Co.

Instrumentation Products Division  
4883 Ruffin Road, San Diego, CA 92123-1898  
(619) 495-3200 • FAX (619) 268-0172 • Tlx 249031  
Outside California 1-800-854-2708 Within California 1-800-227-9781  
© 1990 Beckman Industrial Corporation. Specifications subject to change  
without notice. Fluke is a registered trademark of John Fluke Mfg. Co., Inc.

CIRCLE 98 ON FREE INFORMATION CARD

# DAMARK

INTERNATIONAL INC.

"The 'Great Deal' Catalog!"



**cordata**

### 386SX COMPUTER WITH VGA MONITOR

- 100% IBM compatible.
- 80386SX-16/8 MHz speed, upgradable to 20 MHz.
- One 3-1/2" 1.44 MB floppy disk drive.
- One 5-1/4" 1.2 MB floppy disk drive.
- 40 MB hard drive/28 millisecond access time. • 1 MB RAM on motherboard, expandable to 8 MB. • Expansion slots: three IBM AT compatible accessory slots; one IBM PC/XT compatible accessory slot.
- Three 1/2" peripheral bay. • 1 serial port.
- 1 parallel port. • Built-in VGA video support.
- Battery backed real time clock/calendar.
- 80387SX-16 math co-processor socket.
- 101 key detachable IBM style keyboard.
- Zero wait state. • Phoenix BIOS.
- Included MS-DOS 4.0. Does not include software shown on screen.
- Dim.: 16" W x 18" D x 5" H. • Model # CPC8248.
- One Year Warranty through Cordata.
- Factory New! Factory Perfect!

#### VGA monitor:

- 14" non-glare color monitor.
- 100% IBM compatible.
- .42 mm dot pitch.
- 256 colors.
- Resolution: 640x480.
- Dim.: 14.72" W x 12.40" H x 15.64" D.

Mfr. Sugg. Retail: **\$2,968.00**  
DAMARK PRICE: **\$1499.99**

Item No. B-2213-143578  
Insured Ship/Hand: \$49.00

**FOR FASTEST SERVICE  
CALL TOLL FREE  
1-800-729-9000**



DAMARK INTERNATIONAL, INC.  
7101 Winnetka Ave. N., Minneapolis, MN 55428-1619  
Customer Service: 612-531-0082

Please rush me: **Cordata Computer(s)**  
@ \$1499.99 each, plus \$49.00 s/h each.  
Item No. B-2213-143578 MN res. add 6% sales tax.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City, State, Zip \_\_\_\_\_  
 Check/MO  VISA  Master Card  Discover  
Card No. \_\_\_\_\_  
Exp. Date \_\_\_\_\_ / Ph. # ( ) \_\_\_\_\_  
Signature \_\_\_\_\_  
Copyright 1990 DAMARK International, Inc. All rights reserved.

**DELIVERY TO 48 U.S. STATES ONLY**

handle the dynamics of a Lucasfilm movie, the THX system was licensed to theaters. As a former "THX engineer," I was involved in some of the first installations. The theater had to meet certain acoustical criteria concerning the overall noise level, reverberation time, and more. If a theater couldn't meet those criteria, it could not get a THX system. If it could, the theater was shut down while the screen was removed so that the THX wall could be built and the speakers installed. The THX crossover was put in along with amplifiers that also had to meet certain standards.

Thus, if a movie patron went to a THX theater, they would be listening to the same system that the sound was mixed on. The "quality control" consisted of periodic checks of alignment. As for the letters "THX," I remember that Tom Holman designed the crossover or X-over.

ROBERT HUGHES  
San Francisco, CA

Since Mr. Hughes was there, and I merely got my information second-hand, I will have to bow to his expertise—and thank him for the additional background on THX. My original point

is still valid, however: THX is just a special case of Dolby Stereo, and one should not expect to be able to rent or purchase videotapes or laser discs recorded using a "THX process."

JOSEF BERNARD

### CHAOS vs. CLASSICAL PHYSICS

While sitting in my den the other day, reading James Gleick's fascinating book called *Chaos*, I took a break to thumb through the new issue of **Radio-Electronics**. In the "Letters" column, I read with astonishment the letter from Jon Rolph criticizing Don Lancaster's ideas about the size of the brain's computer and its relationship to other computers. I'm astonished because of its parallel to one of the main themes in *Chaos*. The painful, "feet-of-clay" conservatism that has hampered the emerging super science of chaos for nearly a decade appears from Mr. Rolph's letter to have infected computer science as well. Chaos's pioneer physicists and mathematicians, men like Mandelbrot and Feigenbaum, literally risked their careers by publishing the new and radical ideas embodied in chaos and fractal geometry. Still considered a renegade science by many, those new ideas have rattled the rusty old cages of many disciplines. Mr. Rolph's suggestion that any radical departure from the classical understanding of a science might "set us all back a few paces" is the very kind of thinking that has plagued the advancement of chaos as a scientific discipline. The only way we progress in our thinking is to make those conceptual leaps that go beyond proven classical knowledge to provide the theory and hypothesis for the next generation to prove or disprove. Condemning Don Lancaster and *Hardware Hacker* for allowing to appear in print aberrations such as the idea of computer systems "waking up" or four-gigabit brains is not an argument against the fear of new technology, as Mr. Rolph suggests, but a demonstration of that very fear.

I am writing this letter on a desktop computer that itself has nearly four gigabits of memory. It is my personal workstation, and I consid-



**Banner  
Technical  
Books, Inc.**  
1203 Grant Ave.  
Rockford, IL 61103

CIRCLE 67 ON FREE INFORMATION CARD

er it to be quite "awake" in many respects. It clearly has a personality of sorts. It expects my interaction with it to follow certain behavior patterns and complains if I deviate from them. It has a strong instinct toward self-preservation. It stops and asks me if I'm sure before it allows me to reformat its disk memory. Other computers, those that do real-world control applications, are aware of at least some of their surroundings and are able to interact with them. That all suggests a form of awareness that has obviously escaped Mr. Rolph. While he waits for his network to wake up and assault him, Heinlein style, he is sleeping through a revolution in computers.

I applaud Don Lancaster for his imaginative thinking; I have been a follower since the days of the "TV Typewriter." I also applaud **Radio-Electronics**, for providing a forum for him and other innovative thinkers.

PETER A. BARNES  
Cincinnati, OH

#### SHARING FREEWARE

I have thoroughly enjoyed each of the articles in **Radio-Electronics**; it is one of the few publications that I actually read cover-to-cover. It is also one of the few magazines in my field that contains something I can share with everyone on at work, at any level of expertise. I'm not saying that I agree with everything in its pages, but that it promotes discussion on the art of electronics.

One thing I'd like to share with other **Radio-Electronics** readers is that Linear Technology Corporation is supplying—for free—an improved freeware PSPICE version from Microsim. It provides 28 op-amp models, which model bench data. I don't like to keep lots of inventory in my lab at work or my home workshop. This excellent simulator lets me be certain a circuit does what it should, and if a circuit doesn't work (i.e., an amp oscillates), I can quickly work out the bugs. Impedance matching, feedback, and other work becomes play, because parts values can be swept to cover a range. The freeware simulates a digital storage scope and a digital signal processor.

ROBERT KESSERLING  
Plano, TX

R-E

## ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.  
DEGREE**

THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

### COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

**COIE** 4251 CYPRESS DRIVE  
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD

## New AOR Scanner



**AR1000**

Total Price, Freight Prepaid  
(Express Shipping Optional)

**\$499**

- Continuous coverage (except UHF TV 600-805)
- AM, FM and wide band FM tuning modes.
- 10 Scan Banks, 10 Search Banks
- Selectable Priority Channel
- Selectable Search Increments, 5-95kHz
- Permanent memory backup
- 25 Day Satisfaction Guarantee. Full refund if not Satisfied.
- No Frequencies cut out.
- All normal accessories included.
- Size: 6 7/8" H x 1 3/4" D x 2 1/2" W  
Wt. 12 oz.


**ACE**  
COMMUNICATIONS

10701 E. 106th St. Indianapolis, IN 46256  
Toll Free 800-445-7717

VISA and MasterCard  
(COD slightly higher)  
FAX (317) 849-8794

CIRCLE 182 ON FREE INFORMATION CARD  
[www.americanradiohistory.com](http://www.americanradiohistory.com)
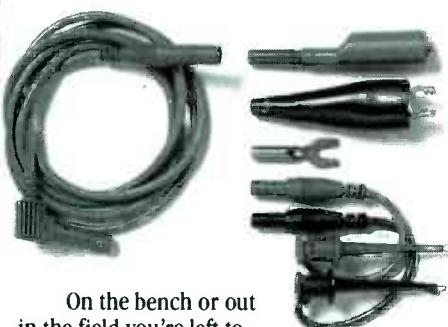
# DMM Test Leads That Will Last. At Last.




On the bench or out in the field you're left to your own devices. That's why Pomona has developed 12 different DMM Test Lead Kits. You can reliably attach different probes or clips to the same lead because Pomona's "Pop Jack" coupler holds tight, just like a Chinese finger puzzle until you "unlock" it. Silicone insulated wire feels great, won't be burned by the bump of a soldering iron, and stays flexible in cold temperatures.

**Choice Quality, Choice Selection.** These, and a host of other features like field repairability, low-cost slide-on tips, extendable and replaceable probe tips, and a rugged pouch or case to fit in pocket or toolbox, make them the best choice. Someone's finally making test leads that will last. See your nearest Authorized Pomona Distributor or contact

POMONA ELECTRONICS

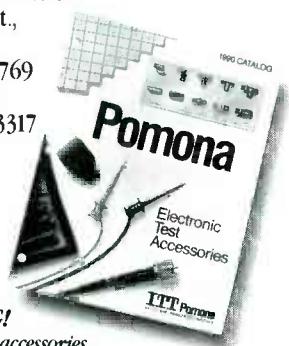1500 E. Ninth St.,  
P.O. Box 2767  
Pomona, CA 91769  
(714) 623-3463  
FAX (714) 629-3317




**FREE  
1990 CATALOG!**  
Thousands of test accessories  
and solutions in 138 pages.  
Call or write for your **FREE**  
copy today!

**ITT Pomona**  
AN ITT EMC WORLDWIDE COMPANY  
*Discover our strengths.*

CIRCLE 101 ON FREE INFORMATION CARD

# EQUIPMENT REPORTS
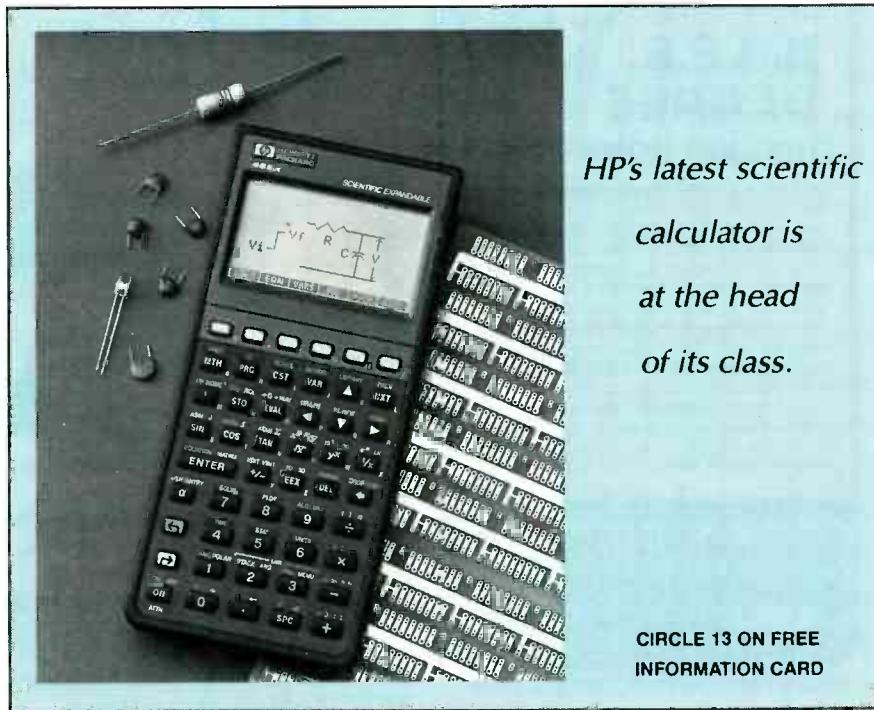
## Hewlett-Packard 48SX Scientific Expandable Calculator



**HP's latest scientific calculator is at the head of its class.**

**CIRCLE 13 ON FREE INFORMATION CARD**

**S**eptember is back-to-school time for many of tomorrow's engineers. It's the time that many students—along with those of us who haven't been students for some time—start looking for the perfect scientific calculator. We may have found that perfect calculator, the HP 48SX from Hewlett-Packard (Inquiries manager, Hewlett-Packard Company, 1000 N.E. Circle Blvd., Corvallis, OR 97330).

The calculator, introduced earlier this year, boasts more than 2100 functions. It allows equations to be entered the same way they would be written, and an impressive array of graphics functions lets you plot the equations. An RS-232 interface is available as an option, and an infrared interface is also offered. The standard built-in memory consists of 256K of ROM and 32K of RAM, but plug-in cards allow you to expand memory to 512K of ROM and 288K of RAM.

### Using the 48SX

Without question, the 48SX is the most powerful and advanced hand-

held calculator available. Getting access to all of that power is not always easy because some functions don't work the way you would intuitively expect. Also, the larger than 800-page (!) manual, while excellent on specifics and details, does not give a good overview of what the calculator has to offer. (We would recommend stopping by an HP dealer, who should have a demo disk or RAM card that does provide a good overview.)

The HP 48SX offers several impressive and important features. Its *EquationWriter* application allows equations to be entered as you would write them. Its graphics capabilities integrate calculus and graphics functions to find roots, minima and maxima, slopes, area under a curve, etc. A unique *automatic unit management* feature converts unlike units of measurements (148 different units in 16 categories such as force and energy) automatically. An equation-solver function allows you to find the numerical solution to an equation without isolating the dependent variable. For example, if Ohm's law was entered as an equation, you could enter the nu-






merical values of the known variables, and the calculator would solve for the missing one.

The calculator's keyboard contains 49 keys, most of which perform three or four different functions. Each key's primary function is on the keyface, while its secondary functions are shown in orange, blue, and white legends around the key, and are accessed by using the appropriate shift key. Some secondary functions (lower-case letters, Greek letters, and special characters), which are not shown on the calculator's face, are also available. The top row of keys are "soft" keys—they take on the function shown on the bottom, menu line of the display.

Most mathematical operations are performed by entering arguments on to the stack (which is a last-in, first-out sequence of storage locations) and then executing commands to manipulate the stack contents. Although the display can show the contents of up to four stack locations, the actual stack size can be much larger, and is



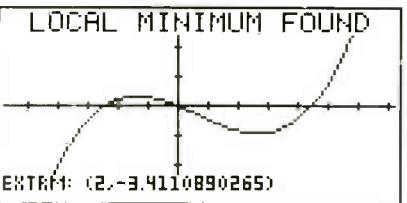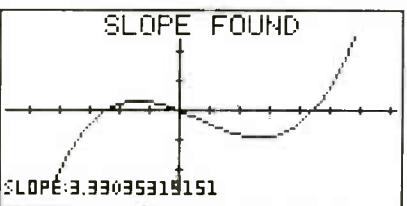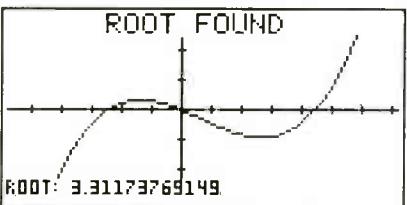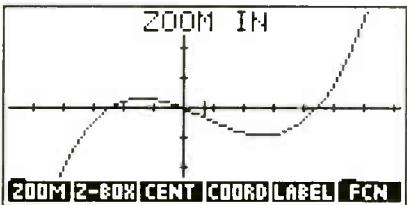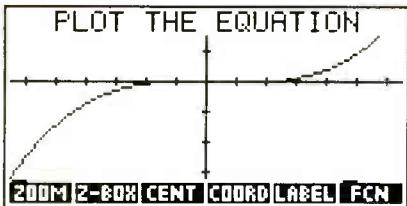**A SERIAL INTERFACE KIT** is available as an option to allow you to link the calculator to a PC or Macintosh so you can take advantage of the computer's storage, printing, and display capabilities.



**THE HP 48SX INTEGRATES GRAPHICS AND CALCULUS** functions to automatically find roots, intersections, minima and maxima, derivatives, and the like.

limited only by available RAM.

As you might guess, the calculator uses *reverse Polish notation* to solve equations. For example, to find the sum of 2 + 2, you would enter both addends on the stack, and then perform the addition. The keystrokes would be: "2 <enter> 2 <enter> +." The number 4 would appear at the top of the stack.


Understanding the stack is the key to understanding how to use the calculator. Even when you enter an equation "as you would write it," you cannot solve it, plot it, or do anything else with it until you put it on the stack. Unfortunately, when you do

move the equation onto the stack, it loses its "textbook appearance" and takes on a form more common to computers. That can be disconcerting and confusing until you get used to it—and the learning curve can be a steep one if you've never had any similar experience.

You can name an equation that is stored on the stack. That's helpful because the name can be used to identify an equation that might otherwise be very difficult to recognize once it's moved to the stack—especially if the equation contains integrals.

While the 48SX's built-in functions are impressive, it's important to remember that the calculator can be custom programmed through its built-in programming language. And we've barely mentioned the calculator's built-in functions! The 48SX can handle all sorts of operations with arrays and matrices, statistics, algebra, calculus, logical operations, vectors, complex numbers, and more. It can also produce eight different types of plots from function plots to histograms, and from scatter plots to polar and parametric plots.
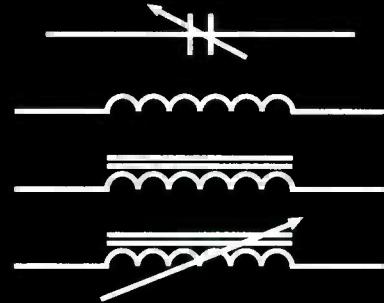
## Which symbol represents a variable inductor?



**What is the principle disadvantage of neon lights?**

**What are out-of-phase signals?**

**Heath Video Courses speed your learning curve!**

Learn basic electronics at home at your own pace with four, 60-minute video tapes. Know the variable inductor symbol. Recognize a PN junction. Understand oscillator fundamentals. Clearly SEE what most basic electronic books can only describe.

**DC ELECTRONICS.** Covers electron movement to troubleshooting and repairing a simple electronic circuit. **EV-3101-A.**

**AC ELECTRONICS.** Follow-up to DC Electronics. Covers the principles of AC, voltage and electrical measurement. Includes motors, generators and test instrument meter movements. **EV-3102-A.**

**SEMICONDUCTORS.** Complete the DC/AC videos and you're ready to learn how semiconductor devices are made, plus the principles of discrete devices, integrated circuits & optoelectronic devices. **EV-3103-A.**

**ELECTRONIC CIRCUITS.** Complete the basic course with amplifier configurations, biasing, coupling, audio amplifiers, closed-loop vs. open-loop operation and more. **EV-3104-A.**

An activity-filled workbook and explanation of how to solve each problem comes with each tape so you learn three ways—video, workbook and hands-on!

**Order today!**

**Call Toll free,**

**24-hours a day.**

**1-800-253-0570.**

We accept VISA, MasterCard, American Express and Heath Revolving Charge card. Use Order Code 601-018.

**VIDEO TAPES**

**\$39.95**

**EACH**

**Heath®**  
Benton Harbor, MI

**Call for a FREE catalog 1-800-441-HEATH.**

\*Price does not include shipping and handling, or applicable sales tax.

©1990, Heath Company  
Subsidiary of Bull Data Systems, Inc.

**CIRCLE 86 ON FREE INFORMATION CARD**

## DIGITAL VIDEO STABILIZER ELIMINATES ALL VIDEO COPY PROTECTIONS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. Digital Video Stabilizer: RXII completely eliminates all copy protections and jamming signals and brings you crystal clear pictures.

### FEATURES:

- Easy to use and a snap to install
- State-of-the-art integrated circuit technology
- 100% automatic - no need for any troublesome adjustments
- Compatible to all types of VCRs and TVs
- The best and most exciting Video Stabilizer in the market
- Light weight (8 ounces) and Compact (1x3.5x5")
- Beautiful deluxe gift box
- Uses a standard 9 Volt battery which will last 1-2 years.

(Dealers Welcome)

To Order: \$49.95 ea + \$4 for FAST UPS SHIPPING

**1-800-445-9285 or 516-694-1240**

Visa, M/C, COD M-F: 9-6 (battery not included)

SCO ELECTRONICS INC.

Dept. CBY9 581 W. Merrick Rd. Valley Stream NY 11580

Unconditional 30 days Money Back Guarantee

CIRCLE 190 ON FREE INFORMATION CARD

## CABLE TV DESCRAMBLER



1 Unit 10+

Jerrold S.B. ....	\$74	....\$55
Jerrold SB w/Trimode....	\$90	....\$70
Oak N-12 (w/VS).....	\$89	....\$65
Scientific Atlanta.....	\$109	....\$75
Pioneer.....	\$109	....\$75
Panasonic converter.....	\$98	....\$79
73 channel converter.....	\$79	....\$59

We Beat Anyone's Price!

30 Days Money Back Quaranty

Free Catalog

Visa, M/C, COD or send money order to:

**US Cable TV Inc.** Dept. KCT9

4100 N. Powerline Rd., Suite F-4

Pompano Beach, Fl 33073

**1-800-445-9285**

Please have make and model number of the equipment used in your area ready.

No Florida Sales!

It's not the intent of US Cable TV Inc. to defraud any pay TV operator and we will not assist any company or individual in doing so.

CIRCLE 191 ON FREE INFORMATION CARD

## Equation Library

Hewlett-Packard calls the 48SX an expandable calculator. One way it can be expanded is with plug-in cards, such as the *HP Solve Equation Library Applications Card*, which contains more than 300 science and engineering equations. The library's main menu contains such entries as ELECTRICITY, FLUIDS, HEAT TRANSFER, OPTICS, OSCILLATIONS, and SOLID STATE DEVICES. Each main entry contains sub-entries and equations, and in some cases, pictorial representations.

The equation library also contains a library of constants. Avogadro's number, Planck's constant, and the rest mass of an electron are among the 40 physical constants in the library (in both SI and English units).

A periodic table is available, as are various financial applications. And of course, things wouldn't be complete without a game of some sort. Minehunt should provide a pleasant diversion for both the bored and the frazzled engineer.

Although the equation library is the only currently available ROM card, HP does plan to introduce special cards to customize the HP 48SX for specialized applications.

## Serial interface kit

For those more comfortable working with a large monitor and standard QWERTY keyboard, an RS-232 interface allows you to take full control of the calculator from your PC or Macintosh. Programs, plots, and data can be stored on disks—a convenient way to swap them with other users. The interface kit gives your PC as much or greater power (although not the speed) of many comparable math software packages. But try putting one of those packages in your pocket and using it without a computer attached!

Of course, the power of the HP 48SX doesn't come for free. The calculator itself costs \$350. The serial interface carries a list price of \$99.95, as does the *HP Solve Equation Library Application card*. RAM cards cost \$79.95 (32K) or \$250 (128K).

With the 48SX, Hewlett-Packard maintains its leadership position in the scientific-calculator business. While we're inclined to say that the 48SX is the last calculator you'll ever need, we won't—HP is probably already hard at work to make its successor even more impressive. **R-E**



## CHEMICAL SOLUTIONS

### FREE CHEMTRONICS CATALOG!

Comprehensive new source for over 200 products used in electronic manufacturing and field service. E-Series products are CO<sub>2</sub> propelled for ozone safety. Precision cleaning agents, flux removers, bulk solvents, circuit refrigerants, precision dusters, non-residual wipers, premoistened pads/swabs, antistatic compounds, conformal coatings, lubricants, adhesives, desoldering braids and soldering products. Complete with technical specifications and application guide.



Chemtronics Inc.  
8125 Cobb Centre Drive  
Kennesaw, GA 30144  
1-800-645-5244  
in GA 404-424-4888

CIRCLE 54 ON FREE INFORMATION CARD

Try the

## Radio-Electronics bulletin board system

**(RE-BBS)**  
**516-293-2283**

The more you use it the more useful it becomes.

We support 300 and 1200 baud operation.

Parameters: 8N1 (8 data bits, no parity, 1 stop bit) or 7E1 (7 data bits, even parity, 1 stop bit).

Add yourself to our user files to increase your access.

Communicate with other R-E readers.

Leave your comments on R-E with the SYSOP.

**RE-BBS**  
**516-293-2283**


# 5 sure steps to a fast start as a high-paid computer service technician

## 1. Choose training that's right for today's good jobs

Jobs for computer service technicians will almost double in the next 10 years, according to the latest Department of Labor projections. For you, that means unlimited opportunities for advancement, a new career, or even a computer service business of your own.

But to succeed in computer service today, you need training—complete, practical training that gives you the confidence to service any brand of computer. You need NRI training.

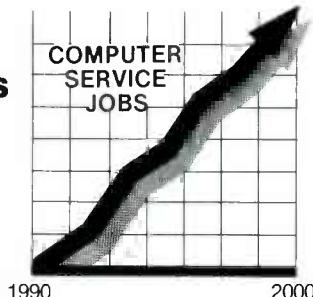Only NRI—the leader in career-building, at-home electronics training for more than 75 years—gives you practical knowledge, hands-on skill, and real-world experience with a powerful AT-compatible computer you keep. Only NRI starts you with the basics, then builds your knowledge step by step until you have everything you need for a fast start as a high-paid computer service technician.



studying diagrams, schematics, and photos that make the subject even clearer. Then you do. You build, examine, remove, test, repair, replace. You discover for yourself the feel of the real thing, the confidence gained only with experience.

## 3. Get inside a powerful computer system

If you really want to get ahead in computer service, you have to get inside a state-of-the-art computer system. That's why NRI includes the powerful new West Coast 1010 ES computer as the centerpiece of your hands-on training.

As you build this fully IBM AT-compatible micro from the keyboard up, performing key tests and demonstrations at each stage of assembly, you actually see for yourself how every section of your computer works.

You assemble and test your computer's 101-key "intelligent" keyboard, install the power supply and 1.2 meg 5 1/4" floppy disk drive, then interface the high-resolution monitor. But that's not all.

You go on to install a powerful 20 megabyte hard disk drive—today's most-wanted computer peripheral—included in your training to dramatically increase the data storage capacity of your



## 2. Go beyond "book learning" to get true hands-on experience


NRI knows you learn better by doing. So NRI training works overtime to give you that invaluable practical experience.

You first read about the subject, then you do. You build, examine, remove, test, repair, replace.

You discover for yourself the feel of the real thing, the confidence gained only with experience.

computer while giving you lightning-quick data access.

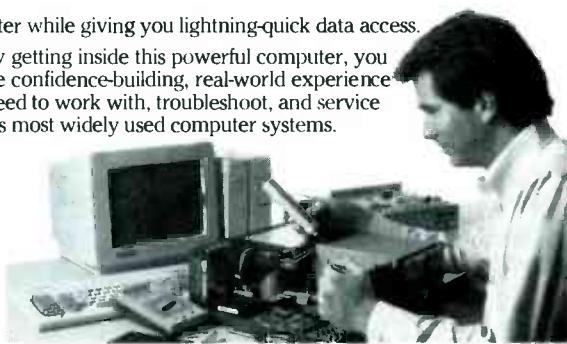By getting inside this powerful computer, you get the confidence-building, real-world experience you need to work with, troubleshoot, and service today's most widely used computer systems.



## 4. Make sure you've always got someone to turn to for help




Throughout your NRI training, you've got the full support of your personal NRI instructor and the entire NRI technical staff. Always ready to answer your questions and help you if you should hit a snag, your instructors will make you feel as if you're in a classroom of

one, giving you as much time and personal attention as you need.
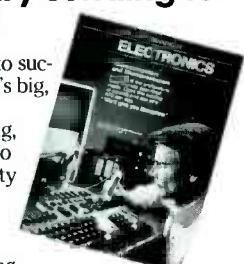
## 5. Step into a bright new future in computer service—start by sending for your FREE catalog today!

Discover for yourself how easy NRI makes it to succeed in computer service. Send today for NRI's big, 100-page, full-color catalog describing every aspect of NRI's one-of-a-kind computer training, as well as training in robotics, TV/video/audio servicing, electronic music technology, security electronics, and other growing high-tech career fields.

If the coupon is missing, write to: NRI School of Electronics, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008. AT & IBM are registered trademarks of International Business Machines Corp.



**NRI** School of Electronics

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW, Washington, DC 20008

For career courses  
approved under GI Bill  
 check for details.

**CHECK ONE CATALOG ONLY**  
 Computers and Microprocessors  
 Robotics  
 TV/Video/Audio Servicing  
 Telecommunications

Security Electronics  
 Electronic Music Technology  
 Digital Electronics Servicing  
 Computer Programming  
 Basic Electronics

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Accredited Member, National Home Study Council

3-090

# NEW PRODUCTS

Use the Free Information Card for more details on these products.

**FIBER-OPTIC DESIGNER'S KITS.** Providing a learn-by-doing approach to the design and use of fiber optics in data communications, Sintec's *Fiber-Optic Kits* are available in both simplex and duplex versions, for single or bi-directional links. No previous training or experience is needed to complete these hands-on courses. Each contains all the components required to construct a 10-meter data link, which can be extended to 60 meters with optional extension packages. The link operates off a single +5-volt power supply and interfaces to all TTL/CMOS logic devices. Each kit contains fiber-optic emitter(s), detector(s), printed wiring board(s), all necessary electronic components, and 10 meters of



CIRCLE 15 ON FREE INFORMATION CARD

either simplex or duplex cable. The fiber-optic connections for interfacing to the emitter, the detector, and two bulkheads are also included, along with a fiber-optic splice. The connections are made from a dry, non-polished interface that is easy to handle and requires no special tools. The parts are packaged in an impact-resistant plastic

box, which also contains assembly and fiber-termination instructions.

Prices for the fiber-optics designer's kits range from \$59.95 to \$89.95, depending on the version and the length.—**Sintec Company**, 28 8th Street, P.O. Box 410, Frenchtown, NJ 08825; Tel. 201-996-4095; Fax 201-996-3891.

**DIGITAL/ANALOG MULTIMETER.** Sporting both 3 1/2-digit and linear bar-graph readouts for measurement display to 4,000 counts, *B&K-Precision*'s model 2919 handheld digital/analog multimeter is designed for situations where the accuracy of a digital readout and the responsiveness of an ana-

log display are needed. The 41-segment bar graph, which is updated 20 times per second to follow changing values, simplifies peaking or level adjustments. "Data hold" immediately freezes the displayed digital reading, and "peak hold" holds the highest digital value obtained during a measurement, while "min/max" memory stores the lowest and highest reading observed.

The model 2912 also offers selectable auto- or manual ranging; measurement of voltage, current, and resistance; diode check; and an audible continuity check. Additional functions include capacitance measurement up to 40 mF and frequency to 400 kHz. The meter is

rated at 0.3% accuracy on DC volts, and spans 40 ranges, including the frequency counter and capacitance functions. It is well-protected against reverse polarity and overloads, and features high-energy fusing to protect the  $\mu$ A/mA current ranges.

The 2912 handheld analog/digital multimeter costs \$149.00.—**B&K-Precision**, Division of Maxtec International Corporation, 6470 West Cortland Street, Chicago, IL 60635; Tel. 312-89-9087.

**COAXIAL ADAPTER KIT.** Pomona's Model 5698 *Universal Adapter Kit* allows lab workers, field-service/installation technicians, and designers to quickly "mix and match" al-

most any combination of coaxial end termination styles, including banana plugs. The specially assembled kit allows users to make their own adapter combinations, such as SMA to BNC, or BNC to double banana plugs for connecting coax to instruments. The kit includes two male and two female of each the following: BNC, TNC, SMA, and "N" adapters. Four intermediate coupling nuts, one double banana plug, and one double banana jack/binding post round out the assortment.

Each of the double-banana jack/plug adapters are fitted with an integral coupler to accept any threaded coaxial connector. Individual connectors can be joined with a coupling nut to any other



CIRCLE 17 ON FREE INFORMATION CARD

to make the required coaxial assembly. The high-quality adapters, which come equipped with gold-plated center pins and silver-plated bodies, are packaged in a convenient reusable plastic case.

The model 5698 *Universal Adapter Kit* costs \$99.00.—**ITT Pomona Electronics**, 1500 East Ninth Street, P.O. Box 2767, Pomona, CA 91769; Tel. 714-623-3463, Fax 714-629-3317.



CIRCLE 16 ON FREE INFORMATION CARD



CIRCLE 18 ON FREE INFORMATION CARD

**BATTERY TESTER.** A quick, inexpensive means to determine the condition of a wide variety of batteries is provided by the *BT-20A Battery Tester* from A.W. Sperry. The compact, handheld instrument can be used to test all popular batteries from 1.25- to 22.5-volts DC—including hearing-aid batteries: "AAA," "AA," "C,"

and "D" cells; 6-volt lanterns; 3-volt lithium batteries; and 5.6- to 6-volt photo cells. The rugged tester is reliable and easy to use, and comes with a one-year warranty.

The model *BT-20A* battery tester costs \$15.95.—  
**A.W. Sperry Instruments Inc.**, 245 Marcus Boulevard, Hauppauge, NY 11788; Tel. 516-231-7050.

### HANDHELD LOGIC ANALYZER.

Intended as an affordable alternative to multiple logic probes, *Global Specialties*' model *LM-8 TTL* logic analyzer has trigger word recognition that allows it to be used in place of more complex logic analyzers for troubleshooting 8-, 16-, and 32-bit microprocessor circuits. The *LM-8* has eight input channels, an external clock input, and an oscilloscope trigger out-

put. The number of channels can be expanded to as many as 32 by linking four pods together and triggering from a 32-bit trigger word. The captured data can be displayed by the built-in LED's or on an oscilloscope. Each channel's trigger can be set to 0, 1, or "don't care." The logic status of each channel is continuously displayed on the LED's. Pulse stretching allows high-frequency or short-duration pulses to be viewed. The maximum

clock frequency is 25 MHz, with pulses as narrow as 10-ns wide being captured and displayed.

The *LM-8* provides two operating modes: RUN and TRIGGERED. In the RUN mode, the data is continuously updated every time the trigger word is recognized. In the TRIGGER mode, the data is captured and displayed until the trigger word is recognized, at which time the analyzer is halted and the last data held.

The *LM-8* handheld logic analyzer, complete with grabber leads for each data channel, costs \$249.95.—

**Global Specialties**, 70 Fulton Terrace, New Haven, CT 06512; Tel. 1-800-572-1028.



CIRCLE 19 ON FREE INFORMATION CARD

**MULTIMETER LEADS.** Silicon-rubber multimeter leads from *Test Probes, Inc.* remain soft and flexible even under conditions of



Model	UTC3000	2600II	2210A	1300II/A
Function	Freq. Period, Ratio, Interval, Avg. Preseale	Frequency	Frequency	Frequency
Range	10Hz-2.4GHz	10MHz-2.4GHz	10Hz-2.4GHz	1MHz-1.3GHz
Display	10 Digit LCD w/Function Annunciators	10 Digit LCD	8 Digit LED	8 Digit LED
RF Signal Strength Indicator	16 Segment Adjustable Bargraph	16 Segment Adjustable Bargraph	•	•
Price	\$375.	\$325.	\$239.	\$179.

Sensitivity: <1 to <10mV typical. Time Base:  $\pm 1\text{ppm}$ ;  $\pm .5\text{ppm}$ , add \$75. LED Models:  $\pm 2\text{ppm}$ , add \$80. LCD Models: Nicads & AC charger/adapter included. Carry Case, Antennas and Probes extra. One year parts & labor warranty on all products.

## OEI OPTOELECTRONICS

The only name in HANDI-COUNTERS

### Check These Incredible Features

#### On The All New UTC3000

- 10Hz to 2.4GHz Range. Simply amazing!
- 10 Digit LCD Display. 11Hz resolution to over 150 MHz direct. Readable in bright sunlight.
- RF Signal Strength Bargraph. 16 Segment, Zero, & Full Scale adjustment SEE the input signal!
- Super Sensitivity. <1mV 10-200MHz. <5mV to 2GHz for efficient antenna pickup.
- 6 Functions. Frequency, Period, Ratio, Time Interval, Average, & Preseale.
- Hold Button. Locks in your exact Measurement FAST!
- Extruded Aluminum Enclosure. Designed to fit every hand.
- Priced Right! Only \$375. Includes Nicads, AC Charger/Adapter, Or Select Our Most Popular

**HANDI-COUNTER**, the model 2210A that set the standard in handheld frequency counter technology! Value Priced at only \$239.

Professionals and Hobbyists all over the world have chosen **OEI** for 16 years! Shouldn't YOU?

**HANDI-COUNTERS!** ...Only from **OEI**! Choose the model that fits your needs... and your budget! **CALL NOW!**



Toll Free Order Line: 1-800-327-5912 FL(305)771-2050 • FAX(305)771-2052

Visa, MC, COD, Cash, M.O. accepted. Personal Check allow 3 weeks. 5% Shipping, Handling. (Maximum \$10) U.S. & Canada. 15% outside continental U.S.A. In FL add 6% sales tax. Full-line Product and Accessory Catalog available on request.

CIRCLE 184 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)




CIRCLE 20 ON FREE INFORMATION CARD

extreme cold. The *TLS2000* multimeter leads cost \$30.00.—**Test Probes, Inc.**, 9178 Brown Deer Road, San Diego, CA 92121; Tel. 619-535-9292.
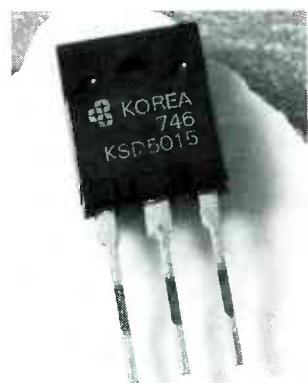
### PRE-ISOLATED POWER TRANSISTORS

For use in color monitors, power supplies, and high-voltage switching applications, **Samsung** is offering pre-



CIRCLE 21 ON FREE INFORMATION CARD

## LEARN TO BUILD & PROGRAM COMPUTERS WITH THIS KIT!

INCLUDES ALL PARTS, ASSEMBLY & LESSON MANUAL



MODEL  
MM-8000

\$129.00



Starting from scratch you build a complete computer system. Our Micro-Master® trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses the same machine language as IBM PC. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 E PROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. ADD 5% For Shipping.

**C&S SALES INC.** (800) 292-7711  
1245 Rosewood, Deerfield, IL 60015 (312) 541-0710  
15 Day Money Back Guarantee Write For Free Catalog

CIRCLE 109 ON FREE INFORMATION CARD

The *TLS2000* multimeter leads cost \$30.00.—**Test Probes, Inc.**, 9178 Brown Deer Road, San Diego, CA 92121; Tel. 619-535-9292.

isolated bipolar power transistors in TO-3PF packages that simplify mounting procedures. The isolated packages offer better EMI control for ungrounded heat sinks, require less mounting hardware, and are cost effective. The power transistors can handle 1500-volt collector-base voltage. The devices have a 5,000-volt isolation rating, eliminate bushings and isolation pads, and have no exposed metal surfaces other than the leads.

The pre-isolated power transistors have excellent thermal characteristics when mounted to a heat sink and an industry-standard footprint. The devices are built with special oversized lead frames for good heat-spreading performance. A thin, tightly controlled thermal epoxy over a back-mounting surface further improves their heat-spreading capabilities.

Eight devices—KSD5010-KSD5017—are available. When ordered in quantities between 100 and 999, the prices range from \$1.55 to \$2.10 each.—**Samsung Semiconductor**, 3725 North First Street, San Jose, CA 95134-1708; Tel. 408-434-5400.

**DIGITAL CLAMP METER.** Four advanced digital clamp meters introduced by **C.G. Instruments** have 3 1/2-digit displays and offer up to 4,000 counts. All four meters are UL listed and have rugged, drop-proof enclosures. They feature large clamping jaw openings to allow easy measurements of cables and bus bars up to 2.95 inches in diameter.

The *Soar 632 AC Clamp Meter* (shown in photo) has a basic accuracy of  $\pm 1\%$ , provides 3200 counts, and has an analog bar-graph indicator. Its features include auto and man-




CIRCLE 22 ON FREE INFORMATION CARD

ual range select, data-hold function, audible continuity test, and low power consumption. The 632 measures AC current to 1000 amps in two ranges, AC volts to 630 volts in two ranges, AC/DC volts up to 630 volts, and ohms to 3.2 Kohms in two ranges. The *Soar 641* and *Soar 642* each provide 4000 counts and feature an analog bar-graph indicator, data hold, peak hold, max hold, averaging functions, and diode audible continuity test capabilities.

The meters measure AC to 1000 amps in three ranges, AC/DC volts to 630 volts in three ranges, ohms to 4 Kohm in two ranges, frequency from 20 Hz to 999.9 Hz with 0.1 Hz resolution, and temperature from  $-50^\circ$  to  $+130^\circ\text{C}$ . The model 641 has an average-type sensing mode; the 642 offers true RMS. The fourth instrument in the group is the *Soar 643*, a true RMS, multifunction, AC/DC current clamp meter with 4000 count that measures AC/DC current to 1000 amps as well as all the features of the models 641 and 642.

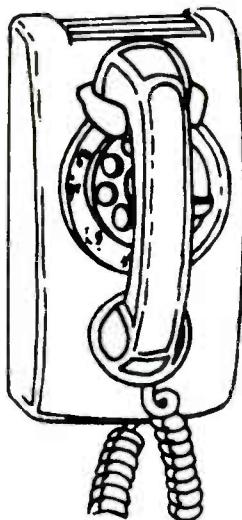List prices for the digital clamp meters start at \$124.95.—**C.G. Instruments Corp.**, 434 Windsor Park Drive, Dayton, OH 45459; Tel. 513-434-6952; Fax 513-434-7643. R-E




## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$940.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.


Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

FAX: 516-293-3115

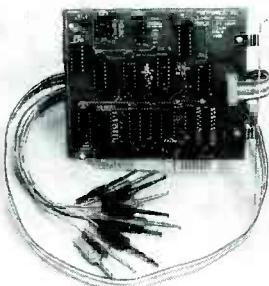

**LOW COST PC LOGIC ANALYZER.** Designed for students and hobbyists working with 5V TTI/CMOS signals in the KHz range. 36" data cable—eight channels, external clock, ground. Selectable trigger & clock edge, internal clock (1Hz-100Khz). Full-featured software, state table graphics, file/print utilities, etc. Over 100,000 samples/sec on 12 Mhz AT. LA1—\$99.95. PHOTRONICS, INC. 109 Camille St., Amite, LA 70422 (504) 222-4146.

CIRCLE 199 ON FREE INFORMATION CARD

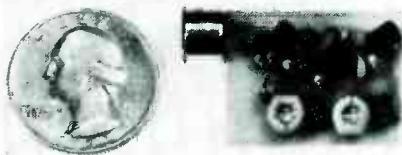

**SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER** on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHZ. Use with any FM radio. Complete kit \$29.95 + \$1.50 S + H. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD



**APPLIANCE REPAIR HANDBOOKS**—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. \$2.65 to \$7.90 each. Free brochure. APPLIANCE SERVICE, P.O. Box 789, Lombard, IL 60148. (312) 932-9550.


CIRCLE 84 ON FREE INFORMATION CARD



**CABLE TV CONVERTERS AND DE-SCRAMBLERS** SB-3 \$79.00 TRI-BI \$95.00 MLD-\$79.00 M35B \$69.00 DRZ-DIC \$149.00. Special combos available. We ship COD. Quantity discounts. Call for pricing on other products. Dealers wanted. FREE CATALOG. We stand behind our products where others fail. One year warranty. ACE PRODUCTS. P.O. Box 582, Saco, ME 04072 1 (800) 234-0726.

CIRCLE 75 ON FREE INFORMATION CARD

## ONE HOUR PROTOTYPING

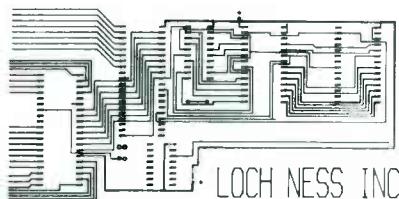

LOCH NESS INC.


**1 HOUR PROTOTYPING!!** Develop Multi-layered Printed Circuit Boards in Less than 1 Hour with the New Loch Ness Quick-circuit Kit! Process is Patent Pending. No dangerous UV lights! No hole drilling! No mistakes! Kit comes with everything to make 216 sq. inches of PCB. Money back guarantee. Send \$65.00 to LOCH NESS, INC., 3700 Colfax Avenue South, Minneapolis, MN 55409. 1-800-323-8623.

CIRCLE 193 ON FREE INFORMATION CARD



**THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME**, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered—never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHZ. Complete kit \$29.95 + \$1.50 S + H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD

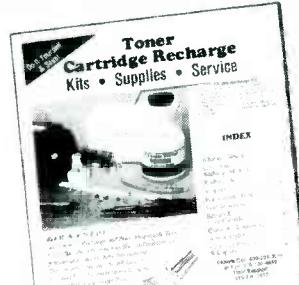


**GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME**—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from \$9.95 in qty and you can sell recharged toner cartridges for \$40.00 to \$55.00 each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. CHENESKO PRODUCTS, 62 N Coleman Rd., Centereach, NY 11720, 516-736-7977, 800-221-3516, Fax: 516-732-4650

CIRCLE 183 ON FREE INFORMATION CARD
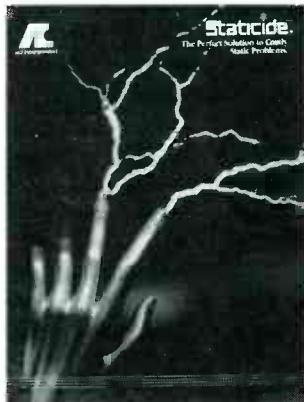
# NEW LIT

Use the Free Information Card for fast response.



CIRCLE 23 ON FREE INFORMATION CARD

**STATICIDE: THE PERFECT SOLUTION TO COSTLY STATIC PROBLEMS.** ACL Incorporated, 1960 East Devon Ave., Elk Grove Village, IL 60007; Tel.

**708-981-9212; fax 708-981-9278; free.**

This 8-page, full-color catalog of static-control products features Staticide liquids, wipes, floor finish, electrostatic locators, work-surface cleaners, and surface-resistivity meters. New products include lint-free wipes, dual-tipped foam swabs, and the *Tech Essentials* cleaning kit line.

### CORDLESS TELEPHONE BATTERIES.


**Power Pak, Inc., 6216 Oakton Street, Morton Grove, IL 60053; Tel. 1-800-637-2212; free.**

This guide to replacement batteries for cordless telephones is written to

help the user make an intelligent, well-informed selection. The brochure is filled with specifications and complete cross-reference material, along with other information about replacement batteries.



CIRCLE 24 ON FREE INFORMATION CARD

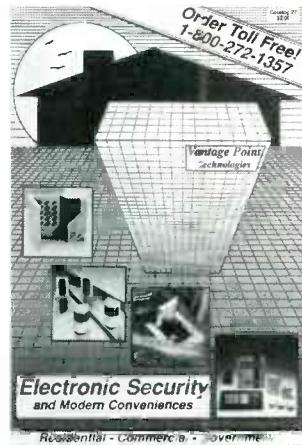

CIRCLE 25 ON FREE INFORMATION CARD

**ELECTRONIC SECURITY AND MODERN CONVENiences.** Vantage Point Technologies, 630 Nordahl Road, Suite P9, San

## CRAMOLIN® DeOxidizer

DEOXIDIZES • CLEANS • PRESERVES • LUBRICATES • IMPROVES CONDUCTIVITY

For All Metals, Including Gold!

CRAMOLIN® DeOxidizer... is a fast-acting deoxidizing solution that cleans, preserves, and lubricates all metal surfaces including gold.

When applied to metal contacts, connectors and other metal surfaces, CRAMOLIN® DeOxidizer removes resistive oxides and forms a protective molecular layer that adheres to metal surfaces, preventing future oxidation. CRAMOLIN® DeOxidizer maintains maximum electrical conductivity, reduces wear, and has excellent migration properties.

#### IDEAL FOR:

- Switches & Relays • Connecting Cables & Adaptors
- Edge Connectors • Terminal Strips • Plugs & Sockets
- Gold Plated Connectors • Potentiometers • Battery Contacts

#### USED BY THOSE WHO DEMAND THE BEST;

- Bell & Howell • Capital Records • Dolby Laboratories
- Hewlett Packard • John Fluke Mfg. • McIntosh Labs
- MCI (Sony) • Motorola • NASA • Nakamichi
- RCA • Switchcraft



- Economical/ Long Lasting
- Ozone Safe Propellents
- Operates in Any Position
- Contents Completely Dispensed
- Uniform Spray Pattern

Since 1956  
**CAIG**  
LABORATORIES, INC.

P.O. Box J • Escondido, CA 92025-0051  
(619) 743-7143 • FAX: (619) 743-2460

CIRCLE 50 ON FREE INFORMATION CARD

## CABLE - TV

### SIGNAL REMOVERS

- FOR ELIMINATION OF SEVERE INTERFERENCE
- FOR "CENSORING" OF ADULT BROADCASTS



- ATTENUATION - 45 dB TYPICAL
- BANDWIDTH - 4 MHz AT 5 dB POINTS
- INSERTION LOSS - 2 dB

MODEL	TUNING RANGE	FOR CHANNELS	PASSBAND	PRICE	SHIPPING
23H	50-66 MHz	2.3 (or 6 meter ham)	50-300 MHz	\$30	NO SHIPPING
46FM	66-108 MHz	4.5.6 (or any FM)	50-300 MHz	\$30	or C.O.D. CHARGES
1417	120-144 MHz	14(A) 15(B) 16(C) 17(D)	50-400 MHz	\$30	
1822	144-174 MHz	18(E) 19(F) 20(G) 21(H) 22(I)	50-400 MHz	\$30	
713	174-216 MHz	7.8.9.10.11.12.13	50-400 MHz	\$30	

3 for \$75 - 10 for \$200 - mix or match

CALL TOLL FREE FOR C.O.D. OR SEND CHECK TO ORDER  
FAST DELIVERY  
30 DAY MONEY BACK GUARANTEE (3 FILTER LIMIT)

**Star Circuits**

P. O. Box 94917  
Las Vegas, NV 89193-4917

**1-800-433-6319**

**Marcos, CA 92069;  
Tel. 800-272-1375 or  
619-565-1863; free.**

Electronic security systems and accessories designed for do-it-yourself installations are described in a clear, easy-to-understand style in this 32-page catalog. The brochure covers a broad range of high-tech systems for residential, commercial, and government needs—ranging from no-wire home alarms to state-of-the art computer-based building-management system. Some of the products described include burglar-alarm systems, motion detectors, glass protection, switches, fire detectors, sirens, vehicle alarms, notification systems, CCTV, and building-access systems, along with special tools and books. Helpful installation and product tips are provided throughout the catalog.

R-E

## Cable TV

### Descrambler Article Parts

We stock the exact Parts for several articles published in Radio-Electronics magazine on building your own Cable TV Descrambler.

#### February 1984 SB-3 Type

701 Parts Pkg.....\$19.00  
Includes all original parts.  
702 PC Board.....7.95  
Original 3X4 etched, drilled and Silk-Screen pc board.  
704 AC Adaptor.....7.95  
12 to 18 Volt DC @ 200ma.  
701, 702 & 704.....29.00  
All three for special saving.

#### February 1987 Tri-Mode

301 Parts Pkg.....29.00  
Includes all original parts.  
302 PC Board.....7.95  
Original 5X8 etched, drilled and Silk-Screen pc board.  
304 AC Adaptor.....7.95  
12 to 18 Volt DC @ 200ma.  
301, 302 & 304.....39.00  
All three for special savings.  
Tri-Mode Tutorial.....7.95  
26 pages of in-depth info.

#### May 1990 Universal

901 Parts Pkg.....\$49.00  
Includes all original parts.  
902 PC Board.....9.95  
Original 4X7 etched, drilled and Silk-Screened pc board.  
904 AC Adaptor.....8.95  
12 Volts AC @ 350ma.  
901, 902 & 904.....59.00  
All three for special savings.  
CD22402E.....12.95  
Video sync IC (IC-9)

#### Snooper Stopper...\$39.00

Prevent Descrambler detection with snooper stopper/data blocker and protect your privacy.  
Includes free article on Cable Snooping.

#### Macrovision Kit...\$29.00

Macrovision.....now you see it, now you don't with our macro-scrubber kit.  
Originally Published in Radio-Electronics.

#### 58 Channel Cable TV Converter with infra-red remote .....\$69.95

Re-Manufactured Jerrold 400 with new remote. Channel 3 output.  
Compatible with all External Descramblers.

## CALL TOLL FREE 1-800-332-3557

Outside USA Call 1-508-699-6935

Visa, MasterCard and COD. Free Catalog.  
Add \$4.00 S&H, \$6.50 Outside USA.  
D & D Electronics, Inc. PO Box 3310, N. Attleboro, Ma. 02761



CIRCLE 194 ON FREE INFORMATION CARD

# VALUE PRICING ON BK PRECISION

SAVE!

FULL 3-YEAR  
WARRANTY ON  
ALL B&K SCOPES

from  
**JOSEPH ELECTRONICS**

**BONUS VALUE!**  
EXTRA UNIVERSAL SWITCHABLE  
SCOPE PROBE \$19.00

Only with B&K Scope purchases. Limit 2 per scope.

\$39 Value


3-position — 1x, ref, 10x •  
Risetime less than 1.5 nsec •  
Excludes interference even on  
most sensitive ranges • Rug-  
ged; withstands heat, humidity •  
Universal for all scopes.



#### 20 MHz DUAL-TRACE OSCILLOSCOPE

1 mV/div sensitivity • 20MHz response at a true -3dB • AUTO/NORM triggered sweep operation with AC, TVH, TVW and Line coupling • Calibrated 18-step timebase with x10 magnifier • X-Y operation • Built-in calibration source • Bright, sharp CRT with P31 phosphor • Tilt stand and soft handle. Includes Probes. Model 2120

Reg. \$549  
**\$397.50**

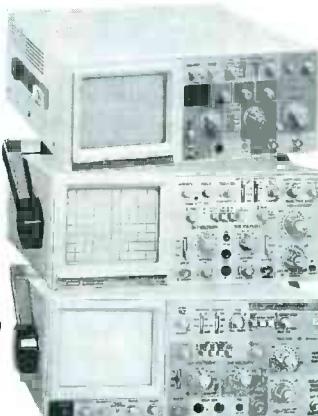

#### 20 MHz DUAL-TRACE DELAYED SWEEP SCOPE

1 mV/div sensitivity • Delayed sweep in 18 ranges • Built-in component tester for capacitors, inductors, diodes, transistors, zener diodes • 20MHz response at a true -3dB • AUTO/NORM triggered sweep operation with AC, TVH, TVW and Line coupling • Calibrated 20-step timebase with x10 magnifier • X-Y operation • Built-in calibration source • Bright, sharp CRT with P31 phosphor • Tilt stand; soft handle. Probes incl. Model 2125

Reg. \$646  
**\$525.00**

#### 60 MHz DUAL-TRACE DUAL TIME BASE SCOPE

1 mV/div sensitivity • Sweep to 5 ns/div • 22 calibrated ranges — main time base • 19 calibrated ranges — delayed time base • 12kV accelerating voltage • Signal delay line • Beam finder • V mode • Component tester • Channel 1 output, Z axis input • X-Y operation • Single sweep. Probes included. Model 2160

Reg. \$1099  
**\$888.00**

#### HAND-HELD 3 1/2 DIGIT LCD 'TEST BENCH' MULTIMETER

41 voltage ranges • Measures AC & DC with 0.5% DCV accuracy • DC & AC currents 200 µA to 20A • Resistance 0.1Ω to 2000 MΩ • Frequency 20 kHz to 200 kHz • Capacitance up to 20pF • Logic Level (TTL) • Transistor gain • Diode junction test • Drop-resistant case • Tilt stand. Model 388-HD



**OUR BEST  
PRICE EVER \$108.50**

#### DUAL TRACE DIGITAL/ANALOG STORAGE SCOPE

20 MHz analog bandwidth • 10Ms/sampling rate • 2k memory per channel • 20MHz equivalent time sampling • Pre-trigger capture. Probes included.

Model 2522  
Reg. \$995  
**\$848.00**

#### 100 MHz 3-TRACE DELAYED SWEEP SCOPE

1 mV/div sensitivity • Sweeps to 2ns/div • 23 calibrated ranges; 20 on delayed time base • Calibrated delay time multiplier • Signal delay line • 19kV accelerating voltage • V mode triggering • Channel 1 output. Probes included.

Model 2190  
Reg. \$1645  
**\$1325.00**

#### 0-30V DC 0-3A POWER SUPPLY

Low ripple • Regulated constant volt or current output • 2 current ranges • Isolated output — float, ground either polarity • Overload, reverse polarity protection • Parallel, series capability • 1-year warranty.

Model 1630  
Reg. \$375  
**\$248.00**

#### 0-16V DC 0-10A POWER SUPPLY

Continuously variable voltage & current • Constant-voltage & constant-current modes • Voltage & current analog meters • 2A and 10A current range limits. 1-year warranty.

Model 1646  
Reg. \$489  
**\$398.00**

#### 0-150V AC 2A POWER SUPPLY

Variable isolated 0-150 VAC, 2 amp continuous output • Voltage or current display • Isolation transformer eliminates shock hazard. 1-year warranty.

Model 1653  
Reg. \$239  
**\$188.00**

CALL TOLL-FREE - SAME-DAY SHIPPING

**Joseph 1.800.323.5925**  
8830 N. Milwaukee Av. Niles, IL 60648 • 708-297-4200 FAX 708-297-6923













Call or write for our 528 pg. Catalog. Only \$4.95 -- FREE with order.



# SELECT 5 BOOKS
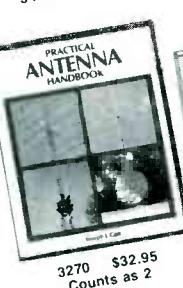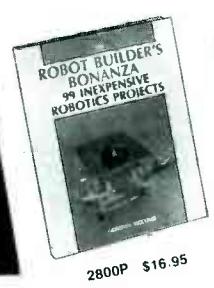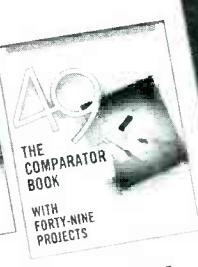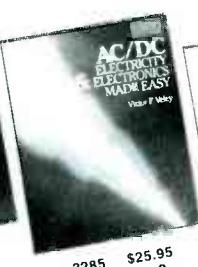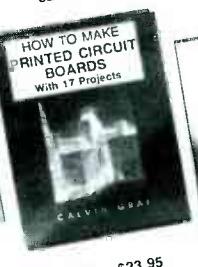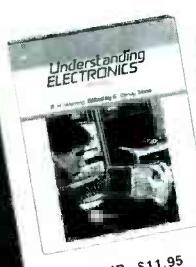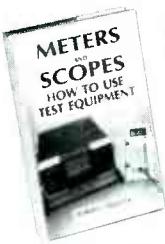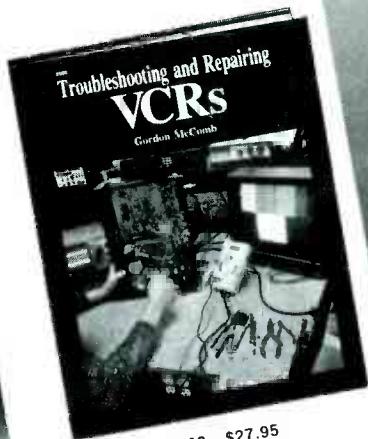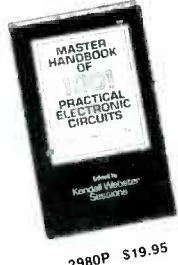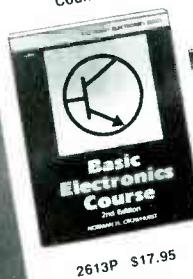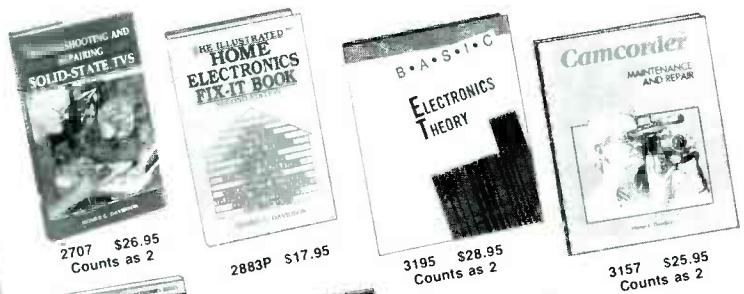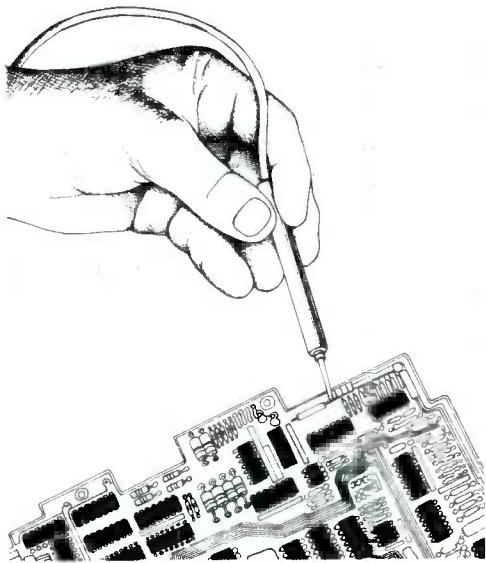
## for only \$4<sup>95</sup>

(values to \$130.70)  
and get a *FREE* Gift!



# For over 25 years, your most complete source for electronics books.

An Absolutely No-Risk Guarantee.



**Membership Benefits • Big Savings.** In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' prices. • **Bonus Books.** Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. • **Club News Bulletins.** 15 times per year you will receive the Book Club News, describing all the current selections—mains, alternates, extras—plus bonus offers and special sales, with scores of titles to choose from. • **Automatic Order.** If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. You will have at least 10 days to decide. As a member, you agree to purchase at least 3 books within the next 12 months and may resign at any time thereafter. • **Ironclad No-Risk Guarantee.** If not satisfied with your books, return them within 10 days without obligation! • **Exceptional Quality.** All books are quality publishers' editions especially selected by our Editorial Board.

All books are hardcover unless number is followed by a "P" for paperback. (Publishers' Prices Shown)

©1990 ELECTRONICS BOOK CLUB, Blue Ridge Summit, PA 17294-0810

**Call Toll-Free**  
**1-800-233-1128 to join Now!**

## FREE when you join!

### 15 Easy Electronic Projects From Delton T. Horn

Projects you can build—some unique, some old favorites—from the author's vast treasury of electronics know-how.

*MM*  
\$7.95  
Value!

### Delton T. Horn's All-Time Favorite Electronic Projects



## ELECTRONICS Book Club

Blue Ridge Summit, PA 17294-0810

YES! Please accept my membership in the Electronics Book Club and send the 5 volumes listed below, plus my FREE copy of *Delton T. Horn's All-Time Favorite Electronic Projects* (3105P), billing me \$4.95. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase at least 3 books at regular Club prices during the next 12 months and may resign any time thereafter. A shipping/handling charge and sales tax will be added to all orders.

--	--	--	--	--

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Phone \_\_\_\_\_

Signature \_\_\_\_\_

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club.

RE990

# Radio Shack Parts Place<sup>SM</sup>

## YOUR SOURCE FOR PROJECT AND REPAIR ELECTRONICS

### Try Our Special-Order "Hotline"



#### ICs, Crystals, Tubes, Much More

Your Radio Shack store manager can special-order a wide variety of parts and accessories from our main warehouse. Over 200,000 items are available including vacuum tubes, ICs, microprocessors, phono cartridges and styli, crystals for scanners and computers, even SAMS Photofacts® manuals. Best of all, there are no handling charges or minimum order requirements. Your order is sent directly to the Radio Shack near you and we notify you when it arrives. Delivery time for most items is about a week.

#### Infrared Module

##### Complete, Easy-to-Use IR Detector




Heart of a remote-control project! Combines detector, limiter, bandpass, demod, integrator and comparator in a compact 3-lead module. #276-137 . . . . . 3.49

#### Neater Wiring



(1) Heat-Shrink Tubing,  $\frac{1}{16}$  to  $\frac{1}{2}$ " sizes. #278-1627 . . . . . Pkg. of 7/1.79  
 (2) Cable Tie/Markers. For cables up to  $\frac{5}{8}$ " dia. #278-1648 . . . . . Pkg. of 10/2.49  
 (3) Wire Markers. 630 "peel and stick" characters. #278-1650 . . . . . Set/1.79

#### Resistance Items

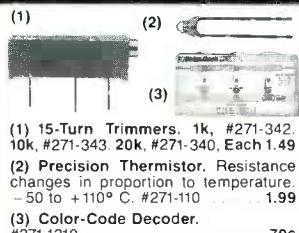

(1) 15-Turn Trimmers. 1k, #271-342. 10k, #271-343. 20k, #271-340. Each 1.49  
 (2) Precision Thermistor. Resistance changes in proportion to temperature. -50 to +110° C. #271-110 . . . . . 1.99  
 (3) Color-Code Decoder. #271-1210 . . . . . 79c

#### Shielded D-Sub Hoods

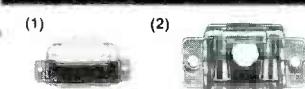



Fig.	Description	Cat. No.	Each
1	9-Position Metal	276-1508	2.19
	25-Position Metal	276-1510	2.79
2	9-Pos. Metalized	276-1513	1.49
	25-Pos. Metalized	276-1536	1.99

#### TNC and Mini-UHF Connectors



(1) TNC Twist-On Male for RG-58 Cable. #278-140 . . . . . 1.99  
 (2) TNC Double-Female. #278-142. 1.99

Fig.	Accepts	Fits TNC	Cat. No.	Each
3	PL-259	Female	278-118	3.49
4	BNC Male	Female	278-145	4.99

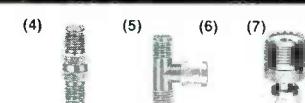

(5) Mini-UHF Double-Female. Joins two male mini-UHFs. #278-172 . . . . . 2.49  
 (6) Mini-UHF T Adapter. Female-male-female power divider. #278-173 . . . . . 3.99  
 (7) UHF Adapter. Accepts PL-259. Fits female Mini-UHF. #278-174 . . . . . 3.99

#### Electronic Counter Module



Prewired! Great for a traffic or event counter. Counts up to 99,999. Advanced (or reset) by external switch closure or digital circuit. Accepts count rate up to 7 Hz. Has  $\frac{1}{2}$ " liquid crystal display. Requires "AA" battery. With data. #277-302 . . . . . 16.95

#### Foldup Autoranging DVM



Select the function and this precision Micronta® meter sets the range. Has automatic power-off when shut, detented hinge for best viewing angle. Measures to 1000 VDC, 500 VAC, 10A AC/DC, 2 megohms resistance. Requires 2 "AA" batteries. #22-193 . . . . . 69.95

Since 1921 Radio Shack has been the place to obtain up-to-date electronic parts as well as quality tools, test equipment and accessories. Today, with our big in-store selection and convenient special-order service, Radio Shack continues its tradition of supplying high-tech products at competitive prices. We're America's Technology Store with over 7000 locations—NOBODY COMPARES

Prices apply at participating Radio Shack stores and dealers. Radio Shack is a division of Tandy Corporation

#### Battery Special-Order Service



##### Hundreds of Types Available

In addition to our large in-store stock, Radio Shack can now supply almost any currently manufactured consumer-type battery—for cordless phones, computer memory, camcorders, walkie-talkies, pagers and more. Batteries are sent from our main warehouse to the Radio Shack near you. We notify you when they arrive and there's no postage or handling charge.

#### Tantalum Caps



High capacitance in a tiny size

μF	WVDC	Cat. No.	Each
0.1	35	272-1432	.59
0.47	35	272-1433	.59
1.0	35	272-1434	.59
2.2	35	272-1435	.69
10	16	272-1436	.79
22	16	272-1437	1.19

#### "Snap" RFI Choke



Snap-Together Toroid Cores. Effective "roadblock" to radio-frequency interference. Just wind on AC, phone, computer, coax or audio cable, then snap choke together. #273-104 . . . . . Set of 2/7.95

#### Rod Antennas



For projects or replacing damaged antennas on cordless handsets and bases, walkie-talkies and radios. We have over a dozen styles in stock. For example:

Sections	Extended	Cat. No.	Each
5	13"	270-1407	2.79
6	17 3/4"	270-1409	2.59
4	34 3/4"	270-1402	3.79

#### Solderless IDC-Type Connectors

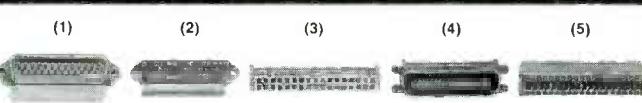


Fig.	Description	Cat. No.	Each
1	25-Position D-Sub Male	276-1559	3.99
2	25-Position D-Sub Female	276-1565	3.99
3	34-Position Header	276-1525	2.49
4	36-Position Male Printer Connector	276-1533	4.99
5	34-Position Card-Edge Connector	276-1564	1.99

#### Dual-Power Soldering Iron



Go from 15 to 30 watts with the flick of a switch. Has replaceable tip. 8 1/4" long. UL listed AC. #64-2055 . . . . . 9.49  
 Replacement Tip. #64-2065 . . . . . 1.19  
 Chisel Tip. #64-2056 . . . . . 1.19

CIRCLE 78 ON FREE INFORMATION CARD

# BUILD R-E'S VOCAL STRIPPER



**Build this lead  
vocal filter  
and test  
your singing  
ability.**

TERRY J. WEEDEER

ALMOST EVERYONE ENJOYS LISTENING TO music, and just about as many people enjoy singing along to their favorite songs. If you're one of the many people who loves to sing, you may be interested in a clever audio device that filters out lead vocals from a stereo recording, leaving just the background music. For under \$50.00, you can build this unique audio filtering device. Impress your friends with this Karaoke-like audio system and enjoy hours of singing pleasure.

Filtering out the vocal tracks from a recording is not as simple as merely eliminating the midrange frequencies. Along with

the vocals, the midrange frequencies contain a large portion of the music. Vocal filtering is quite easy, however, if you take advantage of the way stereo recordings are mixed.

#### Stereo mixing

When mixing is done in a studio, each instrument or voice is assigned a position relative to left (L) and right (R) channels. Some instruments are recorded at higher levels on the right channel so that their sounds seem to come from the right side of the stage. Others are recorded on the left channel for the opposite effect. Lead vocals and instru-

ments such as the bass drum and bass guitar are usually recorded at the same level on both channels so they seem to come from center stage. That is what makes lead vocal filtering possible.

Vocal signals, which consist primarily of mid-high range frequencies, can be filtered out by a series of filtering stages shown in Fig. 1. Bass instruments, corresponding to a lower frequency range, can be diverted to a final mixing stage so that the music is not filtered out along with the vocals.

A signal from one channel is inverted and subtracted from the

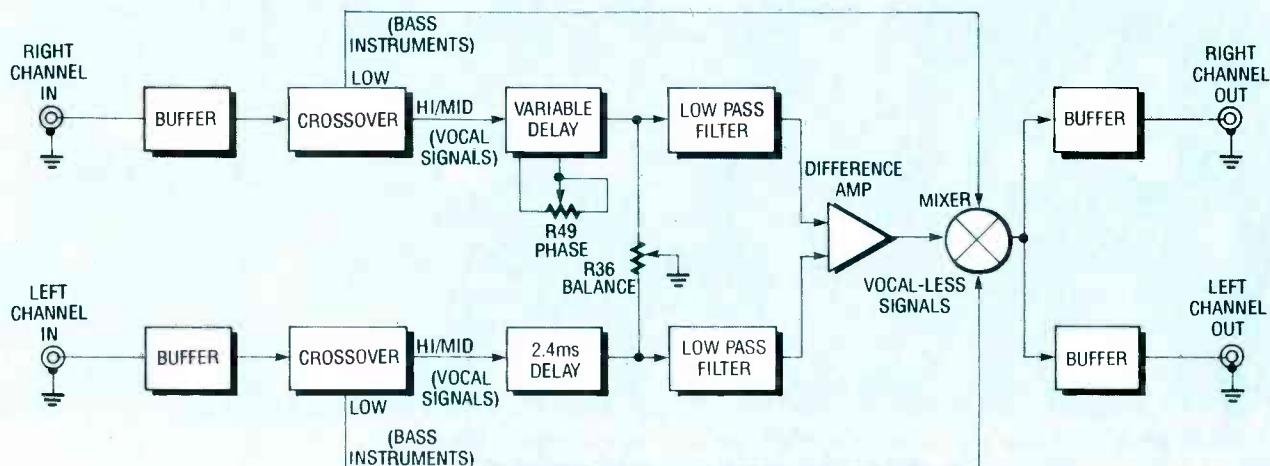


FIG 1—BLOCK DIAGRAM OF FILTER NETWORK. Right channel signal is inverted and subtracted from the left channel, cancelling the lead vocals. Low frequencies are bypassed by an active crossover and remixed with the difference signal, without the vocals.

other (L-R), which causes the lead vocals that are common to both channels to cancel out. The music common to the left and right channel remains unchanged. Unfortunately, along with the lead vocals, all low frequencies are common to both channels and must bypass the cancellation circuit. A simple active crossover removes the low frequencies so that they can be remixed with the vocal-less signal at a later stage.

From the active crossover stage, all midrange and high fre-

quencies pass through a variable delay stage, which is used to align the left and right channel signals so that they are exactly 180° out of phase with each other. Proper signal cancellation is achieved only when both signals are 180° out of phase. The low-pass filter stage filters out unwanted high frequencies from the variable delay stage. The output of the low-pass filter enters a difference amp, where the lead vocal signals cancel, and is then remixed with the low frequencies at the final mixing stage.

## Here's how it works

The schematic of the lead vocal filter is shown in Fig. 2. The left and right channel signals are coupled through C1 and C2 to buffer amps IC4-a and IC4-b. From the buffer amps, the left and right channel signals pass through active crossovers IC5-a and IC5-b, sending all low frequencies to a final mixer IC6-c, and all middle and high frequencies to analog delay lines IC1 and IC2, RD5106 256-sample bucket-brigades. Integrated circuit IC2 delays the left channel signal by

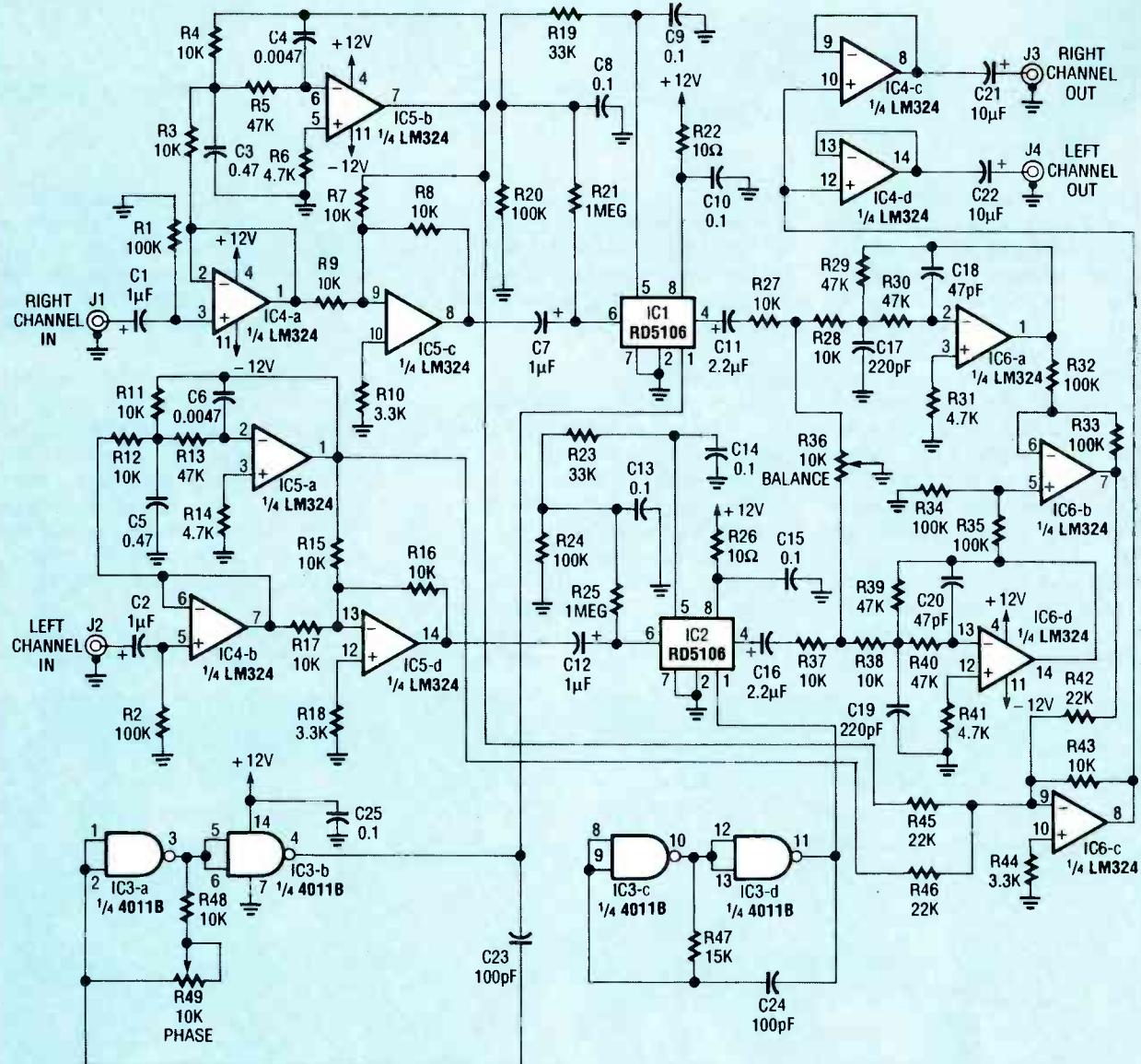


FIG. 2—SCHEMATIC OF LEAD VOCAL FILTER. Right and left channel signals pass through IC4-a and -b buffer amps into active crossover IC5; low frequencies are sent to IC6-c mixer, middle and high frequencies are sent to analog delay lines of IC1 and IC2. That output passes through IC6-a and -d to filter high frequency sample steps. IC6-b signals are remixed with low frequencies by IC6-c and are sent to final output via IC4-c and -d buffers.

2.4 ms. set by the fixed-frequency clock generated by  $\frac{1}{2}$ -IC3, R47, and C24. The right channel signal is delayed by IC1 with a variable-frequency clock generated by  $\frac{1}{2}$ -IC3, R48, R49, and C23. Potentiometer R49 is used for phase adjustment.

The output of each delay line

**All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.**

R1, R2, R20, R24, R32, R33-R35—100,000 ohms

R3, R4, R7-R9, R11, R12, R15, R16, R17, R27, R28, R37, R38, R43, R48—10,000 ohms

R5, R13, R29, R30, R39, R40—47,000 ohms

R6, R14, R31, R41—4700 ohms

R10, R18, R44—3300 ohms

R19, R23—33,000 ohms

R21, R25—1 megohm

R22, R26—10 ohms

R36, R49—10,000 ohms, potentiometer

R42, R45, R46—22,000 ohms

R47—15,000 ohms

**Capacitors**

C1, C2, C7, C12—1  $\mu$ F tantalum

C3, C5—0.47  $\mu$ F tantalum

C4, C6—0.0047  $\mu$ F Mylar

C8, C9, C10, C13, C14, C15, C25—0.1  $\mu$ F Mylar

C11, C16—2.2  $\mu$ F tantalum

C17, C19—220 pF ceramic disc

C18, C20—47 pF ceramic disc

C21, C22—10  $\mu$ F electrolytic

C23, C24—100 pF ceramic disc

**Semiconductors**

IC1, IC2—RD5106 256-sample bucket-brigade analog delay line, EG & G-Reticon

IC3—4011 quad two-input NAND gate

IC4-IC6—LM324 quad op-amp

**Miscellaneous:** Perforated circuit board, standoffs, mounting hardware, hookup wire, shielded cable, 18-AWG power supply cord, strain relief, and four RCA jacks for J1-J4.

**Power supply parts**

F1—0.5 amp fuse and fuseholder

T1—24 VAC center-tapped transformer

BR1—1.5-amp bridge rectifier, 100 PIV

C1, C2—1000  $\mu$ F, 25 volts, electrolytic

C3, C4—10  $\mu$ F, 16 volts, electrolytic

C5, C6—0.1  $\mu$ F, ceramic disc

D1, D2—12-volt Zener diode

R1, R2—220 ohms

R3—1000 ohms

S1—SPST switch, 1 amp


LED1—light emitting diode, any color

**Note: The following are available from Weeder Technologies, 14773 Lindsey Rd., Mt. Orab, Ohio 45154: An etched, drilled, and plated PC board, \$15.00; a basic parts kit including all resistors, capacitors and semiconductors (not including power-supply components), \$29.00. Please include \$2.00 for shipping and handling in the U.S., \$3.00 in Canada. Ohio residents add 5.5% sales tax. Allow 4 to 6 weeks for delivery.**


from IC1 and IC2 passes through low-pass-filters IC6-a and -d, and their associated parts, to filter out high-frequency sample-steps produced by IC1 and IC2. Balance control R36 is adjusted for equal amplitude of the left and right channels. IC6-b is a difference amplifier which cancels all lead vocals that are common to both channels. The resulting signal from IC6-b is remixed with low frequencies by IC6-c and is then sent to the output via buffers IC4-c and IC4-d.

etched and drilled PC board is available from the source in the Parts List or you can make your own from the foil pattern provided here. Mount the vocal filter components as shown in the parts placement diagram, Fig. 3. Use shielded wire to connect the RCA jacks, and ground them properly, either by mounting them to a grounded chassis or by soldering ground wires to their cases. The DC power supply leads from the power-supply board should be twisted to reduce noise transmission.

If you don't use PC mounted potentiometers for R49 and R36, be sure to keep their connecting leads short and twist them to re-

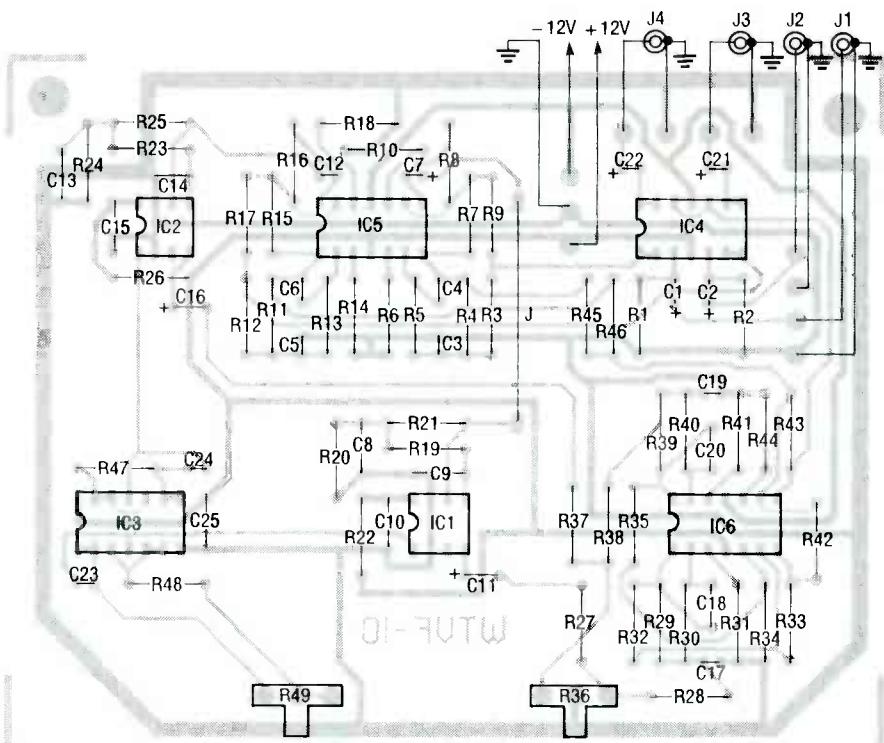

**FIG. 3—PARTS PLACEMENT DIAGRAM.** Remember to connect the jumper lead, use shielded cables for the RCA jacks and twist the supply leads before soldering to the LED and main PC board.

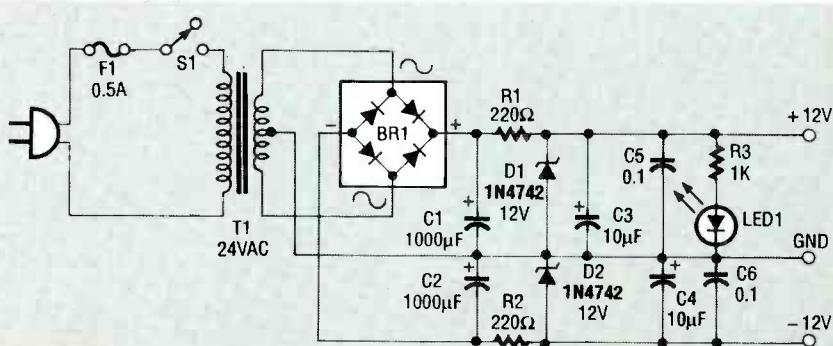

**FIG. 4—POWER SUPPLY SCHEMATIC** for the lead vocal filter circuit.


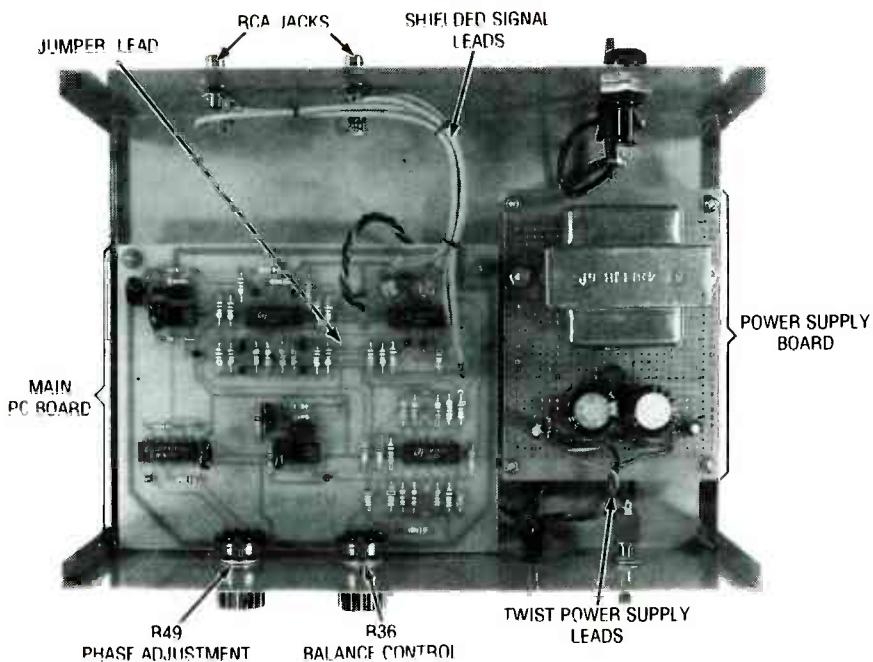


FIG. 5—AN INTERNAL VIEW OF THE LEAD VOCAL FILTER

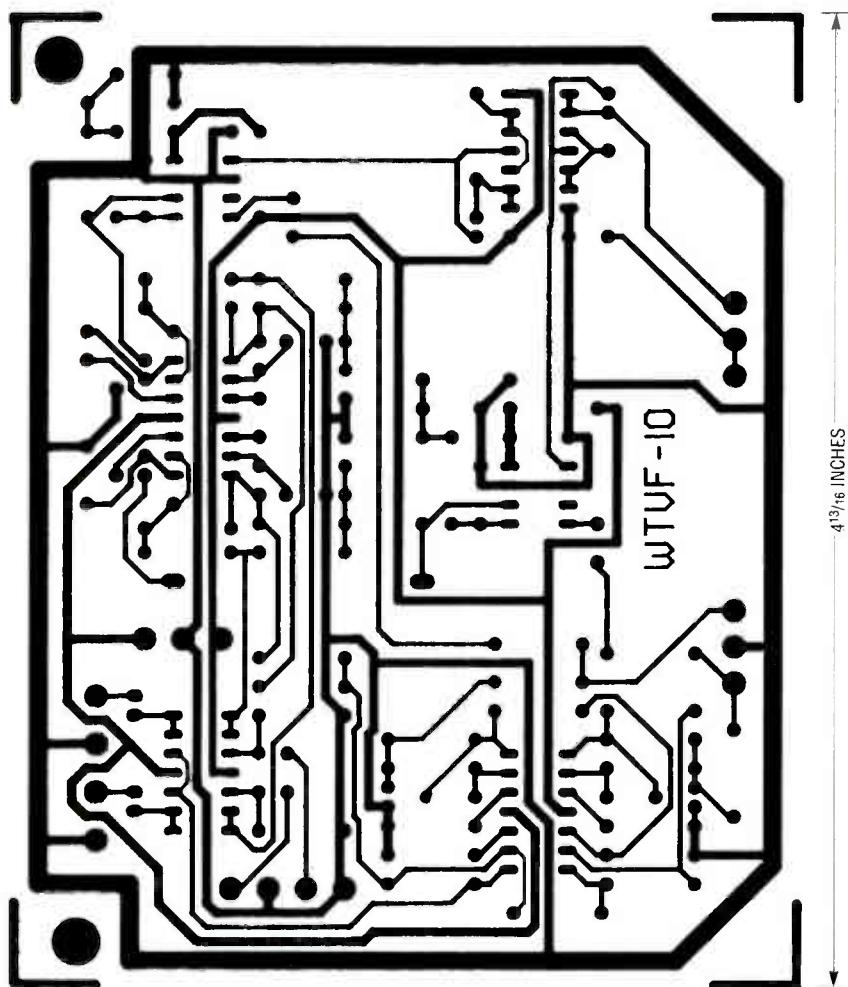

duce noise and hum pickup. It is preferable, though, to use shielded leads for these connections. These potentiometers

should be grounded by mounting to a grounded chassis.

A simple power supply, like the one shown in Fig. 4, may be used

for this device. The power supply can be mounted on a perforated circuit board, as long as you closely follow the component connections shown on the schematic. Although optimum performance is obtained with a  $\pm 12$  volt supply, the vocal filter gives good results using two 9-volt batteries connected in series.

The power supply and main PC board should be adequately enclosed before operating the vocal filter. A metal enclosure is recommended, as a 120-volt line potential is exposed in the power supply circuit (see Fig. 5).

#### Hook up and operation


The vocal filter should be connected into the tape loop of your stereo system. Use shielded cables with phono connectors to connect inputs J1 and J2 to the "record" tape monitor jacks on your stereo, and outputs J3 and J4 to the "play" side. To use the vocal filter with a tape deck that normally uses tape monitor jacks, plug the output "play" jacks of the tape deck into J1 and J2 of the vocal filter. Plug J3 and J4 into the input or "play" jacks of the stereo. Make sure you apply power to the vocal filter before turning on the stereo; sensitive components in the vocal filter may be damaged if a signal is applied before power is turned on.

Set R36 to its middle position, play a stereo sound track or tune in an FM stereo broadcast, and switch in the tape monitor. Adjust R49 for minimum lead vocals, then adjust R36. Repeat that process until the lead vocals are suppressed.

If you think the vocal filter is not working, tune in to a mono FM broadcast. If you can't find one, tune to a stereo station, and adjust the tuning knob either way, just enough so the stereo light goes off. If the vocal filter operates properly, you should be able to adjust R36 and R49 to filter out all music except low frequencies.

With a little help from **Radio Electronics**, you now have the know-how to build a fairly simple audio filtering device in just a few short evenings. Once completed, you can use this system to practice singing alone, or be creative and have all your friends over for a Karaoke party!

# Build R-E's

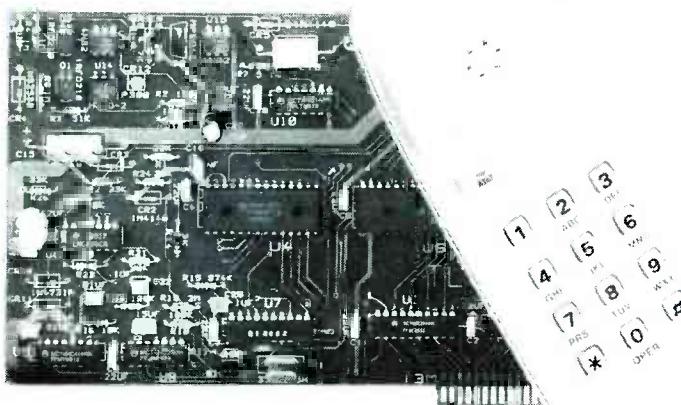

# TELEPHONE-LINE CONTROLLER

***Take full control of  
incoming and  
outgoing  
telephone  
calls.***

MORDECHAI SAAD

WITH THE EVER INCREASING VARIETY of pay telephone services such as Dial-A-Sex, Dial-A-Party, and Dial-A-Friend, the telephone abuses at home and in the office are reaching alarming proportions. For many years, only large corporations were able to afford PBX (private branch extension) systems with facilities to restrict the use of certain numbers. However, now you can build an inexpensive, microprocessor-controlled, integrated telephone line controller that can selectively restrict outgoing calls, selectively restrict incoming calls, selectively dial an array of numbers for promotions, and record all activities on the telephone line, including the time, date, and duration of each call.

The controller uses an IBM PC or clone as a host. However, the card is almost a stand-alone device. It includes its own microprocessor and runs its own operating program. The computer is needed to load the operating program into the controller's static RAM, to initialize operations, and to let the user interact with the controller. The host computer may access the SRAM for reloading firmware, sending and retrieving data, and alternating modes and functions. An internal power supply allows the line controller to operate even when the host computer is turned off.

The line controller does not have to be installed on the phone line at the point of entry to restrict outgoing calls and screen unwanted incoming calls. The card can be plugged into a modu-

lar telephone outlet at any point along the indoor phone line, without any modification of the existing installation (see Fig. 1).

## How it works

The controller is fully programmable and can perform a wide variety of functions. Using the software provided on the RE BBS, the controller can prevent a number from being dialed if the prefix matches a number on your "list to restrict" (see Fig. 2). If, for example, the list contains the number 9311, then dialing 931-1882 (or 931-1xxx) will be prevented. A list containing 0-9 will prevent all outside calls, and a list containing 0, 1, 20, 21, 30, 31, 40, 41...90, 91 will prevent the use of all area codes, operator, and international. The list can consist of up to 128 prefixes, up to 6 digits each.

The user may choose to have the controller automatically list all outgoing calls made on the computer screen. The list will consist of the destination telephone number, date, time, and duration of each call.

The user can screen incoming calls and limit them to as many as 32 relatives and friends. In that case, the card would have to be used in conjunction with a telephone answering machine. The answering machine would prompt the caller to enter his own number. Then, only the numbers that match one on the list will be allowed to go through. Any

matching number, along with time and date, will be stored in memory for later use. The user can then make a list of the incoming calls appear on the screen.

The card can be used to automatically dial a number from the keyboard, a number selected from a menu, or a pre-selected range of numbers. The redial function is not limited to the last dialed number, as the user may select a number from a list of previously dialed numbers.

## Circuitry

The line controller contains a microprocessor, memory to hold the software and data, interface circuitry for the host computer, a telephone line interface, and a wall transformer to maintain power when the host computer is off.

A schematic of the circuit is shown in Fig. 3. In the center of the diagram is the microprocessor (IC6, a 65SC02), which is an 8-bit CMOS version of the 6502 used in Apple, Atari, Commodore, and other computers. The static memory, IC4, is an 8K×8 SRAM. The host computer is used to write the program to IC4. The bi-directional tri-state buffer (IC5) is enabled by the pro-

# Join the Electronics and Control Engineers' Book Club®

**TROUBLESHOOTING ELECTRONIC EQUIPMENT WITHOUT SERVICE DATA, Second Edition.** By R.G. Middleton. 320 pp., illus. This indispensable new edition features all the information that made the first edition so successful, plus the latest developments in digital testing, phase checks, IC troubleshooting, and repair of VCRs, stereos, TVs, tape recorders, and much, much more.

585092-3 Pub. Pr., \$30.00 Club Pr., \$22.50

**PRINTED CIRCUITS HANDBOOK, Third Edition.** By C.F. Coombs, Jr. 960 pp., 556 illus. Here in one handy volume is all the information you need to design, manufacture, test, and repair printed wiring boards and assemblies. This new edition features ten all-new chapters, including three on SMT.

126/097 Pub. Pr., \$64.95 Club Pr., \$45.50

**SOUND SYSTEM ENGINEERING, Second Edition.** By D. Davis and C. Davis. 665 pp., illus. The definitive source for all professionals responsible for audio system design, covering everything from concert halls to virtually every oscillator in use today. Packed with proven strategies for solving design and engineering problems and cutting your clients' costs.


584657-8 Pub. Pr., \$39.95 Club Pr., \$31.50

**McGRAW-HILL ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS, Second Edition.** S. Parker, Editor-in-Chief. 1,047 pp., 1,250 illus. Featuring 160 new and revised articles, this new edition treats the entire spectrum of applications, devices, systems, and theory in areas ranging from the flow of electricity to hardware, software, robotics, and IC fabrication.

454/99X Pub. Pr., \$79.50 Club Pr., \$54.95

**COMMUNICATIONS RECEIVERS: Principles and Design.** By Ulrich L. Rohde and T.T.N. Bucher. 608 pp., 402 illus. Everything you need to know if you design or work with communications receivers, from theory to practical design approaches. Coverage includes all types of receivers: shortwave, broadcast, radar, military, marine, aeronautical, and more.

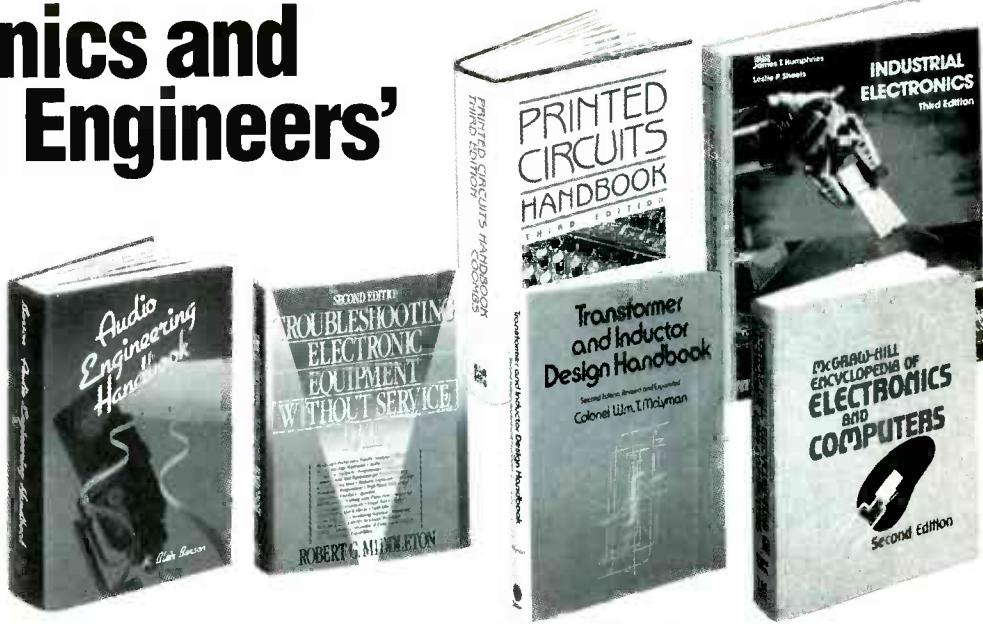535/701 Pub. Pr., \$64.95 Club Pr., \$44.50



- your one source for engineering books from over 100 different publishers
- the latest and best information in your field
- discounts of up to 40% off publishers' list prices

New Members!  
Take any one of these great professional books **\$2.89**  
for only  
as a premium with your first selection!

Spectacular values up to **\$204.95**

**HANDBOOK OF TRANSDUCERS.** By H.N. Norton. 554 pp., illus. Get fast answers to all of your questions about commercially available transducers. This up-to-date reference explains how they operate, how to select the right transducer for a given measurement, and the characteristics and relative merits of each category of transducer.

585142-3 Pub. Pr., \$44.00 Club Pr., \$34.50

**DESIGNING WITH FIELD-EFFECT TRANSISTORS, Second Ed.** By Siliconix Inc., Revised by E. Oxner. 320 pp., illus. This on-the-job guide provides page after page of practical data, tables, examples, and design and specification strategies to help you capitalize on recent breakthroughs in MOSFET design. Coverage includes FET operating principles and procedures . . . step-by-step fabrication methods . . . how to bias FETs for desired performance . . . and much more.

575/371 Pub. Pr., \$39.95 Club Pr., \$29.95

**CIARCIA'S CIRCUIT CELLAR, Volume VII.** By S. Ciarcia. 256 pp., 100 illus., softcover. More do-it-yourself circuits from the master—Steve Ciarcia. Step-by-step guidance on projects ranging from a gray-scale video digitizer and the Circuit Cellar AT Computer to parallel interfacing and the Neighborhood Strategic Defense Initiative.


109/699 Pub. Pr., \$19.95 Club Pr., \$15.95

**THE COMPACT DISC: A Handbook of Theory and Use.** By K.C. Pohlmann. 288 pp., illus. softcover. The most readable and comprehensive guide to CD technology offers clear descriptions of disc design and manufacturing . . . player circuitry . . . and comparisons of different types of players—all without complicated theoretical or mathematical discussions.

585096-6 Pub. Pr., \$29.95 Club Pr., \$22.50
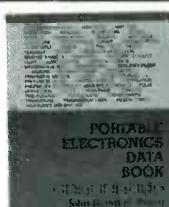
## PORTABLE ELECTRONICS DATA BOOK

360 pp., 6 x 9, illus., softcover 585390-6  
A-to-Z coverage of all the essential facts, figures, and formulas you need, in a format that's easy to use and easy to carry. John Douglas-Young has filled this handy on-the-job companion with equations, algorithms, calculus formulas, and BASIC programs in areas ranging from alternating current and amplifiers to transducers and waveguides . . . and they're all yours ABSOLUTELY FREE!



A \$33.00  
Value—Yours  
ABSOLUTELY  
FREE  
when you join!

**MOBILE CELLULAR TELECOMMUNICATIONS SYSTEMS.** By W.C.Y. Lee. 442 pp., 215 illus. A to Z coverage of state-of-the-art cellular systems, from design to implementation and troubleshooting. Clearly explains spectrum efficiency, propagation models and prediction, interference treatment, and more.

370/303 Pub. Pr., \$62.95 Club Pr., \$44.50

**TRANSFORMER AND INDUCTOR DESIGN HANDBOOK, Second Edition.** By Col. W.T. McLyman. 440 pp., illus. All the information you need to design today's lighter, smaller transformers and inductors, without relying on outmoded approximation methods. In ready-reference tabular format, this new edition covers the latest equations in transformer and gapped design applications.

584646-2 Pub. Pr., \$55.00 Club Pr., \$38.50

**ENCYCLOPEDIA OF TELECOMMUNICATIONS.** Edited by R. Meyers. 575 pp., illus. The expertise of 40 recognized leaders in the field is captured in this A to Z reference. Areas covered range from fiber optics, intelligent systems, and networking, to signal processing, mathematical relationships, and theory.

584897-X Pub. Pr., \$49.95 Club Pr., \$37.50

**PROGRAMMABLE LOGIC DESIGNER'S GUIDE.** By R.C. Alford. 304 pp., illus., softcover. This practical guidebook shows you how to design devices that provide all the logic functions a circuit requires and avoid the compromises inherent in conventional methods. Covers design philosophy, PLD families, hardware, software, and programming languages.

585141-5 Pub. Pr., \$29.95 Club Pr., \$22.50

**SURFACE-MOUNT TECHNOLOGY FOR PC BOARD DESIGN.** By J.K. Hollomon, Jr. 504 pp., illus., softcover. Get a real working understanding of SMT. This up-to-date guide provides a proven, step-by-step approach to SMT design as it thoroughly covers components, methods, and techniques for maximizing quality, reliability, and profitability.

585235-7 Pub. Pr., \$49.95 Club Pr., \$36.50

**INDUSTRIAL ELECTRONICS, Third Ed.** By J.T. Humphries and L.P. Sheets. 651 pp., illus. A clear, convenient guide to the components and systems used in modern industry. Included is an extensive collection of manufacturers' data sheets, along with many quick-access tables and charts.

585226-8 Pub. Pr., \$41.95 Club Pr., \$31.95

**BUILD YOUR OWN UNIVERSAL COMPUTER INTERFACE.** By B. Chubb. 309 pp., illus., softcover. Guiding you from theory to step-by-step assembly instructions, this lively manual shows you how to construct a computer interface and hook it up to virtually any IBM or IBM compatible personal computer, including the XT, XT-286, AT, and System/2 Model 30. 585080-X Pub. Pr., \$19.95 Club Pr., \$15.95

**DIGITAL FILTERS AND SIGNAL PROCESSING, Second Ed.** By L.B. Jackson. 410 pp., illus. An acclaimed guide to signal processing theory, design methods, and implementation strategies. Using an intuitive approach, the author covers state-space representation, A/D and D/A conversion, the DFT, FFT, and much more.

585269-1 Pub. Pr., \$52.50 Club Pr., \$39.50

**SWITCHGEAR AND CONTROL HANDBOOK, Second Ed.** Edited by R.W. Smeaton. 1,056 pp., 789 illus. The only handbook that treats all aspects of switchgear control, including design, applications, safety, and maintenance. Updated to reflect the changes brought about by the use of computers, solid-state devices, and programmable controls.

584/494 Pub. Pr., \$85.00 Club Pr., \$59.95

**ANTENNA APPLICATIONS REFERENCE GUIDE.** Edited by R.C. Johnson and H. Jasik. 496 pp., 368 illus. and tables. Covers the major applications of antenna technology in all areas of communications and their design methods. Emphasizes important new applications such as earth station, satellite, seeker, aircraft, and microwave-relay antennas.

322/848 Pub. Pr., \$59.95 Club Pr., \$42.50

**RADIO HANDBOOK, Twenty-Third Ed.** Edited by W.L. Orr. 667 pp., 1,073 illus. and tables. The latest edition of the most complete, current resource on radio technology and its applications. Expert contributors show you how to select, design, build, test and operate all kinds of equipment.

584638-1 Pub. Pr., \$29.95 Club Pr., \$23.95

**AUDIO ENGINEERING HANDBOOK.** Edited by K.B. Benson. 1056 pp., 722 illus. The ideal on-the-job reference for professionals who design, operate, and service audio equipment. It's a one-volume source of fundamental audio acoustics engineering information and practical how-to source book covering generation, transmission, storage, and reproduction of the audio signal.

047/774 Pub. Pr., \$86.95 Club Pr., \$59.95

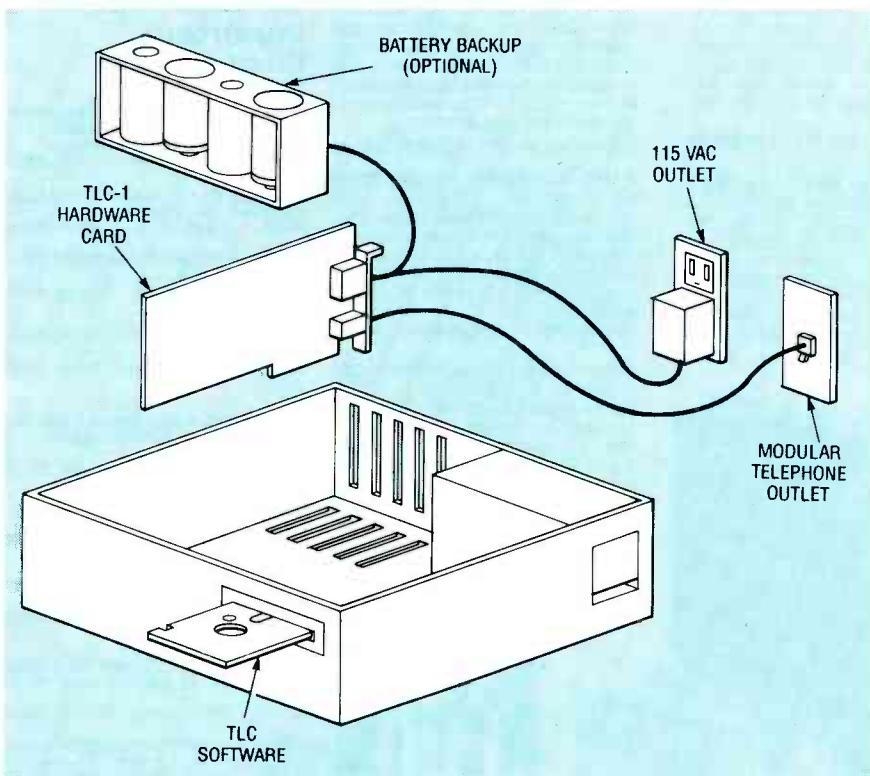


FIG. 1—THE ADD-ON-CARD can be plugged into a modular telephone outlet at any point along the indoor phone line, without any modification to the existing installation.

1/ 25 Records	Tel. No.	Description
1.	0	Operator
2.	1	Long Distance
3.	20	Long Distance
4.	21	Long Distance
5.	30	Long Distance
6.	31	Long Distance
7.	40	Long Distance
8.	41	Long Distance
9.	50	Long Distance
10.	51	Long Distance
11.	540	General Information
12.	550	Group Talk Line

Home PgUp ↑ ↓ PgDn End Ins Del Esc F9=More F10=Help

FIG. 2—THE CONTROLLER CAN PREVENT a number from being dialed if the prefix matches a number on your "list to restrict."

cessor on pin 1 (the direction pin) according to whether the host computer wants to read from or write to the SRAM. Components C16, R1, and D3 provide the processor with a power-on reset.

The peripheral interface adapter (PIA) IC3 is responsible for synchronizing the control of the


buses between the host processor (80xx) and the controller's 6502. The DTMF (dual-tone multi-frequency) transceiver, IC7, is constantly monitoring the telephone line for DTMF activities, as well as for incoming calls. When dialing, the transceiver generates DTMF signals.

Resistors R17 and R18 set the gain of IC7 to 1, C24 provides AC coupling for the incoming signals, and D10 and D11 are 4.3 volt-Zener diodes: when connected back to back they limit the voltage swing on the secondary of T1 to 5 volts (4.3 + 0.7), thereby protecting IC7 and IC11 from voltage transients. The transmitter output of the DTMF transceiver is buffered by IC11-b to drive the 600-ohm line transformer T1. IC11-b is configured as an inverting amplifier with a gain of 1. By connecting the non-inverting input to a reference voltage of 2.5 volts, the output swing can extend to both rails, centered around 2.5 volts.

The other side of T1's secondary is connected to the output of IC11-a which is configured as a voltage follower to buffer the voltage reference of IC7, and is also used as a return for the line transformer T1. The on-chip clock oscillator of IC7 uses a 3.58-MHz crystal, and the output is coupled to the input of 4-bit binary counter IC8-a via C21. The first-stage output of the counter is the source of the 1.79-MHz clock for the processor. The fourth bit of IC8-a outputs 224 kHz, which IC8-b divides down to 14 kHz. The 14-state counter, IC9, divides the 14 kHz by 1024 down to 13.65 Hz, which is the real-time clock. The 13.65-Hz clock signal is used to tag events such as outgoing calls, incoming calls, and duration of calls, with a relative time and date. The host computer converts it to absolute time and date.

Varistors R27-R29 are used as surge suppressors, preventing the tip and ring terminals from exceeding a differential potential of 150 volts with respect to chassis ground and to each other. Bridge-rectifier BR2 is used to correctly polarize the telephone line on its way to the line-status and -control circuitry. The ring-detector circuitry is connected directly to tip and ring. It detects an AC signal greater than 100 volts p-p. Capacitor C18 blocks the 48-volts DC from opto-coupler IC15's LED, and R11 limits the LED's current.

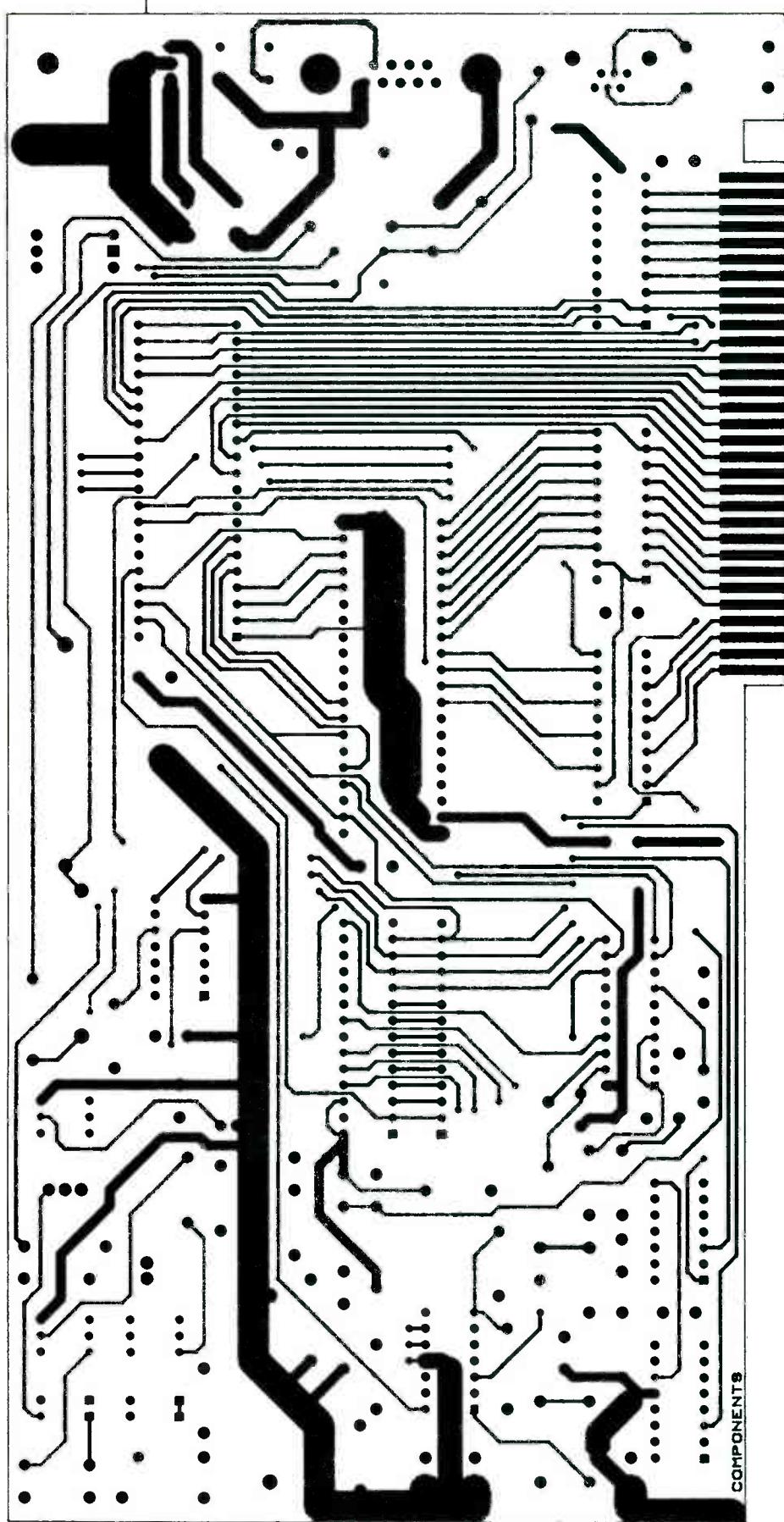When a ring signal is present, the opto-coupler's output transistor is on, which causes C26 to



YOU CAN MAKE YOUR OWN PC BOARD for the telephone line controller. This pattern is for the component side of the board.

discharge, pulling the input of IC10-d to ground. The processor reads the output of IC10-d (high when ringing) into data line DO by enabling IC1. Resistor R10 charges C26 at a rate where the brief pauses between rings will not reach the threshold of IC10-d, thereby maintaining IC10-d's output high.

Schmitt trigger IC10-e and IC14 allow the controller to "pick-up," or get on line. The processor sets the input of IC10-e. The output of IC10-e then drives the LED part of opto-coupler IC14 to ground via R7. The transistor part of IC14 then turns on, driving Q3. At this point, the following components are conducting the loop current in a clockwise order: R13,  $\frac{1}{4}$  of BR2, Q3, LED1, R9,  $\frac{1}{4}$  of BR2, and R12. LED1 is there only to indicate that the controller has "picked-up."

A circuit made up of transistors Q1 and Q2, IC13, and IC10-c continually monitors the telephone line. When any telephone on the line is picked up, the voltage between the tip and ring drops from 48- to 7-volts DC and, as a result, Q2 turns off. Transistor Q1 then turns on, turning on the transistor in the opto-coupler IC13, causing the output of IC10-c to go high. That tells the processor that somebody is on the line. The processor reads that signal on data line D1 via IC1. IC10-a and -b provide the internal microprocessor with a reset pulse on power up, and on bus-transfer command.

The card can get its power from the host computer via D2, at least while the host computer is in operation, and the external wall transformer is not connected. The existence of external power

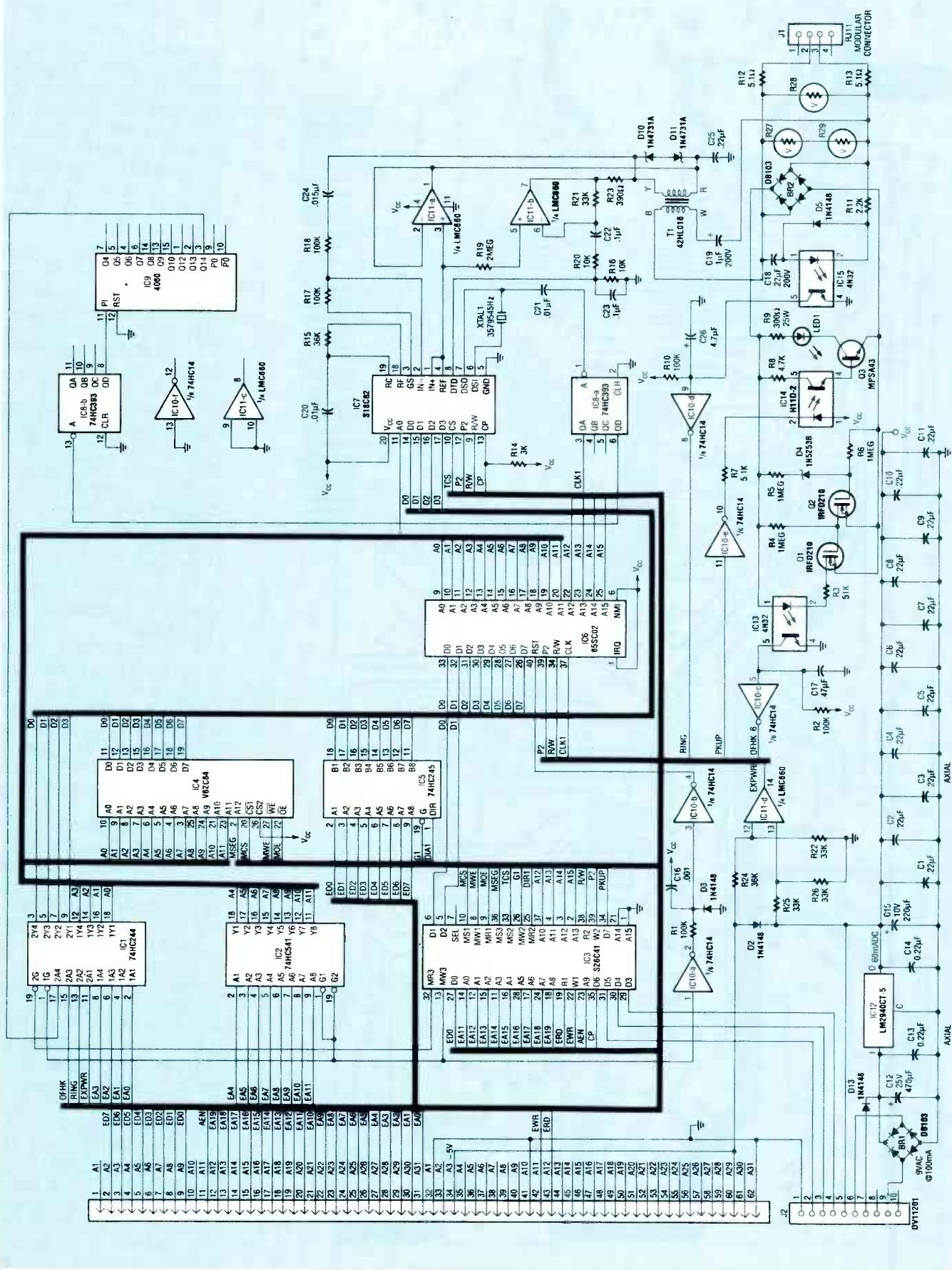


FIG. 3—SCHEMATIC OF THE LINE CONTROLLER. The 8-bit CMOS microprocessor (IC6) is used to coordinate everything.

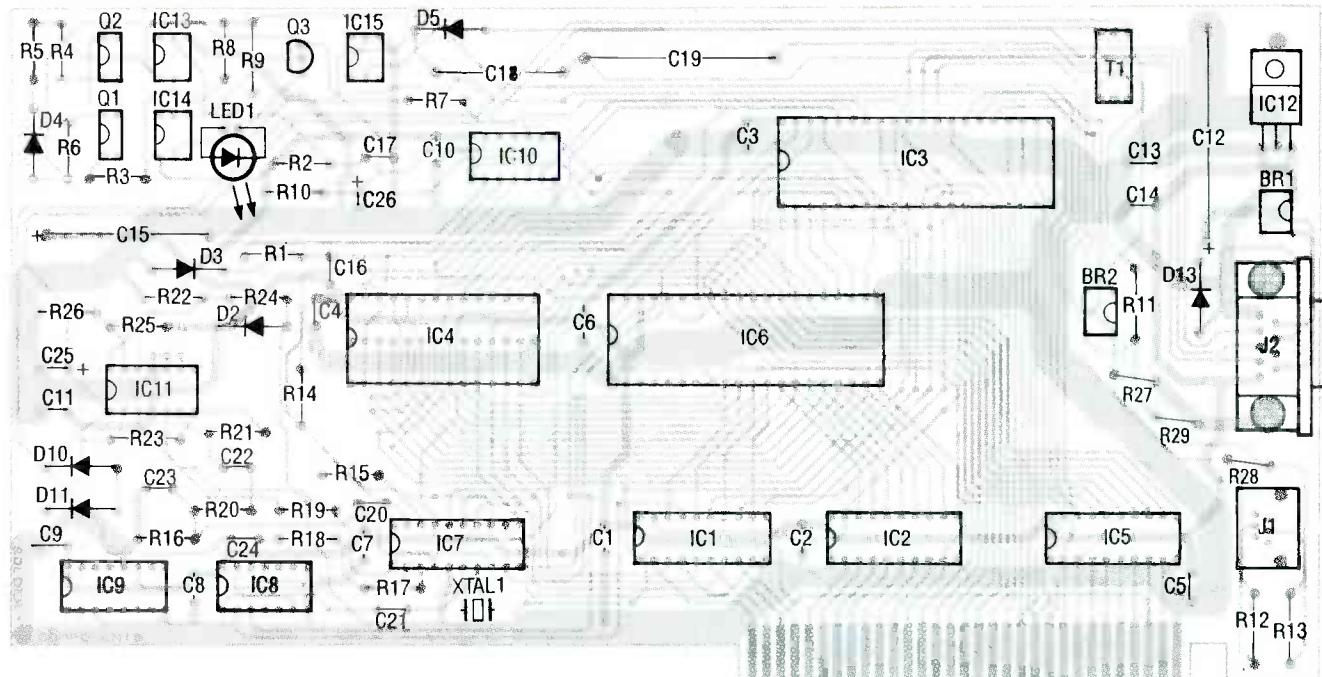


FIG. 4—PARTS-PLACEMENT DIAGRAM. The card is assembled on a double-sided PC board that fits in an expansion slot on your motherboard.

## PARTS LIST

All resistors are  $\frac{1}{2}$ -watt, 2%, unless otherwise indicated.

R1, R2, R10, R17, R18—100,000 ohms  
 R3—51,000 ohms  
 R4—R6—1 megohm  
 R7—5100 ohms  
 R8—4700 ohms  
 R9—300 ohms,  $\frac{1}{2}$ -watt  
 R11—2200 ohms  
 R12, R13—5100 ohms  
 R14—3000 ohms  
 R15, R24—36,000 ohms  
 R16, R20—10,000 ohms  
 R19—2 megohms  
 R21, R22, R25, R26—33,000 ohms  
 R23—390 ohms  
 R27—R29—P7056 125-volt surge suppressor

### Capacitors


C1—C11, C13, C14, C25—0.22  $\mu$ F, 50 volts, ceramic  
 C12—470  $\mu$ F, 25 volts, electrolytic  
 C15—220  $\mu$ F, 10 volts, electrolytic  
 C16—1000 pF, 100 volts, ceramic  
 C17—0.47  $\mu$ F, 50 volts, ceramic  
 C18—0.22  $\mu$ F, 250 volts  
 C19—1  $\mu$ F, 250 volts  
 C20, C21—0.01  $\mu$ F, 100 volts, ceramic  
 C22, C23—0.1  $\mu$ F, 50 volts, ceramic  
 C24—0.015  $\mu$ F, 100 volts, ceramic  
 C26—4.7  $\mu$ F, 25 volts, electrolytic

### Semiconductors

IC1—74HC244 octal tri-state buffer  
 IC2—74HC541 octal tri-state buffer  
 IC3—S26C41 interface adapter  
 IC4—V62C64 8K  $\times$  8 SRAM  
 IC5—74HC245 octal transceiver  
 IC6—65SC02 8-bit microprocessor  
 IC7—S18C62 DTMF processor  
 IC8—74HC393 dual 4-stage counter  
 IC9—74HC4060 14-state counter  
 IC10—74HC14 hex Schmitt trigger  
 IC11—LMC660 quad op-amp  
 IC12—LM2940CT-5 + 5-volt regulator  
 IC13, IC15—4N32 optoisolator  
 IC14—H11D-2 optoisolator  
 BR1, BR2—DB103 bridge rectifier  
 D2, D3, D5, D13—1N4148 switching diode  
 D4—1N5253B 25-volt Zener diode  
 D1, D6—D9, D12—not used  
 D10, D11—1N4731A 4.3-volt Zener diode  
 LED1—P300 light-emitting diode (any color)  
 Q1, Q2—IRFD210 N-channel hex DIP  
 Q3—MPSA43 H.V. NPN transistor  
 Other components  
 J1—H9032 modular connector  
 J2—8926 747844-1 female D-subminiature connector  
 T1—42HL016 600/600-ohm transformer  
 XTA\_1—3.579545-MHz crystal

**Miscellaneous:** PC board, 9-volt 200-mA AC wall adapter, E09P male D-subminiature connector, battery holder, PC bracket, hardware, solder, etc.

**Note:** The following items are available from AC&C, 717 E. Jericho Tpk., Suite 101, Huntington Station, N.Y. 11746: A PC board (TLC-1) and OGC Restrainer software (on 5 1/4-inch floppy disk), \$55.00; A wall transformer, modular phone cord, three connectors, and a metal PC mounting bracket \$36.00; all the above mentioned items, and all components including semiconductors, resistors, capacitors, and optoelectronics devices; \$198.00. Be sure to add \$5.50 to any order for shipping and handling. For technical information, write to AC&C, and please include a self-addressed stamped envelope. AC&C is constantly adding software functions for the entire product line, and for those with unique applications, AC&C is ready to work on your custom software requirements.

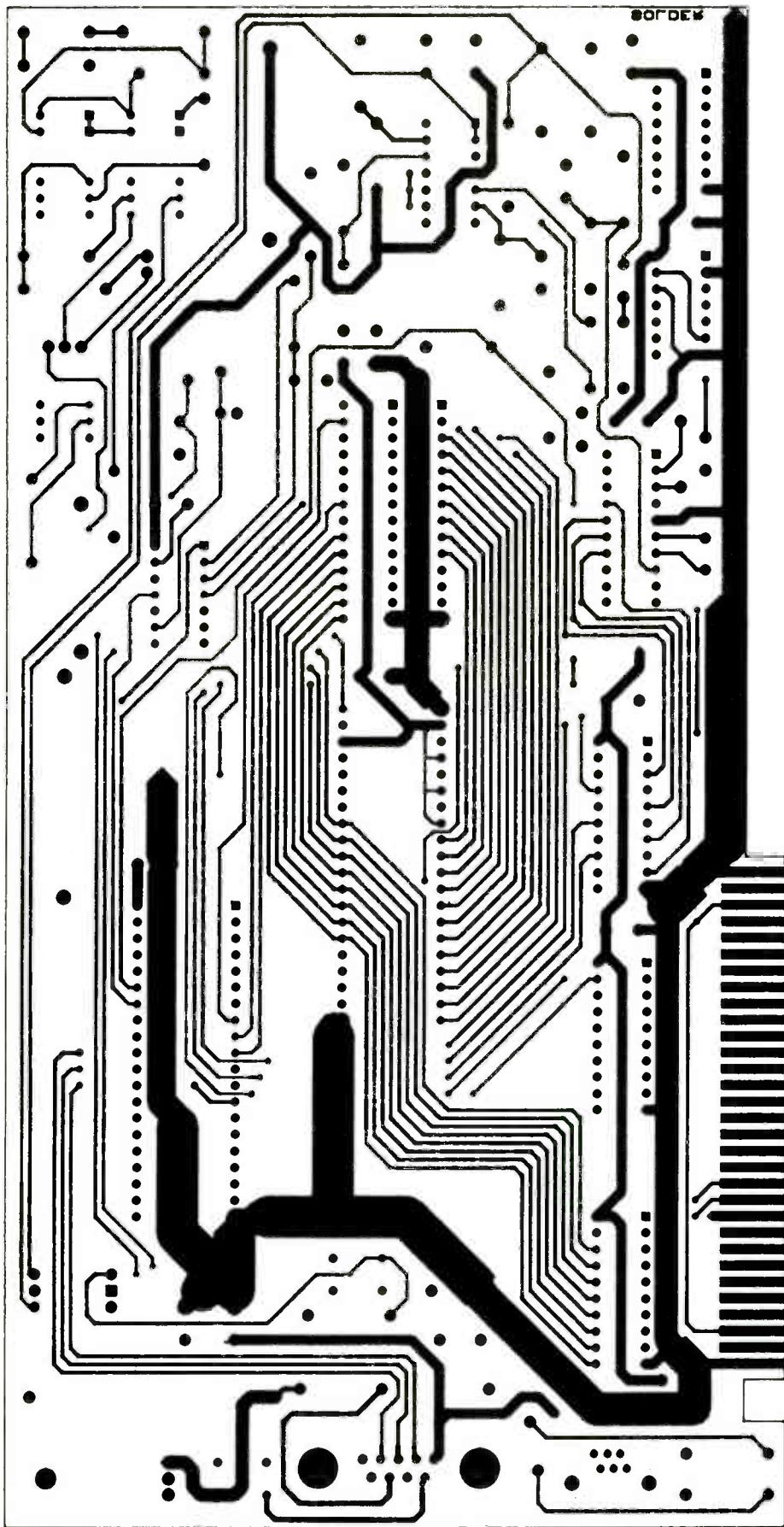

THIS IS THE FOIL PATTERN for the solder side of the telephone line controller PC board.

(AC line transformer, and or battery backup) is detected by IC11-d, in order to alert the user before shutting off power on the host computer. Resistors R24 and R22 are set to provide the non-inverting input of IC11-d with 2.39 volts.

When external power exists, the cathode of D2 is at 5 volts. When external power does not exist, the voltage drops to 4.3 volts; resistors R25 and R26 divide the voltage by 2, to 2.5 and 2.15 respectively, to drive the inverting input of IC11-d. The output, therefore, will go high when the external power does not exist and vice-versa. The 5-volt regulator IC12 provides the circuits with power as long as it is supplied with at least 6.5-volts DC or 7 volts AC RMS.

A provision has been made for future interface with external hardware on a three-line serial communication; see pins 2-4 of connector J2. Also, ground and  $V_{CC}$  is brought to pins 1 and 5 respectively. The connection of a battery to pin 7 is optional; when used, it ensures proper operation during power interruptions.

### Construction

Construction of the card is straightforward. Figure 4 shows a parts-placement diagram. The PC board can be made from the foil patterns provided, or you can purchase one from the source mentioned in the parts list. When building the board, just be sure to install the IC's last, as they are more susceptible to damage than the other components. The only other thing that needs explaining is the bracket that holds the card down in the computer. You must take a "blank" IBM- (Continued on page 82)

# DATA DISKS: HIGH SPEED DEVICE SELECTION FOR THE 90'S


ED PRESTWOOD\*

TRADITIONALLY, DEVICE SELECTION involved paging through hard copy selection guides and data books until a suitable device was located. Now, with the revolution in electronic data processing, the technical community is quickly moving toward high-speed computer-assisted software for selecting semiconductors and other electrical components. The process is not only faster and simpler, it also results in better device selections.

What began as a simple foray into PC-assisted device selection is rapidly becoming the preferred method of device selection by today's engineers. For one thing, data disks routinely save users hours in the device-selection process. Second, and perhaps even more important, there's a tremendous cost advantage for engineers to design in components that not only perform well, but are cost-effective as well. Selecting the ideal device at the best price often results in the savings of thousands of dollars for companies that take the time to optimize their designs. Some companies are even using data disks to find better, less expensive replacements for components in existing designs.
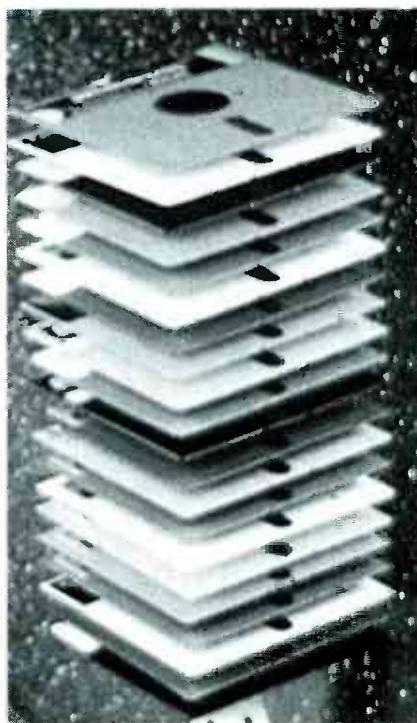
## What are data disks?

Data disks are selection guides on floppy disks. Manufacturers are now providing data disk's to



customers as a supplement to conventional literature to speed up and simplify the device selection process. Data disks are not intended or designed to replace data sheets; instead, they are computer-assisted selection guides that recommend several suitable devices for the user's application. They run on popular PC's and help users select the ideal device or product for their application in seconds rather than minutes or even hours. Some data disks integrate cross reference support for as many as 27,000 competitive devices.

***Finding the right component for a particular application is easier than ever, with the help of today's data disks.***

After the data disk recommends several suitable candidates, it's up to the user to obtain the appropriate data sheet to make a final intelligent selection. To make it easier to order the proper literature, some disks even contain listings of technical literature for the devices on the disk. The Motorola data disk, for instance, lists every application note, article reprint, engineering bulletin, training course, data sheet, and data book available for over 13,000 integrated circuits and discrete semiconductors.

## What do data disks do?

One of the simplest functions provided by these electronic selection guides is the part number search. Users enter the device number they are interested in, press the Enter key, and the program conducts the search. When the part is found, all information concerning it is displayed. The more sophisticated disks automatically search every product category on the disk for a spec-

\*Ed Prestwood is president of Cybersoft, Inc., a Tempe, AZ company specializing in the production of data disks.

ified part number. A useful variation of the part number search is the partial part number search. In a partial device number search (also called a substring search), the user enters a portion of a device number—"6800," for instance. The program then locates every device that contains "6800" somewhere in its part number and displays the list in a tabular format on the screen. One similar feature is called the complementary device number search. This option will locate the electrical complement for any discrete device specified by the user.

A few of the currently available data disks provide a useful cross-referencing feature. If the specified part number isn't on the disk, the program automatically looks for it in a special cross-reference file. If it's listed, the software automatically looks up the manufacturer's equivalent device and displays the information for that device. Some data disks tell users if the cross-reference device is a "similar replacement" or a "direct replacement." The Harris Op Amps data disk even tells users about the pin-to-pin compatibility and the degree of electrical equivalency. The Harris disk also provides comments regarding the suitability of the device as a substitute for the requested device number.

For most users, the most valuable capability of data disks is the parametric search function. After this function is selected, the program displays a menu of parameters for the devices in the selected product category. Users then select the parameters for their application from a menu and enter minimum or maximum values appropriate for their application. Some data search disks provide pop-up menus that list choices for parameters such as package, temperature range, Zener voltage, etc. After entering the values, pressing a single key will display all the devices that meet or exceed the specified requirements.

Like any good spreadsheet, the better data disks allow users to conduct "what if?" sessions. High-end data disks, such as those developed by CyberSoft, actually remember the previous parametric search and permit users to conduct the search over

and over, "tweaking" just one or two parameters with each pass. That permits users to make whatever compromises are necessary to optimize the cost-performance tradeoffs.

Data disks also provide a host of other features, such as the ability to limit searches to military components, surface mount components, or military surface mount components. Many data disks include a printable "Information Request Form" so that users can order technical literature and sample devices. Most data disks also contain sales office and/or distributor contact lists. Help files, screen-color utilities, and printer utilities (including network and spooler

support) are also available on some disks. The Burr-Brown data disk even has a provision for displaying new product information that users can download from the Burr-Brown BBS in Tucson, Arizona. Thoughtful manufacturers also include a phone number for users to call to obtain the latest versions of their data disks. Many offer free subscription services.

### **Are all disks created equal?**

By no means. Several of the data disks available today are highly polished, professional software packages. A few, however, carry the mark of the novice. The differences matter little, however, when a manufacturer

## **SOME AVAILABLE DATA DISKS**

### **Analog Devices**

Two Technology Way  
Norwood, MA 02062  
Bill Schweber (617) 329-4700  
**CIRCLE 225 ON FREE INFORMATION CARD**

### **Best Power Technology**

P.O. Box 280  
Necedah, WI 54646  
Literature Center (800) 356-5794  
**CIRCLE 226 ON FREE INFORMATION CARD**

### **Bourns**

1200 Columbia Avenue  
Riverside, CA 92507  
Customer Service (714) 781-5500  
**CIRCLE 227 ON FREE INFORMATION CARD**

### **Burr-Brown**

P.O. Box 11400  
Tucson, AZ 85734  
Customer Support (800) 548-6132  
**CIRCLE 228 ON FREE INFORMATION CARD**

### **Cuttler-Hammer**

Dept H293  
4201 N. 27th Street  
Milwaukee WI 53216  
Diane Nuesslein (800) 833-3927  
**CIRCLE 229 ON FREE INFORMATION CARD**

### **Equipto**

351 Woodlawn Avenue  
Aurora IL 60506  
Customer Service (708) 897-4691  
**CIRCLE 230 ON FREE INFORMATION CARD**

### **Harris Semiconductors**

P.O. Box 883, M/S CB-1-25  
Melbourne, FL 32901  
Literature Center (407) 724-3739  
**CIRCLE 231 ON FREE INFORMATION CARD**

### **Lambda**

515 Broad Hollow Road  
Melville, NY 11747  
Customer Service (800) 526-2324  
**CIRCLE 232 ON FREE INFORMATION CARD**

### **Motorola**

P.O. Box 20924  
Phoenix, AZ 85036  
Literature Center (800) 521-6274  
**CIRCLE 233 ON FREE INFORMATION CARD**

### **Newport**

P.O. Box 8020  
Fountain Valley, CA 92728  
Technical Hotline (714) 965-5406  
**CIRCLE 234 ON FREE INFORMATION CARD**

### **Philips Components**

George Washington Hwy.  
Smithfield, RI 02917  
Cindy Taylor (401) 232-0500  
**CIRCLE 235 ON FREE INFORMATION CARD**

### **Precision Monolithics**

1500 Space Park Drive  
Santa Clara, CA 95052  
Literature Center (800) 843-1515  
**CIRCLE 236 ON FREE INFORMATION CARD**

### **Titan Severe Environments**

20151 Nordhoff Street  
Cathsworth, CA 91311  
John Van Putten (818) 709-7117  
**CIRCLE 237 ON FREE INFORMATION CARD**

### **Western Digital**

17900 Von Karman Ave.  
Irvine, CA 92714  
Literature Center (800) 832-4778  
**CIRCLE 238 ON FREE INFORMATION CARD**

### **Xentek**

P.O. Box 1987  
Vista, CA 92083  
Larry Merchell (619) 727-0940  
**CIRCLE 239 ON FREE INFORMATION CARD**

has the only data disk for their given product line. But with new disks becoming available every few weeks, the competition to provide the most convenient and powerful user interface is intensifying. All the manufacturers mentioned here have improved their disks with each new revision. It may seem ironic, but today and throughout the 90's, the battle for share-of-mind will be fought and won on the basis of

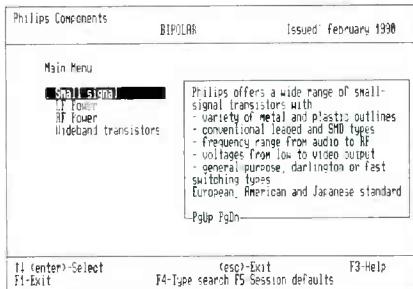


FIG. 1—THE MAIN MENU from Philips Components' Discrete Semiconductors Transistors data disk.

the ease of selection rather than solely on the reputation of the manufacturer.

A few of the data disks available today provide automatic multi-level sort capability, which is a definite advantage in today's competitive market. CyberSoft, Inc. introduced the multi-level sort feature when it developed the first Motorola data disk in 1987. The multi-level sorting algorithm sorts each and every column selected by the user. It sorts on the first selected parameter, the second parameter, the third, and so on across all the parameters selected by the user. The procedure takes place in milliseconds and assures users that the absolute best device in the database for the specified application is always listed first, and so on.

The automatic multi-level sort is arguably the very best way to display data. A less useful compromise to the automatic multi-level sort is the manual column-by-column sort that users can conduct after the search has been completed.

One feature users should be aware of is called the "early-abort" search algorithm. Some data disks search their databases and abort the search after a specified number of devices are located (10 and 15 are common

numbers). That's an awful approach to searching a database, since the 16th device—or the 2,016th, for that matter—may be the ideal device for the specified application. Look for disks that search the entire database for parameters selected by the user, then report back the total number of "hits." The best way for the software to "know" how many devices meet the user's requirements is by searching the entire database.

Another very useful feature that separates the men from the boys is called parameter queuing. That is, the program automatically displays the parameters in the same sequence that the user selected them in. If a user selects  $r_{DS(on)}$  as his or her

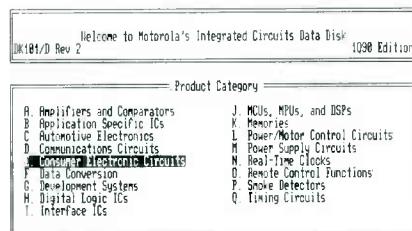


FIG. 2—MOTOROLA'S IC data disk gives access to a wide variety of product categories.

most important parameter, it is displayed in the first column. Likewise, if the user specifies breakdown voltage as the second most important parameter, it will be displayed in the second column. Automatic parameter queuing, coupled with automatic multi-level sorting, provide users with the most useful and convenient display sequence possible. Burr-Brown, Harris, and Motorola support both of these important features in their data disks.

Data disks also vary greatly in the amount of data they store. The number of devices is not a reliable indicator of the amount of information contained on the disk because there may be only five or six columns of information available for each device. CyberSoft, who developed the Burr-Brown, Harris, Motorola, Titan, and Western Digital data disks, supports up to 64 columns of data for every device, which can add up to a lot of data. A final

consideration when gauging the amount of information on a disk is the number of cross references supported. Motorola's data search disk contains well over 25,000 cross-references, which can be a great convenience for designers and technicians alike.

Some data disks include pricing information. Most engineers insist on seeing price information, even if it's only "ball park" pricing. Relative pricing greatly simplifies designing to a budget. If two devices will work in a specified application and one costs half as much as the other, it generally pays to take a good look at the less expensive component. Some disks, like the Titan Data disk, provide users with volume pricing based on the quantities ordered.

One other feature that appears only on high-end data disks is footnote support. All too often, a device that looks ideal may be inappropriate because of some subtle characteristic that isn't obvious by looking at the tabular



FIG. 3—A SAMPLE DEVICE INFORMATION screen from Western Digital's data disk.

data itself. All data disks developed by CyberSoft provide extensive footnoting capabilities.

Another important thing to look for in a data disk is good customer support. Some companies, like Burr-Brown, Motorola, and Western Digital, are placing their data disks onto corporate Bulletin Boards so users can download their latest data disk (and/or new product updates) in minutes. Others, like Equipto, provide a dedicated customer service number that users can call. Within minutes, Equipto sends FAX information on any component covered in their data disk to their customers. Equipto's disk, coupled with their dedicated support line, has not only dramat-

ically increased sales leads, it's also propelled them into a record sales year.

### Who's offering data disks?

Over the past four years, a number of companies have provided data disks to their customers. Disks are distributed at trade shows, technical colleges and universities, and through "shareware" catalogs. More and more of the 6,000+ bulletin board services across the United States have data disks waiting to be downloaded at no charge. The following list shows a sampling of the data disks that are free for the asking.

• **Analog Devices**—This disk provides pricing information and covers Analog Devices' line of op amps and data conversion circuits. Disks containing SPICE emulation models for Analog Devices op amps are under development and will soon be available.

• **Best Power Technology**—This disk, available in English, French, German, or Spanish, is a "brochure-on-a-floppy" for their broad line of computer-grade uninterruptible power supplies.

• **Bourns**—Bourns "Selectrim" data disk provides coverage for Bourns' complete line of trimmer potentiometers.

• **Burr-Brown**—This data disk covers Burr-Brown's entire line of op amps, instrumentation amplifiers, isolation amplifiers, analog circuit functions, D/A and A/D converters, analog circuit multiplexers, sample/hold amplifiers, voltage-to-frequency converters, and data-acquisition components.

• **Cuttler-Hammer**—Billed by the company as an "Expert System" program, this data search disk leads specifiers through a series of pertinent questions that results ultimately in the recommendation of the appropriate photoelectric or proximity transducer for a given specified application.

• **Equipto**—The Equipto disk incorporates more graphics than most data disks. It helps users specify the optimal modular enclosure (including vertical racks and slope front consoles) for electronic equipment. Also includes computer furniture, instrument cabinets, and EMI/RFI shielded enclosures.

• **Harris**—Harris' first entry in the data disk arena covers their broad line of operational amplifiers, including devices from the recent merger of GE, RCA, and Intersil. Look for additional Harris product lines to be added soon. A disk containing SPICE macro models for several Harris op amps is also available.

• **Lambda**—Lambda offers a disk covering their broad line of AC-DC switching and linear power supplies, DC-DC power supplies and converters, supplies for laboratory and test equipment, power semiconductors and power systems. It also includes pricing information.

• **Motorola**—Motorola offers two IBM disks containing all the selection guide information for both IC's and discretes. These disks operate stand-alone or in concert when copied onto a hard drive. This disk is also available on a single microfloppy for Macintosh PC's. It features 124 product categories, 13,000 device numbers, 27,000 competitive cross references, and half a million parameters. Motorola also offers SPICE models for their power MOSFET's and scatter parameters for selected small signal RF devices.

• **Newport**—The Newport Optics Catalog on a floppy features their line of optical lenses. Includes over 2,100 cross reference products for several of Newport's major competitors products.

• **Philips Components**—This company is offering four data disks, covering diodes, FET's, hybrid amplifiers, optocouplers, power MOSFET's, small-signal transistors, and trigger devices. Competitive cross references and pricing are supported.

• **Precision Monolithics**—The "Precision Decisions" data disk provides data for PMI's IC product line, including op amps, data conversion circuits, and sample and hold circuits. Includes prices and industry cross references. A disk containing SPICE emulation models is also available.

• **Titan Severe Environment Systems**—The Titan disk features the company's full line of SECS militarized and ruggedized board-level and system products, including microcomputers, memory, parallel and serial interface, bus interface,

analog, and peripheral controller modules. The data disk also includes product overviews and general pricing information.

• **Western Digital (WD)**—Provides extensive coverage for WD's line of VLSI chip set solutions for XT, AT, 386 and 486 PC architectures, including their Micro-channel products. Prints product overviews and provides a useful "Related Solutions" section. WD also offers a two-disk set of utilities and schematics captured using the ORCAD/STD III v3.22 software. This data search disk set facilitates the development of design solutions based on the AT-compatible WD286-LPM16 motherboard.

• **Xentek**—This disk provides pricing information and major parameters for Xentek's line of standard linear power supplies. Extreme isolation transformers and switching power supplies will be added in the near future.

### Gimmick or trend?

Data disks have come a long way from the first ones that appeared in the mid 1980's. What may have begun as a marketing gimmick is now evolving into a useful engineering trend. Today's data disks cover virtually every discrete and IC product category. New disks are also covering power supplies, sensors, resistors, VLSI chip sets, plastics, and even optics and lasers.

The major force driving the data disk market is that companies are motivated to make it as easy as possible for customers to select and purchase their products. The thrust and cut of competition has helped create a healthy win-win situation: manufacturers view their data disks as marketing tools; users view data disks as time-saving engineering tools. Since introducing their first data disk, Equipto reports an increase in sales leads from 12,000 per year to approximately 75,000 better qualified sales leads per year! That kind of result, coupled with increasing customer demand for faster, easier, and better device-selection tools will continue to assure the proliferation of data disks. For more information, contact CyberSoft, Inc., at 1820 W. Drake Drive, Suite 108, Tempe, AZ 85283, (602)491-0022. R-E

LAST MONTH WE FINISHED BUILDING THE MOTHERBOARD AND THE motor-controller board. Then we covered the operating theory of the power board. So, now let's get to building whatever we haven't covered yet, including the control panel, power board, and mechanical assembly.

### Construction

Fabricate an aluminum sheet-metal enclosure to house the control-panel electronics; we showed you how to wire everything last month.

As for the manual controller, drill holes in a plastic box to accommodate the components; we showed you a schematic of the controller last month. Feed the ribbon cable through a hole on the side of the plastic box and put a knot on the inside of the box so that the wire can't be pulled through. Fasten the top cover to the box and attach the knob to the potentiometer (P1).

### Power-board construction

Following Fig. 1, mount the following components on the solder side (back side) of the PC board: R42, R52, R54, D7-D9, D20-D29, and all E-terminals (they are basically solder posts that allow you to solder heavy-gauge wire to the PC board). Those components are mounted on the solder side in order to create more space for the other components. It is probably a good idea to add a  $\frac{1}{8}$ -inch piece of sleeving insulation to the leads of those components before assembly (with the exception of the E-terminals). That will prevent any accidental shorting of the exposed component leads. After they are installed, trim the component leads. Now install the remaining parts on the component side with the exception of the power MOSFET's.

The MOSFET's require the installation of heat sinks and insulators before assembly. For each MOSFET, place an insulator on the PC board and then cover with a heat sink. Carefully clip off the center lead (drain) of the MOSFET as close to the device body as possible. The lead is not used because the drain connection is also provided by the metal tab on the MOSFET. Bend the MOSFET leads at a  $90^\circ$  angle and insert into the PC board so the device lies flush with the heat sink. Secure the device and heat sink to the PC board with 4-40 hardware.


The high-current jumpers should now be installed on the solder side of the PC board; solder them to the E-terminals. The jumpers are required because the etched traces on the PC board can not handle 15-30 amperes. The jumpers should be made of solid insulated 18-gauge wire. Figure 2 illustrates the three types of jumpers. Install the jumpers on the solder side

***Let's mow the lawn already—  
rather, let's watch the lawn get  
mowed!***

# Build the Lawn Ranger



**RAYMOND RAFAELS**

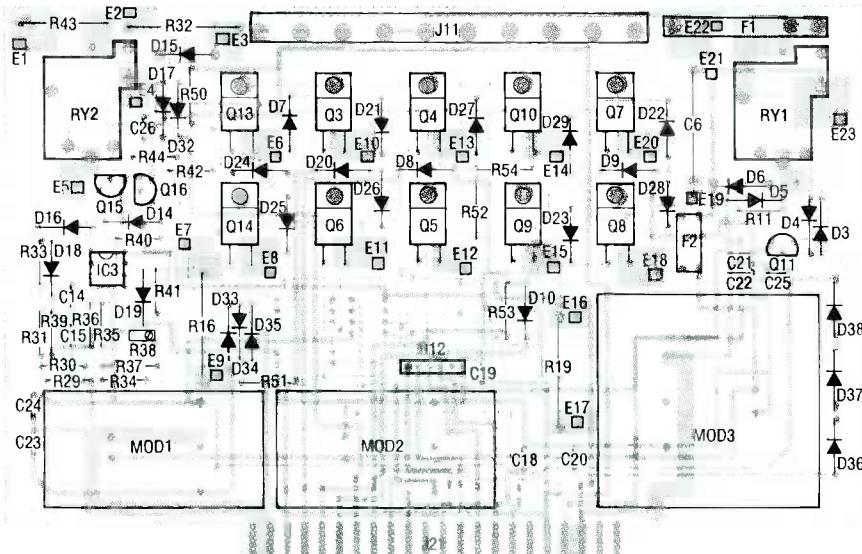

**FIG. 1—PARTS PLACEMENT DIAGRAM** for the power board. Remember that several components must be mounted on the solder side of the board to leave room for the other components (see text).

of the board as follows:

## TYPE-A JUMPERS

E-23 to drain of Q8  
E-18 to drain of Q9  
E-20 to drain of Q10  
E-13 to drain of Q5  
E-10 to drain of Q6

## TYPE-B JUMPERS


Drain of Q4 to Drain of Q7  
Drain of Q3 to Drain of Q4  
Drain of Q8 to Drain of Q14  
Drain of Q7 to Drain of Q18  
(mount on component side)  
Drain of Q13 to Drain of Q14  
(mount on component side)

## TYPE-C JUMPERS

- E-23 to E-21
- E-18 to J11-10
- E-19 to J11-8
- E-20 to J11-9
- E-17 to J11-8
- E-14 to E-15
- E-15 to E-16
- E-13 to J11-7
- E-10 to J11-6
- E-12 to E-11
- E-11 to E-7
- J21-23 to J11-3
- E-6 to E-8
- E-2 to E-6
- E-5 to J11-2
- E-1 to E-17
- E-1 to E-9
- E-3 to E-4
- E-22 to J11-4
- E-22 to J11-5

### Grass-sensor assembly

### Build the mechanical portion

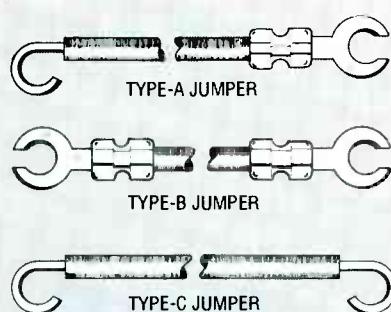

**FIG. 2—HERE ARE THE THREE TYPES OF JUMPERS.** They are used to handle the high currents that exist on the power board.

of the sensor assembly as shown in Fig. 3, and wire the grass sensors themselves as shown in Fig. 4. The length of the ribbon cable that connects the sensor assembly to J1 on the motor-controller board should be approximately 3½ feet long. Crimp J1 onto the end of the ribbon cable using an IDC crimping tool or vise.

## Power-board testing

Inspect all solder joints and jumper connections to ensure that everything is properly assembled. Place the power board on a flat surface (not plugged into the motherboard) and temporarily jumper J11-3, J11-8, and J21-44 with clip leads. Now connect the +24-volt input to the PC board through J11-4 (+) and J11-3 (ground). You should hear the relay "click" on. Measure the DC voltages at J21-32, J21-18,

J21-30, J21-31, and J21-19. The voltage readings should match the values listed on the schematic diagram that we showed you last month. If all the voltages read correctly, the DC/DC converters are working properly. Remove the test clip leads from the PC board.

## Mechanical assembly

Figure 3 shows the mechanical assembly of the Lawn Ranger. Although it does not include all of the details, detailed mechanical drawings can be purchased from Technical Solutions. However, the chances are that you won't follow the original plans exactly—just as long as you follow the general layout. Also, make sure that the cutting section is safely constructed, and that the blade shield protects the cutting deck a full 360 degrees. **WARNING**—The cutting blades should not be connected until it has been proven that the Lawn Ranger has been properly constructed, is fully functional, and safe.

Many of the mechanical parts are available from various manufacturers listed in Table 1. The rest of the mechanical components shown in Fig. 3 are not available from TSI; you must either fabricate them yourself or have a local machine shop make them for you.

## WHAT'S BEEN COVERED

This series on the Lawn Ranger began in the June issue. In that issue, we covered the general operation of the unit, the software, and we discussed and built the CPU board.

In the July issue, we went over the electronic control system, the motor controller board, D/A converter circuitry, grass-sensor circuitry, motherboard, and velocity-feedback loops. We gave you the parts lists for the motor-controller board and the motherboard, although we didn't get to build them that month.

In August, we began with the construction of the motherboard and the motor-controller board. Then we covered the operation of the power board, drive motors, cutting motors, hand-held controller, and the Lawn Ranger's electronic control panel.

In this issue we have finished up the series. We hope you have found it to be an interesting and worthwhile project. R-E

# SHOPPER

#### Executive Offices

Larry Steckler,  
EHF, CET, Publisher  
Arline Fishman,  
Advertising Director  
500-B Bi-County Blvd.  
Farmingdale, NY 11735

1-516-293-3000  
FAX 1-516-293-3115

#### NATIONAL REPRESENTATIVE

Joe Shere  
P.O. Box 169  
Idyllwild, CA 92349  
1-714-659-9743  
FAX 1-714-659-2469

#### CLOSING DATES:

	Reservations in N.Y.	Final Film in N.Y.
Issue		
Sept. 1990	June 11, 1990	June 18, 1990
Nov.	Aug. 13	Aug. 20
Jan. 1991	Oct. 15	Oct. 22
Mar.	Dec. 13	Dec. 20
May	Feb. 13, 1991	Feb. 20, 1991

A  
**GERNSBACK**  
PUBLICATION

## ADVERTISERS INDEX

Alfa Electronics .....	28	Information Unlimited .....	37
All Electronic .....	8	Jensen Tools, Inc. ....	36
AndraTech .....	32	Kelvin Electronics .....	29
B.G. Micro .....	35	L-Com, Inc. ....	28
Battery Tech. ....	32	Mondo-Tronics, Inc. ....	36
Becktron .....	16	Needham's Electronics. ....	26
The Book Source .....	6	O W I. ....	20
Calco International .....	16	Omnitron. ....	27
Command Productions. ....	21	P.C. Boards .....	22
Computer Disk Service .....	30	PMC Electronics .....	20
Consumertronics .....	24	Paladin Electronics .....	34
d b Computer Products. ....	14	Periphex, Inc. ....	30
D & D. ....	17	Prelco .....	25
Dalbani Corporation .....	13	Ramsey. ....	3
Davilyn .....	7	Sescom. ....	20
E.T. Tech, Inc. ....	26	Sky Vision .....	40
Electric Rainbow .....	23	Surplus Sales of Nebraska .....	16
Electrified Discounters .....	11	Surplus Traders .....	12
Electronic Goldmine .....	19	Tanner Electronics. ....	10
Electronics Parts Outlet .....	26	Tech Services .....	34
Electronics Clearing House. ....	30	Top Sales Co. ....	18
Electronics 1 2 3 .....	18	TransWorld .....	32
Gems Computers, Inc. ....	33	Ucando .....	34
J.F. Glaser. ....	10	United Electronic Supply .....	31
Gott Electric .....	4	Universal View .....	39
The Grapevine Group. ....	36	Video Repair .....	24
Gray Maher .....	22	Viejo .....	34
IQ Systems. ....	2	Walling Co. ....	36

**BREAK THE SYSTEM  
WIN - \$25,000**

**THE TymCard®  
\$25,000 CHALLENGE**

***IQ, Inc.*, in an attempt to improve the security of it's product,  
offers this challenge:**

***IQ, Inc.***, is about to release an anti-fraud "smart card" called *TymCard*, to be used by long distance telephone companies to help eliminate calling card fraud. We believe our product to be unbeatable. To detect any possible flaws in our system. ***IQ, Inc.***, is offering a prize of \$25,000 to the first person who can demonstrate that he or she has been able to access the system, at any time, by being able to generate a valid code at will. Accessing the system DOES NOT mean "breaking" one or more existing TymCards as that only allows temporary and insignificant access to the system.

**EXAMPLE:** If you knew the numbers of one or more TELCO calling cards, you would be able to make long distance calls that would be charged to that card - until you were discovered - and that number was deactivated. If, however, you had a "Blue Box", you would be able to make calls at any time. You were able to "break the system" without need for any calling card numbers. The only permanent solution, as far as TELCO was concerned, was to change the system which, in effect, "deactivated" the Blue Box.

A condition of this challenge is that you supply to ***IQ, Inc.***, the details on how you were able to "crack the system" and assist ***IQ, Inc.***, to correct the flaw.

Each respondent to this challenge will be invited to a meeting with members of our staff. At this meeting you will be given much more technical information about *TymCard* as well as a description of the service.

Please note that there is absolutely and positively no charge to you to accept this challenge. If you desire to "borrow" an ACTIVE *TymCard* that will allow you to test the system at any time, we ask for a \$50.00 cash deposit. This deposit will be returned to you, in full, upon the *TymCard* being returned to ***IQ, Inc.***, as agreed.

**If you are interested, please call (818) 592-0423 for information as to the  
time and location of the next meeting.**

**NOTE:** If you are not located in the Los Angeles area please call the number to arrange for complete information to be sent to you by mail.

# ★ ALL NEW KITS ★

## 2 MTR & 220 BOOSTER AMP

Here's a great booster for any 2 meter or 220 MHz hand-held unit. These power boosters deliver over 30 watts of output allowing you to hit the repeaters full quieting while the low noise preamp remarkably improves receptions. Ramsey Electronics has sold thousands of 2 mtr amp kits but, now, we offer completely wired and tested 2 mtr as well 220 MHz units. Both have all the features of the high priced boosters at a fraction of the cost.

PA-10 2 MTR POWER BOOSTER (10 X power gain)

Fully wired & tested ..... \$79.95

PA-20 220 MHz POWER BOOSTER (8 X power gain)

Fully wired & tested ..... \$79.95



- 30 WATTS OUTPUT
- LOW NOISE PREAMP
- LOW COST
- RUGGED CAST ALUMINUM CASE
- ONE YEAR WARRANTY

Complete kit SG-7

**PERSONAL SPEED RADAR**

Low cost microwave doppler radar kit "clocks" cars, planes, boats, horses, bikes, sailboats, models, runners or virtually anything that moves. Operates at 2.6 GHz with over 1/4 mile range. LED digital readout displays speeds in miles per hour, kilometers per hour or feet per second. Easy to assemble, perfect for mounting to your car or boat. Uses two 1/2 coffee cans for antenna (not included) and runs on 12 VDC. Easy to build—no microwave circuitry is PC stripline. Kit includes deluxe ABS plastic case with Speedy graphics for a professional look. A very useful and full-of-fun kit.



## RADIOS

### 20, 40 & 80 METERS HAM RECEIVERS

Sensitive all mode, AM, CW, SSB receivers for 3.5—4.0 or 70—7.5 MHz. Direct conversion design using NE602 IC as featured in QST and ARRL handbooks. Less than 1 µV sensitivity, varactor diode tuned, 250 mw audio output. Runs on 9VDC, has RF gain control. This kit is very easy to build, lots of fun and educational—ideal for the beginner or the old pro. The optional matching case kit features a rugged ABS plastic case with screened graphics. Included are machined aluminum knobs for a well-finished professional look.

20 MTR receiver kit HR-2 **\$24.95**

40 MTR receiver kit HR-4 **\$24.95**

80 MTR receiver kit HR-8 **\$24.95**

Receiver case CHR **\$12.95**



### QRP TRANSMITTER KITS, 20, 40 & 80 METERS

Operate a mini ham shack. These little CW rigs are ideal mates to our 40 and 80 meter receivers. Features include smooth variable tuning, one watt output and excellent keying characteristics. Runs on 12 VDC and is VSWR protected. See how far you can stretch your signal with one of these mini rigs. Optional ABS cases are available.

20 MTR QRP kit **\$29.95**

40 MTR QRP kit **\$29.95**

80 MTR QRP kit **\$29.95**

Case kit HR-80 **\$29.95**

Case kit HR-80 **\$12.95**

### AIRCRAFT RECEIVER KIT

Hear exciting aircraft communications—picks up planes up to 100 miles away. Receives 110—136 MHz AM air band, varactor tuned superhet design with AGC, ceramic filter and adjustable squelch. Runs on 9V battery, 250 mw audio output, 1 µV sensitivity. Optional matching ABS plastic case lets you take it anywhere, features screened graphics and machined aluminum knobs for a real professional look. Compact—great for airshows or for just plain hanging around the airport.

Complete kit AR-1 **\$24.95**

Receiver case kit CAR-1 **\$12.95**



### SHORTWAVE RECEIVER KIT

A fantastic receiver that captures the world with just a 12" antenna! Receives 4—11 MHz in 2 MHz bands, varactor tuned, superhet design with AGC, RF gain control, and 250 mw audio output. Uses new Sigitics mixer chip for less than a microvolt sensitivity, runs on 9V battery. This is a fascinating scout, school or club project, and will provide hours of fun even to the most serious DXer. Add the optional case kit and you have a real nice looking shortwave set.

Complete kit SR-1 **\$24.95**

Receiver case kit CSR-1 **\$12.95**

### PACKET RADIO

Compatible C64/128 packet radio interface. Uses famous German Digicom software. Features EXAR IC chip set for reliable operation—runs HF or VHF tones. Includes FREE disk software, PC board, all necessary parts and full documentation.

Complete kit PC-1 **\$49.95**

### FM COMMUNICATIONS/ 2 MTR, 10 MTR & 220 RECEIVERS

Sensitive superhet FM receiver tunes any 5 MHz segment of band. Listen to ham operations, high band calls, weather or mobile phone etc. Easy to build receiver features varactor tuning, IC mixer stage, ceramic IF filters and dual conversion design with adjustable squelch. Less than 1 µV sensitivity, runs on 9 V battery, with 50 mw audio output. Optional ABS case with screened graphics and machined aluminum knobs provide a nice professional look.

2 MTR kit FR-7 **\$29.95**

10 MTR kit FR-10 **\$29.95**

220 MHz kit FR-20 **\$29.95**

Receiver case kit CFR-7 **\$12.95**

### NEW MINIKITS—NEW MINIKITS

#### BROADBAND PREAMP

A sensitive all purpose preamp, ideal for scanners, TV sets, VHF, UHF rigs, counters, etc. Features low noise, 4 dB NF, 10 dB gain, 100 KHz—1 GHz operation. Runs on 9—12 VDC, 50 ohms input.

Complete kit SA-7 **\$14.95**

#### LIGHT BEAM COMMUNICATORS

Transmits modulated infrared light up to 30 feet without lenses, up to 1/4 mile using lenses. Uses 30 KHz carrier to noise-free operation, transmits thru windows, etc. Features remote control, mounting to IR remote controls. Transmitter has sensitive mike input, receiver uses PIN detector and drives speaker output. Units operates on 9—12 VDC.

Transmitter kit, LB-6 **\$8.95**

Receiver kit, LB-5 **\$9.95**

#### HIGH POWER FM WIRELESS MIKE

A high power unit that will transmit up to 1/2 mile to any FM broadcast radio. Sensitve input accepts any type of mike, will pick up normal voices 10 feet away using the available mini-electric mike cartridge. Operates on 9—12 VDC.

FM-4 kit **\$12.95**

Sensitive microphone cartridge **\$2.95**

# RAMSEY ELECTRONICS

Quality Test Gear & Electronic Kits for Professionals and Hobbyists



**\$49.95**

wired includes  
AC adapter  
PR-2 kit \$39.95

#### PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for sniffing RF • ideal receiver/TV preamp • 3 db NF



**\$69.95**

wired  
PS-2 kit \$49.95

#### PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies up in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner




**\$89.95**

wired includes  
AC adapter

#### PS-10B 1.5 GHZ PRESCALER

Extends the range of your present counter to 1.5 MHz • 2 stage preamp • divide by 1000 • 1000 Hz resolution • BNC connectors • 1.5 GHz in, 1.5 MHz out • drives any counter.

#### COM-3

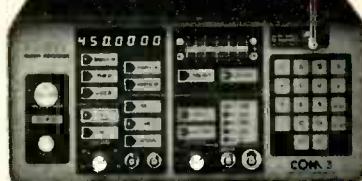

**\$2795.00**

#### THE COMMUNICATIONS SERVICE MONITOR THAT WORKS HARDER FOR LESS.

Introducing COM-3... the new service monitor designed by service technicians for service technicians. It works harder for less... giving you advanced testing capabilities at a very affordable price.

FEATURES • Direct entry keyboard with programmable memory • Audio & transmitter frequency counter • LED bar graph frequency/error deviation display • 0.1-10,000 µV output levels • High receive sensitivity, less than 5 µV • 100 KHz to 999.9995 MHz Continuous frequency coverage • Transmit protection, up to 100 watts • CTS tone encoder, 1 KHz and external modulation

### MINI KITS—EASY TO ASSEMBLE—FUN TO USE



**\$5.95**

Complete kit TD-1



#### COLOR ORGAN

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 110VAC.


ML-1 Kit **\$8.95**



VIDEO MODULATOR

Converts any TV to video monitor. Super stable for over ch 4-6. Runs on 5V accepts std video signal. Best unit on the market! Complete kit, JM-7

**\$12.95**

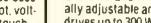

#### LED BLINKY KIT

Alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, warning panel lights. Runs on 3 to 15 volts.

BL-1 Kit **\$3.95**



#### UNIVERSAL TIMER

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs.

UT-5 Kit **\$5.95**



#### MAD BLASTER

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio. Runs on 6-15 VDC.

MB-1 Kit **\$4.95**



#### WHISPER LIGHT

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC.

WL-1 Kit **\$6.95**



#### FM MINI MIKE

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case mike, on/off switch, antenna, battery and super instructions. This is the finest unit available.

FM-3 Kit **\$16.95**

FM-3 Wired and Tested **19.95**

Complete kit MD-3 **\$16.95**

Case kit, CS-7 **12.95**

**NEW**

**NEW**



#### TELEPHONE TRANSMITTER

Low cost with professional performance. Features include: self phone line powered, tunable from 76 to 100 MHz, polarity selector, 10.7 MHz IF, integrated circuit detector, 50 mw audio amplifier, 9V external power source, operation on each side, compact (6" square), for bug detection or reception.

FR-1 KIT **\$14.95**

# GOTT ELECTRONICS

<b>COMBO PLUS by AST RESEARCH INC.</b>	<b>\$29.95</b>	<b>COMPUTER POWER CABLES BY BELDEN</b>	<b>\$2</b>
Memory Expansion & I/O Board for IBM PC, XT & Compatibles, real-time Clock-Calendar with battery backup, RS-232C Serial port, parallel printer port, SuperPak™, SuperSpool™, clock software, and the RAMCLEAR memory initialization utility program (available with 64, 128, 192, or 256 kilobytes of RAM memory \$9.00 per 64K increments.		10 AMP, 18/3, 6"	
<b>SIX PACK PLUS</b>	<b>\$39.95</b>	<b>TOSHIBA T3100 EXPANSION INTERFACE PA7313E</b>	<b>\$99.00</b>
Same as Combo Plus but expands to 384 KB of memory		<b>EXPANSION BOX PA7310U</b>	<b>\$299.00</b>
<b>SONY BATTERY PACK NP-11</b>	<b>\$39.95</b>	Interfaces Toshiba laptops to IBM BUS to use IBM add-on boards.	
(9.6V,1000MA) for laptop computers and camcorders, nickel-cadmium battery		<b>LCD DISPLAY (MODEL LM585) BY HITACHI</b>	<b>\$199</b>
<b>ASYNC CLUSTER ADAPTER by AST RESEARCH INC.</b>	<b>\$199.00</b>	640 x 200 Graphic and Alphanumeric	
Multichannel Board providing four individually addressable RS-232 Serial Ports on IBM PC/XT/AT and compatibles (uses AST-FourPort/XNTM Enhanced Xenix™ Communications Version #2.0) (ASYNC CLUSTER ADAPTER Cable additional \$15.00).		<b>LCD DISPLAY (MODEL EA-Y40025AT) BY EPSON</b>	<b>\$35</b>
<b>1/4" STREAMING TAPE CONTROLLER by ADAPTEC,</b>	<b>\$33.95</b>	40 characters X 2 lines	
<b>SCSI to QIC-36,</b> Model ACB-3530A	(Manual \$5.00)	<b>POWER SUPPLY</b>	<b>9.95</b>
<b>FLOPPY DISK CONTROLLER BOARD</b>	<b>\$19.95</b>	For computer related equipment, Input 120V AC, 60Hz, 30W; Output +5V DC, 1000MA, +/- 12V DC, 200MA	
Dual 360K or 720K switch selectable		<b>CCD DOCUMENT SCANNER</b>	<b>\$39.95</b>
<b>BEZEL</b>	<b>\$2.00</b>	Uses a 4096-element line imaging chip. Can use for robotics, astronomy, machine vision, high resolution slow scan TV, etc. Supplied with documentation.	
For full height hard drive, black with rectangular LED lower lefthand corner, double-sided tape for mounting, 3-3/8"x5-7/8"		<b>STEPPER MOTOR</b>	<b>\$29.95</b>
<b>LASER PLATFORM ARRAY</b>	<b>\$499.00</b>	By Oriental Motor, Model #PH566-A-Q5, high precision, 500 steps per revolution, 0.72° per step.	
10 MW HeNe Laser, power supply, 2 beam splitters, 5 front surface mirrors, AO modulator, AO driver, polygon scanner, photo detectors, 3 special lenses, polarizer, over \$5,000 worth of optical components plus documentation. Sold many of these to Fortune 500 companies, universities, and research labs. Applications include research, design and engineering. An experimenter's dream.		<b>HITACHI LCD DOT MATRIX LM215B</b>	<b>\$29.00</b>
<b>NEW! NEC 10 Mil HeNe LASER Plus Power Supply</b>	<b>\$200.00</b>	Graphic and Alphanumeric, 480 Dot(W) x 128 Dot(H) High quality device easily interfaced with microprocessor. Bit map graphics and text. Other applications possible. Driving voltages available at microprocessor port, CMOS/TTL-compatible signal level, built-in RAM for display data storage, built-in CMOS LCD driver and controller, supports full ASCII and extended character set, character size 5x7 or 7x9, dimensions 10.6" L x 4.3" W x 4/100" D	
<b>LASER POWER SUPPLY</b>	<b>\$39.95</b>	<b>HITACHI DIGITIZING TABLET HICOMSCAN HDG-111</b>	
Semi-kit. Units removed from laser video disk players, comprised of power cable, transformer and circuit board. Will power 1 to 10 MW HeNe laser. Excellent bargain.		Input device through which graphic data is input to a computer.	
<b>SHARP LASER DIODE</b>	<b>\$8.95</b>	11" x 10" Dimension	<b>\$199.00</b>
LT022MC, 5mW at 780nm, single transverse mode.		4-Button CURSOR for Digitizing Tablet	<b>\$29.95</b>
<b>MIRRORS, PRECISION FRONT SURFACE</b>		Manual	<b>\$5.00</b>
For use with lasers.		<b>EDGE CARD CONNECTORS</b>	
13-7/8"x1-3/16"      \$7.00      19-1/2"x1-5/8"	<b>\$10.00</b>	22/44 Connector, .156 spacing	<b>10pcs/\$7.50</b>
<b>GREEN FLUORESCENT TUBE</b> for scanners	<b>\$2.00</b>	25/50 Connector, for Apple	<b>10pcs/\$10.00</b>
<b>STAGE/STUDIO QUARTZLINE LAMP</b>		<b>COAX CONNECTOR</b> Part #CP-N1	<b>\$1.50</b>
FEL(Q1000/4CL) 1000W, 120V 3200		<b>MONITOR BOARD WITH POWER SUPPLY/HI VOLTAGE</b>	<b>\$7.95</b>
<b>INTEL 27128A-20 EPROM (New)</b>	<b>\$9.95</b>	Video, brightness, focus, vertical, and horizontal with flyback transformer and high voltage parts, Model 99-0493-001 rev D	
<b>INTEL 2732A-3 EPROM (New)</b>	<b>\$4.00</b>	<b>Replacement CABLES for IBM-like keyboards</b>	<b>\$2.99</b>
<b>INTEL P-8031</b>	<b>\$2.00</b>	<b>APPLE MANUAL</b> (LaserWriter and LaserWriter Plus)	<b>\$5.00</b>
<b>TRIAC: Hitachi FSM16F4</b> 400 volts 16 AMPS	<b>\$3.00</b>	<b>WATERTIGHT ALARM BELL</b>	<b>\$19.95</b>
<b>DIODES 6A 200V</b> Motorola Part No. MR752	<b>30 for \$10.00</b>	By Henschel Corp., Type IC/BID3, size 3", 24V DC	
<b>RF CONNECTOR APPLIED ENGINEERING PRODUCTS</b>	<b>\$2.50</b>	<b>5 LB. SOLDER</b>	<b>\$25.00</b>
Model 2005-1551-003		Wire, Rosin Core, Tin/Lead 60/40, Flux 2.2%, Dia. .036 (20Ga)	
<b>GOLD WIRE WRAP SOCKETS</b>		<b>HARD DRIVE CONTROLLERS:</b>	
14 pin-10 pcs/\$5      16 pin-10 pcs/\$6		Western Digital ST-506 (10-200 Mb)	
<b>SOLID STATE RELAY, CRYDON D1240</b>	<b>\$19.95</b>	XT-WD1002A-WX1      \$29      AT-WD1003WAH      \$39	
input 3-32 VDC, output 120 VAC 40A		<b>HP NUMERIC DISPLAY 5082-7300</b>	<b>\$4.95</b>
<b>BIPOLAR LEDs</b>	<b>10 PCS/\$6</b>	<b>DATA LINK CONNECTOR</b>	<b>\$7.75</b>
<b>MOTOR, AIRPAX</b>	<b>\$9.95</b>	(AMP Part #501107-2) Fiber optic field mountable connector used with 125 NM fiber clad OD. This connector mates with AT&T 40 MB/s and 1 MB/s data link products. AT&T F. Eq. Ref. No. 1005B.	
120VAC 60Hz 2-12:1 gear train, toothed pinion		<b>AMP OPTIMATE FIBER OPTIC CABLE ASSEMBLY</b>	<b>\$49</b>
<b>COMPUMOTOR:MOTOR-DRIVE SYSTEMS</b>	<b>\$1.50</b>	with Biconic Connectors (AMP Part #501450-2) 5 meters long.	
Model M57-83      \$ 773		<b>SYMBOL LASERSCAN 2000</b>	
Model M57-102      \$ 942		<b>VISIBLE LASER DIODE SCANNER</b>	<b>\$899</b>
Model M106-178      \$1695		Hand-held point-of-sale bar code scanner manufactured by Symbol Technologies, Inc.	
<b>VGA RT. ANGLE PC BOARD MOUNT CONNECTOR</b>		<b>ORIGINAL IBM MODEL 1130700</b>	
Hi Density DB 15	<b>10 pcs/\$10.00</b>	<b>COMPUTER PC POWER SUPPLY</b>	<b>\$19.95</b>
		63W 115VAC.	
		<b>ORIGINAL IBM MODEL 154001438</b>	
		<b>COMPUTER PC-XT POWER SUPPLY</b>	<b>\$29.95</b>
		130W 115VAC.	

# GOTT ELECTRONICS

## LASERS

### Laser Platform Array Kit Price \$499

Can be used for research, design, and engineering in the medical, industrial, and educational sectors. An experimenter's dream in the fields of holography, interferometry, graphic arts, light shows, and projection. The Laser Deck Consists of:

- A 10 milliwatt (maximum output) Helium-Neon laser tube (NEC Part #GLG 5261) which emits a red beam. The tube is hard seal and 15.5" long by 1.75" in diameter. It is mounted by two transverse mounting fixtures.
- The laser power supply (NEC Part #GLS5281A) powers the laser tube and has an input voltage of 115 to 120 VAC. Output sustaining voltage is 2800 to 3300 VDC.
- This unit sits on an 18.5 lb precision cast aluminum plate.
- The acoustic-optic modulator (NEC Part #OD8813A) is a 140 Mhz broad band amplifier and will take TTL and video signals. The A-O driver is on the deck also and requires 24 volts to operate.
- The polygon motor unit (Mfr: Japan Electronics) is a ten-sided first surface mirror mounted on an electric motor that spins at approx. 26,000 rpm. The driver for the polygon unit is on the deck and requires 24 volts to operate.
- In addition to the main items above, there are (5) special surface mirrors, (2) beam splitters and (3) special lenses all attached by optical mounts which guide the laser beam to various sensors and places to give the desired result, a reproduced copy of information.
- We have available an excellent 24 volt LAMBDA™ power supply at 49.95 that will power both the Acoustic-optic modulator and driver and polygon motor unit and driver.

**Laser Beam Modulator \$398** MC14016 tube of 25 \$5.00  
(Acoustic-Optic Modulator and Driver) Tri-state switch, CMOS

## COMPUTER POWER SUPPLY


### 130W 115 VAC IBM-XT Model 1501438

(+5V, +12V, -5V, 12V)

These are brand new supplies. They make an excellent workbench power supply for experimenting. They can also be used in XT computers and other electronic equipment.

Priced to move

1 .....	\$29.95
2-9 .....	\$25.00
10-25 .....	\$20.00

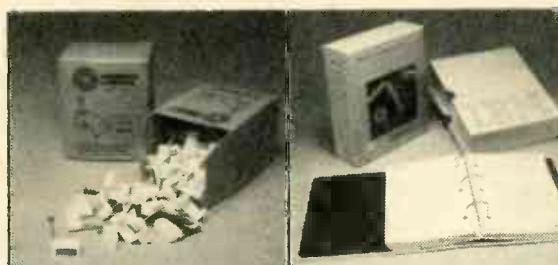

### CABLE NAILS by the box WOW!

Black or White

Each box, 100 nails. #814W-AB 13 mm for dual RG-59 cable. Manufactured by ABERDEEN. Used to tack when running cable. They have a hardened nail and tough plastic construction.

1 .....	\$2.00
2-9 .....	\$1.50
10-25 .....	\$1.25

### The REAL THING HARD TO FIND

The complete IBM DOS 3.3 manual in Spanish. Excellent for the bilingual schools and trade schools. We had a hard time finding these, so let's just blow them out to you.

1-9 .....	\$17.95
10-49 .....	\$15.00
50-99 .....	\$12.95
100-up .....	\$11.95

EL DOS de IBM es la base para miles de programas de aplicación. Muchas facilidades en el manejo de datos están a su disposición. Y usted puede desarrollar nuevas aplicaciones en una amplia gama de lenguajes de programación soportados.

## COMPUTER SWITCHING POWER SUPPLY

### 63W 115VAC IBM-PC Model 1130700

(+5V, +12V, -5V, 12V)

Brand New Supplies. Good for the workbench. Can be used for external drive. Full of good parts, 12VDC fan, caps, transistors, etc. We have over 1,000 of these units. Priced to move.

1 .....	\$19.95
2-9 .....	\$16.95
10-25 .....	\$14.95

## POWER CABLE

### 15'7" Long, 115V 20A

14/3 grounded 3-wire. Male plug one end, other end 3 wires. Black. Can be used on power tools, air conditioning, electrical appliances, and wherever. These are real beauties, difficult to find. We have over 4,000.

1-9 .....	\$5.00
10-49 .....	\$4.50
50-99 .....	\$4.00
1K .....	\$3.00

**ORDERS :** COD, Cashier's Check or Money Order

**Technical Support (213) 316-0916**

**FAX: (213) 316-9189**

**24-HOUR ORDER LINE: 800-544-9244**

\$15.00 minimum order. CA residents add 6.75%

# GOTT ELECTRONICS

2227 DuFour Avenue, Redondo Beach, CA 90278

# Amazing Pocket Reference!

480 pages of tables, formulas, & conversions and it fits in your shirt pocket!

(Size 3.2" x 5.4" x 0.6")

*The Greatest pocket reference of all time!*


## NEW RELEASE!

» Every engineer, geologist, manager, foreman, contractor, purchasing agent, maintenance person, and craftsman needs this book!

» A must for every student!

» The handyman's dream!

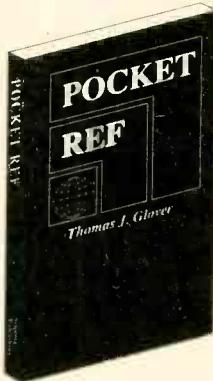**100% MONEY BACK GUARANTEE  
IF NOT COMPLETELY SATISFIED!**



**\$9.95\***

\* Plus shipping and handling and Colorado residents sales tax. See order form below.

## A UNIQUE PRESENT

- Air
  - Properties of Air
  - Density of Moist Air
  - General Gas Laws
  - Air Tool CFM vs PSI
  - Air Hose Friction
- Automotive
  - Antifreeze Table
  - Spark plug Torques
  - Battery Charging
  - Oil Viscosity vs Temp
  - Tire Size vs Load Rate
  - Tire Manufacturer Codes
- Carpentry and Construction
  - Lumber Sizes & Grades
  - Hardwood Grades
  - Wood Characteristics
  - Plywood & Panel Grades
  - Floor Joist Span Limits
  - Insulation R Values
  - Concrete & Mortar
- Chemistry & Physics
  - Element Tables
  - Periodic Table
  - pH of Acids & Bases
  - Elementary Particles
  - Radioisotopes
- Computers and Printers
  - Computer ASCII Codes
  - IBM® PC Error Codes
  - IBM® Interrupts-IO Map
  - IBM® Memory Map
  - 80286 Hard Disk Types
  - Printer Control Codes
  - Cable Wiring
  - Modem Commands
- Electrical
  - Electric Wire Size vs Load
  - Copper Wire Resistance
  - Electric Motor Specs
  - Wire Classes & Insulation
  - Wire Color Codes
  - NEMA Motor Frames
  - Wire & Sheet Guages
  - Electric HP vs Torque
  - Resistor Color Codes
  - Resistor Standard Values
  - Capacitor Color Codes
  - Pilot Lamp Specs
  - Fuse & Battery Specs
  - RF Coil Winding Data
  - Wire Size vs Turns/Inch
  - Wire Size vs Voltage Drop
  - Ampacity vs Temperature
  - Decibel Tables
  - Electric/Electronic Formulas
- General Information
  - US & State Holidays
  - Signs of the Zodiac
  - Flowers of the Months
  - Anniversary Names
  - Radio Alphabet
  - Morse & TEN Radio Codes
  - Paper Sizes (Intl)
  - Military Rank & Grade
  - State Information
  - Climate Data of the US
  - Time Zones of the US
  - Time Zones of the World
  - Telephone Area Codes
  - World Airport Elevations
  - Lost Credit Card Phone #'s
  - Airline 1-800 Phone #'s
  - Temperature Conversion
  - Sound Intensities
  - Body Weight vs Height
  - Wind Strength Scale
  - Wind Chill Factors
  - Firewood Comparisons
  - Frequency Spectrum
  - Sun & Planet Data
- Geology
  - Mineral Tables
  - Crystal Systems
  - Mohs Hardness Scale
  - Earthquake Scales
  - Geologic Time Scale
- Glues, Solvents, Paints and Finishes
- Hardware
  - Bolt Torque Tables
  - Wood Screw Specs
  - Sheet Metal Specs
  - Nail Sizes and Weights
  - Wire Rope Cable Clamps
- Math
  - Inch-Foot-MM-Drill Number
  - Math Formulas & Tables
  - Roman Numerals
  - Numeric Prefixes
  - Triangle Formulas
  - Plane Geometry Formula
  - Solid Geometry Formula
- Mining & Milling
  - Sieve Sizes & Met Tables
  - Stock Pile Volume & Weight
  - Dumping Angles
  - Mining Equipment Specs
- Money & Currency
  - Currency Exchange Rates
  - Interest & NPV Tables
- Plumbing & Pipe
- Rope, Cable, & Chain
- Steel & Metals
- Survey & Mapping
  - Percent Grade to Degrees
  - Mapping Scales & Areas
  - Stadia/Apparent Dip Tables
  - Magnetic Declination
- Tools
  - Tap-Die-Drill Sizes
  - Drill & Cut Lubricants
  - Fire Extinguishers
  - Sand Paper & Abrasives
  - Saw Blades
- Water
  - Water Friction Losses
  - Water Discharge Tables
  - Weld Electrode & Solder
  - Water Pollution & Hardness
- Weights of Materials
- Welding
- 3200 Conversion Factors

**And MUCH, MUCH more, this isn't even 1/2 of the contents of Pocket Ref!**

Please send me \_\_\_\_\_ copies of Pocket Ref

1 to 9 books = \$9.95 each      | Plus  
10 to 24 books = \$9.00 each      | Shipping ⇒  
25 to 54 books = \$8.50 each

### Total Shipping & Handling per Order

1 book = \$2.00	6 books = \$6.00	11 books = \$8.50
2 books = \$4.00	7 books = \$6.50	12 books = \$9.00
3 books = \$4.50	8 books = \$7.00	13 books = \$9.50
4 books = \$5.00	9 books = \$7.50	> 14 books = \$10.00
5 books = \$5.50	10 books = \$8.00	

Name: \_\_\_\_\_

Company: \_\_\_\_\_

Address: \_\_\_\_\_

Colorado Residents  
add 4.7% sales tax  
on the book + ship-  
ping total.

City/State/Zip: \_\_\_\_\_

Phone: (\_\_\_\_) \_\_\_\_\_

Payment enclosed (mark one): Check   Money Order   Visa   MasterCard

Card #: \_\_\_\_\_

Exp. Date: \_\_\_\_\_

Signature: \_\_\_\_\_

**The Book Source, Dept 954, P.O.Box 620820, Littleton, CO 80162**

**TOLL FREE ORDER LINE !!! • (800) 873-7157**

CIRCLE 342 ON FREE INFORMATION CARD

**Davlyn**  
CORP.

13406 Saticoy Street  
North Hollywood, CA 91605-3475

VISA

(Call for free catalog.)




**A.C. POWER SUPPLY**

**STACO MODEL E1010VA**

This unit has been designed and constructed for rigorous industrial, classroom or laboratory applications. These power supplies are brand new. Current list price \$750.00. Specifications: Input: 120 VAC 50/60 Hz. Output: 0-120 VAC 10 amps. Includes manual with schematics. Features: Ammeter, voltmeter, convenience outlet, power indicator and circuit breaker. Dimension: 10" x 15" x 6". Weight: 22 lbs.


Price: \$165

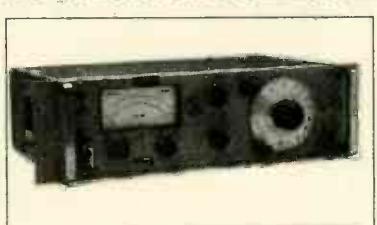

**HP 333A DISTORTION ANALYZER**

Covers 5 Hz to 600 kHz range. Measures down to 0.1% fullscale distortion. Includes auto nulling feature to speed up time consuming portion of measurements. Also includes switchable high-pass filter to attenuate frequencies below components.


Price: \$695.00

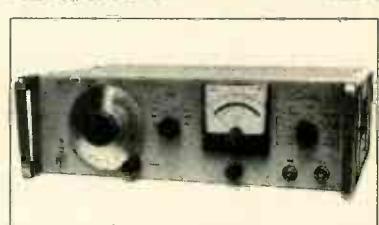

**HP 651A TEST OSCILLATOR**

Frequency range is 10 Hz to 10 MHz in six bands. Dial calibration, 1 to 10. Dial accuracy is  $\pm 2\%$ , 100 Hz to 1 MHz,  $\pm 3\%$ , 10 Hz to 10 MHz. Output of 200 mW (3.16 V input 50  $\Omega$ ); 16 mW (3.16 V input 600  $\Omega$ ); 6.32 V open circuit. Output monitor voltmeter monitors level at input of attenuator in volts or dB; accuracy is  $\pm 2\%$  at full scale; frequency response is flat within  $\pm 2\%$ , 100 Hz to 1 MHz;  $\pm 3\%$ , 10 Hz to 100 Hz;  $\pm 4\%$ , 4 MHz to 10 MHz. Attenuation range is 90 dB in 10 dB steps; overall accuracy is  $\pm 0.1$  dB.


Price: \$295.00

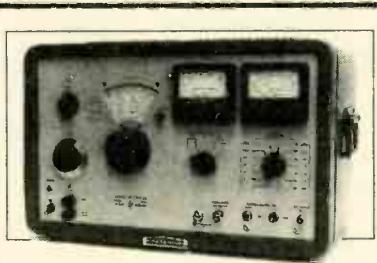

**HEWLITT PACKARD**

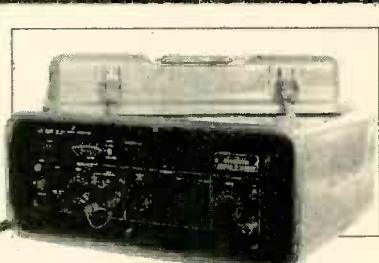
**MODEL 606A SIGNAL GENERATOR**

Signal Generator: Freq. 50kHz to 65 mHz in 6 bands  $\pm 1\%$ , freq. cal 100kHz and 1 mHz, RF output 0.1 uV to 3.0V at 50 ohms  $\pm 1$ dB over freq. range, output VVXR—30 DBC leverage 0.10V, modulation 0 to 100% +0.5dB over freq. range. Internal: 400 Hz/1000Hz  $\pm 5\%$ ; External: DC to kHz. Power 15230V, 50 to 1000 Hz, 135 watts. Size: 20 1/4" (W) x 12 1/2" (H) x 14 1/4" (L). Wt. 46 lbs. Price: \$250.00



**HEWLITT PACKARD 8640B-OPT 323  
SOLID STATE SIGNAL GENERATOR**

(w/o synchronizer) Frequency range: 450 kHz to 512 MHz, to 1100 MHz with external frequency doubler option (not supplied). Ten Frequency bands in octave increments from 500 kHz; band 11 for doubler use. Accuracy: 6 digit LED read out. Stability:  $< 1000$  ppm. Output power:  $-145$  dBm to  $+10$  dBm (0.013 V to 2 V) into 50  $\Omega$ . Level flatness is  $< +0.5$  dB from 0.5 to 512 MHz. Impedance is 50  $\Omega$ . VSWR  $< 2.0$  on 2 V and 1 V range  $< 1.3$  on other ranges. Spectral Purity: Harmonics at 1 V output  $> 35$  dB below fundamental of 0.5 to 128 MHz;  $> 30$  dB below fundamental of 128 to 512 MHz. Modulation: Internal AM, FM and PM, external AM, FM, and PM. Pulse frequency: 0.05 to 5 kHz. General: Power Requirements: 100, 120, 220, 240 V, 48 Hz to 420 Hz, 2 amps. Note: OPT 323 built to military specifications. Ruggedized performance for better operation under severe environment. Size: 6" (H) x 19" (W) x 13 3/4" (D). Wt. 60 lbs. Includes ruggedized case and manual. Price: \$1850.00

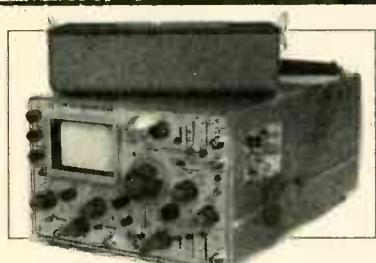

**TEKTRONIX MODEL 453  
OSCILLOSCOPE**

Vertical, 2 Channels. Bandwidth and risetime: 10 mV/div to 20 mV/div; DC to 50 MHz, 7 ns. 10 mV/div; DC to 45 MHz, 7.8 ns. 5 mV/div; DC to 40 MHz, 8.75 ns. Calibrated Deflection: 5 mV to 10 V/div in 11 calibrated steps (1-2-5 sequence). Input RC: 1 megohm  $\pm 2\%$ , 20 pf  $\pm 3\%$ . Modes: Channel 1, Channel 2 (normal or inverted), added alternate and chopped. Has vertical delay line. Horizontal: Time Base A: 0.1 us/div to 55/div in 24 steps. Length continuously variable from 4 div to 11.0  $\pm 0.5$  div. Time Base B: 0.1 us/div to 0.5 sec/div in 21 calibrated steps (1-2-5 sequence). X 10 Magnifier: Increases sweep rate to 10 n sec/div. Triggers after delay time or starts after delay. Time Base A Trigger Modes: DC internal/external: AC, AC/CLF reject, AC HF reject. X-Y operation Ch 1 horizontal, Ch 2 vertical, 5 mV/div to 10 V/div in 11 calibrated steps. B.W. is DC to  $\geq 5$  MHz ( $-3$  dB). Horizontal Amplifier (ext in) 270 mV/div or 2.75 V/div in external  $\pm 10$  position. Calibrated sweep delay: 0.2 us to 50 sec. General: Power Requirements: 90 to 272 V @ 48 to 440 Hz. Size: 7 1/4" (H) x 12 1/2" (W) x 20 1/2" (D)  $>$  Wt. 27 3/4 lbs. Includes manual. Price: \$400.00



**L.R.  
TANK  
PERISCOPE**

Type M-24. Rugged military construction. Contains two independent infrared image converter tubes plus correction lenses, prisms, and eyepieces. The binocular viewing system is directly connected to a prism-type periscope. The image tubes have dynamic focus provided by a built-in adjustable voltage divider. This unit requires 10 to 15 KV at low current for operation. Unable to supply power supply. (Dimensions: 18" high x 9" wide x 4 1/2" thick. Weight 17 lbs.) Stock #OP 9001 Price: \$200.00

Current Hewlett Packard Price \$12,050.00

**(818) 787-3334**

**(800) 235-6222**

**OUTSIDE CALIF.**


**FAX (818) 787-4732**

QUALITY PARTS • DISCOUNT PRICES • FAST SHIPPING

# ALL ELECTRONICS CORP.
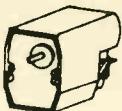
## MINIATURE GEAR MOTORS

Buehler series 61.13  
Miniature DC gearhead  
motors. Reversible.  
Motor and gearhead  
enclosed in rugged  
die-cast housing. 1.55" X 1.122" X 1.475".  
Long-life bronze bearings. 0.115" diameter  
flatted shaft. Two types available:




18 volts dc (nominal) @ 50 ma.  
10 rpm @ 14 Vdc (no load)  
17 rpm @ 24 Vdc (no load)  
**CAT# MOTG-18 \$5.50 each**

38 volts dc (nominal) @ 70 ma.  
274 rpm @ 24 Vdc (no load)  
451 rpm @ 38 Vdc (no load)  
**CAT# MOTG-38 \$5.50 each**
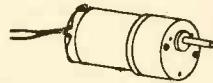
## 12 VDC GEARHEAD MOTOR

Soho# GBL 35-DH-21080-10Y  
Powerful little  
gearhead motor.

40 RPM @  
12 Vdc. 0.5 amps  
(no load). 32 RPM with load.



Operates at lower voltages with reduced  
speed and torque. 6.3 pound inches  
torque. Stall: 27 pound inches. 3.1" long X  
1.375" diameter. Shaft: 0.187" dia. X 0.75"  
long. **CAT# MOTG-14 \$11.50 each**  
10 for \$100.00

## STEPPING MOTORS


Airpax# C82711-M1  
17 Vdc 23.25 ohm  
dual coil, permanent  
magnet stepper motor. 7.5 degrees per  
step. 2.25" dia. X .91" thick. 0.25" dia.  
shaft is 0.6" long. Two hole mounting  
flange, 2.625" centers. 6 wire leads.  
**CAT# SMT-6 \$6.00 each • 10 for \$50.00**




Airpax# C 82710  
12 Vdc, 36 ohm dual coil permanent mag-  
net stepper motor. 7.5 degrees per step.  
2.25" dia. body X 0.93" high. Mounts on  
2.675" centers. 6 wire leads.  
**CAT# SMT-7 \$7.00 each • 10 for \$65.00**
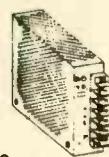
## POWER SUPPLIES

**5 VOLT, 5 AMP**  
Lambda# LUS-9A-5  
Switching power supply.  
Input: 85-132 Vac 47-440Hz  
or 110-165 Vdc 37 watts  
Output: 5 Vdc ± 5% @ 5 amps.  
Overvoltage and overcurrent protection.  
120 mV ripple. 5.2" X 3.8" X 1.375". Grey,  
vented metal case. UL and CSA listed.  
**CAT# PS-55 \$14.00 each**



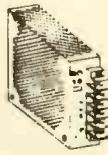**12 VDC 2.1 AMP**  
Lambda# LUS-9A-12  
Fully enclosed switching  
power supply with screw  
terminal connections.  
Input: 120 Vac 60 Hz.  
Output: 12 Vdc ± 5% @ 2.1A overvoltage  
and overcurrent protection. Compact venti-  
lated case measures 5.24" X 3.81" X 1.38"  
overall. Includes instruction sheet.  
**CAT# PS-122 \$23.50 each**



**24 VOLT DC - 2.4 AMP**  
Power-One Inc. # HC24-2.4  
Input: 115/230 Vac  
(wired for 115Vac)  
Output: 24 Vdc @ 2.4 amp. Brand new  
open frame power supply with line and  
load regulation, remote sensing, overload  
and short circuit protection. 5.62" X 4.87"  
X 2.50". CSA rated.  
**CAT# PS-2424 \$30.00 each**



## 6 or 10 mhz HU-18/U STYLE CRYSTALS - SPECIAL PRICE

**6 mhz CAT# CRY-618S**  
**10 mhz CAT# CRY-1018S**  
**MINIMUM ORDER  
100 PIECES**  
100 of either VALUE \$75.00  
500 of either VALUE \$300.00  
1000 of either VALUE \$500.00




## CHOKE GRAB BAG

8 pieces, 2 each of  
4 different tunable  
chokes. Actual values unknown.  
**CAT# GRCK \$1.00 each**


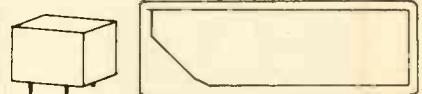
## ELECTROLUMINESCENT STRIP(GLOW STRIP) AND INVERTER




Electroluminescent strips used for back-  
lighting control panels or as decorative or  
emergency prime lighting source. They are  
thin, tough and flexible and operate on low  
current. They operate on AC voltage, and  
the preferred power source is a miniature  
DC to AC inverter. We received a supply  
of glow strips that have a bit of an odd  
shape. The strips are 2.15" wide X 5.88"  
long and are 0.035" thick. The luminescent  
area is 5.3" long X 1.72" wide and has  
one corner cut off, leaving a useful area  
of fairly good proportions. We are selling  
the strips and inverters as a package.  
Inverter operates on 6 Vdc.

Glow strip, inverter and hook-up diagram  
**CAT# GS-500 \$5.00 per set**

## EXTRA INVERTERS

Input: 6 Vdc Output: 225 Vac  
**CAT# INV-1 \$2.00 each**

## DIGITAL CLOCK AND APPLIANCE TIMER

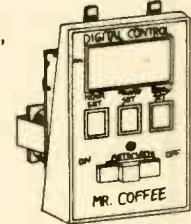

Turn on lights, radio,  
VCR automatically.  
Digital clock and  
appliance timer  
removed from  
automatic electric  
coffee makers due  
to design changes.

Operates on 120 Vac and is capable of  
turning on appliances drawing up to 10  
amps. Because of the application they  
were designed for they automatically turn  
off after two hours. Guaranteed to work  
but some have surface blemishes. 4.2" X  
2.45" X 1.1" deep. Beige or ivory with  
brown trim. **CAT# MCT \$6.50 each**

**TOLL FREE ORDER LINES 1-800-826-5432**

**FAX (818) 781-2653 • INFORMATION (818) 904-0524**

Minimum Order \$10.00 • All Orders Can Be Charged To Visa, Mastercard Or Discovercard • Quantities Limited •  
California, Add Sales Tax • Shipping And Handling \$3.50 For the 48 Continental United States - All Others Including  
Alaska, Hawaii, P.R. And Canada Must Pay Full Shipping • No C.O.D. • Prices Subject to change without notice.

QUALITY PARTS • DISCOUNT PRICES • FAST SHIPPING

# ALL ELECTRONICS CORP.

## LED'S

Special purchase on two types of rectangular LEDs. Both styles have a face which is 5 mm X 2.1 mm.




Red LED 10 mm long and 4 mm wide at the base.  
CAT# RLED-5 10 for \$1.00  
200 for \$15.00 • 1000 for \$50.00

Green LED 8 mm long and 2.1 mm wide throughout.

CAT# RLED-6 10 for \$1.00  
200 for \$15.00 • 1000 for \$50.00
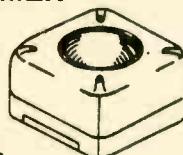
## ONE MINUTE TIMER

Originally used as a game timer this white box with a blue button will drive you crazy. Box measures 3 1/4" square X 2" high. When the button is pressed 4 LEDs light and a beeper pulses. Every 15 seconds one led goes out and the speed of the beeping increases. At the end of 60 seconds the unit gives off a long beep followed by a low squelch, all LEDs shut off and the unit stops. If at any time during the cycle you want the unit to stop, press the blue button and the beeping stops and in ten seconds the unit shuts off. Unit requires a 9 volt transistor battery (not included) to operate.




CAT# TMR-1 \$2.25 each • 10 for \$20.00

9 volt Alkaline battery

CAT# BAT-9 \$1.70 each
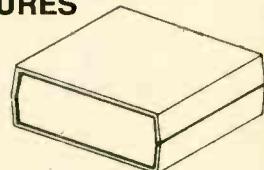
## ABS INSTRUMENT ENCLOSURES

Molded ABS Instrument enclosures are available in ivory, beige, grey, blue,



and black. Front and rear panels in matching .090" thick ABS plastic or, as an option, anodized satin finish aluminum. Integral P.C. board mounting standoffs and two sets of vertical mounting slots for front and rear subpanel P.C. boards. Includes 6-32 pan head screws and anti-skid rubber feet. All enclosures are 6" wide X 6.25" deep. Front and rear panels available in 2.25", 2.625", and 3" heights.

color	panel ht.	cat #	1-9	10-99	100+
ivory	2 1/4"	MB 1A	\$7.50	6.50	6.00
beige	"	MB-2A	"	"	"
grey	"	MB-3A	"	"	"
blue	"	MB-4A	"	"	"
black	"	MB-5A	"	"	"
ivory	2 5/8"	MB-1B	\$7.75	6.75	6.25
beige	"	MB-2B	"	"	"
blue	"	MB-4B	"	"	"
black	"	MB-5B	"	"	"
ivory	3"	MB-1C	\$8.00	7.00	6.50
beige	"	MB-2C	"	"	"
grey	"	MB-3C	"	"	"
blue	"	MB-4C	"	"	"
black	"	MB-5C	"	"	"

## RELAYS

### 6 VOLT D.C. - D.P.D.T.

Sigma# 70 HE22-6DC.

2 amp contacts.

52 ohm coil.

Polycarbonate cover.

1 1/8" high X 9/10" X 3/4"



CAT# RLY-62PC \$2.50 each

### 24 Vdc - D.P.D.T. - PC MOUNT


Fujitsu# FRL-264 D024/02CK

10 amp contacts.

685 ohm coil.

1.354" X .858" X 1.110".

Clear plastic case.

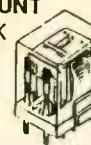

CAT# RLY-229 \$2.50 each

### 24 Vdc - D.P.D.T. - PC MOUNT

Omron# MX2P-OE-UZ-006004

492 ohm coil.

Contacts rated

3 amps @ 120 Vac

or 5 amps at 30 Vdc.

Clear polycarbonate dustcover 1.03" X 0.875" X 0.69". UL and CSA listed.

CAT# RLY-230 \$1.75 each



Satin finish aluminum front or rear panels.

panel ht.	cat #	1-9	10-99	100+
2 1/4"	PNL-1	\$1.00	.85	.70
2 5/8"	PNL-2	\$1.20	1.10	1.00
3"	PNL-3	\$1.40	1.25	1.10

## NEON INDICATOR 120 VOLT



Good looking neon indicator

RATED: 120 volts @ 1/3 watt. Mounts in 5/16" hole. Red lens with chrome ring.

CAT# IND-100 75¢ each  
10 for \$7.00 • 100 for \$65.00


## REFLECTIVE OPTO SENSOR

IR emitter and sensor pair pointing in the same direction. Light from emitter bounces off object to be detected by sensor.

TRW/Optron# OPB5447-2

Rectangular package with 28" color coded leads.

CAT# OSR-4 2 for \$1.00

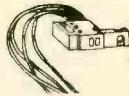

CALL OR WRITE FOR OUR  
**FREE** 60 PAGE CATALOG

WITH OVER 4000 PARTS!  
OUTSIDE THE U.S.A. PLEASE SEND  
\$2.00 POSTAGE FOR A CATALOG

**TOLL FREE**  
**PHONE ORDERS**  
**1-800-826-5432**

MAIL ORDERS TO:  
**ALL ELECTRONICS**  
P.O. BOX 567  
VAN NUYS, CA 91408

If you mail to the computer marketplace . . .

## MAILING LISTS TO TARGET YOUR KEY PROSPECTS

### 1) HEATHKIT

Over 97,000 electronic hobbyists who purchase ham radios, home computers, educational courses.

### 2) NUTS & VOLTS

83,000 Subscribers/buyers of parts and accessories for ham radios, computer hardware and software, CB gear, cable TV.

### 3) KENSINGTON MICROWARE

An active file of 273,000 buyers and inquirers of micro computer peripherals. Select IBM-PC, Macintosh, Apple users.

### 4) JDR MICRODEVICES

NEW! A large list of micro computer users.

For details, call or FAX:

**J.F. Glaser Inc.**  
999 Main Street / Suite 103  
Glen Ellyn, IL 60137  
708-469-2075  
FAX: 708-790-5244

AUDIO POWER DRIVER ICs: NE540H.....\$1.49 LM391N-80....\$1.29				CMOS	TLC555.....\$0.69	AUDIO AMPS.	TDA2002 (8W).....\$0.99
				TIMERS	TLC556.....\$0.99	(TO-220 CASE)	TDA2030 (14W).....\$1.49
<b>ALPHA-NUMERIC LED ARRAY</b>	<b>CRYSTALS</b>	\$1.25		<b>STEPPER MOTOR</b>	<b>\$3.95</b>		
 7x5 LED Matrix. For Moving Message Signs, Etc. By IEE. # 2057 - c/c rows. Your Choice: # 2058 - c/a rows. \$2.95 ea. With Hook-Up (SIZE: 2 X 1.5 in) (8 For \$17.95) RARE SURPLUS FIND! NEW!	1.843 4.000 2.000 4.915 2.457 5.068 3.120 8.000 3.579 10.000 3.680 11.059	14.318 20.000 ALL IN MHZ		IBM Surplus. 8 wire. 4 windings. 7V @ 350 mA 1.8° (200 steps per rev.) DC. res. 20 ohm ea. 25 oz. in. torque. Works great on 5vdc. W/Data FOR ROBOTICS	IBM Surplus. 8 wire. 4 windings. 7V @ 350 mA 1.8° (200 steps per rev.) DC. res. 20 ohm ea. 25 oz. in. torque. Works great on 5vdc. W/Data FOR ROBOTICS		TRIAC: BT139-500 12 AMP 500 PRV. TO-220 \$0.99
<b>RS232 DRIVERS</b>	<b>MOS POWER FETS. ALL NEW!</b>			<b>CMOS 8032 MICROPROCESSOR</b>			<b>TRIAC DRIVERS</b>
1488.....\$0.49 1489.....\$0.49 MAX232....\$2.49	IRF 521 (TO-220) N-CH.....\$0.59 IRF 531 (TO-220) N-CH.....\$0.89 IRF 9531 (TO-220) P-CH.....\$0.99 IRF 243 (TO -3) N-CH.....\$1.19 IRF 253 (TO -3) N-CH.....\$1.49 VN67AB (TO -5) N-CH.....\$0.79 VN10K (TO -92) N-CH.....\$0.49 IRFD110 (DIP) N-CH.....\$0.89			80C32 By Matra. 40 pin DIP 12 MHZ. Very low power. \$3.95			MOC3010 MOC3040 MOC3011 MOC3041 \$0.99
<b>J FETS FOR HAMSI</b>	<b>PLASTIC TRANSISTORS: 6 FOR \$1</b>			<b>STATIC RAMS</b>			<b>LINEARS</b>
MPF102 or 2N5486 \$0.49 Your Choice	VN67AB (TO -5) N-CH.....\$0.79 VN10K (TO -92) N-CH.....\$0.49 IRFD110 (DIP) N-CH.....\$0.89			6116LP-15.....\$1.95 6264P-15.....\$2.95 62256LP-10.....\$8.95 2114.....\$0.89 7198-S45P.....\$1.99			OP07 (DIP).....\$1.49
<b>CAPS FOR HAMS !</b>	<b>BY PASS CAPS</b>			<b>VOLT. REG. ICs</b>			TL062 (house #).....\$0.49
High Voltage ! Very Dangerous. 110 MFD 450V AXIAL.....\$1.90 800 MFD 450V CAN.....\$3.95 5100 MFD 350V CAN.....\$6.95 ALL NEW. NAME BRANDS ! HARD TO FIND.	.1 MFD 50V RADIAL (.10 in. spacing) 10/\$1 (.30 in. spacing) DIP 8/\$1	7805.....\$0.49 7812.....\$0.49 7815.....\$0.49 7824.....\$0.49 7905.....\$0.49 7912.....\$0.49 7915.....\$0.49 7924.....\$0.49		LM317.....\$0.69 LM337.....\$0.69 78H12.....\$4.95 78H05.....\$3.95 723.....\$0.49 TL494.....\$1.19 TL495.....\$1.19 TL497.....\$1.49			TL072 (DIP).....\$0.59
<b>CAPS FOR POWER SUPPLIES</b>	<b>CMOS EPROMS</b>			<b>FULL WAVE BRIDGES</b>			LM324 (DIP).....\$0.49
8200 MFD 50V...RADIAL.....\$0.99 12,000 MFD 75V...CAN.....\$2.95 21,500 MFD 40V...CAN.....\$2.95 41,000 MFD 35V...CAN.....\$3.95 47,000 MFD 25V...CAN.....\$2.95 105,000 MFD 25V...CAN.....\$2.95	27C32HQ (house #).\$1.49 27C64-2 (Intel).\$2.99 27C256 (TI).\$3.50 27C512 (TI).\$5.50			1.5A 400V.....\$0.49 2A 200V.....\$0.49 10A 400V.....\$0.99 4-element, 35A 600V.....\$2.95			LM358 (DIP).....\$0.49
<b>TANNER ELECTRONICS</b>	214-242-8702			coated. F:5.7 10in. F.L. \$9.95			MC4741 (DIP).....\$0.59
1301 W.Beltline Rd. #105 Carrollton, Tx 75006	FAX: 214-709-5041			fixed aperture of 1.75 in. NEW			LM318 (DIP).....\$0.99
							LF356 (can).....\$0.89
							5532 (DIP).....\$0.99
							5534 (DIP).....\$0.99
							MC3403 (DIP).....\$0.49
							TLO84 (DIP).....\$0.99
							RC4558 (DIP).....\$0.49
							4136 (DIP).....\$0.69
							LM339 (DIP).....\$0.49
							75491 (DIP).....\$0.69
							75492 (DIP).....\$0.69
							ULN2003 (DIP).....\$0.69
							LM3900 (DIP).....\$0.59
							LM2900 (DIP).....\$0.79
							XR2240 (DIP).....\$0.99
							<b>MOSFETS FOR RF</b>
							3N204 Your Choice: 40820 MPF131 \$0.59

# Electrified

WE WILL TRY TO BEAT ANY PRICE ON ANYTHING FROM ANYWHERE!!!  
A TRULY PROFESSIONAL STAFF WITH A COMMITMENT TO SERVICE!!!

## ★ COMPUTER COUNTRY ★

### AWESOME 80286 TURBO - 10/16MHz

Fully IBM Compatible Zero Wait State\*

512K Installed - Full Size Case  
200 Watt Power Supply  
Award BIOS - 101 Keyboard  
Up to 4 MB on Motherboard  
8 I/O Slots - 80287 Socket  
Reset and Turbo Button  
Keylock and 3 LEDs  
Clock/Calendar  
1 YEAR WARRANTY

Now  
16MHz

**\$399**

Now  
16MHz

#### System Options

512K Upgrade for 286	1 MB
Controller 160 or 300	99
Controller w/ Dual HD/HD	79
1.2 MB - 5 1/4 Drive	79
380K - 5 1/4 Drive	79
720K - 3 1/2 Drive	79
1.44 MB - 3 1/2 Drive Red DOSE	119
2048K - Hard Drive	169
3048K - Hard Drive	199
4048K - Hard Drive	249
AT&T Copy Monitor & AT&T Card	29
AT&T 17" Black & White Mono TTL	29
AT&T Card	29
12" Monochrome Hi Res TTL Monitor	69
Mono Graphics Card w/Printer Port	39
Serial Card or Parallel Card	19
Clock Calendar Card	29
Par/San/Clk/Game Card	49

Drive Warranties Vary - Call for Details

### 80386 20 MHz Power

1MB - Installed - Expands to 8 MB on Board - Zero Wait State - Norton Landmark - 28 7-Slots - 1 - 32 Bit, 5 - 16 Bit, 1 - 8 Bit Mini Tower Case - 200 Watt Power Supply - 4 - Drive Bays 2 - 5 1/4" - 1/2 Ht & 2 - 3 1/2" 80387 Socket - Clock Calendar 101 - Keyboard - 1 Year Warranty Fully IBM Compatible.

**\$995** Add \$400 for 386/25 MHz

### THE SUPER SYSTEM

#### 8088-1-10Mghz TURBO COMPUTER SYSTEM

##### 1-Drive IBM Compatible System with 256K Memory

System Includes: 256K INSTALLED 8088-1 Processor - 1-Half Height, 360K, 5 1/4 Drive INSTALLED - Dual Speed - 4.77 Mghz and 10Mghz - TURBO - 8 slots - 8087 Socket - 150 Watt Power Supply - Deluxe Keyboard - Full Size Case or 4-1/2 Ht. Drives - 1 Year Parts-and-Labor Warranty on Base Unit (Drive Warranties Vary)

System Options:  
Add a 2nd 360K 5 1/4 Drive \$79  
All Hard Drives Include Controllers  
Add a 10MB Drive 149  
Add a 20MB Drive 199  
Add a 30MB Drive 249  
Add a 40MB Drive 299  
AT&T Color Monitor & AT&T Card 249

Super inexpensive

**\$299**

Quantity Pricing Available

NOW 10 Mhz

### HARD DRIVE DEALS

#### MINISCRIBE 8450 XT 40MB Hard Drive Kits 40MB - 1/2HT - 5 1/4" Frame 3 1/2" Drive-45MS Access Speed

##### 8-Bit RLL Controller INCLUDED

Limited Quantities  
1 Year Warranty  
from Miniscribe

**\$279**

MINISCRIBE-3085-85MB-MFM-5 1/4"-1/2HT  
MINISCRIBE 3675-62MB-RLL-5 1/4"- NEW  
MINISCRIBE-8450-40MB-RLL-3 1/2"- NEW  
SEAGATE-ST-138R-32MB-RLL-3 1/2"-  
MINISCRIBE-8438F-30MB-RLL-3 1/2"-NEW  
SEAGATE-ST-238-30MB-RLL-3 1/4"-1/2HT  
TANDON-TM-262-20MB-MFM-3 1/2"-  
WESTERN DIGITAL-MFM-XT Cont. w/ Cables  
RLL Controllers for XT and AT's Available

**\$499**  
\$299  
\$239  
\$199  
\$179  
\$179  
\$149  
\$49  
CALL!

MINISCRIBE Warranty-6 Months-NEW DRIVES  
Seagate & Tandon Warranty-90 Days-OEM Pulls  
QUANTITY PRICING AVAILABLE  
CALL FOR DETAILS!

### MONITOR MANIA

#### PRINCETON GRAPHICS

Ultra Sync 14 Color Monitor  
14" Multisync - Ultra Hi-Res 31 Dot Pitch  
800x600 Refurbished

Mint Condition - Full 1-Year Warranty From Princeton  
Monitor Cards  
On Special

Only **\$449**

#### IBM — VGA COLOR

13" Viewing Area - 640x480 - 31 Dot Pitch  
IBM Model #7544/S01 BRAND NEW

High Performance Graphics

90 Day Warranty

Only **\$399**

#### UNBELIEVABLE VALUE

AMDEK 600T — Color  
14" -RGB-Color-600x200, Green/Amber Switch, Tilt & Swivel  
BRAND NEW List \$550 ONLY **\$209**

#### AMSTRAD COLOR VGA 28 Dot Pitch

Ultra-Hi-Res-12" VGA-PC-Model 12HR  
Tilt & Swivel - 720 x 480 -  
Anti-Glare Screen Only **\$299**

1 YEAR WARRANTY-BRAND NEW

NCR - 15" - GREEN - TTL with NCR  
Monitor Card - 640x400 LIST \$438 ONLY  
BRAND NEW 90 Day Warranty **\$149**

AT&T CRT-327 - 12" TTL-Black &  
White Monitor & AT&T 1024HP Card  
H-Resolution-800x480-Tilt & Swivel  
Works On All IBM AT/XT's & Compatibles

90 Day Warranty List \$1390  
Quantity Pricing: 6\$115.12-\$109.24-\$105 Over 24-Call ONLY **\$119**

AT&T CRT-327 - 12" TTL-Black &  
White Monitor & AT&T 1024HP Card  
H-Resolution-800x480-Tilt & Swivel  
Works On All IBM AT/XT's & Compatibles

90 Day Warranty List \$1390  
Quantity Pricing: 6\$115.12-\$109.24-\$105 Over 24-Call ONLY **\$119**

## ★ ★ Electrified Discounters ★ ★

HOURS: Mon Thurs 9AM - 7PM  
Fri Sat 10AM - 6PM

ORDERS  
ONLY

**(800) 678-8585**

Customer Service & Technical Support  
**(203) 287-1976**

### SUPER SOFTWARE SET

For IBM or IBM Compatibles - 3 Outstanding Packages at One Amazing Price  
DAG - EASY ACCOUNTING  
Includes: GL, A/R, A/P, Purchase Order - Billing, Inventory & Forecasting

PRACTIWORD - WORD PROCESSOR

Easy to use Word Processor - with Multi Level Help System

PRACTIBASE - DATA BASE MANAGER

A Powerful Relational Database Manager

List Price \$269.95

DAC EASY ACCOUNTING TUTOR

AVAILABLE - Call for Pricing

**\$39.95**

### PRINTER POWER

#### SAVE 80% IBM 5182 COLOR PRINTER

BRAND NEW • Heavy Duty

List \$1,995

**\$399**

• Wide Carriage (132 Column)  
• 200 CPS Draft - 110 CPS Correspondence  
35CPS NLO - Prints Black, 4 Colors, and 8 Colors  
• Bi-Directional Dot Matrix - 9 Wire-Parallel Interface  
• Tractor included

FRONT - BOTTOM - IDEAR PAPER FEED -

Paper Rack Available - Stacks Printed Paper ONLY \$12.95

Easy Change Cartridge Ribbons - Available

30 Day Warranty QUANTITY PRICING - CALL!!!

### TOSHIBA P-321SL

#### AMAZING PACKAGE

Brand New

24-PIN-216CPS-72NLQ-Narrow Carriage  
Parallel and Serial Interface-32K Buffer-Tractor  
Full Manufacturer's Warranty - 1 Year Parts and Labor

Package Includes: P 321SL Printer, Cut Sheet Feeder  
12-Black Multistrike Ribbons, 3 Font Cartridges

SAVE 72% Package Price List **\$399**

### THE BEST PRINTER VALUE IN THE USA!!

#### MPI — PRINTMATE — 350

300 CPS - 60M-LQ - Wide Carriage

18 - Wire Technology - IBM/Epson Codes - Variable Width  
Tractor Up to 6-Part Form - Front Key Pad with Over 50

Functions - 90 Day Warranty - Parallel Interface (Serial Optional)

Quantity Pricing Available Amazing

CALL! BRAND NEW List \$625

**\$200**

CITIZEN MSP - 50

BFAND NEW! - Color Optional!

300 CPS 50-NLQ - Narrow Carriage, 9 Wire - Epson/IBM Compatible  
Push or Pull Tractor - Zero Tear Off

Color Kit (7 Colors) Top or Bottom Feed, Automatic Paper Loading

Serial Interface 512K Buffer - 18 Month Manufacturers Warranty

Font Card and Sanitizer \$29. Parallel Interface

Black or Color Ribbons Available Call Only **\$269**

Quantity Pricing: 3-\$249, 6-\$275, 12-\$299, 24-\$325

BRAND NEW **\$259**

SEIKOSHA SL-80AI

24 Pin - 135CPS - 54NLQ Below Dealer Cost

RITEMAN BY C-ITOH 120CPS-60CPS Expanded Narrow Carriage-Parallel Interface

90 Day Warranty - Quantity Pricing Available

The Best Color Monitor & Card Deal In The USA

### AT&T

#### 318H with AT&T Color Card

Works on All IBM AT/XT's & Compatibles

12" - Super Hi-Res — CGA — Color Monitor  
600x400 — 31 Dot Pitch — Anti-Glare Screen

Tilt & Swivel - 90 Day Warranty

Comes with the AT&T VDC-400 Color Card

Better Than EGA Resolution! Brand New Condition

Factory Rebuilt

List \$849

The Best CGA Resolution You Can Buy

Quantity Pricing: 3-\$269, 6-\$259,

12-\$249, 24-\$239 Over 24-Call ONLY **\$279**

### 30-DAY MONEY BACK GUARANTEE!

Full Refund of HARDWARE

Price on all Advertised Products

Catalog Sent with All Orders

Dealer Inquiries Invited

All Prices Listed are Cash Discounted Add 2

1/2% for MasterCard, Visa or AMEX. Not

responsible for typographical errors. Com

pany reserves the right to cancel any order

14% down payment required. 3 months to

pay balance. 20% interest. 18 months to

pay balance. 24 months to pay balance.

Computers are not guaranteed. Some system

options may be refurbished. IBM is a

registered trademark of International

Business Machines Inc.


# SURPLUS SALE

WE HAVE AVAILABLE OVER 125,000 SURPLUS PLUG-IN WALL ADAPTERS. THESE ARE ALL BRAND NEW IN A WIDE RANGE OF VOLTAGES AND CURRENTS IN BOTH AC AND DC OUTPUTS. WE ALSO HAVE 220/240VAC ADAPTERS AND DUAL OUTPUT VOLTAGE POWER SUPPLIES. PHONE OR FAX US FOR OUR LATEST ADAPTER CATALOG OR CALL FOR AVAILABILITY AND PRICE QUOTE ON YOUR NEEDS. WE ARE ALSO INTERESTED IN PURCHASING YOUR EXCESS ADAPTER INVENTORY. CONTACT US TODAY!

## SPECIAL PURCHASE!

### 9VDC/500ma WALL ADAPTERS

23,000 IN STOCK  
AT PRESS TIME!!

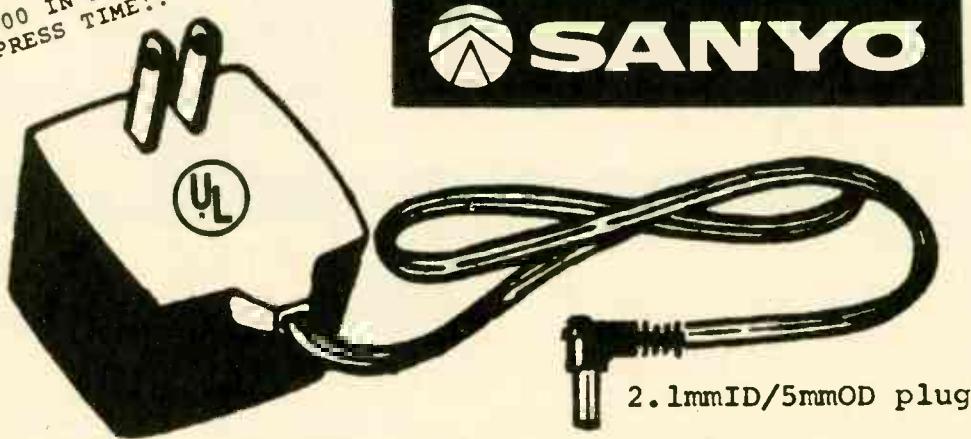

VG610

CR610....CSA APPROVED VERSION...P.O.R.

SURPLUS TRADERS specializes in the distribution of surplus parts and equipment to the electronic, computer and hi-tech industry. We publish a wholesale surplus catalog which is available to the trade at no charge. Please make your request on your company letterhead or accompanied by your business card. If you indicate your areas of interest or specialization - we will key our computer to target special offers in your field of interest. Hobbyists and those not in the trade may obtain our catalog for a handling charge of \$2.

\$1.95EA/1000  
\$2.25EA/500  
\$2.95EA/100  
\$3.25EA/50

**SURPLUS  
TRADERS**  
P.O. Box 276  
Winters Lane  
Alburg, Vermont 05440  
514-739-9328  
(Fax 514-345-8303)




## PRICES

Our competitive prices have placed us at the top. We have low, low prices because we mark down each item the lowest % we can afford.
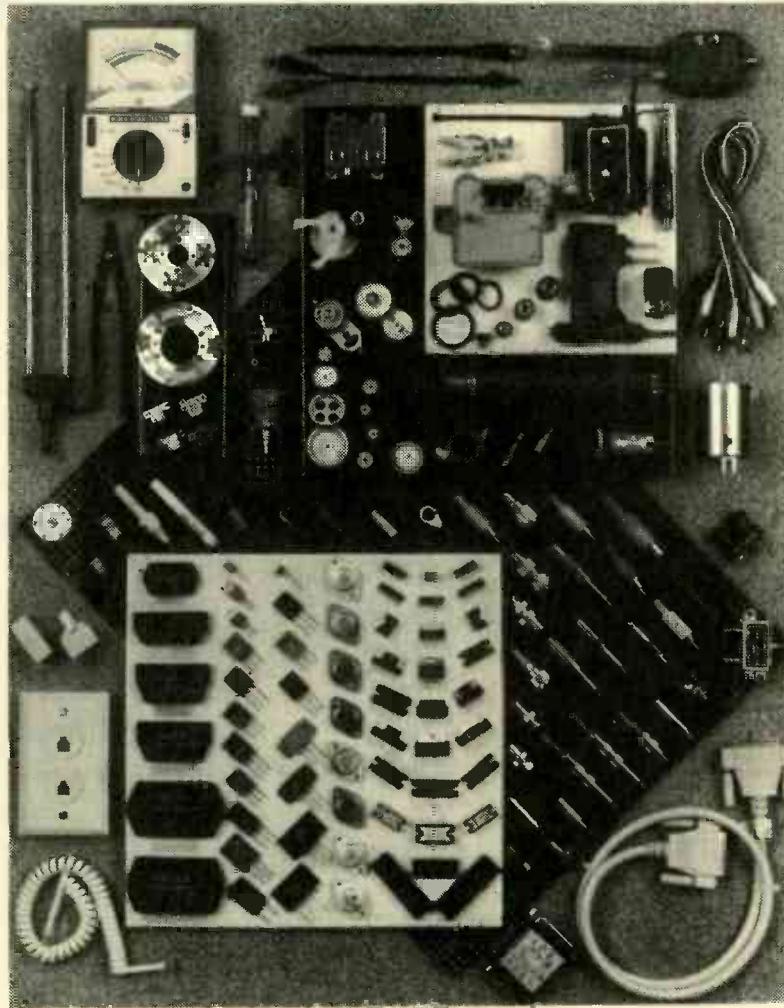
## SERVICE

For decades, our 23,000 customers have been satisfied because we are aggressive in making sure we do all we can to help customers save and grow.



## QUALITY

We sell high quality merchandise. If it wasn't good, we wouldn't buy it ourselves. Your satisfaction is guaranteed.

## SHIPPING

We ship anywhere in the world within 24 hours from the date of your confirmation. We can use:

- \* Airmail
- \* Airlines
- \*DHL
- \*UPS
- \*other means of transport

**CALL FOR A FREE CATALOG:**

**1-800-325-2264**




Computers, Components, Tools And Supplies

# Computer Products

4025 Edwards Road  
Cincinnati, OH 45209


1 (800) 423-4499

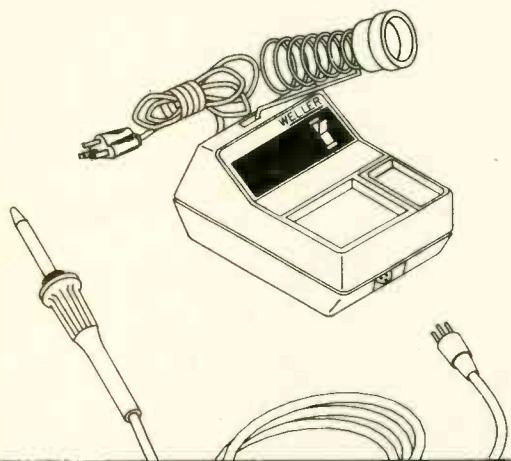Weller WTCP Professional  
Soldering Station.....\$99.99




Cyrix Fasmath coprocessor  
Fully compatible with Intel  
but much faster.....  
80387-16 .....\$299.99  
80387-20 .....\$349.99  
80387-25 .....\$429.99  
80387-33 .....\$529.99

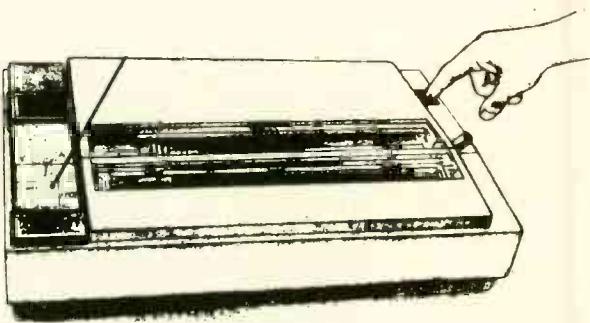
Facit B3350 Wide Carriage Printer  
18 pin, includes cable.....\$329.99



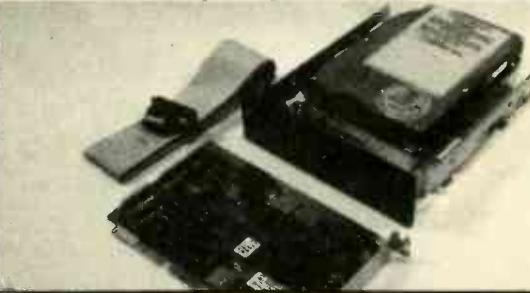MiniScribe M8450 Hard Drive Kit  
42.6 megabytes - 46 ms access  
with 16 bit card, cables....\$249.99



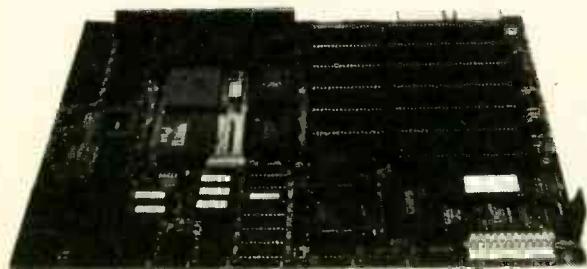db is one of the midwest's  
largest suppliers of electronic  
and computer parts!!! ICs,  
resistors, capacitors. Call or  
write for our free catalog.



db Kit Systems - All the top  
quality parts necessary to  
assemble your own custom  
PC, AT, 386 or 486 system.



386-33 cache main board  
0K memory..... \$1,399.99

MicroSoft Bus Mouse  
The real thing.....\$39.99

# Microsoft Mouse


EasyPrint shares printers  
for 2 PCs.....\$79.99



SQZ Plus from Symantec  
The best spreadsheet file  
utility for Lotus.....\$49.99

SQZ!  
plus

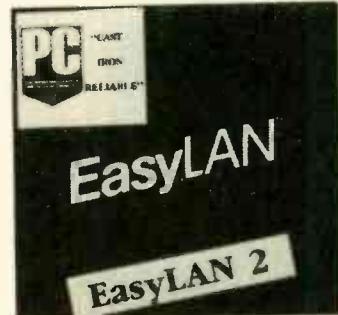EasyLan PC to PC Network Special  
Full resource sharing network  
with hardware, software, cables




The whole works.....\$179.99

Reference File, The first really  
serious pop-up database  
management system.....\$49.99



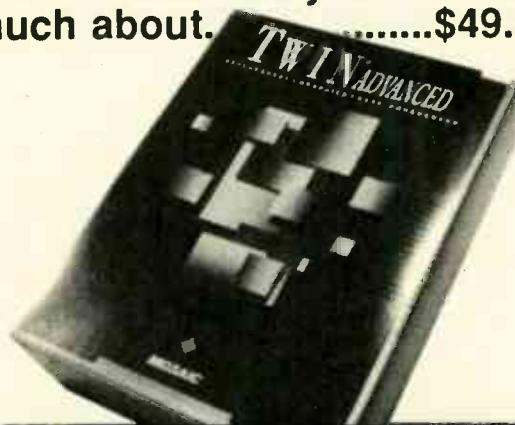Twin Advanced, Spreadsheet -  
Graphics - Data Management -  
This is the one that you've heard  
so much about. ....\$49.99




**db Computer Products**

prices and availability subject to change without notice  
cash mail order prices - shipping and handling extra

4025 Edwards Road, Cincinnati, OH 45209 (800) 423-4499

# NOW YOU CAN AFFORD A LOGIC ANALYZER

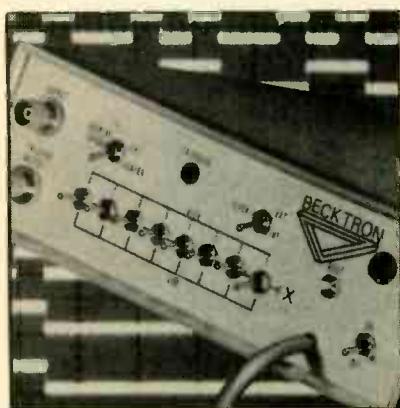

BECKTRON's A-96

The A-96 will convert any oscilloscope into an eight channel logic analyzer with;

- \* 2K MEMORY PER CHANNEL
- \* PRE-TRIGGER AND POST TRIGGER DATA CAPTURE
- \* INTERNAL AND EXTERNAL CLOCKING
- \* STORING UP TO SIXTEEN THOUSAND LOGIC EVENTS

The A-96 is so technologically advanced that it's simple to use and at \$389.00 it's affordable. For full information call BECKTRON at 1-800-592-4141 and request the "A-96 INFO PACKAGE" Master card, Visa and C.O.D. orders excepted

## ALL PURPOSE TERMINALS



MANUFACTURED BY  
RCA

**\$85**

RCA's APT is a high quality, self-contained computer, a smart terminal, loaded with many features. Originally selling for about \$500, this terminal is a super value for anyone needing a computer to access bulletin boards, word process or simply free up a larger PC.

- Built-in dual speed telephone modem with RJ-11 port for easy hookup.
- Composite video or RF (channels 3&4) allow use of either a monochrome or TV type monitor.
- Parallel printer port for connection of a Centronics type printer.
- Serial (DB-25) RS-232 port allows connection of TNC, hard drive, modem or other peripheral.
- Keyboard selectable 40 or 80 column display.
- Built in word processor with word wrap feature.
- All terminal parameters are fully adjustable allowing emulation of many terminal systems.
- Also includes acoustical coupler input, auto log-on, 8 customizable function keys plus more!

Our APT's are very clean units removed from service. Instruction manual, wall cube power supply and TV / APT selector switch included. Optional 6' Centronics printer cable- \$25. Add \$5 for UPS.

## IRON POWDER TOROID CORES

CORE	O. D.	L / M	1-10	11-99	CORE	O. D.	L / M	1-10	11-99	CORE	O. D.	L / M	1-10	11-99
15.6	.050"	10	.35	.25	144.2	.440"	.52	.70	.60	115.6	1.57"	.115	3.25	2.75
12.2	.125"	48	.35	.30	144.6	.440"	.42	.70	.60	120.2	2.00"	.120	4.00	3.60
12.6	.125"	17	.35	.30	150.2	.500"	.49	.80	.68	120.6	2.00"	.100	4.75	4.25
12.17	.125"	7.5	.40	.35	150.6	.500"	.40	.80	.68	120.52	2.00"	.900	3.00	2.40
116.52	.160"	150	.35	.30	150.17	.500"	.18	.90	.78	122.5-28	2.25"	.215	6.00	5.40
125.2	.255"	34	.40	.35	150.26B	.500"	.420	.90	.78	122.5-6	2.25"	.100	6.00	5.40
125.6	.255"	27	.40	.35	150.52	.500"	.350	.80	.68	130.2	3.04"	.114	6.00	5.40
125.17	.255"	12	.40	.35	168.2	.690"	.57	.80	.68	130.20	3.04"	.228	13.00	12.
130.2	.307"	43	.40	.35	168.6	.690"	.47	.80	.68	130.6-52	3.04"	.850	8.00	7.20
130.6	.307"	36	.40	.35	168.52	.690"	.420	.80	.68	140.2	4.00"	.180	13.00	12.
130.17	.307"	16	.40	.35	168.2	.795"	.55	.95	.82	140.20	4.00"	.360	22.00	20.
130.52	.307"	73	.40	.35	170.6	.795"	.45	.95	.82	140.52	4.00"	.1400	12.00	11.
137.2	.375"	40	.60	.50	180.52	.795"	.500	.85	.72	1520.2	5.20"	.200	22.00	20.
137.6	.375"	30	.60	.50	171.30	1.30"	.15	3.00	.240					
137.17	.375"	15	.60	.50	1517.2	1.57"	.140	3.25	.275					

Toroid cores are used in most radio frequency projects because of their relative small size. EMI/RFI filters are made with a core in the interference's frequency range. The suffix of each core (eg. -2 or -6) indicates the mix.

- 2 mix - Maximum Q range: .25-10 MHz.
- 6 mix - Maximum Q range: 2-30 MHz.
- 17 mix - Maximum Q range: 20-200 MHz.
- 26 mix - Maximum Q range: DC, 8 MHz.
- 52 mix - Maximum Q range: DC, 1 MHz.

\* Note: Toroids operate at 4 to 100 times the stated frequency range with reduced Q and efficiency.

**"Where the hard to find parts are found..... and on hand"**

Catalog 6 included with your order (\$3 a la carte), 200 pages, over 10,000 electronic PARTS including almost any capacitor (transmitting to monolithic), resistor, inductor, wire or cable, toroid & ferrite, Collins replacement part, antenna, connector (rf, computer, IC, electrical), shaft, coupling, knob, motor, transistor, diode, IC, switch, relay (solid state to contactors), project box, rubber feet, hardware (stainless, brass, etc.), tubing, fan or blower, tube (receiving to transmitting) or tube socket. Please add adequate shipping (\$3 min). We accept Visa, MC, Amexco, checks, COD add \$3.

1315 Jones St. • Omaha, Nebraska 68102 • 402-346-4750 • fax: 346-2939

**Surplus Sales of Nebraska**

## BACK-UP ALARM

- Prevents possible backing accidents
- Detects unseen objects behind a vehicle
- Gives out a warning signal to the driver
- Eliminates the guesswork when parking in reverse
- Never again will heavy rain, snow, or fog be a problem



- Easy installation on to the bumper
- Available in black, silver, chrome, red, ivory to match the color of your bumper
- 30 day satisfaction guarantee: Full refund if not satisfied

**\$49.99**

+ \$2.50 shipping & Handling

Send check or money order to:

**Calco International**

18040 Sherman Way Suite 511  
Reseda, CA 91335

**Tel: (818) 708-2334**

**Fax: (818) 708-2362**

## PENCIL-TYPE DMM/LOGIC TESTER

The Voltmaster 90S from Bel Merit Corporation provides a full range of digital-multimeter and logic-test functions in an easily portable package. It has a 3½-digit LCD with function annunciators and automatic polarity indication. It offers automatic and manual range selection and data hold. Its functions include logic test, diode test, audible continuity check by buzzer, AC/DC current measurement to 200 mA, AC/DC voltage measurement to 500 volts, and ohm measurement to 20 megohms. All ranges are protected. The Voltmaster 90S comes with an operating manual, two 1.5V batteries, power leads for logic tests, and test leads.



**CIRCLE 320 ON FREE INFORMATION CARD**

The Voltmaster 90S pencil-style DMM and logic tester costs \$49.95. —**Bel Merit Corporation**, 14775 Carmenita Road, Norwalk, CA 90650; Tel. 213-802-3666.

# Cable TV

## Descrambler Article Parts

We stock the exact Parts for several articles published in Radio-Electronics magazine on building your own Cable TV Descrambler.

### February 1984 SB-3 Type

**701** Parts Pkg.....\$19.00

*Includes all original parts.*

**702** PC Board.....7.95

*Original 3X4 etched, drilled and Silk-Screen pc board.*

**704** AC Adaptor.....7.95

*12 to 18 Volt DC @ 200ma.*

**701, 702 & 704**.....29.00

*All three for special saving.*

### February 1987 Tri-Mode

**301** Parts Pkg.....29.00

*Includes all original parts.*

**302** PC Board.....7.95

*Original 5X8 etched, drilled and Silk-Screen pc board.*

**304** AC Adaptor.....7.95

*12 to 18 Volt DC @ 200ma.*

**301, 302 & 304**.....39.00

*All three for special savings.*

Tri-Mode Tutorial..7.95

*26 pages of in-depth info.*

### May 1990 Universal

**901** Parts Pkg.....\$49.00

*Includes all original parts.*

**902** PC Board.....9.95

*Original 4X7 etched, drilled and Silk-Screened pc board.*

**904** AC Adaptor.....8.95

*12 Volts AC @ 350ma.*

**901, 902 & 904**.....59.00

*All three for special savings.*

**CD22402E**.....12.95

*Video sync IC (IC-9)*

### Snooper Stopper...\$39.00

*Prevent Descrambler detection with snooper stopper/data blocker and protect your privacy.  
Includes free article on Cable Snooping.*

### Macrovision Kit...\$29.00

*Macrovision....now you see it, now you don't with our macro-scrubber kit.  
Originally Published in Radio-Electronics.*

### Signal Eliminator (tunable notch filter).....\$29.95

*ELIMINATE a channel that you find unsuitable or CLEAR UP a channel that contains severe interference by eliminating it. NOTE: If picture and sound are effected, this is interference and CAN BE removed. If only the picture is effected, this usually IS NOT interference and CANNOT be removed. Works on Cable or Broadcast TV.*

# 23H Tunes 50-66 Mhz & 6 Meter Ham , For channels 2 or 3..

# 46FM Tunes 66-108 Mhz; or any FM station. For channels 4, 5 or 6.

# 713 Tunes 174-216 Mhz For channels 7, 8, 9, 10, 11, 12 or 13.

# 1417 Tunes 120-144 Mhz For channels 14 (A), 15 (B), 16 (C) or 17 (D).

# 1822 Tunes 144-174 Mhz For channels 18 (E), 19 (F), 20 (G), 21 (H), 22 (I).

### 58 Channel Cable TV Converter with infra-red remote .....\$69.95

*Re-Manufactured Jerrold 400 with new remote. Channel 3 output.  
Compatible with all External Descramblers.*

# CALL TOLL FREE 1-800-332-3557

Outside USA Call 1-508-699-6935

Visa, MasterCard and COD. Free Catalog.

Add \$4.00 S&H, \$6.50 Outside USA.

D & D Electronics, Inc. PO Box 3310, N. Attleboro, Ma. 02761

VISA

MC

## 5 SECOND EPROM ERASER

- A REVOLUTIONARY PRODUCT.
- INCREDIBLE SPEED, ONLY 5 SECONDS.
- ONCE YOU USE IT, YOU'LL LOVE IT.
- SAVE YOUR TIME & MONEY.
- A MUST ITEM FOR THOSE PEOPLE HAVE EVERYTHING.
- DIMENSION: 7" X 4" X 3".
- ONE YEAR WARRANTY (EXCEPT UV TUBE).


IEE-9088 \$249.99



## RF REMOTE CONTROL SYSTEM

19683 digital coding  
2 tiny transmitters  
ON/OFF confirming signal  
Dry contact relay output  
FCC approved

SA-432 \$49.99

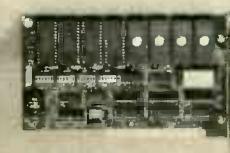

## ROM/SRAM DISK CARD

For diskless PC station  
Load DOS & files instantly  
Battery back-up for SRAM  
watch-dog timer rebooting  
RDC-512 (512 KB, 0KB) \$179.99  
RDC-1024 (1024 KB, 0KB) \$199.99

## BARGAIN SALE

SYNTAX Proto-typing PCB COMBO-1	\$9.99
SYNTAX Proto-typing PCB COMBO-2	\$11.99
SYNTAX Proto-typing PCB COMBO-3	\$39.99
SYNTAX Proto-typing PCB COMBO-4	\$11.99
SYNTAX Proto-typing PCB SUPER COMBO	\$69.99

## ELECTRONICS

1 2 3

A DIVISION OF MING E&P, INC.

1. Exclusive Items at good price.
2. Unique items at better price.
3. Popular Items at the best price.

1-800-669-4406

ORDER DESK ONLY

## DIGITAL VOICE RECORDER

- ADM RECORDING SYSTEM.
- INSTANT RECORD & PLAY BACK.
- 4 MEGA BIT DRAM, PROVIDE YOU 2 MINUTES OF HIGH QUALITY VOICE.
- 16 SELECTABLE PHRASE CHANNELS.
- PLASTIC HOUSING W/ MIC & AC ADAPTER.
- BUILT-IN 500MW AUDIO AMP & SPEAKER.
- FULLY ASSEMBLED & TESTED.

DVR-120 \$189.99



## DEXXA MOUSE

Superior tactile feedback switch  
50-750 adjustable dpi  
Opto-mechanical design  
Microsoft mouse compatible  
UL and FCC approved

DLX-MOUSE \$39.99



## PIR DETECTOR


Very small size (2.5"X1.7"X1.4")  
Advanced SMT design  
Extra high RFI immunity  
Adjustable pulse count feature  
Security industry quality

RK-3000 \$49.99

1. Price are subject to change without notice.
2. VISA, MASTER CARD and COD(add \$3) accepted.
3. Freight charge add \$5 UPS Ground, \$8 UPS Blue, \$15 UPS Red.

977 S. Meridian Ave., Alhambra, CA 91803

TEL: (818) 281-4065 FAX: (818) 576-8748

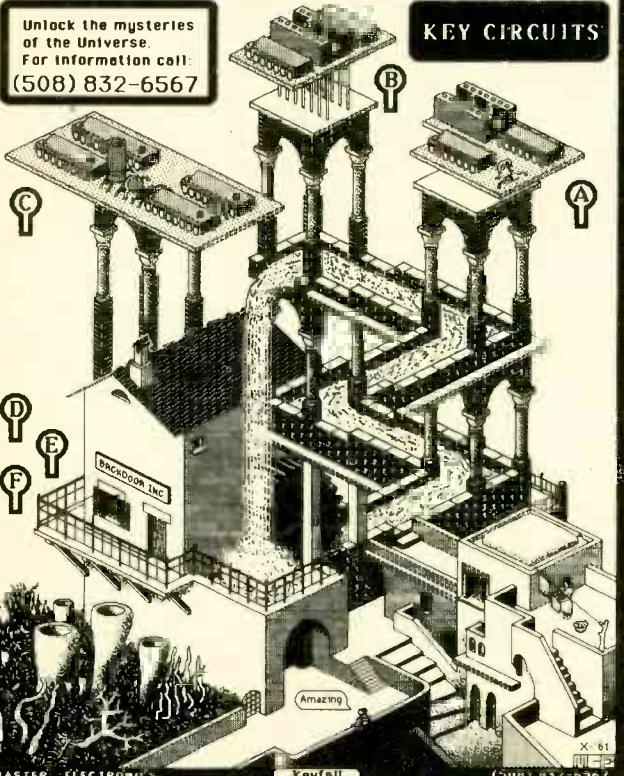

**BRIEF:** The SA10 and SA20 are the most sophisticated and reliable stand alone descramblers ever made for S. A. equipment. They are highly integrated premium descramblers designed to "S. A. Specifications" for superior performance.

They have no "jitters", no video level problems, no alignment or quality control problems, and no sensitivity or basic design problems associated with the simple video and clock circuits of the SA-3. (THIS IS NOT AN SA-3 CLONE OF ANY KIND!)

The SA10 and SA20 have a great looking cabinet enclosure, the quality of which would fit in beautifully with a component home stereo/entertainment system. Also the power supply is built into the enclosure.

The SA10 and SA20 are available from **MASTER ELECTRONICS** (THE S. A. SPECIALISTS) who sell only S. A. related equipment and only the best of that. **MASTER ELECTRONICS** is dedicated to customer satisfaction and is ready to offer their services at competitive prices. **MASTER ELECTRONICS** and the SA10/SA20 ASSAULT DESCRAMBLERS are ready to blow away the competition.

- Superior Performance
- Conforms to S. A. Specs.
- Drop Field Capable (SA20)
- Auto Scramble Detect
- False Firing Switch

- High Quality Control
- Handsome Enclosure
- Built In Power Supply
- Power On L.E.D.
- Competitive Pricing

KITS  
DESIGNED  
AND MADE  
IN U.S.A.

# THE ELECTRONIC GOLDMINE

MINIMUM ORDER: \$10.00 plus \$3.00 Shipping and Handling  
We accept MasterCard, Visa and Money Orders  
Call or send for our free catalog.

P.O BOX 5408, Scottsdale, AZ 85261  
PHONE ORDERS: (602) 451-7454

## MINI GEIGER COUNTER KIT

- ★ Detects ALL Types of Radiation
- ★ Uses Sensitive Alpha Window Tube
- ★ Operates from 9V Battery (not incl.)
- ★ Comes with PC Board, Parts, Tube and Instr.
- ★ Size of PC Board: 3" x 1.9"
- ★ Skill Level 2



C6430 \$59.95

## ELECTRONIC WHEEL OF FORTUNE KIT

- ★ 10 LEDs spin as speaker clicks
- ★ Operates from 9V battery (not incl.)
- ★ Skill level 3



C3806 \$14.98

## LED FLASHER KIT



- ★ One red and one green LED alternately flash
- ★ Operates on 9V battery (not incl.)
- ★ Skill level 1

C3287 \$3.00 **Sale**

## 120VAC XENON STROBE KIT

- ★ Complete Variable Rate
- ★ Comes with PC Board, Parts and Instructions
- ★ Skill Level 2

Remember, all of  
our kits contain all  
parts, PC board  
and instructions!

C3071 \$13.70

## 3V XENON WARNING FLASHER KIT



- ★ Bright white flashes of light
- ★ Requires only 2AA or C cells
- ★ Skill level 2

C3207 \$10.00

## BATTERY OPERATED BLACK LIGHT KIT




- ★ Detects invisible Fluorescent Inks, Minerals, etc.
- ★ Uses Large Unfilled U Shaped Black Light Tube
- ★ Operates from any 6V Battery Source (not incl.)

C6356 \$13.95
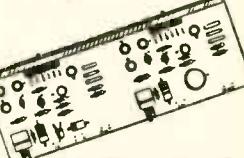
## 20W+20W STEREO AMP KIT

- ★ Boost Car Stereos, Tape Players, Portable Radios, etc.
- ★ Features 2 Separate 20W RMS Amps w/Level Controls
- ★ Operates from Std. 12V Car Battery
- ★ Skill Level 2



C6442 \$19.95

**FREE CATALOG**  
WITH  
OVER 1400  
DIFFERENT  
ITEMS  
INCLUDING  
135 KITS!  
REQUEST YOUR  
COPY TODAY!

## \$1 BLOWOUT SALE

Tremendous bargains on prime components only \$1.00 per pack

<input type="checkbox"/> 50	1% Precision Resistors*	G705
<input type="checkbox"/> 20	Plastic Transistor PC Leads	G706
<input type="checkbox"/> 30	Capacitors-Disc & Electrolytic*	G707
<input type="checkbox"/> 2	CDS Cells	G708
<input type="checkbox"/> 2	Solar Sensors	G709
<input type="checkbox"/> 40	Tiny 1/8W Resistors*	G710
<input type="checkbox"/> 10	1N4004 Diodes	G711
<input type="checkbox"/> 12	LEDs-Different Colors, Sizes*	G712
<input type="checkbox"/> 4	Circuit Board with Bubble Readout	G713
<input type="checkbox"/> 20	Surface Mtg. Chip Capacitors*	G714
<input type="checkbox"/> 20	Surface Mtg. Chip Resistors*	G715
<input type="checkbox"/> 20	Silver Mica Capacitors*	G716
<input type="checkbox"/> 20	Micro Red LEDs on Strip	G717
<input type="checkbox"/> 10	Tantalum Capacitor*	G718
<input type="checkbox"/> 20	9V Mini Zeners	G719
<input type="checkbox"/> 10	3MM Ultrabright Green LEDs	G720
<input type="checkbox"/> 10	Small Single Turn Trim Resistors*	G721

Items marked with \* are assortments and will contain several different values.

**\$1.00 Each**

## FIBER OPTICS

Small diameter unjacketed fiber optic strand. Perfect for 1000's of applications. Fun to use and experiment with.

G722

5Ft piece for 49¢ Each

## BLUE BUTTON TIMER

**Sale**

Unique game timer features 4 LEDs that extinguish one at a time over a ONE minute period as the unit increases its beeping. Great timer for games. Operates from 9V battery (not incl.).



G723  
\$2.95

## ZIPPER CLOSE BAGS

HIGH QUALITY!  
2 mil bags with white block to write on. Sold in packages of 100 only.

2 x 3	G663	100/\$3.30
3 x 4	G664	100/\$3.75
3 x 5	G665	100/\$4.00
4 x 6	G666	100/\$5.50



## 9VDC ADAPTER

**Great  
Bargain!**



Perfect for almost all 9V battery powered items. Has 9V snap, filtered output. For 120VAC.

G724 \$1.69

## POPULAR ITEMS

### COLOR BURST CRYSTAL



Miniature Case. 3.579545MHz  
G615 \$1.00 Each  
10 for \$9.00

### BAG OF HEAT SHRINK



Handy assortment of 25pcs of various sizes/colors 1" to 3" L and .06" to 5'Dia.  
G179 \$1.00

### COPPER CLAD PC BOARD



Thin flexible PC material can be cut with scissors. Double sided 4" x 6".  
G591 75¢

### ELECTREC MICROPHONE



Sensitive type. 1Ft cable.  
G703 69¢

### #65 DRILL BITS




Tungsten carbide. Most popular size for PC boards.  
G725 3 for \$2.00

### INVERTER TRANSFORMER



Small 4 lead transformer for use with 555 IC to convert 12VDC to 250V for strobe/fluorescent tubes with schematic.  
N1703 \$2.00 Each  
1,000 for \$1,500

### MAGIC SOUND SWITCH

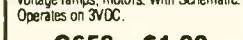

Triggers with clap of hand. Turn on low voltage lamps, motors. With Schematic. Operates on 3VDC.  
G658 \$1.00

### 4KV TRIGGER COIL



For strobe tube  
3 Lead N1700  
1.25 Each 1,000 for \$650  
4 Lead N1701  
1.45 Each 1,000 for \$700

### HORSESHOE STROBE TUBE



Standard 1-1/4" tall  
A1034 \$3.75

### LASER LIKE LED



300MCD Ultrabright clear  
jumbo case red LEDs  
A1012 3 for \$1.00  
1,000 for \$220

### FLASHING RED LED



Flashes when 5VDC is applied.  
Red diffused case.  
G301 79¢



**Learn at home  
in your spare time**



**Earn up to  
\$30 an hour  
and more!**

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!

## GUARANTEED PASS...

Here's our famous warranty  
that you **will** get your FCC License  
or your money will be refunded.

## You can earn more money if you get an FCC License

Not satisfied with your present income? Add prestige and earning power to your electronics career by getting your FCC Government License.

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License".

This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Broadcast, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business.

You don't need a college degree to qualify, but you do need a Commercial FCC License.

### No Previous Experience Necessary

Our proven course is designed so even beginners can start fast. Step-by-step, you start with the very basics—and continue lesson by lesson at your own pace...in your own home.

The course is written in everyday language, complete with photos, diagrams and audio cassette tapes that make it simple and easy to understand.

No need to quit your job or go to school. This proven FCC training "Self-Study" system is easy, fast and low cost!

### Get Started Immediately!

Thousands of high-paying jobs are waiting for ambitious people who have an FCC License. So, mail us the coupon and we'll rush you complete information FREE by return mail.

### Read What Others Are Saying

"Yes, I got my FCC license. I also got a pay increase and am now studying for the Radar Endorsement."  
— JC, Hope, AK

"I studied for only one weekend with your course and didn't miss any questions on the test."  
— HS, Tampa, FL

"When given my exam and I began, I could barely believe my eyes, it was just like sitting at home studying your course."  
— TB, Hines, OR

"I got my license which changed my life immediately. I am now in Communications servicing FM 2-way equipment. This was accomplished only because of your material."  
— MK, Glenn Falls, NY

"Your study tapes and manuals were wonderful. I've passed my test today and I owe it all to your books and tapes. Thank you so very much."  
— TB, Bloomington, IN

### COMMAND PRODUCTIONS

D-93

FCC LICENSE TRAINING  
Custom House POB 2824  
San Francisco, CA 94126-2824

YES! Please rush FREE details immediately on how I can study at home for my FCC License.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

**Mail This Coupon Today!**

# GRAY MATTER COMPUTING

**XT SYSTEM:** 8088-10 with 640K, 360K Floppy, 2 parallel, 2 serial, 1 game port, 101 keyboard, clock/calendar, monographic card & monitor. \$399.00

**AT SYSTEM:** 286-12, 1MB RAM, 1.2 Floppy, 2 ser, 2 par, 1 game, 101 keyboard, 1:1 hd/fd Controller, monographic video card & monitor. \$699.00

**386-25/64K Cache system includes 2MB RAM, 1.2 Floppy, 1:1 hd/fd Controller, 2 ser, 1 par, 1 game port, 101 keyboard, 16 bit VGA Card & monitor.** \$2085.00

*We will happily configure a system to fit your needs.*

CALL  
TODAY

1:1 AT MFM HD/FDController	\$119.00
1:1 AT RLL Combo Controller	\$130.00
XT MFM & RLL Controllers	\$51, \$59
360K & 1.2MB Floppy Drives	\$60, \$76
720K & 1.44MB Floppy Drives	\$65, \$78
CMS Jumbo Tape Backup	\$295.00

#### Hard Drives:

40MB MR535 MFM 28ms RLL cert	\$350.00
72MB Maxtor XT1085 FH 28ms	\$625.00
80MB HH1090 MFM 28ms	\$625.00
100MB CP3104 IDE (AT) with kit	\$695.00
200MB CP3204 IDE (AT) with kit	\$1070.00

4357 Mt. Hukee Avenue

619-278-8211

San Diego, CA 92117

PCBoards

### P-C-B ARTWORK MADE EASY!

Create Printed Circuit Artwork on your  
IBM or Compatible

- \* MENU DRIVEN
- \* HELP SCREENS
- \* ADVANCED FEATURES
- \* EXTREMELY USER FRIENDLY
- \* AUTO GROUND PLANES
- \* 1X and 2X PRINTER ARTWORK
- \* 1X HP LaserJet ARTWORK

\* HP and HI PLOTTER DRIVER optional 49.00

REQUIREMENTS: IBM PC or Compatible, 384K RAM  
DOS 3.0 or later. IBM compatible printers.

PCBoards - layout program 99.00

PCRoute - auto-router 99.00

Supercad - schematic pgm. 99.00

**DEMO PKG. - 10.00**

Call or write for more information

PCBoards


2110 14th Ave. South, Birmingham, AL 35205  
(205) 933-1122

### PORTABLE DATA LOGGERS.

A line of full-featured, rugged, data-gathering products that tie directly to thermocouples or voltage- or current-output devices has been introduced by MetraByte. The DDL-400 Series data loggers, and the variety of available hardware and software accessories, allow the user to configure a system to meet specific application requirements in the lab, factory, or field. The IBM-compatible, programmable, menu-driven data loggers offer 16 analog input channels, four digital inputs, and 16 alarm outputs. A sealed-membrane keyboard on the front panel controls functions such as data-logging interval, Hi/Lo alarm limits, channel select/skip, and time/date settings. The LCD readout shows channel data, alarm limits and status, time, and date.

Each data logger requires a TCV-16 I/O panel,

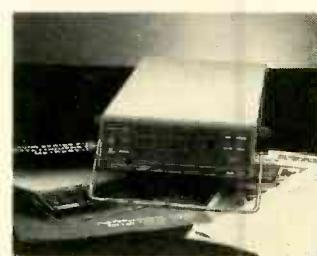a slide-in module that has 16 single-ended inputs for thermocouple, voltage, or current signals as well as 16 logic-level alarm outputs and four digital input channels for contact closures or logic levels. Each channel is independently configured by a 10-position range switch. Optional Applications Software allows remote control of one or more data loggers.




CIRCLE 321 ON FREE INFORMATION CARD

Every alarm in the system is independently and continuously checked at full speed at least every four seconds. Limit values are stored in non-volatile memory.

*continued on page 28*

# RAINBOW KITS

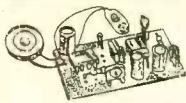

## RADAR SIGNAL DETECTOR

If you think that a sensitive radar detector is a complicated piece of equipment, take a look at this new kit. This simple, yet effective, detector circuit can be built in less than an hour and can be tuned to respond to signals between 50MHz to 500GHz. It's a fun kit to build and play with. A cigarette lighter plug is included. Size 1" x 3/4" operates on 9 to 15v DC.

KIT RSD-1 \$12.95

## STROBE LIGHT


If you need an attention getter, or warning light, you need the strobe light kit. Use it for emergency light for autos, for model planes or radio towers. Even use it on your bicycle. Operates on 6 or 12v DC and has a variable strobe rate.

KIT ST-1 \$8.95

## DIGITAL THERMOMETER

Have you ever wanted to tell temperature changes fast & accurately? The DT-1 kit will turn your digital volt meter into an accurate digital thermometer with .1 degree resolution. It gives you a 250 degree window with a range from -40F to 300F degrees. It has a remote sensor .25" sq. that can be mounted many feet from the meter if need be.

KIT DT-1 \$8.95

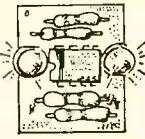

## BLINKIE LIGHTS

Want to attract attention? These kits are perfect for decorating name tags, lighting up your hat, or flashing lights for your model trains. Some people use them to simulate a burglar alarm for autos. Put it in a box, set it on your dash and it looks like the real thing. Each kit contains two LEDs that alternates flashing. Operates on a 9v battery. Size .5" x .5".

KIT RB-2 \$3.45

## CAPACITANCE METER

This easy to build kit will turn your digital volt meter into a CAPACITOR METER. Turn that junk box of unmarked capacitors into a fortune. Measures capacitors from (2pF to 2.2uF. Operates on a 9v battery. Size 1.75" x 1.75".

KIT CA-2 \$12.95

## WIRELESS FM MIKE


Small but mighty .8" x 1" PCB, will really stomp out a signal well over 400 yds. This is a buffered wireless mike that operates on 80 to 120 MHz FM. Comes complete with a microphone, and 9v battery connector. Operates on 6 to 12v DC. KIT WM-1 \$12.95



## SUPER SNOOPER-BIG EAR

Use this BIG EAR amplifier to listen through walls, hear conversations across the room. Beef up the sensitivity with a parabolic reflector and hear blocks away. Due to the size, the BIG EAR can be hidden about anywhere. Use the earphones from a pocket transistor radio to listen. Makes an ultra-sensitive intercom. Can also be used as a general purpose 1.5W amp. We supply a mini-microphone in the kit. You can also use any 8 to 45 ohm speaker. Operates on 6 to 12v DC. Size 1" x 1.75".


KIT TEL-B1 \$10.95

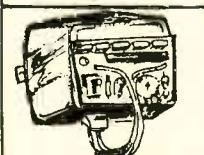

## AC LINE MONITOR

This is something every computer user, photographer, or anyone that must maintain a safe usable AC line voltage should have handy. Monitor the voltage of your motor home's 110v AC generator inside the motor home. Every technician's bench needs this item. The AC line monitor will indicate, with multi-color LEDs, what voltage is being distributed to your equipment at that particular outlet.

KIT LM-110 \$10.95

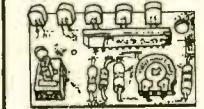

## 12V BATTERY MONITOR

Have you ever been in your car, boat, or camper — you try to start your motor but the battery is dead? The BATTERY MONITOR kit uses the cigarette lighter plug outlet to monitor the true battery voltage. Multi-color LEDs indicate the voltage in 1v steps from 11v to 15v, green means great, yellow is good, and red — call the tow truck or get out the oars. Size 1.2" x 1.75".


KIT LM-12 \$5.95



## PHONE BUG

Small but mighty, so small it fits anywhere. Telephone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at great distances away. Variable tunes 70MHz to 130MHz. It can also be used to make any phone a speaker phone. Size .55" x 1".

KIT TEL-B1 \$10.95

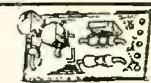

## PHONE RECORDING SWITCH


This telephone line powered switch is small enough to install anywhere only .9" x .6". Every time someone picks up the phone, the tape recorder will record both sides of the conversation automatically. Use it in your office to record all phone conversations so you don't lose that important address you wrote on the back of an envelope.

KIT TEL-SW 1 \$10.95

## BUSY PHONE LIGHT

Add this little kit to any or all of your phones. When any extensions are in use the LED will light. Uses a 9v battery. P.C. Board 1" x 1/2". Complete with etched & drilled PCB, all parts and schematics.

KIT TEL-LIT-1 \$9.95

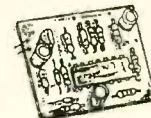

## VOICE ACTIVATED SWITCH

This vox can be used to operate a tape recorder, ham radio, CB radio. Use it to turn on an alarm. The output can operate a load up to 100ma. It will operate a relay, lights, motor, or LEDs. What could you do with a sound activated switch? Size 1.5" x 1.25".

KIT VOX-1 \$6.95

## LIE DETECTOR

This kit can be great fun at parties. Lie and an audible tone will change, the more you lie the more the tone changes. When you lie your palms & forehead sweat. This kit allows you to measure these changes. Only a very slight amount of change will cause the tone to increase in frequency. Operates on 6 to 12v DC. Size 1.2" x 1.75".

KIT LD-1 \$9.95

# THE STRIPPER

XXXXX RATED



## VIDEO STABILIZER

If you rent movies you need THE STRIPPER

When watching rental movies you will notice annoying picture flashing from dark to light, color shifts, unwanted lines, & picture jitters. This is caused by the copy protection installed in the video tape by the manufacturer. THE STRIPPER completely eliminates all copy protection and gives you crystal clear copies.

## WE HAVE THE ENHANCING SWITCH

SOME NEW COPYGUARD SCHEMES REQUIRE ADDITIONAL CIRCUITRY TO CLEAR THE PICTURE COMPLETELY OF UNWANTED LINES AND PICTURE INTERRUPTION. THIS IS THE PURPOSE OF THE ENHANCING SWITCH. NO OTHER UNIT ON THE MARKET HAS THIS FEATURE!

THE STRIPPER'S intended use is to stabilize and restore crystal clear pictures to prerecorded video tapes for your personal viewing enjoyment. Electronic Rainbow doesn't recommend using The Stripper to duplicate perfect copies from rental tapes in your own home for your personal use.

COMPLETELY  
BUILT \$49.95

WARNING: Use of this device to duplicate copyright material may be against certain federal & state laws.



THIS MANUAL  
CONTAINS ALL  
SCHEMATICS, PARTS &  
P.C. BOARD LAYOUTS  
FOR ALL OF THE  
RAINBOW KITS. USE  
YOUR OWN PARTS TO  
CONSTRUCT ANY OF  
OUR KITS.

KIT BOOK \$14.95

\$5.00 OFF IF YOU  
BUY ANY KIT.

## TV NOTCH FILTERS

OUR TV FILTERS ELIMINATE UNWANTED TV CHANNELS OR ANY INTERFERENCE THAT ALTERS BOTH THE SOUND AND VIDEO.

Channels available 2 thru 6 & 14 thru 22  
Specify a specific channel when ordering

CHOICE

1495 EACH

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

Please add sufficient postage

We will accept telephone orders for Visa & Mastercard



To Order Call  
317-291-7262



ELECTRONIC RAINBOW

6254 LaPas Trail • Indianapolis, IN 46268

**TOP SECRET**  
MANUALS

**CONSUMER ELECTRONICS**  
2011 CRESCENT DR., P.O. DRAWER 537  
ALAMOGORDO, NM 88310  
**1-505-434-0234**

Add \$3 ship. (USA, Canada). All items are in stock. COD (UPS cash only), VISA and MasterCard OK. 100+ More Computer and Electronic Offers! **FREE** Tech. Catalog with order, else \$2 in business since 1971. As seen on TV.

#### ROBOFONE AUTODIALER

Powerful, versatile menu-driven program allows you to dial any number (up to 10,000) or mix of local and long distance phone numbers in any order, over any length of time, whether you are at home or away (choice) and log the times, commands and results to monitor, printer and/or disk. Quick-dial directory of up to 600 numbers! **BUSY** regial options. Direct modem command and control! All Result Codes, including VOICE and RINGING. Optional shell to terminal program upon CONNECT. Exit to Menu or DOS (for batching). Ideal as a "Wargames" dialer, phone call logger and telemarketing dialer. **Disk\* + Manual \$29.** With **LABELS** and **LETTERS** programs \$49. Optional **TeMark**. Interface **\$29.50**.

#### HARD DRIVE MANUAL

Relates to all Hard Drive and Controller implementations (emphasis on PC/XT/AT/386). How to select interface, initialize, set up, use them. How to maintain, troubleshoot, repair them. How to protect them from mistakes, sabotage, prying eyes, sticky fingers. How to recover damaged and lost files. Includes software reviews. Much info found nowhere else! **\$29. SAVE \$5!**

#### DISK SERVICE MANUAL

Maintain, troubleshoot, repair, adjust, align Floppy Drives without special equipment or software. 5.25" / 3.5" / 8" PC/XT/AT/386, Apple, Commodore, Kaypro, Tandy, Epson, Atari, TI, HP, DEC, etc. systems. **\$29. SAVE \$5!**

#### DISK DRIVE TUTORIAL

Theory, practical facts on Floppy Drives, FDCs, Formating, Software Protection for the systems described above. Invaluable advice and tips on how to best select, interface and use Drives and Disks. **\$19.**

#### COMPUTER PHREAKING

TROJAN HORSES, VIRUSES, WORMS, etc., and Counter Measures - includes Disk\* with 250K+ of phreaking text files and disk-protection programs, and the great **FLUSHOT**! (Editor's Choice, PC MAGAZINE). Dozens of Computer Crime and Abuse Methods, and Counter Measures. How systems are penetrated. BBS Advice, Password Defeats, 200 Phreak-Term Glossary; much more! **2 Manuals + 2 Disks \$29.**

#### BRAIN VIRUS ANTIDOTE

The PAKISTANI BRAIN VIRUS plagued dozens of universities and businesses. The mildly destructive original version is hacked into highly virulent strains! BRAIN VIRUS ANTIDOTE consists of the antidote, source code and write-up. **Disk\* (NOT infected) \$19.**

#### BEYOND VAN ECK PHREAKING

Eavesdropping on VDT video signals using an ordinary TV! Ranges up to 1 KI Planks, counter-measures. Includes legal Van Eck uses. Now includes original VAN ECK DESIGN! \$29.

#### ATMs

ATM Crimes, Abuses, Security, Vulnerabilities 100+ methods described - from Reg. E to ciphers, Case Histories, Law, Countermeasures, detailed Security Checklist, International Photo! Recently, a crook stole \$237,000 from one bank's ATMs (still unsolved)! **2 Manuals \$39.**

#### ABSOLUTE SECURITY

Dozens of simple, versatile, secure Computer Security methods, tips. Plus our Invulnerable Cipher Program (COM and its BAS Source). Plus \$1,000 CIPHER CONTEST rules with CipherText Manual + Disk\* \$29.

#### CRYPTANALYSIS TECH.

5 Powerful Menu-Driven Crypto Programs in COM and its BAS Source to Analyze, Decrypt "Secure" Ciphertexts. Examples. Recommended in the prestigious COMPUTERS & SECURITY. Manual + Disk\* \$29.

#### STOCKPRO

Unique, Powerful, Shred, Unconventional Common Stock Investment Strategy. Created for NMSU. Basis of expansive consulting system. Manual + Disk\* \$29.

#### PRINTER/PLOTTER MANUAL

Types, Descriptions, Specs, and 100+ Interfaces (Parallel, Serial). Detailed Plans of X-Switchers, Buffers, and Serial-To-Parallel and Parallel-To-Serial Devices. Many service, repair, buy, use tips. **\$19.**

#### SUPER RE-INKING METHOD

Re-Ink Cloth Ribbons for about 50 cents. and 10 minutes each. Plans for El Cheapo Motor-Driven Re-inker. Commonly used Ink (5 colors) and carrier described. **\$14.**

#### SOFTWARE PROTECTION

Unique system that highly discourages costly software piracy while not interfering with legit archival copies. No known method of defeat. No special equipment required. Easy, automatic to install. Can be used with any other micro system. **Disk\* + Manual \$59. (was \$95).**

#### SPECIAL PROJECTS


We Design, Build, Repair, Modify, Maintain and Consult on any Device, System or Project - Computerized, Electronic, Electrical, Mechanical, Optical - many Invention prototypes. Confidentiality guaranteed. Describe and include \$25 non-refundable fee. We then provide you cost, time estimates.

#### TECH. RESEARCH SERVICES

Unique 42K electronic, computer design articles in database accessible by title, Subject, Digital, I/P, C, analog, video, microprogram software. Provide us keys, we return listing. \$25 non-refundable search fee (1-20 words/phrases). Save you R&D \$55!

\*Software supports PC/MS-DOS, MS-DOS, PS/2; Mono, Hercules, CGA, EGA, VGA, 5.25", 3.5", hard (specify your floppy drive size).

## REMOVE IC'S FASTER

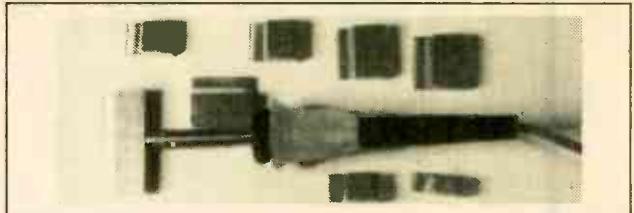

with this simple invention than any other method, including \$6,000 vacuum desoldering stations. Salvages hundreds of good IC's per hour from junk boards, and also speeds up repairs. Won't damage IC's or circuit board. Removes 6 thru 40 pin IC's. This is a money making labor saving tool. Order now. We pay shipping on prepaid orders.

Complete set of 8 desoldering bits

**\$89.95**

## LEARN THE SECRETS OF HOW TO FIX ELECTRONIC EQUIPMENT FASTER ON OUR

## REPAIR TECHNIQUES ON VIDEOTAPE

Learn our techniques and make more money repairing electronic equipment. These tapes are packed with much practical information that will save enough of your valuable time to quickly pay for the tapes.

Learn from an expert what fails, why it fails, how to find it faster, and how to fix it faster.

Much of this information is available nowhere else.

These tapes start at the beginning for beginners, but cover each subject so thoroughly, that even old pros will learn valuable new techniques and skills.

Send payment with order and we will pay shipping. Order all 14 tapes and send payment with order and get a 10% discount. (Send \$503.37 for all 14 tapes.) Order now.

How to use a Voltmeter (1 hr. 51 min.) \$39.95

How to use a logic probe and logic pulser \$39.95

All about resistors and their failure modes (1 hr.) \$39.95

All about capacitors and their failure modes (1 hr. 28 min.) \$39.95

All about inductors and their failure modes, Part 1. Includes inductors, transformers, flybacks, pinball coils, solenoids. \$39.95

All about inductors and their failure modes, Part 2. Includes magnetic clutches, relays of all types, other devices. (58 min.) \$39.95

All about diodes and their failure modes. Includes rectifiers, SCR's, Zeners, triacs, LED's (55 min.) \$39.95

All about transistor failure modes (\$6 min.) \$39.95

How to solder like a pro — with lots of time saving circuit board repair techniques, including some of the fastest ways to change IC's you ever saw (1 hr. 30 min.) \$39.95

All about electrical contacts, connectors, connections their failure modes, common and uncommon problems, symptoms, good cures. \$39.95

How to use the oscilloscope (to track down digital failures) \$39.95

How to read schematics and use them for troubleshooting, Part 1. Covers monitors, how to find monitor problems with wiring diagrams, gives symptoms, where to look, covers both raster scan and X-Y monitors (56 min.) \$39.95

How to troubleshoot digital integrated circuits — includes microprocessors, what goes wrong & how to find it, how to use the best literature on IC's and where to get it (1 hr. 45 min.) \$39.95

How to select and hire the best electronic technician. It takes one to know one, and believe us they are not all created equally excellent. This tape will save management and you a lot of grief if it keeps them from hiring a dud. \$39.95

## VIDEO REPAIR SCHOOL

P.O. BOX 813-RE  
SELMER, TN 38375

**(601) 287-1594**

CIRCLE 351 ON FREE INFORMATION CARD

# PRELCO

605 Chestnut St • Union, N.J. 07083  
TEL: 201-851-8600 FAX: 201-686-4656



2N5308	0.29	AN6291	3.50	CA3217E	3.45	LA5512	1.25	MM5368N	3.00	TC9145P	2.20	UPC1382C	1.70	221-192	1.25
2N5635	6.90	AN6306	3.95	CA3218E	1.75	LA5521D	1.25	MM5387	1.90	TCA830	1.50	UPC1391	1.40	221-193	2.10
2N5636	6.50	AN6307	3.95	CA3224E	2.45	LA6358	1.10	MM5402N	0.45	TCA830SM	1.50	UPC1470	1.10	221-213	0.90
2N6045	0.79	AN6326	2.95	CA3234E	5.95	LA7031	1.90	MM5458N	1.50	TCA4500	1.75	UPC1473	1.10	221-261	6.10
2N6497	0.69	AN6327	3.10	CA3236E	5.95	LA7032	5.20	MC7317BN	1.50	TOPC4621	2.75	UPC1613	1.35	221-267	9.95
2N6558	0.49	AN6328	3.25	CA3237E	1.75	LA7090	2.00	MN1280R	2.00	TD62105P	1.80	UPC1614	1.60	221-285-02	5.50
2SA843	1.95	AN6337	2.65	CA3238E	1.75	LA7210	2.55	MN6183A	3.95	TDA1057	1.65	UPC1620C	2.75	221-285-03	5.50
2SB171	0.35	AN6341	2.95	CA7607E	1.65	LA7607	1.50	MN6188	3.75	TDA1083	2.30	UPD261	2.95	221-291	1.95
2SB173	0.35	AN6342	2.10	CA7611E	1.65	LA7520	2.75	MN6178	2.40	TDA1170	2.40	UPD282	2.95	221-303	3.40
2SB178	0.40	AN6343	3.90	CD22402E	8.95	LA7630	2.75	MN15823	3.75	TDA1190Z	2.10	UPD940C	3.95	221-304	1.90
2SB179	0.45	AN6346	3.85	CX770	3.75	LA7620	3.75	MP1908	3.40	TDA1220A	2.45	UPD948	6.65	221-343	0.75
2SB186	0.50	AN6350	6.25	CX20017	6.10	LA7900	2.25	MPC574J	1.55	TDA1578A	0.95	UPD1200	8.95	221-347	2.80
2SB187	0.55	AN6359	3.90	CX23035	3.95	LA7830	2.05	MPSA13	0.35	TDA2003V	1.25	UPD1203C	2.00	221-418	6.95
2SB189	0.60	AN6360	3.95	CXA1019	4.90	LA7910	1.10	MPSU10	0.55	TDA2008V	1.65	UPD1704C	2.25	221-419	1.80
2SB459	0.40	AN6361	3.95	DN6838	1.75	LB1403	1.10	MRF421C	13.95	TDA2030H	1.55	UPD1709	6.50	221-493	4.40
2SB512	0.40	AN6362	4.50	DTA114	0.56	LB1405	1.35	MRF448C	6.90	TDA2577	2.85	UPD1937C	2.10	221-516	6.75
2SB546	0.65	AN6368	5.25	DTA124ES	0.60	LB1409	2.10	MRF841	12.75	TDA2820M	1.50	UPD1943G	2.50	221-528	2.60
2SB582	0.55	AN6387	5.10	DTC114ES	0.45	LC4081B	0.45	MRF644	7.95	TDA2826M	1.55	UPD1986C	1.65	221-545	2.75
2SB710	0.40	AN7025	1.60	DTC114F	0.45	LM317T	0.75	MRF901	1.10	TDA3190	2.00	UPD1987C	1.65	442-58	2.35
2SB834	0.50	AN7110	1.50	DTC124ES	0.56	LM324N	0.95	MRF911	1.25	TDA3564N	6.10	UPD4027	0.45	442-62	1.05
2SC535	0.25	AN7111	1.50	DTC144	0.56	LM337MT	0.60	MSL2318	2.75	TDA3570	4.20	UPD4066B	0.35	442-74	1.98
2SC708	0.85	AN7115	1.50	DTC144ES	0.56	LM340T-5	0.30	MSL9372	3.75	TDA3653CQ	3.85	UPD4081	0.45	6603-1	1.15
2SC800	0.20	AN7142	1.75	GH3F	1.95	LM340T-6	0.30	MSM5525	2.75	TDA4505A	8.75	UPD4556B	0.50	5606-1	1.50
2SC929	0.30	AN7143	2.75	HA1138	2.99	LM340T-8	0.30	MUR3005	1.72	TL783C	1.35	UPD6104C	2.10	56023-1	1.10
2SC930	0.30	AN7145	2.95	HA1158	1.39	LM340T-12	0.30	MUR3015	1.72	TLP560G	1.50	UPD6111	8.45	56024-1	1.50
2SC945	0.15	AN7148	1.80	HA1197	1.80	LM340T-18	0.30	PH302	0.90	TMC1073	3.40	UPD7538C	4.95	56025	1.05
2SC1000	0.25	AN7205	1.50	HA1338	5.90	LM350T	1.75	RC555N	0.15	TMS1025	4.95	UPD7610B	5.45	57B316-10	1.95
2SC1023	0.35	AN7213	0.85	HA1389	2.70	LM377N	2.80	SAB3096	3.75	TMS1045	5.60	X0137	3.95	61042-4	0.25
2SC1096	0.55	AN7222	1.50	HA1389R	2.70	LM380N	1.25	SAB3037	2.95	TMS1071	4.50	121-868	0.45	610419-2	0.25
2SC1359	0.20	AN7224	1.75	HA11227	1.50	LM384N	1.55	SAT1039P	1.60	TMS1751	2.45	121-1014	0.80	610442-1	0.80
2SC1449	0.55	AN7310	1.10	HA11423	2.25	LM556CN	0.55	SN29764	0.75	TMS1944	2.90	121-1028	0.70	610456-2	0.25
2SC1674	0.30	AN7320	1.25	HA11714	5.50	LM1310N	1.35	STA401A	2.50	TMS1952	2.90	121-1035	0.70	610457-2	0.60
2SC1815	0.15	AN7410	1.50	HA11747	7.50	LM1818N	2.50	STK011	4.45	TMS3450	2.90	121-1037	0.75	610471-1	0.70
2SC1923	0.20	AN7420	1.30	HA12003	1.25	LM1822N	5.95	STK433	5.20	TMS3451	2.45	14DN158	5.80	610551-1	0.75
2SC1941	0.65	AN7812F	0.85	HA12413	1.50	LM1823N	5.95	STK4192II	11.50	TMS3452	2.45	14DN197	6.90	612024-1	2.20
2SC1959	0.15	AN7815F	0.85	HA17458	0.90	LM1868N	2.40	STK5372	5.30	TMS3495	2.45	14DN209	8.75	612042-2	2.75
2SC1975	1.95	AN7818	0.65	HD36290	5.70	LM1877N	2.65	STK5471	5.10	TRC2073D	1.50	14DN233	5.10	612044-1	1.50
2SC2058	0.25	AN78M05	0.45	HD38941	3.75	LM1880J	2.95	STK5476	5.10	U1416B	3.10	15-35059	1.25	612069-1	2.35
2SC2120	0.20	AN78M05F	0.65	HD614042	7.90	LM1895N	2.75	STR380	4.75	U1417B	2.30	15-37701	2.95	612070-1	1.80
2SC2230	0.75	AY-385-00	2.45	IR2403	1.80	LM2877P	1.80	STR381A	4.75	U1420B	2.75	15-37702	1.85	612072-1	1.95
2SC2271	0.75	AY-385-01	2.45	IR2410	1.50	LM2901N	1.75	STR451	6.25	U1767	1.75	15-37704	1.75	612076-4	2.85
2SC2482	0.75	BA235	1.80	IR2E01	1.50	LM8361	3.10	STR2013	5.80	ULN2110A	1.45	15-39207	4.95	612076-7	2.85
2SC3038	1.25	BA308	1.50	IR2E02	1.50	LM8560	3.10	STR3115	4.75	ULN2212	2.45	15-39208	2.25	612094	2.15
2SC3298A	1.10	BA328	1.00	IRC5	0.95	LU116278	3.00	STR3125	4.75	ULN2216	1.00	15-39209	2.50	612105	5.10
2SD777	0.75	BA521	1.25	KA33V	1.55	M5218P	0.90	STR3135	4.75	ULN2224	1.95	15-41627	2.20	612120-1	3.80
2SD91	2.05	BA526	1.50	KA1222	1.50	M5278L56	0.50	STR30123	4.75	ULN2228	1.50	15-41764	4.10	612298-1	3.10
2SD187	0.50	BA532	1.25	KA2101	0.55	M47020	2.45	STR30130	4.75	ULN2229	1.85	15-43098	4.40	612305-1	1.30
2SD200	2.85	BA612	0.90	KA2102A	1.80	M51307BSP	8.25	TA7117P	2.70	ULN2281A	2.10	15-43703	1.35	612331-2	5.50
2SD261	1.50	BA718	0.65	KA2130A	1.45	M54516P	1.80	TA7137P	1.10	ULN2280B	1.50	15-45300	1.30	612337-3	4.70
2SD400	1.50	BA728	1.25	KA2206	1.75	M58618P	2.95	TA7142P	2.45	ULN3810A	1.85	221-42	1.70	612337-5	4.70
2SD880	0.60	BA1310	1.75	KA2261	1.45	M58626P	2.65	TA7157P	1.80	ULN3859	1.45	221-43	2.35	612338-3	5.10
2SD1159	0.75	BA1320	1.45	KA2263	1.85	M58659P	2.45	TA7159P	2.10	UPA53C	1.60	221-45-01	2.60	612347-2	1.95
2SD1227M	1.10	BA3308	1.25	KA2281	1.20	MAB8461P	4.10	TA7223P	1.45	UPA80C	1.50	221-46	1.75	612351-1	1.10
2SD1265	0.85	BA3812L	1.25	KA2912	2.50	MB3106	1.35	TA7230P	1.75	UPC27C	2.25	221-69	1.95	612405-1	2.25
2SD1266	0.90	BA4210	1.75	KA3213	0.85	M88726	2.45	TA7267P	2.25	UPC358C	1.85	221-77	3.20	612442-1	4.95
2SD1384	0.70	BA4232AL	1.95	KIA7137	1.10	M88803	8.75	TA7325P	1.25	UPC393C	1.80	221-78	2.85	612445-1	2.65
2SD1397	1.85	BA4234L	1.95	KIA7640	2.75	MBR3035	2.15	TA7330P	2.55	UPC554C	1.80	221-79-01	1.75	612479-3	0.75
2SD1427	1.75	BA4402	1.00	LS630	1.55	MCR3045	2.15	TA7331P	1.60	UPC571H	1.20	221-87-01	2.15	612480-1	1.55
AN217	1.80	BA4403	1.25	LA1180	1.80	MC1309P	1.25	TA7335P	0.90	UPC574	1.80	221-92	0.95	DM32	1.10
AN236	2.65	BA4558	0.90	LA1185	1.50	MC1351P	2.95	TA7342P	1.25	UPC675C	1.25	221-97	1.75	DM50	1.20
AN240P	1.40	BA5101	1.85	LA1201	0.95	MC1357P	1.45	TA7439P	1.85	UPC585	4.45	221-97-01	1.75	DM82	0.75
AN262	1.75	BA5102	1.85	LA1210	1.85	MC1394P	1.40	TA7539P	1.40	UPC587C	1.25	221-97-02	1.75	DM106	0.18
AN277	2.45	BA5115	2.75	LA1222	1.65	MC3367P	1.75	TA7558P	1.26	UPC592H	4.10	221-102-01	2.65	DM112	0.75
AN278	1.50	BA6104	2.95	LA1231	1.55	MC7805CT	0.30	TA778P	1.50	UPC1018C	2.75	221-104	1.95	DM163	0.75
AN302	3.50	BA6209	1.90	LA1245	1.75	MC7813CT	0.30	TA7807P	1.65	UPC1026	1.25	221-105	2.10	DS102	0.19
AN305	3.50	BA6238A	2.50	LA1260	1.60	MC7815CG	0.25	TA7811P	1.65	UPC1032H	1.75	221-106	2.20	IC-13	2.35
AN318	3.75	BA6993	1.80	LA1365	0.85	MC7818CG	0.25	TA7813P	2.30	UPC1197C	1.45	221-111-01	0.75	IC-27	2.10
AN360	1.00	BFW92A	1.25	LA3115	1.35	MC78M05CT	0.20	TA7814P	2.55	UPC1204C	1.55	221-140	3.75	IC-32	2.40
AN362	1.85	BN5111	3.75	LA3155	1.25	MC78M06CT	0.20	TA7828P	1.75	UPC1213C	2.50	221-157-02	1		

# NEW AFFORDABLE - PRECISION TEST EQUIPMENT

E.T. Tech., Inc. - Division of Empire Telecommunication Inc.

## SIGNAL SYNTHESIZERS



**SG-100**  
**\$685**


.100000 Hz. -  
99.9999 KHz.

**SG-100**

Six Digit resolution, .005% accuracy low distortion sine wave, output and adjustable to 20 Vp-p with 50 ohm output impedance and TTL. GPIB Option.

**SG-102 - \$955** - Dual signal independent output or phase locked to one of 16 phases.

## SYNTHESIZER FUNCTION GENERATOR

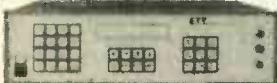

**SFG-33**  
**\$1275**

.100000 Hz. -  
32.9999 MHz.

**SFG-33**

Waveforms are provided with six digit resolution, .005% crystal accuracy. Waveforms are sine, triangle, square, and rising and falling ramps, with dc offset and 20 Vp-p 50 ohm output over 80 dB range and TTL.

**SFG-330 - \$1789** - Keyboard and GPIB entry dBv and recall features. Options: 66 MHz. and dual Quad output.

## SYNTHESIZER PULSE GENERATOR



**PGS-33**  
**\$1355**

.100000 Hz. -  
33 MHz.

**PGS-33**

Provides digital pulse train synthesis with six digit resolution. Control of single and dual pulse delay and duration. Multi-modes including burst pulse train and variable duty cycle. Output to 20 Vp-p with 50 ohm impedance. D.C. offset with TTL.

## DUAL SIGNAL & PHASE SYNTHESIS

**SG-112** **\$1350** .100000 Hz. - 99.9999 KHz.

Dual signal low distortion digital synthesis. Independent or locked signals. Locked signal phase resolution to .01 degrees.

**PM-100** **\$855**

Measures test signal phase to .01 degrees as compared to reference from 10 Hz. to 2 MHz.

## SIGNAL DIGITIZER & SCOPE MEMORY WAVEFORM GENERATOR

**SD-200** **\$795**

Signal digitizer captures signal transient for scope display. Adjustable sampling with 200 nsec. maximum, stores 8 Kilo-byte with 5% amplitude resolution. Pretrigger display enables analog scope to operate as a storage scope.

**SD-240** **\$1395**

Waveform Generator captures signals and allows for signal data entry with a light pen.

To order or for more information call or write:

125 South Van Brunt Street, Englewood, N.J. 07631  
Phone 201 569-3339 Fax 201 569-5838

**E.T. Tech., Inc.**

## EPROM PROGRAMMERS

### Stand-Alone Gang Programmer



**\$750.00**


- 8 ZIF Sockets for Fast Gang Programming and Easy Soldering
- 20 Key Tactile Keypad (not membrane)
- 20 x 4 Line LCD Display
- Completely stand-alone or PC driven
- Programs E(E)PROMs
- 1 Megabit of DRAM
- User upgradable to 32 Megabit
- .3/.6" ZIF socket, RS-232, Parallel In and Out
- 32K internal Flash EEPROM for easy firmware upgrades
- Quick Pulse Algorithm (27256 in 5 sec, 1 Megabit in 17 sec.)
- 2 year warranty
- Made in U.S.A.
- Technical support by phone
- Complete manual and schematic
- Single Socket Programmer also available. \$550.00
- Split and Shuttle 16 & 32 bit
- 100 User Definable Macros, 10 User Definable Configurations
- Intelligent Identifier
- Binary, Intel Hex, and Motorola S

### Internal Programmer for PC

**\$139.95**

New Intelligent Averaging Algorithm. Programs 64A in 10 sec., 256 in 1 min., 1 Meg (27010, 011) in 2 min. 45 sec., 2 Meg (27C2001) in 5 min. Internal card with external 40 pin ZIF.

2 ft. Cable 40 pin ZIF

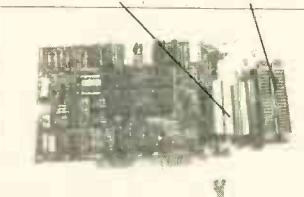

- Reads, verifies, and programs 2716, 32, 32A, 64, 64A, 128, 128A, 256, 512, 513, 010, 011, 301, 27C2001, MCM 88764, 2532
- Automatically sets programming voltage
- Load and save buffer to disk
- Binary, Intel Hex, and Motorola S formats
- Upgradable to 32 Meg EEPROMs
- No personality modules required
- 1 year warranty • 10 day money back guarantee
- Adapters available for 8748, 49, 51, 751, 52, 55, TMS 7742, 27210, 57C1024, and memory cards
- Made in U.S.A.

### NEEDHAM'S ELECTRONICS

4539 Orange Grove Ave. • Sacramento, CA 95841  
Mon. - Fri. 8am - 5pm PST

C.O.D.

Call for more information  
**(916) 924-8037**  
FAX (916) 972-9960

**NUDE! ♥ NUDE! ♥ NUDE!**

## “NAKED” WORKSTATION CASE & POWER SUPPLY

At the scandalously low price of  
**only \$59.95 for both!**

It's brand new...it just isn't wearing a plastic front panel, bezel, key switch or LEDs.

Featuring:

- 230 watt 110/120 power supply (AT style, back switch!)
- Eight (8) 1/2-height slots for drives (6 front, 2 back)
- Accepts eight (8)-slot mother board (full or baby)
- Extra 12-volt cooling fan
- Speaker for mother board
- Six (6) rail sets included

...With all this, it's worth twice the price!

*And more bargains...*

## SWITCHING POWER SUPPLY


Only \$9.95!

Fully enclosed with switch and D.I.N. power connector.


- 5v at 4.5 amps
- 12v at .3 amps
- 12v at 1.4 amps
- -12v at 1.2 amps

Electronic Parts Outlet • 2815 Fondren • Houston, TX. 77063  
(713) 784-0140 • FAX: (713) 784-9740

*Three locations in Texas....Come visit our retail stores!*

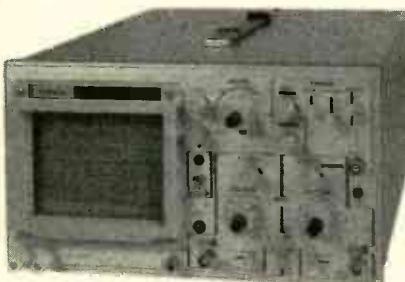**ELENCO****BK PRECISION****HITACHI****OSCILLOSCOPES****ELENCO****Model MO-1251****20MHz Dual Trace**

Component Tester

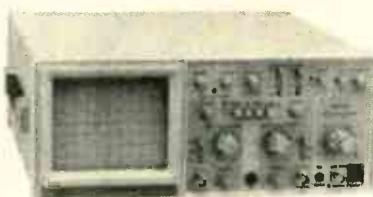**\$355**MO-1252 - 35-50MHz, Dual Trace,  
Delayed Trigger **\$475**P-1 Scope Probe - 65MHz, X1 X10 **\$18.95**  
P-2 Scope Probe - 100MHz, X1 X10 **\$22.95****B+K PRECISION****Model 2120**  
**20MHz Dual Trace****\$389**2125 - 20MHz, DT, Delayed Sweep, Component Tester **\$479**  
1541 - 40MHz, DT **\$650**  
2160 - 60MHz, DT, Delayed Sweep **\$899****HITACHI****Model V-212**  
**20MHz Dual Trace****\$399****Other Models**

V-522 - 50MHz, DT	<b>\$845</b>
V-523 - 50MHz, DT, Delayed Sweep	<b>\$930</b>
V-525 - 50MHz, DT	<b>\$975</b>
V-660 - 60Hz, DT	<b>\$1,050</b>
V-665 - 60MHz, DT, w/cursor	<b>\$1,290</b>
V-1060 - 100MHz, DT	<b>\$1,370</b>
V-1065 - 100MHz, DT, w/cursor	<b>\$1,650</b>
V-1085 - 100MHz, QT, w/cursor	<b>\$1,950</b>
V-1100A - 100MHz, QT	<b>\$2,200</b>
V-1150 - 150MHz, QT	<b>\$2,675</b>

**Digital Storage Scopes**

VC-6023 - 20MHz, 20MS/s	<b>\$1,695</b>
VC-6024 - 50MHz, 20MS/s	<b>\$1,950</b>
VC-6025 - 50MHz, 20MS/s	<b>\$2,195</b>
VC-6045 - 100MHz, 40MS/s	<b>\$2,885</b>
VC-6145 - 100MHz, 100MS/s	<b>\$4,595</b>

All scopes include probes, schematics, operators manual, and 3 year warranty on parts &amp; labor. Many accessories available for all scopes. Call or write for complete specifications on these and many other fine oscilloscopes.

**ELENCO TEST EQUIPMENT****Digital Triple Power Supply****XP-765****\$245**0-20V at 1A  
0-20V at 1A  
5V at 5AFully regulated, Short circuit protected with  
2 current limit controls, 3 separate supplies  
XP-660 with Analog Meters \$175**GF-8016 Function Generator  
with Freq. Counter****\$245**Sine, Square, Triangle  
Pulse, Ramp, .2 to 2MHz  
Freq Counter .1 - 10MHzGF-8015 without Freq. Meter **\$179****Multimeter with  
Capacitance and  
Transistor Tester****\$49 CM-1500A**Reads Volts, Ohms  
Current, Capacitors,  
Transistors and  
Diodes / with case**Digital Capacitance  
Meter****CM-1550****\$55**9 Ranges  
.1pf-20,000pf  
.5% basic accy  
Zero ctr w/ case**Quad Power Supply****\$55**2-20V @ 2A  
12V @ 1A  
5V @ 3A  
-5V @ .5A

Fully regulated and short circuit protected

**Wide Band Signal Generators****SG-9000 \$125**RF Freq 100K-450MHz  
AM Modulation of 1KHz  
Variable RF outputSG-9500 with Digital Display  
and 150MHz built-in Freq Ctr **\$245****Digital LCR Meter****LC-1801****\$120**Measures:  
Coils 1uH-200H  
Caps .1pf-200uf  
Res .01-20M**Digital Multimeter****M-1000****\$24.95**19 Ranges  
DCV-1000  
ACV-750  
DCA-10A  
Res-2M  $\Omega$   
Diode check**Triple Power Supply****XP-620**Assembled **\$60**Kit **\$40**2 to 15V @ 1A,  
-2 to -15V @ 1A  
(or 4 to 30V @ 1A)  
and 5V @ 3AContains all the desired features for doing experiments.  
Features short circuit protection, all supplies**Four-Function Frequency Counters****F-100 120MH****\$175****F-1000 1.2GH****\$255**Frequency, Period, Totalize,  
Self Check with High Stabilized Crystal Oven  
Oscillator, 3 digit LED display**10 Function  
Multimeter****CM-365****\$59.95**AC + DC Voltage & Amps  
Resistance to 2000 $\Omega$   
Diode, Logic, & Trans test  
Capacitance to 2000F  
Frequency Counter**AM/FM Radio Kit****AM/FM 08 \$24.95**Manual teaches AM & FM  
Theory is easy to  
understand language  
Many more kits available**OMNITRON**

ELECTRONICS

280 N. Midland Ave. BLDG. Z-2A  
Saddle Brook, NJ 07662

UPS Shipping: Continental USA 5% (MAX FRT \$20)

Money Order, Checks Accepted

School Purchase Orders - NET 30

Sorry no CODs

Add 5% for credit card

100 Page Catalog 53 (FREE with order)

**201-703-9800****201-703-9804 (FAX)**

# DIGITAL METERS

NEW



**DMM 2360 129.95**


**DMM + LCR Meter**

**Most Versatile DMM**

- Inductance:  $1\mu\text{H}$  -  $40\text{H}$
- Capacitance:  $1\text{pF}$  -  $40\text{pF}$
- Temperature:  $-40$  -  $302^\circ\text{F}$
- Frequency:  $1\text{Hz}$  -  $4\text{MHz}$
- Logic test:  $20\text{MHz}$
- Diode test
- Continuity beeper
- Volt, current, ohm
- 3999 count display
- Peak hold
- Auto power off

**DMM 135 \$79.95**

**MEASURE TEMPERATURE**

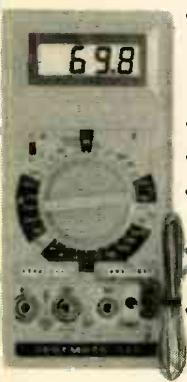

- $0^\circ$  -  $1400^\circ\text{F}$
- $-20^\circ$  -  $750^\circ\text{C}$
- $1^\circ$ ,  $1^\circ$  resolution
- $C: 1\text{pF}$  -  $20\mu\text{F}$
- $.1\Omega$  -  $2000\text{M}\Omega$
- Volt, current, continuity
- Diode, hFE tests
- Type K thermocouple included

**DMM 175A \$94.95**

**DMM MEASURES 20 MHz**




- Frequency  
1 Hz - 20 MHz
- Logic test  
20 MHz
- $C: 1\text{pF}$  -  $20\mu\text{F}$
- $.1\Omega$  -  $2000\text{M}\Omega$
- Volt, current, continuity
- LED, diode, hFE tests

**DMM 5365 \$79.95**



- Frequency  
1 Hz - 200 KHz
- Logic test 20 MHz
- $C: 1\text{pF}$  -  $20\mu\text{F}$
- $.1\Omega$  -  $2000\text{M}\Omega$
- Volt, current, continuity
- Diode, hFE tests
- Compact size

**LCR Meter**

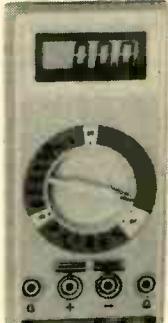

**\$119.95**

- Inductance:  $1\mu\text{H}$  -  $200\text{H}$
- Capacitance:  $1\text{pF}$  -  $200\mu\text{F}$
- Resistance:  $.01\Omega$  -  $20\text{M}\Omega$

**NAME BRAND QUALITY & RELIABILITY**  
**15 DAY MONEY BACK GUARANTEE**  
**ONE YEAR REPLACEMENT WARRANTY**  
**PROMPT DELIVERY & SERVICE**

**ALFA ELECTRONICS**  
**P.O. BOX 8089, PRINCETON, NJ 08543**  
**(800) 526-ALFA**  
**FAX: (609) 275-9536**

## TECHNICAL SCHOOL CLOSED!

Selling hundreds of HEATH Co. test and training equipment at up to 60% off their catalog prices. Use Heath catalog for description. Condition: new to slightly used, unfortunately many without manuals. All professionally wired & tested, or in original kit form as noted. First come, first served. Check or major credit cards. Sorry, no COD or open accounts. Add \$4.50 for mailing and handling.

### HEATH TEST EQUIPMENT

SK101	12 VDC-3A Power Supply	39.50
1271	Function Generator	69.50
1274	12.5V Sweep Pulse Generator	135.00
1277	Pulse Generator	147.00
2250	Digital Capacitance Meter	115.00
2320K	Handheld 3.5 Digit DMM Kit	49.50
2320W	Handheld 3.5 Digit DMM Wired	59.50
2420	Deluxe Universal Counter	255.00
2717A	Reg. H.V. Power Supply	165.00
2718	Triple Output DC Supply	129.50
2760	8-15V Battery Eliminator	135.00
3117	Decade Resistance Box	49.50
3120	Semiconductor Checker	69.50
4200A	Laser Trainer, Wired	225.00
4200K	Laser Trainer, Kit	195.00
4225	Dual Trace 25 MHz Oscilloscope	375.00
4226	Dual Trace 25 MHz Oscilloscope	385.00
5217	Battery Operated V.O.M.	39.50
5228	Vacuum Tube Voltmeter	89.50
HCA3000	Deluxe Coax Connector Adaptor Kit	89.50
PKW105	Deluxe 10:1 Combo Probe Kit	22.50

### HEATH EDUCATIONAL SYSTEMS

1000	Analogy/Digital Ckt Trainer	215.00
3300	Plug-in Bread Board Trainer	85.00
3400	Microprocessor Trainer	185.00
3400C	Portable Carry Case for M.T.	18.50
3567	Trainer Accessory Back Pack	95.00
3600	Analog Educational Trainer	88.50
3700	Digital Techniques Trainer	79.50
6201	Digital Experiment Module	77.50
ET100	Microcomputer Trainer	395.00
ZVM133	Terminal for Above	245.00
EWD100	Dual 5.5" Disk Drive	158.00

### MISCELLANEOUS

700	T-1 Portable Data Terminal	99.50
HP-15C	H-P Scientific Calculator/Manual	68.50
545A	Hewlett Packard Logic Probe	156.00
546A	Hewlett Packard Logic Pulser	210.00
547A	Hewlett Packard Current Tracer	378.00
548A	Hewlett Packard Logic Clip	192.00
5022A	All in One Carry Case	91.80
SP100	Serial-Parallel Converter, 110VAC	58.00

**HEATH LEARNING COURSES**  
Note: The small kits of component parts usually supplied with manuals are not available and prices reflect this omission. All courses are new and unused.

3140A	Concepts of Electronics Course	28.50
E4201	Fiber Optics Learning Course	56.50
EC1001	Passive Circuit Design Course	28.50
EE1004	Digital Circuit Design Course 2 vol.	59.50
ED6201	Lab Experiments Digital Techniques	19.50
EE101	Operational Amplifiers	29.50
EE102	Active Filters Course	19.50
EE103	I.C. Timers Course	22.50
EET104	Phase Locked Loops Course	29.50
EET105	Opto Electronics Course	36.50
EE110	Laser Technologies Course	59.50
EE3201A	Digital Techniques Course 2 vol.	49.50
EE8088	Adv'd Microprocessors Course, 2 vol	59.50

### EDUCATIONAL BOOKS

These books are brand new & represent a saving over publishers list prices. All hard bound except as noted.	
Lab Experiments Digital Tech (soft)	PUR
TTL Cook Book, Lancaster (soft), Sam	8.85
Assembly Language Program (soft), Intel	PUR
Electricity 1-7, Miley, Hayden	PUR
Decision Making Under Uncertainty, Hull, P-Hall	PUR
Fundamentals of Digital Electronics, P-Hall	PUR
Concise Intro to Engineering Economics	12.50
Industrial Ventilation, Edward Bros.	16.50
BOOKS BY MC GRAW HILL	
Guru Basic Electronics, 5th Ed.	10.50
Software Reliability, Musa Iamino	10.50
Intro to Uni Systems, Byers, 5th Ed. (soft)	9.50
Digital Electronics, Toltham 2nd Ed. (soft)	9.85
A Reference Guide to Practical Electronics (soft)	3.75
Digital Electronics thru Experiments	5.95
BOOKS BY MERRILL	
Experiments in Electronic Devices, 2nd Ed.	9.50
Electronic Devices, Floyd, 2nd Ed.	24.50
Digital Experiments-Trouble shoot, Cox (soft)	10.50
Experiments Electronic Circuits, Stanley, 2nd Ed.	11.50
Principles of Electronic Circuits, Floyd, 2nd Ed.	16.50
Principles of Electronic Circuits, Floyd, 3rd Ed.	23.50
Digital Fundamentals, Floyd, 3rd Ed.	14.50

**LCM Tech**

1755 Osgood St., North Andover, MA 01845  
 CALL: 508/682-6936 FAX: 508/689-9484  
 ORDER TOLL FREE: 800/343-1455 RE

## NEW PRODUCTS

*continued from page 22*

Expansion from stand-alone data logger to complete data-logging system is simple and easy. As many as five data loggers (for a total of 80 channels) can be networked together using the RS-422 ports at the rear of each unit. By wiring a network into a PC, up to 800 channels can be monitored.

No programming experience is required for set up. Once data is taken it can be sent to a printer, logged to a PC, or sent to one of the DB-2000 Series data buffers. Suggested applications are in temperature monitoring and control, field-environment experiments, benchtop data gathering, industrial-equipment monitoring, and remote data gathering.

Prices for the expansion data logger range from \$995.00 to \$1295.00; the DDL-SW applications soft-

ware and LTN-03 Labtech Notebook software cost \$495.00 and \$995.00, respectively; and the TCV-16 I/O module costs \$345.00. A complete line of accessories, including cables, adapters, data buffers, battery-backup systems, rack-mount kits, and driver relays, is also available. — **Metra Byte Corp.**, 440 Myles Standish Blvd., Taunton, MA 02780; Tel: 508-880-3000.

## PRESERVATION PLAN ON IT

*Write:*

**National Trust for Historic Preservation**  
 Department PA  
 1785 Massachusetts Ave., N.W.  
 Washington, D.C. 20036



SUPER

KELVIN

Electronics

INDUSTRIAL QUALITY  
AT DISCOUNT PRICES

## BREADBOARDS FOR LESS!

DURABLE - MADE OF THE HIGHEST QUALITY PLASTIC - DESIGNED TO WITHSTAND THOUSANDS OF INSERTION CYCLES

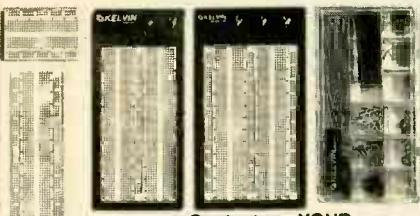


Fig.	Stock No.	Contact Points	YOUR COST
A	680093	500	\$ 4.25 ea
B	680097	840	\$ 5.95 ea
C	680098	1380	\$11.75 ea
D	680099	1580	\$15.75 ea

## WIRE JUMPER KIT

Use with Quick test sockets and bus strips.

Stock No.	Description	Points	YOUR COST
330290	350 Piece Set		\$ 7.75 ea

K.I.S. SYSTEMS  
KELVIN INTERFACE SYSTEMSNEW HARDWARE  
NEW SOFTWARE

USER FRIENDLY

ONLY  
**\$199**

EDUCATIONAL  
ACTIVITYGET 5 COMPLETE  
CLASSROOM SETUPS  
FOR UNDER \$1000ROBOTIC CONTROL SYSTEM  
AVAILABLE for IBM or APPLE

SYSTEM INCLUDES:

- Robotic Arm
- 2 Joysticks
- Power Supply
- Software
- K.I.S. Interface Module
- Demonstration Video

UPGRADABLE - ADDS THE ABILITY TO CONTROL  
AN ADDITIONAL 4 DC MOTORS UP TO 1 AMP EACH FOR  
PROBLEM SOLVING ACTIVITIES SUCH AS CONVEYORS,  
ELEVATORS, PLOTTERS & ROBOTIC CARS.

## TIMER - LM555

Stock No. 600021


**20 C** ea. (in 100+ Qty)



## L.E.D. RED (in 100+ Qty)

Stock No. 260020

**6 C** ea.

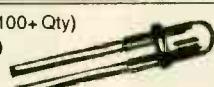

## Transistors (in 100+ Qty)

2N2222 **18 C** ea.PN2222 **.08 C** ea.

## Project BUZZER

6-9V DC, 80 dB

Stock No. 680089

**\$1.59 ea** **\$1.39/10+ ea.**



## 9V Battery Snap &amp; Holder

Snap .15 ea. .10 ea/100+




Holder .20 ea. .10 ea/100+

## PRO 400

The Professionals' Choice

with 20MHz FREQUENCY COUNTER excellent for  
COMPUTER, TV, VCR REPAIR and ENGINEERING.YOU CAN'T  
GO WRONG!

MONEY BACK GUARANTEE!

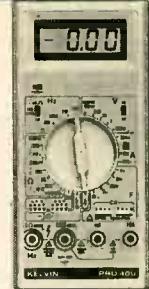

**\$69.95**

Stock No. 990092

30 DAY MONEY BACK GUARANTEE!

## KELVIN 100

Stock No. **\$23.95**AC/DC VOLTAGE  
DC CURRENT  
RESISTANCE  
DIODE TEST  
BATTERY TEST  
LOW BATTERY Warning  
ACCURACY +/- 0.5%

## KELVIN 150

Stock No. **\$29.95**AC/DC VOLTAGE  
DC CURRENT  
RESISTANCE  
DIODE & BATTERY TEST  
LOW BATTERY Warning  
ACCURACY +/- 0.5%  
CONTINUITY TEST  
TRANSISTOR CHECK

## KELVIN 200

Stock No. **\$39.95**AC/DC VOLTAGE  
AC/DC CURRENT  
RESISTANCE  
DIODE TEST  
LOW BATTERY Warning  
ACCURACY +/- 0.5%  
CONTINUITY TEST/BUZZER  
TRANSISTOR CHECKER  
CAPACITANCE CHECKERINDUSTRIAL  
QUALITYYOU CAN'T  
GO WRONG!30 DAY  
MONEY BACK  
GUARANTEE!

## CARRYING CASE

Stock No. 990093

\$4.95 ea


WE STOCK  
A COMPLETE LINE OF FUSES  
FAST ACTING - SLO-BLO TYPE - PIGTAIL

## 3AG FUSE BLOCK

Black laminated phenolic. 1/2" wide  
1 7/8" long. For 1/4" x 1 1/4" long fuses. Solder lug connections.

Stock No. YOUR COST


380030 \$.45 ea

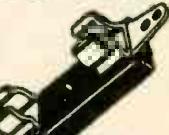FUSE MOUNTING  
BLOCK

Dual fuse block 2 1/4" x 1" long. Black bakelite base. For 1/4" x 1 1/4" fuses. Mounting centers 5/8" (15.8mm).

Stock No. YOUR COST

380010 \$.62 ea

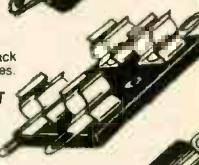

## FUSE POST

## TYPE HKP

Bayonet type. 2 3/16" L for 1/4" x 1 1/4" fuses. 15 Ampere 250V. Panel hole size 1/2" (12.7mm). Complete with mounting nut.

Stock No. YOUR COST

380001 \$.90 ea

KELVIN BRAND  
HI-SPEED, HI-QUALITY  
PRINTED CIRCUIT ETCHANT

Ready-to-use solution of ferric chloride printed circuit etchant in plastic container.

Stock No. SPECIAL BUY

440017 \$ 6.25 per gallon



## KELVIN BRAND

## HI-SPEED DRY

## PRINTED CIRCUIT ETCHANT

Clean, safe, economical, indefinite shelf life. 4 lbs. will make 2 gallons of recommended 20% etching solution.

Stock No. YOUR COST

440026 \$.8.40 ea \$ 7.00/4lb bag

## KELVIN BRAND COPPER CLAD BOARD

NEMA grade FR-2 1/16" thick, unpunched clad on one side.

Stock No. Size YOUR COST

440002 4 1/2" x 6" \$1.55 ea

440003 5" x 7" \$2.40 ea

440015 8 1/2" x 12 1/2" \$4.90 ea



## ETCH RESIST INK PENS

Black felt tip pen for making resist circuits directly on PC boards.

Dries instantly for neat, easy application.

Can be removed with PC Board Stripping Solution.

Stock No. Model Description YOUR COST

440115 22-220 Draws 1/32" wide \$1.48 ea

440116 22-222 Draws 1/64" wide \$1.85 ea



KELVIN

Electronics

7 Fairchild Ave. Plainview, NY 11803

Call: 1 (800) 645-9212

1 (516) 349-7620

FAX: 1 (516) 349-7830

FREE CATALOG  
CIRCLE RESPONSE  
CARD



## ELECTRONIC CLEARING HOUSE, INC.

P.O. BOX 2006 • OLDSMAR, FLORIDA 34677  
813-855-4740 • FAX 813-855-6326

### WEATHERPROOF 8 OHM SPEAKER

Size 3" x 3" x 2" can be mounted  
Hardware included  
4.5' Cord 3.5mm Plug



#SPK305

\$9.95

### NEW ITEM - VOLT PEN

Determines presence of  
AC voltage through insulated wires. Contact with  
bare wire not required.  
Locates live wires in junction boxes, blown fuses,  
breaks in insulated wire & cable, defective circuit  
breakers, defective in-line circuits, etc.



#TKS10 1 - 4 \$17.95  
5+ \$15.95

### IC'S MEMORY CHIP/D-RAM SOCKET PULLS

64K X 1 — 150 NS  
#IC64 \$1.75  
256K X 1 — 150 NS  
#IC25 \$2.50

### AXIAL ELECTROLYTIC KIT 50 PIECES

5 each of the following values:  
1UF 150V 6UF 150V  
3UF 150V 10UF 100V  
2UF 350V 20UF 100V  
2.2UF 250V 150UF 150V  
3.3UF 250V 220UF 100V  
#AE50 \$9.50

### ZENER DIODE KIT 100 PIECES

5 each of the following values:  
3.6V 6.8V 18V 36V  
3.9V 8.2V 20V 39V  
4.7V 9.1V 27V 43V  
5.6V 12V 30V 47V  
6.2V 16V 33V 56V  
ALL 1 WATT  
#WZD20 \$15.00

### LED'S

T 1 3/4 Clear Lens; Light as Red



#LED25 Bag of 25 \$2.50

**DEALER INQUIRIES WELCOME.**  
CALL OR WRITE FOR A COPY OF OUR FREE FLYER.  
PRICES DO NOT INCLUDE SHIPPING.  
FLORIDA RESIDENTS ADD 6% SALES TAX.  
MINIMUM ORDER \$10.00 — COD (CASH ONLY)  
SHIPPING AND HANDLING ADD \$3.75

### ZENER DIODE KIT

150 PIECES

5 each of the following values  
2.4V 5.6V 8.7V 16V 25V  
2.7V 6.0V 9.1V 17V 27V  
3.0V 6.2V 10V 18V 28V  
3.3V 6.8V 12V 19V 30V  
3.9V 7.5V 13V 20V 33V  
4.7V 8.2V 15V 22V 56V  
ALL 500 MW  
#MZD30 \$22.50

### MONOLYTIC KIT

100 PIECES

5 each of the following values  
10PF 470PF .0047UF 0.47UF  
33PF 680PF .0068UF .1UF  
68PF 1000PF .01UF .22UF  
100PF .0022UF .015UF .33UF  
220PF 0.033UF .022UF .47UF  
ALL MINIMUM 50V  
RANGES 5-10-20%

#MK20 \$10.00

### 3 AMP RECTIFIER KIT

24 PIECES

3 each of the following values:  
5400 5401 5402 5403  
5404 5405 5406 5407  
#RRK24 \$2.50

### CERAMIC DISC KIT

105 PIECES

15 each of the following most  
popular values:  
(All 1 KV) (Some Short Leads)  
5PF 25PF 350PF 910PF  
.0015PF .0039PF .01PF  
#CD105 \$5.00

### RESISTOR KIT

200 PIECES

1 & 2 WATT 5 & 10%  
10 each of 20 assorted values  
#REK200 \$2.00

### CAPACITOR KIT

100 PIECES

Radial Mylar — All 100V 10%  
10 each of the following values:  
.0015 .0056 .033 .068 .15  
.0022 .01 .047 .1 .47  
#CPK15 \$12.00

### TRANSISTOR KIT

PNP NPN

5 each of the following values:  
2N4400 2N4401  
2N4403 2N5401  
#TRK20 \$2.50

## CAMCORDER REPLACEMENT BATTERIES FROM THE BATTERY STORE

- Low Cost Allows Extra Spare Batteries
- Buy Direct From The Battery Manufacturer
- Eliminate "Memory" Problem
- Extended Run Time Models Available
- 6 Month Warranty
- Other Battery Types Available
- Overnight Shipment by UPS

8mm	NP-22 Sony	\$27.00
	NP-55/77 Sony	\$31.00
	E-77K Canon	\$46.00
	VP-BP81 Olympus/Nikon	\$41.00
VHS	BP80 Panasonic	\$34.00
	CB-120 RCA/Hitachi	\$49.00
	NP-009 RCA/Pentax	\$49.00
	BP-96FL RCA/Hitachi	\$49.00
VHS-C	BN-V6GU JVC/Zenith	\$31.00
	VMP-51 RCA/Hitachi	\$49.00

\*Add \$4.00 shipping & handling per battery

**Batteries are our only business.** The true value of any battery system is determined by service, performance and dependability. Make your choice Periphex. Nobody has a better battery or offers a better value.

**Periphex Inc.**

149 Palmer Road • Southbury, CT 06488

(800) 634-8132 • In CT (203) 284-3985

FAX: (203) 282-6943



## COMPUTER DISK SERVICE

### SPECIALIZED DRIVE REPAIR

**Special  
Low Prices!**

\$ 75.00	SEAGATE 5 1/4" ST 238, ST 225
	MINISCRIBE 5 1/4" 3425, 3435, 3438
	MINISCRIBE 3 1/2" 8425, 8438
\$ 120.00	SEAGATE ST 251 MINISCRIBE 3650

FOR SALE NEW!!	380mb Scsi 16ms INTERNAL \$ 1,000.00
	MINISCRIBE 9380S EXTERNAL KIT
	CALL FOR PRICE
	1 YEAR WARRANTY

- Class 100 clean room
- Servowriting capabilities (Call for prices)
- Volume discount
- 120 day warranty on all repairs
- 7-10 day turn around time
- 24 hour turn around - ADD 30%
- Ask about our data recovery (Call for quote)

COMPUTER DISK SERVICE  
3537 OLD CONEJO ROAD, Suite # 115  
NEWBURY PARK, CA 91320

PH (805) 499-6355  
FAX (805) 499-0346

## SPECIALS

LIMITED QUANTITIES

# CABLE CONVERTERS

*SIGMA*

**SIGMA 550—86 CHANNEL \$99.95 EACH**

TOP CHANNEL ROLLOVER,  
LAST CHANNEL MEMORY,  
PARENTAL LOCKOUT,  
FAVORITE CHANNEL, SURGE  
PROTECTION, 4 db AMP,  
DECODER COMPATIBLE,  
1 YEAR WARRANTY.

**\$79.95 EACH 5 LOT**

**\$75.00 EACH 10 LOT**

**\$67.50 EACH 20 LOT**

**\$65.00 EACH 50 LOT**

**COMING SOON 'NORTH COAST' CONVERTERS**  
TOP OF THE LINE

*SAN JOSE SPECIAL!*

**SCIENTIFIC ATLANTA 6700 A/B \$99.95 EACH**

**\$79.95 EACH 5 LOT**

**\$75.00 EACH 10 LOT**

**\$69.95 EACH 20 LOT**

**\$65.00 EACH 50 LOT**

54 CHANNEL A/B TWINLINE,  
10 CHANNEL RECALL,  
CHANNEL 3 OUTPUT,  
ZENITH COMPATIBLE

**UNITED ELECTRONIC SUPPLY**

P.O. BOX 1206, ELGIN, IL 60121

**(708) 697-0600**

# BATTERIES

Replacements (All New — Made in the U.S.A.)

## CAMCORDER (batteries)

JVC	GR-C series	\$35.95
PANASONIC	PVBP80 (12V @ 2.3amps)	\$35.95
LCS2012-VBNC	LCS2012-BVBN	\$35.95
RCA/HITACHI	Full size VHS	\$39.95
SONY	VHS-C	\$39.95
NP22		\$32.95
NP55		\$32.95

MasterCard and Visa  
cards accepted. NYS  
residents add 8 1/4%  
sales tax. Add \$3.50  
for postage/handling.



## COMMUNICATIONS (complete battery packs and inserts)

ICOM	PB-2 (500mah @ 7.2V)	\$33.00
	PB-5 (500mah @ 7.2V)	\$44.28
	•7(S) (1200mah @ 13.2V)	\$63.00
	•8(S) (1200mah @ 9.6V)	\$59.00
	base charge only, one inch longer	
KENWOOD		
	KNB-1 (500mah @ 10.8V)	\$39.00
	KNB-4 (2200mah @ 7.2V)	\$65.00
	PB-1 (1100mah @ 12V)	\$64.00
YAESU		
	FNB-2 (500mah @ 11V)	\$20.00
	••FNB-10 (600mah @ 7.2V)	\$30.00
	••FNB-10(S) (1000mah @ 7.2V)	\$45.95
	FNB-12 (500mah @ 12V)	\$44.00
	••FNB-12(S) (600mah @ 12V)	\$49.00

\*same size case as FNB-12

## SPECIALS!!!

CELLULAR BATTERIES  
AND ELIMINATORS  
MOTOROLA  
PANASONIC  
MITSUBISHI  
OKI  
\$55.00  
NEC  
NOVATEL  
NOKIA-MOBIRA  
DIAMONDTEL  
TECHNOPHONE

MOTOROLA-FLIP PHONE  
SERIES  
AUDIOVOX  
\$75.00

## CORDLESS PHONE (batteries)

ATT	4110, 4310, 5210, 5310	\$ 9.00
Freedom 400		\$ 8.00
Nomad 200, 250, 400		\$ 8.00
<b>COBRA</b>		
CP-100, 200, 300, 400, series	\$ 8.00	
CP-464S to CP-475S series	\$ 9.00	
<b>PANASONIC</b>		
KX-T3805, PQP-25F301A	\$11.00	
KX-series most models	\$ 8.00	
<b>SONY</b>		
SSP-80	\$ 9.00	
<b>UNIDEN</b>		
EX-series most models	\$ 8.00	
XE-series	\$ 9.00	

Prices subject to change without notice.

## DEALERS WANTED (QUANTITY DISCOUNTS)



## BATTERY-TECH INC.

28-25 215th PLACE, BAYSIDE, NEW YORK 11360

IN NEW YORK (718) 631-4275

FAX: (718) 461-1978


TELEX: 51060 16395

CIRCLE 347 ON FREE INFORMATION CARD

- If you don't see it as for it
- Custom battery packs
- High capacity packs
- Nickel Cadmium cells
- Alkaline
- Lithium
- Get-Cells (Lead Acid)
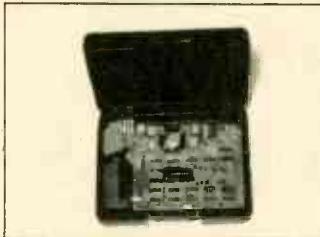
## MS-DOS EPROM PROGRAMMING SYSTEM NEEDS NO INTERNAL CARD

**EPROMS**  
2708 (3 supply)  
2758, 2716  
27C16, 2516  
2532\*, 2564\*  
68764\*, 68766\*  
2732, 2732A  
27C32, 2764  
2764A, 27C64  
27128, 27128A  
27C128, 27256  
27C256, 27512  
27C512, 27C010\*  
27010\*, 27C001\*



**EEPROMS**  
2804, 2816A  
2864A, 28256\*

**MicroControllers**  
8741A\*, 8742\*  
8748\*, 8749H\*  
8749\*, 8749H\*  
8751\*, 87C51\*  
8752\*, 8744H\*

\*Socket Adapter  
Required  
(Diagrams Included)

CONNECTS TO YOUR SYSTEM'S  
PARALLEL PRINTER INTERFACE

A FULL FEATURED, EASY-TO-USE SYSTEM WORKS WITH ANY DESKTOP OR LAPTOP MACHINE  
ADAPTIVE, HIGH-SPEED ALGORITHM MINIMIZES PROGRAMMING TIME AND INSURES VALID DATA  
SYSTEM PROGRAMS ALL STANDARD DEVICES OR EQUIVALENTS FROM ANY MANUFACTURER  
ALL SYSTEM COMPONENTS FIT NEATLY INTO CASE FOR TRAVEL OR STORAGE

### SYSTEM SOFTWARE COMMANDS

- PROGRAM EPROM(S) OR  
FROM DISK FILE
- READ DISK FILE INTO  
BUFFER
- READ EPROM(S) INTO  
BUFFER
- BUFFER EDITOR** HAS 18 BYTE LEVEL COMMANDS FOR DETAILED OPERATIONS
- SAVE EPROM(S) OR  
BUFFER TO DISK
- PROGRAM EPROM(S)  
FROM BUFFER
- COMPARE EPROM(S)  
WITH BUFFER
- COPY EPROM(S)  
ERASED
- BUFFER EDITOR
- SELECT DEVICE TYPE
- DEVICE CHECKSUM

SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK, CONNECTING CABLE, OPERATION MANUAL & SOFTWARE \$239

SOFTWARE AVAILABLE ON 3 1/2" OR 5 1/4" DISK  
TO ORDER SEND CHECK, MONEY ORDER, WRITE OR CALL:



ANDRTECH  
P.O. BOX 222  
MILFORD, OHIO 45150  
(513) 831-9708



CALL OR WRITE FOR MORE INFO. — ADD \$5.00 FOR SHIPPING - \$4.00 COD

## CABLE TV “BOXES”

Converters—Descramblers  
Remote Controls  
Accessories

★ Guaranteed Best Prices ★

★ 1 Year Warranty—C.O.D.'s ★

★ Immediate Shipping ★

★ FREE CATALOG ★

Call or Write

## TRANS-WORLD CABLE CO.

12062 Southwest 117th Court Suite 126

Miami, Florida 33186

1-800-442-9333



# Call for Outstanding Pricing on Tailored Computer Systems

# ALWAYS AT A DISCOUNT

Quality & Service to the Smart Mail Order Shopper for over 4 Years

MOTHERBOARDS • XT - 286 - 386 - 486	
XT, 8MHz Turbo, 8, 640 Max, 8 slots, w/BIOS & CPU	62
XT, 10MHz Turbo, 8, 640 Max, 8 slots, w/BIOS & CPU	74

OUR BEST SELLING VLSI 12MHz MOTHERBOARD	139
12MHz 286, 8ws, to 4mb, 8 slots, AMI BIOS, Baby size	

AT, 286-12, Baby Sz, 8ws, 8k to 4mb, NEAT CHIP, EEMS, Shad	239
AT, 286-12, Baby Sz, 8ws, 8k to 8mb, NEAT CHIP, EEMS, Shad	245
AT, 386-16SX, Baby Sz, 8ws, 8k to 8mb, NEAT CHIP, EEMS, Shad	365
AT, 386-25/33, 32k Cache, Baby Sz, 8ws, 16mb, 8 Slots, AMI BIOS, 1139/1375	

CONTROLLERS	14
FDC-2, 360K/720K, XT Only	31
LONGSHINE FDC +, 360K/720K/1.2mb/1.44mb, XT/AT	

SUPER FDC, Control 4 Internal Drives, XT/AT	39
All Drive Types	

COMPACTICARD II, 4 Drives, 360K/720K/1.2mb/1.44mb	94
COMPACTICARD II, Co-Exist, Ctrls 2 Dr, All Types	75
COMPACTICARD IV, 4 Dr, All Types, Co-Exist or Stand Alone Boot From Any Drive, Easy Installation	

WESTERN DIGITAL XT-GEN, Ctrls 2 H/D, MFM, XT Only	112
WESTERN DIGITAL 27X, Ctrls 2 H/D, MFM, XT	43
WESTERN DIGITAL 27X, Ctrls 2 H/D, MFM, XT	

WESTERN DIGITAL 1003-MM2, 2FD/2HD, 2:1, MFM, AT	102
WESTERN DIGITAL 1006-MM2, 2FD/2HD, 1:1, MFM, AT	
WESTERN DIGITAL 1003-SR2, 2FD/2HD, 2:1, RLL, AT	

WESTERN DIGITAL 1006-SR2, 2FD/2HD, 1:1, RLL, AT	102
LONGSHINE 6220, 2FC/2HD, XT Only	
LONGSHINE 6622, 2FD/2HD, 1:1, MFM, AT	

WA-3, 2FD/2HD, 2:1, MFM, AT	75
WA-6, 2FD/2HD, 1:1, RLL, AT	85
WA-8, 2FD/2HD, 1:1, MFM, AT	

OTC 7280, 2FD/2HD, 1:1, MFM, AT	99
OTC 7287, 2FD/2HD, 1:1, RLL, AT	

POWER SUPPLIES	62
150w XT, Standard Size for PC/XT Systems	
150w XT, UL Approved	

200w XT, Standard Physical Size for PC/XT	48
220w AT, Standard Physical Size for IBM AT	52
220w AT, UL Approved	

220w AT, UL Approved	62
FLOPPY DISK DRIVES	

TEAC 360K, 5-1/4, FD55R, Black/Beige, (Best)	66
TEAC 1.2mb, 5-1/4, FD55GFR, Beige/Black, (Best)	78
TEAC 720K, 3-1/2, FD235SF, with 5-1/4 Kit, Beige Only	66

TEAC 1.2mb, 5-1/4, FD55GFR, Beige/Black, (Best)	78
FUJITSU 360K, 5-1/4, M2551A, Black/Beige	63
FUJITSU 1.2mb, 5-1/4, M2552A, Black/Beige	73

TOSHIBA 1.2mb, 5-1/4, M2553A, Black/Beige	69
MINI MICRO 1.2mb, 5-1/4, MMFD-560K, Beige, Mfg Samsung	74
HARD DISK DRIVES	

40mb, RLL, Mini-Micro—Mfg. by Samsung, 3.25 HH w/5.25 kit, 35ms	239
40/60mb, MFM-RLL, MITSUBISHI MR535, 5.25 HH, less than 28ms Shockmounted, Voi Coil, Surface Mounted Technology	
SEAGATE	

20mb, MFM, ST-125, 3.25 HH w/5.25 kit, 40ms/28ms	235/280
20mb, RLL, ST-225R, 5.25 HH, 70ms - Dr. Only/ w/crt	199/249
30mb, RLL, ST-238R, 5.25 HH, 65ms - Dr. Only/ w/crt	219/282

30mb, MFM, ST-138R, 3.25 HH w/5.25 kit, 40/28ms	288/299
40mb, RLL, ST-250R, 5.25 HH, 70ms w/ controller (XT)	312
40mb, MFM, ST-151, 3.25 HH w/5.25 kit, 24ms	394

60mb, RLL, ST-277R-1, 5.25 HH, 28ms (65mb)	388
80mb, MFM, ST-409T, 5.25 HH, 28ms	585
VIDEO DISPLAY CARDS	

MONOCHROME GRAPHICS Card, w/Par. Port, LPT1	21
DUAL MONO/COLOR Graphics Card, 2 in one Card	29
CGA Color Graphics Adaptor, M Printer Port	

EVEREX ENHANCER, 640x350, No Printer Port	112
SUPER EGA OEM, 800x600, Auto Switching	
VGA GRAPHICS 800x600 SUPER VGA 1024x768 16bit	

VGA 1P ATI, 800x600, 8bit, 256	179
ATI VGA, OEM, 1024x768, 16bit, 256K, w/Mouse, (VP)	230
VGA 800x600 (Oak), 16bit	

VIDEO DISPLAY CARDS	89
ALL-PURPOSE DUST CLEANER with 5 SLIP-ON ADAPTER TOOLS BLOWS AWAY DUST PARTICLES FROM: VCR's - COMPUTERS - CAMERAS	

With a push of the button, blow away dust, oxide particles and simple dirt from hard reach areas. Attach appropriate adapter from tools furnished and Blow Master cleans VCR heads, computer keyboards, terminals, disk drives, camera optics and dozens of other delicate devices. Includes a brush attachment. 2 AA batt. (not included). 7.95*	7.95*
---	-------

## ALL OEM MONITORS MANUFACTURED BY SAMSUNG

### MONOCHROME

12" yundai 1200, 720x348, Amb T/S

12" MM OEM 1252, 720x350, Amb., Tilt & Swivel

14" MM OEM 1457, 720x350, Amb/Wht, Flat Scr, T/S

14" EVERVISION, 720x350, Amb., Flat Screen, T/S

14" MM OEM MM1464, 640x200, .52 Dot, T/S

14" MM OEM 1453, 640x200, .31 Dot, (Best Value)

14" RELYSY RE-5154, 640x350, .31 Dot, (Best Value)

14" NEC 3D, 1024x768, .28 Dot, Analog/TTL, T/S

14" VIEW PERFECT VP-3.024x768, .29 Dot, SUNY Tube, Sharp

14" RELYSY RE-5155, 800x600, .31 Dot, A/TTL, T/S

14" RELYSY RE-9513, 720x480, .31 Dot, Analog, T/S

14" MM OEM 14681, 720x400, .31 Dot, Analog, T/S

14" NEC 2A, 800x600, .31 Dot, Analog, T/S

14" I/O #1, 1 Ser, 1 Par, COM 1-2, LPT1-3

14" I/O #2, 2 Serial, 2 Parallel, COM 1-2, LPT1-3

14" I/O PLU, Clock, Parallel, Serial, Game (for XT)

14" 384K MULTI I/O, 8 to 384K, Cal, Cik, Ser, Par, Game (XT)

14" MULTI I/O, w/Floppy Ctr, Cal, Ser, Par, Game (XT)

14" SUPER MULTI I/O, w/Floppy Ctr—Controls, 360/720K, 1-2 and 1.44mb FDD, Cal, Cik, Ser, Par, Game Parts (XT)

BARE BONES

XT

AT 286

10MHz Desktop Barebone Sys., XT/AT Like Case, 101 KB, 150W P/S, Floppy Ctr, 360 Hoppy On/Off, 256K Memory

279

AT 286

12MHz 286 Desktop Barebone System, 0 to 4mb M/B, 0, Full

Size AT Case, 220w P/S, 101 Enhanced Keyboard, Floppy/Hard

Drive Controller, 1.2mb Floppy Disk Drive

MOODEMS

1200 GVC, Internal, with PC TALK III Software

1200 EVEREX, Internal, with BITCOM Software

1200 GVC, External with PC TALK III Software

2400 ECOM ZOOM, Internal with PC TALK III Software

2400 EVEREX, Internal with BITCOM Software

2400 ECOM ZOOM, External with PROCOMM Software

2400 GVC, External, with PC TALK III Software

2400 EVEREX, External, with BITCOM Software

MS DOS 3.3 W/GW Basic, OEM Version

MS DOS 3.3, Actual MICROSOFT

MS DOS 4.01 W/GW Basic, OEM Version—No Basic Manual

MS DOS 4.01 W/AC Basic—No Basic Manual

MS DOS 4.01 W/AC MICROSOFT—No Basic Manual

## LEARN ELECTRONICS FROM VHS VIDEO TAPES!

At  
Ucando  
your Success  
is our  
Business!



Our Video Tapes  
Are Designed  
To Make Learning Electronics  
Fun and Easy!

© 1989

- **PART 1-DC, 53 min.....\$32.95**  
Electronics and You—VT-201
- **PART 2-AC, 71 min.....\$32.95**  
Electronics and You—VT-202
- **PART 3-SEMICONDUCTORS, 47 min.....\$32.95**  
Electronics and You—VT-205
- **PART 4-POWER SUPPLY 55 min.....\$32.95**  
Electronics and You—VT-206

- **PART 5-AMPLIFIERS 52 min.....\$32.95**  
Electronics and You—VT-207
- **PART 6-OSCILLATORS 54 min.....\$32.95**  
Electronics and You—VT-208
- **VCR MAINTENANCE & REPAIR VT-203—54 min.....\$32.95**
- **INTRODUCTION TO VCR REPAIR VT-204—110 Min.....\$59.95**


ORDER  
NOW!

CALL TOLL FREE AT  
**1-800-678-6113**

or  
mail check or money order to:  
**UCANDO VIDEOS**

P.O. BOX 928 • GREENVILLE, OH 45331

VISA  
AND  
MASTERCARD  
ACCEPTED

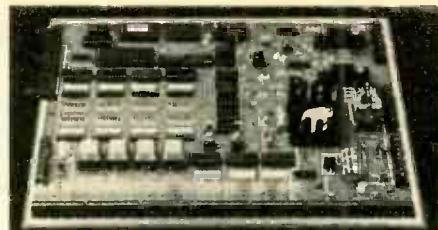

### Knight Patrol™

#### Talking Home Alarm Kit

A high end alarm system at an affordable price!  
Features include:

- ♦ State of the art PCF 8200 Speech Synthesizer
- ♦ 21 Sensor Zones, 2 Arming Circuits
- ♦ 2 Five Watt Audio Amplifiers
- ♦ Auxiliary Alarm
- ♦ Real Time 24 Hr. Clock
- ♦ A 10A & 3A Relay Circuit for Sirens, etc.
- ♦ Alert/Sleep Monitoring Modes (verbal status)
- ♦ Trigger Memory (verbal status)
- ♦ Self Diagnostics & Performance Monitoring
- ♦ Microprocessor Controlled
- ♦ Pleasant Female Voice
- ♦ Expandability & so much MORE!

Available as a kit or pre-assembled. Send for our FREE catalog! A complete line of peripherals is also available. Complete Circuit Board kit \$220 plus \$10.50 S.H. (Ca. residents add 6.75% tax).



#### Paladin Electronics

19425-B Soledad Cyn Rd  
Suite 333, Dept. PE  
Canyon Country, CA 91351

"We protect your castle"

CIRCLE 343 ON FREE INFORMATION CARD

## Double your income! Computer maintenance/service — a \$10 billion industry.

If you are presently servicing TVs, VCRs, camcorders or any other electronic equipment, computer repair can **double your income**.

National research results indicate that computer technicians bill out at double the hourly rate of electronic equipment technicians.

Tech-Serv can put you into computer repair quickly, economically and efficiently and with a complete support program including a **proven marketing plan**.

We provide:

#### RECOGNITION

Nationally recognized trademarks and logos give you immediate recognition as a professional computer repair specialist by being a Tech-Serv Authorized Computer Repair Center in your market area.

#### DOCUMENTATION

We provide manuals, schematics, documentation and advanced diagnostic software.

#### NEW HARDWARE

CPU's: IBM, Apple, Compaq, and others. Printers: Okidata, Epson, HP Lasers and others at huge discounts.

#### PARTS & BOARD REPAIR

Single source for parts and board repair. 24-hour express turnaround.

#### TRAINING

Hands on training: IBM, Compaq, Apple, and compatibles at 3 separate levels:

- Level 1: 8086-8088 Based Machines DOS System Configuration and upgrades
- Level 2: 80286/80386 Machines, Letter Quality and Laser Printers
- Level 3: System Networks Configuration, Installation and Repair

#### FINANCING

Available for qualified businesses.

#### OVER 165 DEALERS WORLDWIDE

Find out why more and more electronic professionals are adding computer repair to their businesses or starting their own computer repair businesses.

**Call Tech-Serv at (212)967-1865 now.**

**techserv**<sup>SM</sup>  
AUTHORIZED DEALER

SERVICING THE WORLD OF MICROS

253 West 28th Street, New York, NY 10001

©1989 Tech-Serv Corp.

### EARN

**\$65/HRI!**



Over 8 million Fax machines in homes/offices — predictions are for over 25 million by 1992!

- Work from your home/van
- Home study program gets you started servicing fax machines in 2 weeks!
- No special tools/equipment needed - no need for a background in electronics!
- Earn additional profits selling fax supplies!
- Fax machines are not cheap - therefore, you can get good \$\$ for the repair.
- Average Fax machine requires professional service every 18 months.
- Home study training program includes full instructions on **EVERY ASPECT** of Fax maintenance/repair. **FULL COVERAGE** of how to set up your home-based service business.

#### FREE DETAILS

CALL 1-800-537-0589

Or write to: Viejo Publications, Inc.

3540 Wilshire BL. #310

Dept RES Los Angeles, CA 90010

CIRCLE 349 ON FREE INFORMATION CARD

# B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228

(214) 271-5546

FAX (214) 271-2462



7400

WE ALSO CARRY

DYNAMIC RAM

TEXT TO SPEECH BOARD

7400	.17	7474	.30	74162	.50
7401	.17	7475	.35	74163	.50
7402	.17	7482	.30	74164	.70
7403	.17	7483	.45	74165	.70
7404	.17	7484	.30	74166	.90
7405	.17	7485	.55	74173	.75
7406	.23	7486	.30	74174	.70
7407	.23	7488	.30	74175	.80
7408	.22	7490	.37	74176	.50
7409	.17	7492	.30	74177	.50
7410	.17	7493	.30	74180	.50
7413	.33	7496	.30	74191	.35
7414	.25	7497	.30	74193	.80
7416	.20	74102	.35	74194	.25
7417	.20	74107	.20	74195	.80
7420	.17	74111	.35	74197	.25
7425	.25	74120	.30	74199	1.00
7426	.17	74125	.40	74221	.80
7427	.25	74126	.19	74251	.25
7428	.25	74128	.19	74259	.70
7430	.15	74136	.19	74265	.50
7432	.27	74144	.20	74273	1.75
7433	.25	74145	.40	74276	.50
7437	.17	74148	.90	74279	.50
7438	.22	74150	.25	74283	.50
7440	.19	74151	.50	74365	.60
7442	.35	74153	.35	74366	.60
7450	.17	74154	.19	74367	.50
7451	.18	74156	.30	74368	.30
7453	.22	74157	.30	74376	.30
7454	.22	74160	.80	74390	1.40
7473	.28	74161	.50		

74LS

LS00	.14	LS122	.35	LS241	.60
LS02	.14	LS123	.45	LS242	.65
LS03	.14	LS125	.30	LS243	.50
LS04	.14	LS126	.35	LS244	.55
LS05	.14	LS132	.35	LS245	.55
LS08	.14	LS133	.25	LS251	.45
LS09	.14	LS138	.35	LS253	.40
LS10	.14	LS139	.35	LS257	.35
LS11	.14	LS145	.75	LS258	.45
LS12	.20	LS148	.35	LS259	1.00
LS13	.25	LS151	.35	LS260	.40
LS14	.30	LS153	.35	LS266	.30
LS15	.20	LS154	.85	LS273	.75
LS20	.14	LS155	.50	LS279	.30
LS21	.16	LS156	.42	LS280	.80
LS26	.14	LS157	.30	LS283	.35
LS27	.20	LS158	.25	LS290	.70
LS28	.15	LS160	.25	LS298	.65
LS30	.14	LS161	.35	LS323	2.25
LS32	.16	LS162	.45	LS353	1.00
LS33	.25	LS163	.36	LS357	.80
LS37	.24	LS164	.45	LS363	.75
LS38	.24	LS165	.60	LS365	.30
LS42	.35	LS166	.75	LS367	.35
LS51	.15	LS169	.90	LS368	.30
LS54	.20	LS173	.60	LS373	.50
LS55	.20	LS174	.35	LS374	.45
LS74	.22	LS175	.35	LS375	.35
LS75	.25	LS181	.125	LS377	.75
LS83	.30	LS191	.45	LS378	.80
LS85	.45	LS192	.65	LS390	.80
LS86	.20	LS193	.65	LS393	.75
LS90	.35	LS194	.40	LS399	1.00
LS92	.30	LS195	.52	LS541	1.20
LS95	.30	LS196	.55	LS645	.75
LS107	.28	LS197	.75	LS646	.75
LS109	.20	LS221	.50	LS670	.80
LS112	.25	LS240	.50		
LS113	.25		26LS32	.75	
LS114	.25		25LS2569	1.50	

NETWORK

\$25.00

(LAN) NETWORK  
THAT REALLY WORKS!

CALL OR WRITE  
FOR DETAILS.

WE ALSO CARRY

POWER SUPPLIES  
74S  
74ALS  
74F  
74HC  
CMOS  
LINEAR  
UART  
Z80  
PROMS  
CRYSTALS  
DIP SWITCHES  
OSCILLATORS  
DRIVES  
VOLTAGE REGULATORS  
F.D. CONTROLLERS  
CLOCK CIRCUITS  
DRIVERS  
RECEIVERS  
CRT CONTROLLERS

MUCH, MUCH MORE!  
CALL OR WRITE FOR  
FREE CATALOG.

6500

6502	2.00
6520	1.25
6522	2.75
6530	3.00
6532	4.25
6545	2.10
6551	2.45

6800

6800	1.40	6852	3.30
6802	2.50	6860	3.35
6803	3.00	6868	3.30
6805	2.95	6809EP	1.29
6809EP	2.75	68440	4.00
6809P	2.50	68A54	3.00
6810	1.25	68809	4.00
6845P	2.20	68810	2.00
6845S	2.20	68845	4.95
6850	1.75	68854	4.00

THREE CHIP SET

1488, 1489, 16450

B.G. SPECIAL

\$6.50

LM317K	1.40	7815K	.60
LM317T	.50	7818K	.60
LM337T	.50	7824T	.35
7805T	.35	7875T	.30
7805T	.25	7905K	.75
7806T	.28	7905T	.40
7806T	.50	79M05T	.25
7810T	.28	7912T	.35
7812T	.40	7912K	.50
7812CK	1.00	7915K	.30
78M12T	.25	LM350K	3.35
7815T	.30	78H05K	3.75

DYNAMIC RAM

2108-4 8KX1	1.50
2118-4 16KX1-5Volt	.70
4027-4KX1-250 n.s.	.80
4116-16KX1-250 n.s.	.40
4116-16KX1-200 n.s.	.75
4116-16KX1-150 n.s.	.90
4164-64K 200 n.s.	1.25
4164 150 n.s.	1.50
4164 120 n.s.	1.50
4164-100	1.75
41256 150 n.s.	1.75
41256 120 n.s.	2.05
41256 100 n.s.	2.35
41256-80	2.90
41256-60	4.00
1 Meg - 100 n.s.	8.00
1 Meg - 80 n.s.	8.35
414256-80 n.s. 256 x 4	9.00
SIPPS & SIMMS AVAILABLE	

STATIC RAM

2016-2KX8 200 n.s.	1.00
2101-1 - 256X4 500 n.s.	.75
21L02-1 350 n.s.	.65
2102AL-4 L.P. 450 n.s.	.49
2111-1 256X4 500 n.s.	1.00
2112A-2	2.50
2114L-3 1KX4 300 n.s.	.45
2125A-2 1KX1 70 n.s.	1.70
2147 4KX1	1.95
6116P-4	1.20
6117	1.20
6264-15	1.40
62256 32KX8	6.50

EPROM SPECIAL

We bought a large quantity of 2708s, 2710s, 2532s, 2732s, 2764s, 27128 and 27256 from a computer manufacturer who redesigned their boards. We removed them from sockets, erased and verified them, and now we offer the savings to you. Complete satisfaction guaranteed.	
---	--

8000/80000

8031	2.95	(16450)	6.50
8035	1.00	(16550)	12.00
8039	1.00	8251	1.10
8085	1.55	8253-5	1.75
8086	1.55	8254	1.80
8087	87.50	8255	1.50
8087-1	167.50	8255-5	1.75
8087-2	127.50	8257	1.50
8088	2.70	8259A	1.85
80C98	.40	8259C-5	2.10
8155	2.25	8275	10.95
8156	2.25	8279	2.25
8202A	8.00	8284	1.49
8212	1.25	8286	3.50
8214	2.00	8287	2.49
8216	1.25	8288	3.50
8224	1.25	8530	3.00
8228	1.75	8741	7.00
8237-5	2.80	8748	7.00
8243	1.75	8749	7.00
8250	2.95	8755	7.00
80286-8 PLCC	8.50		
80287-8	191.50		
80287-10	227.50		
V-20-10MHZ	6.50		

PC/XT COMPATIBLE.

MAKE YOUR COMPUTER TALK!

PRICE CUT



A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE NEW GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER. THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT (EXTERNAL POWER SUPPLY) WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. TO USE THE BOARD IT IS ONLY NECESSARY TO SEND ENGLISH TEXT TO THE RS232 INPUT ON THE BOARD. THE BOARD INCLUDES A 1500 BYTE TEXT BUFFER AND HANDSHAKE LINE TO ALLOW YOU TO SEND DATA TO THE BOARD; THE SAME AS YOU WOULD SEND DATA TO AN RS232 SERIAL PRINTER. YOU CAN SET UP BATCH FILES THAT WILL MAKE YOUR COMPUTER GREET YOU WITH "GOOD MORNING MASTER," ETC. EVERY TIME YOU TURN IT ON. DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4 INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED.

FOR INFORMATION ON A LOW COST SPEECH SYNTHESIZER SYSTEM FOR THE VISUALLY IMPAIRED, PLEASE SEND FOR FREE PACKET T.M.I.

STAND ALONE POWER SUPPLY

FOR ABOVE

ADD \$2.50 SHIPPING & HANDLING

\$19.99

IBM PC, XT COMPATIBLE KEYBOARD

CHEAP PRICE  
EXCELLENT QUALITY

COMPUTER MANUFACTURERS EXCESS.  
BRAND NEW UNITS MANUFACTURED BY HONEYWELL.

COILED CONNECTING CABLE.  
HAS SAME MAKE AND BREAK CODES AS STANDARD PC, XT KEYBOARD.

WORKS FINE WITH CLONES AND COMPATIBLES.

ADJUSTABLE REAR ELEVATION CONTROL (3 LEVEL). ORIGINAL COST IN EXCESS OF \$65.00 EACH.

\$19.95 or 3/\$47.50

Add \$3.00 each for shipping

SOCKETS

Low Profile SOLDER TAIL</
---------------------------

# AMIGA-Commodore AMIGA Chips...Parts...Upgrades

6526	\$12.25
6567	\$14.95
6581	\$11.25
PLA (82S100)	\$12.95
All 901 Roms	\$10.95
41256/120	\$2.95
A501-512K Ram	\$99.50
*Fatter/Super Agnus	\$99.50
8362 Denise	\$39.95
8364 Paula	\$49.94
8520A	\$17.95
1.3 Kickstart Rom	\$27.95
256 x 4/100	\$9.50
1 MEG x 1/120	\$9.40

\*Includes Chip Puller (many others in stock)

Commodore Diagnostician \$6.95 prepaid

## • NEW, POWERFUL • REPAIRABLE C-64 POWER SUPPLY

- 13-month warranty
- Complete schematic included
- External fuse—runs cool
- UL Approved
- Heavy duty—perfect for "packet radio"
- Conservatively rated @ 1.8 amps
- Made by Commodore sub-contractor

**\$23.95  
PLUS  
UPS**

Amiga Upgrade..New 1 Megabyte "Fatter AGNUS" Chip 8372  
\$99.50 with simple step/step 10 min. Instructions and chip puller.

SEND FOR CATALOG ON EXCLUSIVE NEW PRODUCTS

THE GRAPEVINE GROUP, INC.

35 Charlotte Drive, Wesley Hills, N.Y. 10977  
1-800-292-7445 • (914) 354-4448  
FAX (914) 354-6698

Dealer Prices Available

Prices Subject To Change

THE ULTIMATE  
PERSONAL

## UV ERASER

D][ AC  
**39 95**

Add 3<sup>95</sup>  
Shipping & Handling

Also Available

D][ ACT  
**49 95**

AC with internal 2 - 8 minute  
timer and time out beeper.

D][ B with  
SAA bat  
**49 95**

Battery powered for 100 cycles.  
Internal 2 - 8 min. timer.  
Optional AC adaptor. 7<sup>95</sup>

**WALLING CO.**

4401 S. Juniper • Tempe, AZ 85282

- Molded Plastic Case
- Shirt Pocket Size
- Auto Start
- Erases most EPROM's/EPLD's in 3 minutes
- Handles all sizes up to four at a time
- Regulated lamp output for uniform  
erase time



Dealer inquiries welcome.  
6 month unconditional guarantee.  
Order direct or call for dealer near you.  
(602) 838-1277 1-800-338-9813

# Motorless Motion!

Robotics! Engines! Inventions!  
Thin Shape Memory Alloy wires  
contract like living muscle when  
electrically activated.

Space Wings - Sleek silver wings  
flap silently using only 5 cm of  
SMA wire. Assemble this futuristic  
kit in under an hour. Stands 15 cm  
high. Perches on your PC or desk  
lamp. Annoys cats. With printed  
circuit board, parts, info on SMAs,  
and complete instructions. Runs on  
two AA batteries (not included).

**3-001 Space Wings Kit \$19.95**



Send a business size Self-Addressed Stamped Envelope for latest catalog.

Order Today - Send check or money order (sorry no credit cards).  
CA orders add 7.25% tax. All orders add \$4 P&H (\$8 to Canada).

**Mondo-tronics • 2476 Verna Ct.  
San Leandro, CA 94577 • USA**

CIRCLE 337 ON FREE INFORMATION CARD

### 4-Piece Electronics Pliers Kit

★ U.S. Made ★ Lifetime Guarantee

Finest quality alloy steel pliers with  
color-coded cushion grip handles.  
Includes 4-1/2" miniature diagonal  
cutter, 5-1/2" diagonal cutter, 6-3/4"  
chain nose with cutter, 4-3/4" miniature  
chain nose and vinyl roll pouch. Charge  
Visa, MasterCard, American Express or  
send check or money order.

**RES-82 Pliers Kit ... \$39.00**

We pay the shipping charges.

**JENSEN TOOLS INC.**

7815 S. 46th St. Phoenix, AZ 85044 • Phone (602) 968-6231 • FAX (602) 438-1690

CIRCLE 338 ON FREE INFORMATION CARD

# Give.

American Heart  
Association



Are you in  
**DEFUALT**  
On a Student Loan?


If you're in default on a  
guaranteed student loan (FISL,  
GSL, Stafford, SLS, or PLUS  
loan), you may be eligible for  
a special program that lets you  
pay it back without penalty or  
collection charges.

You must pay your loan in full  
by August 31, 1990 to take  
advantage of this special  
program. For information,  
call the guarantee agency that  
holds your loan, or call the  
U.S. Department of  
Education's toll-free number:

**(800) 333-INFO**

# ALL NEW! NEON PRODUCTS

## PLASMA FIRE SABER™

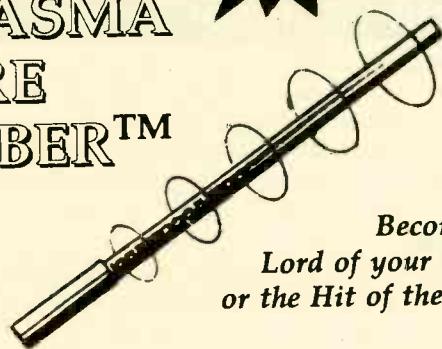

*Become the  
Lord of your Galaxy  
or the Hit of the Party!*

Length of visible plasma fire field is controlled by your touch. Creates a bizarre and spectacular effect.

Available in Star Fire Red, Photon Blue, Nova Purple, and Phasor Green. Please specify color.

PFS20 FIRE SABRE (battery not included) ..... \$89.50

PFS2K EASY TO BUILD KIT - Excellent Science Project! ..... \$59.50

Quantity	10-24	25-99	100+	1,000+
Discounts	\$45.00	\$40.00	\$35.00	Price on Req

## Outdoor Neon Lighting for Garden, Walkways PLASMA STIK LITES™

Experience the mystifying beauty of PLASMA STIK LIGHTING™

Highly Efficient Cold Cathode design uses UL 10 volt adapter.

- Safe, Easy to Install - simply push into ground
- Weatherproof, durable construction
- Economical to operate - less than 2 watts

Basic system includes one STIK LITE and a power adapter capable of driving up to 3 extra "AD-ON's". Buy extra STIK LITE as needed. Specify color(s).


STIK Basic System, 1 Stik Lite  
with power adapter for 3 AD-ON's ..... \$49.50  
EXTRA STIK LITE AD-ON's, Each ..... \$29.50



STIK LITES  
Available in:

- Garden Green
- Pool Blue
- Walkway White
- Warning Red

## MUSICAL NEON & DANCING PLASMA FIRE™

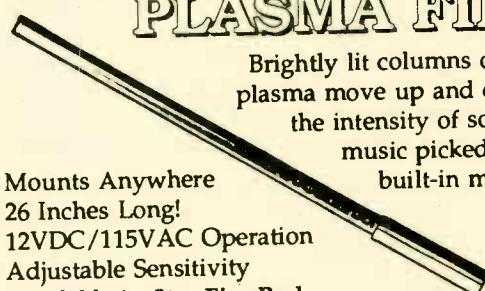

Brightly lit columns of colorful plasma move up and down with the intensity of sounds and music picked up by the built-in microphone.

- Mounts Anywhere
- 26 Inches Long!
- 12VDC/115VAC Operation
- Adjustable Sensitivity
- Available in Star Fire Red, Photon Blue, Nova Purple and Phasor Green (please specify)

DPL20 DANCING PLASMA ..... \$99.50

DPL2K EASY TO BUILD KIT ..... \$69.50


Quantity	10-24	25-99	100+	1,000+
Discounts	\$52.00	\$47.00	\$40.00	Price on Req

## Decor HI LITE NEON™

Brightly lit columns of colorful neon for enhancing, lighting or decorating.

Available in-

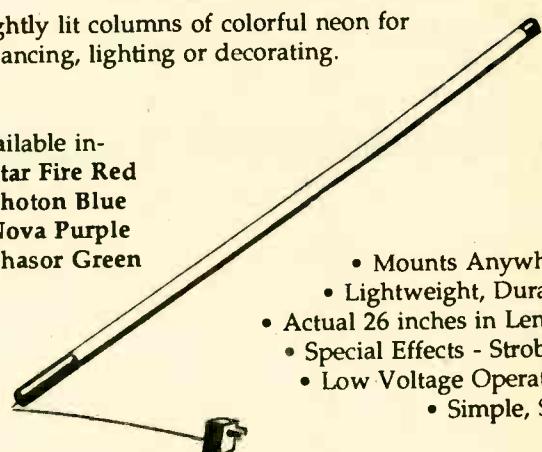- Star Fire Red
- Photon Blue
- Nova Purple
- Phasor Green



- Mounts Anywhere
- Lightweight, Durable
- Actual 26 inches in Length
- Special Effects - Strobing
- Low Voltage Operation
- Simple, Safe

DNE10 DECOR NEON ..... \$79.50

DNE1K EASY TO BUILD KIT ..... \$59.50

Quantity	10-24	25-99	100+	1,000+
Discounts	\$39.00	\$35.00	\$30.00	Price on Req

Most products on this sheet are made possible through a recently obtained patent for single ended energizing of neon display signs and lighting systems. Ref U.S. Patent #4,742,278. All requests for quantity or dealer discounts are welcome. You may fax us at 603-672-5406. Phone orders 800-221-1705 or 603-673-4730 for 24 hour service. Call 603-673-6493 for information.

**FAX ORDERS: 1-603-672-5406**

**PHONE ORDERS: 1-800-221-1705**

INFORMATION UNLIMITED

P.O. Box 716

Amherst, New Hampshire 03031

603-673-4730

ORDERS: 800-221-1705

# USE R-E SHOPPER CLASSIFIEDS

## READ BY MORE THAN 100,000 ELECTRONICS BUYERS AND SELLERS AND TRADERS

### INSTRUCTION FOR PLACING YOUR AD!

#### HOW TO WRITE YOUR AD

TYPE or PRINT your classified ad copy CLEARLY (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for the additional ads (a photocopy of this form works well). Choose a category from the list below and write that category number into the space at the top of the order form. If you do not specify a category, we will place your ad under Miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. Payment in full must accompany your order. We do permit repeat ad or multiple ads in the same issue, but in all cases, full payment must accompany your order.

#### WHAT WE DO

The first two words of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

#### RATES

Our classified ad rate is 40¢ per word. Minimum charge is \$6.00

**AD RATES: 40¢ per word, Minimum \$6.00.**

Send your ads with payment to:

**Radio-Electronics SHOPPER, 500-B BI-County Blvd. Farmingdale, NY 11735**

#### CATEGORIES

100 — Antique Electronics	270 — Computer Equipment Wanted	450 — Ham Gear Wanted	630 — Repairs-Services
130 — Audio-Video-Lasers	300 — Computer Hardware	480 — Miscellaneous Electronics For Sale	660 — Satellite Equipment
160 — Business Opportunities	330 — Computer Software	510 — Miscellaneous Electronics Wanted	690 — Security
190 — Cable TV	360 — Education	540 — Music & Accessories	710 — Telephone
210 — CB-Scanners	390 — FAX	570 — Plans-Kits-Schematics	720 — Test Equipment
240 — Components	420 — Ham Gear For Sale	600 — Publications	

#### CLASSIFIED AD COPY ORDER FORM

Ad No. 1—Place this ad in Category # \_\_\_\_\_

1 - \$6.00	2 - \$6.00	3 - \$6.00	4 - \$6.00
5 - \$6.00	6 - \$6.00	7 - \$6.00	8 - \$6.00
9 - \$6.00	10 - \$6.00	11 - \$6.00	12 - \$6.00
13 - \$6.00	14 - \$6.00	15 - \$6.00	16 - \$6.40
17 - \$6.80	18 - \$7.20	19 - \$7.60	20 - \$8.00
21 - \$8.40	22 - \$8.80	23 - \$9.20	24 - \$9.60
25 - \$10.00	26 - \$10.40	27 - \$10.80	28 - \$11.20

29 - \$11.60      30 - \$12.00      31 - \$12.40      32 - \$12.80

33 - \$12.80      34 - \$13.60      35 - \$14.00      36 - \$14.40

37 - \$14.80      38 - \$15.20      39 - \$15.60      40 - \$16.00

Ad No 1—Total words \_\_\_\_\_ x .40 per word = \$ \_\_\_\_\_

All Caps words \_\_\_\_\_ x .10 per word = \$ \_\_\_\_\_

Bold words \_\_\_\_\_ x .10 per word = \$ \_\_\_\_\_

Bold Cap words \_\_\_\_\_ x .20 per word = \$ \_\_\_\_\_

**TOTAL COST OF AD No. 1 \$ \_\_\_\_\_**

Card # \_\_\_\_\_

Expiration Date \_\_\_\_\_ / \_\_\_\_\_

Signature \_\_\_\_\_

Total classified ad Payment \$ \_\_\_\_\_ enclosed.

[ ] Check [ ] MasterCharge [ ] Visa (\$15.00 minimum credit card order)

Name \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_ City State Zip \_\_\_\_\_

# CABLE TV BLOWOUT

BRAND NEW

## Scientific Atlanta Combo

Model 8536.  
Works on all SA systems  
Channel 3 output  
Original equipment

Lots of:  
1 5  
\$260 \$225  
Lots of 10  
**\$215**



## Zenith SSAV-1

Add-on descrambler  
with power supply  
Original equipment

Lots of:  
1 5  
\$125 \$115  
Lots of 10  
**\$95**



BRAND NEW

## Jerrold JRX 3 DIC Combo

With wire remote  
Channel 3 output  
36 channels  
Original equipment

Lots of:  
1 5  
\$84 \$74  
Lots of 10  
**\$55**



BRAND NEW

## Panasonic Converter TZPZ145N

w/female control, 83 channel  
Standard/Hrc switchable  
Favorite channel memory  
Channel scan,  
last channel recall  
Channel 2 or 3


Lots of:  
1 5  
\$85 \$76  
Lots of 10  
**\$71**


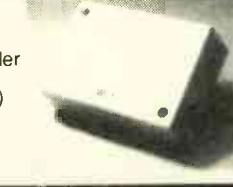
## Oak N-12

Minicode descrambler  
Non vari-sync  
(Vari-sync available)  
Original equipment

Lots of:  
1 5  
\$84 \$69  
Lots of 10  
**\$59**



## Jerrold 450 Combo DRZ 3 DIC

With new remote,  
68 channel  
original equipment  
automatic fine tuning

Lots of:  
1 5  
\$169 \$135  
Lots of 10  
**\$125**



## Hamlin Tag-Alone Descrambler

MLD-1200  
Available channel  
2 or 3 output  
Original equipment

Lots of:  
1 5  
\$64 \$55  
Lots of 10  
**\$45**



## BRAND NEW Jerrold Tri-bi

Add-on  
descrambler

Lots of:  
1 5  
\$95 \$75  
Lots of 10  
**\$65**



## Notch Filter

Available all channels



## BRAND NEW Scientific Atlanta

SA-3  
Add-on descrambler

Lots of:  
1 5  
\$109 \$86  
Lots of 10  
**\$70**



## MMDS

Microwave antenna,  
wireless cable, Parabolic  
antenna, Conifer Down-  
Converter, Zenith  
Decoder, Cable Converter,  
Conifer Power Supply  
60' Coaxial Wire

Lots of:  
1 5  
\$475 \$400  
Lots of 10  
**\$350**



WE WILL MEET OR BEAT  
ANY ADVERTISED PRICE  
IN THIS MAGAZINE!

## Jerrold 400 Combo DRX3 DIC

With new remote,  
61 channel  
manual fine tuning  
Original equipment

Lots of:  
1 5  
\$134 \$115  
Lots of 10  
**\$95**



## Oak M-35 Combo

Non vari-sync  
(Vari-sync available)  
Original equipment

Lots of:  
1 5  
\$79 \$60  
Lots of 10  
**\$50**



## BRAND NEW Jerrold SB-3 or SB-2

Add-on  
descrambler

Lots of:  
1 5  
\$74 \$65  
Lots of 10  
**\$55**



## MMDS Zenith

SSAV-1  
Add-on Descrambler  
for wireless  
cable systems

Lots of:  
1 5  
\$225 \$200  
Lots of 10  
**\$175**



## BRAND NEW Texscan

Converter with remote  
61 channel, Standard  
Automatic fine tuning  
Channel 3 output

Lots of:  
1 5  
\$64 \$59  
Lots of 10  
**\$54**



# UNIVERSAL VIEW

520 GLENBROOK RD., SUITE 202  
STAMFORD, CT 06906

PLEASE PRINT:  Cashier's Check  Money Order  COD

Quantity	Item	Price ea.	Total

Name:

Address:

City/State/Zip:

ORDERS ONLY:

**1-800-622-9022**

FREE CATALOG & INFO:

**(203) 975-7543**

10 AM - 5:30 PM EASTERN TIME

NO CONNECTICUT SALES. It is not the intent of  
UNIVERSAL VIEW to defraud any pay television operator and we  
will not assist any company or individual in doing so.

WAIVER. I, the undersigned, am a consenting adult of at least 21 years of age, and fully understand that ownership of a cable decoder does not give the owner of the decoder the right to decode or view premium cable channels without proper authorization from their local cable company, and hereby declare under penalty of perjury that all products purchased, at any time, will only be used on cable TV systems with proper authorization from local officials or cable company officers in accordance with all applicable federal and state laws. Federal and various state laws provide for substantial criminal and civil penalties for unauthorized use.

Signature

Date

# FREE CATALOG

## Loaded With Satellite TV Products At Discount Prices

- Complete Systems
- Upgrades
- 2ft to 24ft Dishes

- Parts
- Accessories
- Major Brands

- Factory Fresh
- USA Warranty
- Fast Delivery



### Satellite TV Anywhere




#### WORLD SATELLITE TV AND SCRAMBLING METHODS
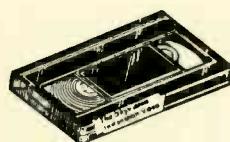
##### "The Technicians' Handbook"

This thorough text is a must-buy for technicians, satellite professionals and curious do-it-yourselfers. The design, operation and repair of satellite antennas, feeds, LNBs, receivers and modulators are examined in detail. An in-depth study of scrambling methods and broadcast formats including the VideoCipher II, Oak Orion, FilmNet, Sky Channel, EuroCypher, D2 MAC, BSB and Teleclub Payview III. Circuit and block diagrams of all components are presented and clearly examined throughout the handbook. This information is a prelude to the chapters on troubleshooting and setting up a test bench. This expert guidance on testing, servicing and tuning is complimented by a wealth of detailed illustrations.


340 pages, 8 1/2 x 10 3/8 over 200 photos, diagrams, wiring schematics and 16 tables / appendices / index  
Order #21T ..... S&H \$4 (U.S.) ..... \$39.95


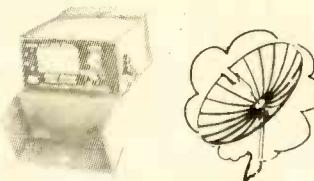
#### THE SKYVISION DO-IT-YOURSELF INSTALLATION VIDEO

"Now You Can Watch It Being Done"  
Installing or "Tuning up" your satellite system made simple. From start to finish, the Skyvision Do-It-Yourself Installation Video is a step-by-step video that will help you set-up your systems in no time flat. It's like having our trained technicians right at your site helping you with every step.

Order #SK10 VHS ..... S&H \$3 (U.S.) ..... \$33.95  
Order #SK11 Beta ..... S&H \$3 (U.S.) ..... \$33.95



#### TUNE YOUR DISH TO ITS MAXIMUM!

##### "With The Pico Signal Meter"

A must for the serious dealer or satellite system owner. Saves time, frustration and money. Use when installing a new system, moving your dish, re-alignment of a dish that has been moved by wind, frost heaves etc., gets you right on the satellite belt for the best possible pictures! The PP-1450 Pico Peaker is a super sensitive signal meter used for antenna aiming, focusing, peaking and polarity alignment. The multi-purpose Peaker can be used on any receiver system with block down-converted frequencies between 70 and 1500 MHz. (Does not work with older single conversion receivers - Ask for Bulz-I-Meter) The Peaker comes in an attractive case with neck strap.

Order #PP-1450 ..... S&H \$5 (U.S.) ..... \$89.95

Optional jump cable kit. Connects Peaker to LNB  
(Kit includes 2ea. 12' coax cables w/ splicer).  
Order #C212 ..... S&H \$3 ..... \$7.95



#### IRDs / RECEIVERS / SYSTEMS

##### "Save \$\$\$ on Packages"

System package includes: ORBITRON 10 foot mesh dish, 50degree LNB, 18" Jack Arm, Feed-horn and Receiver/IRD of your choice, plus a FREE detailed installation Video.

IRD/Receiver	System
UNIDEN UST2200	(Receiver) \$219
UNIDEN UST9000	(Receiver) \$449 \$999
UNIDEN UST7700	(IRD) \$899 \$1449
UNIDEN UST9900	(IRD) \$1019 \$1569
UNIDEN UST4200	(slave recv.) \$679
UNIDEN UST4400	(IRD) \$909 \$1459
UNIDEN UST4800	(IRD) \$1539 \$2089
HTS V	(IRD) \$1049 \$1599
HTS VIII Plus	(IRD) \$1229 \$1779
HTS X	(IRD) \$1419 \$1969
DRAKE ESR324b	(Receiver) \$239
DRAKE ESR924i	(Receiver) \$599 \$1149
DRAKE ESR1024	(IRD) \$909 \$1459
DRAKE ESR1224	(IRD) \$1039 \$1589
DRAKE ESR1424	(IRD) \$1209 \$1759
ECHOSTAR 3000	(Slave recv.) \$729
ECHOSTAR 4000	(IRD) \$849 \$1399

Just a partial listing of hundreds of products listed in the Skyvision catalog. Ask for yours today!

## Skyvision Inc.®

2048 College Way Fergus Falls, MN 56537 - Toll Free 800-334-6455

Mail in coupon or call Toll FREE today for the SKYVISION Satellite TV Product Catalog.

Delivered free to your mail box in U.S. and its holdings.

\* International requests add \$8.00 to cover shipping and handling.

Send Skyvision Satellite TV Products Catalog

Name \_\_\_\_\_ Phone ( ) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Install A System, Upgrade or Repair Yourself And Save \$\$\$

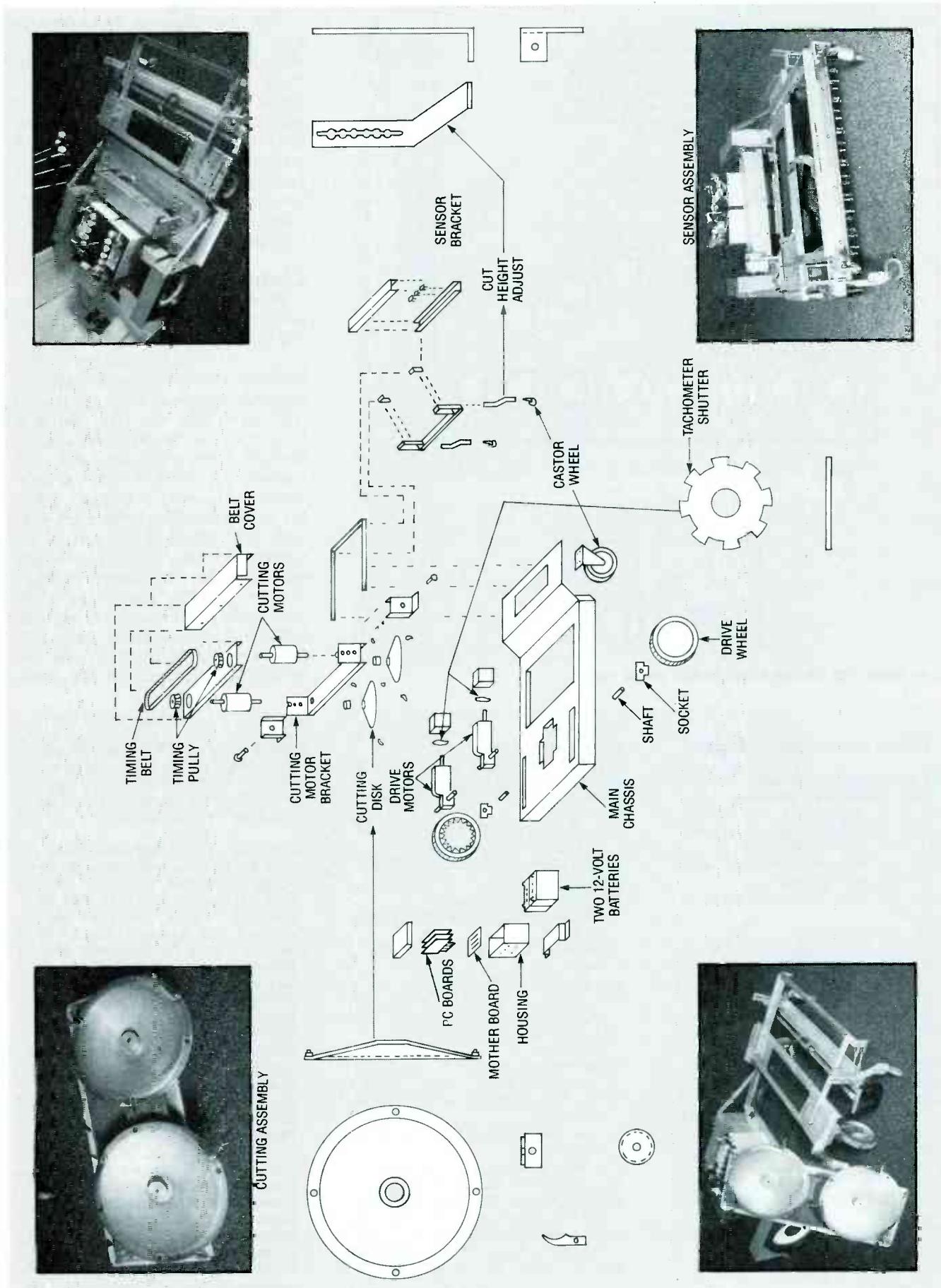


FIG. 3—THE MECHANICAL ASSEMBLY of the Lawn Ranger.

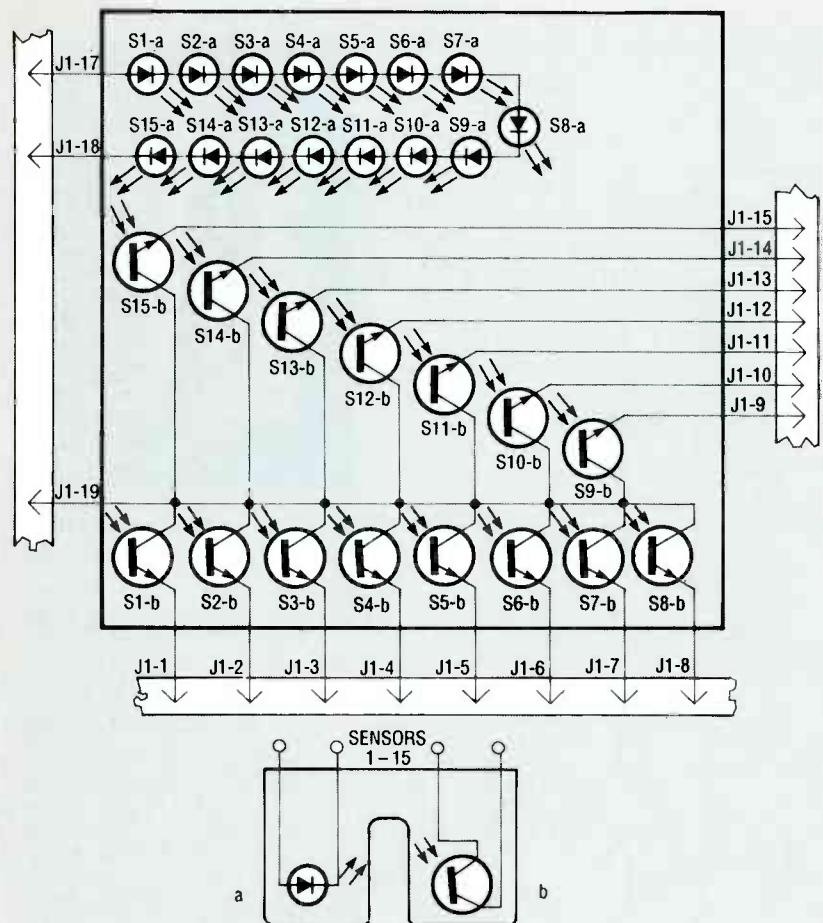


FIG. 4—WIRE THE GRASS SENSORS as shown here.

#### PARTS LIST—POWER BOARD

All resistors are  $\frac{1}{2}$ -watt, 5%, unless otherwise indicated.

R1—R10, R13—R15, R17, R18, R20—R28, R45—R49—not used

R11, R44, R50—3300 ohms

R12—680,000 ohms, 6-pin,  $\frac{1}{4}$ -watt, SIP resistor network

R16, R19, R32, R43—0.01 ohm, 5 watts

R29—150,000 ohms

R30, R31, R34, R35—270,000 ohms

R33, R36—1 megohm

R37—147,000 ohms,  $\frac{1}{4}$ -watt, 1%

R38—10,000 ohms, potentiometer

R39—82,000 ohms

R40—100,000 ohms

R41—27,000 ohms

R42—22,000 ohms

R51—R54—560,000 ohms

#### Capacitors

C1—C5, C7—C13, C16, C17—not used

C6—1000  $\mu$ F, 35 volts, axial electrolytic

C14, C15, C23—C26—0.1  $\mu$ F, 50 volts

C18, C21—100  $\mu$ F, 50 volts, radial electrolytic

C19, C20—100  $\mu$ F, 16 volts, radial electrolytic

C22—220  $\mu$ F, 16 volts, radial electrolytic

#### Semiconductors

IC1, IC2—not used

IC3—LF412N op amp

D1, D2, D11—D13, D30, D31—not used

D3, D4, D16, D17, D20—D24, D33—D38—1N4001 diode

D5, D14, D18, D19, D32—1N4148 diode

D6, D15—1N5402 diode

D7—D10—1N5256B 30-volt Zener diode

D25—D29—1N4740 10-volt Zener diode

Q1, Q2, Q12—not used

Q3—Q10, Q13, Q14—IRFZ42 MOSFET

Q11, Q15, Q16—293904 NPN transistor

#### Other components

J1—terminal strip

RY1—T90N1D12-24 relay (Potter Brumfield)

RY2—68P-111P-US-DC24 relay (Omron)

F1—3AG 30-amp fast-blow fuse

F2—2AG 0.5-amp fast-blow fuse

MOD1—Model DC2-2-24/12,  $\pm$  12-volt DC converter (Power General)

MOD2—Model DC2-2-24/15,  $\pm$  15-volt DC converter (Power General)

MOD1—Model 710, 5-volt DC converter (Power General)

#### Chassis wiring

Wire the chassis as shown in Fig. 5. Use 18-gauge stranded wire for the high-current cutting- and drive-motor connections. Secure the cable harness with tie wraps and secure the cable harness to the Lawn Ranger's chassis. Make sure all external cables from the motors, electronic control panel, bumper switch, and grass sensors are connected properly.

#### Control-system test

Remove all input power and insert the power board into J21 on the motherboard. Repeat the test procedure that was just described, except measure the DC supply voltages at edge connector J23 and J22 on the motherboard. The supply voltages should agree with the values indicated on the CPU and motor-controller board schematics (refer to **Radio-Electronics**, June and July 1990). If the values are correct, remove the input power and plug the CPU board in edge-connector J23. Reapply the +24-volt input power and recheck the voltage levels. If all is well, perform the digital-board check-out procedure outlined in the June

**Miscellaneous:** 3AG fuse holder, 2AG fuse holder, solder posts for the "E" terminals, 18-gauge solid insulated wire, 18-gauge stranded insulated wire, solder, etc.

**Note:** The following equipment can be purchased from Technical Solutions, Inc., P.O. Box 284, Damascus, MD 20872 (301-253-4933): etched and drilled PC boards for CPU Board, Motor Controller Board, Power Board, and Motherboard, \$39 each; programmed EPROM, \$39; grass sensors, \$8.99 each; hand-held manual controller kit, \$39; full kit for CPU Board, \$129 (PC board, EPROM, all parts); full kit for Motor Controller Board, \$169 (PC board and all parts); full kit for Motherboard, \$69 (PC board and all parts); Power Board kit (PC board, and all parts except DC/DC converters), \$149; Detailed drawing package, \$79; Lawn Ranger demo videotape and information package, \$19; complete electronic kit with everything mentioned above, \$777. Please add \$8.00 for S/H for all orders. Maryland residents add sales tax.

issue while the boards are plugged into the motherboard.

Now plug the motor-controller board into J22 on the motherboard. Also, plug the grass-sensor connector (J1) into the motor-controller board. Reapply the +24-volt input power to the power board.

If you have an oscilloscope, verify that a 5-volt 10-kHz square wave is found at the following points: J22-34, J1-1 through J1-15, and J22-2 through J22-16. The square wave is a gating pulse created by the CPU board which is used to turn the grass sensors on and off. The gating technique is used in order to conserve battery power and extend the life of the grass sensors. If you don't have a scope. Use an AC voltmeter to read the voltage levels at those points. The square wave should create a reading of approximately 4.5-volts AC. If the square wave is not there, you should read 0 volts on the AC voltmeter.

Now it is time to check the Pulse Width Modulator (PWM) circuitry. Plug the hand-held controller into J4 on the motor-controller board. Temporarily jumper J22-40 to ground. Turn the steering control knob (the potentiometer on the hand-held controller) counterclockwise until you see a 30-volt square wave at J22-26 (L. REV), J11-7 (L. MOTOR -), J22-27 (R. FOR), and J11-9 (R. MOTOR +). If you don't have a scope, an AC voltmeter should give you a reading of 0 to 35.5 volts AC, depending upon the knob setting. Test points J22-25 (L. FOR) and J22-28 (R. REV) should read 0 volts.

The "left wheel reverse" (L. REV) and "right wheel forward" (R. FOR) signals become active since the Lawn Ranger has been commanded to turn to the left. If the steering knob is turned clockwise, the robot circuitry will be commanded to turn to the right. That causes J22-25, J11-6, J22-28, and J11-10 to become active with the 30-volt PWM square wave, and J22-26 and J22-27 to read 0-volts DC. If the steering knob is centered, J22-25, J11-6, J22-27, and J11-9 will be enabled and a voltmeter placed at J22-28 and J22-26 will read 0 volts since the robot has been commanded to steer straight.

TABLE 1—SUPPLIERS

Manufacturer	Description	Model #	Qty
Motor Products Owosso 201 S. Delany Rd. Owosso, MI 48867 (517) 725-5151	cutting motors, 3,000 RPM @ 80 oz-in torque, 24 volt DC	LES-25A	2
RAE Corporation 5801 West Elm St. McHenry, IL 60050-7480 (800) 323-7049	drive motors, 187 RPM @ 30 in-lb torque, 24 volt DC	P-20705	2
McMaster-Carr P.O. Box 440 New Erunswick, NJ 08903-0440 (201) 329-3200	slip joint hinge (for plastic top) rubber sheet (for front of plastic top) 1/16" yoke ends ball joints	1606A41 8635K11 6071K12 6072K35	1 1 4 4
Stock Drive Products 2101 Jericho Pike New Hyde Park, NY 11040 (516) 328-0200	timing pulley timing belt	6A4-14DF0 6R4-08005	2 1
General Battery P.O. Box 1425 Reading, PA 19612-4205 (215) 378-0500	lead-acid battery	22NF	2
Tape Switch 100 Schmitt Blvd. Farmington, NY 11735 (516) 694-6312	bumper switch, 8 oz	102-BPH	1
Agri-Fab 303 W. Raymond Sullivan, IL 61951 (217) 728-4334	drive wheels drive gear	3108-148 2692-006	2 2
Colson 3700 Airport Rd. Jonesboro, AR 72401 (800) 643-5515	Caster Wheels	2-6056-45	2
Power General P.O. Box 189 Canton, MA 02021 (617) 828-6216	+ 5 volt DC + 30 volt DC ± 12 volt DC	710 DC2-2-24/ DC2-2-24/	1 1 1
Pioneer 9100 Gaither Rd. Gaithersburg, MD 20877 (301) 921-0660	E-terminals	160-2085-02-01	30
Tectni-edge 389 Liberty St. Ferry, NJ 07643-1008 (201) 641-7776	hook blade	TE-28	6

#### Control panel test

Disconnect J11-2, J11-6, J11-7, J11-9, and J11-10 on the terminal block. Ensure that the cable from the electronic control panel is connected to J5 on the CPU board and that the batteries are connected to J11-4 and J11-5 on the power board. Turn the igni-

tion key; the red power-on LED should begin to flash. This indicates that power has been switched on to all circuits. Push the STOP button. The Lawn Ranger should turn off. Check that the cutting-motor connection J11-2 is still disconnected. Turn the ignition key again and

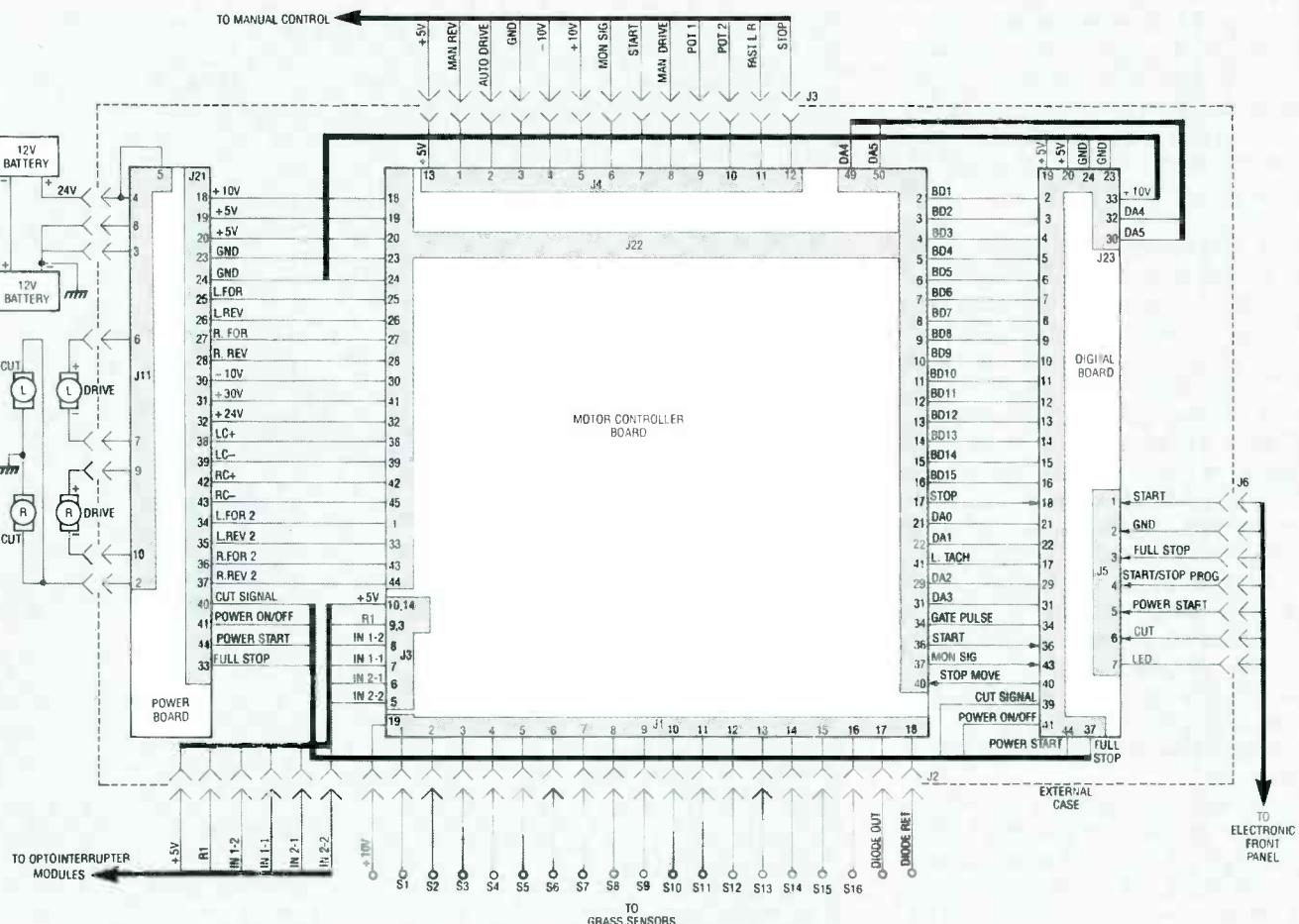


FIG. 5—WIRING DIAGRAM FOR THE CHASSIS. Use 18-gauge stranded wire for any high-current connections.

then push the CUT button. The voltage at J11-2 should now read +30-volts DC. Press the bumper switch and the Lawn Ranger should turn itself off. Turn the unit on again and push the RUN button. J23-40 (STOP MOVE) should now read +10-volts DC. Reconnect the motor wires to

J11-6, J11-7, J11-9, and J11-10 on the terminal block.

#### Drive-motor test


Make sure that the hand-held controller is connected to J4 on the motor-controller board, and that everything is connected on the terminal block J11 except for

J11-2 (cutting motors). Turn the ignition key (the power LED should be flashing), and turn the steering knob to its centered position. Squeeze the hand switch on the manual controller. Both rear drive motors and wheels should be spinning forward. Push the REVERSE button. The wheels should slowly stop and then turn in reverse. Turn the steering knob and observe the drive wheels as they change speed for steering. Release the hand switch and the Lawn Ranger will turn itself off.

#### Cutting-motor test

WITHOUT THE CUTTING BLADES ATTACHED TO THE CUTTING DISKS, reconnect the cutting motor wire to J11-2. Put the Lawn Ranger on a flat level hard surface, and keep the cutting deck area free of obstructions. With your hands away from the cutting deck area, push the cut button: the cutting disks will begin to spin. Push the STOP button: the cutting disks should stop within three seconds. If the

*continued on page 70*

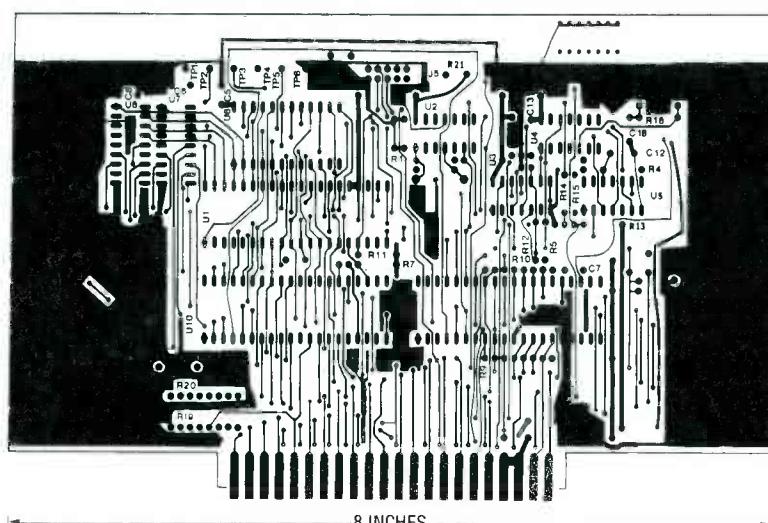

CPU BOARD COMPONENT SIDE AT HALF SIZE.

# BUILD R-E'S DIGITAL DASHBOARD

Update your dashboard with six accurate, good-looking gauges.

ROSS ORTMAN

OUR DIGITAL GAUGE STORY BEGAN IN the July issue; this month we will build all of them. Note that in all of the parts lists, except for the displays, the part number for the A/D converter (IC2) was listed incorrectly. It should be a CA3162E, as shown in the schematics—speaking of which, the captions for Figs. 4 and 6 should be reversed.

## Construction

Each digital gauge is built using two different PC boards. The display board contains the seven-segment displays along with the driver components, as well as the annunciator light bar. The main board contains the A/D converter, all input circuitry, and the 5-volt regulator.

The boards are mounted one on top of another, separated by standoffs. A typical gauge is shown in Fig. 8. With the display board facing toward you, the main board is mounted directly behind it, with its components also facing toward you. Electrical connections from board to board are made using short pieces of bare wire between matching pads on both boards. A piece of 9-conductor ribbon cable can be used instead. Once assembled, the boards can be folded apart to allow for easy testing, troubleshooting, or calibrating.

Each gauge uses either a two- or three-digit display board. Table 1 shows which boards are to be used with each gauge. When stuffing the three digit display board, begin with R1 and R2 as shown in Fig. 9, and install R3 only if the board is to be used with the voltage gauge, as R3 supplies power to the decimal point. Install DISP1–DISP3 and



LED1, keeping them flat against the board, and then install Q1–Q3. The transistors must be installed to a height just below the height of the displays. Using a good silicone sealant or other similar glue, secure a photographic legend or some other form of annunciator lettering to the LED light bar. If the two-digit display board is to be used, install everything in the same manner as the three digit board, but use only DISP1 and DISP2, and Q1 and Q2 (see Fig. 10).

Although the use of sockets is normally recommended, IC1 must be kept below the height of the seven-segment displays. Therefore, IC1 must be soldered directly to the board. Be careful when soldering the IC.

Referring to Table 1, note that the same main board is used for the voltage, oil-pressure, water-temperature, and miscellaneous temperature gauges. However, the actual components soldered to the board are different for each gauge, and not all PC pads are

used on all boards. Install only the components specified in each parts-placement diagram.

Figure 11 shows the component placement for the voltage gauge. Solder the parts to the board in smallest-to-largest order, clipping and saving the leads. The parts-placement diagram for the oil-pressure gauge is shown in Fig. 12, the water-temperature gauge in Fig. 13, and the miscellaneous temperature gauge in Fig. 14.

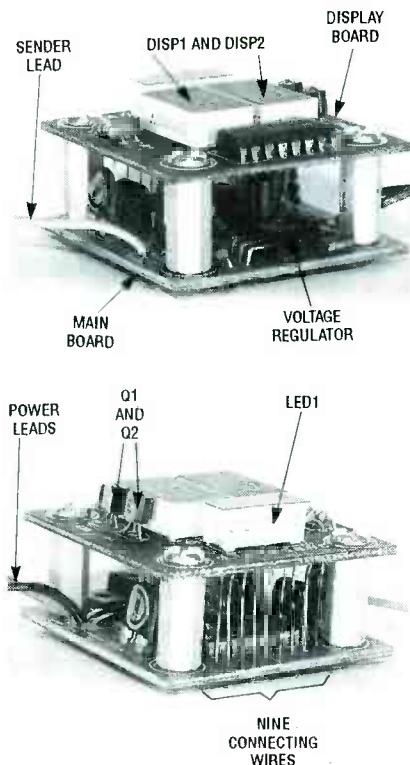


FIG. 8—THE BOARDS ARE MOUNTED one on top of another, separated with standoffs. A typical gauge is shown here.

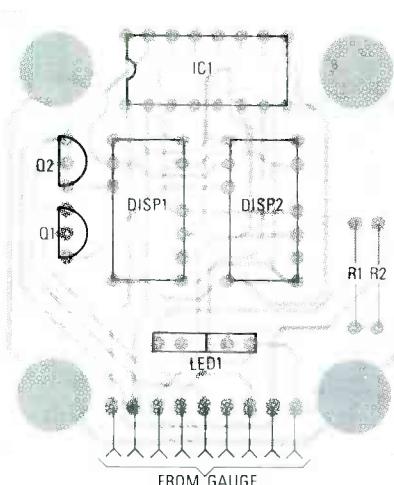


FIG. 10—THE TWO-DIGIT DISPLAY BOARD is the same as the three-digit board, but uses only DISP1 and DISP2.

The fuel gauge and vacuum gauge each has its own main board. Figure 15 shows the parts-placement diagram for the fuel gauge, and Fig. 16 for the vacuum gauge. Note that the resistors and diodes on the fuel- and vacuum-gauge main boards must be installed standing on

then need an appropriate length of wire that will run out to the actual sender, and you should crimp on a  $\frac{1}{4}$ -inch male solderless terminal to one end, and set it aside for now.

The miscellaneous temperature gauge will need both a sender wire and a ground return wire. Install the sender wire as previously described, and cut a 4" piece of black wire to be soldered into the hole just above the sender wire. A  $\frac{1}{4}$ -inch male solderless terminal goes on the end of the ground return wire.

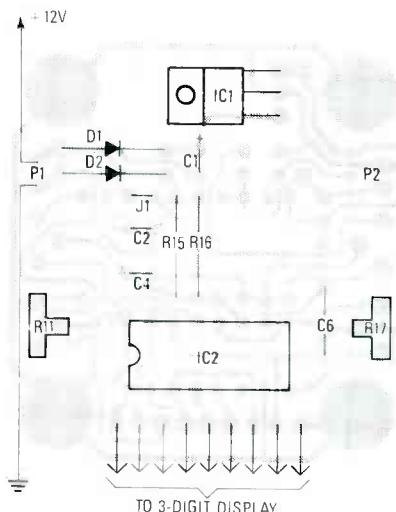


FIG. 11—VOLTAGE GAUGE parts placement. Solder the parts to the board in smallest-to-largest order, clipping and saving the leads.

TABLE 1

Digital Gauge	Main Board	Display Board
Voltmeter	43B21	43B15 3-digit
Oil Pressure	43B21	43B16 2-digit
Water Temp	43B21	43B15 3-digit
Misc Temp	43B21	43B15 3-digit
Fuel	43B20	43B16 2-digit
Vacuum	43B17	43B16 2-digit

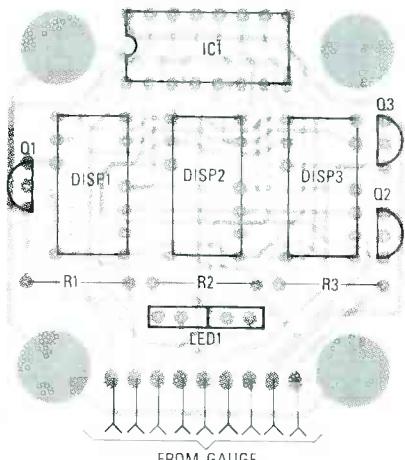


FIG. 9—WHEN STUFFING THE THREE-digit display board, install R3 only if the board is to be used with the voltage gauge. Otherwise it is not used.

end. Be sure to observe the polarity of the diodes.

After all of the components are installed on each board, solder a red wire containing a fuse holder and fuse into its respective hole. A black ground wire is soldered into the hole next to the power wire.

The oil-pressure, water-temperature, and fuel gauges all need one sender wire attached to the main board. Cut a 4-inch piece of wire and solder one end to the main-board location marked P2, "sender," and be sure to put it in the hole that is farthest from the upper-right-hand corner of the board. Next, crimp on a  $\frac{1}{4}$ -inch female solderless terminal to the other end of the wire. You will

#### VOLTAGE GAUGE

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1—R10, R12—R14—not used  
R11—10,000 ohms, PC-mounted trimmer potentiometer  
R15—100,000 ohms  
R16—1000 ohms  
R17—50,000 ohms, PC-mounted trimmer potentiometer

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic  
C2, C5—10  $\mu$ F, 35 volts, electrolytic  
C3, C4—not used  
C6—0.33  $\mu$ F, 50 volts, stacked film

#### Semiconductors

IC1—LM340T-5, 5-volt regulator  
IC2—CA3162E, A/D converter

D1, D2—1N4002 diode

**Miscellaneous:** 43B21 main PC board, 3-digit display board, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire

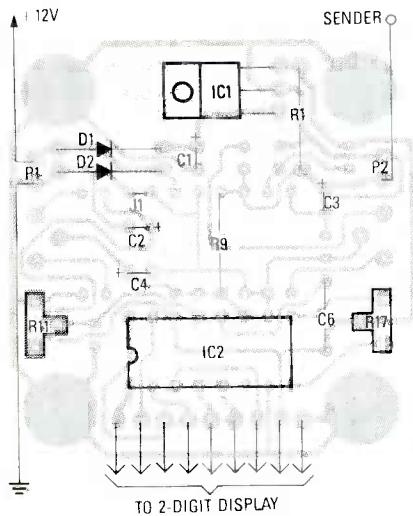


FIG. 12—OIL-PRESSURE GAUGE parts placement.

#### OIL-PRESSURE GAUGE

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1—470 ohms  
 R2—R8, R10, R12—R16—not used  
 R9—100,000 ohms  
 R11—10,000 ohms, PC-mounted trimmer potentiometer  
 R17—50,000 ohms, PC-mounted trimmer potentiometer

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic  
 C2, C3, C4—10  $\mu$ F, 35 volts, electrolytic  
 C5—not used

C6—0.33  $\mu$ F, 50 volts, stacked film  
**Semiconductors**

IC1—LM340T-5, 5-volt regulator  
 IC2—CA3136E, A/D converter  
 D1, D2—1N4002 diode

**Miscellaneous:** 43B21 main PC board, 15G5 oil-pressure sender, 2-digit display board, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire

The main boards are now ready to be connected to the display boards. The first step is to place the four standoffs between the boards and secure them with eight  $\frac{5}{16}$ -inch #6 screws. Assemble the boards with the foil side of the display board facing the component side of the main board. The holes for the board-to-board connecting wire should line up on the same edge. After the two boards are secured to each other, lay the assembly face down and begin inserting pieces of bare wire or scraps of component

leads through the holes in the main board and down into the respective holes in the display board. After a few wires have been inserted, solder the connections. Continue until all nine wires have been installed.

The temperature probe for the miscellaneous temperature gauge is constructed from the 1N4148 diode, a 10-foot length of coax cable, and a male and female crimp-on connector. On one end

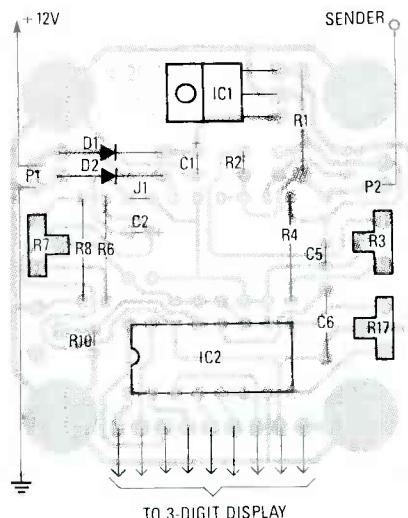


FIG. 13—WATER-TEMPERATURE gauge parts placement.

#### WATER-TEMPERATURE GAUGE

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1—100 ohms,  $\frac{1}{2}$ -watt  
 R2—430,000 ohms  
 R3, R7—10,000 ohms, PC-mounted trimmer potentiometer  
 R4, R8—22,000 ohms  
 R5, R9, R11—R16—not used  
 R6—470,000 ohms  
 R10—2200 ohms  
 R17—50,000 ohms, PC-mounted trimmer potentiometer

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic  
 C2, C5—10  $\mu$ F, 35 volts, electrolytic  
 C3, C4—not used  
 C6—0.33  $\mu$ F, 50 volts, stacked film

**Semiconductors**

D1, D2—1N4002 diode  
 IC1—LM340T-5, 5-volt regulator  
 IC2—CA3136E, A/D converter

**Miscellaneous:** 43B21 main PC board, 14G11 water-temperature sender, 3-digit display board, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire.

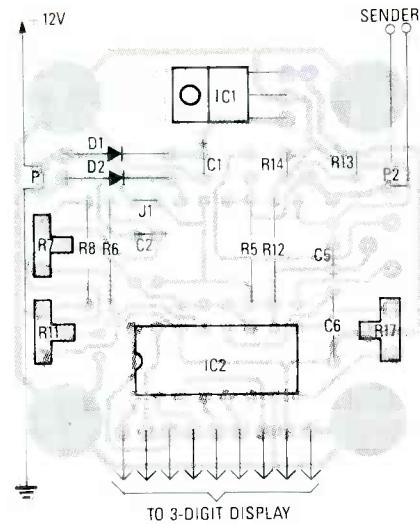


FIG. 14—MISCELLANEOUS temperature gauge parts placement.

#### MISCELLANEOUS

#### TEMPERATURE GAUGE

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1—R4, R9, R10, R15, R16—not used

R5—2200 ohms

R6—6800 ohms

R7—1000 ohms, PC-mounted trimmer potentiometer

R8—470 ohms

R11—10,000 ohms, PC-mounted trimmer potentiometer

R12—10,000 ohms

R13—1000 ohms

R14—220 ohms

R17—50,000 ohms, PC-mounted trimmer potentiometer

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic

C2, C5—10  $\mu$ F, 35 volts, electrolytic

C3, C4—not used

C6—0.33  $\mu$ F, 50 volts, stacked film

#### Semiconductors

IC1—LM340T-5, 5-volt regulator

IC2—CA3136E, A/D converter

D1, D2—1N4002 diode

**Miscellaneous:** 43B21 main PC board, 1N4148 diode for temperature probe, 3-digit display board, coax cable, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire.

of the coax cable, strip off about  $\frac{3}{4}$ -inch of the outer insulation, unbraid the outer conductor, and twist toward one side. Next, strip about  $\frac{1}{4}$ -inch of the cable's inner insulation.

Position the 1N4148 diode so that the band, or cathode, is touching the outer conductor of

the coax cable. The diode will lay right against the inner-conductor insulation. Very carefully solder both sides of the diode, the cathode side to the outer conductor and the anode side to the inner conductor. After clipping the excess lead length, coat the diode and exposed wires with a good quality epoxy or sealer. Apply several coats to ensure a good seal. Only the end of the cable with the diode is coated. On the other end of the cable, strip and separate the inner and outer conductors. Crimp the male terminal to the center conductor and the female terminal to the shield.

The solid-state vacuum sensor is mounted to the vacuum gauge by first removing the two screws near IC3 that hold the main board to the standoffs. Place the sensor bracket on the back side of the main board and align the holes on the two tabs with the board mounting holes and reinsert the two screws (see Fig. 17). Next, insert the sensor leads into the main board with the lettering on the sensor body facing away from the bracket. Insert the remaining hardware and tighten the sensor to the bracket. Do not overtighten the mounting screws as you damage the sensor. It is a good idea to only hand tighten the screws and apply a small drop of glue to keep them from coming loose. Very carefully solder the leads of the sensor to the board, working from the back side of the board. Be careful not to melt the case of the sensor with the soldering iron.

### Calibration

After the gauges are completely assembled, turn all the calibration potentiometers to the center of their rotation. Next, connect each gauge to a 12-volt DC power supply or battery. At this point, all the display digits should light as should the LED light bar.

The calibration process for all of the digital gauges begins with zeroing the A/D converter. To do that, pins 10 and 11 of the CA3162E A/D converter must be shorted together. Use a small screwdriver or jumper wire. Once connected, the display should now read zero or very close to it. Adjust the zero calibration potentiometer (see each schematic for

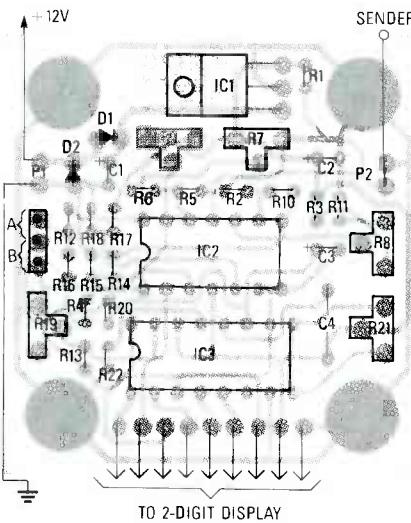


FIG. 15—PARTS-PLACEMENT DIAGRAM for the fuel gauge.

### FUEL GAUGE

**All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.**

R1—470 ohms  
 R2, R5, R10, R12, R14, R15, R16—  
 100,000 ohms  
 R3—33,000 ohms  
 R4—47,000 ohms  
 R6—1.8 megohms  
 R7, R19—100,000 ohms, PC-  
 mounted trimmer potentiometer  
 R8—10,000 ohms, PC-mounted  
 trimmer potentiometer  
 R9—200,000 ohms, PC-mounted  
 trimmer potentiometer  
 R11—2700 ohms  
 R13—8200 ohms  
 R17—22,000 ohms  
 R18—1000 ohms  
 R20—470,000 ohms  
 R21—50,000 ohms, PC-mounted  
 trimmer potentiometer  
 R22—2200 ohms

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic  
 C2, C3—10  $\mu$ F, 35 volts, electrolytic  
 C4—0.33  $\mu$ F, 50 volts, stacked film

#### Semiconductors

IC1—LM340T-5, 5-volt regulator  
 IC2—LM324, quad op-amp  
 IC3—CA3162E, A/D converter  
 D1, D2—1N4002 diode

**Miscellaneous:** 43B20 main PC board, 2-digit display board, 0.1" 3-conductor header, 2-conductor jumper, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire.

exact potentiometer number) so that the display reads "000" or "00." Then remove the jumper.

The voltage gauge is calibrated

by connecting a good quality bench voltmeter across the power supply that is used to power the gauge. Carefully adjust R11, the gain adjust potentiometer, so the reading is the same as the reading on your bench voltmeter.

The calibration process for the oil-pressure gauge requires connecting a precision 47-ohm resistor to the sensor lead and

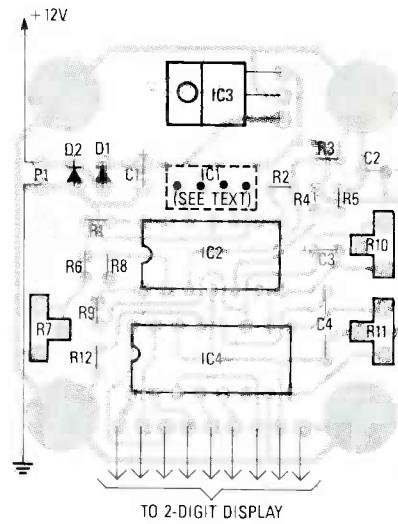


FIG. 16—PARTS-PLACEMENT DIAGRAM FOR THE vacuum gauge.

### VACUUM GAUGE

**All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.**

R1, R2—10,000 ohms  
 R3, R8—100,000 ohms  
 R4—22,000 ohms  
 R5—1000 ohms  
 R6—680,000 ohms  
 R7, R10—200,000 ohms, PC-  
 mounted trimmer potentiometer  
 R9—82,000 ohms

R11—50,000 ohms, PC-mounted  
 trimmer potentiometer

R12—2200 ohms

#### Capacitors

C1—47  $\mu$ F, 25 volts, electrolytic  
 C2, C3—10  $\mu$ F, 35 volts, electrolytic  
 C4—0.33  $\mu$ F, 50 volts, stacked film

#### Semiconductors

IC1—Sensym SX30DN vacuum sensor (Dakota Digital #69G18 includes mounting bracket)  
 IC2—LM324, quad op-amp  
 IC3—LM340T-5, 5-volt regulator  
 IC4—CA3162E, A/D converter  
 D1, D2—1N4002 diode

**Miscellaneous:** 43B17 main PC board, 2-digit display board, in-line fuse holder, 1-amp fuse, four 6-32  $\times$  0.625" standoffs, eight  $\frac{5}{16}$ -inch #6 screws, bronze or red plexiglass, mounting hardware, hookup wire.

carefully adjusting R11 so the reading is at "47." Actually, any resistor between 33 and 91 ohms can be used to calibrate the unit. Just set the display to coincide with the value of the resistor.

The water-temperature gauge is calibrated by connecting the sending unit and adjusting for freezing and boiling temperatures. First, prepare a bowl of water with several ice cubes in it, and a pot of boiling water. Place the sending unit in the boiling water with its base submerged in the water and the terminal above the water line. After waiting about a minute for the sending unit to stabilize, adjust the "high adjust" potentiometer (R7) for a reading of "212" on the display. Next, place the sending unit in the ice water using the same precautions not to let the center terminal come in contact with the water. Wait a minute for the sending unit to stabilize and adjust the "low adjust" potentiometer (R3) for a reading of "032" on the display. Repeat the high- and low-adjustment procedures until a good balance has been reached.

To calibrate the fuel gauge, you must determine the empty and full resistance of your vehicle's sender. For most Fords, it's 73 ohms empty to 10 ohms full. GM vehicles run from 0 ohms empty to 90 ohms full, and AMC, marine, and most aftermarket senders use the scale of 244 ohms full to 33 ohms empty. The calibration range of our fuel gauge will easily accept the input from virtually any brand of sending unit.

Obtain two resistor values that are very close to the empty and full resistances of the sending unit that will be used. If your system requires you to use the "A" circuit, you will begin calibrating the fuel gauge by first turning R9 fully counterclockwise. Be sure the jumper is in the "A" position. With the "empty" resistance connected to the lead wire, adjust R7 for a reading between "00" and "05." Because the gauge has a large RC circuit for averaging, allow plenty of time for the reading to settle. Next, connect the "full" resistance and adjust R9 for a reading between "95" and "99." It is usually better to have some headroom to avoid over-range and under-range conditions due to sending-unit tolerance. After

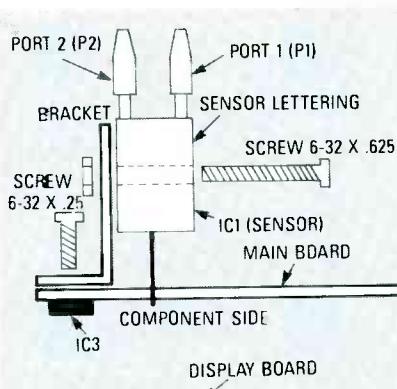


FIG. 17—PLACE THE SENSOR BRACKET on the back side of the main board and align the holes on the two tabs with the board mounting holes.

the empty and full settings are adjusted, repeat the two steps until a good balance has been reached.

If the "B" circuit is being used, begin the procedure by turning R19 fully clockwise. Connect the "empty" resistance and adjust R8 for a reading of "00" to "05" on the display. Reconnect to the "full" resistance and adjust R19 for a reading between "95" and "99." Repeat the two steps until a good balance has been obtained.

The calibration procedures for the miscellaneous temperature gauge are almost identical to the water-temperature gauge. Prepare a bowl of water with several ice cubes and a pot of boiling water. Place the temperature probe in the boiling water, wait 30 seconds for it to stabilize, and adjust R11 for a reading of "212" on the display. Next, place the sending unit in the ice water. Wait another 30 seconds for the sending unit to stabilize, and adjust the "low adjust" potentiometer (R7) for a reading of "032" on the display. Repeat the high- and low-adjustment procedures until a good balance has been reached.

The calibration process for the vacuum gauge begins by turning R10 fully clockwise and adjusting R7 for a reading of "00" on the display. That zeros the offset of the pressure/vacuum sending unit. Next, connect a piece of  $\frac{1}{64}$ -inch vacuum line to P2 (port 2) on the sending unit. The other end must go to an accurate vacuum source that you will use as a standard for full-scale calibration of the vacuum gauge. The vacuum source can be a hand-held

### 3-DIGIT DISPLAY BOARD

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1, R2—220 ohms

R3—220 ohms (voltmeter only)

#### Semiconductors

IC1—CA3161E, Display driver

DISP1—DISP3—0.43" 7-segment C.A. LED display (Panasonic LN514RA)

Q1—Q3—2N3906 PNP transistor

LED1—5- x 15-mm LED, (Panasonic LN0202RP)

### 2-DIGIT DISPLAY BOARD

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise indicated.

R1, R2—220 ohms

#### Semiconductors

IC1—CA3161E, display driver

DISP1, DISP2—0.43" 7-segment C.A. LED display (Panasonic LN514RA)

Q1, Q2—2N3906 PNP transistor

LED1—5- x 15-mm LED, (Panasonic LN0202RP)

**Note:** The following items are available from Dakota Digital, 11301 Kuhle Drive, Sioux Falls, SD 57107 (605) 332-6513: a PC-board set for each gauge (includes main PC board and display board) is \$6.95. A parts kit for each gauge (includes PC boards, components, and manual) is \$29.95. Each gauge assembled and tested is \$39.95. Stock numbers are as follows: voltage-gauge kit #2005-KIT, assembled and tested #3005-UNIT; oil-pressure gauge kit #2006-KIT, assembled and tested #3006-UNIT (order oil-pressure sender separately); water-temperature gauge kit #2007-KIT, assembled and tested #3007-UNIT (order water-temperature sender separately); miscellaneous temperature gauge kit #2008-KIT, assembled and tested #3008-UNIT; fuel-gauge kit #2009-KIT, assembled and tested #3009-UNIT; vacuum-gauge kit #2010-KIT, assembled and tested #3010-UNIT (order vacuum sensor separately). Oil-pressure sender (#15G5), \$15.50; water-temperature sender (#14G11), \$5.50; vacuum sensor (#69G18), \$19.95; RCA CA3161E driver (#69G16), \$1.95; RCA CA3162 A/D converter (#69G15), \$7.95. All orders add 4% shipping and handling (\$1.50 minimum), Visa and Mastercard accepted.


vacuum pump that has an accurate dial gauge, or you can connect the vacuum gauge and an automotive tune-up vacuum gauge to a running engine and use its reading as your standard. Once a known amount of vacuum is connected to the vacuum gauge, adjust R10 for a full-scale reading.

### Installation


A good enclosure will protect the units from shock, dirt, and shorting. The enclosure must also have a front panel that will enhance the viewing of the displays. That is especially important for bright days, where bare LED displays can be very difficult to read.

The digital gauges can be mounted by the same bolts that hold the two boards together. That allows the point of mounting to be from the front or back of the unit. For rear mounting, the screws that hold the main board to the spacers are removed. From here, additional spacers are used to mount the unit to a panel located behind the digital gauge. The length of the spacers will depend on how far the mounting panel is from the front panel. The unit can also be mounted directly to the front panel by removing the screws holding the display board to the spacers. Here again, additional spacers will be used to keep the unit away from the front panel and provide a secure mounting. If mounted from the front panel, use an attractive screw that will enhance the look of the front panel. Hex-head screws, Allen screws, or Torx screws can be used. As with any type of enclosure, you will also need to drill or cut vent holes to allow heat to escape.


For the front panel, bronze or smoked plexiglass is recommended. That material is not only durable, but it will also keep outside light from shining into the display area and allow the LED's to shine through, thus creating a more visible and readable display. Red filter plexiglass will also work well as long as only red LED's are used. The front panel should be masked to allow only the LED's and annunciator to show, thus hiding the rest of the display board. Masking can be done by taping over the area

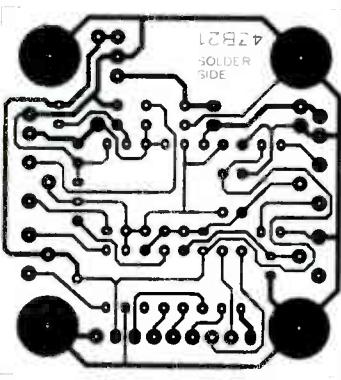

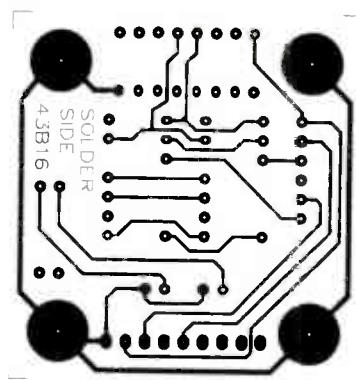
43B21  
SOLDER SIDE  
1 13/16 INCHES  
VOLTS, OIL, WATER, AND MISC. TEMP.



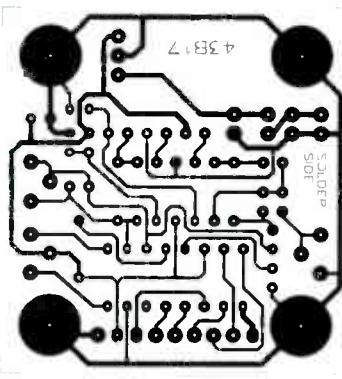
43B16  
SOLDER SIDE  
1 13/16 INCHES  
2-DIGIT DISPLAY SOLDER SIDE.



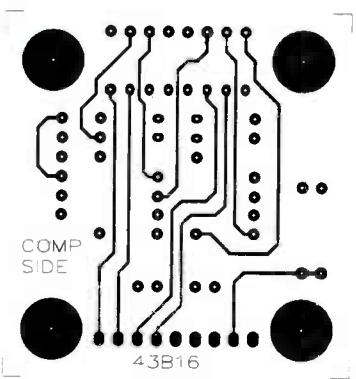
43B17  
SOLDER SIDE  
1 13/16 INCHES  
VACUUM GAUGE FOIL PATTERN.



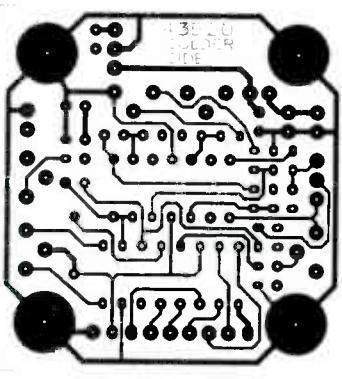
43B16  
COMP SIDE  
1 13/16 INCHES  
2-DIGIT DISPLAY COMPONENT SIDE.



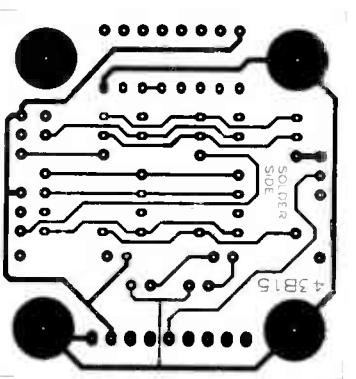
43B20  
SOLDER SIDE  
1 13/16 INCHES  
SOLDER SIDE OF THE FUEL GAUGE.



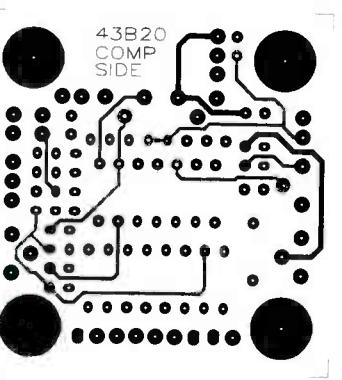43B15  
SOLDER SIDE  
1 13/16 INCHES  
3-DIGIT DISPLAY SOLDER SIDE.



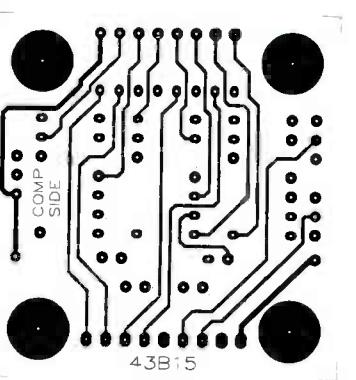43B20  
COMP SIDE  
1 13/16 INCHES  
COMPONENT SIDE OF THE FUEL GAUGE.



43B15  
COMP SIDE  
1 13/16 INCHES  
3-DIGIT DISPLAY COMPONENT SIDE.

where the displays will be located and painting the uncovered area black on the back side.

Both the oil-pressure gauge and the water-temperature gauge require sending units to be mounted to the engine. The oil-pressure sending unit mounts directly to the block of the engine. Its  $\frac{1}{8}$ -inch pipe thread fits GM motors directly while Ford motors, along with some other manufacturers using  $\frac{1}{4}$ -inch thread, will require a  $\frac{1}{4}$ - to  $\frac{1}{8}$ -inch adapter. The water-temperature sending unit is made to mount directly to the block or water pump of a Ford motor using standard  $\frac{3}{8}$ -inch pipe thread. GM motors will require a  $\frac{1}{2}$ - to  $\frac{3}{8}$ -inch adapter. Should your application be somewhat different, adapters and fittings can be obtained from your local hardware or automotive store.

You may also wish to keep your original gauge or idiot light that came factory with your car. That can be done in one of two ways. A "T" fitting can be used to mount both the original sender and the new sender. Otherwise you have to find another location that is occupied by a plug that can be replaced with the sending unit. That lets you keep the factory dashboard functions intact.

When connecting the fuel gauge to the fuel sender, the easiest method is to find the factory wiring harness connection that runs back to the fuel tank. A second option is to run a new wire. The original fuel gauge cannot be connected to the same sender that the new digital fuel gauge is using. The two will interfere with each other's readings.

When connecting any of the gauges to the motor or fuel tank, be sure that the sender has a good connection to chassis ground. Failure to properly ground the gauge or the sender will result in erratic or incorrect readings.

The temperature probe for the miscellaneous temperature gauge can be mounted in one of several ways. When monitoring air temperature, inside or out, the probe should be placed in an area where a good average temperature exists. Inside, that may be under the dash, away from any heating or cooling vents and

out of any sunlight. Outside, under the front grill area of the car will provide the most accurate point as it is out of the sun and not affected too much by engine heat.

If the goal is to measure the temperature of the transmission fluid, engine oil, differential, or coolant, mount the sensor in a manner that maintains good thermal contact to the outer plate of the item being monitored. Heat sink compound should also be used to ensure good thermal contact. For example, when monitoring oil temperature, mount the sensor to the bottom, back side of the oil pan, where there will be very little air movement to cool the sensor.

Remove one of the oil pan bolts and manufacture a bracket that will hold the probe to the oil pan. This can be a simple piece of aluminum or thin steel cut in such a way so when the oil pan bolt is inserted through the bracket and into the block, the sensor will be lightly compressed between the bracket and the oil pan. Do not make it too tight, as excessive pressure on the LN4148 diode will break its glass housing. You may want to hold the sensor by the cable near the diode to be safe. Apply heat sink compound to the sensor and the oil pan where contact is to be made. Be sure the oil pan is free of dirt. Then route the coax cable up through the firewall to the location of the gauge.

The vacuum gauge is connected to the intake manifold via  $\frac{7}{64}$ -inch vacuum hose. Run the hose through a location in the firewall and to the intake manifold, or vacuum "T" usually located near the rear of the engine compartment. Connect the vacuum hose to P2 (port 2) on the sending unit.

Once a suitable panel or enclosure has been constructed, and the gauges mounted to it, install the assembly into the vehicle and connect the power to a source that is on only when the ignition key is in the "on" position. Be sure to secure any hook-up wires so they will not present a hazard to you or your vehicle. Your new digital gauge system is now ready to display important vehicle information and keep you up to date on its condition. **R-E**

# SAME DAY SHIPPING

## 3-1/2 Digit Pocket DMM

- Reading up to 450V or 32MΩ
- Auto/manual ranging
- 32-segment bar graph
- Auto power-off
- Low battery indicator
- Continuity beeper
- Diode test
- Includes test leads, batteries and case

HMC PRICED!

**\$45**




RE-3060

## Xcelite Compact Tool Set

- Interchangeable blades
- 4 screwdriver sizes
- 7 nutdriver sizes
- Handle and extension
- Snap-shut plastic case

HMC PRICED!

**\$35**

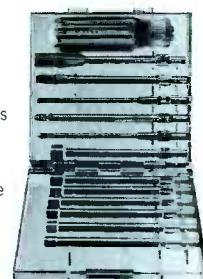

RE-99PS50

## 6-Outlet Surge Suppressor

- Protects against spikes, surges, and line noise
- 15-amp circuit breaker
- Lighted power switch
- "Protected" LED indicator
- 6-foot power cord

HMC PRICED!

**\$39**



RE-TR6

## Refillable Butane Iron

- Cordless, flameless
- Flint igniter in cap
- Temperature adjustable
- 90-minutes of continuous use
- Tip included



RE-PBI

**\$26**

HMC PRICED!



Send for your...

## FREE CATALOG!

Products to Design, Assemble, Test and Repair "Electronics"



TO ORDER, CALL

**1 800 482-4440**  
in MA (617) 821-1870

Prices good until October 31, 1990.

**HMC**  
HUB Material Company

33 Springdale Avenue Canton, MA 02021

CIRCLE 188 ON FREE INFORMATION CARD

# INTRODUCTION TO MICROWAVE TECHNOLOGY

LAST MONTH, WE EXAMINED SOME basic concepts of the electromagnetic spectrum, some basic parameters of electromagnetic waves (such as amplitude, frequency, period, and wavelength), and some early methods of RF generation, including the spark-gap generator, and the Barkhausen-Kurz Oscillator or BKO. This month, we'll examine some early microwave RF sources in greater depth, to try and appreciate the problems faced by early designers.

In the early days of radio, the term "microwave" meant anything above about 100 MHz. The region above modern CB was usually called "UHF," which an early textbook referred to jokingly as "unbelievably high frequen-

cies." Many recent European receivers mark the FM band (88–108 MHz) with a "U," after the German "ultra kurz welle" (ultra-short waves). Such early designations were indicative of the problems of generating RF power at such frequencies because of device limitations.

One of the earliest problems inhibiting full use of the RF spectrum was the inability to generate enough RF power at frequencies of value. For many years generating RF signals at useful power levels was limited to the Medium-Frequency (MF) band. Various problems limited devices then in common use. But from 1920–45, advantage was taken of inherent limitations of vacuum tubes to enable the generation of

RF power at higher frequencies.

The definition of what constitutes high frequencies has varied according to the difficulty of generating RF power at those ranges. Until the early-1920's, when hams opened the HF shortwave region (3–30 MHz), commercial radio used the MF range with:  $\lambda < 200$  m/cyc, or:  $f < 1.5$  MHz. The technology of that period worked well at MF, but its effectiveness dropped rapidly with increased frequency.

Even in the early days of radio, higher frequencies were examined. Early radio pioneer Heinrich Hertz, in 1887–88, used 31.3 MHz–1.25 GHz for short range investigations across his lab, and 1.25 GHz is a microwave frequency even now! Guglielmo Marconi used 500 MHz for short-range experiments, but switched to MF when he found that lower frequencies yielded propagation over greater distances.

*Learn about early RF oscillators  
in our continuing series on  
microwave circuits*

JOSEPH J. CARR

Besides the fact that RF was easier to generate in this region, the detectors of that period ("Branly coherers," after Prof. Edouard Branly) were far more sensitive in the MF range. In addition, experimenters of the period also ran into some realities of electromagnetic propagation. On December 12, 1901 Marconi and his coworkers achieved the first confirmed transatlantic transmission, of 313 kHz from Poldhu, Great Britain, to Marconi's receiver at St. Johns, Newfoundland, Canada. A transmitter power of 10 kW was used to achieve that feat.

Vacuum tubes made possible operation on yet higher frequencies. Commercial, military and amateur radio moved to the HF shortwave region in the mid-1920's. Difficulties with devices above 25 MHz caused the region above modern CB to be called "ultra-high frequencies" (UHF). Today, "UHF" designates 300–900 MHz. Advances in vacuum tubes during World War II allowed practical use of up to 450 MHz, so the UHF definition was changed.

The three traditional methods for generating RF energy were spark gaps, Alexanderson alternators, and vacuum tubes.

### Spark gap generators

An electric arc produces tremendous energy at both harmonic and non-harmonic spurious frequencies. For example, any AM receiver will pick up noise from lightning. Similarly, arcs from motors or ignition systems also produce large amounts of wide-bandwidth RF noise. Figure 1 shows a simple spark-gap RF power generator. Until 1938, when they were declared illegal, circuits like these were used to make crude radio transmitters. Some early experimenters stole

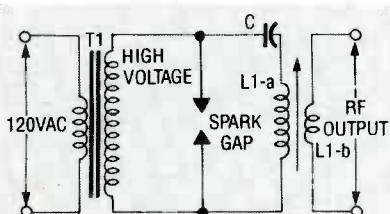


FIG. 1—A SIMPLE SPARK-GAP RF POWER GENERATOR used as a crude transmitter; they were declared illegal in 1938.

Ford Model-A ignition coils from their family car to make spark-gap transmitters. Today, spark-gap RF generators are used for medical electrocautery.

The power for a spark-gap generator comes from a high-voltage AC power transformer, T1. The secondary voltage is high enough to ionize the air between the spark gap electrodes. A series-resonant LC tank (L1-a-C1) picks off the RF energy. Unfortunately, a spark gap is very wideband; an 800-kHz spark-gap generator actually produces significant power levels from 10–3000 kHz, and weak harmonics up to the microwave range. A secondary is wound onto L1-a for RF output.

Figure 2 shows a method used in 1930 to generate microwave RF up to 75 GHz. A spark gap goes inside a cavity acting as a resonant tank. A coupling loop picks off the RF output, and delivers it to the load. Unfortunately, spark gaps are very inefficient. Since their RF power has wide bandwidth, only a small amount is available over any narrow band approximating a single

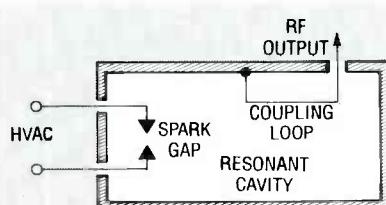


FIG. 2—A SPARK-GAP TRANSMITTER USED IN THE 1930's. The spark gap and cavity are a resonant tank, and the coupling loop picks off the RF. However, bandwidth is very wide, with only a small amount of power per frequency; efficiency is under 1% at 75 GHz.

frequency. Also, as frequency increases, the power drops dramatically. At 75 GHz, the efficiency is far below 1%, since the majority of the RF power is outside the microwave range.

### Alexanderson alternators

The two main problems with spark-gap transmitters are limited efficiency and spectral purity. The Alexanderson alternator attempted to overcome those problems; it was identical, except for the use of rectifiers, to the alternator on modern cars. A magnet would rotate inside a coil. The frequency of the AC generated by

the stator is related to the number of poles on the magnet, the number of coil pairs in the stator, and the speed of rotation. If a magnet were spun at 1 rev/s inside a two-pole stator, a 1-Hz signal would be generated. By increasing the number of magnets, the number of stator poles, and the rotation speed, frequencies up to 1 MHz could be generated, although most alternators produced 30–200 kHz.

The alternators in communications use an electromagnet to generate RF. Telegraphy was possible, by interrupting the coil current with a telegraph key. In 1916, engineers from the Naval Research Lab (NRL), Washington, D.C., used the U.S. Navy radio station at Arlington, VA (call sign NAA), to produce the world's first voice transmission over radio. NAA, also known as Radio Arlington, had a 100-kW, 113-kHz alternator, and dominated voice radio before World War I. NAA engineers varied the electromagnet current using a voice signal, to create AM. Because of its low operating frequency, the Alexanderson alternator was of limited microwave value.

### Vacuum-tube oscillators

Although this series is about microwave devices, we must take a brief look at vacuum tubes, in order to understand the limitations and problems of microwave oscillators. In 1885, Thomas A. Edison noted the Edison effect, that a positively charged electrode inside an evacuated glass bulb drew current. In 1905, Alexander Fleming of Great Britain used that effect to make the diode rectifier, using a heated cathode to emit electrons, and an anode to collect them. In 1907, Lee De Forest of the U.S. inserted a grid to modulate the anode current, to make the triode.

Figure 3 shows the basic triode, with cathode, grid, and anode. In some models, the cathode is a direct heater, while here it's a hollow tube with indirect filament. In either case, the object is to heat the cathode until electrons boil off into the surrounding volume; a process called thermionic emission. This electron cloud is called space charge. A positive anode or plate

placed nearby attracts these electrons, creating anode current.

The porous grid is between cathode and anode. If the grid is negatively biased, it can control anode current. If negative enough, the anode current goes to zero. When  $V_i$  is superposed on  $V_G$ , the total grid voltage is  $V_i + V_G$ . If  $V_i$  is negative, the total bias increases, so the anode current decreases. Conversely, when  $V_i$  is positive the total bias decreases, so the anode current increases. Thus,  $V_i$  modulates the anode current.

Early vacuum tubes were quite limited in bandwidth; devices that operated above 15 MHz were rare. The primary problems were lead inductance, interelectrode

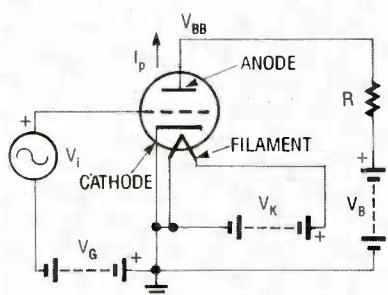


FIG. 3—THE TRIODE, WITH CATHODE, GRID, AND ANODE. The cathode thermionically emits space charge electrons, attracted to the anode as current. Total grid voltage is  $V_i + V_G$ , and  $V_i$  modulates anode current. If  $V_i$  is negative, bias increases and anode current decreases, and vice-versa.

capacitance, Gain-Bandwidth Product (GBP), transit time/angle, and interelectrode spacing. Making the electrodes smaller decreases capacitance, but severely limits operating power, and was deemed useless. Moving the elements further apart also decreases capacitance, but increases transit time. Transit time/angle problems occur when the time required for electrons to pass from cathode to anode approximates the signal period.

### The Barkhausen-Kurz Oscillators

An early solution to the bandwidth problem in vacuum tubes was to exploit transit time, as in the Barkhausen-Kurz Oscillator or BKO. The BKO in Fig. 4-a used a triode with reversed anode bias. The BKO had a cylindrical anode, since flat or rectangular

anodes wouldn't work in BKO mode. Both anode and cathode were negative, while the grid was positive.

Figure 4-b shows BKO operation. Cathode electrons were attracted by the positive grid toward the anode, but its negative bias repelled them. Since the cathode was negative, a similar effect occurred there. Electrons traveled circularly about the grid, with the operating frequency set by the rotation rate. Output power was taken from the grid, a principal limitation of the BKO. The small grid size limited RF power, so it normally ran white hot.

### Other approaches

Later devices used magnetic fields to control current, instead of the electric field of the BKO. These included the magnetron, an "M-type" crossed-field device invented by Hull in 1921, the par-

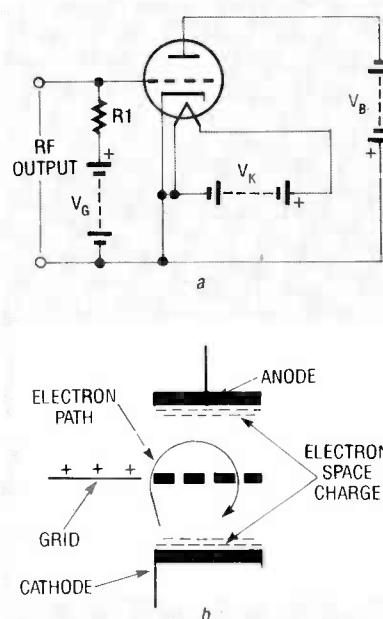


FIG. 4—THE BARKHAUSEN-KURZ O SCILLATOR (BKO) used transit time to increase bandwidth. In (a), both cathode and anode are negative; the grid is positive. In (b), cathode electrons are alternately attracted toward and repelled from the anode, traveling circularly about the grid with rotation rate setting operating frequency. The small grid produced only limited RF output power, so it ran white hot.

allel-field "O-type" device invented by both the Heil's in 1935, and the Varian brothers in 1939. Next month, we'll examine the magnetron in depth.

R-E

## LAWN RANGER

continued from page 58

cutting disks take too long to come up to speed, adjust R38 on the power board. If they take too long to stop, check relay RY2 and resistor R43. Disconnect J11-2.

### Automatic guidance test


By blocking grass sensors with your fingers or electrical tape, you can simulate a grass border that the Lawn Ranger can follow. As you block different grass sensors, you can verify that the motor controller is working properly by observing the drive wheels as they change in both speed and direction.

Before turning the Lawn Ranger on, ensure that the cutting blades and disks are disconnected. Place the rear end of the unit up on blocks so the wheels do not touch the ground. Ensure that the grass sensors are not blocked by grass or other objects and that the manual controller is disconnected. Turn the ignition key clockwise and push the START button. The right wheel should spin clockwise and the left wheel should spin counter clockwise. The Lawn Ranger will initiate a left turn because it cannot detect tall grass. If it were allowed to move on the ground, you would see it steer to the left in a counter-clockwise circle. It would continue to move in a circle searching for tall grass for approximately 6 seconds and then turn itself off.

Now it is time to test the full range of the steering. Block sensors 1–8 with electrical tape. Adjust potentiometer R203 as described in the July issue. Now, Adjust R201 and R202 until both wheels spin at the same rate. You can calculate wheel speed by counting the number of revolutions that each wheel performs within one minute (rpm's). This test validates that the Lawn Ranger steers straight ahead when the grass border is in the center of the grass-sensor assembly (between sensors 8 and 9).

Clear all the grass sensors so they are free of obstructions; the Lawn Ranger should return to its left turn mode. Now, block sensor 1, then 2, then 3, and so on, until

continued on page 79

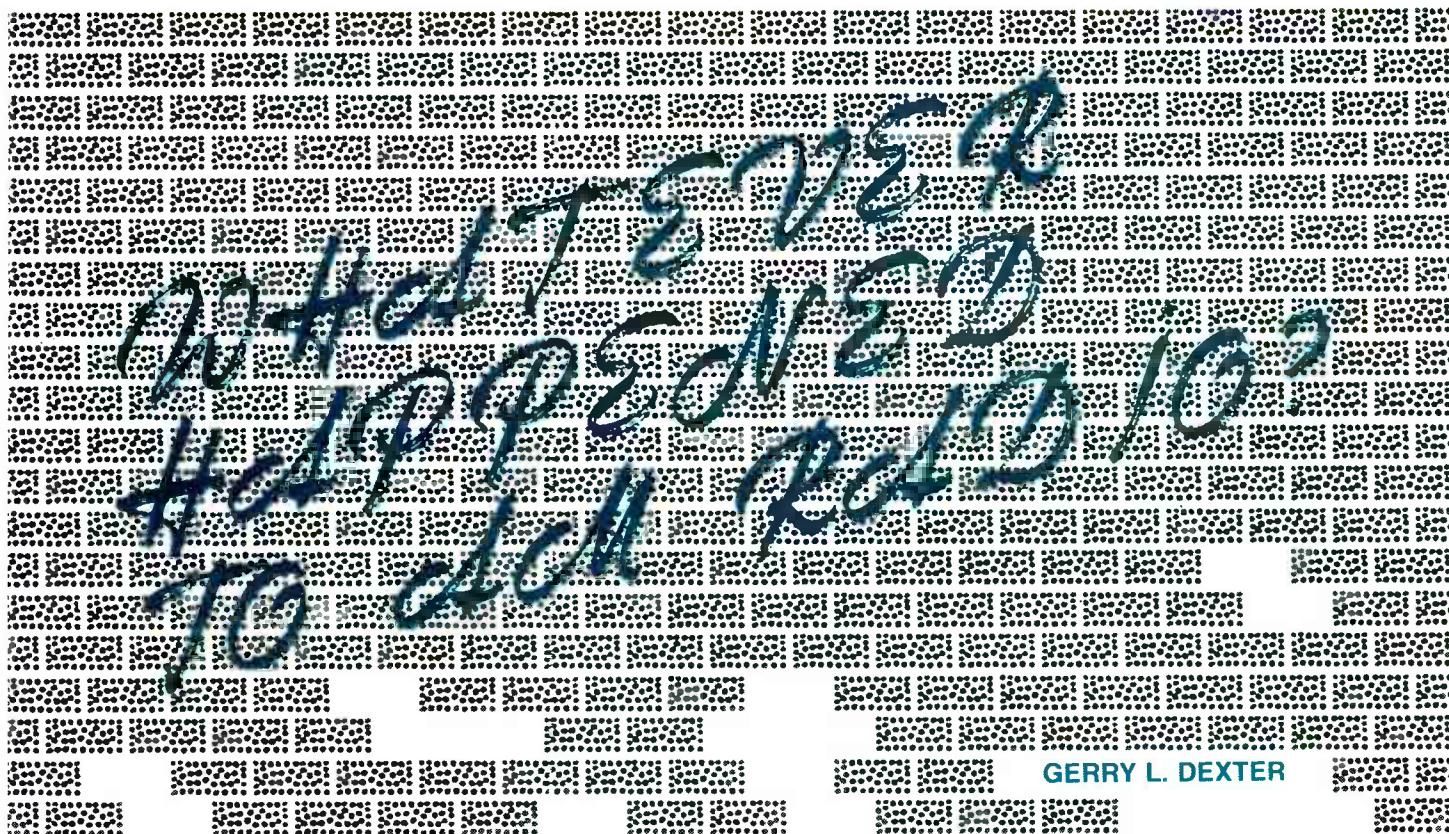

GERRY L. DEXTER

## AM radio is seeing hard times.

MOLLY WOULD CRY OUT, "NO, NO, McGee—not the front closet!" But Fibber McGee would open the door anyway, and there'd follow several seconds of crashes, bangs, thumps, and thuds as Fibber's famous overstuffed closet emptied out. The radio audience loved that, as well as the show and its characters.

Fibber McGee and Molly were part of the "Golden Age" of radio in the 1930's, 1940's, and early 1950's, when amplitude modulation (AM) was king, and Jack Armstrong, Gangbusters, Gabreal Heater, the Lux Radio Theater, Edward R. Murrow, and hundreds of other shows and personalities ruled the airways. It was even bigger then than TV is now, because there was really no competition except movies and newspapers. Now, those days are gone and AM is seeing hard times. The present AM is a far cry from a decade ago.

### The trouble with AM

Surprisingly, AM's problems are only partially due to TV. When

TV skyrocketed in the 1950's, AM radio actually prospered, despite a period when it took some blows. Once the Top 40 arose, with repetitive song cycles, energetic disc jockeys, time, temperature, and contests, AM found its fortunes again. Actually, most of AM's troubles come from frequency modulation (FM) competition. AM and FM may both be radio, but there are some important differences in the way information is transmitted.

Both AM and FM transmitters radiate "carrier" wave RF modulated to contain transmitted information. In AM, the carrier wave amplitude is proportional to the audio amplitude, but the carrier frequency is constant. Figure 1 shows the components of an amplitude modulated waveform; (a) is the carrier RF signal, (b) is the audio-modulation signal and (c) shows the amplitude-modulated carrier signal. In FM, the carrier amplitude is constant, while the carrier frequency varies in proportion to the audio signal rate. Figure 2-a shows an

FM audio signal, and Fig. 2-b is the frequency-modulated carrier.

The AM band is much lower in the RF spectrum than FM: AM spans 535–1605 kHz, while FM spans 88–108 MHz. AM channels are 10 kHz wide and FM channels are 200 kHz wide, so you would be able to squeeze only about 5.5 FM channels onto the entire AM band. There are 107 AM channels presently available, and 100 on FM.

FM signals normally don't propagate beyond 75 miles, which is considered the line-of-sight limit and is within the Very High Frequency (VHF) range. The VHF range used by broadcasters is subject to signal scattering from obstructions such as building edges or hills and is prone to fading in and out under certain conditions. In contrast, AM signals often travel very great distances. The difference between AM and FM signal propagation is due to the great difference in their carrier frequencies, not their modulation differences.

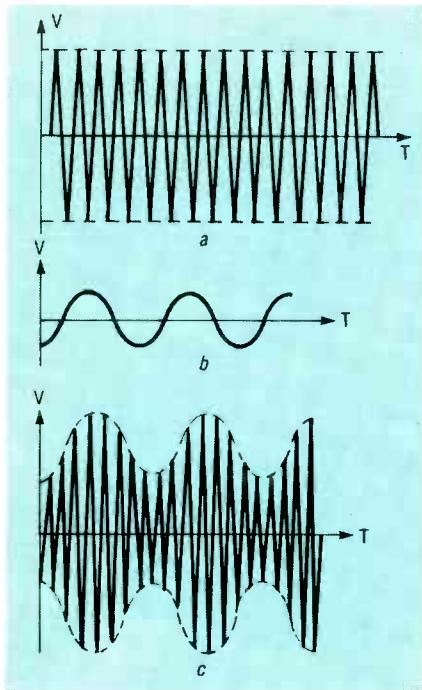


FIG. 1—AM SIGNAL COMPONENTS; (a) is the carrier signal, (b) is the modulating signal, and (c) is the amplitude modulated signal at a constant frequency.

Two characteristics of FM operation are responsible for its high fidelity response: wide bandwidth transmission and constant carrier amplitude. The wide bandwidth allows a wider range of audio frequencies to be processed, up to 15 kHz for FM, compared to only 5 kHz for AM. The source of most noise in AM transmission and reception is from atmospheric or static noise resulting from lightning, fluorescent device radiation, and electronic machinery, especially during hot weather. AM transmission is, therefore, amplitude-sensitive. By maintaining a constant carrier amplitude in FM, static noise can virtually be eliminated. FM was originally used for stereo because of its high fidelity.

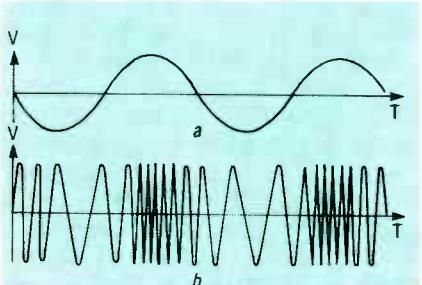


FIG. 2—HERE IS AN FM SIGNAL; (a) is the audio modulating signal and (b) is the frequency modulated carrier signal at a constant amplitude.

## FM popularity

After World War II, AM stations began adding FM. There weren't many FM stations back then, so FM programming consisted primarily of classical music to take advantage of the high fidelity; otherwise they just duplicated AM programming. FM grew slowly, because consumer-electronics manufacturers and the public were mesmerized by TV. Some AM stations gave up on FM, relinquishing their FCC FM station licenses. They regretted it later, when FM became prominent but, by then, most FM frequency allocations were gone.

Several factors contributed to the prominence of FM. Stereo arrived in the early 1960's, becoming the foundation of further success. The availability of FM stereo receivers, component systems, AM/FM portables, and AM/FM car stereos followed. The FCC eventually ruled that most combined AM/FM stations had to program AM and FM broadcasts separately, forcing broadcasters to create competitive FM programming. There then arose a couple of generations of listeners who used radio mainly for music, not comedy, drama, or news.

The growth of FM over AM in the last 16 years has been dramatic. In 1972, AM had 75% of the radio audience; that was reversed by 1988. FM is considered the stereo music medium, which is what most listeners want. However, not all AM is in trouble: large markets capable of developing major audience shares command sale prices of tens of millions of dollars. However, the average AM station is far less glamorous.

## AM's battle against FM

Most mid-size markets have a couple of AM stations at the bottom of the ratings. The top two or three in a market get by on community service, creative programming, good management, and poor competition. Most AM stations that are considered to be on shaky grounds are those that broadcast daytime-only stations, especially those that have no FM companion station, and aren't part of a broadcasting group under one owner. They sink or swim on their own and most drown; about 65% lose money.

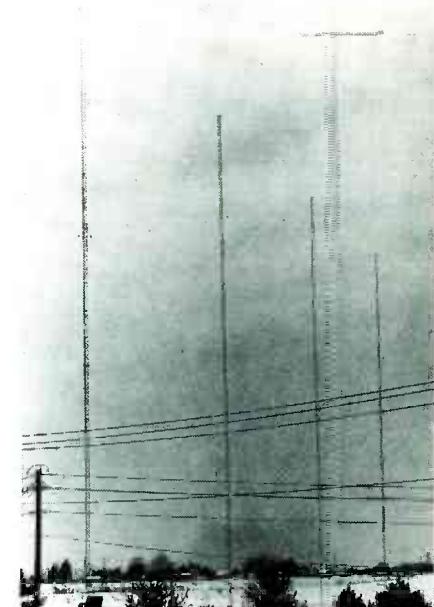


FIG. 3—AM RADIO TRANSMITTING TOWERS aren't the beacons of comedy and drama they were in the good old days.

The FCC helped by giving most daytime stations post-sunset broadcast authorizations, but the rules often dictate transmitter powers as low as 1–50 watts! Even for a small-town station, that's not enough power to provide the needed coverage, especially if there's competition. AM's crowded frequencies are another problem, especially for night listening when signals propagate farther. Interference obviously turns listeners away. Many AM channels are a jumble of noise at night, with half a dozen stations fighting to be heard and none succeeding.

In the 1960's and most of the 1970's, AM rode high, and many broadcasters and investors wanted part of the market. Hundreds of new stations began during that period, crowding the AM dial. Many towns of 20,000 people have two or three AM stations competing for large FM audiences. The economic downturn of the late 1970's and early 80's hurt many AM stations, especially those in rust and farm belts, which suffered most from the sluggish economy.

AM radio generally gets a small slice of local advertising, with the larger chunk going to FM. TV, cable, newspaper, shopping, and billboard competition is very heavy. Falling revenues mean less money for promotional or inno-

vative program changes, or high-quality air personalities that might hold an audience. In 1988, AM and FM each had about 5,000 commercial stations: AM stations did \$1.7-\$1.9 billion of business, while FM stations did \$4.8-\$5 billion. FM's early lack of commercial success helped draw listeners because of fewer commercials. And, while FM stations do air more commercials today, they still air about half as many as AM stations—they just charge more.

### AM solutions

AM station managers know the problems, and try to find solutions. They know audiences don't see AM as a music medium. A National Association of Broadcasters survey on public attitudes toward AM found that 75% of respondents want good programming with good technical sound. The survey showed both a strong preference for news-talk-information on AM, and an older audience. Some stations try drastic cures. "Narrowcasting" or "niche programming" describes programming aimed at very specific audiences:

- In New York, WFAN (once WNBC, flagship station of the NBC network) runs an all-sports format; play-by-play, sports talk, and news.
- In Los Angeles, with 100 competing stations, KMNY devotes itself to money, and how to have more of it, syndicating some programs to other stations.
- All-kiddie radio by KPAL, Little Rock, Arkansas, includes children's music, stories, and school news reported by children.
- In Florida, WWNN broadcasts self-help and positive-thinking radio programs.
- Several stations now use single-theme approaches to music. There are all-Elvis stations, and at least one playing only Beatles music.

Whether these formats will last is yet to be seen. For example, all-weather and traffic formats have been tried and abandoned in Los Angeles and Minneapolis. AM stations can also inexpensively subscribe to satellite program services. Services with a "big city" feel have proven successful for smaller stations, especially when such services can mean

### BETTER RECEIVERS FOR BETTER SOUND

One of the main reasons why AM has taken a back seat to FM is because of AM's inherently poor fidelity. The National Association of Broadcasters (NAB) is trying to do something about that. Specifically, the NAB is trying to convince electronic manufacturers to incorporate three design improvements into their AM receivers. Those improvements, which are in accordance with the National Radio Systems Committee (NRSC) suggested guidelines are: the ability to receive frequencies within the expanded band, AM stereo compatibility and, de-emphasis circuitry.


Manufacturers will be able to make units that receive transmitted signals in the expanded bandwidth fairly easily and inexpensively. However, they are much more reluctant to jump into mass production of AM stereo receivers—adapting current product designs to incorporate stereo reception can be an expensive proposition.

Another stumbling block that manufacturers face is that there are two mutually incompatible systems on the market. Motorola's C-Quam and Kahn Communications are two AM stereo systems that are currently in use by broadcasters today. C-Quam is used by approximately 500 broadcasters, while only about 100 broadcasters use the Kahn System. The only commercially available AM stereo receivers on the market are compatible with Motorola's C-Quam transmitter design. Sony, Sanyo and Sansui previously made IC stereo detectors that were compatible with both the C-Quam and Kahn transmission systems, and about 20 such receiver models were once produced by those companies. However, those chips and receivers are no longer in production because of various legal battles between Kahn and Motorola. We may again see some Kahn-compatible receivers after the legal dispute is over.

There are still many varied opinions in the broadcasting field about which system is better. Broadcast engineers profess the advantages of each system, and may choose one system over another because of their specific transmission needs, or personal preferences. When AM stereo was first introduced years ago, FCC's "let the marketplace decide" attitude sealed the fate of AM stereo by causing a relentless battle between various competing systems. Now, more than eight years after the introduction of AM stereo, the two survivors, Kahn and Motorola, are still battling it out. The FCC's lack of direction during the early stages has hindered the acceptance of AM stereo, and has hurt not only electronic manufacturers, but consumers, too.

savings through staff cutbacks, or when staff can be freed to develop more local and major news programming. It's easy to insert local news, sports, weather, and other features.

Frequency boosting, or pre-emphasis is a design modification that the NRSC is recommending to reduce noise transmission for higher fidelity. Within the time interval that an AM signal carrier is transmitted and received, the carrier signal may be affected by noise. The greatest impact that noise has on the carrier is changing the amplitude. FM is much less subject to that type of noise distortion because it is transmitted at a constant amplitude. The sound volume of an AM detector is proportional to the carrier amplitude. If the noise signals cause a much larger amplitude change than the unwanted noise amplitude deviations, during transmission and reception, then the noise will not be noticeable. That relationship is called the signal-to-noise ratio—the higher the value, the better the sound quality.

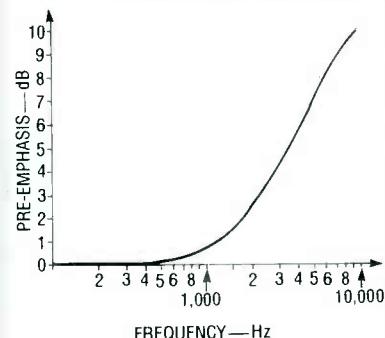

**PRE-EMPHASIS CHARACTERISTIC suggested by the NRSC for AM transmission.**

In a pre-emphasis circuit, a portion of the transmitted signal is boosted, or pre-emphasized, causing a larger carrier amplitude deviation. The receiver conversely de-emphasizes, or attenuates that signal. The overall effect is to increase the signal-to-noise ratio. The accompanying figure shows the 75  $\mu$ s pre-emphasis characteristic suggested for use.

The NAB is working closely with the electronic industry to develop a certification for improved AM receiver designs which follow NRSC guidelines. One idea is to authorize the use of a quality mark that will identify receivers that comply with NRSC standards. Broadcasters are also receptive to the idea of promoting the new design standards in AM receivers. Clearly, AM stereo compatibility and the efforts to improve AM sound quality are complicated issues which are still being worked out. Perhaps with the cooperation of the electronic industry, broadcasters, and the FCC, AM will continue as a viable communications medium.

Not long ago, AM operators thought the answer was AM stereo, but it's been a disappointing panacea. Most broadcast experts feel that the FCC ruined things by refusing to pick a specific AM



FIG. 4—TALK SHOWS, OFTEN WITH LIVE GUESTS, are a programming staple of stations of all sizes.



FIG. 5—WELL-RUN SMALL-TOWN STATIONS with a solid history are likely to continue a successful tradition.

stereo approach from the half-dozen stations competing for FCC approval. Instead, the FCC let the market decide, and so far it hasn't. In the last seven years, AM stereo has barely affected the minds of broadcasters or the public.

Two AM stereo systems are still competing: Motorola's C-Quam, and the system developed by Kahn Communications. Broadcasters haven't reached a consensus on which should be standard. Only 10% of AM stations now have stereo. The audience percentage that use AM stereo gear is still low, and there's

no real impetus to switch, which can cost up to \$100,000—half a year's income or more for some small stations.

#### AM's expanded band

An important change affecting AM broadcasters as well as radio receiver manufacturers is that of AM frequency band expansion, or "AM improvement." In 1988, the World Administrative Radio Conference agreed to expand the AM radio upper bound from 1600 kHz to 1700 kHz, effective July 1, 1990. Ten additional channel slots will be available as a result of the expansion. With 20 to 30

stations per channel, a total of approximately 200 to 300 new AM stations in the U.S. could conceivably occupy the expanded band.

The primary objective of the FCC in authorizing transmission in the upper range is to unclutter the existing band and reduce the overall levels of broadcast interference. Stations who are considered as causing the most interference will be given highest priority by the FCC for transmission in the upper band. Some night-time broadcasters are considered to be the "worst offenders," and the FCC is hoping that most of those stations will voluntarily migrate into the upper band. The advantage of changing into the upper band is that the adjacent stations will experience less interference, and the listener will receive a much clearer broadcast.

After a transition period, the FCC will make new AM stations available for new licensees, so that broadcasters can make full use of the entire expanded band. Stations who are licensed to broadcast within the new upper range will be able to transmit full-time, with power restrictions of minimum 1 kilowatts after sunset and 10 kilowatts during daylight hours.

Many problems, however, still need to be solved. Existing services, such as the Traveler's Information Stations (TIS) will need to move or—because the TIS are considered by the FCC to be secondary broadcasters—may have to relinquish their transmitting rights.

So, can we see the future of AM? Clearly, it'll hardly vanish from your dial. Most stations will likely solve problems by new programming, promotion, management, and technology. Some may not have their prior success, having to live with less. But those with bleak futures may die out due to survival of the fittest. That sort of periodic adjustment befalls most industries, when change creates a new operating climate, killing off and weeding out the weak, leaving what's left leaner and meaner. Meanwhile, those who live and work in the world of AM radio today can only echo Molly's long ago words: "Taint funny McGee!"

R-E

# HARDWARE HACKER

## Perpetual motion, independent research, the magnetocaloric effect, and audio voltmeters.

DON LANCASTER

**I**t's not at all obvious to me why we need all of the foot dragging, in-fighting, and squabbling going on today over HDTV high-quality video-display standards. It seems that several government agencies are now battling each other to win the coveted role of chief obstructionist.

To me, it is entirely obvious that HDTV *will* use square pixels, *will not* have interlace, *will* use fully programmable, rather than hard-wired (single standard) receivers and displays, *will* be totally digital, *will* use a real-time JPEG compression, and *will* follow Japanese set standards.

It is also totally obvious to me that terrestrial broadcasting will serve a negligible to totally vanishing role in HDTV, while the computing, satellite, VCR, and cable uses will overwhelmingly dominate. And any intermediate or interim "transition" steps will prove to be a monumental waste of time and money, done by the wrong people for the wrong reasons.

So, let's just ban the networks and the feds from *any* HDTV input whatsoever, and then get on with it. They are the enemy, not Japan. Our topics this month seem to range from the ridiculous to the sublime...

### Perpetual motion

It may be the New Age nineties, or just a sunspot cycle peak, but a surprisingly large number of all you hardware hackers are busy at work building your own perpetual motion machines. I simply cannot believe the number of helpline calls and visitor drop-ins I am getting on this.

Since perpetual motion is definitely real as far as its history and its ongoing activities are concerned, maybe we should take a brief look here.

I guess I was in the seventh grade when I built my first perpetual motion machine. Figure 1 shows the details. I took a gyroscope and hung several magnets on it so that like poles faced each other. The magnets were at an angle so that the repulsion would

have a tangential component. As the poles repelled each other, the gyroscope would accelerate.

Or so I thought at the time. Very strangely, the gyroscope locked up instead of spinning. Seems it latched itself into a minimum reluctance field position and just sat there.

These days, I guess I don't really understand why perpetual motion is desirable. Since unlimited free energy would hasten the entropic heat death of the planet, perpetual motion is both environmentally unconscionable and socially reprehensible. The first thing we should do to a successful perpetual motion machine designer is to just stake him to an anthill, and then leave him out there until the next meeting of the steering committee.

Nonetheless, perpetual motion is a fascinating topic. Some very good books on this subject are available from *Lindsay Publications*, while a few of the more opportune ongoing perpetual-motion scams are available to you through *H&A Industries* or the *Tesla Book Company*.

After working with a bunch of them, the perpetual-motion buildees these days all appear to share several common traits. None of them have ever attended an introductory college physics course, or else they seem to have slept through it.

While all of them claim they "just can't find anything at all" on their idea, they studiously go out of their way to avoid doing any real or honest library research. As we've found out

several times in the past, any hardware hacker anywhere can instantly get the very latest scoop on anything by way of the *Dialog Information Service*. More on this shortly.

A disproportionate number of the perpetual-motion buildees seem to belong to one particular religion that happens to be very big on faith and on self-reliance.

There's often a very heavy dose of paranoia, usually aimed at the patent office, a local university, those oil companies, Detroit (who could not possibly suppress anything except quality or profits), an ex-boss, or else "them" in general.

Almost always, the buildees think *linearly* instead of *cyclically*. Thus, while a power stroke of the repelling magnets or their freezing milk bottle makes a lot of sense to them, they usually ignore the inevitable repetitive and cyclic energy supplying steps as needed to get to that stage.

There's also the *Cosmic cupcake* syndrome, the *Few chips shy of a full board* affliction, and the *Boy a whole flock of them flew over that time* concept. But we need not get into any of these here.

Finally, there is the *magic bullet*. Their idea almost but not quite works. So, all we need to fix it is better gears, stronger magnets, a larger milk bottle, or a different rear axle ratio. Or more bucks for research.

Several of us folks around here at **Radio-Electronics** editorial have now somehow gotten some silly ideas into our collective heads. For some unbeknownst reason, many of us presently feel that:

(A) Neither matter nor energy can be created or destroyed, except by an atomic process.

(B) Available energy always seems to convert itself from higher quality forms into lower and less useful ones. Not once have the dishes ever washed themselves. Nor have those pool balls ever re-racked themselves.

(C) Nearly all physical and elec-

### NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:

Don Lancaster

**Synergetics**

Box 809

Thatcher, AZ 85552

(602) 428-4073

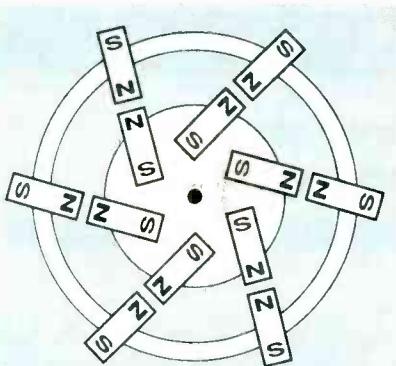


FIG. 1—MY VERY FIRST PERPETUAL MOTION MACHINE. As the like poles of the magnets repel each other, they accelerate the rotor on a gyroscope. Sadly, it latched, rather than speeding up. But maybe if I used stronger magnets...

tronic processes end up producing unrecoverable low-grade heat energy, usually through friction or electrical resistance.

(D) Despite a House-Senate compromise committee, Congress is not expected to repeal the three laws of thermodynamics this session. Para-

phrased, these three laws are (1) You can't win; (2) You can't break even; and (3) Yes, the dice are crooked, but it's the only game in town.

I guess one of the reasons some of us around here feel this way is that not once in the entire history of hardware hacking has even one reproducible counter example to these silly ideas of ours ever been successfully and unarguably demonstrated.

Naturally, you are free to agree or disagree with us as you wish. But if you disagree, we do make only one simple request: Provide us with an experiment that can be *independently* duplicated by *disinterested* outsiders which causes your effect to show up at least reasonably well. Then we will all believe.

#### Doing serious research

So, what is the best way to research any topic? I don't know how many calls and letters I have gotten from people who live in such a "remote" area and will claim that "absolutely nothing" is available locally. Believe it or not, one of these letters was from Cambridge, MA and yet another was from Palo Alto, CA.

Well, I've been sitting right here watching Gila Monsters on this sand dune smack dab in the middle of the Upper Sonoran desert for nearly two decades now. While almost everything I do is local (and much of it done underground or in mountaintop wilderness areas), I've had no problems whatsoever handling top-quality research on all kinds of very rewarding and well-paying topics.

So don't give me any "remote" bull. Admittedly, my tiny and isolated town of 2400 does have its own symphony orchestra, but that's another story.

Figure 2 lists a few of my key secrets to doing independent hacker research. The overwhelming reason you cannot find something is because you are not looking. You are instead going through some inept motions and keeping yourself busy, rather than by taking obvious steps and handling all of them in a logical manner.

Research is not an activity that you turn on or off. Instead, you put yourself in a *continuous* research mode in which you gather and collect *everything*, needed or not, or expected or not. Never mind the topic. The subject does not matter in the

least, since chance favors the prepared mind. Thus, your own personal resource file is far and away the most important place to look, should any specific need come up.

Set a minimum goal of eight cubic yards for your personal resource files. At least for a bare bones start-up. Then let it grow from there.

Your foremost outside resource should be all of the trade journals. I subscribe to over 400 of them. As we have seen in the past, any and all fields have all their own private technical magazines which are intended for a select group of insiders. Most of these are free, provided you tell them what they want to hear on their qualification cards. Many do include bingo cards, annual directories, and tech info.

Naturally, you'll circle everything even remotely usable on the bingo cards. If in doubt, circle it. If you do not personally rent the largest box in your local post office, you've missed the point here completely.

Electronic trade journal examples include *E.E. Times*, *Electronics*, *EDN*, *Electronic Products*, *Electronic De-*

#### RARE EARTH RESOURCES

##### Aesar

Box 8247 Ward Hill  
Haverhill, MA 01835  
(800) 343-1990

**CIRCLE 259 ON FREE INFORMATION CARD**

##### Alfa Products

PO Box 8247  
Ward Hill, MA 01835  
(800) 343-0660

**CIRCLE 260 ON FREE INFORMATION CARD**

##### Cerac

PO Box 1178  
Milwaukee, WI 53201  
(414) 289-9800

**CIRCLE 261 ON FREE INFORMATION CARD**

##### ESPI

5310 Derry  
Agoura, CA 91301  
(800) 638-2581

**CIRCLE 262 ON FREE INFORMATION CARD**

##### Fisher Scientific

711 Forbes Avenue  
Pittsburgh, PA 15219  
(412) 562-8300

**CIRCLE 263 ON FREE INFORMATION CARD**

##### Goodfellow

301 Lindenwood Drive Ste 1  
Malvern, PA 19355  
(800) 821-2870

**CIRCLE 264 ON FREE INFORMATION CARD**

**SYNERGETICS**  
Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073

**CIRCLE 83 ON FREE INFORMATION CARD**

- (1) - If you can't find it, you ain't lookin'.
- (2) - Research is a continuous activity done on a total lifestyle basis. You cannot turn it on and off at will.
- (3) - Anticipate what you are going to research in the future and get started on it long ahead of any actual or possible need.
- (4) - Your own personal resource file should be your first and foremost starting place. Your beginning file should fill at least eight cubic yards, and should expand from there.
- (5) - The free trade journals are far and away your most important external resource. A complete listing appears in *Uhlricht's Periodicals Dictionary*. Use those bingo cards!
- (6) - The *Dialog Information Service* at your local library can instantly find anything for you from anywhere at anytime.
- (7) - Other important library resources are the *Science Citations Index*, the *Thomas Registry of Manufacturers*, Interlibrary loan, the *UMI* reprint service, and the *Encyclopedia of Associations*.
- (8) - Form an extensive network of contacts outside of your circle of family, friends, or work associates. Clubs, helplines, and BBS systems are ideal for this sort of thing.
- (9) - Let your subconscious be your guide, starting from fundamental principles and guidelines. Go with the vibes.
- (10) - Quest *tinajas*.

FIG. 2—SEVERAL OF MY INSIDER secrets on independent research.

sign, and dozens more. We'll look at these names and numbers in some future sidebar.

For now, you go to the library and view the Hacker's Holy Grail, that is otherwise known as the *Uhlricht's Periodicals Dictionary*. This one hardware hacking resource is far and away more important than all of the rest put together. Use and enjoy.

The second most important outside Hardware Hacking research resource is the *Dialog Information Service*. It's also at your local library. For a small fee, *Dialog* will instantly research anything, anywhere, anytime. As an example, we'll shortly be looking at magnetic refrigeration. To get from knowing virtually nothing on the topic to having eighteen of the most recent worldwide key abstracts in hand took me a total of seven minutes and cost me a total of \$27.57.

There's lots of other goodies in the library, should you snoop around in enough nooks and crannies. In general, the least valuable things in any library are its takeout books. There's that free *Interlibrary Loan Service* which lets you get anything from anywhere, and the faster *UMI* service which can get you any reprint of anything provided you know the exact title, journal, and pages. For much less than *Dialog*, as long as you don't mind waiting a few days.

There's also a *Thomas Registry of Manufacturers* that lists who makes everything, but I've found this to be of limited utility. Also, check into the *Encyclopedia of Associations*, and, if you can't locate *Uhlricht's*, then the *International Standard Periodicals Dictionary* is almost as good.

Another library favorite of mine is the virtually unknown *Science Citations Index*. Unlike all the others, this one lets you move *forward* through time, rather than back into older and older material. It works by listing who put whom into their bibliographies.

For instance, any competent new technical paper on active filters *must* reference *Sallen and Key*. Anything new on cold fusion absolutely *must* list *Pons and Fleischman*. Anything new on unfocused solar collectors simply *must* cite *Winston*, and so on. If they don't, then they aren't worth reading anyhow.

Simply shove any of these names through the index, and you'll generate all of the newer papers in the field. After a while, new author names will start cropping up and repeating. You then use the *avalanche effect* to find the latest and the best, just by starting with one or two ancient authors.

And do not ignore the library's kidie, young adult, or popular press books. Excellent, understandable, and readable backgrounds are easily

picked up in the *Doubleday Science Series*, or the *Life Science Library*.

Beyond the library, you'll want to collect the specialty direct-mail books catalogs. We've covered this resource in depth in a previous column and contest. More details appear in my *Hardware Hacker II* reprints.

Let's see. What else is there? You'll definitely want to set up some sort of extensive personal network that involves people strictly *outside* of any friends, family, or work associates. Obviously, my help line works like a champ here. Electronic bulletin board systems are another great route to networking. So are clubs.

Your own personal experiments can very much clarify any topic, as can teaching a class on it. The purpose of research is to get the effect you are after to show up reasonably well in as simple and as cheap a way as possible.

But stay in school forever. While there's lots of possibilities here, the best I've found are local community college courses, and that self-study material from *Heath*.

Finally, simply let things gel. Take Bowseretta up the mountain. Quest a *tinaja*. Map that terminal crawlway. Any field has an order and a flow to it. Often in directions that "they" don't care to admit. Start with a few fundamentals, think about it for a while, and a pretty fair picture of the rest may fall in place without much in the way of conscious intervention.

Remember that sincerity is everything. Once you've got that faked, all else follows.


### This month's contest

Tellyawhat. I am about to reveal here for the first time a stunning new technological breakthrough, one that is eminently hackable, besides being a sure fire winner for a research topic, school paper, or science-fair entry.

Only instead of me doing all the work, let's try doing it together. See how much you can improve your research skills along the way.

Just show me an easily done and **Radio-Electronics**-compatible method to demo the magnetocaloric effect described below, at room or lower temperatures. Or else add in any way (patents, papers, articles, data sheets, etc.) to our ongoing magnetic refrigeration dialog below.

There'll be all the usual *Incredible*

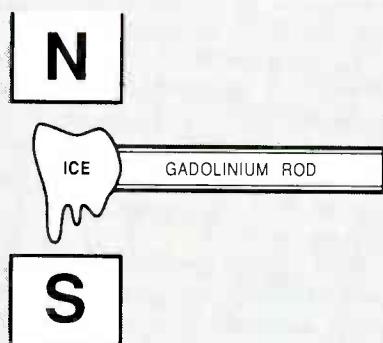

**FIG. 3—THE MAGNETOCALORIC EFFECT**, very greatly oversimplified. Gadolinium and other rare earth alloys can absorb heat energy in the presence of a magnetic field and release it otherwise. The efficiency can be as much as 40:1 better than mechanical cooling. Magnetic refrigeration is usable over an absolute zero to above room temperature range. Important first uses will be in cryogenics, superconductivity, liquefied gases, and hydrogen fuels.

Secret Money Machine book prizes, along with an all-expense-paid (FOB Thatcher, AZ) *tinaja* quest going to the very best of all. As usual, send your written entries directly to me here at **Synergetics**, rather than directly over to **Radio-Electronics** editorial.

### Magnetic refrigeration

There's apparently a brand new way to cool things that is just turning the corner from laboratory to preliminary product development. If what has happened so far is to be believed, it should completely blow away many traditional cooling schemes, particularly at very low temperatures.

This genuine breakthrough is called the *magnetocaloric effect*, and I have grossly oversimplified it in Fig. 3. The latest key papers appear in the listings of Fig. 4.

Basically, if you take critical rare earth elements or their alloys, they will absorb heat when magnetized and release heat otherwise, acting as a heat pump. At least over certain temperature ranges and over specified magnetic field strengths. Gadolinium is one popular material.

Heat transfer operations take place in and around the *Curie Point*. Most magnetic materials lose many of their properties when they exceed their Curie Point temperature.

The magnetocaloric effect can be tuned over a range of absolute zero to above room temperature. Efficiencies as much as 40:1 better than me-

### Magnetocaloric Effect in Strong Magnetic Fields

A.M. Tishin, *Cryogenics (UK)*, February 1990, v30 #2, pp 127-136.

### Magnetocaloric Effects in Rare Earth Magnetic Materials

A.S. Andreenko, et. al., *Soviet Physics (USA)*, August 1989, v32 #8, pp 649-664.

### Magnetocaloric Effect in Thulium

C.B. Zimm, et. al., *Cryogenics (UK)*, September 1989, v29 #9, pp 937-938.

### Magnetic Refrigeration

*Superconductivity Industries*, Spring 1989, v2 #1, pp 32-41.

### Magnetocaloric Effect and Refrigerant Capacity of Tb-Dy Alloys

S.A. Nitkin, et.al., *Physics Status Solidi (East Germany)*, May 1989, pp 117-121.

### Magnetic Refrigerator for Superconducting Magnets at 1.8K

V.A. Altov, et.al., *ICEC 12 (UK)*, 1988, pp 635-640.

### Magneto-thermal Properties of Sintered Gadolinium

E. Gmelin, et. al., *ICEC 12 (UK)*, 1988, pp 432-436.

### Determination of the Cooling Capacity of Magnetic Refrigerants

S. Nikitin, et. al., *Soviet Technical Physics Letters*, April 1988, v14 #4, pp 327-328.

### Magnetic Refrigerator

T. Hashimoto, *Refrigeration (Japan)*, 1988, v63 #733, pp 1189-1201.

### Magnetic Field Changes in the Entropy of Europium Sulphide

P. Bredy, et.al., *Cryogenics (UK)*, Sept 88, v28 #9, pp 605-606.

### Magnethermal Conductivity of Er-Al for Cryogenic Applications

C.B. Zimm, et.al., *Journal of Applied Physics*, 15 April 1985, v57 #8, p4294-4296.

### Adiabatic Temperature Changes in Ferromagnetic Intermetallic Compounds

C.B. Zimm, et.al., *Journal of Applied Physics*, 15 April 1985, v57 #8, p3829.

### Magnetic Refrigeration

T. Hashimoto, et. al., *Solid State Physics (Japan)*, March 1985, v20 #3, p161-175.

### Characteristics of Magnetocaloric Refrigerants below 20K

T. Hashimoto, et.al., *ICEC 9 (Japan)*, May 1989, pp 26-29.

### A Composite Material for Magnetic Refrigeration Using Internal Heat Transfer

B. Daudin, et.al., *Cryogenics (Great Britain)*, September 1982, v22 #9, pp 439-440.

### Magnetic Refrigeration from 10K to Room Temperature

T. Hashimoto, et.al., *Cryogenics (Great Britain)*, November 1981, v21 #11, pp 647-653.


### T-S Diagram for Gadolinium Near the Curie Temperature

S. Benford, et.al., *Journal of Applied Physics*, March 1981, v52 #3, pp 2110-2112.

### The Magnetocaloric Effect in Dysprosium

S. Benford, et.al., *Journal of Applied Physics*, March 1979, v50 #3, pp 1868-1870.

**FIG. 4—A FEW OF THE RECENT PAPERS** on magnetic refrigeration and the new magnetocaloric effect.

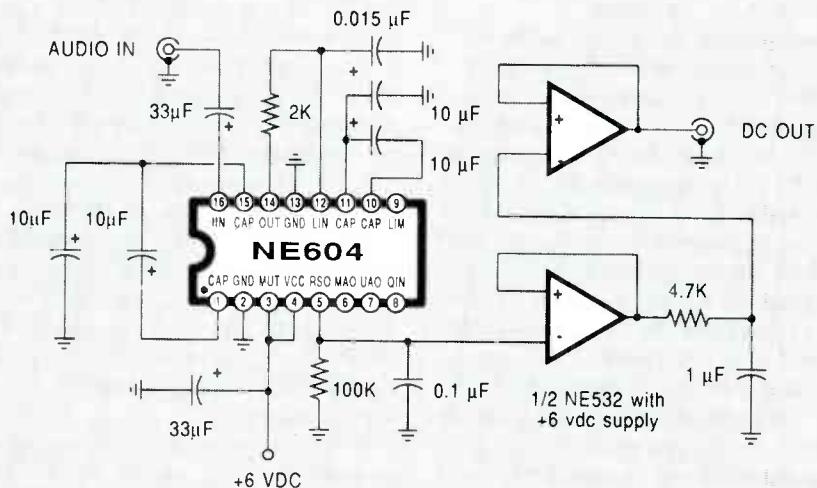

**FIG. 5—AN AUDIO VOLTMETER** having a range of 0 to -80 dBm. Use this one to calibrate microphones and speakers, or as a receiver "S" meter. Output is 0.5 volts at -80 dBm and 5 volts at 0 dBm. Sensitivity is 10 microvolts.


chanical refrigeration have been bandied about. Yes, the effect can be done using no moving parts.

Obvious applications for magnetic refrigeration include cryogenics and superconductivity, the production of


liquid gases (especially hydrogen as a fuel), and as Freon replacements for traditional room air conditioners. A few sources of gadolinium and its related rare earths are shown in our *continued on page 90*

## LAWN RANGER


continued from page 70

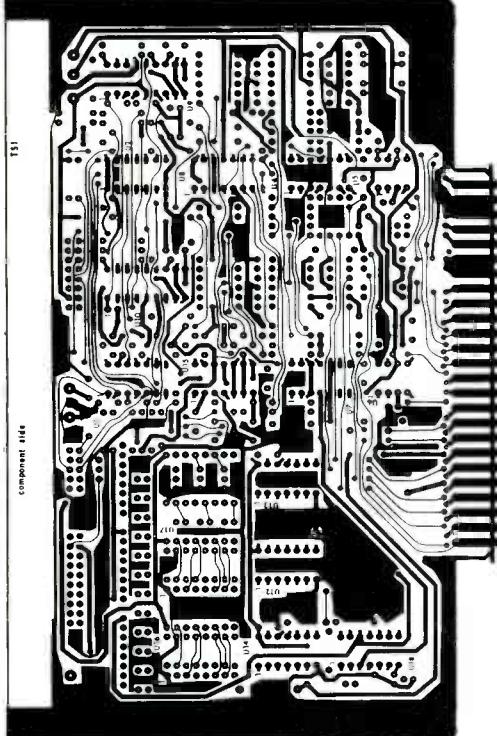

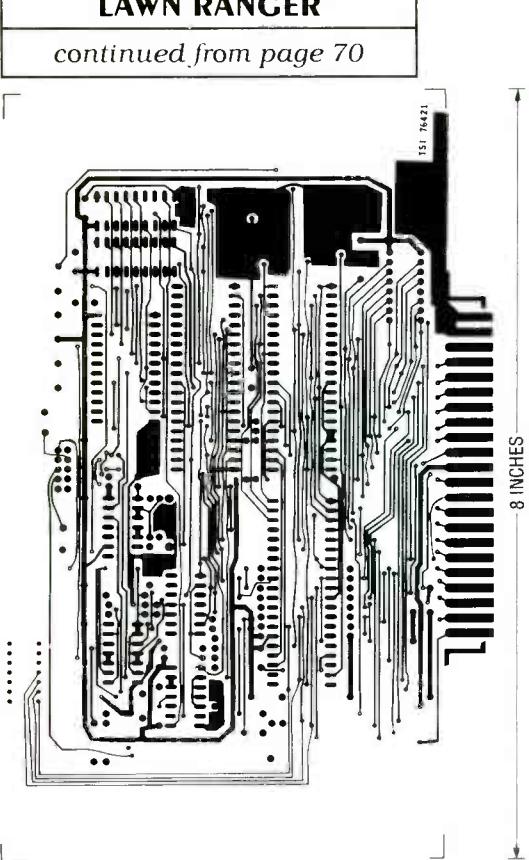
MOTOR CONTROLLER BOARD COMPONENT SIDE AT HALF SIZE.




CPU BOARD SOLDER SIDE AT HALF SIZE.

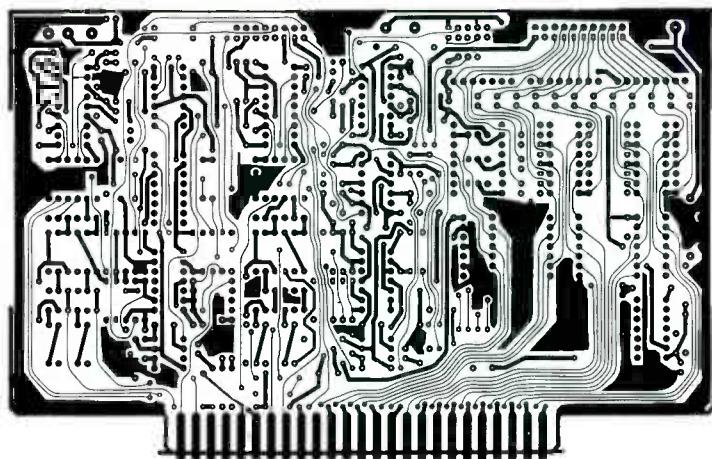

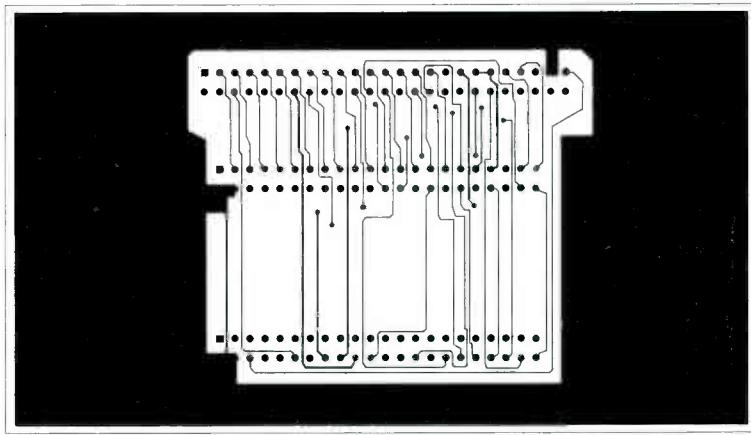MOTOR CONTROLLER BOARD SOLDER SIDE AT HALF SIZE.



MOTHERBOARD SOLDER SIDE AT HALF SIZE.

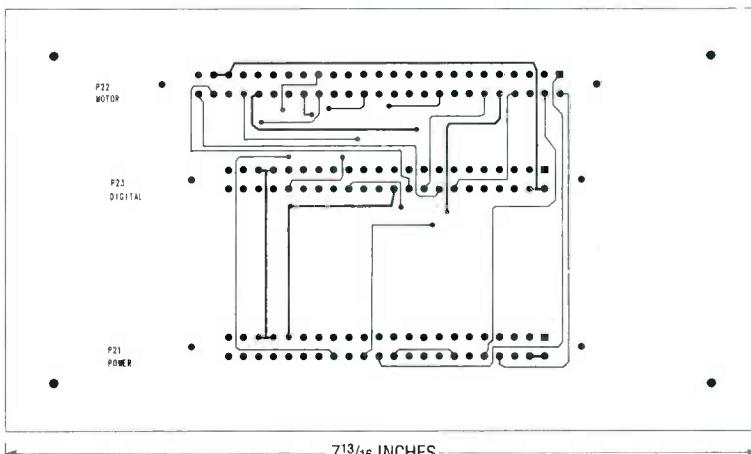

MOTHERBOARD COMPONENT SIDE AT HALF SIZE.

all the sensors are blocked. You should notice that the left wheel will slowly change from a counter-clockwise to a clockwise direction and the right wheel will change from a clockwise to a counter-clockwise rotation. If the


Lawn Ranger has passed all tests so far, it is ready for outdoor testing.

If it did not pass one or more of the tests, double check the operation of the CPU board as described in the June issue.
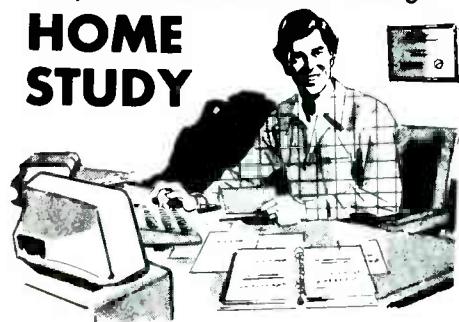
### Outdoor guidance testing

Now it is time to have some real fun! Make sure your neighbors or friends are out because they will love to see the capabilities of your new creation. Cut a six-foot thick square border around a small grassy test area with a conventional lawn mower (don't use the Lawn Ranger yet). Connect the manual controller, squeeze the

Put Professional Knowledge and a  
**COLLEGE DEGREE**  
 in your Technical Career through  
**HOME STUDY**



Add prestige and earning power to your technical career by earning your Associate or Bachelor degree through directed home study.

Grantham College of Engineering awards accredited degrees in  
**electronics and computers.**

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Grantham offers two degree programs—one with major emphasis in **electronics**, the other with major emphasis in **computers**. Associate and bachelor degrees are awarded in each program, and both programs are available completely by correspondence.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.


**Write for our free catalog** (see address below), or phone us at toll-free 1-800-955-2527 (for catalog requests only) and ask for our "degree catalog."

Accredited by


the Accrediting Commission of the  
 National Home Study Council

**GRANTHAM**  
**College of Engineering**

250 Frontage Road  
 Slidell, LA 70460

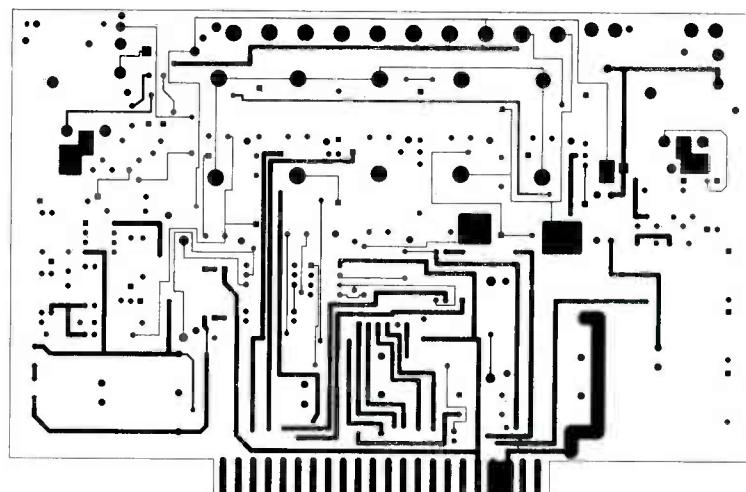

POWER BOARD COMPONENT SIDE AT HALF SIZE.

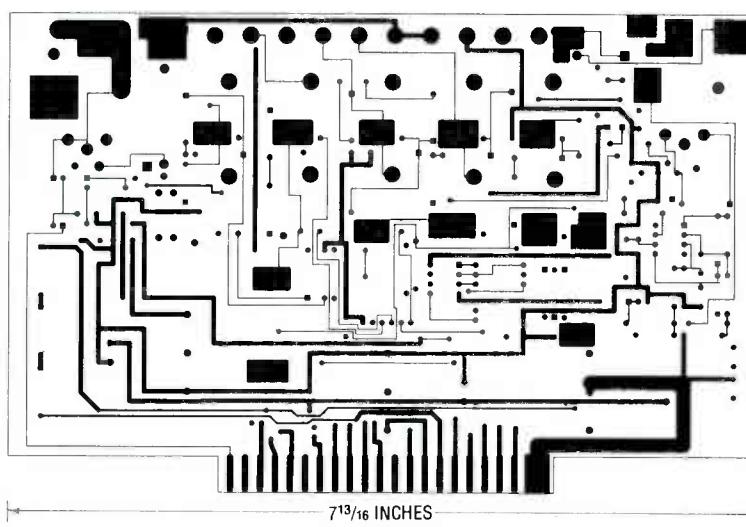

POWER BOARD SOLDER SIDE AT HALF SIZE.

hand switch and turn the Lawn Ranger on. "Walk" the unit to the cutting area and place it on the edge of the grass border with the tall grass positioned to the left—see Fig. 1 of the June issue.

Adjust the height of the grass sensors so their tips lie approximately one inch above the cut grass. The uncut grass should be around two inches higher than the cut grass for your first test. Remove the manual controller and push the RUN button. The mower will begin to track along the border you previously cut. It should continue tracking this border until you stop it. If it passes this test, you are ready to connect the cutting blades and really show off.

#### Final test

Now you are ready to connect the blades as shown in Fig. 3 (make sure the batteries are dis-

connected before attaching blades). Double check the shields that surround the cutting blades; they should be able to withstand a force as high as 60 pounds upon impact to allow for safe operation.

After the blades are attached, grab yourself a cold drink and "walk" the Lawn Ranger with the manual controller to the test area. Set up the mower as described above and connect the cutting-motor wire to J11-2. Remove the manual controller and turn the Lawn Ranger on.

Push the CUT and RUN button. Now, watch in amazement as the mower automatically cuts the grass contained within the test area. You will love the way it "turns on a dime" when it reaches the end of a row. When it is finished with the job, it will steer in a tight circle searching for tall grass and then turn off. R-E

# AUDIO UPDATE

## The Sound of Audio: An AES conference report

LARRY KLEIN

Last month I wrote about an audiophile High End Hi-Fi Show. This column is about an altogether different kind of "show" sponsored by the Audio Engineering Society (AES). Properly billed as a conference, rather than a show, "The Sound of Audio" was a wide-ranging exploration of the latest findings on the perception, measurement, recording, and reproduction of sound. A variety of papers were presented along with a special session on the reviewing of audio products featuring reviewers from both "slick" and "underground" publications. Given my 20 years in charge of product reviewing for *Stereo Review*, I heard nothing new—although the session gave me a chance to say hello to a lot of old friends. However, the pertinent and intelligent questions from the audience led me to make a mental note to discuss the somewhat controversial topic of equipment reviews in a future *Audio Update* column. Now, on with the conference.

### Psychoacoustics

Because of my ongoing interest in psychoacoustics, I found the several sessions devoted to audio perception both interesting and enlightening. As you may know, psychoacoustics deals with subjective sonic perceptions, as contrasted to objective sonic measurements. A simple example: For a sound to be heard subjectively as twice as loud, its objective increase in sound-pressure level must be approximately 10 dB.

The three presenters were all university researchers, and their talks included some of their own original research in addition to the very latest findings in the field. Rather than attempting to synthesize three lengthy, and sometimes complex, papers, I'll extract (and paraphrase when necessary) some of the opinions and findings that caught my ear.

- Despite hundreds of years of investigation into human hearing, many

mysteries and confusions remain. One author discussing the difficulties of operating in the area of qualitative judgments (Is it twice as loud or 1½ times as loud?) urged that because we are trying to measure the behavior of a very complex biological system that we be skeptical of the derived numbers—they might not mean what we think they do. I got a strong feeling that there is an enormous amount of research that remains to be done, and that digital manipulation of the testing signals is an important new facilitating tool.

- There is more to hearing loss than a simple reduction of sensitivity to

### WHO IS AES?

The AES is an international organization whose membership includes more than 10,000 persons involved on a professional, semiprofessional, and amateur level in all aspects of audio. For further information on The Sound of Audio conference, on how to become a member of the AES, and/or a catalog of available publications and technical papers, write to: Audio Engineering Society, 60 East 42nd Street, New York, NY 10165-0075.

various frequency areas. Unfortunately, at the frequencies where there is a hearing loss there are also additional changes that affect perception. Thus, we generally cannot restore normal perception by simply restoring normal sensitivity with a hearing aid or by using equalizers or tone controls in a hi-fi system. The study of the perceptual consequences of hearing loss is an important and very active research area of psychoacoustics and audiology.

- The ear has an incredible absolute sensitivity: At 3 kHz, where the ear is most sensitive, a sound at the threshold of hearing produces a displacement of the eardrum that is about  $\frac{1}{100}$  of the diameter of a hydrogen molecule! The threshold of pain (ranging

from 140 dB at 20 Hz to about 120 dB at 2 kHz) is generally given as the upper intensity limit of hearing. Unlike the eye, whose iris visibly adjusts itself to the ambient illumination, the ear maintains its approximately 120-dB dynamic range by dividing different intensity levels among separate groups of nerve fibers. Each of the fiber groups can handle a range of only 30–40 dB. At levels about 40 dB or so, only about 15–20% of the ear's 30,000 nerve fibers are handling the incoming sounds.

- It is almost always incorrect to refer to the *loudness* of a sound as, say, 90 dB SPL. Sound pressure level is a physical measurement and only indirectly related to loudness, which is a subjective evaluation. A sound measuring 90 dB could be, depending on its frequency spectrum, loud or quite soft.
- There's a new interest in sound-localization research. Some recent findings include: Complex, broadband sounds are localized best, high frequencies must be present for accurate judgment of a sound source's apparent height, and localization is most precise for signals in front and at ear level.

It has been generally accepted that our brain localizes sound sources by using the intensity and timing difference between the sounds reaching each of our ears. Although research has shown that the specific convolutions of our external ears (pinnae) cause reflective cancellations and reinforcements of signals before they reach our ear canals, only recently has it been understood that this direction-dependent spectral filtering plays an important role in our ability to localize sound sources.

Another recent experiment on directional perception sought to determine the relative importance of interaural arrival-time versus sound-intensity differences in determining localization. By digitally manipulating the signal, the experimenters were

## ELECTRONICS PAPERBACKS



◀  **BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS, BK-1** .... \$5.75. Circuits for a number of useful building blocks are presented. Combine these circuits to build the devices you need.

◀  **BP192—MORE ADVANCED POWER SUPPLY PROJECTS** .... \$5.95. Topics covered include switched-mode power supplies, precision regulators, dual tracking regulators and computer-controlled supplies.



◀  **BP190—MORE ADVANCED ELECTRONIC SECURITY PROJECTS** .... \$5.95. Projects include a passive infra-red detector, a fibre-optic loop alarm, computer-based alarms and an ultrasonic intruder detector.

◀  **BP113—30 SOLDER-LESS BREADBOARD PROJECTS, BK-2** .... \$5.95. All projects are based on CMOS logic ICs. Many components are common to several projects. Each project includes a brief circuit description, component layout and parts list.

Electronic Music Projects



◀  **BP74—ELECTRONIC MUSIC PROJECTS** .... \$5.95. Provides a number of circuits for Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser Units, Tremolo Generator and more.

◀  **BP255—INTERNATIONAL RADIO STATIONS GUIDE** .... \$7.95. Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around than ever more complex radio bands.



MAIL TO: Electronic Technology Today, Inc.  
P.O. Box 240  
Massapequa Park, NY 11762-0240

### SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00	\$1.25	\$30.01 to \$40.00	\$5.00
\$5.01 to 10.00	\$2.00	\$40.01 to \$50.00	\$6.00
\$10.01 to \$20.00	\$3.00	\$50.01 and above	\$7.50
\$20.01 to \$30.00	\$4.00		

**SORRY, No orders accepted outside of USA and Canada**

Total price of merchandise	\$
Shipping (see chart)	\$
Subtotal	\$
Sales Tax (NYS only)	\$
Total Enclosed	\$

Name		
Address		
City	State	Zip

able to feed the test subjects conflicting intensity and timing information. The expectation was that the subjects would "split the difference," but instead it turns out that the difference in interaural arrival time was the dominant localizing factor—as long as frequencies below 2 kHz were part of the signal.

The authors concluded that this newly discovered time-difference dominance means that "modification of the intensity ratio between the right and left channels of a stereo recording cannot be expected to have any influence on the apparent position of the resultant sound image." I think I missed the author's point, because as far as I can tell my preamplifier's balance control (which operates by adjusting the relative gain levels of the right and left channels) works as well as ever.

The final paper on the localization of sound sources related a series of complex experiments that set up "unnatural" acoustic conditions (such as having one reflecting wall in an otherwise anechoic environment) and used highly controlled, and equally unnatural, special acoustic test signals. It turns out that the subjects *unconsciously* evaluated the plausibility of the test signals against their real-word experience and ignored or re-weighted sounds that made no sense. An example of a nonsensical signal would be one in which the arrival-time differences between the ears exceed the maximum possible (about 765 microseconds) for the human head, or one in which the delayed reflected sound was louder than the direct sound.

The paper didn't cover another related phenomena—the ear/brain's ability to localize sounds where they "should" be rather than at their actual source. For example, when listening to a performer on stage from anywhere in the audience, most people hear the sound coming from the performer rather than from the auditorium's speakers—assuming the sound system isn't grossly misbalanced. And, on a cozier level, most people have no problem when viewing the TV while wearing headphones in placing the dialogue at the actors' mouths rather than at the real source—directly over their own ears.

Next month we will look at some of the other papers dealing mostly with the hardware of audio.

R-E

## TELEPHONE LINE

continued from page 46

PC type bracket, and cut openings for J1 and J2.

### Installation

With the modified bracket installed on the card, it is very simple to install in an IBM PC or clone. All you have to do is locate an unused slot in your computer's expansion bus. Make sure the computer is off during the installation. Remove the blank mounting bracket from the back of the computer (if one exists), and insert the new card into the slot. Install the mounting screw, and then plug in the phone line and the AC adapter and battery backup if used, and you're ready to roll.

### Software

The software is menu driven and, in most cases, a single key stroke is all it takes to change mode or to perform an operation. Screen colors are used for highlights, and for separation of fields. The only thing you have to remember is to type TLC and hit return (from the DOS prompt). All programming, functions, and mode selections thereafter are done using menus. (See sources box for custom software.)

The software consists of two programs: the operating program and the resident program (which are available on the RE-BBS—516-293-2283). The operating program runs on the host computer and provides the interface with the controller's hardware. The resident program is what the operating program loads into the on-board SRAM. The resident program is the actual program that determines what the controller will perform. But it is the operating program that is used to select, configure, and load the resident program.

### User registration cards

Although the software is not copy protected, we strongly recommend users to register their copies; doing so will automatically put you on AC&C's mailing list. AC&C will inform users of new applications software, functions, and updates.

R-E

# DRAWING BOARD

This month begins our discussion on control circuitry.

ROBERT GROSSBLATT

**D**esigning and building electronic controllers used to be a really difficult job if you wanted the circuit to have enough intelligence to do even fairly complex jobs. The reason for that was that there weren't any single-component solutions to electronic intelligence. But when IC's were developed, and affordable microprocessors appeared on the market, things began to change dramatically.

The major change in controllers was the home computer in general and the marketing of cheap motherboards. That's because all the intelligence you'd ever need could be handled by an eighty dollar clone and a bit of software...almost.

The reason for the "almost" is that, even though a cheap PC clone has all the brains and memory needed to control your home's security system or the environmental control system of the space shuttle, there's no convenient way to let the computer talk to the outside world.

All home computers have the capability of talking to an external device since they have to deal with video, keyboards, printers, and so on. How they do that depends on the particular computer since different microprocessors handle I/O in their own unique and often strangely wonderful way. Fortunately for all of us, just about all of the popular clone computers are built around the 80XXX family—from the original 8080, the Z-80, to the 8088 and its more powerful kin, the 80286, 80386, and whatever other surprises Intel comes up with in the future.

All those microprocessors deal with I/O in the same way; through the use of only two instructions IN and OUT. The chip understands that it can be told to address two completely different kinds of locations: memory and ports. If you think of the computer as being an active controller, the former kinds of locations are for thinking and the latter are for doing.

It's really that basic.

If you look at the pinouts of any of the 80XXX family, you'll see that there's one pin labelled IO/MEM. On the 8088, for example, you can see that in Fig. 1 on pin 28. That's the control pin that lets external circuitry know whether the microprocessor is doing a memory operation or an I/O (port) operation.

In ordinary use, most people are

happily unaware of what kind of instruction is being executed even though both kinds happen all the time. Remember that printers, modems, mice, joysticks, and so on are all treated by the 8088 as I/O devices.

Interestingly enough, even though chips like the 8088 make it easy to deal with I/O, designing the circuitry to be controlled is always a pain in the neck, since even the lowly 8088 can handle more than 64,000 different port addresses. That means that anything designed to be driven by the 8088 has to be able to recognize when a particular address shows up on the bus—and that means designing the circuitry necessary to keep an eye on as many as sixteen different address lines to decode the few that you're interested in.

Some months ago I published the details of the Port-A-Matic (**Radio-Electronics**, January and February 1990) which would decode some of the address lines and indicate when the 8088 was talking to particular ports. If you glance through the text of the article, you'll get an idea of just how tedious address decoding can really be.

When you're going to use a store-bought computer as the basis for a controller, it makes a lot of sense to see if you can possibly get away with not having to do address decoding.

You need circuitry to create a working port. This usually takes the form of address decoders, latches, and a wad of logical glue to hold the whole thing together. If the port you're designing has any special needs, that means even more silicon. An example of that would be something like a port aimed specifically at serial stuff where you had to have UART's, line drivers, and so on.

There are several standard port locations in the magical kingdom of cloneland, and I've listed the most popular ones in Table 1. Notice, as we just discussed, that most of the ports actually use several sequential port

1	GND	V <sub>CC</sub>	40
2	A <sub>14</sub>	A <sub>15</sub>	39
3	A <sub>13</sub>	A <sub>16</sub> /S <sub>3</sub>	38
4	A <sub>12</sub>	A <sub>17</sub> /S <sub>4</sub>	37
5	A <sub>11</sub>	A <sub>18</sub> /S <sub>5</sub>	36
6	A <sub>10</sub>	A <sub>19</sub> /S <sub>6</sub>	35
7	A <sub>9</sub>	S <sub>50</sub>	34
8	A <sub>8</sub>	MN/MX	33
9	AD <sub>7</sub>	RD	32
10	AD <sub>6</sub>	HOLD	31
11	AD <sub>5</sub>	HLDA	30
12	AD <sub>4</sub>	WR	29
13	AD <sub>3</sub>	IO/MEM	28
14	AD <sub>2</sub>	DT/R	27
15	AD <sub>1</sub>	DEN	26
16	AD <sub>0</sub>	ALE	25
17	NMI	INTA	24
18	INTR	TEST	23
19	CLK	READY	22
20	GND	RESET	21

FIG. 1—LOOKING AT THE PINOUTS of the 8088, pin 28 (IO/MEM) is the control pin that lets external circuitry know whether the microprocessor is doing a memory operation or an I/O (port) operation.

# R-E Engineering Admart

**Rates:** Ads are  $2\frac{1}{4}'' \times 2\frac{1}{8}''$ . One insertion \$950. Six insertions \$925 each. Twelve insertions \$895 each. Closing date same as regular rate card. Send order with remittance to **Engineering Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Engineering ads are accepted for this Admart.**

## INCREASE YOUR EARNING POWER!

LEARN TO DESIGN WITH  
SINGLE CHIP MICROCOMPUTERS!

### SINGLE CHIP MICROCOMPUTER PRIMER FOR MOTOROLA 6805

Includes:  
 • Professional Quality MS-DOS Software  
 • Editor  
 • Assembler  
 • Simulator/Debugger  
 • Programmer Schematics  
 • Single Chip Microcomputer Primer Lesson Book

Price \$195

MC6805-1 Program for Motorola MC68705P3,P5,U3,U5,R3,R5  
 Parts kit w/ driver program \$150  
 Fully assembled w/ driver program \$125  
 Fully assembled w/ driver, assembler, simulator/debugger \$495

MC6805-3 Program for Motorola MC68HC705C8, 805C4  
 Parts kit w/ driver program \$175  
 Fully assembled w/ driver program \$160  
 Fully assembled w/ driver, assembler, simulator/debugger \$495



The Engineers Collaborative Inc.

Emulators Programmers Assemblers Simulators/Debuggers  
 Rt. #3, Box 8C TEL: (802) 525-3458  
 Barton, VT, USA 05822 FAX: (802) 525-3451

**CIRCLE 185 ON FREE INFORMATION CARD**

addresses to handle data, control, and status. That is important to keep in mind because one of the major drawbacks of designing around someone else's hardware is that things aren't set up the way you'd like them to be.

There are actually two problems: The first is that not all the data bits may be used, and the second is that some of the bits may be designed to be either read only or write only. The best way to see that is to look at the port that's available on most clone systems—LPT1, the main printer port.

Just about every clone board I've seen (including the more well-known name brands) that provide an LPT1 port uses the same I/O address space. The three I/O ports that go into making the printer port are 03BCh (the data port), 03BDh (the status port), and 03BE (the control port). The computer uses the data bits at those locations as summarized in Table 2.

The control port at 03BEh is designed to be both written to and read from, although bits 5, 6, and 7 are unused. Bit 4 is used by the port but is designed as a hardware flag to enable the interrupt that the computer uses to find out whether or not the printer can accept data. The bottom line is that bit 4 is only used internally and doesn't show up on the port connector. Keep that in mind because

## FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The NEW EXAM covers updated marine and aviation rules and regulations, transistor and digital circuitry.

**THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE** contains vital information. **VIDEO SEMINAR KITS ARE NOW AVAILABLE.**

**WPT PUBLICATION**  
 979 Young Street, Suite E  
 Woodburn, Oregon 97071  
 Phone (503) 981-5159 Dept. 50

**CIRCLE 179 ON FREE INFORMATION CARD**

MIDI  
Projects

## MIDI PROJECTS

**BP182**—MIDI interfacing enables any so equipped instruments, regardless of the manufacturer, to be easily connected together and used as a system with easy computer control of these music systems. Combine a computer and some MIDI instruments and you can have what's virtually a programmable orchestra. To get your copy send \$6.95 plus \$1.25 for shipping in the U.S. to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.

status port, has restrictions as well. All eight bits are used, but the port's only configured for output.

Every one of the boards I've seen that has a printer port on it uses some kind of a latch near the end of the hardware chain making up the data port. Usually it's a 74LS373 (boards with discreet components), or a work-alike latch buried in silicon if the board has custom LSI or ASIC chips. Data sent to the port at 03BCh will stay there until it's either changed or cleared by the computer.

It's important to completely understand the parallel-port setup before you start using it as anything other than a printer port since not all the bits are implemented or designed to be both input and output.

**R-E**

**TABLE 1 - COMMON PORT ASSIGNMENTS**

PORT	COMMENT
3F8h	FIRST SERIAL PORT (COM1)
2F8h	SECOND SERIAL PORT (COM2)
3BCh	FIRST PARALLEL PORT (LPT1)
3F5h	FLOPPY DISK DATA PORT
201h	FIRST JOYSTICK DATA PORT

there's no hardware available to get the upper four bits out to the external world.

The status port at 03BD is designed so that there are even more restrictions on its use. Not only are the first three bits (0, 1, and 2) not used (and consequently not supported in hardware), but it's only set up as an input port. You can read the state of some of the bits but there's no hardware available to let you write to the port.

The data port at 03BCh, like the

**TABLE 2**

### BIT ASSIGNMENTS FOR LPT1 WITH A BASE PORT OF 03BCh

#### DATA PORT - 03BCh - WRITE ONLY

BITS 0-7 - DATA

#### STATUS PORT - 03BDh - READ ONLY

BITS	0-2	-	UNUSED
BIT	3	-	ERROR
BIT	4	-	SELECT STATUS
BIT	5	-	PAPER OUT
BIT	6	-	ACK
BIT	7	-	BUSY

#### CONTROL PORT - 03BEh - READ/WRITE

BIT	0	-	STROBE
BIT	1	-	AUTOFEED
BIT	2	-	INIT
BIT	3	-	SELECT
BIT	4	-	IRQ7 ENABLE
BITS	5-7	-	UNUSED

# How to build a high-paying career, even a business of your own, in computer programming.



**RICK BRUSH,  
NRI PROGRAMMER/ANALYST**

**Start with training that gives you hands-on programming experience—at home and at your own pace. Training that begins with BASIC, then continues with Pascal, C, and COBOL—today's hottest computer languages. Training that even includes a powerful IBM-compatible computer, modem, and programming software you keep.**

**Start with real-world training. The kind of training only NRI provides.**

Now with NRI's new at-home training in Computer Programming, you can be one of today's highly paid, creative team of computer wizards who give computers the power to carry out an astonishing range of business, professional, and personal applications. Now, with NRI, you can be a computer programmer, ready to build a high-paying career—even a business of your own—making computers do anything you want them to do.

**The only programming course that includes a powerful computer system and software you keep.**

Unlike any other school, NRI gives you hands-on programming experience with a powerful IBM-compatible West Coast computer system, including 2400

baud internal modem, 640K RAM, disk drive, monitor, and invaluable programming software—BASIC, Pascal, C, and COBOL—all yours to keep.

You get the experience and the know-how, the computer and the software to get to the heart of *every* programming problem, design imaginative solutions, then use your choice of four key computer languages to build original, working programs.

**No matter what your background, NRI gives you everything you need to succeed in programming, today's top-growth computer career field.**


You need no previous experience to build a successful programming career with NRI training. Indeed, your NRI lessons start by walking you step by step through the fundamentals, giving you an expert understanding of the programming design techniques used every day by successful micro and mainframe programmers. And then the fun really begins.

C, and COBOL. Then, rounding out your training, you use your modem to "talk" to your instructor, meet other NRI students, even download programs through NRI's exclusive programmers network, PRONET.

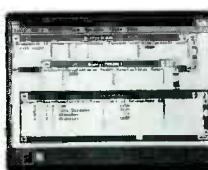**Your career in computer programming begins with your FREE catalog from NRI.**


For all the details about NRI's at-home training in Computer Programming, send the coupon today. Soon you'll receive NRI's fascinating, information-packed, full-color catalog.

Open it up and you'll find vivid descriptions of every aspect of your NRI training. You'll see the computer system included in your course up close in a special, poster-sized foldout section. And, best of all, you'll find out how your NRI training will make it easy for you to build that high-paying career—even a business of your own—in computer programming.



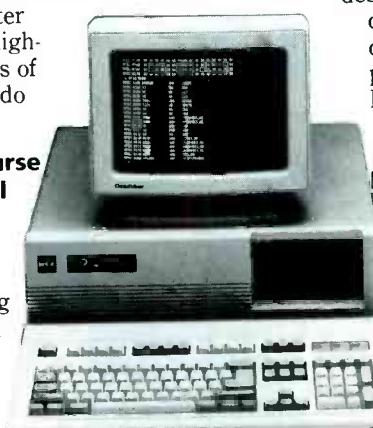**You master today's hottest computer languages, gaining the skills you need to build programs for a wide variety of real-world applications.**

With your personal NRI instructor on call and ready to help, you use your computer and software to actually design, code, run, debug, and document programs in BASIC, Pascal,



**NRI School of Computer Programming**

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW  
Washington, DC 20008



**YES! Please rush me my FREE catalog describing NRI's at-home training in Computer Programming.**

NAME *(please print)* AGE

ADDRESS

CITY/STATE/ZIP

Accredited by the National Home Study Council

10-090

**Only NRI gives you an IBM-compatible computer with modem, 640K RAM, disk drive, monitor, and software—BASIC, Pascal, C, and COBOL—all yours to keep!**

# COMPUTER CONNECTIONS

## The long-anticipated release of Windows 3.0 and ToolBook, a "software construction set."

JEFF HOLTZMAN

**A** few days ago Microsoft finally released the long-anticipated and much-hyped new version of Windows. The company spared no expense in the formal product introduction; the initial event cost \$3 million, and the company will spend another \$7 million between the time when I write this and you read it. According to some reports, Windows 3.0 represents the culmination of a seven-year, \$200 million development effort. Clearly, Microsoft means business.

In case you just emerged from detention in Siberia, I'll give a brief rundown of salient new features.

The most conspicuous change is in the user interface. It is simply gorgeous. Mac users will no longer be able to sneer at Windows.

No longer are there separate versions of the product for different CPU's. The same version of Windows 3.0 runs on 8088, 80286, and 80386 processors. However, the program runs in different modes (real, standard, enhanced, respectively) depending on the host processor. Officially, 3.0 will run on an 8088, but a 286 or better is strongly recommended. On a recommended processor, 3.0 breaks the 640K memory limit. Rather, it will when appropriate software is released. For the immediate future, you must run old Windows applications in real mode; however, it appears that most vendors of significant Windows applications are scrambling to convert their products as quickly as possible. The situation will undoubtedly ease considerably by the time you read this.

Another immediate problem that will undoubtedly be fixed quickly is hardware drivers. The program presently comes with precious few. For example, even though 3.0 recognized my Video Seven VRAM VGA card, it provided built-in support only for a 256-color mode at standard resolution (640 x 480), not the 800 x 600 and 1024 x 768 high-res modes. Nor

would it recognize the Novell drivers on my office PC. However, updated drivers were available from the vendors almost immediately.

In general, the lack of hardware support is a problem, but not as great a problem as it used to be, because 3.0 lets you alter your hardware configuration on the fly. With previous versions, if you wanted to change *anything*, you had to re-install the whole package, possibly wiping out important setup information in the process. Now hardware and software upgrades will be easy to accommodate.

Most of the applications that come with Windows have been upgraded. For example, the terminal program now does XMODEM and Kermit file transfers, the calculator now has scientific and programmer functions, the clock now has both analog and digital displays, a macro recorder is now included, a solitaire game has

been added, etc. In addition, the Windows environment itself is now customizable. You can use one of several predefined background patterns, or create your own, or create (or scan in) an image to use as "wallpaper."

Microsoft has finally disposed of the clunky old MS-DOS Executive; the new Program and Task managers (which bear strong resemblance to the corresponding OS/2 functions) provide a visual approach to running programs. The File Manager (which resembles that in DOS 4.0) provides a much more intuitive means of copying, moving, deleting, and searching for files than the old MS-DOS executive. Windows now also provides a significant interface for network users.

As for hardware, Microsoft has tried to position Windows as needing a 286 + 2MB of RAM versus OS/2's 386 + 4MB. From what I can tell,

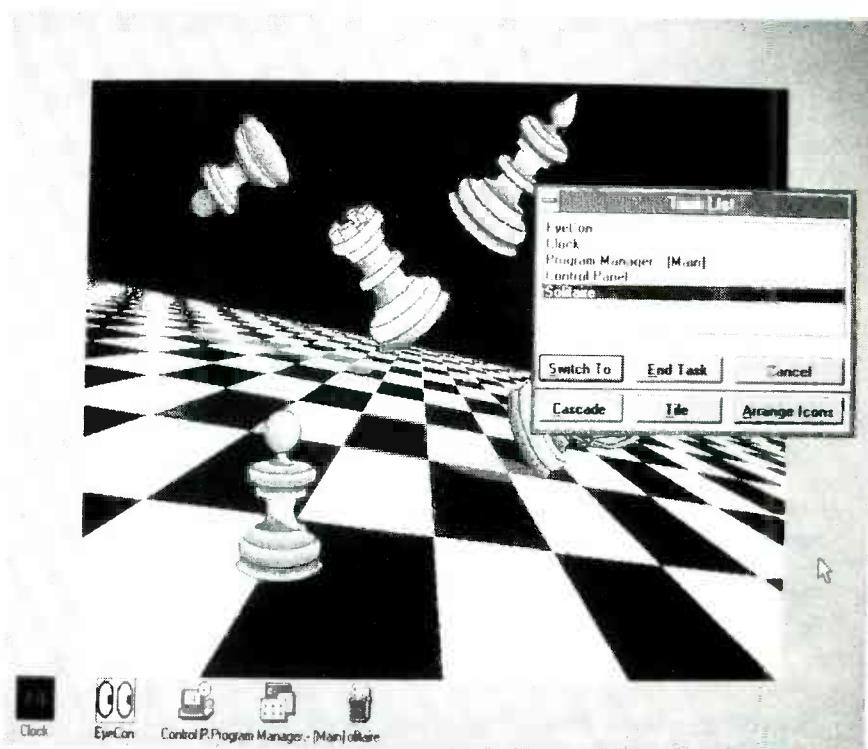


FIG. 1

# R-E Computer Admart

**Rates:** Ads are  $2\frac{1}{4}'' \times 2\frac{7}{8}''$ . One insertion \$950. Six insertions \$925. each. Twelve insertions \$895. each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Computer ads are accepted for this Admart.


## GETTING THE MOST FROM YOUR PRINTER



**BP181**—It is probable that 80% of dot-matrix printer users only ever use 20% of the features offered by their printers. This book will help you unlock the special features and capabilities that you probably don't even know exist. To order your copy send \$6.95 plus \$1.50 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.
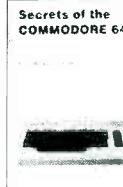
## SECRETS OF THE COMMODORE 64

**BP135**—A beginners guide to the Commodore 64 presents masses of useful data and programming tips, as well as describing how to get the best from the powerful sound and graphics facilities. We look at how the memory is organized, random numbers and ways of generating them, graphics-color-and simple animation, and even a chapter on machine code. Get your copy today. Send \$5.00 plus \$1.25 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.



## ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)

QUANTITY ONE PRICES SHOWN FOR JULY 1, 1990

OUTS OF OKLAHOMA NO SALES TAX

DYNAMIC RAM	
1MB	COMP DeskPro 386S \$225.00
SIMM	AST Preem386/33MHz 200.00
SIMM	1Mx9 80 ns 75.00
SIMM	256Kx9 100 ns 27.00
1Mbit	1Mx1 80 ns 7.25
41256	256Kx1 60 ns 4.15
41256	256Kx1 80 ns 3.10
41256	256Kx1 100 ns 2.15
41256	256Kx1 120 ns 1.95
4464	64Kx4 100 ns 2.50
41264*	64Kx4 100 ns 5.95
EPROM	
27C1000	128Kx8 200 ns \$17.50
27512	64Kx8 200 ns 7.80
27256	32Kx8 150 ns 6.50
27128	16Kx8 250 ns 3.75
STATIC RAM	
62256P-10	32Kx8 100 ns \$7.50
62264P-12	8Kx8 120 ns 4.50
6116AP-12	2Kx8 120 ns 4.25

80387-8 80387-16 80387-25  
\$20.00 \$20.00 \$20.00

OPEN 6 DAYS. 7:30 AM 10 PM. SHIP VIA FED-EX ON SAT.

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY 10:00 AM. (918) 267-4961

MasterCard VISA or UPS CASH COD

MICROPROCESSORS UNLIMITED, INC.

24,000 S Peoria Ave., Beggs, OK 74421

NO minimum order. Please hold prices subject to change.

Shipping insurance extra up to \$1 for packing materials.

CIRCLE 61 ON FREE INFORMATION CARD

those distinctions are driven by the marketing folks, not the technical people. A desktop publisher running PageMaker or a heavy-duty financial analyst running Excel simply needs all the memory, hard disk, and CPU speed he or she can possibly obtain. On the other hand, the average user might go a long way using just the built-in applications.

On a 386, Windows now (finally!) lets you run several non-Windows applications simultaneously in an efficient manner.

At long last the documentation includes useful information on setup and configuration. I drastically increased performance of a 3MB Dell System 300 by setting up a dedicated swap area on disk, as described in Chapter 13 of the *User's Guide*.

### What's it all mean?

By itself, none of the built-in Windows applications can compete with any serious DOS product. But the Windows apps work together as a group very well. And that's one thing that vaulted the Mac to its place of eminence.

When you stop looking at Windows as a DOS add-on or competitor, but as a product in its own right, it takes on a new glow of its own.

You might compare Windows 3.0

to everything-but-the-kitchen-sink programs like Sidekick Plus and PC Tools. Actually, those are not programs but nearly complete environments that contain most of the tools the average DOS user needs to accomplish daily tasks. Windows 3.0 provides similar functionality, but one that is couched in a sparkling user interface, and is built around an architecture that can accommodate user evolution.

I think 3.0 is going to be a wildly successful product, for several very good reasons:

- Unlike OS/2, Windows has significant applications (Excel, Ami, Word, PageMaker, Corel Draw, Designer, Crosstalk) available now in all application categories except database management.

### ITEMS DISCUSSED

- Windows 3.0 (\$149, upgrade \$50 + \$5.50 S/H), Microsoft Corp., 16011 NE 36th Way, Box 97017, Redmond, WA 98073-9717. (206) 882-8080. Upgrades: (800) 323-3577.

CIRCLE 11 ON FREE INFORMATION CARD

- ToolBook 1.0 (\$395), Asymetrix Corp., 110 110th Avenue NE, Suite 717, Bellevue, WA 98004. (206) 462-0501. Orders: (800) 624-8999, ext. 299H.

CIRCLE 12 ON FREE INFORMATION CARD

- The industry hasn't seen such a high level of end-user interest in a product in years.
- The enhanced user interface is going to attract users in a way that previous versions were unable to duplicate (and that DOS never could).
- The ability to write programs that can cleanly access 16MB of memory will attract developers.
- The ease of setup and reconfiguration will attract corporate managers and tech support people.
- And rumors still persist about IBM's pending introduction of a low-cost "multimedia" home PC, for which Windows 3.0 would be the perfect operating environment. Maybe it will turn out to be the elusive PC "for the rest of us" that Apple has promoted but not properly marketed for so long.

By the time you read this, much of the smoke will have cleared. Meanwhile, it's going to be an interesting summer.

### ToolBook tames Windows

First out of the starting gate is not a revamped version of an old Windows product, but a brand-new one called ToolBook. If the word HyperCard means anything to you, then you'll have some idea of what ToolBook is about.

ToolBook is billed as "a software construction set." It consists of a set

of tools that let you build applications by designing screens and linking them to one another. Tools include a graphics editor and a programming language called OpenScript. The editor allows you to create buttons that, when selected on-screen, cause something to happen. What happens depends on scripts you write. The script language provides a rich environment for programming, as it includes full control structures (if/then/else, case, do while, do until, etc.), a single-stepping debugger, a macro recorder, and hundreds of functions.

Writing programs for ToolBook is not like writing BASIC, Pascal, or C programs. Rather, OpenScript is an object-oriented message-passing language, just like the underlying Windows architecture (and OS/2 as well). However, once you start wrapping your mind around that concept, you find that development is no more difficult than in a traditional language—in fact, it's a good deal easier, because many of the grubby, low-level details are hidden from view. ToolBook comes with many sample scripts to help you get started. In addition, at least one company (Heizer Software of Pleasant Hill, CA) has announced a program that will convert HyperCard stacks to ToolBook format.

One extremely powerful facet of OpenScript is that it's extensible. You'll have to understand low-level Windows programming to do so, but the results could well be worth it. Suppose, for example, that you had developed a six-voice stereo music synthesizer and you wanted to build the user interface for it in ToolBook. You would write a dynamic link library (DLL) to control the hardware, link it to ToolBook, and get to work.

Windows 3.0 is currently shipping with a sample ToolBook application called DayBook, which provides a highly intuitive set of daily, weekly, and monthly calendars that provide time- and contact-management functions like some DOS-based desktop organizers.

The only sad thing about ToolBook is its price: about \$400. By contrast, Apple includes a copy of HyperCard free with every Mac.

If you're looking for a way to get into Windows programming, but without incurring the extraordinary learning curve involved, ToolBook is the way to go.

R-E

## HARDWARE HACKER

continued from page 78

expensive report on this magnetic refrigeration is now available through *Technical Insights*. Much more on all

### NAMES AND NUMBERS

#### Alumilite

225 Parsons Street  
Kalamazoo, MI 49007  
(616) 342-1259  
**CIRCLE 240 ON FREE INFORMATION CARD**

#### Automotive Electronics

7 East 12th Street  
New York, NY 10003  
(212) 741-4184  
**CIRCLE 241 ON FREE INFORMATION CARD**

#### CMA

19 Gardner Road  
Fairfield, NJ 07004  
(201) 575-6460  
**CIRCLE 242 ON FREE INFORMATION CARD**

#### Dialog Information Service

3460 Hillview Avenue  
Palo Alto, CA 94304  
(415) 858-2700  
**CIRCLE 243 ON FREE INFORMATION CARD**

#### Electronic Goldmine

Box 5408  
Scottsdale, AZ 85261  
(602) 451-6454  
**CIRCLE 244 ON FREE INFORMATION CARD**

#### H & A Industries

Route 2  
Box 35E  
Bowling Green, MO 63334  
**CIRCLE 245 ON FREE INFORMATION CARD**

#### Heathkit

Box 1288  
Benton Harbor, MI 49022  
(616) 982-3200  
**CIRCLE 246 ON FREE INFORMATION CARD**

#### Lindsay Publications

Box 12  
Bradley, IL 60915  
(815) 468-3668  
**CIRCLE 247 ON FREE INFORMATION CARD**

#### Micro Linear

2092 Concourse Drive  
San Jose, CA 95131  
(408) 433-5200  
**CIRCLE 248 ON FREE INFORMATION CARD**

#### Rare Earth Resources sidebar

This is all so new and so hot (Uh—better make that so *cold*) that I don't have too much for you beyond these key papers of Fig. 4. One very detailed and thorough but ridiculously

#### Micron

2805 East Columbia Road  
Boise, ID 83706  
(408) 433-5200  
**CIRCLE 249 ON FREE INFORMATION CARD**

#### National Semiconductor

475 Ellis Street  
Mountain View, CA 94043  
(800) 632-3531  
**CIRCLE 250 ON FREE INFORMATION CARD**

#### SGS-Thompson

1000 East Bell Road  
Phoenix, AZ 85022  
(602) 867-6259  
**CIRCLE 251 ON FREE INFORMATION CARD**

#### Short Circuits

Box 285  
Barnegat, NJ 08005  
(609) 698-3080  
**CIRCLE 252 ON FREE INFORMATION CARD**

#### Signetics/Philips

811 East Arques Avenue  
Sunnyvale, CA 94088  
(408) 991-2000  
**CIRCLE 253 ON FREE INFORMATION CARD**

#### Synergetics

Box 809  
Thatcher, AZ 85552  
(602) 428-4073  
**CIRCLE 254 ON FREE INFORMATION CARD**

#### Technical Insights

Box 1304  
Fort Lee, NJ 07024  
(201) 568-4744  
**CIRCLE 255 ON FREE INFORMATION CARD**

#### Tesla Book Company

Box 1649  
Greenville, TX 75403  
(214) 454-6819  
**CIRCLE 256 ON FREE INFORMATION CARD**

#### UMI

300 North Zeeb Road  
Ann Arbor, MI 48106  
(800) 521-3044  
**CIRCLE 257 ON FREE INFORMATION CARD**

#### Synergetics

Box 809  
Thatcher, AZ 85552  
(602) 428-4073  
**CIRCLE 258 ON FREE INFORMATION CARD**

this when I actually get the papers and can do some hacking of my own.

#### An audio voltmeter

*Signetics* has an intriguing cellular  
*continued on page 92*

# MARKET CENTER

## FOR SALE

**GREAT buys!** Surplus prices, ICs, linears, transformers, PS, stepping motors, vacuum pump, phototransistor, meters, LSASE, **FERTIK'S**, 5400 Ella, Phila., PA 19120.

**DESCRAMBLERS.** All brands. Special: Combo Jerrold 400 and SB3 \$165.00. Complete cable descrambler kit \$39.00. Complete satellite descrambler kit \$45.00. Free catalog. **MJM INDUSTRY**, Box 531, Bronx, NY 10461-0208.

**T.V. notch filters, surveillance equipment, brochure \$1.00.** **D.K. VIDEO**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

**TUBES:** "oldest," "latest." Parts, components, schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., RE, Hammond, IN 46324.

**ENGINEERING** software, PC/MSDOS. Hobbyists — students — engineers. Circuit design \$49.00, PCB layout \$99.00, Logic simulation \$29.00, FFT analysis \$69.00, Mathematics \$39.00, Circuit analysis \$29.00. Call or write for free catalog. (614) 491-0832, **BSOFT SOFTWARE**, 444 Colton Rd., Columbus, OH 43207.

**RESTRICTED** technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. Huge selection. Free brochures. **MENTOR-Z**, Drawer 1549, Asbury Park, NJ 07712.

## WIRELESS CABLE RECEIVERS 1.9 TO 2.7 GHz



30 CH PARABOLIC DISH SYSTEM \$173.99  
30 CH ROD ANTENNA SYSTEM \$193.90  
30 CH CRYSTAL CONTROLLED SYSTEM \$294.95  
  
SUN MICROWAVE INT'L. INC. SEND \$1.00 FOR  
P.O. BOX #34522 CATALOG ON THESE  
PHOENIX, AZ 85057 AND OTHER FINE  
(602) 230-0640 VIDEO PRODUCTS  
QUANTITY DISCOUNTS LIFETIME WARRANTY  
MEMBER OF THE BETTER BUSINESS BUREAU

**TOCOM** VIP converters w/remote from \$199.00. Tocom super chips turn on everything, \$69.00 each. Phone (219) 935-4128.

**BRAND** name computers from \$299.00 factory fresh complete systems, IBM, Laser, Emerson, closeouts, **DIGITECH**, (602) 722-4215.

**DESIGN** PLDs on IBM/PC, two 360K disks w/application book. Parts and programming services available. \$10.00 postpaid, B. **LEWIS**, PO Box 223, Palm Harbor, FL 34682.

**DESCRAMBLERS — converters, free information and price list, wholesale prices, SASE, S.A.C.**, 4112 N. Simmons, N. Las Vegas, NV 89030.

**PROTOQUICK** Z8, single board computer with prototype area, \$69.00. **SOFTWARE SCIENCE**, 3750 Roundbottom Road, Cincinnati, OH 45244. (513) 561-2060.

**CABLE TV** converters: Jerrold, Oak, Scientific Atlantic, Zenith & many others. "New MTS" stereo add-on: mute & volume. Ideal for 400 and 450 owners! (1) (800) 826-7623, Amex, Visa, M/C accepted. **B & B INC.**, 4030 Beau-D-Rue Drive, Eagan, MN 55122.

**TUBES**, new, up to 90% off, SASE, **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

**PROGRAMMABLE** stepper motor drive & control for under \$100, IBM PC/XT compatible, **Commodore 64**, or other with 25 pin parallel port. PCB, interface, & software. Send for detailed literature to: **MASE**, R.D. #2 Box 166, Mohrsville, PA 19541.

**FREE catalog.** Interfaces for IBM compatibles. Digital I/O and analog input. Control relays, motors, lights, measure temperature, voltage. **JOHN BELL ENGINEERING, INC.**, 400 Oxford Way, Belmont, CA 94002. (415) 592-8411.

**RENTAL** movie stabilizer. Connect between VCRs or to monitor. Satisfaction guaranteed. \$69.95, \$4.00 handling. 1 (800) 367-7909.

**CABLE** descramblers (Jerrold) from \$40.00. Tocom VIP test chip. Fully activates unit. \$50.00. Call (213) 867-0081.

**PRINTED** circuit boards etched & drilled. Free delivery. **K & F ELECTRONICS, INC.**, 33041 Groesbeck, Fraser, MI 48026. (313) 294-8720.

**T.V. converter descramblers**, wholesale to all, Tocoms, Zeniths, Oaks, Hamlin, Jerrold, SA, COD orders accepted. **S.A.C.**, info (702) 647-3799, orders 1 (800) 622-3799.

**LASERS.** 1mw to 2kw, worlds largest selection of new & used surplus. Free catalog. **MWK INDUSTRIES**, 1269 Pomona Road, Corona, CA 91720. (714) 278-0563.

## FREE CATALOG

**FAMOUS "FIRESTIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962**

**FIRESTIK ANTENNA COMPANY  
2614 EAST ADAMS  
PHOENIX, ARIZONA 85034**

**TEST equipment** pre-owned now at affordable prices. Signal generators from \$50.00. Oscilloscopes from \$50.00. Other equipment, including manuals available. Send \$1.00 for catalog, refund on 1st order. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (708) 982-1973.

**CABLE-TV** **Scientific Atlanta 8580** Qty/price each 1/289, 5/249, 10/239, 6PM to 10PM EDT weekdays, (301) 791-5019. No Maryland orders accepted.

**DESCRAMBLERS:** dealers! We have new Z-Tac descramblers, only \$185.00 in 10 lots, with other systems available. 1 (800) 695-CABL.

**Quality Microwave TV Antennas**  
WIRELESS CABLE-1 9 to 2.7 Ghz. 40db Gain (+)  
36-Channel System Complete \$149.95  
12-Channel System Complete \$114.95  
Call or Write for "FREE" Catalog  
  
**Phillips-Tech Electronics**  
P.O. Box 8533 • Scottsdale, AZ 85252  
(602) 947-7700 [S3.00 Credit all phone orders!]  
MasterCard • Visa • C.O.D. • Quantity Pricing

**CABLE** descramblers, all brands in stock, wholesale prices to retail customers, C.O.D. orders accepted. **MOUNT HOOD ELECTRONICS** (206) 896-6837.

**LOTTERY** — IBM computer disk for all lotteries \$10.00. **ROBERTS**, Box 63/6025, Margate, FL 33063.

**OAK** Sigma descrambler, channel 3 output, rare hard-to-find factory equipment, with free documentation, \$150.00. Oak Sigma modification documentation \$20.00 postpaid. Oak VN12-4 (or Hamlin) descramblers with free remote control converter, \$85.00. Eagle remote control converter descrambler combos, \$100.00. Send moneyorder, ship postpaid within 3 days. **SURPLUS ELECTRONICS**, POB 10009, Colorado Springs, CO 80932.

## CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Thousands of satisfied customers since 1976! Catalog \$2.

**CBC INTERNATIONAL**  
P.O. BOX 31500RE, PHOENIX, AZ 85046

**MINIATURE** electronics like James Bond. Catalog \$4.00, refundable. **F & P ENTERPRISES**, Box 51272, Palo Alto, CA 94303-L.

## CABLE TV DESCRAMBLERS! BARGAIN HEADQUARTERS!



•JERROLD™ •TOCOM •HAMLIN  
•OAK •ZENITH  
•SCIENTIFIC ATLANTA

6 month warranty! We ship C.O.D.!  
Lowest retail/wholesale prices!

FREE CATALOG:  
Global Cable Network  
1032 Irving St. Suite 109  
S.F., CA 94122  
NO CALIFORNIA SALES!!!

**ORDER TODAY! 800-327-8544**

**CABLE TV** converters and descramblers liquidation! Zenith, Tocom, Hamlin, Oak, Jerrold, Scientific Atlanta. Quantity discount! Order now Visa/MC/COD 1 (800) 962-6836.

**SURPLUS** electronics, motors, speakers, power supplies, adapters, etc... send for free catalog. **WINDSOR DISTRIBUTORS**, 19 Freeman Street, Newark, NJ 07105.

**CABLE TV** converters and descramblers. We sell only the best. Low prices. **SB-3 \$79.00**. We ship C.O.D. Free catalog. **ACE PRODUCTS**, PO Box 582, Dept. E, Saco, ME 04072. 1 (800) 234-0726.

**FREE CATALOG!**  
**1-800-648-7938**  
For all information 1-702-362-9026  
**JERROLD HAMLIN OAK ETC.**

## CABLE TV DESCRAMBLERS

•Compare our low Low Retail Prices!  
•Guaranteed Prices & Warranties!  
•Orders Shipped Immediately!  
**REPUBLIC CABLE PRODUCTS INC.**  
4080 Paradise Rd. #15 Dept. RE-90  
Las Vegas, NV 89109

## CABLE TV DESCRAMBLERS

**CABLE TV** converters and descramblers bargain headquarters! Jerrold, Tocom, Zenith, Hamlin, Scientific Atlanta. Oak M35B only \$60.00. Free Catalog! GCN, 1032 Irving Street #109, San Francisco, CA 94122. Order now! Visa/MC/COD 1 (800) 327-8544.

# 3 FOR 1 SPECIAL

## ON SUB-MINIATURE VOICE FM TRANSMITTERS.

### KITS CONTAIN PC BOARDS



\*FMX-1 LONG RANGE (3 MI) ULTRA SENSITIVE FM VOICE XMTR with fine tune, range control plus..... \$34.50



\*TELX-1 TELEPHONE FM XMTR (3 MI) automatically operates when phone is used. Crystal clear clarity with fine tune and range control. Non detectable..... \$34.50



\*ATR-1 AUTOMATIC TELEPHONE RECORDING DEVICE tapes telephone conversation all automatically..... \$19.50

ALL THREE OF ABOVE FOR..... \$69.50

CALL OR SEND VISA, MASTER CHARGE, MONEYORDER, ETC. TO AMAZING CONCEPTS, BOX 716, AMHERST, NH 03031. (603) 673-4730.

## CABLE TV

### TB-3 (Tri-Bi) or SA-3

#### Quantity Prices

10	20
----	----

**\$48.**      **\$43.**

Each

Each

50	100
----	-----

**\$39.**      **\$35.**

Each

Each

Hours open 10:00 am to 4:00 pm Eastern time

Minimum order 5 units 55.00 ea.

Dealers wanted. We ship COD.

King Wholesale

**1-800-729-0036**

Fax number 6173400053

"No one beats the King's prices!"

## DESCRAMBLERS

### HARDWARE HACKER

continued from page 90

radio log-amplifier chip in their NE604 and described in their new ap-note AN-1991. Figure 5 shows you how to use this chip to build an audio level meter usable over an incredible 0 to -80 dBm decibel range. It accepts audio levels as low as ten microvolts, and should be useful for speaker and microphone testing, as well as for a receiver "S" meter.

Reasonably priced and wide-range log amps are a rarity, so this is a welcome chip. Be sure to let me know what other uses you can come up with for this gem.

#### New tech literature

Three free new data books from SGS do include their *Power Bipolar Transistors*, *Zener and Rectifier Diodes*, and their new *1990 Shortform Catalog*. From *Micron*, a *MOS Data Book* mainly on static and dynamic memories. From *Micro Linear*, a *1990 Data Book* has just come out featuring A/D, D/A, telecomm, and power-supply circuits. And, speaking of tele-

comm, be sure to pick up the new *Telecommunications Data Book* from *National*.

Two hacker surplus sources with ultra-low prices include *Short Circuits* and the *Electronic Goldmine*.

*Automotive Electronics* is a very interesting new trade journal, while *Electronic Components and Applications* is an outstanding quarterly tech journal from *Philips*. The cost is a tad high at \$20 per year for what should be a free house organ. The latest issue includes info on solid-state visible laser diodes, pagers, phase-lock loop circuits, and oscilloscope tubes.

Our free mechanical samples this month include *Alumilite*, an easily castable urethane that sets in three minutes and easily holds small details; and the *Cycle-Flex* mechanical drive cables and fittings from *CMA*.

Turning to my own products, I do have complete autographed sets of book-on-demand published *Hardware Hacker II* reprints for all my **Radio-Electronics** columns here waiting just for you. And, for more information on self-directed research, check into my *Incredible Secret Money Machine*.

Finally, I do have a new and free mailer for you which includes dozens of insider hardware hacking secret sources. Write or call for info.

Our usual reminder here that most of the items mentioned appear either in the *Names and Numbers* or the *Rare Earth Resources* sidebars.

As always, this is your column and you can get technical help and off-the-wall networking per that *Need Help?* box. The best calling times are weekdays 8-5 in *Mountain Standard Time*. Let's hear from you.

**R-E**

Try the

**Radio Electronics**

bulletin board  
system

**(RE-BBS)**  
**516-293-2283**

The more you use it the  
more useful it becomes.

We support 300 and 1200  
baud operation.

Parameters: 8N1 (8 data  
bits, no parity, 1 stop bit)  
or 7E1 (7 data bits, even  
parity, 1 stop bit).

Add yourself to our user  
files to increase your  
access.

Communicate with other  
R-E readers.

Leave your comments on  
R-E with the SYSOP.

**RE-BBS**  
**516-293-2283**



*Megahertz... that's when something  
is really painful.*



# CONSOLIDATED

ELECTRONICS

COMPATIBLE WITH  
NEW PRICE LIST!

CONSUMER & INDUSTRIAL EDITION

37TH EDITION

## THE ULTIMATE ELECTRONICS CATALOG

Order your 260 page catalog and price list with over 14,000 money saving electronic parts and equipment! Send \$3.00 in a check or money order, or call 1-800-543-3568 today and use your Mastercard or Visa. Consolidated Electronics, Incorporated 705 Watervliet Ave., Dayton, Ohio 45420-2599

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 70 ON FREE INFORMATION CARD

### DIGITAL V.O.M./D.P.M. SALES—SERVICE—PARTS

FLUKE-BECKMAN-SIMPSON-ETC.  
U.S. MADE ONLY. QUOTATION PRIOR TO WORK. FAST SERVICE, 90 DAY WARRANTY. STANDARDS TRACEABLE TO NBS. SINCE 1948. CALIBRATION CERTIFICATE AVAILABLE.

INDUSTRIAL INSTRUMENT WKS. INC.  
5745 SALMEN, HARAHAN, LA 70123 504/733-8355

PROJECTION TV. Convert your TV to project 7 foot picture... Easy... Results comparable to \$2,500 projectors... Plans and 8" lens \$27.95... Professional systems available... Illustrated catalog free... MACROCOMA, 15GA Main Street, Washington Crossing, PA 18977. Creditcard orders 24Hrs. (215) 736-3979.

### CABLE TV DESCRAMBLER LIQUIDATION!

- Major Makes & Models!
- Will match or beat anyone's prices!
- Dealer discounts at 5 units!
- Examples:  
HAMLIN COMBOS . . . \$44 ea. (Min. 5)  
OAK ADD/ON . . . \$40 ea. (Min. 5)  
OAK M35B . . . \$60 ea. (Min. 5)

#### WEST COAST ELECTRONICS

For Information: 818-709-1758  
Catalogs & Orders: 800-628-9656

DEVICES unavailable in USA. Kits, parts, plans. Catalog \$2.00. WORDWAND, 612 Orange Street, Palm Harbor, FL 34683.

KITS — alarms, games, and test equipment. Send \$1.00 for catalog. RAKJAB, PO Box 1875, Apopka, FL 32704.

# CABLE TV

## "BOXES"

Converters—Descramblers  
Remote Controls—Accessories

★ Guaranteed Best Prices ★

★ 1 Year Warranty — C.O.D.'s ★

★ Immediate Shipping ★

★ FREE CATALOG ★

Call or Write

TRANS-WORLD CABLE CO.

12062 Southwest 117th Court, Suite 126

Miami, Florida 33186

1-800-442-9333



SURVEILLANCE transmitter kits! Four models of each; telephone, room, combination telephone/room transmitters tune from 65 to 305 MHz. Catalog with Popular Communications and Popular Electronics book reviews of "Electronic Eavesdropping Equipment Design," \$1.00. SHEFFIELD ELECTRONICS, 7223 Stony Island Ave., Chicago, IL 60649-2806.

INVESTIGATORS, experimenters — Quality plans. Micro and restricted devices. Free catalog. Self addressed stamped envelope required KELLEY SECURITY INC., Suite 90, 2531 Sawtelle Blvd., Los Angeles, CA 90064.

FREE laser catalog lightshows, pointers, holography, etc. lowest prices! Write to: MIDWEST LASER PRODUCTS, PO Box 2187, Bridgeview, IL 60455 or call (708) 403-6984.

PC/TV Interface — RGB to TV/video/VCR. Switchable between PC and composite video inputs. Channels 3 or 4, RF output. Complete PC card kits \$59.95. PC board only \$19.95 Mass residents add 5% sales tax. INOVONICS CORP. 9 Bartlett St., Dept. 36, Andover, MA 01810.

## Only A Few Days Left!

There are only a few days left in August and that is when our Super Special 13th Anniversary Sale on one of the broadest lines of Digital Semiconductors ends. Imagine **PRIME** Integrated Circuits for as low as 10 cents each! And for this sale, we didn't just pick a few components to serve as "Loss Leaders," but we cut prices on more than 500 items from the 74LS, 74HC, 74HCT, 4000 CMOS and Z80 Microprocessor Families in our inventory. Results: Prices so low that no other supplier can dare to come close to. Even our normal "Lower-Than-Anyone-Else" Prices for these products will be at least 20% higher after this sale is over! So, you can afford to stock up on what you need for the next several months now and still be money ahead in the future. For a complete listing of all the items on sale refer to the last issue of *Radio Electronics*. But please hurry because our Sale will Absolutely end on August 31st, 1990.



International  
Components  
Corporation

For a FREE copy of our New Catalog (Available Mid October),  
please circle Reader Service Card.

1803 N.W. Lincoln Way • Toledo, OR 97391

PHONE (All 50 States & Canada): 1-800-325-0101

FAX: (503) 336-4400 • Hours: 6:00 AM - 6:00 PM PST



CIRCLE 187 ON FREE INFORMATION CARD

## CABLE TV EQUIPMENT



JERROLD-OAK-SCIENTIFIC ATLANTA-HAMLIN ZENITH MANY MORE CALL TODAY!

✓ Only quality products sold ✓ Easy to use  
✓ Satisfaction guaranteed ✓ Knowledgeable sales staff  
✓ Most orders shipped within 24 hours

### CALL FOR YOUR FREE CATALOG

MC 1-800-228-7404 VISA

MAKE THE CONNECTION

WITH  
**NU-TEK ELECTRONICS**

5114 Balcones Wood Dr. #307 Dept. 298  
Austin, TX 78759

**FLUKE SUPER SALE**

Model	Model	Model
73	\$ 68	83
75	\$ 99	85
77	\$135	87

VISA  
MC  
\$180  
\$208  
\$246

**KELVIN** Electronics  
7 Fairchild Ave., Plainview, NY 11803  
(516) 349-7620 1 (800) 645-9212

**SURVEILLANCE** — audio/video equipment — debugging, industrial or private, 500 item catalog \$7.00. **SECURITY SYSTEMS**, 3017G Hudson, New Orleans, LA 70131.

### CABLE DESCRAMBLERS OAK M35B COMBO \$39.95

Jerrold, Zenith, Hamlin, Sci. Atlanta, Pioneer & MORE! OUR PRICES ARE BELOW WHOLESALE!

**CABLE + PLUS**

14417 Chase St. #481-A Panorama City, CA 91402  
1-800-822-9955 • Other Info. 1-818-785-4500  
NO CALIF. SALES — DEALERS WANTED

### SATELLITE TV

**FREE** catalog — Lowest prices worldwide, save 40-60%. Systems, upgrades, parts, all major brands factory fresh and warrantied. **SKYVISION, INC.**, 2009 Collegeway, Fergus Falls, MN 56537. 1 (800) 334-6455. International (218) 739-5231.

**CABLE TV** secrets — the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers listed included. \$9.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

**FREE** catalog 32 pages. Satellite systems, accessories and upgrades lowest prices all major brands no-one undersells **WEST INC.**, since 1977 1 (800) 222-9064.

## K.D. VIDEO

FOR ALL YOUR CABLE TV NEEDS

WE SPECIALIZE IN DEALER PRICING

QTY	1	10	20
Jerrold (Type) SB-3	89.00	56.00	48.00
Jerrold (Type) Tri-Bi	119.00	69.00	65.00
Scientific Atlanta SA-3	129.00	80.00	75.00
Hamlin MLD-1200	99.00	59.00	45.00
Oak N-12 Vari-Sync	99.00	59.00	58.00
Jerrold 550 Converter	99.00	75.00	68.00
Jerrold 400 DRX-3DIC (With Built in SB-3)	169.00	109.00	100.00

1-800-327-3407

Call us for prices on large quantities

K.D. Video PO Box 29538, Mpls., MN 55429

THIS SPACE CONTRIBUTED AS A PUBLIC SERVICE

When someone in your family gets cancer, everyone in your family needs help.

Nobody knows better than we do how much help and understanding is needed. That's why our service and rehabilitation programs emphasize the whole family, not just the cancer patient.

Among our regular services we provide information and guidance to patients and families, transport patients to and from treatment, supply home care items and assist patients in their return to everyday life.

Life is what concerns us. So you can see we are even more than the research organization we are so well known to be

No one faces cancer alone.

AMERICAN CANCER SOCIETY

THIS SPACE CONTRIBUTED AS A PUBLIC SERVICE

A defense against cancer can be cooked up in your kitchen.

There is evidence that diet and cancer are related. Follow these modifications in your daily diet to reduce chances of getting cancer:

1. Eat more high-fiber foods such as fruits and vegetables and whole grain cereals.
2. Include dark green and deep yellow fruits and vegetables rich in vitamins A and C.
3. Include cabbage, broccoli, Brussels sprouts, kohlrabi and cauliflower.
4. Be moderate in consumption of salt-cured, smoked, and nitrite-cured foods.
5. Cut down on total fat intake from animal sources and fats and oils.
6. Avoid obesity.
7. Be moderate in consumption of alcoholic beverages.

No one faces cancer alone.

AMERICAN CANCER SOCIETY

# MCM ELECTRONICS

*The Best Of All Worlds!*

POWER CORDS • BATTERIES •  
ALARM EQUIP. • ENT. • LAMPS •  
CLOTHES DRYERS • TOOLS • TECHN.  
CONVERTORS • SEMICONDUCTORS  
ANTI-STATIC PRODUCTS •  
ITEMS • MICROWAVE OVEN PARTS •  
LEADS • CHEMICAL EQUIPMENT • CABLES •  
POWER CENTERS • TRIPS • TUBES • COMPUTER  
MICROWAVE OVEN PARTS • TRANSISTORS • ADAPTORS • SPEAKERS •  
HARDWARE • BOOKS • FLYBALLS • POWER CORDS • BATTERIES •  
ITCHES • TELEPHONE ACCESSORIES • EQUIPMENT • LAMP  
VALS • AUTO ELECTRONICS • TEST LEADS •  
ARTS & ACCESSORIES • TEST EQUIPMENT •  
SERVING EQUIPMENT • FUSES • POWER CORDS •  
ANTI-STATIC PRODUCTS •  
SYSTEMS • MICROWAVE OVEN PARTS •  
LEADS • CHEMICALS • TOOLS •  
EQUIPMENT • CATV CONNECTORS •  
POWER CENTERS & OUTLET STRIPS •  
WIRE • CABLE • ALL



Place just one order from our new 192-page catalog of over 15,000 in-stock products and discover why thousands of satisfied customers have chosen MCM as their #1 supplier of parts and components. Choose from an extensive selection of high-quality products from some of the most respected names in the industry like RCA/GE, Switchcraft, Weller, PIC, Excelite, Pyle, Cambridge, Mueller and many more. Enjoy TOLL-FREE or FAX ordering, convenient hours, fast delivery, a variety of payment options and superior customer service support, too. Make MCM your #1 choice and start enjoying the best of all worlds today!

Get Your **FREE, ONE-YEAR SUBSCRIPTION** to the MCM Electronics Catalogs, Call **TOLL-FREE, 1-800-543-4330.**



**MCM ELECTRONICS**  
650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459-4072  
A PREMIER Company

SOURCE NO. RE-65

CIRCLE 87 ON FREE INFORMATION CARD

# CATV CONVERTERS AT LOWEST PRICES

Panasonic, Jerrold, Tocom, Pioneer, Scientific Atlanta, Zenith, Oak, Hamlin, Eagle, and all other brands

**Microwave Antennas**  
(wireless cable) with matching descramblers

Call Mon-Fri 10AM - 5:30PM  
Eastern time or write for

## FREE CATALOG



NO CONNECTICUT SALES. It is not the intent of Universal View to defraud any pay television operator and we will not assist any company or individual in doing so. We do not sell or sign any cable company or individual off at least 21 years of age, and fully understand that persons under the age of 18 years old are not given the right to subscribe or receive service. We do not give the right to receive or view premium cable channels in areas where they are not authorized to receive them. We do not sell or sign any cable company or individual off at least 21 years of age, and fully understand that persons under the age of 18 years old are not given the right to receive or view premium cable channels in areas where they are not authorized to receive them. We do not sell or sign any cable company or individual off at least 21 years of age, and fully understand that persons under the age of 18 years old are not given the right to receive or view premium cable channels in areas where they are not authorized to receive them.

SIGNATURE

DATE

# UNIVERSAL View

520 GLENBROOK ROAD, SUITE NO 202  
STAMFORD, CT 06906

Orders Only: **1-800-622-9022**  
(203) 975-7543

CIRCLE 64 ON FREE INFORMATION CARD

# Parts Express

International Inc.

## EMINENCE



## MOTOROLA

## Polydax

## 1-800-338-0531

## PIONEER

### 18" EMINENCE WOOFER

MADE IN USA

100 oz. magnet, 3" voice coil. 250 watts RMS, 350 watts max. 8 ohm, 30 Hz resonant frequency. 22-2700 Hz response. Efficiency: 95 dB 1W/1M. Paper cone, treated accordian surround. Net weight: 29 lbs.

#290-200 \$98.90 (1-3) \$89.50 (4-up)



### 3-WAY 100W CROSSOVER

12 dB/octave rolloff.  
800Hz, 5000Hz  
crossover points. 8  
ohm. 100 watts RMS.  
#260-210 \$12.50 (1-9) \$9.95 (10-up)



### SPEAKER CONTROL PANEL

Panel with 50 watt L-pads for tweeter and midrange and built-in LED power meter. 5" x 2 1/2" 100 watt version available  
#260-235 \$14.50 (1-5) \$12.90 (6-up)



### 12" POLY WOOFER

Super duty, 40 oz. magnet. 100 watts RMS, 145 watts max. 4 and 8 ohm compatible (6 ohm). 2" voice coil. fs = 25 Hz. QTS = .166. VAS = 10.8 cu ft. Response: 25-1500 Hz. Net weight: 9 lbs. Pioneer #A30GU40 51D  
#290-125 \$36.80 (1-3) \$34.50 (4-up)



### 15" WOOFER

Original Sanyo woofer. Paper cone with vented dust cap and treated cloth surround. 60 oz. magnet. 60 watts RMS, 85 watts max. 8 ohm. Resonance: 26 Hz. Response: 25-2,500 Hz.

#291-155 \$23.80 (1-5) \$21.90 (6-up)



### 12" SUB WOOFER

Dual voice coil subwoofer. 30 oz. magnet, 2" voice coils. 100 watts RMS, 145 watts max. fs = 25 Hz. 6 ohm (4 and 8 ohm compatible). SPL = 99 dB 1W/1M. Response: 25-700 Hz. QTS = .31, VAS = 10.3 cu. ft. Pioneer #A30GU30-5SD. Net weight: 6 lbs.

#290-145 \$39.80 (1-3) \$36.80 (4-up)



### PIONEER HORN

Mylar dome. 2.93 oz. barium ferrite magnet. 8 ohm. Response: 1800-20000 Hz. 35W RMS, 50W max. fs = 2000 Hz. SPL = 106 dB. Pioneer #AHE60-51F

#270-050 \$6.50 (1-9) \$5.90 (10-up)



### 15" THRUSTER WOOFER

Thruster by Eminence. Made in USA. Poly foam surround, 56 oz. magnet. 2-1/2", 2 layer voice coil. 150 watts RMS, 210 watts max. 4 ohm. fs = 23.5 Hz. QTS = .33, VAS = 17.9 cu ft. SPL = 94.8 dB 1W/1M. Net weight: 15 lbs.

#290-180 \$43.50 (1-3) \$39.80 (4-up)



### GRILL FRAME KIT

With this kit you can make speaker grill frames up to 30" x 40". Kit includes 4 corner pieces, 2 7" frame bars. Grill mounting kit included.

#260-333 \$8.50 (1-9) \$7.80 (10-up)



### TITANIUM COMPOSITE TWEETER

Titanium is deposited on a polymer dome to combine the advantages of both hard and soft dome technologies. 8 ohm. Ferro fluid cooled voice coil. fs = 1200 Hz. SPL = 90 dB 1W/1M. 50 watts RMS, 70 watts max. 4" round. Polydax part #DTW100T125

#270-047 \$27.50 (1-9) \$24.80 (10-up)



**Parts Express**  
International Inc.

1989 CATALOG  
CALL TOLL FREE 1-800-334-6531

FREE CATALOG

## LEARN TV/VCR REPAIR

Now you can train at home in spare time for a money-making career as a TV-VCR Repair Specialist. No previous experience necessary. No need to quit your job or school. Everything is explained in easy-to-understand language with plenty of drawings, diagrams and photos. We show you how to troubleshoot and repair video-cassette recorders and TV sets, how to handle house calls and shop repairs for almost any make of television or VCR. Tools are included with your course so you can get "hands-on" practice as you follow your lessons step by step. Send for free facts about the exciting opportunities in TV VCR Repair and find out how you can start making money in this great career. MAIL COUPON TODAY

ICS SCHOOL OF TV/VCR REPAIR, Dept. DE080  
925 Oak Street, Scranton, PA 18515

Please send me full information and color brochure on how I can learn TV VCR Repair at home in my spare time. I understand there is no obligation and no salesman will visit me.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. # \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone ( ) \_\_\_\_\_

ELECTRONIC review Detailed electronics reviewing for bettering grades, interviews, and promotions. Over 300 pages \$39.95 include \$4.25 shipping. **USER-Graphics**, Education Department, 7136 Everett, Boise, ID 83704-7415.

LEARN IBM PC assembly language. 80 programs. Disk \$5.00. Book \$18.00. ZIPFAST, Box 12238, Lexington, KY 40581-2238.

TURN your love into a living! The professional video industry needs qualified technicians. Institute of Audio Research, the world leader in audio education, announces the **Video Technology Program** for people like you. In under a year turn your flair for electronics into highly marketable skills. Grads work in broadcast television, production companies, manufacturers, corporate communications, etc. Financial aid available if qualified. HS diploma or GED required. **INSTITUTE OF AUDIO RESEARCH**, 64 University Place, New York, NY 10003. (800) 544-2501. NY, NJ, CT (212) 777-8550.

## ANTIQUE RADIO CLASSIFIED

### Free Sample!

Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.



6-Month Trial: \$13. 1-Yr: \$24 (\$36-1st Class).  
A.R.C., P.O. Box 802-L6, Carlisle, MA 01741

## WANTED

**INVENTIONS/new products/ideas wanted:** Call TLCI for free information. 1 (800) 468-7200 24 hours/day - USA/Canada.

**TRAVEL!** High income! Radio officers wanted for shipboard employment. Must have FCC Second Telegraph license. Rae Echols, **AMERICAN RADIO ASSOCIATION**, 5700 Hammonds Ferry, Linthicum Heights, MD 21090. (301) 850-5379.

**INVENTORS!** Confused? Need help? Call **IMPAC** for free information package. In US and Canada: 1 (800) 225-5800.

**WANTED: Australian Kit Supplier** is seeking bulk suppliers of any interesting new and disposal electronic components and assemblies: Eg: image converter tubes (RCA 6032, RCA 6929, XX1080 etc.), laser tubes/diodes/accessories, lens assemblies, small C.R.O. tubes, etc. etc., **OATLEY ELECTRONICS**, PO Box 89, Oatley, N.S.W. 2223, Sydney, Australia Ph: (02) 5794985 Fax: (02) 5707910.

**NUTS & VOLTS**  
MAGAZINE


P.O. Box 1111-E  
Placentia, CA 92670  
714-832-7721

**GIVE YOURSELF A BREAK — A PRICE BREAK!**  
NUTS & VOLTS WILL ~~Save~~ YOU MONEY  
ON ELECTRONIC PARTS & EQUIPMENT  
PLUS SHOW YOU WHERE TO FIND UNIQUE,  
UNUSUAL AND HARD-TO-FIND ITEMS.  
SUBSCRIBE TODAY!  
Orders Only 800-783-4624

Air Mail  
Foreign 1 YR \$55.00

A National Publication For The Buying And Selling Of Electronic Equipment
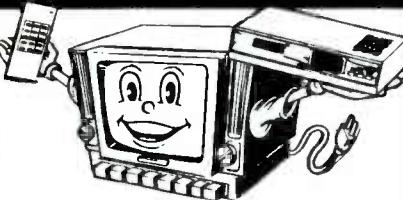
## CABLE T.V. CONVERTERS WHY PAY A HIGH MONTHLY FEE?



All Jerrold, Oak, Hamlin, Zenith, Scientific Atlanta, Magnavox and all specialized cable equipment available for shipment within 24 hours. For fast service MC / VISA or C.O.D. telephone orders accepted (800) 648-3030 60 Day Guarantee (Quantity Discounts) 8 A.M. to 5 P.M. C.S.T. **CLOSED WEEKENDS**. Send self-addressed Stamped envelope (60¢ postage) for Catalog.

**MIDWEST ELECTRONICS INC.**

P.O. Box 5000  
Suite 311 (R)  
Carpentersville, IL 60110

No Illinois Orders Accepted.

## BUSINESS OPPORTUNITIES

**EASY** work! Excellent pay! Assemble products at home. Call for information. (504) 641-8003 Ext. 5192.

**MAKE** \$50/hr working evenings or weekends in your own electronics business. Send for free facts. **INDUSTRY**, Box 531, Bronx, NY 10461.

## TUBES - 2000 TYPES DISCOUNT PRICES!



Early, hard-to-find, and modern tubes. Also transformers, capacitors and parts for tube equipment. Send \$2.00 for 24 page wholesale catalog.

## ANTIQUE ELECTRONIC SUPPLY

688 W. First St. • Tempe, AZ 85281 • 602/894-9503

**LEARN** to clean/repair fax machines. Huge new market! Earn \$85/hour. No experience necessary. Free details call 1 (800) 537-0589 or write to: **VIEJO PUBLICATIONS**, 3540 Wilshire Blvd. #310, Dept. FX200, LA, CA 90010.

**MAKE** \$75,000 to \$250,000 yearly or more fixing IBM color monitors (and most brands). No investment. Start doing it from your home. (A telephone required.) Information, USA, Canada \$1.00 cash. US funds. other countries \$8.00 **RANDALL DISPLAY**, Box 2168-R, Van Nuys, CA 91404 USA.

**INVENTORS:** We submit ideas to industry. Find out what we can do for you. Call 1 (800) 288-IDEA.

# AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

<b>PLANS PARTS IN STOCK</b>	GRA1 — ANTI GRAVITY GENERATOR	\$10.00
	LC7 — 40 WATT BURNING CUTTING LASER	\$20.00
	RUB4 — HI POWER PULSED DRILLING LASER	\$20.00
	BTCS — 1 MILLION VOLT TESLA COIL	\$20.00
	MCP1 — HI VELOCITY COIL GUN	\$15.00
	LLS1 — LASER LIGHT SHOW 3 METHODS	\$20.00
	EH1 — ELECTRONIC HYPNOTISM TECHNIQUES	\$8.00
	ELM1 — LOWER POWERED COIL GUN LAUNCHER	\$8.00
	JACOB LADDER 3 MODELS	\$10.00
	SD5 — SEE IN THE DARK	\$10.00
	LEV1 — LEVITATION DEVICE	\$10.00

<b>KITS ASSISTANCE PROGRAM AVAILABLE</b>	FMV1K — 3 MILE FM VOICE TRANSMITTER	\$34.50
	PFS1K — HAND CONTROLLED PLASMA FIRE SABER	\$49.50
	NIG7K — HI FIUX NEGATIVE ION GENERATOR	\$34.50
	PG5K — PLASMA LIGHTNING GLOBE	\$49.50
	LHC2K — VISIBLE SIMULATED 3 COLOR LASER	\$44.50
	HOD1K — HOMING/TRACKING BEEPER TRANSMITTER	\$44.50
	LGU6K — 2.5 MW HAND-HELD VISIBLE LASER GUN	\$249.50
	BTC3K — 250,000 VOLT TABLE TOP TESLA COIL	\$249.50
	IOG2K — ION RAY GUN, project energy without wires	\$129.95
	TKE1K — TELEKINETIC ENHANCER/ELECTRIC MAN	\$79.50
	VWP7K — 3 MILE AUTO TELEPHONE TRANSMITTER	\$49.50

<b>ASSEMBLED</b>	<b>ASSEMBLED IN OUR LABS</b>	
	LIST10 — INFINITY XMTR Listen in via phone lines	\$199.50
	IPG70 — INVISIBLE PAIN FIELD BLAST WAVE GENERATOR	\$74.50
	ITM10 — 100,000 VOLT INTIMIDATOR UP TO 20'	\$99.50
	TAT30 — AUTOMATIC TELEPHONE RECORDING DEVICE	\$24.50
	PSP40 — PHASOR SONIC BLAST WAVE PISTOL	\$89.50
	DNE10 — ALL NEW 26" VIVID COLORED NEON STICK	\$74.50
	LGU20 — .5 TO 1MW VISIBLE RED HeNe LASER GUN	\$199.50
	BLS10 — 100,000 WATT BLASTER DEFENSE WAND	\$89.50

**EASY ORDERING PROCEDURE** - TOLL FREE 1-800-221-1705  
or 24 HRS ON 1-603-673-4730 or FAX IT TO 1-603-672-5406  
VISA, MC, CHECK, MO IN US FUNDS. INCLUDE 10% SHIPPING. ORDERS  
\$100.00 & UP ONLY ADD \$10.00. CATALOG \$1.00 OR FREE WITH ORDER.

**INFORMATION UNLIMITED**  
P.O. BOX 716, DEPT. R2, AMHERST, NH 03031

# MARK V ELECTRONICS, INC.

## Competitive Pricing \* Fast Shipping

▲ indicates the level of difficulty in the assembling of our Products.

<i>Special Offer</i>	Amplifier	TA-3600	TA-477	TA-802	TA-1000A
	Metal Cabinet	LG-1925	LG-1925	LG-1924	LG-1924
	Transformer	#007	#003	#001	#001
	Kit Set	\$138.60	\$115.20	\$91.75	\$104.12
	Asmb. Set	\$160.20	\$130.50	\$104.15	\$122.92

Due to this special offer & low price, we can only exchange or repair any of these units (TA-3600, TA-477, TA-802 & TA-1000A) within 15 days of your receipt.

The above prices are for the complete sets. For separate unit price, please see below.

## AMPLIFIERS

### KIT ASSMB.

TA-3600

TA-477

TA-802


TA-1000A

## ORDER IN CALIFORNIA 800-521-MARK

## ORDER OUTSIDE CA 800-423-3483

## FREE CATALOG & INFORMATION (213)888-8988

## FAX (213) 888-6868

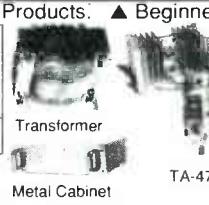

## MISCELLANEOUS

### KIT ASSMB.

TA-3600

TA-477

TA-802

TA-1000A

TA-377A

TA-377B

TA-377C

TA-377D

TA-377E

TA-377F

TA-377G

TA-377H

TA-377I

TA-377J

TA-377K

TA-377L

TA-377M

TA-377N

TA-377O

TA-377P

TA-377Q

TA-377R

TA-377S

TA-377T

TA-377U

TA-377V

TA-377W

TA-377X

TA-377Y

TA-377Z

TA-377AA

TA-377BB

TA-377CC

TA-377DD

TA-377EE

TA-377FF

TA-377GG

TA-377HH

TA-377II

TA-377JJ

TA-377KK

TA-377LL

TA-377MM

TA-377NN

TA-377OO

TA-377PP

TA-377QQ

TA-377RR

TA-377SS

TA-377TT

TA-377UU

TA-377VV

TA-377WW

TA-377XX

TA-377YY

TA-377ZZ

TA-377AA

TA-377BB

TA-377CC

TA-377DD

TA-377EE

TA-377FF

TA-377GG

TA-377HH

TA-377II

TA-377JJ

TA-377KK

TA-377LL

TA-377MM

TA-377NN

TA-377OO

TA-377PP

TA-377QQ

TA-377RR

TA-377SS

TA-377TT

TA-377UU

TA-377VV

TA-377WW

TA-377XX

TA-377YY

TA-377ZZ

TA-377AA

TA-377BB

TA-377CC

TA-377DD

TA-377EE

TA-377FF

TA-377GG

TA-377HH

TA-377II

TA-377JJ

TA-377KK

TA-377LL

TA-377MM

TA-377NN

TA-377OO

TA-377PP

TA-377QQ

TA-377RR

TA-377SS

TA-377TT

TA-377UU

TA-377VV

TA-377WW

TA-377XX

TA-377YY

TA-377ZZ

TA-377AA

TA-377BB

TA-377CC

TA-377DD

TA-377EE

TA-377FF

TA-377GG

TA-377HH

TA-377II

TA-377JJ

TA-377KK

TA-377LL

TA-377MM

TA-377NN

TA-377OO

TA-377PP

TA-377QQ

TA-377RR

TA-377SS

TA-377TT

TA-377UU

TA-377VV

TA-377WW

TA-377XX

TA-377YY

TA-377ZZ

TA-377AA

TA-377BB

TA-377CC

TA-377DD

TA-377EE

TA-377FF

TA-377GG

TA-377HH

TA-3

# THE ELECTRONIC GOLDMINE

## BATTERY OPERATED BLACK LIGHT KIT

- ★ Detects Invisible Fluorescent Inks, Fluorescent Minerals, etc.
- ★ Uses Large Unfiltered U Shaped Black Light Tube



**UNIQUE**

- ★ Comes with PC Board, Parts, Tube and Instructions
- ★ Operates from Any 6V Battery Source (not incl.)
- ★ Size of Board: 7" x 1.8"

**C6356 \$19.95**

## MINI GEIGER COUNTER KIT

- ★ Detects ALL Types of Radiation
- ★ Uses Sensitive Alpha Window Tube
- ★ Operates from 9V Battery (not incl.)
- ★ Comes with PC Board, Parts, Tube and Instructions
- ★ Size of PC Board: 3" x 1.9"

**C6430 \$59.95**

## 20W + 20W STEREO AMP KIT

- ★ Boost Car Stereo, Tape Players, Portable Radios, etc.
- ★ Features 2 Separate 20W RMS Amps with Level Controls
- ★ Operates on Standard 12V Car Battery
- ★ Comes with PC Board, Parts and Instructions you supply speakers
- ★ Size of PC Board: 6" x 2.25"


**C6442 \$19.95**

## INFRARED DETECTOR KIT

- ★ Detects ALL Types of Infrared (TV/VCR Remotes, LEDs)
- ★ Produces Sound and Bright Red LED Output
- ★ Operates on 9V Battery (not incl.)
- ★ Comes with PC Board, Parts and Instructions
- ★ Size of PC Board: 2.5" x 1.4"



**G514 \$1.29**

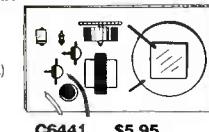

**C6441 \$5.95**

## INFRARED MODULE

Small infrared receiver module is sensitive to almost all infrared remote controllers and features high gain. Has only 3 hookups. Operates from 9VDC and is very sensitive (will light an LED or close a low voltage relay from up to 50ft away). Module and hookup diagram only—you provide output device of LED or relay. Size of PC Board: 9" x 3" x 4".



**INFRARED LED**  
Jumbo clear case  
A1013 2/\$1.00 100/\$40.00  
\$2.00 EACH 100/\$70.00



**INVERTER TRANSFORMER**

Small 4 lead transformer to be used with 556 IC circuit to convert 12VDC to 250VAC for strobes fluorescent tubes. Comes with schematic.

N1703 \$2.00 EACH 100/\$70.00

**MINIMUM ORDER: \$10.00 plus \$3.00 shipping and handling.**

We accept MC, Visa and Money Orders.

**SEND ORDERS TO:** The Electronic Goldmine  
P.O. Box 5408 Scottsdale, AZ 85261  
PHONE ORDERS: (602) 451-7454

**CIRCLE 176 ON FREE INFORMATION CARD**

## PRESENTING ★ ★ ★ ★ CABLE TV DESCRAMBLERS ★ ★ ★ ★

### STARRING ★ ★ ★ ★ JERROLD, HAMLIN, OAK AND OTHER FAMOUS MANUFACTURERS

- FINEST WARRANTY PROGRAM AVAILABLE
- LOWEST RETAIL/WHOLESALE PRICES IN U.S.
- ORDERS SHIPPED FROM STOCK WITHIN 24 HOURS

FOR FREE CATALOG ONLY 1-800-345-8927

FOR ALL INFORMATION 1-818-709-9937

**PACIFIC CABLE CO., INC.**  
7325½ Reseda Blvd., Dept. 1000  
Reseda, CA 91335

## BEST BY MAIL

Rates: Write National, Box 5, Sarasota, FL 34230

BOOKS · CATALOGS · MAGAZINES

FREE CATALOG: DESIGNER Clothing, OMEGA, 101(Re) Clematis, Pensacola, FL 32503-2834.

## BUSINESS OPPORTUNITIES

900 PHONE NUMBERS-\$5,000 + possible weekly, little money needed, I'll teach you. Send \$9.95 + \$1.00 S/H. RSI, Box 660(Re), H.V., PA 19006.

## MONEYMAKING OPPORTUNITIES

CLUE INTO PROFITS as a Private Investigator! Details \$1.00! PPS, 11504 Hughes, Houston, TX 77089.

ARE YOU ITCHING to make more money? Details. Grayco, 16123 Crystalcreek, Cerritos, CA 90701.

## OF INTEREST TO ALL

HAVE SOME FUN! Introductions. Confessions. Jokes. Advice. 1-900-FUN-1990. \$9.95 minute.

BANISHED 1,500 YEARS! Translation of Ancient Manuscript, Gospel of Jesus Rediscovered. Free details. Rare Books(Re), 11246 South Postoak, Suite 306, Houston, TX 77035.

ROBOTS! FULLY ASSEMBLED and kits, robot arms, PC interfaces, motor sensors. \$30.00 to \$80,000.00. Catalog \$5.00 refundable with order. HTO, P.O. Box 3084, RSF, CA 92067.

## INVENTORS

**INVENTORS!** Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service 1 (800) 338-5656. In Massachusetts or Canada call (413) 568-3753.

## COMPUTER KITS

General Technics Computer Kits include a complete line of 386, 286, and 300 models. They are designed to offer the highest degree of compatibility with other computers. They're also fun, easy to build, educational, fully IBM compatible, very powerful, and at wholesale prices. All kits are pre-assembled and tested by step assembly manual. Software, one year warranty and our 24 hour support/online phone line. Assembly is available.



ask for your free catalog

# UNICORN - YOUR I.C. SOURCE!

## COLLIMATOR PEN (INFRA-RED)



- Output: 2.5 mW (max.)
- Current: 90-150 mA
- Operating Voltage: 2.2-2.5V
- Wavelength: 820nm
- Collimation: .18mrad (typ.)
- Size: 11mm diameter

**STOCK#** SB1052 **PRICE** \$39.99

## LASER DIODE (INFRA-RED)



- Output: 10 mW (max.)
- Current: 90-150 mA
- Operating Voltage: 2.2-2.5V
- Wavelength: 820nm

**STOCK#** SB1053 **PRICE** \$9.99

## LASER DIODE (VISIBLE-RED)



- Output: 5 mW (max.)
- Current: 65-100 mA
- Operating Voltage: 1.75-2.2V
- Wavelength: 780nm

**STOCK#** LS022 **PRICE** \$19.99

## LASER DIODE (VISIBLE-RED)



- Output: 5 mW (max.)
- Current: 20 mA
- Operating Voltage: 2.2-3.0V
- Wavelength: 665nm

**STOCK#** LS3200 **PRICE** \$129.99

## EPROMS

STOCK#	PINS	DESCRIPTION	1-24	25-99	100+
1702	24	256 x 4 1us	3.99	3.79	3.41
2708	24	1024 x 8 450ns	6.49	6.17	5.55
2758	24	1024 x 8 450ns	3.99	3.79	3.41
2716	24	2048 x 8 450ns (25v)	3.29	3.13	2.82
2716-1	24	2048 x 8 350ns (25v)	3.79	3.60	3.24
TMS2716	24	2048 x 8 450ns	6.29	5.98	5.38
27C16	24	2048 x 8 450ns (25v-CMOS)	3.99	3.79	3.41
2732	24	4096 x 8 450ns (25v)	3.79	3.60	3.24
2732A-2	24	4096 x 8 200ns (21v)	3.79	3.60	3.24
2732A	24	4096 x 8 250ns (21v)	3.69	3.51	3.16
2732A-4	24	4096 x 8 450ns (21v)	3.19	3.03	2.73
TMS2532	24	4096 x 8 450ns (25v)	5.79	5.50	4.95
TMS2532P	24	4096 x 8 450ns (25v-One Time Programmable)	1.99	1.89	1.70
27C32	24	4096 x 8 450ns (25v-CMOS)	4.19	3.98	3.58
2764-20	28	8192 x 8 200ns (21v)	3.99	3.79	3.41
2764	28	8192 x 8 250ns (21v)	3.79	3.60	3.24
2764A-20	28	8192 x 8 200ns (12.5v)	3.99	3.79	3.41
2764A	28	8192 x 8 250ns (12.5v)	3.29	3.13	2.82
TMS2564	28	8192 x 8 250ns (25v)	6.79	6.45	5.81
27C64	28	8192 x 8 250ns (21v-CMOS)	4.19	3.98	3.58
27128-20	28	16,384 x 8 200ns (21v)	5.79	5.50	4.95
27128	28	16,384 x 8 250ns (21v)	5.09	4.84	4.35
27C128A	28	16,384 x 8 250ns (21v)	5.79	5.50	4.95
27256-20	28	32,728 x 8 200ns (12.5v)	5.29	5.03	4.53
27256	28	32,768 x 8 250ns (12.5v)	4.79	4.55	4.09
27C256	28	32,768 x 8 250ns (12.5v-CMOS)	5.29	5.03	4.53
27512-20	28	65,536 x 8 200ns (12.5v)	7.49	7.12	6.41
27C512	28	65,536 x 8 250ns (12.5v)	6.99	6.64	5.98
27C1024	32	131,072 x 8 200ns (12.5v-CMOS)	17.99	17.59	15.38
68764	24	8192 x 8 450ns	13.99	13.29	11.96
68766	24	8192 x 8 450ns	14.99	14.24	12.82



**UNICORN**  
ELECTRONICS



10010 Canoga Ave., Unit B-8 • Chatsworth, CA 91311

OUTSIDE CALIFORNIA: (800) 824-3432 (Orders Only)

IN CALIFORNIA: (818) 341-8833

ORDER BY FAX: (818) 998-7975

Minimum Order: \$15.00

**CIRCLE 186 ON FREE INFORMATION CARD**

[www.americanradiohistory.com](http://www.americanradiohistory.com)

QUALITY PARTS • DISCOUNT PRICES • FAST SHIPPING

# ALL ELECTRONICS CORP.

## PIEZO BUZZER

Star# HMB-06  
Operates from 4-6 Vdc.  
TTL compatible.  
Draws 20 mA @ 6 Vdc. Emits high pitched  
signal. 0.62 diameter, 0.55" high. PC pins.  
CAT# PBZ-06 \$1.50 each



## PHOTO RESISTOR

100 ohms light  
16K ohms dark.  
0.18" dia. X .08" high.  
0.18" long leads. CAT# PRE-7 2 for \$1.00  
100 for \$45.00 • 1000 for \$400.00



## SWITCHES

ITT PUSH BUTTON  
ITT MDPL series. 3/4" X  
1/2" grey rectangular key  
cap. S.P.S.T. N.O. Push  
to close. RATED: 0.1 amp switching.  
0.25 amp carry current. P.C. mount.  
CAT# PB-8 65¢ each • 10 for \$6.00  
100 for \$50.00



## SPDT PUSHBUTTON

Marquardt# 1843  
Rated 6 amps @ 125/250 Vac.  
Black plastic pushbutton.  
Switch body: .92" X .94" X .65".  
CAT# PB-18 \$1.65 ea. • 10 for \$15.00



## PUSHBUTTON SWITCH

GC/Thornsen# 35-420  
S.P.S.T. normally open momentary  
pushbutton switch. Red plastic  
actuator. 0.57" diameter. Chrome  
bezel 0.68" diameter. Threaded bushing  
mounts in .50" diameter hole. Rated  
3 amp @ 250Vac. Solder loop terminals.  
CAT# PB-20 \$1.00 each



## THUMBWHEEL SWITCH

1 pole 10 position  
decimal encoded  
switches which  
interlock to make  
up desired number  
or digits. Terminates to 11 pc pins (1 com-  
mon and 10 poles). Each section measures  
.31" wide X .20" high X .78" deep. End plates  
can be added to form a 94" high bezel.  
CAT# SWTH-9 \$1.25 each  
10 for \$10.00

2 END PLATES - CAT# SW-9EC \$1.00/Set

ALL PLUG DIRECTLY  
INTO 120 VAC  
OUTLET

6 Vac @ 600 ma. CAT# ACTX-660 \$3.50  
8.3 Vdc @ 10 ma. CAT# DCTX-8310 \$1.50  
12 Vdc @ 500 ma. CAT# DCTX-125 \$4.50  
9 Vdc @ 1 amp. CAT# DCTX-951 \$5.00  
24 Vac @ 625 ma. CAT# ACTX-2462 \$3.00

12 VOLT D.C. - S.P.D.T.

Aromat# RSD-6V

Super small relay.

Rated: 1 amp @

30 Vdc, TTL direct drive possi-  
ble. Operates on 4.3 to 14 Vdc.

Coil: 220 ohms. 1 3/16" X 13/32" X 7/16". CAT# RSD-6V

\$1.50 each • 10 for \$13.50

12 VOLT D.C.  
D.P.D.T.

DIP RELAY

Miniature relay

fits standard 16 pin (dip) sockets

or will directly mount to p.c.

boards. GI Clare# LM44D00

280 ohm • 30 each

CAT# CRLY-12 \$2.50 each

24 VOLT D.C. COIL

KUP style

11 pin base

can be socketed.

direct soldered or quick

connect terminals can be used.

1 3/8" X 1 1/2" X 2". 3.P.D.T. •

5 amp contacts • 470 ohm

CAT# RLY-3524 \$2.25 each

## 16 CHARACTER LCD DISPLAY

Hitachi# LM015  
16 character dot matrix LCD display with built-in  
controller/decoder. Interfaces with 4 or 8 bit MPU.  
Displays alphanumeric, kanji characters and  
symbols. CMOS - low power dissipation.  
Operates on 5 Vdc. Module size: 3.14" X 1.40".  
Display area: 2.53" X 0.54".  
Character size: 0.25" high X 0.115" wide.  
Programming and hook-up instructions included.  
CAT# LCD-1 \$9.50 each



## INSTRUMENT ENCLOSURES

High quality molded ABS  
instrument enclosures.  
Integrated PC board  
stands off and two sets of  
vertical mounting slots for  
front and rear sub panels. All enclosures are  
6" wide X 6 1/4" deep. Choice of three heights.  
Includes non-skid rubber feet and hardware.  
Available in beige, ivory, black, and blue.  
Panel ht. CAT#  
2 1/4" CAT# MB-A \$7.50 each 10 for \$65.00  
2 5/8" CAT# MB-B \$7.75 each 10 for \$67.50  
3" CAT# MB-C \$8.00 each 10 for \$70.00  
Please specify color.



## SOUND ACTIVATED SWITCH

PC board with electret mike responds  
to sounds in immediate vicinity. Originally  
part of sound activated light organ. Shuts  
off when sound is not present. Includes  
hook-up diagram.  
CAT# SAB-2 \$2.50 each



## SWITCHES

ITT PUSH BUTTON  
ITT MDPL series. 3/4" X  
1/2" grey rectangular key  
cap. S.P.S.T. N.O. Push  
to close. RATED: 0.1 amp switching.  
0.25 amp carry current. P.C. mount.  
CAT# PB-8 65¢ each • 10 for \$6.00  
100 for \$50.00



## SPDT PUSHBUTTON

Marquardt# 1843  
Rated 6 amps @ 125/250 Vac.  
Black plastic pushbutton.  
Switch body: .92" X .94" X .65".  
CAT# PB-18 \$1.65 ea. • 10 for \$15.00



## PUSHBUTTON SWITCH

GC/Thornsen# 35-420  
S.P.S.T. normally open momentary  
pushbutton switch. Red plastic  
actuator. 0.57" diameter. Chrome  
bezel 0.68" diameter. Threaded bushing  
mounts in .50" diameter hole. Rated  
3 amp @ 250Vac. Solder loop terminals.  
CAT# PB-20 \$1.00 each



## THUMBWHEEL SWITCH

1 pole 10 position  
decimal encoded  
switches which  
interlock to make  
up desired number  
or digits. Terminates to 11 pc pins (1 com-  
mon and 10 poles). Each section measures  
.31" wide X .20" high X .78" deep. End plates  
can be added to form a 94" high bezel.  
CAT# SWTH-9 \$1.25 each  
10 for \$10.00

2 END PLATES - CAT# SW-9EC \$1.00/Set

## NICKEL-CAD BATTERIES (RECHARGEABLE)

AAA SIZE \$1.50 each  
1.2 volts 180 mAh  
CAT# NCB-AAA

AA SIZE \$2.00 each  
1.25 volts 500 mAh  
CAT# NCB-AA

AA SIZE \$2.20 each  
WITH SOLDER TABS  
CAT# NCB-SAA

C SIZE \$4.25 each  
1.2 volts 1200 mAh  
CAT# NCB-C

D SIZE \$4.50 each  
1.2 volts 1200 mAh  
CAT# NCB-D

## XENON TUBE

1" long flashtube with 3 1/2" red,  
and black leads. Ideal for elec-  
tronic flash or strobe projects.  
CAT# FLT-3 2 for \$1.00

## RELAYS

### 6 VOLT D.C. - S.P.D.T.

Aromat# RSD-6V

Super small relay.  
Rated: 1 amp @

30 Vdc, TTL direct drive possi-  
ble. Operates on 4.3 to 14 Vdc.

Coil: 220 ohms. 1 3/16" X 13/32" X 7/16". CAT# RSD-6V

\$1.50 each • 10 for \$13.50

### 12 VOLT D.C. COIL

D.P.D.T.

DIP RELAY

Miniature relay

fits standard 16 pin (dip) sockets

or will directly mount to p.c.

boards. GI Clare# LM44D00

280 ohm • 30 each

CAT# CRLY-12 \$2.50 each

### 24 VOLT D.C. COIL

KUP style

11 pin base

can be socketed.

direct soldered or quick

connect terminals can be used.

1 3/8" X 1 1/2" X 2". 3.P.D.T. •

5 amp contacts • 470 ohm

CAT# RLY-3524 \$2.25 each

## 0 - 6 HOUR AUTO SHUT-OFF TIMER

M.H. Rhodes, Inc Mark-Time# 90007

Timer fits standard  
3" deep wallbox. Rated  
20 amps @ 125 Vac Turn  
knob to desired time.  
Includes hardware, beige  
wallplate, and knob. UL  
and CSA listed. CAT# TMC-6  
\$5.75 each • 10 for \$50.00



## SPECIAL PURCHASE 210 MFD 330 V PHOTOFORCE CAPACITOR

Rubicon CE photoflash capacitor.  
0.79" dia. X 1.1" high. These are  
new capacitors that have been  
prepped with 1.4" black and red  
wires soldered to the terminals.  
CAT# PPC-210 \$2.50 each  
10 for \$22.50 • 100 for \$200.00  
Large quantities available. Call for pricing.



## STEPPER MOTOR

Airpax P/N C82711-M1  
17 Vdc dual coil.  
Permanent magnet stepper.  
22.5 ohm coil. 7.5 degrees per step.  
CAT# SMT-6 \$6.00 each • 10 for \$50.00



## ELECTRONIC GAME BOARD

The inner workings of an electronic Scrabble  
game. Operates on 6 Vdc. 8 digit alpha-  
numeric readout, 45 button keypad, 14 transis-  
tors, 2 I.C.'s, 1 piezo element and other good-  
ies. Top and bottom row of keypad buttons  
are function keys, middle 3 rows are alphabetic.  
No instructions available. 6" X 4.45".  
CAT# ST-4 \$1.75 each 10 for \$15.00

## RG-11/U 75 OHM VIDEO CABLE

100 ft. or 200 ft. rolls  
of RG 11/U terminated  
to heavy duty F connectors.  
Includes 75 ohm terminator  
and F-61 splices on one end.  
New cables manufactured for IBM PC net-  
works. IBM P/N 1501908 PC/SCOPE.  
CAT# RG-11-1 100 ft. roll \$15.00  
CAT# RG-11-2 200 ft. roll \$27.50



## LED'S

STANDARD JUMBO  
DIFFUSED T 1-3/4 size

RED CAT# LED-1  
10 for \$1.50 • 100 for \$13.00

GREEN CAT# LED-2  
10 for \$2.00 • 100 for \$17.00

YELLOW CAT# LED-3  
10 for \$2.00 • 100 for \$17.00

## FLASHING LED

with built in flashing circuit  
operates on 5 volts...

RED \$1.00 each  
CAT# LED-4 10 for \$9.50

GREEN \$1.00 each  
CAT# LED-4G 10 for \$9.50

## LED HOLDER

Two piece holder.  
CAT# HLED-1 10 for 65¢

## RECTANGULAR LED, SPECIAL

#HLM0301

Red diffused  
rectangle 0.28" X 0.1" X 0.29"  
high. Ideal for bargraphs, chasers,  
etc. CAT# RLED-4  
10 for \$1.50 • 100 for \$12.00  
100 for \$100.00

## LED GRAB BAG

50 assorted

L.E.D.'s  
Many different  
shapes, colors, sizes. Round,  
rectangular, curved, etc.

CAT# GRLED  
\$4.00 per assortment

## OPTO SENSOR

U shaped package  
with mounting ears.

1/8" opening.

3/4" mounting ears.

CAT# OSU-6 50¢ each

10 for \$4.50 • 100 for \$40.00

## REFLECTIVE OPTO SENSOR

Optek# K-8711

Wedge shaped device with IR

emitter and receiver pointing

the same direction. Light rays

from emitter bounce off nearby

object and register on receiver.

Effective range approx. 0.15".

CAT# OSR-1 75¢ each


## L.E.D. FLASHER KIT

Two L.E.D.'s flash in  
unison when a 9 volt  
battery is attached.  
This kit includes a  
p.c. board, all the parts  
and instructions to make a simple flasher  
circuit. A quick and easy project for anyone  
with basic soldering skills.  
CAT# LEDKIT \$1.75 per kit


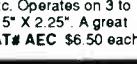
## LED CHASER KIT

Build this variable  
speed led chaser.  
10 leds flash  
sequentially at  
whatever speed  
you set them for.  
Easy to build kit includes p.c. board  
and instructions. Ideal for special lighting  
effects, costumes, etc. Operates on 3 to  
9 volts. PC board is 5" X 2.25". A great  
one hour project. CAT# AEC \$6.50 each



## STEPPING MOTOR CONTROLLER KIT

Learn about  
stepping  
motors while  
building this  
simple circuit.

Includes circuit board and all parts  
except 12 Vdc power supply.

CAT# SMKIT \$18.00 each

## RECHARGEABLE BATTERY PACK (USED)

Four AA nickel cad-  
mium batteries con-  
nected in series to  
make a 4.8 volt pack.  
Batteries are in a  
2 X 2 configuration  
with a 2 pin connector  
attached. The four  
batteries can be  
separated into single  
AA size solder tab  
nickel cadmium batteries  
or resoldered into other configurations.

SPECIAL SALE PRICE NOW

\$3.00 per pack • 10 packs for \$25.00

CAT# NCB-41AAU




ALL ELECTRONICS CORP.  
SPECIALTY PARTS

Call Or Write For Our  
Free 60 Page Catalog

Outside the U.S.A. send \$2.00  
postage for a catalog.

MAIL ORDERS TO: ALL ELECTRONICS CORP. • P.O. BOX 567 • VAN NUYS, CA 91408

CIRCLE 107 ON FREE INFORMATION CARD

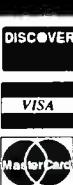

**Intel Math Coprocessors**

8088 or 8086 Systems

8087	5MHz	\$89.95
8087-2	8MHz	\$129.95
8087-1	10MHz	\$169.95

80286 Systems

80287	6MHz	\$139.95
80287-8	8MHz	\$209.95
80287-10	10MHz	\$239.95

80386 Systems

80387-16	16MHz	\$349.95
80387-20	20MHz	\$399.95
80387-25	25MHz	\$499.95
80387-33	33MHz	\$649.95

SIP Modules

41256A9A-80	80ns, 256Kx9	\$54.95
41256A9A-10	100ns, 256Kx9	\$44.95
421000A9A-70	70ns, 1Mx9	\$169.95
421000A9A-80	80ns, 1Mx9	\$124.95
421000A9A-10	100ns, 1Mx9	\$116.95
94000L-80	80ns, 4Mx9	\$499.95
94000L-10	100ns, 4Mx9	\$499.95

SIMM Modules

41256A9B-80	80ns, 256Kx9	\$49.95
41256A9B-10	100ns, 256Kx9	\$39.95
421000A8B-10	100ns, 1Mx8	\$109.95
421000A9B-70	70ns, 1Mx9	\$139.95
421000A9B-80	80ns, 1Mx9	\$119.95
421000A9B-10	100ns, 1Mx9	\$113.95
94000S-80	80ns, 4Mx9	\$499.95
94000S-10	100ns, 4Mx9	\$499.95

NEC V20 & V30 Chips

UPD70108-5	5MHz, V20 Chip	\$5.25
UPD70108-8	8MHz, V20 Chip	\$6.95
UPD70108-10	10MHz, V20 Chip	\$10.95
UPD70116-8	8MHz, V30 Chip	\$7.95
UPD70116-10	10MHz, V30 Chip	\$13.49

Dynamic RAMs

TMS4416-12	120ns, 16Kx4	\$2.25
TMS4416-15	150ns, 16Kx4	\$2.00
4116-12	120ns, 16Kx1	\$1.49
4116-15	150ns, 16Kx1	\$1.09
4116-20	200ns, 16Kx1	\$0.89
4164-100	100ns, 64Kx1	\$2.75
4164-120	120ns, 64Kx1	\$2.39
4164-150	150ns, 64Kx1	\$2.15
4164-200	200ns, 64Kx1	\$1.75
41256-60	60ns, 256Kx1	\$5.25
41256-80	80ns, 256Kx1	\$3.75
41256-100	100ns, 256Kx1	\$3.15
41256-120	120ns, 256Kx1	\$2.95
41256-150	150ns, 256Kx1	\$2.59
41464-80	80ns, 64Kx4	\$5.95
41464-10	100ns, 64Kx4	\$4.95
41464-12	120ns, 64Kx4	\$3.95
41464-15	150ns, 64Kx4	\$3.59
511000P-70	70ns, 1Mx1	\$13.95
511000P-80	80ns, 1Mx1	\$12.95
511000P-10	100ns, 1Mx1	\$12.35
514256P-80	80ns, 256Kx4	\$13.45
514256P-10	100ns, 256Kx4	\$12.95

Static RAMs


6116P-3	150ns, 16Kx1(CMOS)	\$2.79
6264LP-10	100ns, 64Kx1(CMOS)	\$6.95
6264LP-15	100ns, 64Kx1(CMOS)	\$4.95
43256-10L	100ns, 256Kx1	\$10.95
43256-15L	150ns, 256Kx1	\$9.95
62256LP-15	150ns, 256Kx1 (CMOS)	\$10.95

PROTOTYPING PRODUCTS  
 Jameco Solderless Breadboards

JE24	3.25 x 2.125	400	0	\$4.95
JE23	6.5 x 2.125	830	0	\$6.95
JE24	6.5 x 3.125	1,360	2	\$12.95
JE25	6.5 x 4.25	1,660	3	\$17.95
JE26	6.875 x 5.75	2,390	4	\$22.95
JE27	7.25 x 7.5	3,220	4	\$32.95

Prototype  
 Design Stations

WM2

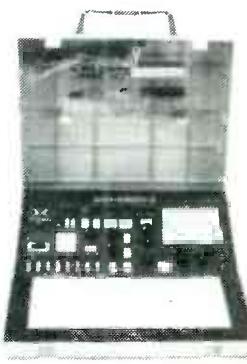

WM1 & WM2 Features:

- Removable solderless breadboard
- Variable and fixed DC power supply
- Multi-frequency signal generator
- Analog multimeter
- 8 bicolor LEDs (red & green)
- 8 logic switches
- Logic probe
- Lighted power switch
- Fuse overload protected
- Sturdy ruggedized case

WM1 Special Features:

- 4 potentiometers
- Built-in speaker

WM2 Special Features:

- Pulse Generator
- Binary coded decimal (BCD) to 7-segment decoder/driver
- DB25 connector
- Frequency counter (1Hz to 1MHz)

WM1 Analog Prototype Station ..... \$199.95

WM2 Digital Prototype Station ..... \$249.95

A.R.T. EPROM Programmer



UVP EPROM Eraser



Soldering and Desoldering Stations

60 Watt Analog Display Soldering Station • Electronic temperature control from 200° to 878°F • Cartridge heating element for a longer life of the soldering tip

XY1683 ..... \$59.95

60 Watt Analog Display Soldering Station • Electronic temperature control from 200° to 878°F • Ceramic heating element for a steady temperature and long life

XY2660 ..... \$89.95

60 Watt Digital Display Soldering Station • Electronic temperature control from 200° to 878°F • Temperature displayed on easy to read .560" H 3-digit LED readout • Nichrome heating element

XY960 ..... \$99.95

30 Watt Electronic Temperature Controlled Desoldering Station • Electronic temperature control from 212° to 842°F • Self-contained high rotary vacuum pump

XY999 ..... \$279.95



Request Jameco's 1990 Catalog for a Complete  
Listing of Components, Test/Measurement  
Equipment and Computer Products



Jameco 20MHz 80386 Desktop Computer Kit



- Fully IBM Compatible
- Free Concurrent 386 (Disk Operating System) Software Included
- 4MB RAM Included, Expandable to 8MB on board, 16MB with optional expansion board
- 8/16/20MHz Keyboard Switchable Operation
- AMI BIOS ROMs Included
- Laptop Case w/200 Watt Power Supply
- Conner High-Performance IDE 3.5" 40MB Hard Disk Drive
- Teac 1.2MB Floppy DSHD Disk Drive
- Multi I/O Card with Universal Floppy Controller
- Fujitsu 101-Key (Enhanced) Keyboard

Shown with VGA Option (not included)  
JE2059 Multiscan Monitor and VGA Card....\$669.90 (See Below)

**JE3551** 20MHz 80386 Compatible Kit.....\$1949.95

Jameco IBM  
PC/XT/AT  
Compatible  
Cards



JE1057

- JE1043 360KB/720KB/1.2MB/1.44MB Floppy Disk Controller Card (PC/XT/AT) .. \$49.95
- JE1050 Monochrome Graphics Card w/Parallel Printer Port (PC/XT/AT) .. \$49.95
- JE1052 Color Graphics Card w/ Parallel Printer Port (PC/XT/AT) .. \$49.95
- JE1055 EGA Card w/ 256KB Video RAM (PC/XT/AT) .. \$139.95
- JE1057 8/16-Bit VGA Card w/ 256KB Video RAM (PC/XT/AT) .. \$199.95
- JE1060 I/O Card w/ Serial, Game, Printer Port & Real Time Clock (PC/XT) .. \$59.95
- JE1062 RS232 Serial Half Card (PC/XT/AT) .. \$29.95
- JE1065 I/O Card w/ Serial, Game and Parallel Printer Port (AT) .. \$59.95
- JE1077 Multi I/O Card w/ 360KB/720KB/1.2MB/1.44MB Floppy Controller (AT) .. \$99.95

EGA, VGA & Multiscan Monitor Packages

Relisys 14" EGA monitor and EGA card package  
(640 x 350 max. resolution)

**JE1059** EGA Monitor & EGA Card.....\$509.90



Relisys 14" Multiscan monitor and 16-bit VGA card package  
(640 x 480 max. resolution)

**JE2059** Multiscan Monitor & VGA Card.....\$669.90



Relisys 14" VGA monitor and 16-bit VGA card package  
(640 x 480 max. resolution)

**JE2061** VGA Monitor & VGA Card.....\$629.90

JE2061

IBM PC/XT/AT  
Compatible Keyboards



FKB4700

**JE2015** 84-Key Standard AT Style Layout .. \$59.95

**FKB4700** 101-Key Enhanced Layout with 12 Function Keys .. \$69.95

MEI 100-Key  
Microtype Keyboard



- IBM PC/XT/AT/386 Compatible
- Saves an amazing 60% of the desk space used by equivalent standard keyboards

**MIRU**.....\$129.95

Jameco  
Digitizer Tablet



- AutoCAD 10 template and four-button puck
- Resolution: up to 1016 lines per inch
- Accuracy: ±0.25"
- Emulates three of the world's most popular formats: Summagraphics MM, Summagraphics Bit Pad One, Calcomp 2000
- EEPROM allows custom configuration

**JCAD** Digitizer Tablet \$199.95

**Stylus** Two Button Stylus .. \$39.95

Floppy  
Disk  
Drives

MF353B

Sony

**MPF11** 3.5" 720KB Disk Drive .....\$69.95

**SMK** 5.25" Installation Kit for MPF11 ..\$14.95

Mitsubishi

**MF353B** 3.5" 720KB Internal Drive .... \$99.95

**MF355B** 3.5" 1.44MB Internal Drive .. \$119.95

**DD1** MF355B Software for systems without

1.44MB disk drive BIOS capability .. \$14.95

Teac

**FD55B** 5.25" 360KB Internal Drive ... \$89.95

**FD55G** 5.25" 1.2MB Internal Drive.... \$99.95

Hard Drives & Tape Back-Up



MiniScribe (XT-MFM)

**M8425XT** 20MB (68ms) 3.5"HH ..... \$289.95

MiniScribe (XT-RLL)

**M8438XT** 30MB (68ms) 3.5"HH ..... \$299.95

**M8450XT** 40MB (46ms) 3.5"HH .. \$369.95

Above Drives Include Hard Disk Drive, Controller & Cables

Conner (AT-IDE)

**CP3044** 40MB (25ms) 3.5"Low Profile \$429.95

**CP3184** 80MB (25ms) 3.5"HH ..... \$649.95

**CP3104** 100MB (25ms) 3.5"HH ..... \$699.95

Modems



9600E  
Pictured

External Modems

**1200C** Datatronics 1200 Baud \$89.95

**2400C** Datatronics 2400 Baud \$149.95

**9600E** Prometheus 9600 Baud \$699.95

Internal Modems

**1200B** Jameco 1200 Baud ..... \$49.95

**2400B** Jameco 2400 Baud ..... \$99.95

Modems listed above Include ProComm Software

IBM  
Compatible  
Cases and  
Power  
Supplies



**JE1010** Flip Top Standard PC/XT Case.....\$39.95

**JE1011** Slide Standard PC/XT Case .. \$39.95

**JE1030** 150 watt PC/XT Power Supply.....\$59.95

**JE1032** 200 watt Baby AT Power Supply ..\$89.95

**JE1035** 300 watt AT Power Supply ..\$139.95

**JE2011** Vertical Case w/300W Pwr. Supply ..\$269.95

**JE2012** Mini Vertical Case w/200W Pwr. Supply ..\$169.95

**JE2019** Flip Top Baby AT Case.....\$69.95



1355 Shoreway Road, Belmont, CA 94002

24 Hour Order Hotline

(415) 592-8097

\$50.00 Minimum Order

FAX's (415) 592-2503 or (415) 595-2664

Telex 176043 - Ans. Back: Jameco Blmt

Data Sheets - 50¢ each

For a FREE 48-Page Flier send \$2.00 to cover

First Class Postage and Handling

© 1990 Jameco Electronics 9/90

CA Residents Add

6.25%, 6.75% or 7.25% Sales Tax  
Shipping - Add 5% plus \$1.50 Insurance

(May vary according to weight and shipping method)

Terms: Prices subject to change without notice.

Items subject to availability and prior sale.

Complete list of terms/warranties is available upon request.

IBM is a registered trademark of International Business Machines



Please  
refer to  
**Key 2**  
when  
ordering

Customer Service • Technical Assistance • Credit Department • All Other Inquiries • (415) 592-8097 • 7AM - 4PM P.S.T.

CIRCLE 114 ON FREE INFORMATION CARD

www.americanradiohistory.com

SEPTEMBER 1990

## COMPUTERS FOR LE\$\$

10 MHz 8088 System.....\$369

- 4.77/10 MHz 8088 Motherboard
- 256 KB RAM (640KB max)
- 150 Watt Power Supply
- Floppy Disk Controller
- One 5.25" 360 KB Floppy Drive
- MonoGraphics Card w/ Parallel Port
- 101 Key Enhanced Keyboard
- Case (3 LEDs, 2 Buttons, Key-Lock)
- 12" Amber Monochrome Monitor

12 MHz 80286 System.....\$669

- 12 MHz 80286 Motherboard
- 0 Wait State
- 512 KB RAM (4 MB max)
- 200 Watt Power Supply
- Floppy Disk Controller
- One 5.25" 1.2 MB Floppy Drive
- MonoGraphics Card w/ Parallel Port
- 101 Key Enhanced Keyboard
- Case (3 LEDs, 2 Buttons, Key-Lock)
- 12" Amber Monochrome Monitor

One Year Parts & Labor Warranty  
30 Day Satisfaction Guarantee  
Shipping & Handling Extra

VISA & M/C add 3% Amex add 4%  
Price & Availability subject to change  
without prior notice

**JINCO COMPUTERS INC.**  
5122 Walnut Grove Avenue  
San Gabriel, CA 91776  
**Tel: (818) 309-1108**

CIRCLE 177 ON FREE INFORMATION CARD

<b>CABLE TV DESCRAMBLERS</b>	
JERROLD™ Tri-Bi Mode.	\$105.00
JERROLD™ SB-3 OR 2	\$89.00
Hamlin MLD-1200.....	\$99.95
Oak N-12 W/V.S.....	\$99.95
Oak-M-35-B W/V.S.....	\$99.00
OAK E-13.....	\$99.95
Zenith SS AAVI.....	\$185.00
Eagle PD-3.....	\$120.00
Scientific Atlanta.....	\$129.95
SA-Combo's.....	CALL
Tocom.....	\$350.00
Oak N-12 W/Auto.....	\$140.00
Jerrold Starcom CSV....	\$139.95
10 Lot	
\$85.00	
\$65.00	
\$62.00	
\$62.00	
\$78.00	
\$58.00	
\$145.00	
\$85.00	
\$105.00	
Call	
M.D. ELECTRONICS	
WILL MATCH ANY	
ADVERTISED PRICE	
IN THIS MAGAZINE	

\*NEW STARGATE 2000  
CABLE CONVERTER



1-\$89.00 10-\$69.00 100-Call

Last channel recall-Favorite channel select-  
75 channel-Channel scan-Manual fine tune-  
One year warranty-surge protection-HRC & Standard switchable-and much more. Call Today!

INFORMATION(402)554-0417

Orders Call Toll Free  
**1-800-624-1150**

**M.D. ELECTRONICS**  
115 NEW YORK MALL  
SUITE 133E  
OMAHA, NE. 68114

M.C.  
VISA  
C.O.D.

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		
108 AMC Sales .....	13	—	Pacific Cable.....93, 96
182 Ace Communications.....	15	56	Parts Express.....96
75 Ace Products.....	25	199	Photronics.....25
107 All Electronics .....	99	101	Pomona Electronics.....15
— Amazing Concepts.....	92, 97	78	Radio Shack.....32
84 Appliance Service.....	25	190	SCO Electronics.....18
67 Banner Technical Books .....	14	180	Sencore.....8
98 Beckman Industrial .....	13	—	Star Circuits.....26
109 C&S Sales .....	24, CV3	185	TECI.....84
— CB City .....	91	92	Tektronix.....CV4
70 CEI .....	94	186	Unicorn.....98
— CIE .....	11	64	Universal View.....96
50 Caig Laboratories .....	26	191	U.S. Cable.....18
54 Chemtronics .....	18	178	Viejo Publications.....13
183 Chenesko Products.....	25	179	WPT Publications.....84
— Command Products .....	17		
— Computer Book Club .....	5		
58 Cook's Institute .....	15		
194 D&D Electronics .....	27		
— Damark International .....	14		
127 Deco Industries .....	25		
176 Electronic Goldmine .....	98		
— Electronic Tech. Today .....	67		
— Electronics Book Club .....	28		
121 Fluke Manufacturing .....	CV2		
189 Global Specialties .....	3		
— Grantham College .....	80		
188 HUB Material Company .....	67		
86 Heathkit .....	17		
187 International Components Corp. .	94		
114 Jameco .....	100		
177 Jinco Computers .....	102		
192 Joseph Electronics .....	27		
— King Wholesale .....	92		
193 Loch Ness, Inc. ....	25		
87 MCM Electronics .....	95		
181 MD Electronics .....	102		
93 Mark V. Electronics .....	97		
— McGraw Hill Book Club .....	38		
61 Microprocessors Unltd. ....	89		
117 Mouser .....	82		
— NRI Schools .....	21, 87		
184 Optoelectronics .....	23		

### ADVERTISING SALES OFFICE

**Gernsback Publications, Inc.**

**500-B Bi-County Blvd.**

**Farmingdale, NY 11735**

**1-(516) 293-3000**

**President: Larry Steckler**

**Vice President: Cathy Steckler**

**For Advertising ONLY**

**516-293-3000**

**Fax 1-516-293-3115**

**Larry Steckler**

publisher

**Arline Fishman**

advertising director

**Denise Haven**

advertising assistant

**Christina Estrada**

advertising associate

**Kelly McQuade**

credit manager

**Subscriber Customer Service**

**1-800-288-0652**

**Order Entry for New Subscribers**

**1-800-999-7139**

**7:00 AM - 6:00 PM M-F MST**

### SALES OFFICES

#### EAST/SOUTHEAST

**Stanley Levitan**, Eastern Sales Manager

Radio-Electronics

259-23 57th Avenue

Little Neck, NY 11362

1-718-428-6037, 1-212-293-3000

Fax 1-718-225-8594

#### MIDWEST/Texas/Arkansas/Oklahoma

**Ralph Bergen**, Midwest Sales Manager

Radio-Electronics

540 Frontage Road—Suite 339

Northfield, IL 60093

1-708-446-1444

Fax 1-708-446-8451

#### PACIFIC COAST/ Mountain States

**Marvin Green**, Pacific Sales Manager

Radio-Electronics

5430 Van Nuys Blvd. Suite 316

Van Nuys, CA 91401

1-818-986-2001

Fax 1-818-986-2009

# ELENCO & HITACHI PRODUCTS AT DISCOUNT PRICES

**NEW!** RSOs (Real-Time & Storage Oscilloscopes) From HITACHI  
The RSO - it's the new solution

View, Acquire, Test, Transfer and Document Your Waveform Data

## 4-Channel, 100MS/s Model

100MS/s (25MS/s on 4 channels simultaneously), 100MHz, 4kw x 1ch., 2kw x 2ch., 1kw x 4ch. VC-6145 \$4,695.00

## Compact, Full Feature Models

40MS/s, 100MHz, 4kw x 1ch., 2kw x 2ch.

## Introductory Price

VC-6045 \$3,049.00

20MS/s, 50MHz, 2kw x 2ch.

VC-6025 \$2,295.00

## Low Cost/High Value Models


20MS/s, 50MHz, 2kw x 2ch.

VC-6024 \$2,049.00

20MS/s, 20MHz, 2kw x 2ch.

VC-6023 \$1,749.00

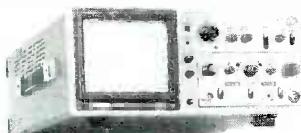RSOs from Hitachi feature such functions as roll mode, averaging, save memory, smoothing, interpolation, pretriggering, cursor measurements, plotter interface, and RS-232C interface. With the comfort of analog and the power of digital.



V-422 40MHz Dual Trace \$795

<b>V-212</b> <b>\$435</b> DC to 20MHz Dual Channel	<b>Hitachi Portable Scopes</b> DC to 50MHz, 2-Channel, DC offset function, Alternate magnifier function V-525 CRT Readout, Cursor Meas. \$1,025 V-523 Delayed Sweep \$995 V-522 Basic Model \$895
---	--

## 20MHz Elenco Oscilloscope



**\$375**

MO-1251

- Dual Trace
- Component Tester
- 6" CRT
- X-Y Operation
- TV Sync
- 2 p-1 Probes

**FREE DMM**  
with purchase of  
**ANY SCOPE**

**SCOPE PROBES**  
P-1 65MHz, 1x, 10x \$19.95  
P-2 100MHz, 1x, 10x \$23.95

## Compact Series Scopes



Delayed Sweep  
Lightweight (13lbs)  
2mV Sens  
3 Yr Warranty


Model V-1065  
Shown

This series provides many new functions such as CRT Readout, Cursor measurements (V-1085/1065/665), Frequency Ctr (V-1085), Sweep time Autoranging and Trigger Lock using a 6-inch CRT. You don't feel the compactness in terms of performance and operation.

V-660	60MHz Dual Trace	\$1,195
V-665	60MHz Dual Trace w/Cursor	\$1,345
V-1060	100MHz Dual Trace	\$1,425
V-1065	100MHz Dual Trace w/Cursor	\$1,695
V-1085	100MHz Quad Trace w/Cursor	\$2,045
V-1100A	100MHz Quad Trace w/Cursor	\$2,295
V-1150	150MHz Quad Trace w/Cursor	\$2,775

## Elenco 35MHz Dual Trace

Good to 50MHz **\$495**

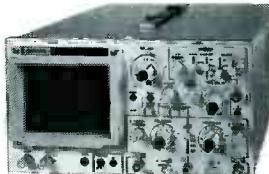

MO-1252

- High luminance 6" CRT
- 1mV Sensitivity
- 6KV Acceleration Voltage
- 10ns Rise Time
- X-Y Operation • Z Axis
- Delayed Triggering Sweep
- Includes 2 P-1 Probes

All scopes include probes, schematics, operators manual, and 3 year (2 yrs for Elenco scopes) world wide warranty on parts & labor. Many accessories available for all Hitachi scopes. Call or write for complete specifications on these and many other fine oscilloscopes.

**WE NOW  
CARRY  
COMPLETE LINE  
OF  
FLUKE  
MULTIMETERS  
Models**

21F 83  
23F 85  
25F 87  
27F 8050A  
73 8060A  
75 8062A  
77F + More

**CALL FOR  
SPECIAL PRICING**



**True RMS 4 1/2  
Digit Multimeter**

**M-7000**

**\$135**

.05% DC Accuracy  
.1% Resistance  
with Freq. Counter  
and deluxe case



**10 Function  
Multimeter**

**CM-365**

**\$65**

AC + DC Voltage & Amps  
Resistance to 2000MΩ  
Diode, Logic, & Trans test  
Capacitance to 200uF

**Digital Capacitance Meter**

**CM-1550**

**\$58.95**

9 Ranges  
.1pF-20,000uF  
.5% basic accy  
Zero control  
with case

**Digital LCR Meter**

**LC-1801**

**\$125**

Measures:  
Coil 1uH-200H  
Caps 1pF-200uF  
Res .01-20M



**Function Generator  
Blox**

**#9600**

**\$28.95**

Provides sine, triangle, square  
wave from 1Hz to 1MHz  
AM or FM capability

**Triple Power Supply XP-620**

Assembled \$65

Kit \$45

2 to 15V at 1A,  
-2 to -15V at 1A  
(or 4 to 30V at 1A)  
and 5V at 3A

Contains all the desired features for doing experiments.

Features short circuit protection, all supplies.

**Wide Band Signal Generators**

**SG-9000**

**\$129**

RF Freq 100K-450MHz  
AM Modulation of 1KHz  
Variable RF output

SG-9500 w Digital Display and 150MHz built-in Counter \$249



**AC Current Meter**

**ST-1010**

**\$69.95**

1000 Amps  
Data & Peak hold  
8 Functions  
Deluxe Case



**Decade Blox**

**#9610 or**

**#9620**

**\$18.95**

#9610 Resistor Blox  
47 ohm to 1M & 100K pot  
#9620 Capacitor Blox  
47pf to 10MFD

**Quad Power Supply XP-580**

**\$59.95**

2-20V at 2A

12V at 1A

5V at 3A

-5V at .5A

Fully regulated and short circuit protected

XP-575 without meters \$39.95

**LEARN TO BUILD AND PROGRAM  
COMPUTERS WITH THIS KIT!**

**INCLUDES: All Parts, Assembly and Lesson Manual**

**Model**

**MM-8000**

**\$129.00**



Starting from scratch you build a complete system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses similar machine language as IBM PC. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 E<sup>2</sup> PROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language.

**ROBOTICS KIT FOR ABOVE (MM-8010) \$71.95**



**Digital Triple Power Supply**

**XP-765**

**\$249**

0-20V at 1A  
0-20V at 1A  
5V at 5A

Fully regulated, Short circuit protected with  
2 limit control, 3 separate supplies  
XP-660 with Analog Meters \$175

**WE WILL NOT BE UNDERSOLD!**  
UPS Shipping: 48 States 5%  
(\$10 Max) IL Res., 7% Tax



**C & S SALES INC.**  
1245 Rosewood, Deerfield, IL 60015  
(800) 292-7711 (708) 541-0710

CIRCLE 109 ON FREE INFORMATION CARD

**15 Day Money Back Guarantee  
2 Year Warranty**

Prices subject to change

**WRITE FOR FREE CATALOG**

# On the line, on the bench, or on the road. The low-cost solution is Tek.

Do you debug the design? Verify the production run? Service the finished product? Then for low-cost solutions built for your application, there's only one place to go.

Tek's 2200 Series oscilloscope family.

There are ten scopes in the 2200 Series, from 20 to 100 MHz and \$695 to \$5495. And three of them demonstrate functional power at its best: the 100 MHz 2232, 50 MHz 2211, and 100 MHz 2245A.

If you can't afford to miss a thing, get the 2232 digital storage oscilloscope.

With 100 MS/s sampling, ten nanosecond glitch capture, waveform cursors, a 4K record length and 30K of battery-backed memory, it makes routine work of problems other scopes can't even see.

For the best performance value in digital storage, try the Tek 2211.

It offers a standard hardcopy interface, measurement cursors, 20 MS/s sampling and a 4K record length per channel, plus digital/analog operation — all for only \$2695.

And for the ultimate in low-cost troubleshooting: the \$1995 2245A. It's a 100 MHz real-time scope with auto setup, cursors, four independent channels, dual time bases and more.

So if you want the best low-cost solution on the line, on the bench, or on the road with you, just get on the phone.

And call your local Tek representative today.

## It's on us.

Purchase a 2232, 2211, or 2245A by October 15, 1990 and you can receive a **\$345 digital multimeter free!**\*



The CDM250 measures current, voltage and resistance, has overload protection and is UL certified. To get yours, contact your local representative or distributor and place your order with **Option 4X**. Or call Tek direct at:

## 1-800-426-2200 Ext. 225



**Tektronix**  
COMMITTED TO EXCELLENCE

### CIRCLE 92 ON FREE INFORMATION CARD

\*Offer valid in U.S. only. You must ask for Option 4X and date purchase order between July 15 and October 15, 1990 to qualify.

© 1990 Tektronix Inc. BOB-101