

PRACTICAL WIRELESS

NOVEMBER
1967

216

FREE inside
P.W. DATA-RULE

- * INSTANT CONVERSION FACTORS
- * COMPONENT TOLERANCES at a glance
- * COLOUR CODES * 17 SCALES
- * PARALLEL/SERIES RESISTOR CHART
- * MATHEMATICAL SLIDE RULE




Build your own
**TRANSISTORISED
CAR RADIO**



SOLDERING EQUIPMENT

FOR
THE
RADIO
CONSTRUCTOR

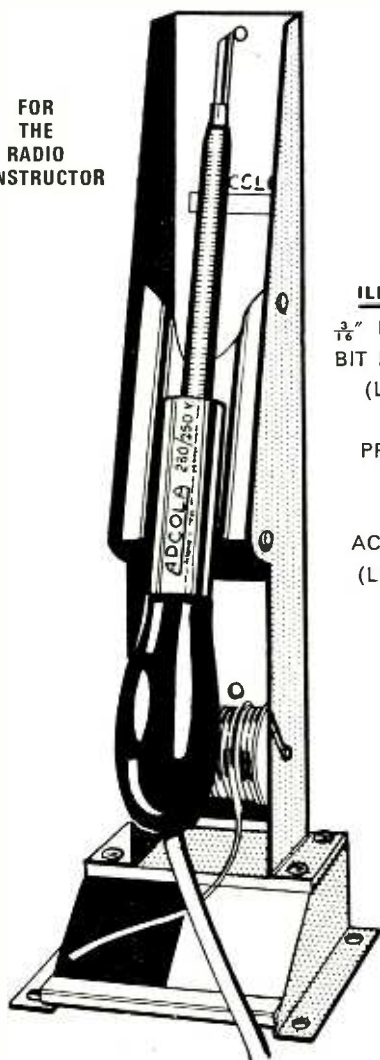

ILLUSTRATED
3/16" DETACHABLE
BIT INSTRUMENT
(List No. 64)
IN
PROTECTIVE
SHIELD
WITH
ACCESSORIES
(List No. 700)

FOR CATALOGUES APPLY DIRECT

ADCOLA PRODUCTS LTD.
ADCOLA HOUSE
GAUDEN ROAD
LONDON, S.W.4

Telephones:
01 622 0291

Telegrams: "SOLJOINT" LONDON SW4


EXPERIMENTER'S PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS
with **PARTS** and **TRANSISTORS** from your **SPARES BOX**

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for building.

40 TRANSISTORISED PROJECTS

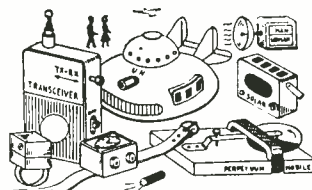A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time including 10 new circuits.



EXPERIMENTER'S PRINTED CIRCUIT KIT 8/6


Postage & Pack. 1/6 (UK)
Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand,
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Seismic Car Alarm. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone - "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

PHOTOELECTRIC KIT

BUILD 12 EXCITING PHOTOELECTRIC DEVICES

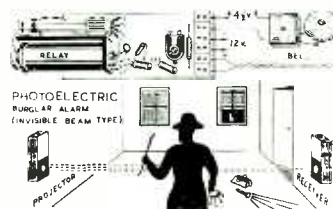CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Cadmium Sulphide Photocell, Latching Relay, 2 Transistors, Condenser, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT 39/6

Postage & Pack. 2/6 (UK)

Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0

Australia, New Zealand,
S. Africa, Canada & U.S.A.
Also Essential Data Circuits
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-light Alarm. (4) Relay-Less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1, Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE OPTICAL KIT 29/6 p.p. 1/6


Obtainable from larger electronic components distributors or direct from

EXPERIMENTAL ELECTRONIC ENG. KITS
YORK ELECTRICS, 333 York Rd., London S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects assembled.

Transistorised FM Tuner

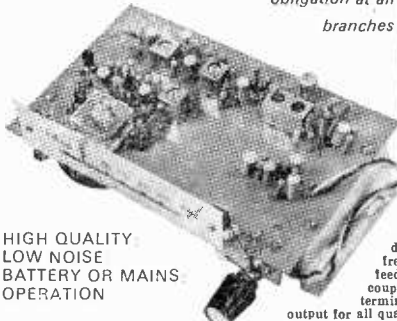CALLERS WELCOME Demonstration without
obligation at all
branches



HIGH QUALITY
LOW NOISE
BATTERY OR MAINS
OPERATION

REDUCED PRICE DUE
TO HUGE SALES

HITACHI DE LUXE TAPE RECORDERS

Limited UNREPEATABLE offer of these superb
reproducers just in. All A.C. mains. Hi Fi heads. Hi
flux speakers, dynamic mikes, sound level meters,
tapes, spare spools, super single hand controls, in-
structions fabulous finish and performance.

TRA500 2 track 2 speed 5 spool
compact. Normally £30.00
now only **18 Gns.**
TRA505 4 track 1" and 3 1/2" 5" spools, 3 heads
Plays stereo records overrecords and
plays back 2 tracks simultaneously. Foot-
ate indicator. 11" x 11" x 5 1/2". normally £50
8s. Large semi-professional 50-13,500
TR722 CPS on 7" spools large **24 Gns.**
splicer. Wt. 20 lbs. (lists £47.70).

BARGAIN PARCELS

Including variable condensers, i.f. coils, loudspeaker
plus/speakers, knobs, pots, condensers, resistors, nuts,
bolts, cabinet fittings, switches, transformer choke,
rectifier, transistors at a small fraction of list value.
Due to heavy demand we now pack them in several
sizes—be amazed—try one now.

3 lbs. (most 3/-) 9/-
7 lbs. (pct 4 1/2-) 17/6
14 lbs. (pct 6/-) 29/-

JASON
KITS

FANTASTICALLY POPULAR

★ TAPE ★

We offer you fully tensilized polyester/mylar
and P.V.C. tapes of identical quality hi-fi. wide
range recording characteristics as top grade
tapes. Quality control manufacture. They
are truly worth a few more coppers than
acetate, sub-standard, jointed or cheap imports.
TRY ONE AND PROVE IT YOURSELF.

Standard Play		Long Play	
3in. 1500ft.	2/3	3in. 2250ft.	2/9
4in. 3000ft.	4/6	4in. 4500ft.	5/6
5in. 6000ft.	7/6	5in. 9000ft.	10/6
5in. 9000ft.	10/6	5in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6

Double Play		Triple Play	
3in. 3000ft.	4/-	4in. 9000ft.	13/-
4in. 6000ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5in. 2,400ft.	34/-
5in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	Quadruple Play	
		3in. 600ft.	8/6

Postage 1/- incl.
Post Free less 5% on three reels.
Quantity and Trade enquiries invited.
NOTE. Large tape stocks at all branches.

LATEST (Post 5/-) GARRARD

SRP12	£4.7.6
SP25 (de-luxe die cast)	£9.19.0
ATS	£5.10.0
Model 1,000	£6.5.0
Model 2,000	£6.10.0
Model 3,000	£8.10.0
AT80 Mk. II	£10.19.0
AT70	£8.10.0
LAB80 Mk. II	£24.19.0
401	£27.10.0
Mono dual cartridges	12/6
Stereo ceramic cartridges	19/6

PLINTHS

Universal fitting de luxe Teak
for SP25, 1000, 2,000, 3,000, AT80
Ditto Perseus Clear
View Cover Complete **£5.15.0**
LAB80, 401, Superb Teak/Perseus
top finish plinth **£9.19.0**
Normally £12.10.

This beautifully compact 6
transistor machine (size 6 x 4 x
2 1/2 in.) will give quieter, more
interference free reception. Months
of use from a standard 9 volt battery
or its small power requirements can be
drawn from any amplifier. Low noise
freq. changer. Smooth 2 rank tuning
feeding no less than three I.F. stages
coupled to a double-tuned discriminator
terminating in an L.F. stage giving ample
output for all quality amplifiers.

£6.10.0
(3 FOR £18)

STEREO PORTABLE CABINETS

Latest black and silver metal finish. Con-
sisting of centre cabinet size 16 1/2 in. x 13 in. x
8 in. deep with lift up lid together with two
10 x 6 speaker cabinets which clip on ends
of main cabinet size 4 1/2 in. x 13 in. x 8 in.
making overall size of 25 1/2 in. x 13 in. x 8 in.
High quality chrome fittings. Will take almost
any autochanger or tape deck.

Approx. half price at
Ditto, but less chrome, takes
7 x 4 speaker. **£2.19.9**
MONO PORTABLE CABINETS. B.S.R.
tape deck or single record player. **19/6**
new, attractive finish, half price
AUTOCHANGE PORTABLE CABINETS.
As used on 18 gns. record player. Due to
fortunate purchase we offer complete
with motor board and all fittings **49/-**
at only
PLEASE NOTE. A wide range of cabinets
to callers at all branches.

100 HI-STABS 9/-
1% to 5%, 100Ω to 5 mΩ.
CO-AX, low loss, 6d. yd. 25 yds. 11/6;
50 yds. 22/-; 100 yds. 42/6. Plus 1/3

100 RESISTORS 6/6
SIZES—1-3 watt.
MICROPHONE CABLE. Highest quality,
black, grey, white, 8d. per yard.

100 CONDENSERS 9/6
Miniature Ceramic, Silver, Mica etc., 3pF
to 5μF. LIST VALUE OVER £4.

25 ELECTROLYTICS
Assorted 2 to 500 mfd 6 to 400
volt. LIST VALUE OVER £5. **9/6**

50 TAG STRIPS 7/6
Mixed sizes 2 to 15 way.

25 POTENTIOMETERS
Including with switch, long and
short spindle, pre-sets, log and lin.
unused, 1k-2mΩ. **9/6**
LIST
VALUE APPROX. £4.

CONNECTING WIRE
P.V.C. Bright Colours. Five 25ft.
coils only. **4/-**

Storkists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear Rogers, Truport, Ferrograph, Wharfedale, etc.
Post: 1 lb. 1/5, 1 1/2 lb. 2/6, 2 lb. 2/9, 4 lb. 3/3, 6 lb. 4/-, 14 lb. 5/6.

A very wide range of electronic components await
you at all branches. Your enquiries welcomed.

**TECHNICAL
TRADING**

LONDON 10 Tottenham Court Road. W.1.
Tel. MU5eum 2639

BRIGHTON Park Crescent Place
Tel. 690722

PORTSMOUTH 350-352 Fratton Road.
Tel. 22034

SOUTHAMPTON 72 East Street
Tel. 25551

WORTHING 182 Montague Street
Tel. 2555

All Mail Orders to Brighton Please

★ GUARANTEED VALVES ★

BY RETURN OF POST—GUARANTEED 3 MONTHS

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days
ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE
TRANSIT INSURANCE. POSTAGE 1 valve 8d. 2-11 6d. per valve. Free over 12

1L4	2/3	6Q7G	7/-	30C15	11/6	ECC81	4/9	EZ81	6/-	PY88	8/8
184	4/9	6Q7GT	8/9	30C17	10/6	ECC82	5/6	FC4	8/-	PY800	7/-
2D21	5/8	6S1T	6/9	30F1	9/-	ECC83	6/-	GZ32	9/6	PY801	7/8
304	5/8	6S1TGT	6/9	30F1L	9/6	ECC84	6/9	GZ34	10/6	PZ30	9/6
5U4G	6/-	6SN7GT	6/9	30L15	11/6	ECC85	5/9	KT51	12/-	SP61	2/9
5Y3GT	6/6	6U4GT	9/6	30L17	11/6	ECC88	9/6	KT63	5/9	TDD4	7/-
5Z4G	6/9	6V8G	4/9	30P4	11/6	ECC89	7/9	KT66	19/6	U14/18	7/8
5Z4GT	9/6	6V8GT	4/9	30P12	9/-	ECC82	7/8	KTW61	5/9	U25	9/8
9/30L2	9/6	6X4	4/8	30P1L	11/-	ECH42	10/6	KTW63	5/-	U26	9/6
6ASG	7/6	6X5G	5/-	35A5	9/6	ECH51	6/9	KTZ63	7/-	U35	12/6
6AK5	4/9	6X5GT	6/9	35L8GT	8/6	ECL80	5/9	NU14	7/-	U191	12/6
6AQ5	5/-	7B6	11/6	35W4	6/6	ECL82	7/6	N37	9/6	U281	9/6
6AT6	5/-	7B7	7/6	35Z4GT	5/9	ECL83	10/8	N78	13/-	U282	15/-
6AU6	7/-	7C5	9/6	35L8GT	8/6	ECL86	9/6	N108	13/-	U801	19/-
6BA6	5/6	7C6	7/6	42	6/6	EP38	4/9	PC36	9/6	UABC80	8/6
6BE6	5/6	7H7	7/6	80	7/6	EP39	7/-	PC37	7/6	UAF42	9/9
6BH6	6/6	7S7	14/6	185BTA	19/6	EP40	10/-	PC384	6/5	UB41	6/6
6BJ6	7/-	7Y4	7/-	807	9/6	EP41	9/6	PC385	7/6	UBC41	8/9
6BR7	9/6	10C1	11/-	955	3/6	EP42	6/9	PC388	11/9	UBC41	8/9
6BW6	7/6	10C2	12/6	956	3/6	EP50	3/3	PC389	11/-	UBF90	7/8
6BW7	5/-	10F1	7/6	AZ31	8/6	EP80	4/9	PCF89	8/9	UBF89	7/9
6C4	3/-	10L1D11	14/6	DAF91	3/9	EP85	6/3	PCF80	6/9	UBL21	10/3
6C6	4/-	10P13	9/6	DAF96	7/3	EP86	7/6	PCF82	6/9	UCC35	7/6
6C9	11/-	10P14	9/6	DF91	3/-	EP89	6/6	PCF86	8/3	UCF90	8/9
80D6G	17/-	12A76	6/6	DF96	7/3	EP91	3/6	PCF82	7/9	UCH21	10/8
6D6	4/-	12A77	4/9	DK91	5/8	EP183	8/-	PCL83	9/6	UCH42	8/6
6F1	6/6	12A76	5/-	DL92	8/6	EP184	8/6	PCL84	9/6	UCH31	7/-
6F6G	5/-	12A77	5/6	DK96	7/3	EL32	5/-	PCL82	9/6	UCL82	8/6
6F13	4/6	12A77	6/-	DL92	6/-	EL33	12/-	PCL86	9/6	UCL83	10/6
6F14	7/6	12B8A	7/-	DL94	6/6	EL34	11/6	PCL83	8/6	UF41	9/-
6F15	9/6	12B8E	6/6	DL96	7/3	EL41	9/9	PL36	11/-	UF42	6/6
6F23	8/-	12T7GT	9/-	DT86	6/-	EL42	8/9	PL81	7/9	UF85	7/6
6J5G	4/-	12T7GT	6/-	DT87	6/-	EL84	6/6	PL82	5/9	UF89	6/9
6J5GT	6/6	12K8GT	9/6	EAB30	6/9	EM50	7/-	PL83	8/-	UL41	10/-
6J6	3/3	12Q7GT	6/6	EAF42	8/-	EM81	7/6	PL84	7/-	UL44	14/-
6J7G	5/6	12S17	5/6	EB41	4/6	EM84	7/9	PY31	7/6	UL46	10/6
6J7GT	9/6	14S7	14/6	EB49	2/9	EY51	7/6	PY32	9/6	UL84	6/8
6K7G	2/8	19A45	5/6	EB33	7/6	EY98	7/6	PY83	7/6	UM80	9/6
6K7GT	5/6	20D1	8/6	EB34	9/6	EY98	8/6	PY80	5/9	UY21	8/9
6K8GS	9/6	20F2	9/6	EB39	6/9	EY40	7/6	PY81	5/9	UY41	7/-
6L1	9/6	29L1	16/-	EBF80	7/8	EZ41	8/6	PY82	5/6	UY85	5/6
6L6G	8/6	20P1	9/6	EBF89	7/-	EZ80	5/6	PY83	5/9	VR105	5/-
6L18	7/8	20P3	9/6	6P25	12/-	25L6GT	7/-	EBL21	11/-	VR150	5/-
6LD20	8/6	20P4	17/9	6P28	9/6	25Z4G	7/-	ECC40	9/6	X86	7/8

TRANSISTORS

GUARANTEED TOP QUALITY

Mullard Matched Output
Kits OC18D and 2-OC81 **12/6**
R.F. Kits OC44, OC45 (2) **11/-**
3 transistors.

AP114	6/6	OC44	5/-
AP115	6/-	OC45	4/6
AP116	6/-	OC72	5/-
AP117	5/6	OC81	5/-
AP127	5/6	OC81D	4/6
OC28	7/6	OC170	6/-
OC35	9/-	OC171	6/-

GERMANIUM DIODES

General Purpose miniature 8d.
detector or 6/8 doz.
Gold Bonded Top Grade 1/-
(9/6 doz.).

SILICON RECTIFIERS

Guaranteed performance. Top
Makes. Tested 250v. working.
100mA **2/9** 500mA **5/-**
(3 for 6/6) (3 for 12/6)

FREE FLOG LIST NO 2 Scores Special Bargains

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

NAME

ADDRESS

Block Capitals Please..... PW 11

10 Tottenham Court Road. W.1. Tel. MU5eum 2639

Park Crescent Place Tel. 690722

350-352 Fratton Road. Tel. 22034

72 East Street Tel. 25551

182 Montague Street Tel. 2555


All Mail Orders to Brighton Please

LINEAR

LT55 6 WATT AMPLIFIER

A High Fidelity unit providing excellent results at modest output levels.

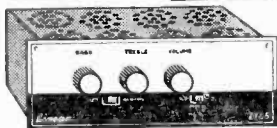Frequency Response
30-20,000 cps—2dB
Sensitivity 5 mv (max)
Harmonic Distortion
0.5% at 1,000 cps.
Output for 3-8-15 ohm Loudspeakers.
Input Sockets for "Mike," Gram and Radio
Tuner/Tape Recorder.




Recommended 8 gns
Retail price
Size 9½ × 2½ × 5½ in.
Controls (5) Volume, Bass,
Treble, Mains Switch, Input
Selector Switch.

LTA15 15 WATT AMPLIFIER

High Fidelity Output
switched inputs for
Gram, "Mike," Tape,
and Radio.

Frequency Response
10-40,000 cps—3dB

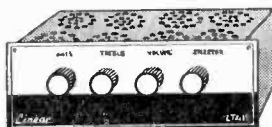Bass Control
+18dB to -16dB at 40 cps
Treble Control
+17dB to -14dB at 14 Kc/s
Hum and Noise -80dB
Harmonic Distortion 0.2% at rated output.



Recommended 16 gns
Retail price
Size 9½ × 3½ × 5½ in.
Output for 3-8-15 ohm Loud-
speakers.

Please send a stamped addressed envelope for full descriptive details of above units,
also TUNER/AMPLIFIERS STEREO and MONO

Wholesale and Retail
enquiries to:

AVAILABLE FROM YOUR LOCAL HI-FI DEALER

NEW RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors

If required an attractive wood cabinet with Satin Teak veneer finish can be supplied for any model.
Price from 70s.

LT66 12 WATT STEREO AMPLIFIER

A twin channel version of the LT55 providing up to 6 watts High Fidelity output on each channel.

Switched Input Facilities
Socket (1) Tape or crystal PU
(2) Radio Tuner (3) Ceramic PU
Microphone

Controls (6) Volume, Bass, Treble,
Balance, Mains Switch, Input
Selector Switch. Stereo/Mono Switch.

Facia Plate Rigid Perspex with black/silver background and matching black edged knobs with spun silver centres.




Recommended 15 gns
Retail price
Size 12 × 3½ × 6 in.

PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER

A successor to our popular
Concord 30 watt unit.

Input Sensitivity 2 mv (max)

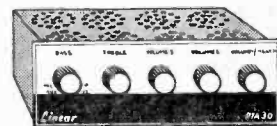- ★ Output 30 watts.
- ★ Output Terminals or Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms.
- ★ Three individually controlled Jack Inputs for mixing purposes.



Recommended 20 gns
Retail price
Size 12 × 3½ × 6 in.

Housed in fully enclosed stove
enamelled steel case.

Controls Vol (1) Vol (2) Vol (3)
with mains switch, Treble "lift"
and "cut", Bass "lift" and "cut"

AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS
SUITABLE FOR ANY KIND OF "MIKE" AND INSTRUMENT
PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.

LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS

HOME RADIO (Mitcham) LTD. 187 LONDON RD., MITCHAM, CR4 2YQ, SURREY (MIT 3282)

STRIKE

while the
iron's HOT!



A wonderful offer by HOME RADIO LTD. and WELLER ELECTRIC LTD!

Here's good news! In co-operation with Weller Electric Ltd., the world's largest manufacturers of soldering irons, we are now including in our components catalogue a special Voucher worth 5/- if used to purchase a Weller Soldering Iron. This is in addition to five other Vouchers in the Catalogue, each worth a shilling when used as directed. At the modest price of 7/6 plus 2/- p. & p. our catalogue would be a wonderful buy even if it contained no vouchers! It has over 250 pages, detailing more than 6,000 items, about 1,000 of them illustrated. You have nothing to lose and everything to gain. Send the attached coupon today, with your cheque or P.O. for nine shillings and sixpence.

Please write your name and address in block capitals

NAME

ADDRESS

HOME RADIO LTD., Dept. PW, 187 LONDON ROAD, MITCHAM.
CR4 2YQ

VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

**On 'SATISFACTION or
REFUND of FEE' terms**

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

**WHICH OF THESE IS
YOUR PET SUBJECT ?**

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications — Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elec.
Electrical Science — Electri-
cal Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work — Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

**WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

Which qualification would increase your earning power?
A.M.I.Mech.E., A.M.S.E. A.M.I.C.E., A.M.I.E.R.E. B.Sc.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Chem.E., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF
EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depis.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

**132 PAGES OF EXPERT
CAREER - GUIDANCE**

**PRACTICAL
EQUIPMENT**

**INCLUDING
TOOLS**

Basic Practical and Theore-
tic Courses for beginners in
Radio, T.V., Electronics, Etc.
A.M.I.E.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
F.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

The specialist Elec-
tronics Division of
B.I.E.T.
NOW offers you a
real laboratory train-
ing at home with
practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading
"ENGINEERING OPPORTUNI-
TIES", and if you are earning less than
£30 a week you should send for your
copy now—FREE and without
obligation.

POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

3d. stamp if posted in
an unsealed envelope.

Please send me a FREE copy of "ENGINEERING
OPPORTUNITIES." I am interested in (state subject,
exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE



THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

NEW MART

Dept PW9

30/32, SHUDEHILL MANCHESTER 4.

Telephone (061) 832 7710

FREE GIFT OFFER

OF A BRAND NEW WORLD FAMOUS E.M.I. FISK SOLARSCOPE VALUE £2 20 WITH EVERY ORDER VALUE £5 AND OVER. THIS UNIQUE INSTRUMENT WHICH IS A BOON TO SHORT WAVE LISTENERS CLEARLY SHOWS THE AREAS OF DAYLIGHT AND DARKNESS ALL OVER THE EARTH AT ANY GIVEN HOUR.

MINI-MOTORS 3V to 4.5V operation. Ideal for mini-racing cars, toys "Large" (1 1/8" x 7/16" x 1 1/2 in.) 3/11, Medium (1 x 3/8" x 1 1/4 in.) 3/9, Small (9/16" x 1/2 x 1 in.) 3/8. P. & P. 9d. each.

BRAND NEW! Why use Sapphire Stylus in your record-player when at very little extra cost you can have a first-grade GENUINE DIAMOND STYLUS at 7/11 plus 6d. P.P. Available as replacements for the following popular types only at present: BSR TC8LP — BSR TC8 STEREO — BSR TC8 LP/STEREO — COLLARO STUDIO "O" LP/ROSETTE — GARRARD GCS LP-ACOS GP 65/67LP-ROSETTE BF40/LP-GARRARD GCS LP.

SPEAKERS. 12in. round high quality British fitted tweeter cone, 6 watts, in 3Ω or 15Ω. 29/6 P.P. 3/6. ROUND 12in. R. & A. 3Ω 25/6, P.P. 3/6. 2 1/2" round speaker 80Ω for your miniature equipment—4/- each, P. & P. 1/- Many other speakers from 2in. to 13in. available. Extension type, with vol. control, attractive finish: includes 7 x 4in. speaker. 32/6, P. & P. 4/6. Attractive extension speaker with two Jacks to suit all transistor sets for home or car. 17/6, P. & P. 2/6.

TWEETER. 2 1/2in. Black plastic cone, round on Square Frame. E.M.I. 3Ω—12/6, plus 1/6 P. & P.

MICROPHONES. LAPEL/HAND MIKE—14in. dia. Lapel Clip, ideal for tape recording. With lead. Very sensitive 7/6. P. & P. 1/-.

CRYSTAL HAND MIKE. Robust and sensitive. Cream plastic case. Just the thing for tape recorders 5/6. P. & P. 1/6.

ACOS MIC 40—World famous Desk Mike, 18/6 plus P. & P. 1/3.

ACOS MIC 45—Splendid Curved Hand Grip Crystal Mike, 14/6 plus P. & P. 1/6.

ACOS MIC 60—"Stick" Type Crystal Mike 18/6 plus P. & P. 1/6.

ACOS ROUND Crystal Mike Insert, 1 1/2in. dia. 7/6, P. & P. 6d.

TELESCOPICTOP STAND. HEAVY BASE. Standard thread. 49/6, Carr. & Pkg. 4/6

TELEPHONE PICK-UP COIL. For recording or amplifying both sides of telephone conversation. Suction cup fitting to telephone. with lead, 7/6. P. & P. 1/-

INTER-COMM. DE-LUXE 2-WAY. Ideal for offices, workshops, theatres, etc. Highly efficient, safe BABY ALARM. No mains—works off PP3 battery, which lasts for months, obtainable everywhere. Buzzer call system, complete with lead, plugs, battery, in handsome carton. 55/-, P. & P. 2/6.

PHOTO-ELECTRIC CELL. (APC.1) Suitable replacement for ORP 12. Max. volts 200; current 1A; Power ratio 250W. Res. range 500Ω to 2 megΩ. Price 7/6 each, P. & P. 6d.

4 TRANSISTOR 3W AMPLIFIER. Size 2 1/2 x 2 1/4 x 1 1/4. 3, 8 or 15Ω output. 9 volt battery operated. Highly sensitive. Price (less battery) 52/6. P. & P. 1/6.

RECORD PLAYER DECKS. GARRARD

SP25 DE LUXE 4-SPEED SINGLE PLAYER

59

9

6

MODEL 3000 4-SPEED AUTO-CHANGE

57

19

6

All latest models. All fitted Mono Cartridge. Stereo 10/- extra. Carr. & Pkg. all models 7/6.

B.S.R. AUTOMATIC RECORD-CHANGER DECKS. LATEST MODELS.

UA25—Very popular—4 speed. Cap. six 7in., 10in., 12in. records £5 19 6

UA1588—Slim Design—first class 4 speed. Two-tone grey £6 2 6

UA 15/883D—As above, but with low mass p.u. arm, reducing record wear and heavier 10in. turntable, finished in pearl grey and black £6 18 9

P. & P. on all above 7/6. Price includes Free Gift.

MAGNAVOX "363" TAPE DECKS. LATEST MODELS.

World-famous. Made to highest standards. Size 13 1/2 x 11 x 5 1/2 in. below board. For 200/250V 50 cycles a.c. 3 speed, digit counter, piano key controls. 7in. reels. Every modern feature. Speeds 17 3/4 and 7 1/4 i.p.s.

With 1/2 track Braintime heads £10 10 0

With 1/2 track Marriot heads £13 0 0

P. & P. 10/- Price includes Free Gift.

PICK-UP CARTRIDGE REPLACEMENTS

STANDARD FIXING FOR MOST RECORD-PLAYER ARMS. ALL TURN-OVER TYPES WITH STYLUS FOR L.P. & 78 R.P.M.

ACOS GP167-2 MONO 12/6 each. ACOS GP173-2 STEREO 25/- each. ACOS GP191-1 MONO-DE-LUXE 17/6 each. Postage and packing 9d. each.

Finest Quality British made MYLAR Recording Tape Fully Guaranteed. In Cartons.

3in. 240ft. Message 5/- 5in. 1200ft. Long Play 12/6

5in. 600 Standard Play 8/6 7in. 1800ft. Long Play 19/6

5 1/2in. 850 Standard Play 11/6 5in. 1200ft. Double Play 15/-

7in. 1200 Standard Play 12/6 5 1/2in. 1800ft. Double Play 22/6

5in. 900ft. Long Play 10/- 7in. 2400ft. Double Play 24/-

P. & P. 1/- per reel. Four reels and over post paid.

POCKET MULTI-TEST METER. 1000Ω per volt. Volts 0/10/50/250/500/1000 a.c. and d.c. Current: 0.1-100-500mA. Resistance: 0-100kΩ. Complete with test probes, instructions. 57/6. P. & P. 1/6.

MULTI-TEST METER. Pocket size: 4 1/2 x 3 1/2 x 1 1/2 in. 20,000Ω per volt D.C. Volts (20,000Ω P.V.) 0/5/25/250/500/2500 D.C. Current 0-50 micro amp/2-5mA/250mA A.C. volts (10,000Ω P.V.) 0/10/50/100/500/1000 Resistance: 0/6kΩ—0/6 megΩ. Capacity: 10μF to 200μF. 0.01μF to 1μF. Decibels: -20 to +22dB. COMPLETE WITH battery, instructions, leads, 72/6. P. & P. 1/6.

TRANSISTORS: Some popular types from our range:

OC44 and OC45 3/6 each. OC71 2/9. OC72 2/6. OC81 and OC81D 3/- each. OC169 3/9. OC170 3/8. AF117 4/-. OC26 7/6. GETS 5/9. General purpose (Approx. OC71) 1/- each.

NEW HIGH FREQUENCY TRANSISTORS. Sinclair ST140—4/-, ST141—6/- both capable of operating up to 700 Mc/s. ALSO MAT 100—7/9, MAT 101—8/6, MAT 120—7/9, MAT 121—8/6, AIT 140—15/-, High speed switching transistors—BSY 26 BSY 28. BSY 65—5/- each.


THYRISTORS. 100 PIV 5A: 12/6; 200 PIV 5A: 15/-, All Transistors. Postage 6d. up to 3. Over 12 sent P. & P. paid.

R.F. FIELD INDICATOR. Ideal for use with radio controlled models. Checks radiation from existing antenna. Tunes 1 to 250Mc in 5 bands. Sensitive 200mA meter movement. 5 section plug-in aerial. Phone jack and crystal earpiece for monitoring. No battery required. Powerful magnet for attaching to metal surfaces. Complete with instructions. 47/6. P. & P. 2/6.

TERMS. Cash with order. No C.O.D. Orders total £5 and over sent carriage paid (excepting Record player decks where carriage is shown). Guaranteed money refunded if goods returned perfect within 7 days of despatch.

REMEMBER THE NOVEL FREE GIFT EXCLUSIVE TO US!

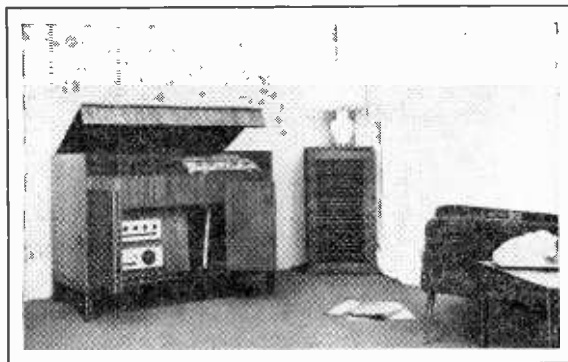Callers welcome—Very many more lines to choose from. Open 9.30 a.m.—6 p.m. Mon. Sat. STOCKISTS OF ALL SINCLAIR, CIR-KIT MARTIN KITS—DETAILS WITH PLEASURE.



HOUSING HI-FI?

Whatever your set-up there's a Record Housing Cabinet to meet your needs. Amplifiers, tuners,

turntables, loudspeakers, records, tapes, tape decks and even a complete tape recorder—you name it we'll house it! The room setting above features our Schubert Equipment Cabinet 42 gns., and Hi-Flex Speaker Enclosure £12.19.0. These are examples of the Record Housing range of equipment cabinets. speaker cabinets and record cabinets—over 20 different models priced from 7 gns. Send for free catalogue and list of over 600 stockists (U.K. only)

FREE HI-FI HOUSING ADVISORY SERVICE

Simply tell us the equipment you propose to house and we will be pleased to recommend the most suitable cabinet. Remember—housing HI-FI is our business.

RECORD HOUSING

(Dept. P.W.11), Brook Road, London, N.22. Tel: 01-888 7487



This gun for SALE!

FOR 'INSTANT HEAT'...SAFE...EFFICIENT SOLDERING

With a Weller 'Expert' Dual Heat Gun in hand you can successfully tackle any soldering job—from a small printed circuit up to sheet metal work! You get INSTANT HEAT at the press of a trigger—and tip is cool within 10 seconds of releasing trigger. Completely safe for operator . . .

and components. Simple to use . . . speedy and accurate. Dual Heat 120-140 watts.

Expert Dual Heat Gun 66/- (Kit 89/6). Also available: Marksman Soldering Iron 29/- (Kit 38/-).



Manufactured by the world's largest makers of quality soldering tools.

Write for literature on Weller Soldering Equipment. To: WELLER ELECTRIC LIMITED Horsham, Sussex. Telephone: Horsham 61747



Lasky's Radio

SPECIAL INTEREST ITEMS!

SOLID STATE MULTIPLEX STEREO AM/FM TUNER/AMPLIFIER CHASSIS

Model T10E—made for U.K. use by famous North American manufacturer and originally installed in De Luxe Hi-Fi consoles costing several hundred pounds. The chassis of outstanding appearance and quality and offers many unique features plus an extremely comprehensive specification.

Features • Separate transistorised AM and FM tuners • 3 AM wavebands—L.W., MW and Continental T.R. band • full FM cover with 5 push button preselected stations (sep. tuning controls for AM and FM ranges) • built in multiplex decoder with unique FMX feature which provides automatic switching from mono to stereo when stereo signal is received and vice versa • unique split amplifier facility for simultaneous play of radio plus any other source • channel reverse • switched inputs for tape and auxiliaries (sep. sockets for tape in and out) • switched extension speaker outlet • thermal safety trip • socket for stereo headphones.

Tech. spec.: Output 10 watts RMS per channel; output imp. 8 Ω p.c.; sensitivity 50mV for 8W output at 1 Kc.; input imp. 100 K Ω p.c.; 12 unique turner type function controls, 8 push button wavechange and station selection controls, vol., bass, treble and balance controls, push button (loudness) control; illuminated tuning scale; AM ranges: MW 520-1640 Kc/s, LW 140-290 Kc/s, Continental TR 170-345 Kc/s, FM range 88-108 Mc/s with switched AFT. Operates on 200/250V A.C., 50 or 60 c/s. Size 17½ x 8 x 12in.

LASKY'S PRICE 59 Gns Post & Packing 20/-

A range of Hi-Fi Console Cabinets by the same famous manufacturer are available at almost 1/2 price and may be seen at our Hi-Fi Audio Centre.

TWO BAND TRANSISTOR CAR RADIO BARGAIN! MODEL CR-62

A new high quality imported all transistor superhet car radio that really breaks the quality/price barrier. A unique feature of this set is the four M/W band station preselection buttons which you yourself set to your own four favourite stations—this is in addition to full M/W band cover over 535-1605 Kc/s and full L/W band cover over 150-300 Kc/s (IF frequency 455 Kc/s). Externally adjustable aerial trimmers ensure maximum output. Six transistor (including one drift type) and one diode circuit provides powerful 2W output. The set is adjustable for use on either positive or negative ground 12V systems (external line fuse fitted). Standard mounting size 6½ x 5½ x 2in.—front panel 1½in. larger all round—finished in anodised aluminium with black push buttons. Complete with mounting brackets, full installation instructions and 2 baffle boards (for round or elliptical speaker). Fully guaranteed.

LASKY'S PRICE £9.19.6 Post 5/-

6 x 4in. elliptical 8 Ω dynamic speaker 17/6 extra—Post FREE.

SPECIAL OFFER—LOCKING CAR AERIAL Model 83003 five section 402 extension heavy chrome telescopic wing mounting type with unique locking device to protect the antenna when closed. Complete with mounting bracket, lead and plug and two "keys". **LASKY'S SPECIAL PRICE 39/8** Post Free with the Model CR-62. Sep. Post 2/6.

MICROPHONE BARGAIN

STC MODEL 414

A high quality omni directional moving coil microphone—suitable for use with sound reinforcement and P.A. systems, tape recorders, transistor amplifiers etc. Attractive grey moulded case for free standing or hand held use—size 2½ x 2½ x 2½in. Complete with 6ft. of screened cable. New and unused in makers cartons—fully guaranteed.

Type A low imp. 200 Ω **Lasky's Price £1.19.6** Post 2/-
Type B high imp. 50K Ω **Lasky's Price £2. 5.0**



NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE AT RECORD LOW PRICES


3in. Message tape, 150ft.	2 6	5½in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	3 9	5½in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5½in. Long play, 1200ft. Mylar	15 0
3½in. Triple play, 600ft. Mylar	10 0	5½in. Triple play, 2400ft. Mylar	45 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet.	12 6
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 600ft. PVC	8 6	7in. Double play, 2400ft. Mylar	26 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5½in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free

Musicaettes—over 200 titles in stock Philips, Mercury, Fontana, C.R.S., Pye, Reprise, W.B. Send S.A.E. for full list.

CONSTRUCTORS BARGAINS

THE SKYROVER De Luxe

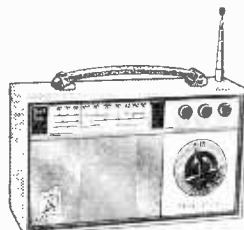

LONG WAVEBAND COVER FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free.

This conversion is suitable for receivers that have already been constructed.

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched bandspread ranges, 13M., 16M., 19M. and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. Superhet, 470 Kc/s. All Mullard Transistors and Diodes. Uses 4 U2 batteries, 5in. Ceramic Magnet P.M. Speaker, 500 mW Output. Telescope and Ferrite Rod Aerial. Tone Control. Volume Control. Tuning Control and Waveband Selector. In wood cabinet, size 11½ x 6½ x 3in. covered with washable material, plastic trim and carrying handle. Car aerial socket fitted.

Can now be built for **£8.19.6** Post 5/- extra

H.P. Terms: 60/- deposit and 11 monthly payments of 12/9. Total H.P.P. £10.0.3.

Four U2 batteries 3/4 extra.

Data 2/6 extra: refunded if you purchase the parcel. All components available separately.

SPECIAL PURCHASE—VALVE UHF TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructors. Add 2/6 Post and Packing on each.

In metal case size 4 x 6 x 1½in. Fully tunable—complete with PC86 and PC88 valves.

LASKY'S PRICE 29/6 Without valves 7/6

NEW! LASKY'S CLEAR PLASTIC PANEL METERS

Precision made in Japan by HIOKI. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 Post on each.

Type KR-52 3 x 2½in. (illustrated)
1 mA DC 32/6 100 μ A 47/6
5 mA DC 32/6 500 μ A 37/6
300 V DC 32/6 1 mA A Meter 39/6

Type MK-38A 1½in. square
1 mA DC 22/6
5 mA DC 22/6
300 V DC 22/6
100 μ A 22/6
500 μ A 27/6
1 mA A Meter 29/6

Type MK-45A 2in. square
1 mA DC 25/-
5 mA DC 25/-
300 V DC 25/-
500 μ A 25/-
1 mA A Meter 35/-

Type KR-65 3½ x 3in.
1 mA DC 36/-
5 mA DC 35/-
300 V DC 35/-
100 μ A 49/6
500 μ A 42/6
1 mA A Meter 39/6


Type MK-65A 3in. square
1 mA DC 36/-
5 mA DC 35/-
300 V DC 35/-
500 μ A 39/6
1 mA A Meter 37/6



TRANSISTOR FM TUNER CHASSIS

Fully tunable—range 88 to 108 Mc/s. Completely wired on printed circuit. 10-3 Mc/s. IF. 6 transistors and 3 diodes. Slow motion tuning drive. Size 6½ x 4 x 2½in. Operates from any 9V. D.C. source. Full data and circuit supplied.

LASKY'S PRICE £7.19.6 Post 5/- extra.

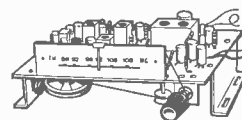

GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case size 3 x 2½ x 1½in. Circuit supplied.

LASKY'S PRICE 15/11 Post 2/-. ECC85 valve 9/- extra.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 2/6; 873A, 874P 3/6; OC45, OC46, OC47, OC81D 4/6; OC44, OC70, OC76, OC81 5/6; (match pair 10/6); AP117, OC200 6/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, PC206 19/6; OC28 24/6; OC75 8/-.

TRANSFILTERS

by BRUSH CRYSTAL CO. Available from stock.

TO—01B 465 kc/s. ± 2 kc/s. TO—02D 470 kc/s. ± 1 kc/s. **9/6 each**
TO—01D 470 kc/s. ± 2 kc/s. TF—01B 465 kc/s. ± 2 kc/s. **Post 6d.**
TO—02B 465 kc/s. ± 1 kc/s. TP—01D 470 kc/s. ± 2 kc/s.

Branches
207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271
33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605
Open all day Saturday, early closing 1 p.m. Thursday
152/3 FLEET STREET, LONDON, E.C.4 Tel.: FLEet St 2833
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

High Fidelity Audio Centres
42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573
Open all day Thursday, early closing 1 p.m. Saturday
118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789
Open all day Saturday, early closing 1 p.m. Thursday

HI-FI AMPLIFIERS — TUNERS — RECORD PLAYERS

20+20
STEREO
AMP.
AA-22U



GARRARD
PLAYER
AT-60



10W
POWER
AMP.
MA-12



9+9W
STEREO
AMP.
S-99



TRANSISTOR MIXER. Model TM-1. Four channels. Battery operated. Kit £11.16.6. Assembled £16.17.6

TRANSISTOR STEREO AMPLIFIER. Model AA-22U. 20 + 20W $\pm$ 1dB over 15 to 30,000 c/s into 8 Ω . 5 stereo inputs each channel. Versatile controls. 20 transistor, 10 diode circuit. Modern low silhouette styling... matches AFM-1, AFM-2 Tuners. Kit £39.10.0. Assembled £57.10.0 (Cabinet £25.0 extra).

GARRARD AUTO/RECORD PLAYER. Model AT-60, less cartridge £14.12.10. With Decca Deram pick-up £19.7.4 incl. P.T.

LOW-COST MONO AMPLIFIER. Model MA-5. 5W. Built in pre-amp. Inputs for Gram, Radio. Separate bass, treble, volume controls. Easy printed circuit construction. Modern functional appearance. Kit £11.9.6. Assembled £15.15.0

HI-FI MONO AMPLIFIER. Model MA-12. 10W output, wide freq. range, low distortion. Use with control units. Models UMC-1 (Mono) or USC-1 (Stereo). Kit £12.18.0 Assembled £16.18.0

CONTROL UNITS. Mono, UMC-1. Kit £9.2.6. Assembled £14.2.6. Stereo, USC-1. Kit £19.19.0. Assembled £27.5.0.

DE LUXE STEREO AMPLIFIER. Model S-33H. 3 + 3W output. Three stereo inputs... ceramic/crystal pickup, radio tuner and aux. Separate bass, treble, volume and balance controls. Easy printed circuit construction. Attractive styling. Kit £15.17.6 Assembled £21.7.6

HI-FI STEREO AMPLIFIER. Model S-99. 9 + 9W output. Ganged controls. Stereo/Mono gram, radio and tape inputs. Push-button selection. Printed circuit construction. Matches FM-4U and AFM-1 tuners in styling. Kit £28.9.6 Assembled £38.9.6



ENJOY YOURSELF & SAVE MONEY

Finished models provide years of superlative performances

HIGH PERFORMANCE CAR RADIO CR-1



Superb long and medium wave entertainment wherever you drive. Complete your motoring pleasure with this compact outstanding unit.

● 8 Latest semi-conductors (6 transistors, 2 diodes) ● For 12 volt positive or 12 volt negative earth systems ● Powerful output (4 watts) ● Pre-assembled and aligned tuning unit ● Push-button tone and wave change controls ● Positive manual tuning ● Easy circuit board assembly ● Instant operation, no warm-up time ● Tastefully styled to harmonise with any car colour scheme ● High quality output stage will operate two loudspeakers if desired. Can be built for a total price.

Kit (less spkr.) £12.17.0 incl. P.T. (6" x 4" LS £1.4.5 extra).

RADIOS



Oxford



UXR-1

"OXFORD" LUXURY PORTABLE Model UXR-2. 7 transistor, 3 diode circuit. 7" x 4" LS. Push button LW/LM and Tone. Specially designed for use as a domestic or personal portable receiver. Many features, including solid leather case.

Kit £14.18.0 incl. P.T.

TRANSISTOR PORTABLE. Model UXR-1. Pre-aligned I.F. transformers. printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case.

Kit £12.11.0 incl. P.T.

JUNIOR EXPERIMENTAL WORKSHOP Model EW-1. More than a toy! Will make over 20 exciting electronic devices, incl.: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present!

Kit £7.13.6 incl. P.T.

TRANSISTOR STEREO FM TUNER. Elegantly designed to match the Stereo Amplifier, model AA-22U seen above. Many special features include built-in power supply. Available in two units sold separately, can be built for a **TOTAL PRICE KIT (STEREO) £24.18.0** incl. P.T. Cabinet £25.0 extra. (MONO) version £20.19.0 Kit.

WHEN IN LONDON VISIT THE HEATHKIT CENTRE

233 Tottenham Court Road, W.1
We open MONDAY-FRIDAY 9 a.m.—5.30 p.m.
SATURDAY 9 a.m.—1.0 p.m.
Telephone No.: 01-636-7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

TEST INSTRUMENTS

Our wide range includes:

3" LOW-PRICED SERVICE OSCILLOSCOPE. Model OS-2. Compact size 5" x 7 $\frac{3}{4}$ " x 12" deep. Wt. only 9 $\frac{3}{4}$ lb. "Y" bandwidth 2 c/s-3 Mc/s $\pm$ 3dB Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges, fitted mu-metal CRT Shield. Modern functional styling. Kit £23.18.0 Assembled £31.18.0

5" GEN.-PURPOSE OSCILLOSCOPE. Model 10-12U. An outstanding model with professional specification and styling. "Y" bandwidth 3c/s-4.5 Mc/s $\pm$ 3dB. T/B 10 c/s-500 kc/s. Kit £35.17.6. Assembled £45.15.0

DE LUXE LARGE-SCALE VALVE VOLTMETER. Model 1M-13U. Circuit and specification based on the well-known model V-7A but with many worth-while refinements, 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling.

Kit £18.18.0 Assembled £26.18.0

VALVE VOLTMETER. Model V-7A. 7 voltage ranges d.c. volts to 1,500 A.C. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1 Ω to 1,000M Ω with internal battery. D.C. input resistance 11M Ω . dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery.

Kit £13.18.6 Assembled £19.18.6


MULTIMETER. Model MM-1U. Ranges 0-1.5V to 1,500V a.c. and d.c.; 150 μ A to 15A d.c.; 0-2 Ω to 20M Ω 4 $\frac{1}{2}$ " 50 μ A meter.

Kit £12.18.0 Assembled £18.11.6

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamentals and 200 Mc/s on harmonics. Up to 100mV output. Large accurate, calibrated dial scales. Factory wired and aligned coil and band switch assemblies. Ideal for the service shop. Kit £13.18.0. Assembled £20.8.0.

TV ALIGNMENT GENERATOR. Model HFW-1. Covers 3-6 Mc/s—220 Mc/s with 0-42 Mc/s max. sweep width. Stable all-electronic sweep circuit. Built-in marker oscillators—5 Mc/s crystal and 20 to 60 Mc/s variable. AGC circuit. Positive action return trace blanking. Kit £38.18.0. Assembled £49.15.0.

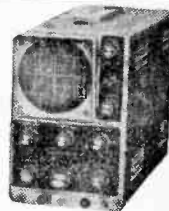TRANSISTOR POWER SUPPLY. Model IP-20U. Up to 50V, 1.5A output Ideal for Laboratory use. Compact size. Kit £35.8.0 Assembled £47.8.9



OS-2




VVM, 1M-13U



V-7A



RF-1U

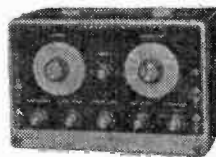

HFW-1

Prices and specifications subject to change without notice

VALVE TUNERS



TUNERS
←FM
AM/FM→



★ **HI-FI FM TUNER. Model FM-4U.** Covers 88-108 Mc/s. Fly-wheel tuning. Pre assembled and aligned. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s and I.F. amplifier unit, with power supply and valves (£13.13.0). For free standing or cabinet mounting. **Total Kit £16.8.0**

★ **HI-FI AM/FM TUNER. Model AFM-1.** Covers AM 16 to 50 200-550 and 900-2000 metres FM 88-108 Mc/s. Pre-aligned Tuning Heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£22.11.6). Printed circuit board, 8 valves. Built-in power supply. **Total Kit £27.5.0**


★ Models available in two units for your convenience.

MULTIPLEX DECODER. Model SD.1. Convert above models to stereo at low cost. Transistorised circuit. Self powered. Compact, matching unit. **Kit £8.10.0. Assembled £12.5.0.**

LATEST MODELS



STEREO AMPLIFIER, TS-23

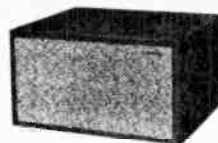

AVON SPEAKER

Low-priced 3 + 3 watt TRANSISTOR AMPLIFIER, TS-23

Breaks the price barrier in quality stereo amplifier cost. Incorporates all the essential features for good quality reproduction from gram, radio and other sources. 3W rms (15Ω) each channel. Good frequency response. Modern, compact, slim-line styling. Ganged controls. 6 position selector switch. 16 transistor, 4 diode circuit. Walnut veneered cabinet, optional extra. **Kit (Amplifier) £17.15.0 Cabinet £2.0.0 extra.**

Good performance from a Mini speaker with the 'AVON' BOOKSHELF **SPEAKER SYSTEM.** Occupies the minimum space consistent with first class reproduction. Only 7½" x 13½" x 8½" deep. Two special speakers 6½" BASS, 3½" HF unit and crossover network. **Kit £4.18.0 incl. P.T. Walnut veneered, Fully finished cabinet, kit £8.18.0. TOTAL PRICE KIT £13.16.0 incl. P.T.**

Build Britain's Best Electronic Kits



No special kit-building skills or Electronic knowledge required

SPEAKER SYSTEMS



SSU-1

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical horizontal models with legs, **Kit £12.12.0** without legs, **Kit £11.17.6 incl. P.T.**

The **BERKELEY SLIM-LINE SPEAKER SYSTEM**, fully finished walnut veneered cabinet for faster construction. Special 12" bass unit and 4" mid/high frequency unit. Range 30-17,000 c/s. Size 26" x 17" only 7½" deep. Modern attractive styling. Excellent value. **Kit £19.10.0 Assembled £24.0.0**


COTSWOLD SPEAKER SYSTEMS. Outstanding performance for price. **MFS:** Size 36" x 16½" x 14" deep. **Kit £25.12.0 Assembled £33.17.0** **STANDARD:** Size 26" x 23" x 14½" deep. **Kit £25.12.0 Assembled £33.17.0**

Berkeley

- Deferred terms available in UK over £10.
- Extended terms over £75 UK only.
- Full specification sheet of any model available upon request
- Prices quoted are Mail Order, retail prices in general slightly higher.

New! Portable Stereo Record Player, SRP-1

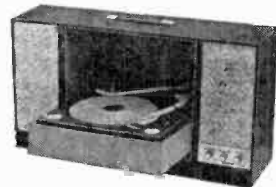Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two 8in. x 5in. special loudspeakers. For 220-250v ac mains operation. Overall cabinet size 15½" x 3½" x 10½in.




Compact, economical stereo and mono record playing for the whole Family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.

KIT £27.15.0 Assembled price on request.

"AMATEUR" EQUIPMENT

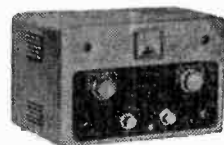80-10m TRANSMITTER, DX-40U. Power inputs 75W. C.W., 60W peak CC phone. Output 40W to aerial. Provision for VFO. **Kit £29.19.0 Assembled £41.8.0**



DX-40U

AMATEUR BANDS RECEIVER Model RA-1. To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage. **Kit £39.6.6 Assembled £52.10.0**



RA-1

160-10M TRANSMITTER. Model DX-100U. Careful design has achieved high performance and stability. Completely self-contained. **Kit £81.10.0 Assembled £106.15.0**



Send for
this
Catalogue
it's FREE

36 pages, many models in colour... Hi-Fi Audio, Radio... Amateur gear, Britain's largest selection of top quality, electronic kits.

Mail for your own copy Today! →

To DAYSTROM LTD. Gloucester. Tel. Glos. 20217.
Please send me FREE CATALOGUE YES/NO
Further details of model(s)

NAME

ADDRESS

DEPT. P.W.11

R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.—5.45 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers
Tel. 769-0199/1649

0A2 5/9	6BH6 7/1	6K6GT 5/1	787 17/9	20F2 14/1	5016GT 6/1	DH77 4/1	ECF82 7/1	EM81 7/1	PCF89 10/1	R130 25/1	UM80 6/1
0C3 5/1	6B76 7/1	6K7M 5/9	7Y4 7/6	20L1 17/1	75 7/1	DK32 7/9	ECH21 12/6	EM84 7/1	PCF189 9/8	SP4 8/1	U16 13/6
1A7 7/9	6BQ7A 7/1	6K7G 1/9	9BW6 7/1	20P4 19/1	78 7/1	DK91 5/1	ECH35 11/1	ESU150 20/1	PCF80 6/3	SP41 3/8	U17 13/6
1D5 7/1	6BR7 8/6	6K7GT 4/6	10C1 12/6	20P5 18/1	80 5/1	DK92 8/1	ECH42 9/1	EY51 7/1	PCF82 6/1	SP41 3/8	U19 8/1
1H5 7/1	6BR8 5/1	6K8M 8/6	10C2 12/6	25A6 5/9	85A2 7/8	DK96 7/1	ECH81 5/3	EY86 6/6	PCF84 8/1	SU28 19/6	U21 9/8
1L15 5/1	6BS7 16/9	6K8G 3/1	10F1 9/1	3516GT 5/6	150B2 9/6	DL66 15/1	ECH83 7/1	EZ35 4/6	PCF86 8/1	SU2150 12/6	U41 6/3
1N6GT 8/1	6BW6 7/1	6K8GT 7/1	10F3 3/1	25Y5 6/1	150C4 7/6	DL92 4/9	ECL80 6/6	EZ40 7/1	PCF801 9/8	T41 15/1	U56 5/1
1R5 5/1	6BW7 9/6	6K25 20/1	10F9 9/9	25Z4 6/3	801 6/1	DL93 3/6	ECL82 6/3	EZ41 8/1	PCF802 9/8	TDD4 10/1	VMP4G 17/1
184 5/1	6C4 2/9	6L1 9/8	10F18 9/1	25Z5 7/1	807 7/1	DL94 5/9	ECL83 9/6	EZ80 5/1	PCF803 10/9	U10 7/8	VP4B 25/1
185 4/1	6C6G 4/1	6L6G 7/1	10L1 8/1	25Z6 8/6	813 7/5	DL95 6/6	ECL86 8/9	EZ81 5/1	PCF806 12/1	U14 7/8	VR105/30
1T4 3/1	6C8 3/9	6L18 5/1	10LD11 15/1	2817 5/1	866A 13/8	DL96 7/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
3A4 3/8	6C8G 6/1	6Q7G 8/1	10P13 15/6	30C1 6/3	954 4/6	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
3Q4 6/6	6CH6G 20/1	6Q7GT 8/6	11E3 4/2	30C15 13/8	1625 5/6	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
3C5 6/6	6CH6 5/6	6SA7M 7/1	11E3 4/2	30C17 14/1	4022AR 50/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
384 4/9	6CW4 12/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
3V4 5/9	6D6 2/9	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
5R4GY 8/9	6E5 7/6	6SH7 3/3	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
5U4G 4/1	6F1 9/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
5V4G 8/1	6F5G 8/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
5Y3GT 5/1	6F6G 4/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
5Z4G 6/9	6F8G 4/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6/30L2 13/1	6F11 7/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6A7 15/1	6F13 5/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6A8G 12/6	6F14 12/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AC7 3/1	6F23 13/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AK5 4/1	6F24 12/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AL5 3/1	6F25 12/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AM6 2/6	6F28 11/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AM6 2/6	6F28 11/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AQ5 5/6	6H6 2/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AS7G 15/1	6J5M 6/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AT6 4/1	6J5G 2/6	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6AU6 5/6	6J5GT 4/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6B8G 2/1	6J6 3/1	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6B4G 15/1	6J7M 7/8	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6BA6 4/6	6J7G 4/9	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30
6BE6 4/6	6J7GT 6/8	6S7 7/1	12A7 7/1	30C18 13/6	5763 10/1	DM70 5/1	ECL86 8/9	EZ81 5/1	PCF808 11/8	U19 35/1	VR150/30

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Postage 6d. per valve. C.W.O. No C.O.D.

Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service


SEND S.A.E. FOR LIST OF 2,000 TYPES

SETS OF VALVES
DAF96, DF96, DK96, DL96 ... Set of 4, 25/6

BRAND NEW TRANSISTORS
AC127 7/6 OC25 11/1 OC71 4/8 OC81 4/1 OC82D 6/1
AF114 7/1 OC28 16/1 OC72 6/1 OC81mp 8/1 OC83 6/1
AF115 7/1 OC35 11/8 OC75 6/1 OC82 12/6 OC170 7/1
AF116 7/1 OC44 4/8 OC76 8/1 OC81D 4/1 OC171 8/1
AF117 5/1 OC46 4/1 OC77 8/1 OC82 8/1 OC200 7/6

SOLDERING

—you need the Antex
SOLDERING TOOL KIT

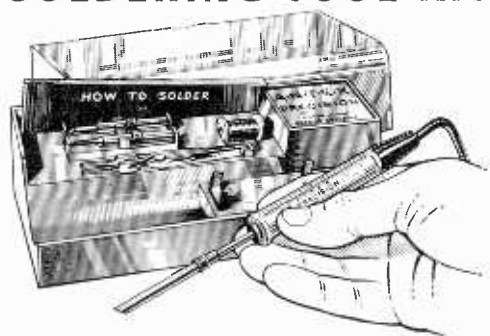

- Model CN240 15W Precision Iron with $\frac{3}{16}$ " bit.
- Two spare Interchangeable Bits ($\frac{5}{32}$ " and $\frac{3}{32}$ ")
- Reel of Solder ● Heat Sink ● Cleaning Pad
- PLUS 36-page booklet on "How-to-Solder"

49⁶/₁₀

British made. From The Army & Navy Stores, Harrods, and Radio Shops, or if unobtainable locally, direct from:

ANTEX LTD

GROSVENOR HSE · CROYDON · CR91QE

Telephone: 01-686 2774

TECHNICAL TOPICS FOR THE RADIO AMATEUR, By J. Pat Hawker. G3VA.

First Edition 10s. 8d. post paid

NEW 1968 EDITION BRITISH AMATEUR RADIO CALL BOOK

New Format 6s. 6d. post paid


We keep a good selection of log books in stock
RSGB Radio Station Log (spiral bound) 7/3
Listener's and Observer's Log (spiral bound) 7/3
V.H.F. and U.H.F. Contest Log (spiral bound) 7/3
These three log books all contain 50 pages. 11 $\frac{1}{2}$ x 8 $\frac{1}{2}$ in., but we also have:
RSGB Standard Log (10 x 8 in., 112 pages) 7/3
Mobile Mini-Log (6 $\frac{1}{2}$ x 4 $\frac{1}{2}$ in., 50 pages) 4/1

Details of other publications and information on membership of the Society, may be obtained from:

RADIO SOCIETY of GREAT BRITAIN, Dept. PW,
28 LITTLE RUSSELL STREET, London, WC1



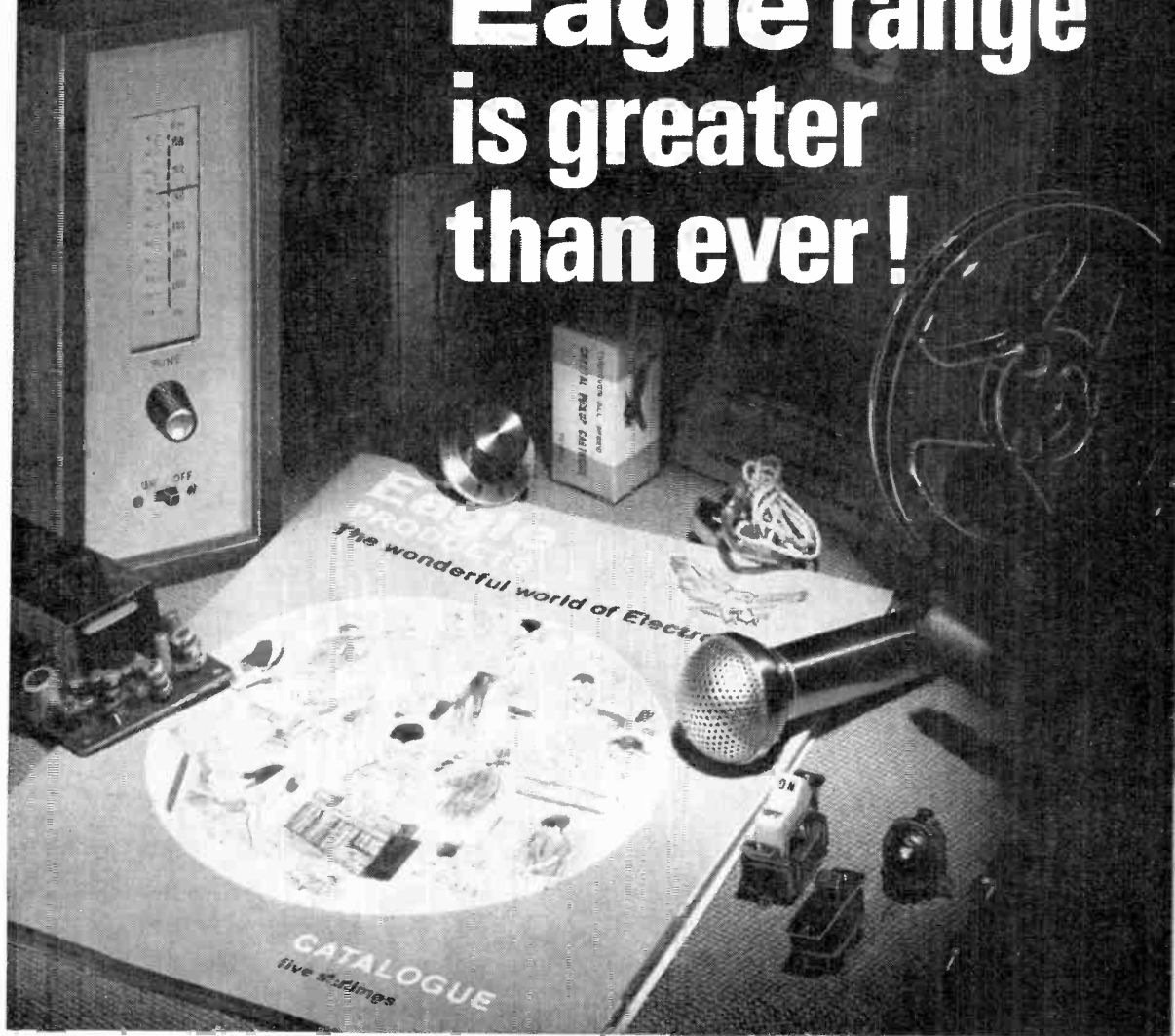The latest Eagle range is greater than ever!



It's now ready—the new Eagle Catalogue presenting “The Wonderful World of Electronics”. Hundreds of items for the Radio Hobbyist, Hi-Fi Enthusiast, Serviceman, Do-it-Yourself, etc. The widest ever choice of sensibly priced Electronic Components, Audio and Tape Accessories, Educational Projects, Home Lighting, Intercoms, Hi-Fi Amplifiers, Tuners, Tape Recorders, Loudspeakers and Speaker Systems all of which are fully illustrated together with technical specifications. There's something for everyone in Eagle's Wonderful World of Electronics so send for your copy now or call in at one of the 6000 Eagle Stockists today.

To: EAGLE PRODUCTS, Dept. P.W.11,
Coptic Street, London, W.C.1.

Please send me catalogue of the entire “Eagle”
range. I enclose 5s.


Name

Address

VIKING TRANSISTOR

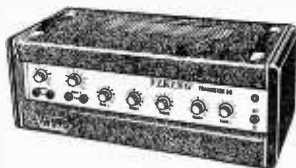40-50 WATT AMPLIFIER

OPERATING INSTRUCTIONS GENERAL. An extremely, reliable lightweight amplifier capable of giving 40-50 watts of undistorted sound, made possible by the use of the latest semi-conductors (transistors) and techniques which ensure space-age reliability under the most rugged conditions. It is designed as a general purpose amplifier particularly suitable for use with musical instruments that require exceptionally high treble response (not recommended for Bass Guitar). Tremolo facilities are available on Channel 1 only. **INPUTS—CONTROLS—CHANNEL 1** (Tremolo): this contains two high gain input jack sockets controlled by Volume Control 1 which is mounted directly above the two sockets marked tremolo. **BASS 1:** gives a controlled boost to the lower frequencies on Channel 1 only. **TREBLE 1:** gives a controlled boost to the high frequencies on Channel 1 only. **TREMOLO:** this operates on Channel 1 only and the variations of intensity and speed of the Tremolo beat is adjusted by the controls **DEPTH** and **SPEED**. A socket is provided in the rear of the amplifier so that the Tremolo may be switched on and off by the use of a footswitch plugged into the socket. If you wish the Tremolo to be used without the footswitch, this is possible as the footswitch is only used to short out the effect. **INPUTS AND CONTROLS—CHANNEL 2** (Normal): this contains two high gain input jack sockets controlled by Volume Control 2 which is mounted directly above the sockets marked Normal. **TREBLE 2:** gives a controlled boost to the treble frequencies on Channel 2 only. **MAINS VOLTAGE:** fully adjustable, 200-250 volts, A.C. 50 cycles. **POWER OUTPUT:** 40-50 watts sine wave British rating. Very little distortion. **OUTPUT IMPEDANCE:** 3 ohms. Price 21 gns. plus £1 postage and packing.



VALVE VERSION OF THE ABOVE AMPLIFIER 40-50 watt, A.C. mains 200/250 volts for 3 and 15 ohm speakers. Price 27 gns. plus £1 postage and packing (No tremolo facilities on this amplifier).



POCKET MULTI-METER

Size 3 1/4" x 2 1/4" x 1 1/4". Meter size 2 1/4" x 1 1/4". Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000. D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test leads, battery and full instructions. 49/6. P. & P. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

600 mW SOLID STATE 4-TRANSISTOR AMPLIFIER

Features NPN and PNP Complementary Symmetrical Output Stage. The elimination of transformer ensures maximum efficiency and frequency response. Automatic heat compensation. Combined AC/DC feed back. Class B output stage. i.e. output power is proportional to total current consumption, this ensures long battery life. Under no signal condition (1Q) current drain is approx. 12mA at 9 volts (4mA in the output pair). Printed circuit construction, size 2 1/4" x 1 1/4" x 1/2". Speaker output impedance 12 ohms. Output power 600mW at 5% distortion, 400mW at 2-5% distortion, 750mW at 10% distortion. Supply 9 volts. Total current consumption at a reasonable listening level approx. 35-40mA at full power (speech and music), average 65mA. Sensitivity for 50mW output is 10mV. Frequency response —3dB points 90c/s and 12Kc/s. Price 15/-, plus 1/- P. & P.

Features NPN and PNP Complementary Symmetrical Output Stage. The elimination of transformer ensures maximum efficiency and frequency response. Automatic heat compensation. Combined AC/DC feed back. Class B output stage. i.e. output power is proportional to total current consumption, this ensures long battery life. Under no signal condition (1Q) current drain is approx. 12mA at 9 volts (4mA in the output pair). Printed circuit construction, size 2 1/4" x 1 1/4" x 1/2". Speaker output impedance 12 ohms. Output power 600mW at 5% distortion, 400mW at 2-5% distortion, 750mW at 10% distortion. Supply 9 volts. Total current consumption at a reasonable listening level approx. 35-40mA at full power (speech and music), average 65mA. Sensitivity for 50mW output is 10mV. Frequency response —3dB points 90c/s and 12Kc/s. Price 15/-, plus 1/- P. & P.

8-watt 4-valve PUSH-PULL AMPLIFIER & METAL RECTIFIER

Size: 9" x 6" x 1 1/2". A.C. Mains, 200-250V, 4 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £4.4.0. P. & P. 11/-, 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.



GEC KETTLE ELEMENT

3,000W WITH AUTOMATIC EJECTION 200/240 v. Size of hole required 1 1/4". List Price 32/-. Our PRICE 15/-, P. & P. 1/6.



RADIO & TV COMPONENTS (Acton) LTD

21c High Street, Acton, London, W3

Shop Hours 9 a.m.—6 p.m. Early Closing Wednesday

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope

Also at 323 EDGWARE ROAD, LONDON, W.2. Personal shoppers only. Early Closing Thursday. All orders by post to our Acton address.


STAR SR 150 COMMUNICATION RECEIVER

Frequency range: 535 Kc/s—30Mc/s. 4 wavebands. 5 valve superhet. Incorporates BFO, bandspread tuning, "S" meter, external telescopic aerial and ferrite aerial. Built-in 4in. speaker. Easy-to-read dial. For 240V A.C. operation. Complete, brand new, with full instruction manual. 15 gns., P. & P. 10/-.



TRANSISTORISED 1 1/2 WATT AMPLIFIER

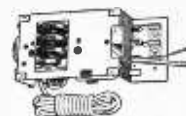Incorporating Mullard transistors type: 2, AC128's, 2, OC75's, and 2, AA129's. Separate bass and treble volume controls. Complete with Power Supply AC mains, 240V. Size 7 1/4" x 3 1/4" x 2". Price 50/- plus 2/6 P. & P.




ANTI-THIEF CAR BURGLAR ALARM

The Melguard Safermatic consists of an electrical device housed in small metal box 4" x 2" x 1 1/4", which has been designed and developed to provide protection required by the average motorist at an economic cost. Using this system, an alarm and the immobilised condition is set automatically as soon as you park the car. Should you leave the key in the ignition, no one but you can drive the car away. Upon entering the vehicle the method of starting the car is by switching on the ignition, depressing two hidden switches, and simultaneously operating the starter. Location of the switches is known only to you. Should the alarm be set off it can be stopped by following the normal starting procedure. For 12V operation. List price 79/6, our price 29/6 plus 2/6 P. & P. Full easy-to-follow instructions supplied.


3 to 4 Watt AMPLIFIER

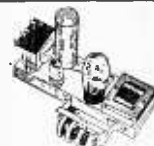3-4 watt Amplifier built and tested. Chassis size 7 x 3 1/4 x 1 1/4. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohm speaker. Valves ECC81 and 6V8. £25.0 plus 5/6 p. & p. The above in Kit Form, £11.4.6 plus 5/6 p. & p.




"MUSETTE" 6-Transistor Superhet Portable Radio

★ 2 1/2" Speaker. ★ 6 Transistor Superhet Output 200mW. ★ Plastic Cabinet in red, size 4 1/2" x 3" x 1 1/2" and gold speaker grille. ★ Horizontal Tuning Scale. ★ Ferrite Rod Internal Aerial. ★ IF 460 kc/s. ★ All components Ferrite Rod and Tuning Assembly mount on printed board. ★ Operated from PP3 Battery. ★ Fully comprehensive instructions and point-to-point wiring diagram. ★ Printed Circuit Board. ★ Tunable over medium and long waveband. ★ Car aerial and earpiece socket.

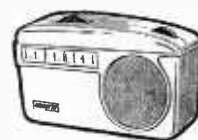

Price 39/6, inc. carrying strap. Circuit Diagram 2/6 free with parts. P. & P. 3/6.

NEW TRANSISTORISED SIGNAL GENERATOR

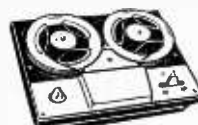

Size 5 1/2 x 3 1/2 x 1 1/4 in. For IF and RF alignment and AF output 700 c/s frequency coverage 450 kc/s to 3 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. 39/6 P. & P. 3/6.

BSR TAPE DECKS

200/250V A.C. mains

Type TD2 Tape speed 3 1/2 twin track, £519.6. Type TD10 2-track, 3 speed, plus rev. counter—£719.6. Type TD10 4-track, 3 speed, plus rev. counter—£95.0. P. & P. on each 7/6.

FIRST QUALITY P.V.C. TAPE

5 1/2" Std. 850ft. 9/-	5" L.P. 850ft. 10/6
7" Std. 1200ft. 11/6	3" T.P. 600ft. 10/6
3" L.P. 240ft. 4/-	5" T.P. 1800ft. 25/6
5 1/2" L.P. 1200ft. 11/6	5 1/2" T.P. 2400ft. 32/6
7 1/2" L.P. 1800ft. 18/6	7" T.P. 3600ft. 42/6
5 1/2" D.P. 1800ft. 18/6	4" T.P. 900ft. 15/-

P. & P. on each 1/6, 4 or more post free.

EXTRACTOR FAN



AC Mains 230/250 v. complete with pull switch. Size 6" x 6" x 4". Price 27/6 plus 5/- P. & P.

DEOR DOORBELL

Complete with mains transformer 240v. AC & bell push. Price 12/6 plus 5/6 P. & P.



Elegant Seven Mk II A. COMBINED PORTABLE and CAR RADIO


SPECIAL OFFER

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.

- ★ De luxe grey wooden cabinet size 12½" x 8½" x 3½".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 1½" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350mW.
- ★ Ready etched and drilled printed circuit board back printed for fool proof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave, 168-535 metres and 1250-2000 metres.
- ★ All components ferrite rod and tuning assembly mount on printed board.
- ★ 5" P.M. speaker.
- ★ Parts list and circuit diagram 2s. 6d. free with parts.

ONLY £4.4.0

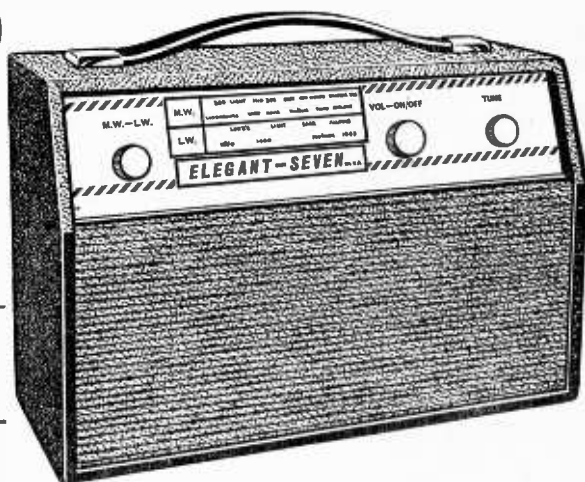Plus 7/6 P. & P. Parts List and circuit diagram 2/6 FREE with parts.



POWER SUPPLY KIT

To purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser. A.C. mains 200/250 volts. Output 9v 100mA. 9/6 extra.

RADIO & TV COMPONENTS (ACTON) LTD.

All orders by post to be sent to our Acton address

323 EDGWARE ROAD, LONDON, W2

Personal shoppers only. Early closing Thursday.

21C HIGH STREET, ACTON, LONDON, W3

OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

All enquiries stamped addressed envelope

RADIO CLEARANCE (1965) LTD.

27 TOTTENHAM COURT ROAD, LONDON, W.1

Tel. (01) 636-9188
(01) 636-4666/7

ELECTROLYTIC CONDENSERS

										s. d.												s. d.	
1µF	25v	3" x 1"	W.E.	1	6	50µF	12v	3" x 1"	W.E.	1	6	2,500µF	30v	3" x 1"	T.2	7	6						
1µF	350v	1" x 1"	W.E.	2	0	50µF	25v	1" x 1"	W.E.	1	6	2,500µF	50v	4" x 1"	T.2	10	0						
2µF	12v	3" x 1"	W.E.	1	6	50µF	50v	1½" x 1"	W.E.	1	9	4,000µF	25v	3" x 1"	T.2	9	0						
2µF	150v	3" x 1"	W.E.	1	6	50µF	275v	1½" x 1"	T.1	3	0	5,000µF	25v	3" x 1"	T.2	10	0						
2µF	275v	3" x 1"	W.E.	2	0	50µF	350v	2" x 1"	T.1	3	6	10,000µF	25v	4" x 1"	T.2	27	6						
2µF	350v	1" x 1"	W.E.	2	0	64µF	450v	2" x 1"	T.1	4	6	30,000µF	30v	4½" x 2"	T.2	45	0						
2µF	500v	1½" x 1"	W.E.	2	6	100µF	15v	1" x 1"	W.E.	1	6	32 x 32µF	350v	2½" x 1"	T.3	4	6						
4µF	25v	1" x 1"	W.E.	1	6	100µF	25v	1" x 1"	W.E.	1	6	50 x 50µF	350v	2" x 1"	T.3	6	6						
4µF	150v	3" x 1"	W.E.	1	6	100µF	50v	1½" x 1"	W.E.	2	6	60 x 100µF	275v	2" x 1"	T.2	6	0						
4µF	275v	1" x 1"	W.E.	2	0	100µF	100v	1½" x 1"	T.1	4	0	60 x 250µF	350v	4" x 1"	T.2	12	6						
4µF	350v	1" x 1"	W.E.	2	6	100µF	250v	3" x 1"	T.1	4	6	100 x 100µF	150v	3" x 1"	T.3	4	6						
4µF	500v	1½" x 1"	W.E.	3	0	100µF	350v	3" x 1"	T.2	5	0	100 x 200µF	275v	4" x 1"	T.2	9	6						
5µF Rev	20v	1½" x 1"	W.E.	2	6	100µF	450v	3" x 1"	T.2	7	6	150 x 200µF	350v	4" x 1"	T.2	12	6						
5µF	50v	3" x 1"	W.E.	1	6	125µF	500v	4" x 1"	T.2	9	0	250 x 250µF	325v	4½" x 1"	T.2	14	0						
5µF	70v	3" x 1"	W.E.	1	6	200µF	275v	2" x 1"	T.2	6	0												
6µF Rev	50v	1½" x 1"	W.E.	2	6	200µF	350v	3" x 1"	T.2	7	6												
8µF Rev	20v	1½" x 1"	W.E.	2	6	250µF	12v	1" x 1"	W.E.	2	6												
8µF	150v	1" x 1"	W.E.	1	6	250µF	18v	1" x 1"	W.E.	2	6												
8µF	275v	1½" x 1"	W.E.	2	0	250µF	25v	1½" x 1"	W.E.	3	0												
8µF	350v	1½" x 1"	W.E.	2	6	250µF	50v	1½" x 1"	W.E.	4	6												
8µF	500v	1½" x 1"	W.E.	3	0	350µF	12v	1½" x 1"	W.E.	2	6												
10µF	6v	3" x 1"	W.E.	1	6	350µF	25v	1½" x 1"	T.1	3	0												
10µF	50v	3" x 1"	W.E.	1	6	400µF	15v	1½" x 1"	W.E.	3	0												
10µF	150v	1" x 1"	W.E.	1	9	400µF	30v	1½" x 1"	W.E.	3	6	8 x 8µF	450v	1½" x 1"	T.1	4	0						
10µF	300v	1½" x 1"	W.E.	2	0	400µF	50v	1½" x 1"	W.E.	4	0	8 x 16µF	450v	2" x 1"	T.1	4	6						
10µF	250v	1½" x 1"	W.E.	2	0	400µF	275v	4" x 1"	T.2	9	0	16 x 16µF	275v	2" x 3"	T.1	4	0						
16µF	350v	1½" x 1"	W.E.	3	0	500µF	6v	1½" x 1"	W.E.	1	6	16 x 16µF	450v	2" x 1"	T.1	4	6						
16µF	500v	1½" x 1"	W.E.	2	0	500µF	15v	1½" x 1"	W.E.	2	6	16 x 32µF	275v	1½" x 1"	T.1	4	0						
25µF	12v	3" x 1"	W.E.	1	6	500µF	25v	1½" x 1"	W.E.	3	6	32 x 32µF	275v	2" x 1"	T.3	4	0						
25µF	25v	3" x 1"	W.E.	1	6	1,000µF	15v	2" x 1"	W.E.	3	9	50 x 50µF	300v	2" x 1"	T.2	4	6						
25µF	50v	1" x 1"	W.E.	1	9	1,000µF	18v	1½" x 1"	W.E.	3	9	50 x 150µF	300v	3½" x 1"	T.2	6	6						
30µF	6v	3" x 1"	W.E.	1	6	1,000µF	25v	1½" x 1"	W.E.	4	6	80 x 250µF	275v	4" x 1½"	T.2	9	6						
30µF	10v	2" x 1"	W.E.	1	6	1,000µF	50v	2" x 1"	T.2	7	6	80 x 40µF	450v	4" x 1½"	T.2	12	6						
32µF	150v	1½" x 1"	T.1	2	6	1,500µF	25v	1½" x 1"	W.E.	5	6	100 x 100µF	275v	3" x 1½"	T.2	6	6						
32µF	350v	2" x 1"	T.3	3	6	1,500µF	50v	3" x 1"	W.E.	7	6	100 x 400µF	275v	4½" x 1½"	T.2	13	6						
32µF	450v	1½" x 1"	W.E.	4	6	2,000µF	25v	3" x 1"	T.2	6	0	200 x 200µF	300v	4" x 1½"	T.2	12	6						
32µF	500v	2" x 1½"	T.2	4	6	2,000µF	50v	2½" x 1½"	T.2	9	0	300 x 300µF	300v	4½" x 1½"	T.2	14	0						

TERMINATION CODING

W.E.

Wire Ended.

T.1

Tag each end of condenser

T.2

Single end tag termination

T.3

Single end tag termination
Twist prong fixing.

TERMINATION CODING

W.E.	Wire Ended.			
T.1	Tag each end of condenser			
T.2	Single end tag termination			
T.3	Single end tag termination			
	Twist along fixing.			
8 x 8µF	450v	1½" x 1"	T.1	4 0
8 x 16µF	450v	2" x 1"	T.1	4 6
16 x 16µF	275v	2" x 1"	T.1	4 0
16 x 16µF	450v	2" x 1"	T.1	4 6
16 x 32µF	275v	1½" x 1"	T.1	4 0
32 x 32µF	275v	2" x 1"	T.3	4 0
50 x 50µF	300v	2" x 1½"	T.2	4 6
50 x 150µF	300v	3½" x 1"	T.2	6 6
60 x 250µF	275v	4" x 1½"	T.2	9 0
80 x 40µF	450v	4" x 1½"	T.2	12 6
100 x 100µF	275v	3" x 1½"	T.2	6 6
100 x 400µF	275v	4½" x 1½"	T.2	13 6
200 x 200µF	300v	4" x 1½"	T.2	12 6
300 x 300µF	300v	4" x 1½"	T.2	14 0

The above list represents just part of the extensive range of electrolytic condensers we carry in stock. All condensers are new and carry a twelve month guarantee. Please do not hesitate to contact us for quotations on bulk quantities. If you do not see the exact condenser you require please let us know your exact requirements.
Please send S.A.E. for Lists of Transformers, Transistors, Diodes, Rectifiers, Speakers and other components at Bargain Prices.

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE, YORKS. Telephone: Cleckheaton 2866

VALVE LIST—Ex Equipment. 3 months' guarantee
10F1, EF80, EB91, ECL80, EF50, PY82, PZ30, 20P3. All at 10/- per doz. Post paid. Single valves, post 7d.

ARP12 1/6	EL38 5/-	PY81 1/6	U801 8/6	5U4G 4/-
EB91 9d.	EY86 5/-	PY82 1/6	10C2 5/-	6B8 1/8
EBF80 3/-	KT36 5/-	PZ30 5/-	10P13 2/6	6K7 1/9
ECC81 3/-	PCC84 2/-	U25 5/-	185BT 8/6	6K25 5/-
ECC82 3/-	PCF80 2/-	U191 5/-	20D1 3/-	6P25 5/-
ECC83 4/-	PCL82 4/-	U281 5/-	20L1 5/-	6U4 5/-
ECL80 1/6	PL36 5/-	U282 5/-	20P1 5/-	6V6 1/9
EF50 1/-	PL38 7/-	U301 5/-	20P3 2/6	6P28 5/-
EF80 1/6	PL81 4/-	U329 5/-	20P4 8/6	EY51 2/6
EF91 9d.	PY33 5/-	U251 5/-		

NEW VALVES EX UNITS

IT4, 2/-; 1L4, 2/-; IA3, 2/6; IS5, 2/6; 12AT7, 3/-; 3A4, 2/6; EF91, 2/-; EB91, 1/3; EL91, 2/-; UU8, 4/-; 6SN7, 2/6; 10P13, 4/-; box of 50 ARP12 Valves, 22/-, post paid.

New Boxed TV Tubes. 14in. MW36/44, 40/-. Carriage 10/-, 12 months' guarantee.

90 degree Tubes. Twelve months' guarantee. Slight glass fault, 30/- and 50/-. Carriage 10/-.

Special Offer. 19 Sets, Mark 3, in good clean condition. Parts removed, B section, 807 valve and TX section made US. Receiver Bench Tested, all you would need is a Power Pack. Price 35/-, Carriage 10/-.

19 Sets in fair condition as above and also removed is the meter and relay, 10/-. Carriage 10/-. Not tested.

Speakers, removed from TV sets, all 3 ohm PM. and perfect, 6 x 4in. and 6in. round, 3/-, post 2/9. 6 for 22/-, post paid. 7 x 4in., 5/-, post 2/9. 6 for 34/-, post paid. 8in. round, 6/6, post 3/6. 10 x 5in., 10/-, post 3/6. 8 x 5in., 6/6, post 3/6.

New 12in. Speakers with built in tweeter, 28/6, post paid.
Ex Equipment Ekco L.O.P.T. U25 type or U26, 17/6, post 2/-.
Silicon Rectifiers. 500mA 800 PIV, 2/6. 6 amps 400 PIV, 4/-.

Thyristors. 5 Amp 100 PIV, 6/6. 5 Amp 200 PIV, 8/-, 5 Amp. 300 PIV, 10/-. 5 Amp 400 PIV, 12/-, post paid.

Reclaimed Tubes. Six months' guarantee, AW43/80, 40/-. MW43/80, 30/-. MW43/69, 30/-. CRM172, 30/-. CRM142, 17/-. 12in. Tubes, 10/-. 17in. Tubes, perfect but without guarantee, 17/-.

Carriage on any Tube in G.B., 10/-.
Ex Washing Machine Motors. Fully guaranteed. Single phase 1/2 h.p., 26/-, Sixth h.p., 15/-, Plus carriage, 10/-.

Jap Personal Earpiece, small or large plug, 1/11. Post paid.
Top Grade Diodes, 3/6 per dozen. Post paid. No duds.

Top Grade Mylar Tapes, 7in. Standard, 11/6. L.P., 14/-. 7in. D.P., 19/6. 5in. Standard, 7/9. L.P., 10/-. Post 1/6 per tape.

New Test Set Type 5B. Complete with valves and 0-1 mA 3in. meter LESS crystal. 35/-, Carr. 10/-.

Special Offer. Good MW43/64 tubes 17in. 10/-. Carriage 10/-.

Small S.W. Chassis 6in. x 4in. Complete with Slow Motion Drives and Condensers. 3/9. Post 6/6.

88 Set RX TX, less Send-Receive Switch. Crystals and Valves. 3/3.

Post 5/-.

U.S.A. tube unit B.C. 993A. Complete with 16 valves, tuning meter 3 inch tube type 3EP1. Used condition not guaranteed. 27/-, carriage 10/-.

U.S.A. tube unit, complete with two 5FP7 tubes 6H6 valves relay ECT 12/6, carriage 10/-, Used condition, not guaranteed.

Electronic Scrap, Half Cwt. 10/-. Carriage 20/-.

U.S.A. Battery Set Type 486-9 Mcs. Complete with six valves in clean condition. Not tested. 10/- and p/p 6/6.

Electric Clock Movement with train of Brass Gear Wheels. Tested 230-250 Volts A/C. 8/6 plus p/p 4/6.

Un-tested 13 Channel TV Sets 17 inch 50/-, 14 inch 30/-, Carriage 15/-.

Our new Walk Round Room is now open. Full of Surplus Bargains. Also our Special Department, nothing over sixpence.

THE PEMBRIDGE COLLEGE OF ELECTRONICS FOR TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course, of sixteen months' duration, provides a fundamental training for radio and television engineers. It includes theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Exactly half the time is spent on practical work and the course provides excellent practical experience on valve and transistor radio receivers and high-fidelity equipment and all well known makes of television receivers.

The Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Next Course commences 3rd January, 1968.

To: **The Pembridge College of Electronics (Dept. P11)**

34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name

Address

CMP 5

JOYSTICK

VFA ONLY 7' 6" LONG

WHAT'S A JOYSTICK V.F.A?

DAFT QUESTION

EVERYONE KNOWS IT'S THE 'JET AGE' AERIAL!
BUT DO YOU KNOW SOMEONE ONCE ASKED
'WHAT'S A JET PLANE?'

AND PRECIOUS FEW PEOPLE KNEW THE ANSWER
THAT'S PROGRESS!!


Bring your station right up-to-date with a Jet-age aerial!!

REMEMBER—THE PERFORMANCE OF THE JOYSTICK SYSTEM IS
SUBSTANTIATED BY MASSES OF CUSTOMER TESTIMONIALS—ALSO
BY THE FULL MONEY-BACK GUARANTEE—

WHAT'S YOUR PROBLEM?

YOU CAN ACCOMMODATE THE HANDSOME JOYSTICK
V.F.A. SYSTEM IN THE SMALLEST APARTMENT AND
THE WORLD IS AT YOUR SERVICE—

IT IS SIMPLICITY ITSELF!

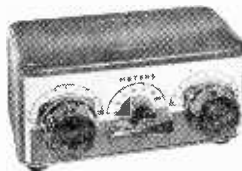

Joymatch Type 3A—General short
wave coverage for SWL. Band-
switched for amateur bands. One of
our range of Joymatch tuners.

Your Joystick V.F.A. stockist:

- BATH:** Ryland Huntley, 15 Old Bond Street.
BIRMINGHAM: Chas. H. Young Ltd., 170-172 Corporation St.,
R.S.C. Hi-Fi Centres Ltd., 61, Western Arcade.
BRADFORD: R.S.C. Hi-Fi Centres Ltd., 10 North Parade.
BRIGHTON: Technical Trading Co., Park Crescent Place.
BRISTOL: R.S.C. Hi-Fi Centres Ltd., 14 Lower Castle Street, Bristol 1.
CARDIFF: Wesak Radio, 54 Daniel St., Cathays.
CHELtenham: Spa Radio, 335-337 High Street.
CHESTERFIELD: J. & A. Twedy (Electronic Supplies) Ltd., 64 Lordsmill Street.
COVENTRY: Swanco Products Ltd., 247 Humber Avenue.
DARLINGTON: R.S.C. Hi-Fi Centres Ltd., 13 Post House Wynd.
LOUGHBOROUGH: Taurus Electrical Services, 26 Nottingham Rd.
LUTON: Coventry Radio Ltd., 189-191 Dunstable Road.
MANCHESTER: R.S.C. Hi-Fi Centres Ltd., 60A Oldham Street.
MIDDLESBROUGH: R.S.C. Hi-Fi Centres Ltd., 106 Newport Road.
NEWARK: George Francis (G3TWV), 93 Bahlerton Gate.
NEWCASTLE-UNDER-LYME: Sidney T. Chadwick, "Ham Radio,"
53 George Street.
NEWCASTLE-UPON-TYNE: R.S.C. Hi-Fi Centres Ltd., 41 Blackett
Street.
NEWPORT (MON.): K. F. Paul Ltd., 14 Dock Street.
NOTTINGHAM: Pete's Electronics Ltd., 165 Arkwright Street.
PORTSMOUTH: Technical Trading Co., 350-352 Fratton Road.
PURLEY (Croydon): G3HSC, 45 Green Lane (for demonstration
phone 660 2896).
SCARBOROUGH: Derwent Radio Ltd., 28 Hillcrest Avenue.
SHEFFIELD: R.S.C. Hi-Fi Centres Ltd., 13 Exchange Street,
Castle Market Buildings.
SOUTHAMPTON: Technical Trading Co., 72 East Street.
ST. HELENS: Harold Stott, 18 Westfield Street.
STOKE-ON-TRENT: See Sidney T. Chadwick, Newcastle-under-L.
WALSALL STAFFS: Normal Service Ltd., 113 Lichfield Street.
WORCESTER: Jack Porter Ltd., 30-31 College Street.
WORTHING: G.W.M. Radio Ltd., 40-42 Portland Road.
Technical Trading Co., Montague Street.
- DERBY:** R.S.C. Hi-Fi Centres Ltd., 29 Osma-ton Road, The Spot.
EDINBURGH: R.S.C. Hi-Fi Centres Ltd., 133 Leith Street.
GLASGOW: R.S.C. Hi-Fi Centres Ltd., 326 Argyle Street.
R.S.C. Hi-Fi Centres Ltd., 403 Sauchiehall Street.
HALIFAX: Albert Hind Ltd., 16-18 Waterhouse Street.
HARTLEPOOL: The Radio Shop, 58 Park Road.
HARWICH: C. H. Bernard & Sons Ltd., George Street.
HUDDERSFIELD: Radio Craft (Hudd) Ltd., 38 King Street.
HULL: R.S.C. Hi-Fi Centres Ltd., 91 Paragon Street.
Short Wave (Hull), 24A Newland Avenue.
ILFORD: Radio Developments Ltd., 298 Clayhall Avenue,
Barkingside.
LEEDS: R.S.C. Hi-Fi Centres Ltd., County (Mecca) Arcade, Briggate.
LEICESTER: R.S.C. Hi-Fi Centres Ltd., 32 High Street.
8, May Ltd., 12-14 Church Gate.
LIVERPOOL: R.S.C. Hi-Fi Centres Ltd., 73 Dale Street, Liverpool 2.
Stephen-James Ltd., 70 Priory Road.
LONDON: G. W. Smith & Co. (Radio) Ltd., 3 & 34 Lisle St., W.C.2.
Lasky's Radio Ltd., 118 Edgware Road, W.2.
Lasky's Radio Ltd., 297 Edgware Road, W.2.
Lasky's Radio Ltd., 33 Tottenham Court Road, W.1.
Lasky's Radio Ltd., 42 Tottenham Court Road, W.1.
Lasky's Radio Ltd., 162-3 Fleet Street, E.C.4.
R T & I Electronics Ltd., Ashville Old Hall, Ashville Rd., E.11.
Alfred Imhof Ltd., 112-116 New Oxford Street, W.C.2.

By the time this list appears in print it will be incomplete—so please write
to us for your local stockist, or order direct from:

PARTRIDGE ELECTRONICS LIMITED (Dept. PWK)
CAISTER HOUSE, PROSPECT ROAD, BROADSTAIRS, KENT
Tel: 0843 62535

THIS BROCHURE GIVES YOU THE FACTS
AND ONLY THE FACTS!

SEND TODAY

PARTRIDGE ELECTRONICS LIMITED (DEPT. PWK)
CAISTER HOUSE, PROSPECT ROAD, BROADSTAIRS, KENT

NAME..... CALL/BRs No.

ADDRESS



UK Pat. No. 1,045,481
and world patents granted or pending.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

R-S-C TAI2 13 WATT STEREO AMPLIFIER



Heavy cast construction. Latest high efficiency ceramic magnets. Treated cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range. Impedance 3 or 15 ohms. Response 40-18,000 c.p.s.

HF800D 8in. 8 watt	59/9	HF120 12in. 12 watt	69/9
HF810D 8in. 10 watt	24.18.9	HF126 12in. 12 watt	79/9
HF100D 10in. 8 watt	69/8	HF126 12in. 15 watt	89/9
HF100D 10in. 15 watt	25.18.9	HF127 12in. 15 watt	5 Gns.
		HF127 12in. 30 watt	9 Gns.

RECORD PLAYING UNITS All types available on Credit Terms. Ready for plugging in to Amplifier or Tape Recorder.

RP2 Consisting of Garrard SP25 fitted Goldring C890 high compliance ceramic Stereo/Mono ctrege with dmd stylus. above. Only **19 1/2 Gns.**

RP3 As above but with Goldring Lenco GL68 Transcription unit and C890 Cartridge **26 1/2 Gns.**

Normally over £33. Carr. 15/-

RP3M with Pickering Magnetic Cart-ridge **34 1/2 Gns.**

HIGH FIDELITY LOUDSPEAKER UNITS Cabinets of latest styling Satin Teak or Walnut, acoustically lined (and ported where appropriate). Credit terms available on all units.

The FULTON Size 11 x 14 x 7in. Fitted Volume Control. Ideal as sensitive ext. unit for Tape Recorder etc. Incorporates Audiotrine HF810 8in. speaker with cast chassis and treated cone surround. Response 45-13,000 cps. **£5.15.0**

Rating 8 watts. Imp. 3-8-15 ohms. Carr. 7/6

The DORSET Size 20 x 11 x 8in. Response 45-18,000 c.p.s. Rating 10 watts. Fitted Audiotrine HF810D speaker. Impedance 3 or 15 ohms. **£8.19.9**

Carr. 9/6

The DORCHESTER Size 24 x 15 x 10in. Fitted Audiotrine HF101D Speaker Rating 12 watts. Impedance 3 or 15 ohms. Frequency Response **12 1/2 Gns.**

30-20,000 c.p.s. Carr. 15/-

The GLOUCESTER Size 25 x 16 x 10in. 12in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Smooth response 40-20,000 c.p.s. Impedance 15 ohms. **12 1/2 Gns.**

Carr. 15/-

The BRONTE Size 22 x 15 x 9in. Fitted Wharfedale Super 8 RSDD or Audiotrine HF 815D Speaker, with Roll surround and dual cone. Rating 6/10 watts. Impedance 3 or 15 ohms. **13 Gns.**

Carr. 16/6

TA 6 WATT HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. A.C. mains operated Frequency Response 30-20,000 cps -2dB. Harmonic Distortion 0.3% at 1000 cps. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio or Tape. Input Selector Switch. Output for 3-15 ohm speakers. Max. Sensitivity 5mV. Fully enclosed enamelled case. 9 1/2 x 21 x 5 1/2ins. Attractive brushed silver facia plate 10 1/2 x 3 1/2ins. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 7/6.

Or factory built with 12 months guarantee **£7.19.11.**

R.S.C. SUPER 15 HI-FI AMPLIFIER

FULL TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 3-4 ohms.

LATEST MULLARD TRANSISTORS. AD148, AD149, OC127Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107.

5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads.

FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5mV. Radio/Aux or Ceramic P.U. 110 mV.

FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s.

TREBLE CONTROL: +15dB to -14dB at 10Kc/s. **NEG FEEDBACK:** 52dB.

BASS CONTROL: +12dB to -15dB at 50 c/s. **HUM LEVEL:** -75dB.

HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.25%. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6

Supplied factory built 15 1/2 Gns. Carr. 12/6. Deposit 49/- and 9 monthly payments 35/- (Total £184.0). Or fitted in beautiful walnut or Teak veneered cabinet as illustrated. 4 Gns. extra.

ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS.

AUDIOTRINE PLINTHS



for Record Playing Units. Teak finish out for Garrard 1000, 2000, 3000, AT6 Mk 2. AT60, SP25 or Goldring GL68. Available with clear Perspex cover as illustrated. **£5.19.11**

HI-FI LOUDSPEAKER ENCLOSURES

All types of pleasing modern design acoustically lined and ported and beautifully finished in light Teak or Walnut veneer. Credit terms available

SE8. Size 20 x 11 x 8in. Gives pleasing results with any 8in. Hi-Fi speaker. Carr. 7/6

SE9. For optimum performance with any Hi-Fi 8in. speaker. Size 22 x 15 x 9in. Carr. 7/6

SE10. For outstanding results with 10in. Hi-Fi Speaker. Size 24 x 15 x 10in. **£6.19.9**

Carr. 10/-

SE12. For outstanding performance with any 12in. Hi-Fi speaker. Cut 8 Gns. 10/- for tweeter. Size 25x16x10 1/2in.

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST: S.A.E. for leaflet.

ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS. Incorporating latest Magnavox Tape Clock. High Flux P.M. Speaker, empty Tape Spool, Reel of Best Quality Tape and handsome Portable Cabinet of latest styling. finished dark grey leathercloth. Size 14 1/2 x 17 x 8 1/2in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. Deposit 4 Gns. and 9 monthly payments 59/6 (Total 29 1/2 Gns.) 4 Track Model 3 Gns. extra. Carr. 19/6.

R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER

High-sensitivity 200-250v. A.C. Mains operation. ★Sharp A.M. Rejection. ★Drift-free reception. ★Output ample for any amplifier (approx. 500 m.v.). ★Simple alignment instructions. ★Output available for feeding tuning meter. ★Output for feeding Stereo Multiplexer. ★Tuner head using silicone Planar Transistors. ★Designed for standard 80 ohm co-axial input. Made to visually match our Super 15 and 30 amplifiers and of the same high standard of durability and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only first grade transistors and components used. Our latest product giving you the best at half the cost of comparable units. Stereo vrsn. Carr. 16/-

26 1/2 Gns.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349

BRISTOL 14 Lower Castle St. (Half-day Wed.) Tel. 22904

BIRMINGHAM 30/31 St. Western Arcade opp. Snow Hill Station (Central) 1279. No half-day

DERBY 26 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361

DARLINGTON 13 Post House Wynd (Half-day Wed.)

EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766

GLASGOW 326 Argyle St. (No half-day) Tel. City 4158
403 Sauchiehall St. (Opp. Locarno) Tel. 332-1572

HULL 91 Paragon Street. (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries please. Hi-Fi Catalogue 4/6

Open all day Sat. except High Holborn

LEICESTER 32 High Street. (Half-day Thurs.) Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggate (No half-day) Tel. 28252

LIVERPOOL 73 Dale St. (No half-day) Tel. Central 3573

LONDON 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629
96 High Holborn, WC1. Tel. HOL 9874 (Half-day Sat.)
60A-60B Oldham Street (No half-day) Tel. CENTRAL 2778

MANCHESTER 106 Newport Rd (Half-day Wed) Tel. 47096

MIDDLESBROUGH 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469

NEWCASTLE UPON TYNE 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716

SHEFFIELD

LONDON-NEWCASTLE-GLASGOW

New branches now open—see addresses

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



high quality output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Provision for use as straight (mono) 10 watt. Valves ECC83, ECC83, EL84, EL84, E281. For 2-3 ohm speakers. Complete kit with full wiring diagrams and instructions. Or supplied factory assembled with 12 months' Carr. 11/6 **£8.15.0** Terms: Dep. 36/- and 9 monthly payments 25/- (Total £13.4.9).

R.S.C. STEREO/20 HI-FI AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE. (7) valves ECC83, (2) ECC83, (4) E281. Frequency Response: +2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 5 millivolts max. Harmonic Distortion: (each channel): 0.2%. *Four-position tone compensation and Input Selector Switch. *Stereo/Mono switch. *Neon panel indicator. *Handsome Perspex Frontplate. *Separate Bass "Lift" and "Cut" controls. Output transformers are high-quality sectionally wound. Outputs for 3 and 15 ohm speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 months guarantee. Or deposit £3 and 9 monthly payments 43/2 (Total £22.8.6). Send S.A.E. for leaflet. Carr. 12/6 **19 Gns.**



R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "Lift" and "cut". Hum level 70dB down. Negative Feedback 15dB. Reserve power supply 300V 5 mA, 6.3V. 1.5A. for Radio Tuner or Tape Pre-amp. For A.C. mains 200-250V. Speaker output 3 ohms. Complete in every detail with fully punched enameled chassis, point-to-point wiring diagrams and instructions. Or assembled ready for use 6 Gns. plus 5/9 carr. **£4.17.9**

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stage. Power figures equal to the best expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000c.p.s. Specially designed sectionally wound ultra linear output transformer with 807 output valves. All first grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis, point-to-point wiring diagrams and instructions. **12 Gns.** Carr. 12/6 Supplied factory built with EL34 output valves. 12 months guarantee for 15 Gns. If required perforated cover with carrying handles can be supplied for 21/-. Send s.a.e. for leaflet. TERMS: Deposit 48/- and 9 monthly payments of 33/7 (Total £17.10.3).

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP Two input sockets with associated controls allow mixing of "mike" and gram, etc., etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84, E281. High quality sectionally wound output transformer and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR Bass AND TREBLE. Frequency response +15dB 30-20,000c.p.s. negative feedback loops. Hum level -60dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic P.U.s, all types "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Reserve L.T. and H.T. for Radio Tuner or Tape Pre-amp. Size approx. 12 x 9 x 7in. For A.C. mains 200-250V. 50 c.p.s. Output for 3 and 15 ohm speakers. Full instructions and point-to-point wiring diagrams (or factory built £11.15.0). **£8.15.0** Metal cover with 2 handles available for 21/-. TERMS ON ASSEMBLED UNITS. Carr. 11/6 Deposit 36/6 and 9 monthly payments of 25/9 (Total £13.3.3). Send S.A.E. for leaflet. R.S.C. A11 TRANSISTORISED VERSION of above complete kit 9 Gns. Carr. 9/6.

R.S.C. BASS-REGENT 50 WATT AMPLIFIER



AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape, and general public address. *UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 12in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response. *4 Jack inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes". *Cabinets covered in two-tone Rexine/Vynal with gold trimming. Fitted carrying handles. *Separate Bass and Treble Controls giving "Lift" and "cut". **49 1/2 Gns.** Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at three times the price. Or deposit £7.17.6 and 9 monthly payments of £5.10.10 (Total £55 Gns.). Carr. 30/-

B20 MULTI-PURPOSE AMPLIFIER especially suitable for Bass Guitar

Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynal. Size approx. 24 x 21 x 11in. Send S.A.E. for leaflet. **29 1/2 Gns.** Or Deposit £4.14.6 and 9 monthly payments of 4/- (Total £34.8.6). Carr. 17/6.



G80 80 WATT AMPLIFIER

2 Channels, 6 inputs, Tremolo, 2 Columns and 1 Bass Speaker unit with two 15in. Extra Heavy Duty Speakers. **99 Gns.** Carr. £3

R.S.C. BATTERY/MAINS CONVERSION UNITS



Type BM1. An all-dry battery eliminator. Size 5 1/4 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200-250V. 50c/s is available. Complete kit with diagram 47/9 or ready for use 59/11.

G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, Vocal Groups, etc.

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Heavy Duty 12in. 20 watt Speaker. Cabinet covered in attractive Rexine/Vynal. Size 18 x 18 x 8in. Deposit 3 Gns. Carr. and 9 monthly payments of 43/7 **19 1/2 Gns.** (Total £22.15.3). S.A.E. for leaflet.

SELENIUM RECTIFIERS F.W. (Bridged)

All 612v. D.C. output. Max. A.C. input 15v. 1a. 3/11. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.

HEAVY DUTY SELENIUM RECTIFIERS 19/9

12v. 15 amps. F.W. (Bridged). Only

POWER PACK KIT

Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing capacitors, chassis and circuit. 200-250V. C. **22/11** mains. Output 250V. 60mA 6.3V. 2a. Supplied with case in lieu of chassis 26/11. Or assembled 39/11.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1 Switched Equalisation. Positions for Recording at 11in., 3 1/2in., 7 1/2in. per sec. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most Tape Decks. Terms available. **10 1/2 Gns.**

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynal. Ideal for vocalists and Public Address. 15 ohm matching. Type C58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in. Or deposit 44/- and 9 monthly pmts 34/9 (Total £18.1.6) Carr. 10/- Type C412, 40 watts. Fitted four 12in. 12,000line 10 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- Or Deposit £3.13.0 and 9 monthly payments of 50/- (Total £26.3.0). **15 Gns.** Carr. 10/- **22 Gns.**




30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group

A 4 Input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. Latest valves. Strong Rexine covered cabinet with carrying handles. Attractive black/gold perspex fascia. For 200-250V. A.C. mains. For 3 or 15 ohm speak- **17 Gns.** Carr. 12/6 For leaflet, deposit £3 and 9 monthly payments of 37/5 (Total £18.10.9).

12in. HIGH QUALITY L'SPEAKERS

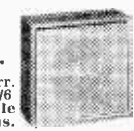In teak veneered cabinets. 10 Watt Model. Gauss 12,000 lines. 3 or 15 ohms. Carr. 7/6 **5 Gns.**



20 Watt Model. 15 ohm. Size 18x18x10in. Gauss 12,000lines. Rexine covered £1 extra. Terms available 30 Watt Model. Rexine covered 10 Gns. **8 Gns.** Carr. 10/6

LOUDSPEAKERS

Limited number at fraction of list price 15 ohms impedance. Brand new, guaranteed. Terms available. Carr. 6/9 **12in. 20 watt DUAL CONE Heavy Duty £5.11.9** **£7.19.9** Normally **12in. HEAVY DUTY 30 watts Carr. 10/-** £13 approx. **15in. EXTRA HEAVY DUTY 40 watts Carr. 15/-** **12 Gns.** Massive units. Gauss 17,000 lines. Usually app. £19.

HIGH FIDELITY 12in. 10 WATT SPEAKERS 59/11

Flux Density 12,000 lines. Impedance 3 or 15 ohms.

TRANSISTOR SALE

Mullard OC71, OC72, OC81, 2/11, OC44, OC45, 3/11, OC75, 7/9, AF17 6/9, Post 6d. for 3.

JASON VHF/FM TUNER

Complete kit with valves. **£6.19.11**

INTEREST CHARGES REFUNDED

on H.P. and Credit Sale Accounts settled in 3 months. Deposit 3/- in £

R.S.C. GRAM AMPLIFIER KIT. 4 watts output. Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250V. A.C. Fully insulated chassis. Circuit, etc. supplied. Only 49/11.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interwired and Impreg- Primary 200-250V. 50c/s. Screened. MIDGET CLAMPED TYPE 8 1/2 x 2 1/2 in.

250v., 60ma, 6.3v. 2a	14/11
250-250v., 60ma, 6.3v. 2a	14/11
FULLY SHROUDED UPRIGHT MOUNTING	
250-250v., 60ma, 6.3v. 2a, 0-5-6.3v. 2a	19/9
250-250v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	38/9
300-300v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	38/9
300-300v., 130ma, 6.3v. 4a, c.t., 6.3v. 1a	41/9
For Mullard 510 Amplifier	
350-350v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	38/9
350-350v., 150ma, 6.3v. 4a, 0-5-6.3v. 3a	38/9
425-0-425v., 200ma, 6.3v. 4a, c.t., 5v. 3a	67/9
425-0-425v., 200ma, 6.3v. 4a, 6.3v. 4a, 5v. 3a	69/9
450-0-450v., 250ma, 6.3v. 4a, c.t., 5v. 3a	79/9

TOP SHROUDED DROP-TYPE TRANSFORMERS

250-0-250v., 70ma, 6.3v. 2a, 0-5-6.3v. 2a	19/9
250-0-250v., 100ma, 6.3v. 2a, 6.3v. 1a	21/9
250-0-250v., 100ma, 6.3v. 2a, 0-5-6.3v. 2a	22/9
350-0-350v., 80ma, 6.3v. 2a, 0-5-6.3v. 2a	23/9
250-0-250v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	32/9
300-0-300v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	32/9
300-0-300v., 130ma, 6.3v. 4a, 0-5-6.3v. 1a	39/9
Suitable for Mullard 510 Amplifier	
350-0-350v., 100ma, 6.3v. 4a, 0-5-6.3v. 3a	39/9
350-0-350v., 150ma, 6.3v. 4a, 0-5-6.3v. 3a	39/11

FLAMEPROOF TRANSFORMER POWER PACK TYPE

1.3v. 1.5a 0/9, 6.3v. 2a 7/9, 6.3v. 3a 8/9, 6.3v. 4a 10/9, 12v. 1a 8/9, 12v. 3a or 24v. 1.6a 19/9, 0-9-18v. 1 1/2a 15/9, 0-12-25-42v. 2a 27/9.	
--	--

CHARGER TRANSFORMERS 0-9-15v. 1 1/2a, 13/11

2 1/2a, 16/11, 3a, 18/11, 5a, 21/11, 6a, 25/11, 8a, 31/11, AUTO (Step Up/Step Down) TRANSFORMERS	
--	--

0-110/120v.-200-250v. 50-80 watts, 14/9	
150 watts, 29/11, 250 watts, 49/9, 500 watts, 99/9	

OUTPUT TRANSFORMERS

Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω	7/9
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω	11/9
Push-Pull 10 watts 6V6 ECL86 to 3 Ω, 5 Ω or 15 Ω	11/9
Push-Pull EL84 to 3 Ω or 15 Ω 10-12 watts	19/9
Push-Pull Ultra Linear for Mullard 510, etc.	26/9
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω	29/9
Push-Pull 20 watt high quality sectionally wound, EL34, 6L6, KT66, etc., to 3 or 15 Ω fully shrouded	55/9

SMOOTHING CHOKES


150mA, 7-10H, 200 Ω 12/9.	
100mA, 10H, 200 Ω 11/9.	
80mA, 10H, 350 Ω 7/9.	
60mA, 10H, 400 Ω 4/11.	



How to build yourself a high fidelity loudspeaker for £13 in half a day (using the Super 8)

You'll be astounded by your own ability—for this Wharfedale kit enables you to build a Column Speaker of outstanding quality. It occupies only one square foot of floor space yet has a frequency range from 40 Hz to 20,000 Hz. Suitable for either Stereo or Mono.

Principle of construction of system in concrete column :

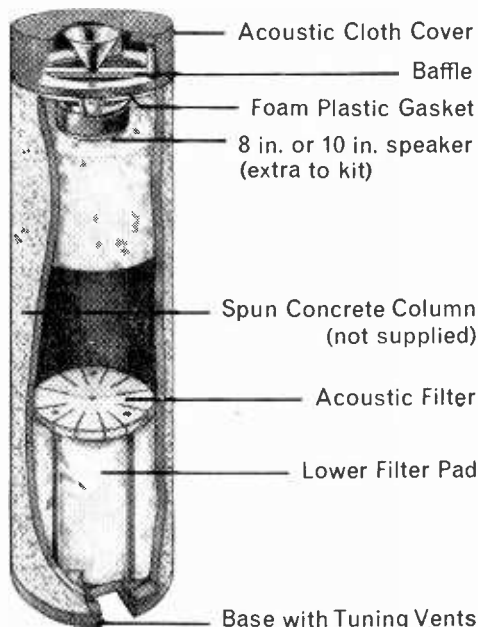

SUPER 8
Impedance 10/15 ohms.
Pole size 1" diameter.
Frequency range: 40–20,000 Hz. Aluminium voice coil. Roll surround and double diaphragm. Weight: 4½ lb.
£7. 2. 0.



SUPER 10
Impedance 10/15 ohms.
Pole size 1" diameter.
Frequency range: 30–20,000 Hz. Aluminium voice coil. Roll surround and double diaphragm. Weight: 10½ lb.
£11. 16. 8.

Send this coupon for our free instruction leaflet on the Concrete Column Speaker.

PLEASE SEND ME LITERATURE

NAME

ADDRESS

PW/11.

I AM INTERESTED IN—
CONCRETE COLUMN SPEAKER ☐ COMPLETE SPEAKER SYSTEMS ☐
SPEAKER UNITS/D.I.Y. CABINETS ☐ AMPLIFIERS ☐
STEREO RADIO TUNERS ☐



RANK WHARFEDALE LTD., IDLE, BRADFORD, YORKSHIRE.

COCKTAIL/STEREOGRAM CABINET £25




Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35½in., width 52½in., depth 14½in. Legs 19in. extra

STEREO RADIO-GRAM CABINETS £15

Superbly made and styled in Veneered English Walnut

LIFT UP LID TO CHANGER AND RECORD STORAGE COMPARTMENT

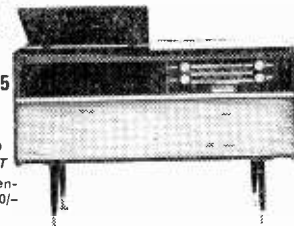Position 8" x 5" Twin Speaker, Dimensions: 45 x 15½ x 15½. Legs 19in. Carr. 30/- Other Models—Send for List



17in.—£11.10.0

3 Star Guarantee

★ Tube ★ Valves

★ Components Carr. 30/-

TWO-YEAR GUARANTEE EX-RENTAL TELEVISIONS

FREE ILLUSTRATED LIST OF TELEVISIONS

17"–19"–21"–23"

WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

TWO-YEAR GUARANTEED
TUBES 100% REGUNNED

14in.—69/6 17in.—89/6

21in. and ALL SLIMLINE TUBES 99/6

EXCHANGE BOWLS. Carr. 10/6

EX MAINTENANCE TESTED TUBES

17in.—35/-

Carr. 5/- (not slimline)

DUKE & CO. (LONDON) LTD.

6213/3 Romford Road E.12

Tel. 01-478-6001/2/3

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94
Set of 4 for 18/6, DAF96, DF96, DK96, DL96, 4 for 24/6

1A7GT	7/6	7Y4	6/8	DH81	12/6	EF183	6/8	PCL85	3/3	UCH42	8/9
1N6GT	7/3	10F1	9/9	DK32	7/9	EF184	5/8	PCL86	3/3	UCH81	6/-
1N6GT	7/9	10P13	10/6	DK91	5/6	EH90	6/6	PEN44	6/9	UCL82	7/-
1R5	5/6	12AT7*	3/9	DK92	8/-	EL33	6/8	PEN36C15/	6/9	UCL83	8/9
184	4/9	12AU6	4/9	DK96	6/6	EL41	3/6	PPL20013/6	6/9	UF41	8/-
185	3/9	12AU7	4/9	DL33	6/9	EL84	4/9	PL36	9/-	UF80	7/-
1T4	2/9	12AX7	4/9	DL35	5/-	EL90	5/-	PL81	6/9	UF89	5/9
3A5	7/-	12K8GT	7/6	DL92	4/9	EL95	5/-	PL82	6/6	UL41	8/9
3Q4	5/6	20F2	11/6	DL94	5/6	EM80	5/9	PL83	6/3	UL44	20/-
384	4/9	20L1	14/6	DL96	6/-	EM81	6/9	PL84	6/3	UL84	6/-
3V4	5/6	20P1	9/-	DY86	5/9	EM84	6/3	PL500	13/6	UY21	8/9
5U4G	4/6	20P3	14/9	DY87	5/9	EM87	6/6	FX25	7/9	UY41	5/6
5V4G	7/9	20P4	17/-	EABCB80	6/-	EY51	6/3	PY32	5/6	UY85	4/9
5Y3GT	5/-	25U4GT11/6	6/-	EAF42	8/6	EY86	6/-	PY33	8/6	VP4B	10/6
5Z4G	7/6	30C15	11/6	EB91	2/3	EZ40	6/9	PY80	5/3	VP1321	21/-
6/30L2	11/9	30C17	12/6	EB93	7/-	EZ41	6/9	PY81	5/3	W77	3/3
6AL5	2/3	30C18	11/9	EB94	6/6	EZ80	4/6	PY82	5/-	Z77	3/6
6AM6	3/6	30P5	12/-	EBP80	6/-	EZ81	4/6	PY83	5/9	Transistor	3/6
6AQ5	4/9	30FL1	13/9	EBP89	5/9	GZ32	9/-	PY88	7/3	AC107	10/-
6AT6	4/-	30FL14	12/6	ECC81	3/9	KT61	6/6	PY800	6/-	AC127	6/-
6BA6	4/6	30L15	12/-	ECC82	4/9	KT81	12/-	PY801	6/-	AD140	15/6
6BE6	4/3	30L17	13/-	ECC83	7/-	N18	5/8	R19	7/-	AF102	18/-
6BG6G	15/-	30P4	12/-	ECC84	6/6	N78	14/9	R29	12/6	AF115	6/-
6BJ6	6/9	30P12	11/-	ECC85	5/6	N108	13/6	U25	11/6	AF116	6/6
6BW6	7/3	30P19	12/-	ECC80	7/-	PC86	8/-	U26	11/6	AF117	5/-
6C86	6/6	30PL1	14/6	ECC82	6/9	PC88	8/-	U47	13/6	AF118	8/6
6F1	7/9	30PL13	14/6	ECC86	9/-	PC97	5/9	U49	13/6	AF124	7/6
6F13	3/6	30PL14	14/6	ECC85	6/-	PC900	7/9	U52	4/6	AF125	7/6
6F14	9/-	35L6GT	7/6	ECH42	9/-	PC984	5/6	U78	3/6	AF126	7/-
6F23	12/6	35W4	4/6	ECH81	5/3	PC989	9/9	U191	11/6	AF127	7/-
6K7G	1/6	35Z4GT	4/6	ECH84	6/6	PCC180	8/6	U301	13/-	OC22	9/9
6K8Q	4/3	6063	12/6	ECL80	6/-	PCF80	6/6	U401	18/-	OC25	9/6
6K8GT	7/6	AZ31	9/-	ECL82	6/3	PCF82	6/-	U492	9/-	OC26	6/9
6L18	6/-	B38	4/9	ECL86	7/9	PCF86	9/-	UAB300	9/-	OC44	3/6
6V6G	3/6	B729	12/6	EF39	3/9	PCF80010/6	6/6	UAF42	7/9	OC45	3/3
6V6GT	6/6	DAC32	7/3	EF41	9/6	PCF801	8/9	UB41	6/6	OC71	3/6
6X4	3/6	DAF91	3/9	EF80	4/9	PCF802	9/6	UBC41	6/9	OC72	4/9
6X6GT	5/9	DAF96	6/-	EF85	5/-	PCF80511/9	6/6	UBF80	6/-	OC75	5/9
7B6	10/9	DFC90	7/-	EF86	6/3	PCF80611/9	6/6	UBF89	5/9	OC81	3/6
7B7	7/-	DF33	7/9	EF89	5/-	PCF80811/3	6/6	UBL21	9/-	OC81D	3/6
7C5	12/-	DF91	2/9	EF91	3/6	PCL82	6/9	UCC84	7/9	OC82	5/9
7C6	6/9	DF96	6/-	EF92	3/3	PCL83	8/6	UCC85	6/6	OC82D	5/9
7H7	5/6	DH77	4/-	EF97	7/6	PCL84	7/-	UCF80	8/3	OC170	5/-

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

BUILD YOURSELF A QUALITY TRANSISTOR RADIO-GUARANTEED RESULTS BACKED BY OUR SUPER AFTER SALES SERVICE!

THE MAGNIFICENT ROAMER 7 MKIV

SEVEN WAVEBAND PORTABLE AND CAR RADIO WITH A SUPER SPECIFICATION GIVING OUTSTANDING PERFORMANCE!

● 7 FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.


- Extra tuning of Luxembourg, etc.
- Built in ferrite rod aerial for Medium and Long Waves.
- 5 Section 22 inch chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening.
- Socket for Car Aerial.
- Powerful push pull output.
- 7 transistors and two diodes including Philco Micro-Alloy R.F. Transistors.
- Famous make 7in. x 4in. P.M. speaker for rich-tone volume.
- Air spaced ganged tuning condenser.
- Separate on/off switch, volume control, wave change switches and tuning control.
- Attractive case with hand and shoulder straps. Size 9in. x 7in. x 4in. approx.
- First grade components.
- Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build with guaranteed results.

Total building costs

£5.19.6

P. & P.
5/6

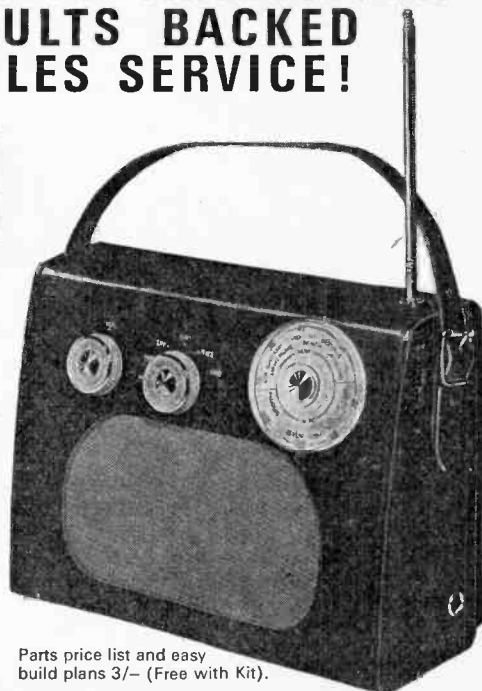Parts price list and easy
build plans 3/- (Free with Kit).



TRANSONA FIVE

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Fully tunable. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone super dynamic 3in. speaker, all first grade components. Easy build plans and parts price list 1/6. (FREE with kit).

Total building costs

42'6

P. & P.
3/6



MELODY SIX

TWO WAVEBAND PORTABLE WITH 3in. SPEAKER

Handsome leather-look case size 6½ x 3½ x 1½in. with gilt trim and hand and shoulder straps. Fully tunable over both Medium and Long waves. Incorporates pre-tagged circuit board, 8 stages—6 transistors and 2 diodes, ferrite rod aerial, push-pull output, wave change slide switch, tuning condenser, volume control, 3in. moving coil speaker etc. Easy build plans and parts price list 2/-. (FREE with kit).

Total building costs

59'6

P. & P.
3/6



ROAMER SIX


SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings, size 7½ x 5½ x 1½in. World wide reception. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components, 8 stages—5 transistors and 2 diodes including Philco Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra.) Easy build plans and parts price list 2/- (FREE with kit).

Total building costs

79'6

P. & P.
3/6

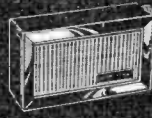

POCKET FIVE

TWO WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black and gold case. Size 5½ x 1½ x 3½in. Fully tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone 3in. moving coil speaker etc. Easy build plans and parts price list 1/6 (FREE with kit).

POCKET FIVE Medium and Long Wave version with miniature speaker **ONLY 29/6**. P. & P. 3/6.

Total building costs

42'6

P. & P.
3/6



MELODY MAKER 6

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Smart pocket size case, 6½ x 3½ x 1½in. with gilt fittings. Fully tunable over both Medium and Long Waves with extra M.W. band for easier tuning of Luxembourg, etc. 8 stages—6 transistors and 2 diodes, top grade 3in. speaker, 2 R.F. stages for extra boost, high "Q" ferrite rod aerial. Easy build plans and parts price list 2/- (FREE with kit).

Total building costs

69'6

P. & P.
3/6



SUPER SEVEN

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings and carrying strap. The ideal radio for home, car or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts. Price list 2/- (FREE with kit).

Total building costs

79'6

P. & P.
3/6

RADIO EXCHANGE CO.

Callers side entrance Barratts Shoe Shop • Open 9-5 p.m.
Saturday 9-12.30 p.m.

61 HIGH STREET, BEDFORD


Telephone: Bedford 52367

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

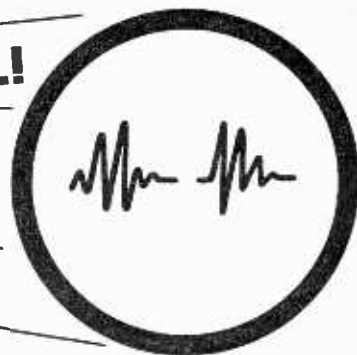


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .

1 ▶ OWN and HANDLE a

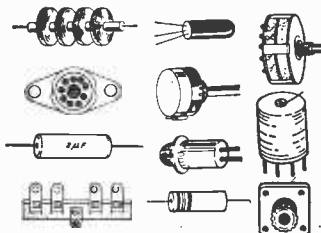complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

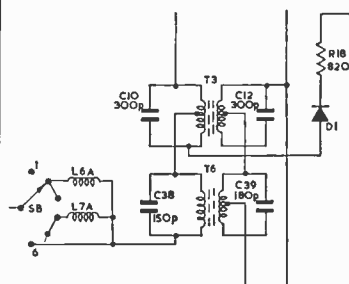

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE

**POST NOW
for
BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME **BLOCK CAPS**

ADDRESS **PLEASE PW11**

PRACTICAL WIRELESS

VOL 43 No 7

issue 729

NOVEMBER 1967

TOPIC OF THE MONTH

Successful Servicing

WHEN we began the series "Repairing Radio Sets" in the April issue, we little realised how successful it would be. True we liked the material supplied by the joint authors, but long before the first half of the series ended in September it was clear that P.W. had come up with something of special interest. And this bore out the remark in the April leader that "inside most radio enthusiasts is a service engineer trying to break out"!

The second half of the series is due to start in the Spring and should be equally well received. And it has already been suggested that a further series, covering tape recorders, would be welcome. This can be arranged and if sufficient interest is shown we will make the necessary arrangements.

One reason we are so pleased at the response to Repairing Radio Sets is to see such an obviously keen interest in the actual subject matter. The repairing of faulty equipment, or the putting right of equipment which has never functioned properly, can be one of the most rewarding aspects of the hobby. Of course, it would be pleasant to have sets which never go wrong or constructional projects which work perfectly first time without even minor adjustments, but in that way many enthusiasts would learn little of what goes on behind the front panel.

There is nothing like having a sticky fault, and successfully diagnosing it, to provide a good understanding of what makes circuits work, or fail. The necessary probings, circuit tracing, testing, meter readings and brain searching should all help to expand both theoretical and practical knowledge.

Many beginners fail dismally in repairing sets because their basic approach is wrong. You might sometimes be lucky in finding the proverbial "loose screw" or disconnected wire, but little reliance can be placed on such fortuitous clues. Successful repair work needs not luck but a clear logical approach based on theory.

If our articles have only shown the way to get the mind thinking in a logical and progressive way when tackling faulty equipment then we are more than satisfied.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	475
News and Comment	476
Practically Wireless <i>by Henry</i>	486
New Books	493
Showtime '67	494
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	505
Letters to the Editor	521

CONSTRUCTIONAL

Transistor Car Radio <i>by L. McNamara B.Sc.</i>	478
3 Watt Record Amplifier <i>by R. V. Askey</i>	489
2 Voltmeters for the Workshop, Part II <i>by Graeme Lynn</i>	497
Simple 2 Metre Converter <i>by J. Oliver, G8ANJ</i>	502
Crystal Calibration Oscillator, Part II <i>by R. C. Kitching</i>	513
Wireless Intercom <i>by P. J. Smith</i>	525

OTHER FEATURES

P.W. Data Rule <i>by I. J. Kampel</i>	483
Semiconductor Audio <i>by R. Leyland</i>	500
Guide to Surplus Communication Receivers, Part IV <i>by K. Adkins, B.Sc.</i>	509

DECEMBER ISSUE WILL BE PUBLISHED ON
NOVEMBER 3rd

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes London, W.C.2. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1967. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

NEWS AND COMMENT...

G.B.—U.S. RESEARCH STATION

The Ministry of Defence and the United States Department of Defence are to collaborate in the construction and operation of a radio research station at Orfordness, Suffolk. The station will conduct joint research into problems of long-range propagation of radio signals.

The station will consist of a large aerial array and some associated buildings. Most of the technical equipment will be of American design and manufacture.

B.A.E.C. REDESIGN NEWSLETTER

The British Amateur Electronics Club have completely redesigned their sixth Newsletter. It now has a format measuring 8 x 10in. and contains, for the first time, letters written by members all over the British Isles.

The B.A.E.C. is starting a series of meetings at the Penarth Secondary School, St. Cyres Road (Off Redlands Road) Penarth, Glamorgan, every Thursday evening at 7 p.m. and further details can be obtained from Cyril Bogod, "Dickens", 26 Forrest Road, Penarth, Glamorgan.

TRIBUTE TO FARADAY

Michael Faraday from whose famous experiments at the Royal Institution in Albemarle Street so much of modern electrical technology stems died 100 years ago, on 25 August 1867.

The grave in which Faraday and his wife are buried, and which was entrusted to the care of the Institution of Electrical Engineers in 1937, is in Highgate Cemetery.

To mark this centenary of Faraday's death, wreaths were laid on the grave on 25 August 1967, by Sir Albert Mumford, K.B.E., Past-President of the Institution of Electrical Engineers and Lord Kings Norton of Wotton Underwood, Vice-President of the Royal Institution.

BBC WORLD SERVICE



Malcolm Nisbet, compere of the BBC World Service's Newest programme, "World Radio Club", holds aloft the target area of his programme and the Club card. To become a member of this programme for short wave enthusiasts, listeners simply write to: World Radio Club, BBC, Bush House, London, W.C.2.

Malcolm himself is a DXer and he gives DX news as well as tips to newcomers.

HEATHCRAFT MINI-DRILL



For people needing a small, efficient and versatile drill for those delicate jobs for which the big drill is far too clumsy, Heathcraft offer the *Mini-Drill*. Measuring only five inches long this midget powerhouse with its variety of miniature chucks and tools, will prove invaluable for a wide range of uses. There are three models—*Standard*, *Super* and *Deluxe*, all battery powered. The *Standard* operates from a 4.5 volt battery, while the *Super* and *Deluxe* models work from 9 volts. The latter two models will also operate from 12 volts.

Current consumption for the *Super* model, using a 9 volt supply is 900mA surge on switching on, falling almost at once to 480mA nominal. For 12 volt supplies consumption is 2 amps surge, 550mA nominal.

The *Super* model is supplied complete with three chucks and six tools which include a midget buffing wheel, a small grindstone and a drill which is just right for drilling a hole in printed circuit boards to allow the wire ends of resistors etc., to pass through. Using the grinding wheel on a piece of copper laminate board it is possible to grind away unwanted copper foil and thus "draw" a printed circuit.

Further details available from Heathcraft Metal Products Ltd., 54 Poland Street, London, W.1.

MOSAIC BREADBOARDING KIT


A "kit" of Mosaic breadboarding elements, comprising a range of devices from which prototype complex circuits may be built up, has been introduced by Semiconductor Division of the Plessey Components Group.

In the long term, it is anticipated that all equipment not requiring high-speed logic will utilise the MOS technique. The new kit, which is designated Mk100, offers two main advantages. It provides the customer with a comprehensive range of devices, and it costs considerably less than the same number of elements bought individually.

The Mk100 kit, which is the first of a projected range, contains 50 devices.

NEWS AND COMMENT

R.N.W.W. TRANSMITTER

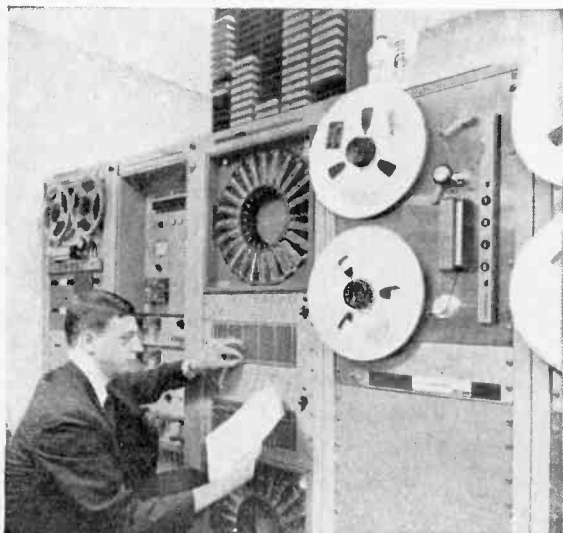

Steve Grayson, host of Radio New York Worldwide's special weekly programme for international radio enthusiasts... DXing Worldwide which is broadcast on Saturdays at 1735GMT, and on Sundays at 1935GMT (beamed to the British Isles, Western Europe and all of Latin America), is shown programming Radio New York Worldwide's "local" New York City stereo f.m. outlet, WRFM. The equipment displayed is essentially a completely automatic radio station which could run for as long as 15 hours unattended!

ELECTRONICS AID THE POLICE

The new headquarters for the Dunbartonshire Constabulary is equipped with the latest electronic devices to aid the police in their fight against crime.

The bulk of this equipment is in the Information Room where there are separate compartments for the telephone switchboard and teleprinters and a glass-fronted booth containing a single console occupied by a radio operator where he has access to the radio circuits, the headquarters telephone system, the 999 emergency telephone system and the message recording system.

There is a three position radiotelephone control system using three Pye 5 station control units. Each unit is equipped to control five stations but, at the moment, only terminates two stations—one being the county v.h.f. system for communication with mobiles and the other regional inter-force link. Therefore, further expansion can be obtained by the addition of up to three more stations.

OVER THE CANAL

Emergency plans by B.S.R. Ltd. to beat the Suez canal closure have halved the time taken to make deliveries to Japan. Record changers are air freighted from London airport to San Francisco and from there proceed by ship to Tokyo. Time taken is $2\frac{1}{2}$ weeks compared with 5 weeks for shipping via Suez.

PROBING FOR AURORAL SECRETS

New light on the origins of the spectacular Aurora Borealis (the Northern Lights) has come from an experiment mounted by the British Radio and Space Research Station on a rocket flight from Andoya in Norway.

Mullard channel electron multipliers, in an experiment, detected the particles causing the brilliant light patterns seen from Earth. The channel electron multipliers in the Nike-Apache rocket fired into the Aurora revealed that the flow of electrons in the Aurora pulsated. The fact that the waves of fast electrons arrived just half a second before the waves of slower electrons meant that the source producing the waves could be pinpointed to a position 35,000 miles above the equator. This is the first time that a source of particles causing the light fluctuations in an Aurora has been located; and it is the advent of the channel electron multiplier, which enables very low energy electrons at a rate of below one every second to be detected.

The channel electron multiplier is essentially a tube of special glass formed into a spiral. When an electrical potential is applied between the ends of the tube in a vacuum, electrons entering the low-voltage end initiate a cascade of secondary electrons which emerge from the high-voltage end. Because the multiplier operates in the environmental vacuum of space, the electrons enter the device without having to penetrate any "window". Thus the device will detect particles with energies down to only a few electron volts.


C.R. TEST BRIDGE



From Nombrex Ltd., Exmouth, Devon, comes Model 32.

This transistorised Capacitance-Resistance Bridge Model 32 is a re-designed version of their previous C-R bridge. Using the same unique basic circuitry, this model incorporates additional features and new bridge characteristics resulting in improved performance, increased accuracy of measurement and scale discrimination.

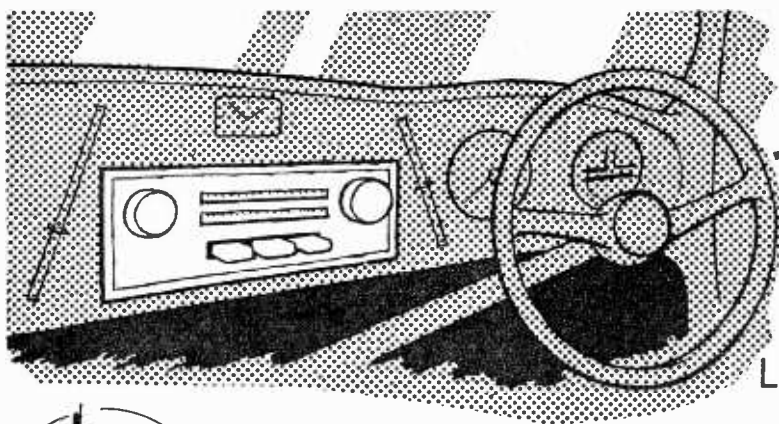The measurement facilities cover a wide range of Resistance and Capacitance, together with provision for indication of leakage and Power Factor in the larger values of capacitors. The design includes new modern styling of case and controls, easy rear access to battery and provision for alternative operation from external battery or mains supply unit. Price is £10 10s.



TRANSISTOR CAR RADIO

L. McNamara B.Sc.

COVER
SUBJECT

READERS will realise that few, if any, kit manufacturers provide for the needs of those who must operate their car radios on a 6-volt system, such as is found in the Volkswagen and a few other Continental cars. Since a completely new design had to be evolved, it was decided to incorporate transfilters.

Two types of transfilter are used. One is a two-terminal device which works as a capacitor at the resonant frequency, but at other frequencies there is no interaction between the crystal and the applied field, so that it is equivalent to an open circuit. The resulting negative feedback attenuates any amplification at off-resonant frequencies.

The other type of transfilter is a three-terminal unit which performs the matching function of a transformer. This follows from the fact that the amplitude of the mechanical oscillation depends on the voltage applied across the crystal, while the power absorbed, which is a measure of the current, depends on the area of the electrodes. Therefore, the dot or input terminal of the transfilter, presents a high impedance to the preceding stage, since there is a large displacement in the crystal at that point, while the contact area is small. The output or ring terminal on the other hand, provides the low impedance drive to the base of the following transistor, corresponding as it does to a small amplitude of oscillation over a large area. The disadvantage of the slightly higher price of the transfilters is more than balanced by the reliability and convenience in operation, which is assured on the long term by the manufacturer's tests, which indicate that the resonance point of a unit will vary by less than 0.2% in ten years, and by less than 0.1% between -20 deg. C and +60 deg. C.

STABILITY

This question of stability with temperature is especially important in a car radio, since it will be required to operate under conditions ranging from below freezing after a night in the open in mid-winter to perhaps 40 deg. C. if the car has been standing in direct sunshine for a few hours in mid-summer. It was therefore decided to use silicon transistors except for Tr6, since they have a much greater tolerance of high temperatures than the more conventional germanium types. These were

the obvious choice for the mixer and i.f. amplifier stages. They are n-p-n devices and the polarity will be the opposite of that to which many constructors are accustomed.

The fact that n-p-n i.f. transistors are to be used leads to a rearrangement of the decoupling components between the audio and i.f. stages. The negative line must be regarded as "quiet" and the positive line decoupled with respect to this. The decision to employ transfilters results in the relevant transistors needing collector load resistors, since there is no ohmic conduction through the crystals of the transfilters as there is in the windings of a tuned transformer. The resistors cope with the d.c. element in the collector current, while the transfilter deals only with the superimposed i.f. signal.

A.V.C.

The same considerations apply to the design of the a.v.c. system. The i.f. and audio components developed across the diode must be removed in order to provide a constant control potential on the a.v.c. line. The i.f. component is suppressed by the 0.01μF capacitor across the volume control, but whereas the electrolytic to suppress the audio can be taken to the chassis at the end of the a.v.c. line when a transformer is used, such procedure would short the i.f. signal in a transfilter set; the a.v.c. line must therefore be smoothed first, and the i.f. signal voltage developed across a resistive load forming part of the base potential divider for Tr2. This is the purpose of the two 3.3kΩ resistors, R7 and R10. It will be further noted that the diode is reversed when compared to the orthodox p-n-p arrangement. This again results from the fact that the n-p-n circuit must be a complete reversal, so that the a.v.c. line must be negative-going with increasing signal in order to bias back the first i.f. amplifier transistor and reduce its gain.

The a.f. section, too, is unconventional, and consists of a 3-transistor complementary amplifier, with two p-n-p transistors and one n-p-n, all direct coupled and transformerless. The normal transistor portable utilises a pair of transistors in class B push-pull, but the adoption of this arrangement in a set designed for 6-volt operation would either limit power, since each transistor would have a collector-to-emitter potential of only 3 volts, or involve two transformers if each was to get 6 volts. On the other hand the drain of even a 2 or 3 watt output stage using a single power transistor in class A is very small for a car battery, even if it is not feasible


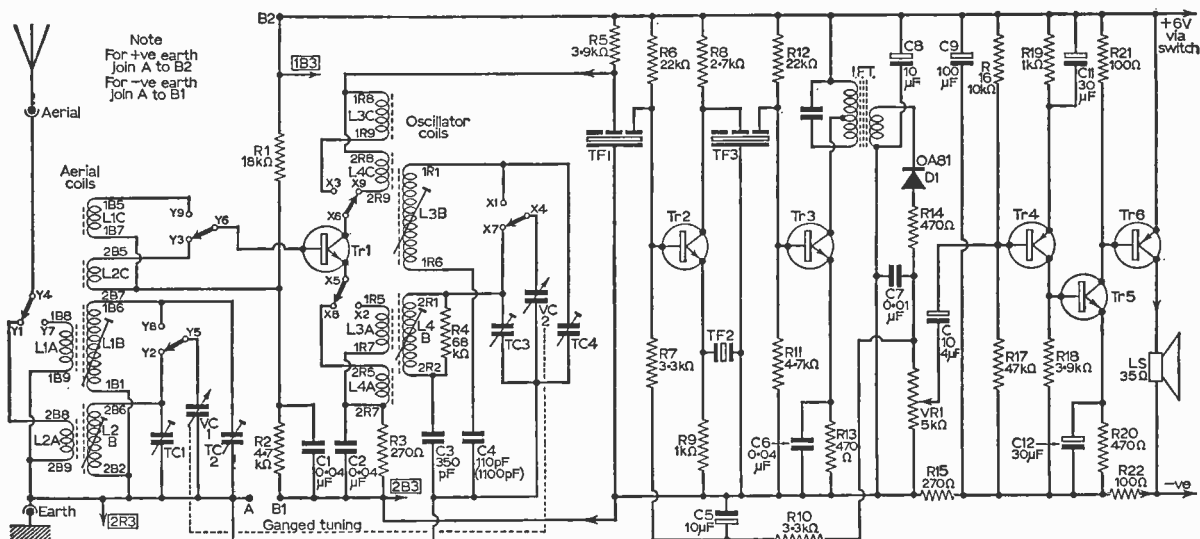


Fig. 1: ▲ Theoretical circuit diagram of the car radio. The numbering around the coils is to assist wiring. (See Table 1.)

Fig. 2: ► Printed circuit board and layout of components as used in the prototype. Alternatively "Circuit-kit" adhesive copper foil strip could be used modifying the layout accordingly.

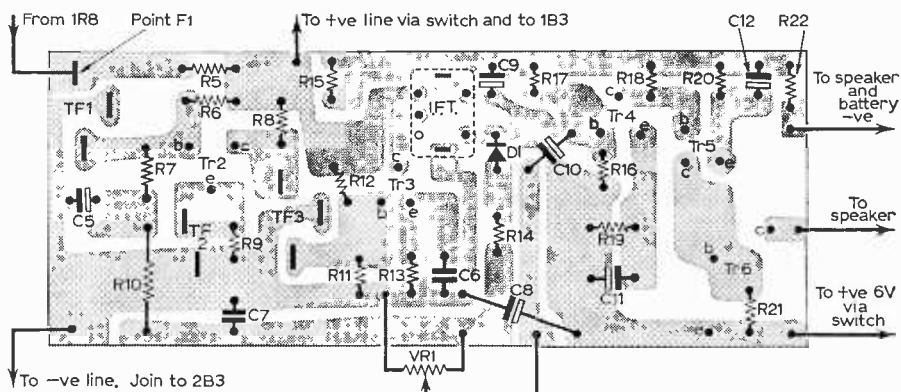

for economy reasons in a portable. Further, the output impedance of a power transistor so driven will not be a serious mismatch to an ordinary loud-speaker, and in fact PRACTICAL WIRELESS published an amplifier along these lines as long ago as November 1959. Now, as then, it is more economical and convenient to use a p-n-p power transistor, but the current model differs from that of eight years ago in that direct coupling from an n-p-n driver is now possible.

By a similar complementary reversal this n-p-n driver follows a p-n-p preamplifier transistor. The audio n-p-n is again a silicon type, but germanium had to be employed for the p-n-p types. However, the output transistor is kept at a reasonable temperature since it uses the case of the radio as a heat sink, and both it and the preamplifier transistor are operated well within their allowed dissipations. There is therefore no danger of their destruction from thermal runaway. A second decoupling network is incorporated between the driver and output stages. The result is a powerful and sensitive audio amplifier using the absolute minimum of components consistent with quality.

Denco transistor coils are used in the aerial circuit because the ferrite type of aerial usually found in transistor sets would not be able to pick up any signal since the whole set is closely screened in its metal case. Neither would it be more effective in matching the signal received at the car aerial into


the mixer transistor. In fact, a ferrite aerial would merely increase the noise level due to engine interference etc., without the smallest compensating advantage. This aerial coil demands a 300pF tuning capacitor, so that oscillator coils from the same range to match this gang must be used. In practice a definite advantage accrued from the use of these coils, since, due to the close tolerance to which they were manufactured, alignment was easy, and simplified further by the fact that the i.f. circuits were already almost perfectly aligned. There is also the advantage that any constructor who is not interested in the Droitwich transmissions on the long wave, but would prefer the 160 metre amateur band and marine reception, can obtain this simply by using range 3 coils (180—57 metres) instead of range 1 (2000—750 metres) and changing the value of C4 from 110pF to 1,100pF. This would be especially useful in a boat.

EARTHING

Design procedure for the circuit allowed for either positive or negative earths. The prototype was so assembled that the positive and negative lines in the set were insulated from the chassis, so that when the set is installed, either can be earthed, and the other taken through a fuse to the battery. The case of the output transistor must, of course, be insulated anyway, as it is carrying the output to the loudspeaker.



The tuning capacitor must be bolted to the chassis

of the set, so the tuned and coupling windings on all the aerial and oscillator coils must be returned to the chassis earth, and *not* to the receiver positive or negative. It is most important that these be distinguished from the windings working into the emitter, base and collector of Tr1 which are referred to the potentials of the receiver circuitry. This procedure does not interfere with the operation of the circuits of the receiver, since there can be no potential difference at signal frequency between the

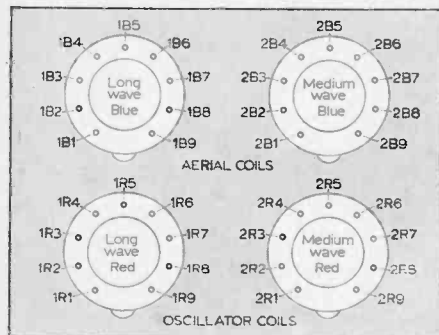

▲ Fig. 3: Details of the numbering on the coils together with pin identification on the push-button switch bank. (See Table 1.)

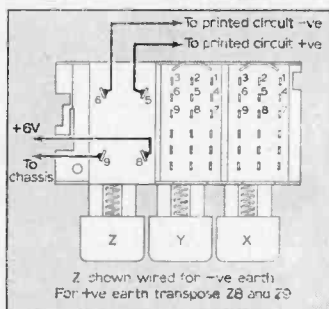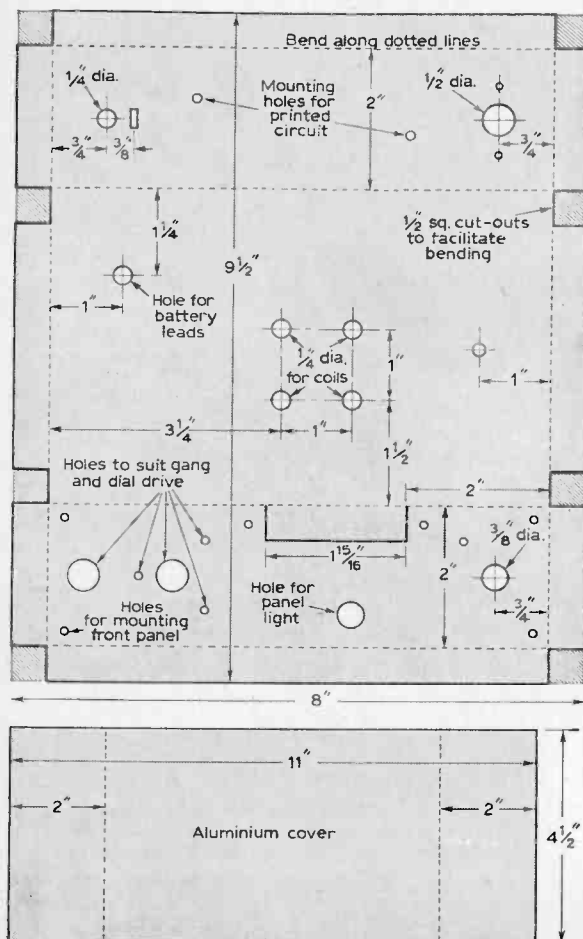▼ Fig. 4: Layout and drilling dimensions of the chassis-cum-case.



chassis and the positive or negative lines. In any case, the practical details involved in this arrangement, as also in regard to the output transistor, are fully covered in the construction information.

Building the car radio begins with the preparation of the etched circuit for the i.f. and audio amplifier panel. The experienced constructor will find little difficulty in marking the copper laminate for component locations in accordance with the diagram, painting the conductor pattern, and removing the unwanted copper with ferric chloride solution. The alternative of the "Cir-kit" adhesive system of assembling a copper foil circuit board, although not employed by the writer, would probably be equally satisfactory, and avoid the use of chemicals.

Only the locations of the pins of the i.f. transformer and of the transistors are critical; some leeway is allowable with the resistors and transistors. Drilling component mounting holes and connecting the parts into

the circuit follow standard procedure. Flying leads about 6 inches long are inserted for the connections to be made later to the volume control, on/off switch, power transistor and tuning circuits.

METAL WORK

The metal work is fully illustrated in Fig. 4. The chassis is of 16 gauge aluminium and two pieces are required, 9 1/2 x 8 in. for the chassis itself, and 11 x 4 1/2 in. for a cover. The chassis is cut to size and drilled with the holes marked while still flat; this task is more difficult if an attempt is made to bend it to shape first. The shaded areas represent waste material and should be removed with a fine hacksaw or fretsaw with metal-cutting blade. On the front panel there are holes to suit the tuning capacitor, the volume control and tuning control spindles; also cut-outs for the switch-block and in the corners to permit folding of the flanges; finally, mounting holes for the gang and the plastic dial will also be required. The bottom of the chassis carries the tuning coils, the board with the trimmers, and a grommet for the leads to the battery and the loudspeaker. Again, there are cut-outs to provide for the later folding. The rear panel must be prepared to receive the amplifier circuit board, power transistor, and the aerial socket. When prepared, the sheet is bent carefully to channel section, with a flange along each edge to receive the self-tapping screws which will secure the cover.

MOUNTING COMPONENTS

It is now possible to mount the components on the chassis. It will probably be simpler to insert the i.f. and audio board first with stand-off spacers to prevent the soldered side from making contact with the chassis. The output power transistor is mounted beside it, also insulated by the manufacturer's kit of a mica disc which fits over the pins and a shaped washer to go over the collector bolt after this has passed through the mounting hole, to prevent any metal-to-metal contact between the chassis and the bolt or its nut. On the other side of the circuit board the aerial socket is fitted. The tuning capacitor,

Tuning drum turned fully clockwise

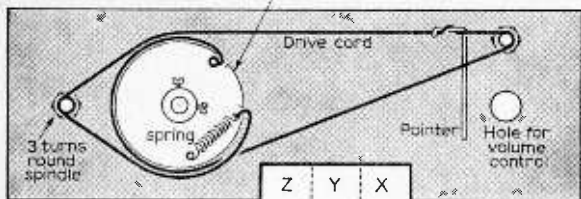


Fig. 5: Details of the positioning of the dial drive for the tuning capacitor.

coils and switch blocks are next added remembering the maker's warning that the coil fixing nuts should be no more than finger-tight.

The trimmers are mounted on a small piece of plain paxolin, wired underneath, and fixed to the chassis by a long bolt passing through stand-off spacers. Leads about 4 inches long are left from each trimmer, with one of similar length to carry the earth connection to all four. The volume control fits on the front panel, with a bolt carrying a pulley beside it. The tuning spindle mounts beside the gang, but the fitting of the drive cord in accordance with Fig. 1 is better left until later. Provision for a dial bulb is made on the front panel.

F.C. WIRING

It is now possible to begin wiring the frequency changer stage. The coils used have formers fitted with nine pins and intended for plug-in-use. As only six pins are needed for the windings of each coil, there are three blank pins available for use as terminals for mounting other components. It is therefore unnecessary to prepare an r.f. circuit board. The point of separate earths for the tuned and coupling windings applies to the wiring of this stage, and this complicates the task. Therefore the instructions for this wiring operation are given in the form of a programme routine, Table 1. For easier trouble-shooting, should it be required later, the switch is arranged so that all oscillator wiring is to one wafer, and all aerial connections to the other. It is advised that the programme should be followed carefully, as this is the heart of the set; each point should be cancelled by a pencil mark on the programme as it is completed to avoid any possible confusion. The positive, negative and signal leads to the i.f. and audio strip are included in the programme, as are the trimmer connections. Wiring should be as short as possible to avoid stray capacitance.

If there is a positive earth in the car, the switch is in the negative line, and vice versa. The positive and negative lines from the printed circuit are both brought to the on/off wafer of the switch, and one

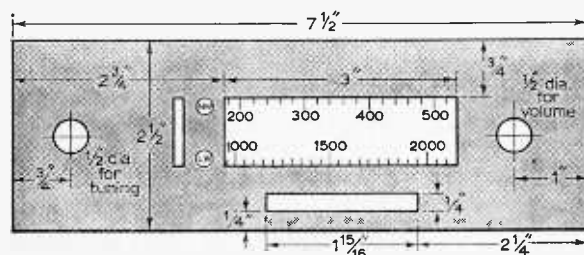


Fig. 6: Layout and drilling details for the front panel.

★ components list

Resistors:

R1	18kΩ	R12	22kΩ
R2	4.7kΩ	R13	470Ω
R3	270Ω	R14	470Ω
R4	68kΩ	R15	270Ω
R5	3.9kΩ	R16	10kΩ
R6	22kΩ	R17	47kΩ
R7	3.3kΩ	R18	3.9kΩ
R8	2.7kΩ	R19	1kΩ
R9	1kΩ	R20	470Ω
R10	3.3kΩ	R21	100Ω
R11	4.7kΩ	R22	100Ω
VR1	5kΩ		

Capacitors:

C1	0.04μF	C7	0.01μF
C2	0.04μF	C8	10μF
C3	350pF ± 2%	C9	100μF
C4	110pF ± 2% see text	C10	4μF
C5	10μF	C11	30μF
C6	0.04μF	C12	30μF
TC1	3-30pF Trimmers		
TC2	3-30pF (miniature)		
TC3	3-30pF compression		
TC4	3-30pF type)		
VC1	2 gang 300pF		
VC2			

Electrolytics not less than 6V working.

Semiconductors:

Tr1	2N708, 2N2368, BSY25 etc.
Tr2	2N708, 2N2368, BSY25 etc.
Tr3	2N708, 2N2368, BSY25 etc.
Tr4	2S303
Tr5	2S017
Tr6	V60/30P, OC16 etc.
D1	OA81

Transfilters:

TF1	TO-O2D	(Brush Clevite)
TF2	TF-O1D	
TF3	TO-O2D	

Coils:

L1A	Blue range one	These coils are Denco miniature transistor dual purpose coils	
L1B			
L1C			
L2A	Blue range two		
L2B			
L2C			
L3A	Red range one		
L3B			
L3C			
L4A	Red range two		
L4B			
L4C			

Miscellaneous:

Aerial socket; dial bulb and M.E.S. socket—6.3V; dial drum 1½ in.; pulley for dial drive; knobs; aluminium sheet; perspex for dial; printed circuit board; paxolin panel for trimmers; nuts; bolts; self-tapping screws; push-button switch unit (Henry's Radio type 41); 35Ω loudspeaker.

of them earthed by a short wire, while the other, as indicated, goes through the switch and the usual type of in-line auto fuseholder to the car battery.

Construction is now complete, and alignment may begin. However, it is a wise precaution to meter the current drawn by the set when first switched on; this gives an immediate check on any really obvious mistakes in the power supply wiring. A current of about 40mA is quite normal. The medium wave should be aligned first. With the aerial plugged in,

Table 1.

Coding. 1=long wave; 2=medium wave; R=red (oscillator); B=blue (aerial). The pin number is designated counting clockwise from the pip looking directly at the base of the former. For example 1B3=long wave aerial coil, pin 3 and 2R6 would be medium wave oscillator coil pin 6.

1. 1B1, 1B9, 2B1, 2B9 2R3 to chassis.
2. 1B3 to +ve line on P.C. board, and via R1 to 1B7.
3. 1B5 to Y9 on switch.
4. 1B6 to Y8.
5. 1B7 to 2B7, also via R2/C1 to 2B3
6. 1B8 to Y7.
7. 2B3 to -ve line on P.C. board.
8. 2B5 to Y3.
9. 2B6 to Y2.
10. 2B8 to Y1.
11. 1R1 to X1.
12. 1R5 to X2.
13. 1R6 via 110pF to 2R3.
14. 1R7 to 2R7.
15. 1R8 to 2R8, and to F1 on P.C. board.
16. 1R9 to X3.
17. 2R1 to X7, and via R4 to 2R2.
18. 2R2 via 3C to 2R3.
19. 2R5 to X8.
20. 2R7 via R3/C2 to 2B3.
21. 2R9 to X9.
22. X4 to VC2.
23. X5 to emitter Tr1.
24. X6 to collector Tr1.
25. Y4 to aerial socket.
26. Y5 to VC1.
27. Y6 to base Tr1.
28. Trimmer between X1, X7, Y2, Y8 and chassis.

If the trawler band is required instead of long wave, read 1R3 for 1R6, and use 1100pF instead of 110pF for C4.

the local station should be audible, since it is a very sensitive circuit and the i.f. stage is already practically aligned, thanks to the transfilters. A few turns of the core of the i.f.t. will complete this section.

In the mixer stage, the core of the m.w. oscillator coil will first be set to tune a station at the low frequency (or longer wavelength) end of the band at the appropriate section of the travel of the tuning capacitor. This is then peaked with the aerial coil core. The oscillator and aerial trimmers are then used in that order to tune a station at the high frequency (Luxembourg) end of the medium waveband. If necessary, the low frequency adjustment on the cores may be repeated, until there is no further improvement, and then the long (or trawler) band is treated in the same fashion.

It only remains to provide a smooth professional finish to the project. The cover is fixed to the flange of the chassis by a series of self-tapping screws, and a coat of paint applied to the metal. The cord drive is installed, and a dial prepared. In the prototype a sheet of perspex was used. It was shaped to permit the controls to protrude, and holes were drilled for fixing to the front of the chassis. The writer used four tapped spacing pieces; these were screwed to the chassis so as to accept screws through the holes in the dial. The dial itself was made slightly larger than the fascia aperture into which the set had to fit; the edges were bevelled with a file, and the resulting appearance was quite pleasing. The painting of the dial is best done from the reverse side, so that the outside retains its smooth finish.

Lettering on the prototype was typed and set on the reverse side before the painting; a masking tape was placed in the position of the aperture for viewing the sliding index of the tuning scale, and the paint applied. When two coats are dry, the masking tape is removed by cutting the paint layer with a razor blade and carefully peeling it off, while the typed lettering is securely fixed below the paint layer.

The set was installed in the car from the rear of the fascia, and secured to the bodywork with a strong metal strap and self-tapping screws. The dial is then attached from the front with the screws in the tapped spacers already referred to. Two knobs complete a project that the successful constructor can be proud of, as a really up-to-date and reliable addition for his motoring pleasure. The details of the car aerial fitting and any interference suppression that may be needed will not be dealt with; these are standard procedures more appropriate to strictly motoring magazines.

WHAT'S THAT?

TWO FUZZ BOXES!

You remember those gorgeous gold units at the R.S.G.B. Exhibition

AND a 2-Tone YODELLER

AND a WATER LEVEL ALARM


PLUS a surprise feature we know you will like in **PRACTICAL ELECTRONICS** November issue, out October 13.

Practical Wireless Binders

A first class magazine deserves first class treatment. Store your copies of *Practical Wireless* with a new Easi-binder, specially designed to hold 12 copies of the new large size. It has a special pocket for storing those blueprints and data sheets too. Yours for 14s. 6d. from: Binding Dept., George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Note. Please state the volume number required otherwise a blank cover will be sent.

★ THIS MONTH'S FREE GIFT

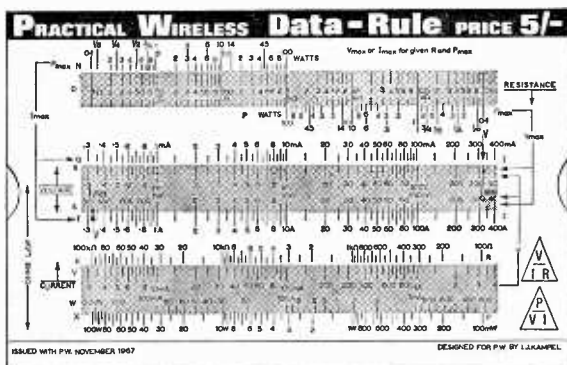

described by I. J. KAMPEL

SPECIFICATIONS

Reciprocals

Component tolerance limits.

Maximum current or voltage for given power dissipation in given resistance, giving absolute values (fixed decimal point).

Ohm's Law scales giving voltage-current-resistance and power-voltage-current relationships in absolute values over the most useful ranges. PLUS normal division and multiplication facilities of a mathematical slide-rule where, as is usual, the decimal point is fixed by inspection.

Decibel power, voltage or current ratios with matching or different impedances.

Preferred resistor values table.

Preferred parallel resistor (or series capacitor) chart.

Resistor colour code table.

Log x

Capacitance/inductance combinations for resonance for 30kc/s—300Mc/s. i.e. covering: LF; MF; HF; VHF; UHF, and giving absolute capacitance inductance values.

Direct conversion with fixed decimal point between the following units:

Newtons—Kgm.f.	B.T.U's—kW.hrs
Decibels—Nepers	x—x
kW—H.P.	kW.hrs—Joules
Degrees—Radians	Ft/lbs—kW.hrs
ft/lb f/s—H.P.	Ft/lbs—H.P. hrs
lbs—Dynes	Foules—Ft.lb.f
inches—Metres	Gilberts—Amp-turns
Coulombs—Amp/hrs	Lux—Ft. candles

THE following explanation should be sufficient for a person already familiar with the slide rule and the ABAC to use the Data-Rule immediately. A short series of articles will follow explaining in greater detail how to use the calculator to its fullest extent.

UNITS CONVERSION

To avoid confusion, the units on the rule are either electrical or electronic or, like the lux-foot-candle conversion, closely related. The latter conversion would be useful when considering photo-devices for example. To convert between units shown on the slider, adjust the slider to expose the desired units in windows I and J. Note that these windows are duplicated on either side of the rule, and which of these windows will be used will be dependent on the individual conversion. Quite simply, use the most convenient window initially, and if it is found that the required section of the scale is not exposed in the window, then re-adjust the units in the opposite window. Window I relates to the upper of the two lower scales, namely scale L, whilst window J refers to scale M. For accurate conversion, ensure that the arrow in the window J is accurately aligned with the arrow on the envelope of the rule.

Taking scale L as the magnitude indicated (1–10), to convert from the units in window I (scale L) to the units in window J (scale M), multiply the indicated magnitude on scale M (1–10) by the multiplication factor that will appear in either the bottom left, or bottom right corner of the rule. This conversion factor will set the correct magnitude of the answer. Only one of the conversion factor windows will show a factor at any given setting, and this will always be the window on the same side of the rule as the initial units setting in windows I and J. If it is necessary to multiply the indicated magnitude in scale L by some factor, the conversion answer should be also multiplied by this same factor.

Note that when the factor appears as say: $\times 10^7$, this corresponds to $\times 10^{-7}$, the bar being employed to indicate a negative index for reasons of space. Naturally, a factor of $\times 10^8$ would represent $\times 1,000$, and $\times 10^1$ would represent $\times 0.1$. Note also that $\times 10^0$ indicates $\times 1$.

E.g. Convert 72×10^6 joules into kW.hrs.

Firstly convert to standard form. Thus 72×10^6 joules becomes 7.2×10^7 joules. Now set the slider so that JOULES appears in window I and kW.hr. in window J, using the left-hand window. Read off the answer 2, on scale M, opposite 7.2 on scale L. Thus the complete answer is 2 multiplied by the original factor, multiplied by the indicated conversion factor, namely $\times 10^6$, and is given by: $2 \times 10^7 \times 10^6 = 20$ kW.hr.

Note that had we set the units in the right-hand I-J window, then the required figure on scale L, that is 7.2, is out of the window, thus indicating that the slider should be re-set with the units conversion in the opposite I-J window. To apply the reverse conversion, that is converting the units in window J to those in window I, then the procedure is simply reversed.

E.g. Convert 60° into radians.

Since conversion into the units in scale M requires the M quantity to be multiplied by the conversion factor, the reverse conversion requires the M quantity to be divided by the conversion factor, the resultant answer is L being again multiplied by the factor of the original M

quantity. Thus, converting 60° to the standard form, this is 6.0×10^1 . With RADIANS-DEGREES conversion in the right-hand window, read off 1.05 in scale L opposite 6.0 in scale M. Thus the final result is:

$$\frac{1.05}{\text{conv. factor}} \times \text{original multiple} = \frac{1.05 \times 10}{10} = 1.05 \text{ radians.}$$

To decide whether the conversion factor is divided or multiplied, an easy method is provided on either side of the rule just above the conversion factor boxes. The boxed "SIGN" indicates that in "downwards" units conversion, i.e. converting units in window I to those in window J, then the sign is unchanged, i.e. multiply the converted figure by the indicated factor. If the conversion is "upwards" however, the sign must be changed i.e. multiply the converted figure by the indicated factor, but changing the index sign.

In the previous two examples, JOULES to kW.hr. is a "downward" conversion, the index is unchanged, and so the indicated multiplication conversion factor is unchanged, i.e. 10^{-6} . In the second example, degrees to radians is an "upward" conversion, and the conversion factor's index sign is changed, and we proceed as follows: Converting 6.0×10^1 degrees to radians, read off 1.05 as before, multiply by the original factor, 10^1 , then multiply by the conversion factor, *index sign changed*, giving 10^{-1} , and the result: $1.05 \times 10^1 \times 10^{-1} = 1.05$ radians.

DECIBEL EQUIVALENTS

(Assuming input and output impedances equal)

To find the decibel equivalent of a power ratio, where:

$$N \text{ dB} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}}$$

locate the power ratio in scale L, placing the ratio opposite 1 on scale M. If the ratio is between 1 and 10, the decibel equivalent is given directly above in window H, using the upper half since this is a *power* ratio. If the ratio is greater than 10, then add 10dB for every factor of 10, as indicated on the immediate right of the window.
E.g. To find the decibel equivalent of power ratio 30

Place 3 on scale L opposite 1 on scale M. Since the absolute value is really 3×10^1 there is a single factor of 10 involved in the answer, and thus 10dB must be added to the indicated answer. In window H, on the upper scale we read off 4.8 (actually 4.77), and adding 10dB, we have: $4.8 + 10 = 14.8$ dB (actual answer 14.77dB). Since this is an analogue device, the difference between actual value and read value depends on reading accuracy. Working in the reverse direction, say we wish to complete the following example:

E.g. Convert 35dB into a power ratio.

Firstly we must determine the whole number of tens in this value. Thus, taking the nearest multiple of 10 below the value, we obtain 30, indicating that 10dB has been added three times to represent a $\times 10^3$ power ratio factor. Now bearing this in mind, take the remaining dB figure, i.e. $35 - 30 = 5$ dB, and place this in the upper section of window H. The value 3.16 is then read in scale L opposite 1 on scale M. Thus the final power ratio will be 3.16×10^3 .

To find either the current or voltage ratio decibel equivalent, where: $N \text{ dB} = 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}}$

proceed exactly as before, only now, as indicated by window H, the lower scale is used in the window for current and voltage ratio conversions.

E.g. Find the decibel equivalent of voltage (or current) ratio 7.08.

The only difference that could occur in this conversion

is that where the ratio is over 10, 20dB are added per factor of 10, instead of the previous 10dB, as indicated to the right of window H. In this example the ratio is between 1 and 10 and this does not, therefore, arise. Place 7.08 opposite the appropriate point in scale M, and read off the final answer 17dB opposite the lower arrow in window H.

E.g. Convert 25dB to a current ratio.

Determine the number of multiples of 20dB in the quantity, i.e. only a single 20dB, leaving 5dB. The 20dB indicates a ratio factor of $\times 10$, and by placing 5dB in window H opposite the lower arrow, we may read of the ratio 1.78 in scale L, giving the final result 1.78×10 or simply 17.8.

(When input and output impedances differ)

In this case proceed as before when converting from ratio to decibel equivalent, and then continue as indicated: Having obtained the basic dB figure, correction is made for the differing impedance by adding to this the figure obtained from: $\times \text{dB} = 10 \log_{10} \frac{\text{input impedance}}{\text{output impedance}}$

Having determined the indicated impedance ratio, this figure of $\times \text{dB}$ is determined by setting the ratio in L and reading off 'x' in the upper portion of window H. Simply then add to two dB figures obtained.

LOG x

Convert the value to standard form. Place the number in scale L opposite 10 in scale M, and read the decimal portion of the logarithm opposite the arrow in window K. Place in front of this the index of the multiple to obtain the full logarithm, using a bar sign for a negative index.

E.g. Find $\log_{10} 27$.

Firstly convert to form: 2.7×10^1 giving the whole number portion of the logarithm as the index 1. Place 2.7 in L opposite 10 in M. In window K read of the decimal portion of the log, namely .43, thus giving the complete log as 1.43 (actual value 1.4314).

E.g. Find antilog 2.2041 (or the number whose log is 2.2041).

The whole number portion of the log gives us the multiple 10^{-2} . Set 2.041 (significant figures 204 in practice) in window K, and read 1.6 in scale L opposite 10 in M. Thus the number is 1.6×10^{-2} , or 0.016.

RESONANCE

Resonance for an inductance and capacitance in a parallel circuit may be computed from the ABAC provided. The full formula for the parallel circuit is:

$$f_{\text{res}} = \frac{\sqrt{L/C - R^2}}{2\pi L}$$

In radio circuits, however, in most cases R can be assumed negligible compared with $2\pi fL$, and therefore

$$C \approx \frac{1}{(2\pi f)^2 L}$$

and the frequency expression may be simplified to

$$f_{\text{res}} = \frac{1}{2\pi\sqrt{LC}}$$

The ABAC scales are based upon this latter expression. Given values for two of the scales, the straight line through these two points will intersect the third scale at the other value for resonance. Adjusting the slider for the appropriate frequency range in window A will automatically set absolute values to the ABAC scales by means of windows B to G.

E.g. A capacitor is measured at 3.76pF. What inductance is required for the circuit to resonate at 150 Mc/s?

Adjust the slider for the appropriate frequency range,

V.H.F., in window A. Place a straight edge across the scales to intersect 150Mc/s on the f scale, and 3.76pF on the C scale. This is seen to intersect the L scale at 0.3μH, the correct value of inductance.

RECIPROCAL

The decimal point should be placed by inspection in this conversion, however this is a relatively simple matter. To find the reciprocal of a number, set the significant figures of the number opposite either the 1 or the 10 of scale M, in scale L. The reciprocal significant figures may then be read off at the point on scale Y directly above.

E.g. Find the reciprocal of 6.

Place the 6 in scale L opposite the 1 of scale M, and read off 1.67 in scale Z opposite the end scale mark of Y. Since the reciprocal is 1/6, this must be less than 1, and 1/6 may be approximated to 0.1 mentally. Thus the true result is 0.167.

COMPONENT TOLERANCE

Suppose we have a nominal value of 500 for a component value. This could be ohms, microfarads, or any system of units. If we wished to know the allowable deviation in say a ±5% tolerance, then proceed as follows. Adjust the slider to place the 5 in scale Z opposite the central arrow section of the component tolerance scale, combined in scale Y. We may now read off that an increase of 5% would take us up to the value 550, whilst a decrease of 5% would take us down to 450. The values assume the same magnitude as the original number, or to be more explicit, in absolute values, the original value set on scale Z was 5×10^2 , therefore the other tolerance values are as read off, times the same multiple, i.e. 5.5×10^2 and 4.5×10^2 .

For example, if we calculate a resistance value of 80Ω is required, and estimate a ±5% tolerance is acceptable, by setting 8 in scale Z opposite the tolerance arrow, and referring to the preferred resistor values in the table at the upper right-hand corner of the calculator, we see that the value of 82Ω is within the ±5% tolerance, whilst the nearest value below, 68Ω, is seen to be well outside the required tolerance. The indicated tolerances are the usual resistor tolerances, neglecting 1% which may be estimated.

$V_{\max}$ OR $I_{\max}$ FOR GIVEN R AND $P_{\max}$

Turn to the reverse side of the rule for these scales, the three-windowed side of the envelope.

On this side of the rule, as indicated by the coloured symbol to the left of the central scale, the central window, a voltage scale, is used in conjunction with both the upper and the lower windows. The upper window is used in conjunction with the middle scale, as is the lower window, but they are not used in conjunction with each other. For the values of $V_{\max}$ and $I_{\max}$ in a given resistance, at a specified power, the upper two windows are employed.

If we set a resistance and a power, and require to know the maximum current which can then be drawn by the resistance to keep within that power rating, set the resistance value of scale O opposite the appropriate power dissipation in scale N. The value of $I_{\max}$ is then read off on either scale Q or scale T, opposite the $I_{\max}$ mark to be seen in the central window. There are two $I_{\max}$ marks, but only one will indicate a value, the other being off the slide (the exception being when the slide is practically centrally situated, in which case both marks

will indicate the answer). The actual arithmetic process involved is

$$I_{\max} = \sqrt{\frac{P_{\max}}{R}}$$

but the calculator performs this calculation automatically. E.g. Say we wish to know the maximum current that may be drawn through a 3W rating resistor of value 40Ω. Place 40Ω on scale O opposite 3W in scale N. Read off the value for $I_{\max}$ on scale Q, opposite the $I_{\max}$ arrow in the central window as 274mA.

Had we instead, with the same resistor, wished to know the maximum voltage which may be applied, then we would proceed as follows. Place the 40Ω on scale O opposite 3W on scale P, giving the answer of 11V on scale R opposite the arrow marked in colour V on scale Q. The answer of $V_{\max}$ could have appeared alternatively opposite V on scale T had the slider passed out of the left-hand side of the sleeve.

In this latter operation, the calculator automatically evaluates the arithmetic process of $V_{\max} = \sqrt{P_{\max} \cdot R}$. The choice of either scale N or scale P for the power is simply made since the $I_{\max}$ at the left of the calculator indicates, with a coloured line, the upper scale, N, and the $V_{\max}$ at the right of the calculator indicates the lower scale, P with a coloured line. The real purpose of these scales is for resistor ratings, and potentiometer ratings, in circuit design.

OHM'S LAW CALCULATIONS

The above processes could be done in two stages by the Ohm's Law scales, the lower two scales, however these are best employed for direct $V = IR$ and $P = VI$ relationships. Since these scales must be limited somewhere, the most useful ranges have been covered. Should any particular calculation require values out of the bounds of these lower scales, then the calculation may be done conventionally with the normal slide rule scales L and M.

VIR Relationships.

The upper right-hand triangular symbol indicates that the middle window is here used in conjunction with the upper lower window scales, U and V. For any voltage V, set opposite one of the V arrows on the central window, the current resistance values are found adjacent in scales U and V.

E.g. What current will flow in 2kΩ with a voltage of 20V?

Set 20V in scale R opposite the coloured V mark in scale Q, and read off the answer, 10mA, in scale V, opposite 2kΩ in scale U.

E.g. What voltage will 3mA develop across 40kΩ?

Set 3mA in scale V opposite 40kΩ in scale U and read the voltage, 120V, opposite the V arrow in scale R.

PVI Relationships.

The lower right-hand triangular symbol indicates that the middle scale is used in conjunction with the lower scales of the lower window, W and X. Proceed as before.

E.g. What power will be dissipated if the voltage across a load is 5V, and the current is 80mA?

Set 5V in scale R opposite the coloured V mark in scale Q, and read off the answer 400mW in scale X opposite 80mA in scale W.

USE AS SLIDE RULE

There is the limitation with this calculator that no cursor is possible, and therefore use as a slide rule is limited, but nevertheless useful when the rule is at hand and a slide rule is not.

Multiplication

Place either the 1 or the 10 of scale L opposite one of

"Why
Can't
They?"

practically wireless

commentary by HENRY

ONE of our contemporaries has lately been beating its illustrious head against the high blank wall of the "ideal" in searching for their readers' notion of a perfect tape recorder.

One reader wants at least three heads on every machine; another asks for variable bias; another wants provision for multi-track sound-on-sound.

Fair enough, but why, if they wanted these desirable features, did they not pay a little extra and procure them in the first place?

Henry was hauled over the coals a while ago for saying: "*You gets what you pays for, mate!*" In so far as electronic equipment is concerned, the axiom holds good. Our correspondence on kits showed very clearly that blind faith and an open purse were no guarantees of satisfaction. One needs to shop around with some knowledge of the goods, before parting with hard-earned cash.

Keeping to the subject of recording, remember the Wesgrove fiasco? Telcan had a good pioneering idea of a linear scan video tape recorder years ago, and poor marketing led to disappointment. Wesgrove took over the idea and brought out a kit which a number of our readers have since, frustratedly, tried to complete and operate. Now that commercial video tape recorders are genuinely with us, at prices that clubs, pubs, local authorities and businesses can afford, the helical scan system has absolutely

usurped the linear scan.

Unfortunately, like Baird battling on with his rotating mirrors, our readers have attempted betterment, and found the cost of improving a dead-end system to be quite exorbitant. Recording heads, which wear quickly when tape rushes past them at a high rate of knots, are virtually unobtainable. Whereas the originals were listed at three or four pounds, replacements have been quoted at twenty pounds or more.

Why? Quite simply because head manufacturers, no ostriches, have developed far better manufacturing techniques. Materials are more rigorously specified. Limits are closer. Standards have changed. The current heads are that much better, and will, inevitably, cost more.

It is futile, and foolish, to cry: "*Why don't they make a radio/amplifier/tape recorder/transmitter/computer/etc., exactly as I require?*" There is always a reason for a particular product to be marketed the way it is. And usually the reason is economic.

Of course it would be nice if the five-quid transistor radio you bought for the beach had another waveband. But by adding that little extra the price would have been nearer those shiny Jap models you thought twice about buying.

And if you had dug a little deeper into your savings, you could have toyed with the idea of the type that sported a larger speaker, or tape outlet and personal listening features. Or, with the knowledge that this magazine had given you, the better class set with battery economy circuits and then anti-fading front ends. And what about f.m.? and while we are about it, might as well go the whole hog and prepare for stereo broadcasting.

Before we know where we are, the covetous eye is glinting at magic boxes that cost two hundred guineas or more—even without



The covetous eye is glinting

leopard skin coats.

"*Why don't they?*" Indeed! I'll tell you why. Because the makers are in business to make a profit, and gear their production to a carefully studied market.

Why not buy basic, buy with care and buy quality, then modify the best to suit your own requirements? There must be a dozen ideas per issue that can be usefully adapted.

Example: some while back there appeared a few articles on automatic recording control systems. Soon afterwards, L. McNamara came up with an excellent in-line audio control unit, employing straightforward transistor circuitry. From this, it needs little ingenuity to add auto-control to your tape recorder. Yet there were letters for months that asked for chapter and verse on specific mods to particular machines that would afford the same facility.

O.K. So you haven't the time to experiment; nor the bottomless spares box that some of our contributors assume. So let's kick the ideas around a bit. Let's discuss a few of those modifications, adaptations and just plain improvements to commercial equipment and see what can be done.


Don't ask "Why don't they...?" Say "Why can't we...?" Any ideas worth passing on are welcome, and will not be ignored. What about it lads?



Digging into the savings

MARCONI TEST EQUIPMENT

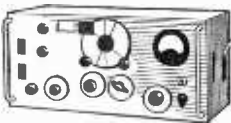TF.144G STANDARD SIGNAL GENERATOR.
85 Kc/s-25 Mc/s. 200/250 v. A.C. £25. Carr. 30/-.
TF.3290 "Q" METER Brand new with all accessories £75. T.F. 195M. BEAT FREQUENCY OSCILLATOR. 0-40 Kc/s. 200/250 v. A.C. £20. Carr. 30/-. All above offered in excellent condition fully tested and checked and offered at a fraction of original cost.



2-WAY RADIOS



Super quality. Brand new and guaranteed.

3 transistor £6.15.0 pr.
4 transistor £7.19.0 pr.
5 transistor £8.4.0 pr.
6 transistor £9.18.6 pr.
6 transistor De Luxe £17.10.0 pr.

10 transistor £22.10.0 pr.
13 transistor 500 MW £31.10.0 pr.

13 Trans. 1W £35.0.0 pr. Post extra.

These cannot be operated in U.K.

SINCLAIR TRANSISTOR

Z12 Amplifier 89/6; Z12 Power Pack 79/6; Stereo 25 Pre-Amplifier £9.19.6; Micro F.M. Radio Kits £5.19.8; Micro 6 Radio Kit 59/6; Micromatic Radio Kit 59/6; Ready built 79/6. Post paid.

COSSOR 1035 Mk II DOUBLE BEAM OSCILLOSCOPES

Latest model using miniature valves. Perfect condition. £45. Carr. 30/-.

GARRARD RECORD PLAYERS

8RP22 Player mono £4.40; 1000 changer mono or stereo £5.15.6; 2000 changer mono or stereo £6.19.8; 3000 Changer mono or stereo £7.19.8; SP25 Player mono or stereo £2.19.8; SP25 with cast turntable £10.19.6; AT60 Changer mono or stereo £10.10.0; AT60 Mk II mono or stereo £11.11.0; A70 less cartridge £18.19.0; LAB80 Mk II Stereo £25.0.0; 401 Transcription 26 gns. Brand new and guaranteed. All plus post and packing 5/-.

LAFAYETTE HI-FIDELITY SOLID STATE STEREO AMPLIFIERS

Latest 1967 models now available. Outstanding performance from modern semi conductors. Provision for all types of inputs and outputs and comprehensive tone controls. Attractive metal cased free standing units.



Model LA-224T 30 watt £25. Carr. 7/6. Model LA-60T 60 watt £37.10.0. Carr. 7/6. DETAILS ON REQUEST

LAFAYETTE MODEL HA-500 SSB/AM/CW 80 THROUGH 6 METRE RECEIVER



New outstanding Ham Bands only receiver covering the 80/40/20/15/10/6 metre bands. Incorporates 10 valves product detector, two mechanical filters, 8 Meter, dual conversion on all bands, crystal calibrator B.F.O. noise limiter, aerial trimmer. I.F.'s 2.608 Mc/s and 455 Kc/s. Output 8 ohms and 500 ohms. Operations 220/240 volt. A.C. Supplied brand new and guaranteed with handbook. 42 gns. Carr 10/- 100 Kc/s crystal 35/-.

★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 8in. x 4in. x 2 1/2in. 3 I.F. stages. Double tuned discriminator. Simple output to battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £8.10.0. P. & P. 2/6.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £5.19.6. P. & P. 3/6.

R.107 RECEIVERS

1.7-17.5 Mc/s. Mains or 12 volt D.C. operation. Perfect condition. £15. Carr. 30/-.

TYPE 13 DOUBLE BEAM OSCILLOSCOPES

5-5 Mc/s Bandwidth. Perfect condition. £22.10.0. Carr. 30/-.

VARIABLE VOLTAGE TRANSFORMERS

Brand New—fully Shrouded. Input 230v 50/60 c/s. Output 0-250 Volts.

1 Amp. £4.10.0
2-5 Amp. £5.17.8
5 Amp. £9.0.0
8 Amp. £13.19.0
10 Amp. £17.0.0
12 Amp. £19.10.0
20 Amp. £32.10.0

Post extra

AMERICAN TAPE

First grade quality American tapes. Brand new. Discount for quantities.
3in., 225ft. L.P. acetate. 4/-
3in., 600ft. T.P. mylar. 10/-
3in., 600ft. std. plastic. 8/6
5in., 900ft. L.P. acetate. 10/-
5in., 1,200ft. D.P. mylar. 15/-
5in., 1,800ft. T.P. mylar. 35/-
5in., 1,200ft. L.P. acetate. 12/6
5in., 1,800ft. D.P. mylar. 22/6
5in., 2,400ft. T.P. mylar. 45/-
7in., 1,200ft. std. acetate. 12/6
7in., 1,800ft. L.P. acetate. 15/-
7in., 1,800ft. L.P. mylar. 20/-
7in., 2,400ft. D.P. mylar. 25/-
7in., 3,600ft. T.P. mylar. 58/6

Postage 2/- Over £3 post paid.

CALLERS WELCOME!

Open 9 a.m. to 8 p.m. every day Monday to Saturday. Trade supplied. All items available as previously advertised.



CATALOGUE

- ★ ELECTRONIC COMPONENTS
- ★ TEST EQUIPMENT
- ★ COMMUNICATIONS EQUIPMENT
- ★ HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and equipment. Over 150 pages fully illustrated, listing thousands of items, many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy.

CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discount for quantity. Available as follows: Type MR 38P, 1 21/32in. square fronts.



100-0-100µA	27/8	200mA	22/8	100V D.C.	22/8
500-0-500µA	22/8	300mA	22/8	150V D.C.	22/8
1-0-1mA	22/8	500mA	22/8	300V D.C.	22/8
1mA	22/8	750mA	22/8	500V D.C.	22/8
2mA	22/8	1A D.C.	22/8	750V D.C.	22/8
5mA	22/8	2A D.C.	22/8	15V A.C.	22/8
10mA	22/8	5A D.C.	22/8	50V A.C.	22/8
20mA	22/8	3V D.C.	22/8	150V A.C.	22/8
50µA	32/8	10V D.C.	22/8	300V A.C.	22/8
100µA	27/8	20V D.C.	22/8	500V A.C.	22/8
200µA	27/8	50V D.C.	22/8	8" Meter 1mA	29/6
500µA	25/-				
50-0-50µA	29/8				


POST EXTRA. Larger sizes available—send for lists.



NEW MODEL 500. 30,000 o.p.v. With overload protection, mirror scale, 0.5/1.2/5/10/25/100/250/500/1,000V. D.C. 0.2/5-110/25/100/250/500/1,000V. A.C. 0.50µA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg./60 Meg. G. £8.17.6. Post Paid.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

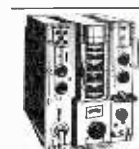Sine: 20 c.p.s. to 200 kc/s on 4 bands. Square: 20 cps to 30 kc/s. Output impedance 5,000 ohms, 200/250 v. A.C. Supplied brand new and guaranteed with instruction manual and leads, £15. Carr. 7/6.



ADMIRALTY B.40 RECEIVERS

Just released by the Ministry. High quality 10 valve receiver, manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 500 Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O., calibrator, I.F. output, etc. Built-in speaker, output for phones. Operation 150/220 volt A.C. Size 19 1/2 x 13 1/2 x 1 1/2 in. Weight 1lb 4oz. Offered in good working condition, £22.10.0. Carr. 30/-. With circuit diagrams. Also available B.41 L.F. version of above. 15 Kc/s-700 Kc/s. £17.10.0, carr. 30/-.

LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save pounds. Supplied semi completed, main components ready mounted, R.F. section already wired and aligned. Full and precise instructions supplied. Specification:—3 valves+rectifier, 4 bands covering 550 kc/s-30 Mc/s. Incorporates 1 R.F. and 2 I.F. stages, "Q" multiplier, B.F.O., A.N.L., "S" meter, bandspread, aerial trimmer etc. Operation 115/230 V.A.C. Price 25 gns. Carr. 10/-.




HAM-1, 4 BAND COMMUNICATION RECEIVER

4 wavebands covering 535 kc/s. to 30 Mc/s. 5 valve superhet circuit. Incorporates "S" meter, B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE WEIGHT AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240 v. A.C. Supplied brand new with handbook. £15.15.0. Carr. 10/-.

LAFAYETTE HA-700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER

8 valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 kc/s, 550-1,600 kc/s, 1.6-4.0 Mc/s, 4-9-14.5 Mc/s, 10-5-30 Mc/s. Circuit incorporates R.F. stage, aerial trimmer, noise limiter, B.F.O., product detector, electrical bandspread, "S" meter, slide rule dial. Output for phones, low to 2K Ω or speaker 4 or 8 ohms. Operation 220/240 volt A.C. Size 7 1/2 in. x 13 in. x 10 in. Supplied brand new and guaranteed with handbook. 36 GNS. Carr. 10/- S.A.E. for leaflet.

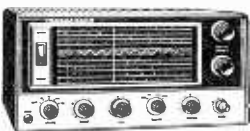

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155

Cables: SMITHEX LESQUARE

3-34 LISLE STREET, LONDON, W.C.2

Everything You need to know about

RADIO, TELEVISION & ELECTRICAL REPAIRS

AMAZING 'KNOW HOW' BOOK

Brings You RIGHT UP TO DATE!

576

PAGES

OVER

470

ILLUSTRATIONS

REVISED AND ENLARGED—this essential handbook for the enthusiast, handyman or professional repairer, is packed with detailed information and easy-to-follow instructions on how to service radio and TV sets (including all-transistor and U.H.F. circuits), audio equipment and domestic appliances of every kind. Shows every step in fault tracing and the use of modern test gear, from simple meters to complex oscilloscopes. Also provides practical guidance on household electrical installation work. 576 pages. Over 470 illustrations. Mammoth value—Special Library Edition, superbly bound in Leathercloth, 50/-, or on easy terms; 13/- down and 3 monthly instalments of 14/- (total credit price 55/-). But first accept 7 Days' Home Trial Offer—without obligation!



COVERS ALL THE LATEST TECHNICAL ADVANCES!


U.H.F. TELEVISION

Here are basic circuits and full instructions to enable you to service modern sets—get perfect 625-line reception.

Getting the best from RADIO AND TELEVISION SETS

How to make adjustments and repairs in order to get the best possible performance from any set.

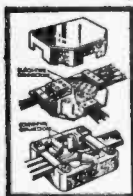
All you need to know about DOMESTIC INSTALLATIONS



Learn from these helpful pages how to carry out modifications and extensions—with efficiency and safety! Complete guidance on lighting and power circuits, practical wiring work, safety regulations, cables, earthing, fuses, etc. Also Fluorescent Lighting, Thermostats and Time Switches.

WATER HEATING

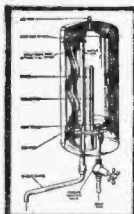All you should know about water heaters and how to install them and keep them in perfect working order. How to service FIRES and SPACE HEATERS.



HOW TO MAINTAIN AND REPAIR DOMESTIC APPLIANCES

From irons, toasters, hair dryers, etc. to cookers, washing machines and refrigerators. Also covers the repair and rewinding of small motors.

SPECIAL SECTION ON COLOUR TELEVISION

Explains clearly and concisely the principles of prospective colour systems.

FAULT FINDING

This grand book is invaluable for tracing faults in radio and TV sets (both valve and transistor circuits). Deals fully with tools and bench work—shows how to make the best use of test instruments. Tells everything you want to know—from how to carry out preliminary tests to how to align tuned circuits.

Servicing DOMESTIC AUDIO EQUIPMENT

How to locate and rectify faults in hi-fi equipment (mono or stereo), record players, tape recorders, etc.

ACT NOW!

Simply complete form, indicating method of payment preferred, and post in a 3d. stamped unsealed envelope. Offer applies in U.K. only. Hurry, make sure of your copy.

ONE GREAT VOLUME covers:

Current, Voltage and Resistance, Coils, Capacitors and Tuning, Valves, Tubes and Transistors, Radio Components, Receiver Design Principles, Transistor-Radio Circuits, Valve-Radio Circuits, Valve-Television Circuits, Transistor-Television Circuits, Colour-Television Systems, Audio Amplifier Circuits, Audio Equipment and Gramophones, Tape Recorders, Radio and Television Aerials, Tools and Bench Work, Test Instruments and Their Use, Fault Tracing and Circuit Testing, Alignment of Tuned Circuits, Television Fault Tracing, Interference Suppression, Domestic Power Supply Circuits, Electrical Wiring Work, Fluorescent Lighting, Thermostats and Time Switches, Motor Repair and Rewinding, Small Appliances, Space and Water Heaters, Electric Cookers, Washing, Drying and Ironing Machines, Electric Refrigerators, Suction Cleaners and Floor Polishers.

SEND NO MONEY NOW!

To: Dept. EB35, Odhams Books Ltd., Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION please send me, on 7 Days' Home Trial, Radio, Television and Electrical Repairs. Within 8 days I will either (a) send the Cash Price of 50/- (plus charge for postage and packing), or (b) send a down payment of 13/- (plus postage charge), followed by a 3 monthly payments of 14/- (Total Credit Price 55/-). Alternatively, I will return volume in good condition, postage paid, within 8 days.

Cross out words NOT applicable below:

I wish to pay by CASH/TERMS. I am (a) houseowner; (b) tenant in house or flat; (c) temporary resident; (d) single; (e) married; (f) over 21; (g) under 21.

PLEASE SIGN HERE

Your Signature
(Or, if you are under 21, signature of parent or guardian)

BLOCK LETTERS BELOW

NAME (Mr./Mrs./Miss)

Full Postal

ADDRESS

EB35/Nov.67

3 WATT RECORD AMPLIFIER

R.V. ASKEY

THIS inexpensive two stage audio amplifier is suitable for use with one of the many crystal cartridges now available. It will provide 3 watts of output to a small elliptical loudspeaker or will drive an 8 inch speaker with more favourable results. The author has found this design most satisfactory and stable over long periods.

Circuit Description

The voltage amplifier is designed around a double diode triode valve—the EBC90. In this application, the diodes are not used and so are strapped together and earthed; thus the valve acts as a straightforward triode pre-amp. C1 serves to decouple and smooth the anode supply to V1, keeping hum and distortion negligible. The omission of a cathode bypass capacitor on V1, introduced some negative feedback and helped to keep distortion to the barest minimum. If more volume is required then R10 could be omitted, but this should be done only if really necessary as some distortion may occur. VR1 is the volume control which is fed into an effective potential-divider tone control arrangement—VR2.

A progressive “top cut” or “bass lift” occurs as the slider of the tone control is turned towards the capacitor end of the control. From the tone control, the signal is fed into the output stage, consisting of a high slope output pentode—the Mullard EL84—this valve delivers approximately 4 watts of undistorted output to 3 ohm speaker via a multi-ratio output transformer. C8 serves as further tone correction while C4 is a decoupling capacitor for the screen voltage on the output valve.

Power Supply

This provides approximately 260V at C6, being rectified by an EZ80 full wave rectifier. R7 acts as smoothing resistor.

Construction and Layout

A wiring diagram is given, as the author considered it was a necessity for the beginner. Layout of components is by no means critical and most components can be wired direct to the valveholders. Care should be taken to use screened wire on all grid leads and to use twin flex tightly twisted for valve heaters. These wires should be kept close to chassis to minimise a.c. mains hum which could be picked up and induced into the first stage.

Negative Feedback

When connecting the negative feedback leads from chassis and C5 to the output transformer secondary, there should be a decrease in volume compared to that obtainable when C5 is returned to chassis direct.

If even more volume is required, the negative feedback could be omitted and C5 connected direct to chassis. No distortion should occur although the overall frequency response may not be so good. If when connecting the feedback, there is an increase in volume with possibly some instability, this points to positive feedback and is an incorrect mode of operation.

★ components list

Resistors

R1	220k Ω	R8	100 Ω
R2	4.7k Ω	R9	100 Ω
R3	33k Ω	R10	15k Ω
R4	47k Ω	Rx	500k Ω
R5	5.6k Ω	VR1	2M Ω log
R6	180 Ω $\frac{1}{2}$ W 5%	VR2	1M Ω lin (or log)
R7	250 Ω 5W		

(All $\frac{1}{4}$ or $\frac{1}{2}$ W 10% unless otherwise stated)

Capacitors

C1, C4	16+16 μ F elec. cond. 450V
C2	0.02 μ F 350V
C3	150pF 150V
C5	50 μ F 50V
C6, C7	32+32 μ F elec. 450V
C8	2,000pF 350V

Valves

V1	EBC90	V3	EZ80
V2	EL84		

Mains Transformer T1

Primary: 200–220–240V.
Secondaries: 250–0–250V, 80mA, 6.3V, 3A.

Output Transformer T2

Elstone MR/T Multi-Ratio for 3/4 watts

Miscellaneous

Two B9A valveholders. One B7G valveholder. S1 double pole on/off switch on VR1. SK1 coax socket. Chassis to suit, screened lead, wire solder, bolts, pilot lamp (if required), etc.

Note: Tags marked 'M.C.' are earthing points to chassis

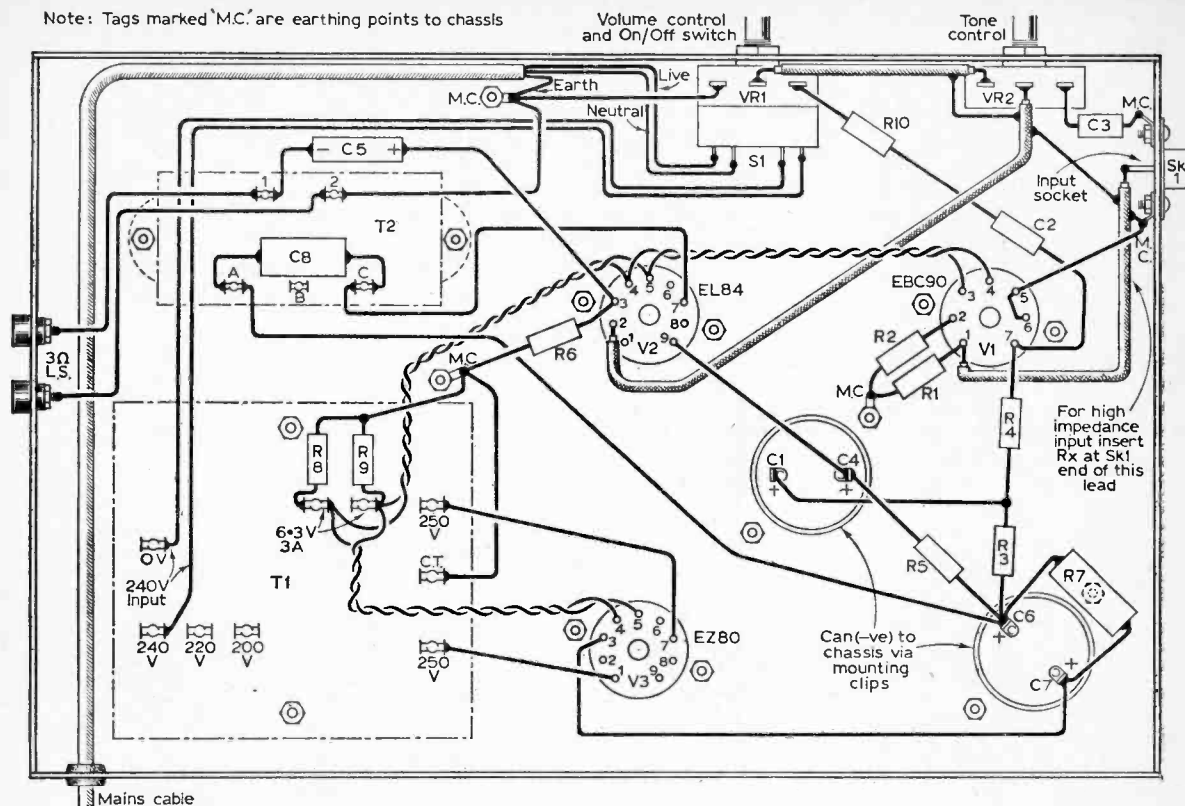


Fig. 2: Underside wiring and layout of the complete amplifier. Note that T1 and T2 are mounted above the chassis.

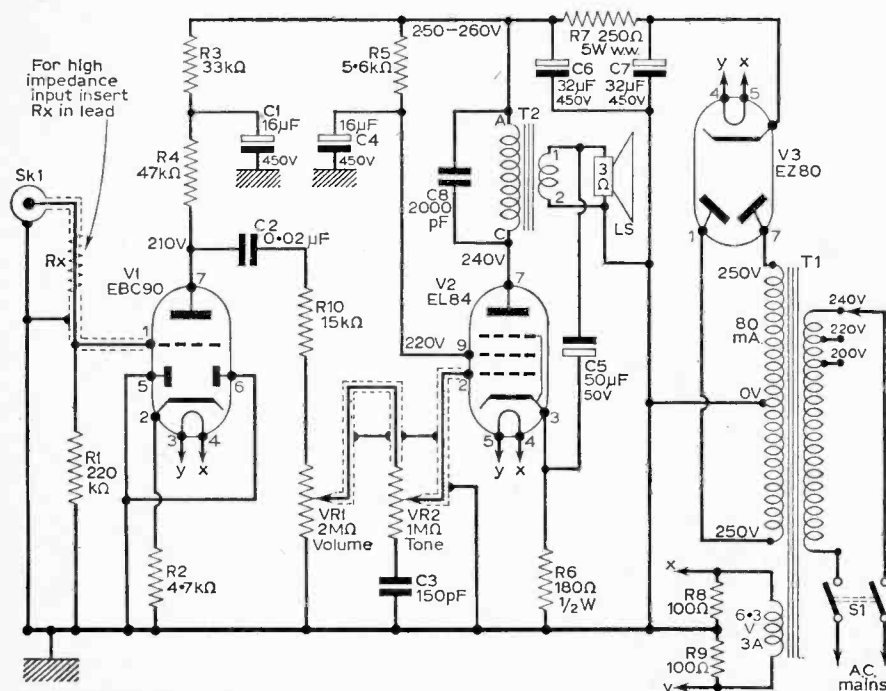


Fig. 1: Circuit diagram of the record amplifier. All screening to be connected to chassis.

Correct operating conditions will be given by reversing the feed-back connections to the transformer secondary.

Conclusion

The constructor will find this two-stage amplifier far more satisfactory than those amplifiers using, for example, an ECL82 or UL84, which are found in some record players.

The author constructed the prototype in a portable cabinet, using a 7 x 4in. elliptical speaker with exceptional results. The recommended cartridge is the Ronnette TX88, using a low input circuit or the Garrard GC8. For a high input circuit, the Acos GP67-2 is recommended.


UNBEATABLE AT ONLY

19.10.0
U.P. terms available.

Carriage 7/6 extra. H.P. terms available.


Carriage 7/6 extra. H.P. terms available

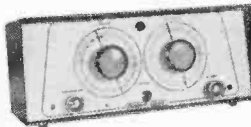***Ideal for SWLs *5 valves (inc. two twin triodes) giving 7 valve line-up *Excellent on amateur and shipping frequencies *Calibrated signal strength meter (illuminated) *Automatic volume control *Separate B.F. oscillator for morse and S.S.B. signals *Two speed vernier tuning**



CR45 MAINS T.R.F. SHORT-WAVE
RECEIVER

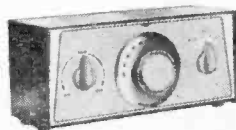**CR45 MAINS T.R.F. SHORT-
RECEIVER**
World wide reception. *Separate electrical band-
spread. *3 slow motion drives. *Output 3 watts
for 2/3 ohm speaker. *Valves ECC81, EL84, EZ80.
Size 12" x 5½" x 7". CODAR-KIT CR.45K with 3 coils
(10-28, 25-75, 60-176 metres). £9.10.0. Carr. 6/-, or
ready built CR.45 £11.7.0. Carr. 6/-. Extra coils 5/-
each.



MINI-CLIPPER—OUR FAMOUS
SHORT-WAVE RECEIVER

R.F. PRE-SELECTOR MODEL P.R.30
15.30Mc s 20dB gain plus substan

R.F. PRE-SELECTOR MODEL 15-30Mc
Provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Power requirements 180-250 volts 12mA H.T. 6.3 volts, 3 amp L.T. Size 8½" x 5" x 4". Ready built complete with cables, plugs and Instructions. £5.10.0. Carr. 4/6. Self-powered P.R.30x £7.4.0. Carr. 4/6.



**CODAR
RADIO
COMPANY**

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX. TEL: 3149
World-wide Mail Order Service

please supply

(stick as required)

☐ I enclose cheque/
M.O./P.O. value of

NAME _____

ADDRESS

I should like
H.P. details

6d stamp enclosed
for leaflets

POST ORDER FORM TODAY

TRANSISTOR STEREO 8+8



A really first-class Hi Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief Specification: Freq. response +3dB 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements at 25V at -6 amp.

QUALITY RECORD PLAYER AMPLIFIER


A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 5in. d. x 6in. h. Ready built and tested. PRICE 89/6. P. & P. 8/-.

DE-LUXE QUALITY PORTABLE R/P CABINET

Uncut motor board size 14 1/2 x 12in. Clearance 2in. below, 6in. above. Will take above amplifier and any B.S.R. or Garrard Autochanger or Single Player Unit (except AT60 and SP25) Size 18 x 15 x 8in. Price £23.9.6. Carr. 9/6.

STEREO AMPLIFIER

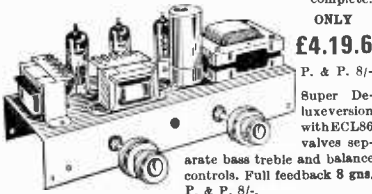Incorporating 2 ECL86s and 1 EZ80 heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY £4.19.6

P. & P. 8/- Super De-lux version with ECL86 valves separate bass treble and balance controls. Full feedback 8 gns. P. & P. 8/-.

10/14 WATT HI-FI AMPLIFIER KIT

A Stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram and record and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6 (Free with parts). All parts sold separately. ONLY £7.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets. £9.5.0. P. & P. 8/6.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1

● Peak output in excess of 14 watts.
● All standard British components.
● Built on printed circuit panel, size 6 x 3in.
● General size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transformers (OET 114 or 81 Mullard OC81D and matched pair of OC81 o/p. ● 9 volt operation.
● Everything supplied, wire battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.
SPECIAL PRICE 45/- P. & P. 3/-
Also ready built and tested, £28/6. P. & P. 3/-
A pair of TAs are ideal for stereo.

BRAND NEW TRANSISTOR BARGAINS
OET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 7/6.
Set of Mullard 6 transistors OC44, 2—OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6. All post free.


3-VALVE AUDIO AMPLIFIER HA34



Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83 EL34, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £24.5.0. P. & P. 6/-.

HSL 'FOUR' AMPLIFIER KIT

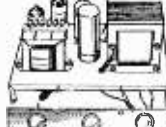A.C. Mains 200/250v., 4 watt, using ECC83, EL84, EZ80 valves.



● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● Chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valve output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy). PRICE 79/6. P. & P. 6/-.

Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit). This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

BRAND NEW T.V. U.H.F. TUNER AND SOUND AND VISION I.F. PANEL

By world famous maker. Suitable for use in conversion of TV sets to BBC2 (625 line reception). OFFERED (less valves) AT THE BARGAIN PRICE OF ONLY 27/6. Post paid. (The components are worth far more than our price for the complete unit and due to the very high value we regret that no correspondence can be entered into regarding this item.)



FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dorman and Wadsworth Ltd. Supplied ready fitted with twin -0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10-7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 30/- P. & P. 3/-.

MATCHED PAIR AM/FM I.F.'s

Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s 110/7Mc/s). Size 1 x 1 1/2 x 2 1/2 in. high. Will match above tuner head. 11/- pair. P. & P. 2/-.

SPECIAL PURCHASE! TURRET TUNERS

By famous maker. Brand new and unused. Complete with POC84 and PCF80 valves 34-38 Mc/s I.F. Biscuits for Channel 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/8.

GORLER F.M. TUNER HEAD

88-100 Mc/s, 10-7 Mc/s I.F. 15/- plus 2/- P. & P. (ECC85 valves 8/6 extra).

TWIN TELESCOPIC AERIAL. Comprising 2-section heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/6.

PRICES

Amplifier Kit £9 10 0 P. & P. 4/6.
Power Pack Kit £2 10 0 P. & P. 4/-.
Cabinet (as illus.) £2 10 0 P. & P. 5/6.

(Special offer—£14.10.0, post free if all above ordered at same time.)

Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.)

SPECIAL PURCHASE!

B.S.R. GU7

9-volt Battery Operated Record Player Units. 4 speeds. Automatic stop. Plays any size record. Complete with mono t/c head and sapphire styl. ONLY 69/6. P. & P. 5/6. (With stereo cartridge 12/6 extra).



4-SPEED PLAYER UNIT BARGAINS

Mains Models. All brand new in maker's original packing. SINGLE PLAYERS
B.S.R. TU/12..... £3.9.6 Carr. 5/6.
GARRARD SP25 De Luxe £10.19.6 Carr. 5/6.
B.S.R. GU7 with unit mounted pickup arm. £4.18.8 Carr. 5/6.

AUTO CHANGERS (Carr 6/6 on each)
Latest B.S.R. L23 Super Slim..... £6.2.6
GARRARD 1000 with Hi-Fi cartridge..... £8.19.6
GARRARD 2000 £7.10.0. GARRARD 3000 £8.5.0
LATEST GARRARD AT60 Mk. II..... £12.0.0
All the above units are complete with t/c mono head and sapphire styl or can be supplied with compatible stereo head for 12/6 extra.

BRAND NEW CARTRIDGE BARGAINS

ACOS 69/1 MONO CARTRIDGE. For E.P. and L.P. Complete with stylus. ONLY 12/6. P. & P. 1/-.

BRAND NEW 3 OHM LOUDSPEAKERS

5in., 12in; 6in. 15/-; 8in. 22/6; 10in. 27/6; 7in. x 4in. 16/-; 10in. x 6in. 27/6.
E.M.I. 8in. x 5in. with high flux magnet, 21/-.
E.M.I. 13 1/2 x 8in. with high flux ceramic magnet, 42/- (15 ohm 45/-). P. & P. 5in. 2/-, 6 1/2 in. 2/6, 10 & 12in. 3/6 per speaker.

35 OHM SPEAKERS

2in. Goodmans' Ideal replacement for most pocket portables. 8/6; 3 1/2 in. 12/6; 7 x 4in. 21/- P. & P. 2/- per speaker.

E.M.I. PLASTIC CONED TWEETERS, 2 1/2 in. 3 ohm. Limited number 12/6 each. P. & P. 1/6.

BRAND NEW HEAVY DUTY 12in. SPEAKERS.

Response 45 c/s—13 Kc/s. 1 1/2 in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 89/6. P. & P. 5/-. Also 25 watt Guitars Model available at £5.5.0. And 35 watt Guitars Model £8.8.0.

VYNAIR AND REXINE SPEAKER AND CABINET FABRICS.

Approx. 54in. wide. Usually 35/- yard. Our Price 13/6 per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

LATEST COLLARO MAGNAVOX 383 TAPE DECK.

DE LUXE. Three speeds, 2 track, takes up to 7in. spools. 10 gns. Plus 7/6 Carr. & ins. on each (Tapes extra). QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 55/- P. & P. 3/-.

ACOS CRYSTAL MIKES.

High imp. for desk or hand use. High sensitivity. 18/6. P. & P. 1/6.

ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES.

Listed at 42/-. OUR PRICE 21/- P. & P. 1/6.

NEON A.C. MAINS INDICATOR.

For panel mounting, cut out size 1 1/2 x 4 x 1/2 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P. & P. 6d. (6 or more post free).

VIBRATORS.

Large selection of 2, 4, 6, 12, 24 and 32 volt. Non sync 8/6; Sync 10/- P. & P. 1/6 per vibrator. S.A.E. with all enquiries.

MAINS TRANSFORMER.

For transistor power supplies. Tapped pri. 200-250 v. Sec. 0-0-40 at 1 amp (with electrostatic screen) and 6.3 v. at 5 amp for dial lamps etc. Drop thro mounting. Stock size 1 1/2 x 3 1/2 in. 27/6. P. & P. 4/6.

MAINS TRANSFORMER.

For transistor power supplies. Pri. 200/240 v. Sec. 0-0-9 v. at 500 mA, 11/- P. & P. 2/6.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.

Stock size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohms and 15 ohm output. 10/- pair, plus 2/- P. & P.

7-10 WATT OUTPUT TRANSFORMERS to match pair of

ECL 86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.

10-12 WATT OUTPUT TRANSFORMERS.

Size 2 1/2 x 2in. Clamp fitting. For two EL84's in push pull. State 3 or 15 ohm impedance. 12/6 P. & P. 2/6.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

new books

Books reviewed on this page are normally obtainable through any retail bookshop. In this instance, the information printed in heavy type should be quoted.

BUILDING YOUR AMATEUR NOVICE STATION
By Howard Pyle, W7OE. Published by Foulsham-Sams.
115 pages, 11 x 8½ in. Price 28s.

THIS is a book originally intended for the American market. To offer it for sale in this country is, in my opinion, a mistake, particularly in view of the fact that it is intended for the newly licensed amateur.

The first four pages are taken up with informing the novice about disregarding this or that; that the transformer quoted might not be available; that anode resistor values can be chosen to drop the anode voltage to any required figure for the valve used. So our poor novice cannot look at the circuit and components list and decide what he needs, but must check through and then go back to the first four pages to find out that the transformer *might* not be obtainable, that certain electrolytic values *might* need changing and so on.

The actual c.w. "station" described has to be seen to be believed. It stands over three feet tall and eleven inches square—and contains three valves—one in the receiver, one in the transmitter and the other in an amplifier for the receiver!

One wonders how many of these novice monstrosities adorn the homes of American Hams. One shrinks to imagine the reaction of the British housewife at the introduction of such a hilarious piece of furniture into her house. Regrettably, it is not possible to recommend this book other than for amusement only.—*DLG*

TRANSISTORS FOR TECHNICAL COLLEGES
By L. Barnes, M.Sc.Tech., A.M.I.E.E. Published by Iliffe Books Ltd. 194 pages, 8½ x 5½ in. Price 42s.

THIS book will suit a number of people with a common interest in transistors. It should prove particularly useful to students taking telecomms and would serve as an introduction in elementary design work for those engineers who have neglected to study semiconductors.

It is presented with great clarity and the chapters follow a sensible order. It was particularly pleasing to find three pages at the beginning of the book devoted to symbols and definitions, thus avoiding any possibility of confusion. Indeed the only confusing thing in the entire book was the drawing which shows a transistor with two collectors and one presumes that the bottom collector is in fact the emitter.

Commencing with a description of the crystal diode and fundamentals of transistor action the book carries on through Transistors in Practice; Approximate Design of Linear Circuits; Parameters and Equivalent Circuits for Low Frequencies; Frequency Effects; Switching Circuits and finishes with a conducted tour of a number of practical and useful experiments. Taken at a steady pace the book makes interesting and very informative reading and is unhesitatingly recommended.—*DLG*

UNDERSTANDING AMPLITUDE MODULATION
By Irving M. Gottlieb. Published by Foulsham-Sams.
160 pages, 8½ x 5½ in. Price 25s.

FOR those interested in amplitude modulation this book will be of great interest and will prove a useful addition to the bookshelf. Starting with fundamentals, it covers a wide field, from high-level to low-level amplitude modulation. There is a very interesting chapter at the end describing techniques for improving the performance of amplitude modulators.

It was most gratifying to observe that Mr. Gottlieb had not forsaken transistors, and the book covers both these devices and valves. Another point in its favour is the marked absence of frightening higher mathematics. Although maths. does enter into the subject, the text is written in such a way that an advanced understanding is not required and where maths. is shown the text covers the same story in words.

Those who read this book and transmit on a.m. will doubtless have second thoughts on what is happening in their own equipment. The author caters for the s.s.b. enthusiasts, too, and even bearing in mind the somewhat narrow interest of the subject, it is still recommended.—*HRO*

ELECTRONICS FOR YOUNG EXPERIMENTERS
By W. E. Pearce, B.Sc. Published by G. Bell and Sons Ltd.
159 pages, 5½ x 8½ in. Price 18s. 6d.

THIS book is intended to provide an understanding of electronics together with an enjoyment of the subject. It is primarily intended for the young experimenter and gives some seventy experiments designed to be carried out at home without any need for elaborate or expensive equipment. Most of the apparatus, in fact, is built during the course of the experiments.

The book opens with details of making and experimenting with electroscopes and electrical machines. From this, the reader is guided through to making electromagnetic devices and then to the construction and conversion of various types of meter, a relay, d.c. and a.c. motors, a magnetic brake, a device for the testing of one's reactions and generating a.c. current using a torch battery.

There is a chapter on inductance which leads on to the setting up of an oscillating circuit and the making of a simple form of oscilloscope.

Finally, there is a chapter on transistors, transistor circuitry and photo-transistors, with the construction of a simple telephone circuit, transistor radio, and a toy electric organ.

Summing up, I think this book would be a valuable asset to those lads who have attained their first or second years in a senior school and who want to study physics, for they could obtain the theoretical knowledge from their science master and gain the practical experience from doing the experiments that are described in this book.—*CRR*

SHOWTIME '67




A REVIEW OF NEW MODELS AND TRENDS AT
THE SERIES OF TRADE EXHIBITIONS IN LONDON
FROM AUGUST 20-25th.

★ Players and Grams

This year, the accent as far as radiograms go, was once again on the Scandinavian-type wood design although one or two manufacturers had veered away from this and adopted Regency-style cabinets and small radiogram-type units on plinths that needed external speakers.

Record players this year seemed to cater, as always, for the mass market, designs seeming not vastly different from previous years. We did think, however, that customers will get "higher fi" for their money this year.

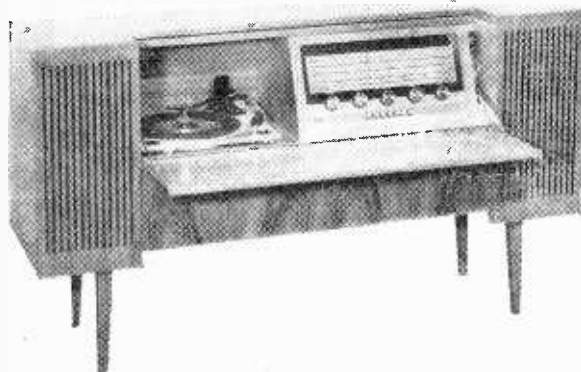A new entrant to the market this year is S.S.C. Luxor from Sweden, who assemble their equipment in Denmark then export it to the U.K. One of the




GEC G988 8W stereogram with long, medium, short and v.h.f. bands.

most significant developments in the radiogram market is the continuation of the audio units (Philips' *Audio Plan*, Ferguson's *Unit Audio* and Dynatron's *Audio Separates*). Philco are also introducing this style of presentation.

A good idea came from Monogram who introduced their *Custom Decorator*, an a.m./f.m. set with stereo radio which can be mounted on the wall, thus saving floor space.

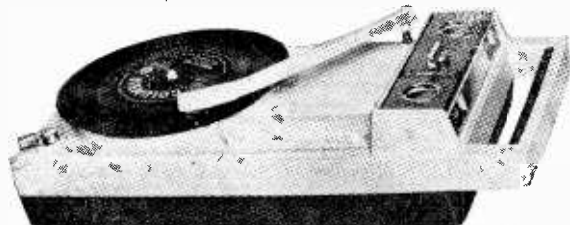Sharp claimed to be exhibiting the smallest stereo radiogram. It was the FXG-702, an a.m./f.m. port-



Alba 3000 portable gram with 2-speed player and m.w./l.w. radio.

able, which can play 12in. records, weighs 3lbs. and sells at £30 17s. 5d. Another compact radiogram was the Alba 3000, measuring $14\frac{1}{2} \times 7\frac{1}{2} \times 3\frac{1}{2}$ in. and with an output of about 600mW—price of this one was 18½ guineas.

Decca introduced their SRG747 radiograms styled in the Regency vogue. The Regency costs 219 guineas and the Queen Anne, 228 guineas—very nice, but you have to have the right decor for these two!


We thought that this year modules (pre-assembled units for i.f., a.f., etc.) would definitely be "in", owing to the fantastic ease of servicing, but it seems as though K-B are still the only people jumping on this band-wagon with their KG041 and KG042 radiograms. Both these units also incorporated fly-wheel tuning which was an extremely useful feature. The KG042, by the way, was finished in a new wood finish on show for the first time this year—canaletto walnut.

As far as record players were concerned, compatibility was definitely the keynote, for most makers exhibited mono models fitted with the kind of cartridge that would play both stereo and mono records. This move means that eventually, only stereo records will be stocked in the shops and mono will be completely "out".

Newcomers to the market this year are Van der Molen, Wyndson and B.M.B. Van der Molen entered the field with their *Sonic Four* record player—a 4-speed autochange unit with the amplifier mounted in a central plinth with a transparent perspex lid. It has two separate speaker enclosures and all three units are styled in teak. The stereo amplifier has outputs of 4W per channel and the recommended list price is 39½ guineas. Wyndson exhibited three models, one of which was housed in a speaker cabinet.

K-B use modular construction in their record players KP036 and KP034. The KP034 having a stereo adaptor costing 13½ guineas which contains the same amplifier as its parent unit and gives stereo output of 7W per channel.

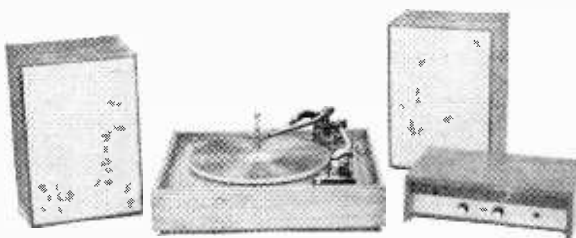Stereo consolettes on show included Pye's successor to the *Black Box*—the *Stereo Princess* in teak cabinet costing £55. HMV have 1967 versions of



B.M.B.'s stereo unit with 6W per channel and using Garrard 3000LM deck. Price ? Under £50!

their *Stereomaster* which can include v.h.f. radio with multiplexer decoding.

Mono consolettes include the Alba 338 which has novel styling. It has a shelf which extends out of one side of the player stand with a record storage rack. It is fully transistorised, has teak cabinet and costs 28½ guineas.

Dansette's introductions can be used with their "cruciform" stand and models on show included the *Bermuda Mk. 2* which had a rather colourful interior design, and the *Regina*, in black with a lid

made of rosewood. Also seen was the *Prince*, an attractive unit with sides of teak and an 8in. reproducer. Both the *Regina* and *Prince* are adaptable for stereo with matching units similar to K-B model KP034.

Winter Trading were exhibiting some very reasonably priced units. Their *Gold Crest* PH333 for 7½in. 45 r.p.m. records only, retailing at 5½ guineas. They also had the *Taya* PHD105 for 45's and 33½ discs, which costs 9½ guineas and a stereo version at 16½ guineas.

★ Radio Receivers

THE display of radio sets this year was disappointing, most manufacturers showing only a small handful and usually accounting for only a very small space in their exhibitions, but one or two interesting trends became evident.

Styling seems to adhere rigidly to the "black and chrome" line, particularly in portables, but for the larger table models the "brown" look continues. Although there were individual variations in shapes, handles, etc., the trends here still followed the same familiar patterns mentioned above.

But although first impressions were that there was nothing really new, closer observation proved different. Portables are now commonly offering a choice of third waveband; i.e., Long and Medium wave plus f.m.—nearly all with a.f.c. Those with-




Benkson's models 202 (left) and 101 (right).

out f.m. offered Shortwave coverage far in excess of the usual 6 to 15Mc/s.

The Hacker *Helmsman*, for instance, gave Long and Medium wave coverage plus Short waves from 1.58 to 30.64Mc/s which should be of interest to the Shortwave types. Sensitivity at 30Mc/s is quoted as 2µV for 50mW output. The set also has a bandspread tuning control and boasts separate ferrite rod aerials for Medium, Long and Marine bands, with provision for an external aerial. Full output is rated at 750mW and the set also has a tone control. Price should be around £33.

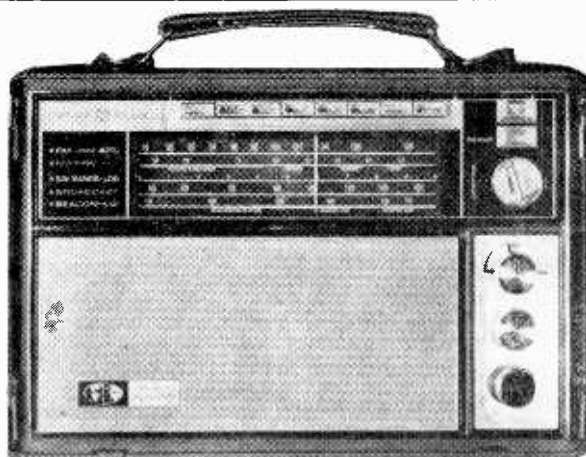An interesting feature of the Hacker range was the use of plug-in modules which should help servicing considerably and is an advantage from the production point of view since the modules are used in various sets. The waveband switch




The World Monitor from Monogram.

brings in a separate oscillator for each range to avoid complicated and "lossy" coil switching.

It was surprising to see how many portables are including the Marine band now. The *World Monitor* by Monogram is an example. This one has broadcast band, Marine band from 1.8 to 5.0Mc/s, Beacon Long wave from 170–370kc/s, six bandspread Shortwave bands—16, 19, 25, 31, 41 and 49 metres, and rounds off with f.m. from 88–108Mc/s. It has two telescopic rod aerials and a tuning meter.

The Grundig *Satellit* at 119 guineas is quite something to see and, as you might guess, is offered for the connoisseur. It even has built-in protection in case lightning strikes the aerial while you are listening!

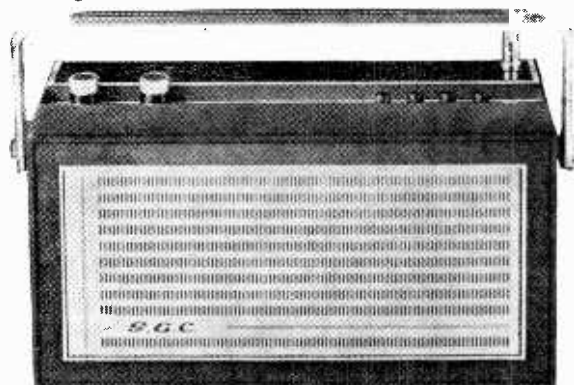In the cheaper price range there were many portables to choose from. Binatone offered their *Cross-world* m.w./l.w. 9-transistor set for £3 19s. 6d., although with nine transistors one does wonder how



GEC G834 10 transistor a.m./f.m. portable with separate car input circuit.

long the battery will last. Benkson also offered radios in the lower price bracket, model 202 m.w./l.w. at £4 19s. 6d. being typical in this range.

In the low price brackets were many imported sets, some with gimmicks, like the Hitachi *Hi-Phonic*, which has a small bezel which illuminates when a station is tuned in. Of interest here too was the Shortwave converter for a standard car radio suitable for both 6 and 12-volt positive or negative earth.

Not too much stereo in evidence this year and those which did put in an appearance were mostly

tuners with a predominance of wood styling as was the trend at the Audio Fair earlier in the year.

All-in-all there was nothing really new or startling. Some makers were "with it" and had changed the tuning dials to cater for the new wording for the Home, Light, etc., to BBC1, BBC2, etc. Portables are still available quite cheaply but the trend is for them to grow more sophisticated and complex with added amenities like increased Short-wave coverage, bandspread, f.m. with a.f.c. After everything is considered, it boils down to the most obvious conclusion: you get what you pay for.


★ Tape Recorders

THE most notable feature in the tape recorder field was the substantial increase in the number of cassette models now on the market for use with C60 or C90 cassettes and for the reproduction of the *Musicassettes* introduced by Philips and E.M.I. last October. Cassette models have now been introduced in the Acme, Alba, Dansette, Eagle, Elizabethan, Elpico, Ferguson, H.M.V., National, Philco, Philips, Stella and Van Der Molen ranges.


Most of these machines are "compact" portable models weighing 3—4 lb. Stereo cassette models were featured by Eagle and Van Der Molen. The Van Der Molen *Sonic Five* is a mains-operated model intended for plugging into radiograms, high fidelity amplifiers, audio plan units or piped music systems, and produces a stereo output of approximately 750mV per channel. The Eagle mains/battery stereo cassette tape recorder Model TP1004 comes with clip-on speakers. Also in this range is a cassette model (TP718) for car use. Other cassette models for use in cars were shown by Philips and Elpico.

New from Philips is a cassette model (RL673) with built-in a.m./f.m. radio. Elizabethan showed two larger cassette models, the LZ613 *Compette*, a mains-operated model with 3W output, and the LZ612 which, at 45 guineas, provides an output of 5½W to a built-in 10in. speaker and may be operated from mains, battery or a car supply.

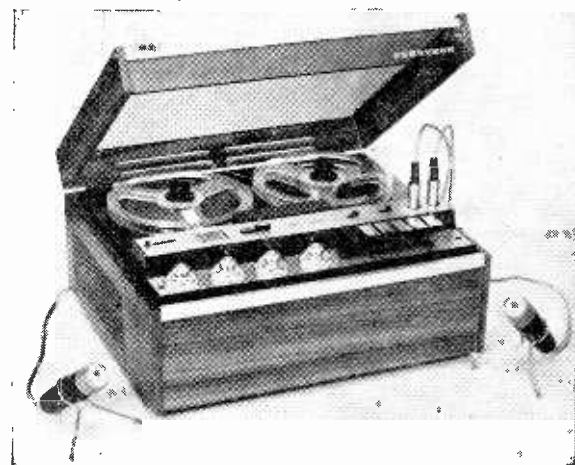Other features of the tape recorder market are an increase in the number of stereo machines available, an increase in the number of models incorporating automatic level control, and an increasing number of fully transistorised models.




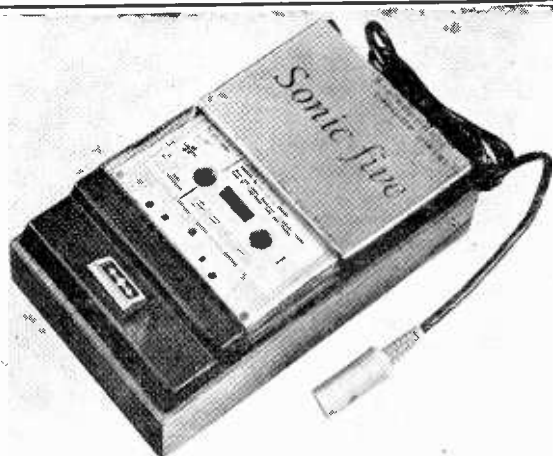Ferguson model 3232 transistorised stereo or mono tape recorder.



Van Der Molen *Sonic Five* stereo cassette player.

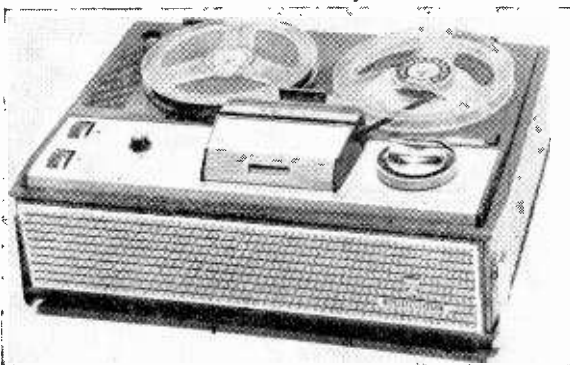Automatic level control is featured in the fully-transistorised Standard Models SR500 and SR550 and National Models RQ113S and RQ401S, the RQ113S being a two-speed portable model selling at £17 6s. 6d. Also shown by National was the




New from Grundig, the model TK145 featuring auto level control.

all-transistor mains/battery portable Model RQ102S and a combined radio and tape Model RQ120S.

New from Grundig is the four-track Model TK145, which closely follows the design of its sister machine, the TK140. The new model incorporates automatic recording level control which may be switched out to enable the machine to be manually controlled. The TK145 sells at 47½ guineas. Also new from Grundig is the TM340, a version of the TK340 for use in an existing Hi-Fi installation.

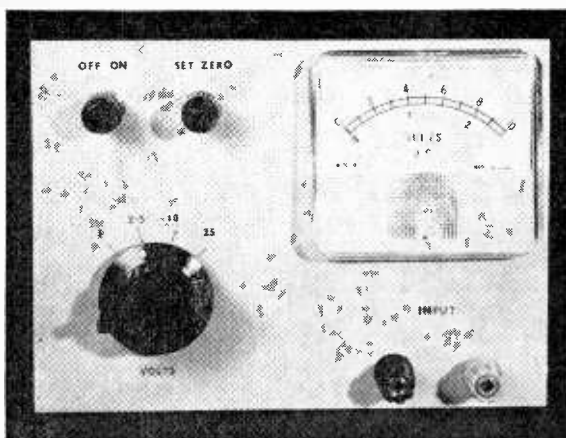The fully transistorised Ferguson Model 3232 provides stereo or mono recording and reproduction at 69 guineas, and is styled to match the Ferguson *Unit Audio* range. It provides 5W per channel.



two voltmeters

FOR THE
WORKSHOP

GRAEME LYNN

PART 2: D.C. VOLTMETER

THE comparatively recent introduction of silicon devices into most types of electronic circuitry has brought possibly one of the most simple measurement problems into the foreground.

Germanium transistors, with their relatively high leakage currents, raised little objection to being presented with the $20k\Omega$ per volt load that one expects from a quality, static voltage measuring instrument. Collector currents in the order of $1mA$ were considered a practical minimum for consistently stable operating points and the $100\mu A$ or so drawn by the external measuring equipment did not radically obscure, for all practical purposes, the voltage under measurement.

For most of us the change over to silicon transistors was a gradual process of exchange whereby silicon transistors in their early expensive days were used only where vitally necessary, usually for their low leakage qualities alone. Under these circumstances they still tended to be run at collector currents in the order of $1mA$, so that measurement techniques remained much the same. However as the economics of silicon semiconductor technology reached levels at which silicon devices could compete in price with other devices, original design

thoughts to take advantage of the low collector current operating feature of silicon transistors, resulting in increased voltage gain due to higher collector loads and the resultant higher input impedances, suggested circuits with collector currents in the order of $100\mu A$ or less. To measure relatively accurately these lower current sources in terms of the voltage present at the emitter, base and collector, the measuring instruments had to draw $10\mu A$ or less current.

The simple, yet effective d.c. voltmeter described here has an input resistance in the order of $0.5M\Omega$ for a full scale deflection of $1V$, thus drawing only $2\mu A$ from the circuit under test.

The circuit is shown in Fig. 6. Transistors $Tr1$ and $Tr2$ are connected in the long-tailed pair configuration and act as a differential amplifier, with the input applied between the two bases. With this arrangement in-phase input signals are effectively cancelled out and only push-pull (i.e. anti-phase) input signals are indicated upon the meter. This mode of operation minimises the effect of V_{be} changes with temperature, and the problem of leakage current at this type of sensitivity may be neglected over the range of $5^\circ C$ to $55^\circ C$ due to the in-

herently low leakage current of the BC108 silicon transistors used. The switch $S1a, b$ and c provides a coverage of $0-25V$ in four steps $0-1V$, $0-2.5V$, $0-10V$, and $0-25V$. On the $2.5V$ range the input resistance is in excess of $1M\Omega$, so that the meter draws only $1\mu A$ from the circuit under measurement. The circuit of Fig. 7, from which the final voltmeter was evolved, has a basic input sensitivity of $30mV$ but unfortunately the input resistance was too low to be of any practical


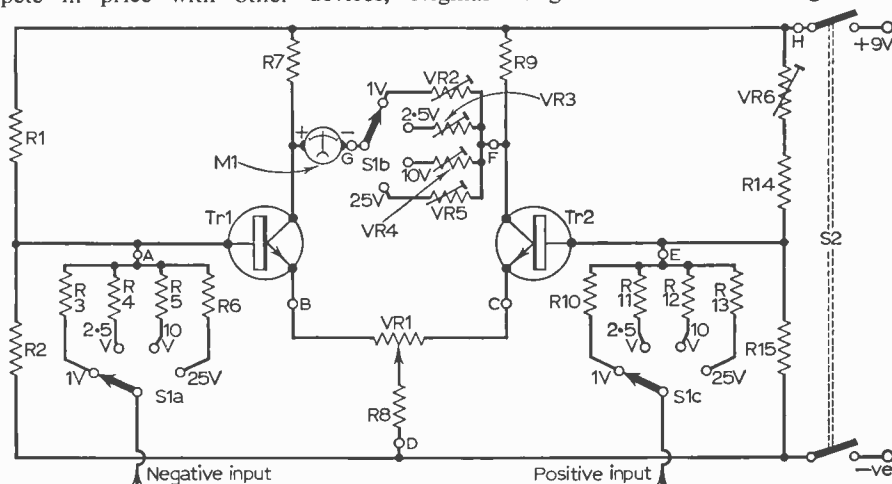


Fig. 6: Circuit diagram of the d.c. voltmeter.

use: hence the inclusion of the series resistors connected to S1 in the final design. A further advantage of the series resistors lies in the ability to measure sources of widely varying resistance without upsetting the d.c. characteristics of the voltmeter.

Circuit

The input voltage, isolated from the common line of the voltmeter, is applied to the bases of Tr1 and Tr2, the positive side to Tr2 base and the negative side to Tr1 base. This input voltage causes the collector voltage of Tr1 to go more positive and the collector voltage of Tr2 to go more negative. The combined voltage change at the collectors applies a voltage differential to the meter thus giving rise to a flow of current through the meter which is suitably calibrated to interpret this change as a reading of voltage. The resistors R3 to R6 and R10 to R13 inclusive provide the necessary reduction in the input voltage so that the transistors are not over-driven as the voltage increases, the variable resistors VR2 to VR5 being introduced to provide a means of making a final accurate setting of the voltage reading on each individual range. VR1 set zero control provides a means of setting the zero reading should the occasion arise but has been kept as small as possible to obviate the introduction of too much unbalanced feedback. The value chosen gives a zero variation of about half scale which is more than adequate for the purpose. VR6 is adjusted so that when the set zero control is in the mid-position the reading on the meter is about zero with the input terminals open circuit, and is included to overcome the out of balance due to h_{fe} variation between

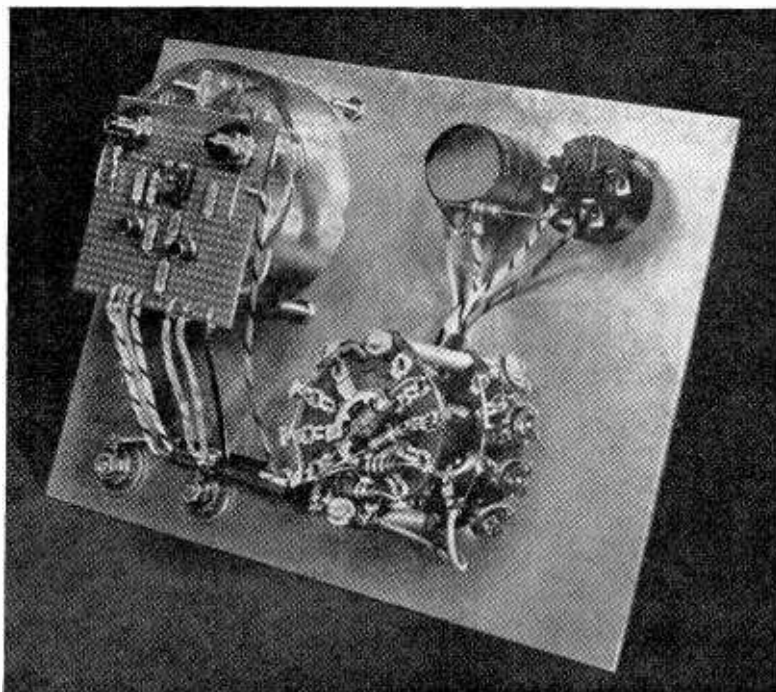

Rear view of the completed unit.

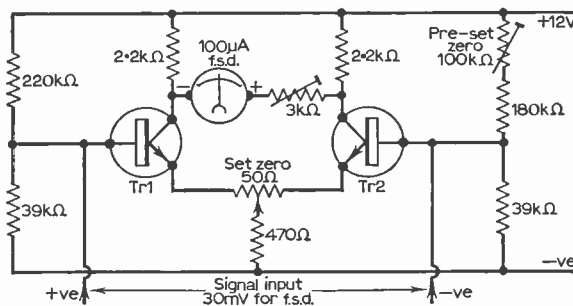


Fig. 7: Circuit from which the final design was evolved.

transistors. The circuit is compensated quite adequately against temperature variation. The collectors of Tr1 and Tr2 sit at approximately 7.5V in the quiescent condition, drawing about $680\mu\text{A}$ each, this current being determined by the biasing resistors R1, R2 and VR6, R14, R15.

Construction

The circuit layout is not at all critical so that the arrangement shown in Fig. 9 need not be adhered to. The board itself was cut from a piece of perforated board having a hole grid of 0.1 in., and 20s.w.g. tinned copper wire was used to form the connections between any components with short leads. The front panel was made from a piece of 18s.w.g. aluminium drilled at the required points (see Fig. 8). The meter was used as the

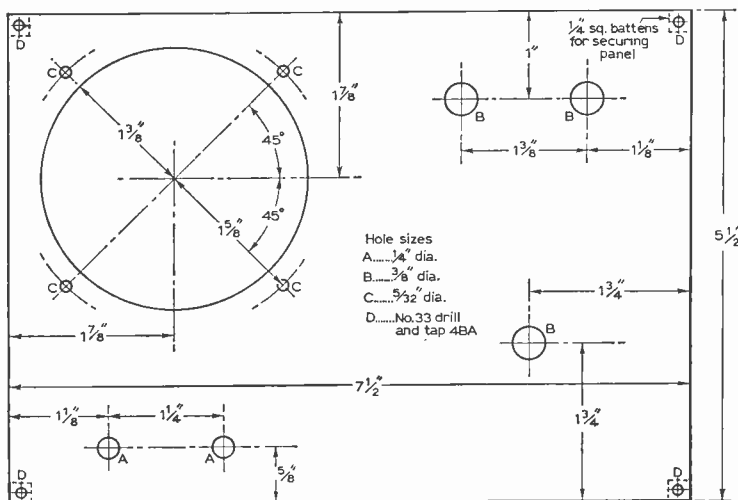


Fig. 8: Front panel drilling details as seen from back of panel.

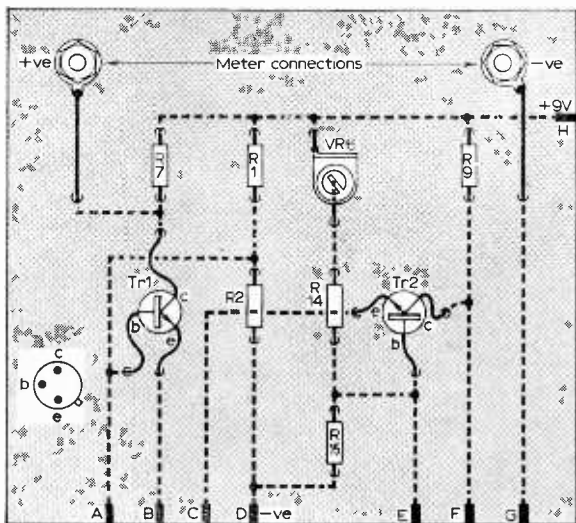


Fig. 9: Layout of the components on the board.

anchoring point for the circuit board, dispensing with the necessity to drill any further holes in the front panel. After all the required holes have been drilled in the front panel the finish was obtained by spraying with one of the many aerosol lacquers available in most hardware stores. When the lacquer was thoroughly dry the lettering was added by the now normal method of dry transfer. It is advisable to coat the lettering with the scratch proof varnish that may be obtained from the manufacturers of the transfers. As the unit is so simple there is no necessity to give any order of construction, all the parts being easily accessible no matter the stage of the construction.

Having ensured that the wiring is correct, switch on without applying any input voltage to the input

★ components list

Resistors:

R1	220k Ω	R9	2.2k Ω
R2	39k Ω	R10	270k Ω
R3	270k Ω	R11	560k Ω
R4	560k Ω	R12	2.7M Ω
R5	2.7M Ω	R13	5.6M Ω
R6	5.6M Ω	R14	180k Ω
R7	2.2k Ω	R15	39k Ω
R8	470 Ω		

All 5% high stability

Potentiometers:

VR1	50 Ω w.w.
VR2-5	All 3k Ω carbon
VR6	100k Ω carbon

Transistors:

Tr1 and Tr2 Both type BC108

Miscellaneous:

M1	100 μ A meter
S1	3-pole 4-way rotary switch
S2	2-pole changeover

terminals. The set zero control should be adjusted to approximately mid-way and then VR6 should be carefully adjusted until the meter reads zero. If the set zero control is now rotated in either direction the meter needle should swing alternately to either side of the meter zero. If this does not occur, check the circuit wiring again. After switching the function switch S1 to 25V a known d.c. signal of 25V should be applied to the input terminals in the correct polarity and VR5 adjusted so that the meter reads full scale deflection. This instruction can then be repeated for all the ranges by applying the appropriate full scale voltages to the input terminals and adjusting the related preset potentiometers. ■

EASILY-MODULATED, INFRA-RED RADIATION

Two new gallium arsenide diodes now available from Mullard emit near infra-red radiation when subjected to a voltage of about 1.5V. The radiation from the diodes, type CAY12 and 101CAY, is coherent and can be easily modulated simply by varying the diode current.

Maximum radiation from the diodes occurs at a wavelength of 0.9 μ m which is also near the peak of the response curve of the phototransistor type BPX25. Hence, one of the diodes and the phototransistor can be used in a very simple compact communications system, as shown in the diagram. A range of 100ft. can be easily achieved and this can be extended by improving the lens system.

This communication system could be used on noisy building sites to form a link between the cabins of tall cranes and the ground. The equipment could also be useful in crowded places where rapid, secret communication free of interference is needed between two points.

The high-frequency performance and high switching speed of these diodes make them suitable for use in a.m. or pulsed communication links. Because the emitted radiation is coherent, the diodes can also be used to start laser actions in other devices.

NEW MOULDED ADAPTABLE BOXES

Egatube Ltd., now have a range of P.V.C. Moulded Adaptable Boxes including sizes 3 x 3in., 4 x 4in., 6 x 4in. and 6 x 6in. in various depths. These boxes provide excellent instrument cases, etc., and can be supplied with flush or overlapping lids.

Special prices are quoted for large quantities. For details of M.A.B. Range, write to Egatube Ltd., St. Asaph, Flintshire.

FRANCE and CANADA AGREE


Never mind the rumpus between the Canadian and French Governments. Both countries are in perfect agreement about the usefulness of participating in the 1968 Electrical Engineers Exhibition at Earls Court, London, taking place from 27th March to 3rd April.

The French Government has decided to participate in the International Exhibition and has taken up 300 square metres of floor space. This is the first time France has decided to take part in the Exhibition.

Canada, too, has now taken up about 300 square metres.

Semiconductor AUDIO

R.LEYLAND

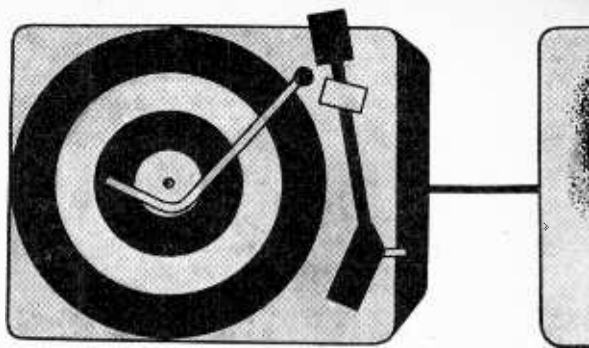

MOST transistor amplifiers, until comparatively recently, included transformers as an integral part of their output stages. An amplifier that does not incorporate transformers is more compact and can have an improved performance. Loudspeaker transformers were the first to show signs of being displaced. Finding a substitute for a driver transformer is more of a problem, and has resulted in circuits that depart considerably from those of earlier amplifiers. There is usually direct coupling, with feedback loops, and often complementary transistor arrangements. The overall action can be understood by considering each of the circuit details in turn.

Power transistors are able to supply large currents, and the power outputs required can be developed in loudspeakers of the usual range of impedance values without any need of a step-down transformer. There is no impedance-matching, and the loudspeaker impedance is chosen according to the power output, and the voltage of the amplifier supply. Providing that the permissible dissipation of the output transistors is not exceeded, by using too low an impedance, a different value of loudspeaker could be used, with little increase of distortion. Too high an impedance will reduce the output available, but this will also depend upon the sensitivity of the loudspeaker.

It is preferable to keep large direct currents out of the loudspeaker, to prevent a continuous displacement of the voice-coil, and this has led to the

single-ended type of push-pull output stage (Fig. 2). A direct coupled loudspeaker would connect on its other side to a centre-tap on the amplifier d.c. supply, but it has become more common to couple it capacitively as shown, and to earth the other side to the supply line. A capacitor value upwards of $200\mu\text{F}$ is usually necessary, depending on the impedance of the loudspeaker, and over $1,000\mu\text{F}$ when it is practicable to extend the low-frequency response.

The large surge of current that occurs in the loudspeaker when the amplifier is switched on can be avoided if two electrolytic capacitors are used instead of one. These in series across the d.c. supply provide at their junction point the equivalent of a centre-tap.

The single-ended output stage consists of a pair of transistors in series across the supply, biased usually so that the transistors amplify in turn on alternate half-cycles. This mode of working, designated Class B, gives a higher efficiency, and has been necessary because of the limited power capability of transistors, and also to conserve battery current in portable equipment. The complete signal waveform is reproduced at the mid-point between the transistors which feed the loudspeaker. Current is drawn from the amplifier d.c. supply.

On one half-cycle of the signal current is drawn from the amplifier d.c. supply through the upper transistor in series with the loudspeaker and capacitor. On the other half-cycle, the capacitor, like a floating battery, supplies a reverse current through the loudspeaker, and this current passes through the lower transistor.

Under no-signal conditions a small direct current flows through the two transistors in series, and their mid-point is stabilised at a voltage about half-way between the positive and negative of the supply. The small quiescent current is needed to produce a smooth transition at the cross-over point, i.e. with Class A conditions for small amplitudes of signal.

At maximum drive, the output potential can swing upward and downward to within about a volt of the supply lines. This saturation or knee voltage is lower for germanium than with silicon transistors, a factor of importance with low-voltage supplies. Silicon transistors also require a slightly higher drive voltage, but have the advantage of being able to function at much higher temperatures.

At maximum drive, the peak voltage across the loudspeaker will thus be about a volt less than half the supply voltage. Dividing the peak voltage by the loudspeaker impedance gives the peak current, and the peak voltage and current multiplied together give


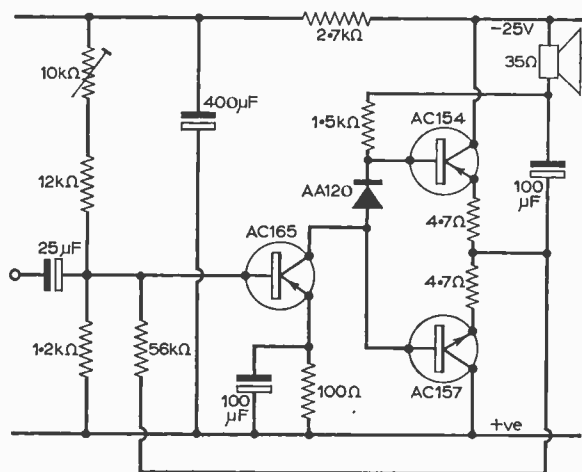


Fig. 1: Transformerless 1-watt amplifier driver and output stages (LP17 transistor package). The output transistors are mounted on a heat sink.

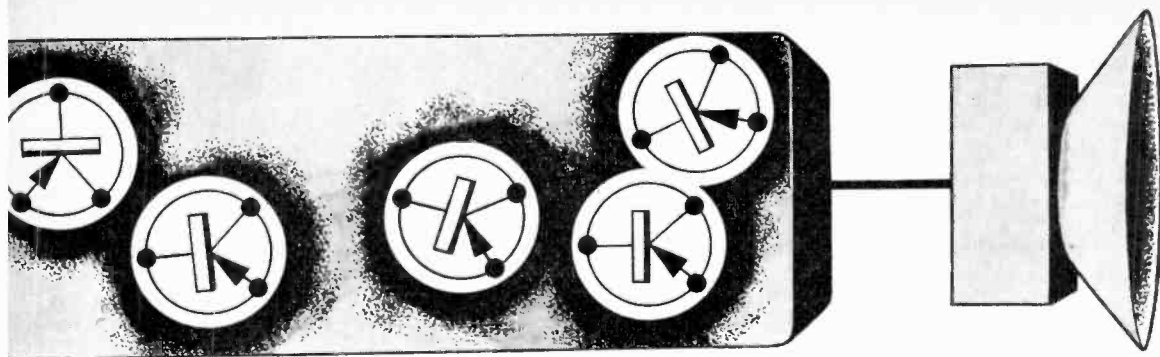

the instantaneous peak power. The average power is half of this peak power (for a sinewave) and is the nominal output on continuous sinewave. The average loudspeaker current is the peak current multiplied by $2/\pi$ or 0.636, and the d.c. required by the output stage is half of this.

In a more accurate assessment, the small voltage drop in the emitter resistors, and in the series resistance (often negligible) of the coupling capacitor, can be allowed for: also the quiescent current.

Some confusion can arise from an amplifier being given a music power rating that may be 20% or more higher than the continuous sinewave rating. The average current consumption on music is only about a third of that with maximum sinewave drive. Thus the voltage drop in the internal resistance of the amplifier d.c. supply is reduced, and a larger peak output can be obtained. Assuming an impedance of several ohms for an unstabilised supply, different ratings will therefore be obtained.

The original single-ended push-pull stage, Fig. 2(a), consisted of a matched pair of transistors of identical type, and required two separate inputs in antiphase, at different direct-voltage levels. For larger output powers, these two transistors may be preceded by others connected as emitter-followers to reduce the drive currents necessary.

It is possible to obtain the antiphase inputs from phase-splitters of types familiar in thermionic valve circuits, and a number of transformerless amplifiers have been developed on these lines. Direct coupling is only partially used in these amplifiers to avoid interdependence of the adjustments for quiescent current and voltage. It will be noticed that the

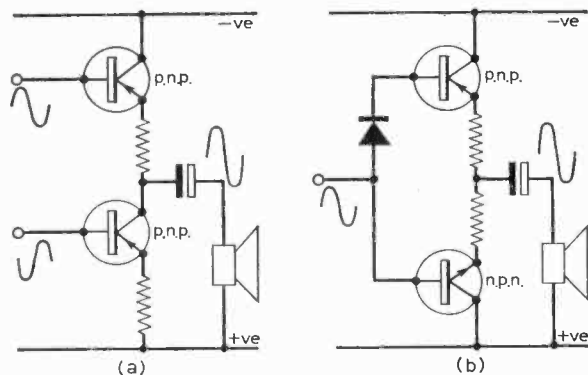


Fig. 2: Transformerless output stages. (a) Single-ended with two pnp transistors, requiring two anti-phase inputs. (b) Complementary pnp-npn circuit requiring one input only.

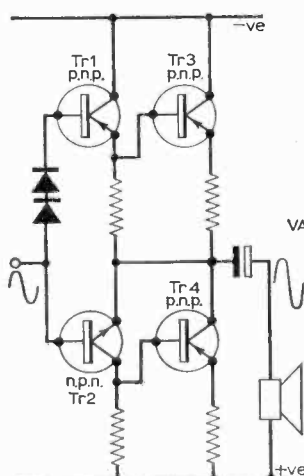


Fig. 3: Complementary driver stage feeding two pnp transistors Tr3 and Tr4 in the output stage.

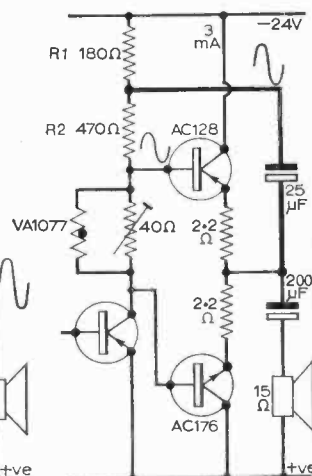


Fig. 4: Complementary output stage driven by a bootstrapped single transistor driver stage. Heavy line is bootstrap connection.

quiescent voltage depends on the upper transistor of the output stage, and the quiescent current on the lower transistor.


A complementary output stage, Fig. 2(b), consisting of a matched pair of transistors, an npn with a pnp one, is more convenient in that it only requires a single input. The existence of these two types of transistor, with opposite polarities, makes this possible, because an input half-cycle that produces conduction in the pnp transistor will cut off current in the npn transistor and vice versa.

It is however easier to match power transistors when both are of identical type. Returning to the original single-ended output stage, Fig. 2(a): for large output powers, the two transistors can be preceded by others to provide the drive currents necessary. These can be complementary transistors, enabling the circuit to work from a single input. The combined circuit, Fig. 3, is "quasi-complementary": the upper and lower sections look different, but have a performance on alternate half-cycles like the complementary matched pair of transistors in Fig. 2(b). Tr1 and Tr2 function as previously described. The output pair Tr3 and Tr4, however, both being pnp types, require input drive signals of the same polarity. For this reason Tr3 input is taken from the emitter circuit of Tr1 while Tr4 input is from Tr2 collector circuit.

—continued on page 526

simple TWO-METRE CONVERTER

J. OLIVER G8ANJ

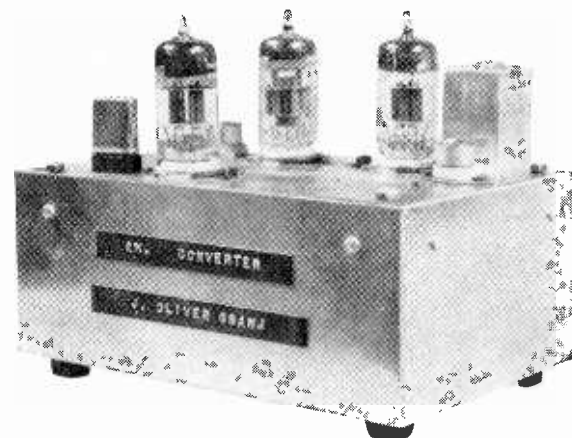

THIS unit was conceived as an introduction to v.h.f. practice, but it was so successful that it has become a permanent part of the station. The circuit is a collection of well tried and reliable elements and no originality is claimed except in the design of the unit as a whole. The entire device may be built for as little as £2 10s, although some constructors may have to purchase a new crystal which will increase the price to between £3 and £4. All these features make it an ideal constructional project for the beginner at v.h.f.

The entire circuit is designed around three double triodes. V1 contains the crystal oscillator and multiplier, V2 a cascode r.f. amplifier and V3 the mixer

and, if required, a cathode follower.

The crystal oscillator is of the Squier type, and uses a 46.7Mc/s 3rd overtone crystal. This crystal was used because it was to hand, but a fundamental type crystal with a frequency of 15.56Mc/s should work equally well, although the tapping point on L1 may have to be adjusted and the value of R1 reduced slightly. The oscillator signal is coupled via C2 to the grid of V1B which is a trebler stage giving an output in the region of 140Mc/s.

The output from V1B is inductively coupled via a link winding (L3, L4), to the tuned circuit in the anode of the r.f. amplifier, thence via C8 to the grid of the mixer V3A. The mixer itself is of the low

noise starved triode type, using half an ECC81, the 4.6Mc/s i.f. signal being developed across the tuned circuit L8, C10. The i.f. output is link coupled to Sk2 by means of L9 overwound on L8.

The r.f. amplifier is a conventional neutralised cascode stage using an E88CC v.h.f. double triode. The aerial signal is coupled from Sk1 to L7 which is self resonant with the input capacity of V2A at 145Mc/s. The output of V2A is coupled directly to the driver grounded grid amplifier V2B, L6 serving as a neutralising coil. The output from V2B is coupled via the self-resonant tuned circuit L5 to the mixer by means of C8.


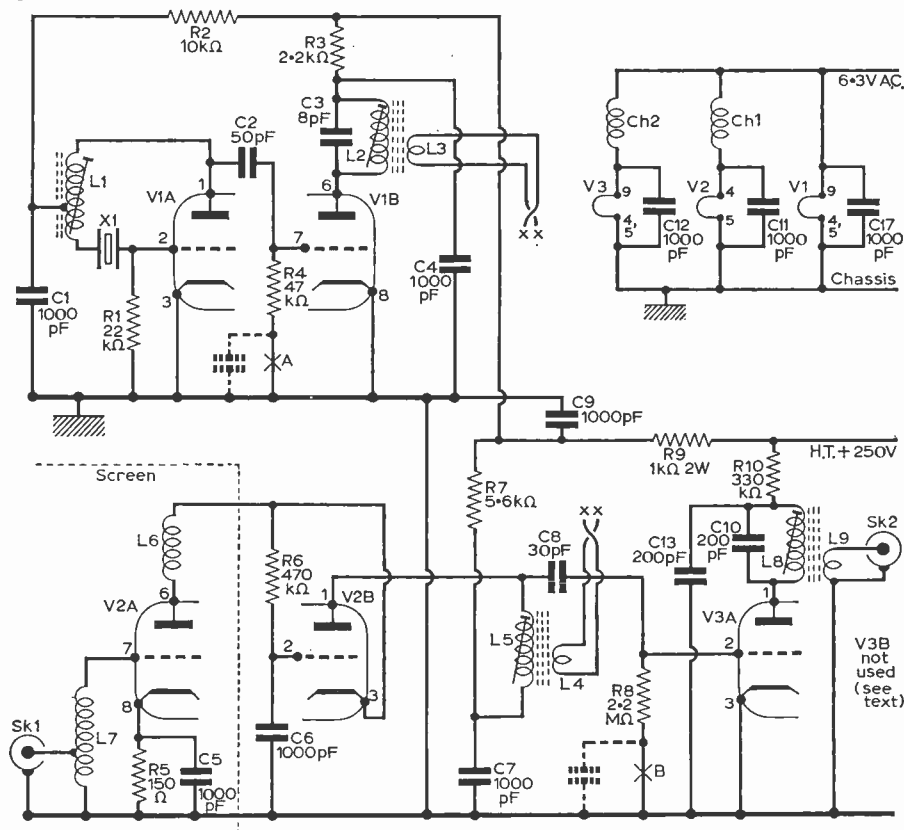
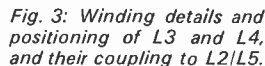


Fig. 1: Complete circuit diagram of the converter. Note that only half of V3 is used in this circuit.


All holes should just be drilled in the chassis plate (Fig. 4) and the screen fabricated from the same material as the chassis. It should be noted that if different types of coil formers are used for L1, L2, L5, L8, the chassis plan may have to be modified accordingly.

Construction should proceed logically, starting by soldering the screen to the chassis, then mounting the valve holders, coaxial sockets and the coil formers for L2 and L5 as these coils are easier to wind *in situ*. The remaining coils should then be wound and mounted in their respective locations. The remaining wiring may then proceed, starting with the heater circuit, followed by the signal circuits and finishing with the h.t. supplies. Care should be taken to ensure that the layout follows the original closely and that all r.f. leads are short and direct, as this will help to prevent instability. All soldered joints should be made with a hot iron and checked carefully afterwards as a bad connection will cause noise and/or spurious oscillations. Most of the wiring

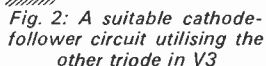

Now plug in V2 and feed the converter output into a suitable communications receiver. The receiver should be tuned to 5.0Mc/s and a signal from a signal generator or grid dip meter loosely coupled to the input of the converter. The signal source should be tuned about on 144—146Mc/s until a signal is heard in the receiver. L8 should be peaked for maximum output, then peak the slug of

Fig. 4: Sizes and drilling dimensions for the chassis. Details of the screen shown in the top left-hand corner.

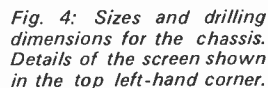

inductance of L6 for lowest noise.

The response curve of the prototype was checked on a Rhode and Schwartz polyscope type S.W.O.B., and the following figures might be of interest to constructors.

Gain 20dB
Bandwidth .. . 1.8Mc/s at 3dB
2nd Channel Rejection .. 17dB


The noise figure of the converter has not been measured, but the background noise on a weak signal, although appreciable, is not objectionable and the converter performs well when compared with more complicated devices. If no signal source is available for the alignment of the signal stages, there is an alternative method which, if carefully followed, should produce equally good results. The core of L8 should be peaked on noise with the receiver tuned to 5Mc/s, and then L5 should be peaked in a similar fashion, making sure that it is tuned to the h.f. side of the oscillator. The converter should then have an aerial (dipole or halo) plugged into Sk1 and the local beacon searched for (alternatively a local station may be used), and, when found, the signals may be re-peaked in the manner described previously.

The tuning of the i.f. coil may be found too sharp; if this is the case, try shunting the tuned circuit with resistors between 10k Ω and 47k Ω retuning in each case. This was not found necessary in the prototype, but some constructors may prefer the flatter response obtained.

Improving the converter

Although the circuit described above performs adequately, some simple improvements can improve its performance considerably. The first such improvement is the inclusion of a cathode follower output stage, utilising the unused triode portion of V3. Figure 2 shows the circuit of such a stage, which, as can be seen, is quite simple, and provided care is taken in the layout no problems should be encountered. The advantage of the cathode follower output is that the whole of the i.f. signal developed at V3A anode is transferred to the input of the main receiver, instead of being stepped down to provide the correct impedance match.

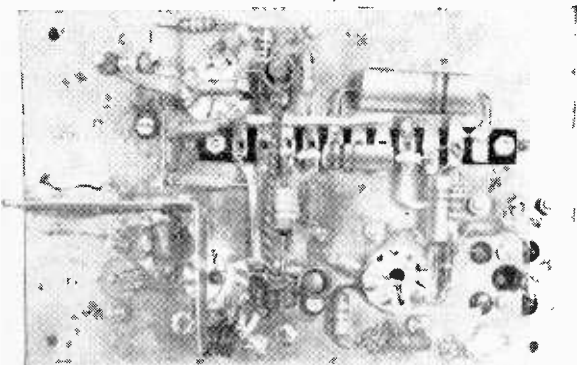The second, and simpler, improvement consists merely in adjusting the value of R10 until the voltage at V3A anode is approximately 60V with no signal present. At this voltage the noise from the



Photograph of the under-chassis wiring on the prototype. Note positioning of components to ensure very short leads. This is very important at the frequencies involved and should be observed.

★ components list

Resistors:

R1 22k Ω
R2 10k Ω
R3 2.2k Ω
R4 47k Ω
R5 150 Ω
R6 470k Ω
R7 5.6k Ω
R8 2.2M Ω
R9 1k Ω 2W
R10 330k Ω

Capacitors:

C1 1000pF ceramic
C2 50pF silver mica
C3 8pF ceramic
C4 1000pF ceramic
C5 1000pF ceramic
C6 1000pF ceramic
C7 1000pF ceramic
C8 30pF silver mica
C9 1000pF ceramic
C10 200pF silver mica
C11 1000pF ceramic
C12 1000pF ceramic
C13 200pF ceramic
C17 1000pF ceramic

Valves:

V1 ECC81
V2 E88CC
V3 ECC81

Crystal:

X1 46.7Mc/s
3rd overtone HC6/U

Coils:

L1 13 turns 38 s.w.g. enam. $\frac{1}{4}$ in. dia. former close wound tapped at 4 turns.
L2 3 turns 22 s.w.g. enam. $\frac{1}{4}$ in. dia. former $\frac{3}{8}$ in. long.
L3 } 1 turn 22 s.w.g. plastic covered wire on each
L4 } end of twisted pair of wires. See Fig. 3.
L5 3 turns 22 s.w.g. enam. $\frac{1}{4}$ in. dia. former $\frac{3}{8}$ in. long.
L6 5 turns 18 s.w.g. enam. $\frac{1}{4}$ in. dia. close wound self supporting.
L7 4 turns 18 s.w.g. enam. $\frac{1}{4}$ in. dia. close wound self supporting tapped at 1 $\frac{1}{2}$ turns.
L8 30 turns 38 s.w.g. enam. $\frac{3}{8}$ in. dia. former close wound.
L9 4 turns 28 s.w.g. enam. overwound on cold end of L8.
Ch1 } 10 turns 32 s.w.g. enam. wound on a 4.7k Ω
Ch2 } $\frac{1}{2}$ W resistor.

Table of values for Fig. 2

Resistors:

R11 470k Ω
R12 2.2k Ω
R13 220 Ω
R14 27k Ω 1W

Capacitors:

C13 200pF silver mica
C14 0.01 μ F ceramic
C15 1500pF ceramic
C16 0.01 μ F ceramic

Miscellaneous:

Three B9A valve holders; coil formers; wire; metal for screen, chassis etc.; tagstrip; crystal holder; nuts, bolts etc.; two co-ax sockets.

mixer when compared with the gain of the stage is optimum, i.e. if the voltage is reduced, the noise will be reduced slightly, but the gain will fall more rapidly. If the h.t. is increased the noise will increase out of all proportion to the gain.

Conclusions

When this converter was used together with an AR88D receiver, a transistor preamplifier and a simple dipole aerial located in a downstairs room, results have been quite satisfactory, stations over most of southern England have been heard. Any power supply is suitable that will provide 250V at 35mA and 6.3V at 1A.

It should be noted that if trouble with i.f. breakthrough is experienced, the chassis of the converter should be earthed to the receiver chassis with a piece of copper braid not more than 6in. long. ■

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

AFRICA

Algeria: *Radiodiffusion Television Algerienne* (21 Boulevard des Martyrs, Algiers) is now using 11,715 to carry the French service. Clear identification is given at 1600. This programme has also been heard around 1800 on 11,835. Fair reception of the Arabic service is possible in the evening on 11,735

Liberia: *Voice of America* relay at Monrovia (Washington D.C. 20547, USA) has a special programme of news items in Swahili, Arabic and English for East and Central Africa from 1530-1600 on 21,560. This station can also be heard at fair strength at 1830 in French on 11,960.

Nigeria: *Nigerian Broadcasting Corporation* (Broadcasting House, Lagos) seems to be experimenting with different frequencies and now uses 15,330 for its 1700-1900 English Tx.

South Africa: *Radio South Africa* (P.O. Box 4559, Johannesburg) now transmits in English as follows: Mondays to Saturdays 0415-0427 15,220/11,900; 0430-0442 17,805/15,220; 0500-0512 11,900/9,525; 0515-0527 21,535/17,805; 0645-0657 17,805/15,220; daily 1000-1455 21,535/17,805/15,270/11,900; 1600-1655 15,220/11,900; 1700-1755, 1800-1855 and 2100-2155 21,535/17,805; 1900-1955 (UK Tx) 21,500/17,790; 2330-0325 11,875/9,705.

MIDDLE EAST

Saudi Arabia: *Saudi Arabian Broadcasting* (Ministry of Information, Airport Road, Jeddah) has an English by Radio transmission at 1900-1930 on 9,670/11,855/15,150.

Syria: *Radio Damascus* (Ommayad Square, Damascus) has Arabic from 1500-2200 on 17,860. From 1800 15,165 is used also. Between 2230 and 0100 both channels are used for Spanish, Portuguese and Arabic transmissions to South America.

ASIA

India: *All India Radio* (P.O. Box 500, New Delhi) now uses 15,080 from 1745-2045 for English to Africa. Other frequencies are 9,690/2045.

NORTH AMERICA

Canada: *Canadian Broadcasting Corporation* (P.O. Box 6000, Montreal) appears to have moved from 15,320 to 15,325 for its afternoon transmission to Europe. Reception is fair as it is on 21,595 and 17,820. The other frequencies used. Interference from Radio Moscow spoils the 17,820 signal.

USA: *Radio New York Worldwide* (485 Madison Avenue, New York, N.Y., 10022) now transmits in English from 1600-2200 on 21,530/17,845/15,440; 1600-1900 17,730; 1900-2200 17,760; 2000-2200 11,970.

Voice of America (United States Information Agency, Washington, D.C., 20547) now has English to Europe 0300-0730 on 3,980/5,965/5,995/7,200/7,270/9,540/

9,635/9,740; 0500-0730 6,040/1,196; 0600-0730 11,705; 0300-0600 11,790; 0400-0730 11,835; 1400-2330 (2345 Sundays) 3,980/5,965/15,290; 1400-2000 11,770; 1400-2215 15,205; 1400-1800 17,855/17,890; 1400-1600 21,455; 1400-2015 21,600; 1600-1800 and 2100-2330 (2345 Sundays) 1,196.

EUROPE

Austria: *Osterreichischen Reudfunk* (P.O. Box 700A, 1040 Vienna) gives fair reception on 11,900 at 1230-1300. Frequent identification in German, French, English and Arabic. Interference comes from Radio Moscow's home service.

Bulgaria: *Radio Sofia* (4 Boulevard Dragen Tsankov, Sofia) excellent reception after 1030 in Turkish on 11,955. At 1100-1110 there is news in Bulgarian. Excellent reception of the Turkish programme is also given from 1000-1100 on 11,765.

Czechoslovakia: *Radio Prague* (Prague 2, Vinohradska 12) now using 15,285/17,840/21,735 for its 1530-1630 English transmission. 17,840 is now being used in addition to 5,930/7,345/11,990/15,345 for the 0330-0430 transmission.

Denmark: *Radio Denmark* (Radio House, Copenhagen V) now airs its Far East transmission on 15,165 half an hour later at 0730-0845. English is at 0815.

Finland: *Radio Finland* (Unioninkatu 16, Helsinki) now has an English news bulletin at 1815 on 9,555/11,805/15,185.

France: *O.R.T.F.* (Maison de l'O.R.T.F., 116 Avenue du President Kennedy, Paris 16) now transmits in English at 0015-0030 on 7,160/9,500/11,725B/15,445B; 0615-0630 11,725B/15,445B; 1100-1115 17,850/21,650; 1300-1330 15,445B/17,720/17,740/21,500B/21,525/21,580; 1915-1930 11,930B/15,190B/15,245/21,580 (B=Brazzaville relay).

Germany: *Deutsche Welle* (Bunderstrasse 1, Postfach 344, Koln) now transmits in English: 0845-0940 15,275/17,845/21,650; 2110-2200 7,275/9,675; 0300-0340 9,530/11,945; 1550-1620 15,275/17,880; 0600-0630 11,785/15,275/17,845; 1100-1115 11,930/15,275/17,875; 2145-2205 11,925/15,275; 0130-0250 9,640/11,945; 0445-0545 9,735/11,945; 1045-1055 11,905/15,315; 1900-1910 15,405/17,785.

Radio Free Europe (1 Englischer Garten, Munich) has been noted recently as follows: 21,720 Czech at 2000; 21,620 Polish 2030; 21,520 Czech 1800; 17,835 Czech 1500; 17,805 Polish 1545; 17,770 Hungarian 1045; 15,355 Hungarian 1700; 15,215 Romanian 1500; 15,170 Hungarian 1800; 15,145 Polish 2045; 15,115 Bulgarian 2030; 11,895 Polish 1530; 11,855 Romanian 1545; 11,815 Hungarian 1830.

Greece: *Radio Athens* (Mourouzi Street 16, Athens 138) now has English at 1340-1350 on 7,295/9,605.

Vatican: *Vatican Radio* (Vatican City) now has English to Europe at 1400 on 9,645/11,740/15,120/1,529.

ANOTHER cool cool month for ten metres I'm afraid. Still the 1-97Mc/s of nothingness persists up there. Many people who sent in logs complained of hearing exactly the same nothing too, although some did confess that one or two Europeans and the occasional W did pop up now and again. Trouble is they popped down again just as quick. Any sunspot experts in the audience care to predict what will happen in the next few months?

FIFTEEN

Let's look at the band that has shown most improvement during the past month.

L. Rowland (Cheshire), Trio 9R—59, 150 ft. end-fed logged—CE6DC, CE8DV, CN8BV, CP1AR, CP6HB, CR6JW, CX9AAN, EL2DD, W6THY, WB6KOH, XW8EZ, YA1DAN, YS2CEN, YV1PP, YV4QG, ZC4MO, ZD8RB, ZS4PU, ZS5KF, ZS6BFI, 4U1ITU, 4X4IL, 5A1TV, 5Z4JW, 9G1BF, 9J2AB, 9L1GB, 9Q5FF, 9U5SK (Burundi), 9V1NP, 9X5AA (Rwanda). All these were on s.s.b.

D. Henbry (Sussex), has just acquired an HA-500 but says it's very fussy about antennas. On fifteen s.s.b. David heard—CE6FK, CEØAE, CX1AAC, CX7AP, HC1KS, HI8XHJ, HR1KAS, JA1CB, JA3COX, JH1BF, KV4FA, MP4BBA, VP2GAR, VP6WR, VS9MB, VU2BK, WA7BEV, YA1FV, YS1RTV, ZE2JE, ZS6AKC, 5N2AAN, 5U7AK, 6O1GB, 8R1C, 9G1GQ.

G. Richards (Isle of Wight), has a GEC 5-valve superhet with an indoor antenna—12 ft. of wire. He managed these on 15 a.m.—CP1LE, CT2AB, EP1LGM, I1BEG, K2ONO, K2VFB, K4YMJ, UB5FG, W2AFB, WA3GMN, W4DNY, W7NUA, W9RHZ.

M. Joyce (Birmingham) RA—1, 12 ft. whip sent in this log but didn't say what mode—CR6DA, CT1BH, DL, DJ, DM, EL9A, ET3WH, F, G, GM, GW, HB9ACG, HI6HJ, HI8XHJ, HP3MC, I, IT1QR, JA1LZP, JA1EBU, JA3EED, KA2VT, KP4AST, KV4CX, KZ5WL, LA, MP4BGE, MP4TBA, OA5HGL, OD5BZ, OE, OH, OZ, PY5IM, PZ1BO, SM, SV1CW, UB5FJ, VE2QS, VE3NB, VU2VKZ, W, YN4WD, ZB2AL, ZC4MO, 4X4KX, 5A1TV, 5Z4JW, 9G1BF, 9V1NV.

TWENTY

Back to the favourite, if you can't hear it on twenty retire to a monastery. Practically everywhere from Europe to the Pacific is on at one time or another.

L. Stockwell (Essex), BC342, 20 ft. wire in the bedroom heard—CP5SK, CT1NL, EA3HI, G4JG, HV3LJ, HB9LS, LX1BA, SV1CC, VE1EI/P, WB3OSW, W4AJP, W8BMK, 4X4FQ.

P. Ridley (Cheshire), H.R.O., 140 ft. long wire switched in his trusty b.f.o. and logged these on s.s.b., CE3ZN, CP1EE, CR6IV, EL2AC, EL3C, EP2BQ, ET3USA, F3CC/FC, HK4TA, HR2VFB, HR6EB, HS4AK, HV3SJ, I2LAG??, KL7MF, KP4AKB, KP4BCL, KR6MB, KR6USA, KV4EU,

M1B (San Marino), OA4MX (Peru), PX1JS, PZ1BW, TF3EA, TI2ES, TI3TS, VK2WD, VK2AVA, VK3BM, VK3HA, VK3IP, VK3XO, VK5TJ, VK6GP, VP6WR, VP7EG, VQ9TC, YA1HD, ZL1KG, ZL3UY, ZL4BX, 4X4FQ, 4X4TP, 5Z4IW, 6Y5GG, 9V1NO, 9V1NQ, 9V1MT.

L. Bousher (a place in Wales I can't pronounce), R1155, 50 ft. long wire got these on s.s.b.—BY2PJ, CE3DM, CE4FY, CN8BV, CP5BQ, CP5AD, HI8LAL, HK4KL, HV3SJ, IS1SCB, JA1AEA, KP4AST, KP4LA, KZ5CZ, KZ5WI, KZ5HI, LU3MBQ, LU3FBT, LU8DKA, LU9DM, OA4XX, OA6AD, OA6BL, PJ2AQ, PY2DVR, PY3BXW, SVØWL, TI2PAS, TL8DL, TF3EA, UQ2KBH, VK3PG, VP1KL, VP2AA, VP6WR, VP8IU, VS9ALV, VU2BN, VU2WB, XW8AX, YV5AYB, YV5BPJ, YV7AV, ZC4AK, ZE1AE, 3A2CP, 3C1AE, 5Z4KN, 6O1GB, 8R1C, 8R1S, 9K2AB, 9G1TV, 9M2NF. Cor, how much do you want for that 1155 OM?

EIGHTY AND FORTY

Two brave r.f.-gathering warriors sent in their conquests this month. These are the bands where they separate the men from the boys—so I'm told.

C. Lewis (Devon), R1155A, 120 ft. long wire, heard this lot on a loudspeaker when tuning around 7Mc/s—CN8AW, CN8BV, DJ8SW, F5LA, I1KDB, IT1ZGY, PAØAB, SM4MI, UA9EU, VK2ABA (Wow!), ZD8RB, 9H1AM, 9M2DW. On 3-5Mc/s—DL6FU/M, F2WW, K2BXV, K4DPQ, ON4TT, PAØLM, VE2ED, VE2BF, W3EBK, W3FBB, W3KQY, W4FFO, W4UFO.

P. Baker (S. Wales), HE30, 100 ft., end fed sums up the bands by saying: 1-8—Full of G's, G mobiles (I heard that), GW, GM and E14AN on s.s.b. 3-5—Full of QRN and QSB. 7-0—Some very good openings after dark. 14-0—S. America and the Caribbean area very plentiful from 0700—0830. 21—Half the time dead as a doornail, the other half wide open. 28—Useless.

Paul listened on forty s.s.b. between 2200 and 2400 for—CN8AW, DJ8RR/M, EA6BH, EA8EZ, HI8XAL, LX1WR, OX3BS, OX3WX, PY1CWA, PY4ND, PY7AKQ, PZ1CF, VS9MB (Maldives Is.), ZB2AP, ZC4MO, ZD8RD, ZS5KY, 4X4BK, 9M2DW, 9V1VT.

CONTESTS

Eyes down, here comes the contest list for the keen types for October. If you are contest-minded then this month will drive you up the proverbial creek. Knee-deep in contests and some of them all on the same day too. October 7th/8th—1296Mc/s contest, RAEN contest, VK/ZL contest, WADM contest. On 14th/15th—RSGB 21/28Mc/s contest, hope ten is fully recovered by then, 14th—15th, 432Mc/s contest, VK/ZL contest phone section, 15th—D/F National Final. 21st/22nd—CQ WW DX contest, 28th/29th—RSGB 7Mc/s DX contest (phone section) good one to get your feet wet on forty.

That's the story for this month, deadline for logs is, as usual, the 20th.

INCREASE YOUR KNOWLEDGE



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES


CHOOSE THE RIGHT COURSE FROM
RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING,
ELECTRONIC TECHNICIANS, SERVOMECH-
ANISMS, TELEMETRY, CLOSED CIRCUIT TV,
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns'. Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

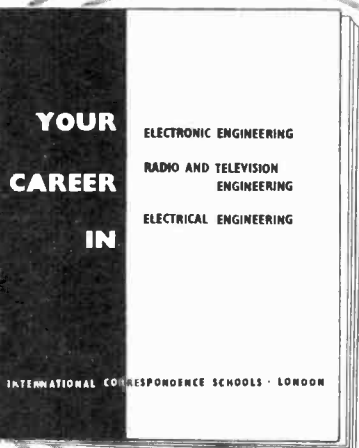Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor Portable, Signal Generator, Multitester and professional type Valve Voltmeter. At the end of the course you have valuable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio and Electronic Courses open a new world to the keen amateur.



THERE IS AN **ICS** COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio television and electronics **PLUS** details of over 150 specialised subjects.

PLEASE SEND FREE BOOK ON.....

NAME


ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 17, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
11/67

Special next month!

BUILD THIS LOW-COST HI-FI

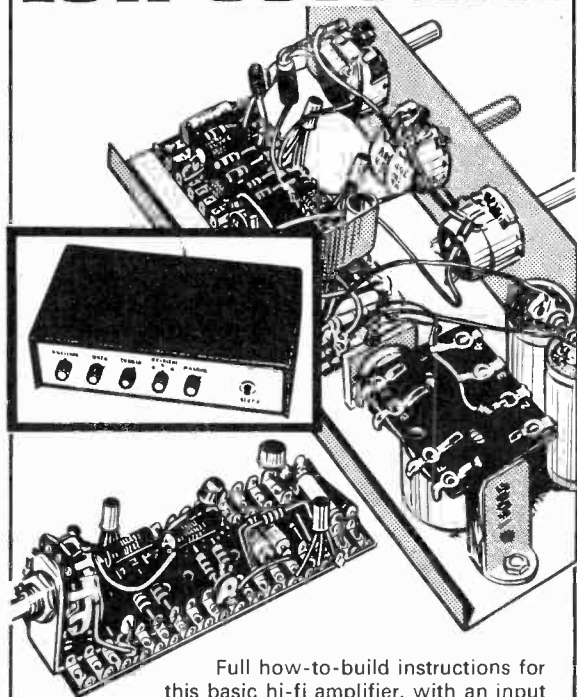

Full how-to-build instructions for this basic hi-fi amplifier, with an input sensitivity of 3mV and an output of 1 watt 30–50,000 c/s, are included in the November PRACTICAL WIRELESS. A suitable pre-amp and a companion power amplifier, giving 5 or 15 watts into 15 or 3 ohms respectively, are also detailed, and the feature includes power circuitry for all units.

Other Outstanding Features

I.C. f.m. Tuner built on a printed circuit board.

Midget Transistor Transmitter using only 2 silicon planar transistors.

Repairing Moving Coil Meters Discusses typical faults and their remedies.

PRACTICAL WIRELESS

December issue on sale Nov. 3rd
RESERVE YOUR COPY NOW!

THE MW COLUMN

ONCE again the main m.w. DX season is with us, although signals may be weak for a while. But welcome to our old friends and to newcomers in this side of DX listening.


Conditions have been quite good throughout the summer with many "deep" South Americans—Uruguay, Paraguay and Ecuador are now coming through. As we get into darker months, conditions generally will improve but the South Americans may diminish somewhat. By now, Asia should be putting in an appearance (try afternoons from 1500 and evenings 2100-2330). From October they *may* be heard from as early as 1300 but at the time of writing I have had no luck with the Chinese stations which often peak around 2130. A few North Americans can be heard after the French stations sign off at 2300 and although they are very weak now, they should be getting much stronger by mid-October.

At the time of writing nothing very exciting has been logged, only run-of-the-mill items. The best signals have been *Radio Americas*, Swan Island (1157), China (1523), WCAU Philadelphia (1210), St. Pierre et Miquelon (1375), WBT Charlotte (1110), YVQJ Barcelona (1080), WHN N.Y. (1050), WBZ Boston (1030), KDKA Pittsburg (1020), CFRB and WINS (both 1010), CHNS Halifax (960), CKNB and CHER (both on 950), CMB Montreal (940), CJON St. Johns (930), WGY Schenectady (810), CFDR Dartmouth (790), WABC N.Y. (770), WAVY Portsmouth (1350), WLCY (1380), WNJR Newark (1430), WMEX Boston (1510), WKCY (1530), WHAM Rochester (1180), WNEW N.Y. (1130), CJCH Halifax (920), WWL New Orleans (880).

Conditions have not been very good during the last few nights before writing this column but they should start picking up by the time you read this. We ask readers to listen (particularly during October) for stations on the West Coast of North America which, if they appear, will come through between 0300-0600. Key stations are KING Seattle on 1090 and KOMO Seattle on 1000. When trying for KOMO you will experience QRM from WCFL Chicago and the Mexican station also on the same frequency. One technique on possible sessions is to stay tuned to WCFL and wait for it to fade down, when KOMO may appear. Dates, times, and general notes on *any* West Coast stations received will be greatly appreciated.

Many readers must have built the loop aerial described last season—at least I have sent out well over a hundred copies of the instructions. So we are expecting good support from you this year in sending along news of stations heard and other m.w. information. With the more unusual stations, times are very important as are signal reports and other notes. Let's make this year a bumper one for DX.

Alistair Woodland

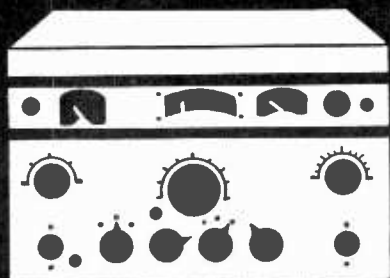

GUIDE TO SURPLUS COMMUNICATIONS RECEIVERS

K.ADKINS

PART 4

The PCR Series

The PCR was manufactured in fairly large numbers for the British Army by Pye and Philips. It was designed for the reception of broadcast stations, rather than for communications purposes, but has features which make it suitable for reception on the amateur bands.

Four versions exist: they have most features in common. The PCR is probably the cheapest, general coverage, ready-to-use communications receiver available. Unfortunately it does not have a b.f.o., and is therefore unsuitable for c.w. and s.s.b. reception.

The PCR has 6 octal valves, including an r.f. stage, two i.f. stages, and a 6V6 output stage. It has a 180 degree illuminated and calibrated dial, with flywheel tuning. Other panel controls are audio gain, aerial trimmer, tone control, and output sockets for headphones. It has an internal 5 inch loudspeaker, although certain versions do not. The overall sensitivity is from 1 to 2 μ V. Signal to noise ratio is 10dB at 6 μ V.

The frequency ranges are 850-2,000m, 200-500m and 6 to 18Mc/s. It has a black metal cabinet, size 17in. x 8in. x 10in. An external power unit is required, and must supply 250V d.c. and 12V. External power units are available for a.c. mains or for 12V car battery. In addition, some receivers were fitted with internal a.c. mains power units.

Modifications: The PCR operates perfectly satisfactorily without modification. However, the obvious modification is to add a b.f.o. An "S" meter would also be a worthwhile addition for the serious user.

Availability: PCR receivers first came on to the market in large quantities in late 1961, reconditioned by REME and in very good condition indeed. They were sold for a standard price of £6 19s. 6d., less power supply. Mains power supplies were an extra £2, and either the original external power unit was provided, or the receiver could be fitted with an internal mains supply for the same price. By late 1963 all the PCR's of the 1961 release had been sold. No manuals were issued.

PCR1

This version has a slightly different frequency range, as follows:— 860-2080m, 190-570m, 5-6 to 18Mc/s. It contains an internal speaker, like the PCR.

Availability: The PCR1 was not released with the PCR model in 1961. The first PCR1's came on to the market in the summer of 1966 at a price of £8



Photograph by courtesy of G. W. Smith (Radio) Ltd.

19s 6d., for grade 2 condition. Some have been available recently at a similar price. External power units were £2 for the a.c. version and 15s. 6d. for the 12V d.c. version. No PCR1 manuals have been issued.

PCR2

This is also similar to the PCR, but the frequency range is:— 850-2,000m, 200-550m and 6 to 23Mc/s. It does **not** have an internal speaker.

Availability: The PCR2 came on to the market at the same time as the PCR in a slightly inferior condition, although still in grade 2 category. They sold at between £5 and £7, without power units. Both external and internal power units were available on the same basis as for the PCR. The PCR2 was available until 1964, although it is believed that a very small number was released during late 1965. They are not available at the time of writing. PCR2 manuals are not obtainable.

PCR3

The PCR3, otherwise similar to the PCR, has a frequency range of 200-550m, 2-5-7Mc/s, 7-23Mc/s. It does **not** have an internal speaker (*photo above*).

Availability: The PCR3 first appeared in 1963 in grade 2 condition, at about £8, without power supplies. Power supplies were available.

During the summer of 1966, a new batch of PCR3's were released in grade 1 condition, at £8 19s. 6d., without power supplies. Power supplies could be fitted internally for £2 extra. 12V d.c. power units were available at 19s. 6d. Some PCR3's have been available recently at a similar price. PCR3 manuals are not available.

The R107

The R107 was first manufactured in large numbers during the last war for the British Army. It is popular with short wave listeners, being completely self contained. In fact, if one has a maximum of £15 to spend, the R107 is often the obvious choice. It performs very satisfactorily on the l.f. bands. The main drawback is its size and weight "built like a battleship and looks like one!" The receiver was built to withstand rough conditions and is very reliable.

The R107 covers 1.2 to 17Mc/s in three bands. It contains 9 valves, including one r.f. stage and two i.f. stages. Sensitivity is from 2 to $6\mu\text{V}$. The internal power supplies are for either 100/250V a.c. or 12V d.c. There is also a built-in speaker. Outputs are available for headphones and line.

Bandwidth is switched for either 3kc/s or 7.5kc/s. There is also an audio filter. Provision is made for dipole or open wire antennae. R.F., i.f. and audio gains are provided. The a.g.c. is switched, and there is a b.f.o. control. A test panel is provided on the front panel for the checking of certain internal circuits.


Inside the set, there are three main replaceable chassis units—r.f., i.f. and audio; and power. These units have been obtainable separately on the surplus market. The overall size of the receiver is 24in. x 13in. x 17in.

Modifications: The R107 operates perfectly satisfactorily without any modification at all. In fact, it is rather difficult to modify. Most amateurs would desire an "S" meter, and there exists a simple modification for fitting one.

Availability: R107 receivers have been quite easy to obtain, all in either brand new or very good used condition. They were more plentiful during 1960 to 1962, when they were selling at £12 to £15. Since 1963, they have been less easy to obtain, but grade 2 receivers can still be obtained occasionally for about £14. Those sold earlier can now be acquired on the secondhand market for about £10 or a little more.

During 1963, a quantity of replaceable chassis units, (the r.f. unit and the power unit) were placed on the market in brand new condition for about £2 each. These have not re-appeared since. Other spares, such as i.f. transformers, have been available in the past. The R107T, a superior version, was not made in large quantities but they can be obtained secondhand.

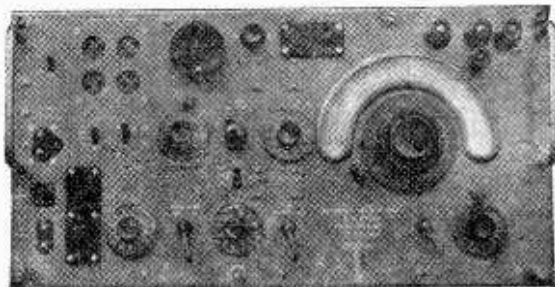The R107 manual was not included with the receiver when sold brand new, but it has been pos-



Photograph by courtesy of Messrs. A. J. Thompson.

sible to obtain them from the West End, and there are probably quite a large number in amateur hands.

The R109

The R109 was manufactured for the British Army and is little known, although it was made in fairly large numbers. Most of the R109's that exist were released several years ago, and the receiver is rather scarce nowadays. The main features are a frequency range of 2-8Mc/s, an internal 6V d.c. vibrator pack and an internal speaker. A variation, the R109A, has a frequency range of 2-12Mc/s.

Modifications: Faced with the lack of information on this receiver it is difficult to suggest modifications. However, from a general impression, it would seem that the receiver is not suitable for serious use on the amateur bands.

Availability: R109's were available before the period covered by this report in grade 2 condition until the middle of 1960 for about £4 and R109A's for about £5. It is believed that a few R109's in grade 3 condition were available for £2 10s. at the end of 1960.

Between the end of 1961 and the beginning of 1963, R109's were again placed on the market, presumably for the last time. R109's in grade 1 condition, with a set of spare valves, could be obtained for about £7; and the R109A, in similar condition, for about £8. None have been available since.

R109 manuals probably exist in small numbers, although they would be very difficult to obtain as the R109 itself is very rarely used by the amateur band listener.

to be continued

PRACTICAL TELEVISION

★ **CO-CHANNEL INTERFERENCE:** Because the number of TV channels is limited, it is necessary for more than one station to work on the same channel number and co-channel interference can be caused. This problem will become even more acute as further u.h.f. channels are exploited. In this article, methods of combating this type of interference are illustrated and brief details of a filter unit are given.

★ **HELICAL AERIAL:** Used on the continent for u.h.f. reception, this unusual design of aerial is primarily intended for indoors, but there is no reason why an outdoor version may not be constructed to improve reception.

PLUS ALL THE REGULAR FEATURES WHICH GO TO MAKE UP THIS FACT PACKED MAGAZINE.

on sale November 20th—2s


THE STAR ROAMER SHORT WAVE RECEIVER-KIT

*Longwave, standard
and three shortwaves*

*S-meter indicates
optimum tuning*

*Switchable automatic
volume control*

Antenna trimmer

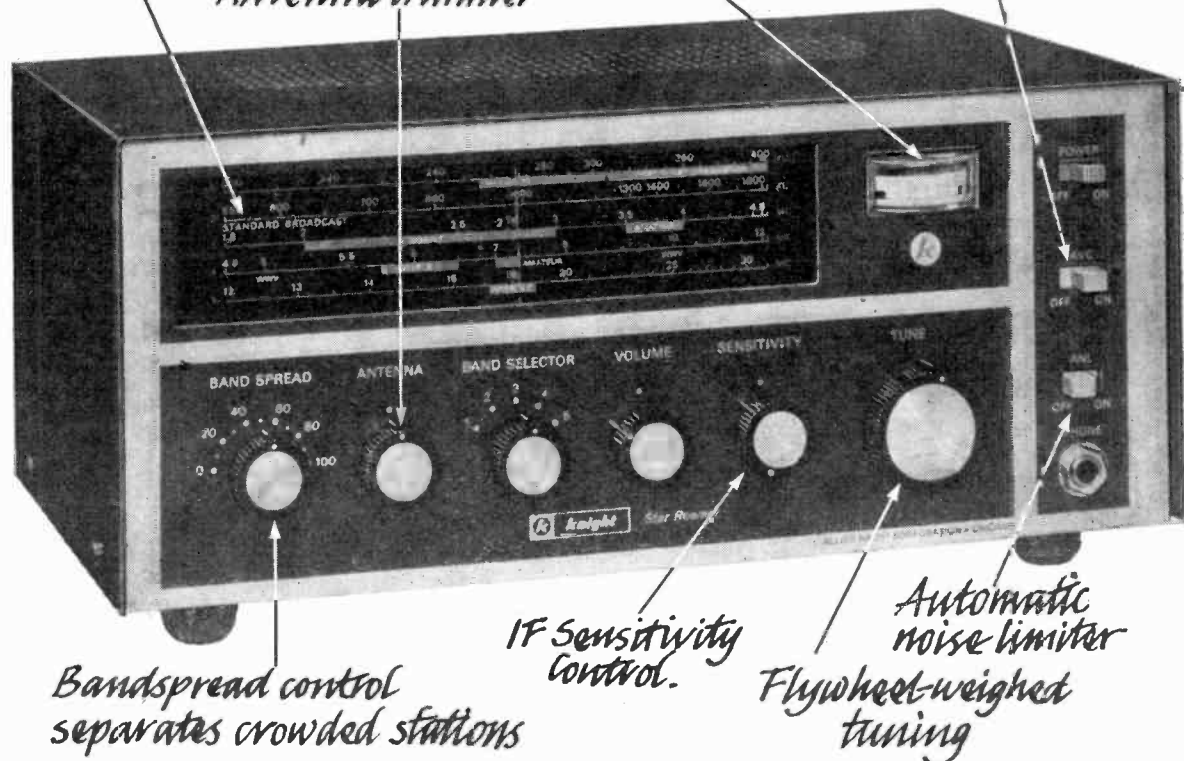

—JUST LOOK AT THE FEATURES

What better introduction to the world of short wave listening than the Star Roamer—a kit that's instructive, fun to build and that gives perfect reception on stations right round the world. Listen to the news as it happens, where it happens—distress calls, weather reports, ham conversations, etc., etc.—they all come in and stay in loud and clear on the Star Roamer. Plus, of course, perfect AM for standard broadcasts. Kit building saves you money, but with Knightkit there is an added bonus. The finished equipment looks and sounds professional—a beautifully finished charcoal grey cabinet and matching front with ham-type operating features and performance. Easy to build, the Star Roamer is a perfect gift for enthusiast and novice alike.

Knightkits are new to the U.K. and obtainable only from Electronics. The range is very wide—Hi-Fi gear, test equipment like 'scopes and multimeters, photographic light meters, electronic car tuning equipment—it takes a 70-page brochure to give all the details and you get a FREE copy by filling in the coupon. The Star Roamer costs just £28.6s.2d and credit terms are available if required. Like all Knightkits it is fully guaranteed and for any construction problem, however small, our Service Department is ready to advise and assist. The tuning ranges cover 200 to 400 Kc/s and 550 Kc/s to 30 Mc/s in five ranges with band spread control for the difficult stations. IF sensitivity control helps pick up distant stations and develops beat note for code

reception and practice. AVC prevents signal blasting and fading and ANL cuts static to a minimum. Illuminated S-meter shows signal strength for correct tuning and antenna trimmer peaks received signal. A code key jack for morse practice.

Please send me your FREE brochure K11 giving full details of your range of kits,

Send to Electronics (Prop. STC) Limited, Edinburgh Way, Harlow, Essex.

NAME _____

ADDRESS _____



knight-kit by

Quality Built-in, Built-up by you

electronics

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values, details of which are given in the latest edition of the Constructors' Booklet priced at 2/-.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial	RA2W.....		12/6
Driver Transformer	LFDT4/1.....		9/6
Output Transformer.....	OPT1		10/6
Printed Circuit.....	PCA1		9/6


I.F. TRANSFORMERS & COILS FOR VALVE CIRCUITS

Production of Tuning Coils (Type "H") and I.F. Transformers is being continued and details of these and our other components are given in an illustrated folder which will be forwarded on request with 4d. postage please


WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

HI-FI WITH THESE PLUS FEATURES

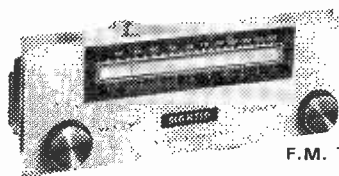RELIABILITY, QUALITY, ADD-ON-ABILITY, AND TRUE ECONOMY



F.M. TUNER

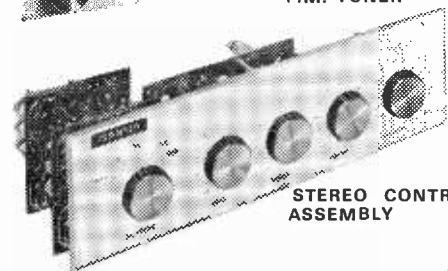

STEREO CONTROL ASSEMBLY

MARTIN AUDIOKITS are available for Mono, and can be doubled up for stereo, or as complete stereo units. 3 ohm and 15 ohm systems are available. There is a special pre-amp for low output pick-ups and escutcheon panels to suit the arrangement you choose. The tuner is styled to match.

You can do so much with MARTIN kits. The system of using pre-fabricated transistorised units which can be interlinked in a variety of ways enables you to assemble the combination of your choice and then extend it unit by unit until you possess a full stereo gramophone and radio assembly. When new units are produced, they can be added to existing equipment very easily with the advantage that you can continue to use equipment you already have.

so that your installation is always up to date. Most important of all is the power and quality which MARTIN Audiokits give you. Their sturdy construction assures compactness without sacrifice to quality or efficiency. They offer excellent value, are very easily installed and will give years of unflinching service. That is why people prefer MARTIN—it's simple to instal, good to listen to, and looks completely professional.

AMPLIFIER SYSTEMS • TUNERS • RECORDERS

From Radio and Hi-Fi Stockists

MARTIN ELECTRONICS LTD. 154/5 HIGH STREET, BRENTFORD, MIDDLESEX. ISLeworth 1161/2

Trade enquiries invited

MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex

Please send Recordakit/F.M. Tuner/Audiokit Hi-Fi Leaflets. (Strike out items not wanted)


Name

Address

PW11

CRYSTAL CALIBRATION OSCILLATOR

R. C. KITCHING

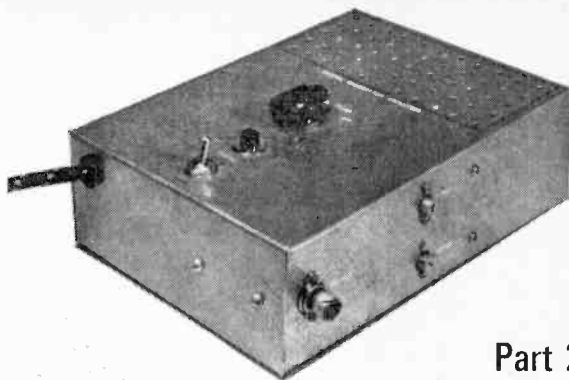

Part 2

FOR the sake of simplicity, the unit was built into a box consisting of the usual four-sided chassis with a baseplate fixed to flanges on the bottom with self-tapping screws. A chassis-panel mounted across the width carries the three valves, the crystals, the tag strips and the bulk of the minor components, the larger and heavier components (the mains transformer, electrolytic capacitors and trimmers) being mounted on the sides of the box.

Heat from the valves is kept away from the crystals by the use of a small screen.

The mains switch, function switch and the neon warning lamp—the controls of major interest—are mounted on the top of the box; the preset capacitors,

the output socket and the grommet for the mains cable are mounted out of the way on the sides of the box.

CHASSIS DETAILS

The constructor who is fortunate enough to have a workshop set aside with a solid bench, a vice and the requisite tools, and who is reasonably competent at working with metal, may decide to undertake the metalwork himself. Those less fortunate and/or less able, however, are advised to buy the (blank) chassis, baseplate, chassis-panel and screen ready made. They can be obtained from: H. L. Smith & Co. Ltd., 287/289 Edgware Road, London W.2 at a cost, including postage and packing, of 17/-.

When ordering, ask for:

Chassis type N length 8 in.; width 6 in.; depth $2\frac{1}{2}$ in.; flange $\frac{3}{8}$ in.

Baseplate 8 in. x 6 in. to fit above.


Chassis-panel B to fit width of chassis.

Screen type A length $2\frac{1}{4}$ in.; width $2\frac{1}{4}$ in.; flange $\frac{3}{8}$ in. x $2\frac{1}{4}$ in.

All in 18 s.w.g. aluminium.

Figure 6 shows the positions of the controls, screws etc. on the box. This layout has been found to be perfectly satisfactory in the prototype.

Figures 6-8 give the dimensions of the box, baseplate, screen and chassis-panel respectively and show all the holes that have to be drilled. The exact location of some of the holes is not given because they will vary with the size of the components used. For the same reason, the sizes of the holes have not been given; the constructor should have no difficulty in determining these for himself. It is for this reason important for the constructor to have all the relevant components to hand before drilling any holes. Also if the transformer it is intended to use is taller than $2\frac{1}{8}$ in. or more than $2\frac{1}{2}$ in. from one side of the windings to the other, a larger box will be required. When all the holes have been drilled, a finish can be applied to the exterior of the unit. A coat of brush or spray-on crackle paint is easily applied, and will considerably enhance the appearance of the unit. The paint should be left until it has dried hard: the relevant components can then be mounted. Transfers may be mounted at this stage as indicated in Fig. 6. Rubber feet should be glued to the corners of the base so that the unit is lifted clear of the bench and ventilation thus improved.

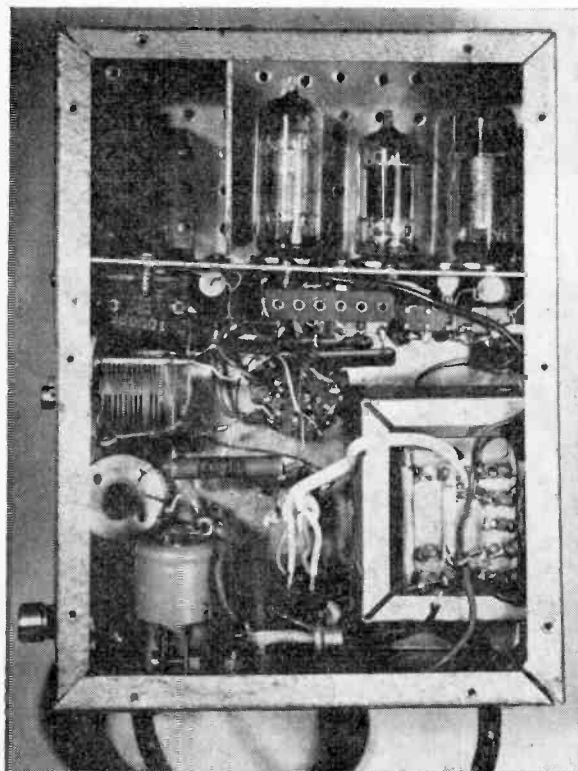

Photograph of the completed unit with the baseplate removed.

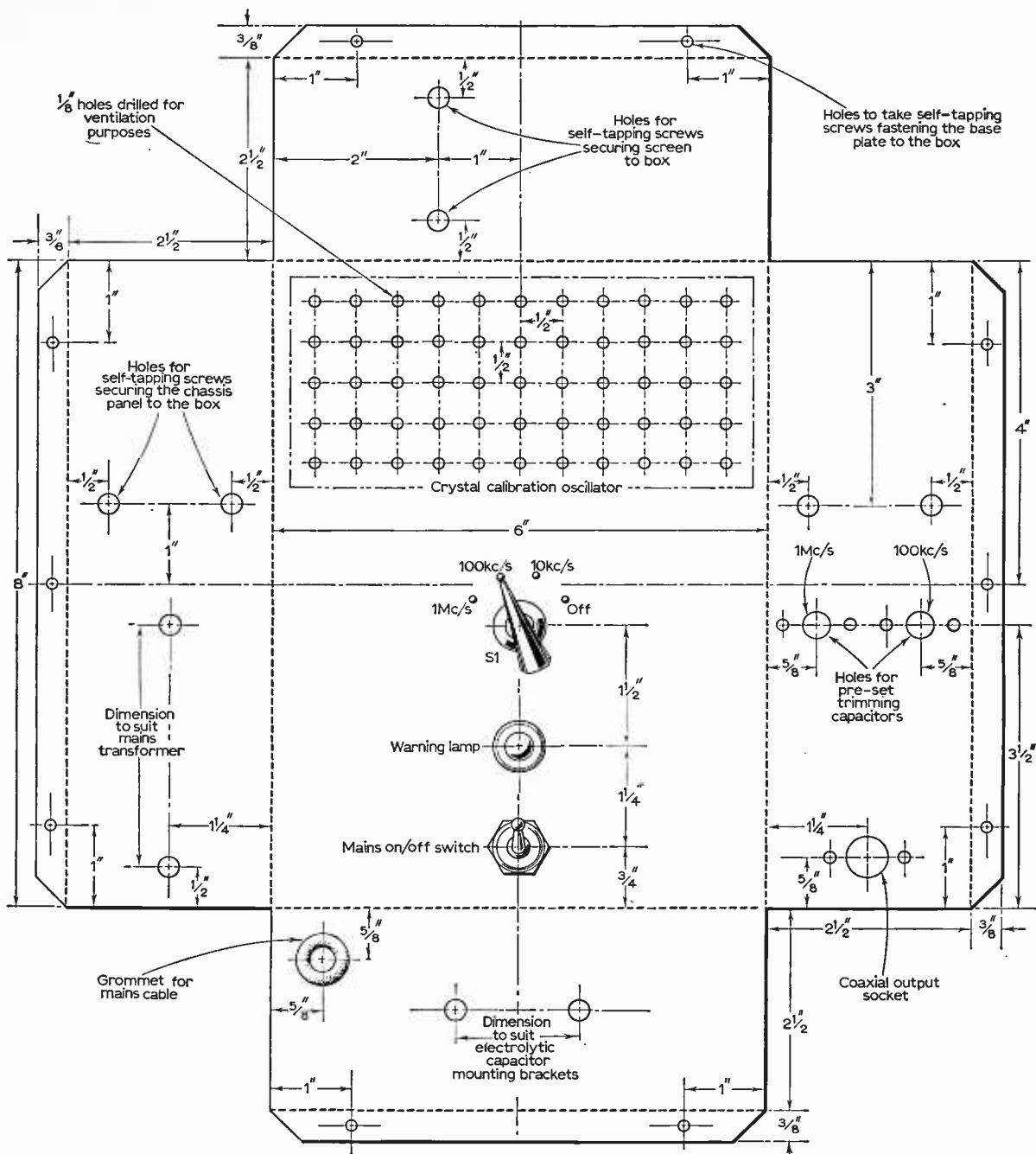


Fig. 6: Details of the chassis with positions of main controls and lettering indicated.

Details of the chassis-panel are shown in Fig. 8. Constructors who intend making the panel themselves should note that the length and breadth are $5\frac{7}{8}$ in. x $2\frac{3}{8}$ in. respectively when the inner dimensions of the box are being considered.

CONSTRUCTION

The electrical construction is best performed in three stages: (1) Wiring of components associated

with the box (i.e. power supply unit, switch etc.). (2) Wiring of components on the chassis-panel. (3) Interconnections between (1) and (2).

Stages (1) and (2) should be performed with the chassis-panel removed from the box. For stage (3) the chassis-panel is placed *in situ* but parallel to the top of the box so that easy access may be had to all the tags, especially those of the valveholders.

Figures 9 and 10 give full details of the layout and wiring of the components, and the novice is advised to adhere to these.

AN IMPORTANT ANNOUNCEMENT TO THE MANY
THOUSANDS WHO HAVE BOUGHT AND WILL BUY

THE COMMON



CORE SERIES

THERE IS NOW ADDED
THE 'NUMBERS GAME'

Play it with **TRAINER-TESTER** Response Sheet No. E3 and the eleven

ADJUNCTIVE PROGRAMMING SUPPLEMENTS TO

**basic electricity and
basic electronics**



WHAT'S THE 'NUMBERS GAME'?-

Each Supplement contains three things: a list of 50 four-choice Questions very carefully chosen to see whether the Reader has grasped the information which the volume in question has given him; an erasable Response Sheet on which you rub out an oblong of special ink to reveal a coded answer; and a key to the code which tells you if your answer to the question was correct. If it wasn't, the key gives you "remedial feedback" showing you exactly where you should go for re-study before you try the Question again. Each Supplement will cost 5s.

Fuller details will be sent on application to

THE TECHNICAL PRESS LTD

112 WESTBOURNE GROVE, LONDON, W.2

Incidentally BASIC TELEVISION part 1, 21s, is now ready and *THE TIMES EDUCATIONAL SUPPLEMENT* says of it "... the information (covering 405 and 625 line systems) is up to date and substantially non-mathematical. The volume can be thoroughly recommended as a primer training manual. Indeed, some television engineers will find it of value as a revision course."

(See 7 DAYS' FREE TRIAL offer in advertisement on page 533)

BENTLEY ACoustic CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone Primrose 9090

ALL GOODS LISTED BELOW, ACTUALLY IN STOCK, ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A2	5/-	6CW4	12/-	10P13	12/-	50CD6G	41/-	DK40	10/6	EF40	8/9	KT63	4/-	Q875/20		U282	12/3	AF127	3/6	0A73	3/1
0B2	6/-	6D3	7/6	10P14	13/-	50L6GT	6/-	DK91	4/9	EF41	9/-	KT66	16/6	10/6		U301	12/6	AF139	27/6	0A79	3/1
0Z4	4/3	6D6	3/-	12A6	5/-	52KU	14/8	DK92	7/6	EF42	3/6	KT74	12/6	Q8150/18		U329	9/8	AF178	18/6	0A81	2/-
1A3	2/6	6E5	9/6	12A06	8/-	53KU	14/8	DK96	8/8	EF50	2/6	KT76	7/6	9/6		U403	6/8	AF179	18/6	0A85	3/1
1A4	12/6	6F1	9/6	12AD6	9/-	72	6/8	DL33	6/8	EF54	6/-	KT88	27/6	R10	15/-	U404	6/-	AF180	9/6	0A86	4/1
1A5	5/-	6F6G	4/-	12A26	7/6	77	5/-	DL35	4/9	EF80	4/6	KTW61	4/3	R11	19/-	U801	18/-	AF181	14/-	0A90	3/-
1A7GT	7/6	6F6GT/M		12AH7	5/-	78	4/9	DL72	15/-	EF83	9/9	KTW62	12/6	R12	5/6	U4020	6/-	AF186	20/-	0A91	3/-
1C1	4/9		7/6	12AT6	4/8	80	5/3	DL75	30/-	EF85	4/9	KTW63	4/3	R16	34/11	VMP40	17/-	AF212	5/-	0A95	2/-
1C2	7/6	6F7G	5/-	12AT7	3/8	85A2	8/8	DL82	4/9	EF86	6/3	KTZ41	6/-	R17	17/6	VMS43	12/6	AF212	5/-	0A95	2/-
1C3	6/8	6F8G	5/-	12A06	4/8	90AG	87/8	DL84	5/6	EF89	4/9	L63	4/8	R18	17/6	VP2	3/6	AF212	5/-	0A95	2/-
1C4	4/9	6F12	3/6	12A07	4/8	90B3	87/8	DL86	6/-	EF91	3/3	LP2	9/6	R19	6/9	VP2B	9/6	AF212	5/-	0A95	2/-
1C5	10/8	6F13	2/6	12A06	5/9	90CG	34/8	DL810	10/6	EF92	2/6	MHD4	7/6	R22	7/6	VP4	14/6	AF212	5/-	0A95	2/-
1D5	6/-	6F14	15/-	12AX7	4/8	90CV	33/8	DM70	6/-	EF97	8/-	MHLD6		RG1/240A		VP4A	14/6	BA115	2/8	0A211	13/6
1D6	9/6	6F15	10/9	12AX7	9/9	90C1	16/-	DM71	9/9	EF98	9/-					VP4B	11/-	BA116	9/-	0A230	18/6
1FD1	6/-	6F17	12/6	12BA6	6/-	100B2	14/8	DW4/350		EF183	6/3	ML6	8/-	RK34	65/-	VP4C	7/6	BA129	6/8	0A230	18/6
1FD9	3/3	6F18	7/6	12B6	5/3	150C2	6/-			EF184	5/9	M4B	20/5	S130	25/-	VP23	2/6	BA130	2/-	0A230	18/6
1G6	6/-	6F22	8/1	12B7	6/-	181	15/-	DW4/500		EH90	7/6	MS4	12/6	SP4B	19/8	VP41	5/-	BCY10	5/-	0A230	18/6
1H5GT	7/6	6P24	10/-	12E1	17/8	185B	35/-			EL32	3/6	MU12/14	4/3	SP13C	12/6	VR75	21/-	BCY12	5/-	0A230	18/6
1L4	2/6	6F32	3/6	12F5GT	2/6	301	20/-	DY86	5/6	EL33	12/-	MX40	12/6	SP42	12/6	VR105	5/-	BCY33	5/-	0A230	18/6
1LD5	5/-	6G6G	2/6	12G7GT	6/8	302	16/8	DY87	5/6	EL34	9/9	N37	23/3	VP5	5/6	VP45	5/6	BCY38	5/-	0A230	18/6
1LN6	4/8	6H6GT	1/6	12K5	8/-	303	13/8	E80F	24/-	EL36	3/6	N78	38/4	TD2DA12/6		VT81A	16/6	BCY38	5/-	0A230	18/6
1NGGT	7/9	6H6GT	1/6	12K7GT	13/8	305	16/8	E83F	24/-	EL36	3/6	N108	28/-	TD4	7/6	VT501	3/-	BCY39	5/-	0A230	18/6
1P1	6/-	6J5GT	4/9	12K8GT	7/8	306	13/-	E88CC	12/-	EL37	16/6	N339	25/-	TH4B	10/-	VU111	6/-	BC107	10/8	0A230	18/6
1P10	4/9	6J6	3/-	12Q7GT	3/8	807	11/9	E180F	17/6	EL41	8/6	TH21C	10/8	TH21C	10/8	VU120	12/-	BFY50	5/-	0A230	18/6
1P11	5/6	6J7G	4/9	12A2GT		958	2/-	E1148	1/9	EL42	7/6	TH30C	14/6	TH30C	14/6	VU120	12/-	BFY51	5/-	0A230	18/6
1R5	4/9	6J7GT	8/6		6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1R4	4/9	6P28	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1R5	3/3	6K7G	1/3	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1T2	34/11	6K7GT	4/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1T4	2/6	6K8G	3/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1U4	5/6	6K8GT	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
1U5	6/8	6K26	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
2D13C	7/6	6L12	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
2D21	5/6	6L6GT	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
2X2	3/6	6L7GT/M		12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3A4	3/6	6L8	5/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3A5	8/-	6L18	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3B7	5/-	6L20	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3D6	3/6	6L20	6/8	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3Q4	5/3	6N7GT	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3Q6GT	6/6	6P1	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
384	4/9	6P25	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
3V4	5/6	6P28	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
4D1	3/9	6P28	25/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
5B4G	4/9	6Q7G	5/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
5U4G	4/9	6Q7GT	8/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
5V4G	8/-	6R7G	5/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
5V9GT	7/6	6H7GT	12/-	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
5Z9	7/6	6A7GT	7/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6Z4G	7/6	6B7G	6/6	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6J012	9/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6B8G	7/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6AC7	3/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A05	2/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A07	5/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A15	2/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A17	5/6	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A18	4/9	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A19	4/9	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42	7/6	TH33	13/6	TH33	13/6	W101	26/2	BFY52	5/-	0A230	18/6
6A20	4/9	6B8GT	7/9	12B7	6/9	1821	10/8	EASO		EL42											

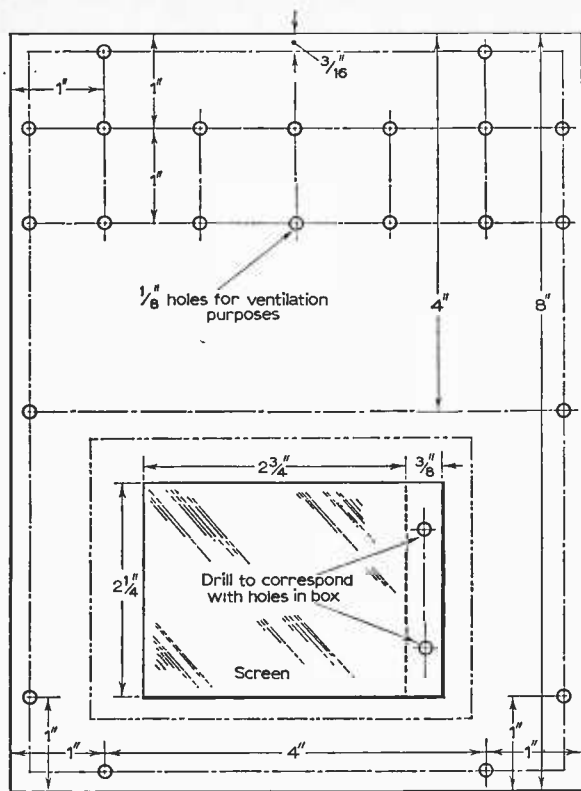


Fig. 7: Details of the baseplate and lower insert, screen for crystals.

When the electrical construction is completed, a careful check must be made and, when the constructor is satisfied that all is well, the unit is ready for testing and making the necessary adjustments.

TESTING AND ADJUSTING

(1) Check with a multimeter on the resistance range that the h.t. line is in open-circuit with the chassis. If there is a short or low resistance, disconnect each stage from the h.t. in turn and check it individually.

(2) Wrap a piece of insulated wire round V1 pin 7 and place this near the aerial lead of a receiver tuned to, or to a low multiple of, 1Mc/s.

(3) Plug the unit into the mains and switch on; the neon lamp and the valves should glow.

(4) Check the h.t. voltage, which should have risen to about 350V on switching on gradually falling to about 250V as the valves start to draw anode current.

(5) With S1 in the 1Mc/s position a fairly loud hiss should be heard in the speaker. On switching to the 100kc/s crystal, another hiss should be heard though it will probably be slightly weaker than the other. If no hiss can be heard, then the oscillator is obviously failing to function and the wiring and components (including the valve) should be checked. If only one of the crystals fails to oscillate, then either that crystal or its associated circuitry is under suspicion.

The constructor should experience no difficulty in making even surplus crystals oscillate in this circuit, though should the crystal prove stubborn then the constructor should experiment with the position of the cathode tap by varying the value of C1 and/or C2.

(6) When the crystal oscillator is operating satisfactorily, the piece of wire can be removed from the anode of V1 and the output lead be plugged into the output socket. The clip (see Fig. 11) connected to the inner conductor of the output lead is clipped on to the aerial lead of the receiver and the clip connected to the outer to the chassis of the receiver (via an 0.01μF 250V capacitor in the case of an a.c./d.c. receiver). The original hisses should now be much stronger and furthermore harmonics should be audible well down into the s.w. spectrum.

(7) The receiver is now tuned to either an MSF transmission on 5.0Mc/s or 2.5Mc/s, or to the Light Programme on 200kc/s and, with the 100kc/s crystal in circuit, TC1 adjusted for zero beat.

The 1Mc/s crystal is then switched into circuit and made to zero beat with the MSF transmission on 5.0Mc/s by adjusting TC2.


CHECKING THE MULTIVIBRATOR

(8) The 10kc/s multivibrator can now be checked. Set the slider of VR1 so that it is near the centre of its travel. On moving S1 to the 10kc/s position, a very faint, high-pitched note should emanate from the multivibrator circuit. If the tuning control of the receiver is now moved, a number of swishes should be heard in the speaker. These swishes will become closer together as the frequency of the receiver is increased and farther apart as the frequency is decreased. It is thus easier to carry out adjustments to VR1 on the most l.f. range of the receiver.

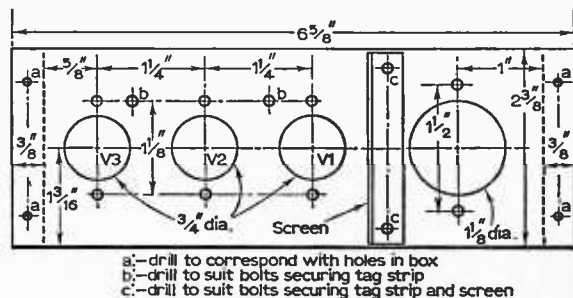(9) Note the position of two adjacent 100kc/s bars in this range. With the switch in the 10kc/s position, count the 10kc/s bars between the two points—there should be nine, or eleven including both 100kc/s points. If this is not so, adjust VR1 until it is.

Should it be found impossible to reduce the frequency to 10kc/s the probability is that Cx is too large so that too much sync is being applied. This state of affairs is unlikely by virtue of the nature of Cx. The remedy, however, is simply to unwrap the insulated wire until the frequency can be reduced to 10kc/s.

The unit has now been completed and constructors who have taken time and trouble over both



a.—drill to correspond with holes in box
b.—drill to suit bolts securing tag strip
c.—drill to suit bolts securing tag strip and screen

Fig. 8: Details of the chassis-panel.

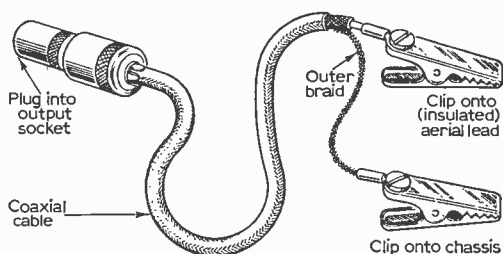
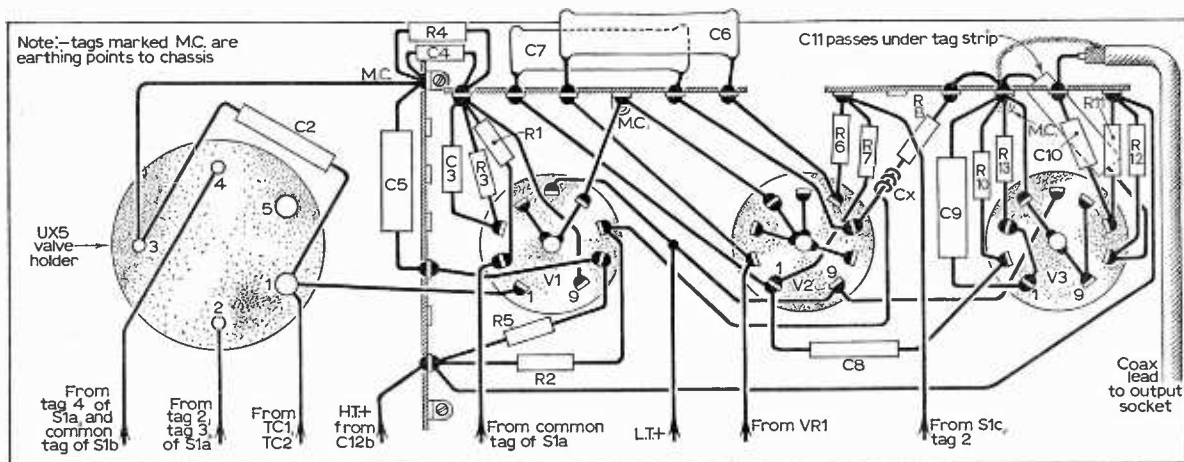
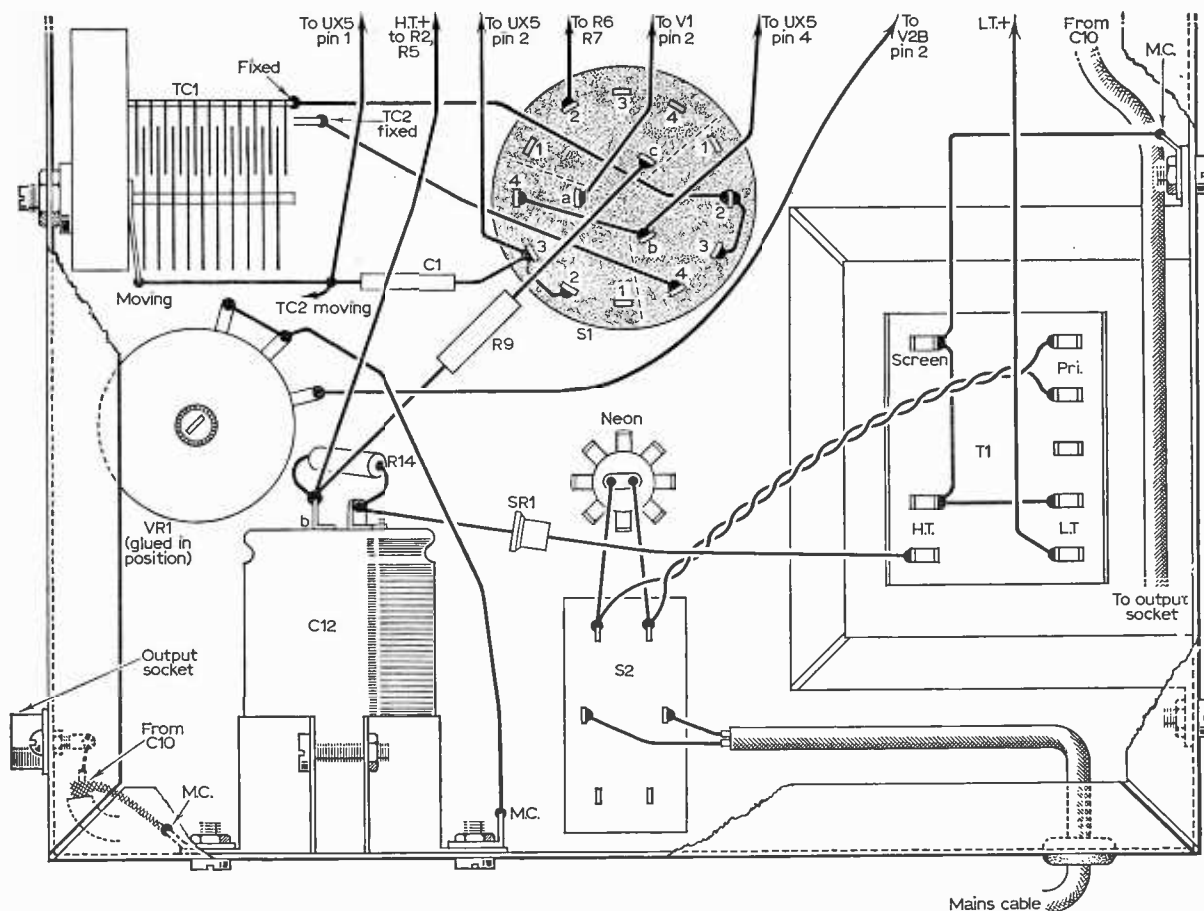


Fig. 9 (top): Wiring of the components mounted on the main chassis.

Fig. 10 (centre): Wiring of the components mounted on the chassis-panel.

Fig. 11 (left): Output lead and clips.

sides of the construction will find that they have at their disposal a professional looking crystal calibration oscillator of high dependability, providing excellent facilities for calibrating to a very high degree of accuracy a great variety of equipment operating in the range 10—30,000kc/s.

HALF REV. PER MINUTE
Made by famous Smith Electric, mains operated and quite powerful. Size $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. deep. Secondary use as process timer. Internal switch can be made to break circuit within a period up to 2 mins. 17/6 P. & P. 2/6 unless ordered with other goods.



4 pole, 2 way—3 pole, 3 way—
4 pole, 3 way—2 pole, 4 way—
3 pole, 4 way—2 pole, 6 way—
1 pole, 12 way. All at 3/6 each
36/- dozen, your assortment.

An Instant Thermostat. Simply push it into 15A wall socket and plug your fire or other appliance into it. Knob setting. Will save its cost in a season. Normally £3. We offer at 19/6. plus 2/- post.



<i>Type</i>	<i>Price</i>	<i>Type</i>	<i>Price</i>	<i>Type</i>	<i>Price</i>
2N1278	15/-	0A5	5/-	0C75	3/-
2N1728	10/-	0A10	6/-	0C76	3/-
2N1742	25/-	0A47	3/-	0C77	7/-
2N1747	25/-	0A70	3/-	0C78	3/-
2N1748	10/-	0A79	2/-	0C78D	3/-
AC107	9/-	0A81	2/-	0C81	3/-
AC127	4/-	0A85	2/-	0C81D	3/-
ACV17	8/-	0A90	2/-	0C82	3/-
ACV18	5/-	0A91	2/-	0C82B	3/-
ACV19	6/-	0C200	3/3	0C83	3/-
ACV20	6/-	0A202	4/3	0C84	4/-
ACV21	6/-	0C20	12/-	0C139	8/-
ACV22	4/-	0C22	10/-	0C140	12/-
AF114	4/-	0C23	8/-	0C170	5/-
AF115	4/-	0C24	15/-	0C200	4/-
AF116	4/-	0C25	15/-	0C201	12/-
AF117	4/-	0C26	7/-	0C201	12/-
AF118	4/-	0C28	8/-	0C202	13/-
AF139	12/-	0C29	17/-	0C203	12/-
AF186	17/-	0C35	10/-	0C271	15/-
AF212	15/-	0C36	15/-	0R12	8/-
AF213	15/-	0C38	12/-	0P60	10/-
BC107	14/-	0C42	6/-	8B078	8/-
BY100	4/-	0C44	3/-	8B305	6/-
BY213	7/-	0C45	3/-	8B251	10/-
MAT100	7/-	0C46	3/-	8T140	3/-
MAT101	8/-	0C47	3/-	8T141	4/-
MAT102	8/-	0C71	3/-		
MAT121	8/-	0C72	3/-		

Piv	50V	100V	300V	400V
1 amp	6/6	7/6	8/6	9/6
3 amp	7/6	8/6	9/6	10/6
25 amp	30/-	35/-	47/6	60/-

Tested and guaranteed.			
750mA	100v. 1/8	1 Amp.	100v. 3/4
	200v. 1/8		200v. 4/5
	400v. 3/8		400v. 6/5
2A	100v. 3/8		
	200v. 5/8	10 Amp.	100v. 9/8
	400v. 7/8		200v. 12/10
	600v. 9/8		400v. 14/10
Sub-miniature glass encased—only approx. $\frac{1}{2}$ in. long wire ended.			
	400mA. 50v. 1/6	100v. 2/8	200v. 4/6

Each kit comprises seven items—Choke. 2 tube emils, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new Grolux® tubes for fish tanks and indoor plants. Grolux® tubes are super-silent, make no resin glows. Kit A—5-20 w. 19/6. Kit B—30-40 w. 17/6. Kit C—80 w. 17/6. Kit D—125 w. 22/-, Kit E—65 w. 19/6. Kit MP1 is for 6in., 9in. and 12in. miniature tubes 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 for first kit then 3/6 for each kit ordered. Kit MP1 3/6 on first kit then 3/6 on each two kits ordered.

Standard type and size with good length of spindle—made by Morganite. List price is 10/- each but if you act quickly you can have them at 12/- doz. (or 1/8 each if less than doz.). Following valves in stock all "In"—10K + 10K—100K + 100K—500K + 500K All new and unused. Post 2/9 on 1st doz. then 1/- per doz. 6 doz. or more Post free.



12 hour, 15A to control heating, lighting, radio, immersion heaters, etc. Regular price £4.4.0. Limited quantity 39/6. P. & P. 3/-.

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instructions—uses silica enclosed elements designed for the correct infra-red wave length (3 microns). Price for 750 watts element, all parts, metal casing as illustrated. 19/6, plus 3/6 post and insurance. Pull switch 3/- extra.



CONTROL DRILL SPEEDS

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by fingertip control. Kit includes all parts, case, everything and full instructions. 19/8, plus 2/6 post and insurance. Or available made up 32/6.

Will save time and improve efficiency. Ideal in home—office—shop—surgery, etc. Complete outfit comprises Master unit and three substations the master and have full two-way working. Not fitted with 60ft. twin flex and they plug into 3 packet of staples—and battery. Nothing else 1/6 post and insurance.

low stylus pressure—large diameter turn-table for max. stability adjustments include pick-up height—pick-up dropping position and stylus pressure. Size is 13½ x 11½ in. clearance 4½ in. above, 2½ in. below—fitted with latest hi-compliance cartridge for stereo—and mono. L.P. and 78. Supplied complete with mounting template and service sheet. Offered this month at the Special Snip price of \$68.96 plus 7/6 carriage and insurance.

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed-back loops—sensitivity 5mV. Price 19/6. Post and insurance 2/6. Speakers: 3in. 12/6, 5in. 13/6, 6 x 4in. 14/6.



An excellent opportunity to re-equip your house or workshop. Or if you are a contractor to restock for future ring main jobs. We offer 12 GEC switch sockets, Brown Bakelite surface mounting. Latest ring main type listed at 6/6 each. You can have a box of 12 for 30/- only—thus showing you a saving of £2.8.0. Postage and insurance 4/6 extra.

Battery operated and with all accessories. Really fantastic offer a British made £21.00 but for only £6.19.6 brilliantly designed for speed and efficiency—cassette takes normal spools drops in and out for easy loading—all normal functions—accessories include stethoscope, earpiece, crystal microphone has on/off switch telephone pick-up—tape reference pad—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY. £6.19.6 plus 7/6 post and insurance. Footswitch 15/6 extra. Spare Cassettes at 7/6 each, three for £1.



for test meter, hi-fi amp. etc. 1st button operates mains on/off switch, the other two operate change over switches. Knobs engraved on/off, bass, treble but engraving easily removed leaving clean surface for remarking. 2/9 each, 24/- doz.



With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. Deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4/5 volts. Supplied complete with 2 spools ready to install. Record, Replay head is the sensitive M4 type intended for use with transistor amplifier. Price £415.0. Post and insurance 4/6.

These infra-red binoculars when fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical system as well as the infra-red cell. These optical systems can be used as lenses for T.V. cameras—light cells, etc. (details supplied). The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order but sold without a guarantee. Price £3.17.8, plus 10/- carr. and ins. Handbook 2/6.



3 heat positions to suit changes in weather: 1kW, 1½kW and 2½kW; also blows cold for summer, has thermostatic safety cut-out. Proper price £5.17.6. Yours for only £3.15.0, plus 7/6 post and insurance.

BSR Record Player for normal mains operation. This is the famous BSR Model G.U.7. Four speeds with automatic stop. Plays any size of record and is complete with crystal cartridge and sapphire stylus. Special snip price this month 67/6 plus postage and insurance 6/6.



PP3 Eliminator. Play your pocket radio from the mains! Save £s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 8/6 plus 1/- post.

26 yards length 70W. Self-regulating temperature control. 10/- post free.

Intended for driving battery operated tape recorders and record players. Laminated, 6 Pole armature with Brush Gear and rapid start switch. Normally 25/-. Our price 7/6, plus post and insurance 1/6.



Type "A" amp. for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob. Quickly adjustable from 30-80°F. 9/8 plus 1/8 post. Suitable box for wall mounting. 5/-, P. & P. 1/1.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Stivvic Co. Spindle adjustable from 30-80°F. Internal screw alters the setting so this could be adjustable over 30 to 1000°F. Suitable for controlling furnace, oven, kitchen immersion heater or to make flame-start or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stast as it cuts in and out at freezing point. 2/3 amps. Has many uses, one of which would be to keep the loft from freezing, if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/1.

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA. (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers. Zener diode and instructions. Real snip at only 14/8, plus 3/6 postage.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. SAE with enquiries please.

(Dept. P. W.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

TECHNICAL TRAINING

*in radio television
and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multimeter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME

ADDRESS


11/67

INTERNATIONAL CORRESPONDENCE SCHOOLS



5 WATT, PUSH-PULL OUTPUT AMPLIFIER. 200-250 Volts A.C. ECC80, ECC83, 2-EL84. Bass, treble, vol/on-off. £5.15.0 (7/6 P. & P.) Size 12 x 8 1/2 x 5 in. high.

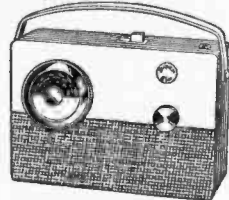
20 ELEMENT MAST CLIPPING BBC-2 OUTDOOR AERIAL. State Station required 55/- (7/6 carr.). BBC-2 Coax Cable 1/8 yd.



6 TRANSISTOR "SUPER SIX". M.W. and L.W. kit, £4 (5/- P. & P.). Wooden cabinet 11 x 7 1/2 x 3 1/2 in. All parts may be purchased separately. 3 1/2 in. 10,000 line speaker, or 7 x 4 in. 6000 line.

TESTED AND ASSEMBLED I.F. TRANSISTOR STRIP. 3 IFs (double tuned), osc., diode, 3-AP117, P.C. board 4 1/2 x 2 1/2 in., 470KHZ, 25/- (2/6 P. & P.).

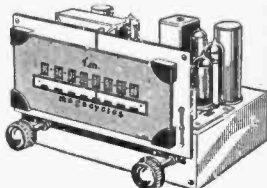
8-12 VOLT TRANSISTOR AMPLIFIERS (1) 200mW for 3 ohm speaker 12/-, (2) 350mW with switch, vol. control, for 3 ohm speaker 40/-, (3) 1 w. for 8 or 15 ohm speaker, 52/8, (4) 3 w. for 8 or 15 ohm speaker 67/8 (2/6 P. & P. each type). Type (1) can be supplied in metal box 3 1/2 x 2 1/2 x 1 1/2 in. high with vol. on-off. Internal PF3 battery or larger externally. Socket for input and output only 40/-. Post paid.



VHF/FM TUNER. 88-102MHz. Self-powered. Valves ECC85, EF89, 6BW7, ECC82, two diodes and metal rect. 8 x 6 x 5 1/2 in. high. Full instruction book, circuit diagrams etc. 2/8; free with chassis. With front panel and brackets £7.19.8 tax paid and carr. paid. Can be supplied built for £8.17.8.

TRANSISTORISED F.M. TUNER. Size 6 x 4 x 2 1/2 in. Model A1005. Requires 9v. 10mA. 88-108MHz printed circuit. Cap. tuned; 3 I.F. stages; double tuned disc; 10mV output with 10 microv. input. Transistors 2SA235 x 2; 2SA350 x 3; 8175 and diodes 1N34, 1N60 (2). Only £7.5.0 (4/6 P. & P.). Compare this price before purchasing elsewhere.

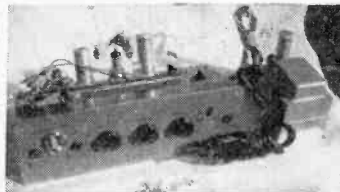2 x 4 WATT STEREO AMPLIFIER. Printed circuit. Separate power pack. Metal rectifier, ECC83 and 2-EL84. Negative feedback. Vol., base, treble each channel. Muting switch and on/off. £5.10.0 (7/6 P. & P.).



**TAPE
AMPLIFIER FOR
MAGNAVOX
TAPE DECKS —
2 or 4 TRACK**


Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Plastic front panel "gold" finish—12 1/2 x 4 1/2 in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol./Mic.; Vol./Gram; Mic. Input; Gram. Input; Monitor; Speaker Socket. Valves 6BX7; 12AX7; EM84; EL84; 6X4. Separate power pack. Complete amp. and power pack, £8.17.8. (6/- P. & P.). Resine covered cabinet (tan) 15 1/2 x 17 x 9 1/2 in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck 85/- (8/- carr.). 3 speed Magnavox 2 track tape deck £10.17.8; 4-track £12.15.0. Complete Recorders (with speed compensation) 2-track £29; 4-track £32 (carr. 25/-). Worth £10 more on normal retail prices.

SALE OF VALVES (NEW)

Unrepeatable after Stocks Cleared

1/- ea. ARP35; 1/8 ea. OC3L, EB34, 6B8G, 7475, 1F2, 2/8 ea. DF92, EC31, EY91, 3/- ea. DL93, E2124, EC70, EF70, EL32, F0063, 2X24, 6F32, 6J6, 6K7G, 6K8G, 3/8 ea. DAF91, DL92, 4/- ea. AC/P4, DL73, DM70, E2221, EL35, OD3, 86F17, TT1, VR150/30, 1N21B, 2D21, 5A173G, 6X8G, 6X10G, 5/- ea. DF96, EB33, EN91, FVD7, HL133DD, KT65, 1A5, M8079, ME41, ML4, O2, OF2, PFY31, PZ30, R17, UBC41, V2053, VU71, VU/33A, Z66, 1D13, 1H5G, 2B35, 5U4G, 6AG7, 6AK7, 6AS6, 6BW6, 6CH6, 6K6, 6K6GT/G, 6K7, 6K8, 6L6G, 6N7G, 68A7, 68G7, 68L7, 11E2, 88A2, 95A1, 354V, 6057, 6/- ea. E2134, EL36, EL41, GZ30, GZ37, 6726, 7/6 ea. QV04-7, 807, 1834, 10/- ea. EM34, M8142, 8130P, VX3193, VX9192, XB1, 78C1, 150B2; 12/6 ea. EL37, EL38, G187M, 6B4G, 15/- ea. A18340, EC334, 6CD6G, 12E1, 20/- ea. 85A1, Z759, 30/- ea. 5B/254M, 5P/225M, 50/-, VX5029 60/-, 4X150A, TDI-100A; add 1/6 per order P. & P.

NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS

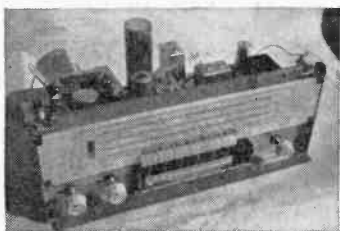

M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial cream and red. 15 x 3 in. 190-650M; 18-51M; 60-187M; VIF 86-100 Mc/s. Valves: ECC85, ECC81, EF89, 2 x ECL86, EM84 and Rect. Price £19.19.0, carr. paid or £6.13.0 deposit and 5 monthly payments of 56/8. Total H.P. price £20.15.8. Cream moulded escutcheon included.

BATTERY ELIMINATOR

90V H.T. and 1-4V L.T. Size 5 x 3 x 3 in. State valve line-up. Fully built. 125mA L.T. or 250mA L.T. "Open" type for mounting inside set. 50/- post paid.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE Aldershot 22240
CLOSED WEDNESDAY AFTERNOON CATALOGUE 6d.

LETTERS...

To all 19 set swl's

I HAVE modified two sets as from March—April 1966 P.W. (Mr. S. Simpson modifications). He does say in his notes that the b.f.o. het. tone control is slight in shift operation. I found by earthing the centre pin of the het. tone control pot, it works perfectly on c/w and s.s.b. signals with no trouble at all. Hoping it may be of use.—**C. Skinner** (*Blackpool*).

Burndept line-up

With reference to the letter from W. M. MacKenzie, Gosport, Hants., in the September issue requesting information re the valve line-up of a Burndept 285.

The following is an extract from the Mullard Valve Replacement Guide 1950: VP4B, TH4B, VP4B, 2D4A, 2D4A, AC/SP1 (Mazda), 6B5 (Brimar), IW4/350.—**G. Roberts** (*Holyhead, Anglesey*).

[We would like to thank the many readers who wrote to us offering to help Mr. MacKenzie. It is very gratifying to note that so many readers believe in the true spirit of amateur radio.]—Editor.

Offer of components

I have in my possession certain components that I would like to offer to P.W. readers. The components include valves, resistors, transistors, capacitors, etc.

I would like to hear from any reader who is interested.—**S. G. Deane** (40 Thackeray Avenue, Tottenham, London, N.17).

Tarnished halo?

I agree with your view expressed in the September editorial, that it is difficult to provide articles which will please everyone. Your magazine carries articles on a wide variety of topics, and so it doesn't grow stale.

Nevertheless you regularly commit two sins. (Perhaps your halo is a bit tarnished!) First, some of your advertisements come in the middle of features or constructional articles. In this position they make the articles

more difficult to read.

Second, there are often errors in the illustrations, the components list or the text of your constructional articles. This should *never* be allowed to happen. The less well-educated constructor or the man with little or no test equipment has to wait two months before the errors are corrected. If every reader were able to correct these errors on sight, there would be no point in having constructional articles at all.—**A. G. Pope** (*Reading, Berks.*).

Vintage portable

I have, complete though in very "tatty" condition, what I would think ranks amongst one of the first portable radios, viz. McMichael Duplex Four Type "S.M.C." together with Installation and Operating Instructions, though I did have ideas of renovating same time will just not allow, so if any readers are interested please get in touch with me.—**R. A. Thomas** (6 Hamble House Gardens, Hamble, Southampton).

More science fiction?

With reference to Mr. J. Perry's letter (P.W. July), I would draw his attention to one of many misleading statements directed at the layman, i.e.:

ELECTRICITY EXTRAORDINARY

"An all-in-the-ear hearing aid the size of a man's thumbnail and weighing only half an ounce . . . A wrist-watch that runs for years without winding . . . A radio receiver that fits behind the badge of a policeman's helmet . . . These are not dreams of the future: they are already here, made possible by the development of the transistor—the miniature electric battery which experts say will soon provide the power for all our radios, clocks and household appliances."

This amazing insight into modern electronic science was given to the readers of *Readers Digest* in November 1957.

Perhaps in the last ten years we have forgotten the true func-

tion of the transistor, or is it that our transistor research boffins don't read enough American science fiction magazines.—**T. Jones** (*Oldham, Lancs.*)

Goodbye, Mr Dodd!

With reference to the Topic of the Month in the September issue of PRACTICAL WIRELESS.

W. N. Stevens has proved somewhat hypocritical in his observations and appears to confuse his own warped opinions with the contrasting actual facts. He states that "... it matters not only what you say but how you say it". True Sir, quite true but to imply, quite erroneously, that the Editorial team is a "bunch of mutinous dogs" is clearly not etiquette nor polite, and certainly not becoming to a gentleman.

We find in other Topics of the Month suggestions like sending gunboats down the Rhine. Quite clearly the writer of these idioms is bent on a facetious tack, coupled with the dastardly attack on his own kith and kin, the very team who produce this splendid magazine. With such a one at the helm how true to say 'don't let us get complacent.—**W. E. Dodd & Associates** (London, W.C.2).

[Readers, please note that Mr. Dodd is in fact one of the mutinous dogs referred to and is suffering from a stricken conscience. We are glad he is not complacent as he stands in grave peril of redeployment as from now. Gad, sir—what is this younger generation coming to!]

—Editor.

A bit of fluff

No doubt a lot of readers frequently have trouble with fluff and dust accumulations on stylus tips. I find that a toothbrush head, chopped down and mounted appropriately on the deck, suffices to clean the tip as the pick-up returns to its resting position as each record drops. This is only an amateurish modification of course, but on my own set, I haven't had record slip for quite a while.—**S. A. Gough** (*Burnley, Lancs.*).

the numbers to be multiplied in scale M. The product may then be read off in scale M opposite the other number in scale L. If this is off the scale, use the opposite end of scale L in setting against the original number.

For example only one calculation is really necessary. *E.g.* 270×4.5 .

Place the 1 of scale L opposite the 2.7 of scale M, then look for 4.5 on scale L. This is seen to be outside the window. Thus reset the 10 of scale L opposite the 2.7 of scale M, and read off the answer, as 1.22 (actually 1.215) opposite 4.5 on scale L. This is not yet corrected in terms of the decimal point, and this is done by approximation, mentally multiplying say $300 \times 5 = 1,500$, thus signifying the answer as 1,220 within reading accuracies (actually 1,215).

Division is best explained by a direct example. *E.g.* $445 \div 20$.

Set 20 in scale L opposite 445 in scale M (actually setting 2.0 and 4.45 of course) and read the answer, 22.25 in scale M opposite the 1 of scale L.

OTHER DATA

Other useful data is provided on the rule, such as the preferred resistor values, a useful thing to have in mind when designing circuitry. Also the resistor colour code is tabulated for quick reference. Finally the preferred resistors in parallel to give a more exact non-standard resistance, may be determined from the chart provided.

Using this chart, magnitudes are selected by inspection. For example, say we calculate that we exactly

require a resistance of $41k\Omega$. We see from the preferred resistors table this is not a standard resistance, and could check say the nearest value, $43k\Omega$ with the tolerance scale, and possibly also $30k\Omega$, seeing these are outside our required tolerance, perhaps $\pm 2\%$. The chart is employed to get the values of two standard resistances in parallel to give the required value. Look for $41k\Omega$ in the right-hand scale of the chart, where of course we assume the scale is 0-100k Ω . Look across the line estimated to be 41, and find the nearest point of intersection of two coloured lines to this value. These are seen to be 56 and 150. Now since two resistors in parallel must give a resistance lower than the lowest of these resistors, and also remembering the other useful rule of thumb that two resistors of the same value in parallel give a resistance of half their value, we know that both resistors must be greater than $41k\Omega$, and we realise that the required parallel values are $56k\Omega$ and $150k\Omega$.

Compare this with trial and error using values in the formula

$$\frac{R_1 \times R_2}{R_1 + R_2}$$

We may further determine approximately the tolerance we are within by using the formula with the two resistance values thus found, giving a resistance of approximately $40.8k\Omega$. The tolerance scale then tells us the tolerance, but remember to make allowance for say the $\pm 1\%$ tolerance of the parallel resistors. Unless these are measured to a greater accuracy than $\pm 1\%$ in this example, not much is to be gained from using the parallel combination.

CQ! CQ! CQ! CQ! CQ! CQ!

CORRESPONDENTS WANTED

... anyone interested in the field of radio—especially in the Commonwealth or Japan. I am 26 years old.—Corrigan Lupasha, P.O. Box 85, Chingola, Zambia.

... anyone interested in electronics and who will willingly send circuit diagrams for the latest communication receivers and the like. In exchange, Indian gifts will be sent. I am an electronics engineer.—V. K. K. Royan, The Royan Electronic Centre, Malayanthankudy, Puthalam, p.o., (Kanyakumari District) Madras State, South India.

... anyone of my own age (13 years old) who is interested in short wave listening.—B. Mellor, 47 Back Green, Churwell, Nr. Leeds, Yorkshire.

... anyone of my own age (17 years old) living in Great Britain who has an interest in short wave, sport and Blue music. My call sign is HA3ME.—Buzsaki Gyorgy, Pecs II, Liszt F.u.2., Hungary.

... anyone of my own age (13 years old) interested in radio. I have a 19A set and I am on the look-out for a 1154.—Andrew Downes, 43 Banchory Place, Tullibody, Alloa, Clacks, Scotland.

INFORMATION WANTED

... official handbook or a circuit diagram and any information on the ex-Army wireless set 31, assembly cat. No. ZA4765 Mark 2.—K. M. Jiwa, 199b Sentul Pasar, Kuala Lumpur, Malaysia.

... technical details of the Grunther c.r.t. tester.—R. Gascoyne, 20 River Close, Stoke Canon, Exeter.

... any service manuals or service sheets that readers do not require, as I am a rehabilitate of St. Lyes and would find these very useful.—D. Marchant, St. Lyes College for the Training and Rehabilitation of the Disabled, Exeter.

... information on the correct pin and voltage connections for the 78 receiver.—J. E. Warr, 40 Palmeira Road, Bexleyheath, Kent.

... information on the ex-U.S. Navy crystal controlled calibrator type LR1.—G. V. Haylock, G2DHV, 28 Longlands Road, Sidcup, Kent.

... details of a machine that prints Morse code as it comes through on a receiver.—G. M. Breckin, 161 Longside Road, Holcombe Brook, Bury, Lancashire.

... AR77E handbook or circuit, to buy or loan.—A. D. Besford, 49 Blake Road, Great Yarmouth, Norfolk.

... manual on the 46 set.—A. Giles, 20 Fieldway, Dagenham, Essex.

... the circuit of the W.S. 19 Mk. 3 'B' set and the issues of P.W. dealing with Versatile Double Trace Oscilloscope.—P. Mellor, 219 Allerton Road, Liverpool 18.

... an old German transceiver in a wooden case, range 3-6 Mc/s. The only markings on it are Type Ha5 K 39c 12V=100-220V. F.Nr. 1711/brd 1942. The valves are of an unusual side-contact type.—R. Edger, Adenac, 148 Freshfield Road, Brighton 7.

... details of the S-meter circuitry in the R.C.A. AR88LF receiver.—A. J. Jenkins, 2 Dunvegan Close, West Molesey, Surrey.

... circuit or manual on receivers BC779, MCRI, Hammarlund 'Super Pro'. In return, can help on service sheets 1925-65 and back issues of various magazines etc.—W. Pryce, 34 Heol Padell, Swansea Road Est., Merthyr Tydfil, Glamorgan.

... Information as to the whereabouts of a tuning Indicator which fits in at the side of and behind the tuning scale of a 1935 Telsen receiver. I want to replace this component. The model number of the Telsen receiver may be D5852.—W. Wright, Muirpark House, Tranent, East Lothian, Scotland.

... Information on the conversion of general coverage to bandspread coils (on amateur bands) for the H.R.O. receiver.—N. Page, 39 Stanley Road, Wellingborough, Northamptonshire.

... circuit and any information at all on G.M. Compass Mk. 4 amplifier type A, having an A.M. ref. No. 6B/2036. It is made by Sperry Gyroscope Co. The unit contains 3 x CV136, CV138, CV135. On front panel is one 6-pin socket. On the side under the heading modifications are the numbers B39, B57, B79, B111, B120 and B159 and a serial number SE/R10/56.—M. Hardisty, Gleneagle, Carlton, Carlisle.

... information, diagram or even notes on the R1475.—T. R. Smith, 36 Homestall, Park Barn, Guildford, Surrey.

TAPESPENDENTS WANTED

Sir,—I would like to tapespond with...

... any female enthusiast of my own age (18) 7½, 3½, and 1½ i.p.s., 7in. reels and Collaro Studio Deck.—Peter J. Russell, 71 Bray's Road, Sheldon, Birmingham, 26.

... anyone from Australia, New Zealand and South Africa. I am 16 years old and my interests are Hi-Fi, stereo reproduction and radio. My recorder is a Ferrograph 2 track 3½ and 7½ i.p.s. and spool size is up to 7in.—Robert Fisher, 26 Grange Road, Plympton, Devon.

WANTED

... I have assembled the Signal Generator from page 703 of the December 1961 issue of P.W. and would like to know if any reader could help me with data for winding my own coils as they are not available on the Indian Market.—D. P. De, C.P.C. Office, P.O. Durgachak, Dist. Midnapore, West Bengal, India.

SWITCHED F.M. TUNER

by W. Groome

AUGUST/SEPTEMBER 1967 "PRACTICAL WIRELESS"
The value of R21 is quoted as 220 Ω —this is incorrect and should read 220k Ω .

In Fig. 2, page 251, the jumper wire from hole Q21 should lead to V33, to which R10 is also connected. Hole V32 should be a conductor break.

Referring to Fig. 4, page 252, two rows of lettering are given for the leads of Tr1 (OC171) which conflict with each other—only the upper row is correct.

DE LUXE PLAYERS

4-Speed Mono Players 2-tone Cabinets 17" x 15" x 8 1/2". High flux loudspeaker and High Quality Amplifiers ready built. Quality output. Volume and Bass control. Special instructions enable assembly in 30 minutes, only 5 wires to join. 12 months' guarantee.

TO BUILD YOURSELF

Post 2/6 per item.
PORTABLE CABINET As illustrated. To fit standard player or autochanger. **69/6**
RCS AMPLIFIER 3 WATT. Ready made and tested with UCL82 triode pentode valve **59/6**
SINGLE PLAY MONO BSR GU7 **24.19.6**
Garrard SRP12 **24.19.6**
Garrard SP25 **210.19.6**
Philips AG1016 **212. 9.6**
Garrard A.70 **219.19.6**
Garrard LAB80 **224.19.6**
Garrard 401 **229.19.6**
All with mono cartridge (Stereo 12/6 extra)

SUPERIOR AMPLIFIER. Ready made and tested. Guaranteed better sound! Fully isolated AC Mains Transformer 4 watt output. ECL82 triode pentode valve. Volume and tone controls with knobs. Quality Loudspeaker. **89/6**
AUTOCHANGE MONO BSR Superium **25.19.6**
Garrard 1000 **25.19.6**
Garrard 2000 **26.19.6**
Garrard 3000 **28. 9.6**
Garrard AT60 Mk. II diecast turntable **212.19.6**

GARRARD TEAKWOOD BASE WB.1. Ready cut for mountings 1000, 2000, 3000, SP25, AT60. GARRARD PERSPEX COVER SP.1. for WB.1 59/-

A.18 TRANSCRIPTION TONE ARM with tracking template and two place-in shells. Original price £13.19.6. OUR PRICE **90/-**
Decca Deram Stereo Diamond Cartridge £4.10.0 extra.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
1in. 14/6 1in. 15/9 1in. 18/- 1in. 20/6 2 1/2in. 37/9
1in. 14/6 1in. 18/- 1in. 18/6 1in. 22/8 2 1/2in. 44/6
1in. 15/6 1 1/2in. 18/- 1in. 20/- 2in. 34/3 1in. sq. 31/6

ACOS XTAL GP67 PICK-UP ARM Complete, 15/-
ACOS LP-78 Turnover Head and Stylus 20/-; Stereo 30/-
SPEAKER FRET Tykan various colours. 52in. wide, from 10/-; 26in. wide from 5/-; 12in. SAMPLES S.A.E.
EXPANDED METAL GID or Silver 12" x 12in. 6/-.

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 8/9; 2 1/2 amp. 11/3; 4 1/2 amp. 17/6.
CHARGER TRANSFORMERS. P. & P. 2/6. Input 200/250 v. for 6 or 12 v. 1 1/2 amps. 17/6; 2 amps. 21/-; 4 amps. 25/-.
MOVING COIL MULTIMETER TK 25. 0-1000v. A.C./D.C. ohms 0 to 100k. **47/6**
MOVING COIL MULTIMETER EP10K. 0-1000v. A.C./D.C. ohms 0 to 3 meg. etc. **79/6**
MOVING COIL MULTIMETER EP20K. 0-2000v. D.C. 20,000 ohms per volt. 0-10,000v. A.C. Ohms 0 to 6 meg. 50 Microamps full scale. **99/6**

NEW MULLARD TRANSISTORS
OC71 6/-; OC72 7/6; OC81 6/-; OC91 6/-; AF115 8/-; AF114 8/6; OC44 8/-; OC45 8/-; OC171 9/-; OC170 9/-; AF117 7/-; OC26 12/6; AD140 15/-; OC35 15/-; Holders 1/3.

ARDENTE TRANSISTOR TRANSFORMERS
D3035, 7.3 CT. 1 Push Pull to 3 ohms for OC72, OC81. 11/-
D3034, 1.75:1 CT. Push Pull Driver for OC72, OC81. 11/-
D3058, 11.5:1 Output to 3 ohms for OC72, OC81. 11/-

TRANSISTOR MAINS ELIMINATORS. FAMOUS "POWER MITE". 9 VOLT. SAME SIZE AS PP3 BATTERY. FULLY SMOOTHED. 150mA. FULL WAVE CIRCUIT. **45/-**
SPECIAL 9 VOLT 500mA POWER PACK. 49/6

WEYRAD P50 — Transistor Coils
RA2W 6 in. Ferrite Aerial with car aerial coil. 12/6
One P50/1AC. 5/4
P50/2CC 470 kc/s. 5/7
3rd I.F. P50/3CC. 8/-
Spare Cores. 12/6
Driver Trans. LFDT4. 9/6
Printed Circuit. PCA1. 9/6
W.B. Tuning Gang. 10/6
Weyrad Booklet. 2/-

VOLUME CONTROLS
Long spindles. Midget Size 5 K. ohms to 2 meg. LOG or LIN. L/8 3/-. D.F. 5/6.
STEREO L/8 10/6. D.F. 14/6.

COAXIAL PLUG 1/-. PANEL SOCKETS 1/-. LINE SOCKETS 2/-. OUTLET BOXES, SURFACE OR FLUSH 4/6.
BALANCED TWIN FEEDERS 1/-. yd. 80 or 300 ohms.
TELESCOPIC CHROME AERIALS. 8in. extends to 23in. 6/6 each. CAR AERIAL PLUGS 1/6. Sockets 1/3.

SPECIAL PURCHASE!
B.S.R. GU7
9 volt Battery
Operated Record
Player Decks
4 speeds, automatic stop. Plays any size record. Complete with mono LP/78 xtal and sapphire stylus. **69/6** P. & P.
(With stereo cartridge 12/6 extra). ONLY 5/6

RETURN OF POST DISPATCH Post and Packing 1/6 unless otherwise stated, C.O.D. 5/- extra. Full List 1/-.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON

Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

THE E.A.R. RECORD PLAYER CABINET

Sturdily built wooden cabinet covered in Blue and Grey leathercloth. Size 15" x 17" x 8in. Motor Board 14" x 12in. ready cut out for B.S.R. Monarch UA12/14/15/16/25 decks. Gilt fittings, strong carrying handle. Amplifier space size 14" x 7" x 3in. is completely enclosed. The baffle board is cut out for a 6in. dia. speaker. Post 5/6. 59/6

NEW TUBULAR ELECTROLYTICS CAN TYPES
2/350 v. . . . 2/3 100/25 v. . . . 2/6 8/800 v. . . . 9/6
4/350 v. . . . 2/3 250/25 v. . . . 2/6 18/800 v. . . . 12/6
8/450 v. . . . 2/3 500/25 v. . . . 4/6 18+18/500 v. 7/6
16/450 v. . . . 3/- 8+8/450 v. . . . 3/- 32+32/450 v. 9/-
32/450 v. . . . 3/9 8+16/450 v. . . . 3/9 80+80/350 v. 7/6
25/25 v. . . . 1/9 16+16/450 v. 4/3 60+100/350 v. 11/6
50/50 v. . . . 2/- 32+32/350 v. 4/6 100+200/275 v. 12/6
SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250 mfd. 15v. 2/8; 500, 1000 mfd. 12v. 3/6; 2000 mfd. 25v. 9/6.
CERAMIC 500 v. 1 p.f. to 0.01 mfd. 9d. Discs 1/-.

PAPER TUBULARS
350v.-0.1 9d., 0.52/6; 1 mfd. 3/-; 3 mfd. 150v. 3/-.
500v.-0.001 to 0.05 9d., 0.11/-; 0.25 1/6; 0.5 3/-.
1.000v.-0.001, 0.002, 0.004, 0.01, 0.02, 0.04, 0.1, 0.2/6.
E.T. CONDENSERS. 0.001 mfd. 7kV, 6/6; 20kV, 10/6.
SILVER MICA. Close tolerance (plus or minus 1 p.p.), 5 to 47 pF. 1/-; ditto 10 50 to 800 pF. 1/-; 1000 to 5000 pF. 2/-.
TWIN GANG. "0-0" 208 pF. +178 pF. 10/6; 365 pF. minia-
ture 10/-; 500 pF. standard with trimmers, 9/6; 600pF.
midset less trimmers, 7/6; 500 pF. slow motion, standard 9/-;
small 3-gang 500 pF. 15/6. Single "0" 365 pF. 7/6. Twin 15/6.
SHORT WAVE. Single 10 pF. 25 pF. 50 pF. 75 pF.
100 pF. 180 pF. 5/6 each. Can be ganged. Couplers 9d. each.
TUNING. Solid dielectric. 100 pF. 300 pF. 500 pF. 8/6 each.
TRIMMERS. Compression ceramic 30, 50, 70 pF. 9d.
100 pF. 150 pF. 1/3; 500 pF. 1/6; 600 pF. 750 pF. 1/6.

250v. RECTIFIERS. Selenium 1 watt 100mA 5/-; BY100/10/-.
CONTACT COOLED 1 watt 60mA 7/6; 85mA 9/6.
Full wave 75mA 10/-; 150mA 19/6; T.V. recta. from 10/-.

NEW B.A.S.F. LIBRARY BOXED TAPE
7 in. L.P. 1,800 ft. 45/-; 7 in. D.P. 2,400 ft. 70/-
60 min. Cassette C60 (For Philips, etc.) 17/6
Spare Spools 8/6. Tape Splicer 5/-, Leader, Tape 4/6.
Tape Heads: Collaro 2 track 23/6. B.S.R. 4 track 39/6.

MAINS TRANSFORMERS

250-0-250 80mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 25/-
350-0-350 80mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 29/6
MT. 510/300-0-300V. 10mA. 6.3 v. 4 a. 29/6
MINIATURE 250 20 mA. 6.3 v. 1 a. 10/6
MIDGET 250 45 mA. 6.3 v. 2 a. 15/6
SMALL 250-0-250 50 mA. 6.3 v. 2 a. 19/6
HEATER TRANS. 6.3 v. 1 a. 8/6; 6.3 v. 4 a. 10/6
Ditto tapped sec. 1.4 v. 2.3 a. 5 v. 5.3 v. 1 1/2 amp. 10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 250 mA. 25/-
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 42, 60, 29/6
AUTO TRANSFORMERS 0-115-230 v. Input/Output, 80w. 18/6; 150w. 25/-; 500w. 92/6; 1000w. 175/-.

CRYSTAL MIKE INSERTS

1 1/2 x 1in. 6/6; BM3 1 x 1in. 7/6; ACOS 1 1/2 x 1in. 8/6
MOVING COIL MIKE with Remote Control Switch. 19/6
ALL PURPOSE HEADPHONES
MOVING COIL HEADPHONES 100 ohms (ex. Govt.) 12/6
H.R. HEADPHONES 2000 ohms. 12/6, 4000 ohms. 15/-
H.R. HEADPHONES 2000 ohms Super quality 25/-.

1967
GRAM
CHASSIS
Post 5/-
Three Wavebands: Long, Med. Short, Gram. EBC. EL84, EZ80.
12-month guarantee. A.C. 200-250 v. Ferrite Aerial
5 watts 3 ohm. Chassis 13 1/2in. x 7in. x 5in. dial size
13in. x 4in. Two pilot Lamps. Four Knobs. **£10.10**
Aligned calibrated. Chassis isolated from mains.
DE LUXE STEREO GRAM CHASSIS V.H.F. M.W. SW
19-50cm. SW 60-180m. Magnetic eye, push buttons. **£19.19**
6 valve plus rect. Size 15 x 7 1/2 x 6in. high.

TAPE DECK AMPLIFIERS FOR B.S.R. T.D.2 ETC.
With Pre Amplifier, Oscillator, all valves, "magic eye" tuning
indicator, 3 watt 3 stage amplifier especially built for B.S.R.
T.D.2 Tape Deck. Boils directly to tape deck chassis. Inputs
for mike and record. Output 3-5 ohms. A.C. 200/250v.
Ready built. PRICE 27/18.6. Carriage and Insurance 5/6.

BLANK ALUMINIUM CHASSIS 18 a.w.g. 2 1/2in. sides,
7 x 4in. 5/6; 8 x 7in. 6/6; 11 x 3in. 8/6; 11 x 7in. 7/6;
13 x 9in. 9/6; 14 x 11in. 12/6; 15 x 14in. 15/6;
ALUMINIUM PANELS 18 a.w.g. 12 x 12in. 5/6; 14 x 9in.
4/6; 12 x 8in. 3/6; 10 x 7in. 2/6; 8 x 6in. 2/-; 6 x 4in. 1/6.

ALL PURPOSE TRANSISTOR PRE-AMPLIFIER
Gain 14:1. 250v. or 9v. Input. Ready built with Mu Metal
input transformer for Mike/Pick-Up. Tuners
Instructions and circuit supplied. Post 2/6. **15/-**

THE INSTANT
BULK TAPE
ERASER AND
RECORDING HEAD
DEMAGNETISER
200/250 v. A.C.
Leaflet S.A.E. **Post 35/-**

BAKER MAJOR "MODULE"



Ideal mono or stereo conversion cabinet, existing cabinets, furniture etc. 12in. Baker Major Full range speaker on 18" x 12in. baffle board with 2 1/2in. tweeter and crossover. Output 30 watts. Response 30-17,000 c.p.s. Impedance 15 ohms. In kit form with instructions

£10.19.6

or fully assembled


£12.10.0 Post Free

'Group 25' 12in. 5 gns. 'Group 35' 12in. 8 1/2 gns. 'Group 50' 15in. 18 gns.


Quality Horn Tweeters 3-16kc/s. 10w. 27/6. Crossover 14/6.
LOUDSPEAKERS P.M. 3 ORMS. 25in. 3in. 4in. 5in., 7in. x 4in. 15/6 each 8in. 22/6; 6in. 18/6; 10in. 30/-; 12in. 30/-; (15 ohms 35/-); 10 x 6in. 30/-; 8 x 5in. 21/-; E.M.T. Double Cone 13 1/2 x 5in., 8 or 15 ohm models. 45/-
SPECIAL OFFER! 1 ohm. 2 1/2in. 5in. 8 ohm. 2 1/2in. 7 1/2in. 15/6 25 ohm. 5in. 6 x 4in. 35 ohm. 3in. 5in. 7 x 4in. EACH—ANY TYPE 15 ohm. 3in. 5in. 7 x 4in., JACK SOCKET Std. open-circuit 2/6. closed circuit 4/6; Chrome Lead Socket 7/6. DIN 3-pin 1/3. 5-pin 1/6; Lead 3/6. Photo Plug 1/-; Socket 1/6. JACK Plug 8d. Chrome 8d. 2.5mm.; 3.5mm.; 7/6; DIN 3-pin 3/6; 5-pin 5/6.

WAVE-CHANGE SWITCHES WITH LONG SPINDLES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 3/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 3/6 each. 4-way. CHANGE "MAKETS" 1 p. 12-way, 2 p. 6-way 3 p. 4-way. 4 p. 3-way, 6 p. 2-way. Prices include click spindles, adjustable stops, spaces, etc. 1 waler. 10/6; 2 waler. 15/-; 3 waler. 19/6. TOGGLE SWITCHES. 2 p. 2/-; sp. 2/-; 3 p. 2/-; 4 p. 2/-; 5 p. 2/-; 522 p. 2/-;

BARGAIN OPPORTUNITIES

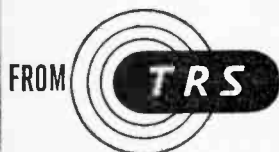

FREE LIBRARY WALLET ONLY FROM T.R.S.

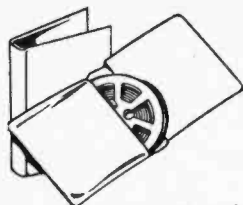

With each reel of this tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with space for a reel of tape each side. This is professional quality full frequency tape with metallised leader/stop folios. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

7in. reel 1800ft. with wallet **22/6**

5in. reel 900ft. with wallet **12/6**
p. & p. 1/6 per reel
5 1/2in. reel 1200ft. with wallet **17/6**
or 7in. reel 1200ft.

GARRARD UNITS & PLINTHS

LM 3000 Record Player with 9T.A. Stereo Cartridge. Brand new as from factory ... **8 gns.**

AT.60 Mk II De-luxe Auto-changer, die-cast turntable. Less cartridge **£10.19.6**

SP.25 De-luxe single record player, die-cast turntable. Less cartridge **9 1/2 gns.**

Packing and carriage on any one of above 7/6 extra.

Garrard Plinth. Ideal mounting for the Garrard Units offered here. Will readily suit any hi-fi set-up. In fine Teak. Complete with useful soft plastic dust cover. Packing and carriage 5/- **75/-**

Garrard clear-view rigid perspex cover (carriage 3/6) **57/6**

Garrard Mono Cartridges from 15/-; Stereo from 25/-.

T.R.S. MULLARD AMPLIFIERS


STEREO 10-10

Valve amplifier to exact Mullard spec. With pre-amp tapped off transformer 3 and 15Ω, all controls, H.T. and L.T. outlet, mono, stereo and speaker phase switching. Complete with escutcheon, knobs, plugs, etc.. Ready built. **£20.0.0** (p. & p. 12/6)

Kit form due shortly **£17.10.0** (p. & p. 12/6)

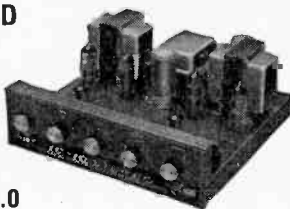3-3 MONO

3 valve 3W amplifier with controls, absolutely complete kit including panel, knobs, etc. (p. & p. 7/6) **£7.10.0**



5-10 MONO

5 valve, 10W basic amplifier kit complete. (p. & p. 7/6) **£9.19.6**

with passive control network and panel **£11.19.6**
2 valve pre-amp kit **£8.12.6**

7 VALVE AM/FM RG REPLACEMENT CHASSIS

A superbly powerful high performance instrument for the keenest enthusiasts. Provides tuning on long, medium and F.M. wavebands. Excellent sensitivity. Permeability tuning on F.M. Large clear dial, A.V.C., good neg. feedback. Magic eye, 3W output. A.C. 200/250V. Circuit diagrams available. Aligned, tested and ready for use (Carr. and Insurance 7/6). **£13.19.6**
S.A.E. brings full details.

VEROBORD—All standard sizes including 24in. x 5in. 3/8; 24in. x 3 1/2in. 3/-; 3 1/2in. x 5in. 5/2; 3 1/2in. x 3 1/2in. 3/8; 24in. x 17in. 12/6. All accessories and tools in stock.

RESISTORS—Modern ratings, full range 10 ohms to 10 megohms. 10% 1/4W, 4d. each; 20% 1W, 6d. each; 2W, 8d. each; 5% Hi-stab. 1W, 5d. each; 1W, 6d. each; 1/2-10 meg. 10% 1/4W, 4d. each; 1/4W, 5d. each. 1% Hi-stab. 1/4W, 1/8 each (below 100Ω, 2/- each).

WIREWOUND RESISTORS—25Ω to 10kΩ 5W, 1/6 each; 10W, 1/9 each; 15W, 2/3 each.

CONDENSERS—Silver Mica. All values 2pF to 1,000pF, 6d. each. Ditto ceramics. 8d. Tub. 450V T.C.C., etc. 0.001-0.01mF, 10d. each; 0.1-350V, 10d. each; 0.02-0.1mF, 500V, 1/- each. T.C.C. 350V 0.25, 1/9 each; 0.5, 2/- each. **CLOSE TOL. 8/MICAS**—10% 5-500pF, 9d.; 600-5,000pF, 1/-; 1% 2-100pF, 11d.; 100-250pF, 1/2; 270-800pF, 1/-; 800-5,000pF, 2/-.

ALUMIN. CHASSIS—18g. Plain undrilled, folded four sides. 2in. deep, 6in. x 4in., 4/6; 8in. x 6in., 5/8; 10in. x 7in., 6/8; 12in. x 6in., 7/6; 12in. x 8in., 3/- each.

ALL SINCLAIR PRODUCTS STOCKED AS ADVERTISED

OUR NEW LISTS

feature more lines than ever at money saving prices. For latest issue please send

6d.

Please include S.A.E. with all enquiries.

TRS RADIO COMPONENT SPECIALISTS

Established 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Tel.: 01-684 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays
A few doors from Thornton Heath Stn. (S.R. Victoria section.)

THE NEW RICHARD ALLAN MID-RANGE & TWEETER MODULE

(£9.7.10 inc. P.T.)

The Mid-range and Tweeter Module is a further development of the well established High Fidelity Module, and is similar to it in that it consists of 5" and 4" units mounted on a rectangular aluminium plate. However, different cone and magnet assemblies are utilised to suit the specialised purpose for which it is intended.

Ideal for adding to existing systems for extra sparkle, filling in the "hole in the middle," or including in new designs, the Mid-range Module is complete with crossover network and is fitted with a sensitivity control for ease of matching to various loudspeakers.

SPECIFICATION

Frequency Range

500-17,000 Hz.

Power Handling

For use with systems up to 20 watts.

Impedance

8 or 15 ohms.

Mid-range unit

5" dia. 12,000 lines, 1" pole.

Tweeter unit

4" dia. 10,000 lines, 1/2" pole.

Size

11" x 6 1/2" x 2 1/4" deep
(28 x 16.5 x 6.4 cm.).

Weight

3 1/2 lbs. (1.6 Kg.).



RICHARD ALLAN RADIO LTD

Bradford Rd, Gomersal,
Cleckheaton, Yorkshire
Tel. Cleckheaton 2442

Richard Allan

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME.....Block

ADDRESS.....Caps.

.....Please

11/67

BRITISH NATIONAL RADIO SCHOOL

WIRELESS INTERCOM

P. J. SMITH

IN order to make a portable intercom system which did not need long wires to join the units, the author decided to make use of the mains wiring in the house to carry the signal from one unit to the other. After much experimenting, this design was produced, bearing in mind two main considerations: simplicity and low cost.

Circuit Description

The audio signal is carried over the mains from one unit to the next by an r.f. carrier wave. Each unit, therefore, consists of an r.f. oscillator and a receiver. It was found that if a high enough r.f. was used, the ordinary "tank" circuit would quite well enough eliminate the mains frequency from the input to the receiver. In fact, in the prototype model, the mains voltage appearing across the coil L1 was of the order of a few microvolts.

A circuit diagram of the unit is given in Fig. 1. All units are the same. The r.f. oscillator just consists of a one-transistor Hartley oscillator circuit which provides enough power for the purpose. The oscillator transistor is Tr2. The receiver circuit, L1, D1, Tr1, Tr3, was chosen for its simplicity and low quiescent current (with good transistors it is in the order of $30\mu\text{A}$). This means that the units may be left in the receive position for stand-by, and attention may be called by sending out a buzz along the mains which will be received and amplified and delivered through the earphone. This buzz may be produced by pressing S3, which makes the oscillator "howl". This produces a loud enough noise to attract attention in a normal room. If, however, this method is not found to be satisfactory, then S3 can be removed and R3 replaced by a relay operating at about 5mA. The contacts of the relay are connected into a buzzer circuit as in Fig. 2. The input signal raises the current in the receiver to about 10mA.

When in operation, bias for Tr1 is provided by the d.c. component from D1 in rectifying the r.f. signal. It *must*, therefore, be connected in the sense shown. Tr1 draws its current from B2 via the base-emitter of Tr3, and in doing so biases Tr3. The gain of the circuit is quite high, and it provides ample amplification to drive the earphone, or a small loudspeaker if matched by a transformer put in place of R3. However, in order to save money, it was decided to use one earphone for both microphone and earphone. This has proved to be very successful.

The necessary switching (send-receive) is carried

out by S1, which also switches the oscillator and receiver power supply from B1, and the live side of the mains to the oscillator output or receiver input. **Great care must be taken at all times while the unit is not guarded. Lethal shocks can easily result from carelessness.**

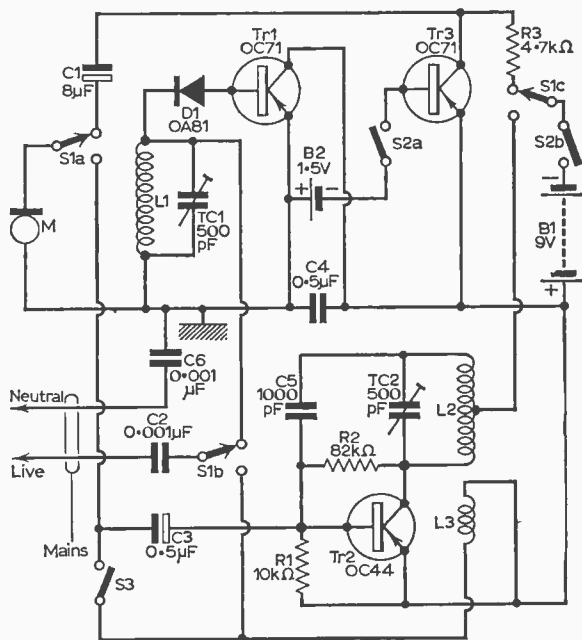


Fig. 1: Complete circuit of the wireless intercom.

S2 is the master on/off switch. This switches off the intercom unit, but does **not** disconnect the mains supply. No attempt must be made to replace B2 by tapping B1. The life of B2 is quite long since Tr1 only draws $10\mu\text{A}$ when in use. Also, the emitters of Tr1 and Tr3 *must* be separate as regards d.c. The return path for a.c. is provided by C4.

Construction

No great care need be taken in the layout of components except that ideally L1 should be screened from L2. In the author's model, each unit was mounted in a 6 x 6 x 3in. junction box divided down the centre by an aluminium screen. The

★ components list

Capacitors:

C1 8 μ F electrolytic 15V
C2 0.001 μ F 750V
C3 0.5 μ F electrolytic 15V
C4 0.5 μ F 250V
C5 1000pF
C6 0.001 μ F 750V
TC1 500pF trimmer

Resistors:

R1 10k Ω
R2 82k Ω
R3 4.7k Ω
all $\frac{1}{4}$ W 10%

Switches:

S1 3-pole 2-way
S2 2-pole 2-way
S3 1-pole 2-way

Semiconductors

Tr1 OC71
Tr2 OC44
Tr3 OC71
D1 OA81


Coils:

L1 90 turns 30 s.w.g. on 1 $\frac{1}{2}$ in. former
L2 90 turns 30 s.w.g. on 1 $\frac{1}{2}$ in. former tapped at 45 turns
L3 12 turns 30 s.w.g. wound on top of L2, 6 turns either side of the centre tap

Miscellaneous:

High impedance earphone (2000 Ω), 9V battery, 1.5V battery.

Fig. 2: Circuit showing alternative arrangement giving bell or buzzer operation to provide more positive calling.

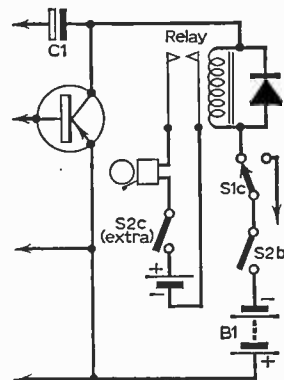

receiver and batteries were put on one side, and the oscillator and switches on the other. Both the oscillator and receiver components were mounted upon tag boards.

While this design is ideal for use around the house, or from house to garage etc., in the author's case, it cannot be used between houses. Other constructors may find that limited house to house communication may be obtained—depending on what mains filtering exists, i.e. in the electricity meter, etc.

Note: The author is at present working on an audio phase-shift oscillator "call" system details of which will be included in an early issue.

SEMICONDUCTOR AUDIO

—continued from page 501

The voltage gain can be closer to unity than for the simple complementary output stage, and the four transistors together constitute a push-pull current amplifier that lowers the impedance level at the input to the loudspeaker, like a single emitter-follower (grounded-collector) stage, but with more power and a higher efficiency.

In the absence of a driver transformer, conditions in the single-transistor driver stage are considerably altered, and greater demands are made upon it. Since the output stage is basically the equivalent of an emitter-follower (see Fig. 4) with a voltage gain less than unity, the driver stage has to develop rather more than the loudspeaker voltage, and its quiescent voltage will be close to that of the mid-point of the output transistors, in order to accommodate the maximum signal swing between the positive and negative supply lines. Direct coupling is used between the driver and the complementary output (or driver) transistors, one reason being that there is no polarising voltage available at this point for an electrolytic capacitor.

The problem in a transformerless driver stage is therefore to produce sufficient drive for full output without incurring distortion. Under maximum signal conditions, the collector current moves towards zero on one peak, and the amplification will decrease. On the other peak, the collector voltage approaches its minimum. These opposite extremes on alternate half-cycles, added sometimes to the effect of unsymmetrical arrangements in the output stage, will tend to make the half-cycles unequal, introducing even-harmonic distortion.

A bootstrapped driver can provide the large amount of drive required with less distortion. The principle, as shown in Fig. 4, is to make an a.c. connection from the output of the output stage to the upper end of the driver load resistance R2

(470 Ω). The smaller 180 Ω resistance, R1, comes effectively in parallel with the load R_L of the output stage, and its only effect is slightly to reduce the value of the load R_L.

The bootstrap connection reduces the shunting effect of R2 across the driver output and increases the effective load impedance of the stage. The voltage amplification is therefore increased, typically three or four times.


If the output impedance of the driver transistor is high, bootstrapping will cause most of the local negative feedback of an emitter-follower type of output stage to be lost, thus converting it into what is virtually a grounded-emitter stage. This implies an increase of distortion in the output stage, but the loss of local negative feedback can be more than made up by overall negative feedback.

An important point to observe is that the bootstrap capacitor, which is charged to about half the supply voltage, will carry the top end of the driver load resistance, R2, to a potential above the upper supply line on one half cycle at maximum output. The effective supply voltage is therefore increased for the driver stage, enabling the required voltage swing to be produced with a smaller change of current. This allows a larger output voltage to be obtained than would otherwise be possible without a driver transformer, and the two peaks are more nearly equalised, even before negative feedback is applied.

In low-power amplifiers, the coupling capacitor to the loudspeaker also serves as the bootstrap capacitor (see Fig. 1). The loudspeaker is then returned to the upper supply line and carries the current of the driver stage. A separate and much smaller bootstrap capacitor, 20 or 25 μ F, is used in fidelity and high power amplifiers, and the loudspeaker can then be earthed to the lower supply line.


To be continued

SINCLAIR Q.14

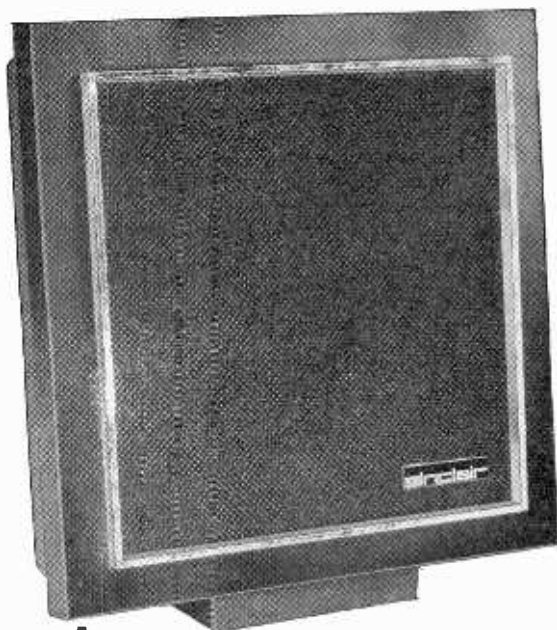

a no-compromise
high fidelity
loudspeaker

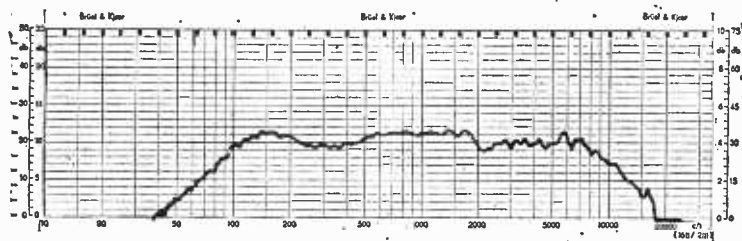- ACOUSTICALLY CONTOURED SOUND CHAMBER
- POWER HANDLING CAPACITY IN EXCESS OF 14 WATTS
- 15 OHMS IMPEDANCE
- AN ALL-BRITISH PRODUCT



INDEPENDENT TEST REPORT

The above curve was taken by an independent testing laboratory and shows clearly why the Sinclair Q.14 achieves such remarkable standards of reproduction. Level response is maintained to assure the user of the finest possible results from the equipment to which the speaker is coupled.

Note—curve taken against vertical 0–25 dB range and plotted on a log. scale.

CONSTRUCTION

The seamless sound, or pressure chamber and mounting baffle are of special high-density ultra-low resonance materials made possible by modern bonding and processing techniques to ensure freedom from spurious coloration.

LOADING

The Sinclair Q.14 has an input impedance of 15 ohms and will comfortably accept loading in excess of 28 watts music power, far greater than that required for average listening requirements.

FREQUENCY RESPONSE

As the independently made test curve shows, remarkably smooth response is maintained between 60 and 15,000 c/s.

DRIVER UNIT

This is a specially designed unit having

exceptionally high compliance due to the method of cone suspension employed. It has a massive ceramic magnet of 11,000 gauss and aluminium speech coil, with the cone treated to ensure brilliant transient response.

CONTOURED PRESSURE CHAMBER

The shape of the sealed sound chamber has been determined mathematically to ensure forward sounding presence and freedom from directional effect. Connections at rear are marked for correct phasing.

SIZE AND STYLING

The Sinclair Q.14 measures 9½ in. square on its front face by 4½ in. deep from front to back. A separate base for free standing position is provided as well as a template for wall or flush mounting. A neat solid aluminium bar inset is used to embellish the front.

*The most challenging
loudspeaker development
in years*

Listen to a Q.14. Hear it in your own home. Then marvel at its performance. The Q.14 is the result of long and thorough investigation into speaker design and behaviour in order to produce one which would out-perform anything within pounds of its price and provide genuine high fidelity standards. How far we have succeeded can be seen from the independently taken test report. It compares excellently with loudspeakers over four times the price. The Sinclair Q.14 is uncommonly versatile, too. It can serve as a free-standing unit for bookshelf, etc., as a corner radiator, or be flush mounted in a multi-unit assembly for P.A. or other heavy-duty requirements. In stereo, you could not ask for better and its design is such that the Q.14 is in keeping with every kind of domestic decor.

With base-plinth, and mounting template. In fitted carton.

Your money inc. postage returned in full if not satisfied.

£6.19.6

Post Free


sinclair

Over to next pages, please

SINCLAIR MICROMATIC



Actual
Size

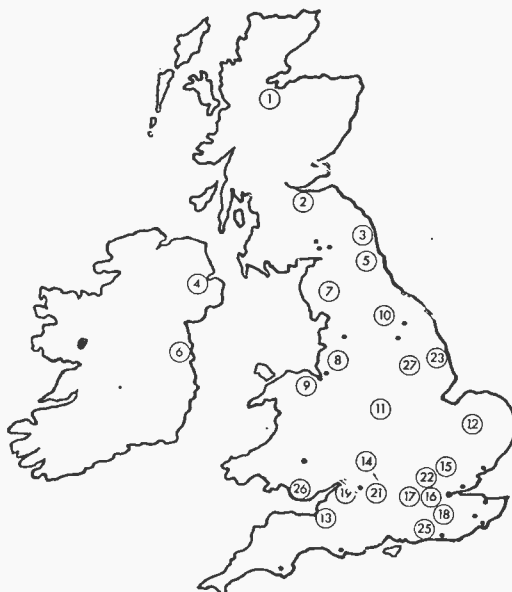

The
world's
smallest
radio

- $1\frac{4}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- SLOW MOTION TUNING OVER MEDIUM WAVEBAND
- FANTASTIC SELECTIVITY AND POWER
- A.G.C. AND BANDSPREAD

Complete kit of parts in fitted pack, with earpiece, solder, and instructions.

59/6

Built, tested and guaranteed 79/6

THE SET THAT PLAYS ANYWHERE

Until you use a Micromatic for yourself, you will never know how fantastically efficient the world's smallest radio is. We have received thousands of letters testifying to the staggering performance of this six-stage transistor set, be it for quality, range, selectivity, sensitivity, long battery life or just playing in difficult places. We have letters galore to prove the excellency of this Sinclair design. That is why it is so fully guaranteed. You can build the Micromatic—or buy it complete, ready for immediate use. The thing is to have one and prove for yourself how good this British product is.

USERS FROM ALL OVER THE COUNTRY WRITE

From North, South, East and West enthusiasts for the world's smallest radio tell us of the wonderful results they get.

- 1 I was pleasantly surprised to find I was able to have it working in a few hours.
W.J., Inverness
- 2 I would like to express my delight in the splendid sensitivity and quality.
D.G.S., Edinburgh
- 3 I find it excellent in every way.
W.A.S., Sunderland
- 4 We are very pleased with it.
J.D.W., Belfast
- 5 Satisfactory results... good compared to any other transistor of any size.
L.W.S., Stockton-on-Tees
- 6 I have found reception is quite satisfactory.
S.C., Dublin
- 7 I am very pleased with its performance.
B.M.H., Cumberland
- 8 I am very satisfied with the kit.
J.H., St. Helens
- 9 A fabulous little performer in every respect.
D.C.M., Mold, Flint
- 10 A thoroughly reliable receiver. Performance is wonderful.
H.S.M., Ripon, Yorks
- 11 Very pleased with the results.
D.T., Kenilworth

- 12 Lost for words... one of the most amazing inventions I have ever known.
L.L., Norwich
- 13 Very pleased.
J.M.H., Burnham on Sea
- 14 Amazed at such reception in these parts.
K.T.R., Gloucester
- 15 The finish and quality is very good.
N.P.C., Bishops Cleeve
- 16 Completed, and working extremely well.
C.W., Harrow
- 17 Very pleased indeed with the Micromatic.
D.M., Slough
- 18 Took only 5 hours to build and worked immediately.
P.D., Reigate
- 19 The light programme came in better than a set costing £15.
D.A.C., Bristol
- 20 Worked a treat.
F.W., Banbury
- 21 Thank you for such a brilliantly designed little set.
E.B.D., Epping
- 22 Fantastic reception from the Continent.
T.G.S., Grimsby
- 23 Stations come in marvellously for such a difficult area.
P.G.H., Brighton
- 24 A marvellous set to build and listen with.
E.K.J., Swansea
- 25 Better than anything I could ever have imagined.
W.T., Sheffield

SINCLAIR MICRO FM AMAZING DUAL PURPOSE FM TUNER/RECEIVER



- Easy to build
- Needs no aligning when built

Less than 3in. x 2in. F.M. Superhet using pulse counting discriminator for superb audio quality. Low I.F. makes alignment unnecessary. Tunes 88-108 Mc/s. The telescopic aerial suffices for good reception in all but poorest areas. Signal to noise ratio —30dB at 30 microvolts. Takes standard 9v. battery. One outlet serves for feeding to amplifier or recorder the other allows set to be used as a pocket portable. Brushed and polished aluminium front, spun aluminium dial. A fascinating set to build which gives excellent reception by any standards. Complete kit including aerial, case, earpiece and instructions.


- 7 Transistors
- Ready to use as soon as built

£5.19.6




SINCLAIR RADIONICS LTD, 22 Newmarket Road,
Cambridge
Phone OCA 3-52996

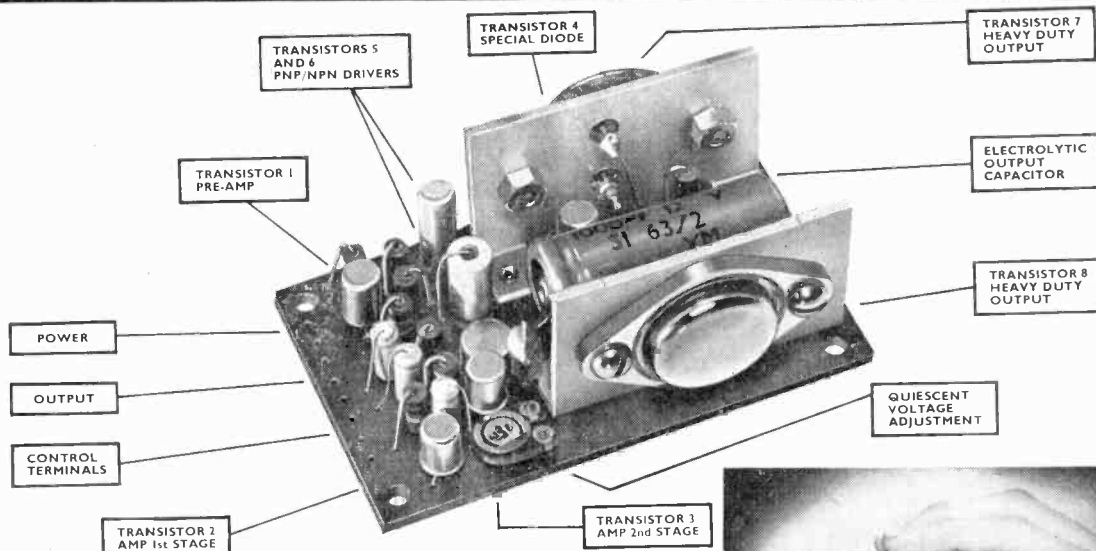THIS 12 WATT HI-FI AMP & PRE-AMP MEASURES ONLY 3" x 1³/₄" x 1¹/₄"



SINCLAIR Z.12

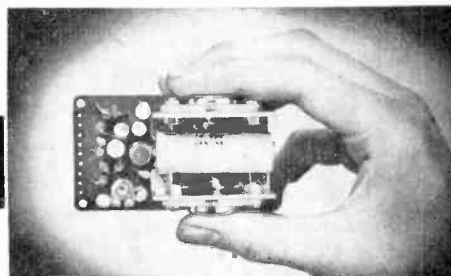

Because of its performance and very small size the Z.12 has completely revolutionised the whole approach to transistor amplifiers. It proves beyond all question that high-fidelity can be combined with very low price. No other amplifier in its field so successfully meets such a wide range of requirements. The Z.12 operates from any power supply between 6 and 20V. D.C. Its output is suitable for any impedance between 1.5 and 15 ohms, making it suitable for any loudspeaker including of course the Sinclair Q.14. This amplifier has facilities for matching to any type of conventional inputs, details of which are given in the Z.12 manual supplied.

Most popular applications for the Z.12 are in mono and stereo high fidelity systems (two are needed for stereo), guitars, electric organs, car radios and P.A. and intercom systems. Its characteristics make the Z.12 useful in many kinds of experimental work.

- 12 WATTS R.M.S. CONTINUOUS SINE WAVE OUTPUT (24W PEAK)
- 15 WATTS MUSIC POWER (30W PEAK)
- 15-50,000 c/s $\pm$ 1bB
- IDEAL FOR BATTERY OPERATION

BUILT, TESTED AND GUARANTEED.

89/6

PZ 3 MAINS POWER SUPPLY UNIT 79/6

SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question. FULL SERVICE FACILITIES AVAILABLE. If you prefer not to cut page, please quote PW11 when ordering.



SINCLAIR STEREO 25

THE SINCLAIR STEREO 25 ensures the highest possible standards of reproduction used with two Z.12s or other first-class stereo power amplifier. The front panel is in solid brushed and polished aluminium with solid aluminium knobs. Frequency response—25 to 30,000 c/s $\pm$ 1dB. Built, tested and guaranteed

£9.19.6

TO REMIND YOU

Sinclair Q.14 Loudspeaker	£6.19.6
Sinclair Micromatic Kit	59/6
Sinclair Micromatic Built	79/6
Sinclair Micro FM Kit	£5.19.6
Sinclair Stereo 25 Pre-amp	£9.19.6
Sinclair PZ.3 Power Unit	79/6

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send

.....

 for which I enclose cash/cheque/money
 order value £.....s.....d

NAME

ADDRESS

PW11

WIRECOMP ELECTRONICS

AUTUMN SALE

FAMOUS JASON EQUIPMENT
AT UP TO 50% BELOW LIST!

The high performance of this top grade equipment is internationally known—NOW due to Wirecomp's massive purchase available at up to half the original list price.

ALL MODELS FOR HOME ASSEMBLY UNLESS STATED

FMT 1 FM Tuner (illustrated)


List Price £6.15.0

SALE PRICE £3.7.6

FMT2 Powered FM Tuner

List price £10.19.6

SALE PRICE £5.10.0

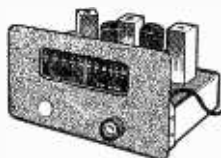

FMT2 Unpowered FM Tuner

List Price £8.15.0

SALE PRICE £4.7.6

FMT3 Powered Fringe FM Tuner

List Price £12.19.6

SALE PRICE £6.10.0

FMT3 Unpowered Fringe FM Tuner


List Price £9.19.6

SALE PRICE £5.0.0

FMT4 Fringe FM Tuner

(illustrated) As powered
FMT3 but factory built and tested.
List Price £20.0.4

Sale Price £12.12

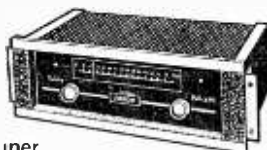

JTV2 Switched TV and FM Tuner

List Price £15.19.6

SALE PRICE £8.0.0

MERCURY II As JTV2 but unpowered.

List Price £11.11.0

SALE PRICE £5.19.6

JTL Stereo Tape Link Preamplifier

List Price £22.1.0

SALE PRICE £11.11.0

Add 5/- Post on each item. Instruction books supplied. NOTE: A few only of the above items are available fully built and tested TO PERSONAL CALLERS ONLY. ALSO a few items of Jason Test Equipment available FOR CALLERS ONLY.

**Maker's Surplus 7 Transistor
Radio Chassis**

Fully built, 500mW output. Covers 180-576M
Medium Wave and 31-94M Short Wave plus
4 band spread ranges. 5in. speaker fitted. Uses 4 x U2 batteries. Less cabinet.

SALE PRICE £4.19.6 Post 3/6

High Quality Speaker Enclosure

Made by famous British manufacturer. Soundly constructed from 1in. chip board and finished in polished medium mahogany with attractive Tygan acoustic grille. Interior fully lagged and vented. Baffle is cut for 10 x 6in. speaker and 2½in. tweeter. Size: 26 x 11 x 11in. Absolutely perfect.

SALE PRICE 39/6 (less speakers)
Carr. & Pack. 7/6.

Water Temperature Thermostats

British made, orig. for use in high quality washing machine, range adjustable between 114°F and 230°F. Rating 200/250V A.C., 20 amps (also D.C. up to 125 V.A.). Size 2½ x 1½ x 1½ with 18in. capillary tube and 6in. bulb. Single hole fixing. 3/16in. spindle.

SALE PRICE 9/11 (Today's value 32/6)
Post free

DON'T DELAY — ALL ITEMS SUBJECT TO AVAILABILITY

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1 Tel: 01-636 0647

MAIL ORDERS TO:

378 HARROW ROAD, PADDINGTON, LONDON, W.2.

Rapid Servicing of Transistor Equipment

Gordon J King

A systematic guide to the servicing of transistor radio and television receivers, tape recorders and high fidelity equipment. Directed at the service technician changing from valves to transistors, students starting a career in electronics, and the enthusiastic amateur.

160 pages

90 illustrations

30s

from all booksellers

or in case of difficulty

31s by post from

GEORGE NEWNES LTD

Tower House

Southampton St., London W.C.2

AC/HLH	6/1	E182CC10	1/6	RF184	6/6
AC74	6/1	E1148	2/6	EH90	7/6
ACOPEN65	6/1	E1266	50/-	E131	15/-
AL60	5/-	E1415	30/-	E132	3/9
AR3	3/-	E1024	12/6	E134	10/-
AR5	7/2	E101	8/1	E135	10/-
ART1	6/1	EAS0	1/-	E138	17/6
ART1P	6/1	EACB80	5/9	E141	8/-
ATP4	2/3	EAC91	3/6	E142	8/6
AT57	5/6	EAF42	8/1	E143	8/6
AZ1	6/1	EB34	1/6	E144	4/6
AZ31	9/-	EB91	3/-	E145	4/3
B6H	15/-	EB33	6/1	E146	7/6
BD78	40/-	EAC41	8/6	E151	4/6
BL63	10/-	EBP80	6/6	E155	5/6
B84	8/6	EBP83	7/6	E160	22/-
B884	37/6	EBP89	6/6	E160	6/6
B1234	18/-	E131	20/-	EM81	7/-
BT35	55/-	E132	20/-	EM84	7/6
BT45	150/-	EK53	12/6	ESU74	80/-
BT5	150/-	EC70	4/-	ESU208	6/1
BY214	7/6	EC90	6/6	EY1	7/6
CC3L	2/6	EC91	3/-	EY6	6/6
CV71	3/-	EC92	3/-	EY91	6/6
CV77	5/6	EC93	16/-	EZ40	6/6
CO2	4/6	EC81	4/-	EZ41	6/6
CV103	4/6	EC82	5/6	EZ80	5/6
CV404	7/-	EC83	8/6	EZ81	4/6
CV4014	8/-	EC85	6/6	F/6067	5/6
CV4015	7/-	EC88	9/6	F/6063	4/-
CV4016	7/-	EC91	4/-	FW4/5006/8	
CV4049	6/1	EC99	6/6	G/5006/8	
CY31	6/6	ECF0	7/-	G1370K	
D1	1/6	ECF82	7/-		20/-
D41	6/6	ECF85	12/6	G50/2G	5/6
D61	7/6	EC142	9/6	G120/1B	17/6
D93	12/6	EC143	7/6		
DA100	46	EC148	6/6	G100/2M	
DAF96	9/6	EC182	6/1	GM4	15/-
DE1	6/6	EC183	10/-	GTE1750	5/6
DET3	8/6	EC184	6/6		
DET20	2/-	EF36	3/4	G1G3	25/-
DET25	15/6	EF37A	7/-	GZ32	10/-
DF91	3/-	EF40	8/6	GZ34	10/-
DF92	3/-	EF50	2/6	I130	3/6
DF96	6/6	EF52	8/6	I131	3/6
DK92	9/6	EF53	8/6	I123	6/6
DK96	9/6	EF71	7/6	I123DD	5/-
DL3	8/6	EF72	5/6	IL41	4/-
DL32	8/6	EF73	5/6	ILV2	2/6
DL33	4/6	EF74	5/6	ILV3	2/6
DL94	5/6	EF75	5/6	KTC8	22/-
DL96	7/-	EF81	0/6	KT32	8/6
DL516	9/6	EF85	4/6	KT44	5/6
DL518	9/6	EF86	4/6	KT45	5/6
ES80C	23/-	EF99	5/6	KT66	16/6
E90CC	10/-	EF91	3/6	KT67	25/-
E92CC	5/6	EF92	5/6	KT71	5/6
E92CC	5/6	EF95	5/6	KT76	8/6
E92CC	5/6	EF98	2/6	KT78	8/6

OC16	20/-	OC81	5/-	OC201	15/-	X C142	15/-
OC22	5/-	OC81D	3/-	OC202	13/-	X C155	12/6
OC26	9/-	OC81M	5/-	OC203	10/-	X C156	15/-
OC35	12/6	OC82	8/-	OC204	15/-	2N247	9/6
OC44	4/6	OC82MD	3/6	OC206	15/-	2N412	7/6
OC45	3/6	OC83	5/-	LAZ12	5/-	2N502	19/6
OC71	3/6	OC122	5/-	ACY28	7/6	2N585	7/6
OC72	5/-	OC170	5/6	BY38	7/8	2N1090	7/6
OC73	8/6	OC200	7/6	X C141	10/-	2N1091	7/6
TS280/40	24/-	YK99	7/8	2C46	30/-	6AQ5	7/8
SC1150	10/-	VR105/30		2C51	12/6	6AQ5W	9/8
S1E12	10/-	VR150/30		2X21	5/-	6A57	4/6
TDOX-20	70/-	VU39	6/-	3A4	4/-	6AT6	4/6
TP22	70/-	VU8208	5/-	3A108A	35/-	6AU6	6/6
TP25	15/-	VU122	5/-	3A1467	55/-	6AX4	8/6
TT11	5/-	VU8124	5/-	3A167/1M	5/-	6184Q	17/6
TT15	35/-	W11	5/-	3B7	5/-	618G	8/6
TR31	45/-	W118	10/-	3D4	9/-	6BA6	5/6
TZ40	10/-	XN55	5/-	3D29	50/-	6BA7	5/6
TZ050/4	4/-	X66	7/6	3Q4	6/-	61E6	6/6
TZ20	16/-	X76M	7/6	3Q56T	7/-	61J5	7/6
U81	18/-	X81M	18/-	384	5/-	6BN6	8/6
U12/4	8/-	X118	8/-	4C37	3/6	6BQ7A	8/6
U27	8/-	XN55	5/-	4V4	3/6	6BR7	17/6
U18	6/-	Y63	5/-	4D1	4/-	6BR8	5/6
U25	13/-	Y65	4/-	5A173G	5/-	6B8W	17/6
U26	13/-	Z246A/1K		5A174D	5/-	6B97	17/6
U37	8/-	Z800U	180/-	5B351M	40/-	6B1W	17/6
U191	11/6	Z801L	10/-	5B253M	35/-	6C4	6/6
UAB801	17/-	Z800T	12/-		15/-	6C5G	6/6
UAF42	9/-	LA3	8/-	5B254M	40/-	6C6	4/6
		1A6GT	5/-	5B255M	35/-	6C8G	3/6

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K. Orders up to 10/-, 1/-; 10/- to £1, 2/-; over £1, 2/- per £1; over £3 post free. C.O.D. 4/- extra.

35W4	5/	2051	5/
35Z3	10/	4043C	35/
35Z4Q7	6/	4183C	20/
35Z6G7	6/	5676	10/
37	4/	5678	10/
38	3/	5704	9/
42	5/8	5678	7/
50CD66(2)78	6/	8060	5/8
50L6GT	3/	8084	7/
53A	7/8	8085	8/
57	6/	8080	22/
59	6/	6146	25/
59	6/	7193	1/8
75	5/8	7475	2/
76	5/	613A	25/
77	5/8	8020	15/
78	6/	9001	3/
80	5/8	9002	4/8
81	9/	9003	6/
84	8/	9004	4/
85A2	6/	9006	2/8
120VPT			
7-pin/2		C.R. Tubes	
2189G	7/	E450/B18	25/
2201A	7/		28/
2201H	7/	69J	75/
225DU	9/	VCR97	55/
282A	100/	VCR517	50/
310C	25/	VCR17B	55/
330B	5/		
357A	7/	VCR517	55/
368A	5/	3FP7	45/
368AS	30/	3EG1	40/
40C	8/	5PC1	30/
446A	8/	5FP7	25/
703A	30/	88D	
705A	10/		
715B	6/	Photo Tubes	
717A	3/	G816	12/8
803	22/8	931A	62/8
807	8/	6097	350/
808	8/		
813	7/	Special	
816	35/	Valves	
829B	50/	ACT6	38
830B	4/	CV103	
832A	45/		\$31.00
835	2/	CY2339	\$20.00
854	14/	K301	24
86A	10/	KR.N2A	
954	4/7		\$31.00
955	2/8	1B23	25/
966	2/	2223	22.10
967	5/	WL417	
988A	4/		30/
1616	3/	3J497E	
1619	5/	4871A	24
1622	10/	725A	24
1626	3/	726A	19/
1629	4/8		

TELEPHONE HANDSET. Standard G.P.O. type; new 12/-, P. & P. 2/-.

"S" Meter for H.R.O. Receivers, Brand new £2.10.0. Carriage paid U.K.

CRYSTALS for H.R.O. in original National Union Housing, 25/-, P. & P. 2/-.

VARIOMETER for No. 19 sets, 17/6, P. & P. 3/-.

INSET MICROPHONE for telephone handset 2/6, P. & P. 2/-.

SIGNAL GENERATOR TYPE TS 418. Signal frequency 400-1,000 Mc/s. direct calibration. Pulse rate 40-400 c (X1 or X10), pulse delay variable, less than 32µsec. to more than 300µsec. Pulse width variable less than 14µsec. to more than 101µsec. Polarity—internal or external sources, positive or negative pulses. AM and CW. Output attenuator 0.2pV to 200mV continuously variable. In fully tested condition, £150. Carriage paid.

FIELD TELEPHONES TYPE "F" housed in portable wooden cases. Excellent for communication in- and out-doors for up to 10 miles. For pair including batteries and 1/6th mile field cable on drum. £5.10.0. Carriage 10/-.

FIELD TELEPHONES TYPE "L". As above but in portable metal cases. Per pair including batteries and 1/6th mile field cable on drum. £3.15.0. Carriage 10/-.

COLLINS TCS MICROPHONE TRANSFORMERS. Turns ratio 4:1 Test voltage 1,000V. $1\frac{1}{2} \times 1\frac{1}{2} \times 2\frac{1}{2}$ in. Ideal for mobile and portable installations. Brand new, 10/-, P. & P. 3/-.

SUB MINIATURE "PENNY SIZE" METERS
1" round, flush, ring nut mounted 500 mA FDS, calibrated 0.1 mA, 20/-, P. & P. 3/-.

LABORATORY TYPE VOLTMETERS
160V AC/DC 8" mirror Scale in wooden boxes, 91/-, 8½" x 3½" with carrying handle, new, 32/-, P. & P. 3/-.

ALL OVERSEAS ENQUIRIES AND ORDERS:
Please address to Colomor (Electronics) Ltd., 170 Goldhawk Road, London W.12. Tel: 01-743 0899.

ALL TEST & COMMUNICATION EQUIPMENT has been thoroughly prepared in our Laboratories by fully qualified Electronic Engineers.

METERS, 4½" x 4½" x 4" long mirror scale panel mounted, calibrated 0-1mA, 55/-, P. & P. 3/-.

29/41FT. AERIALS each consisting of ten 3ft., ⅜in. dia. tubular screw-in sections, 11ft. (6-section) with aerial with adaptor to fit the 7in. rod. Insulated base, stay plate and stay assemblies, pegs, reamer, hammer etc. Absolutely brand new and complete ready to erect. In canvas bag. £3.9.6. P. & P. 10/6.

MINIATURE METERS
General Electric 1½" round flush, clip mounted: 1mA DC, 22/6; 25mA DC, 20/-; 75mA DC, 18/-; 150mA DC, 16/-, P. & P. 3/-.

A.R.88D. RECEIVERS. Fully reconditioned, £55/- Rebuilt model £85. Carriage paid U.K.

MARCONI SIGNAL GENERATOR TYPE TF144
85kc/s-25Mc/s. Excellent laboratory tested condition with all necessary accessories with instruction manual. £45. P. & P. 15/-.

BOONTON STANDARD SIGNAL GENERATOR
MODEL 80. Frequency 2-400 Mc/s in six ranges. A.M. 400 and 1,000 c/s. and external modulation. Provision for pulse modulation. Piston type attenuator, 0.1-10V 100mV. Separate meter for modulation level and carrier level. Precision flywheel. 117V. AC input with instruction manual. £95. Carriage 30/-.

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
(01) 743 4946

MINIATURE MULTIMETER TYPE ITI-1. DC voltage 0-2, 45kV (20,000ohm per volt). AC voltage 0-1000V (10,000 ohm per volt). DC current 0-250mA. Resistance 0-6 megohms. Capacitance 10pF to .1mf. Decibels -20 to +22dB. Dimensions $4\frac{1}{2} \times 3\frac{1}{2} \times 1$ in. Price £3.16.6.

MOVING IRON METERS		
15 VAC	2½" round panel	27/60
500 VAC	2½" round clip fix	25/-
P. & P. all the above 3/- each		
RADIO FREQ.: THERMO-COUPLE METERS		
350mA	2" round plug-in	14/6
1 Amp	2½" round proj.	17/6
P. & P. 3/- each		
DC MOVING COIL METERS		
0-5µA	2½" round proj.	25/-
200µA	2" round panel sealed Calibre-30	22/6
200µA	3½" round panel	30/6
750-0-750µA	2" round plug-in	20/-
1mA	2½" round clip fix, metal clad	27/6
10-0-10mA	2½" round panel	30/6
1mA	2" round panel-sealed	27/6
1mA	3½" round panel	30/6
5mA	2" round clip fix panel or proj.	20/-
0-5-5mA	1½" round panel	17/6
10-0-10mA	2½" round panel	17/6
0-30mA	2½" round panel	17/6
75mA	2½" plug in	14/6
100mA	1½" proj.	17/6
100mA	1½" round panel	17/6
100mA	2½" square panel	19/-
100mA	3½" round panel	25/-
2 Amp	2½" round panel	22/6
5-0-5 Amp	2½" round panel	25/-
8 Amp	2½" round panel	25/-
25 Amp	3½" round proj.	27/6
50 Amp	2½" round panel	27/6
20 VDC	2" square panel	19/-
150 VDC	4" round panel	25/-
1-5K V with res 2"	round panel	25/-
1500 V	Electrostatic 2½" round plug in	27/6

BI-PAK SEMICONDUCTORS

(DEPT S)

8 Radnor House
93/97 Regent St
London W1

Minimum Order 10/- CASH WITH ORDER PLEASE.
Add 1/- postage and packing per Order. GUARANTEED by
return postal service. Overseas add extra for Airmail.

Our vast stocks change daily with hundreds of Semiconductor
bargains becoming available. Just send 2/6 to cover 3 months
mailing of our latest stock lists, eqvt. charts, circuits, etc.

AF117	3/6	M	D	OA91	1/3
AF139	10/-	U	L	OA182	1/6
AF212	10/-	L	V	OA200	3/-
BC107	6/-	A	R	OA202	3/6
BC108	5/-	R	C	OC44	1/9
BFY50	10/-	D	S	OC45	1/9
BFY51	7/6			OC71	2/3
BFY52	10/-			OC73	3/-
OA5	1/9			OC76	3/-
OA10	1/9			OC81D	2/3
OA47	2/-			OC82D	2/3
OA70	1/3			OC170	2/6
OA79	1/9			OC200	4/-
OA81	1/6			OC201	7/6
OA85	1/6			ORP12	8/6

M
U
L
T
I
P
L
I
C
A
T
I
O
N
S

B
R
A
N
D
N
E
W

NEW AND TESTED VALUE PAKS

One 10/- pack of your own choice free with orders
valued 24 or over.

2 Drift Trans. 2N1225 Germ. PNP 100 Mc/s.	10/-
6 Matched Trans. OC44/45/81/81D	10/-
16 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3A 100-400 PIV	10/-
2 10A Silicon Rects. 100 PIV	10/-
2 OC139 Trans. NPN Switching	10/-
1 12A SCR 100 PIV	10/-
3 Sil. Trans. 28303 PNP	10/-
12 Assorted Computer Diodes	10/-
4 NPN Med. Speed Switching Trans.	10/-
5 Zener Diodes 250mW 3-12V	10/-
5 2G417 Trans. Eqvt. AF117	10/-
3 200 Mc/s Sil. Trans. NPN B8Y26/27	10/-
2 Bi-directional Trans. ARY66 PNP	10/-
3 Zener Diodes 400mW 33V 5% Tol.	10/-
4 High Current Trans. OC42 Epyt.	10/-
2 Power Transistors 1 OC26 1 OC39	10/-
5 Silicon Rects. 400 PIV 250mA	10/-
4 OC75 Transistors Mullard Type	10/-
3 NPN Silicon Trans. 70 Mc/s	10/-
1 Power Trans. OC20 100V	10/-
4 OA202 Sil. Diodes Sub-min.	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
8 OA81 Diodes (CV48)	10/-
4 OC72 Transistors Mullard Type	10/-
4 OC77 Transistors Mullard Type	10/-
5 Metal Alloy Transistors Mar Type	10/-
4 Sil. Rects. 400 PIV 500mA	10/-
5 GET884 Trans. Eqvt. OC44	10/-
5 GET883 Trans. Eqvt. OC45	10/-
2 GET29 Germ. PNP Trans. with Heat-sink	10/-
3 VHF Sil. Epox. Trans. NPN 100 Mc/s	10/-
2 2N708 Sil. Trans. 300 Mc/s NPN	10/-
5 GT11/45 Germ. Trans. PNP Eqvt. OC71	10/-
3 GT31 L.F. Low Noise Germ. Trans. PNP	10/-
6 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA85 Germ. Diodes Sub-min. 1N40	10/-
3 NPN Germ. Trans. NPN 773 Epyt. AC130	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
2 OC73 Mullard Trans.	10/-
4 AC138 Trans. PNP High Gain	10/-
2 AC127/128 Comp. pair PNP/NPN	10/-
10 Assorted Gold Bonded Diodes	10/-
6 TK222 Germ. Switching Trans.	10/-

BI-PAK EXCLUSIVE-SILICON TRANS.

Price	2/-	1/9	1/6	1/3	1/-
Qty.	1-24	25-99	99-499	500-999	1000 up

SILICON PLANAR DIODES. 1/- (1-99); 10d. (100-499)
6d. P.I.V. 200mA, Sub-min. 9d. (500-999); 7d. (1000 up)
ALL BRAND NEW-TESTED AND GUARANTEED.
Full Data and List of possible Replacements available.



NEW - UNTESTED DEVICES - NEW


120	Glass Sub-Min.	GERM. DIODES	10/-
50	Mixed Germ.	TRANSISTORS	10/-
20	Mixed Volts	ZENERS	10/-
30	NPN, PNP, MIXED	SILICON TRANS.	10/-
60	200mA Sub-Min.	SILICON DIODES	10/-
20	Germ. 1 Amp.	RECTIFIERS	10/-
40	Like OC81 AC 128	TRANSISTORS	10/-
10	2 Amp. Stud	SIL. RECTIFIERS	10/-
25	Sil. NPN, 200 Mc/s	TRANSISTORS	10/-
16	Top-Hat 750mA	SILICON RECT.	10/-
75	Germ. Diodes	GOLD BONDED	10/-
10	1 Amp. 50-400 PIV	SCR's	20/-

3 2N1307 PNP Switching Trans.	10/-
20 Germ. Diodes General Purpose	10/-
3 OC62H Germ. Diodes Eqvt. OA71	10/-
3 AF116 Mullard Type Trans.	10/-
12 Assorted Germ. Diodes Marked	10/-
1 30 Amp Power Rectifier 100 PIV	10/-
4 AC126 Germ. PNP Trans.	10/-
5 1 Amp Germ. Rect. 200 PIV	10/-
1 ORP61 Photo-conductive cell	10/-
4 Silicon Rects. 100 PIV 750mA	10/-
3 AF117 Trans. Mullard Type	10/-
7 OC81 Type Trans.	10/-
3 OC171 Trans. Mullard Type	10/-
3 2N2926 Sil. Epox. Trans.	10/-
7 OC71 Type Trans.	10/-
2 GKT9 Power Trans. 80VcR. 8A	10/-
25 Trans. Transistors 1018, 8012, etc.	10/-
1 TK400A Power Germ. Trans. ADY32	10/-
2 28701 Sil. Trans. Texas	10/-
2 BFY16 Sil. Trans. STC	10/-
2 Zeners Z2A150F, 15V 1W	10/-
3 BCY43 Sil. Trans. 100 mcs.	10/-
3 12 Volt Zeners 400mW	10/-
2 GKT571 Germ. Trans. OC28	10/-
2 10A 600 PIV Sil. Rects. 18425R	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
2 Zener Diodes 20W 18 and 22V	10/-
1 2N910 NPN Sil. Trans. VCB 100 80 Mc/s	10/-
2 1000 PIV Sil. Rect. 1.5A RS310 AF	10/-
3 High Volt AF Trans. PNP ACY17	10/-
3 B8Y95A Sil. Trans. NPN 200 Mc/s	10/-
3 OC200 Sil. Trans. Mullard	10/-
2 Sil. Power Rects. BYZ13	10/-
1 Sil. Power Trans. NPN 100 Mc/s TK201A	10/-
6 Zener Diodes 3-15V Sub-min.	10/-
1 2N1182 PNP Epitaxial Planar Sil. Trans.	10/-
2 2N697 Epitaxial Planar Trans. Sil.	10/-
4 Germ. Power Trans. Eqvt. OC16 Mullard	10/-
1 Unijunction Trans. 2N2646 Epyt. DsE29	10/-
2 Sil. Trans. 200 Mc/s 60VcR T233/84	10/-
1 Sil. Planar Trans. NPN 100 Mc/s B8Y25	10/-
1 Sil. Trans. 18104 150 Mc/s HFE 200 NPN	10/-
2 SCR's 50 PIV 1A TO 5 can	10/-
1 Tunnel Diode 1N3720 (TD5) G.E.	10/-
1 Unijunction Trans. 2N2160 (U)-5 can (G.E.)	10/-
2 Sil. Rects. 5A 400 PIV Stud Type	10/-
2 Germ. Power Trans. OC28/29	10/-
1 110A Sil. Stud Rect. 800 PIV	10/-
1 Tunnel Diode AEV11 1050 Mc/s STC	10/-
2 2N2712 Sil. Epox. Planar HFE220 max.	10/-
1 2N1287 PNP Sil. Planar TO-5 can	10/-
6 BY100 Type Sil. Rects.	20/-

surprise

surprise

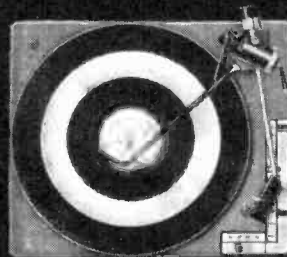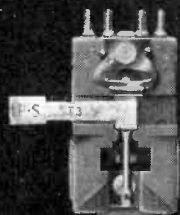

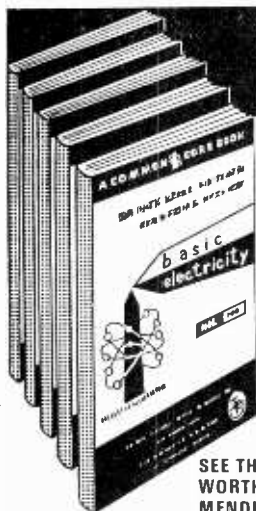

YOURS FREE FOR 7 DAYS

The New 'Picture - Book' way of learning

BASIC

ELECTRICITY (5 Vols)
ELECTRONICS (6 Vols)
ELECTRONIC CIRCUITS (2 Vols)
INDUSTRIAL ELECTRICITY (2 Vols)
SYNCHROS & SERVOMECHANISMS (2 Vols)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

SEE THE "TIMES" PRAISE
 WORTHY REVIEW RECOM-
 MENDING THIS BOOK ON
 PAGE 515.

—NOW READY—
BASIC TELEVISION Pt. 1.

Price 22/- inc. postage.

Complete in two parts, publication date of Pt. 2 to be announced later. Available on 7 days free trial, see coupon.

POST NOW FOR THIS OFFER!

TO SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY, KENT

Please send me Without Obligation to Purchase, one of the above sets on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. Basic Electricity 70/-, Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. Basic Electronics 82/-, Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order.

Tick set required (only ONE set allowed on free trial).

BASIC ELECTRICITY 70/-	☐	BASIC ELECTRONICS 82/-	☐
BASIC ELECTRONIC CIRCUITS 40/-	☐		
BASIC INDUSTRIAL ELECTRICITY 40/-	☐		
BASIC SYNCHROS & SERVOMECHANISMS 38/-	☐		
BASIC TELEVISION PART 1 22/-	☐		

All prices
 include
 postage

Signature
 (If under 21, signature of parent or guardian)

NAME
 BLOCK LETTERS BELOW

FULL POSTAL
 ADDRESS

Perhaps you will be as surprised as the pundits when you hear the facts* about the BSR C1 ceramic cartridge "... another milestone on the public right-of-way to high fidelity"—said *The Gramophone*.

You could even be surprised to know that the BSR UA70 manual/automatic turntable unit is fitted with such a splendid cartridge and that its all round performance is equal to such high standards.

But maybe not ... you could be one of those sensible people who knew all along that BSR don't just make a lot of autochangers but a lot of *very good* autochangers.

If you'd like to read the independent test reports write to Arthur Nicholls at:

BSR Limited,
Monarch Works, Cradley Heath, Warley, Worcs.



for better
 sound reproduction

BSR UA70 SPECIFICATION

Turntable
 Wow Less than -2%
 Flutter Less than -06%
 Long term speed variation
 Less than -5%
 (mains voltage $\pm 10\%$)

Rumble (ref.1kHz) —29 dB
Pick-up arm
 Counterbalanced lightweight arm with calibrated tracking pressure control, integral cueing device and automatic lock.
 Tracking pressure (depending on cartridge)
 2 grams. min.

Cartridge
 The now famous C1 ceramic
 Compliance 5.2×10^{-6} cm/dynes
 Frequency response 20-15,000 Hz
 ± 2 dB

Standard UA70 player £12.18.3*

C1 Ceramic Cartridge
 sapphire stylus £2. 7.0*
 diamond stylus £3. 1.9*

*Inc. P.T. surcharge

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4. 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

SITUATIONS VACANT

TV and Radio, City & Guilds, 'R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

RADIO & TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City & Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russel Street, Reading.

Interesting opening for 'Ham' exists as **ASSISTANT R.F. HEATING ENGINEER**. Job requires some ability in general engineering workshop practice, including welding and silver soldering, in addition to a knowledge of the construction of amateur transmitters. Associated with this work is a growing amount of transistor servicing. Training in any of the above skills will be given. Please write, giving full details of experience, etc. to:

R. A. MOIR
Personnel Manager
Weyburn Engineering Co. Ltd.
Elstead, Godalming, Surrey.

ALDERMASTON COURT POSTAL TRAINING for B.Sc. (Eng) Part I, A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams & Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.), write for 132-page handbook—FREE. Please state interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TRAINEE SERVICE ENGINEERS

Applications are invited for trainee hearing aid service engineers. Candidates must have practical aptitudes and possess sound knowledge in transistor circuitry. Excellent salary and above average fringe benefits which include a pension scheme. Promotion envisaged for ambitious, competent young men. For specific details write or telephone Mr. May

BOONCHORD LTD.

Marylebone Lane, London W.1. Tel: 935-9506

SITUATIONS VACANT

(continued)

RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£812, at 25—£1046 (highest age pay on entry) rising on 1.1.68 to; at 19—£828, at 25—£1,076.

Prospects of promotion to grades in salary range £1,159—£1,941. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

Recruitment Officer (RT),
Government Communications
Headquarters
Oakley, Priors Road
CHELTENHAM, Glos.

EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

EDUCATIONAL

(continued)

BE TRANSISTOR-WISE—21 practical lessons at home from scratch, to a sound understanding of semiconductor diodes and transistors. Full instructions on soldering, making measurements, simple calculations and graphs. All material supplied. £7.10.0.
ELECTRONIC EXPERIMENTS, Brinklow, Rugby.

TRAIN TODAY FOR TOMORROW

Start training TODAY for one of the many first-class posts open to technically qualified men in the Radio and Electronics industry. ICS provide specialized training courses in all branches of Radio, Television and Electronics—one of these courses will help YOU to get a higher paid job. Why not fill in the coupon below and find out how?

Courses include:

- **RADIO/TV ENG. & SERVICING**
- **AUDIO FREQUENCY**
- **CLOSED CIRCUIT TV**
- **ELECTRONICS**—many new courses
- **ELECTRONIC MAINTENANCE**
- **INTRUMENTATION AND SERVOMECHANISMS**
- **COMPUTERS**
- **PRACTICAL RADIO** (with kits)
- **NEW PROGRAMMED COURSE ON ELECTRONIC FUNDAMENTALS**

Guaranteed Coaching for:

- **Inst. Electronic & Radio Eng.**
- **C. & G. Telecom. Techns' Certs.**
- **C. & G. Supplementary Studies**
- **R.T.E.B. Radio/T.V. Servicing Cert.**
- **Radio Amateurs' Examination**
- **P.M.G. Certs. in Radiotelegraphy**

Start today—The ICS Way

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 173, Parkgate Rd., London, S.W.11.
Please send FREE book on

Name
Address
..... 11.67

(continued on next page)

EDUCATIONAL (continued)

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132 page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

BECOME 'Technically qualified' in your spare time, guaranteed diploma and exam-home-study courses in radio, T.V. servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. **WILLEN** (Dept. 40), 61a Broadway, London, E.15.

SURPLUS HANDBOOKS

19 set Circuit and Notes ..	4/6 p/p 6d.
1155 set Circuit and Notes ..	4/6 p/p 6d.
H.R.O. Technical Instructions ..	3/6 p/p 6d.
38 set Technical Instructions ..	3/6 p/p 6d.
46 set Working Instructions ..	3/6 p/p 6d.
88 set Technical Instructions ..	5/- p/p 6d.
BC.221 Circuit and Notes ..	3/6 p/p 6d.
Wavemeter Class D Tech. Instr. ..	3/6 p/p 6d.
18 set Circuit and Notes ..	3/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes ..	3/6 p/p 6d.
CR.100/B.28 Circuit and Notes ..	8/6 p/p 9d.
R.107 Circuit and Notes ..	5/- p/p 6d.
AR.88D Instruction Manual ..	15/- p/p 1/6
82 set Circuit and Notes ..	4/6 p/p 6d.
Circuit Diagram 3/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.	
52 set Sender and Receiver circuits 6/- post free	

Resistor colour code Indicator, 1/6 p/p 6d.

S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

SERVICE SHEETS

SERVICE SHEETS. RADIO. TV. 5,000 Models. List 1/6. S.A.E. Enquiries. **TELRAV**, Maudling Bk., Preston.

SERVICE SHEETS (75,000) 4/- each: please add loose 4d. stamp: callers welcome: always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS for all makes, Radio, TV., Tape Recorders, 1925-1967. Prices from 1/-. Catalogue 6,000 models 2/6d. Free fault-finding guide with all Sheets. Please send stamped addressed envelope with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex.

RADIO TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**. 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (continued)

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon

Name:

Address:

To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street,
London, W.1

Please supply Service Sheets for the following

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1967 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable)

I enclose remittance of
(which includes postage)

MAIL ORDERS ONLY (Nov.) PW

ELECTRICAL

240 VOLT ELECTRIC POWER FROM YOUR 12 volt or 6 volt CAR BATTERY

Run your mains AC/DC equipment direct from your car battery with this compact low battery consumption dynamotor. Size only 5in. x 3in. Sturdy construction. Converts a 12 volt input to a 240 volt output. Huge purchase enables us to offer them at only 39/6 each, post and packing 6/-, 6 volt input model only 35/-, p.p. 6/-. Thousands already sold.



COLLAPSIBLE AERIAL
IN 5 SECTIONS fully adjustable
CLOSED 13" highly efficient
OPEN 5'-6" whip aerial. Made to
BASE exacting specifications. Cop-
per plated sections. Brass base.
An ideal aerial for TX/RX use. Easily
adaptable for cars, scooters, walkie
talkies etc. Brand new in maker's boxes.
Only 17/6 each, post and packing 2/6.
Two aerials for 30/-, post free.

Dept. PW3,

S. & R. SUPPLIES,
14 CLIFTON GROVE, LEEDS 9

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC—using finest professional equipment 45 rpm—18/-. S.A.E. leaflet. **DEROY**, High Bank, Hawk Street, Carnforth, Lancs.

GEE'S Recording Tape and Audio Accessories cost less! Send 1/- for illustrated catalogue. **Gee Bros. Radio**, 15 Little Newport Street, London, W.C.2. Gerrard 6794.

WANTED

WE BUY New Valves and Transistors. State price. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. **R.H.S.** Stamford House, 538 Great Horton Road, Bradford 7.

PRACTICAL WIRELESS for June 1957 and any others pre-1967 wanted. **E. GEORGE**, Box 170; 25 Navarino Road, London E.8.

WANTED: New valves, transistors etc.; state price. **E.A.V. Factors**, 202 Mansfield Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. Send for packing instructions. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croydon.

VALVES WANTED, brand new popular types boxed. **DURHAM SUPPLIES (C)**, 175 Durham Road, Bradford 8, Yorkshire.

FOR SALE

SPECIAL VALUE. 9 transistor 5 diode AM/FM superhet measuring 6½ x 3½ x 1½. This is not a kit but a high quality radio with excellent reproduction on both medium and VHF wave bands. Costs less than the majority of FM tuners. Only £7.7.0 post free from **DIRECT SALES**, 79 Vicarage Lane, London E15, with money back guarantee.

MINIFLUX 4-Track stereophonic/monophonic record/playback heads. List Price 6 gns.—Special Offer 55/- each. **MINIFLUX 4-Track** stereophonic/monophonic Ferrite Erase Heads. List Price £3.10.0.—Special Offer 32/6 each, or supplied together (one of each) at £3.17.6. **SKN4 ½-track** stereophonic record/play heads for Transistor Circuits at 55/- each. Also available ½-track and full-track monophonic Ferrite Erase Heads. All heads complete with technical specifications. Send S.A.E. for details. **LEE ELECTRONICS**, 400 Edgware Rd., Paddington 5521.

SEE MY CAT. for this and that. Tools, materials, mechanical and electrical gear—lots of unusual stuff. This Cat. is free for the asking. **K. R. WHISTON** (Dept. PWC), New Mills, Stockport.

NEW LOW PRICES

Med/long wave band table/portable	£41.9.6
Micro-radio 2 x 2in. loudspeaker output	£2.14.6
Med. wave pocket portable 6 transistors	£2.14.6
All complete with carrying case, personal ear-phone and batteries	
Intercoms—2 station	£2.9.6
4 station	£5.14.6
Complete with connecting leads and batteries	
Clock/radio alarm complete with personal ear-phone	£8.4.6
Seven day money back guarantee for postal buyers. Post Free Personal callers welcome.	
DIRECT SALES (PW) 79 VICARAGE LANE, LONDON E.15	

(continued on next page)

FOR SALE (continued)

★ HAMMERITE HAMMER PATTERN ENAMEL ★
AIR DRYING • JUST BRUSH ON

TRIAL TIN
(covers 5 sq. ft.)
3/9
+ 9d. post.

24oz. tins 3/9, 1 pint 8/-, 1 pint 16/-, Carr. orders up to 5/-, 9d; up to 10/-, 1/9; over 10/-, 3/-. Colours: blue, silver, black, bronze. No primer needed. Panels transfers, fire-proof spray thinners. List Free. **INDUSTRIALISTS**

SAVE TIME AND ££££'s
(2 pints will do a Mini!).

AMAZING RESULTS • JUST TRY IT!
FINNIGAN SPECIALITY PAINTS (PW)
Mickley Square, Stockfield, Northumberland
Tel. Stockfield 2280

YUKAN. SO PROFESSIONAL THE YUKAN SELF-SPRAY
Get these AIR DRYING GREY HAMMER OR BLACK WRINKLE (CRACKLE) Finishes

Yukan Aerosol spraykit contains 16 oz. fine quality durable easy instant spray. No stove baking required. Finishes available in grey, blue, gold, bronze, Modern Eggshell Black Wrinkle (Crackle) all at 14/11 in our counter or 5/- carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Plastic finish (12 oz. self-spray cans 14/11) 13/1 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable 12 oz. on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 12 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or P.O. for total amount to:
YUKAN, Dept.
307a EDGWARE ROAD
LONDON, W.2
Open all day Saturdays Closed Thursday afternoons

Dept. PW/11

CURSONS TRANSISTORS

ALL GUARANTEED

1/- each, BAY31, BAY50, DK10, OA70, OA81, OA10, OA200, OA90, OA91, OA259.

2/- each, XA101, XA102, OC71, OC72, OC81, OC81D, OC44, OC45, GET16, FST3/1, ACY22.

3/- each, OC139, OC140, 2N706, 2N708, 2N2894, BY100, RAS310AF, 2N914, 2N914, BSY25, BSY26, BSY27, BSY95A, AFZ12, BFY18, BFY19, BFY26, BFY36.

7/6 each, RAS308AF, CRS3/40, BLY10, BLY11, BUY10, BUY11, ADY22, ADY23, ADY24, 2N2234, 2N2235, OC22, OC26, OC28, OC35.

ZENER DIODES

3.9v to 26v, 1/2w 3/- each, 1.5w 4/-, 7w 5/- each.

SAE, full new list:—

CURSONS
78 BROAD STREET
CANTERBURY, KENT

FOR SALE (continued)

MORSE MADE EASY !!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 or send A.R. stamp for explanatory booklet to:
G3CHS/P. 45 GREEN LANE, PURLEY, SURREY

MISCELLANEOUS

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

INSTANT ELECTRICITY ANYWHERE!

AMAZING NEW AMERICAN DYNA-MOTOR UNIT which runs from any 12-v. CAR BATTERY and produces a **BIG ELECTRICAL OUTPUT** of 230/240 v. at 220 watts. Marvellous for TELEVISION, ELECTRICAL DRILLS, MAINS LIGHTING and all Universal AC/DC mains equipment. **ONLY £12.10.0 plus 30/- carr.** Send stamped addressed envelope for illustrated details. Open 7 days a week.

SCIENTIFIC PRODUCTS (Dept. N)

Onward Building (rear of Fleetwood Arms Hotel), Mount Street, Fleetwood, Lancs.



SEE THE WORLD-FAMOUS
HEATHKIT
Electronic Kits
at
233 Tottenham Court Road,
London, W.1 Tel. 01-636-7349
Send for FREE Catalogue
Dept. TC3

RECEIVERS & COMPONENTS

BARGAIN PARCELS! 120 (minimum) radio parts, etc., mostly new 12/6. G. HART, Lings Lane, Chelmondston, Ipswich, Suffolk.

EXPORT SURPLUS—VHF TRANSMITTERS

A limited quantity of low powered "export" VHF transmitters, tunable over 80–110 Mc/s are available. The units are completely self-contained in a plastic case and need no external aerial. These units may be used for a wide variety of purposes and contain a jack point for crystal microphone, pick-up, etc.

Size 3 1/2 x 2 1/2 x 1 1/2 in.; powered by RM675H mercury cells; consumption 5mA; range in excess of 150 yds. in open space. Price £55.0. (without batteries).

Cash with order to
Carman-Wagborn Ltd., 1 Larch Grove, CHELMSFORD, Essex. Money refunded if not satisfied with purchase.

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 12/6 Post Free. **WHIT-SAM ELECTRICAL**, 18 Woodrow Close, Perivale, Middlesex.

RECEIVERS & COMPONENTS (continued)

SEMICONDUCTORS

AC107 4/-	BC107 5/6	BF180 10/-	OC71 3/-
AF114 4/-	BC108 4/9	BFY50 7/-	OC75 3/-
AF117 3/6	BC109 5/6	BSX20 6/-	OC81 3/-
AF239 12/6	BCY30 4/9	BSY95 6/-	OC81D 2/6
AFY19 17/6	BF115 5/3	OC35 6/6	2N706 2/-

SPECIALS

12—Ge diodes like OA93—100% tested	3/-
12—Si diodes—signal, rect., etc.—100%	7/6
12—Zeners, assorted—100% tested—fab1	10/-
6—200 PIV 500mA rects—tested at 300v	10/-
6—400 PIV 500mA rects—tested at 600v	12/-
6—800 PIV 500mA rects—tested at 1000v	15/-
2—OC28 Vcb = 80v for inverters	13/6
5—Thyristors 5A and 10A—cheap!	20/-
5—OC170—guaranteed the best available	20/-
6—BY100—individually checked at 1250v	22/6
2—AF239—Improved AF139—for UHF Rx	24/-

If you must use valves—see October PW or send SAE. All items post paid. Money-back guarantee.

J. R. HARTLEY


2 Waterloo Terrace
Bridgnorth, Shropshire

DICTAPHONES containing countless components. For full details and list S.A.E. G. SIMPKIN, 72 Nightingale Road, N.22.

WORLD WIDE COVERAGE

SHIPPING AMATEUR BROADCAST

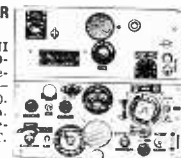CANADIAN MARCONI RECEIVER No. 62. 10-valve 3 switched wavebands covering 1.75–16 Mc/s (19–170 metres). Size 15 x 14 x 12 in. Fully tested. Power requirements 150v. H.T. 60mA, 12v. 3A. £9.19.8. Carr. 20/-.



MURPHY B40 NAVAL RECEIVERS

5 bands 650Kc/s–30 Mc/s. 10 valves. Built in speaker, phones output, 2 H.F. and 3 I.F. stages, xtal bandpass filter, noise limiter etc. etc. 150/230v A.C. Size 19 1/2 x 13 1/2 x 16 in. Cost well over £500. Supplied tested, working with circuit diagram £22.10.0. Carr. 30/-.

SPECIAL OFFER: Both above receivers £30. Carr. £3.

32R. TELESCOPIC AERIAL MASTS

Comprising 20ft. 4 section tubular steel telescopic mast and 12ft. folding whip; can be erected in less than 5 minutes. Closest to 5ft. 9in. Weight 21lb. Must have cost well over £20. Price 70/-, Carr. 10/-.

NATIONAL H.R.O. SENIOR RECEIVERS 5T MODEL

In excellent tested condition. Complete with 9 coils 60Kc/s–30 Mc/s and Power Unit, £31.10.0. Carr. 30/-.

REJECTOR UNITS 1.2-10Mc/s

Switched, 4 ranges. Primarily designed as station rejector for R.C. Suitable for harmonic suppression and many other uses with slight alteration. Tuning dial with lock. Aerial in and out sockets. Brand new 25/-, P. & P. 5/-.



4 VALVE 4 WATT AMPLIFIER

"C" Core transformers A.C. Mains 110/230 volts 600 ohms of high impedance input. Output 3 or 600 ohms (state choice). Controls: On/Off switch, Gain control, Indicator light. Valve inspection panel. 19 x 7 x 7 in. Brand new in maker's carton. 79/8, Carr. 10/-.

ROTARY TRANSFORMER

12v. D.C. input. 250v. D.C. output at 125mA. Size 3 1/2 x 5 1/2 in. Brand new, 17/6, P. & P. 5/-.

R.F. ANTENNA TUNER (A.T.U.)

Calibrated scale, ideal 160/80/40 metres. Limited number only. Brand new with instructions, 17/6, P. & P. 7/6.

ALL 19 SETS AND PARTS AVAILABLE

S.A.E. ALL ENQUIRIES—LIST 1/-

A.J.T.HOMPSON (Dept. P.W.)

"ELLING LODGE", CODICOTE, HITCHIN, HERTS.
Phone: CODICOTE 242

(continued on next page)


RECEIVERS & COMPONENTS (continued)

ARDEEN (RADIO). Every transistor we sell is comprehensively guaranteed (12 months). Top manufacturers new, tested products only: 2N2926: AC126, 128; OC44. 45. 71. 81. 81D: 4/-, OC170. 171; BC108. 109; AF126. 127: 4/6. BC107 (replaces 50 other N.P.N.s.—details supplied), 5/- each, 3 for 13/6. Bridge Rectifiers: 30V 150 m.A., 4/-; 300 m.A., 5/-, 700 m.A., 9/-. Components List 6d. Capacitors: 25V: 250p, 2/6; 500p, 3/6. By return post: Mail Order Only. C.W.O. 280 Croxsted Road, S.E.24.

WILSON ELECTRONICS

2/- each AC126, 127, 128, OC75, 819T (OC83).
2/6 each OC44, 45, 81D, 81, 82D, 82.
3/- each OC71, 72, 170, 84, AF118, AF119.
3/6 each AF115, 116, 117, 125, 127.
4/- each AF114, OC171, 172.
7/- each OC22, 23, 25, 26, 28, 30, 200.
11/6 each AD140, 149, OC35, 36, 38.
Resistors 1 watt, 5% 10Ω to 10MΩ 4/6 doz.
Caps 15V F, 10, 30, 50, 100 mfd. 1/- each.
Mylers -001, -002, -005, -02, -05 5/- doz.
Lists 6d. P. & P. 6d. per order.
20 Bradbourne Avenue, Wilford, Nottingham.

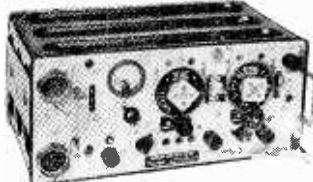JOHN'S RADIO (Dept. B) OLD CO-OP. WHITEHALL ROAD, DRIFHLINGTON, BRADFORD FAMOUS ARMY SHORT-WAVE TRANSRECEIVER MK. III




This set is made up of 3 separate units: (1) a two valve amplifier using a 6V6 output valve; (2) (some only, not built in the very latest models) a V.H.F. transreceiver covering 229-241 Mc/s using 4 valves; (3) the main short wave transmitter/receiver covering in two switched bands, just below 2 Mc/s—4 Mc/s, and 4 Mc/s—8 Mc/s (approx. 160-37.5 metres) using 9 valves. For R.T., C.W. and M.C.W. The receiver is a superheterodyne having 1 R.F. stage, frequency changer, two I.F. (465 Kc/s) signal detector, A.V.C. and output stage. A B.F.O. included for C.W. or single side-band reception. T.X. output valve 607, other valves octal bases. Many extras, e.g. netting switch, quick flick dial settings, squelch etc. Power requirements LT 12 volts, HT receiver 275 volts D.C. HT transmitter 500 volts D.C., size approx. 17½ x 7½ x 11ins. Every set supplied in new or as new condition in carton with book including circuits, only £24.10.0d., or grade 2 slightly used 50/- carriage both 15/-.

A FULL KIT of brand new attachments for this set including all connectors, control box, headphones and mike, aerial tuning unit, co-axial lead etc. at only 45/- carriage 5/-.

WE MAKE A MAINS 200/250 VOLT POWER UNIT in inverted metal case to plug direct into set power socket to run (1) receiver, 70/- post 5/-, (2) TX and RX, £6.10.0 post 7/6d. (3) 12 Volt D.C. P.U. for receiver, 50/- carriage 5/-.

A charge of 10/- to unpack and test the receiver of these sets is made only if requested.

V.H.F. TRANSRECEIVER MK. 1/1

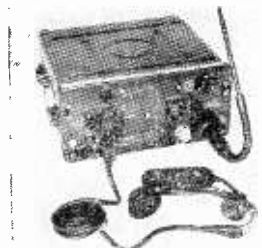

This is a modern self contained tunable V.H.F. low powered frequency modulated transreceiver for R.T. communication up to 8-10 miles. Made for the Ministry of Supply at an extremely high cost by well known British makers, using 15 midget B.G. 7 valves, receiver incorporating R.F. amplifier. Double superhet and A.F.C. Slow motion tuning with the dial calibrated in 41 channels each 200 Kc/s apart. The frequency covered is 39 mc/s—48 mc/s. Also has built-in Crystal calibrator which gives pipe to coincide with marks on the tuning dial. Power required LT 4½ volts, HT 150 volts, tapped at 90 volts for receiver. Every set supplied complete with valves and crystals. New in carton, complete with adjustable whip aerial and circuit. Price £24.10.0 carriage 10/-. Headset or hand telephone 30/-. Internal power unit stabilised for 200/250 volts AC input £26.10.0 extra.

RECEIVERS & COMPONENTS (continued)

Pocket-Size TRANSISTOR TESTER

Tests Transistors in or out of set — Tests both P.N.P. and N.P.N.
Price 30/- Battery and Post Free.

300 m/W AMPLIFIER KITS

Comprising: Full instruction manual — Transformers — Printed circuit — Transistors — Resistors — Electrolytics — Potentiometer — Flex — Copper wire — and solder etc.
Price 35/- post free.

9-VOLT POWER PACK KITS

Comprising: Full instruction manual — Resistors — Transformer — Electrolytics — Mains lead — Flex — Printed circuit — Screws and nuts etc.
Price 27/6. Post Free.

BROOK & HILL ELECTRONICS

695/697 SEVEN SISTERS ROAD,
LONDON N.15

(50 yds. from Wards Corner).

R & R RADIO

(Proprietor: B. Green)

51 Rossendale Road, Rawtenstall
Rossendale, Lancs.
Tel: Rossendale 3152

Boxed Valves		Fully Guaranteed	
EF80	4/-	PCC84	5/-
ECC82	4/-	PCF80	5/3
ECL80	6/-	PL81	5/-
EB91	2/-	PY81	5/-
EF85	5/-	PY800	5/-
EY86	5/6	PL36	7/6
		PY33	7/6
		30P19	7/6
		P304	7/6
		U191	7/6
		U310	7/6
		PCL83	7/6

Radio chassis, modern valve type in clean condition. Less valves, 25/- post paid.
Fireball tuners complete with valves, £1 post paid.
Tuners less cover cans and valves, 9/- post paid.
Your selected tuner, if available, 25/- post paid.
Postage, one valve 9d. extra, two valves 6d. each extra, three or more 2d. per valve extra.
Stamped addressed envelope with all enquiries please

VALVES

... salvaged but tested and guaranteed for 3 months. Our assortment 12/- doz., selected to your requirements 5/- each, if unable to supply immediate cash refund.

Large bags of capacitors and resistors, 5/- per bag.

HURRY, HURRY. Stocks good but selling fast.

R. J. ELECTRONICS
280 Lake Road
Portsmouth, Hants.

AERIALS


HIGH QUALITY AERIALS AT A NEW LOW PRICE

UHF outdoor or loft, 7 element, 29/6.
11 element 38/-. 18 element 52/-.
Combined loft BBC/ITV with mountings V plus 5 45/-. Chimney H plus 5 70/-.
Dipole plus 5 50/-. Low loss coax 1/5 yard. All types aerials, mounts and brackets on request. P. & P. 5/- on all above items.

TIMM'S ELECTRONICS
6 Jubilee Road, Weston-super-Mare,
Somerset

1/2 PRICE SPECIAL RADIO CHASSIS OFFERS

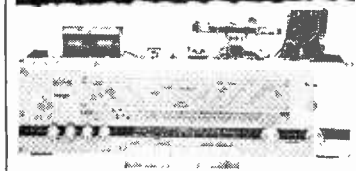HI-FI KUBA ROYAL
STEREOPHONIC TUNER AMPLIFIER



High Fidelity stereo/tuner amplifier. A four wave band tuner unit integrated with a powerful 16 watt high fidelity push-pull stereo amplifier. The most advanced comprehensive chassis yet designed.
8 Piano Key Selectors.
Separate bass and treble controls.
Full tape recording and play back facilities. Complete with a 4 speaker system (2-4in. tweeters, 2-10in. bass speakers) plus BSR 4 speed record changer. Model UA70 with ceramic cartridge and diamond stylus.
Fully guaranteed for one year including all valves.

Special Package offer only £74.5.0. (Chassis only 49/ Gns.)

Terms
£24.15.0 deposit followed by 24 Monthly Payments of £2.11.7 (total H.P. £86.13.0) + 17/6 P. & P. Send £25.12.6 NOW.
For other stereophonic equipment see page 542.



EQUIPMENT CABINETS OF DISTINCTION

- Illustrated in this advertisement is just one fine cabinet from the Lewis Radio Range.
- Each Lewis Radio Cabinet is carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet.
The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE!
Also available comprehensive range of stereophonic radiogram chassis and matching equipment. See page 542
Please send your FREE cabinet catalogue ☐
Stereophonic equipment leaflets ☐

NAME

ADDRESS

(Dept. P117)

Capitals please

Personal callers welcome


LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666

AMATEUR RADIO
CHAS. H. YOUNG LTD.

MIDLAND AGENTS FOR EDDYSTONE

Receivers & Components

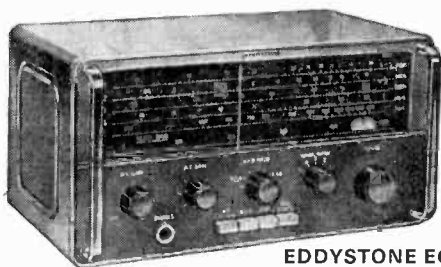

EDDYSTONE EC10

Sensational ALL-TRANSISTOR Communications Receiver, for use in the home, caravan, car or boat, etc.

List Price £53 H.P. Facilities—Part Exchanges

Write for brochure & full details.

**170-172 CORPORATION STREET
BIRMINGHAM 4**

Telephone: 021-236-1635

NORTH COURT AMPLIFIERS



30 WATT AMPLIFIER. A versatile amplifier of outstanding quality. The output of 30 Watts is ideal for Clubs, Factories, Public Address Groups etc.

Four input jack sockets, two high, two low gain are provided to enable mixing.

Loudspeaker can be either 3 or 15 ohm, tone is variable by separate bass and treble controls.

12mV is the minimum required for full output. A.C. mains only 200/250 volts 50 c/s. Six valves, two EF86, one ECC83, one GZ34, two EL34 are used.

A well designed and robust cover can be supplied for those wishing to transport the amplifier at 25/6.

Retail Price £19.17.6

ALSO AVAILABLE

15 Watt amplifier at £15.19.6. Cover can be supplied at 19/11.

5 Watt amplifier at £6.19.11. Cover can be supplied at 12/6.

★ Available from most dealers, but if in difficulty write for name of nearest stockist and fully illustrated brochure to

North Court (Electrical Bradford) Ltd
South Park Mills Pudsey Yorkshire

★ Trade Enquiries Invited.

ERSIN

Multicore
5 CORE SOLDER

for quick
easy faultless
soldering

Containing 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 12 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy.

2/6 each



SIZE 15

21 ft coil of 60/40 Alloy, 22 s.w.g. in a dispenser. Ideal for small components, transistors, diodes, etc.

3/- each



SIZE 12

Ideal for home constructors. Contains 102 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel.

15/- each



BIB MODEL 8 WIRE STRIPPER AND CUTTER

Strips insulation without nicking the wire, cuts wire and splits plastic twin flex. Plastic cushioned handles. 8/6 each

From Electrical or Hardware shops. If unobtainable write to:
Multicore Solders Ltd., Hemel Hempstead, Herts.



ELECTRONICS GALORE!

IN THE

dca CATALOGUE

THE CONVENIENT WAY TO SHOP FOR ALL YOUR ELECTRONIC NEEDS.

EVERYTHING FROM SINGLE COMPONENTS TO COMPLETE EQUIPMENT ALL AT BEST VALUE PRICES.

SEND 2/6d. NOW FOR YOUR COPY TO:—

dca ELECTRONICS LIMITED

28 UXBRIDGE ROAD, EALING, W.5.

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

IR5	4/6	DF91	2/9	ECC85	4/9	EY86	5/6	PCL84	7/-	U191	11/-
IR5	3/9	DF96	5/11	EC135	5/9	EZ40	6/6	PCL85	8/3	UABC80	5/-
IT4	2/9	DK32	7/-	ECH42	8/9	EZ80	3/9	PFL20012/6		UAF42	6/11
384	4/3	DK91	4/6	ECH81	5/3	EZ81	4/-	PL36	9/-	UBC41	6/8
3V4	5/6	DK96	6/3	ECH94	6/3	GZ33	8/9	PL81	6/6	UBF89	5/9
0AQ5	4/6	DL33	6/6	ECL80	5/9	KT61	6/3	PL82	5/9	UCC84	7/9
6F1	6/3	DL35	4/9	ECL82	6/-	N78	14/6	PL83	5/11	UCC85	8/-
6L18	6/-	DL92	4/3	ECL86	7/8	PC86	7/9	PL84	6/-	UCF80	8/-
10P1	9/8	DL94	5/6	EF39	3/8	PC88	7/9	PL500	12/6	UCH42	8/6
10P13	10/3	DL96	5/11	EF80	4/9	PC87	5/3	PY32	8/8	UCH81	5/9
12K8GT	7/-	DY86	5/6	EF85	5/-	PC800	7/6	PY33	8/6	UCL82	6/9
20P2	11/3	DY87	5/6	EF86	6/-	PC884	5/3	PY81	5/-	UCL83	8/6
20P1	8/9	EABC80	5/6	EF89	4/9	PC889	9/9	PY82	4/9	UCC85	8/-
30P4	11/6	EBC41	7/9	EF183	6/-	PC189	8/-	PY83	5/3	UF41	7/9
30P19	11/6	EBF80	5/9	EF184	5/6	PCF80	6/3	PY800	5/11	UF89	5/6
DAC82	6/9	EBF89	5/9	EL34	6/3	PCF82	5/9	PY801	5/11	UL41	8/8
DAF91	3/9	ECC81	3/9	EL41	8/-	PCF801	5/-	R19	6/6	UL84	5/6
DAF96	5/11	ECC82	4/3	FL84	4/3	PCL82	6/3	U23	11/-	UY41	5/3
DF33	7/8	ECC83	4/3	EY51	5/3	PCL83	8/3	U26	11/-	UY85	4/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N.16

NATIONAL AIR TRAFFIC CONTROL SERVICES Radio Technicians

The Board of Trade has vacancies for men wanting vital and interesting work on the latest equipment in TELECOMMUNICATIONS FOR CIVIL AVIATION at Civil Airports, Air Traffic Control Centres, Radar Stations, and other Engineering Establishments.

Qualifications. Practical experience in at least one of the main branches of Telecommunications. Preference will be given to those candidates with City and Guilds Certificates or O.N.C. in Engineering.

Age. 19 or over.

Salary. From £812 (at 19) to £1,046 (at 25 or over); scale maximum £1,201. From 1st January 1968 these rates will become £828 (at 19) to £1,076 (at 25 or over); scale maximum £1,242. Non-contributory pension for established staff.

Career Prospects. Radio Technicians are encouraged to study for higher technical and professional qualifications. They are helped in this by part-time and, in special cases, full-time release. Once qualified, there are excellent prospects of established posts and promotion to higher grades with a salary maximum of £2,174 (£3,105 from 1st January 1968).

Write for details to: Mr. T. H. Mallett, B.Sc. (Eng.) C.Eng., M.I.E.E., Room 754, The Adelphi, London, WC2, marking your envelope "Recruitment EJ 6702/16".

Name _____

Address _____

Not applicable to residents outside the U.K.

ELECTROLYTIC CONDENSERS

0.25µF 3V.	4µF 4V.	16µF 30V.	64µF 10V.
1µF 6V.	4µF 12V.	16µF 150V.	100µF 3V.
1µF 10V.	4µF 25V.	20µF 3V.	100µF 6V.
1µF 15V.	4µF 100V.	20µF 6V.	100µF 9V.
1µF 40V.	5µF 6V.	20µF 9V.	150µF 12V.
1µF 50V.	5µF 25V.	20µF 15V.	150µF 25V.
1.25µF 16V.	5µF 50V.	25µF 6V.	200µF 3V.
2µF 3V.	5µF 70V.	25µF 12V.	200µF 4V.
2µF 9V.	6µF 12V.	25µF 15V.	200µF 12V.
2µF 15V.	6µF 15V.	25µF 25V.	200µF 18V.
2µF 50V.	6µF 40V.	25µF 30V.	200µF 18V.
2µF 70V.	8µF 3V.	30µF 6V.	250µF 2.5V.
2µF 150V.	8µF 6V.	30µF 10V.	250µF 9V.
2.5µF 16V.	8µF 50V.	30µF 15V.	320µF 2.5V.
2.5µF 25V.	8µF 275V.	32µF 1.5V.	350µF 9V.
3µF 3V.	10µF 6V.	40µF 3V.	350µF 12V.
3µF 12V.	10µF 10V.	40µF 6.4V.	500µF 4V.
3µF 25V.	10µF 12V.	50µF 6V.	500µF 6V.
3.2µF 6.4V.	10µF 25V.	50µF 9V.	640µF 2.5V.
3.2µF 6V.	12.5µF 20V.	50µF 12V.	750µF 18V.
3.2µF 64V.	12.5µF 4V.	64µF 2.5V.	
	12.5µF 40V.	64µF 9V.	

All at 1/- each, 9/- per dozen. Mixed packet (our selection) 20 for 10/-, 300/100µF, 275V.; 200/200µF, 275V.; 125/300/50µF, 275V.; 5/- each or 3 for 10/-.

PAPER CONDENSERS

0.001µF 500V.	0.005µF 750V.	0.1µF 350V.	0.5µF 150V.
0.001µF 1000V.	0.02µF 600A.C.	0.1µF 750V.	0.5µF 350V.
0.002µF 500V.	0.02µF 350V.	0.25µF 350V.	0.5µF 500V.

All at 15/- per 100, or mixed packet (our selection) 50 for 10/-.

VERY SPECIAL VALUE! SILVER MICA, POLYSTYRENE, CERAMIC CONDENSERS

Very well assorted. Mixed types and values. 10/- per 100.

RESISTORS

Very small 1/4 watt, 5% long leads, ideal for transistor work, 10/- for 50. 1/2 watt assorted values including printed circuit types, 10/- for 100, 55/- per 1,000.

1/2 watt to 3 watt mixed values and types. 10/- for 100, 55/- per 1,000.

TO CLEAR: 10 Meg. 1/4th watt resistors, £1 per 1,000.

WIRE-WOUND 3 watts, 5 watt—6d. each.

7 watt, 10 watt—9d. each.

Most values. 1Ω to 47K Ω.

TRANSISTORS

OC44, 45, 31D—2/6 each.

OC71 equivalent, 1/- each, £3 per 100.

Switching Transistors ASY22 (pnp) or I.B.M. (npn), 6 for 10/-.

Car radio type Output Transistors type NKT405, 10/- each.

UNMARKED, UNTESTED TRANSISTORS—50 for 10/-.

LIGHT-SENSITIVE TRANSISTORS SIMILAR TO OC71—2/- each.

Packet containing complete set of transistors for Superhet Radio—12G34A; 12G345A; 12G345B; 12G371A; 22G378A; and diode, with specifications, 15/- only.

2N753 N.P.N. silicon planar, 300mW, 250 Mc/s high speed switch.

BSY 28 N.P.N. sil. planar, epitaxial, 300mW 300 Mc/s.

BSY 65 N.P.N. sil. planar, epitaxial, 800mW 100 Mc/s.

AFZ 12 P.N.P. Germanium Alloy Diff. 63mW 180 Mc/s.

All 5/- each.

TELEVISION VALVES, BRAND NEW AND BOXED

PCF80, 7/6; PL81, 7/6; PCL84 7/6; PCC84, 8/6; PY81 8/-; ECC82, 8/6;

PL36, 9/-; EY86, 6/-; PCL83, 9/-; PY33, 9/-; ECL80, 8/6; PCC89, 9/-.

Silicon diodes. Make excellent detectors. Also suitable for keying electronic organs, 1/- each or 20 for 10/-.

BY100 TYPE TELEVISION H.T. RECTIFIERS. SPECIAL PRICE 5/- each, 30/- dozen.

ORP12 light sensitive resistors, 9/- each.

NUTS, SCREWS and WASHERS, very useful assorted packs, 6/- each. SIGNAL INJECTOR, parts and circuit to make, 10/- only.

SIGNAL TRACER, parts and circuit to make, 10/- only.

MOTOR CAR REV. COUNTER (less 1mA meter), parts and circuit to make, 10/- only.

TRANSISTORS, COMPONENTS AND CIRCUIT to convert 1mA meter to 0 to 10 Meg. ohm meter, 10/-.

TRANSISTORISED RUMBLE AND SCRATCH FILTER (for improving reproduction of old records), all components and circuit, 30/-.

SINCLAIR. All products in stock including latest version of MICRO-8—World's smallest radio—and only 59/6!

NEEDLES FOR RECORD PLAYERS, HALF PRICE!

All types below at 3/6 each!

TC8LP; GC2LP; GC3LP; BF40LP; GP67LP; GP37; GP59; TC8 Stereo LP; Studio O L.F.

CARTRIDGES SONOTONE MONO, 10/-; ACOS, 15/-; ACOS STEREO SAPPHIRE, 12/8; DIAMOND, 17/6. All complete with needles!

LAPEL MICROPHONES, Magnetic or Crystal, 10/- each. TAPE RECORDER MICROPHONES. Fantastic value at 12/- each.

ACOS MIC. 45, 30/-; Many others, both crystal and dynamic in stock.

THIN CONNECTING WIRE. 10yd., 1/-; 100yd., 7/6; 500yd., 25/-; post 4/6, 1,000yd., 40/-; Post 6/-.

LOUDSPEAKERS, 12in. Richard Allen, 37/6. 12in. Bakers Guitar, £5/5-. 3in., 4in., 5in., and 5in. x 3in., all at 10/- each; 8in. x 2in., 12/6; 2in. 80 ohm, 7/6.

EARPIECES, Magnetic or Crystal, 5/- each.

VEROBOARD

2in. x 2in. 1/1; 2in. x 5in. 3/11; 2in. x 3in. 3/3; 3in. x 5in. 5/6; 3in. x 3in. 3/11. Terminal Pins, 36 for 3/-; Spot Face Cutter, 7/3.

Special Offer—Cutter and 5 boards, 2in. x 1in., 9/8.

ORDERS BY POST:

To G. F. MILWARD, 17 PEEL CLOSE, DRAYTON BASSETT, Staffs. PLEASE INCLUDE APPROPRIATE POSTAGE COSTS

No enquiries without stamped addressed envelope please

For customers in the Birmingham area, goods may be obtained from: Rock Exchanges, 231 Alum Rock Rd., Birmingham 8 (no postal service)

BI-PRE-PAK LTD

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0802) 46344

LOOK—TRANSISTORS 1/- EACH

SILICON ★ PLANAR ★ N.P.N. ★ P.N.P.
All these types available

2N929	2N131	2N696	2N1131
2N501	2N512	2N507	2N1132
2N2411	2N102	2N1507	2N2906
2N726	2N103	2N1613	2N2904
2N706	2N104	2N1711	2N731
2N706a	2N2220	2N1893	2N732
2N3011			2N733

ALL TESTED AND GUARANTEED TRANSISTORS—UNMARKED. Manufacturers over-runs for the new PRE-PAK range.

NEW FROM THE U.S.A.

"TEXAS" Integrated Circuits

SN7360	Quadruple 2 Input Nand/Nor Gate	19/6
SN7430	8 Input positive Nand Gate	21/6
SN7302	Dual J-K Flip-Flop with preset	35/-
F.E.T.'s.	Field Effect Transistors.	
2N3822	'N' Channel 4-lead	15/-

No.	PRE-PAKS	PRICE
A1.	6—Silicon rectifiers BY160 type	20/-
A2.	10—Relays mixed types and voltages	20/-
A3.	20—Mixed marked and tested trans.	20/-
B1.	50—Unmarked, untested, trans., new	10/-
B2.	30—Trans. new tested, but unmarked	10/-

Transistors	Price
AF114	4/-
AF115	3/-
AF116	3/-
AF117	4/-
AF118	3/6
AF119	3/6
AF178	10/-
BSY95A	5/-
OC22	7/6
OC23	10/-
OC25	8/-
OC26	5/-
OC28	7/6
OC35	5/-
OC36	7/6
OC41	2/6
OC42	2/6
OC44	1/11
OC45	1/9
OC71	2/6
OC72	2/6
OC73	5/-
OC81	2/6
OC81D	2/6
OC83	4/-
OC139	2/6
OC140	5/-
OC170	3/-
OC171	4/-
OC200	5/-
OC201	5/-
2N1302 or 3	4/-
2N1304 or 5	5/-
2N1306 or 7	6/-
2N1308 or 9	8/-

★ ALL OUR SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★


Send for our FREE lists and catalogue of all our products. Check your own equivalents with our free substitution chart.

FIRST EVER LOGIC KITS. Learn for yourself how computers work, even make one for yourself. Full instructions for a noughts and crosses machine, binary counters, timers, etc. L.1 5 gns. L.2 10 gns. No need to purchase both kits, you can start with L.2, which incorporates L.1. DETAILS FREE.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/- CASH WITH ORDER PLEASE, add 1/- post and packing. OVERSEAS ADD EXTRA FOR AIRMAIL.

RADIO CONSTRUCTOR

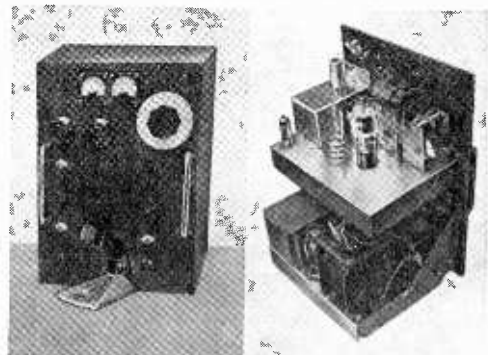SPECIAL SHORT WAVE FEATURE in OCTOBER issue



40 WATT 80 METRE PHONE TRANSMITTER

By F. G. Rayer, G3OGR

Many other constructional articles

ON SALE NOW - 2/6

From your newsagent or 3s. post paid from:

DATA PUBLICATION LTD., 57 MAIDA VALE,
LONDON W. 9.



C.R. Bridge 32 £10.10.0 Transistorised

6d. stamp for all leaflets

NOMBREX SPECIAL OFFER

with first 50 orders received from this advertisement.

WESTEC

ELECTRONICS SLIDE RULE

WITH 90 PAGE INSTRUCTION MANUAL

A unique double-sided 12" rule with 15 scales, simple to advanced maths problems and calculations and hundreds of radio-electronics equations and problems in Ohms Law, frequency, Q, inductance, resonance, reactance, etc.

AT GIFT PRICE £1.10.0

(NORMAL RETAIL PRICE £6.10.0)



R.F. Generator 31 £12.10.0 Transistorised

Post/Pkg. 6/6 each extra
Immediate Delivery C.W.O.

NOMBREX LTD., EXMOUTH, DEVON

RADIO HANDBOOK

by W. ORR, new 17th ed. published by Editors and Engineers. 84/- P. & P. 4/6.

PAL Colour T.V. by Mullard. Circuits described 12/6. P. & P. 1/-.

101 Ways to use your Signal Generator by Middleton. 18/- P. & P. 1/-.

Transistor Electronic Organs by Douglas. 18/- P. & P. 1/-.

Silicon Controlled Rectifiers by Lytel. 21/- P. & P. 1/-.

Loudspeakers and Loudspeaker Cabinets by Van der Wal. 15/- P. & P. 1/-.

T.V. Fault Finding, 405, 625 lines by DATA. 8/6. P. & P. 9d.

Transistor Circuits for Radio Controlled Models by Edvs. 7/6. P. & P. 9d.

Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET
LONDON, W.C.2

(Leicester Square Tube Station)

AMATEUR RADIO G3NAP SPECIALISTS G3PQQ

STOCKISTS

Full range Lafayette Receivers, Partridge "Joystick" antennas and tuners. Eagle products. Electroniques manual and products. R.S.G.B. publications.

Sommerkamp transmitters and receivers. Tokai transceivers (Amateur's licence required), Kw transmitters, receivers, etc. Contactor switchgear mobile equipment. Swan transceivers (Amateur's licence required), etc., etc. SAE Lists.

SWANCO PRODUCTS LTD.

247 HUMBER AVENUE

COVENTRY

Open all day Sat. Tel: COV. 22714

SPECIAL OFFER

1mA m.c. meter, new, 1 1/2" square clear plastic front. Only 18/6, post 1/3, with free multimeter circuits.

EAGLE MULTIMETERS

EP10K 67/8 p.p. 3/-; EP30K 105/- p.p. 4/6; EP10KN 55/- p.p. 4/6; EP20KN 98/- p.p. 4/6; EP30KN 130/- p.p. 4/6, details on request.

Also available IT1-2 (20,000 o.p.v.) 63/-, post 3/-.

FOOTBALL POOL COMPUTER CIRCUIT and three other analogue circuits, 4/6.


DIGITAL COMPUTER CIRCUIT

A simple digital Adder/Subtractor using switches and lamps only. A fascinating demonstration of Binary arithmetic. Full circuit, wiring diagram and notes on the Binary system, 8/6.

PLANET INSTRUMENT CO.

25 (W) DOMINION AVENUE, LEEDS 7

FANTASTIC NEW 1967 BARGAINS FROM CONCORD

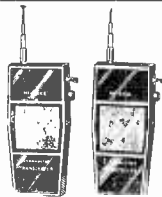


Frustrated Import Shipment
OFFERED BELOW HALF PRICE TO CLEAR
ALL TRANSISTOR 500 only
PERSONAL TRANSCIEVER SETS

OUR PRICE £6.19.6

You've heard about them—You've read about them. NOW'S YOUR CHANCE TO OWN THEM. Highly sensitive two-way transceiver sets have individual volume control and talk-listen switch. Telescopic aerial pulls in the voice from the other set over tremendous distances—no wires—a genuine transceiver as used by official bodies and forces. 500 sets only at £6.19.6 plus 5/6 p. & p. (Batteries, leather cases, etc., 10/6 ex.).

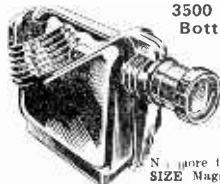Money back if not delighted with the performance. These cannot be operated in U.K.



3500 Bought at "Rock Bottom" Off Leading British Maker
REAL EPISCOPAL PROJECTOR
ONLY 45/-

No more to pay! Projects FULL SIZE Magnified PICTURE on to your wall or screen in BLACK & WHITE OR COLOUR with CRYSTAL CLARITY ANY PHOTOGRAPH, DOCUMENT, picture drawing, stamp, etc. Entertaining and educational—hundreds of uses in home, office, schoolroom, etc. A FULL SIZE precision made scientific instrument WITH REAL GLASS REFLEX LENS. Sturdy, reliable. So simple even a child can use it—plugs into standard mains. BRAND NEW complete with cable, lamp, etc. Offered at fraction of real worth at 45/- plus 5/- p. & p. Satisfaction or money back.

Profit from the credit squeeze
Importers stock bought at miles below actual value
WIDE RANGE HIGH POWER MICROSCOPE only 37/6

not a penny more to pay. Grade A.1 De Luxe model, all metal construction in black crackle with plated parts. Accurate rack and pinion focussing gives crystal clear definition. 3 optically polished lenses on revolving turret, giving 100x, 200x and 300x magnification powers. Adjustable mirror light, reflector and tilting joint. Ideal for students, hobbyists, nature study, etc. Should last a lifetime. Passed by Japanese Board of Inspection. Brand new in box, complete with set of slides at fraction of real worth—ONLY 37/6 Plus 3/6 post & safe packing. Money back g'ter. Demonstrations daily.

NO SOLDERING AMAZING CIGARETTE RADIO ONLY 25/-

Yes a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 cigarettes yet cleverly conceals highly sensitive, fully transistorised circuit (including battery). Even a young boy can assemble it under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file Mr. D. B. of Huddersfield, writes: "... I have fitted the parts in it and it is working wonderfully..." ALL PARTS including Semi-Conductors, A.B.C. Plans, etc. ONLY 25/- plus 2/6 post, etc. Parts available separately.




Don't be put off by amazing low price—see bought bankrupt stock.



NAVAL (Pattern) BINOCULARS
40mm. O.G. lens
45/-


NO MORE TO PAY

including real pikskin case. Superb area magnifications of 15 times. Brand new, Grade A.2 de luxe model by leading optical manufacturer. Full size, metal construction, light-weight, precision ground and polished optical lenses for wide angle, needle sharp definition. Telescopic draw tubes with smooth action centre focusing and inter-pupillary pivot. Takes you into space or just across the road. Save £ & £'s—ONLY 45/- incl. real pikskin case and shoulder strap, plus 4/6 p. & p. Order quickly while limited stocks last. Money back guarantee.

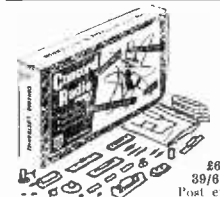

Make 5 different TRANSISTOR RADIOS for 39/6

No soldering. Only 8 components for first radio, to work just look, you get Easy A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, 6 coils, Condensers, Resistors, Tuner, Switch, Screws, etc. YES EVERYTHING! Loud, Clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. TESTIMONIALS GALORE (comp. to course—originally 28. Now only 39/6 plus 4/6 Post etc.)

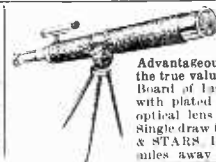

HIGH POWERED TRIPOD TELESCOPE ONLY 45/- NO MORE TO PAY

Advantageous Purchase Direct from Importer. 750 only at fraction of the true value. Special grade A.1 De Luxe model—passed by Japanese Board of Inspection. All Metal construction in Black (crackle finish) with plated parts and simulated leather covering. Special polished optical lens gives astounding magnification power of 900-1 areas. Single draw focusing tube enables you to study the MOON, PLANETS & STARS. Independent view finder permits you to focus on subject miles away or just across the road. Brand new complete with collapsible tripod at unbelievable price of only 45/- plus 5/- post and SAFE PACKING. Satisfaction or your money back.

CONCORD ELECTRONICS LTD. (Dept. P.W.43) 8 Westbourne Grove, London W.2
MAIL ORDERS ONLY



SUPPLIERS OF ELECTRONIC EQUIPMENT TO ...

- * INDUSTRIAL RESEARCH ESTABLISHMENTS
- * RADIO ENTHUSIASTS
- * UNIVERSITIES AND TECHNICAL COLLEGES

OFFICIAL SUPPLIERS TO MANY EDUCATION AUTHORITIES
Usual Educational Discounts

OUR NEW 1967/68 illustrated catalogue NOW AVAILABLE (send 2/- in stamps for your copy)

INCLUDES

Valves, Transistors, Transformers, Loudspeakers, Recording Tape, Coils, Resistors, Condensers, Potentiometers, Chassis, Rectifiers, Test meters, Microphones, Tools. Solder etc.

DISTRIBUTORS OF EAGLE PRODUCTS WHOSE NEW ENLARGED CATALOGUE is now available 5/-

ALPHA RADIO SUPPLY CO
103 Leeds Terrace, Leeds 7, Tel: 25187

AERIAL WIRE: Coils of 25 yds. Single Strand 2/3 + 6d. P. & P.

RELAYS:

1. Miniature Plug-in Relays. 185 Coil 4-5/18v.
2. Change over Contacts 13/6 + 1/6 P. & P.
3. Miniature Plug-in Relays. 130 Coil 4. Light Duty Contacts. 9/16 volts. 15/6 + 1/6 P. & P.
4. Heavy duty Car Alarm Relay 6/12 volts. 3 c/o Contacts. 27/6 + 1/6 P. & P.
5. 6 volt octal base A/C Relays. 2 pairs heavy duty Contacts c/o. Complete with octal base. 23/- + 1/6 P. & P.
6. Single change over Relay. 875 Coil. 18 volts for printed circuit. 15/- + 1/6 P. & P.
7. Bases for Item 1 and 2. 3/6 + 6d. P. & P.

State whether wired or printed circuit.
TEST METER: still available at reduced price of £8.19.6. 20 K per volt ITI-2, and 200 H. TAYLOR Jun. and Minor.

Small robust Test Meter suitable for Field Service. 39/6 + 2/- P. & P.
LOUDSPEAKERS: 8" 2" to 5" from 7/6 to 13/6 + 1/6 P. & P.

Dual Cone Richard Allen, 3 and 15 s 29/6 + 3/- P. & P.

Car Speakers 7" x 4" 13/6 + 2/- P. & P. 8" and 10" Richard Allen.

TEST LEADS: Pairs of Strong Test Leads 4/8 per pr. TRANSFORMERS: 250-0-250 sec. 60 MVA/6-3 volts. 18/9 + 3/6 P. & P.

250-0-250 sec. 100 MVA/6-3 volts. 39/6 + 3/6 P. & P.

TRANSFORMERS SUITABLE FOR SMALL POWER SUPPLIES: 5/11/17 volt 4 amps. 27/6 + 3/6 P. & P.

P. 3 to 30 volts tapped 2 amps. 30/- + 3/6 P. & P.

0-9-15 volts. 11 amps. 16/6 + 3/- P. & P. 75 watt auto transformers. 10/6 + 2/6 P. & P.

OUTPUT TRANSFORMERS: suitable for D1/96 Midgt. 6/6 + 2/6 P. & P. Suitable for EL5/1 Lx4 Singles. 6/6 + 2/6 P. & P. Midgt Choke Output. 6/6 + 2/6 P. & P.

CARBON CONTROLS: 5 K to 2 M Lin. or Log. 3/6. 5 K to 2 M Lin. or Log. with s/W. 5/3 + 1/- P. & P.

WEYRANG RANGE of I/Fs, Coils, Driver & output trs. EAR PIECES: 2-5 m/m or 3-5 m/m Magnetic 2/6.

Crystal 2-5 m/m 3-5 m/m. 5/6.

SINCLAIR PRODUCTS: All units and Mat. Trans. TRANSISTORS: POPULAR RANGE. OC44, OC45, OC71, OC72, OC81, OC82, all at 2/6.


POWER TRANSISTORS: OC26, 10/9, OC28 15/3, OC35, 13/6. ADT49. 15/-.

OSMOR RANGE of I/Fs, Coils, Driver & output trans. Write or call for our free Components List.

BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET, GLASGOW, C.S. Tel. 041 SOUTH 2804.
Member of the Lander Group.

H.A.C. SHORT-WAVE KITS

NEW RELEASE: MODEL "DX"

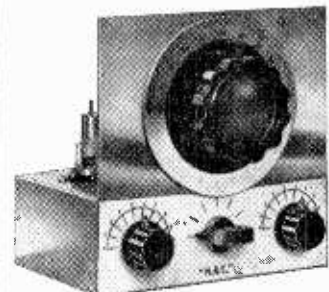

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1967 RANGE


One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6)

Customers say: "Definitely the best one-valve S.W. Kit available at any price." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form, etc., to—

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

1/2 PRICE SPECIAL RADIO CHASSIS OFFERS

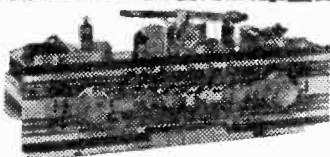HI-FI CONTINENTAL
STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete 29 gns. (Units available separately if required. Chassis only, 21 gns.).

Special terms available of £10.6.6 deposit followed by 18 monthly payments of £17.3 (total H.P. of £34.17.0) + 17/6 P. & P. Send £11.4.0 now.

IMPERIAL HI-FI STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection, Gram Long-Medium Short-FM-ON/OFF. The unit comes complete with two 10" elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only, 29 gns.

Special terms available of £13.16.6 deposit followed by 24 monthly payments of £18.10 (total H.P. £48.8.6) + 17/6 P. & P. Send £14.14.0 now.

EMPRESS HI-FI AM/FM STEREOPHONIC CHASSIS



This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers 4 speed Stereo/Mono autochanger only £35.19.6. Chassis only, 25 gns. Special terms available of £12 deposit followed by 18 monthly payments of £11.17. (total H.P. £40.8.6) + 17/6 P. & P. Send £12.17.6 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. For other Stereophonic Equipment and Cabinets, see page 537.

Send your cheque or P.O. today while stocks last to Dept. P.117.

Personal callers welcome

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 35/-, 11 element, 42/6, 14 element, 50/-, 18 element, 57/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-. Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Pre-amps, from 75/-. State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1). Telescopic loft, 21/-. External S/D. 30/-. "H" 22.10.0.


ITV (Band 3). 3 element loft array, 25/-, 5 element, 35/-, 7 element, 45/-. Wall mounting, 3 element, 35/-, 5 element, 45/-.

Combined BBC/ITV. Loft 1+3, 41/3; 1+5, 48/9; 1+7, 58/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3. VHF transistor pre-amps, 75/-.

COMBINED BBC 1 - ITV - BBC 2 AERIALS 1+3+8, 70/-; 1+5+9, 80/-; 1+5+14, 90/-; 1+7+14, 100/-. Special leaflet available.

F.M. (Band 2). Loft S/D. 12/6, "H" 30/-, 3 element, 52/6. External units available. Co-ax cable, 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/-. Send 6d. stamps for illustrated lists.

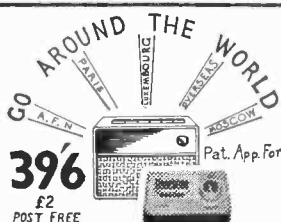K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey-CRO-OJB
LODGE HILL 2266



39/6

£2 POST FREE

On your own TRANSISTOR PORTABLE!
★ Boosts Luxembourg and 'Pop' stations
★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio.
★ Extends Battery life — reduces 'fading'.
★ Use in car, caravan, without aerial.
With PP3 battery (life several months).
D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset.

"GLOBE-KING"

2-4 Metres 10-180 Metres

ALL TRANSISTOR

AMATEUR VHF and SHORT-WAVE KITS

Send stamped addressed envelope for free copy interesting literature describing latest products: Unique VHF kit model SR2/P, 70-150 Mcs., 69/6 p.p. 4/-. Short-Wave kit model TR2, 79/6 p.p. 5/-. "Mini-Amp" self-contained, cabinet size a mere 4" x 9" x 2", 139/6 p.p. 4/-. Despatch: Within 21 days from receipt of order. Overseas enthusiasts send local stamp for literature and special postal charges for your particular country: Sole makers "Globe-King" (Regd.) products: Tel.: 24864: Est. 1943.

JOHNSONS (RADIO)

St. Martins Gate, Worcester

4-STATION INTERCOM



£6/9/6

Solve your communication problems with this Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/Off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 6/8.

WIRELESS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 8 gns. post paid.

INTERCOM/BABY ALARM



Originally 6 gns. OUR PRICE ONLY 57/6

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 60ft. connecting wire. Battery 2/6. P. & P. 3/6.



Transistor TELEPHONE AMPLIFIER
lively Gns.
55/-

Why not boost business efficiency with this Incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 2/6. Full price refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (PW/11)
169 KENSINGTON HIGH STREET, LONDON W.8

FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of diploma courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

Satisfaction or refund of fee

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSES


CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)

(Dept. 849F), 148 HOLBORN
LONDON, E.C.1

NEW SOLID STATE HIGH FIDELITY EQUIPMENT ★★ ★

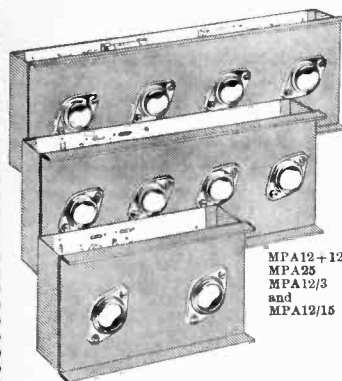
IMPROVED PERFORMANCE · NEW STYLING · NEW MODELS · MONO & STEREO



MPA12+12
MPA25
MPA12/3
and
MPA12/15



MP3

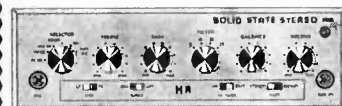

SP4-2

MP3. Mono preamplifier. All silicon low noise zener stabilised circuit. Full range of controls—fully equalised inputs for xtal pu, dyn/xtal mic, radio tuners, tape head and preamp. replay. Supplied built and tested on metal chassis complete with grey/silver front panel, alu. knobs and handbook. Output 250 mV. Supply 12 to 60 volts 3 mA. Overall size 9 1/4" x 1 1/4" in.

MP3 Price £6.19.6, P.P. 3/-

SP6-2. Mono/stereo preamplifier. Uses 8 silicon/germanium devices. Zener stabilised. Completely new low noise design. Full range of controls and filters. Inputs for magnetic/xtal/ceramic cartridges, radio tuners, tape preamp, microphones, tape head, etc. Record output socket. Supplied built and tested on metal chassis with grey/silver front panel and matching knobs. Complete with input sockets and handbook. Output 250 mV per channel. Supply 9 to 60 volts 4 mA. Overall size 12 x 3 1/4 x 3 1/4 in.

SP6-2 Price £14.19.6, P.P. 6/-

SP4. Mono/stereo preamplifier as previously advertised. Complete with front panel and knobs. Size 9 x 3 1/4 x 1 1/4 in.

SP4 Price £10.19.6, P.P. 3/6

MPA12/3 and MPA12/15. 12 watt power amplifiers for use with above preamplifiers. Improved response and performance with even lower distortion levels. MPA12/3 for 3 to 5 ohm speakers, 24/28 volt supply. MPA12/15 for 10 to 16 ohm speakers, 40/45 volt supply, uses 8 silicon and germanium devices. Inputs 100 mV for 12 watts, response ± 1 dB, 30 c/s to 20 kc/s. THD 0.2% at 12 watts. High gain stable push-pull output designs. Built on to metal chassis as illustrated. Overall size 5 x 2 x 3 1/4 in. Complete with handbook.

MPA12/3 Price £4.10.0, P.P. 2/6

MPA12/15 Price £5.0.0, P.P. 2/6

MPA12+12. Twin amplifier for mono/stereo use with above preamplifiers. Consists of two matched MPA12/15 amplifiers (see above) on single chassis. Output for 10 to 16 ohm speakers. 40/45 volts supply. Overall size 10 x 2 x 3 1/4 in.

MPA12+12 Price £9.19.6, P.P. 4/-

MPA25. 25/30 watt power amplifier for use with above preamplifiers. New design and layout with improved response and overall performance. Output for 7 to 16 ohm speaker systems. Input 180 mV for full output. Push-pull circuit. Uses 10 silicon and germanium devices. Supply 50/60 volts. Overall size 8 x 2 x 3 1/4 in.

MPA25 Price £7.10.0, P.P. 3/6

Choice of PREAMPLIFIERS POWER AMPLIFIERS MAINS UNITS

MAINS UNITS

110/240 volt 50/60 c/s input. AC/DC fused. Fully smoothed and isolated. MU series has additional choke/capacitor filtering and panel voltage selectors. All types on metal chassis. PS84/40. Output 24 and 45 volts 1 amp. For use with 1 or 2 MPA12/3, MPA12/15, or 1 MPA12+12. Price 70/-, P.P. 3/-.
MU24/40. Choke smoothed. Output 24 and 45 volts 1 amp. For use with 1 or 2 MPA12/3 and MPA12/15 or 1 MPA12+12. Price 87/6, P.P. 3/6.
MU60. Choke smoothed. Output 50 volts 1 amp. For use with 1 or 2 MPA25. Price 95/-, P.P. 4/-.

RECOMMENDED SYSTEMS

MP3+MPA12/15+PS84 £14.12.6, P.P. 6/6
MP3+MPA12/3+PS84 £13.17.6, P.P. 6/6
MP3+MPA25+MU60 £18.5.0, P.P. 8/-
SP6-2+MPA12+12 or 2MPA12/15+MU40 £28.5.0, P.P. 10/-
SP6-2+2MPA12/3+MU24 £26.15.0, P.P. 10/-
SP6-2+2MPA25+MU60 £33.5.0, P.P. 10/6
SP4+2MPA12/15+PS84 £24.0.0, P.P. 9/-
SP4+2MPA12/3+PS84 £22.15.0, P.P. 9/-
MP3+2MPA12/15+MU40 £20.17.6, P.P. 8/-
MP3+2MPA12/3+MU24 £19.7.6, P.P. 8/-

COMPLETE BROCHURE
FREE ON REQUEST

CHOOSE A SYSTEM TO SUIT YOUR NEEDS
AND SAVE POUNDS

HENRY'S RADIO LTD



303 EDGWARE RD
LONDON W.2

PHONE: (01) 723-1008/9
Open Mon.—Sat. 9 a.m.—6 p.m.
Thurs. 9 a.m.—1 p.m.

Broadway ELECTRONICS

GARRARD 4 SPEED DECKS WITH CARTRIDGE:
Autobrowsers: AT6 Mk. II £8.19.6, AT60 £10.19.6.
3000 £8.8.0, 2000 £6.19.6, 1000 £5.19.6.
AT5—Mono £6.10.0, P. & P. all changes 7/6.

SINGLE PLAYERS:
BP25 with cartridge stereo or mono, cast turntable £10.19.6, P. & P. 7/6.

CARTRIDGES:
Stereo: EV26 25/-, GP83 15/-, Reuter STD/2 17/6.
Mono: Sonotone, 2T88 15/-, Acos, GP67 15/-,
TC8 less bracket 18/6, P. & P. 1/-.

MICROPHONES:
Xtal Hand Mikes.
BM3 and 200C 30/-, P. & P. 2/6. Stand for same 12/6, P. & P. 2/-.
ACOS Mike 45, 21/-, ACOS Mike 40, 18/6.
Dyn, Mike DM-391, 22/6.
CM21 Xtal 12/6.
CM20 Xtal, 9/6.
Magnetic Hm 63C with remote control switch 15/-, Telephone Pick-up 10/6, P. & P. 1/-.
Xtal Lapel Mike 7/6, Guitar Mike 12/6, P. & P. 1/-.

INTERCOM BABY ALARMS
Complete with battery and connecting wire £2.15.0, P. & P. 2/6.

"SATELLITE" TRANSISTOR RADIOS
Complete with case, earphone and battery. All tested before despatch. 6 transistor. Size 2 1/2" wide by 4 1/2" high by 1 1/2" deep. 43/6, P. & P. 2/6.
9 transistor, size 6 1/2" wide by 4" high by 1 1/2" deep, with telescopic aerial. £4.19.6, P. & P. 3/6.

BARGAINS IN TRANSISTORS:
AC127, AF14, 115, 116, 117, 118, 119, OC169, 170, 171, 172, 200, 202, 203, 204, 5/6.
OC72, 75, 82, 83, AAZ12, BY38, BCZ11, 3/6.
OC71, 81, 3/-, R.F. Packs 1 OC44, 2 OC45 8/6, A.F. Packs 1 OC81D, 2 OC81 (Mullard), 8/6.
GET113, Red Spot 2A/-, OC26, 28, 29/6.
ORP12 Light Cell 8/6.
Diodes OA81 2/3, OA91, OA95 1/6, P. & P. 1/-.

TRANSISTOR ELECTROLYTICS:
1, 2, 4, 5, 8, 10, 16, 25, 32, 50, 100 mfd 15 volt working 1/6, P. & P. 1/-.
250 mfd DC 3/-, 500 mfd 12/-, DC 3/-, 500 mfd 25/-, DC 3/6, P. & P. 1/-.


RESISTORS: 1 watt 10% from 4.7 ohm to 10 meg 5d. each, 4/- doz. P. & P. 1/- (minimum order 2/6).

PAPER CONDENSERS for Cross-Over Units 2 mfd 2/6, P. & P. 1/-.




SPEAKER SYSTEMS

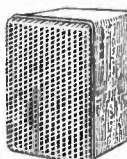THE CAXTON COLUMN
This is a column cabinet. Size 22 1/2 x 6 x 6 1/2 in., fitted with 3 speakers. This will handle 10 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at £3 plus 10/- P. & P.



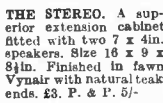THE MILTON. A Hi-Fi Bookcase Cabinet. Size 9 x 5 x 6 in. with 6in. speaker. Finished in Teak cloth with bold silk front. 30/-, P. & P. 3/6.



THE STEREO. A superior extension cabinet fitted with two 7 x 4 in. speakers. Size 16 x 9 x 9 1/2 in. Finished in fawn Vynair with natural teak ends. £3. P. & P. 5/-.



THE IMP. Extension Speaker Cabinet. Wedge shaped size 7 1/2 x 6 1/2 in. fitted with 7 x 4 in. speaker. Covered with attractive walnut with fawn Vynair front. Key-hole slot in back. Only 25/6, Post 2/6. Note: All cabinets new and made with tin. chipboard. All speakers ex TV reconditioned hi flux magnet. All carefully tested before despatch.

HAYDON SPEAKER SYSTEM.
Size 16 1/2 x 15 x 7 1/2 in., fitted 12in. Speaker and volume control. Fabric covered. £4.17.6, P. & P. 10/-.

SPEAKER ENCLOSURES

Tony Corner Cabinet 20 x 10 x 7 in. takes 10 x 6 in. speaker covered in Rexine and Vynair, 45/-, P. & P. 5/-.
Blake Cabinet size 18 x 24 1/2 x 9 1/2 in., fabric covered £4.10.0, P. & P. 10/-.
Haydon, 16 1/2 x 15 x 7 1/2 in. fabric covered suitable for 12in. speaker, 45/-, P. & P. 7/6.
Hi-Fi Bookshelf speaker enclosure foam lined, cabinet size 10 1/2 x 5 1/2 x 7 1/2 in. Teak finish, £3.0.0, P. & P. 3/6.
Wooler for above £3.0.0, P. & P. 2/6. Tweeter 12/6, P. & P. 1/6. Condenser for crossover 2/6. Terminals 2/6 pair, P. & P. 1/-.
PLINTH Teak finish to match above Hi-Fi speaker size 17 1/2 x 14 x 4 in. for Garrard 1000, 2000, 3000, AT60, SP25, £2.17.6, P. & P. 4/6.
SPEAKERS:
Elac Heavy duty Ceramic Magnet 11,000 Hme, 10in. round 10 x 6 in. 3 ohm or 15 ohm, 42/6, P. & P. 3/6.
8in. round 15 or 3 ohm, 38/6, P. & P. 3/6.
E.M.I. 13 1/2 x 8in. 15 or 3 ohm, 42/6, P. & P. 3/6.
E.M.I. Tweeter, 12/6, P. & P. 1/6.
R.T.C. 12in. 20 watt 15 ohm Ceramic magnet £5.5.0, P. & P. 3/6.
8 x 4 in. Elliptical 30 ohm 30/-, P. & P. 3/6.
All other speakers supplied—Goodmans, Bakers, W.B., Wharfedale, Eagle, Tripletone.

EARPIECES WITH CORD AND 3.5 mm. plug. 8 ohm magnetic, 3/-, 250 ohm 4/-, 180 ohm with clip, 6/6.
Xtal 4/-, P. & P. 6d.

TRANSISTOR SPEAKERS 8 ohm 2in. 8/6, 3in. 10/6, 3 1/2 in. 12/6, P. & P. 1/-.

PANEL LIGHTS. 6v Red, Blue, Green, Yellow, White (uses Lilliput bulbs) 3/- each, P. & P. 1/-.

NEON PANEL LIGHTS 200-250v 3/- each, P. & P. 1/-.

ROTARY SWITCHES:
2 pole Mains Switch 3/-, 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 8/6 each, P. & P. 1/-.

PIANO KEY BUSH BUTTON SWITCHES. 7 button. Including mains on/off. 6 banks of 6 P.C.O. 8/6, P. & P. 1/-.

FERROX ROD AERIAL with coils, 8 x 1/4 in. 5/6, P. & P. 1/-.

Stockists of ● Eagle Products ● Goodmans ● V.B. ● Wharfedale ● Bakers ● Tripletone ● Linear, all makes of amplifiers and speakers supplied. S.A.E. please. Trade terms to bona fide dealers.

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON, S.W.17 Telephone BALham 3984

(Closed all day Wednesday)
(four minutes from Tooting Broadway Underground Station)

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/-, No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

0A2	6/-	6AH6	10/-	6P17	6/-	7B5	11/-
0A3	8/-	6AK5	5/-	6P18	7/6	7B7	7/-
0B2	9/-	6AL5	10/-	6P23	14/-	7B8	8/-
0B3	9/-	6AL5	3/-	6P25	14/-	7B9	8/-
0C3	6/-	6AM6	4/-	6P26	6/-	7C5	12/6
0D3	6/-	6AQ5	5/6	6P28	13/-	787	22/6
1A3	4/-	6AQ6	10/-	6P29	6/-	74	8/6
1A5GT	5/-	6AR4	10/-	6P30	6/-	724	6/-
1A7GT	7/-	6AR5	6/-	6P32	3/-	9B3W6	7/-
1AX2	10/-	6AR6	6/-	6P33	15/-	10D1	7/-
1B3GT	8/-	6AS5	5/-	6H6	3/-	10F1	7/-
1C4GT	8/-	6AS6	6/-	6J4	9/-	10F3	8/-
1G6GT	6/-	6AST4	15/-	643GT	5/-	10F9	10/-
1H5GT	6/6	6AT6	4/6	636	3/6	10F18	7/6
1L4	2/6	6AV6	5/-	677	8/-	10L1	7/6
1Q54T	8/-	6AV6	5/-	677G	8/-	10L14	6/6
1R4	5/-	6AW8A	12/6	663GT	8/-	10L14	6/6
1R5	6/-	6B4G	15/-	6K7	7/6	10L14	6/6
184	5/-	6B7	5/-	6K7G	2/-	10L14	6/6
185	4/6	6B8	7/-	6K23	7/6	10L14	6/6
1T4	3/-	6B8G	2/6	6K25	24/-	10L14	6/6
1T5GT	8/-	6BA6	4/-	6L1	10/-	10L14	6/6
1U4	5/-	6BA7	15/-	6L5G	6/-	10P13	15/-
1U5	6/-	6BE6	4/6	6L6GC	8/-	10P14	16/-
1V	8/-	6BG6A	12/6	6L7	5/6	11D3	7/-
1X2B	7/-	6BH6	7/6	6L12	5/-	11D5	7/-
2C2BA	8/-	6D6	7/6	6L13	5/6	11D5	7/-
2C51	8/-	6BK4	20/-	6L16	5/6	12AC5	8/-
2C'W4	12/-	6BK7A	9/-	6L18	6/-	12AD6	9/-
2E21	5/6	6BN6	7/6	6LD3	8/6	12A8G	7/6
2E24	42/6	6BQ7A	7/6	6L12	6/6	12AHTGT	7/6
2E26	22/6	6B6	15/-	6L13	5/6	12AV6	5/6
2K2	4/-	6B87	25/-	6L120	8/-	12A15	5/-
2X2A	8/-	6BW6	6/-	6N74GT	6/6	12A25	5/-
3A5	10/-	6BW7	10/-	6P1	11/-	12A76	4/6
310	3/-	6C4	4/-	6P54T	8/-	12A16	5/-
312A	35/-	6C5GT	6/6	6P25	17/-	12A17	5/6
3E2B	60/-	6C8	4/-	6P28	12/-	12AV6	5/6
3Q4	7/-	6C81	8/-	6Q7	7/-	12A77	8/-
3Q54T	6/6	6C86	5/-	6R7G	6/-	12A78	20/-
3V4	6/-	6CD6A	4/-	6R8A	7/-	12A77	5/6
4B32	80/-			6R8F	5/-	12A77	10/-
4J30A		6CG7	20/-	6R8T	8/-	12A78	9/-
514CY	8/-	6CH6	8/-	6R8T	8/-	12B46	6/-
514CY	8/-	6CL6	9/-	6R8T	4/-	12B56	5/6
514CY	8/-	6CW4	12/-	6R8T	7/-	12B77	6/-
514CY	8/-	6CY5	7/-	6R8TGT	6/-	12B77	6/-
5V4G	7/6	6CY7	11/-	6R8TGT	5/6	12E1	20/-
5Z3	7/6	6D6	7/6	6R8T	6/-	12H6	4/-
5Z4G	7/-	6D6K	8/-	6R8T	7/-	12J54T	3/-
5Z4GT	7/6	6D84	15/-	6R8T	3/-	12K5	10/-
6/3012	12/6	6E8A	11/-	6T8	8/-	12K8	8/-
6A6	4/-	6F1	14/-	6T4GT	12/-	12Q7GT	5/6
6A8G	5/6	6F61B	6/-	6H8	6/6	12S47	10/-
6AB4	6/-	6F6	7/-	6V4GT	6/-	12S47	8/-
6AR7	4/-	6P11	6/-	6X4	4/-	12S47	8/-
6AF4A	9/-	6F13	6/6	6X54T	5/-	12S47	7/-
6AG5	8/-	6P14	15/-	6Y6G	10/-	12S47	5/-
6AG7	6/-	6P15	11/-	6Z4	5/-	12S47	4/-

First Quality Fully Guaranteed

Laerx BRAND

ELECTRONIC VALVES

12S47	4/-	50L6GT	7/6	DAP92	6/-	EC935	17/-
12S47	4/-	50L6GT	7/6	DAP96	6/6	EC940	9/6
12S47	7/6	50L6GT	12/6	DH96	6/6	EC941	4/-
12S47	7/6	50L6GT	12/6	DH101	7/6	EC942	5/6
12S47	15/-	50L6GT	20/-	DK32	7/-	EC943	5/6
12S47	15/-	50L6GT	20/-	DK40	10/-	EC944	5/6
12S47	15/-	50L6GT	20/-	DK92	7/6	EC945	5/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC946	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC947	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC948	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC949	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC950	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC951	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC952	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC953	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC954	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC955	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC956	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC957	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC958	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC959	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC960	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC961	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC962	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC963	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC964	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC965	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC966	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC967	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC968	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC969	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC970	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC971	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC972	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC973	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC974	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC975	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC976	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC977	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC978	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC979	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC980	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC981	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC982	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC983	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC984	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC985	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC986	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC987	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC988	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC989	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC990	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC991	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC992	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC993	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC994	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC995	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC996	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC997	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC998	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC999	7/-
12S47	15/-	50L6GT	20/-	DK96	7/6	EC1000	7/-

EF96	6/-	GTE175M		PCL800	14/-	U25	14/-
EF98	5/6			PCL801	16/-	U26	14/-
EF99	4/-	GZ30	7/-	PEN4D1	10/-	U76	4/-
EF99	4/-	GZ31	5/-	PEN4D1	10/-	U81	10/-
EF99	4/-	GZ32	10/-	PEN4D1	10/-	U91	14/-
EF99	5/-	GZ33	12/6	PEN45	6/6	U92	8/-
EF99	2/6	GZ34	10/-	PEN45D	12/-	U93	8/-
EF99	13/-	GZ37	12/6	PEN45D	12/-	U94	11/-
EF183	6/-	HABC80		PEN46	6/-	U95	17/-
EF184	6/-	HABC90	8/-	PEN220A	6/-	U96	5/6
EF185	20/-	HABC91	4/6	PEN389	9/-	U97	8/-
EF186	14/-	HABC92	5/6	PEN384	7/-	U98	7/-
EF187	14/-	HABC93	5/6	PEN384	7/-	U99	7/-
EF188	14/-	HABC94	5/6	PEN384	7/-	U100	7/-
EF189	14/-	HABC95	5/6	PEN384	7/-	U101	7/-
EF190	14/-	HABC96	5/6	PEN384	7/-	U102	7/-
EF191	14/-	HABC97	5/6	PEN384	7/-	U103	7/-
EF192	14/-	HABC98	5/6	PEN384	7/-	U104	7/-
EF193	14/-	HABC99	5/6	PEN384	7/-	U105	7/-
EF194	14/-	HABC100	5/6	PEN384	7/-	U106	7/-
EF195	14/-	HABC101	5/6	PEN384	7/-	U107	7/-
EF196	14/-	HABC102	5/6	PEN384	7/-	U108	7/-
EF197	14/-	HABC103	5/6	PEN384	7/-	U109	7/-
EF198	14/-	HABC104	5/6	PEN384	7/-	U110	7/-
EF199	14/-	HABC105	5/6	PEN384	7/-	U111	7/-
EF200	14/-	HABC106	5/6	PEN384	7/-	U112	7/-
EF201	14/-	HABC107	5/6	PEN384	7/-	U113	7/-
EF202	14/-	HABC108	5/6	PEN384	7/-	U114	7/-
EF203	14/-	HABC109	5/6	PEN384	7/-	U115	7/-
EF204	14/-	HABC110	5/6	PEN384	7/-	U116	7/-
EF205	14/-	HABC111	5/6	PEN384	7/-	U117	7/-
EF206	14/-	HABC112	5/6	PEN384	7/-	U118	7/-
EF207	14/-	HABC113	5/6	PEN384	7/-	U119	7/-
EF208	14/-	HABC114	5/6	PEN384	7/-	U120	7/-
EF209	14/-	HABC115	5/6	PEN384	7/-	U121	7/-
EF210	14/-	HABC116	5/6	PEN384	7/-	U122	7/-
EF211	14/-	HABC117	5/6	PEN384	7/-	U123	7/-
EF212	14/-	HABC118	5/6	PEN384	7/-	U124	7/-
EF213	14/-	HABC119	5/6	PEN384	7/-	U125	7/-
EF214	14/-	HABC120	5/6	PEN384	7/-	U126	7/-
EF215	14/-	HABC121	5/6	PEN384	7/-	U127	7/-
EF216	14/-	HABC122	5/6	PEN384	7/-	U128	7/-
EF217	14/-	HABC123	5/6	PEN384	7/-	U129	7/-
EF218	14/-	HABC124	5/6	PEN384	7/-	U130	7/-
EF219	14/-	HABC125	5/6	PEN384	7/-	U131	7/-
EF220	14/-	HABC126	5/6	PEN384	7/-	U132	7/-
EF221	14/-	HABC127</					

PRACTICAL WIRELESS

blueprints

The following blueprints are available from stock. **Descriptive text is not available but the date of issue is shown for each blueprint.** Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier }	(Oct. 1962)	5/-	The Celeste 7-transistor Portable Radio }	(June 1963)	5/-
The PW Signal Generator }			The Spinette Record Player }		
The Berkeley Loudspeaker Enclo- sure }	(Dec. 1962)	5/-	Transistor Radio Mains Unit }	(June 1964)	5/-
The Luxembourg Tuner }			7 Mc/s Transceiver }		
The PW Troubadour }	(June 1962)	7/6	The Citizen (December 1961) }		5/-
The PW Everest Tuner }			The Mini-amp (November 1961) }		5/-
The PW Britannic Two }	(May 1962)	6/-	The Beginner's Short Wave Superhet (Dec. 1964) }		5/-
The PW Mercury Six }			The Empire 7 Three-band Receiver (May 1965) }		5/-
Beginner's Short Wave Two }	(Nov. 1963)	5/-	Electronic Hawaiian Guitar (June 1965) }		5/-
S.W. Listener's Guide }			Progressive SW Superhet (February 1966) }		5/-
PW "Sixteen" Multirange Meter }	(Jan. 1964)	5/-	Beginner's 5-Band Receiver }	(Dec. 1966)	5/-
Test Meter Applications Chart }			Home Intercom Unit }		

PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN
★ THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL ★
RADIO, TV OR AUDIO EQUIPMENT.

PRACTICAL WIRELESS

query service

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON


This coupon is available until 3rd November, 1967 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, NOVEMBER 1967

NEW SOLID STATE HIGH FIDELITY EQUIPMENT BRITISH MADE

POWER AMPLIFIERS — PRE AMPLIFIERS —
POWER SUPPLIES


We proudly present this new range of Audio Equipment developed from Dinsdale—each unit or system will compare favourably with other professional equipment available at much higher prices. Brief details are below:

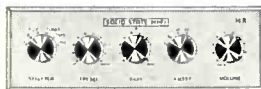

MP3



SP8-2

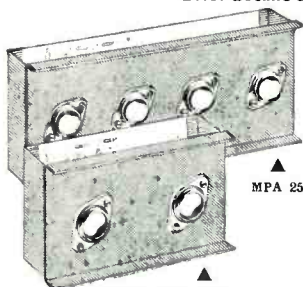

MPA 25

MPA 12/13, MPA 12/15

COMPLETE FULLY ILLUSTRATED
BROCHURE FREE ON REQUEST

System	Comprising	Price
★ A	5 watt mono for 3/5 ohm speakers	£10.3.0
★ 1	12 watt mono for 3 to 5 ohm speakers	£13.17.6
★ 2	12 watt mono for 12 to 16 ohm speakers	£14.12.6
★ 4	24 watt mono two channel for 12 to 16 ohm speakers	£20.15.0
★ 8	20 watt mono/stereo for 12 to 16 ohm speakers	£24.0.0
★ 9	24 watt mono/stereo for 3 to 5 ohm speakers	£26.15.0
★ 14	40 watt mono/stereo for 7 1/2 to 16 ohm speakers	£29.10.0

THE FINEST VALUE IN HIGH FIDELITY — CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

VHF TUNER



57/105 Mc/s Transistor Superhet. Gearing tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in. Complete with dial plate. 5 Mullard Transistors. Plus 4 Diodes. (Cabinet Assembly 20/- extra).

TOTAL COST TO BUILD **£6.19.6** P.P. 2/6


REGENT SIX MW/LW POCKET RADIO TO BUILD



6-Transistor superhet Gearing tuning. Push-pull speaker output. Molded Cabinet 5 x 3 x 1 1/2 in.

TOTAL COST TO BUILD **£3.9.6** P.P. 2/- Full tuning on both bands.

FM STEREO DECODER

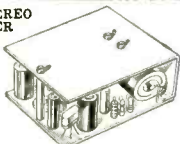

7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. As used by B.B.C. and G.P.O.

Complete Kit Price **£5.19.6** P.P. 2/-

TOURMASTER TRANSISTOR CAR RADIO British Made



7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wavechange. RF stage. Supplied built, boxed, ready to use with Speaker and B.B.C. Car fitting kit and manufacturer's current guarantee. Special Bargain Offer. Buy Now! LIST PRICE 15 GNS. **£7.19.6** P.P. 4/6 Push-button version £11.19.6 P.P. 4/6

BUILD A QUALITY TAPE RECORDER



3-speed version using '383' decks ★ TWO-TRACK Deck £10.10.0. Martin Amplifier, £14.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7 in. 1,200ft. tape, spare spool. Today's Value 24s. **27 gns.** P.P. 15/- ★ FOUR-TRACK Deck £13.10.0. Martin Amplifier £15.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7 in. 1,200ft. tape, spare spool. Today's value 25s. **30 gns.** P.P. 15/-



7-TRANSISTOR MW-LW SUPERHET PORTABLE NEW!

New Printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 Mullard transistors, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial. Easy to build with terrific results. All local and Continental stations.


TOTAL COST TO BUILD **£6.19.6** P.P. 3/6

MW/LW QUALITY TRANSISTOR RADIO TUNER



Fully tunable superhet with excellent sensitivity and selectivity. Output up to 4 volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.

TOTAL COST TO BUILD **£3.19.6** P.P. 2/6

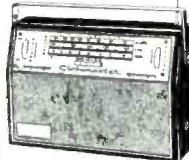

GLOBEMASTER. 6-Mullard Transistors. 7 x 4 in. speaker. Very sensitive, excellent coverage. Full 3-waveband tunable. Push-button wavechange. Superhet printed circuit. Black-chromed cabinet 11 x 7 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt push-pull output. **£7.19.6** P.P. 3/6 TOTAL COST

Send for Free List No. 36 of Transistors and Semi-conductor devices

We have the
★ LARGEST RANGE—OVER 650 TYPES
★ COMPETITIVE PRICES
★ 1st GRADE STOCKS
★ FULLY GUARANTEED
24-PAGE ILLUSTRATED BROCHURE LISTING 2,000 DEVICES. Data and circuits including Valve and Quartz Crystal lists, 1/- post paid.

SILICON CONTROLLED RECTIFIERS From 5/-
FIELD EFFECT TRANSISTORS from 9/6
POWER TRANSISTORS from 6/-
RECTIFIERS, ZENERS, TUNNEL DIODES From 12/6
LIGHT DEVICES, etc.

Send for Full Details on all advertised products Free on Request

BUILD THESE PW/PF DESIGNS
EXPLORER (less chassis) 79/6
or with drilled chassis 99/6
MULTI-BAND SUPERHET 29 0/0
PHOTO FLASH SLAVE UNIT 42/6
SOLID STATE IGNITION 26 19/6
TRANSFILTER PORTABLE 26 6/0
SWITCHED FM TUNER 69/6
SCREENWIPER 39/6
Parts List on request

MAYFAIR PORTABLE

Designed by L. W. ROCHE



ELECTRONIC ORGAN
TOTAL COST
99 GNS.

- Build this superb Instrument stage by stage in your own home
- A truly portable Instrument for all enthusiasts.
- Fully transistorised POLYPHONIC British design
- Call in for a DEMONSTRATION—full details on request.

ORGAN COMPONENTS

We carry a comprehensive stock of organ components for Transistor and Valve Free Phase designs; complete details on request.

CATALOGUE

1967 EDITION, 225 PAGES
6,000 ITEMS, 1,000 ILLUSTRATIONS
★ 20 pages of transistors and semi-conductor devices, valves and crystals
★ 150 pages of components and equipment
★ 50 pages of microphones, decks and Hi-Fi equipment

The most comprehensive—concise—clear components catalogue in Great Britain. Complete with 10/- worth Discount Vouchers. Free with every copy

Send today 8/6 Post paid



WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.

Phone: (01) 723-108/9 Open Mon.—Sat. 9 a.m.—6 p.m., Thurs. 9 a.m.—1 p.m.

HENRY'S RADIO LTD



303 EDGWARE ROAD, LONDON W.2