

Radio-Electronics

SPECIAL ISSUE—HI-FI & STEREO

75c ■ OCT. 1975

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

BUILD WITH ONE IC
4-Channel Synthesizer

BOOKSHELF SPEAKERS
How To Buy A System

HI-FI
ACCESSORIES
That Are
Worth
Owning

R-E LAB HI-FI TESTS

★ **Pioneer CT-F9191**
Tape Deck

★ **Soundcraftsmen**
RP-2212 Equalizer



4-Channel Synthesizer
SO
WH


"QS" Going?

PL
Jack Darr's Service Clinic
Step-By-Step
Troubleshooting Charts

NEW HI-FI
TEST GEAR
For Precise Measurements

PTS ELECTRONICS

Precision Tuner Service

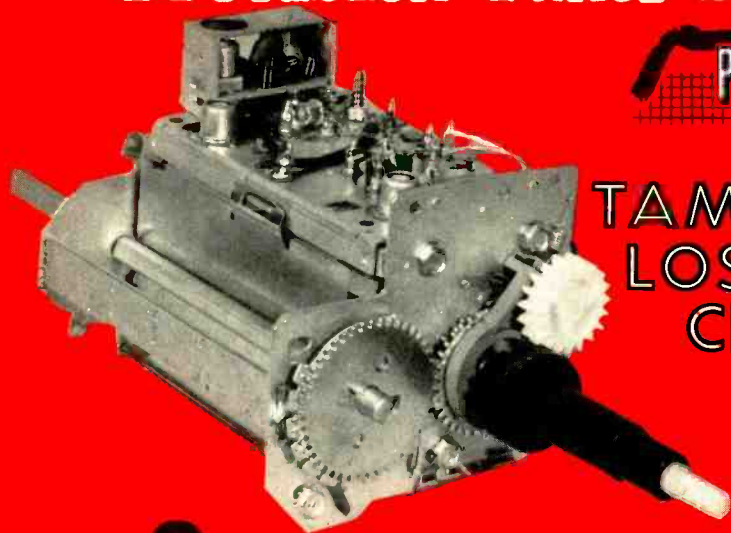

is proud to announce the
GRAND OPENING
of our new Service Centers in

TAMPA
LOS ANGELES
COLUMBUS, OHIO
PHOENIX
BOSTON
NORFOLK
MILWAUKEE

Fast 8 hr. Service!

LET US TAKE CARE OF YOUR TUNER PROBLEMS...

PTS will repair any tuner—no matter how old or new. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located plants. Best Quality—you and your customers are satisfied.

PTS uses only ORIGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.

PTS is recommended by more TV Manufacturers than any other tuner company and is overhauling more tuners than all other tuner services combined.

VHF, UHF \$10.95
UV-COMBO 17.95
IF-SUBCHASSIS 12.50

Major parts and shipping charged at cost. (Dealer net!)

PTS ELECTRONICS, INC.

HOME OFFICE	BLOOMINGTON, INDIANA 47401	5233 S. HIGHWAY 37	812-824-9331
ALABAMA	BIRMINGHAM, ALABAMA 35222	524 32ND ST. SO.	205-323-2657
ARIZONA	PHOENIX, ARIZONA 85061	2412 W. INDIAN SCHOOL RD.	602-279-8718
CALIFORNIA CENTRAL	LOS ANGELES, CA. 90023	4184 PACIFIC WAY	213-266-3728
CALIFORNIA NORTH	SACRAMENTO, CA. NO. 95841	4611 AUBURN BLVD.	916-482-6220
CALIFORNIA SOUTH	SAN DIEGO, CA. SO. 92105	5111 UNIVERSITY AVE.	714-280-7070
COLORADO	ARVADA, COLORADO 80001	4958 ALLISON ST.	303-423-7080
FLORIDA NORTH	JACKSONVILLE, FLA. NO. 32210	1918 BLANDING BLVD.	904-389-9952
FLORIDA CENTRAL	TAMPA, FLA. 33690	2703 S. MACDILL	813-839-5521
FLORIDA SOUTH	MIAMI, FLA. SO. 33168	12934 N.W. 7TH AVE.	305-685-9811
INDIANA	BLOOMINGTON, IND. 47401	5233 S. HIGHWAY 37	812-824-9331
KANSAS	KANSAS CITY, KANSAS 66106	3116 MERRIAM LANE	913-831-1222
LOUISIANA	METAIRIE, LA. 70003	2914 WYCHWOOD DR.	504-885-2349
MARYLAND	SILVER SPRINGS, MD. 20910	1105 SPRING ST.	301-565-0025
MASSACHUSETTS EAST	SOMERVILLE, MASS. 02144	52 HOLLAND ST.	617-666-4770
MASSACHUSETTS WEST	SPRINGFIELD, MASS. 01103	191 CHESTNUT ST.	413-734-2737
MICHIGAN	DETROIT, MICH. 48235	13709 W. 8 MILE RD.	313-862-1783
MINNESOTA	MINNEAPOLIS, MINN. 55408	815 W. LAKE ST.	612-824-2333
MISSOURI	ST. LOUIS, MO. 63130	8456 PAGE BLVD.	314-428-1299
NEW JERSEY	E. PATERSON, N. JERSEY 07407	158 MARKET ST.	201-791-6380
NEW YORK	BUFFALO, NEW YORK 14212	993 SYCAMORE ST.	716-891-4935
NORTH CAROLINA	CHARLOTTE, N. CAR. 28205	724 SEIGLE AVE.	704-332-8007
OHIO SOUTH	CINCINNATI, OHIO 45215	8180 VINE ST.	513-821-2298
OHIO CENTRAL	COLUMBUS, OHIO 43227	4003 E. LIVINGSTON AVE.	614-237-3820
OHIO NORTH	PARMA, OHIO 44134	5682 STATE RD.	216-845-4480
OKLAHOMA	OKLAHOMA CITY, OK. 73106	3007 N. MAY	405-947-2013
OREGON	PORTLAND, OREGON 97213	5220 NE SANDY BLVD.	503-282-9636
PENNSYLVANIA WEST	PITTSBURGH, PA. 15202	257 RIVERVIEW AVE. W.	412-761-7648
PENNSYLVANIA EAST	UPPER DARBY, PA. 19082	1742-44 STATE RD.	215-352-6609
TENNESSEE	MEMPHIS, TENN. 38118	3614 LAMAR AVE.	901-365-1918
TEXAS SOUTH	HOUSTON, TEXAS 77032	4324-26 TELEPHONE AVE.	713-644-6793
TEXAS NORTH	LONGVIEW, TEXAS 75601	MOPAC RD.	214-753-4334
VIRGINIA	NORFOLK, VA. 23504	3118 E. PRINCESS ANNE RD.	804-625-2030
WASHINGTON	SEATTLE, WASH. 98108	432 YALE AVE.	206-623-2320
WISCONSIN	MILWAUKEE, WIS. 53215	3509 W. NATIONAL	414-643-8800

P
T
S
No.
1

We offer you finer, faster...

...Precision
Tuner Service








ELECTRONICS, INC. ...

... Number ONE and still trying harder!
(Not a Franchise Company)

1 YEAR
GUARANTEE

Circle 1 on reader service card

INSIDE the Altair® Computer

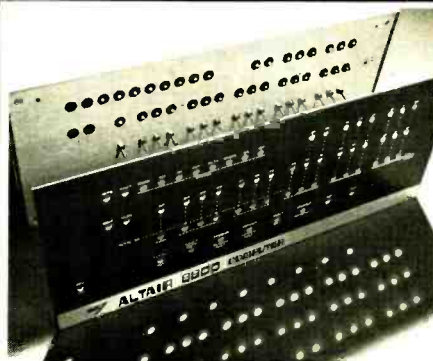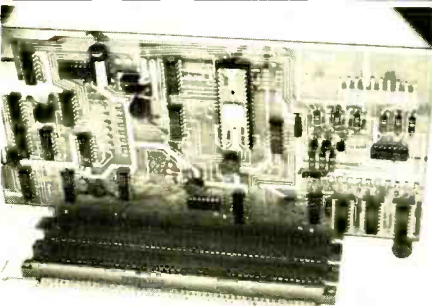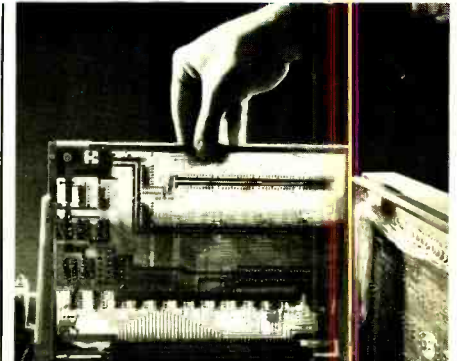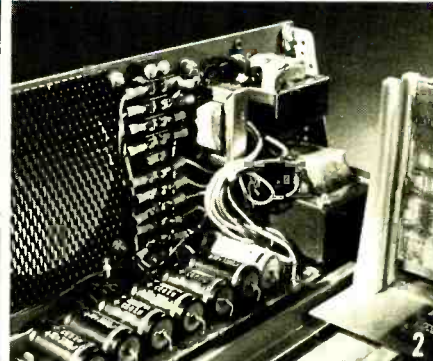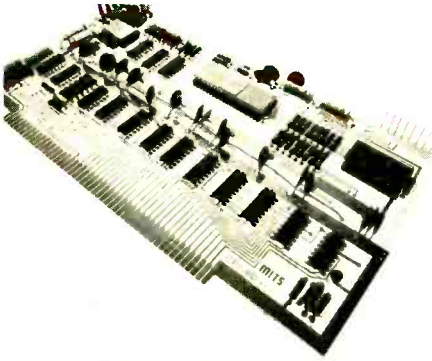

1. Central Processing Unit (CPU) Board.

This double-sided board is the heart of the Altair 8800. It was designed around a powerful, byte oriented, variable word length processor—a complete central processing unit on a single LSI chip using n-channel, silicon gate MOS technology. The CPU board also contains the Altair System Clock—a standard TTL oscillator with a 2.000 MHz crystal as the feedback element.

2. Power Supply. The Altair Power Supply provides two +8, a +16 and a -16 volts. These voltages are unregulated until they reach the individual boards (CPU, Front Panel, Memory, I/O, etc.). Each board has all the necessary regulation for its own operation.

The Altair Power Supply allows you to expand your computer by adding up to 16 boards inside the main case. Provisions for the addition of a cooling fan are part of the Altair design.

3. Expandability and custom designing.

The Altair has been designed to be easily expanded and easily adapted to thousands of applications. The basic Altair comes with one expander board capable of holding four vertical boards. Three additional expander boards can be added inside the main case.

4. Altair Options.

Memory boards now available include a 1024 word memory board, a 2048 word memory board, and a 4096 word memory board. Interface boards include a parallel board and 3 serial boards (RS232, TTL and Teletype). Note: Interface boards allow you to connect the Altair Computer to computer terminals, teletypewriters, line printers, plotters and other devices.

Other Altair Options include additional expander boards, computer terminals, audio-cassette interface board, line printers, ASCII keyboards, floppy disc system, alpha-numeric display and more.

5. All aluminum case and dress panel.

The Altair Computer has been designed both for the hobbyist and for industrial use. It comes in an all aluminum case complete with sub-panel and dress panel.

6. It all adds up to one fantastic computer.

The Altair is comparable to mini-computers costing 10-20 thousand dollars. It can be connected to 256 input/output devices and can directly address up to 65,000 words of memory. It has over 200 machine instructions and a cycle time of 2 microseconds.

You can order the Altair Computer by simply filling out the coupon in this ad or by calling us at 505/265-7553. Or you can ask for free technical consultation or for one of our free Altair System Catalogues.

PRICES:

Altair Computer kit with complete assembly instructions	\$439.00
Assembled and tested Altair Computer	\$621.00
1,024 word memory board	\$97.00 kit and \$189.00 assembled
2,048 word memory board	\$145.00 kit and \$195.00 assembled
4,096 word memory board	\$264.00 kit and \$338.00 assembled
Full Parallel Interface board	\$92.00 kit and \$114.00 assembled
Serial Interface board (RS232)	\$119.00 kit and \$138.00 assembled
Serial Interface board (TTL or teletype)	\$124.00 kit and \$146.00 assembled
Audio Cassette Record Interface	\$123.00 kit and \$174.00 assembled
Expander Board (adds 4 slots to 8800)	\$16.00 kit and \$32.00 assembled

NOTE: Altair Computers come with complete documentation and operating instructions. Altair customers receive software and general computer information through free membership to the Altair User's Club. Software now available includes a resident assembler, system monitor, text editor and BASIC language.

MIT/6328 Linn NE, Albuquerque, NM, 87108 505/265-7553

MIT
"Creative Electronics"

Prices and specifications subject to change without notice. Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units.

Circle 2 on reader service card

MAIL THIS COUPON TODAY!

- ☐ Enclosed is check for \$_____
- ☐ BankAmericard # _____
- ☐ or Master Charge # _____
- ☐ Credit Card Expiration Date _____
- ☐ Altair Computer ☐ Kit ☐ Assembled
- ☐ Options (list on separate sheet)
- Include \$8.00 for postage and handling
- ☐ PLEASE SEND FREE ALTAIR SYSTEM CATALOGUE

NAME _____

ADDRESS _____

CITY _____ STATE & ZIP _____

MIT/6328 Linn NE, Albuquerque, NM, 87108
505/265-7553



Leather Tool Pouch



Genuine Swiss Army Knife



Bicentennial
Pewter
Key Ring



Yellow Hard Hat



Columbia 10-Speed
Bicycles
Men's & Ladies' Models



Skil 16" Gasoline Chain Saw



Skil 3/8"
X-Tra Tool
with Accessories

Weller Cordless
Soldering Iron Kit



Nylon
Installers
Jacket
Blue with Gold
Imprint

10 Spalding Golf Clubs
Woods, Irons & Wedge



Jerrold Levelite,
Model L-200
TV Signal Presence
Indicator



Personalized
Digital
LED Watch —
Your Name
Under Crystal

A Bonanza of FREE GIFTS

...for Professional Antenna Installers

More and more professional installers are choosing Jerrold top-rated antennas, preamplifiers, accessories and MATV equipment. If you are one of the many professionals using Jerrold equipment, this Jerrold Bicentennial Bonanza program will give you the opportunity to gain free

gifts as our way of saying "Thank You." If you are not yet using the Jerrold line, these premium gifts are an incentive for you to try Jerrold products. For complete details on

this program, contact your participating Jerrold distributor today.

For the name of your local Jerrold distributor call the appropriate office listed below.

Available only from your participating Jerrold distributor

JERROLD



a GENERAL INSTRUMENT company

Distributor Sales Division

HEADQUARTERS & EASTERN OFFICE 200 Witmer Rd., Horsham, Penna. 19044, (215) 674-4800
SOUTHERN OFFICE 1 Perimeter Place, Suite 101, Atlanta, Georgia 30339, (404) 432-3102
WESTERN OFFICE 1255 Veterans Blvd., Redwood City, Calif. 94063, (415) 365-5050
MIDWESTERN OFFICE 1334 Atlantic Street, North Kansas City, Mo. 64116, (816) 474-0450

Circle 3 on reader service card

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

OCTOBER 1975 Vol. 46 No. 10

HI-FI STEREO 4-CHANNEL

- 16 **Inside the QS Matrix**
How the magic is performed. **by Hideo Kitahra**
- 36 **R-E Lab Tests Pioneer CT-F9191**
A most complete report on a new front-loading cassette deck. **by Len Feldman**
- 39 **R-E Lab Tests Soundcraftsmen RP 2212**
Detailed report on a new equalizer. **by Len Feldman**
- 41 **How To Buy Bookshelf Speakers**
First of a 3-part series that examines the user's requirements and pits them against the manufacturer's product. **by Art Kleiman**
- 52 **Hi-Fi Add On's You Should Know**
They may not be necessities, but they can add convenience to your music system. **by Fred Petras**

BUILD ONE OF THESE

- 33 **4-Channel Matrix Synthesizer**
Use it with your 4-channel system. It converts 2-channel music sources into 4-channel matrix signals—for about \$20. **by Arnold Nichols**
- 59 **Doorbell Programmer Sets Up Your Prom**
Use it to program the PROM doorbell you built last month. **by Ralph E. Cousino**

TEST EQUIPMENT

- 50 **Super-Fi Testing**
When you test hi-fi gear that has remarkable specs, you've got to use test equipment that's equally remarkable. **by Len Feldman**
- 104 **Equipment Report**
Simpson 432, "Chroma-Line" color-pattern generator.

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Sneak preview of tomorrow's news. **by David Lachenbruch**

TELEVISION


- 62 **Step-By-Step Troubleshooting Charts**
Good color depends on a good video signal. Check the video stages when color isn't right. **by Stan Prentiss**
- 69 **Service Clinic**
DC volume controls. **by Jack Darr**
- 96 **Reader Questions**
R-E's Service Editor solves reader problems.

DEPARTMENTS

- | | |
|------------------------------|-------------------------|
| 12 Advertising Sales Offices | 90 New Literature |
| 108 Advertising Index | 86 New Products |
| 14 Letters | 97 Next Month |
| 6 New & Timely | 111 Reader Service Card |


ON THE COVER

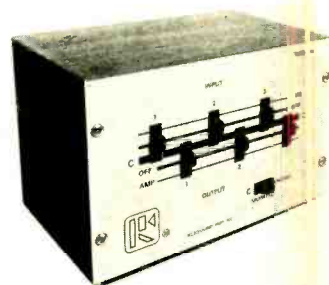R-E's hi-fi test lab puts some of the latest hi-fi gear through its paces. Here the Pioneer CT-F9191 gets a thorough going over. The complete report starts on page 36.



HI-FI ADD-ON ACCESSORIES can make your system easier to use and more interesting to listen to. See the latest products.

... turn to page 52

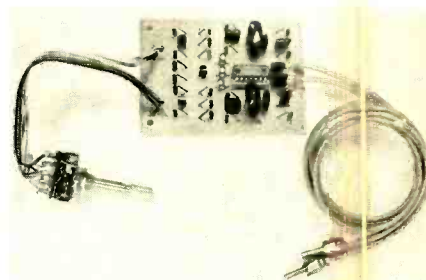

4-CHANNEL MATRIX SYNTHESIZER is easy to build. One IC turns 2-channel stereo into 4-channel matrix sound. ... see page 33

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6410. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1975 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Holographic videodisc

The leading contenders in the home videodisc sweepstakes have been laser-optical systems developed by Philips, MCA and Thomson-CSF; a capacitance system developed by RCA, and the German-British TeD mechanical system. Now along comes Hitachi with the first Japanese-developed system unveiled to date. The Hitachi system, already demonstrated in the lab, uses holography. The disc spins at a lazy 6 rpm, as opposed to 1,800 rpm for the American-standards version of the optical and mechanical systems and 450 rpm for the capacitance system.

The Hitachi system records each frame of the color television picture in the form of a composite hologram about one millimeter in diameter. Actually, three holograms are superimposed—for luminance, chroma and sound—and read out at three different angles while being illuminated by a single laser. In a technical paper on the system, Hitachi scientists said: "More than 2,000 holograms were arranged on a photoresist disc to give several minutes of play of motion pictures in color. Continuous rotation of the disc at 6 rpm gave color motion pictures and sound on a TV monitor."

It's not known whether Hitachi intends to further develop the system, but some industry engineers are encouraged by it. Zenith's Research Vice-President, Robert Adler, said it was an encouraging sign that "there are indeed other alternatives" in approaching the videodisc playing system. If the holographic approach sounds familiar, you may recall RCA's "HoloTape SelectaVision" system, unveiled in 1969 (and since shelved), that used holographic images on Mylar tape. Interestingly, RCA received a British patent in 1969 for a holographic videodisc recording process.

Hitachi's system can ac-

commodate 54,000 frames, or about 30 minutes playing time on a 12-inch record, and records can be reproduced by the standard stamping process.

Unlicensed CB's

The problem of unlicensed Citizens band radio operation was the subject of a recent conference between FCC staff members and two-way radio manufacturers. The FCC is swamped with license applications, with nearly a quarter-million pending, and it's falling farther behind each week as CB sales boom. It currently takes about eight weeks to get a license—which now is done after the equipment is purchased—and this encourages illegal operation. The FCC admits it can't possibly police the band and it has no idea how many illegal operators there are.

The Commission staff proposed a quick-license plan, and most of the manufacturers appeared to agree. This would empower CB dealers to issue temporary licenses at the time the equipment is sold, collect the four-dollar fee and forward the application for a permanent license to the FCC. Using this procedure, a buyer could operate his new CB radio legally as soon as he bought it.

Digital TV tuning

Random-access digital tuning seems to be the wave of the future in color TV. RCA has introduced a new 25-inch color chassis that features a remote hand-held "control center" with a calculator-like keyboard. Selecting a channel ("0" and "7" for Channel 7, or "3" and "5" for Channel 35) turns the set on and tunes it to the proper channel. In the bottom part of the screen, the correct time and channel number appear in white numerals that remain for a few seconds. The

silent ultrasonic remote control is also used to adjust color, tint and volume. When color is being adjusted, the time and channel number appear on the screen in red.

The RCA unit is similar in the way it addresses the set to the Magnavox's "STAR" system, which is now in its second year. The new version of STAR is available on some 19- as well as 25-inch sets and has two calculator-like tuning units—one remote and one affixed to the set.

At least five more digital TV-addressing systems are under development by other companies. Recently demonstrated was General Instrument's "Omega" system that uses up to four LSI's and like the RCA device can accommodate up to 100 channels making it suitable for tuning to special CATV as well as broadcast channels. The system employs a non-volatile memory developed by NCR. This memory will store information—fine tuning, last channel viewed, etc.—for more than 10 years, even if the set has been turned completely off or unplugged. Other digital tuning systems are under development by National Semiconductor in cooperation with Plessey as well as Motorola, Texas Instruments and Fairchild.

Filter tube

What is the next step in color pix tubes after negative matrix? It may be the filter tube. RCA is already in production of the "AccuFilter" tube, being used in its newly introduced 19- and 25-inch sets in both slot-mask and conventional phosphor-dot tubes. The AccuFilter tubes optically filter the appropriate red and blue phosphor dots or strips. RCA claims this system provides up to 25% better contrast in bright room light, with a brightness sacrifice of only about 5%. At a recent technical symposium, Zenith engineers described a somewhat similar

developmental tube called "Chroma-Filter," that uses red, green and blue filters, and has improved contrast but 30% less brightness than the current negative-matrix Chromacolor. A Zenith spokesman said the company is still working on the filter concept. RCA's new AccuFilter tube has been offered to television manufacturers, but it is a premium-priced tube, so it is expected to show up only in high-end models for some time.

TV, 2000 AD

Zenith's Dr. Adler, addressing engineers in Tokyo, gave some of his thoughts on the "possibilities" of television in the next 25 years. The current trend to simpler controls and automatic operation of receivers will continue to the point where color adjustment will be completely automatic. Elimination of ghosts will be a major challenge. The use of television retrace time, particularly in the vertical interval, suggests many possibilities for supplementary services. One is the transmission of alphanumeric data for onscreen display, as is being tested now in England.

Cable TV may be used to send literally millions of single-frame pictures that could be stored for display at home and in business. For many business uses, higher-resolution television pictures might be necessary. The long-sought flat-panel display will be realized in the laboratory before 1980, Dr. Adler said, with gas-discharge devices and electroluminescence the "leading candidates." With the arrival of such large-screen displays, higher-resolution pictures may be desirable and in city areas they may be transmitted, digitally encoded, either from single high-powered microwave antennas or from many lower-powered antennas.

by **DAVID LACHENBRUCH**
CONTRIBUTING EDITOR

New Mallory Ni-Cad Batteries. Rechargeable 1000 times.



Economical recharging —
Mallory BC-1 Charger draws only two watts.

Team these long-life nickel-cadmium cells with an automatic Mallory Charger, and you can recharge them 1000 times, or more.

You'll be sure of having fresh D, C, and AA batteries, while saving money, time and trouble. Mallory Rechargeable Nickel-Cadmium Batteries keep on coming back for more in electronic calculators, tape recorders, radios, cameras, toys, other battery-powered products.

Keep a spare set of Mallory Ni-Cads on hand,

and you'll never run out of battery power again. They recharge to full strength, two or four at a time. And unlike ordinary dry cells that lose voltage during discharge, Mallory Ni-Cads with a full charge maintain operating voltage during the entire work cycle. You get maximum power, continuously, for top product performance.

For the long run, Mallory Rechargeable Ni-Cads ... the 1000-time batteries. Get them now at your Mallory Distributor.

MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46206; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Fastening Devices

DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

Circle 4 on reader service card

www.americanradiohistory.com

Electronic heart mini-checker can be operated by patient

Two new devices—or two variations of one device—weighing only five ounces each, enable a heart patient to check his condition with his doctor immediately over the telephone. (Former devices required that electrodes be applied by a doctor or medical technician, and were often the size of a small typewriter.)

These *CardioBeeper* monitors owe their compactness and light weight to two special integrated circuits designed and developed by ITT Semiconductors, a division of ITT. The complete units are made by Survival Technology, Inc. of Bethesda, MD, and are marketed by Wyeth Laboratories of Philadelphia.

One device is for patients who have a heart condition that requires continued medical follow-up, the other for those who have an implanted heart pacer. Either *CardioBeeper* can transmit an electrocardiogram to the patient's doctor, or can beep signals direct to the patient's attention.



THE NEW MINIATURE HEART MONITOR is demonstrated by Jes Schiaikjer of ITT. The leads to the plastic armpit sensors are seen entering above the shirt button. The **BEEP** and **ECO** (electrocardiogram) contacts are at the bottom of the compact unit, the **TEST** contact at upper right and the lamps at upper left.

To use, a plastic sensor—attached to the monitor by wires—is placed in each armpit. There are no gels, pastes or straps—the two highly sensitive electrodes are inserted simply by unbuttoning the top two shirt buttons or opening the dress slightly.

To transmit an electrocardiogram, the patient phones his doctor and places the monitor against the telephone mouthpiece. The unit generates a variable

tone—frequency-modulated by the heart action—between 1 and 2 kHz that is readily transmitted over any telephone line. From it, the doctor can take an electrocardiogram or pacemaker function on the ECG recorder or scope. Regular checks can be made without the patient's having to visit the doctor's office, or on any occasion the patient may notice a condition that he feels may need attention.

In the other operating mode, an audio beep and one of two flashing lights show the patient his heart or pacemaker rate. One light flashes if the rate is higher than it should be—the other if it is slower. If indications are not normal, the patient follows instructions already supplied by the doctor.

The two modes are selected by touching one of two contacts. The device remains "on" only as long as contact is maintained. Thus the battery, which has a life of 50 hours, cannot be left on and run down. A third contact checks the battery, and is set to drop to zero when there is still 90 minutes of operating power left.

Microprocessors to save 40% of gas used in motor cars?

A tiny electronic device is achieving significant gasoline savings in tests being made by major automobile makers, RCA Chairman Robert Sarnoff told the 29th annual Business Conference of the Indiana University School of Business. Preliminary tests indicate that the device—a microprocessor—will be able to boost mileage up to 40 per cent.

The microprocessor is a miniature computer containing 6,000 transistors and other electronic devices in an area less than a 1/4" square. Installed in a car with appropriate link-ups, it can automatically adjust both choke and throttle for maximum starting efficiency, run the motor with the right fuel mixture for highest fuel savings, and shift gears at precisely the right time for optimum fuel efficiency.

Annual savings could amount to 500 million gallons of gasoline—equivalent to 27 million barrels of crude oil. "Working with the automotive industry as we are, the electronics industry should be able to mass-produce microprocessors by the millions at a cost of no more than \$100 per unit," Mr. Sarnoff said.

Voice-actuated two-way radios make blind skiing practical

Blind skiers are no novelty in this day when people with disabilities are taking part in almost all kinds of human endeavor. And the use of two-way radio in various types of sports is not new. But

Sammy Skobel, blind skier and founder of the American Blind Skiing Foundation, discovered that the standard two-way portable was not entirely suited to blind skiing.

The blind skier needs an assistant when skiing down a hill or when participating in a slalom competition where the skiers must travel a zigzag path around markers strung out in staggered fashion along the course. The guide is often in an unhappy situation, since he must yell at the top of his voice to be heard at all times. After fifteen or twenty minutes his voice starts to weaken, and he must rest for a minute or two.



BLIND SKIER SKOBEL AND GUIDE, with the Motorola voice-actuated two-way radios that will be used between skier and guide in a downhill practice run. With the radios strapped to their waists, the guide will wear a speaker/microphone and Sammy Skobel will wear a speaker on the shoulder of his parka.

Mr. Skobel consulted with Motorola Communications and Electronics for a solution for this sometimes serious problem. The result was a portable two-way radio specially adapted to the needs of the blind skier. The chief difference between it and the regular type is that it is voice-operated. A skier often needs both hands on his poles and cannot push a talk-listen button at will. With the voice-operated setup, all he or his guide have to do is to start talking in a normal voice and the transmitter goes into operation. A speaker worn on the shoulder of the parka near the ear completes the blind skier's radio.

"The radio gives me a feeling of freedom and security," says Skobel. "I can ski almost as if I were alone, but I know that I will be able to hear whatever instructions are necessary and I do not have to worry about becoming separated from my guide."

(continued on page 12)

Vaco.



"V" is for Vaco. And value, too. A good sign in times like these.

Take our new Super Case. A great value with great variety. 48 professional problem solving tools from screwdrivers and nutdrivers to pliers, wrenches, crimping tools, and more! All right at hand. And all unconditionally guaranteed.


You'll find the Super Case and all the other fine Vaco tools, along with problem solving aids, in our new free "Answer Book". From your tool distributor. Or write direct:

Vaco Products Co., 510 N. Dearborn St., Chicago, Illinois 60610.

And remember the sign of the "V". Value . . . variety . . . Vaco!



Circle 5 on reader service card

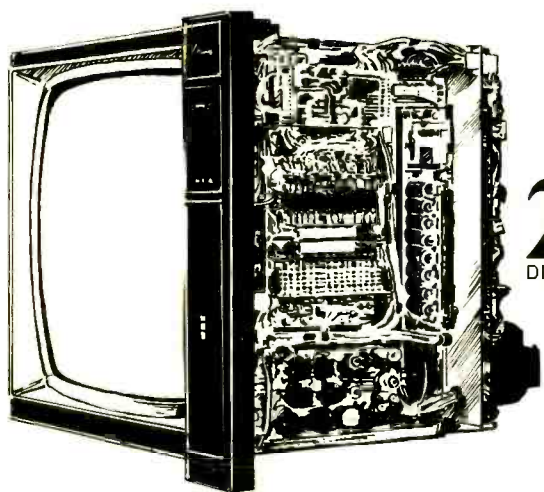

**You get the same
25" hobby-kit color
TV from three
different schools.**



**You get
this designed-
for-learning
25" color TV only
with NRI training.**

No other home-study school gives you a TV like the one you build with NRI's Master Course in Color TV/Audio servicing. Some schools give you three or four plug-in sub-assemblies off the production line to put together a commercial set. Others give you a hobby-kit bought from outside sources. And because neither type was originally designed to train people for TV servicing, lessons and experiments must be "retro-fitted" to the set as it comes.

That's why we went to the trouble to engineer our own, exclusive solid-state TV. It's the only way a student can (1) get the feel of typical commercial circuitry, (2) learn bench techniques while building a complete set from the "ground" up, (3) perform over 25 "in-set" experiments during construction, and (4) end up with a 25" diagonal solid-state color TV with console cabinet and all the modern features you'll find on sets you'll service. Nobody else can give you this combination of advantages because nobody else invested the time and money to design a set with learning in mind.



More know-how per dollar

That's what it all boils down to, the quality of training you get for the money you spend. In our 60-year history, more than a million students have come to NRI and we're fully approved for career study under the G.I. Bill. We must be teaching something right.

Some of those "right" things are bite-size lessons to ease understanding and speed learning . . . personal grading of all tests, with comments or explanations where needed . . . a full-time staff of engineer/instructors to help if you need it . . . plenty of "real-life" kits and experiments to give you hands-on training . . . and fully professional programs oriented to full- or part-time career needs.

NRI passes the savings on to you

You don't pay a big premium to get this unique TV as part of your training, because NRI engineering eliminates the cost of buying from an outside source. And we pay no salesman's commission. We enroll students by mail only. We pass the savings along to you in the form of low tuition fees, extras like a cabinet for the TV, a solid-state radio you learn on as you build, and actual instrument kits for servicing TVs . . . triggered sweep oscilloscope, integrated circuit TV pattern generator, and 3½ digit digital multimeter. You can pay hundreds of dollars more for a similar course and not get a nickel's worth more in training and equipment.

Widest choice of career opportunities

NRI offers not one, but five excellent TV/Audio servicing courses so you can tailor your training to your budget. Or, you can study other opportunity fields like Computer Electronics, Communications, Aircraft or Marine Electronics, Mobile Radio, and more. Free catalog describes them all, showing lesson plans, equipment and kits, and career opportunities. There's no obligation and no salesman will ever call, so send for your copy today. See for yourself why NRI experience, selection, and exclusives give you something no other school can.

If card is missing, write to:



NRI SCHOOLS

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016

Old thrown-out radios now sought by collectors

Take another look at that old Atwater Kent radio with dark mottled tubes standing in brass sockets on a flat stained "breadboard", that you never got around to clearing out of the attic. It may now be negotiable at \$200 or possibly much more. And if you paid \$300 for a Stromberg-Carlson *Treasure Chest* in the 1920's, you may be able to get your money back for it today.

The urge to collect antique radios, long an amateur vocation, has produced collectors who have become dealers, originally to dispose of their duplicates. (Like many other antique dealers, they often refuse to sell the best of their stock, and few models from the 1920's are on sale.)

A recent survey of New York City shows one, Fred Driskill at 2623 Broadway, who has a 1929 Gloritone he is willing to dispose of for \$150, as well as a few earlier ones he apparently has no intention of selling, and later jobs all the way down to \$50.

Unusual designs are featured by another collector-dealer, Alan Moss of 20 East 17th St., who sees prospective customers by appointment only. His prize piece is a peach-toned Sparton offered at \$450, but he has lesser pieces, including a Zenith with a sailboat and sea scene embroidered on the grille cloth for \$40.

Richard Uittla exhibits old radios at two shops, 244 East 60th St. and 304 East 62nd St. Some of his more modern selections sell for as little as \$28.

Not only do these collectors buy and sell old radios, some of them repair them as well. Fred Driskill specializes in restoring ancient sets, and keeps a large stock of components on hand for that purpose. Mr. Moss has his sets repaired by Daniel Schulman of Rudan TV Service and Parts, 344 Third Avenue. He is an old set designer who was responsible for many of the Emerson models.

The survey, which appeared in the *New York Times*, covered only one city but activity is heavy in many parts of the country, notably the West Coast where not only collectors but amateur museums abound.

1975 marks 15th anniversary of satellite weather prediction

TIROS, a Television InfraRed Observation Satellite, went into orbit April 1, 1960, with the hope that an overview of wide areas of the earth might be helpful in predicting weather conditions. Fifteen years and three generations of satellites later, meteorological procedures are al-

most entirely based on satellite observations.

Before satellites, a forecaster was unlikely to know the weather conditions in more than 20% of the Earth outside the continental United States. Two-day and three-day or longer forecasts were unknown and impractical, and knowledge of such phenomena as coastal fog, sea ice conditions and snow cover was sketchy at best.

The weather satellites gave scientists that knowledge, enabling them to improve the accuracy as well as the lead-time of their forecasts. They can now even watch the spawning of hurricanes and typhoons at sea often as long as two weeks before they hit land.

Following the success of TIROS I, nine other satellites followed in quick succession, then nine Environmental Survey Satellites (ESSA) and five ITOS (Improved TIROS) observational satellites. Today, the satellite is not only "one of the most successful space programs" to the scientist, but an essential part of the lay television viewer's evening weather broadcast.

New thousand-dollar car radio has everything, plus dictation

A new, totally electronic automobile sound system includes AM radio (four bands) FM (mono and stereo), plays pre-recorded stereo or mono cassettes, records stereo from the radio, and receives dictation. It is called by its manufacturer, Blaupunkt Car Division of Robert Bosch Corp., the first fully electronic car radio (there are no mechanical parts).



NEW BLAUPUNKT BERLIN ELECTRONIC's control unit—about as big as a pack of king-size cigarettes—is mounted on a flexible column and may be installed on the steering column or other spot convenient to the driver.

The *Berlin Electronic* will be offered by Blaupunkt as a "limited edition," at an installed price of approximately \$1,000. The installation includes four speakers at selected points in the car.

R-E

Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback
editor-in-chief and publisher

Larry Steckler, CET, editor

Robert F. Scott, W2PWG, CET,
technical editor

Arthur Kleiman, associate editor

Jack Darr, CET service editor

Leonard Feldman

contributing high-fidelity editor

David Lachenbruch, contributing editor

Karl Savon, semiconductor editor

Vincent P. Cicenja, production manager

Irene Feldman, production assistant

Harriet I. Matysko, circulation director

Arline R. Bailey, advertising coordinator

Cover photo courtesy Walter Herstatt

Cover design by Louis G. Rubsam

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, Sales Manager
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, IL 60646
(312) 792-3646

PACIFIC COAST/Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810

Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

The new Sansui LM Loudspeakers that set the AES Convention on its ears.



LM 330
CUT-A-WAY

At the Convention of the Audio Engineering Society in Los Angeles last May, Sansui demonstrated a new concept in loudspeaker design.

The reception from these experts—chief engineers of radio and TV stations, record producers, recording engineers and sales executives of audio companies—was even more sensational than we ourselves expected.

And these are the reasons:

Unlike conventional speakers, the LM design incorporates a multi-radiational tweeter device. High frequencies

instead of being lost through encapsulation, are diverted through three special exponential horns and recovered into sound energy that adds a breathtaking sense of ambience, and realism. The LM speakers also display extremely stable and well-defined stereo images. At the same

time, both the transient response and efficiency of the system are greatly increased. An extra large woofer assembly gives exceptionally strong bass response ordinarily available only in much larger and more expensive speakers.

Hear any of the 3 models available at your nearest Sansui franchised dealer. You never heard music so alive before.




Multi-radiational
tweeter

SANSUI ELECTRONICS CORP.

Woodside, New York 11377 • Gardena, California 90247

SANSUI ELECTRIC CO., LTD., Tokyo, Japan • SANSUI AUDIO EUROPE S.A.,
Antwerp, Belgium • ELECTRONIC DISTRIBUTORS (Canada) Vancouver 9, B.C.

Circle 6 on reader service card

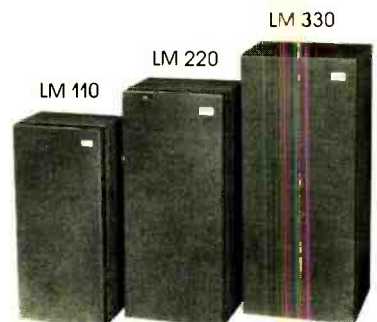

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS


... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

No. T-18—Fits wires up to 3/16" in diameter.

BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

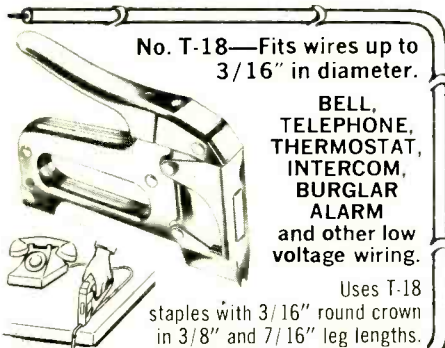Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.




No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE

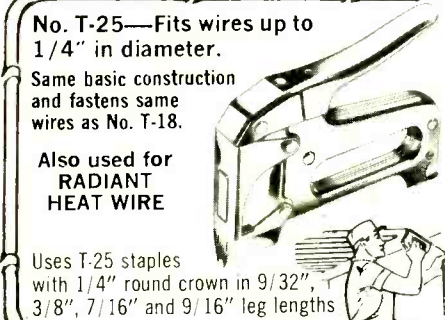Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.




NEW! Intermediate No. T-37—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

Also used for CATV and DRIVE RINGS in stringing wires.

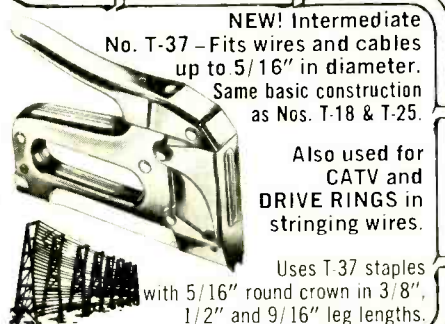Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.




No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT, COPPER TUBING or any non-metallic sheathed cable.

Also used as DRIVE RINGS in stringing wires.

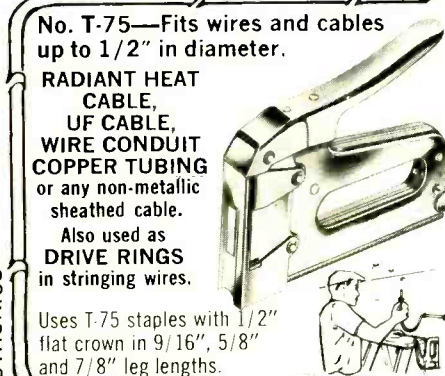Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.



ARROW FASTENER COMPANY, INC.

271 Mayhill Street, Saddle Brook, N. J. 07663

Circle 7 on reader service card

letters

COLOR TV CAMERA





I have finished reading the first two parts of the construction article on building a color TV camera that appeared in the July and August, 1975 issues of **Radio-Electronics**.

I already ordered the parts and am waiting for them to arrive. The assembly looks fairly easy and not to complicated. However, there is one area that is not

fully clear. This is the assembly of the vidicon, deflection yoke, lens and filter. The interior photos in the July issue shows the preamp assembly mounted over this assembly. Can you help?

Thanks for another interesting and useful project.

C. A. STROBEL
New York, N. Y.

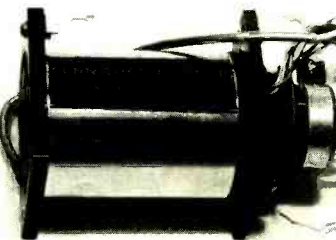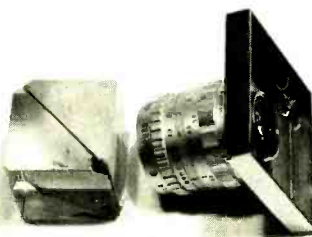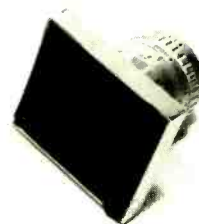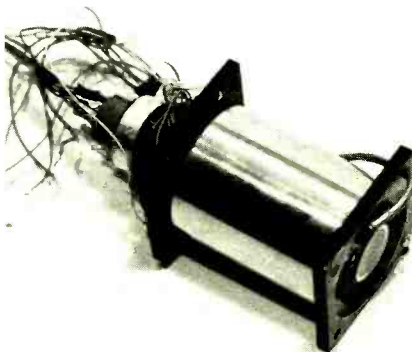


You are absolutely right! The interior photos do not show this assembly and there is nothing in the third and final part of this article that will help clarify this. So, we contacted Gary Davis and he was

kind enough to provide some photos. They appear above.

How about the rest of our readers. Drop us a line and let us know how you're making out with this project.—Editor

ANOTHER TV TYPEWRITER

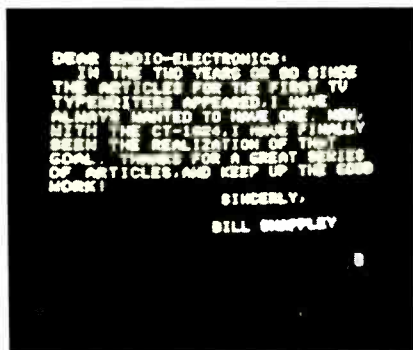

SWTPC

CD-4 DEMODULATOR



TRUE FOUR CHANNEL SOUND

Southwest Technical Products is proud to offer the most advanced CD-4 demodulator available. Our new CD-4 has characteristics superior to anything previously available thanks to the QSI-5022 integrated circuit used in the unit. This IC and the balance of the circuit was designed by Quadracast Systems Inc. under the direction of Mr. Lou Dorren. The QSI-5022 contains all the sub-system functions needed to demodulate a CD-4 disc, from the phono cartridge input to the output drive for the four power amplifiers. It may be used with either an RIAA equalized magnetic cartridge, or a semiconductor cartridge with flat equalization.

INEXPENSIVE

Now anyone can afford to add discrete true 4 channel sound to their system. You no longer need be satisfied with matrix techniques that produce acoustical enhancement, but not true 4 channel sound. The Southwest Technical Products CD-4 demodulator when added to your system will produce four channel sound from a CD-4 encoded disc that will equal, or surpass anything you can buy—no matter what the price.

EASY INSTALLATION

The SWTPC demodulator connects

between the cartridge and the volume-tone control portion of your system. If you did not want tone controls, actually all that would be needed in addition to our CD-4 demodulator would be volume controls for the front and rear amplifiers. The demodulator is self powered from any 115 Volt 60 Cycle line. When normal stereo discs are played on your system a muting system automatically turns off the rear channels. A manual override 2 or 4 channel selector switch is provided on the rear panel.

SIMPLE CONSTRUCTION

As shown in the photograph, the vast majority of the parts mount on the epoxy-fibreglass circuit board. Part numbers and package outlines printed on the top of the board make proper assembly quite simple. Anyone with a minimum of electronic experience should be able to assemble this project without any problems. A copy of the article describing the CD-4 demodulator and assembly instructions are supplied in the kit.

CD-4 Demodulator Kit.....\$50.00 ppd

CD-4 CARTRIDGE

For those who do not already own a CD-4 cartridge, we are offering the "Technics" EPC-451C semiconductor

strain-gauge cartridge at a special low price when purchased with our new CD-4 demodulator kit. This cartridge features a Shibata-type stylus and excellent response out to 50 kHz. This eliminates any chance of "carrier drop-out", or "carrier crosstalk" which result in abnormal noise or distorted sound. The EPC-451C produces a high output (about 30 times that of an average magnetic cartridge) and does not pick up hum from magnetic, or electrostatic fields. Easily replaced stylus.

EPC-451C CD-4 Cartridge.....\$25.00 ppd

TEST RECORD

Lou Dorren has recorded a special test record for Southwest Technical Products Corp. that will allow you to properly adjust your CD-4 demodulator for the best possible sound. This special test and demonstration record is yours for only \$5.00 when purchased with the CD-4 demodulator kit.

CD-4 Test Record.....\$5.00 ppd

WANT MORE INFORMATION?

Send the coupon below and \$0.50 and we will send you by return mail a copy of the article describing our new CD-4 kit along with our catalog of other kit projects.



CD-4 DEMODULATOR

MAIL THIS COUPON TODAY

- ☐ Enclosed is \$ _____ or BAC # _____
☐ or Master Charge # _____ Bank # _____ Expire Date _____
☐ CD-4 Demodulator Kit ☐ Cartridge ☐ Test Record

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

☐ \$0.50 Enclosed for catalog & CD-4 Data

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 782114

Circle 8 on reader service card

QS Matrix Simplified

This approach to 4-channel reproduction has gained acceptance in recent years.

by HIDEO KITAHARA*

WHEN WE ARE SEATED IN A CONCERT HALL listening to a musical performance, we are hearing not only the sounds that reach us directly from the stage but also the sounds

that are reflected by the walls, ceiling and innumerable other objects inside the hall. These reflected sounds arrive at our ears from many directions and with infinitely different time lags. Actually, our ears usually receive much more reflected sound

than direct sounds, and it is these 'indirect' sounds that shape for the most part the peculiar tonal quality of each musical instrument as determined by its dynamic range and other important criteria.

It is generally acknowledged that the conventional monophonic or stereophonic sound reproduction system is not fully able to pick up, store, transmit and reproduce the totality of this important live musical sound field information for subsequent enjoyment at home. Thus the need for a more effective system, possibly using more than two channels of signal transmission, has over the years come to be recognized. The 4-channel or quadriphonic system as we know it today is an answer to this need.

Obviously, whether it uses two or three or four transmission channels, a 4-channel system must resort to using some of the inter-relationships of its transmission channels to contain the infinite number of direct and indirect sounds. And this will be true regardless of the number of transmission channels used, so long as it has a limited number of channels.

These inter-relationships among the transmission channels are created by a matrix, and the 4-channel systems available today are characterized by their use of different matrices. And herein lies the cause of the confusion plaguing many people in the audio and musical industries of the world. All too often, the problem of how to secure an appropriate transmission medium—be it a "discrete" 4-channel disc or a matrixed or "discrete" FM 4-channel broadcast—is debated on the same level as the more fundamental issue of how best to distribute the original musical signals to the available number of transmission channels, be it two, three or four.

It is my opinion that, so long as the infinitely complex original sound field information must be conveyed to the listener's home via a limited number of transmission channels, there should be a solution based on a single theory of signal conversion, one that is compatible for the different number of transmission channels. There indeed is such a solution, and it is the purpose of this paper to examine it. I feel that the problem of how to secure the appropriate transmission medium for any given purpose is quite another matter, and should be discussed from a different standpoint. Also, I have been encouraged by the growing recognition of signal conversion theories as a new, separate field of study in the recent several years, both in Japan and abroad.

The QS 4-channel system gives us signal formats that are appropriate for two, three and four transmission channels in trans-

(continued on page 20)

INTERNATIONAL
FM 2400CH

FREQUENCY METER for testing mobile transmitters and receivers

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended MHz. The range covers 25 to 1000 frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^{\circ}$ to $+104^{\circ}\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^{\circ}$ to $+125^{\circ}$ (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only) \$595.00
RF crystals (with temperature correction) 24.00 ea.
RF crystals (less temperature correction) 18.00 ea.
IF crystals catalog price

Write for catalog!



Circle 9 on reader service card

*Staff Engineer
Sansui Electric Co., Ltd., Japan

change tips... change temperatures



Weller[®] CONTROLLED OUTPUT SOLDERING STATION

...has interchangeable brains in the form of a ferromagnetic sensor mounted in the tip that controls iron temperature through unique "closed-loop" circuit. Change tips...change temperatures. A Weller exclusive! It's that simple. 600, 700, or 800° F...your choice. Switching tips is always easy because Weller's exclusive triple-plated construction prevents oxidation and "freezing"...assures quick interchangeability. And nobody offers as many tip options. Over 50 combinations of configuration, reach, and temperature, one just right for optimum soldering action and maximum tip life on any job.

UL-listed and OSHA-compliant, Weller's Model WTCP-L has its own built-in transformer...24 volt output for operator safety. Non-sinking holder supports and shields the comfort-grip, pencil iron when not in use. Grounded tip guards against static-discharge damage to sensitive workpiece circuitry. Base contains handy, tip-cleaning sponge and receptacle plus off/on switch and red indicator light. And non-burnable silicone power cord prevents annoying self-damage.

Weller's WTCP-L Station has all the functional features you need for today's sophisticated soldering...at the most attractive price. No fancy extras that only add to cost. Also available as WTCP-2 for low-temperature service. See it...*get it*...at your local distributor. Ask, too, about DS-100 de-soldering units. Or request technical information.



Weller-Xcelite Electronics Division
The Cooper Group

P.O. BOX 728 • APEX, NORTH CAROLINA 27502

Circle 7 on reader service card



The latest improvement in picture tubes.

Our labels.



If you can say what you want, you've got it.
That's our simple new labeling system.
The labels tell you what's inside, in simple,
everyday language.
We've kept our standard color coding: red
for all-new; blue for new screen and gun;
green for new gun.

And inside, there's the same great tubes
you've always had from Sylvania.
Trust Sylvania to make life easier. See your
Sylvania distributor.

We're helping you make it.

GTE SYLVANIA



The new B.I.C. 940. It eliminates the big disadvantage common to all high-performance turntables.

High-performance turntables cost a bundle.

The B.I.C. 940 doesn't. And yet at about \$110...

It's a belt-drive instrument with a full 12" platter. Its low-mass tone arm tracks magnificently. It has the stylus force and anti-skate adjustments that are essential for fine-tuning an arm. It has a low-speed (300 rpm), 24-pole motor which is inherently quieter than motors found in some turntables that cost twice as much.

B.I.C.

And when you look over its wow, flutter, and rumble numbers, the standards against which experts measure all turntables, the 940 is right up there with the costliest equipment you can buy.

The B.I.C. is also versatile. It's a multiple-play manual turntable...which means you can operate it in 3-modes: single-play manual, single-play automatic, or when the occasion arises, as a multiple-play turntable that will handle as many as 6 records.

There are shinier turntables made.


There are turntables with more adjustment features.

But for pure, clean, accurate reproduction of what is on your records, this is the optimum way to spend your turntable dollars.

Ask your audio dealer about the B.I.C. 940 and the 2-year "bee-eye-cee" warranty. Or write to British Industries, Westbury, N.Y. 11590.

FREE!

the 1976 Lafayette Electronics Catalog

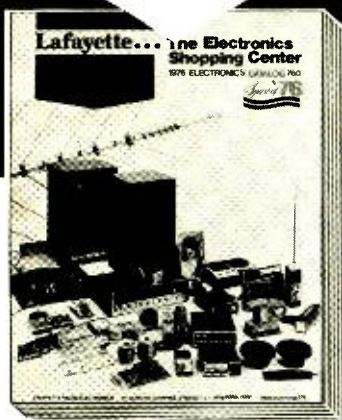

**The most comprehensive
consumer electronics
catalog available!**

**Features Lafayette and Criterion
Products Plus Major Brands**

Stereo/Quad Hi-Fi Components • Tape Equipment • Car Stereo • CB and Communications Gear • Police/Public Service Scanners • TV/FM & Communication Antennas • PA and Test Equipment • Tools • Electronic Calculators and Watches • Portable Radios • Security Systems • PLUS an exciting new Parts Line, Tubes, Batteries, Hardware and More!

- Stores Coast-to-Coast
- BankAmericard and Master Charge

Lafayette

the electronics shopping center

Mail Coupon
Today!

FREE

Dept. 17105
Lafayette Radio Electronics
111 Jericho Turnpike
Syosset, L.I., N.Y. 11791

Send me your FREE 1976 Catalog.

Name _____ Apt. _____

Street _____

City _____ State _____

Zip

Send a 1976 Catalog to my friend

Name _____ Apt. _____

Street _____

City _____ State _____

Zip

Circle 11 on reader service card

QS MATRIX

(continued from page 16)

mitting and reproducing the original sound field information. It is based on a single theory of signal conversion, and is compatible for the different number of transmission channels. When used in a 4-2-4 system with two transmission channels, the QS system provides reproduction results that closely simulate the original sound field and that are not inferior in terms of tonal quality, physical characteristics or in any other high fidelity standards. This is largely made possible by the use of a multi-directional encoding technique and a QS variomatrix decoding technique. Let's look at how the QS system encodes 4-channel sound for 2-channel transmission.

The advent of 4-channel sound has brought a number of benefits to the art of reproducing music. Most of them result from the 4-channel systems capability of storing and transmitting a greater amount of sound information than the 2-channel system. This "4-channel information" can be transmitted by either four separate transmission channels through the use of a special high-frequency signal called a carrier, or by transforming the sound information into amplitude and phase relationships and sending these over the two transmission channels currently used. The former method is best exemplified by a so-called carrier ("discrete") disc (CD-4), while the latter is implemented by a so-called matrix system.

In stereo sound reproduction, sound images are located in the L (left) and R (right) speakers, and between them. Sound images located between the two speakers are obtained by reproducing a given sound from both speakers at a certain ratio of amplitudes or sound levels. For instance, a signal of $L = 1$, $R = 0.1$ will appear as a sound image located slightly inside (to the right of) of the L speaker, while a signal of $L = 1$, $R = 1$ will appear at the exact center of the distance between the two speakers. However, a signal of $L = 1$ and $R = -0.1$ will not seem to fall between the two speakers but will appear to be located slightly outside (to the left) of the L speaker (see Fig. 1). Such a signal is called a reverse-phase signal, and can be easily created on the transmission end. And just as there are infinitely different stereo (in-phase) signals, there can be infinitely different reverse-phase signals, with the two kinds

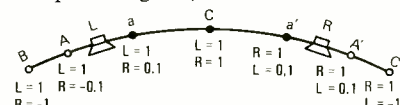


FIG. 1—LOCATION of sound images in stereo reproduction.

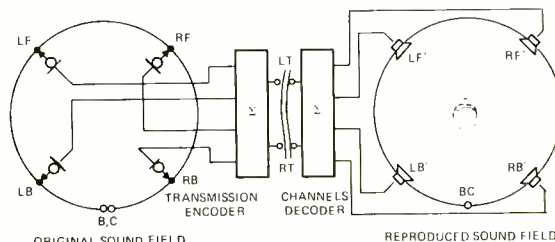


FIG. 2—TRANSMISSION of sound signals by a matrix 4-channel system requires an encoder and decoder.

each possessing different characteristics.

"Encoding" is when stereo (in-phase) signals and reverse-phase signals are combined into two composite signals (hereafter referred to as an LT signal and an RT signal) in such a manner that they can be later reproduced out of four speakers. "Decoding" means unscrambling the combined signals into four signals on the reproduction end. These processes are described below.

Encoding for 4-channel

Basically, to transmit a sound field via two transmission channels, any matrix system distributes a front signal to LT and RT (Left Total and Right Total) in phase, and a rear signal to LT and RT in reverse-phase. Also, as in stereo recording, if a signal is located more to the left (either front or back), it will be distributed in a greater proportion to LT; if it is located more to the right, it will be distributed in a greater proportion to RT.

One important consideration to remember in encoding sound field information is that no part of it should be cancelled or altered by the encoding process.

To elaborate on this point, let's consider a sound field to be a circle and divide it into four equal parts. We now designate the four points dividing the circle (see Fig. 2) as LF (which can be reproduced by a signal of $L = 1$, $R = 0.414$), RF ($L = 0.414$, $R = 1$), LB ($L = 1$, $R = -0.414$) and RB ($L = -0.414$, $R = 1$). This will certainly mean that a front signal is distributed to LT and RT in phase, and that a rear signal is distributed to LT and RT in reverse-phase. However, it also means that if there is a sound source at the rear center (CB), i.e., if signals of identical levels enter LB and RB simultaneously, $LT = 1 - 0.414 = 0.586$ and $RT = 1 - 0.414 = 0.586$, so that the LT and RT signals find themselves in phase, allowing a sound image to be located at the front center (CF) instead of the rear center (CB).

The reason for this is that this technique takes the fact that stereo reproduction uses in-phase signals to create a line of sound images between the L and R speakers, then simply adds reverse-phase signals to stretch that line outside of the two speakers, letting four speakers connected by this stretched line form a circle. The junction points of this line (points B and C in Fig. 2) do not yet meet each other completely, so that the circle is not yet perfect. This is the reason for the undesirable phenomenon described above. In other words, only the information existing over the three-quarters of the circle, excluding the portion between LB and RB, can be transmitted under this condition.

(continued on page 22)

When it comes to a fast-changing market, RCA can keep you ahead of it.

- TEST EQUIPMENT & ACCESSORIES
- SK REPLACEMENT SEMICONDUCTORS
- CAR RADIOS & TAPE PLAYERS
- COLOR & BLACK-AND-WHITE PICTURE TUBES
- RECEIVING TUBES
- ANTENNA HARDWARE
- SCANNERS
- EXACT REPLACEMENT PARTS
- FLAMEPROOF RESISTORS
- STEREO SPEAKER SYSTEMS
- ANTENNA ROTATORS
- BATTERIES
- INDOOR & OUTDOOR ANTENNAS
- AND MORE

Today, your RCA distributor is ready for your every electronics supply need. Because all of these RCA products now come from one RCA division.

This concentration of products is certain to simplify your ordering and stocking requirements. We figure that anything we do to contribute to your efficiency and profits helps us, too. So, we're here to work with you. And we're ready now!

For full information, see your RCA distributor. Or contact RCA Distributor and Special Products Division, Bldg. 206-2, Cherry Hill Offices, Camden, New Jersey 08101.

RCA Distributor and
Special Products Division

GET SOMETHING EXTRA from CHEMTRONICS



FREE!
POPULAR 2 SIDED PROFESSIONAL
ALIGNMENT TOOL WITH THESE
CHEMTRONICS
PRODUCTS



AVAILABLE
FROM YOUR PARTICIPATING
**CHEMTRONICS
DISTRIBUTOR**

QS MATRIX

(continued from page 20)

This is the Scheiber system, and it does not completely fulfill the essential objective of the 4-channel sound reproduction system, which is to faithfully reproduce a live sound field.

However, the unconnected points can be eliminated by using a phase shift technique to realize a complete 4-channel encoding system. What this phase shift means is that, as a signal moves away from the front center point (CF) in the original sound field, the phases of the LT and RT signals are simultaneously changed in proportion to the distance the signal has moved from the CF.

In this manner the reverse-phase relationship (a phase difference of 180°) which otherwise occurs at the junction points of the circle (CB) is scattered over the entire circle to create a continuous circle. Since the LT and RT signals are simultaneously phase-shifted, any front signal which is distributed to LT and RT in phase will remain in phase, while any rear signal which is distributed to LT and RT in reverse phase will remain reverse-phased.

The phase shift as described above will allow the points B and C of Fig. 2 to join each other completely, providing a CB signal and creating a continuous circle.

This technique of phase-shifting the LT and RT signals simultaneously in proportion to the level difference between the two composite signals is an essential and important feature of the QS system. Patents have been approved on this feature of QS in several countries around the world. And with this technique, the QS system is able to encode a signal located anywhere on a circle as well as anywhere inside it.

Decoding a matrix signal

On the playback end, the location of a particular signal, along the left-right axis of the original sound field can be determined from the level difference between the LT and RT signals. Similarly, the location of a particular original signal along the front-back axis can be determined from the phase difference between the two composite signals. In other words, the exact location of a signal is reproduced accurately by detecting the level and phase differences of the encoded signals. For instance, a signal encoded as $LT = 1$, $RT = 0.414$ will be located in the front half of the sound field because there is a zero phase difference between LT-RT (i.e., they are in phase). Such an encoded signal will be reproduced at a particular point (LF) on the left-hand side quarter arc section of the circle because the LT-RT level difference is $LT : RT = 1 : 0.414$.

An actual QS decoder reproduces such a signal at its exact location in the original sound field by making calculations that are in precise contrast to those performed by the encoder.

More specifically, assuming a playback set-up (right hand side of Fig. 2) where four speakers are placed to form a square, the QS decoder reproduces the four speaker positions by adding or subtracting

(continued on page 24)

AUTO-MAGIC? GLIDE-PATH? QUATRAVOX?



Model
Shown: STA-225

399⁹⁵

The Same Price it Was in July, '74

Super Value!
Save on this Complete
STA-225 System



Save
60⁸⁰

Reg. 659.80

Only
\$599

Realistic STA-225 Receiver • Two Optimus-1B
Walnut Veneer Speakers • LAB-34 Changer,
Base, and \$17.95-Value Cartridge

How Come Only Realistic[®] Has These Features?

A demonstration of these Realistic STA-225 features at any Radio Shack store will make you wonder when — if ever — the other "famous" brands will catch up. Maybe we just love audio-philosophers a little better? Auto-Magic gives you precision FMA fine-tuning — automatically. Glide-Path slide controls let you **see** and feel volume and balance settings. And Quatravox lets you enjoy the added realism of synthesized 4-channel sound simply by adding a 2nd speaker pair. Power output is 50 watts per channel, minimum RMS at 8 ohms from 20-20,000 Hz, with no more than 0.5% total harmonic distortion. U.L. listed. #31-2058. There's only one place you can find it... Radio Shack!



Use your
credit card at
participating stores

Radio Shack[®]

A TANDY CORPORATION COMPANY
OVER 3500 STORES • 50 STATES • 7 COUNTRIES



FREE! 1976 CATALOG

See What's Really New in Electronics!
164 Pages • Beautiful Color • Over 2000 Items

Mail to Radio Shack, P.O. Box 1052, Ft. Worth, TX 76101
(Please print)

Name _____

Apt. # _____

Street _____

City _____

State _____

Zip _____

Retail prices may vary at individual stores and dealers

Circle 13 on reader service card

OCTOBER 1975

23

LEADER 5" Quality Scopes Cost Less!

While the Others Keep Raising Prices, Leader Fights Inflation to Save You Money



LBO-506

5" Dual Trace/Dual Channel Automatic Triggered Scope

It's all automatic — hztl sweep; vert'l input & trigger (TV-V, TV-H). Features sep./simul. sweep mode; X5 mag; X-Y display; direct RF input; 10MHz b'width; and 10mV to 20 Vp-pcm vert'l sens. in 11 calib. steps. Probes, leads, adapters included.

A Trend Setter! \$569.95



LBO-501

5" Triggered Scope w/Calibrated Input & Time Base

A real pro performer; with ver't input calibrated in V/cm for accuracy; hztl deflection is time calibrated. Has 10MHz b'width; 0.2μs/cm to 0.2sec/cm sweep, free running or automatic. Offers 20mV to 10Vp-p/cm vert. sensitivity. Probe, leads and adapter included.

SAVE \$60.00 NOW \$399.95




LBO-502

5" Triggered Scope w/Graded Scale

Ideal for most every electronic application: with easy pushbutton operation; 1-2-5 graded scale readings & 15 MHz b'width. Has auto and trig sweep, 17 steps calib., X5 mag; and 10mV to 20mVp-p/cm vert. sensitivity. Complete with probe, leads and adapter.

SAVE \$80.00 NOW \$449.95

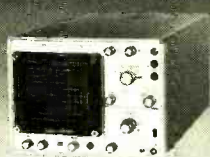

LBO-511

5" Solid State General Service Scope

Features recurrent sweep w/automatic sync and calib ver't input — has 140° phase control; and TV-V & TV-H w/4 sweep ranges to 100KHz. DC coupling and push-pull amps provide distortion-free stability across the 10MHz b'width. Complete with probe, leads and adapter.

SAVE \$50.00 NOW \$299.95

LEADER "Put Us To The Test"

INSTRUMENTS CORP. 151 Dupont Street Plainview, N.Y. 11803 (516) 822-9300

Circle 14 on reader service card

QS MATRIX

(continued from page 22)

the LT and RT signals and reversing the calculations performed during the encoding process. This will mean that $LF' = LT + 0.414RT$, $LB' = LT - 0.414RT$, $RF' = RT + 0.414LT$, $RB' = RT - 0.414LT$. Once these are fixed, any signal can be reproduced at the position it occupied in the original sound field.

There is still one important deficiency with the reproduced signal, however. While the reproduced signal has the same level, phase and directional characteristics as the original sound signal, its directionality is still not distinct enough because it is obscured by the crosstalk.

The QS decoder handles this problem by performing more advanced QS variomatrix calculations that take advantage of the level and phase differences between LT-RT to eliminate the crosstalk altogether, locating a signal with the same sharp sense of directionality as it was located in the original sound field.

QS encoding

QS encoding provides for the reproduction of 4-channel signals with excellent channel separation. QS-encoding also creates signals that are compatible for 2-channel and monophonic playback. Furthermore, QS-encoding can be expanded and developed, if necessary, to incorporate three or four transmission channels in a 4-3-4 or 4-4-4 system.

When played in stereo, QS-encoded 4-channel records create a broader sense of perspective than conventional stereo records, and for this reason AudioLab in Japan and several other record manufacturers are using the QS encoder even in the production of their stereo records.

The reason for this expanded stereo perspective is because, as explained earlier, signals generated in the front half of the original sound field are distributed to LT and RT in phase, or in intermediate phase relationships approaching in-phase. This is the same as traditional stereo recording, and such signals are reproduced as sound images between the L and R speakers. At the same time, signals generated in the rear half of the original sound field are distributed to the L and R speakers in reverse phase or in intermediate phase relationships approaching reverse phase, so that they will be reproduced outside of the left and right speakers (i.e., to the left of the left speaker and to the right of the right speaker). The total effect of this is that there is now a broader sense of stereo perspective offering a particularly good balance of distinctively located sound images and ambience (see Fig. 3). Fig. 4 shows a diagram similar to Fig. 3, but for SQ decoding (CBS). Fig. 5 shows decoded CD-4 signal.

A signal that was panned in a clockwise circle from the rear center position in the original sound field will also be panned in stereo playback, starting on the outside (to the left) of the L speaker, passing through the front center and moving on to the outside (to the right) of the R speaker. This demonstrates the fact that a QS-encoded signal accurately corresponds to the

(continued on page 30)

TeleMatic

MJ-195

MASTER TEST RIG FOR TUBE AND SOLID STATE SERVICING



\$149.95

less 19" picture tube

- 30 KV CAPACITY
- METAL CABINET
- SPEAKER BUILT IN

- HIGH VOLTAGE METER
- STATIC CONVERGENCE
- FRONT PANEL CONNECTIONS

TeleMatic

2245 Pitkin Ave., Brooklyn, N.Y. 11207

FREE! Adaptor Quick Reference Chart

Circle 27 on reader service card

make it at your place.

Take a little time and put a Dynakit together. The savings will be music to your ears. It's easy. Preassembled fully tested circuit boards guarantee that great Dynaco performance. It's fun. Invite a friend to pass the tools and you'll find sharing makes good sense . . . and good music. And if you're too preoccupied, we'll do the work and let you relax. Either way, the price is right, and the sound is **INandCREDIBLE.**

*Free button? Write Cindy
at Box 88, Blackwood,
New Jersey, 08012 for yours
and Dynaco literature, too.*

dynaco
dynakit



Circle 04 on reader service card


Your NEW Heathkit Catalog is ready



waiting to serve you with
more values, more new
kits, than ever before



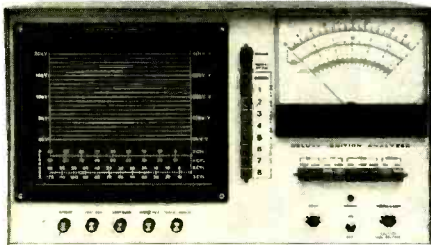Now over 400 do-it-yourself electronic kits for home, hobby, and industry. All designed to give you more for your money...more value, more performance, more satisfaction. All designed so even beginners can build them. Send for your free catalog today.



New Professional 12" Ignition Scope — Kit or Wired

Does more than others for \$1000 less. Spots tough ignition problems on all types of systems in 3, 4, 6, 8 cyl. or 2-rotor Wankel engines; sets itself automatically for no. of cylinders. Big 12" screen has 2 calibrated primary and secondary voltage grids plus dwell angle indications. Special circuit maintains trace length regardless of RPM. Displays "superimposed" patterns, single cyl. pattern, primary or secondary "parade" patterns. "Power balance" feature even helps spot bad valves or rings. 8" meter with tach & DCV ranges. Optional low cost timing light, alternator adaptor & cart. Kit CO-2500 \$379.95; Assembled WO-2500 \$695.



New Automobile Intrusion Alarm Kit

Total Protection. Alarm mounts anywhere; connects to switches on doors, hood, & trunk. Underdash switch arms or disables unit. Adjustable delay time allows you to quickly enter or leave car without triggering alarm, but opening trunk or hood triggers alarm instantly. Alarm sounds car horn in repeated 2-minute cycles. Kit GD-1157 Alarm \$24.95; Kit GDA-1157-1 Siren (gives yelping sound louder than car horn) \$19.95.



New Programmable Digital Stop Watch Kit

Another "first" from Heath. 2 IC counters, 8 digits & 7 functions with typical accuracy to $\pm 0.003\%$ and resolution to 1/100th of a second. Function 1 (Start/Stop Elapsed) times individual events while also counting total. Function 2 (Sequential) times each part of event & displays each separately while timing overall event. Function 3 (Total Activity) accumulates total elapsed time of a series, excluding time between events. Function 4 (Split) displays cumulative time to each "split" point while continuing overall event time. Function 5 (Start/Stop Activity) shows separate time for each event & totals all individual times. Function 6 (Programmed Upcount) counts up to "learned" time. Function 7 (Programmed Downcount) counts down from "learned" time. Stop watch can "learn" time from other functions or be programmed up to 9 hours, 59 minutes, 59 seconds. Has jacks for external triggering devices and alarms. Includes nickel-cadmium batteries & charger. Kit GB-1201, \$99.95.



New Digital Wind Speed & Direction Indicator Kit

Unique. Two big, bright digits show wind speed to 99 mph. As you build, choose 2 readout modes: miles, knots, or kilometers per hour; front panel light shows mode in use. 8 incandescent lights show wind direction at principal compass points; adjacent lighted bulbs give 16 point resolution. Remote transmitter boom clamps to TV mast. Styled in black plastic to match Heathkit GC-1005 Digital Clock and ID-1390A Digital Thermometer. Kit ID-1590, \$69.95 less cable.


New — Two-Way Telephone Amplifier Kits

Now, hands-free telephone use with amplified "talk" and amplified "listen" — with or without dialer. Talk & listen from 10' away. Voice-actuated circuitry switches from talk to listen without feedback or clipped words. Listen button lets you monitor line without built-in microphone activated. Dialer model may be used with or without regular telephone. Includes 4-prong jack & phone coupler connector. Battery powered. Kit GD-1112 (no dial) \$49.95; Kit GD-1162 (w. dial) \$69.95.

New Public Address Sound System Kits

Outperforms those costing twice as much. **TA-1620 Control/Amp.** takes 6 low impedance mikes, each with level, bass & treble controls & reverb sw. Has VU meter, 4 switched response "shaper" circuits, exclusive bass filter, 100 rms watts drives 2 speaker columns. **TA-1625 Booster Amp.** 100 rms watts to drive 2 extra speaker columns. **TS-1630 Speaker Column.** Six 8" full-range drivers response tailored for voice; 60 watt rms rating; 12 ohm impedance. Kit TA-1620 \$449.95; Kit TA-1625 \$179.95; Kit TS-1630 \$199.95.



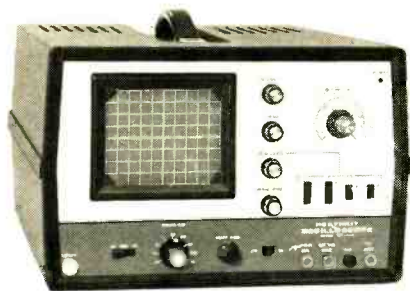

New DC-5 MHz Triggered Scope — Kit or Wired

Best scope value today. Wide bandwidth, 20 mV sensitivity, & stable triggering — ideal for TV, audio and RF servicing. Easy-to-use controls. Trigger circuit (not recurrent type) has normal & automatic modes, switched AC & DC coupling, & front panel external inputs (special TV position allows low freqs. to pass while rejecting high freqs. for easy triggering on complex TV signal. 7 calibrated time bases from 200 ms to 0.2 μ s/cm. 20 mV/cm vertical sensitivity with 9 calibrated attenuator positions up to 10 v/cm, plus variable control. 5" round flat-face CRT (8 x 10 cm graticle). Lightweight, durable blue plastic cabinet with white panel. Kit IO-4540 \$179.95; Assembled SO-4540 \$275.



New — Lowest cost Triggered 5 MHz Scope Kit

The scope everyone can afford, and it has the performance you need. DC-5 MHz band width, 100 mV vertical sensitivity with X1, X10 & X100 attenuation, AC or DC. Automatic, positive locking horizontal sweep continuously adjustable from 20 ms to 200 ns/cm. Stable displays due to zener regulated amplifiers and sweep. 5" round flat-face CRT with 8 x 10 cm graticle. Simplified controls and switches make it easy to use. Lightweight, durable blue plastic cabinet; white panel. It's the best instrument buy in years. Kit IO-4560 \$119.95

**New catalogs
and kits
also available at**

**HEATHKIT ELECTRONIC CENTERS —
Units of Schlumberger Products Corporation
Retail prices slightly higher.**

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.



New Variable Isolated AC Supply

What every tech & hobbyist needs. The IP-5220 isolates equipment under test from the AC power line and provides an AC output which is variable from zero to 140 volts. Great for locating circuit faults caused by high or low voltage or testing equipment with unknown power requirements. Power rating is 360 volt-amperes, continuous. Variable output current rating: 3A. max. Direct output current rating: 10A. Two meters: voltmeter 0-150 VAC; ammeter: 0-1 & 0-3A. Ammeter and variable output socket are fused. Kit IP-5220, \$109.95



New Oscilloscope Calibrator Kit

For time calibration, it generates a 0.5 second to 1 μ sec square wave in 1-2-5 sequence accurate to 0.01% with 200 mV peak ($\leq 3\%$ overshoot) and ≤ 4 ns rise time. Voltage calibration ranges are 1 mV to 100 v. in decade sequence, accuracy within 2%, DC plus variable 2 Hz to 10 kHz in 1-2-5 sequence (internal std. accuracy within 1%). Use it to calibrate scopes up to 35 MHz and voltmeters; it's also a fast rise time squarewave generator and good bench freq. standard. Kit IG-4505 \$44.95



New 21" (diag.) Digital Design Color TV Kit

All the advanced technology of digital circuitry in a smaller screen size. **Electronic touch-to-tune** varactor front end (nothing mechanical to wear out) with computer-like programming board for up to 16 channels. **On-screen channel numbers**, adjustable in brightness, position, and duration. **On-screen digital clock**; a low-cost option; programmable in 12 or 24 hour format, displays 4 or 6 digits. **Fixed-filter IF**, a Heath exclusive that assures better pictures longer, never needs instrument alignment. **100% solid state** — more ICs than any other — sophisticated circuitry that results in less interference, better color tints, improved sensitivity, greater noise immunity, improved picture definition. **Black negative matrix 21V picture tube** for brighter, sharper pictures. **Total touch-tune remote control** — low cost option that operates all functions, including recall of time & channel.

Easier to build & service — thanks to extensive modular design and built-in servicing tools including digital-design dot generator, front access slide-out Service Drawer, new picture centering and pin-cushioning correction circuits, and Test Meter. **Enjoy the best in TV design** — now in smaller size at lower cost. Kit GR-2050 \$599.95. Kit GRA-2000-6, remote control, \$89.95. Kit GRA-2000-1, digital clock accessory, \$29.95. Contemporary or Mediterranean cabinets from \$119.95.

**Use coupon below to order your favorite new kit
or to get your FREE new Heathkit Catalog.**

HEATH Schlumberger	Heath Company Dept. 20-10 Benton Harbor, MI 49022
<input type="checkbox"/> Please send my free 1975 Heathkit Catalog. <input type="checkbox"/> Enclosed is \$_____ plus shipping. Please send model(s)_____	
NAME _____	
ADDRESS _____	
CITY _____	STATE _____ ZIP _____
<small>PRICES ARE FACTORY MAIL ORDER. FOB PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>	
CL-571A	

Circle 100 on reader service card

A PRECISION WAVEFORM GENERATOR AT A PRICE YOU CAN AFFORD.



The Hickok Model 270 Function Generator gives you a lot more waveform generating capability than you'd expect for its price.

- Puts stable, calibrated, high quality sine, square and triangle waveforms from 1 Hz to 500 kHz at your fingertips.
- With external connections you can produce logic pulses, sweeps and ramps, AM and FM outputs, phase and frequency shift keying signals, tone bursts and more.
- Its an audio generator and much more.

Before you buy another function generator, check out the Hickok Model 270. Ask your Hickok distributor for full details or write us for our 4-page technical brochure.

\$166⁰⁰

HICKOK
the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

Circle 16 on reader service card

QS MATRIX

(continued from page 24)

original sound field. A signal generated on the left side of the original sound field will be reproduced on the left side of the reproduced sound field in stereo playback, and vice versa. A signal generated somewhere in the rear and on the left

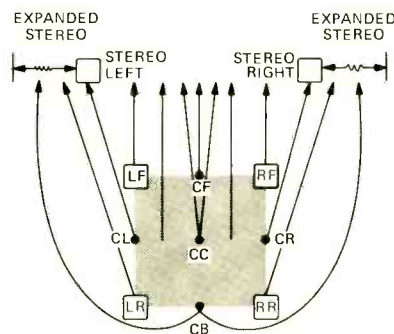


FIG. 3—POSITIONING of sounds when playing a QS record on a stereo system.

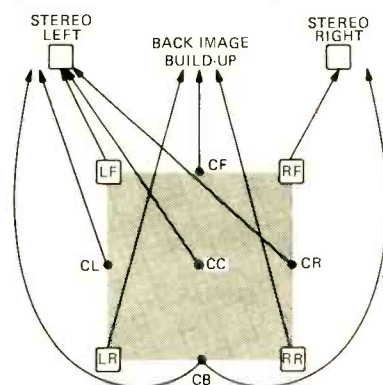


FIG. 4—POSITIONING of sounds when playing a SQ record on a stereo system.

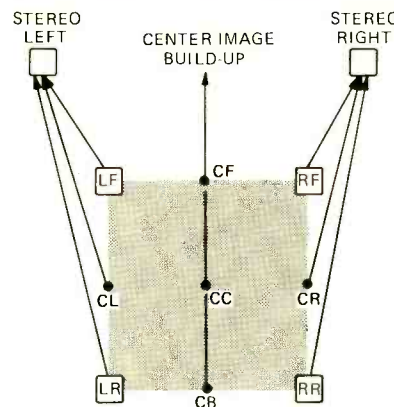


FIG. 5—POSITIONING of sounds when playing a CD-4 record on a stereo system.

will be reproduced farther to the left from the center, and a signal generated somewhere in the rear and on the right will be reproduced farther to the right from the center in stereo playback. Complete left-right symmetry is thus guaranteed.

QS and mono playback

When reproduced monophonically, the present stereo signals give a sound pressure response pattern as shown in Fig. 6, rising in level between the L and R speak-

ers. There are different opinions as to how 4-channel signals should be reproduced in monophonic playback, but the QS-encoded 4-channel signals offer a monophonic sound pressure response pat-

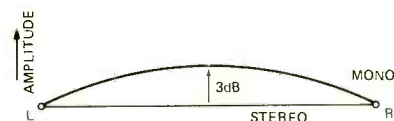


FIG. 6—SOUND PRESSURE RESPONSE for monophonic reproduction of stereo signals.

tern resembling the characteristic of a cardioid microphone. The reproduced level rises as a signal moves closer to the front center position in the original sound field; a signal generated in the rear half of the original sound field is reproduced with a lower level than a front signal, falling in level as it moves closer to the rear center position in the original sound field (see Fig. 7). Consequently, QS-encoded 4-channel records containing on-stage

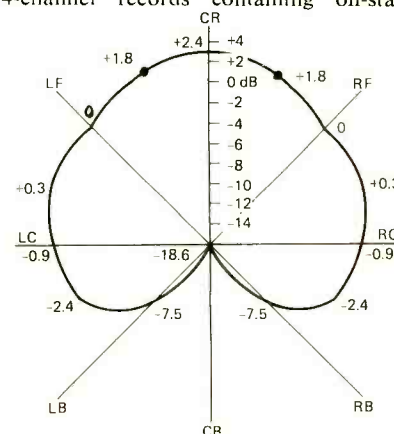


FIG. 7—SOUND PRESSURE RESPONSE of a QS-encoded signal in monophonic reproduction.

music in the front and ambience content in the rear would offer particularly well-balanced monophonic reproduction.

If, for certain applications, it is necessary to emphasize front and rear signals equally in monophonic playback, rear signals may be encoded with a certain amount of phase shift between LT-RT so that the desired monophonic sound pressure response pattern is obtained.

We have demonstrated how the QS system can transmit and reproduce all of the musical information produced in a live sound field via only two signal transmission channels. However, should it happen that more than two channels of signal transmission can be made available without any serious difficulty or inconvenience, the QS encoding theory can be extended as it is, and applied to a number of transmission channels.

For instance, if four transmission channels were available, the original sound field information could be transmitted in QS. Figure 8 presents the sound pressure response pattern of a sound source signal as it is reproduced in 4-channel via only two (LT, RT) transmissions channels, three (LT, RT, t2) transmission channels, and four (LT, RT, t2, t3) transmission channels.

Even if an unlimited number of transmission channels are available, the more

(continued on page 72)

Another advance in tube technology from RCA

RCA, the leading manufacturer of receiving tubes, offers you advanced types to satisfy the needs of the replacement market. We can do this because RCA has unique design capability that comes only with years of tube design and manufacturing experience. This means that when you install RCA-made tubes, you're selling quality tubes with the newest and best innovations in design and performance.

A dynamic approach to receiving tube technology, geared to the rigorous demands of the replacement market, RCA's exclusive, new 6MJ6/6LQ6/6JE6C brings added reliability to horizontal deflection cir-

cuits, the most critical in your customer's set. Manufactured exclusively by RCA, this new rugged horizontal output tube with the integral envelope-top-cap assembly, which totally eliminates loose top-cap problems, represents another significant advance in tube technology from RCA.

You can be certain that RCA will continue to lead the way in the receiving tube business. After all, *your* tube business is *our* tube business and we expect to share this high volume business with you for a long time to come.

See your RCA distributor for all of your tube needs.



Rugged Features of the 6MJ6/6LQ6/6JE6C

- Integral-Envelope-Top-Cap Assembly
- Rigid Cage
- Stable grid alignment
- Excellent Heat Dissipation

RCA

RCA/Electronic Components/Harrison, N.J. 07029

Circle 17 on reader service card

Satisfy frequency measurement requirements in Citizens Band Radios



B&K PRECISION MODEL 1801 \$230

With autoranging 20Hz to 40MHz guaranteed and typical upper limit of 60MHz you can precisely measure the frequency of Citizens' Band transmitters and many other low band radio services. Model 1801's typical accuracy of better than 10PPM is always available for every measurement because there are three decimal point positions automatically selected by the frequency of the signal you are measuring. And you can suppress the first digit for still more resolution above 1MHz by moving the mode switch from Auto to 1 second. This six-digit counter gives you 1Hz resolution!

Discrete, reliable TTL circuitry automatically updates the large, bright readout up to five times per second—which means the 1801 works faster than you can. There's almost no way to make a reading error because Hz or MHz and Overrange are shown by discrete, separate LED's.

If you want to make receiver tests and don't have a signal generator with the required precision, you can measure the output of your generator* with the 1801 and adjust it to the accuracy you need!

* 30mV or more

If you aren't making measurements as accurately and easily as these, you need a B&K-Precision Model 1801 which is in stock at your electronic distributor. Write for detailed specifications.



MHz display of CB channel in AUTO mode.



KHz display of same CB channel showing suppression of leading digits.

B&K PRECISION

PRODUCTS OF DYNASCAN

1801 W. Belle Plaine Avenue
Chicago, IL 60613



BUILD

4-Channel Synthesizer

Build with one IC. This device converts 2-channel stereo program material into matrix 4-channel.

by **ARNOLD NICHOLS**

MANY MUSIC LOVERS HAVE EXPANDED their stereo high-fidelity systems to 4-channel sound. But now they find that they are limited to the relatively small number of new 4-channel records and tapes that they have been able to afford to purchase. In addition, they have been unable to adequately use their existing music library.

In this article you'll discover an easy-to-build one-IC matrix synthesizer that performs the magic of converting your existing 2-channel stereo recordings into matrix 4-channel sound.

Faced with a large 2-channel music library, I designed a solution around a CBS Laboratories circuit, that I've designed into a handy little adapter. By using the synthesizer along with any existing 4-channel matrix system you will be able to play any 2-channel material you now own, or any 2-channel stereo FM broadcast through the adapter and on into your system to get a realistic 4-channel effect.

No, it's not magic. The device is based on stereo enhancement and really works. But to give you a better idea of what I am talking about, let's take a brief look at the difference between 4-channel and 2-channel systems.

How it works

Presence, in a live sound situation (when sitting in a concert hall, or attending a live rock group), is created by the effects of having an infinite

number of direct and indirect sound waves that combine in such manner as to create a feeling of liveness. The human ear, yours and mine, translates this sound field by sensing the relative time delays of these sound waves as they arrive from a variety of directions.

If we placed a single microphone in the concert hall and made a single-channel recording, we would simply be combining all of the individual sound waves with their various time delays, into one single sum signal. This sum signal, when played back, obviously cannot reproduce the total effect of the original sound field.

Now let's put two microphones into that hypothetical concert hall and see what happens. When we record now, for stereo playback of course, we end up with two sum signals; each one somewhat different from the other. When we play back these two signals through a stereo system (2 channel), these two sum signals (one left and one right), recreate appreciably more information than the monophonic signal we described earlier. While the realism is greatly improved over that of the monophonic system, the stereo playback is still lacking in presence.

To get 4-channel sound from that two-channel recording we must find a way to create the sense of sound source position or sound source location that is so peculiar to 4-channel sound. Fortunately a method for doing this does exist. CBS Laboratories has developed a circuit that solves this problem by

analyzing and then synthesizing ordinary 2-channel stereo signals to obtain the separate and indirect sound signals that are characteristic of the output from a 4-channel matrix system.

By using this special decoding system, it is possible to create a 4-channel synthesizer that redistributes the conventional 2-channel stereo signals into a complete sound field made up of four distinct sound sources—front right, front left, rear right, and rear left.

By feeding the output of this simple synthesizer into a matrix decoder (simple, thanks to the use of an integrated circuit) it becomes possible to create the sense of sound position. If you don't use a matrix decoder you'll get 2-channel SQ encoded matrix output.

Any musical instruments or voices that were positioned at the left of the stage when the original 2-channel recording was made, will be heard near the left rear corner. Any sound sources located to right of these will play back in the left front corner. Sound sources originating at the right end play back from the right rear and those a little to the left from the right front.

Fortunately, most 2-channel stereo recordings do contain echo components. And when these sound elements are recovered by the synthesizer the listening area appears to be filled with a natural "live performance" sound.

Using this circuit, built around an MC1312P matrix decoder, successfully creates the impression of sound source

positions. However, the total amount of information that is presented to the listener is less than that actually present in a live sound situation.

The indirect sound components separated by the MC1312P are phase-modulated either 180° or 270°. This is done automatically by a 4-pole phase-shift network system developed by CBS Laboratories, before these signals are sent on to the rear channels.

When these phase-shifted signals are combined with the direct sound components that are reproduced by the front channels, a richer, livelier, more realistic sound is produced.

The added phase modulation takes good advantage of a well-known psychoacoustical phenomenon. Two, in phase, speaker systems position the sound at a point midway between them if their sound amplitudes are equal. However, when the same two speaker systems are connected out-of-phase

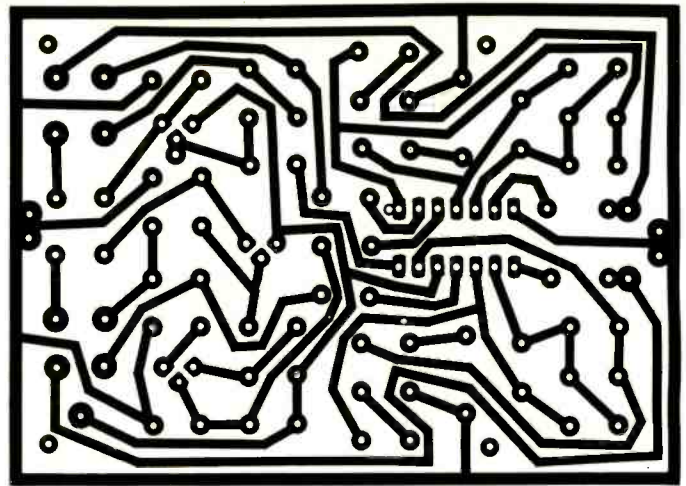


FIG. 2 (right) - FOIL PATTERN of converter shown full-size.

FIG. 3 (below) - COMPONENT PLACEMENT of converter PC board.

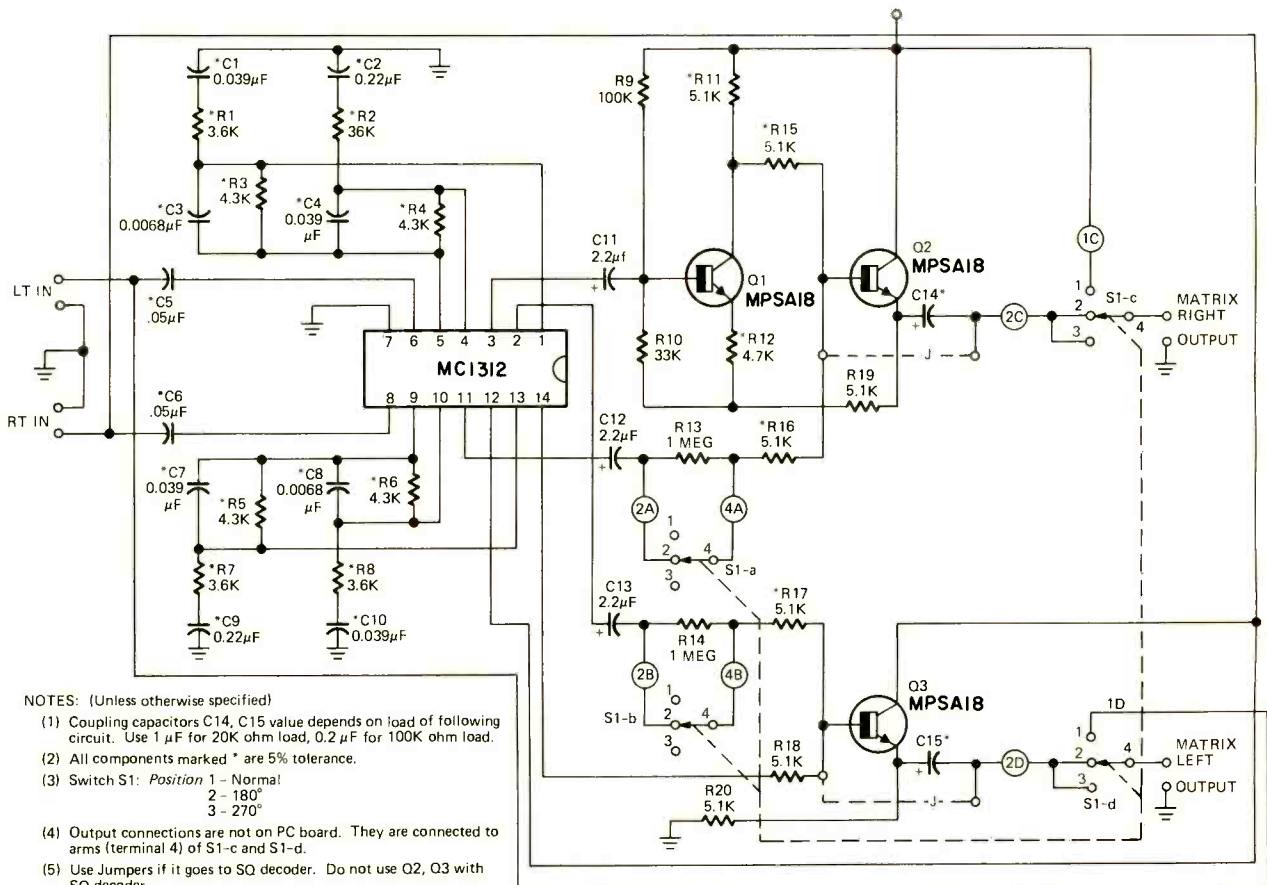
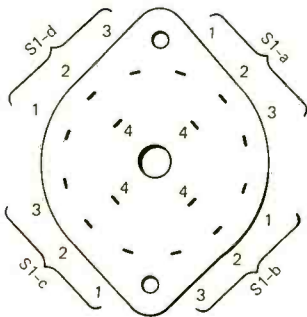
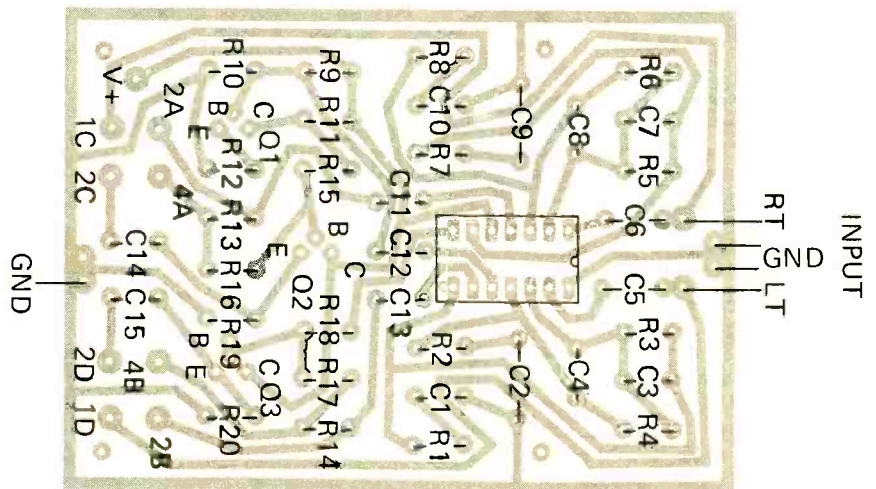


FIG. 1 - SCHEMATIC DIAGRAM of the 2-channel stereo to 4-channel matrix converter.

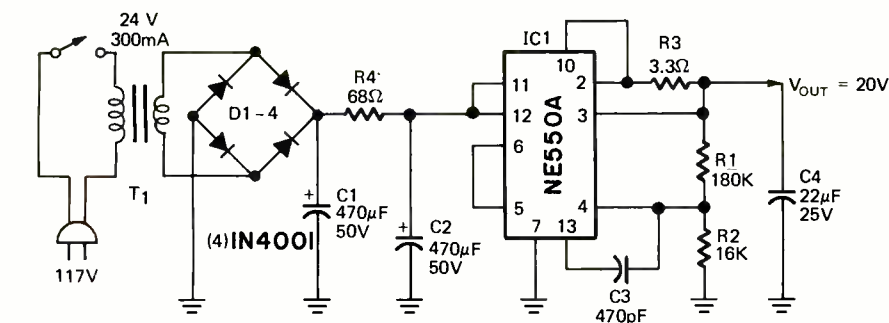


FIG. 4—SCHEMATIC DIAGRAM of power supply.

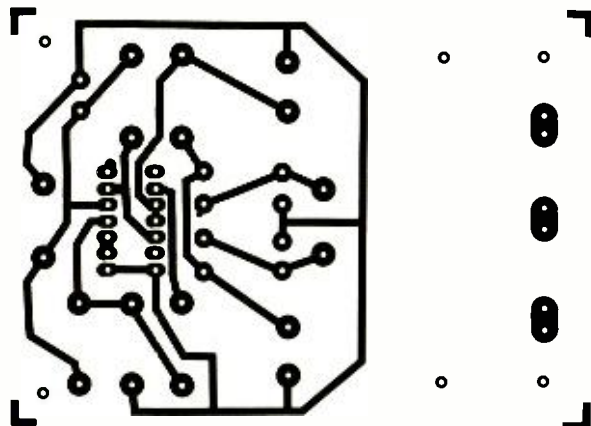


FIG. 5—POWER SUPPLY printed circuit board shown full-size.

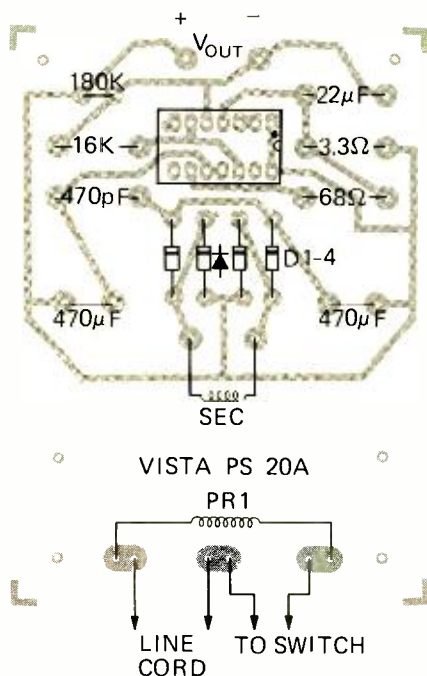


FIG. 6—COMPONENT PLACEMENT of power supply printed circuit board.


with each other, they no longer form a clear sound image. However, the two out-of-phase signals do not totally cancel each other.

When we phase-modulate the signals of either the front or the rear speaker systems under the synthesized 4-channel conditions, what we produce is the same effect we would have gotten if we had placed a number of speaker systems side-by-side around all four

walls of the room—a wall of sound with changing characteristics because of the constantly changing phase relationships. Thus by using a 2-channel sound source and the 4-channel matrix synthesizer we create an effect that rivals that of true 4-channel reproduction.

The synthesizer provides three outputs: 1. Standard stereo, 2. 180° matrix, 3. 270° matrix.

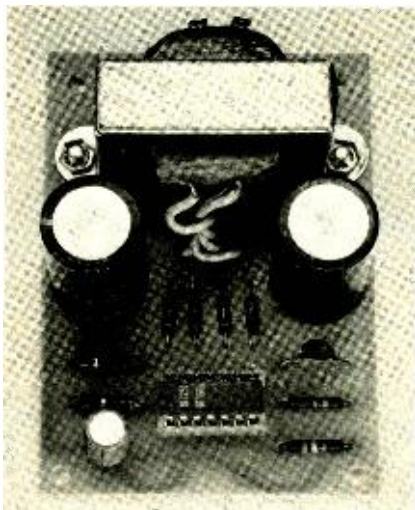If you connect your synthesizer to an SQ decoder or some other matrix decoders you may find that the result is a very strange sounding output. If this occurs, disconnect Q2 and Q3 and add jumpers from the junction of R6 & C14 to S1-b. Add another jumper from the junction of R15 and the base



POWER SUPPLY circuit board shows location of components.

PARTS LIST (SYNTHESIZER)

All resistors ¼-watt, 5%, carbon film (Do not substitute)

R1, R7, R8—3600 ohms
R3, R4, R5, R6—4300 ohms
R9—100,000 ohms
R10—33,000 ohms
R11, R15, R16, R17, R18, R19, R20—5100 ohms
R12—4700 ohms
R13, R14—1 megohm

All capacitors 5% film dielectric unless noted. (Do not substitute)

C1, C7, C10—.039 µF
C2—0.22 µF
C3, C8—0068 µF
C4—.069 µF
C5, C6—.047 µF, 10%
C9—0.22 µF
C11, C12, C13—2.2 µF, tantalum, ± 20%
C14, C15—Use 1 µF for 20K load, 0.2 µF for 100K load (Not supplied in kit)
IC1—MC1312P
Q1, Q2, Q3—MPS A18 (NPN low-noise device. Do not substitute)
S1—4-pole 3-position rotary. (No knob supplied)
Circuit Board
Molex Connectors for IC1 socket
Shielded cable for input (Supplied in kit with RCA type plugs.)

PARTS LIST (POWER SUPPLY)

R1—180,000 ohms, ¼ W, 5%
R2—15,000 ohms, ¼ W, 5%
R3—3,300 ohms, ½ W, 10%
R4—100 ohms, ½ W, 10%
C1—500 or 1,000 µF, 25V, electrolytic
C3—470 pF, ceramic
C4—20 µF, 25V, electrolytic
D1, D2, D3, D4—IN4001
IC1—NE550A voltage regulator (Signetics)
Circuit Board
Molex connectors for IC socket
Line cord (Not supplied in Kit)
SPST switch (Not supplied in kit)

Following items are available from Photovolume Inc., 128 East 28th Street, New York, N.Y.

Synthesizer and Power Supply Kit No. MAT-5	\$19.95
Synthesizer Kit No. MAT-4	\$15.95
Power Supply Kit No. PS-20A	\$ 6.95
Set of 2 circuit boards for power supply and synthesizer No. MATB	\$ 5.75

of Q2 to S1-c.

Building your system is easy. The complete schematic is in Fig. 1. A full size circuit board pattern for the unit is shown in Fig. 2 and the parts placement is in Fig. 3. Assembly is fast and straight forward as long as you take reasonable precautions when soldering the IC and low-noise transistors into place. A separate power supply is also needed. You may be able to take off the necessary voltage from your existing equipment. You'll need a well filtered and regulated 20 volts at 20 mA.

If this voltage is not available, build the power supply shown in Fig. 4. Its printed circuit board layout is in Fig. 5 and parts placement on this circuit

(continued on page 79)

Radio-Electronics®

Tests Pioneer CT-F9191

by LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

THE PIONEER CT-F9191 IS THE FOURTH "front-loading" cassette introduced by that company and in terms of features and performance it is the finest of that quartet of products. Just one look at this attractive unit will convince the skeptics that the cassette deck has indeed "come of age" and deserves to join the ranks of other fine component high-fidelity products. Like all of the recently introduced front loaders, access to all controls and to the cassette compartment is gained through the front panel and the unit looks like any other component such as an amplifier or tuner that can be tucked neatly on a shelf or stacked above or below companion components. A full view of the front panel is shown in Fig. 1.

A curved plastic cover swings out of the way at the press of a button, opening the cassette compartment that accepts cassettes in a vertical position. The cassette is inserted in an easy up-and-into-place motion and the cover door flips down manually. Next to the power ON-OFF toggle switch at the lower left corner are the usual transport controls which are extremely easy to depress (they are of the piano-key type, but more important, they operate electronically, controlling semiconductor logic and solenoid circuits) and any mode can be selected without going through the stop position. The combined use of the separate PAUSE switch and the RECORD and PLAY switch permits the user to set up record levels before tape travel begins. When power is applied, the inside of the cassette compartment is illuminated, which makes it easy to see if the tape is travelling.

A close-up view of the major front panel controls is shown in Fig. 2. Dual concentric rotary knobs control the MIC of DIN input record levels, line input record levels and playback output levels. This arrangement permits mixing of microphone and line inputs, or DIN and line

inputs in each of the two channels. Above these controls are a three-digit counter with its usual rest button. Zero setting of the counter can be used in conjunction with the memory pushbutton. Like most memory-rewind features found on competitive units, the transport will rewind a given tape to the pre-set point determined by the counter's reach 999. But unlike most, if the PLAY transport button is depressed during the rewind cycle, the tape will reach the predetermined point and begin playing over again, if desired. A light above this button tells the user when the button is depressed.

A record limiter circuit is activated by the next button and is particularly useful when recording from live sources or when unpredictably loud transients are likely to be encountered. Next come the


bias and equalization push-button switches with settings for standard (or low noise) and Chrome tapes. This deck is equipped with automatic sensing for the newer Chrome tapes and switching to correct equalization and bias takes place automatically when such tapes are used, completely bypassing the manual bias and EQ buttons. In any case, when Chrome settings are selected, a light above these buttons indicates that fact. Additional push buttons activate an MPX filter circuit and the Dolby noise reduction circuitry. A light above the Dolby button indicates when it is in use. At the extreme right of the panel are a pair of microphone inputs (one for each channel) and the headphone output jack.

Two well illuminated large recording-level and playback-level meters are calibrated all the way from -40 dB to +5 dB, a feature that can only be appreciated fully after you use the deck for serious musical recording work. This wide range calibration permits the recordist to monitor just about the entire dynamic range of anything being recorded. Between the two level meters are a record LED indicator light and a peak-level indicator that flashes whenever instantaneous recording level exceeds +5 dB, preventing over-recording and high distortion levels for signals that are too fast to be registered on the regular VU meters.

The section of the rear panel shown in Fig. 3 contains the familiar combination DIN record/play multiple connector as well as dual pairs of line-input and line-output jacks. This doubling up of input and output pairs (which are simply wired in parallel) is an inexpensive addition, but a mighty handy one if you want to dub to a second deck, or feed two separate playback systems at once. Typical interconnection of the CT-F9191 in a high-fidelity component system is shown in Fig. 4.


Circuit configuration and layout

A view of the internal layout of the Pioneer CT-F9191 is shown in Fig. 5. Note that most of the electronic circuitry is below deck, where it is well shielded. Major modules include separate circuit boards for the record/play amplifier, the Dolby noise reduction circuitry, the electronic control circuitry and the switch assembly. Additional separate assemblies include the power supply (which is regulated by means of a transistor-Zener diode

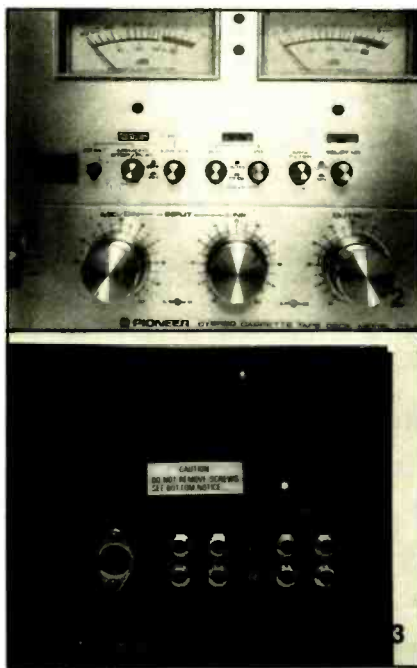


SUMMARY OF MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Frequency Response: (Low-noise, High-output tape) 35 to 13,000 Hz, ± 3 dB; (Chromium dioxide tape) 30 to 14,000 Hz ± 3 dB. **Wow-and-Flutter:** Less than 0.07% WRMS. **Harmonic Distortion:** Less than 1.7% (at 0 dB). **Signal-to-Noise Ratio:** (Dolby off) 52 dB; (Dolby on) 62 dB (Low-noise tapes). **Input Sensitivity:** (Mic.) 0.22 mV, 30K ohms; (Line) 65 mV or more, 100K ohms; (DIN Rec/PB) **Max Input:** 100 mV; Output same as line. **Output Level** (ref: 0 dB): (Line) 315 mV; (Headphone): 40 mV into 8 ohms. **Power Requirements:** 120 V, 50-60 Hz, 53-watts maximum. **Dimensions:** 17 $\frac{1}{8}$ " wide \times 7 $\frac{7}{8}$ " high \times 12 $\frac{1}{2}$ " deep, including walnut grained vinyl cabinet. **Weight:** 29 lbs. **Suggested retail price:** \$450.00 including cabinet.

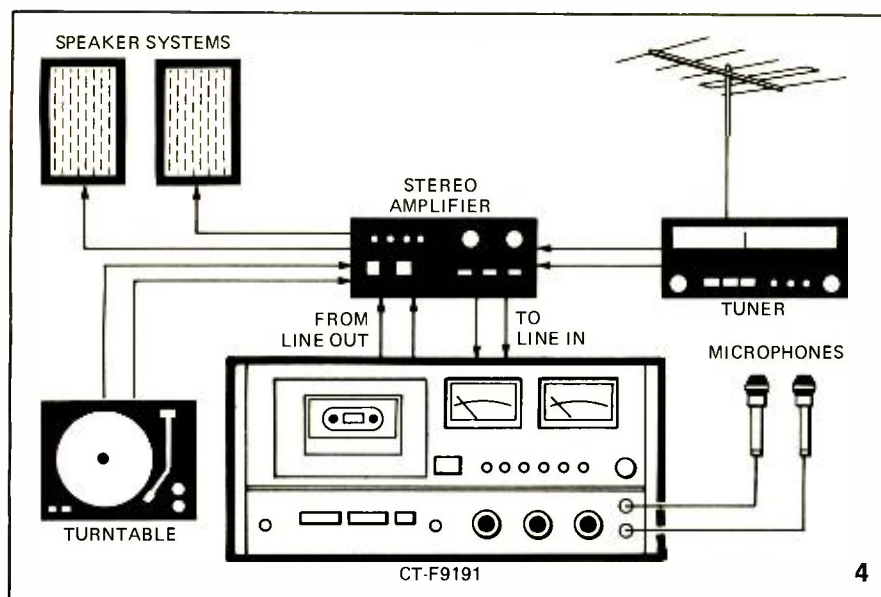

arrangement) and a transistor assembly that operates the record solenoid. An electronically controlled DC motor is used to drive the tape capstan, while a separate DC torque motor is used for the fast forward and rewind drives. The record/play head is a solid ferrite type, while the erase head is of ferrite construction. A three-stage direct coupled input amplifier-equalizer is used in each channel. A logarithmic amplifier circuit is used to drive the wide range meters. Total semiconductor complement in the CT-F9191 consists of 71 transistors, 6 FET's (two of which are used in the Dolby circuit), 75 diodes, 5 Zener diodes and 2 LED's. A complete circuit diagram of the unit, including all con-

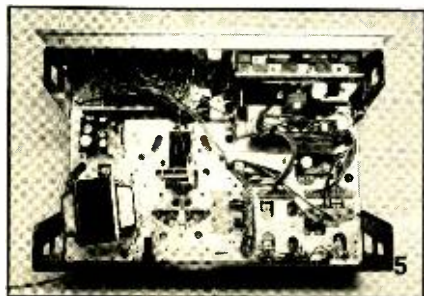

trol electronics, is supplied as a large separate fold-out sheet with the owner's manual.

Laboratory measurements

Measurements of the performance of any tape deck are inevitably influenced by the brand of tape chosen for use in the tests. In our case, we selected TDK type ED-C-60 High-Output, Low-Noise cassettes for all measurements involving the standard settings of the bias and EQ switches and TDK type KR-C-60 (Chrome) cassettes for measurements involving performance with CRO₂ tape. Both of these tapes are listed in the comprehensive table of recommended tapes and switch settings that is provided in the owner's manual.

Results of our measurements are shown in Table I. Frequency response, using our "standard" tape, is plotted in Fig. 6 on a record/playback basis. While two plots

are shown (for 0 dB level and for -20 dB reference recording level), the -20 dB reference curve is the more meaningful one in terms of musical performance. Any properly equalized tape deck (of the

cassette variety) will cause saturation of magnetic tape if high frequencies are recorded at 0 VU level—a condition that seldom occurs when recording actual music (and not test tones). We present both curves only because the manner in which the machine causes saturation (and the frequencies at which this roll-off begins) may be of some interest to readers when comparing the performance of this machine with others to be reviewed in the future. In terms of the more conventional -20 dB reference level, the response of the unit extends from 30 Hz to 12,000 Hz, ± 3 dB with this tape sample. While this may not seem overly impressive to hi-fi addicts, we suggest you read our summary comment regarding this point at the conclusion of this report, following Table II.

Frequency response was considerably wider using the CRO₂ sample tape, as shown in Fig. 7. In this instance, response was flat from 28 Hz to 15,000 Hz, ± 3 dB—better than claimed by the manufacturer. Remember, some variation in response is to be expected depending upon tape brand and type used, and those seeking that last kHz may want to experiment with some of the other tape brands listed by Pioneer as being suitable.


TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer **U.S. Pioneer Electronics**


Model **CT-F9191**

CASSETTE TAPE DECK MEASUREMENTS

FREQUENCY RESPONSE MEASUREMENTS	R-E Measurements		R-E Evaluation
Frequency response, standard tape (Hz—kHz \pm dB)	30—12 \pm 3		Good
Frequency response, CRO ₂ tape (Hz—kHz \pm dB)	28—15 \pm 3		Very good
DISTORTION MEASUREMENTS (RECORD/PLAY)	Low-Noise	CRO ₂	
Harmonic distortion @ -10-VU (1 kHz) (%)	1.0	1.0	Excellent
Harmonic distortion @ -3-VU (1 kHz) (%)	1.4	1.2	Very good
Harmonic distortion @ 0-VU (1 kHz) (%)	1.4	1.6	Excellent
Harmonic distortion @ +3-VU (1 kHz) (%)	1.7	2.4	Excellent/Very good
SIGNAL-TO-NOISE RATIO MEASUREMENTS	Weighted	Unweighted	
Standard tape, Dolby off (dB)	56	50	Excellent
Standard tape, Dolby on (dB)	66	57	(See text)
CRO ₂ tape, Dolby off (dB)	58	51	Very good
CRO ₂ tape, Dolby on (dB)	68	60	(See text)
MECHANICAL PERFORMANCE MEASUREMENTS	WRMS	RMS	
Wow-and-flutter (% WRMS)	0.05	0.08	Excellent
Fast wind and rewind time, C-60 (seconds)	59		Good
COMPONENT MATCHING CHARACTERISTICS			
Microphone input sensitivity (mV)	0.24		
Line input sensitivity (mV)	60		
Line output level (mV)	300		
Phone output level (mV)	40		
Bias frequency (kHz)	N/A		
TRANSPORT MECHANISM EVALUATION			
Action of transport controls			Excellent
Absence of mechanical noise			Very good
Tape head accessibility			Excellent
Construction and internal layout			Very good
Evaluation of extra features, if any			Excellent
CONTROL EVALUATION			
Level indicator(s)			Superb
Level control action			Very good
Adequacy of controls			Excellent
Evaluation of extra controls			Excellent
OVERALL TAPE DECK PERFORMANCE RATING			Excellent

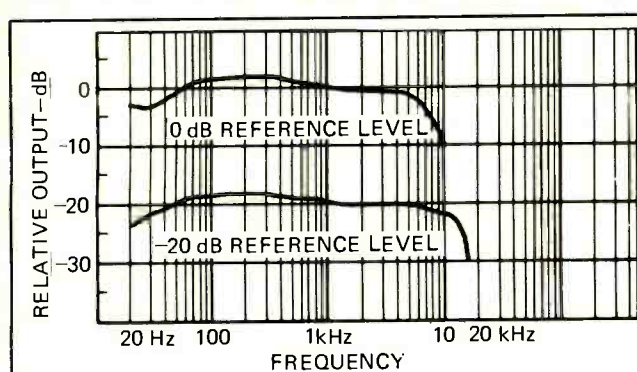

6

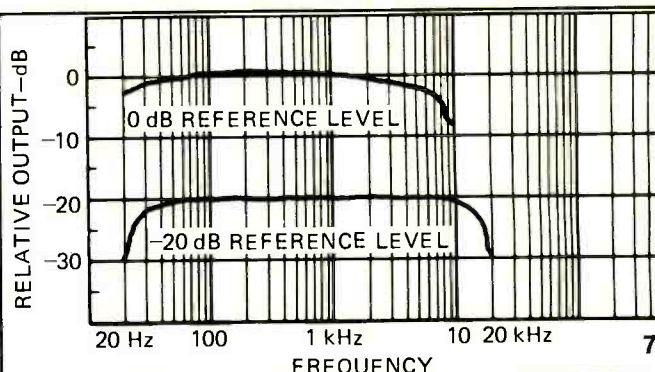

7

Distortion was extremely low with both types of tape, and the CT-F9191 is judged by us to have considerable head room—an important quality for serious recordists. It should be noted, too, that the peak indicator LED flashed on for us at +5.5 dB. At this level, using low-noise tape, we were just approaching the 3% THD point considered to be the top end of recorder capability by the professionals. Using the Chrome sample, the 3% distortion point was reached at +4 dB on the VU meters. Chrome tape generally tends to saturate at a bit lower VU meter readings on most recorders, but it should be recalled that the *actual* recording level (because of changes in bias) is really greater than that obtained with standard tapes. This accounts, in part, for the better S/N ratios obtained with CRO₂ tape.

The signal-to-noise ratios tabulated in Table I are in all cases referenced to the 3% distortion point. While it is generally stated that "Dolby adds 10-dB to S/N ratios," you will note that this improvement holds true for our weighted measurements of noise (we use a type-A weighting network), but is not quite true for the unweighted figures. That is because Dolby operates to reduce noise at high frequencies only (hiss). The fact that Dolby improves S/N by some 7 dB even in the unweighted measurement of noise using standard tape suggests that the low-

frequency noise content, using the CT-F9191 (hum and other low frequency disturbance) is very low indeed. In fact, all the noise measurements tabulated represent excellent performance by a cassette deck.

Wow-and-flutter measured a constant 0.05% WRMS, considerably better than the .07% claimed by the manufacturer, and again, one of the lowest figures we have read for any cassette deck. Other subjective evaluations of machine performance and features will be found in Table I.

Utilization and listening tests

We tried a variety of input signal sources with the CT-F9191 and even did a bit of microphone and line mixing in the course of our lab testing. (We find it handy to "announce" frequencies when recording our tests for frequency response measurements, since on playback we don't have to remember precisely what test frequencies we used.) A simple little feature we neglected to mention earlier is the addition of a plastic reference-ring

at the rear of each set of level-control knobs. These rings act as markers after you have established a preferred level for a particular microphone or line input source. An inexpensive but useful addition that is typical of this fine cassette deck. Nothing has been overlooked, and no unneeded frills have been added.

Our use tests included the recording of music from disc as well as from FM. While there is no published indication of bias frequency, it is evidently high enough so that we did not find it necessary to employ the MPX-filter when recording stereo FM programs. This, of course, may not be so when using poorer quality tuners which have fair amounts of sub-carrier output products.

Our capsule summary, along with overall comments regarding performance of the CT-F9191 will be found in Table II. Several of the performance measurements were repeated after using the machine for a couple of days, and results remained the same, indicating a high degree of mechanical and electrical stability for this new entry from Pioneer.

R-E

TABLE II

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer **U.S. Pioneer Electronics**

Model **CT-F9191**

OVERALL PRODUCT ANALYSIS

Retail price (suggested) \$450.00
Price category Medium-high
Price/performance ratio Excellent
Styling and appearance Excellent
Sound quality Very good
Mechanical performance Excellent

Comments:

Pioneer has been stressing the fact that well-designed cassette decks can do just about everything that more expensive open-reel machines can do—and can do it more conveniently at that. With the exception of the lack of tape monitoring facilities (which requires a three-head machine), the CT-F9191 comes as close to fulfilling that claim as any machine in its price category. Certainly, the "non-professional" recordist may question its somewhat limited frequency response, having been conditioned to believe that any component that does not have a ruler-flat response from 20 Hz to 20 kHz is deficient. Ask any professional recordist about this, and he will tell you that he'd rather have excellent S/N and low distortion than super-high frequency response. Those qualities are supplied in abundance in the Pioneer CT-F9191. Add to that its extra features such as the peak limiter, the wide range VU meters (the only other machine we know of that can register a range of 45-dB costs \$1200.00 or more), its front-load configuration and its many automatic features and the unit will be very hard to beat.

Tests Soundcraftsmen RP2212



by **LEN FELDMAN**
CONTRIBUTING HI-FI EDITOR

AUDIO PERFECTIONISTS HAVE LONG RECOGNIZED the limitations of the typical bass and treble controls found on preamplifiers, amplifiers and integrated receivers. These controls alter the tonal response of nearly half of the entire audio spectrum with one turn of a knob. More often than not, what is needed in a system is a specific "boost" or "cut" for a narrow range of frequencies to compensate for speaker system deficiencies, room acoustic problems or frequency response limitations in other associated components or even the program source itself. Thus, a new category of components is becoming increasingly popular with demanding audiophiles. The octave-by-octave equalizers (and even some third-octave-by-third-octave equalizers) have been in use for some time in the sound reinforcement segment of the audio industry and are used to "equalize" large halls and auditoriums with respect to the public address systems installed in them.

Taking an approach similar to that used in much more expensive and complex professional equalizers, Soundcraftsmen offers a pair of equalizers for home music systems. The more expensive of these, the RP-2212, is shown in Fig. 1. The upper portion of the front panel is divided into two equal and symmetrical sections, each containing ten separate lever controls for a single channel of a stereo system. Since each control affects approximately a one octave frequency-band, the controls are given octave designations, as follows: 20/40, 40/80, 80/160, 160/320, 320/640, 640/1280, 1280/2560, 2560/5120, 5120/10240, 10240/20480. With all the levers set to the center positions (controls are calibrated in 1 dB increments from -12 to +12), each range of frequencies named is neither boosted nor attenuated. By moving a lever up or down, the octave of frequencies affected by that control can be boosted or attenuated by a maximum of 12 dB.

SUMMARY OF MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Frequency Response: 20-Hz to 20,000-Hz ± 0.5 -dB. **Harmonic Distortion:** Less than 0.1% at 2 volts (typically 0.05% at 1 volt in and out). **IM Distortion:** Less than 0.1% at 2 volts (typically 0.05% at 1 volt). **Signal-to-Noise Ratio:** Better than 90-dB referred to 2-volt input. **Input Impedance:** Operates from any signal source 100K ohms or less. **Output Impedance:** Operable into 3K ohms or greater. **Control range:** ± 12 dB, each octave. **Dimensions:** 20" wide \times 7 1/4" high \times 11 3/4" deep (including supplied walnut-grained cabinet). **Suggested retail price:** \$349.50.

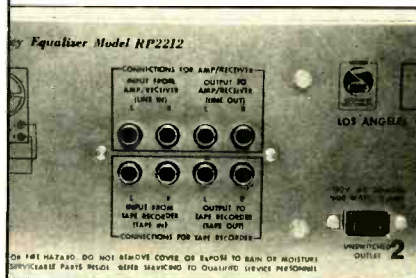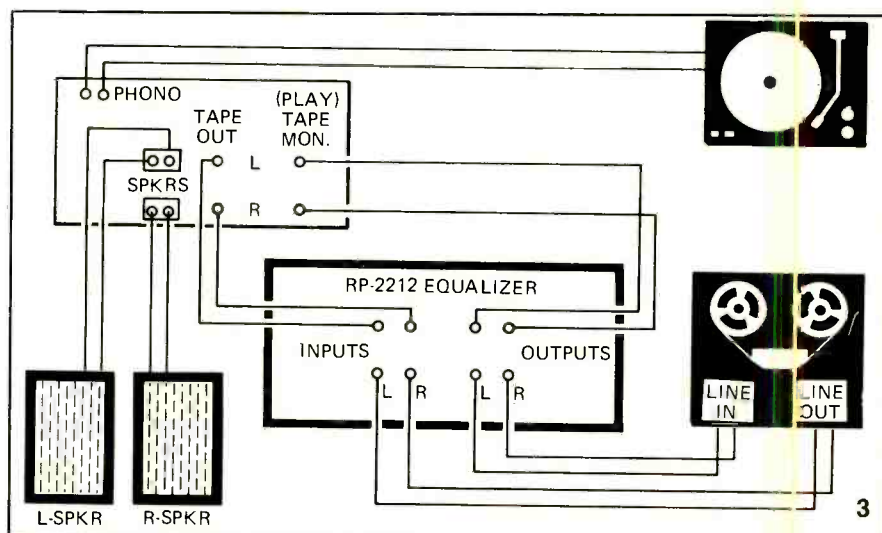


At the center of the panel are a pair of master gain controls that adjust overall gain of the system so that after final equalized settings are established, the music will sound as loud as in its unequalized form. A pair of LED lights associated with each master gain control helps establish this equal loudness setting by blinking equally when the master control is properly set. The less costly model RP20-12 lacks these LED's plus one other feature that we'll discuss in a moment.

Along the bottom of the front panel are a power on/off pushbutton and four more pushbuttons at the lower right. One of these simply tests the LED lights. The sec-

ond button activates the tape monitor circuitry (since the equalizer must be connected to the tape-out/tape in jacks of your present amplifier or receiver, thereby using up your original tape monitoring circuit). The final pair of buttons determine whether the equalized response should be applied to the tape out jacks, or to the line output jacks. By pressing the EQUALIZE TAPE button of this pair, it is possible to pre-equalize programs being fed to your recorder, a feature not possible with regular tape monitoring circuits that are always positioned ahead of any tone control circuits in amplifiers or receivers. This equalize-tape feature is also omitted in the lower cost model RP20-12.

Figure 2 shows a closeup of the connecting jacks on the rear panel of the RP2212, while Fig. 3 illustrates how the unit would be incorporated in a complete stereo high-fidelity component system.


The circuitry of the RP2212 is contained on two glass-epoxy circuit boards (one per stereo channel) and L-C filter circuits are used for each octave. Toroidal inductors are used for the lower three octaves of each channel, while ferrite-core inductors are used for the remaining seven octaves. Internal layout of the RP2212 is shown in Fig. 4. Note the fully shielded and enclosed power supply area at the rear left of Fig. 4. A metal top cover was removed for this photograph and when it is in place, the entire circuitry of the RP2212 is fully sealed within its overall metal housing before it is inserted in the decorative walnut grain

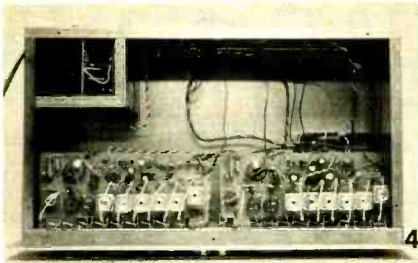

cabinet seen in Fig. 1. It should also be noted, that all resistors used in the octave filters are specially selected, low-noise carbon film types.

Laboratory measurements

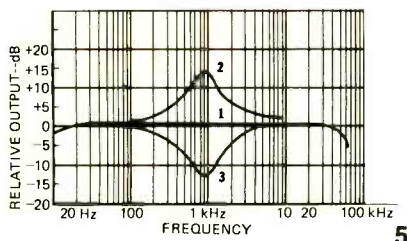Nominal input and output of the RP2212 is 1 volt with all the controls set for a flat response and we measured frequency response from input to output under these conditions. The results are plotted in Fig. 5 (curve 1). Response is flat within 1 dB from 15 Hz to 30 kHz,



with the -3dB roll-off point at 40 kHz. Next, we plotted response of the system with just a single lever adjusted to maximum boost. We chose the 640/1280 octave for this curve, and, as can be seen from curve-2 of Fig. 5, response peaked at almost precisely 960 Hz, the mid-point of that particular octave. Maximum boost


at that frequency was 13.5 dB. Next, we adjusted the same lever for maximum attenuation and obtained curve-3 of Fig. 5. Other levers responded singly in just about the same fashion and we observed a high degree of precision in terms of frequency accuracy of the designated octaves.

Before attempting to equalize our system for a flat acoustic response, we set the levers for an arbitrary curve. Setting the system to any desired curve is greatly facilitated by a series of paper charts that Soundcraftsmen calls Computone charts. When a group of desired settings of controls is determined (and settings may vary depending upon program sources, listening position and other factors), the user simply marks the control settings on the




chart. The chart can then be cut out to the noted settings and placed on the surface of the front panel. Levers are quickly slid up to meet the remaining cardboard template and the desired response curve is quickly reestablished. The technique is illustrated in Fig. 6 which shows the settings we used in this first arbitrary response curve.

Figure 7 shows the individual lever settings we used in this experiment (dash marks), and the resultant response curve (continuous plot) obtained with these settings. As you would expect there is a

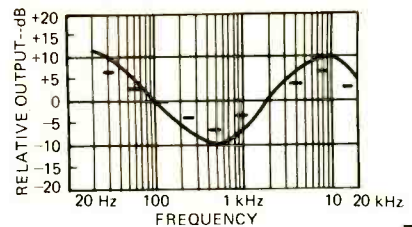

certain amount of interaction between adjacent lever controls, but the response curve corresponds quite well in overall shape with the octave-by-octave settings on the front panel.

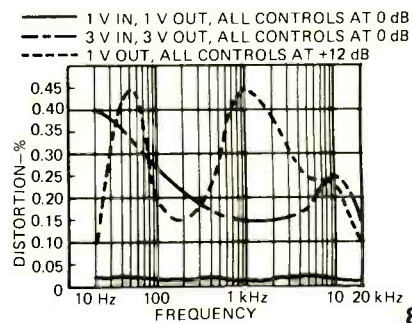
We measured the total harmonic distortion for a variety of input levels and control settings. Results are shown in Fig. 8. With all the control levers at their center position, and an input and output voltage adjusted to 1 volt, THD varied



from 0.01% to 0.02%, well below the 0.1% claimed. Increasing the input level to 3 volts (far more than is likely to be available from any program source connected from the tape out jacks of an amplifier or receiver), THD was still quite low, ranging from a high of 0.4% (at 20 Hz) to a low of 0.15% (at mid frequencies). Finally, we boosted all controls to their maximum (+12 dB) positions and adjusted the output for 1 volt. Even under these extreme conditions, THD never exceeded 0.5% at any frequency measured.

Equalizing a system

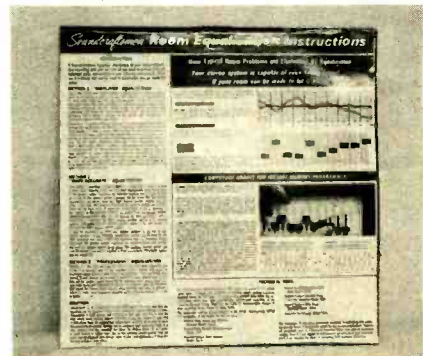Trying to equalize a hi-fi system in a given listening environment would be almost impossible without very elaborate test equipment were it not for a very



cleverly conceived test record that Soundcraftsmen supplies with each RP2212 (See Fig. 9). The recording contains third-octave bands of pink noise on the left channel and a reference tone on the

(continued on page 90)

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Soundcraftsmen**

Model: **#RP-2212**

OVERALL PRODUCT ANALYSIS

Retail Price
Price Category
Price/Performance Ratio
Styling and Appearance
Sound Quality
Mechanical Performance

\$349.95
Medium-high
Very good
Good
Excellent
Excellent

Comments: The Soundcraftsmen RP2212 equalizer can hardly be classified as an accessory, since it costs as much as some complete receivers and amplifiers. Nor is it an item that every audio enthusiast will consider a necessity in his or her hi-fi system. For those who seek the ultimate in tonal compensation, the unit is highly recommended. We consider its ten-octave control (octave-by-octave) to be the *least* required to accomplish true acoustic equalization. There are five-control units on the market which do not have the degree of tonal segmentation required for this type of adjustment, and there are also units (at much higher cost) which break down the audio spectrum into thirds of an octave.

An important word of caution! Inordinate amounts of bass boost using any tone control system may result in flat response for your system, but unless your amplifier has enough reserve power output capability, such high levels of boost may well send the amp into overload clipping at frequencies that are accentuated to that degree. Remember, 10 dB of boost means *ten times the power output* that must be delivered by your amplifier at the boosted frequencies. One of the most useful applications of this equalizer is the pre-equalization of tape recordings, when trying to dub from old discs (or even tapes which had tonal deficiencies) to tape. If you are a serious recordist, don't settle for the lower cost RP20-12, which does as good a job of equalizing for home listening but lacks this important extra feature.

Even if you find your entire system (and room) provides perfectly flat response, you'll find the RP-2212 useful with many program sources, including FM and records which were "pressed" at anything but flat response.

BOOKSHELF SPEAKERS

How To Buy

Understanding the specifications is the first step. But there's more. Knowing how to conduct listening tests, speaker placement and room acoustics are just as important.

by **ARTHUR KLEIMAN**

ASSOCIATE EDITOR

SELECTING A SPEAKER SYSTEM IS FAR FROM an easy task. The vast number of speaker systems currently available can present the potential purchaser with so many choices that he will reach a point of complete indecision. Let's face it, just about everybody and their relatives are manufacturing speaker systems, and a day hardly goes by that a new model or a major breakthrough isn't announced. This coupled with a lack of an industry-wide standard for specifying speaker characteristics creates a nightmarish situation, but not a hopeless one. Armed with the weapon of meaningful specifications and the knowledge of the important considerations simplifies the task.

The speaker system is probably the weakest link in the high-fidelity chain. The purpose of a hi-fi system is to *accurately* reproduce original sounds. The ideal system should not alter the original sound in any way. The response of the total hi-fi system is made up of the response of each individual component. Each component alters the sound in its own way. Each adds its own "color". Of all the components in the system, the speaker system is the worst offender. It alters the sound the most. Therefore, selecting a speaker system is a crucial choice. The idea is to choose the best speaker system for a given amount of money. Best meaning the most accurate. It also means you must consider factors such as size and amplifier-speaker matching parameters.

The first two parts of this article will investigate important speaker specifications and describe how to use them when selecting a speaker system. These specifications include frequency response, dispersion, linearity, efficiency, power handling capacity, maximum sound output and impedance. Manufacturers' specifications for a number of speaker systems are provided. The third and last part of the article covers listening tests, room acoustics, speaker placement and speaker set-up.

Manufacturer's specifications

In this article, specifications for a number of speaker systems are presented. These specifications are manufacturers' specifications and not those measured by **Radio-Electronics** hi-fi lab. **Radio-Electronics** queried 93 manufacturers (see Table I) covering 232 different speaker

systems. Not every manufacturer responded. Of those that did, some gave only a partial reply. Others bent over backwards to provide all of the requested information and more.

Specifications have little or no meaning if the conditions that they are measured under are not known. For example, let's say, I connect a voltmeter with a high input impedance across two terminals in a circuit and measure 100 volts. Now someone comes along with a low-impedance voltmeter and measures 75 volts. If he concludes that the circuit is erratic, he is wrong. The fault is in the testing procedure. This is why "How You Measure" is just as important as what you measure. Also, if the circuit was used in a frequency-dependent application where voltage is irrelevant, the voltage measurement would be meaningless. But a frequency measurement would tell us something meaningful about the performance of the circuit. Therefore, measurement conditions must be specified.

Radio-Electronics mailed a detailed questionnaire to each manufacturer. It specified the conditions that each speaker characteristic was to be measured under. Some readers will question, as some manufacturers have, the validity of the conditions. But for a comparative-only analysis, the conditions outlined are valid. For that matter, almost any set of conditions would be valid for comparative purposes, so long as all the speaker systems are measured under that same set of conditions. These conditions only affect the meaning of the specifications.

Physical size

The small speaker system is very popular today. It is used in the vast majority of hi-fi systems. For this reason, this article is limited to those speakers falling into the "bookshelf" category. However, a much more precise definition of a bookshelf system is necessary.

We decided to call any speaker system measuring $25 \times 15 \times 14$ in. or smaller a bookshelf speaker system, with a few exceptions. These are the direct-reflecting speaker systems that must be placed at least 12 inches away from the wall. Such systems are usually placed on a pedestal and cannot be considered a bookshelf speaker system.

Size is important when selecting a speaker system. Don't try to stuff a large system into a room that won't accommodate it comfortably. The largest size that

the room will accommodate should be determined first. Whether you plan on a 2-channel or 4-channel hi-fi system can also influence this decision. Don't be misled. There is no direct relationship between the size of a speaker system and the quality of sound it produces.

Types of enclosures

The operating principle of the speaker enclosure is unimportant to the ear of the user. What you are looking for is a system that reproduces sound well, and not what kind of system is in the box. However, there are practical considerations. If your hi-fi system uses a low-power amplifier you cannot drive an inefficient acoustic-coupled speaker system. So while you should select a speaker system for its reproduction qualities, don't lose sight of the practical problems. The operating principle is important to the design engineer but it should not influence your final selection. This decision should be based on the quality of sound the speaker produces.

All the bookshelf speaker systems we examined fall into two basic categories—acoustic suspension or bass reflex. The bass reflex enclosure is a high-efficiency system with a bass response that tends to be peaky. This type of response produces what is often referred to as "boom". There are people that prefer a speaker system with a bass that booms, but it detracts from the reproduction accuracy. Not all bass-reflex systems have a boomy bass, but they are more prone to producing it. On the more positive side, the medium-efficiency of these systems suits low-power amplifiers rather well.

The acoustic-suspension speaker system is a low-efficiency system that has a smooth bass response. A smooth bass response produces a natural sounding bass, but the low efficiency requires driving this system with a medium- or high-power amplifier.

The basic design of the acoustic suspension enclosure is fixed. As a result, the majority of manufacturers of these systems refer to them as just that—acoustic suspension. The bass-reflex enclosure is different. The original patent for the bass-reflex enclosure covered many different variations, and manufacturers still introduce new ones periodically. The manufacturers of these systems have come up with many names for the bass-reflex enclosure. These include Center Excited Pipe, Tube Vented Reflex and Resistive Tunnel, to name just a few. Don't get confused. The basic characteristics of the bass-reflex system still apply.

OCTOBER 1975

Frequency response

The frequency response (sound output level vs. frequency with a constant-level drive signal) of a speaker system is important for determining the overall sound quality and the accuracy of reproduction. However, with the advent of graphic equalizers that alter the frequency response to the user's taste, it is possible to compensate, to a degree, for poor response. But this is like using Dolby to reduce tape noise. It works, but a faster tape speed is better.

When a speaker is placed in a listening room, the frequency response is no longer solely dependent upon the speaker system itself, but rather a combination of the frequency response of the speaker system and the room acoustics. The sound energy radiated from a speaker system is reflected off the various surfaces (walls, ceiling, floor, furniture, etc.) in the listening room. The intensity of these reflections vary with frequency and the type of reflective surfaces. The resulting reverberant field will reinforce the sound level at various frequencies. Figure 1 shows the reverberant room and anechoic chamber response of a typical speaker system.

To get a meaningful frequency-response measurement, we must isolate the speaker system from the effects of the listening room. A special chamber called an anechoic chamber, is used for this purpose.

This chamber has no reverberations. A frequency-response measurement made in this chamber represents the response of the speaker system alone. This response can not be obtained in a normal listening room environment (See Fig. 1). The anechoic chamber eliminates the need to define a

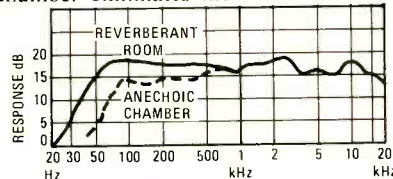


FIG. 1—ACOUSTICAL ENVIRONMENT changes frequency response measurement.

“typical listening room” and provides a common basis for making a comparative judgement.

(When we originally started working on this article we intended to present frequency response charts of every speaker system covered. Unfortunately, we were not able to make these measurements ourselves. Instead we asked the various speaker manufacturers to make them for us according to our specifications. We received this data for many of the speakers, but have decided not to publish it. As we ourselves did not make these measurements we have no way of determining which ones are faithful accurate measurements and which ones have been smoothed

out a bit to improve their appearance. As a result we felt the information we have might be misleading and have decided to omit from this article—Editor)

The second condition outlined in our questionnaire specified that a system called 1/3-octave averaging be used. Consider the frequency graphs shown in Figs. 2 and 3. The response in Fig. 3 appears to be vastly superior to that shown in Fig. 2. Yet both responses were taken from the same speaker system. The graph in Fig. 2 is a point-to-point plot that shows every glitch


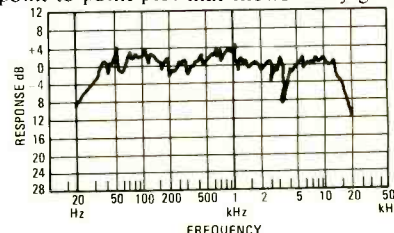



FIG. 2—POINT-TO-POINT response of typical speaker shows every glitch.

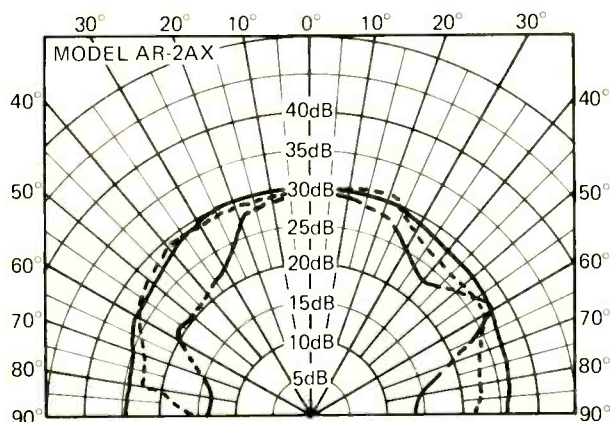in the response. However, it has been suggested that the human ear cannot distinguish between amplitude variations that are less than 1/3-octave wide. Figure 3 is the smoothed version of Fig. 2 where the output over each third of an octave has been averaged. This graph is thought to correspond more nearly to the actual sound that is heard. In any case, for our




— 1 kHz
- - - 7 kHz
- · - 15 kHz

ACOUSTIC
RESEARCH

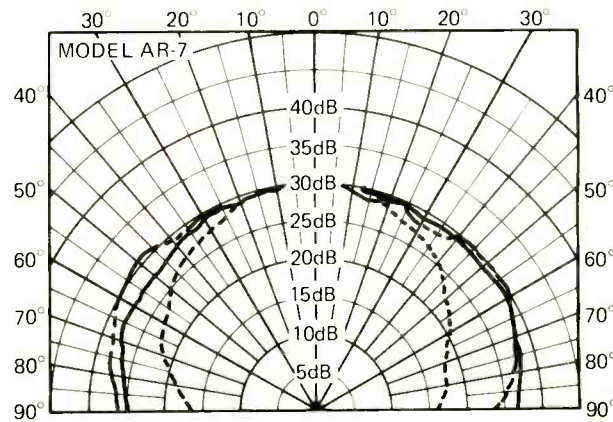


— 1 kHz
- - - 7 kHz
- · - 15 kHz

ACOUSTIC
RESEARCH

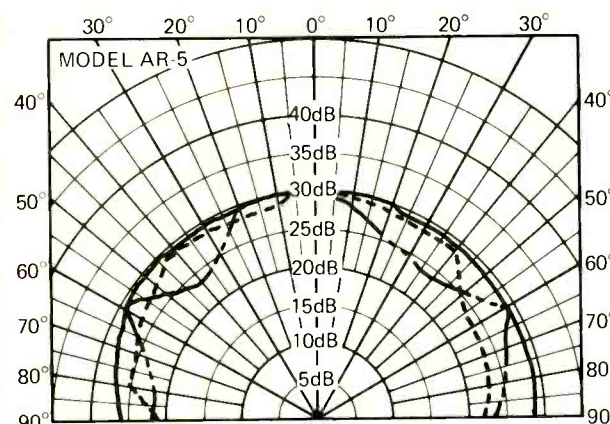

— 1 kHz
- - - 7 kHz
- · - 15 kHz

ACOUSTIC
RESEARCH

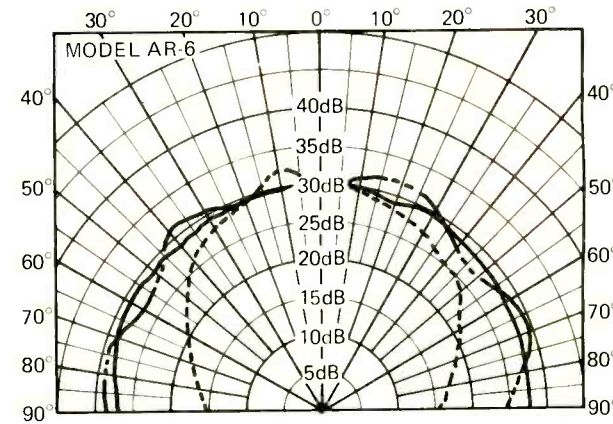

— 1 kHz
- - - 7 kHz
- · - 15 kHz

ACOUSTIC
RESEARCH

purposes, the graph in Fig. 3 is definitely easier to interpret. The other conditions

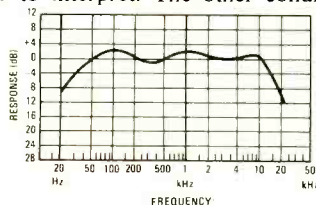


FIG. 3—SMOOTHED response of same speaker shown in Fig. 2 using $\frac{1}{3}$ -octave averaging.

outlined in the questionnaire specified that the frequency response measurement be made at a distance of 1 meter on-axis.

Analyzing a frequency response graph is not a difficult task provided you know what to look for and the graph is accurate to start with. Ideally, the graph should be ruler flat, extending from an infinitesimal fraction of a hertz above DC all the way out to infinity. Unfortunately, speaker systems aren't capable of producing this kind of response and we must accept what is available. Don't expect the response of a speaker system to even approach the response of a typical amplifier.

There are several points to look for in a frequency response graph. They are overall balance, smoothness of response, maximum bandwidth and minimum rates of roll-off. Smoothness of response and maxi-

mum bandwidth are self explanatory. Overall balance refers to the amplitude balance between the bass, mid-range and treble portions of the audio spectrum. In the common three-driver system, the woofer handles the frequencies below 600 Hz, the tweeter handles the frequencies above 5000 Hz and the mid-range driver handles the frequencies in the middle. The "crossover" frequencies vary from speaker system to speaker system and are approximate.


If the overall output of any one of the drivers is relatively lower than the output of the other drivers, problems will arise. For example, suppose the overall bass response of a speaker system is lower than the mid-range and treble response. A speaker system with this deficiency will reproduce bass notes, but not in the proper balance. As a result, the reproduced music will lack the natural "warmth" that the original music had.

A speaker system with this deficiency will also have a poor transient response in the decay (dying away) portion of a bass note. The attack portion of a bass note, which is composed of mid-range frequency components, will be good. The attack is emphasized by the poor transient response in the decay portion. As a result, the attack will be unnaturally "crisp". This unnatural crispness is sometimes praised as "tight" bass. Tight bass can be quite

impressive if you are not aware of the actual sound of the original bass note. It should be avoided however, as it detracts from the reproduction accuracy.


Fast rates of roll-off at the extreme ends of the frequency response graph can produce unnatural sound characteristics. It is not unknown for speaker systems to have a roll-off in the low-frequency end of the spectrum that starts very rapidly and approaches an 18-dB/octave rate. This produces a "heavy" bass effect that some people prefer. However, it again detracts from the reproduction accuracy and should be avoided. Fast rates of roll-off in the high-frequency end of the spectrum produce similar results.

Speaker systems are a compromise of all the above factors and more. Not one factor, however, is more important than any of the other factors. They all affect the reproduction accuracy and should be carefully considered. Don't choose a speaker system with a frequency response that is vastly superior in one or two areas and deficient in the remaining areas. It is better to choose a speaker system that is average in all the areas. This not only applies to frequency response but to the sum total of all the speaker specifications. (Unfortunately, not all manufacturer provide comparable measurements so you must listen to a speaker system to find out how it sounds. Editor) (turn to p. 48)

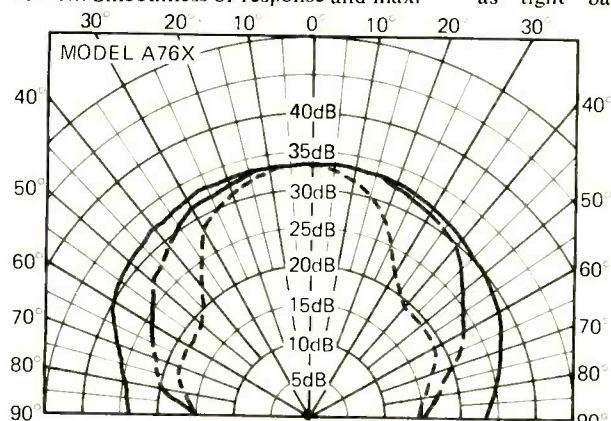


— 1 kHz
- - - 7 kHz
... 16 kHz

AUDIOANALYST

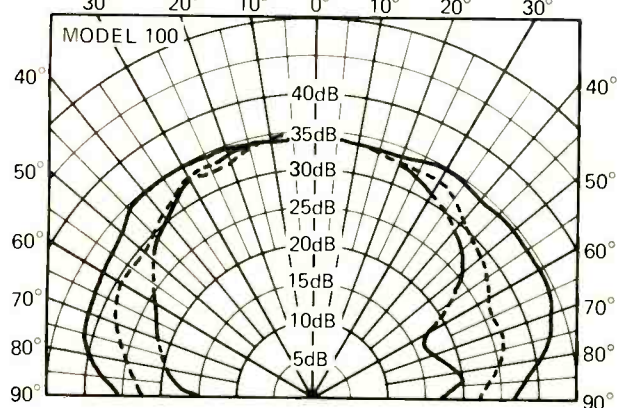


— 5 kHz
- - - 7 kHz
... 10 kHz

AVID

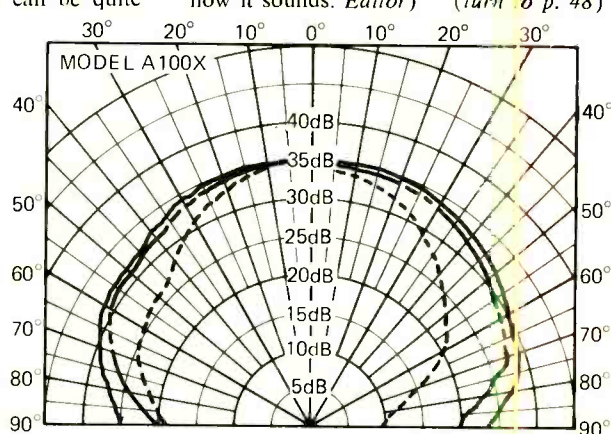

— 1 kHz
- - - 7 kHz
... 15 kHz

AUDIOANALYST

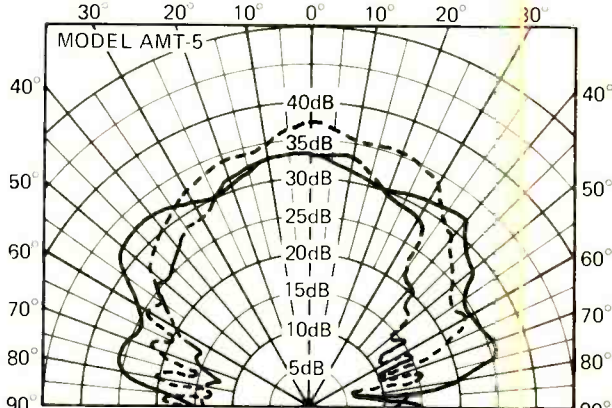


— 4 kHz
- - - 16 kHz
... 20 kHz

ESS

The better the training the better you'll

Send for
FREE
illustrated
career
guide



NTS guide
to careers in
Electronics

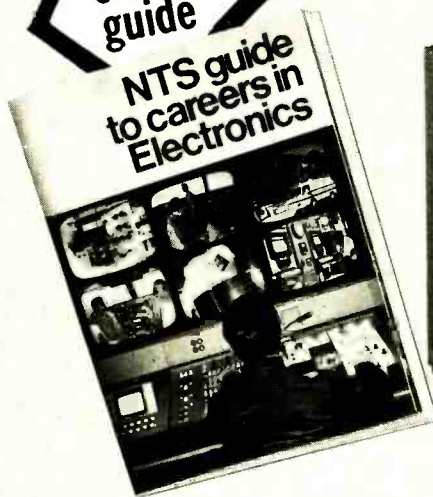


COMPU-TRAINER

IN-CIRCUIT TRANSISTOR TESTER


TROUBLESHOOTER
VOM

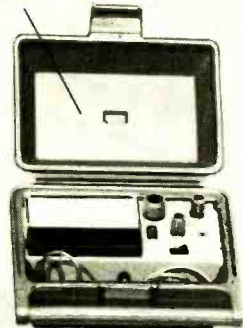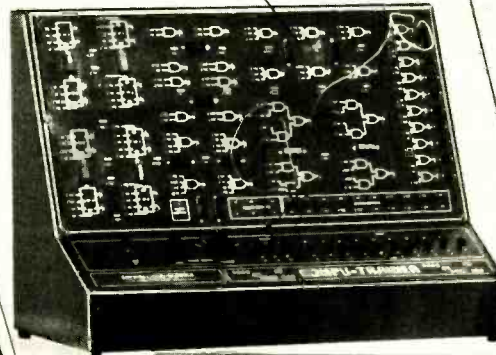

SOLID-STATE
OSCILLOSCOPE

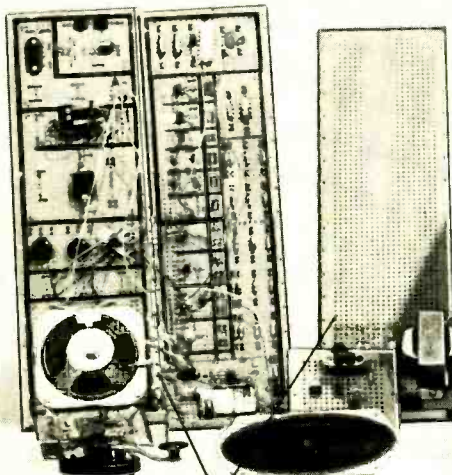

ELECTRO-LAB

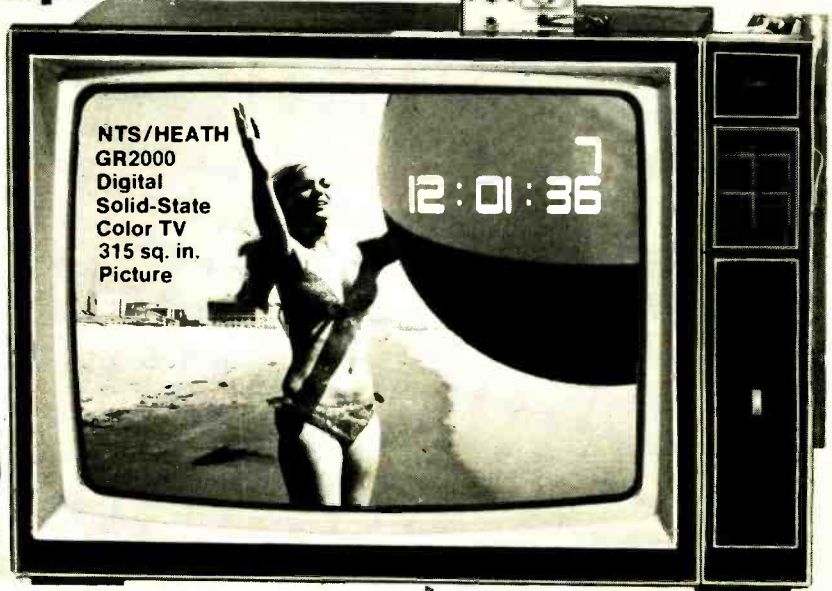

(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multi-meter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.


This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

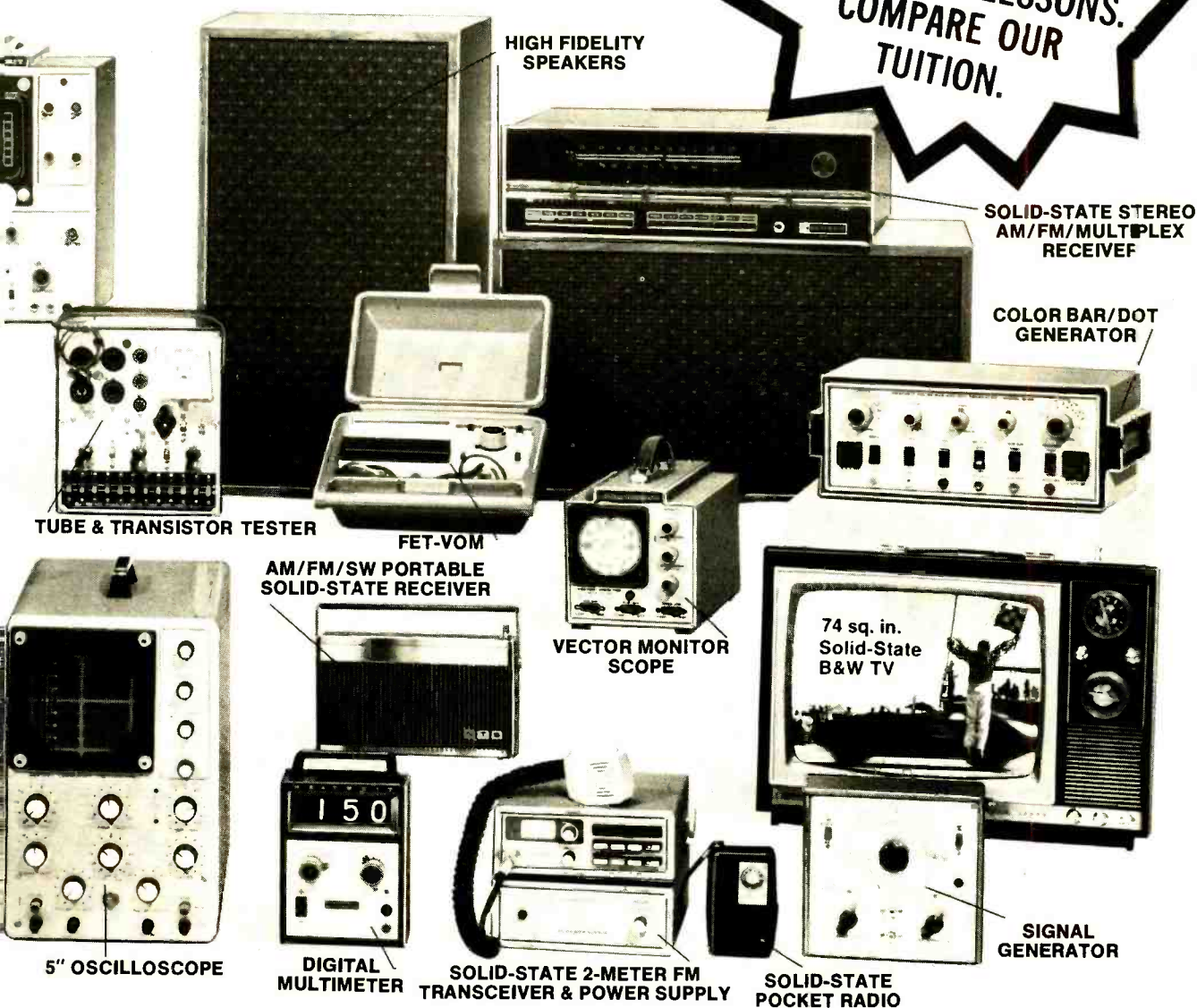COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS
4000 South Figueroa St., Los Angeles, Calif. 90037 Dept. 206-105
Please send FREE Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

☐ Color TV Servicing ☐ Electronics Technology
☐ B & W TV and Radio Servicing ☐ Computer Electronics
☐ Electronic Communications ☐ Basic Electronics
☐ FCC License Course ☐ Audio Electronics Servicing

NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service. _____

☐ Check if interested in G.I. Bill information.
☐ Check if interested ONLY in classroom training in Los Angeles.

OCTOBER 1975

Dispersion

This is one of the most important and misunderstood of all the specifications. It refers to the ability of a speaker system to radiate sound energy in different directions. Many mid- and high-frequency drivers have a tendency to beam the sound energy. This effect increases as the frequency increases. The dispersion graph illustrates this effect.

The dispersion graphs presented in this article are polar co-ordinate graphs. These graphs illustrate the dispersion pattern of

the speaker system. The rays (See Fig. 4.) emanating from the center point—this point represents the speaker system—are marked off in angular degrees with 0° representing on-axis. Circles or semi-circles represent the various relative amplitude levels.

To obtain a dispersion graph, a microphone is placed in front (on-axis) of the speaker system. The speaker system is driven with a constant-level constant-frequency signal. The microphone is rotated around the speaker system (keeping the microphone-speaker distance constant) and


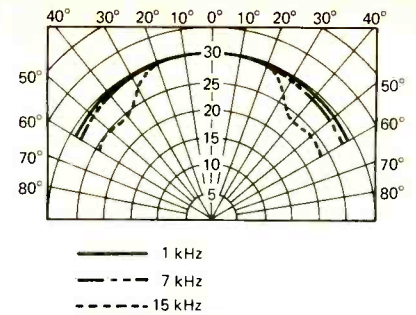
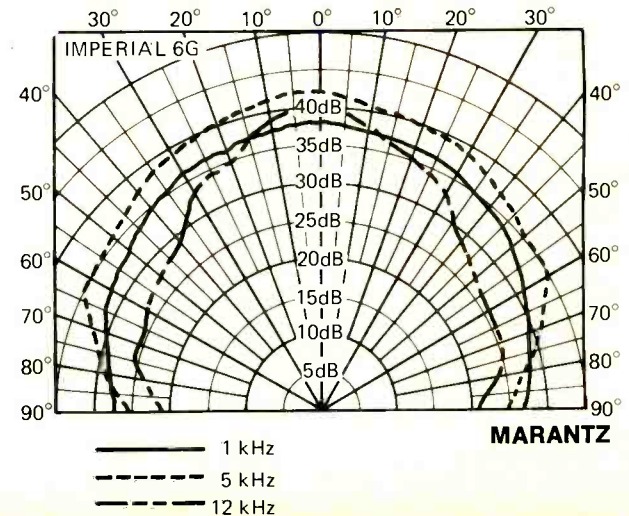
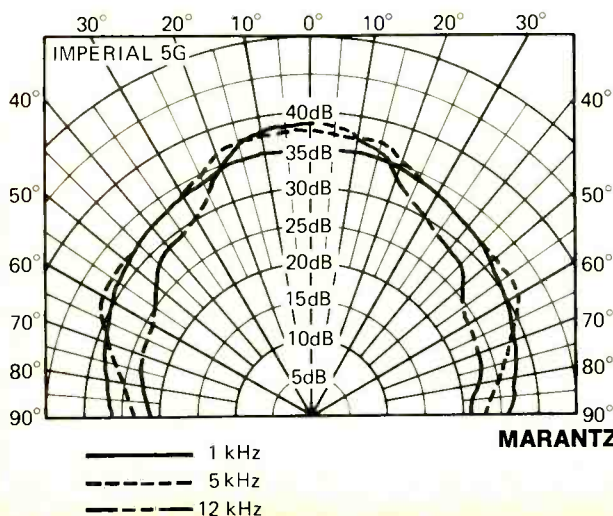
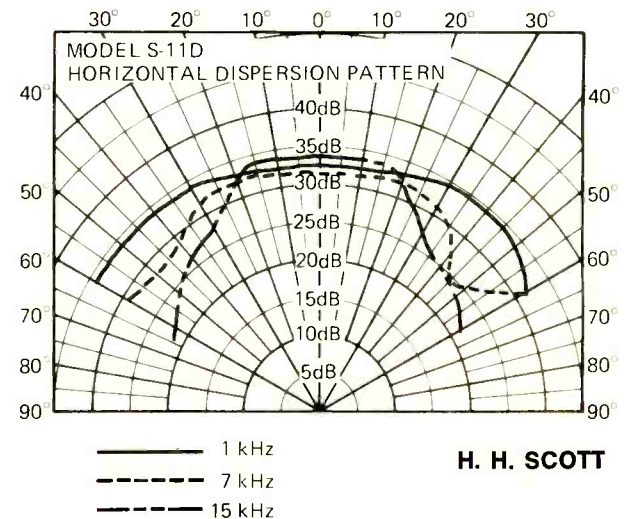
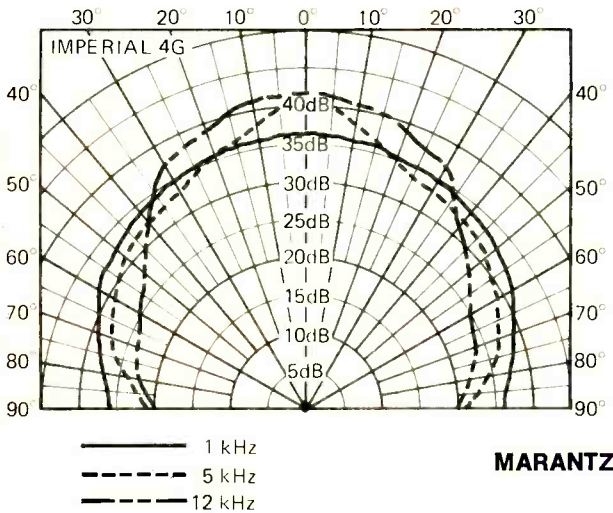
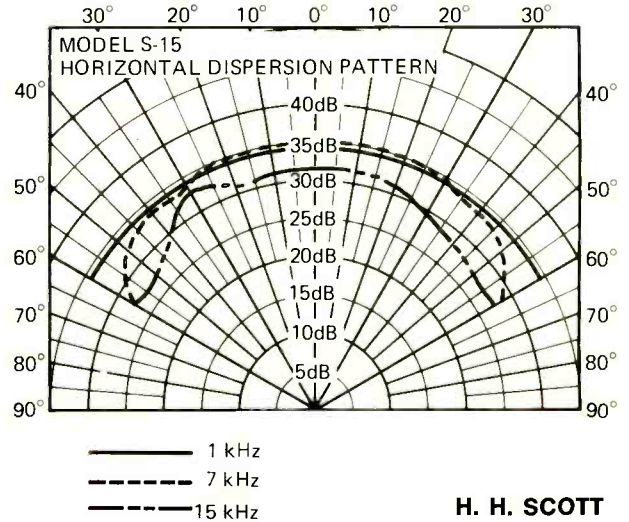


FIG. 4—DISPERSION GRAPH of a typical speaker system.

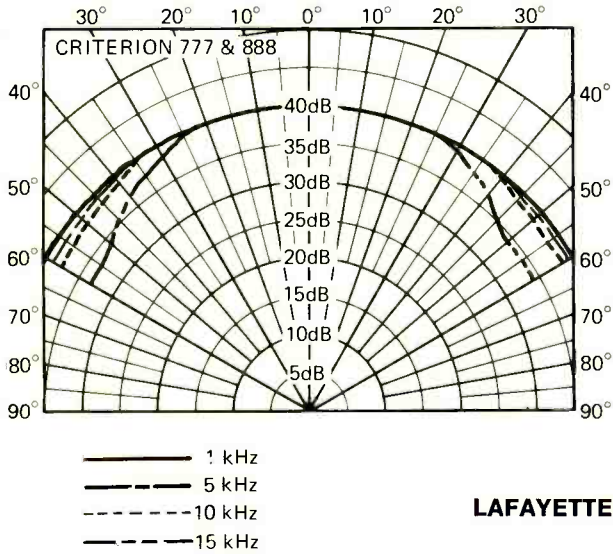







the output is plotted at different angles. At this point the microphone is returned to the front of the speaker and the frequency of the drive signal is changed. In most cases, the amplitude of the drive signal is held constant (usually 1 watt is the standard.) The procedure is then repeated. Of course, you will probably never have to make this measurement, but the explanation will help you understand the graph. The questionnaire specified that a minimum of three different frequencies be plotted.

As stated previously, dispersion is one

of the most important and misunderstood of all the speaker specifications. The off-axis high-frequency sounds of a speaker system with good dispersion will closely approximate the on-axis high-frequency sounds, but this is not the main advantage of good dispersion. When a speaker system is placed in a listening room, the sound reflections create a reverberant field. The majority of what is heard is reflected sound, not direct sound. As a result, we primarily hear the reflected off-axis sound that is radiated by the speaker system even if we are positioned directly on-axis.

Therefore, the sound quality is strongly influenced by the sound energy radiated in the other directions.

The dispersion graph goes hand-in-hand with the frequency response graph. A speaker system with a perfect on-axis frequency response but poor dispersion will sound dull and lacking in high-frequency sound. Concert halls have a sense of spaciousness, a sense of openness, created by the many sound reflections reaching the ear from different directions. Speakers with poor dispersion have a hard confined
(continued on page 88)

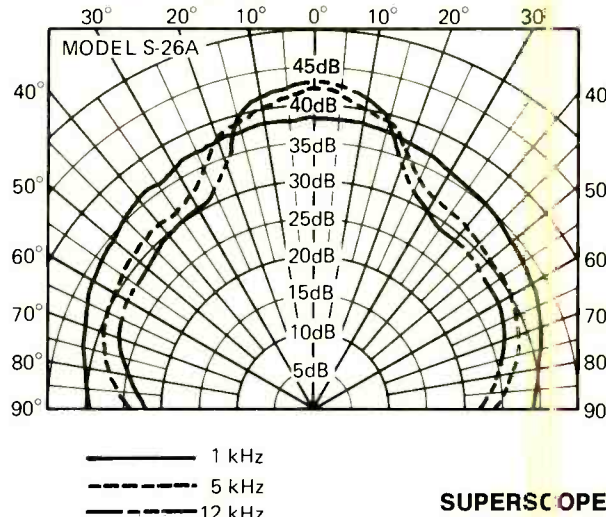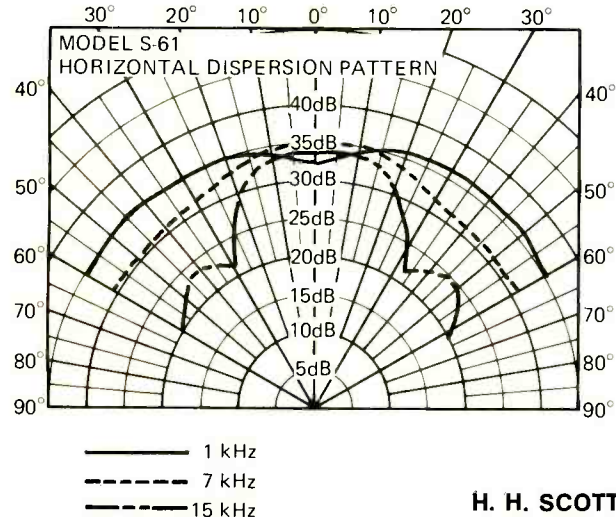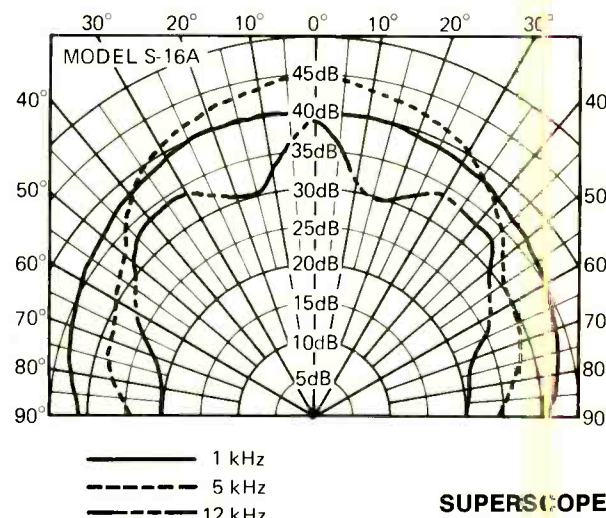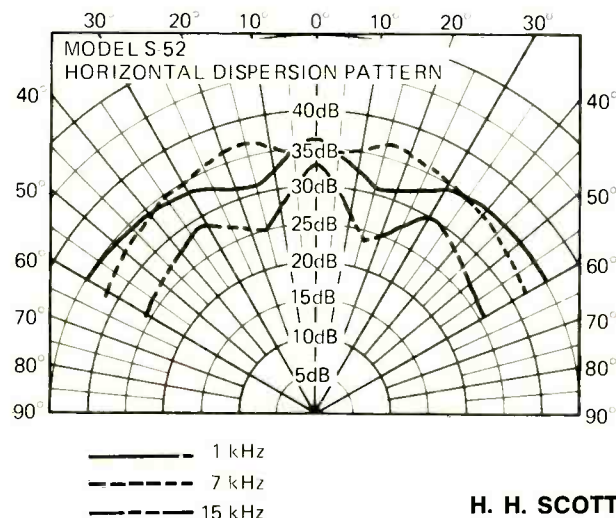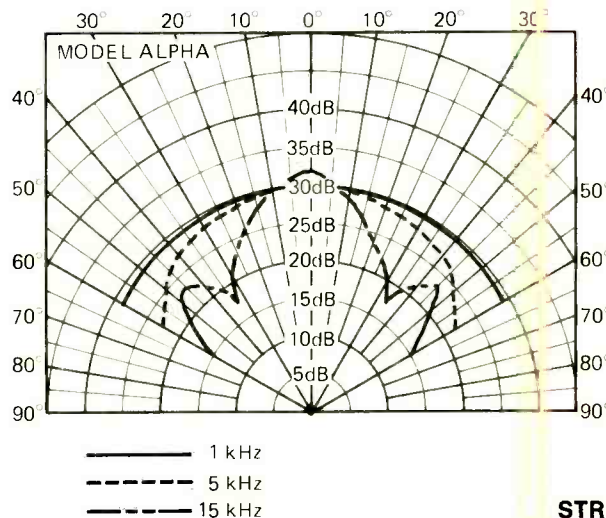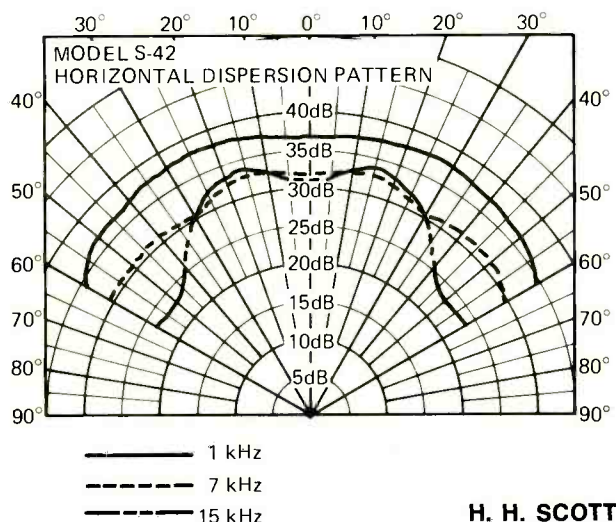

Super-Fi Testing ...the only way to go!

State-of-art audio equipment has progressed from high-fidelity to super-fidelity. Testing this modern equipment requires modern test gear. Here's the inside story on a new distortion analyzer.

the THD products. For the automatic nulling feature to work in a reasonable amount of time, the instrument must be tuned visually to approximately the frequency of the signal being measured. This type of instrument can reduce effective THD measurement time to between 15 seconds and 30 seconds, but as signal levels are changed (corresponding to different levels of power output), the operator must re-set the 100% reference point for each new measurement, at each new frequency—still a time consuming process.


A new laboratory distortion analyzer

performance of tuners and receivers (we use this in our **R-E** Equipment Reports). When we first saw the new model 1700A Distortion Measurement System, we were impressed by the fact that it contained a built-in low-distortion audio oscillator that would enable users to measure THD to around 0.002%. Our best audio oscillator at the time guaranteed a residual THD of 0.02%—or a whole order-of-magnitude worse. We were also impressed with the automatic nulling feature that reduced the nulling time to approximately five seconds per reading. But, we held off spending the approximately \$1500.00 that the instrument cost since we felt that our THD reading capability at the time was adequate and that the savings in time would not pay for the new investment for quite a while. More recently, we learned of a new option that could be purchased when buying with 1700A that changed our thinking completely. With option 003 (as the company calls it), not only does the

The block diagram illustrates the signal path of a radio receiver. The process begins with a **SIGNAL INPUT** (marked with + and -) entering a **BUFFER AMPLIFIER**. The output of the buffer amplifier is split: one path goes to an **OVERLOAD DETECTOR** (which includes an LED indicator), and the other path goes to a **FUNCTION SWITCH**. The **FUNCTION SWITCH** directs the signal to either a **NOTCH FILTER** or a **PHASE-NUL CONTROL**. The **NOTCH FILTER** also receives feedback from the **AMPLITUDE NULL CONTROL**. The signal then passes through a **PHASE-NUL CONTROL** block, which is also influenced by the **AMPLITUDE NULL CONTROL**. The output of the phase-null control goes to a **SUM-POINT BUFFER**, which then feeds into an **AMPLITUDE NULL CONTROL** block. The **AMPLITUDE NULL CONTROL** block has a feedback loop to the **NOTCH FILTER** and also feeds into a **DISTORTION SIGNAL AMPLIFIER**. The **DISTORTION SIGNAL AMPLIFIER** output goes to an **ATTENUATOR**, which then feeds back into the **FUNCTION SWITCH**. The **FUNCTION SWITCH** also directs the signal to an **AC METER** and a **TUNING DETECTOR**. The **TUNING DETECTOR** has a **LOW** and **HIGH** range selector and is connected to a **FILTERS** section. The **FILTERS** section contains a **400 Hz HIGHPASS** filter and an **80 kHz LOWPASS** filter. The output of the filters is connected to a switch that can route the signal to either the **OVERLOAD DETECTOR** or the **AMPLITUDE NULL CONTROL**.

RADIO-ELECTRONICS

FIG. 1—SOUND TECHNOLOGY MODEL 1700A distortion measurement system.

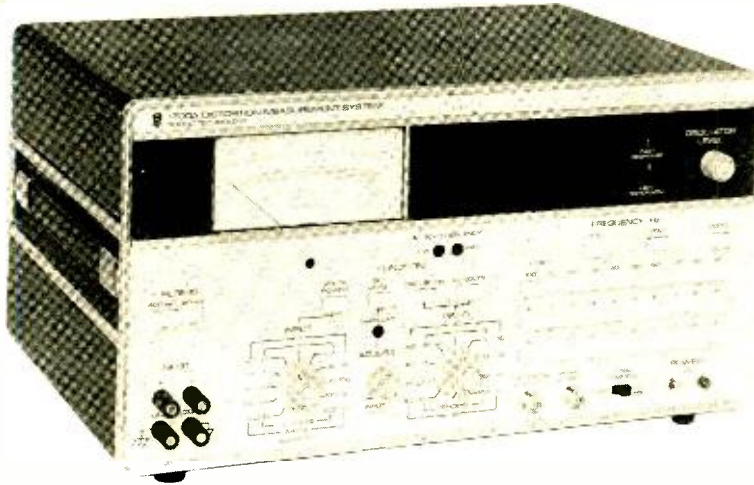

machine measure distortion at any power level and at any frequency from 10 Hz to 110 kHz, but in addition to the automatic nulling feature, there is now an automatic 100% reference level adjust—which means no more fussing with a knob every time you change the output level. You can make successive readings of distortion just about every five seconds, directly in % THD. We figured that this would enable us to measure about 500 readings per hour (allowing time for breath-catching) and that was enough to convince us to buy the unit.

A close-up view of the front panel of the 1700A is shown in Fig. 1. Here are some of the things you can do with it:

1. Use the .001% distortion audio oscillator for testing any audio equipment at frequencies from 10 Hz to 110 kHz.
2. Measure total harmonic distortion down to 0.002% in 5 seconds.
3. Measure AC voltages from 30 microvolts to 300 volts with 2% accuracy at full scale.
4. Measure voltage or signal-to-noise ratios with 100-dB dynamic range.
5. Measure power levels across an external 8-ohm load (the taut-band meter is calibrated in watts, as well as dB's, % and volts).
6. Apply 400 Hz and/or 80 kHz high and low-pass filters to eliminate hum and high-frequency noise components from all measurements.

The 1700A features a differential input, which means that signals can be applied from floating or balanced output sources. This is particularly useful when you are trying to measure noise or THD that is "down in the mud" and might otherwise be influenced by ground loops. It is also essential when trying to measure the output from strapped amplifiers (such as the new 4-channel units which, when strapped for 2-channel operation do not permit connection of a common ground between channels).

How it works

A block diagram of the 1700A Distortion Analyzer section is shown in Fig. 2. The signal to be measured is connected to the input of a buffer amplifier. This circuit has two outputs; a fixed output that may be connected to the AC voltmeter, and a

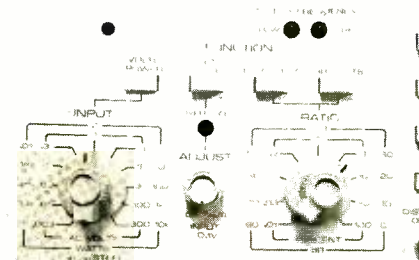


FIG. 3—AUTOMATIC LEVEL SET is accomplished by rotating the ADJUST knob to the AUTO position when making distortion measurements.

variable output (controlled by the ADJUST control on the front panel) that is connected to the notch filter. The voltmeter is an average reading type that measures the signal level selected by the appropriate function switch.

The overload detector monitors the variable output of the buffer amplifier. If an excessively high voltage is applied, the detector turns on the front panel overload indicator that remains illuminated until the user moves to an appropriately higher scale on the front panel input or ratio selector switches.

The notch filter is mechanically coupled to the audio oscillator FREQUENCY selector switches. It suppresses the fundamental frequency from the output of the buffer amplifier. The output of the notch filter is connected to the input of the distortion amplifier through a step attenuator controlled by the front panel RATIO switch. This attenuator adjusts signal level for the distortion amplifier for the various percentages of distortion or voltage ratio readings.

The amplitude null control and phase null control circuits supply the notch filter with its automatic nulling feature. Both circuits monitor the output of the distortion amplifier and feed control signals back to the notch filter. The sum-point buffer supplies reference signal to the tuning indicator and to the amplitude null control circuit.

The tuning indicator circuit, using frequency information from the notch filter, provides the user with a visual indication of the frequency being analyzed versus the input frequency. This circuit operates two lights on the front panel labeled HIGH and LOW. Normally, they will not become illuminated so long as the built-in audio oscillator is used with the analyzer, since the pre-set frequency of this oscillator is close enough in frequency to the tuned settings of the notch filter for the automatic nulling to work quickly and effectively. However, since it is possible to measure the distortion of equipment using other signal sources (such as a separate audio oscillator), the indicators help the operator to select the correct frequency selector buttons on the 1700A for quick and accurate automatic nulling under these conditions.

The switchable low-frequency and high-frequency filters (with cut-off frequencies of 400 Hz and 80 kHz respectively, and 18 dB-per-octave slopes) are connected to the output of the distortion amplifier. Thus, they may be selected only for distortion and dB or voltage ratio measurements.

The function switches select the circuit to be measured by the AC voltmeter. When the VOLTS/POWER switch is depressed, the meter monitors the output via a stepped attenuator from the buffer amplifier. When the SET-LEVEL switch is depressed, the meter monitors the variable output from the buffer amplifier. Depressing the DISTORTION switch connects the signal from the distortion amplifier via the low- and high-frequency filters (if they

(continued on page 77)

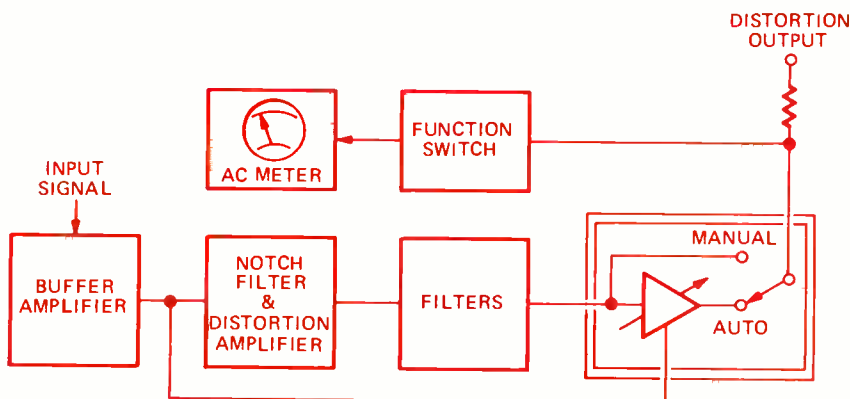


FIG. 4—AUTOMATIC LEVEL ADJUST feature on the model 1700A.

add-ons improve your Hi-Fi rig

Greater operational flexibility and improved performance are gained when these add-ons are incorporated into your component hi-fi rig.

by FRED PETRAS

NOT LONG AGO A "COMPLETE" AUDIO SYSTEM usually consisted of a tuner, a control amp, record player, one to three tape units and speakers. Such a system provided a fair measure of operational flexibility and control of a signal from electrical impulse to reproduced sound.

But audio technology kept improving, and the audiophile abreast of the advances found himself questing even greater flexibility from his rig, and greater capability to accommodate needs generated by the advancing technology.

Today's HI-FI rig not only includes the system mentioned above, but may easily contain as many—or more—*additional* units as in the basic system. Today's audio buff has far more flexibility of operation, far broader capability, and substantially more control of the signal from impulse to sound waves. In effect, many of today's HI-FI systems are mini "sound studios," a result of add-ons widely available to audio buffs, and not necessarily expensive.

The add-ons are in effect, comparable to accessories available to car buffs, but far more functional. They can be regarded as "creative" additions to a HI-FI rig, that make it possible for the enthusiast to be more deeply involved with his equipment and to tailor the sound to his desires . . . with considerable ease and convenience. They can also improve the function and quality of the system. Essentially, the accessories we'll discuss can be regarded as practical, professional devices that en-

hance the pleasure potential of your HI-FI outfit. Why not add some to yours?

Equalizers

One of the most versatile add-ons is the equalizer. It is a multi-function device that helps "tune" the listening room for optimum sound/acoustic qualities; helps change the characteristics of a record by enhancing the music in favor of a vocalist—or vice-versa, change voice characteristics and change musical sounds in other ways; adjusts reproduction of 78 rpm shellac records so they sound as they were meant to; cuts back low frequency response to eliminate hum; helps balance the response of some cartridge recordings so they sound better in the home and does the same for other tape recordings whose response is non-linear; improves broadcasts from radio stations that effect rolloffs at both ends of the sound spectrum; compensates for the boosted highs of Dolbyized tapes; enables the user to sometimes improve the response characteristics of phono cartridges and microphones; and

adjusts the response characteristics of speaker systems to "color" their sound, or to eliminate "coloration."

The practical applications mentioned are obvious; an equalizer enables the buff to create personalized sound reproduction, to satisfy individual preference or specific aural needs and/or sophistication. But there's more . . . an equalizer can be a "fun" device, permitting you to alter sounds to a point of non-recognition, to do zany things to sound just for laughs.

There are equalizers in at least eleven nationally-distributed brands: Altec, BSR, Burwen, Custom Designs, JVC, McIntosh, Quintessence, Realistic, SAE, Soundcraftsmen, and Southwest Technical. They fit slim as well as fat budgets, namely \$69.50 (Realistic) to \$1095 (Burwen). They permit sound alteration in at least four bands, and as many as 24, in a range of plus/minus 12 to 16 dB, and in one case plus 24, minus 12 dB. Their total harmonic distortion is minimal—from 0.001 to 0.5 per cent, and signal/noise ratio maximal—65 to 100 dB. Their size and shape are typical of most audio components, and they can




RUSSOUND MODEL TMS-1W tape recorder selector switch.



BURWEN MODEL DNF 1201 dynamic noise filter.



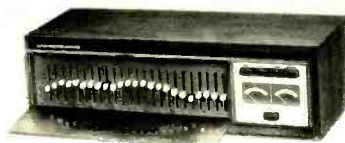RUSSOUND MODEL MP-2 speaker and amplifier switch control.



BSR MODEL FEW-3 frequency equalizer.



PIONEER MODEL SF-850 electronic crossover network.



SCOTT INSTRUMENTS MODEL 451C sound level meter.

be plugged into most any HI-FI rig just like any other component.

Noise reduction systems

Today's audio buff is no longer at the mercy of noise. He can reduce or switch out the annoying hiss and other noises associated with recorded tapes and phono records as well as radio broadcasts—with virtually no effect on the music being reproduced. He can do this through at least five different approaches.

The five approaches break down into two basic types—closed-end and open-end. Within the closed-end group—covering equipment from Dolby and Dolby licensees, JVC, and some from dbx—*professional* noise-reduction units are used in program production at recording studios (and in some cases, radio stations) to code the program material. At the other end, the home *consumer type* noise-reduction units are used to decode the program material for playback. Included in the consumer types are models that permit the home tape recordist to perform both the coding and decoding. Overall recordings (and broadcasts) processed through Dolby equipment benefit by up to 10 dB less noise; under the JVC ANRS approach there is a 5 to 10 dB improvement; and using certain dbx brand equipment, the improvement is as high as a claimed 30 dB. Prices for home type Dolby noise-reduction equipment start at \$89.95 and range to \$400 for a quad model. The JVC unit is \$150. The dbx models sell for \$259 to \$379, the latter a combination two-channel/four-channel instrument.

NOTE: The three record/playback noise reduction systems are incompatible; recordings made under each approach must be played back within that approach for optimum results.

The open-end group covers units from Burwen, Phase Linear and some from dbx. These are playback-only models and are used to reduce noise in *existing* program materials such as records, tapes and radio broadcasts, in a range of 6 to 20 dB. The model from Burwen is priced at \$299. The Phase Linear unit, a preamp containing a noise reduction circuit called an "Auto-



SONY MODEL SB-200 sound-on-sound and echo adaptor and SB-300 tape recorder selector.



SONY MODEL PBR-400 parabolic reflector.

Correlator" is \$599. One dbx unit, Model 117, is \$159, the other, Model 119, is \$189. On the way is a separate "Auto-Correlator" to be priced around \$300.


Each system—closed- and open-ended—uses a proprietary means to achieve noise reduction; it is beyond the scope of this article to delineate the differences. If you decide to buy such equipment, be sure to determine the differences, to most effectively fill your listening needs.

Other add-ons


In record/tape production and in radio broadcasting, it is necessary to compress the dynamic range (ratio between soft and loud passages) of the program material in order not to overload the equipment. Consequently you do not hear the program material in its optimum form, even though it may be quite satisfying to most listeners. For the audio buff seeking the last nuance of reproduction, add-ons are the answer. One such unit is the Robins "Stereo Dynamic Sound Enhancer," priced at \$30. It "expands" the compressed dynamic range of recordings and broadcasts up to 8 dB, to come that much closer to the original sound. Expansion of up to 20 dB is claimed for the dbx Model 117, a noise reduction unit (mentioned earlier) which incorporates compression/expansion in its particular approach to reducing noise.

Radio stations have found that by Dolby processing their FM broadcasts they can triple their effective broadcast range. Hence, many stations have adopted this procedure and more are doing so. And, of course, astute equipment manufacturers have been sizing up the situation and have been getting into the act with tuners and receivers containing Dolby circuitry.

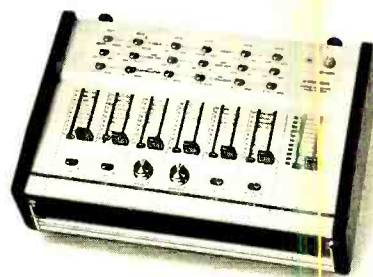Since Dolby broadcasting began back in 1971, there has been a change in the pre-emphasis requirement, from 75 micro-



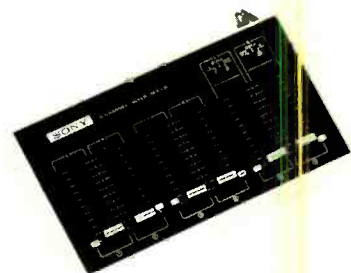PIONEER MODEL MA-62 6-channel mixing amplifier.



SONY MODEL MX-8 passive 6-channel mic/line mixer.

seconds to 25 microseconds. But leave it to smart equipment manufacturers to see a problem, then attempt to solve it. Now available to owners of early Dolbyized tuners and receivers are add-ons that permit dual operation; they convert a 75 microsecond unit to 25 microsecond operation, at a mere \$12.95 investment in a device from Switchcraft. The widget also converts separate Dolby units for optimum results in listening to or taping FM broadcasts.

The AM section of tuners and receivers has been the subject of many blasts at the industry for not improving AM broadcasting and/or reception. The industry has bypassed the complaints, or promised constructive action in the future, a future which has already encompassed many years. But one company has come to the rescue. It is Dymek, with its Model DA3 shielded ferrite antenna system which greatly increases the sensitivity of a receiver's AM section, AM tuner, or AM section of an AM/FM tuner. It also reduces electrical interference and nulls out interfering signals through tilting and tuning. The indoor device comes in a space-age configuration that causes people to ask "What IS it?" The price, \$155.00.

Some audio buffs like to experiment to obtain "super" sound. In addition to using an equalizer, one way is through checking/comparing phono cartridges. The most effective way is on an A/B basis—side by side comparisons. This is difficult unless you have two turntables. But owning two turntables is not always the answer; your preamp, amplifier or receiver is most likely geared to accommodate one turntable with a magnetic cartridge and one with a ceramic cartridge—permitting comparisons of "apples with oranges," but no "apples with apples," so to speak. If you're into cartridge checkouts, it's most likely at the level of magnetic models. To the rescue comes All-Test Devices Corp. with its

Bell & Howell Schools invites you to **BREAK INTO 4-C**

Pick up new professional skills in this exciting field as you build Bell & Howell's new quadraphonic audio center. It's the very first learn-at-home program of its kind!



You've probably heard a lot about 4-channel sound by now. It's the most talked about and impressive technical advancement in sound in years. Separately recorded channels literally wrap a room in sound for a totally new listening experience.

And the excitement doesn't stop there. Thanks to Bell & Howell Schools' brand new learning program, now you can explore quad sound for yourself—from the inside out—and master the technology behind this important advancement right in your own home!

It's your opportunity to break away from the everyday routine and learn new occupational skills that could lead you in exciting new directions. Mail the attached card, postage free, to get the facts today!

Take hold of opportunity with both hands now!

The world around you is changing every day. Forging ahead. The man who keeps pace is the man who continues to learn and grow. He's in the mainstream of life. Interested in what's going on. And he's much more interesting, too.

Bell & Howell Schools' new 4-channel audio program was designed to help you learn and grow. To put you in the mainstream of audio electronics technology. Where you can delve into fascinating electronics principles. Solve challenging problems and get actual hands-on, build-it-yourself experience.

And where you can acquire a sense of satisfaction and accomplishment you may not currently be getting.

Completely different from the typical kind of school you grew up with.

Learning all about quad sound with Bell & Howell Schools is a lot more interesting and convenient than "school" used to be. First of all, we know you can't afford to quit your job. So we set up a program that lets you work at home in your spare time.

There are no classes to attend. No dry lectures to sit through. Everything comes to you in the mail. Lesson by lesson. Exciting package after package. And you work at a flexible pace in the relaxed atmosphere of your workshop—or wherever your favorite spot may be.

Sure, books are important. But they're only the beginning.

With this fascinating learn-at-home program, you do a lot more than just read about electronics. You'll conduct dozens of experiments . . . build your own laboratory equipment for testing out electronics principles . . . and also as part of this program you put together a 4-channel amplifier and FM/FM stereo tuner as you delve into advanced audio technology.



We try to make learning so interesting you look forward to receiving each new lesson. And enthusiastically dive into each new project we send you.

We'll start you off on the right foot.

You may be thinking, "I don't have any training in electronics . . . I might be getting in over my head."

Well, you can stop worrying about that. You don't need previous experience. You'll begin with the basics and acquire a thorough understanding of the fundamentals before moving on.

And remember, it's not just reading. With your very first lesson you get our LAB STARTER KIT, consisting of a simple voltmeter and electronics "bread-board" you can experiment with right away.

Of course, if you're already into electronics, you might be thinking, "I already know the basics . . . I want to get into the advanced stuff right away!"

For you there's an advanced standing program that lets you skip the beginning lessons.

Next you build the exclusive Electro-Lab® electronics training system.

Once you've mastered the basics, we'll send you everything you need to put together these three important testing instruments:

The design console. You use it to set up and examine various kinds of circuits. It's completely modular . . . no soldering!

The digital multimeter. Use it to measure voltage, current and resistance. Displays data accurately in big, clear numbers—just like on a digital clock.

The solid-state "triggered-sweep" oscilloscope. Use it to analyze modern,

HANNEL AUDIO!



state-of-the-art integrated circuits. Triggered-sweep feature locks in signals for easier observation.

These three superb testing instruments are the basis of your own home electronics laboratory. You'll use them throughout the program as you move into more advanced electronics principles and work into audio technology.

Bell & Howell's high performance 4-channel audio center you actually build and experiment with yourself!

You need practical experience with high caliber equipment to develop professional skills and understand the ins and outs of today's audio technology.

So we came up with a system that Bell & Howell is proud to have its name on:

First, there's the sophisticated outstanding 4-channel amplifier with SQ full-logic decoding and front to back separation.



35 watts per channel—Min. RMS into 8 ohms at less than 0.25% total harmonic distortion from 20-20,000 Hz, all channels fully driven.

As you build and experiment with this remarkable piece of equipment, you'll learn about matrix 4-channel and discrete—including CD-4 when processed through an external demodulator.

And with it you'll have the advanced circuitry you need to get into signal tracing low level circuits . . . troubleshooting high power amplifier stages . . . and checking the operation of tone control circuits.

Next, the advanced FM-FM stereo tuner. As you build this superb stereo tuner, you'll come to fully understand how the advanced, "state-of-the-art" features lead to such high performance. You'll learn about all solid-state construction, FET front end for superior sensitivity, crystal IF filters for wide bandwidth and the superior multiplex circuit that produces such excellent stereo separation.

A wealth of knowledge in digestible chunks.

O.K.! So now you might be thinking, "It sounds really interesting . . . but kind of complicated." And you're right. But that is why we use the "hands on" teaching approach.

We've taken all the material and broken it down into short, simple-to-grasp lessons, so you can master one thing at a time before moving on. And we take you through it step by step. From the basics to advanced theory to

applied audio technology. So you actually have an easier time with it.

Special learning opportunities give you extra help and attention.

In case you do run into a problem or two, we're ready to give you more help and personal attention than you'd expect from most learn-at-home programs.

For example, many home study schools ask you to mail in your questions. Bell & Howell Schools gives you a toll-free number to call for answers you need right away.

Few home study schools offer personal contact with instructors. Bell & Howell Schools organizes "help sessions" in 50 major cities at various times during the year—where you can discuss problems with fellow students and instructors in person.

And when you're done, you'll know a lot more than just 4-channel sound!

You'll have covered the complete spectrum of electronics principles, leading to a full understanding of audio technology.

And while no school can promise you a job or income opportunity, you will have occupational skills necessary to become a full-service technician. With the ability to work on the entire range of audio equipment. Such as tape recorders, cassette players, FM antennas and commercial sound systems. You'll know audio technology from the inside out. And you'll be proud of it.

Plus you will have the basic skills that apply to the entire electronics field, including television technology and repair.

For more details, mail card today!

Here's your chance to break out of the mold. And break into 4-channel audio with Bell & Howell Schools. Why not look into it today. Mail the attached postage-paid card now.

Taken for vocational purposes, this program is approved by the state approval agency for Veterans' Benefits.

Wood cabinets available at extra cost.

"Electro-Lab®" is a registered trademark of the Bell & Howell Company

If card has been removed, write:

An Electronics Home Study School
DEVRY INSTITUTE OF TECHNOLOGY

766 R

ONE OF THE
BELL & HOWELL SCHOOLS
4141 Belmont, Chicago, Illinois 60641

Model ATD-25 "Laboratory Reference Phono-Preamplifier" priced at \$150. The add-on was designed to amplify magnetic phono cartridge signals to a level that will drive the high level inputs of any stereo preamplifier, integrated amplifier or receiver. The unit has less than 0.01 per cent 1M distortion, thus giving you two similar sources for comparing magnetic cartridges. (NOTE: There is a caveat in this; All-Test claims that the input involving the ATD-25 will actually be superior to the existing magnetic input. The degree to which it will be superior will relate to the basic quality/price of the equipment; there will be more of a difference if the existing equipment is low priced.)

If cartridge checkouts are not your bag, the ATD-25 will stand on its own original *raison d'être*—as a second, high quality magnetic phono facility that may be superior to an existing one.

Many stereo buffs are not convinced that four-channel sound is a viable entity yet. They are curious however, but not curious enough to make a grand investment in the growing medium. They have an "out" in the form of add-ons that will give them a taste of quadraphonics that may be sufficient to convince them they can live without quad sound, or to convince them they can't, and that they *should* make the grand investment. The add-ons are best described as "quad adaptors." They are low-priced passive devices that create a four-channel effect from stereo records, tapes or broadcasts in conjunction with a second pair of speaker systems. The instruments are priced as little as \$6.95 (Robins) and range up to \$40 in the Utah line. BSR markets a "package" of a quad adaptor and a pair of speaker systems for \$60.

(If you should succumb to the benefits of quad sound, you would be put in the position of evaluating your present equipment *vis-a-vis* the true-quad add-on equipment route, or starting off with a new quad receiver, amplifier or tape deck as your prime sound source. In either case, the subject is too involved to spell out within the scope of this article.)

The Hi-Fi buffs using tape decks in their rigs have an excellent potential for expressing their creativity and expanding the capability of their equipment through add-on mixers. With such equipment they can produce special effects using multiple microphone and other sound sources, to mix and blend the sounds in a variety of ways to suit their fancy. The consumer type mixers generally have six channels of input and two channels of output for the mixed signal to be fed into the stereo tape recorder. However, if you have four-channel equipment, TEAC has a model with six channels in, four out, or if you wish, one, two or three out. Available from Sony, Pioneer and TEAC, the mixers range from \$59.95 for a passive model, up to \$250 for an amplified type. Two models are twin-powered, operating off house current and/or batteries.

Related to the mixers is a sound-on-sound and echo adaptor from Sony, Model SB-200. It is an inexpensive (\$39.95) way to add studio-type special effects in home recordings. Echo can be created, and its intensity regulated, on any three-head tape recorder. The sound-on-sound capability allows multiple source recordings to be



ALL-TEST DEVICES laboratory reference phono preamplifier.



SAE stereo octave equalizer.



JVC MODEL NR-1020 noise reduction unit.



BSR METROTEC sound level meter.

built up with perfect synchronization on any two or three-head tape deck with the ability to record each channel independently.

Another aid to tape recordists is a parabolic reflector from Sony, Model PBR-400, priced at \$79.95. The attachment was designed to pick up high quality sound from a distance. Depending on climatic conditions and surroundings, it has an effective recording range of several hundred yards. It can be used in a variety of ways, including field research recording such as capturing the sounds of birds, recording live concerts, speeches, sporting events, etc. The PBR-400 will improve the sound sensitivity of most omni-directional microphones by 10 to 20 dB over rated sensitivity, the company claims. The reflector is hand operable or can be mounted on a tripod.

A final aid to tape recordists—those into

tape in a big way—are multi-tape recorder switches. These enable the user to interconnect up to three different tape decks so that all or any can record or play at the same time in any combination, operating through a single preamp, amplifier, receiver or mixer. They are ideal for dubbing from one format to one or two others, or recording in all three basic formats simultaneously—as well as for other uses. Typical are models from Russound, the TMS-1W at \$22.95 and \$32.95, depending on finish, and Sony, Model SB-300 at \$44.95.

Audiophiles wanting to expand the playing capability of their rigs beyond just the listening room can do so with add-ons. While many amplifiers and receivers permit connection of an additional pair of speaker systems, you may want to operate speakers in three or four different locations. At your aid is Russound, with its MP-2 speaker amplifier control switch priced at \$69.95. The control does the following: Selects either of two amplifier sources and directs the output of either to any one, two, three or four pairs of stereo speakers from a central location. Changes the volume of one or turns on or off completely without affecting the sound level of the others. Connects any combination of high and low efficiency speakers with any mix of impedances. Maintains proper loading of your amplifier regardless of the number of speakers in use or their volume control settings. Other, less elaborate speaker or speaker/amplifier switching devices are also obtainable from Switchcraft, Audiotex, and Lafayette Radio, as well as Russound. They are priced from \$11 to \$82.50. Russound also has a "super-deluxe" switching center at \$250.00.

The speaker switching boxes also permit the HI-FI "nut" or sound perfectionist to play different kinds of music with different types of speakers—all at the touch of a switch.

Audio buffs experimenting or "playing around" with speaker systems have a handy widget in the form of sound level meters, available from BSR at \$60 and from Scott Instruments at \$98. The meters, with a range of 60 to 116 dB and 45 to 130 dB, respectively, permit checks of speaker systems to help balance their outputs, or, in conjunction with an equalizer, enable the user to obtain precise flat reproduction and accurately tune the speakers to a room setting. They also permit measurements of ambient and background noise, as well as other signals of interest. The BSR model also acts as a quality microphone.

A final add-on that can assure optimum performance of a HI-FI system is the "Turntable Foundation" by Discwasher. The foundation is just that—a solid base on which to place a turntable. Made of thick marble and mounted on eight damping feet, the device filters out vibrations and rumble that can affect the performance of the turntable. If your player is sensitive to feedback generated by subtle or overt vibrations in the listening room, the Discwasher foundation may be just what the doctor ordered. Price, \$40.

Maintenance and prevention

Radio-Electronics readers are familiar
(continued on page 78)

You enjoyed the **TIMESAVING** advantages of the previous models of the Castle Subber® analyst . . . **NOW** you will want to move up to this superior, redesigned model . . . our best yet!

SUBBER®

Mark IV-CUV

*UHF-VHF tuner
and i-f analyst*

net \$64.95



If you haven't joined the ranks of thousands of professional technicians using this **TIMESAVING** instrument . . . **NOW** is your opportunity to own the latest model boasting these improved features:

- TUNES ALL VHF & UHF CHANNELS. Use where prime signals are on either VHF or UHF . . . or both.
- ELECTRONIC FINE TUNING. Smooth, exact tuning ensures precise setting for ease in testing color receivers.
- DUAL 40MHz IF OUTPUT JACKS. Select Hi or Lo impedance output for best coupling match to circuit being substituted . . . tube or transistor.
- BATTERY CONDITION INDICATOR. IC comparator driven LED shows when inbuilt 9v transistor batteries require replacement.

The Mark IV-CUV tunes all 82 VHF & UHF channels for substitution tests of the tuners and entire i-f system of any 40MHz TV receiver. Permits signal injection after the agc controlled stages for the high speed agc system analyzing procedure invented by Castle . . . the first practical method for analyzing agc system defects without confusion.

Mark IV-C


The Mark IV-C tunes all 12 VHF channels for substitution injection tests of the VHF tuner, UHF tuner and entire i-f system of any 40MHz TV receiver.

- ELECTRONIC FINE TUNING. Battery & 120-vac line powered,
- DUAL 40MHz IF OUTPUT JACKS.
- BATTERY CONDITION INDICATOR.

net \$54.95



Made in USA.

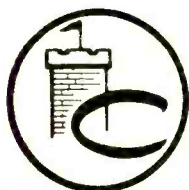


See your stocking distributor . . . or write for more details and complete specifications.

CASTLE TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago, Illinois 60645
Circle 83 on reader service card

Phone: (312) 561-6354

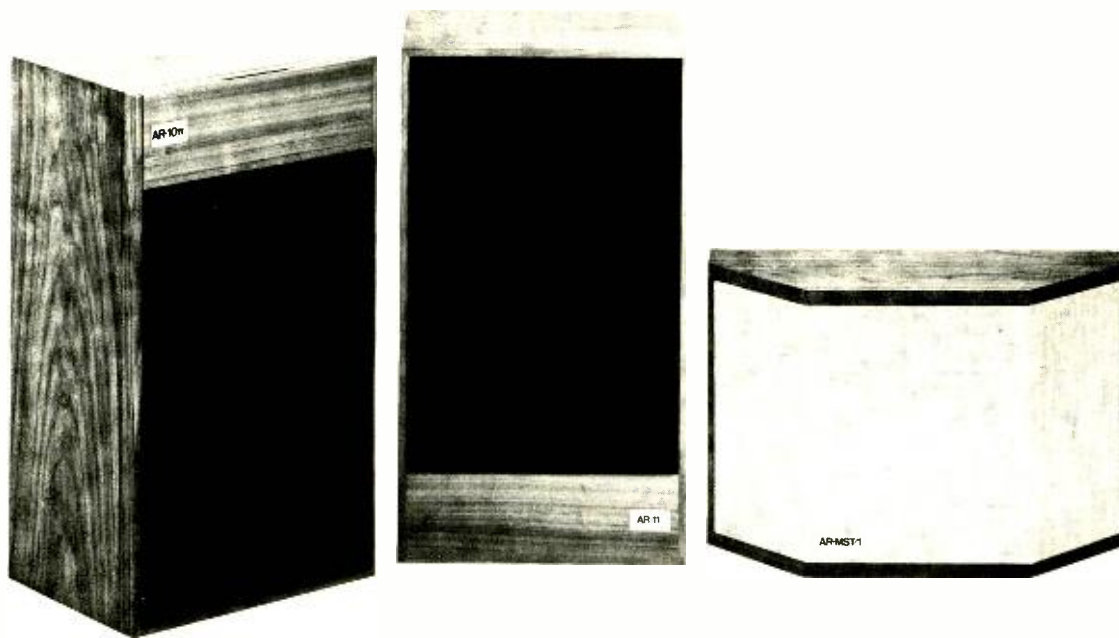Introducing A new family of loudspeakers from Acoustic Research



AR-10 π

The AR-10 π is the most accurate musical reproducer that Acoustic Research has ever made. It shares the characteristics of AR's previous speaker systems, smoothness of response, uniform dispersion, and low distortion. A significant additional feature of the AR-10 π is its ability to deliver uniform flat energy response in most listening rooms.

Further, the designed-in performance of the AR-10 π is preserved, whether the speaker is positioned against a wall, in a corner, or even in the middle of a room. Setting a single switch, called the 'Woofer Environmental Control', will ensure the correct level of bass energy for any of these positions. It is not possible to do this accurately with conventional loudspeaker designs or equalization techniques.

AR-11

The performance, drivers, and crossover of the AR-11 are identical to those of the AR-10 π , except that the AR-11 does not incorporate a Woofer Environmental Control and the associated crossover components.

The AR-11 is designed for optimum performance when placed against a wall, as in the conventional bookshelf position, or slightly away from two adjoining room surfaces.

Both the AR-10 π and the AR-11 use a 12 inch acoustic suspension woofer, a 1 1/2 inch dome midrange, and a newly designed 3/4 inch dome highrange.

AR-MST/1

The AR Miniature Studio Transducer offers at moderate cost the flat energy response of AR's other new speaker systems, together with the high power-handling capability required in many professional applications. Along with the AR-MST/1's small size, light weight, and shallow depth, these characteristics make the speaker especially appropriate for the monitoring of remote-location recordings as well as the accurate reproduction of music in the home, even at relatively high sound levels.

Guarantee

The workmanship and performance of all AR speaker systems are guaranteed for five years.

A complete description of the new family of AR speakers is available free. Mail us the coupon today.

Acoustic Research

10 American Drive
Norwood
Massachusetts 02062
Telephone 617 769 4200



Please send me a complete description of the AR-10 π , AR-11, and AR-MST/1 speaker systems.



Please send me the AR demonstration record 'The Sound of Musical Instruments' (check for \$5 enclosed)

Name _____

Address _____

RE 10

LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

WORLD'S SMALLEST CALCULATOR!

Small but mighty! 8-digit, 4-function electronic calculator does everything big ones do—even has automatic % key... for only \$19.95. Take it anywhere. Fits in your pocket—1/2 size of cigarette pack. 2-oz. dynamo features float-in decimal, constant key, lead zero depression, more! Operates on two 1.5v Mallory PX 825 camera batteries (included). 2 x 2.8 x 0.4" with plenty of room for most fingers. Another Edmund first with advanced technology.

Stock No. 1945EH \$19.95 Ppd.



AM RADIO FITS IN/ON YOUR EAR!

Wear it inconspicuously everywhere, listen as you work (lawn, yard, office), watch (game, beach) or wait. Instant music, news, sports. No gimmick — 6/10 oz. technological wonder w/integrated circuit, 11 transistors, patented ferrite antenna/tuner/volume dial. Works best outdoors. Uses hearing aid batt. (incl.)—up to 100 hrs. playing. New batt. to slip in avail. at drug stores (about 50¢). No lengthy wires, bulky cases, or power-packed!

Stock No. 42,275 EH \$14.95 Ppd.



PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18 3/4" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, tripod socket; req. two 9v trans. batt. (not incl.).

No. 1649EH (5 1/2 LB.) \$299.00 Ppd.

LOW COST MODEL: NO EARPHONES, ELECTR. CIRC.

No. 1665 EH \$199.95 Ppd.

LOWER SENSITIVITY ECON. MOD. W/O ELECTR.

No. 80,242 EH \$89.50 Ppd.



AN ALPHA MONITOR FOR \$34.95?

Yes, because you built it! Use your ability to tune in your brainwaves, an aid to relaxation, concentration. Kit incl. everything you need (except 9v trans. batt.) to own a portable self-cont. BIOFEEDBACK unit for a pittance: steth. earphones, electrode headband, solid-state circuitry; 5 microvolt sensitivity, more! Compl. assembly instructions & op. manual. With basic electronics knowledge, you can do it!

No. 61,069 EH (KIT) \$34.95 Ppd.

No. 71,809 EH (FULLY ASSEMBLED) \$55.00 Ppd.



★ WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE ★
★ FREE BICENTENNIAL LIGHT SHOW ★
★ IN BARRINGTON, N.J. ONLY 10 MINUTES AWAY AT ★
★ EDMUND FACTORY STORE ★

NEW! AUTOMATIC TIME-LAPSE PIX

Terrific bargain! Under \$200! Compares w/others at \$450-\$700! Get fabulous time/motion shots with the versatile 37-ounce portable Edmund Time Machine. Converts almost any camera to a total time lapse system. Comes w/20" cable release for socket cameras, 20" electric cable for electronic remote or single frame socket types. Continuous variable interval from 0.5 to 300 seconds; built-in photocell control, more! Rechargeable power supply.



No. 72,122 EH (6 x 3 1/2 x 2") \$199.95 Ppd.

TOTAL KIRLIAN PHOTOGRAPHY SET

Explore "aura" photography w/ superb new self-contained Kirlian Electrophotography Research Unit. Terrific value — introduced at \$99.95 (\$140 in Sept.)! Has everything but vinyl photo changing bag. Ideal for color or b&w 35mm, sheet or Polaroid film for photos up to 5x7" all without camera or lens. Variable voltage 12v to 32kv. Ultimate safety design—fully encased in plastic; patented electronics. Instrs.



No. 72,104 EH (3x5 7/8x7 7/8") \$99.95 Ppd.

No. 42,240 EH (CHANGING BAG) \$6.50 Ppd.

LOW COST 7X INFRA-RED VIEWER

For Infra-red crime detection surveillance, security system alignment, I.R. Detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl. I.R. light source, 5v or 12v power, 6032 I.R. converter tube, f/4.5 objective lens, adjust. triplet eyepiece. Focuses from 10' to infinity.



No. 1659 EH (11x14 1/4x3") \$275.00 Ppd.

WITHOUT LIGHT SOURCE \$225.00 Ppd.

No. 1648 EH

BUILD THIS COMPUTER, SAVE \$27

Assembled, our amazing electronic digital computer is \$45. New kit lets you build it for almost 1/3 that! Easy to program, fun to operate; solve problems, play games, try to outwit it. Program it, give it problems, get results from electronic readout. Quickly learn "what makes a computer tick," how to program, soon program w/your problems, data. 14 x 15" unit has 3 movable registers, patch cords & plugs; 2 manuals, cards, dice. Req. 3 AA batts., soldering.



No. 72,105 EH (HI-IMPACT PLASTIC) \$17.95 Ppd.

ELECTRONIC DIGITAL STOPWATCH: \$69.95

A price breakthrough! New pocket size 4 oz. timer acc. to ± 2% of last digit (1/100 sec. increments). Compares with others twice the price! Instant error-free read-out to 9999.99 sec. (over 2 3/4 hr.). Starts, stops, re-starts (accumulates). Mechanical pushbutton & electrical remote on/off. w/ any 3.5-150v AC/DC source. Plug-in jack. Incls. 9v batt. Solid state.



No. 1943 EH (2 1/4x4 1/2x7 1/8") \$69.95 Ppd.

DELUXE 2 EVENT STOPWATCH (± 0.01% OF LAST DIGIT)

No. 1653 EH \$149.95 Ppd.



MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4,500 UNUSUAL BARGAINS

Completely new 1976 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Name _____
Address _____
City _____ State _____ Zip _____



COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO.
EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

☐ PLEASE SEND GIANT FREE CATALOG "EH"

☐ Charge my BankAmericard *

☐ Charge my Master Charge * Add Handling Chg.: \$1.00, Orders Under \$5.00 50¢, Orders Over \$5.00

Interbank No. _____

My Card No. Is _____

Card Expiration Date _____

30-DAY MONEY-BACK GUARANTEE.
You must be satisfied or return any purchase in 30 days for full refund.

*\$15.00 minimum

Name _____

Address _____

City _____

State _____

Zip _____

Signature _____

Circle 81 on reader service card



QUALITY ELECTRONIC COMPONENTS

— SAME DAY SERVICE —

NEW DISCOUNT SCHEDULE
SAVES YOU EVEN MORE!

1024 BIT STATIC MOS RAM 2102 . . . \$3.50

INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400N	24c	7415N	22c	74155N	77c	4019AE	58c	4518AE	\$1.28
7401N	24c	7416N	22c	74156N	77c	4020AE	\$1.50	4520AE	\$1.28
7402N	24c	7417N	22c	74157N	77c	4021AE	94c	4521AE	\$1.28
7403N	24c	7418N	24c	74160N	\$1.19	4022AE	\$1.18	4522AE	90c
7404N	24c	7419N	24c	74161N	\$1.11	4023AE	24c	4523AE	\$2.54
7405N	24c	7420N	31c	74162N	\$1.12	4024AE	24c	4524AE	\$1.87
7406N	24c	7421N	31c	74163N	\$1.19	4025AE	24c	4525AE	\$1.87
7407N	24c	7422N	31c	74164N	\$1.11	4026AE	\$1.67	4526AE	98c
7408N	24c	7423N	31c	74165N	77c	4027AE	\$1.04	4527AE	\$3.83
7409N	24c	7424N	31c	74166N	\$1.02	4028AE	\$1.36	4528AE	\$3.83
7410N	24c	7425N	31c	74167N	\$1.02	4029AE	24c	4529AE	\$3.83
7411N	24c	7426N	31c	74168N	\$1.02	4030AE	24c	4530AE	\$3.83
7412N	24c	7427N	\$1.11	74169N	\$1.02	4031AE	\$1.67	4531AE	\$1.45
7413N	24c	7428N	31c	74170N	\$1.02	4032AE	24c	4532AE	\$1.87
7414N	\$1.02	7429N	\$2.13	74171N	\$1.02	4033AE	\$1.36	4533AE	\$1.36
7415N	24c	7430N	48c	74172N	\$1.19	4034AE	\$1.60	4534AE	43c
7416N	24c	7431N	48c	74173N	\$1.11	4035AE	67c	4535AE	43c
7417N	24c	7432N	48c	74174N	\$1.11	4036AE	82c	4536AE	37c
7418N	24c	7433N	48c	74175N	\$1.11	4037AE	82c	4537AE	60c
7419N	24c	7434N	48c	74176N	\$1.11	4038AE	\$2.35	4538AE	\$1.25
7420N	24c	7435N	85c	74177N	24c	4039AE	52c	4539AE	68c
7421N	24c	7436N	85c	74178N	24c	4040AE	52c	4540AE	68c
7422N	24c	7437N	85c	74179N	24c	4041AE	52c	4541AE	68c
7522N	24c	7537N	85c	74279N	24c	4141AE	52c	4641AE	68c
7523N	24c	7538N	85c	74280N	24c	4142AE	52c	4642AE	6

LINEAR INTEGRATED CIRCUITS

1-24 25-99 100 up

GENERAL PURPOSE AMPLIFIERS

SL201B GP amplifier 4.01 3.51 3.01
SL201C GP amplifier 1.87 1.64 1.40

MATCHED NPN TRANSISTORS

SL301A Matched pair 2.72 2.46 1.40
SL301B Matched pair 2.30 2.01 1.72
SL303A Matched triplet 5.47 4.78 4.09
SL303B Matched triplet 3.93 3.43 2.93
SL305B Dual matched pairs 7.37 6.44 5.52
SL312B Matched pair w/tail 2.85 2.56 2.27
SL354A Matched quad 4.22 3.70 3.17
SL360C 2.5GHz matched pair 10.93 9.56 8.18
SL362C 2.5GHz low noise pair 16.26 14.20 12.14
SL365C Transistor array 2.77 2.43 1.90
SL3145C 2.5GHz trans array 14.78 12.94 11.09

AUDIO CIRCUITS

SL141A 3W audio amplifier 4.22 3.70 3.17
SL145A 5W audio amplifier 5.49 4.81 4.12

POWER CONTROL CIRCUITS

SL440 Power control circuit 5.49 4.81 4.12

TRANSISTOR ARRAYS

SL3046 Five-transistor array 1.55 1.61 1.37

LINEAR RF AMPLIFIERS

SL501A RF amplifier 19.25 16.84 14.44
SL501B RF amplifier 5.91 5.17 4.44
SL502A RF amplifier 14.55 13.04 11.55
SL502B RF amplifier 3.88 3.49 3.09
SL503A RF amplifier 16.50 14.78 13.07
SL503B RF amplifier 4.12 3.70 3.27
SL551A RF amplifier 18.82 16.87 14.92
SL551B RF amplifier 5.89 5.28 4.67
SL552A RF amplifier 18.82 16.87 14.92
SL552B RF amplifier 5.89 5.28 4.67
SL553A RF amplifier 21.09 18.90 16.71
SL553B RF amplifier 6.28 5.62 4.96
SL510C RF det. & video amp 25.34 22.18 19.00
SL511C RF det. & video amp 25.34 22.18 19.00

LIMITING WIDEBAND AMPLIFIERS

SL521A Limiting RF amp 27.72 24.26 20.80
SL521B Limiting RF amp 17.58 15.58 13.57
SL521C Limiting RF amp 10.59 9.27 7.95
SL571A Limiting RF amp 37.80 33.08 28.35
SL571B Limiting RF amp 23.39 20.46 17.53
SL571C Limiting RF amp 16.48 15.29 13.60
SL525C Wideband amplifier 5.80 5.20 4.60
SL530C Logarithmic amp 17.58 15.58 13.57
SL550C 200MHz wideband amp 26.19 21.81 18.16
SL1030C 200MHz wideband amp 29.57 25.87 22.18

RADIO COMMUNICATIONS CIRCUITS

SL610C RF amplifier 4.07 3.56 3.06
SL611C RF amplifier 4.07 3.56 3.06
SL612C RF amplifier 4.07 3.56 3.06
SL613C Limiting amp/det. 8.66 7.58 6.49
SL620C VOGA amp 6.15 5.39 4.63
SL621C AGC generator 6.15 5.39 4.63
SL622C AF amp/VOGA 15.21 13.31 11.41
sidetone amplifier

PLESSEY SEMICONDUCTORS

SL623C AM det./AGC amp/11.19 9.79 8.40

SL624C Multimode det. AF amp 5.70 5.00 4.28
SL630C AF amplifier 3.85 3.38 2.90
SL640C DBI bal. modulator 7.55 6.60 5.65
SL641C Receiver mixer 7.55 6.60 5.65
SL645C Square law device 7.55 6.60 5.65
SL650B Mod./phase loc. loop 8.60 8.14 7.66
SL650C Mod./phase loc. loop 8.60 8.14 7.66
SL651B Mod./phase loc. loop 12.06 10.34 8.62
SL651C Mod./phase loc. loop 7.56 6.84 5.40

OPERATIONAL AMPLIFIERS

SL701B Op. amplifier 7.13 6.23 5.39
SL701C Op. amplifier 3.56 3.12 2.67
SL702B Op. amplifier 7.13 6.23 5.39
SL702C Op. amplifier 3.56 3.12 2.67
SL717A Dual comparator 10.35 9.06 7.76
SL717C Dual comparator 6.57 5.74 4.94
SL751B Op. amplifier 8.37 7.50 6.63
SL751C Op. amplifier 4.81 4.30 3.80

TELECOMMUNICATIONS CIRCUIT

SL1001A Linear mod./demod. 3.22 2.83 2.43
SL1001B Linear mod./demod. 3.22 2.83 2.43
SL1002A Lin. amp./remote det. control 7.15 6.26 5.36

TELEVISION CIRCUITS

SLA661 Limit. IF amp/FM det. 4.22 4.22 3.30
SLA662 Limit. IF amp/FM det. 4.73 4.73 3.70
SLA663 Signal processor 10.14 10.14 7.92
SLA664 Signal processor 10.14 10.14 7.92
SLA665 Limit. IF amp/FM det. 4.73 4.73 3.70
SLA666 Limit. IF amp/FM det. 4.73 4.73 3.70
SLA37C IF & AGC for 13.52 13.52 10.56
SLA37D IF & AGC for 13.52 13.52 10.56

NPN TUNERS

SL442 Switch mode power supply control 9.24 7.92 6.60
SL450 Power sup. & Syn. sep. 11.09 9.50 7.92
SL456A TV IF system 7.39 6.34 5.28
SL456B TV IF system 7.39 6.34 5.28
SL457A TV IF system 7.39 6.34 5.28
SL457B TV IF system 7.39 6.34 5.28
SL901 Color demodulator 10.14 10.14 7.92
SL902 Color decoder 13.52 13.52 10.56

DIGITAL INTEGRATED CIRCUITS

Description 1-24 25-99 100 up

PROCESS CONTROL CIRCUITS

SP520 Gray code counter 13.94 12.49 11.04
SP521 Binary rate multip. 13.94 12.49 11.04
SP522 Phase loc./div. & com. 13.94 12.49 11.04

PECL II - SP1000 SERIES

SP1004B Dual 4 I/P OR/NOR gate 1.71 1.48 1.25
SP1005B Dual 4 I/P OR/NOR gate 1.71 1.48 1.25

* FLAT PACK

SP1006B Dual 4 I/P OR/NOR gate 1.71 1.48 1.25

SP1007B Triple 3 I/P NOR gate 1.71 1.48 1.25
SP1008B Triple 3 I/P NOR gate 1.71 1.48 1.25
SP1009B Triple 3 I/P NOR gate 1.71 1.48 1.25
SP1010B Quad 2 I/P NOR gate 1.71 1.48 1.25
SP1011B Quad 2 I/P NOR gate 1.71 1.48 1.25
SP1012B Quad 2 I/P NOR gate 1.71 1.48 1.25
SP1100B Quad 2 I/P NOR gate 1.71 1.48 1.25

SP8641A 10/11 (ECL) at 250MHz 32 20 27 60 23 00

SP8641B 10/11 (ECL) at 19.04 16.32 13.60

SP8642A 10/11 (ECL) at 58.80 50.40 42.00

SP8642B 10/11 (ECL) at 25.20 21.60 18.00

SP8643B 10/11 (ECL) at 35.00 30.00 25.00

SP8650B 16 at 600MHz 70.00 60.00 50.00

SP8651B 16 at 500MHz 53.20 45.00 38.00

SP8652B 16 at 400MHz 42.00 36.00 30.00

SP8653B 16 at 100MHz 63.00 54.00 45.00

SP8654B 16 at 100MHz 21.00 18.00 15.00

SP8655B 16 at 100MHz 98.00 84.00 70.00

SP8656B 16 at 100MHz 21.00 18.00 15.00

SP8657B 16 at 100MHz 53.20 45.00 38.00

SP8658B 16 at 100MHz 18.90 16.20 13.50

SP8659B 16 at 100MHz 37.80 32.40 27.00

SP8660B 10 at 1.1GHz 107.80 92.40 77.00

SP8661B 10 at 1.2GHz 119.00 102.00 85.00

SP8662B 8 at 600MHz 63.00 54.00 45.00

SP8663B 8 at 500MHz 49.00 42.00 35.00

SP8664B 8 at 400MHz 37.80 32.40 27.00

SP8665A 10/11 at 500MHz 116.20 99.60 83.00

SP8666B 10/11 at 500MHz 35.00 30.00 25.00

SP8667A 10/11 at 100MHz 63.00 54.00 45.00

SP8668B 10/11 at 100MHz 19.00 16.80 14.00

SP8669B 10/11 at 100MHz 63.00 54.00 45.00

SP8670B 10/11 at 100MHz 19.00 16.80 14.00

SP8671B 10/11 at 100MHz 63.00 54.00 45.00

SP8672B 10/11 at 100MHz 19.00 16.80 14.00

SP8673B 10/11 at 100MHz 63.00 54.00 45.00

SP8674B 10/11 at 100MHz 19.00 16.80 14.00

SP8675B 10/11 at 100MHz 63.00 54.00 45.00

SP8676B 10/11 at 100MHz 19.00 16.80 14.00

SP8677B 10/11 at 100MHz 63.00 54.00 45.00

SP8678B 10/11 at 100MHz 19.00 16.80 14.00

SP8679B 10/11 at 100MHz 63.00 54.00 45.00

SP8680B 10/11 at 100MHz 19.00 16.80 14.00

SP8681B 10/11 at 100MHz 63.00 54.00 45.00

SP8682B 10/11 at 100MHz 19.00 16.80 14.00

SP8683B 10/11 at 100MHz 63.00 54.00 45.00

SP8684B 10/11 at 100MHz 19.00 16.80 14.00

SP8685B 10/11 at 100MHz 63.00 54.00 45.00

SP8686B 10/11 at 100MHz 19.00 16.80 14.00

SP8687B 10/11 at 100MHz 63.00 54.00 45.00

SP8688B 10/11 at 100MHz 19.00 16.80 14.00

SP8689B 10/11 at 100MHz 63.00 54.00 45.00

SP8690B 10/11 at 100MHz 19.00 16.80 14.00

SP8691B 10/11 at 100MHz 63.00 54.00 45.00

SP8692B 10/11 at 100MHz 19.00 16.80 14.00

SP8693B 10/11 at 100MHz 63.00 54.00 45.00

SP8694B 10/11 at 100MHz 19.00 16.80 14.00

SP8695B 10/11 at 100MHz 63.00 54.00 45.00

SP8696B 10/11 at 100MHz 19.00 16.80 14.00

SP8697B 10/11 at 100MHz 63.00 54.00 45.00

SP8698B 10/11 at 100MHz 19.00 16.80 14.00

SP8699B 10/11 at 100MHz 63.00 54.00 45.00

SP8700B 10/11 at 100MHz 19.00 16.80 14.00

SP8701B 10/11 at 100MHz 63.00 54.00 45.00

SP8702B 10/11 at 100MHz 19.00 16.80 14.00

SP8703B 10/11 at 100MHz 63.00 54.00 45.00

SP8704B 10/11 at 100MHz 19.00 16.80 14.00

SP8705B 10/11 at 100MHz 63.00 54.00 45.00

SP8706B 10/11 at 100MHz 19.00 16.80 14.00

SP8707B 10/11 at 100MHz 63.00 54.00 45.00

SP8708B 10/11 at 100MHz 19.00 16.80 14.00

SP8709B 10/11 at 100MHz 63.00 54.00 45.00

SP8710B 10/11 at 100MHz 19.00 16.80 14.00

SP8711B 10/11 at 100MHz 63.00 54.00 45.00

SP8712B 10/11 at 100MHz 19.00 16.80 14.00

SP8713B 10/11 at 100MHz 63.00 54.00 45.00

SP8714B 10/11 at 100MHz 19.00 16.80 14.00

SP8715B 10/11 at 100MHz 63.00 54.00 45.00

SP8716B 10/11 at 100MHz 19.00 16.80 14.00

SP8717B 10/11 at 100MHz 63.00 54.00 45.00

SP8718B 10/11 at 100MHz 19.00 16.80 14.00

SP8719B 10/11 at 100MHz 63.00 54.00 45.00

SP8720B 10/11 at 100MHz 19.00 16.80 14.00

SP8



POTTER BRUMFIELD

Type KHP Relay
4 PDT 3A Contacts

24 VDC (650 coil) \$1.50 Ea.
120 VAC (10.5 MA coil) \$1.75 Ea.

CMOS

CD4000	\$.29	CD4016	\$.69
CD4001	.29	CD4019	.69
CD4002	.29	CD4023	.29
CD4007	.29	CD4024	1.50
CD4008	1.98	CD4025	.34
CD4009	.59	CD4030	.65
CD4010	.59	74C20	.65
CD4011	.29	74C42	2.00
CD4012	.29	74C157	2.50
CD4013	.69	74C161	3.00
CD4015	1.98	74C195	2.00

RCA 2010

Numitron Digital Display Tube
Incandescent 5-volt 7-segment
with .6" high numeral visible
from 30 ft., standard 9-pin
base (solderable), and left
hand decimal point.
EACH \$5.00 5 FOR \$20.00

Numeric Display 1/4" Single Digit GaAsP LED

SUPER SPECIAL \$9
TEN for \$4.95

COMMON CATHODE WITH RH DECIMA



ACTUAL SIZE

Compact - 10 digits in 3" panel width
Highly legible - bright red 1/4" character easily read
within 10 feet over a wide viewing angle (140°)
Low power - 125 mW per digit at typical brightness

2102-2 MOS 1024 BIT MEMORY (DIP)

FULLY DECODED STATIC RANDOM ACCESS MEMORY
DIRECTLY TTL COMPATIBLE INPUTS AND OUTPUT
SINGLE SV SUPPLY - NO CLOCKS OR REFRESH

\$5.00 ea. 8 for \$34.95

NEW!



FULL WAVE BRIDGE RECTIFIERS
25 AMP 500 PIV

EACH \$2.00 10 FOR \$16.50

CD-2 COUNTER KIT

Unit includes board, 7490, 7475, quad
latch, 7447 seven-segment driver, and
RCA DR2010.



COMPLETE KIT \$10.95

FULLY ASSEMBLED \$15.00

Boards can be supplied separately at
\$2.50 per digit.

NPN TO3 POWER TRANSISTORS

410 (RCA) 200V - 10A
2N3772 70V - 30A
Each \$1.75 10 for \$15.00

2N3055 Transistor (power): PD-115W
VCE-60V; HFE-50; FT-30K; Case TO-3
Each \$1.15 10 pak \$6.95

See the bargains at our YEAR-END SALE!

FREE!! CT5001

With \$25.00 prepaid order
4 Function, 12 Digit Calculator IC
With Data

All IC's are new and fully-tested.
Leads are plated with gold or solder.
Orders for \$5 or more will be shipped
prepaid. Add 55¢ for handling and
postage for smaller orders; residents
of California add sales tax. IC orders
are shipped within 2 workdays--kits
are shipped within 10 days of receipt
of order. \$10 minimum on C.O.D.'s

Mail Orders to: Phone:
P.O. Box 41779 (916) 334-2161
Sacramento, CA
95841

BABYLON ELECTRONICS

MONEY BACK GUARANTEE ON ALL GOODS!
SEND FOR FREE FLYER LISTING 100's OF
MONEY-SAVING BARGAINS!

TTL

7400	\$.20	7453	\$.15
74H00	.25	7454	.20
7401	.30	74L54	.25
74H01	.25	74L55	.25
7402	.25	7460	.16
7403	.25	74L71	.25
7404	.25	7472	.40
74H04	.30	74L72	.60
7405	.30	7473	.25
7406	.40	74L73	.75
7408	.30	7474	.45
7410	.15	74H74	.75
7413	.75	7475	.80
7417	.40	7476	.55
7420	.20	74L78	.70
74L20	.30	7480	.50
74H20	.30	7483	.70
74H22	.30	7489	3.00
7430	.15	7490	1.00
74H30	.30	7492	.45
74L30	.30	7493	1.00
7440	.20	7495	.65
74H40	.30	74L95	1.00
7442	1.00	74107	.25
7447	1.50	74145	1.25
7450	.15	74180	1.00
74H50	.30	74193	1.50
7451	.20	74195	.65
74H51	.25		

Specials

DIP TRIMMER

-12 turn trimpots
which plug into
a DIP socket
-5K and 200K
-1/2" x 1/2" x 1/2"
-4 leads spaced
.3" x .2"

Each \$1.00 10 for \$8.95

MEMORY CHIPS

8223 PROM
8 BIT-32 WORD
MEMORY

\$3.00 EACH 10 FOR \$29.00

WE PROGRAM FOR \$5.00 EACH

82S129 SIGNETIC
1024 BIT-256/4
FIELD PROGRAMMABLE
(WE WILL NOT PROGRAM)
EACH \$5.00 8 FOR \$34.95

TRANSISTOR

2N3904 - HEP736
TO92 PLASTIC - NPN
300 MW - 60V - 8100-300
NEW - FAIRCHILD - MARKED

EACH \$.15 10 FOR \$1.00



give...so more will live
HEART FUND

TV TYPEWRITER / COMPUTER DATA INPUT KEYBOARD



New MICRO-SWITCH
(Honeywell). One of
the finest we have
seen. Encoder is
TTL & CMOS. Ideal
for any project re-
quiring a precision
keyboard. Key
area is 4" x 11 1/2".
We supply pin
data & circuit
diagram.

STOCK NO.R5285 MICRO-SWITCH KEYBOARD \$39.50, 2/75.00

ULTRA SONIC TRANSDUCERS

We have had many requests for ultra sonic transducers, the type
used in burglar alarms, remote control devices and alarm systems.
We have acquires 2 types. One operating at 23KHz. and the other
at 41.5 KHz. Each transducer can operate as a transmitter or
receiver. We supply some basic alarm circuits.

STOCK NO.K9272 23KHz. Transducer \$2.00 ea. 4/7.00

STOCK NO.K6000 41.5 KHz Transducer, \$3.00 ea. 2/5.00

GIANT NIXIE TUBE ASSEMBLY



Another lot of GIANT NIXIE tubes, com-
plete with sockets and driver board. Tubes
are BURROUGHS B7971 15 segment alpha
numeric tubes with 2 1/2" characters. Board
contains 33 transistors, including 15 driver
transistors. Set consists of 2 tubes, 2 sockets
and driver board. We supply tube data.
STK.NO. R6001 6.95 per set, 2/12.00

MINIMUM ORDER \$5.00. Include postage, excess refunded. New
edition of our catalog now available.



DELTA ELECTRONICS CO.

BOX 1, LYNN, MASSACHUSETTS 01903
Phone (617) 388-4705

Circle 96 on reader service card

Circle 94 on reader service card

Wow!
INCREDIBLE
PRICES

**BUY ANY 10
TAKE 15%**
**BUY 100
TAKE 25%**

TUNERS


SN7400	\$1.16	SN7462	\$2.22	SN74122	.48
SN7401	.16	SN7470	.29	SN74123	.85
SN7402	.16	SN7471	.49	SN74125	.59
SN7403	.16	SN7472	.29	SN74126	.59
SN7404	.19	SN7473	.36	SN74132	1.75
SN7405	.19	SN7474	.36	SN74140	2.10
SN7406	.35	SN7475	.59	SN74145	1.05
SN7407	.35	SN7476	.59	SN74148	2.25
SN7408	.19	SN7477	.59	SN74150	.98
SN7409	.19	SN7480	.72	SN74151	.75
SN7410	.16	SN7481	.99	SN74153	.90
SN7411	.45	SN7482	.89	SN74154	1.35
SN7413	.59	SN7483	1.25	SN74155	.95
SN7414	1.65	SN7485	1.25	SN74156	.95
SN7416	.34	SN7486	.37	SN74157	.95
SN7417	.34	SN7488	3.95	SN74160	1.25
SN7421	.16	SN7489	2.45	SN74161	1.25
SN7422	.45	SN7490	.59	SN74163	1.35
SN7423	.29	SN7491	1.10	SN74165	1.50
SN7425	.29	SN7492	.59	SN74167	1.50
SN7426	.25	SN7493	.59	SN74173	1.45
SN7427	.29	SN7494	.95	SN74174	1.39
SN7430	.16	SN7495	.79	SN74175	1.30
SN7432	.25	SN7496	.79	SN74176	1.20
SN7433	.49	SN74100	1.40	SN74177	1.20
SN7437	.34	SN74104	.44	SN74180	.95
SN7438	.34	SN74105	.44	SN74181	2.98
SN7440	.16	SN74106	.52	SN74182	.74
SN7441	1.00	SN74107	.44	SN74184	1.98
SN7442	.70	SN74108	.89	SN74185	1.98
SN7444	1.25	SN74112	.89	SN74190	1.40
SN7445	.89	SN74113	.89	SN74192	1.25
SN7446	1.15	SN74114	.49	SN74193	1.25
SN7447	.99	SN74121	.89	SN74194	1.20
SN7448	.99			SN74195	.85
SN7450	.99			SN74196	1.80
SN7451	.17			SN74197	.90
SN7452	.17			SN74199	1.75
SN7453	.17			SN74200	4.95
SN7454	.17				
SN7455	.22				
SN7460	.17				

\$4.95 6-VOLT NICAD POWER PAK
Includes 1 "A" cell nicad batteries hooked up to give you 6-volts for all types of energy uses. The best batteries made. Rechargeable.

BY TELEDYNE PACKARD-BELL
JUST IN... The "QUADS" are for either 8-track or Quad tapes. An audiophile economy exclusive by Poly Paks. Same type found in the most expensive tape players, tuners, etc. It's a complete Quad system, featuring 4-channel preamp... all the cables necessary to just plug into any stereo quad amplifier or even our 20 & 60-watt tuner amplifier systems (see elsewhere in this catalog). Insert a cartridge to turn on deck. Enjoy up to 80 minutes of non-stop, non-repeat stereo or quad. Remove cartridge deck automatically shuts off. Other features: 4-program indicator lights, automatic or manual program change, push-button channel selector switch, built-in triggering switch that enables you to automatically use 8-track or quad tapes; heavy-duty flywheel for WOW & FLUTTER PROOF sound; flapping front panel tape door mounting front panel flange. Heavy duty cool-proof 115 VAC motor. Requires external 12 VDC supply, for all electronics. Includes schematic, hookups, all cables. Size: 6 1/2" x 6 1/2" x 3 1/2". IT'S READY TO GO!

"QUAD" TAPE DECK

\$1995

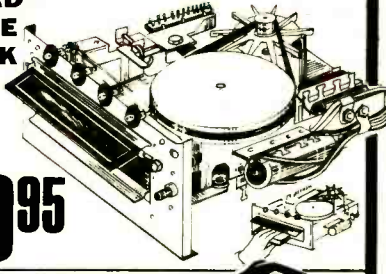

9-FUNCTION, 8-DIGIT MEMORY CALCULATOR KIT
It's the easiest multi-function kit today!

Lightweight, 5 1/4" x 3" x 2" (at back side) x 1 1/4" front side of angular display panel black. Contains fifty unit for business, school, home, and for the youngsters. Slips into any pocket, briefcase with ease. Easy-to-understand pictorial instruction booklet and how-to-use-book.
AC/DC tool KIT INCLUDES: case, 22-key keyboard kit, ON-OFF switch (part of keyboard), PC board, driver and memory calculator chips, 9-digit 'bubble' magnifier LED array, array cable, AC adapter jack & wires, battery case, 6 battery card display, instruction and pictorial step-by-step construction booklet.

DOUBLE MEMORY
Percent, Constant, Display Restore

\$1695



4-DIGIT AM-PM FLUORESCENT CLOCK PANEL

"PANEL OPTICS"
YOU ASKED FOR IT! Found only at Poly Paks at this low price! It's ONLY 1 3/4" x 1 3/16" x 3/8" deep panel. Designed specifically for our MM-5316 fluorescent driving clock chip. Indicates 4-digits, AM-PM, pulsating second indicator, requires minimum of parts to build. Color: BLUE-GREEN; you can use RED or GREEN filters. Character height: 0.5". Filament voltage is 1.75 VAC or DC @ 160 ma. Anode voltage 25V @ 250 microamps per segment. With spec sheets, clock construction diagrams, P.C. board layouts, specs. A DIGITAL CLOCK BUILDER'S SPECIAL.



Made By **TUNG-SOL** D2004

Timer **555**
2 for \$1
OR
558
Dual 741
3 for \$1

CLOCK CHIPS ON A "DIP"
WITH DATA SHEETS
MM5311 6-digit 28-Pin \$5.50
MM5312 4-digit 24-Pin \$5.50
MM5313 6-digit 28-Pin \$5.50
MM5314 6-digit 24-Pin \$5.50
MM5316 4-digit 40-Pin \$5.50 alarm
MM5316-A no alarm 3.95

LED Revolution!

MONSANTO! XCITON! LITRONIX! OPCOA!

5 for \$1

.340x.260	.240x.200
Jumbo	Medium
Red	Red
Green	Yellow
Yellow	Green
Amber	Amber
Clear	Clear
Micro	.210x.125
Red	Yellow
Green	Amber


Micro (Axial) MV-50 style
MV-50 Clear 10 for \$1.
MV-55 Red 6 for \$1.

This unit is not advertised anywhere! Made for Motorola Communications at the original cost of \$4.60 each (for insertion in their Walkie Talkie Program). It's a 60-ohm imp. MIKE. It's an excellent speaker made.

INDUSTRIAL SPEED CONTROL \$4.95

A \$30 item from G.E. Model 533A (made for Xerox) that controls home, shop and industrial lighting tool. A very elaborate circuit for controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, and 115vac, rated at 1100 watts. With variable speed or dimming control in heavy-duty aluminum case. 3 x 2 3/4 x 2. With diagram and hookups.

4 1/2 DIGIT DIGITAL VOLT-METER DVM CHIP

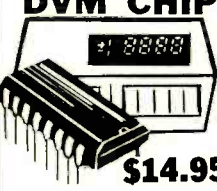

Type MM5330 by National utilizes P channel low-threshold enhancement mode devices and ion implanted depletion mode devices. Provides logic circuit for 4 1/2 digit DVM. All logic for four decade counters, a divide by four counter, a divide by two counter for over-range blanking, latches for all counter stages, an output ROM to generate BCD to 9's complement BCD of the latches and a module 4 counter to sequentially present each of decade latches thru ROM to the BCD output pins. Four outputs to indicate which decade is display. A reset for all counter stages, transfer pulse generator to set the latches. To 400 KHz operation. TTL compatible. With instruction sheets and diagram on "how-to-build a 4 1/2 digit DVM". Ideal with our Litronix 1/2" single, 1 1/2" and dual digits. 16-pin DIP.

\$14.95

LOWEST PRICES IN U.S.A.!

NATIONAL LM-340T VR's
• 22 Pin Case • Amp • POSITIVE VOLTAGE
\$1.75 Each
Type PIV Sale
LM-340-057 5 V 10 for 45c
LM-340-058 5 V 100 for 55c
LM-340-059 5 V 200 for 65c
LM-340-121 12 V 10 for 75c
LM-340-122 12 V 100 for 85c
LM-340-123 12 V 200 for 95c
LM-340-247 24 V 10 for 1.29

"BLASTAWAY" ON 1N4000 RECTIFIER PRICES

Type PIV Sale
1N4001 50 10 for 45c
1N4002 100 10 for 55c
1N4003 200 10 for 65c
1N4004 400 10 for 75c
1N4005 600 10 for 85c
1N4006 800 10 for 95c
1N4007 1000 10 for 1.29

MICROPROCESSORS! ROMS! RAMS! MEMORIES!

8008 Microprocessor	\$44.00
8080 Super 8008	250.00
2102 1024 Static RAM	3.95
1101 256 bit RAM	1.50
1102 1024 bit RAM	2.95
MM5203 1024 bit RAM	2.95
MM5262 2048 bit RAM	6.50
2513 Character generator	12.50
MM5203Q Erasable PROM	19.95
MM5204Q Erasable PROM	19.95
7022A Erasable PROM	19.95
8223 Programmable ROM	2.95

Fabulous POLY PAKS BARREL SALE

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember the "good old days"? They're back again. The same way merchandisers throughout the United States buy from various factories... their overruns in barrels. Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

25 BARRELS PURCHASED FOR THIS SALE! BUY 'EM FROM THE "BARREL" AND SAVE!



- Here is what Poly Paks is Famous for...
- BARREL KIT #1: 75 for \$1.98**
LINEAR OF AMP'S
Marked 14 and/or with 16 pin diodes, may include gates, registers, flip flops, counters. Who knows!
 - BARREL KIT #2: 75 for \$1.98**
LINEAR OF AMP'S
May include 709's, 741's, 703's, 560 series, 555 includes marked and unmarked DIPs.
 - BARREL KIT #3: 100 for \$1.98**
1N4148/914 SWITCHING DIODES
You never saw this before. Imagine famous switching diodes at these prices!
 - BARREL KIT #7: 40 for \$1.98**
VOLUME CONTROL
Singles, duals, variety of values, styles, big ones - equal ones.
 - BARREL KIT #11: 40 for \$1.98**
POWER TAB TRANSISTORS
NPN, plastic TO220 type. Assorted 2N numbers.
 - BARREL KIT #15: 30 for \$1.98**
MOSFET TRANSISTORS
All 4 leaders TO-18 case, includes UHF transistors too!

- BARREL KIT #4: 100 for \$1.98**
SCRS, TRIACS, RECTIFIERS
1N4000 series. May include 25, 60, 100, 200, 400, 600, 800 and 1000V.
- BARREL KIT #5: 40 for \$1.98**
SUBMINIATURE TRANSFORMERS
Amazing, includes 455kcs, osc. antenna, who knows? From transistor radio man.
- BARREL KIT #12: 40 for \$1.98**
POWER TAB TRANSISTORS
PNP, plastic TO220 type. Assorted 2N numbers.
- BARREL KIT #13: 100 for \$1.98**
DISC CAPACITORS
Marked and unmarked. Red case type asst. values.

- BARREL KIT #6: 40 for \$1.98**
SCRS, TRIACS, QUADRACS
All the famous plastic power tab type. Raw factory stock! All the 10 amp types.
- BARREL KIT #9: 30 for \$1.98**
SCRS, TRIACS
All stud types, asst. ampages and voltages.
- BARREL KIT #10: 40 for \$1.98**
RESISTOR NETWORKS
By Corning Glass. in 14-pin dip.
- BARREL KIT #17: 100 for \$1.98**
LINEAR & 7400 DIPS
Marked and unmarked. Included numbers of raw factory stock.

- BARREL KIT #8: 30 for \$1.98**
RELAYS, RELAYS
Raw fallout stock, marked and unmarked stock. Babcock, Leach, etc. All types.
- BARREL KIT #14: 200 for \$1.98**
PRECISION RESISTORS
Marked and unmarked 1/4, 1/2, 2-watt.
- BARREL KIT #16: 100 for \$1.98**
ZENER-RECTIFIER MIX
Subminiature, DO7's, included asst. zeners and rectifiers. It's mixed.

TEST 'EM YOURSELF AND SAVE!
Every kit carries money back guarantee.

7-SEGMENT READOUT SALE!

* Up to 20 mils per seg. at 5V. MAN-1
* All fit into 14-pin IC socket.
Type Size Color Sale 3 for
MAN-1 .27 Red \$2.50 \$6.00
MAN-3MA .12 Red .69 2.00
MAN-4AB .27 Red 1.95 5.00
MAN-5 .27 Green 1.50 4.00
MAN-6 .6 Red 4.50 12.00
MAN-6 .6 Red 3.50 9.00
MAN-7 .27 Red 1.00 2.50
MAN-8 .27 Yellow 1.50 4.00
ALL ABOVE BY MONSANTO

Type Size Color Sale 3 for
SLA-1 .33 Red \$1.95 \$5.00
SLA-1 .33 Green 1.95 5.00
SLA-1 .33 Yellow 1.95 5.00
SLA-3 .7 Green 4.95 12.00
SLA-3 .7 Yellow 4.95 12.00
707 .33 Red 1.95 5.00
704A .33 Red 1.95 5.00
701C .33 Red 1.50 3.00
FND-70 .25 Red 1.50 3.00

A-Common Cathode, others Common Anode
B-With bubble magnifier
C-Plus or Minus 1

LITRONIX "JUMBO'S"

* Singles size: 1 x 3/4 x 5/16
* Duals size: .8 x .9 x .29
* 7-Segment, 25-mils per segment

Type Size Color Sale 3 for
721D .5 Red \$5.95 \$15.00
727E .5 Red 5.95 15.00
746F .6 Red 3.95 11.00
747 .6 Red 3.95 11.00


D-Plus or Minus 1 plus a digit (1 1/2 digits)
E-Dualdigits
F-Plus or Minus 1

Terms: add postage. Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass.
(off Water Street) C.O.D.'S MAY BE HONORED
20c CATALOG on Fiber Optics, IC's, Semi's, Parts
MINIMUM ORDER - \$4.00
POLY PAKS
P.O. BOX 942R, LYNNFIELD, MASS. 01940

equipment reports

Simpson Model 432 "Chroma-Line" Generator

THE FIRST THING I THOUGHT WHEN I UNPACKED the newest thing from Simpson, the Model 432 "Chroma-Line" Generator was "Hey! Isn't that a cute little thing." It's not as big as a cigar box. The second thing I thought was "Oh, shucks. They forgot to send the cables and line cord!" This was an early model, and even the instruction book was a pre-release copy. Searching the packing didn't help, so I settled down to read the manual. That did it. During the

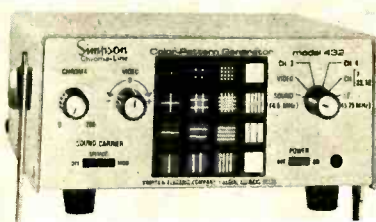

Circle 103 on reader service card

first quick look, I found the page that cleared up the mystery.

Despite the very compact size, and all of the things it can do, they have still managed to find space to put a 23-cubic-inch storage compartment in it! It's on the bottom of the case, with a cover held by two snap fasteners. Taking this off, there was the line cord and all of the hookup cables. So, don't write to the factory when you get one; just pull the two little black knobs to get at it.

This is a very versatile instrument. A 4×4 matrix of pushbuttons can give you any of sixteen different patterns. You can have a single dot in the center of the screen, a 7×11 pattern or a 15×21 pattern of dots. Same with vertical or horizontal lines. You can start out with a single "cross-hair" pattern, one vertical and one horizontal line, go through a 7×11 line pattern, and wind up with a 15×21 cross-hatch. Three color patterns are used; an unkeyed rainbow, three-bar color, and the standard 10 bar keyed rainbow. Last, a very handy one; a white "blank raster" for making purity adjustments.

Any of these signals can be fed into the TV set from the antenna input. Special cables provide either 300-ohm balanced or 75-ohm RF input. You can use any of three VHF channels, 3, 4 or 7. By using the 3rd and 5th harmonics of the channel 7 signal, two UHF channels, 23 and 52 can be used. The RF oscillators used for these are all crystal controlled.

The same patterns can also be fed directly into the IF input of the TV set. This is also a crystal-controlled signal. There is also a video-frequency output, which can be fed directly into the video stages. A 4.5-MHz sound IF signal, again crystal controlled, can be used, modulated or unmodulated. The amplitude of all signals can be adjusted by the level control on the back panel. The sync polarity of the video signal can be set to whatever is needed to match the TV set, and its level adjusted.

On the back panel of the Model 432, beside the RF/IF/video/sound BNC jack, and its level control, there is a banana jack. This can provide trigger signals at either horizontal or vertical frequency for the External Trigger of scopes.

The Model 432 is powered from the AC line, through an isolating transformer. An IC voltage regulator controls all of the IC operating voltages. Short-circuit protection and temperature compensation are also taken care of in this department.

I tried the Model 432 out on some of the dog TV's with which my bench is usually covered, and it came through. (I almost said "with flying colors" but this wasn't the case at all; they were siable as a rock. Beside that, I got roundly chewed out for using this phrase with reference to another color bar generator, a long time ago!)

The compact size of the Model 432 and the logical control arrangement makes it very easy to use, in the home or on the bench. It's small enough to be carried in a tube caddy. Quite an instrument, and one that should give you good service for a long time.

R-E

INTEL 8080 CPU \$139.00
8008 8 BIT MICRO PROCESS-
ING CHIP (with Data Book) \$ 35.00
2102-2 1024 BIT RAM \$ 3.95
5202A UV PROM \$ 19.00
MM5203 UV PROM \$ 19.00
1702A UV PROM \$ 19.95

MINIATURE TRIM POTS 100, 500
5K, 10K, 25K, 50K, 100K, 200K
\$.75 ea. 3/\$2.00

MULTI-TURN TRIM POTS Similar to
Bourns 3010 style, $\frac{1}{4}$ " x $\frac{5}{16}$ " x
 $1\frac{1}{4}$ ". 50, 100, 2000, 10,000 ohms
\$1.50 ea. 3/\$4.00

LIGHT ACTIVATED SCR'S
TO-18, 200V 1A \$1.75

PRINTED CIRCUIT BOARD
 $4\frac{1}{2}$ " x $6\frac{1}{2}$ " single sided epoxy
board, $\frac{1}{16}$ " thick, unetched
\$.50 ea. 5/\$2.20

4 WATT IR LASER DIODE \$7.95
2N 5460 P FET \$.45
TIS 73 N FET \$.45
2N 4891 UJT \$.45
ER 900 TRIGGER DIODES 4/\$1.00
2N 6028 PROG. UJT \$.65

VERIPAX PC BOARD

This board is a $\frac{1}{4}$ " single sided
paper epoxy board, $4\frac{1}{2}$ " x $6\frac{1}{2}$ ".
DRILLED and ETCHED which
will hold up to 21 single 14
pin IC's or 8, 16 or LSI DIP
IC's with busses for power
supply connector. \$5.25

RED-GREEN BIPOLAR LED \$1.30
MT-2 PHOTO TRANS \$.60
MV 5053 YELLOW GREEN
OR ORANGE LED ea. \$.35
RED GAP OSL-3 LED \$.20
14 PIN DIP SOCKETS \$.40
16 PIN DIP SOCKETS \$.50
MOLEX PINS 100/\$1.00
1000/\$8.00

8 PIN MINI DIP SOCKETS \$.32

10 PIN TO-5 TEFLON
PC SOCKETS \$.60

10 WATT ZENERS
3.9, 4.7 OR 18V \$.75 EA.
1. WATT ZENERS 5.6,
10, 12, 15, 18, OR 22V \$.40 EA.

Silicon Power Rectifiers

PRV	1A	3A	12A	50A
100	.06	.14	.30	.80
200	.07	.20	.35	1.15
400	.09	.25	.50	1.40
600	.11	.30	.70	1.80
800	.15	.35	.90	2.30
1000	.20	.45	1.10	2.75

REGULATED MODULAR POWER SUPPLIES

+ -15VDC AT 100ma \$24.95
15VAC INPUT
5VDC AT 1A, 115VAC INPUT \$19.95
12V .5A \$24.95

IN 4148 (IN914) 14/\$1.00
1103 1024 bit RAM \$4.75
NEC 6003 2048 bit RAM \$9.50
1101 256 bit RAM \$1.75
8223 PROM \$4.75
7489 RAM \$2.40

Terms: FOB Cambridge, Mass. Send
Check or Money Order. Include
Postage. Minimum Order \$5.00.
COD's \$20.00.

TRANSISTOR SPECIALS

2N1546 PNP GE TO-3	\$.95
2N5086 PNP Si TO-92	4/\$1.00
2N4898 PNP TO-66	\$.60
2N404 PNP GE TO-5	5/\$1.00
2N3919 NPN Si TO-3 RF	\$1.50
MPSA13 NPN Si TO-92	3/\$1.00
2N3767 NPN Si TO-66	\$.70
2N2222 NPN Si TO-18	5/\$1.00
2N3055 NPN Si TO-3	\$.80
2N3904 NPN Si TO-92	\$.70
2N3906 PNP Si TO-92	5/\$1.00
2N5296 NPN Si TO-220	\$.50
2N6109 PNP Si TO-220	\$.55
2N3866 NPN Si TO-5 Si RF POWER	\$.75
MJ252 NPN Si TO-66	\$.90
2N3638 NPN Si TO-5	5/\$1.00
2N6517 NPN TO-92 Si	3/\$1.00

CAPACITORS DO-33-A 3 DIG. LED
35V at 47 uF TANT 5/\$1.00
35V at 6.8 uF TANT 3/\$1.00
20V at 150 uF TANT \$.40
6V 30 uF TANT 5/\$1.00
12V 200 uF ELECT \$.30
200V 4.7 uF ELECT \$.30
DL 747 \$3.50
Full Wave Bridges
PRV 2A 6A 25A
200 .95 1.25 4.00
400 1.15 1.50 5.00
600 1.35 1.75 6.00

CD201 100X100 IMAGE SENSOR
CHARGED COUPLE DEVICES
USED IN SOLID STATE CAM-
ERAS, WITH APPLICATIONS.
\$145.00

FPA 711-7 LEVEL Diode Array
Optical Tape Readers \$5.95
Low cost Digital Volt Meter
Kit. Kit contains Imeg. Circuit
Schem., PC Boards, LED Dis-
plays, Regulator, Resistors, Ca-
pacitors and Transistors. Outer
case and battery not supplied.
Accurate to \pm one count, has
range of 1 mV to 1999 V DC.
Overall dimensions $1\frac{1}{2}$ " x $3\frac{1}{2}$ " x
5" \$62.00

TTL IC SERIES

74L00	30	7476	45
7400	14	7480	60
7401	17	7483	80
7402	14	7485	1.10
7403	17	7486	40
7404	21	7490	60
7405	20	7491	1.00
7406	35	7492	75
7407	37	7493	60
7408	18	7495	80
7409	22	7496	85
7410	17	8267	1.95
7411	27	74107	40
7412	45	74121	50
7413	72	74123	90
7414	1.75	74125	65
7416	37	74126	70
7417	37	74150	99
7420	17	74151	84
7425	36	74153	1.05
7426	27	74154	1.49
7427	31	74155	1.05
7430	17	74157	1.17
7432	27	74161	1.25
7437	36	74163	1.45
7438	35	75164	1.75
7440	17	74165	1.75
7441	95	74173	1.55
7442	90	74175	1.60
7445	1.05	74177	1.50
7446	1.10	74181	3.00
7447	1.00	74192	1.40
7448	1.00	74193	1.28
7472	33	74195	80
7473	38	74196	1.85
7474	35	75491	1.10
7475	60		

CT7001 CALENDAR ALARM
CLOCK CHIP \$6.95

SPDT MIN. TOGGLE SWITCH
MTA-106 \$1.50

DPDT MIN. TOGGLE SWITCH
MTA-206 \$2.25

C/MOS (DIODE CLAMPED)

74C02	\$.55	CD4019	\$.58
74C10	\$.60	CD4022	\$1.25
74C157	\$2.15	CD4023	\$.30
CD4001	\$.30	CD4024	\$1.00
CD4002	\$.30	CD4025	\$.33
CD4006	\$1.50	CD4026	\$3.20
CD4007	\$.30	CD4027	\$1.23
CD4009	\$.67	CD4028	\$1.09
CD4010	\$.65	CD4029	\$1.42
CD4011	\$.30	CD4030	\$.30
CD4012	\$.30	CD4035	\$1.42
CD4013	\$.53	CD4042	\$.84
CD4015	\$1.17	CD4046	\$2.50
CD4016	\$.65	CD4047	\$3.10
CD4017	\$1.35	CD4050	\$.58
CD4018	\$1.25	CD4055	\$2.70

CD 110 LINEAR 256 X1 BIT SELF
SCANNING CHARGED COUPLED
DEVICE, WITH DATA \$125.00

SANKEN AUDIO POWER AMPS

SI 1010 G 10 WATTS	\$ 6.90
SI 1020 G 20 WATTS	\$13.95
SI 1050 G 50 WATTS	\$24.95

LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$1.50
723 -40 +40V REGULATOR	\$.58
301/748-Hi Per. Op. Amp.	\$.30
320T, 5, 12 or 15V Negative Reg.	\$1.50
741A or 741C OP. AMP.	\$.31
709C OPER. AMP.	\$.25
307 OP. AMP	\$.25
CA 3047 HI PERF. OP. AMP	\$.95
CA 3089 FM IF SYSTEM	\$3.25
340T-5, 8, 12, 15, 18, 24V POS. REG. TO-220	\$1.75
101 OPER. AMP. HI PERFORM.	\$.75
LM 308 Oper. Amp., Low Power	\$1.05
747-DUAL 741	\$.65
556-DUAL TIMER	\$1.30
537-PRECISION OP. AMP.	\$2.60
LM 3900-QUAD OP. AMP.	\$.49
LM 324-QUAD 741	\$1.70
560-PHASE LOCK LOOP	\$2.50
561-PHASE LOCK LOOP	\$2.50
565-PHASE LOCK LOOP	\$1.75
566 FUNCTION GEN.	\$2.50
567-TONE DECODER	\$2.00
703-RF IF AMP.	\$.41
8038 IC VOLT. CONT. OSC	\$4.50
LM370-AGC SQUELCH AMP.	\$1.15
555-2.5s-2 HR. TIMER	\$.65
553 QUAD TIMER	\$3.50
FCD 810 OPTO-ISOLATOR	\$1.35
1456 OP. AMP.	\$.95
1458 DUAL OP. AMP	\$.65
LM 380-2W AUDIO AMP	\$1.29
LM 377-2W Stereo Audio Amp.	\$2.50
LM 381-STEREO PREAMP	\$1.69
LM 382-DUAL AUDIO PREAMP	\$1.69
LM 311-HI PER. COMPARATOR	\$.95
LM 319-Dual Hi Speed Comp.	\$1.15
LM 339-QUAD COMPARATOR	\$1.25

TRIACS SCR'S

PRV	1A	10A	25A	1.5A	6A	35A
100	.40	.70	1.30	.40	.50	1.20
200	.70	1.10	1.75	.60	.70	1.60
400	1.10	1.60	2.60	1.00	1.20	2.20
600	1.70	2.30	3.60		1.50	3.00

Send 20c for our catalog featuring
Transistors and Rectifiers
145 Hampshire St., Cambridge, Mass.

WE SHIP OVER 95%
OF OUR ORDERS THE
DAY WE RECEIVE THEM



SOLID STATE SALES

P.O. BOX 740
SOMERVILLE, MASS. 02143 TEL. 617 547-4005

7400N TTL					
SN7400N	16	SN74451N	27	SN74151N	1.25
SN7401N	16	SN74452N	27	SN74153N	1.35
SN7402N	21	SN74453N	41	SN74154N	1.25
SN7403N	16	SN74454N	25	SN74155N	1.21
SN7404N	21	SN74456N	47	SN74156N	1.30
SN7405N	24	SN74470N	45	SN74157N	1.30
SN7406N	25	SN74472N	39	SN74160N	1.75
SN7407N	45	SN74473N	45	SN74162N	1.45
SN7408N	25	SN74474N	45	SN74163N	1.65
SN7409N	25	SN74475N	80	SN74164N	1.65
SN7410N	20	SN74476N	47	SN74165N	1.65
SN7411N	30	SN74478N	50	SN74166N	1.70
SN7412N	47	SN74482N	1.75	SN74167N	5.50
SN7413N	85	SN74483N	1.15	SN74168N	3.00
SN7414N	70	SN74485N	1.12	SN74172N	18.00
SN7415N	43	SN74486N	45	SN74173N	1.70
SN7416N	33	SN74488N	3.50	SN74174N	1.95
SN7417N	25	SN74489N	3.00	SN74175N	1.95
SN7418N	21	SN74490N	59	SN74176N	90
SN7419N	39	SN74491N	1.20	SN74177N	3.00
SN7420N	37	SN74492N	82	SN74180N	1.05
SN7421N	37	SN74493N	87	SN74181N	3.55
SN7422N	37	SN74494N	91	SN74182N	95
SN7423N	42	SN74495N	91	SN74184N	2.30
SN7424N	26	SN74496N	91	SN74185N	2.30
SN7425N	31	SN74500N	1.25	SN74186N	1.05
SN7426N	41	SN74501N	45	SN74187N	95
SN7427N	37	SN74502N	45	SN74188N	2.30
SN7428N	42	SN74503N	45	SN74189N	2.30
SN7429N	21	SN74504N	1.75	SN74190N	1.50
SN7430N	25	SN74505N	1.75	SN74191N	1.50
SN7431N	1.05	SN74506N	1.15	SN74192N	1.50
SN7432N	1.10	SN74507N	45	SN74193N	1.40
SN7433N	1.08	SN74508N	1.75	SN74194N	1.40
SN7434N	1.05	SN74509N	7.00	SN74195N	1.45
SN7435N	1.10	SN74510N	1.15	SN74196N	1.75
SN7436N	89	SN74511N	1.15	SN74197N	1.00
SN7437N	99	SN74512N	6.00	SN74198N	2.25
SN7438N	26	SN74513N	7.00	SN74199N	2.25
SN7439N	26	SN74514N	7.00	SN74200N	2.25
SN7440N	21	SN74515N	1.15	SN74201N	2.25
SN7441N	21	SN74516N	1.15	SN74202N	2.25
SN7442N	21	SN74517N	1.15	SN74203N	2.25
SN7443N	1.08	SN74518N	2.50	SN74204N	2.25
SN7444N	1.05	SN74519N	1.50	SN74205N	2.25
SN7445N	1.15	SN74520N	1.50	SN74206N	2.25
SN7446N	1.15	SN74521N	1.50	SN74207N	2.25
SN7447N	1.15	SN74522N	1.50	SN74208N	2.25
SN7448N	99	SN74523N	1.50	SN74209N	2.25
SN7449N	26	SN74524N	1.50	SN74210N	2.25
20% Discount for 100 Combined 7400's					
CMOS					
C04000	25	C04001	25	C1400N	65
C04001	25	C04002	25	C14020N	65
C04002	25	C04003	65	C14030N	65
C04003	65	C04004	2.85	C14042N	2.15
C04004	2.85	C04005	1.45	C14073N	2.15
C04005	1.45	C04006	1.90	C14074	1.15
C04006	1.90	C04007	1.50	C14075N	1.15
C04007	1.50	C04008	1.50	C14080N	3.00
C04008	1.50	C04009	2.15	C14095N	2.00
C04009	2.15	C04010	2.75	C14097N	1.75
C04010	2.75	C04011	2.90	C14107N	1.75
C04011	2.90	C04012	2.90	C14151	2.90
C04012	2.90	C04013	2.90	C14154	3.00
C04013	2.90	C04014	2.90	C14155	2.15
C04014	2.90	C04015	2.98	C14160N	2.35
C04015	2.98	C04016	3.25	C14161	3.75
C04016	3.25	C04017	3.75	C14163	3.00
C04017	3.75	C04018	4.45	C14164	3.75
C04018	4.45	C04019	4.45	C14173	2.60
C04019	4.45	C04020	4.45	C14183	2.75
C04020	4.45	C04021	4.45	C14184	2.75
C04021	4.45	C04022	4.45	C14185	2.75
C04149	4.45	C04150	4.45	C14313	2.75
C04150					

JAMES FALL SPECIALS

DIODES

IN4001 50V @ 1 Amp 15/51.00
IN4002 100V @ 1 Amp 15/51.00
IN4003 200V @ 1 Amp 15/51.00
IN4004 400V @ 1 Amp 15/51.00
IN4148 Switching 20/51.00

TRANSISTORS

2N2907A PNP Switching 6/51.00
2N2222A NPN Switching 6/51.00
2N3904 NPN Amp 6/51.00
2N3906 PNP Amp 6/51.00
2N9511 NPN RF 6/51.00
C19681 3.6 Amp SCR 2/51.00

TTL/LINEAR

7400 Gate 7/51.00
7401 Inverter 7/51.00
7402 2-Input AND 7/51.00
7403 3-Input AND 7/51.00
7404 4-Input AND 7/51.00
7405 5-Input AND 7/51.00
7406 6-Input AND 7/51.00
7407 7-Input AND 7/51.00
7408 8-Input AND 7/51.00
7409 9-Input AND 7/51.00
7410 10-Input AND 7/51.00
7411 11-Input AND 7/51.00
7412 12-Input AND 7/51.00
7413 13-Input AND 7/51.00
7414 14-Input AND 7/51.00
7415 15-Input AND 7/51.00
7416 16-Input AND 7/51.00
7417 17-Input AND 7/51.00
7418 18-Input AND 7/51.00
7419 19-Input AND 7/51.00
7420 20-Input AND 7/51.00
7421 21-Input AND 7/51.00
7422 22-Input AND 7/51.00
7423 23-Input AND 7/51.00
7424 24-Input AND 7/51.00
7425 25-Input AND 7/51.00
7426 26-Input AND 7/51.00
7427 27-Input AND 7/51.00
7428 28-Input AND 7/51.00
7429 29-Input AND 7/51.00
7430 30-Input AND 7/51.00
7431 31-Input AND 7/51.00
7432 32-Input AND 7/51.00
7433 33-Input AND 7/51.00
7434 34-Input AND 7/51.00
7435 35-Input AND 7/51.00
7436 36-Input AND 7/51.00
7437 37-Input AND 7/51.00
7438 38-Input AND 7/51.00
7439 39-Input AND 7/51.00
7440 40-Input AND 7/51.00
7441 41-Input AND 7/51.00
7442 42-Input AND 7/51.00
7443 43-Input AND 7/51.00
7444 44-Input AND 7/51.00
7445 45-Input AND 7/51.00
7446 46-Input AND 7/51.00
7447 47-Input AND 7/51.00
7448 48-Input AND 7/51.00
7449 49-Input AND 7/51.00
7450 50-Input AND 7/51.00

CLOCK & CALC. CHIPS

MM5311N 6 Digit 3/95
MM5312N 4 Digit 3/95
MM5313N 6 Digit 3/95
MM5314N 6 Digit 3/95
MM5315N 6 Digit 3/95
MM5400N 6 Digit 3/95

4' POWER SUPPLY CORDS . . .

Black SPECIAL 3/\$1.00

THUMBWHEEL SWITCHES

2N2907A PNP Switching 6/51.00
2N2222A NPN Switching 6/51.00
2N3904 NPN Amp 6/51.00
2N3906 PNP Amp 6/51.00
2N9511 NPN RF 6/51.00
C19681 3.6 Amp SCR 2/51.00

POCKET CALCULATOR KIT

5 function plus constant - addressable memory with individual recall - 8 digit display plus overflow - battery saver - use standard or rechargeable batteries - all necessary parts in ready to assemble form - instructions included 3" x 5" SPECIAL \$12.95 each

394" DIAM. TRIMMER

STANDARD RESISTANCE VALUES
Model TR II
SPECIAL \$4.00

1/16 VECTOR BOARD

12 or 24 Hour 115 Vac 25 VOLTAGE DIVISION
Wattage Case 6" x 3" x 1"
KIT - All Comp. & Case - \$34.95
Wired & Assembled - \$39.95

NEW PROTO BOARD-100

Here's a low cost, big 10 IC capacity breadboard kit with all the quality of Q1 Sockets and the best of the Proto-Board series - complete down to the last nut, bolt and screw. Includes:
2 07 355 Sockets, 1 Q1 358 Bus Strip,
2 5 way binding posts, 4 rubber feet,
screws, nuts, bolts, and easy assembly instructions.

COMPLETE KIT... *Special \$17.95

DISPLAY LEDS

FN700 Com. Cath. 250 .69
MAN 1 Com. An. 270 \$1.95
MAN 2 5x7 Matrix 300 3.95
MAN 3 Com. Cath. 125 .39
MAN 4 Com. Cath. 187 .95
MAN 7 Com. An. 30 1.50
DL33 Com. Cath. 125 .39
DL47 Com. An. 625 2.50

DISCRETE LEDS

MV 10 Red 5/51.00
MV 50 Red 6/51.00
MV 502A Red 5/51.00
MV 502A Green 4/51.00
MV 502A Yellow 4/51.00
MV 502A Orange 4/51.00
MV 502A Red 1K Leads 5/51.00

IC SOLDER TAIL - LOW PROFILE (TIN) SOCKETS

1.24 25.49 50-100 1.24 25.49 50-100
8 pin \$1.17 16 15 24 pin \$3.38 37 36
14 pin \$2.20 22 23 28 pin \$4.45 44 43
16 pin \$2.20 22 23 36 pin \$5.99 58
18 pin \$2.20 22 23 40 pin \$6.32 62 61
22 pin \$3.38 37 36

SOLDER TAIL STANDARD (TIN)

14 pin \$3.38 37 28 pin \$3.99 90 81
16 pin \$3.38 37 28 pin \$3.99 90 81
18 pin \$3.38 37 40 pin \$3.99 90 81
24 pin \$3.38 37 40 pin \$3.99 90 81

SOLDER TAIL STANDARD (GOLD)

8 pin \$3.38 37 24 pin \$3.99 90 81
14 pin \$3.38 37 28 pin \$3.99 90 81
16 pin \$3.38 37 36 pin \$3.99 90 81
18 pin \$3.38 37 40 pin \$3.99 90 81

WIRE WRAP SOCKETS (GOLD) LEVEL 4

10 pin \$4.45 41 37 24 pin \$1.05 85 85
14 pin \$3.38 37 28 pin \$3.99 90 81
16 pin \$3.38 37 36 pin \$3.99 90 81
18 pin \$3.38 37 40 pin \$3.99 90 81

50 PCS. RESISTOR ASSORTMENTS \$1.75 PER ASST.


ASST. 1 5e: 10 OHM 12 OHM 15 OHM 18 OHM 22 OHM 27 OHM 33 OHM 39 OHM 47 OHM 56 OHM 1/4 WATT 5% - 50 PCS.
ASST. 2 5e: 68 OHM 82 OHM 100 OHM 120 OHM 150 OHM 180 OHM 220 OHM 270 OHM 330 OHM 390 OHM 1/4 WATT 5% - 50 PCS.
ASST. 3 5e: 470 OHM 560 OHM 680 OHM 820 OHM 1K 1/4 WATT 5% - 50 PCS.
ASST. 4 5e: 1.2K 1.5K 1.8K 2.2K 2.7K 1/4 WATT 5% - 50 PCS.
ASST. 5 5e: 3.3K 3.9K 4.7K 5.6K 6.8K 1/4 WATT 5% - 50 PCS.
ASST. 6 5e: 8.2K 10K 12K 15K 18K 1/4 WATT 5% - 50 PCS.
ASST. 7 5e: 22K 27K 33K 39K 47K 1/4 WATT 5% - 50 PCS.
ASST. 8 5e: 56K 68K 82K 100K 120K 1/4 WATT 5% - 50 PCS.
ASST. 9 5e: 150K 180K 220K 270K 330K 1/4 WATT 5% - 50 PCS.
ASST. 10 5e: 390K 470K 560K 680K 820K 1/4 WATT 5% - 50 PCS.
ASST. 11 5e: 1M 1.2M 1.5M 1.8M 2.2M 1/4 WATT 5% - 50 PCS.
ASST. 12 5e: 2.7M 3.3M 3.9M 4.7K 5.6K 1/4 WATT 5% - 50 PCS.

PRIME INTEGRATED CIRCUIT ASSORTMENTS

ASST. 8 3ea: SN7400 7401 7402 7403 7404 SSI/TTL \$9.95 ASST.
ASST. 9 2ea: SN7401 7402 7403 7404 7405 MS/TTL \$9.95 ASST.
ASST. 10 2ea: CD4001 4002 4011 4012 4013 CMOS \$7.95 ASST.
ASST. 11 2ea: LM3011 3012 3021 3027 308K LINEAR \$10.95 ASST.

IC'S EXAR KITS

FUNCTION GENERATOR KIT

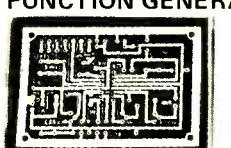

features sine, triangle and square wave.
THD 0.5% typ.
AM/PM capability

XR-2206KA

Includes monolithic function generator IC, PC board, and assembly instruction manual.

XR-2206KB

Same as XR-2206KA above and includes external components for PC board.

TIMERS

XR-555CP Monolithic Timer SPECIAL \$.69
XR-320P Precision Timer 1.55
XR-555CP Dual 555 Timer 1.85
XR-2556CP Dual Timing Circuit 3.20
XR-2240CP Programmable Counter/Timer SPECIAL 3.25

PHASE LOCKED LOOPS

XR-210 FSK Demodulator 5.20
XR-215 High Frequency PLL 6.60
XR-567CT Tone Decoder (mini DIP) 1.95
XR-567CT Tone Decoder (T.O-5) SPECIAL .99

STEREO DECODERS

XR-1310P PLL Stereo Decoder 3.20
XR-1310EP PLL Stereo Decoder 3.20
XR-1800P PLL Stereo Decoder 3.20

WAVEFORM GENERATORS

XR-205 Waveform Generator 8.40
XR-2206CP Monolithic Function Generator SPECIAL 4.49
XR-2207CP Voltage Controlled Oscillator 3.85

OTHER EXAR IC'S

XR-1488CN Dual +15V Tracking Regulator SPECIAL 2.95
XR-1488N Quad Line Driver 5.80
XR-1489AN Quad Line Receiver 4.80
XR-2208CP Operational Multiplier 5.20
XR-2211 CP FSK Demodulator/Tone Decoder 6.70
XR-2261 Monolithic Proportional Servo IC System w/4 ea. Driver Transistor 3.79

Special Requested Items

RC4194 Dual Track V Reg \$5.55 NB191 \$3.00 2533 \$7.95
RC4195 15V Track Reg 3.25 402AP 2.25 6283 \$7.95
F9368 Decoder 3.95 2513 11.00 8787 2.75
L1011011 DVM Chip Set 28.00 2518 7.00 8268 1.15
CA3130 Super CMOS Op Amp 8.95 2524 3.50 8826 3.00
MC1408L7 A/D 8.95 2525 6.00 8880 1.35
F3341 FFO 8.95 2527 5.00 7497 5.00


ZENERS-DIODES-RECTIFIERS

TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE
IN746	3.3	400m	4/1.00	IN4003	200 PIV	1 AMP	1.00
IN751A	5.1	400m	4/1.00	IN4004	400 PIV	1 AMP	1.00
IN752	5.6	400m	4/1.00	IN3600	50 200m	6/1.00	
IN753	6.2	400m	4/1.00	IN4148	75 10m	15 1.00	
IN754	6.8	400m	4/1.00	IN4150	75 10m	12/1.00	
IN755	7.5	400m	4/1.00	IN4174	5.6 1w	28	
IN5232	5.6	500m	28	IN4135	6.2 1w	28	
IN5234	6.2	500m	28	IN4176	6.8 1w	28	
IN5235	6.8	500m	28	IN4178	8.2 1w	28	
IN5236	7.5	500m	28	IN4172	12 1w	28	
IN456	25	61.00	IN4144	15 1w	28		
IN458	150	70	61.00	IN1183	50 PIV	35 AMP	1.60
IN485A	180	40m	51.00	IN1184	100 PIV	35 AMP	1.70
IN4001	50 PIV	1 AMP	09	IN1186	200 PIV	35 AMP	1.80
IN4002	100 PIV	1 AMP	10	IN1188	100 PIV	35 AMP	3.00

TRANSISTORS

TYPE	PRICE	TYPE	PRICE
MPS A06 5/51.00	PN3567 3/51.00	PN3570 4/51.00	
2N2219A 3/51.00	PN3568 4/51.00	2N4400 4/51.00	
2N2221 4/51.00	PN3569 4/51.00	2N4401 4/51.00	
2N2222 4/51.00	2N3104 5/51.00	2N4402 4/51.00	
2N2369 5/51.00	2N3705 5/51.00	2N4403 4/51.00	
2N2380A 5/51.00	2N3706 5/51.00	2N4409 4/51.00	
2N2401 5/51.00	2N3707 5/51.00	2N5086 4/51.00	
2N2402 5/51.00	2N3711 5/51.00	2N5087 4/51.00	
2N2403 5/51.00	2N3712 5/51.00	2N5088 4/51.00	
2N2404 5/51.00	2N3713 5/51.00	2N5089 4/51.00	
2N2405 5/51.00	2N3714 5/51.00	2N5090 4/51.00	
2N2406 5/51.00	2N3715 5/51.00	2N5091 4/51.00	
2N2407 5/51.00	2N3716 5/51.00	2N5092 4/51.00	
2N2408 5/51.00	2N3717 5/51.00	2N5093 4/51.00	
2N2409 5/51.00	2N3718 5/51.00	2N5094 4/51.00	
2N2410 5/51.00	2N3719 5/51.00	2N5095 4/51.00	
2N2411 5/51.00	2N3720 5/51.00	2N5096 4/51.00	
2N2412 5/51.00	2N3721 5/51.00	2N5097 4/51.00	
2N2413 5/51.00	2N3722 5/51.00	2N5098 4/51.00	
2N2414 5/51.00	2N3723 5/51.00	2N5099 4/51.00	
2N2415 5/51.00	2N3724 5/51.00	2N5100 4/51.00	
2N2416 5/51.00	2N3725 5/51.00	2N5101 4/51.00	
2N2417 5/51.00	2N3726 5/51.00	2N5102 4/51.00	
2N2418 5/51.00	2N3727 5/51.00	2N5103 4/51.00	
2N2419 5/51.00	2N3728 5/51.00	2N5104 4/51.00	
2N2420 5/51.00	2N3729 5/51.00	2N5105 4/51.00	

VECTOR WIRE PENCIL \$9.50

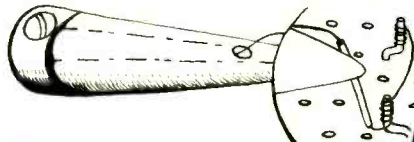

This hand-held tool guides and wraps #36 insulated wire (from a self-contained bobbin) onto component terminals. Make connections by soldering; iron heat melts insulation, permitting good solder bond. A super fast way to work with Vectorboard. With tool, installed bobbin with 250 ft wire, extra bobbin, instructions. Add shipping for 1 pound.

VECTORBOARD, PATTERN "P" PRE-PUNCHED TYPE ALSO AVAILABLE.
8 1/2" x 17" epoxy glass. \$8.95
+ 1 lb. shipping per board.

FLAT, MULTICONDUCTOR RIBBON CABLE NOW AVAILABLE IN MULTIPLES OF 10 CONDUCTORS UP TO 100 CONDUCTORS. 20 FOOT LENGTHS ONLY. COSTS 1¢ PER CONDUCTOR FOOT.

1/2 AMP POWER SUPPLY KITS
SPECIFY 5, 6, 8, OR 12 V.
\$7.95 + 2 LBS SHIPPING

Terms: Orders under \$10 add 50¢. Add shpg where shown. Cal res add tax. No COD.

Get Your MITTS on a

GODBOUT RAM KIT 4Kx8 \$131.07 4/10¢ PER BIT

COMPATIBLE ALTAIR 8800 & OTHER 8 BIT MACHINES
Tri-state buffered out drives 20 TTL loads; good buss drive, low noise susceptibility. Extend feature, memory protect. On board voltage regulation. PRESENTS 1 LPTTL LOAD TO ALTAIR & OTHER BUSES.
-----"THE WHOLE BALL OF WAX", SAYS BILL-----

THE SECRET'S OUT!

THE SECRET MICROCOMPUTER COMPANY IS NATIONAL SEMICONDUCTOR, AND WE'VE GOT THEIR PACE IC... A POWERFUL 16 BIT MICROPROCESSOR IN A 40 PIN DIP AVAILABLE NOW... \$125

LOW POWER EROM BOARD

4K X 8 \$200 ADD \$25 & WE'LL PROGRAM
2K X 8 \$125 ADD \$15 & WE'LL PROGRAM

Put your editor/ assembler or whatever in it. PLUG-IN ALTAIR COMPATIBLE. Fast (1 usec 1 wait). Low power--board runs cool.

MASTERCHARGE® BANKAMERICARD® CALL (415) 357-7007, 24 HRS.


BILL GODBOUT ELECTRONICS

BOX 2355

OAKLAND AIRPORT

CALIFORNIA 94614

Circle 90 on reader service card

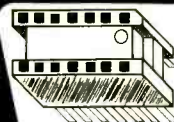


SOCKET SPECIAL

(G) Gold plated contacts (T) Bright tin
14 pin T...11/\$1.95 14 pin G...10/\$1.95
16 pin G...10/\$3.75 24 pin T...5/\$1.95
28 pin T...5/\$1.95 40 pin T...5/\$2.95
LOW PROFILE SOCKETS:
16 pin G...10/\$1.95; 40-pin G...5/\$2.95

WE'VE GOT THAT 16 BIT MICROCOMPUTER KIT YOU WANTED... WRITE FOR DETAILS

CPU BOARD***1K x 16 INTEGRAL RAM***
SERIAL I/O INTERFACE***POWER SUPPLY
AUDIO CASSETTE I/OINTERFALE & EDITOR ASSEMBLER PROGRAMS***

CHEAP CLOCK

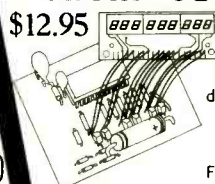

\$12.95 parts mount on mother board; readout and lens mount on daughter board. Readout may be removed. FULL 6 DIGITS less case & transformer

This ad is the iceberg's tip. Send stamp + address for flyer for the whole story, from CMOS to linears to parts to musician's kits to...

CB SPECIALS-R.F. DRIVERS-R.F. POWER OUTPUTS-FETS

2SC481	1.85	2SC778	3.25	2SC1237	4.50	2SD235	1.00	2SK33	1.20
2SC482	1.75	2SC797	2.50	2SC1239	3.50	MRFB004	3.00		
2SC495T	1.75	2SC798	3.10	2SC1243	3.50	4004	3.00	3SK40	4.50
2SC517	4.75	2SC781	3.00	2SC1306	4.75	4005	3.00	3SK45	4.50
2SC710	.70	2SC789	1.00	2SC1307	5.75	40080	1.25	3SK49	4.50
2SC711	.70	2SC799	4.25	2SC1377	5.50	40081	1.50		
2SC735	.70	2SC1013	1.50	2SC1449	3.50	40082	3.00		
2SC756	3.00	2SC1014	1.50	2SC1678	5.75	SK3048	3.25	IN34	.25
2SC773	.85	2SC1017	1.50	2SC1679	5.75	SK3049	4.75	IN60	.25
2SC774	1.75	2SC1018	1.50	2SC1728	3.75			IS1555	.35
2SC775	2.75	2SC1173	1.25	2SC1816	5.50	2SK19	1.75		
2SC776	3.00	2SC1226A	1.25	2SC1957	3.50	2SK30	1.00		

JAPANESE TRANSISTORS

2SA52	.60	2SB187	.60	2SC458	.70	2SC793	2.50	2SC1509	1.25
2SA316	.75	2SB235	1.75	2SC460	.70	2SC815	.75	2SC1569	1.25
2SA473	.75	2SB303	.65	2SC478	.80	2SC828	.75	2SC1756	1.25
2SA483	1.95	2SB324	1.00	2SC491	2.50	2SC829	.75		
2SA489	.80	2SB337	2.10	2SC495	.70	2SC830	1.60	2SD30	.95
2SA490	.70	2SB367	1.60	2SC497	1.60	2SC839	.85	2SD45	2.00
2SA505	.70	2SB370	.65	2SC515	.80	2SC945	.65	2SD65	.75
2SA564	.50	2SB405	.85	2SC535	.95	2SC1010	.80	2SD68	.90
2SA628	.65	2SB407	1.65	2SC536	.65	2SC1012	.80	2SD72	1.00
2SA643	.85	2SB415	.85	2SC537	.70	2SC1051	2.50	2SD88	1.50
2SA647	2.75	2SB461	1.25	2SC563	2.50	2SC1061	1.65	2SD151	2.25
2SA673	.85	2SB463	1.65	2SC605	1.00	2SC1079	3.75	2SD170	2.00
2SA679	3.75	2SB471	1.75	2SC620	.80	2SC1096	1.20	2SD180	2.75
2SA682	.85	2SB474	1.50	2SC627	1.75	2SC1098	1.15	2SD201	1.95
2SA699	1.30	2SB476	1.25	2SC642	3.50	2SC1115	2.75	2SD218	4.75
2SA699A	1.75	2SB481	2.10	2SC643	3.75	2SC1166	.70	2SD300	2.50
2SA705	.55	2SB492	1.25	2SC644	.70	2SC1170	4.00	2SD313	1.10
2SA815	.85	2SB495	.95	2SC681	2.50	2SC1172B	4.25	2SD315	.75
2SA816	.85	2SB507	.90	2SC684	2.10	2SC1209	.55	2SD318	.95
		2SB511	.70	2SC687	2.50	2SC1213	.75	2SD341	.95
				2SC696	2.35	2SC1226	1.25	2SD350	3.25
2SB22	.65			2SC712	.70	2SC1243	1.50	2SD352	.80
2SB54	.70	2SC206	1.00	2SC713	.70	2SC1293	.85	2SD380	5.70
2SB56	.70	2SC240	1.10	2SC732	.70	2SC1308	4.75	2SD389	.90
2SB77	.70	2SC261	.65	2SC733	.70	2SC1347	.80	2SD390	.75
2SB128	2.25	2SC291	.65	2SC739	.70	2SC1383	.75	2SD437	5.50
2SB135	.95	2SC320	.75	2SC756	2.00	2SC1409	1.25		
2SB152	4.50	2SC352	.75	2SC762	1.90	2SC1410	1.25	C106B1	.50
2SB173	.55	2SC353	.75	2SC783	1.00	2SC1447	1.25		
2SB175	.55	2SC371	.70	2SC784	.70	2SC1448	1.25		
2SB178	1.00	2SC372	.70	2SC785	1.00	2SC1507	1.25		
2SB186	.60	2SC394	.70						

POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204	1300V	3.90	BU207	1300V	5.40	2SC1172B	1100V	4.25
BU205	1500V	4.70	BU208	1500V	6.25	2SC1308	1100V	4.95
BU206	1700V	5.90	2SC1170	1100V	4.00	2SC1325	1100V	4.95

OEM SPECIALS

1N270	.10	2N960	.40	2N2219A	.25	2N2913	.75	2N3740	1.00	2N4401	.20
1N914	.10	2N962	.40	2N2221	.20	2N2914	1.20	2N3771	1.75	2N4402	.20
		2N967	.40	2N2221A	.20	2N2916A	3.65	2N3772	1.90	2N4403	.20
2N173	1.75	2N1136	1.15	2N2222	.20	2N3019	1.20	2N3773	2.10	2N4409	.20
2N178	.90	2N1142	1.85	2N2222A	.20	2N3053	.30	2N3819	.25	2N440	.25
2N327A	1.15	2N1302	.25	2N2270	.30	2N3054	.70	2N3823	.55	2N446	.75
2N334	1.20	2N1305	.30	2N2322	1.45	2N3055	.75	2N3856	.20	2N441	.85
2N336	.90	2N1377	1.15	2N2323	1.50	2N3227	1.90	2N3866	.85	2N442	.90
2N338A	1.05	2N1420	.20	2N2324	1.85	2N3247	3.40	2N3903	.20	2N443	1.20
2N398B	.90	2N1483	.95	2N2325	2.00	2N3250	.40	2N3904	.20	2N448	.55
2N404	.20	2N1540	.90	2N2326	2.85	2N3375	4.80	2N3905	.20	2N501	.25
2N443	1.00	2N1543	2.70	2N2327	3.80	2N3393	.20	2N3906	.25	2N504	.40
2N456	1.10	2N1544	.80	2N2328	4.20	2N3394	.20	2N3925	4.25	2N510	.20
2N501A	3.00	2N1549	.95	2N2329	5.75	2N3414	.20	2N3954	4.35	2N513	.15
2N508A	.30	2N1551	3.20	2N2368	.25	2N3415	.25	2N3954A	4.40	2N518	.15
2N555	.45	2N1552	3.25	2N2369	.20	2N3416	.30	2N3955	2.85	2N518	3.75
2N652A	.85	2N1554	1.70	2N2484	.20	2N3417	.30	2N3957	1.25	2N524	.60
2N677C	4.85	2N1557	1.50	2N2712	.25	2N3442	1.85	2N3958	1.20	2N526	.40
2N706	.20	2N1560	2.80	2N2894	.40	2N3553	1.50	2N4037	.60	2N536	.20
2N706B	.35	2N1605	.35	2N2903	3.30	2N3563	.20	2N4093	.85	2N534	.25
2N711	.35	2N1613	.30	2N2904	.20	2N3565	.20	2N4124	.20	2N539	.25
2N711B	.50	2N1711	.30	2N2904A	.25	2N3638	.20	2N4126	.20	2N540	.50
2N718	.20	2N1907	4.10	2N2905	.20	2N3642	.20	2N4141	.20	2N541	.50
2N718A	.25	2N2060	1.85	2N2905A	.25	2N3643	.15	2N4142	.20	2N547	.35
2N720A	1.30	2N2102	.40	2N2906	.20	2N3645	.15	2N4143	.20	2N548	.35
2N918	.20	2N2218	.25	2N2906A	.25	2N3646	.10	2N4220A	.95		
2N930	.20	2N2218A	.30	2N2907	.20	2N3730	1.10	2N4234	1.20		
2N956	.20	2N2219	.20	2N2907A	.25	2N3731	1.60	2N4400	.20		

SILICON UNIJUNCTIONS

2N2646	To-18	.50
2N2647	To-18	.60
2N6027 PUT	To-92	.55
2N6028 PUT	To-92	.70
DSE37	To-18	.25

INTEGRATED CIRC.

UA703C	.40
709C OP. AMP.	.25
741C OP. AMP.	.25
CA3066	3.90
CA3068	6.35
MC1305	1.45
7400	.15

RECTIFIERS

	10	100
1N4001	.60	5.00
1N4002	.70	6.00
1N4003	.80	7.00
1N4004	.90	8.00
1N4005	1.00	9.00
1N4006	1.10	10.00
1N4007	1.20	11.00



New-Tone Electronics
P.O. Box 1738 A
Bloomfield, N.J. 07003
Phone: (201) 762-9020

ALL PARTS GUARANTEED AND TESTED ON PREMISES.

N.J. residents add 5% sales tax. Minimum order \$5.00. All orders add \$1.00 postage. Dealers write or phone for discount prices.

Circle 91 on reader service card

5% OFF ON ORDERS OVER \$50.00
10% OFF ON ORDERS OVER \$100.00
15% OFF ON ORDERS OVER \$250.00

TTL

7400	\$.14	7451	.17	74154	1.25
7401	.16	7453	.17	74155	1.07
7402	.15	7454	.17	74156	1.07
7403	.16	7460	.17	74157	.99
7404	.19	7464	.35	74158	1.79
7405	.19	7465	.35	74160	1.39
7406	.35	7470	.30	74161	1.25
7407	.35	7472	.30	74162	1.49
7408	.18	7473	.35	74163	1.39
7409	.19	7474	.35	74164	1.59
7410	.16	7475	.57	74165	1.59
7411	.25	7476	.39	74166	1.49
7413	.55	7483	.79	74170	2.30
7416	.35	7485	1.10	74173	1.49
7417	.35	7486	.40	74174	1.62
7420	.16	7489	2.48	74175	1.39
7422	.26	7490	.59	74176	.89
7423	.29	7491	.97	74177	.84
7425	.27	7492	.71	74180	.90
7426	.26	7493	.60	74181	2.98
7427	.29	7494	.94	74182	.79
7430	.20	7495	.79	74184	2.29
7432	.23	7496	.79	74185	2.29
7437	.35	74100	1.30	74187	5.95
7438	.35	74105	.44	74190	1.35
7440	.17	74107	.40	74191	1.35
7441	.98	74121	.42	74192	1.25
7442	.77	74122	.45	74193	1.19
7443	.87	74123	.85	74194	1.25
7444	.87	74125	.54	74195	.89
7445	.89	74126	.63	74196	1.25
7446	.93	74141	1.04	74197	.89
7447	.89	74145	1.04	74198	1.79
7448	1.04	74150	.97	74199	1.79
7450	.17	74151	.79	74200	5.90
		74153	.99		

LOW POWER TTL

74L00	\$.25	74LS1	\$.29	75L90	\$ 1.49
74L02	.25	74LS5	.33	74L91	1.45
74L03	.25	74L71	.25	74L93	1.69
74L04	.25	74L72	.39	74L95	1.69
74L06	.25	74L73	.49	74L98	2.79
74L10	.25	74L74	.49	74L164	2.79
74L20	.33	74L78	.79	74L165	2.79
74L30	.33	74L85	1.25		
74L42	1.49	74L86	.69		

HIGH SPEED TTL

74H00	\$.25	74H21	\$.25	74H55	\$.25
74H01	.25	74H22	.25	74H60	.25
74H04	.25	74H30	.25	74H61	.25
74H08	.25	74H40	.25	74H62	.25
74H10	.25	74H50	.25	74H72	.39
74H11	.25	74H52	.25	74H74	.39
74H20	.25	74H53	.25	74H76	.49

8000 SERIES

8091	\$.53	8214	\$ 1.49	8811	\$.59
8092	.53	8220	1.49	8812	.89
8095	1.25	8230	2.19	8822	2.19
8121	.80	8520	1.16	8830	2.19
8123	1.43	8551	1.39	8831	2.19
8130	1.97	8552	2.19	8836	.25
8200	2.33	8554	2.19	8880	1.19
8210	2.79	8810	.69	8263	5.79
				8267	2.59

9000 SERIES

9002	\$.35	9309	\$.79	9601	\$.89
9301	1.03	9312	.79	9602	.79

CMOS

4000A	\$.26	4016A	.56	4050A	.59
4001A	.25	4017A	1.19	4066A	.89
4002A	.25	4020A	1.49	4068A	.44
4006A	1.35	4021A	1.39	4069A	.44
4007A	.26	4022A	1.10	4071A	.26
4008A	1.79	4023A	.25	4072A	.35
4009A	.57	4024A	.89	4073A	.39
4010A	.54	4025A	.25	4075A	.39
4011A	.29	4027A	.59	4078A	.39
4012A	.25	4028A	.98	4081A	.26
4013A	.45	4030A	.44	4082A	.35
4014A	1.49	4035A	1.27	4528A	1.60
4015A	1.49	4042A	1.47	4585A	2.10
		4049A	.59		

74C00	\$.22	74C74	\$ 1.04	74C162	\$ 2.93
74C02	.26	74C76	1.34	74C163	2.66
74C04	.44	74C107	1.13	74C164	2.66
74C08	.68	74C151	2.61	74C173	2.61
74C10	.35	74C154	3.15	74C195	2.66
74C20	.35	74C157	1.76	80C95	1.35
74C42	1.61	74C160	2.48	80C97	1.13
74C73	1.04	74C161	2.93		

OCTOBER SPECIALS

SCHOOL TIME SPECIAL POCKET CALCULATOR KIT

5 function plus constant — addressable memory with individual recall — 8 digit display plus overflow — battery saver — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — instructions included



CALC KIT (WITH BATTERIES)	\$12.95
ASSEMBLED (WITH BATTERIES)	\$14.95
BATTERIES ONLY (DISPOSABLE) SET	\$ 2.00

8038 FUNCTION GENERATOR

Voltage controlled oscillator — sine, square, triangular output 16 PIN DIP \$3.95

MEMORIES

1101	256 bit RAM MOS	\$ 1.50
1103	1024 bit RAM MOS	3.95
2102	1024 bit static RAM	5.55
5203	2048 bit UV eras PROM	17.95
5260	1024 bit RAM	2.49
5261	1024 bit RAM	2.69
5262	2048 bit RAM	5.95
7489	64 bit ROM TTL	2.48
8223	Programmable ROM	3.69
74200	256 bit RAM tri-state	5.90

CALCULATOR & CLOCK CHIPS

5001	12 DIG 4 funct fix dec	\$3.45
5002	Same as 5001 exc btry pwr	3.95
5005	12 DIG 4 funct w/mem	4.95
MMS725	8 DIG 4 funct chain & dec	1.98
MMS736	18 pin 6 DIG 4 funct	4.45
MMS738	8 DIG 5 funct K & mem	5.35
MMS739	9 DIG 4 funct (btry sur)	5.35
MMS311	28 pin BCD 6 dig mux	4.45
MMS312	24 pin 1 pps BCD 4 dig mux	3.95
MMS313	28 pin 1 pps BCD 6 dig mux	4.45
MMS314	24 pin 6 dig mux	4.45
MMS316	40 pin alarm 4 dig	5.39

LED's

MV10B	Red TO 18	\$.22
MV50	Axial leads	.18
MV5020	Jumbo Vis. Red (Red Dome)	.22
	Jumbo Vis. Red (Clear Dome)	.22
ME4	Infra red diff. dome	.54
MAN1	Red 7 seg. .270"	2.19
MAN2	Red alpha num. .32"	4.39
MAN4	Red 7 seg. .190"	1.95
MAN5	Green 7 seg. .270"	3.45
MAN6	.6" high solid seq.	4.25
MAN7	Red 7 seg. .270"	1.19
MAN8	Yellow 7 seg. .270"	3.45
MAN66	.6" high spaced seq.	3.75
MCT2	Opto-iso transistor	.61

MULTIPLE DISPLAYS

NSN33	3 digit .12" red led 12 pin fits IC skt.	\$1.79
HP5082	5 digit .11 led magn. lens com. cath	3.49
FNA37	9 digit 7 seg led RH dec clr. magn. lens	4.95
SP-425-09	9 digit .25" neon direct interface with MOS/LSI, 180 VDC. 7 seg 1.79	

SHIFT REGISTERS

MM5013	1024 bit accum. dynamic	mDIP	\$1.75
MM5016	500/512 bit dynamic	mDIP	1.59
SL5-025	Dual 64 bit static	DIP	1.39

DTL

930	\$.15	937	.15	949	.15
932	.15	944	.15	962	.15
936	.15	946	.15	963	.15

5314 CLOCK CHIP

6 digit multiplexed 7 segment output, fast; slow set, 24 PIN DIP \$3.95

5739 CALCULATOR CHIPS

9 digit, 4 function, chain operation, 9 V battery operation, 16 sec turn-off 22 PIN DIP \$3.95

MEMORIES

1103	Fully decoded RAM MOS 1024 bit dynamic 18 PIN DIP	\$1.49
1702A	2048 bit static PROM electrically programmable and erasable, 24 PIN DIP	\$15.95
2102-2	1024 bit N channel static RAM 16 PIN DIP	\$3.95
5261	Fully decoded RAM MOS 1024 bit dynamic 18 PIN DIP	\$1.79

DTL

7402	Quad 2 input NOR gate	\$.13
7420	Dual 4 input NAND gate	.14
7446	BCD to 7 seg driver	.79
7460	Dual 4 input expander	.10
7493	4 bit binary counter	.51
74175	Quad D flip flop	1.25

Data sheets on request

With order add \$.30 for items less than \$1.00 ea.

LINEAR CIRCUITS

300	Pos V Reg (super 723)	TO-5	\$.71
301	Hi Perf Op Amp	mDIP TO-5	.29
302	Volt follower	TO-5	.53
304	Neg V Reg	TO-5	.80
305	Pos V Reg	TO-5	.71
307	Op AMP (super 741)	mDIP TO-5	.26
308	Micro Pwr Op Amp	mDIP TO-5	.89
309K	5V 1A regulator	DIP	1.35
310	V follower Op Amp	mDIP	1.07
311	Hi perf V Comp	mDIP TO-5	.95
319	Hi Speed Dual Comp	DIP	1.13
320	Neg Reg 5.2, 12, 15	TO-3	1.19
322	Precision Timer	DIP	1.70
324	Quad Op Amp	DIP	1.52
339	Quad Comparator	DIP	1.58
340K	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V)	TO-3	1.69
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V)	TO-220	1.49
372	AF-IF Strip detector	DIP	2.93
373	AM/FM/SSB Strip	DIP	.53
376	Pos V Reg	mDIP	2.42
377	2w Stereo amp	DIP	1.16
380	2w Audio amp	DIP	1.13
380-8	.6w Audio amp	mDIP	1.52
381	Ln Noise Dual preamp	DIP	1.52
382	Lo Noise Dual preamp	DIP	.71
550	Pres V Reg	DIP	.89
555	Timer	mDIP	.89
555A	Dual 555 Timer	DIP	1.49
560	Phase Locked Loop	DIP	2.48
562	Phase Locked Loop	DIP	2.48
565	Phase Locked Loop	DIP TO-5	2.38
566	Function Gen	mDIP TO-5	2.25
567	Tone Decoder	mDIP	2.66
709	Operational AMPL	TO-5 or DIP	.26
710	Hi Speed Volt Comp	DIP	.35
711	Dual Difference Compar	DIP	.26
723	V Reg	DIP	.62
739	Dual Hi Perf Op Amp	DIP	1.07
741	Comp Op AMP	mDIP TO-5	.32
747	Dual 741 Op Amp	DIP or TO-5	.71
748	Freq Adj 741	mDIP	.35
1304	FM Mulp Stereo Demod	DIP	1.07
1307	FM Mulp Stereo Demod	DIP	.74
1458	Dual Comp Op Amp	mDIP	.62
1800	Stereo multiplexer	DIP	2.48
LH2111	Dual LM 211 V Comp	DIP	1.70
3065	TV-FM Sound System	DIP	.62
3075	FM Det-LMTR & Audio preamp	DIP	.71
3900	Quad Amplifier	DIP	.35
7524	Core Mem Sense AMPL	DIP	.71
8864	9 DIG Led Cath Drvr	DIP	2.25
75150	Dual Line Driver	DIP	1.75
75451	Dual Peripheral Driver	mDIP	.35
75452	Dual Peripheral Driver	mDIP	.35
75453	(351) Dual Periph Driver	mDIP	.35
75491	Quad Seq Driver for LED	DIP	.71
75492	Hex Digit driver	DIP	.80

Satisfaction guaranteed. Shipment will be made via first class mail within 3 days from receipt of order. Add \$.50 to cover shipping and handling for orders under \$25.00. Minimum order \$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED

P.O. BOX 1708/ MONTEREY, CA. 93940 USA

PHONE (408) 659-3171



Olson

Electronics Parts and Accessories

SALE

DUAL IN-LINE IC'S

Made in U.S. These IC's are guaranteed against defects. With diagram. Shpg. wt. 1/4 lb.

LOW AS 29¢

Type 7400 Quad 2-Input Pos. NAND Gate. High speed diode-clamped inputs. TR-431. Reg. 69¢ Sale 29¢

Type 7402 Quad 2-Input Pos. NOR Gate. Low noise propagation delay. 12 ns. TR-432. Reg. 69¢ Sale 29¢

Type 7404 Hex Inverter. Low noise, low power dissipation. TR-433. Reg. 79¢ Sale 29¢

Type 7410 Triple 3-Input Pos. NAND Gate. Low output impedance, diode-clamped inputs. TR-434. Reg. 69¢ Sale 29¢

Type 7447 BCD to 7-Segment Decoder/Driver. With common anode displays. TR-435. Reg. 2.99 Sale 59¢

Type 7473 Dual J-K Master/Slave Flip-Flop. TR-436. Reg. 1.19 Sale 39¢

Type 7474 Dual D-Type Edge Triggered Flip-Flop. TR-438. Reg. 69¢ Sale 39¢

Type 7475 4-Bit Latch. Temp. stores binary coded info. TR-437. Reg. 1.89 Sale 79¢

Type 7490 Decade Counter. Binary coded decimal counter with symmetrical divide by 10. TR-439. Reg. 1.89 Sale 79¢

Rechargeable Battery With Charger

6 VDC alkaline rated @ 5 amp/hr. Max. current 1.25 amp. Eveready Reg. #565 4 lbs. 9.98 BA-307. Sale 4.99

BIG 1 LB. Resistor Kit

Over 400 pieces of 1/2, 1 watt sizes. All color coded 2 1/2 lbs. RS-239. 99¢

500-ft. Hook-Up Wire

For almost any type of printed circuit or wiring project. 2 lbs. WW-579. Sale 1.69

PNP Transistors

Big 10 pc. kit. For general lo & hi gain & audio Germanium types. Untested. 1/4 lb. TR-445. Sale 39¢

Reg. 99¢ TR-444. NPN. 39¢

3-6 VDC Motors

Kit 1/5 Small 1/2 lb. MO-333. Sale 55¢

Kit 1/4 Med. 1 lb. MO-334. Sale 79¢

Kit 4 Ass'd. 2 lbs. MO-335. Sale 99¢

Three 60-Min. Cassettes

Pkg. 3 quality cassette recording tapes 60-Min. each 1/2 lb. TA-879. Sale 99¢

12-Digit IC Calculator Chip

40-pin DIP single CAL-Tech #CT-5001 7-seg. decoded display output. overflow lock-out. Specs inc. Reg. 5.98 XM-330. Sale 1.59

8-T Blank Tape

Famous manufacturer's high quality low priced tapes 1/2 lb. TA-854. 89¢

TA-855. 40-Min. 89¢

Reg. 1.19 TA-856. 60-Min. 99¢

50-Pc. 1 Amp Diode Kit

Polarity is marked but easily identified with ohm meter. 200 PIV rated 1/2 lb. DI-051. Sale 69¢

Silicon Rectifiers

1 Amp Epoxy Type Pkg. 1/5 oz. Reg. Sale

DI-028 50 PIV IN4001. 89¢ 39¢

DI-029 100 PIV IN4002. 99¢ 39¢

DI-030 200 PIV IN4003. 1.19 39¢

DI-031 400 PIV IN4004. 1.39 39¢

Switching Diodes

Pkg. 10 IN4148 for low current applications. 10 mA. 75 PIV. 1/2 lb. XM-382. Sale 59¢

LED'S 2V 10 mA

Gallium phosphide. Large red high quality LED. 1/2 lb. Pkg. 5 PL-233. Sale 59¢

FREE Olson Catalogs

WITH THOUSANDS OF ELECTRONIC BARGAINS

Next 7 issues FREE!

FREE Send Today

SCR Assortment

Hobby Pak! of ass't values & case types. Pkg. of 25. Untested. Wt. 1 lb. TR-446. Sale 99¢

ORDER TODAY! Send to Olson Electronics, 260 S. Forge St., Akron, Ohio 44327. Allow for postage. C.O.D. 20% Deposit, Ohio Residents Add 4% Sales Tax.

Olson electronics Dept. LC
260 S. Forge St., Akron, Ohio 44327

NAME _____

ADDRESS _____ APT _____

CITY _____ STATE _____ ZIP _____

DMM? Have it calibrated. 2 1/2 and 3 1/2 digit DMM's. Postcard for details. **XENOPHONICS**, P. O. Box 3126, Annapolis, MD 21403

FREE catalog, plus FREE diagrams & instructions for constructing a novel **ELECTRONIC ORGAN** with the parts you probably have on hand. We'll include a circuit and complete directions for assembling an amazing **XYLOPHONE**

Phone or write. Our Telephone Machine will record your name, address & zip. Night calls cost only 22¢ **CORTLANDT ELECTR.**, 114 West Broadway (Dial 212-964-8044) New York, N.Y. 10013

COMPUTER terminals, portable, hard copy, acoustic coupler, **ASCII**, **TTY** compatible. Easily modified for **ALTAIR**, TV typewriter. Limited quantity \$395, as is, working, with schematic. Information **SASA** or 25¢ **ABACUS**, 4692 Eagle Rock Blvd., Los Angeles, CA 90041

CASSETTES

Plain white cassette labels. Norelco cassette cleaners, famous brand cassettes. Send for open reel and cassette discount catalog.

	1-9	10-99	100	1000	10M
Cassette Labels		.02 .015	.01	.006	
Norelco Cassette Cleaner	.65	.60 .55	.50	.45	
10" Metal, NAB, Used Reel	1.00	1.00 .90	.80	.75	
10" Fiberglass used 3/8" Hole	.50	.50 .40	.35	.30	
Scotch Cassette SC90HE	2.72	2.55	2.44		

*Buy 2, SC90HE, get 1 free.

Plus Postage by Weight and Zone. Minimum Order \$5.00

OPEN REEL STEREO TAPE BUYERS!

At last! An open reel catalog, including titles, songs, etc. of 95 long play, 2-3 hour albums by American Airlines or Ampex 4 track stereo tapes. Send \$1.00 — and we will also mail you a 140-page Harrison stereo tape guide — so you'll get both for \$1.00 — and this \$1.00 is refundable on your first \$10.00 purchase of open reel stereo tapes at our 30% discount.

We've Got the "Spirit" The Prices And The Address To Prove It
Saxitone's Bicentennial Tape Shoppe
1776 Columbia Rd., N.W., Wash. D.C. 20009

PLANS & KITS

ADD a converter to any digital volt meter to read directly in dBw, dBw and RMS power on 4, 8, 16, 600 ohms. Complete manual available for \$3.75. **C.C. & S.S.**, 2309 Santa Monica Blvd., Santa Monica, CA 90404

DIGITAL plans, design manuals, others. Free info. **T. WONG**, 103 E. Broadway, New York, NY 10002

TV-GAMES, more than just a ping-pong game. Plans—\$5.00, full description and specs—\$1.00. **ADVANCE ELECTRONICS**, P. O. Box 1128, Cupertino, CA 95014

BUILD that electronic organ you always wanted at a price you can afford. Third edition of "Organ Builder's Guide", pictured product kit line, circuits, block diagrams, design rationale using IC divider and independent generators with diode keying. \$3.00 Postpaid. Also, free brochure on keyboards. **DEVTRONIX ORGAN PRODUCTS**, Dept. B, 5872 Amapola Drive, San Jose, CA 95129

BUILD YOUR OWN TV CAMERA

Ideal for home & business

THE ECONOMICAL ANSWER TO HOME MONITORING OF NURSERIES, ENTRANCES, DRIVEWAYS, BUSINESSES AND INDUSTRIAL SURVEILLANCE...TV...AMATEUR TV PLUS HUNDREDS OF OTHER APPLICATIONS. MODEL TV-1A, SERIES D - KIT FORM 318; ASSEMBLED \$275. SOLID-STATE. WORKS ON ANY TV SET. OPTIONAL SOUND KIT \$78.95. PHONE or WRITE for catalog. Dial 402-987-3771

BOX 453-RE **ATV Research** DAKOTA CITY, NE 68731

ELECTRONIC musical chime. Program any 10 note melody: Plans \$3.50. **TV ping pong** game. Plays through your set's antenna terminals: Plans \$3.25. **ARS SYSTEMS**, Box 1922L, Sunnyvale, CA 94088

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **SANDERS**, Dept. A-25, Box 92102, Houston, TX 77010

FREE catalog. Most unusual electronic kits available. Music accessories, surf, wind synthesizers, wind chimes, many others. **PAIA ELECTRONICS**, Box B14359, Oklahoma City, OK 73114

ELECTRONIC assembly business. Big profits Start home, spare time. Investment unnecessary. Send free literature. **BARTA**, Box 248AW, Walnut Creek, CA 94597

MEMORY SYSTEM \$125.00

1024 core memory system, 1024 words memory, 8, 9, or 10 bits/word. Random access, with all logic, register, timing, control, core select and sense functions in one package. New, with 60 page booklet includes schematics. Measures only 9x4x1 inches. Good start for mini-computer.

TONE GEN. BOARD

3 Octave tone gen. board from Magnus Organ. Unused with instructions & amp. \$9.95 2 for \$18.

PIANO KEYBOARD \$9.90

2 Octave keyboard For use with above organ or synthesizer, etc.

MULTI-USE XFMR \$8.95

Output 18 V @ 6 amp; 17 V @ 6 amps; 10 V @ 10 amp. Brand new. \$8.95 ea., 2 for \$15; 10 for \$50.

BELLTONE PAGER

Made for Bell System. Clip-on belt or pocket pager-receiver. Used condition, complete radio receiver on freq. of 35 Mhz with reed-decoder tone alert. An interesting & useful experimenters gadget. Limited quantity.

#SP-125 \$5.00 each 6/\$25

Please add shipping cost on above.

FREE catalog

Meshna **SURPLUS ELECTRONIC MATERIAL**
P.O. Box 62
19 ALLERTON STREET
E. LYNN MASS. 01904

Circle 87 on reader service card


VISTA

DIGITAL CROSSHATCH

Gives professional, accurate Color T.V. convergence. Digital IC's coupled with a crystal time-base oscillator provide sync for precise horizontal & vertical lines. Accurate 8x7 dot or cross-hatch pattern A.C. power 2 x 3/4 x 6 in. Wt. 24 oz. Fits in tool kit. **COMES COMPLETE WITH ALL PARTS, CASE CRYSTAL AND GUIDE TO ASSEMBLY & USE.**

KIT \$31.95

COMPLETELY ASSEMBLED \$41.95

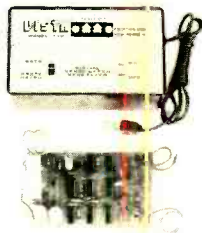

Shipping Prepaid in USA & Canada
NY State Add Sales Tax
PHOTOLUM CORP.
118 EAST 28 STREET
NEW YORK, N.Y. 10018

Circle 88 on reader service card

FREE flyer. Semis, components, electronic hardware. Lowest prices. **VANGUARD ELECTRONICS LTD.**, Box 1193, Edmonton, Alberta, Canada T5J 2M5

SUPERDESIGNED: New CB, experimenter, computer, power sources, signal generators, speech compressors, more. Free catalog. **MINITRON**, Box 184, Anoka, MN 55303

SURPRISE! Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! **GBS**, Box 100B, Greenbank, WV 24944

NEW Canadian Magazine, "Electronics Workshop," \$5.00 yearly, sample \$1.00. **ETHCO**, Box 741 "A", Montreal

RECONDITIONED test equipment. \$0.50 for catalog. **WALTER**, 2697 Nickel, San Pablo, CA 94806

CATALOG

GOVERNMENT SURPLUS
ELECTRONIC EQUIPMENT

For 1975

FREE UPON REQUEST! Write for
Copy of Catalog WS-75 Now!
Address: Attention Dept. RE

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

LOW-cost digital/analog test equipment. Logic probes from \$9.95. Free catalog. **ELECTRO INDUSTRIES**, 4201 Irving Park, Chicago, IL 60641

ELECTRONIC parts! New! Solid State devices! Free flyer: **DARTEK ELECTRONICS**, Box 2460, Dartmouth, Nova Scotia, Canada N.S. inquiries.

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, CA 92105

BURGLAR alarm dialing unit automatically calls police. \$29.95. Free literature. **S&S SYSTEMS** Box 12375G, North Kansas City, MO 64116

PACE, 16 bit CPU: \$250.00. 8080 CPU: \$120.00. AY5-1008 TTY terminal RX: \$5.50. AY5-1010 TTY terminal TX: \$5.50. KR205, function generator: \$7.75. XR210, FSK MOD/DEMOM: \$4.95. 53-key ASCII encoded keyboard: \$25.00. Audio cassette computer interface board: \$14.50. #6032 I-R converter: \$9.50. Main & memory P.C.B. (TVT-II): \$35.00. **ELECTRONIC DISCOUNT SALES**, 138 N. 81st St., Mesa, AZ 85207

MINIS — DEC • DG

CAI • CASC • HP • HIS • IBM
INT • LOCK • MICRO • SEL
TEMPO • UNIVAC • VARIAN • XLO
• PRINTERS • PAPER TAPE
• CARD • MAGNETIC
READERS • TAPE

— SAME DAY SHIPMENT —
Call 617 261-1100

AMERICAN USED COMPUTER CORP.

P.O. Box 68
Kenmore Station, Boston, Mass. 02215

member COMPUTER DEALERS ASSOCIATION

MICROWAVE, RF, AF test equipment. Bargain prices. Free Catalog. **ALR ELECTRONICS**, P.O. Box 706, Flushing, NY 11352

DYNACO-A-R, transistors, repairs—boards—& units, speaker service. Send for prices & details: **BEAR ELECTRONICS**, 177-R, Hillcrest Road, Mt. Vernon, NY 10552

FREE catalog. Ultrasonic devices, LED's, transistors, IC's, keyboards, unique components. Low prices. **CHANEY's**, Box 15431, Lakewood, CO 80215

TTL

SN7400	\$.15	SN74121	.38
7401	.15	74122	.44
7402	.15	74123	.44
7403	.15	74125	.54
7404	.18	74126	.54
7405	.18	74128	.84
7406	.34	74132	1.45
7407	.18	74133	.94
7408	.18	74141	.94
7409	.18	74142	3.70
7410	.25	74143	3.98
7411	.25	74144	3.98
7412	.30	74145	.98
7413	.30	74147	2.50
7414	1.49	74148	1.90
7415	.33	74150	.94
7416	.33	74151	.69
7417	.33	74153	.79
7418	.32	74154	1.09
7419	.32	74155	.79
7420	.27	74156	.79
7421	.24	74157	.69
7422	.27	74159	3.50
7423	.24	74160	.99
7424	.15	74161	.99
7425	.24	74162	.99
7426	.24	74163	.99
7427	.29	74164	1.10
7428	.29	74165	1.10
7429	.15	74166	1.35
7430	.85	74170	2.50
7431	.85	74172	8.75
7432	.85	74173	1.35
7433	.85	74174	1.15
7434	.87	74175	.99
7435	.87	74176	.79
7436	.85	74177	.79
7437	.15	74178	1.95
7438	.15	74179	1.95
7439	.15	74180	.79
7440	.15	74181	2.50
7441	.28	74182	.69
7442	.28	74184	1.95
7443	.34	74185	1.95
7444	.34	74186	13.95
7445	.48	74188	4.75
7446	.48	74190	1.10
7447	.48	74191	1.33
7448	.48	74192	1.10
7449	.48	74193	1.10
7450	.69	74194	1.05
7451	.78	74195	.74
7452	1.95	74196	.99
7453	1.08	74197	.89
7454	.34	74198	1.69
7455	2.35	74199	1.69
7456	4.90	74201	1.69
7457	.79	74246	1.95
7458	.49	74247	1.85
7459	.49	74248	1.75
7460	.79	74249	1.75
7461	.74	74251	1.40
7462	.74	74252	.85
7463	1.25	74253	2.75
7464	.43	74278	2.45
7465	.43	74279	.95
7466	.43	74280	1.07
7467	.74	74284	4.50
7468	.54	74285	4.50
7469	.74	74290	.85
7470	1.98	74293	.85
7471	1.35	74298	1.98
7472	1.40	74367	.95

CMOS

CD4000	\$.24	CD4033	1.95
4001	.24	4035	1.50
4002	.24	4040	1.24
4003	1.50	4041	.89
4004	.24	4042	.79
4005	.24	4043	.79
4006	.24	4044	.79
4007	.24	4045	.79
4008	.24	4046	.79
4009	.24	4047	.79
4010	.24	4048	.79
4011	.24	4049	.79
4012	.24	4050	.79
4013	.24	4051	1.50
4014	1.24	4052	1.50
4015	1.24	4053	1.50
4016	1.24	4054	1.99
4017	1.24	4055	1.99
4018	1.24	4056	1.99
4019	1.24	4057	1.99
4020	1.24	4058	1.99
4021	1.24	4059	1.99
4022	1.24	4060	1.99
4023	.24	4061	1.24
4024	.24	4062	1.24
4025	.24	4063	1.24
4026	.24	4064	1.24
4027	.24	4065	1.24
4028	.24	4066	1.24
4029	.24	4067	1.24
4030	.24	4068	1.24

LINEAR I.C.'s

LM300H	Positive Voltage Regulator	(metal can)	.69
LM301AH	Hi Performance Op Amp	(metal can)	.35
LM304H	Negative Voltage Regulator	(metal can)	.75
LM305H	Positive Voltage Regulator	(metal can)	.78
LM307H	Op Amp (Super 741)	(mini dip)	.28
LM307 mini	Op Amp (Super 741)	(mini dip)	.28
LM309H	SV 1 Amp Voltage Regulator	(metal can)	.99
LM309K	SV 1 Amp Voltage Regulator	(metal can)	.99
LM310H	Voltage Follower Op Amp	(metal can)	1.09
LM312H	Quad Op Amp	(DIP)	1.75
LM313H	Quad Op Amp	(DIP)	1.75
LM315H	Timer	(mini dip)	.54
LM356H	Dual Timer	(DIP)	.99
LM709H	Op Amp	(metal can)	.29
LM709C mini	Op Amp	(mini dip)	.29
LM709CN	Op Amp	(DIP)	.29
LM711CN	Dual Difference Comparator	(metal can)	.50
LM723CN	Voltage Regulator	(14 pin DIP)	.54
LM723CN	Voltage Regulator	(14 pin DIP)	.54
LM741CN	Op Amp	(metal can)	.29
LM741CN	Op Amp	(mini dip)	.28
LM741CN	Op Amp	(14 pin DIP)	.29
LM747CN	Dual 741 Op Amp	(metal can)	.65
LM747CN	Dual 741 Op Amp	(14 pin DIP)	.75
LM748 mini	Dual 741 Op Amp	(mini dip)	.29
LM1458H	Dual Op Amp	(metal can)	.65
LM3046	Transistor Array		.85
LM3900	Quad Amplifier		.79

MEMORIES

AY5-1013P	UART	\$ 9.00
AY5-2376	Keyboard Encoder ROM	19.95
1101AP	256 Bit Static RAM MOS	3.95
1402AT	Dual 512 Bit Dyn MOS S/R	3.75
1404AT	Single 1024 Bit Dyn MOS S/R	3.50
1702A	2048 Bit Erasable Eect. Reprogrammable	23.95
2102P	Static MOS RAM	3.95
8008B	8 Bit Static RAM MOS	44.00
8080	8 Bit Parallel Processing Unit	195.00
TMS4030NL	4K RAM 4096 Bit	19.95

EXAR I.C.'s

XR-100K	XR-Chip Custom IC Design Kit	79.00
XR-B101	NPN Transistor Array, Small Signal	3.45
XR-B102	PNP Transistor Array, Small Signal	3.45
XR-C101	NPN Transistor Array, Lateral & Substrate	3.45
XR-C102	NPN Transistor Array, Power & Schottky	3.45
XR-C103	Diffused Resistor Array	3.45
XR-C104	Diffused & Pinch Resistor Array	3.45
XR-C105	Diffused Modulator & NPN, PNP Current Source	3.45
XR-C106	Multi-Function IC	20.95
XR-2000	Waveform Generator IC	24.50
XR-2005K	Waveform Generator Kit	3.89
XR-210	FSK Modulator Demodulator	3.89
XR-210M	FSK Modulator Demodulator	3.89
XR-215	General Purpose PLL	9.71
XR-320	Timing Circuit	1.13
XR-555CP	Dual Timing Circuit	7.91
XR-556M	Dual Timing Circuit	2.15
XR-556CN	Dual Timing Circuit	1.25
XR-556CP	Dual Timing Circuit	1.25
XR-567M	Tone Decoder	1.37
XR-567CN	Tone Decoder	1.25
XR-567CP	Tone Decoder	1.25
XR-1310P	Stereo Demodulator	2.39
XR-1468CN	+5V Tracking Voltage Regulator	2.50
XR-1468CP	+5V Tracking Voltage Regulator	1.85
XR-1488N	Quad Line Driver	4.25
XR-1488P	Quad Line Driver	3.85
XR-1489AN	Quad Line Receiver	3.85
XR-1489AP	Quad Line Receiver	3.85
XR-1568M	+15 Volt Tracking Voltage Regulator	10.73
XR-1568CN	+15 Volt Tracking Voltage Regulator	5.35
XR-206N	Monolithic Function Generator	8.35
XR-206CP	Monolithic Function Generator	7.67
XR-206CN	Monolithic Function Generator	4.61
XR-206CP	Monolithic Function Generator	3.83
XR-2207M	Voltage-Controlled Oscillator	11.50
XR-2207N	Voltage-Controlled Oscillator	5.03
XR-2207CN	Voltage-Controlled Oscillator	3.55
XR-2207CP	Voltage-Controlled Oscillator	3.55
XR-2208M	Operational Multiplier	13.50
XR-2208CN	Operational Multiplier	6.65
XR-2208CP	Operational Multiplier	5.93
XR-2208M	Operational Multiplier	4.19
XR-2208CN	Operational Multiplier	3.89
XR-2208CP	Operational Multiplier	3.89
XR-2211CN	FSK Demodulator/Tone Decoder	14.63
XR-2211CP	FSK Demodulator/Tone Decoder	6.59
XR-2240P	Programmable Timer/Counter	2.63
XR-2240CP	Programmable Timer/Counter	3.59
XR-2240M	Programmable Timer/Counter	7.91
XR-2240CN	Programmable Timer/Counter	4.27
XR-2240CP	Programmable Timer/Counter	3.59
XR-2555M	Dual 555 Timer	1.91
XR-2555CN	Dual 555 Timer	1.91
XR-2555CP	Dual 555 Timer	2.39
XR-2567M	Dual 567 Tone Decoder	12.70
XR-2567CN	Dual 567 Tone Decoder	5.92
XR-2567CP	Dual 567 Tone Decoder	3.88

PLASTIC POWER TRANSISTORS

TIP29A	PNP 1A 60V	\$.45
TIP30A	PNP 1A 60V	.49
TIP31A	PNP 3A 60V	.52
TIP32A	PNP 6A 60V	.59
TIP33A	PNP 10A 60V	.99
TIP35	PNP 25A 40V	1.99
TIP36	PNP 25A 40V	2.25
TIP41A	PNP 6A 60V	.65
TIP42A	PNP 6A 60V	.75
TIP47	PNP 1A 250V	.88
TIP48	PNP 1A 250V	.88
TIP49	PNP 1A 350V	.99
TIP110	PNP 2A 60V	.92
TIP121	PNP 5A 60V	1.64
TIP127	PNP 5A 100V	2.02
TIP2955	PNP 15A 60V	.89
TIP3055	PNP 15A 60V	.85

I.C. SOCKETS

8 Pin DIL	\$.18
16 Pin DIL	.24
14 Pin DIL	.22
24 Pin DIL	.59

LED's & OPTO ISOLATORS

DL707	7 Seg 0.3"	\$1.70
DL747	7 Seg 0.63"	2.45
RL2	Red Led .19"	.23
TIL209	Red Led .125"	.19
TIL111	Opto-Coupler	1.20
TIL220	Red Led .240"	.24
IL15	Opto-Isolator	1.25
IL16	Opto-Isolator	1.40
TIL312	7 Seg 0.3"	1.70
TIL313	7 Seg 0.3"	1.70

PLASTIC TRANSISTORS

2N3415	\$.17	74LS08	.42	74LS136	.68
2N3563	.15	74LS09	.42	74LS138	1.94
2N3564	.15	74LS11	.42	74LS139	1.94
2N3565	.15	74LS111	.42	74LS145	1.58
2N3566	.15	74LS12	.42	74LS151	1.58
2N3567	.15	74LS13	.94	74LS152	1.94
2N3568	.15	74LS14	2.22	74LS155	1.94
2N3569	.15	74LS15	.42	74LS156	1.94
2N3640	.15	74LS20	.42	74LS157	1.58
2N3641	.15	74LS21	.42	74LS158	1.58
2N3643	.15	74LS22	.42	74LS164	2.27
2N3702	.17	74LS26	.54	74LS170	5.36
2N3703	.17	74LS27	.47	74LS171	5.36
2N3704	.17	74LS28	.54	74LS175	2.27
2N3705	.17	74LS30	.42	74LS181	6.30
2N3706	.17	74LS32	.54	74LS182	2.87
2N3707	.17	74LS33	.54	74LS191	2.87
2N3708	.17	74LS37	.54	74LS192	2.87
2N3709	.17	74LS38	.54	74LS193	2.87
2N3710	.17	74LS42	1.25	74LS195A	2.27
2N3819	.29	74LS48	1.25	74LS196	2.27
2N3820	.35	74LS49	1.25	74LS197	2.27
2N3903	.15	74LS51	.42	74LS221	1.41
2N3904	.15	74LS54	.42	74LS247	1.25
2N3905	.15	74LS55	.42	74LS248	1.25
2N3906	.15	74LS57	.68	74LS251	1.25
2N3907	.15	74LS58	.68	74LS252	1.25
2N4059	.15	74LS75	.84	74LS253	2.27
2N4060	.15	74LS76	.68	74LS254	1.94
2N4061	.15	74LS78	.68	74LS258	1.94
2N4062	.17	74LS558A	2.27	74LS261	5.36
2N4123	.15	74LS585	2.88	74LS266	.68
2N4124	.15	74LS59	1.25	74LS270	2.27
2N4125	.15	74LS91	1.25	74LS283	2.27
2N4126	.15	74LS92	1.25	74LS290	2.27
2N4201	.15	74LS93	1.25	74LS293	2.27
2N4250	.15	74LS93S	1.25	74LS295A	2.27
2N4400	.15	74LS95A	2.27	74LS365	.68
2N4403	.15	74LS96	1.94	74LS367	.68
2N4407	.16	74LS107	.68	74LS368	.68
2N4409	.16	74LS108	.68	74LS375	.84
2N4449	.16	74LS112	.68	74LS376	.68
2N5523	.39	74LS113	.68	74LS370	6.30

NEW KITS! NEW KITS!

JAMES ELECTRONICS

P. O. BOX 822 BELMONT, CALIFORNIA 94002
(415) 592 8097

DIGITAL VOLTMETER



This is a 3 1/2 digit, 0.2 volt Digital Voltmeter, with a 5% full scale accuracy. It is based around the Siliconix LD1110, LD1111 DVM chip set. The voltmeter uses MAN7 readouts (3" high) to provide a highly readable display. The unit requires the following supply voltages: 12, -12, 5. The unit comes complete with all components to build the unit pictured at the left, that is a complete DVM less power supply.

\$39.95 Per Kit

LOGIC PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a max. 10 mA max. It uses a MAN7 readout to indicate any of the following states by these symbols: (HI)—1 (LOW)—0 (PULSE)—P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.



\$9.95 Per Kit

DIGITAL COUNTER



This is a 4 digit counter unit which will count up to 9999 and then provide an over flow pulse. It is based around the Mostek MK5007 digital counter chip. The unit performs the following functions: Count Input, RESET, Latch, Overflow. The counter operates up to 250 kHz. The counter is an ideal unit to be used as a frequency counter, where the only extra components needed would be a timebase, divider chain and gate. The unit requires 5V, and -12V. The unit comes complete as shown on the left less power supply.

\$29.95 Per Kit

ONE KILOBYTE RANDOM ACCESS MEMORY

This memory card is for the most part a universal unit that can be used in almost any microcomputer from a HOMEBREW to an ALTAIR 8800. It uses an array of 2102 1k x 1 static random access memories to produce a 1024 x 8 memory compatible with most standard microcomputer systems. We provide everything from the super low noise vector logic card, to fine quality low profile sockets, to the right 2102's. We even include timing diagrams and tantalum bypass capacitor.



\$69.95 Per Kit

5 VOLT 1 AMP T²L SUPPLY



5 VOLT 1 AMP
T²L SUPPLY

This is a standard TTL power supply using the well known LM3090 regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

\$9.95 Per Kit

PLASTIC INSTRUMENT CASE

These cases are fine quality units made by a German manufacturing firm which fit to the dimensions of our DVM and COUNTER kit with room enough left for power supply or batteries. Excellent for many other projects as well. Dimensions 2" x 3 1/8" x 5 7/8".



\$5.95 Per Case

Satisfaction Guaranteed. \$5.00 Min. Order, U.S. Funds. Add \$1.25 for Postage — Write for FREE 1975 Catalog California Residents — Add 6% Sales Tax

JAMES

P. O. BOX 822, BELMONT, CA. 94002
PHONE ORDERS — (415) 592-8097

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **\$1.40 per word** . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.


BUSINESS OPPORTUNITIES

ELECTRONIC assembly business. Big profits. Start home, spare time. Investment, knowledge, experience unnecessary. Free literature from: **BARTA**, Box 248BX, Walnut Creek, CA 94597

OWN YOUR OWN PICTURE TUBE REBUILDING BUSINESS

With Lakeside Industries re-building equipment you can rebuild any picture tube!

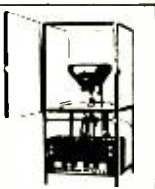For complete details send name, address zip code to
LAKE-SIDE INDUSTRIES
3520 W. Fullerton Ave
Chicago, Ill. 60647
Phone: 312-342-3399



EDUCATION & INSTRUCTION

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

DESIGN your own power supply and regulator circuits. Twenty pages of circuit analysis and design examples. 8 1/2" x 11", \$2.00. **HUTCHINSON**, 10818-RES Brentway, Houston, TX 77070

BROADCAST station: Start your own. Get free tapes, records. Become a disc jockey. Complete details free. **EGW**, Box 5516-FK, Walnut Creek, CA 94596

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests—Answers for FCC 1st and 2nd class Radio telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money back guarantee.

COMMAND PRODUCTIONS P.O. BOX 26348 E
RADIO ENGINEERING DIV. SAN FRANCISCO, CAL 94126



UNDERSTAND digital electronics — calculators, microprocessors, computers. New programmed learning courses. Design of Digital Systems, 6 volumes, only \$14.95. Digital Computer Logic, 4 volumes, \$9.95. Both \$19.95. Unconditional refund if dissatisfied. **CAMBRIDGE LEARNING ENTERPRISES**, 300 East 56th St., New York, NY 10022

LEARN design techniques. Electronics design Newsletter. Digital, linear construction projects, design theory and procedures. Annual subscription \$6.00, sample copy \$1.00. **VALLEY WEST**, Box 2119-A, Sunnyvale, CA 94087

SEMICONDUCTOR and parts literature, **J. & J. ELECTRONICS**, Box 1437R, Winnipeg, Manitoba, Canada, U.S. Inquiries Invited

WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! **BARRY**, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

FOR SALE

FREE. 1975 TECO Electronics Consumer Catalog. Hundreds of quality items. Amateur radios, CB radios, antennas, calculators, audio, etc. **TECO ELECTRONICS**, Dept. A, PO Box 1050, Garland, TX 75040

RECORDS-TAPES! Discounts to 75%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-105, New Rochelle, NY 10801

CANADIAN discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush \$1. **ETCO-RE**, 521 5th Ave., NYC, 10017

NEW ELECTRONIC SURPLUS COMPONENTS

— SAME DAY SHIPMENT —
Call 617 261-1100

AMERICAN USED COMPUTER CORP.
P.O. Box 68
Kenmore Station, Boston, Mass. 02218
member COMPUTER DEALERS ASSOCIATION

LOW-noise resistors—1/4W, 5%, carbon film from 10—3.3 megohms for 3 1/2¢ each. Fifty of one value for \$1.25. 1N4148 diodes for 6¢. 75¢ postage. Free samples/specifications. **COMPONENTS CENTER—RE**, Box 134 New York, NY 10038

COMPUTER freaks, we have parts, kits, boards, C8080, C8008, P2101, P2111, C702A, 91L02A. Write for catalog. **A.R.B., LTJ**, PO Box 1392, Scottsdale, AZ 85252

JAPANESE transistors. All transistors original factory made. Free catalog. **WEST PACIFIC ELECTRONICS**, P.O. Box 25837, W. Los Angeles, CA 90025

FREE catalog. IC's, Semis. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que. Canada, H3C-1H8 US Inquiries

PRINTED CIRCUIT

PHOTO ETCH KITS; DATAK PRODUCTS; TAPE RESIST; ALPHA NUMERIC COMPONENT DESIGNATIONS; ARTHWORK; CARBIDE DRILL BITS; BUBBLE ETCHERS
SEND S.A.S.E. FOR FLYER
TRUMBULL
833 BALRA DR., EL CERRITO, CA 94530

next month

NOVEMBER 1975

■ Build A Portable Electronic Music Synthesizer

Circuit boards and solid state electronics make it easy to build. The effects it can create are superb.

■ Make Your Calculator Into A Stopwatch

Add-on circuit can turn a calculator into a precision timer.

■ Square Waves And Audio Testing

You've got to know what you're doing before you can make accurate measurements.

■ All About Probes

The right probe matched to right test instrument makes a powerful combination. See what's available and how to use it.

■ Screen-Read Board

Use it with TV Typewriter II.

PLUS

Step-By-Step Troubleshooting Charts

Jack Darr's Service Clinic

State-Of-Solid-State

Accuracy like a VTVM... Convenience like a VOM...


NEW BATTERY-OPERATED FET
SOLID-STATE VOLT-OHMMETER #116

Easy-to-build KIT

\$36.90 =116K

Factory-Wired & Tested

\$49.49 =116W

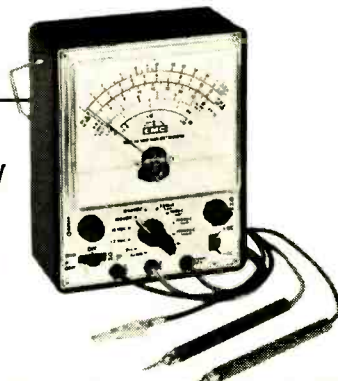

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 megohms input or DC, 1 megohm on AC • 500-times more sensitive than a standard 20,000 ohms-per-volt VOM • Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 0-1.2, 12, 120, 1200V; 4 DC voltage ranges: 0-1.2, 12, 120, 1200V; 4 Resistance ranges: 0-1K, 0-100K, 0-10 meg., 0-1000 meg.; 4DB ranges: -24 to +56DB.

Sensitive easy-to-read 4 1/2" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5 1/4" H x 6 3/4" W x 2 7/8" D. 3 lbs.

Send FREE catalog of complete EMC line and name of nearest distributor.

RE-10

Name _____

Address _____

City _____

State _____ Zip _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012



**You
can study
FM
two-way
radio
at
home!**

Thousands have increased their knowledge of FM two-way radio through the MTI home-study courses. Now, newly revised and better than ever!

Cut me in, send free information. (No salesman will call)

Name _____

Address _____

Code _____

☐ I am a Veteran

☐ I am a serviceman on active duty

MTI

Formerly

MOTOROLA TRAINING INSTITUTE

College Hill Road, Summerdale, Pennsylvania 17093

Circle 105 on reader service card

OCTOBER 1975

97

FOR TIGHT SPOTS!

CHAPMAN

Midget RATCHET SET plus ADAPTERS

Seventeen different interchangeable adapters with a screwdriver attachment and extension, plus the world's mightiest MIDGET RATCHET in a compact 4" x 6" steel case. The strength of this twenty tooth stainless steel ratchet far exceeds torque standards set by military specifications. Requiring only an 18° working arc, reverse action is obtained by simply turning the ratchet over. Kit includes 12 Allen Hex Adapters from .050" to 3/8", 2 popular Phillips sizes (#1 and #2), 2 Slotted Head sizes (1/4" and 3/8"), plus a 1/4" Square Drive for use with standard sockets.

Only \$13.60

Send Check
or Money Order

**POCKET SIZE
NO. 6320 KIT**

Send Check
or Money Order to ...

THE CHAPMAN MANUFACTURING COMPANY

DURHAM, CONNECTICUT 06422 Dept. RE-10

Circle 79 on reader service card

FREE

'75 CATALOG

**Fast... Flameless
CONCENTRATED HEAT
up to 1000°F.**



MILWAUKEE

HEAT-BLO GUN

The Heat Gun of a Thousand Uses

A model for every need ranging from 150° to 1000°F., without an open flame. Safe and easy to operate... use wherever concentrated heat is needed. Fingertip switch control permits operator to aim heat right at desired point. Temperature can be varied by air intake adjustment. Also blows cold air when desired.

MEETS DOZENS OF NEEDS in laboratory and on production lines... softens plastics... dries paint, glue or photo prints... thaws... defrosts... heat seals... does blister packs... preheats for welding or soldering... desoldering... excellent for softening, repairing and retexturing molded plastics... shrinks vinyl to fit upholstery.

Sturdy adjustable metal stand permits positioning on bench or machine, on assembly lines, etc.

MILWAUKEE LOCK & MFG. CO.

5078 N. 37TH STREET • MILWAUKEE, WIS. 53209

Circle 80 on reader service card

reader questions

LOSS OF VERTICAL SWEEP

I replaced a bad 820-ohm vertical output tube cathode resistor in this CTC25 RCA, and fixed the complaint of loss of vertical sweep. (I thought.) After about 30 minutes of cooking, out went the same resistor! The raster and sound went with it this time. After waiting a while, I turned it on again. Same thing, about half vertical sweep and the 820-ohm resistor was burned up. This happened on the set, and also on my test-jig. I'm baffled. Any suggestions?—A.C., Cleveland, OH.

Thanks to the test-jig, you've eliminated the yoke, etc. Let's see. Something is causing the 6GF7 tube to draw too much current (or is it?) With a new tube, a short isn't too likely. So let us look elsewhere.

Follow the 6GF7 cathode circuit; it goes through the 820-ohm resistor, and also through a pair of resistors which are connected to the suppressor grid of the 6JE6 horizontal output tube. (This is done to feed a little positive voltage to this grid to get rid of UHF snivets.)

These are, of course, a part of the vertical output tube's cathode circuit. However! If you have an intermittent short in the 6JE6, this can burn up the 820-ohm resistor in the vertical. So, you lose vertical sweep. Your loss of raster and sound could be trying to tell us this is the cause. Try a new 6JE6. This has been known to happen.

PM MAGNET FOR TAPE ERASE?

I tore up an old electric generator and found a couple of big magnets. These are powerful enough to fully erase a 10 1/2" reel of recording tape. Do you think this method will hurt anything?—R.G., Baltimore, MD.

I really don't think so. After all, there are quite a few small tape recorders which use a little PM magnet as the erase head, and others that use an electromagnetic head with a DC supply. Can't see any difference.

WHY WAS THE GRID VOLTAGE NORMAL?

I wrote you a short while ago about a problem with a Sylvania D0-5-1. The horizontal output grid was approximately 20 volts positive, with all of the resulting symptoms that this causes. I strongly suspected the regulator stage, 6CL8, but I had checked everything in the plate and cathode of that stage. Also checked the few components in the grid circuit of the 42KN6 all to no avail. I didn't go into the grid circuit of the regulator, since I had +18 volts DC and the 50-volt P-P proper waveform on the grid.

Sounds like the grid circuit is fine, doesn't it? WRONG! Anyway, I followed your suggestions of checking X2, the resistors in the 42KN6 grid circuit, etc. Still had the same problem. I was stumped. Then, I sat down and thought. As a last resort, I'd go into the grid circuit of the 6CL8 regulator. There it was.

Resistor R119, 270K 5%, had increased to 300K. Resistor R120, 27K up to 29K, and R121, 3.9 megohms was up to 7 megohms.

Change these three resistors, and the set works fine. What confused me from the start was the fact that I did have +18 volts on the grid of the regulator. Well within the ballpark. The proper waveform was there, but a little high; 50 volts when it should have been 34 V P-P.

So I thought I'd take time to give you some field feedback on this weird problem and let you know what it was. I still have one question. I'd like to find out why the grid voltage of the regulator was so close to normal.—Mike McDaniel, Patrick AFB, FL.

(So would I, Mike. If any of our readers know, let me know.)

R-E

A Government FCC License can help you qualify for an exciting, rewarding career in ELECTRONICS, the Science of the Seventies. Read how you can prepare at home in your spare time to pass the FCC Licensing examination.

If you're out to bag a better job in Electronics, a Government FCC License can give you a shot at job opportunities with *real* futures.

According to the U.S. Office of Education Bulletin (4th Edition): "The demand for people with technical skills is growing twice as fast as for any other group, while jobs for the untrained are rapidly disappearing." There are new openings every year in many different industries for electronics specialists. And you don't need a college education to qualify.

But you *do* need knowledge . . . knowledge of electronics fundamentals. And one of the nationally accepted methods of measuring this knowledge . . . is the licensing program of the FCC (Federal Communications Commission).

Importance of an FCC License and CIE's Warranty of Success

If you want to work in commercial broadcasting . . . television or AM or FM broadcasting . . . as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

But even if you aren't planning a career which involves radio transmission of any kind, an FCC "ticket" is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you really know your stuff.

So why doesn't everyone who wants a good job in Electronics get an FCC License?

It's not that simple. To get an FCC License, you must pass a Government licensing exam.

A good way to prepare for your FCC License exam is to take one of the CIE career courses which include FCC License preparation. We are confident you can successfully earn your license, if you're willing to put forth an effort, because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

That's why we can offer this time-tested Warranty of Success: when you successfully complete any CIE career course which includes FCC License preparation, you will be able to pass the Government FCC Examination for the License for which the course prepared you or you will be entitled to a full refund of an amount equal to the cash price of tuition for CIE's Course No. 3, "First Class FCC License," in effect at the time you enrolled. This warranty is good from the date you enroll until the last date allowed for completion of your course.

CIE HAS CAREER COURSES THAT INCLUDE "HANDS ON" TRAINING

ELECTRONICS TECHNOLOGY with LABORATORY Courses . . . takes beginner from fundamentals to skills required of technician or engineering assistant. Includes Experimental Electronics Laboratory for "hands on" training.

COLOR TV MAINTENANCE and REPAIR . . . several CIE courses combine electronics theory with the actual construction, testing and troubleshooting a big screen, stolid state color TV.

With CIE you learn at home

With CIE, you learn in your spare time at home . . . or wherever else is convenient. No classroom time, ever. No one to make you go too fast . . . or too slow. With CIE's Auto-Programmed® Lessons you'll pick up facts, figures, and electronics theories you may have considered "complicated" . . . even if you've had trouble studying before.

You can have attractive job opportunities

There have already been many exciting developments and breakthroughs in Electronics and some people might assume there will be no new frontiers . . . no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications. Once you have the solid technical background you need, you can practically choose the career field you want . . . work for a big corporation, a small company or even go into business for yourself.

Yes, Electronics can be the door to a whole new world of career opportunities for you. And CIE training can be your key.

Send for FREE school catalog

Discover the opportunities open to people with electronics training. Learn how CIE career courses can help you build new skills and knowledge and prepare you for a meaningful, rewarding career. We have courses for the beginner, for the hobbyist, for the electronics technician, and for the electronics engineer. Whether you are just starting out in Electronics or are a college-trained engineer in need of updating (or anywhere in between), CIE has a course designed for you.

Send today for our FREE school catalog and complete package of career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE . . . or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114. Do it TODAY.

APPROVED UNDER G. I. BILL

All CIE *career* courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Please send me your FREE school catalog and career information package today.

I am especially interested in:

- | | |
|--|--|
| <input type="checkbox"/> Electronics Technician | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> FCC License Preparation | <input type="checkbox"/> Electronics Engineering |
| <input type="checkbox"/> Color TV Maintenance | <input type="checkbox"/> Other _____ |
| <input type="checkbox"/> Mobile Communications | |

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____ Age _____

Check box for G.I. Bill information.


☐ Veteran ☐ On Active Duty

RE-59

Circle 78 on reader service card

Hunting for
a better job?

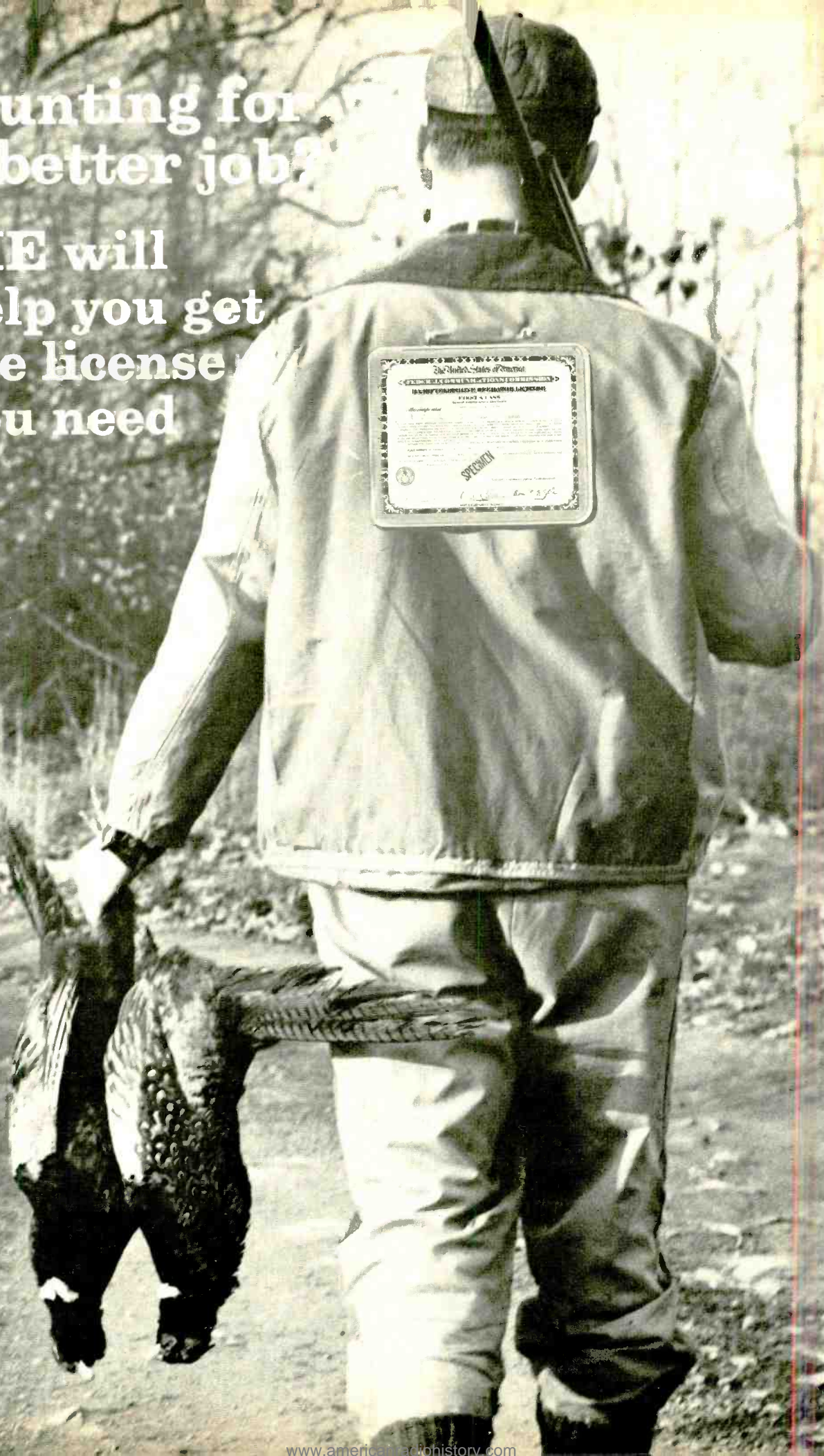CIE will
help you get
the license
you need





endeco soldering & desoldering equipment

SOLDERING IRONS

Pencil style. Safety light. Two heats — 20w and 40w. 6 tips. Unbreakable handle. 2 and 3 wire neoprene cords.

DESOLDERING IRONS

Pencil style. Safety light. Some operate at 40w, idle at 20w. 8 tip sizes. 2 and 3 wire neoprene cords.



SOLDERING & DESOLDERING KITS

Everything needed to solder or desolder or both. All in a handy lifetime metal box with hasp.

See your distributor or write...

Enterprise Development Corp.

5127 E. 65th St. • Indianapolis IN 46220
PHONE (317) 251-1231

Circle 75 on reader service card

TROUBLESHOOTING

(continued from page 68)

voltage reading, while still hooked up to the pix tube. The raster will be out and the high-voltage will be zero or very low. Service-switch test helps here too, since it takes much less beam current to make three lines than a full raster. Confirm by disconnecting the high-voltage lead and measuring.

Contrast problems

If the picture has ample brightness, very good fine-detail but is pale and washed-out looking, you have poor contrast. First step, check to see if the CONTRAST control has any effect at all. If it does not, the big capacitor on the video output cathode is probably open. This, of course, can be intermittent since it is a low-voltage electrolytic.

The picture is pale but the CONTRAST control does have a reaction. This shows a loss of video *gain* in one or more of the stages. The video signal doesn't have enough amplitude to cut the beam off completely and give you good blacks. Quick-check: feed an audio signal into the input of the video amplifier stage and make signal-tracing tests through the whole circuit with a scope. You do *not* have to have a calibrated scope; just look for a stage where you have a good input and less output than input. (Look out for cathode-followers!) Check peak-to-peak amplitude of the video detector output signal. This kind of problem can also be due to AGC trouble, weak IF tubes, etc.

The picture is weak, the CONTRAST control reacts and there is horizontal smearing. This type of trouble can be caused by an open peaking coil somewhere in the video amplifier. If it is in the grid or input circuits, the DC voltages won't be too badly upset but the loss of fine detail will be very obvious. (Use a vertical lines pattern from a bar-dot generator, etc.)

Delay line problems

The delay line used in these sets is simple, and causes few problems. If the coil should open, you'll lose the video. If it has been replaced by the wrong part, you may see two or three very sharp "rings" just to the right of any sharp vertical lines in the picture. Always use an oscilloscope to check delay lines. The video signal in and out should be the same amplitude.

Oddball problems


We can have "picture problems" in a video amplifier which is working perfectly. This sounds odd, but it's true. The troubles will be due to something that is being *fed into* the video stages, upsetting the picture. The most common of these is in the blanking circuits.

Other faults in blanking circuits can cause the normal blanking pulse to be distorted. For example, they may be flattened and widened. This will make it "hang over" into the picture. This usually blanks out part of the picture on the left. Look for leaking capacitors or diodes, and resistors which have drifted off-value, thus changing the time-constants.

R-E

ALLISON

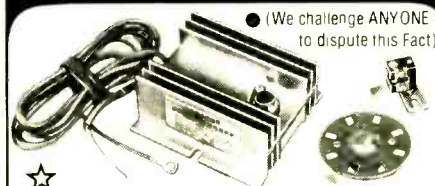'OPTO-ELECTRIC' The BEST...the ULTIMATE of ALL Ignition Systems!



(We challenge ANYONE to dispute this Fact!)



Never wears out or needs any Maintenance!



gives you Maximum Power with continuous PEAK PERFORMANCE

while reducing Maintenance and Operating Costs!



★ The Allison OPTO-ELECTRIC System eliminates the Points and Condenser, replacing them with an OPTO-ELECTRONIC TRIGGER, using a Light-Emitting Diode and Photo transistor. The System operates on a beam of Light. As there are NO moving parts in rubbing contact, Friction-wear is completely eliminated. Timing adjustments are PERMANENT.


● Gives 40-Times more Timing accuracy than ANY system using "Mechanical Breaker-Points"! UNLIMITED RPM! "Electronically-Controlled" DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spark strength does not fall off at high RPM. POSITIVE SPARK helps eliminate "Misfire" for faster acceleration and improved Engine Performance. Sparkplugs LAST 3 to 10-Times LONGER.

● Easier Starting under any condition! Smoother running... (NO TIMING FLUCTUATION as with Magnetic Impulse Units). All SOLID-STATE Components UNaffected by Temperature, Moisture, or Vibration! Only Highest grade materials used. Guarantees you Solid, Dependable Performance!

● PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage. SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the Time, and that's the name of the game for the BEST in GAS MILEAGE AND ECONOMY.

★ Perfect Timing and Dwell never change.

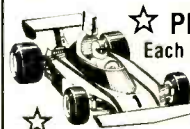● Pays for itself! Eliminates ignition Tune-Ups forever! "INFINITE LIFE" Once installed Never needs replacing!



★ PROVEN RELIABILITY!

Each Unit Tested to 15,000 RPM.

● Road and Race Proven. (Opto-Electric Systems won at INDY Two years in a row!)

You CAN install the ALLISON System in ALL the U.S. made & Foreign Cars! (4, 6, or 8-Cylinder).

"EASIEST-TO-INSTALL" UNIT ON THE MARKET. (Not necessary to dismantle Distributor as with other systems)

★ If you want the BEST, and SAVE! This is IT!

ORDER with CONFIDENCE... SATISFACTION GUARANTEED or Full Refund

10-YEAR FACTORY WARRANTY! (Free Repair or Replacement)

● Send Check or M.O.

State Make, Year, Engine Size (Calif. Res. add Tax)

★ (So New...it's Sold ONLY FROM FACTORY DIRECT).

● You may use your MASTER CHARGE or BANKAMERICARD. Send us (1) Your Number, (2) Interbank No. (3) Exp. Date

★ Before buying any other Type ignition system

Send Postcard for your FREE BROCHURE.

★ If you have already installed a C-D ignition system, Modernize and Increase its Efficiency... CONVERT YOUR "C-D" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT"...Only \$34.95

● Our BEST Salesmen are the users of our ALLISON System!



● America's Oldest and Largest Mfg. of Opto-Electronic Ignition Systems.

ALLISON
AUTOMOTIVE COMPANY

1267-L, East EDNA PL., COVINA, CAL. 91722

Circle 77 on reader service card

OCTOBER 1975

91

EDI

THOUSANDS OF BARGAINS—TOP VALUES IN Electronic Parts

Transistors, Modules, Speakers, Stereo, Hi-Fi, Photo Cells and thousands of other Electronic Parts. Send for FREE Catalog

ELECTRONIC DISTRIBUTORS INC.
Dept. TA-2, 4900 Elston
Chicago, Ill. 60630

☐ RUSH CATALOG

Name

Address

City

State

Zip Code

Circle 21 on reader service card

Design Engineers rely on Data Precision DMM's.

Now you can too. At Affordable Prices

Data Precision multimeters have been on the job and in the field with design engineers and technicians for a long time.

When reliable measurements are needed... they are proven performers.

A Full Range, 5-Function, 4½ Digit Portable Multimeter.



\$295.00


Model 245 is the smallest, lightest, and most accurate 4½ digit portable DMM you can buy.

It's rugged. Dependable. Precise.

Model 245 measures DC and AC current, DC and AC volts, and resistance with .005% resolution and a basic accuracy of $\pm .05\%$.

It features a bright .33" display, autopolarity, auto-decimal positioning, rechargeable battery or line operation, fused probes, carrying case and one year warranty.

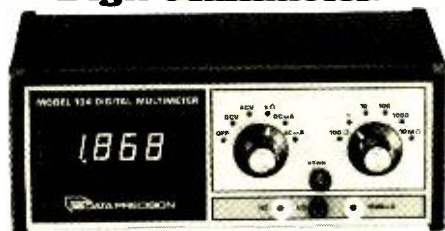A Full Range, 5-Function, 3½ Digit Multimeter.



\$189.00

Competitively priced to its analog equivalent, the Model 134 is 5 to 10 times more accurate and it is convenient, readable and free from operator error.

Model 134 measures DC volts, AC volts, DC current, AC current and resistance with a basic accuracy of $\pm 0.2\%$ through a total of 22 range scales.

It features auto-decimal positioning, autopolarity, 100% overranging, and a full ½ inch, bright, easy-to-read display, fused probes and one year warranty.

Contact Data Precision or the Data Precision representative nearest you. Data Precision Corporation Audubon Road Wakefield, MA 01880, Phone (617) 246-1600

DATA PRECISION®
...years ahead

Circle 74 on reader service card

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

CREATIVE COMPUTING, a new magazine that looks at the effect of the computer on privacy, automation and jobs, medical care, pollution control, space exploration and people in general. In education, it treats computers as tools for teaching math, science, english and social studies. An emphasis on classroom activities contains book reviews, games, puzzles, fiction, poetry, cartoons and humor. Published bi-monthly, subscriptions \$8.00 a year, \$6.00 for students. Sample copy, \$1.00.—**Creative Computing**, P.O. Box 789M, Morristown, NJ 07960.

ELECTRICAL PRODUCTS, in this 1975 mail order catalog, items range from tool connector boxes to stripping tools, insulated terminals and splices, connectors of several varieties, indicator lamps, cable straps, cable cutters and much, much more. A 24-page catalog by a company new to the mail order business.—**AMP Special Industries**, Valley Forge, PA 19482.

Circle 47 on reader service card

TAPE PLAYER PARTS CATALOG #5. A 48-page catalog devoted exclusively to tape player parts. Lists a full line of tape player parts for almost all manufacturers and the illustrated parts section enables the user to select the parts he needs quickly. The only one of its kind that we know of and is available only from PTS Electronics, Inc. Copies are available from all branches for \$2.00 each.—**PTS Electronics, Inc.**, P.O. Box 272, Bloomington, IN 47401.

Circle 48 on reader service card

R-E LAB TEST REPORT

(continued from page 40)

right channel. (Later, the channels on the record are reversed.) Even without a sound-level meter, you can compare the level heard as each third-octave is played against the reference tone and move the levers, one at a time, until equal apparent volume is heard. If you do own (or can borrow) a sound-level meter, you can disregard the reference tone (by rotating your balance control so that you hear only the pink noise bands, octave by octave) and move the levers until the sound level meters reads the same for each octave on the recording. Using either method, we were able to complete the entire job (both channels) in under twenty minutes. Surprisingly, using the simpler method with no test equipment, our results were within 2 dB of the settings obtained using a sound-level meter. In our case, we were using fairly small speaker systems which are known to roll off below about 50 Hz, and sure enough, our final settings on the RP-2212 confirmed this fact. The 20/40 lever ended up at +6, while the 40/80 lever was set to +2. Room acoustics accounted for some of our other octave by octave settings which ranged from +3 dB to -4 dB. Since the RP2212 is equipped with a bypass feature (both equalize buttons in the out position) it is a simple matter to compare equalized with unequalized results.


Insertion of the RP2212 into our listening system introduced absolutely no degradation of signal-to-noise ratio. Our measurement of S/N for the RP-2212 itself was -96 dB referred to a 1 volt input and output, quite a bit better than claimed, and certainly better than the limitations imposed by our phono system and our other components.

An overall product analysis of the Soundcraftsmen RP2212 equalizer, together with our summary comments, appears in Table I.

R-E

tweeter for example, will produce a symmetrical dispersion pattern while a horn tweeter will produce an unsymmetrical pattern—wider in one direction than the other. Due to space limitations, it is impossible to provide both (vertical and horizontal) sets of dispersion graphs. Always assume that the manufacturer has provided the widest dispersion graph if the direction is not specified.

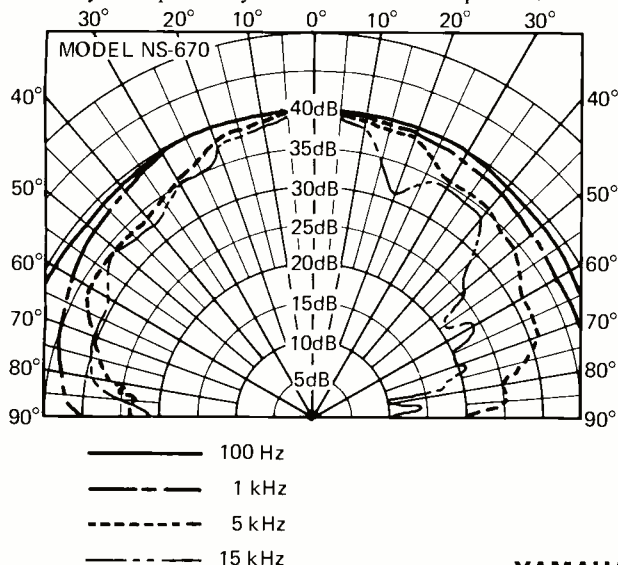Choose a speaker system with maximum dispersion. The more dispersion a speaker system has, the more realistic sounding it is. A speaker system with an excellent dispersion characteristic will be between 5-dB to 10-dB down from the on-axis output at 15 kHz. Very few speaker systems achieve this dispersion.



YAMAHA

Frequency response and dispersion are important specifications, but there's more. Next month, such specifications as distortion, linearity, efficiency, power handling capacity, maximum output and impedance will be discussed. A table listing these specifications—and others—from many manufacturers will be presented.

And that's not all. The third and concluding part of the article covers listening tests, room acoustics and speaker placement.

(continued next month)

MATCHED PAIR OF FET'S

After accidentally applying too much voltage to my FET VOM, the needle now pegs to the left in all positions except battery-check and DC current. I had trouble with this a while back, and the factory said it was a bad FET. What do you think?—E.D., Tappan, NY.

I think you're right. I did the same thing to one of mine and blew one of the FET's. You'll probably have two, since this is almost certain to use a bridge circuit. I got a matched pair of FET's and fixed mine.


Now, you can get "dual FET's"; these are in the same case and isolated from each other. They're made on the same substrate so that they almost have to match characteristics. I do not mean the dual-gate type FET, but two FET's in one package. Incidentally, if you can't locate this, RCA's SK-3116 FET's match very well, on testing.

PURPLE AND GREEN SCREEN

The screen of this RCA CTC-38 has a purple band about 5 inches wide and the rest of it is green. Voltages all seem to check out. Picture tube OK. Where do I go from here?—C.B., Bronx, NY.

Check No. 1. Turn the color control off. If this is a permanent thing, start checking some bypass and filter capacitors. Most likely cause would be some kind of screw-ball feedback through the demodulators or bandpass amplifiers. Check that electrolytic on the +140 volt line. Scope points that are bypassed. If you see anything there, check the bypass.

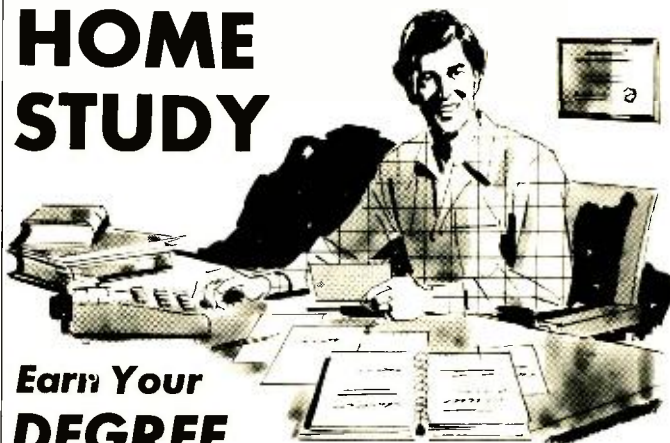Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through HOME STUDY



Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of independent study.

The Grantham correspondence degree program in electronics is comprehensive. It begins with basics, written in very simple language, and continues through the B.S.E.E. degree level. Throughout the entire program, heavy emphasis is placed on clear explanations written in great detail, progressing from the simple to the complex, in easy steps.

Our free bulletin gives complete details on the curriculum, the degrees awarded, the requirements for each degree, and how to enroll.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study

Mail the coupon below for free bulletin.

Grantham School of Engineering RE 10-75
2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for _____ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.


Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Circle 102 on reader service card

New

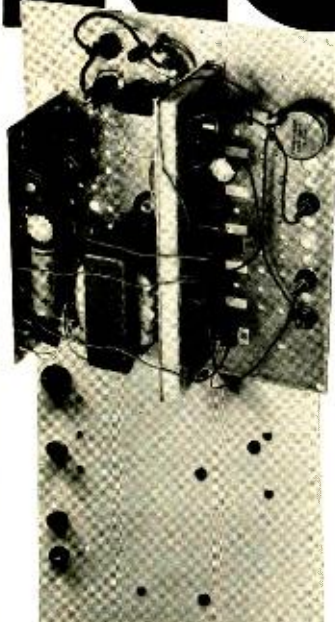

... UNIVERSAL ELECTRONIC INSTRUMENT DESIGN AND BUILD YOUR OWN ELECTRONIC INSTRUMENT IN HOURS, NOT DAYS!

Think of it. No circuit board to assemble or solder; just push your electronic components into the SK-10; no panels to lay out and machine — simply mount your parts ... combine your design with the self-contained power supplies and you've got a finished instrument.

Available in 3 kit versions to meet your unique requirements, it combines the SK-10 socket with the UMP-01 universal panel and gives the designer an instrument in 1/10th the time it would take with custom instruments.

From \$50.00 to \$85.00 depending on the power supplies you want. Write for free literature.

CIRCUIT DESIGN, INC.

Div. of E&L Instruments
P.O. Box 24
Shelton, Conn. 06484

Circle 72 on reader service card

ONE MARK AHEAD OF THE REST....



ADR Audio, one mark ahead of its competitors with the lowest prices of Famous Brand audio components, has now added complete CB & Video depts. All orders promptly shipped from the ADR warehouse in factory sealed cartons, fully warranted, fully insured. Send for our special price quote & newest money saving catalogue. It's your move ...

FOR IMMEDIATE QUOTE
CALL (202) 723-6060

A.D.R. AUDIO
6200 CHILLUM PLACE N.W.
WASHINGTON, D.C. 20011

Circle 76 on reader service card


LOOK FOR
THE
NOVEMBER
ISSUE OF
RADIO-
ELECTRONICS
AT YOUR
NEWSDEALER
OCT. 21

BOOKSHELF SPEAKERS


(continued from page 49)

sound that is lacking in the realistic concert hall qualities.

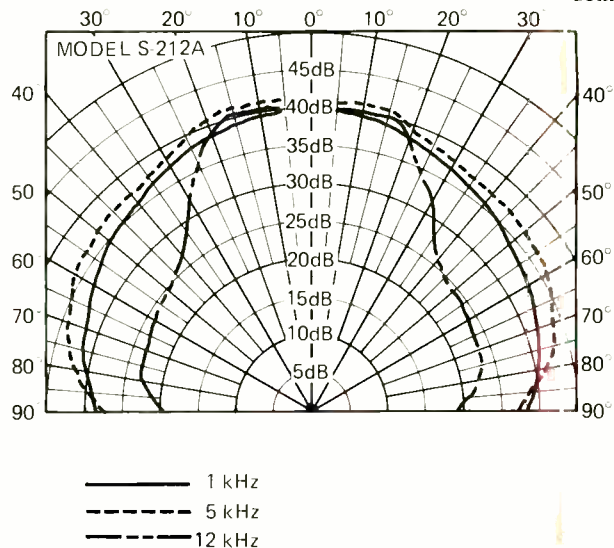
Different types of high-frequency drivers produce different dispersion patterns. Remember, dispersion is a measure of the ability of a speaker to radiate sound energy in different directions. This includes both the vertical and horizontal directions. A dome



SUPERSCOPE

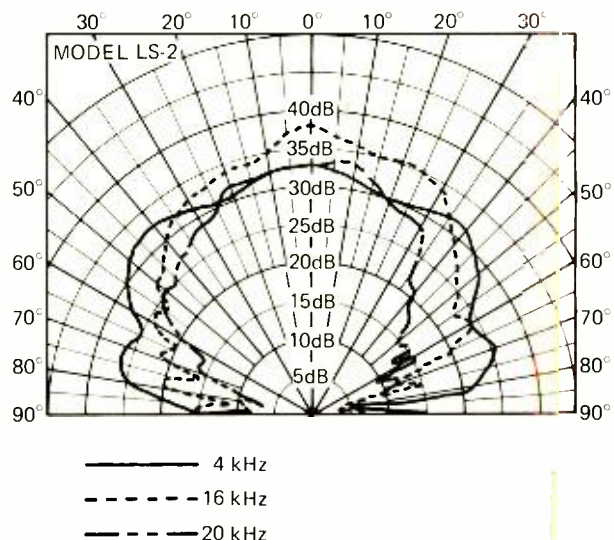

TEMPEST

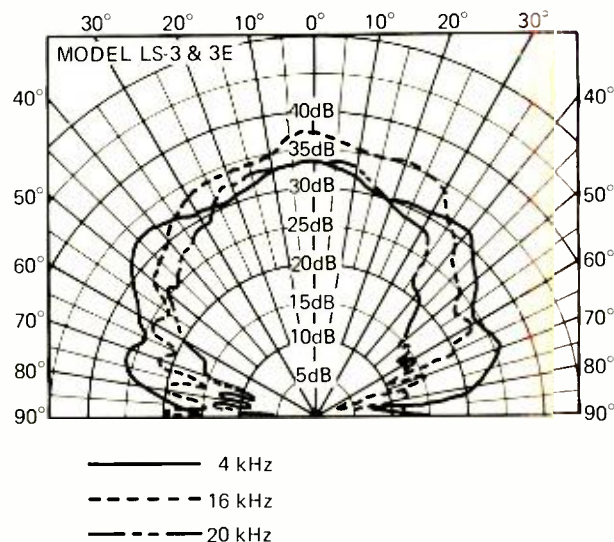

TEMPEST


ator in one integrated unit. Automatic self-tuning maintains a uniform power level for rapid, thorough cleaning action. The stand-



ard units operate from 120 VAC, to 60 Hz. Accessories include self-suspending trays, baskets and covers. Prices start at \$98 for the 1½ quart model to \$317 for the 8-quart model.—Tooltronics, Inc., 710 Ivy St., Glendale, CA 91204

Circle 44 on reader service card

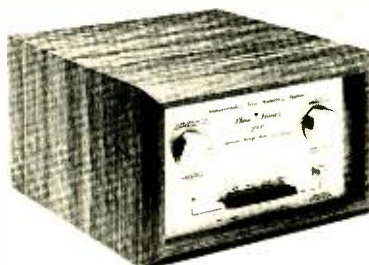
NOISE REDUCTION SYSTEM. The Autocorrelator model 1000 is an outboard unit that may be inserted into the tape-monitor path of almost any hi-fi system. It features noise reduction of up to 10 dB on any stereo source without high-frequency loss or the need for pre-encoding—a dynamic range-recovery system that selectively expands any



program material 7.5 dB without audible ill-effect—a dynamic low-pass filter which removes low-frequency noise without affecting the program material. An additional tape-monitor circuit replaces the one occupied. Price \$349.—Phase Linear, PO Box 1335, Lynnwood, WA 98036

Circle 45 on reader service card

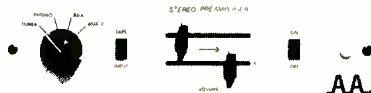STEREO PHONO PREAMP, designed without tone controls, is for use with an equalizer. Phono sensitivity is 10 mV for 1 volt output; 47K input impedance, hum and noise 76 dB below 10 mV input. RIAA equalization ±0.5



dB. The high-level inputs (FM, AUX 1, AUX 2) are passive. Input impedance is 50K without output load, 25K with 50K output load. Output impedance 0 to 12.5K, varies with volume control setting.—\$74.95 kit; \$99.95 wired.—Ace Audio Co., 25 Aberdeen Drive, Huntington, NY 11743

Circle 46 on reader service card



the audio amateur?

What a trip old Richard's Rhine journey could have become had he built his own mixers, 900 watt amps, octave equalizers, 24 inch woofers, electronic crossovers, and home brew electrostatics. Sounds what sounds!

Ask our Rhine maidens for details.

the Audio Amateur Peterborough, N. H. 03458R
Send for a free prospectus.

Name _____
Street _____
City _____ State _____ Zip _____

Circle 70 on reader service card

Test Equip. Special Discount Prices



- ☐ TRANSISTOR RADIO asst type good, bad, broken, as-is, potluck 1.50
- ☐ TAPE RECORDER assorted types good, bad, broken, as-is, potluck 4.00
- ☐ 200 ASST. ½ W RESISTORS Top Brands, Short Leads, Excellent Selection 1.00
- ☐ 75-ASST ¼ WATT RESISTORS stand, choice ohms, some in 5% 1.00
- ☐ 100-ASST ½ WATT RESISTORS stand, choice ohms, some in 5% 1.00
- ☐ 70-ASST 1 WATT RESISTORS stand, choice ohms, some in 5% 1.00
- ☐ 35-ASST 2 WATT RESISTORS stand, choice ohms, some in 5% 1.00
- ☐ 50-PRECISION RESISTORS asst, list-price \$50 less 98% 1.00
- ☐ 20-ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt 1.00
- ☐ 250-ASST SOLDERING LUGS best types and sizes 1.00
- ☐ 250-ASST WOOD SCREWS finest popular selection 1.00
- ☐ 250-ASST Self Tapping SCREWS #6, #8, etc. 1.00
- ☐ 100-ASST 6/32 SCREWS and 100-6/32 HEX NUTS 1.00
- ☐ 100-ASST 8/32 SCREWS and 100-8/32 HEX NUTS 1.00
- ☐ 100-ASST 2/56 SCREWS and 100-2/56 HEX NUTS 1.00
- ☐ 100-ASST 4/40 SCREWS and 100-4/40 HEX NUTS 1.00
- ☐ 100-ASST 5/40 SCREWS and 100-5/40 HEX NUTS 1.00
- ☐ 500-ASSORTED RIVETS most useful selected sizes 1.00
- ☐ 300 ASSORTED WASHERS most useful selected sizes 1.00
- ☐ 100-ASST RUBBER BUMPERS for cabinet bottoms—other uses 1.00
- ☐ 100-ASST RUBBER GROMMETS best sizes 1.00

MARKET SCOOP COLUMN

- ☐ 4-ASSTD. PHILCO SWITCHES —PUSH—PUSH TYPE #V2-3-4, & Sig. Sw. With knobs latest type 2.99
- ☐ POWER TRANSFORMER (PT-43)—110V Pri.—12V Sec. Used in many transistor Power supplies 2.29
- ☐ COMPLETE CONVERGENCE ASSY.—Inc. Yoke, Board & Plug Conn. Adaptable to most 90° sets 3.95
- ☐ COLOR DELAY LINE—Used in most color sets 1.69
- ☐ Silicon NPN HV TRANSISTOR RCA—SK-3021—Hep-240 1.00
- ☐ RCA—SK-3026—Hep-241 Transistor Specials—Your Choice SK3006, SK3018, SK3020 SK3122, SK3124 1.00
- ☐ Transistor Specials—Your Choice SK3005, SK3021, SK3040 1.98
- ☐ TACHOMETER 2 1/4" Sq. Panel Meter 1 VDC, full scale 33 Ohm coil resistance 0-6000 R.P.M. 2.00
- ☐ 1-CASSETTE type dynamic Mike with universal plugs—200 Ohms 2.99
- ☐ VU 1" PANEL METER 0-20 db Scale 1.29
- ☐ 100' GREY SPEAKER WIRE 2 Cond. mini zip, 101 uses 2.00
- ☐ WAHL-CORDLESS SOLDER IRON Complete with Auto (Charger-Fast Heating-Compact Sub-min for Trans Radios 15.95
- ☐ 5-Audio Output TRANSFORM 456-ke for Transistor Radios 1.00
- ☐ 5-I.F. COIL TRANSFORMERS 456-ke for Transistor Radios 1.00
- ☐ 8" UNIVERSAL SPEAKER Top quality Special buy 1.59
- ☐ 12" UNIVERSAL SPEAKER Top Quality... Large Magnet 5.99
- ☐ 10" PHILCO SPEAKER Top Quality... Large Magnet 3.95
- ☐ 8" UNIVERSAL SPEAKER Large Magnet—Special Buy 2.99
- ☐ 3" UNIVERSAL TWEETER 1 oz. Magnet 1.29
- ☐ 2 1/2"x4" SPEAKER Special Buy 10 for \$5 69¢
- ☐ 4"x6" "QUAM" 16 OHM SPK. Large magnet... Special BUY (10 for \$15.00) 1.79
- ☐ 8" HEAVY DUTY 10 OZ. SPEAKER Ceramic Type—8 Ohm 4.50
- ☐ 1-6"x9" Heavy Duty 10 oz. Speaker Ceramic Type... 8 Ohm 4.50
- ☐ 3-ELECTROLYTIC CON. 2-1000 100/80/20 MFD—300 Volts 2.00

- ☐ 3 SPEAKER—7 WAY SELECTOR 1.00
- ☐ SWITCH Wall Mount 1.50
- ☐ 7 TUBE AM-FM STEREO AMPLIFIER CHASSIS. Completely assembled—AS IS needs slight adjustments 17.50
- ☐ 110° TV DEFLECTION YOKE for all types TV's incl schematic 4.95
- ☐ "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE 6.95
- ☐ 90° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) 2.95
- ☐ 90° TV DEFLECTION YOKE for all type TV's (Blk. & Wht.) 3.95
- ☐ 70° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) 2.00
- ☐ 70° TV DEFLECTION YOKE for all type TV's (Blk. & Wht.) 2.00
- ☐ OLYMPIC & SHARP FLYBACK Part #8FT522 Equip. Stancor #HO-408—Thorndarson #Fly339 2.00
- ☐ 90° COLOR YOKE For all Rectangular 19 to 25" 7.95
- ☐ 70 COLORE YOKE For all round color CRT's DELMONICO NIVICO COLOR FLYBACK Part #A20411-B 7.95
- ☐ RCA 110° FLYBACK TRANSFORMER For Blk. & Wht. sets 18KV—For all types TV's, Inc. schematic 3 FOR 10.00 3.95
- ☐ WESTINGHOUSE FM TUNER #476-V-015D0 1 Transistor 3.99
- ☐ WESTINGHOUSE FM TUNER (12D78 Tube) 1.00
- ☐ UHF TUNER—Transistor Type Used in all TV sets 2.95
- ☐ G.E. UHF TUNER—TRANSISTOR TYPE Model #55X4 3.95
- ☐ ADMIRALTY TUNER Model #94C308-1 (2HA5-4LJ8) 7.95
- ☐ Model #794C411-3 (Transistor) 7.95
- ☐ WELLS GARDNER TUNER Part #7A 120-1 (4GS7-2HA7 Tubes) 7.95
- ☐ G.E.—TV TUNER (2GK5-4LJ8) Model #EP 86x11 7.95
- ☐ PHILCO VHF/VHF TUNER Transistors 9.95
- ☐ GET TV TUNER ET 86x196, (6GK5-6BL8) 5.95
- ☐ UNIVERSAL TV Antenna Back of set mounting... 5 section rods 2.99
- ☐ BLUE LATERAL Magnet Assy. Replacement for most color TV's 5-10K—2 WATT BIAS POTS 1.79
- ☐ Used in solid state application 1.00
- ☐ COLOR CONVERGENCE ASSY. Universal type—good for most sets 2.49

- ☐ COLOR-TV RECTIFIER—Used in most color sets—6500 kv 3 for 1.95
- ☐ 4 — TV ALIGNMENT TOOLS most useful assortment #1 1.00
- ☐ 4 — TV ALIGNMENT TOOLS For Color TV #2 1.49
- ☐ 6 — TV COLOR ALIGNMENT TOOLS Most popular type 2.79
- ☐ TV TWIN LEAD-IN 300 ohm 500'—\$7 100'—\$1.50, 50' 1.00
- ☐ CO-AX CABLE RG59 (Black) 250'—\$10, 100'—\$4.50, 50' 2.09
- ☐ 5-DUAL DIODE—MOST POPULAR TYPES Common cathode or Series connected CONVERGENCE RECTIFIER—For COLOR TV 4 Cell—Used in RCA—Philco, etc. 1.00
- ☐ TV DAMPER DIODE Single—Replace RCA part #120818 Dual—RCA part #135932 \$2.29 \$3.95
- ☐ COLOR POWER TRANS. —Good for most sets 26R150 List Price—\$36.75 6.95
- ☐ 6-Top Brand SILICON RECT. 1 amp, 1000 PIV. 1.00
- ☐ 5-PNP TRANSISTOR general purpose, TO-5 case 1.00
- ☐ 25-ASSORTED TRANSISTORS big factory scoop—solid as-is 1.00
- ☐ 5-9 VOLT MOTORS Excellent for hobbyist 1.00
- ☐ 2-ELECTROLYTIC COND 1000 mfd.—25V 1.00
- ☐ ELECTROLYTIC CONDENSER 300 mfd.—200V 1.00
- ☐ 2-ELECTROLYTIC CONDENS. ERS 80/100/60 MFD—160V 1.00
- ☐ 2-ELECTROLYTIC COND 200/30/4—mfd—350V 1.00
- ☐ 3-ELECTROLYTIC COND 100 mfd.—100V. 50 mfd.—75V 1.00
- ☐ 2-ELECTROLYTIC COND 40 mfd.—500V. 40 mfd.—400V 1.00
- ☐ 8-MINI PILOT BULBS With 8" Leads—6.3V 30MA (5000 Hrs) 1.00
- ☐ 8-MINI PILOT BULBS With 12" Leads—6.3V, 150MA (5000 Hrs.) 1.00
- ☐ 32—TEST PROD WIRE DELUXE QUALITY red & black 1.00
- ☐ 10-MINI ELECTROLYTIC Cond For Transistor & miniature work 1.00
- ☐ 2-Colorburst Quartz-Crystal For most color TV sets 3579.545 KC 1.09
- ☐ 5 ASST GLOBAL VARISTOR Popular replacements for most COLOR TV 1.00
- ☐ UHF or VHF Matching Trans. Simple Fool-proof installation 1.00

Minimum Order \$5.00

IMMEDIATE DELIVERY... Scientific light packing for safe delivery at minimum cost.

HANDY WAY TO ORDER... Send check or money order, add extra for shipping. Lists of new offers will be returned in your order.

Please specify refund on shipping overpayment desired: ☐ CHECK ☐ POSTAGE STAMPS ☐ MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N.Y. 10024

TELEPHONE 212-874 5500

Circle 71 on reader service card

DELUXE DIGITAL COLOR CONVERGENCE GENERATOR


NOW AT A PRICE EVERYONE CAN AFFORD

ROCK SOLID PATTERNS
ALL IC COUNTDOWN CIRCUITS
QUARTZ CRYSTAL OSCILLATORS
2 FULL YEARS' WARRANTY



MODEL SG-200 \$99⁹⁵

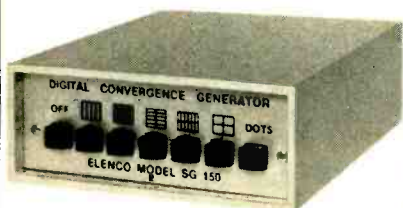10 Patterns: Full & Gated Rainbow, 4 Crosshatch, 4 Dot, Die Casted 1/8" Aluminum Case.



MODEL SG-150 \$75⁹⁵

10 Patterns: B&W Bars, White Field, 4 Crosshatch, 4 Dot.



MODEL SG-100
ONLY \$59⁹⁵

2 Patterns: 20 x 16 Crosshatch, 320 Dots, weight only 17 oz.

FULL 15 DAYS MONEY BACK GUARANTEE

See Your Distributor or Write:

ELENCO ELECTRONICS INC.
8744 W. North Ter., Niles, Ill. 60648

312-564-0919 MODEL SG-

- ☐ My check or money order enclosed.
☐ COD—Add \$2.50 mailing & handling.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

DISTRIBUTORS' INQUIRIES INVITED

Circle 69 on reader service card

NEW PRODUCTS

(continued from page 81)

tion 100 watts, intermodulation distortion at rated output maximum 0.1%, frequency response at 1 watt 8 to 25,000 Hz \pm 1 dB, power consumption 400 watts max. \$1500.00. Size 21 1/4" X 6 1/2" X 13. Weighs 42 lbs.—**H. H. Scott, Inc.**, 111 Powdermill Rd., Maynard, MA 01754

Circle 38 on reader service card

AM-FM/STEREO CASSETTE PLAYER, the model CP650, is a complete car entertainment system with many convenience features. It offers a built-in AM-FM/Stereo radio, AM/FM slide bar selector, fast-forward con-



trol, pushbutton cassette ejector, FM local-distant control, AM/FM indicator and stereo balance control.

Pushbuttons provide finger-tip tuning of any five preselected AM or FM stations. Can be mounted in almost any dashboard without the need for any kits or alterations.—**Audiovox Corp.**, 150 Marcus Blvd., Hauppauge, NY 11787

Circle 39 on reader service card

FM/AM STEREO TUNER, model TX-7500 contains new internal circuit innovations for improved selectivity, sensitivity and stable stereo FM performance. Features include: 4-section variable capacitor and phase-linear FET in FM front end; 6-stage limiter, three double-tuned phase-linear ceramic filters, monolithic IC with wide-band quadrature detector in FM IF section; phase-lock-loop stereo multiplex decoder; center-of-channel and signal strength meters; positive acting reed-relay FM muting circuit; switchable noise filter.



Specifications: IHF sensitivity—1.9 μ V, 50 dB quieting—4 μ V mono; 50 μ V stereo, signal-to-noise ratio: 73 dB mono; 68 dB stereo, total harmonic distortion: (1 kHz mono) 0.2%; (1 kHz stereo) 0.3%; (10 kHz mono) 0.2% (10 kHz stereo) 0.6%. Capture ratio 1 dB, selectivity 80 dB, stereo separation 40 dB (1 kHz); 35 dB (50 Hz to 10 kHz). Image rejection 85 dB, 1F and spurious rejection 90 dB, AM suppression 55 dB and sub-carrier suppression 65 dB. Muting threshold: 2.2 μ V. Output level: (fixed) 650 mV; (variable) 50 mV to 1.5 V. Power requirements: 120 V 60 Hz, 20 watts. Dimensions: 16 1/2" wide by 5 1/2" high by 14 3/8" deep. Net weight: 18 lbs. 2 oz. Price: \$249.95. Case in walnut is \$34.95 additional.—**U.S. Pioneer Electronics**, 75 Oxford Drive, Moonachie, NJ 07074

Circle 40 on reader service card

DIGITAL CLOCK/THERMOMETER, model ES 142, displays 12- or 24-hour time in six digits, and Fahrenheit or Celsius temperature in three digits, from -50°F to +150°F. Displays are planar gas discharge, .55 in. in height. Included is a temperature probe and 25 feet of cable. Any cable length up to 500 feet may be ordered. Unit is housed in an aluminum



case with simulated walnut sides and sells for \$225. The Thermometer may be purchased separately at a cost of \$150. The part number is ES 240.—**ESE**, 505 1/2 Centinela Ave., Inglewood, CA 90302

Circle 41 on reader service card

POWER AMPLIFIER, model D-150A, replaces the earlier Crown D-150. Can drive any load safely, even those below 4 ohms. Unit has a power rating of 90 watts per channel into an 8-ohm load over a bandwidth of 1 Hz—20 kHz, at a rated RMS sum total harmonic distortion of 0.05%. Front panel level control for each channel; on-off switch and pilot light. Rear panel stereo-mono switch permits user to change from stereo to mono with no internal wiring changes. Output stages include



class AB + B configuration. No quiescent bias current is used in the output transistors for better efficiency and wide band response.

Specifications include: frequency response: \pm 0.1 dB from DC—20 kHz at 1 watt into 8 ohms; \pm 1 dB DC—100 kHz. At 1 kHz power output is 90 watts RMS into 8 ohms, per channel, both channels operating, 0.1% total harmonic distortion. Damping factor greater than 400. Output Impedance less than 15 milliohms in series with less than 0 microhenries. Input Sensitivity 1.19 volts \pm 2% for 80 watts into 8 ohms.—**Crown International**, 1718 W. Mishawaka Rd., Elkhart, IN 46514

Circle 42 on reader service card

FM DEVIATION MONITOR, the model 205D, measures peak carrier modulation deviation of 2-way radio transmitters. Carrier frequency range 25—1000 MHz. Frequency deviation measurement is 5% of full-scale and is measured on three deviation scales: 0—2.0 kHz (for tone squelch, etc.), 0—6.0 kHz (for upper



reading at 5 kHz) and 0—20.0 kHz (for wide-band modulation). The precision discriminator is linear to 2% over a 100 kHz bandwidth. RF sensitivity is 15 mV or better to 450 MHz. FM limiting holds to within 2% or less over a 100:1 range of input voltage. The 205D operates from 12 VDC or 120 V, 50 to 400 Hz. \$525.—**Lampkin Laboratories, Inc.**, PO Box 9048, Bradenton, FL 33506

Circle 43 on reader service card

ULTRASONIC CLEANERS for bench-top installations are available in sizes ranging from 1 1/2 to 8 quarts. The *Ultra-Clean* units are compact in design with the tank and gener-

program which gives you in electronic circuit design

only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

Electronic circuit design—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. *Yet, only CREI teaches electronic circuit design at home.*

ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which *you* must have to move to the top in advanced electronics.

CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.



Send now for our full-color, eighty page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong *personal* help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. *And he may offer to pay all or part of your tuition cost.* Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. *If they are willing to pay for CREI training for their employees, you know it must be good.*

Send for Advanced Electronics today. You'll be glad you did.



CREI Dept. E-1405F
3939 Wisconsin Avenue
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name _____ Age _____

Address _____

City _____ State _____ ZIP _____

If you have previous training in electronics, check here ☐

Employed by _____

Type of Present Work _____

Veterans and servicemen, check here for G. I. Bill information ☐


CREI

**CAPITOL
RADIO
ENGINEERING
INSTITUTE**

WASHINGTON, D.C. 20016


CREI—the only home-study college-level training

and now

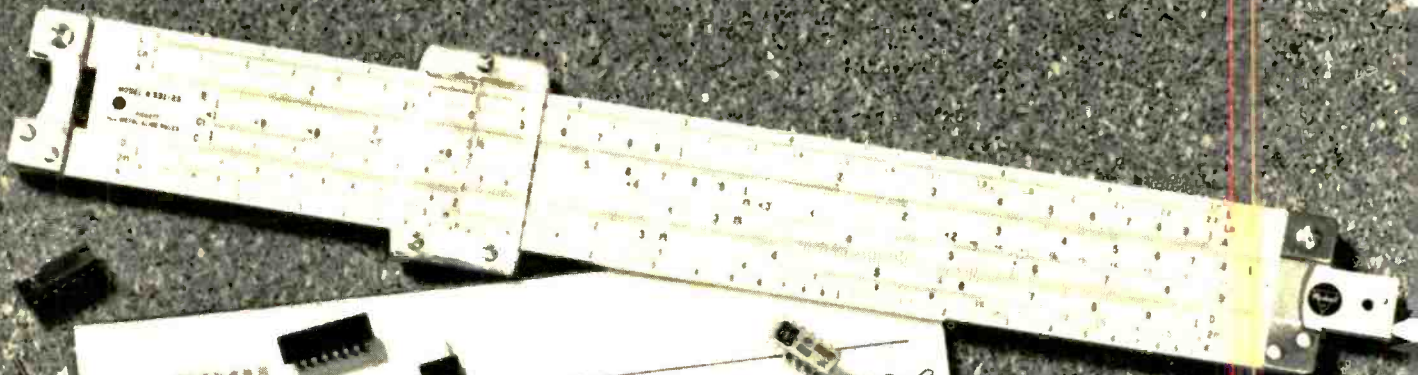

CREI

COMPARATOR
CONTROLLED
CLOCK

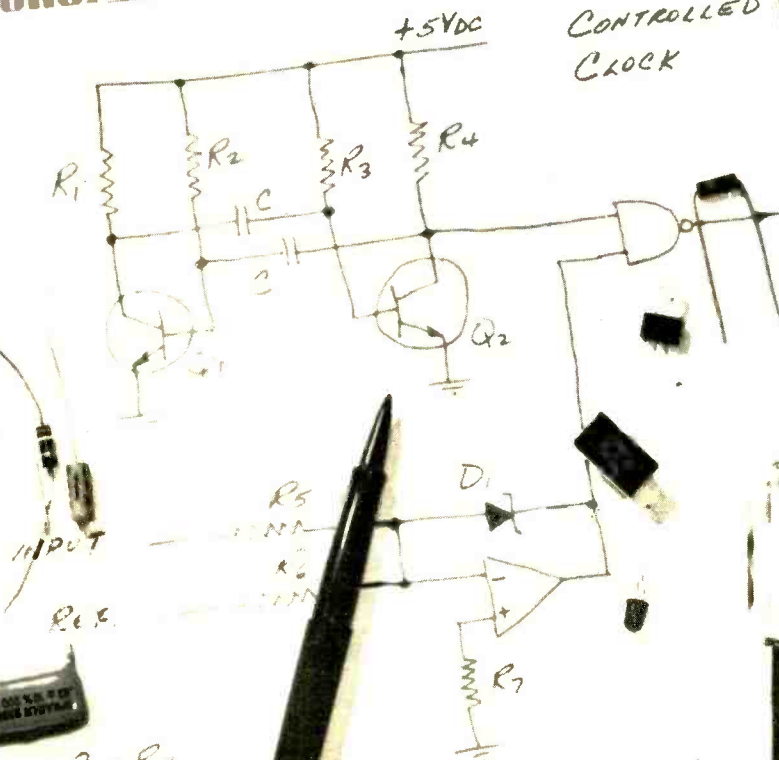

$$R_1 = R_4$$

$$R_2 = R_3 = R$$

$$T = .7RC$$

$$f = \frac{1}{2T}$$





and draws less than 1 ampere of battery power. Arming the system is a throw of a hidden switch within the vehicle. The hidden switch must be turned off within 15 seconds of entering the vehicle or alarm will sound. Unit can be provided with automatic turn-off and reset features. No fender hole or lock. Built to withstand all weather conditions. Components are guaranteed for 90 days. **Wolo Manufacturing Corp.**, 37 Jefry Lane, Hicksville, NY 11801

Circle 37 on reader service card

DIGITAL RECEIVER, model RD 1000, the manufacturer's top-of-the-line unit uses a true digital frequency synthesis tuner coupled with a conservatively designed power amplifier section rated at 100 watts minimum continuous power per channel with both channels driven into 8 ohms at a maximum of 0.15% total harmonic distortion. Tuner section includes the phase-locked-loop and quartz crystal frequency standard and has the addition of a memory section programmable by the user. Up to ten FM station frequencies may be entered through the tuner section's keyboard. These selections are retained in the memory and any one may be called up at any time by pressing a single button. The memory is non-destructive, retaining the programmed station selections. Even when the unit is turned off or disconnected from the power line.



Additional tuning modes include manual selection by punching in the desired FM station frequency, and scanning up or down the FM band in either STEREO ONLY or ALL STATION modes. The digital display is a solid-state 7-segment unit which can be read from across the room. Signal strength is indicated by a series of four LED's instead of a conventional meter. Another LED indicates whether a stereo signal is being received and yet another lights up if multipath reception occurs. Specifications include: Tuner Section—Tuning accuracy within 0.001%, sensitivity for 30 dB signal to noise ratio, 15 kHz deviation 0.9 μ V, IHF sensitivity 1.7 μ V, sensitivity for 3 dB below full quieting 4.8 μ V, frequency response 20 to 15,000 Hz \pm 1 dB, total harmonic distortion, mono 0.2%, total harmonic distortion, stereo 0.3%, stereo separation at 1 kHz 40 dB, selectivity 100 dB, capture ratio 1 dB, cross modulation rejection 95 dB, spurious response rejection 100 dB, image rejection 85 dB, AM suppression 75 dB, subcarrier suppression 65 dB, warm-up drift 0.001%, station acquisition time 10 milliseconds, automatic scanning speed 5 channels per second, FM deemphasis 25, 50 or 75 μ s switch selectable. Amplifier Section—minimum continuous power output per channel, both channels driven into 8 ohms across 20 to 20,000 Hz at no more than 0.15% total harmonic distortion.

(continued on page 86)

Now...the most enjoyable do-it-yourself project of your life—a Schober Electronic Organ!

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you—whatever you are, whatever your skill (or lack of it)—how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.



Circle 68 on reader service card

Five superb models with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished—lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builders—owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives—first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!

The **Schober Organ Corp.**, Dept. RE-143
43 West 61st Street, New York, N. Y. 10023

- ☐ Please send me Schober Organ Catalog.
☐ Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

You'll never know how much good you can do until you do it.

You can help people

In fact, there's a crying need for you. Your talents. Your training. Your concerns. They make you valuable to your business. They can make you priceless to your community.

If you can spare even a few hours a week, call the Voluntary Action Center in your town. Or write "Volunteer," Washington, D.C. 20013.

It'll do you good to see how much good you can do.

Volunteer.
The National Center for Voluntary Action

A Public Service of This Magazine & The Advertising Council

312 FASCINATING PAGES!

A FLICK OF THE SWITCH new 1930-1950 book



- Re-live the great days of radio broadcast and the beginnings of TV-electronics.
- Browse through 1,000 pictures and interesting old ads.
- Discover the rewards of radio collecting and restoration.
- Own a First Edition of this valuable reference book.

This new book includes broadcasting, home radio-TV, Amateur radio, World War II radio-electronics, the radioman, collecting and "how it works." \$9.95 hard-cover, \$6.95 handbook.

Other valuable books are Vintage Radio (1887-1929) \$7.95 hard-cover, \$5.95 handbook; Radio Collector's Guide (1921-1932) \$4.95; 1927 Radio Encyclopedia \$12.95 hard-cover, \$9.95 soft-cover; 1926-1938 Radio Diagrams, \$7.00. Also, we'll furnish any pre-1951 diagram for \$3.50. 10-day return privileges.

Send today to Vintage Radio, Dept. R, Box 2045, Palos Verdes Peninsula, CA., 90274. Postage paid. Cal. residents add 6% tax.

TOTAL _____

Name _____
Address _____
City _____ St. _____ Zip _____


FREE Radio Age Guide with each order FREE

NEW VINTAGE RADIO BOOK

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

DISTRIBUTION AMPLIFIER, model IDA-45, for use in Master Antenna TV (MATV) systems with up to 35 channel capability. The new amplifier meets or exceeds FCC rules Part 76. It is fully adaptable to 2-way communications systems as required for a CATV/MATV interface amplifier. Radiation shielding exceeds 90 dB. Gain is at least 45 dB over a range of 50 to 300 MHz. Push-pull output circuitry cancels second harmonic distortion. Used to interface with CATV, output levels

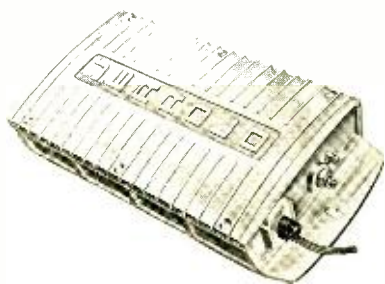

can be as high as +48 dBmV per channel in 35 channel systems or up to +54 dBmV per channel in 12-channel systems. At these levels, cross modulation does not exceed -57 dB, second order beat -68 dB and triple beat -72 dB. In standard MATV applications where cross modulation specs are -46 dB, output level can be as high as +52.5 dBmV with 30 channels or +57 dBmV with 12 channels. Noise figure is 8 dB and response is flat with ± 0.4 dB. Plug-in accessory modules make the new amplifier versatile. Overload control compensates for input signal level fluctuations. \$438.00. —**Jerold Electronics Corp.**, 200 Witmer Rd., Horsham, PA 19044

Circle 31 on reader service card

STEREO RECEIVER, model 525, features a quadrature FM detector, zero-center tuning meter. FET front end. IF section using solid-state, tuned filters and integrated circuits. Multiplex detector uses phase-locked-loop circuitry and the AM section has a high usable sensitivity. Power amplifier uses trans-




formerless, complementary-symmetry output circuit to insure wideband response and low distortion at all power levels up to the unit's rated 25 watts per channel (Min. RMS, both channels driven into 8 ohms, from 20 to 20 kHz with no more than 0.5% total harmonic

distortion). \$349.90.—**Pilot Radio Sales**, 165 West Putnam Ave., Greenwich, CT 06930

Circle 32 on reader service card

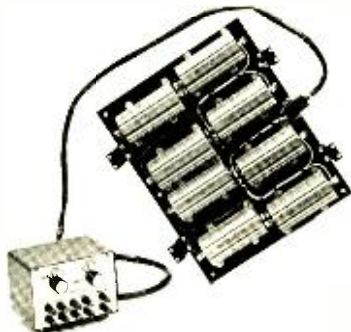AUDIO DUMMY LOAD, the model 250, for audio power amplifiers under test. It features 4, 8 and 16-ohm loads composed of 1% resistors. Power handling capability is 1000 watts RMS in monaural mode, 500 watts RMS in stereo and 250 watts RMS per channel in



4-channel mode. The load resistors are on a heat sink that can be mounted on or under the service bench. Input terminals and mode and selector switches are connected to the load through a cable. A switch position is provided for by-pass operation and jacks are provided for scope monitoring. \$250.00 FOB. —**B.P.I.**, 7853 Balboa Ave., San Diego, CA 92111

Circle 33 on reader service card

FASTENING AND HOLDING DEVICES made of nylon or flame-retardant plastic are now available for use in electrical and electronic applications. The family of devices includes



printed-circuit board guides, circuit board supports, plastic spacers, cable clamps and

hangers, component clips, tension clips, strain-relief bushings, wire ties, wire saddles, continuous grommets and spiral wrappings. —**Mallory Distributor Products Co.**, 3029 E. Washington St., Indianapolis, IN 46206

Circle 34 on reader service card


DESOLDERING AID, *Wik-It*, is a special chemically treated metal braid which, when laid on the soldered joint and then heated with the soldering iron, will suck up the molten solder by capillary action; leaving a joint that is now clean and free of solder. When the solder is removed from the joint,



you just snip off about 1/2 inch of *Wik-It* which is then ready for use again. The braid comes in different sizes to suit transistor and IC applications as well as vacuum tube circuits and heavy wire work. Lengths range from 5 to 100 feet. Typically, *Wik-It* is a 5-foot length in a handy plastic spool with prices ranging from \$1.59 to \$1.79, depending on width. —**Wik-It Electronics Corp.**, 140 Commercial St., Sunnyvale, CA 94086

Circle 35 on reader service card

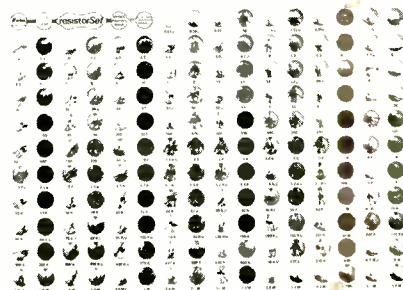RESISTOR SET, *RS-10*, is designed so the experimenter, lab technician, service technician or electronic designer will never be delayed by the lack of a specific carbon-film resistor. The *RS-10* contains 2725 1/4-watt, 5% carbon-film resistors in 170 different values ranging from 0.51 ohm to 5.6 meg-



ohms. The quantity of each resistor value supplied has been determined by service-industry use analysis. Quantities range from five-of-a-kind for seldom-used values to twenty each of the most popular resistances. \$126.00.—**Energy Electronic Products Corp.**, 6060 Manchester Ave., Los Angeles, CA 90045

Circle 36 on reader service card

KEYLESS VEHICLE ALARM, model 512-K. Electronic burglar alarm kit can be installed in any vehicle in 30 minutes. Warning police-type sound. Unit uses solid-state components

BUILD MATRIX SYNTHESIZER

(continued from page 35)

board is in Fig. 6. After it is completed, check it out and make sure it delivers proper voltages before connecting it to the synthesizer.

After you've built and added your synthesizer to your hi-fi system you'll have to consider the question of how to position your speakers for the most effective sound reproduction. There are several different approaches that you can take.

First there is the conventional 4-corner approach shown in Fig. 7. This

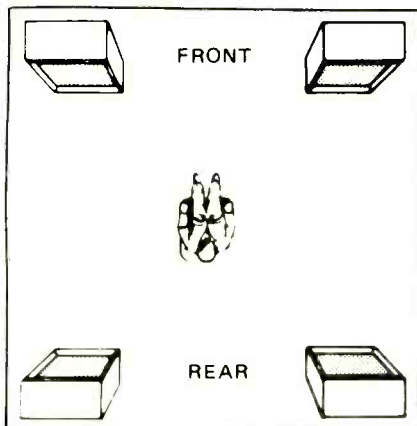


FIG. 7—CONVENTIONAL 4-CORNER speaker placement approximates live sound field.

is the most widely accepted speaker setup for 4-channel listening. It surrounds the listener with sound closely approximating the live sound field. This speaker placement is particularly effective for playback of modern music, rhythm and blues, popular music and some varieties of modern music. When live recordings are played back, audience sound and hand clapping are often heard from the rear speakers and help make the listener feel that he is a part of the audience.

By having the rear speakers up front and having them face the front speakers as in Fig. 8, the sound field becomes similar to that of a stage sitting in front

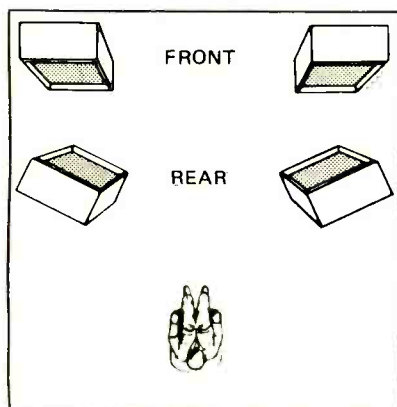


FIG. 8—SPEAKER PLACEMENT places listener in position of original audience.

of you. Now you are placed in the position of the original audience. Listening to classical music with this speaker arrangement is particularly effective.

Since this 4-channel synthesizer derives its information for reorganizing the information already present in the original 2-channel stereo program material, the effectiveness of the sound you will hear is determined by the amount of directional information that is present and available for synthesizing in your 2-channel source.

Most stereo program sources are suitable for synthesizing with the effectiveness of the conversion being limited

only by the method by which the original material was prepared. Occasionally using the synthesizer rear channel sound may be "shaky" while that from the front channels is not.

Overall, the synthesizer is a great way to turn your current library of 2-channel music into 4-channel surround sound at a reasonable cost. Naturally, synthesizing 2-channel sound into 4-channel sound is not the same as listening to 4-channel music, but it does come close; close enough, in my opinion, to make it a worthwhile project that will deliver real satisfaction to the experimenter and hours of listening pleasure.

R-E

BARGAIN BONANZA OF EDLIE HIGHEST QUALITY KITS ONLY NEW PRODUCTS

- ☐ (G175) 70 1/2w CARBON RESISTORS \$1.00
Asst. values. Some 5%.
- ☐ (G154) 150 CUT LEAD RESISTORS \$1.00
Carbon, all leads long enough for soldering.
- ☐ (G149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00
- ☐ (G132) 20 DUAL POTS \$1.00
- ☐ (G138) 10 SLIDE SWITCHES \$1.00
All types: DPDT, SPST.
- ☐ (G134) 8 ROTARY SWITCHES \$1.00
Some multiple gang.
- ☐ (G128) 13 MINIATURE ELECTROLYTIC CAPACITORS \$1.00
Axial & upright, popular values.
- ☐ (G144) TRANSISTOR REPAIR KIT \$1.19
Various parts used to repair transistorized devices.
- ☐ (G137) 10 INSTRUMENT KNOBS \$1.00
Made by Rathenon, etc. With set screws. "1/4" shaft."
- ☐ (G164) 4 ROLLS OF WIRE \$1.00
Approx. 25 ft. per roll, 20-28ga.
- ☐ (G140) TAPE RECORDER SPARE PARTS KIT \$2.95
Parts for repairing most tape recorders: capacitors, meter, pilot lamp, jacks, and MUCH MORE.
- ☐ (G167) 10 MINIATURE POTENTIOMETERS \$1.00
- ☐ (G182) 2 MISC. METERS \$1.00
Miniature.
- ☐ (G156) 60 DISC CAPACITORS \$1.00
Asst. from .0001 to .1, most 600V, Z5U, NPO, N750, etc.

SURPLUS TUBES

All guaranteed for 1 full year.
ANY 3 FOR \$1.25

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.

- | | | | |
|------|-------|------|--------|
| 3A3 | 6AQ5 | 6DE4 | 6X4 |
| 3AF4 | 6AQ7 | 6DR7 | 10EW7 |
| 3BN6 | 6AT6 | 6DW4 | 12AE7 |
| 3DG4 | 6AU6 | 6EA8 | 12AL5 |
| 3EJ7 | 6AV6 | 6EB8 | 12AL11 |
| 3KT6 | 6AV11 | 6EJ7 | 12AT7 |
| 3Q4 | 6AX4 | 6EM7 | 12AU7 |
| 4BC5 | 6AX5 | 6ER5 | 12AV6 |
| 4BN6 | 6AY3 | 6EY6 | 12BE6 |
| 4BU8 | 6AY11 | 6GF7 | 12BH7 |
| 4BZ7 | 6BA6 | 6GH8 | 12C8 |
| 4CY5 | 6BG6 | 6GN8 | 17J28 |
| 4HA5 | 6BJ8 | 6GU7 | 18FW6 |
| 5V6 | 6BQ6 | 6K6 | 21KQ6 |
| 5Y3 | 6BZ6 | 6K11 | 25L6 |
| 6AC7 | 6CB6 | 6LB6 | 35EH5 |
| 6AF4 | 6CG7 | 6SN7 | 35Z5 |
| 6AG5 | 6CL6 | 6T8 | 36AM3 |
| 6AG7 | 6CM7 | 6V6 | 50A5 |
| 6AL5 | 6DA4 | 6W4 | 50L6 |

(G147) 4 lb. GRAB BAG SPECIAL \$1.00

Full of exotic and exciting electronics parts.

(G155) TUBE BONANZA! \$1.00

20 asst. popular tubes, untested.

(G141) 6 RCA JACK STRIPS \$1.00

From 2-6 per strip.

(G142) 50 PRECISION RESISTORS \$1.00

All 1%, 1/2w and 1w, low and high ohmages.

(G150) 15 HI-FI KNOBS \$1.00

Every one superb! Purchased from Harmon, Kardon, Fisher, etc.

(G102) CALCULATOR KEYBOARD \$2.95

Wild Rover C-1380. Can be used with CT5001. 4 function, clear, clear entry and constant. 7 cm x 9 cm.

(G100) MJ4032/MJ4035 DARLINGTON PAIR. High power 150W, HFE 2500 typ. TO-3 case. With data. \$7.50 pair

(G009) TO-3 MICA WAFERS 10 for 25¢

(G1104) IC REMOVAL AND INSERTION TOOL \$4.95

"Pul-n-sertic" extracts and inserts ICs without damage.

(G271) 1N4148 High Speed switching diode. Full leads. 12 for \$1.00

MONEY BACK GUARANTEE

Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

WRITE FOR FREE VALUE PACKED CATALOG

Listing thousands of components, tubes, transistors, IC's, kits, test equipment.

BONUS FREE CAPACITOR KIT With Every \$5 Purchase

30 AMP STUD RECTIFIERS

- ☐ GLSS54 50V \$1.19
- ☐ GLSS55 100V \$1.39
- ☐ GLSS56 200V \$1.59
- ☐ GLSS57 400V \$1.79
- ☐ GLSS58 750V \$1.99

(G1336) TO-3 TRANSISTOR sockets. 12 for \$1.00

(G298) 1 WATT ZENERS 60¢

available in 5V, 9.1V, 12V, 24V.

(G1092) Z-5 SILICONE HEAT SINK COMPOUND \$2.95

1 oz. tube

(G008) 14 pin DIP sockets 3 for \$1.00

(G260) 2N3638A PNP high speed switch. HFE 100 TO-105 case. 2 for \$1.00

THIS MONTH'S SPECIALS!

TTL

- | | | | |
|------|--------|-------|-----|
| 7400 | 17¢ | 7446 | 80¢ |
| 7401 | 18¢ | 7447 | 80¢ |
| 7402 | 23¢ | 7448 | 80¢ |
| 7403 | 23¢ | 7473 | 49¢ |
| 7404 | 23¢ | 7474 | 49¢ |
| 7405 | 23¢ | 7475 | 85¢ |
| 7406 | 23¢ | 7476 | 53¢ |
| 7410 | 23¢ | 7480 | 79¢ |
| 7411 | 27¢ | 7482 | 79¢ |
| 7413 | 40¢ | 7483 | 69¢ |
| 7420 | 23¢ | 7495 | 79¢ |
| 7430 | 23¢ | 74121 | 57¢ |
| 7440 | 30¢ | 74122 | 57¢ |
| 7442 | \$1.12 | 74123 | 67¢ |

LINEARS

- ☐ LM309K 5v la reg. \$1.15
- ☐ 555 Timer .75¢
- ☐ 566 Function gen. \$1.75
- ☐ 567 Tone decoder \$1.95
- ☐ 709 Op amp .40¢
- ☐ 741 comp. op amp .39¢
- ☐ 2102 1024 bit RAM \$4.95
- ☐ 8038 volt cont osc \$4.25

CLOCK CHIPS WITH DATA

- ☐ MM5314 6 dig clock \$4.95
- ☐ CT7001 alarm & date \$5.95

LED'S

- ☐ (G223) 10 Asst LEDs \$1.00
- ☐ (G242) 5 Jumbo Green LEDs \$1.00
- ☐ (G242) 5 Med Yellow LEDs \$1.00
- ☐ (G001) 5 Jumbo Red LEDs \$1.00
- ☐ (G011) 5 Med Red LEDs \$1.00
- ☐ (G012) 5 Mini Red LEDs \$1.00
- ☐ (G293) DL707 (equiv) 7 seg red LED, .3" char, comm anode \$1.00
- ☐ (G007) DL747 7 seg red LED, .6" char, comm anode \$1.95
- ☐ (G013) MAN 5 (equiv) 7 seg green LED, .27 char, comm anode \$1.49
- ☐ (G014) MAN 8 (equiv) 7 seg yellow LED, .27 char, comm anode \$1.49

IC BREADBOARDS & TERMINALS

Boards have .042 holes. Made of 1/16" polyester glass.

- ☐ (GB663) 3"x4" 94¢
- ☐ (GB664) 3"x6" \$1.29
- ☐ (GB665) 4"x6" \$1.65
- ☐ (FB666) 4"x8" \$2.12

Push-in terminals

- ☐ (GP6601-20) pkg 20/90¢
- ☐ (GB6601-100) pkg 100/\$2.89

Push-in flanged pins

- ☐ (GB6602-20) pkg 20/90¢
- ☐ (GB6602-100) pkg 100/\$2.89

Push-in flea clips

- ☐ (GB6603-20) pkg 20/90¢
- ☐ (FB6603-100) pkg 100/\$2.89

EDLIE ELECTRONICS, INC., 2700-G HEMPSTEAD TPKE., LEVITTOWN, N.Y. 11756

Circle 67 on reader service card

FREE EICO CATALOG

346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO—283 Malta Street,
Brooklyn, N.Y. 11207

Leadership in creative electronics
since 1945.



Circle 64 on reader service card

HI-FI ACCESSORIES

(continued from page 57)

with all the traditional "little" items needed to keep sound reproduction systems in order—record brushes, wipers, tape head cleaning kits, stylus pressure gauges, head demagnetizers, stroboscopes, etc. But there are a few more.

Pickering, for example, has a stylus timer that helps keep a check on how long your stylus has been used. Mountable on virtually any turntable or player, the timer features a "coulometer," a mercury-filled, hermetically sealed, capillary tube whose indicator dot travels at a rate proportional to the flow of electric current that passes through the instrument. It measures elapsed time in 100 hour increments, up to 1,000 hours. It is then reversed to start another "watchdog" cycle. Pickering advises a first inspection of a new stylus after 250 hours of use, subsequent inspections after each 100 hours additional use. The company says that stylus life varies with usage, quality of the diamond and its finish, the cleanliness of record grooves, and even the quality of the records played. A stylus "likely would exhibit considerable wear even under ideal conditions" at about 1,000 hours, says Pickering. A stitch in time . . . can save a lot of records from stylus destruction. The price, \$13.95.

A fairly recent entrant in the maintenance products arena is the "Vac-O-Rec," an electric-powered record vacuum cleaner priced at \$24.95. Slip a record into its slot and the record begins to revolve; as it moves, mohair brushes loosen particles on the record surface, and these are removed through vacuum cleaning. Simultaneously, a static reduction circuit reduces the record's dust-attracting electromagnetism "from as high as 20,000 volts to a low, near-neutral, voltage," the company's literature for the cleaner states.

The audio buff who has moved up the scale to very high powered equipment can—careful as he may be—run into the problem of blowing out speakers because of power overloads. Two companies have auxiliary products to prevent this. One is Robins with its "Stereo Speaker Protector" at \$29.50, and Hartley Products with its "Stereo Speaker Sentry" at \$35. In use, the buff sets controls to maximum power levels (up to 100 watts). Any burst of power beyond the control figure are instantly limited, preventing them from damaging the speakers.

The final add-on is also a protective device. It is the HR "Control 1" that prevents a HI-FI system from being left on accidentally. Plug the amplifier and any other units of the rig into the outlets of the control; if no signal comes out of the amplifier for 10 minutes, the HI-FI system is shut down. Price, \$39.95 from HR Mfg. Co., Sarasota, Fla.

R-E



FREE catalog

over 2000

unique tools,
handy kits,
precision
instruments,
technical
supplies.

Our 23rd year of service to the World's
finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

National Camera 2000 West Union Ave., Dept. G&A
Englewood, Colorado, 80110
Phone (303) 789-1893

Circle 65 on reader service card

FREE burglar — fire alarm catalog



over 500
systems,
detectors,
controls,
sounders,
tools, locks,
supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 96 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today.



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

Circle 66 on reader service card

are actuated) to the meter. When the DB/VOLTS switch is depressed, it connects the variable output from the buffer amplifier directly to the attenuator at the input of the distortion amplifier and hence to the meter.

That extra option

Externally, the only difference between the basic 1700A and the version of the instrument that includes the self-adjusting 100% reference feature can be found by examining the ADJUST knob on the front panel (See Fig. 3). When the option is included, this switch includes an AUTO position. When the knob is rotated fully counterclockwise, past the CAL position, the automatic level setting circuitry is activated (See Fig. 4).

The input signal to the notch filter (or the variable output of the buffer amplifier) is connected to an AC to DC converter. The DC signal from this converter is directly proportional to the notch filter input signal level and drives a voltage-to-current converter that regulates the controlling current of a multiplier IC stage. This multiplier IC is used as a variable-gain amplifier (with a gain variation of from 1 to 3.16). The gain is inversely proportional to the controlling current and the magnitude of the AC signal to the notch filter. A simplified block diagram of this optional circuitry (which can be retro-fitted to older models of the 1700A) is shown in Fig. 5.

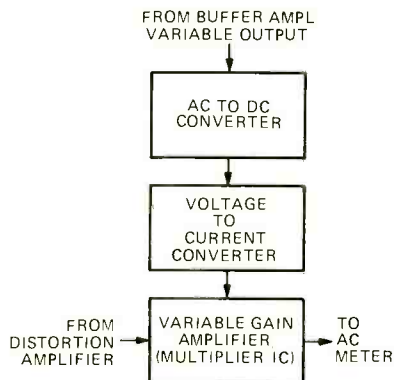


FIG. 5—CONTROL SIGNALS applied to variable gain amplifier for direct reading of THD without 100% reference settings.

Whenever distortion measurements are made, it is useful to be able to examine the distortion products themselves on an oscilloscope display. Often, noise voltages or unexpected beats (as between recovered FM multiplex audio signals and sub-carrier products, or between the bias oscillator of a tape deck and incoming signal frequencies) may be mistaken for harmonic distortion unless a visual display accompanies the readings. It is also helpful to be able to define the nature of the distortion and what harmonics predominate (e.g., 2nd harmonic, 3rd harmonic etc.). A front panel jack delivers the distortion voltages for viewing on any oscilloscope, and Fig. 6 illustrates the distortion viewed while testing a Pioneer CT-9191 (lower trace) while viewing the

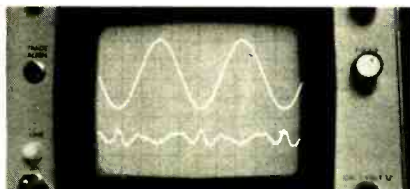


FIG. 6—TAPE DECK OUTPUT SIGNAL (upper trace) and distortion products (lower trace) as observed from the DISTORTION OUTPUT jack on the 1700A distortion measurement system.

total audio signal (upper trace) for frequency reference.

The audio oscillator

The built-in audio oscillator of the Sound Technology 1700A is basically a Wein bridge type with an ultra-low distortion amplitude control circuit. This circuit provides wide frequency range, fast settling-time, flat frequency-response and very low residual-distortion. The oscillator has two operating modes; FAST RESPONSE and LOW DISTORTION. When fast response is selected the oscillator settles fairly rapidly after a frequency change is punched in on the front panel frequency selector buttons. When the low distortion mode is selected, the oscillator settling time to 0.002% distortion is less than 5 seconds. Built-in circuitry automatically controls the oscillator through these modes whenever there is an amplitude disturbance, such as a change of frequency settings. The combination of multiplier buttons and numbered buttons on the front panel permit selection of frequencies from 10 Hz to 110 kHz in four overlapping ranges with three-digit resolution (a frequency of 442 Hz could, for example, be chosen with accuracy to 1 Hz, while a frequency of 20,200 Hz could be chosen to accuracy of 100 Hz). A closeup of the frequency selector section of the front panel of the 1700A is shown in Fig. 7.

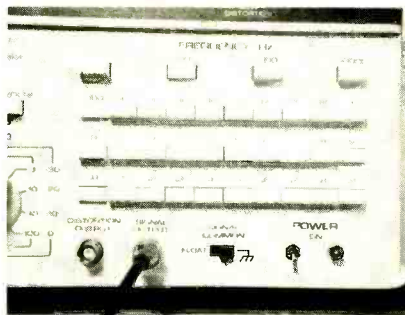


FIG. 7—FREQUENCY SELECTOR section on front panel of 1700A.

Manufacturers of high-powered, high quality audio amplifiers who have previously boasted of unmeasurable distortion figures had better re-phrase their future advertisements. With sophisticated measuring equipment such as the Sound Technology 1700A around, just about the lowest distortion these fine products deliver can now be measured—accurately.

This makes three months of R-E Lab Tested reports on hi-fi equipment. We'd like to know how you like them. Drop us a postcard and let us know. Write Hi-Fi Test Reports, Radio-Electronics, 200 Park Avenue South, New York, NY 10003.

R-E

\$5 REBATE
CERTIFICATES
(see below)

Polaris
40 KV
DUAL RANGE
Probe

MEASURES
VOLTAGE
AND
CURRENT

FOR
TODAY
AND
TOMORROW

MODEL
#651

Only
\$29⁹⁵

SPECIFICATIONS

Range One:
40,000 Volts D.C.
Range Two: 0-400 MA. D.C.
Accuracy: $\pm 2\%$ Full Scale
Meter Movement: 50 μ A

Polaris
DC POWER SUPPLY
0-25 VOLTS 250 MA

TEST & SERVICE
SOLID STATE EQUIPMENT

MODEL
TPS 225

Only

\$29⁹⁵



- Operates on 105/125 V.A.C.
- Adjustable Voltage Output
- Meter Measures Voltage & Current
- Extremely Low Ripple


Polaris
COBRA CURVE TRACER

RAPID TRANSISTOR
& DIODE TESTER

MODEL CT 751

Only

\$22⁹⁵

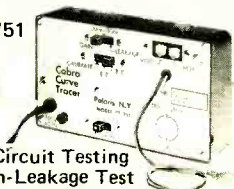

- In & Out of Circuit Testing
- Gain-Junction-Leakage Test
- In Circuit Test Leads
- Checks Diodes for Function & Polarity

Polaris New York

2862 Fulton St., Bklyn, N.Y. 11207

Please send me rebate certificates and information on _____ Expires in 60 Days.

Probe ☐ Power Supply ☐ Curve Tracer ☐

Name _____

Street _____

City _____ State _____ Zip _____

My supplier is _____

SOLD THROUGH DISTRIBUTORS ONLY

Circle 63 on reader service card

SYNTHESIZER KITS

KEYBOARD MODELS
PRICED FROM
\$230

but
did you know
we also have

THE SURF
A BIRD
THE WIND
PING-PONG
WIND CHIMES
DRUMMER BOY
SYNTHESPIN MK-II
THE PYGMY AMP
A CHATTER JAMMER
INFINITY PLUS SUSTAIN
BALANCED MODULATOR
THE SEQUENCER & MIXER
GNOME MICRO-SYNTHESIZER
AND MANY MORE IN OUR
FREE CATALOG

PAIA ELECTRONICS
BOX R14369, OKLAHOMA CITY, OK 73114
Circle 30 on reader service card

Some stores
sell test
equipment
at discount
prices.

At Fordham
we discount
their discount
prices.

B&K, EICO, RCA, SENCORE
FLUKE, HICKOK and LEADER


Complete line of tubes,
tools and electronic supplies

FREE CATALOG
FORDHAM

RADIO SUPPLY CO., INC.

558 Morris Ave., Bronx, N.Y. 10451
Tel: (212) 585-0330

Circle 61 on reader service card

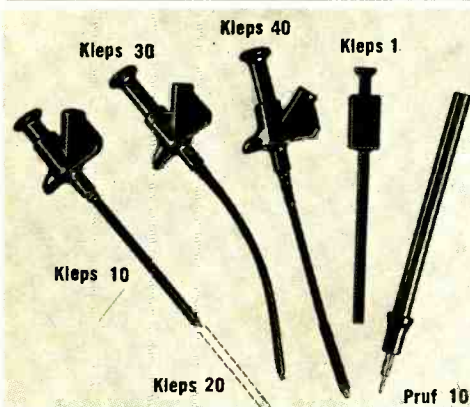

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. \$1.39

Kleps 20. Same, but 7" long. \$1.49

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$2.59

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$.99

Prof 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$.89

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.

130 Spencer Place, Mamaroneck, N.Y. 10543

In Canada: Rye Industries (Canada) Ltd.

Circle 62 on reader service card



For
faster
service

USE
ZIP
CODE

on
all
mail

QS MATRIX

(continued on page 74)

with clearly defined directionalities.

Furthermore, the QS variomatrix circuit may be combined with a simple peripheral circuit to create a QS synthesizer circuit (Fig. 11) for converting conventional 2-channel stereo records into 4-channel media. Or, with another simple peripheral circuit, the QS variomatrix circuit can be easily adopted into a phase matrix circuit for the decoding and repro-

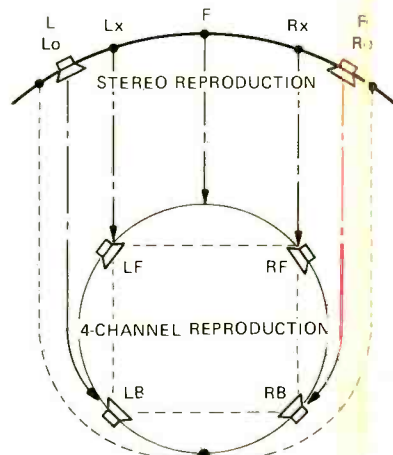


FIG. 11—4-CHANNEL REPRODUCTION of 2-channel signals by QS synthesizer.

duction of CBS SQ 4-channel records. In each application, the QS variomatrix circuit works to enhance the inter-channel separation, without affecting the tonal quality in any way. Each application is already widely available to the consumer in QS variomatrix equipped high fidelity components.

For manufacturers of home audio equipment around the world, the QS variomatrix circuit is available today as an IC. This makes it practical and economical to offer the many QS advantages in their own 4-channel components. R-E

Notes

QS is a trademark of Sansui Electric Co., Ltd. The phenomenon in which, when a loud sound and a weak sound differing in level by more than a certain margin reach the human ear simultaneously from different directions, the directionality of the weak sound is masked by that of the loud sound to the extent that the ear does not perceive the directionality of the weak sound.

SQ is a trademark of CBS Laboratories.

The QS System is protected by U.S. Patent No. 3,777,076, U.S. Patent No. 3,872,249 and other patents.

Thanks to you
It's working



The United Way

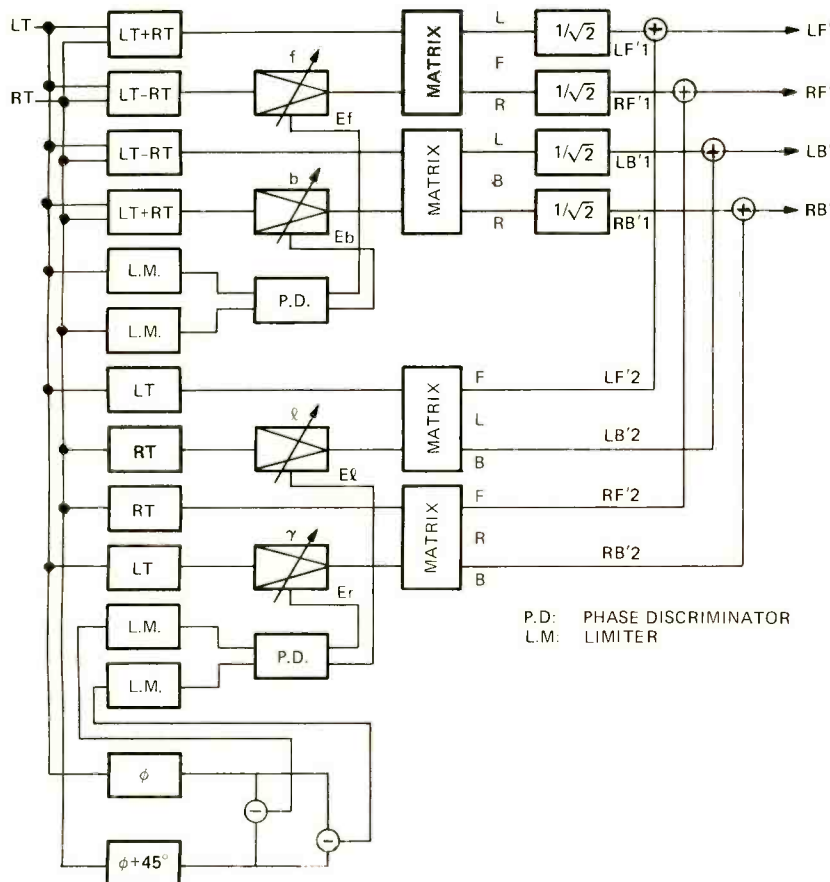


FIG. 9—QS VARIOMATRIX decoder that increases the interchannel separation.

LED WRISTWATCH

MODULE BASIC PARTS KIT

FEATURING AN LSI CMOS INTEGRATED CIRCUIT WITH HOURS, MINUTES, SEC, AND DATE. YOUR CHOICE OF 12 OR 24 HOUR IC. PLEASE SPECIFY

\$29.95
+ 1.00 P&H

FOR JUST 29.95 YOU WILL RECEIVE THE BASIC ESSENTIALS. YOU NEED ONLY SUPPLY A FEW CAPACITORS AND RESISTORS AND THE READILY AVAILABLE MAN 3 DISPLAYS. THE MODULE HOUSING IS UP TO YOU.

THE BASIC PARTS KIT CONTAINS PC FOIL LAYOUT, IC, INSTRUCTIONS, TRIMMER, CRISTAL AND 4 DRIVERS




ALPHA ELECTRONICS

DEPT 2 PO BOX 1005
MERRITT ISLAND, FLA. 32952

TO ORDER OR FOR INFORMATION
CALL TOLL FREE
800-327-2084

Circle 28 on reader service card

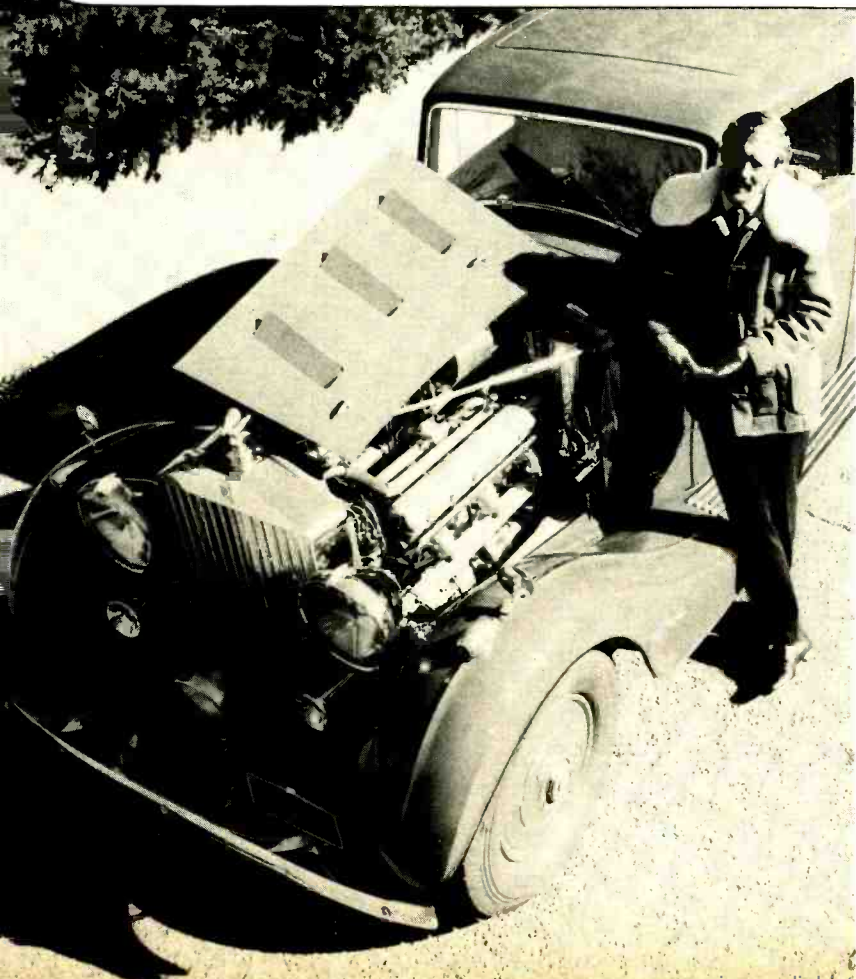You don't have to buy a new car to get an electronic ignition.



Let's face it. After 37 years, even a Phantom III can use a lift. That's why I put a Delta Mark Ten B Capacitive Discharge Ignition on my Phantom . . . to give her a spark I'd pit against any '75 model car. I went to Delta because they aren't Johnny-come-latelys. Delta's been making electronic ignition systems for over a decade.

Whatever kind of car you drive, you can give it the same great Delta performance I gave mine.

- Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
- The Mark Ten B really does save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
- Because the Mark Ten B keeps your car in better tune, you actually can save on expensive gasoline.
- With a Mark Ten B, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name _____
Address _____
City _____ State _____ Zip _____



DELTA PRODUCTS, INC.

P.O. Box 1147, Dept. RE, Grand Junction, Colo. 81501
303-242-9000

Mark Ten B, assembled	\$64.95 ppd	Standard Mark Ten, assembled	\$49.95 ppd
Mark Ten B, kit	\$49.95 ppd	Deitakit®	\$34.95 ppd

Circle 29 on reader service card

MATHEMATICS ELECTRONICS

We are proud to announce two great new courses for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

**The INDIANA
HOME STUDY INSTITUTE**
DEPT. RE-1075, P.O. BOX 1189
PANAMA CITY, FLA 32401

Circle 25 on reader service card

A Major Advance...



- *INSURES PROPER COMBUSTION
- *EASIER STARTING
- *LONGER POINTS and PLUG LIFE
- *INCREASE MILEAGE up to 40%
- *EASY INSTALLATION (12v neg. gnd.)

Labtronics' Multiple Restrike (M-R) Ignition produces a high energy repetitive spark on each power stroke to effectively ignite the air/fuel mixture. M-R statistically insures more complete combustion - resulting in greater energy and increased efficiency. Send for Labtronics' free literature on the M-R system. Better yet, experience M-R and enjoy the pleasure and the economy of a well-performing engine.

■ Model VI \$79.95 • 1 Year Warranty •
■ Model VI-B \$59.95
■ Brochure • 30 Day Money
P.P.D. in U.S.A. • Back Guarantee •
Send Check or Money Order to:
Labtronics, Incorporated
3635 Hillside, Ypsilanti, Michigan 48197

DEDICATED TO EFFICIENCY

Circle 26 on reader service card

New Value For The Cost- Conscious Buyer \$1050 includes:

- 10 MHz at 10 mV/div • Dual Trace
- Compact Size (4" X 9" X 11") • Probes and Batteries



If your requirement dictates a portable oscilloscope with dual trace and 10 MHz at 10 mV/div sensitivity, but your budget demands frugality, then you should consider the new TELEQUIPMENT D32. It offers 10 mV/div to 5 V/div in 9 calibrated steps, automatic selection of chopped or alternate mode, depending on sweep speed setting, plus automatic selection of tv line or frame display. It also offers a choice of battery or ac line operation... with up to 4 hours continuous operation from 6 rechargeable, 'D' cell batteries. The batteries, two probes, and a molded front-panel protective cover are all included as standard equipment.

We feel the D32, at only 10 lbs., is

well suited as a servicing tool. Especially for industrial manufacturing, computer peripherals, and voice communication equipment. And it should be considered for servicing the rapidly increasing number of consumer electronic products.

If you agree and would like a demonstration at your convenience and in your environment, or simply additional information, contact your local Tektronix Field Office or write: Tektronix, Inc., P.O. Box 500, Beaverton, Oregon, 97077.

U.S. Sales Price FOB Beaverton, Oregon



TEKTRONIX®
committed to
technical excellence

Circle 15 on reader service card

Circle 23 on reader service card for demonstration

QS MATRIX

(continued from page 72)

on to the control block. The latter receives input signals pre-arranged in the form of an $LT + RT$ sum signal and an $LT - RT$ difference signal; and it instantaneously adjusts the level of either the sum or difference signal according to the information received from the phase discriminator block, determining from moment to moment the four matrix parameters or coefficients (f, b, l, r) that will enable the matrix block to create maximum inter-channel separation when it compounds the sum signal and the difference signal to retrieve the original sound source signal.

In other words, if an LF signal in the original sound field is encoded by the QS system and then decoded by simple calculations, it will yield a sound pressure response pattern as shown by the solid line in Fig. 3. This indicates crosstalk of -3db in each of the two adjacent channels. The QS variomatrix circuit, however, varies the LB' matrix coefficient in the RB' direction to reduce the crosstalk of the LF signal in the LB' channel and eventually bring it down to $-\infty$ (0) at a point where the LB' matrix coefficient coincides with the RB' matrix coefficient. Simultaneously, the QS variomatrix circuit also controls the RF' matrix coefficient in the RB' direction, and eventually accomplishes a circular sound pressure response pattern (shown by the dotted line in Fig. 10) that is devoid of any crosstalk, just as in the reproduction of a discrete 4-channel tape recording.

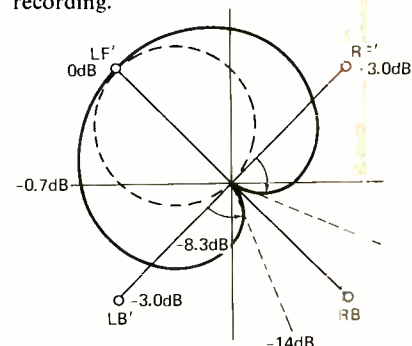



FIG. 10—CHANGE in sound pressure response created by variomatrix circuit

Should there be a concurrent signal of a lower level, it will be reproduced with maximum inter-channel separation if it is located in the same direction as the predominant signal LF; if it is located in a different direction, it will be reproduced in such a way that its directionality is more and more obscure as it moves farther away in direction from the LF signal in the original sound field. Even then, however, the level of the signal will be entirely preserved so that, due to the directional masking effect of the human ear**, the listener will perceive the predominant signal and the concurrent lower-level signal in much the same way as he would have heard them had he been present in the original sound field. Thus, what the QS variomatrix circuit does is to reproduce sound signals generated in the original sound field with accuracy and

(text continues on page 76)

five new breadboard testers from CSC

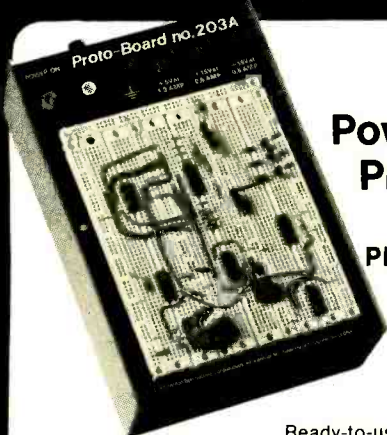Continental Specialties Corp. offers a total line of breadboard test devices ... everything from inexpensive kits to high-power professional units and logic monitors too. Each high quality, compact unit comes with a guarantee of complete satisfaction or your money back within 10 days. Here are but five of the "hottest" items we make...



Power for the Professional!

**New Proto Boards
PB-203 and PB-203A
with built-in
regulated
short-proof
power supplies!**

Ready-to-use. Just plug in and start building! 2 extra floating 5-way binding posts for external signals (PB-203 only). Completely self-contained with power switch, indicator lamp and power fuse. 24 14-pin DIP capacity. All metal construction ... no chipping or cracking as with plastic cases. Two-tone quality case makes both PB-203 and PB-203A aesthetically, as well as technically attractive.

PB-203

- 3 QT-59S Sockets
- 4 QT-59B Bus Strips
- 1 QT-47B Bus Strip
- Fuse • Power Switch
- Power-On Light
- 9.75"L x 6.6"W x 3.25"H
- Weight: 5 lbs.
- 5V, 1 AMP regulated power supply

75.

Add \$2.50 shipping/handling

OUTPUT SPECIFICATIONS

Output Voltage 5V \pm ¼V
Ripple & Noise @ ½ AMP
10 millivolts
Load Regulation Better than 1%

PB-203A

- 3 QT-59S Sockets
- 4 QT-59B Bus Strips
- 1 QT-47B Bus Strip
- Fuse • Power Switch
- Power-On Light
- 9.75"L x 6.6"W x 3.25"H
- Weight: 5 lbs.
- 5V, 1 AMP regulated power supply (same as PB-203)
- +15V, ½ AMP regulated power supply
- -15V, ½ AMP regulated power supply


120.

Add \$2.50 shipping/handling

OUTPUT SPECIFICATIONS

Output Voltage 15V, internally adjustable
Ripple & Noise @ ¼ AMP,
10 millivolts
Load Regulation Better than 1%

PROTO BOARD 100

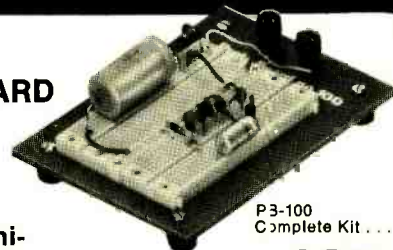

A complete mini-breadboard budget kit with full IC capacity

PB-100 Complete Kit ...

19⁹⁵

Add \$1.50 shipping/handling

The PB-100 is a low cost, big 10 IC capacity breadboard kit, complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws and easy assembly instructions. 4.50" (114.3mm) wide x 6.00" (152.4mm) long x 1.35" (34.3mm) high. Order your PB-100 kit! Start building and testing now!


CSC PROTO-CLIP offers power-on ... hands-off signal tracing ... under \$5!

Trace signals or troubleshoot fast. Inject signals or wire unused circuits into existing boards. Flexible plastic web* construction eliminates springs and pivots. Plus, the narrow throat is perfect for high density pc boards.

Order now!
PC-14 14-pin Proto-Clip: \$4.50 ea.
PC-16 16-pin Proto-Clip: \$4.75 ea.

Add \$1.00 shipping and handling

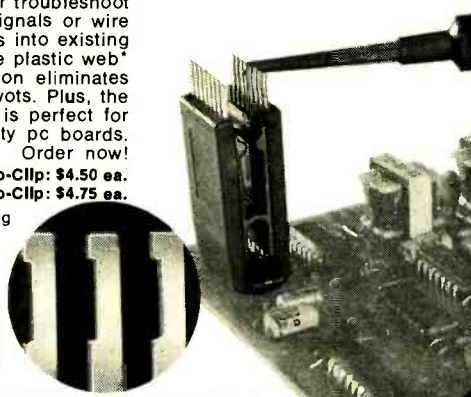Scope probes, test leads lock onto unique toothed grips



©COPYRIGHT CONTINENTAL SPECIALTIES CORPORATION 1975

**Continental Specialties Corp.
LOGIC MONITOR
brings ICs to life
faster than a scope ...
safer than a
voltmeter**


LM-1 **84⁹⁵ each**

Add \$2.50 shipping/handling

Self-contained, pocket size. No adjustments or calibrations needed. Puts life into digital designs. Just clip to any DIP IC up to 16 pins. NO POWER SUPPLY NEEDED!

Simultaneously displays static and dynamic logic states of TTL, TTL,

HTL or CMOS on 16 large high intensity LEDs. Watch signals work through counters, shift registers, timers, adders, flip flops, decoders, entire systems. Concentrate on signal flow and input/output truth tables. Forget probe grounds, pin counting or sync polarity. Precision plastic guides and flexible plastic web* insure positive connections. Versatile. Fast. Accurate. Indispensable. Order yours today!

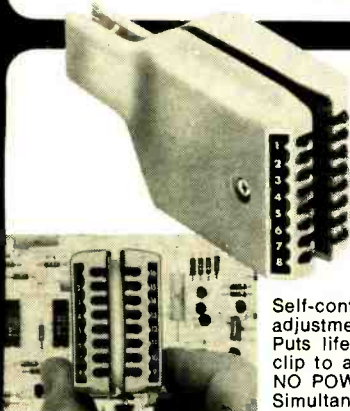

All Continental Specialties breadboard test devices are made in the USA, and are available off-the-shelf from your local distributor or CSC. Direct purchases may be charged on BankAmericard, Master Charge or American Express. You get a FREE English/Metric conversion slide rule with each order. Foreign orders please add 10% for shipping/handling. Prices are subject to change. Write or phone for complete illustrated catalog, plus the name and address of the CSC dealer nearest you.

*Patents Pending



CONTINENTAL SPECIALTIES CORP.
44 Kendall St., Box 1942, New Haven, CT 06509 • 203/624-3103

West Coast Office: Box 7809, San Francisco, CA 94119 • 415/421-8872
CANADA: Available thru Len Finkler Ltd., Ontario

"ORDER NOW ... EVERYTHING IS OFF-THE-SHELF ... SHIPPED IN 24 HOURS."

Circle 24 on reader service card

QS MATRIX

(continued from page 30)

essential characteristics of a sound source signal, especially its density, need to be all encoded in the first and second transmission channels, so long as the compatibility of the encoded signals with 2-channel stereo and monophonic playback remains a prime requisite. Then the third, fourth and any other higher-order channels will be available for use mainly to define the directionality of the reproduced signal with greater sharpness.

On the other hand, once two transmission channels are secured, the directionality, or the information pertaining to the location of a sound source in the original

live sound field, can be transmitted in the form of amplitude and phase relationships as explained earlier. And once that is done, certain advanced calculations can be performed on the playback end to unscramble the transmitted signal and reproduce it with nearly the same sharply defined directionality as if four entirely separate transmission channels were utilized.

Directionality enhancement

There are two methods to sharpen the directionality of a signal reproduced by a matrix 4-channel system. One is a so-called gain control method which uses an AGC (automatic gain control) circuit to reduce the gain in those channels where the unwanted crosstalk appears. The other

MEGASPARK™ BREAKERLESS ELECTRONIC IGNITION

Install It Yourself



Only
\$48.50
Std. Mdl. 400

optically-controlled MEGASPARK—the next generation in dependable electronic ignition—gives you:

- Peak Engine Performance
- Reduced Maintenance
- Perfect Engine Timing and Dwell
- Unmatched Fuel Economy
- Lowest Operating Expense
- Lifetime Guarantee

Points and condensor are replaced by a supremely accurate opto-electronic sensor, so you eliminate tune-ups forever; timing and dwell never need resetting.

Made in U.S.A.

FAST SWITCHING FOR PEAK POWER. MEGASPARK incorporates the dependable new High Power Darlington Amplifier for fast switching and cool, long-life operation. With fast 1/4 micro-second switching—a MEGASPARK standard—a "fatter," longer duration, "complete combustion" spark is achieved; ideal for lean mixture engines.

OPTICS ELIMINATE MECHANICAL PROBLEMS. Don't chance cheap, low-power, slow switching ignition systems that run hot and lose their efficiency. Only MEGASPARK infra-red light beam is absolutely accurate at all RPM's. Magnetic pickup sensors are unsatisfactory because they cause fluctuations in timing.

POWER TO SPARE IN SUB-ZERO WEATHER. MEGASPARK means quick starts on cold, damp mornings even at 4 volts in minus temperatures. Heat, vibration or hard knocks won't hurt MEGASPARK. Solid-state controlled optics assure absolute cylinder-to-cylinder firing accuracy. Extended dwell means increased coil saturation and higher spark intensity at all RPM's, under any load or road condition.

CUT MAINTENANCE AND FUEL COSTS. MEGASPARK pays for itself quickly; saves you money. MEGASPARK means economy because your tune-up is locked-in! You'll get better gas mileage; spark plugs last longer; pickup and power is enhanced; service and tune-up costs go way down.

LIFETIME WARRANTY


Because we know how reliable these units are, ISI offers **FREE** factory repair or replacement on all MEGASPARKS should they ever fail to deliver satisfactory performance. No time limit!

ATTENTION CD IGNITION OWNERS

Convert your CD to opto-electronic operation with MEGASPARK 300 for only \$34.50. Works perfectly with ALL CD units.

Use your standard coil or check the box below for our special discount offer on famous Mallory Voltmaster Mark II Coils.

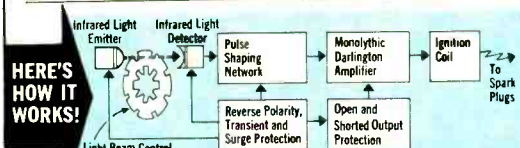Installation? No Problem! Detailed Instructions Furnished! Fits All Cars—4, 6, 8 Cylinder—Domestic and Foreign—Rotarys, too.



MODEL 500 High performance model for superior sparking and engine efficiency. Delivers 20% more power than Model 400.

MODEL 400 Standard model exceeds requirements of all cars.

MODEL 300 Trigger Unit modernizes previously installed CD ignitions.

IGNITION SYSTEMS INC., 2547 - 8th St., Space S, Berkeley, CA 94710, (415) 845-3584

Enclosed is my check ☐; money order ☐; in the amount indicated. Please RUSH — Satisfaction Guaranteed.

- ☐ MEGASPARK 500 @ \$64.50
 - ☐ MEGASPARK 400 @ \$48.50
 - ☐ MEGASPARK 300 @ \$34.50
 - ☐ VOLTMASTER Mark II Coil @ \$19.95
- Add for Postage and Insurance. **\$1.00**
California residents add sales tax
TOTAL:

☐ SEND FREE ILLUSTRATED BROCHURE

Charge my

- ☐ MASTER CHARGE
- ☐ BANKAMERICARD (Please provide full credit card info)

IMPORTANT: Indicate make and model of car, engine displacement and number of cylinders.

NAME


ADDRESS

CITY


STATE

ZIP


Circle 101 on reader service card

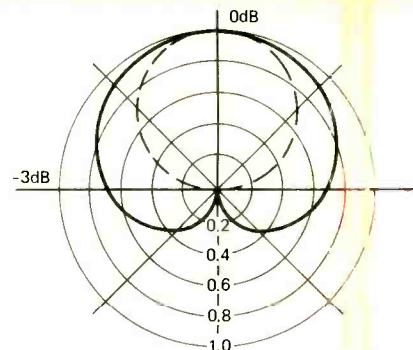

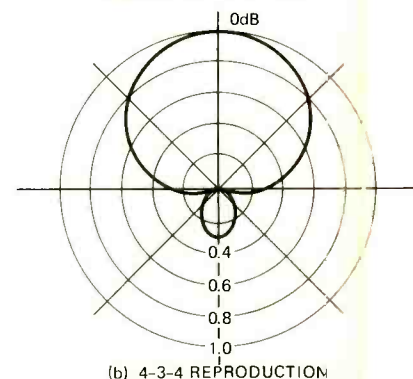(*DOTTED LINE INDICATES QS VARIO-MATRIX)
(a) 4-2-4 REPRODUCTION



(b) 4-3-4 REPRODUCTION

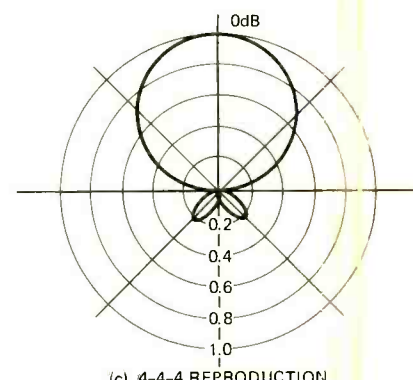

(c) 4-4-4 REPRODUCTION

FIG. 8—SOUND PRESSURE RESPONSE of a QS-encoded signal transmitted via (a) two, (b) three, and (c) four transmission channels.

method does not tamper with the gain in the four channels but instead adjusts the parameters of the decoding matrix automatically and continuously so as to eliminate only the unwanted crosstalk. The QS variomatrix circuit is representative of the second method.

When a QS-encoded signal is decoded through a basic QS decoder it yields a sound field that fairly accurately reflects the original sound field. But insufficient separation among the reproduced channels prevents the directionality of the signal from being clearly defined.

The QS variomatrix technique rectifies this condition. It increases the interchannel separation to place the reproduced signal more sharply in focus. In an actual QS decoder, the technique is implemented in the form of a QS variomatrix circuit consisting of three functional blocks (Fig. 9): a phase discriminator block, a control block, and a decoding matrix.

The phase discriminator block phase-discriminates the phase difference and level difference between the LT and RT encoded signals to detect the location of the input signal. It then converts this information into DC levels and passes it


(continued on page 74)

RCA SK Series

Fix it with SK. The RCA quality replacement.

Count on top quality in SK replacement semi-conductors. Because they carry the name RCA, a top manufacturer of OEM devices. Same strict AQL standards, same strict Director of Quality Assurance. That's how we protect you from callbacks, so you can make more profitable use of your time. RCA's higher-than-ever 410 to 1 replacement ratio will help you save time too. Your key to fast, easy replacement is RCA's new 1975 SK Replacement Guide. Get your copy at the RCA distributor where you buy SK parts.

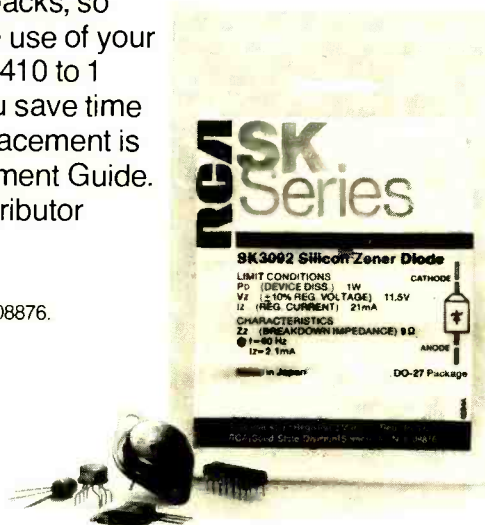RCA Solid State, Box 3200, Somerville, N.J. 08876.



It's OK if it's **sk**

Circle 22 on reader service card

★ **FREE!** ★



NEW CATALOG OF HARD-TO-FIND PRECISION TOOLS

Jensen's new 112-page catalog is jam-packed with more than 2500 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, instrument mechanics, schools, laboratories and government agencies. This wanted catalog also contains Jensen's world-famous line of more than 40 tool kits. Plus 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!



JENSEN TOOLS and ALLOYS
4117 N. 44th Street, Phoenix, Arizona 85018

A BLISS & LAUGHLIN INDUSTRY

Circle 19 on reader service card



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled \$53.95

TIGER SST assembled \$42.95

Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation

P.O. Box 1727 B
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

Circle 20 on reader service card

a closed switch. Carefully regulated DC supplies are used.

You'll find DC control techniques used in many other circuits. For a practical example, in the RCA CIC-49 chassis, the sound volume is DC controlled by a circuit very much like the one discussed before. This comes from the PM-200 module, and consists of a 3K resistor, a 40K control, bypassed by a .047-μF capacitor.

The color is controlled by another DC control circuit. This circuit regulates the gain of the second bandpass stage, in the IC on Module MAC. The tint is also controlled in this way, in the MAE module. In the MAL module, the brightness is adjusted by the same type of circuitry. Even the horizontal hold control, instead of the familiar coil or variable resistor, is a DC-control type.

These are the manual adjustments. Practically all of the automatic control circuits use the same principle. AFPC, ACC, color killer, brightness limiter, AGC, AFT, and even the DC clamping level of the video output. Of course, the horizontal AFC circuit still uses the same old principle that we've seen for so long. This is actually a phase-locked loop, and the horizontal oscillator is a VCO (Voltage Controlled Oscillator). For that matter, so is the 3.58-MHz color oscillator in practically all sets.

Servicing

You'll find two basic types of circuit used for these control applications. In one, the DC voltage will be picked up from the DC power supply and fed through a voltage divider. One section of the voltage divider is a variable resistor for the manual controls, and the other section is an adjustable resistor for the setting of automatic circuits. The voltage from the control goes to one terminal of the IC.

In the other type of control circuit, the DC control voltage actually comes through the IC internal circuitry. Sometimes from a voltage regulator or current-mirror, sometimes from internal voltage-dividers. These can be made up of resistors, or with diodes or transistors.

To check either type, read the DC supply voltage first. With the external-divider type, be sure that all of the resistors are within tolerance. Leaky bypasses or drifting resistors can cause problems. With the types where the DC voltage is developed inside the IC, check the DC supply voltage to the IC and then check all DC voltages that are supplied by the IC. Also, check for the presence of the normal signal input; video, sync, keying pulses, etc. In many circuits, such as the IF-AGC-video amp IC's, all of the "action" takes place inside the IC itself. **R-E**

(Reader Questions are on page 96.)

**Meet
the
family...**



Our companies have been in the microphone and tape recorder business now for over forty years. In that time we have built up quite a family... professional mixers, tape recorders, microphones, headphones—the lot.

All of these products are made to the same high acoustic and mechanical quality that has set standards throughout the world. For example, if your finances do not quite run to a new Revox tape recorder, try to find a secondhand one—in stock condition it will outperform other makes of new equipment at the same price!

All of our family is described in great detail in a series of technical data sheets and application charts. If you are at all interested in better equipment, we will send you this information. Just mail the attached coupon to:

Revox Corporation,
155 Michael Dr.
Syosset, New York 11791.

The illustration contains optional extras.
Please tell me where I can see and buy
Name _____
Address _____
*As and when available from our dealers.

- Revox ☐ A700
- Revox ☐ A77
- Revox ☐ Good used machines
- Beyer ☐ Microphones
- Beyer ☐ Headphones
- Lamb ☐ Mixer

R-E's Service Clinic

DC volume controls

Old idea, new technique.

by JACK DARR
SERVICE EDITOR

THE TERM "DC VOLUME CONTROL" sounds strange. Actually, this isn't new. Back in 1928, a variable DC voltage was used to control the volume. Specifically, the filament voltages of the O1A tubes was varied! (This was "filament" then, not "heater".) A similar approach could be used with modern tubes, but it isn't for several reasons. You get into problems.

The standard volume control circuit for many years has been a simple signal-voltage divider (see Fig. 1). To get

this purpose, filtered if necessary.

This technique is especially simple in receivers using IC's. IC terminals are provided that can be used to control the gain of an amplifier stage, by varying a little DC voltage. The signal literally "never leaves the premises" of the IC. (One of my pet terms in IC terminology refers to anything outside the IC as being in the "outside world"!)

Anyhow, all you need is a couple of extra transistors, and this is very simple. A couple of dabs of silicon and there you are.

Figure 2 shows a typical circuit in a sound-detector output-IC. Only the control circuitry is shown. Transistors Q1 and Q2 are the actual volume control stage. The dual pair (Q3 through Q6) are a "current-mirror" stage. Current-mirror stages are common in most op-amps and similar IC applications. The output of the dual current-mirror stage feeds the volume-control stage. The DC voltage on the VOLUME control adjusts the bias on the volume-control stage (Q1 and Q6).

The setting of the VOLUME-control adjusts the base voltage of one side of the current-mirror pair (Q6) that in turn controls the signal fed to the common base of transistors Q1 and Q2. This is called a double-differential amplifier system. The output of transistor Q2 is directly coupled to the audio amplifier, which is more or less a stock op-amp type of circuit. If all of this looks very complicated; it is, but this is all inside the IC. If a circuit such as this doesn't work, and the DC supply and signal input voltages are normal, just replace the IC!

DC voltages can be used to control a great many things. For an already-familiar example, the frequency of a TV tuner can be controlled by applying a carefully-regulated DC voltage to a varactor diode. Quite a few set-makers are already using tuners which contain nothing but a row of varactor diodes. A set of preset pots are adjusted to apply the DC voltage to the tuning diodes, and that's all there is to it. Actually, this is pretty complex, but the operation is simple!

In the same tuners, you'll find another form of DC control. Switching-diodes are used for changing between low- and high-VHF channels, UHF, etc. Reverse-biased, the diodes are open switches; forward-biased they become

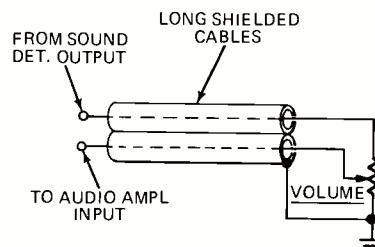


FIG. 1—OLD VOLUME CONTROL circuit with long signal-carrying cables. Cables must be shielded.

the signal from the sound-detector output to the front-panel control, then back to the audio output grid, you had to run two well-shielded cables. This was necessary to get the audio signal to the control and back through all of the assorted interference floating around inside a TV set. Using a DC control voltage can be done much more easily. Single wires can be used for

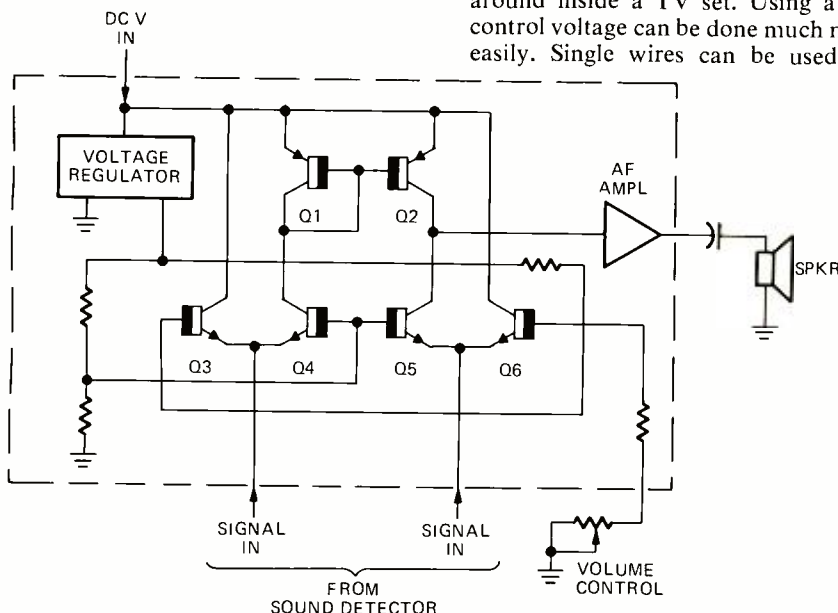


FIG. 2—DC-CONTROLLED VOLUME circuit. All components except volume control are inside the IC.

picture tube cathodes, where the signal must be positive-going sync, and count the number of stages. (If need be, he can reverse the polarity of the video detector diode!)

In certain sets you'll see what looks like an odd number of stages for the correct polarity. Look closely, one of these may be a cathode-follower. In tube or transistor circuits, this does not invert the signal. In the complete circuit seen in Fig. 2, note that the "2d video" stage is a cathode follower for the *video* alone. Color signals are taken off at its plate; this is a combination stage! An emitter-follower transistor stage does the same thing.

In some sets, you'll find a transistor video amplifier. These can cause some unusual problems if a transistor base-collector short develops. The signal will still pass through the stage, but it will lose the voltage gain of this stage. It will also lose one polarity inversion! So, you'll come out with a negative picture, but in the black-and-white signal *only*. This results in a very weird-looking color picture! To make sure, simply turn the color completely off. The black-and-white picture will then be quite obviously negative. This can also happen if someone pulls out plug-in transistor video amplifier and replaces it backward!

General rules

The first thing you must do when checking for video problems is get the *raster* on the pix tube. Check DC voltages on cathodes, grids, screens and the high voltage. DC voltage problems caused by the video stages, can upset the bias on the picture tube. This can cause two different problems; excessive negative bias can cut the raster off, or excessive positive bias can cause the picture tube to draw a very heavy beam current, overloading the high-voltage supply and once again the raster goes out. Quick-check: disconnect the high-voltage lead. If the high-voltage comes back, you have a bias problem in the video stages.

Clear this up first. Then if you still have a blank raster, look for signal problems with a test signal and the scope. Quick-check: a blank raster could be video troubles or a loss of signal from the IF's etc. To find out, feed an *audio* signal (any frequency) directly into the input of the video stages. Set this at the normal input level of about 2 volts P-P. If the video stages are OK, you'll see dark horizontal bars on the screen. If the video amps have normal gain, the dark parts of the bars will be black.

A square wave is a good test signal, or you can use the video signal output provided on many color-bar generators. The color-bar pattern is fine. You can also use the vertical-line or crosshatch patterns. This will test not only the gain but the horizontal resolution of the video amps (high-frequency bandpass).

If you see a good signal here, the trouble must be ahead of the video detector; check IF's, AGC, etc.

Troubles

Video troubles can be divided into two classes; those that affect the DC voltages and so the raster, and those which affect only the video signal. We must check out

the no-raster problems first, of course. The troubleshooting chart shows the steps, in order. If we can't see the raster, we can't tell much about picture quality!

There is a good deal of overlap. Problems which affect the DC voltages inevitably upset the picture quality, and vice versa. The picture-only problems will be things like smear, which also have multiple causes—often not in the video stages. Let's take them up one at a time.

No-raster problems

One of the most common problems is "black screen; sound OK, tubes lit, no sign of overheating, etc." There are many things that can cause this. The first thing which must be checked is the high-voltage. This will instantly tell us *where* to start—in the HV supply or in the video-picture-tube circuits. Quick-check: flip the SERVICE switch to SERVICE. If we can get three bright lines by turning up the screen controls, the high-voltage supply is OK (also, the picture tube is good! Two for the price of one). No service switch? Turn the set off, disconnect ultor lead, turn set on and measure the high-voltage. If it comes back to normal or above, you have a bias problem.

Cutoff problems

Picture tube cathode voltages too far positive will cut off the beam current. This could happen if the video output tube was dead or had an open circuit in its heater supply. The contrast control could be open, this would break the plate-cathode circuit. In all of these cases, the video output tube can not draw plate current. With no load, its plate voltage rises to the supply voltage, usually about +400 volts, enough to cut off the picture tube.

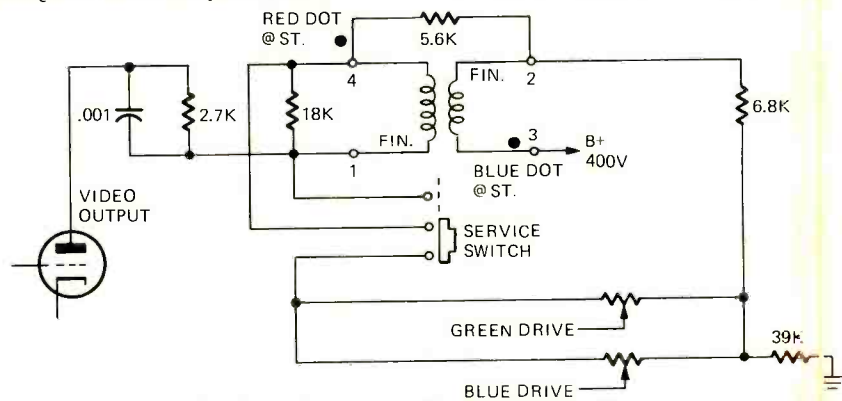


FIG. 3—PEAKING TRANSFORMER as used in RCA and other TV sets.

This is the same effect as making the grids too far negative. This can happen if there is a DC voltage *supply* problem in the color-difference amplifiers. Since there are three of these, one for each grid of the picture tube, the cause has to be something *common* to all. An open circuit or bad joint at the point where the three plate-load resistors connect to the supply is a common cause. Anything which *reduces* the diff-amp plate voltages simultaneously will do it.

In the later RGB circuits and especially in solid-state sets with individual modules feeding combined video and color to the picture tube cathodes, this would almost have to be a problem in the common voltage-supply. (Notice that I said "almost"?)

The key clue to a cutoff condition in the pix tube will be the fact that the high-voltage, still hooked up to the picture tube, will be up to its normal value. It may be slightly high because there's no beam current and therefore no load on the supply.

No or very low high-voltage

Here again we have no raster. However, now we have no high-voltage or perhaps very low high-voltage while the lead is connected to the picture tube. Using the service-switch test or disconnecting the high-voltage lead and finding full high-voltage, shows that the high-voltage supply is being badly overloaded. (You will find cases where the high-voltage will be pulled down to zero.)

Here, we have the opposite condition. The picture tube is being biased or drawing excessive beam current. The video amplifier plate may be low or less positive. A bad video amplifier tube or a bias problem on its grid will cause it to draw excessive plate current and therefore will pull its plate voltage down. In many circuits, there is a parallel-feed to the video amplifier plate and picture tube cathodes. A higher DC voltage is fed to the cathodes through a peaking transformer (see Fig. 3). RCA and many others use this. If one of its windings open, it will break the path to the +400-volt supply and the cathode voltage of the picture tube will drop to about 150-200 volts.

The grid voltages can go more positive, too. This can happen if something breaks their common plate-cathode circuit. They generally have a common cathode resistor, a bad solder joint or open resistor will do it. Also, in some sets, their heater circuit can be open due to a bad solder joint on the PC board. If this occurs, both tubes

(two twin triodes) will not draw plate current. As a result, their plates will jump to the supply value and so will the picture tube grids. Several sets use a triple triode (6MD8, etc.); if this tube goes dead, same reaction.

Either of these problem can also be due to trouble in the brightness control circuit. This usually has a high negative voltage to one end of the pot and a positive voltage to the other. If either of these should be lost, the BRIGHTNESS control will not function properly. Many late-model sets include a brightness-limiter circuit. This, of course, is subject to troubles, so check it too.

The key clue to this one is the high-
(continued on page 91)

MORE SKILLED MEN BY 1985.

America still needs men who are willing to work with their hands. Men trained for growing service careers like Auto Mechanics, Electrician, TV Repair, Air Conditioning, Electronics and Engineering.

According to a publication of the U.S. Office of Education, "You no longer need four years of college to start out on a scientific or technical career."

"You can break into any field—from medicine to computers to engineering to the space program—with only a year or two of education. Just become a technician."*

Tens of thousands of jobs are opening up every year for skilled men, according to the U.S. Department of Labor. (See chart.)

But the key word is *skilled*. And that's where we come in. We're ICS, International Correspondence Schools.

While we can't guarantee you a job, for over 80 years we've

taken *men* and turned them into *skilled men*. And we can do the same for you.

An ideal way to learn

As an ICS student, you study at home, on your own schedule. You waste no time traveling to and from class. And you never have to miss a paycheck.

But you're never alone. Skilled instructors are always ready to help you.

If you ever have doubts or problems, or just want to talk with an instructor, you can call ICS from anywhere in the continental United States, day or night, using our special toll-free Dial-a-Question® service.


ICS training works

Since 1890, millions of men and women around the world have turned to ICS for career training. More than 70 of America's largest 100 corporations (including Ford, U.S. Steel, Mobil Oil, GE and RCA) use ICS training for their own employees.

Free Demonstration Lesson

If you want more—more money, more security, more day-to-day satisfaction and more future—our free Career Guidance Booklet and free Demonstration Lesson can help you get started in the right direction. Just check the box next to the field that interests you most and mail the postpaid card or coupon today. There's no obligation.

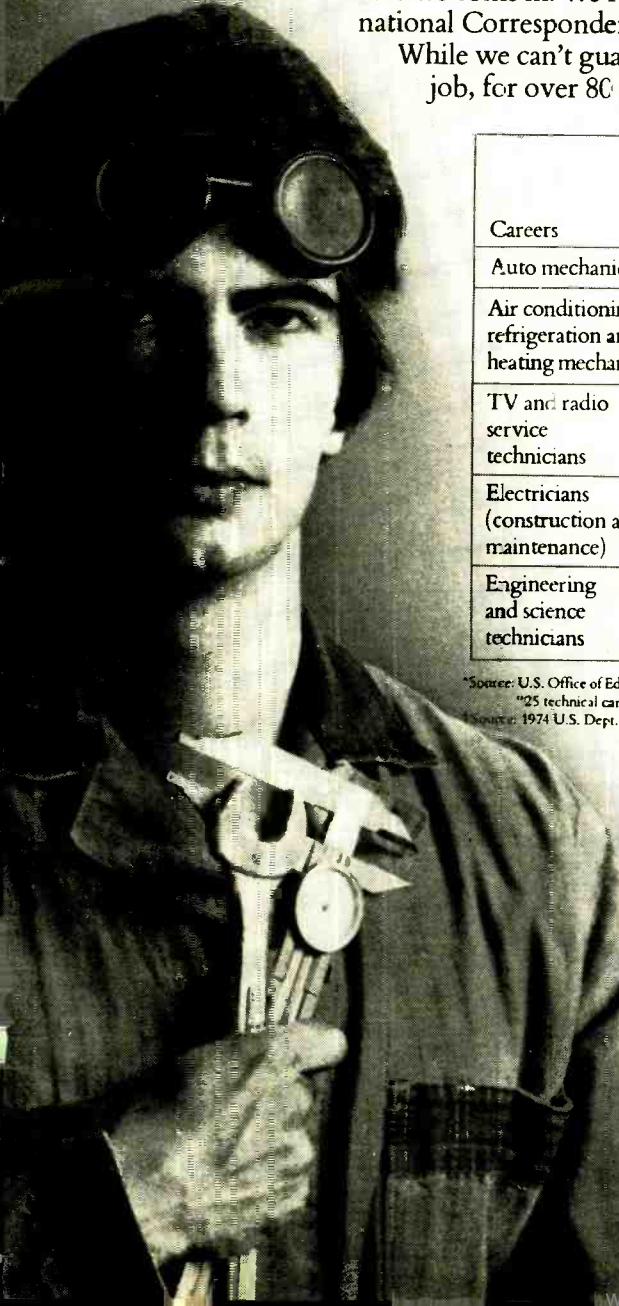Remember, it's your life. You might as well make the most of it.



Careers	Average annual job openings, 1972-85†	Percent increase in new job openings, 1972-85†
Auto mechanics	22,300	18.4%
Air conditioning refrigeration and heating mechanics	13,100	96.3%
TV and radio service technicians	4,400	18.1%
Electricians (construction and maintenance)	20,900	30.0%
Engineering and science technicians	39,600	48.9%

*Source: U.S. Office of Education publication.

†25 technical careers you can learn in 2 years or less."

†Source: 1974 U.S. Dept. of Labor Occupational Manpower and Training Needs

ICS International Correspondence Schools, Scranton, Pa. 18515

Please mail me the Free Career Guidance Booklet and Free Demonstration Lesson for the field I have checked below. I understand I am under no obligation.

- ☐ Electrician
- ☐ Engineering
- ☐ Accounting
- ☐ Drafting
- ☐ Electronics Technician
- ☐ TV Service and Repair
- ☐ Airline/Travel
- ☐ Surveying and Mapping
- ☐ Construction Electrician

- ☐ Diesel Mechanic
- ☐ Air Conditioning and Refrig.
- ☐ Automotive Mechanics
- ☐ Business Management
- ☐ Civil Engineering
- ☐ Interior Decorating
- ☐ Restaurant/Club Mgt.
- ☐ Income Tax
- ☐ Motel/Hotel Management

- ☐ Mechanical Engineering
- ☐ ICS High School Diploma
- ☐ High School Equivalency


- College Degree Programs
Associate in Specialized Business in:
- ☐ Accounting
 - ☐ Business Management


Name _____ Age _____
Address _____ City _____
State _____ Zip _____ Telephone _____

Canadian residents use Scranton, Pa. address for service from ICS Canadian, Ltd. In Hawaii: 931 University Ave., Honolulu, Hawaii 96814.
Approved for veterans' training. Approved for Federally insured student loans. Accredited member National Home Study Council.

XA806J

AMERICA NEEDS ONE MILLION

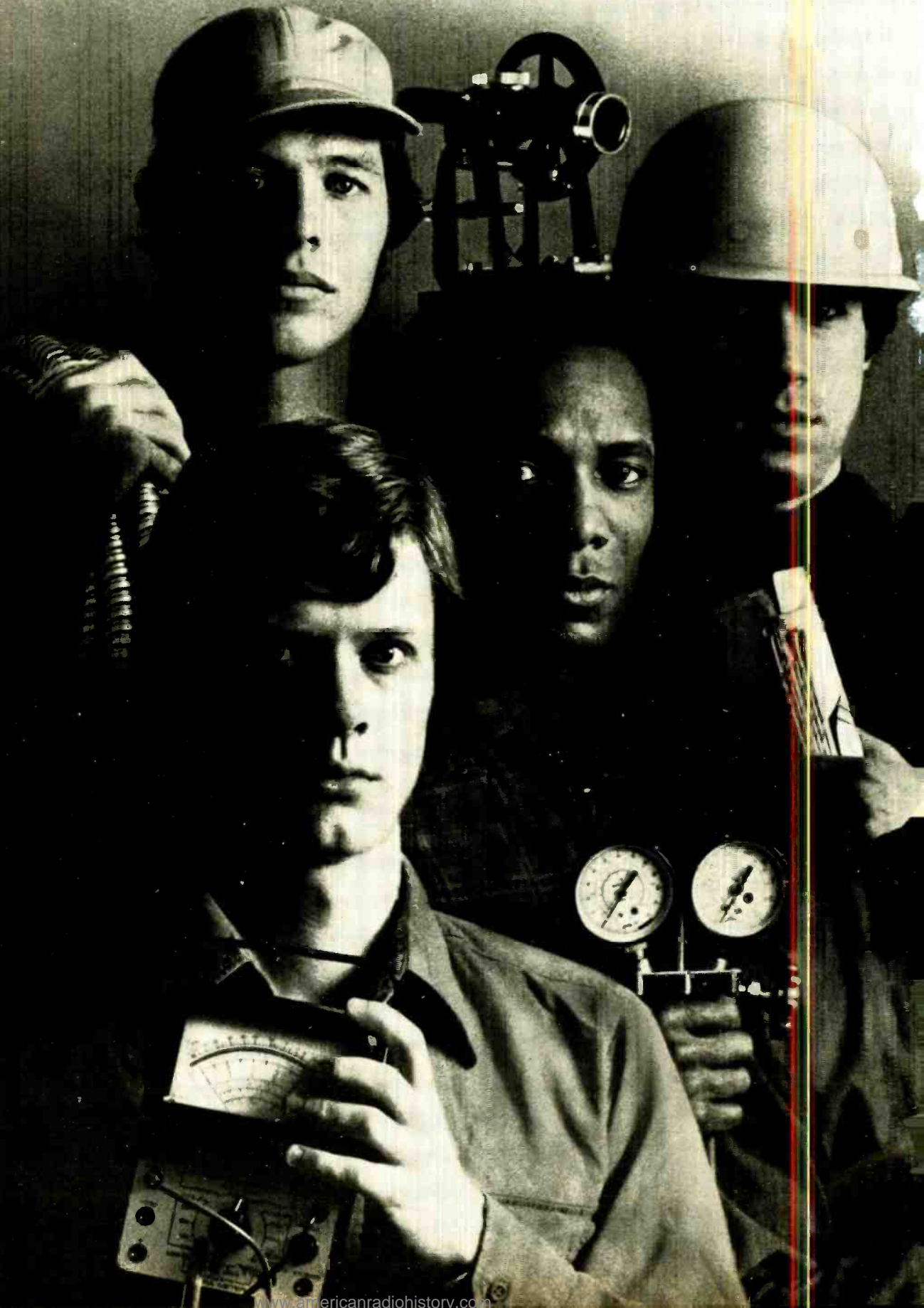

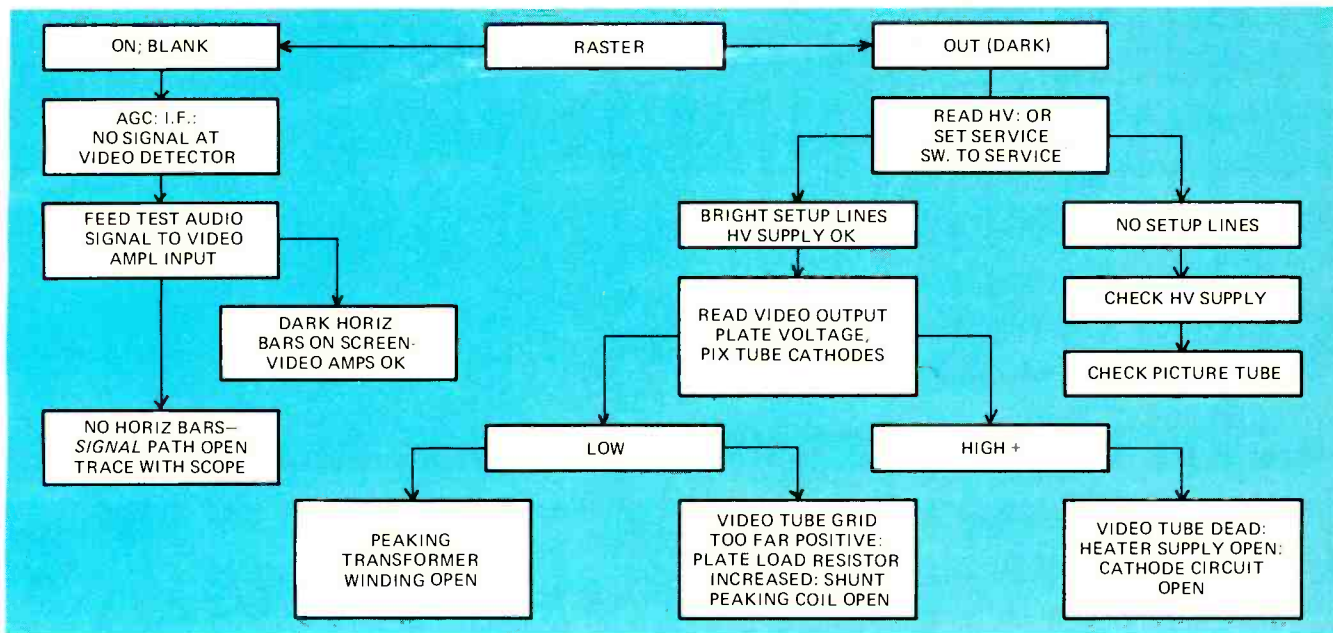

For instance, if whites are slightly bluish, the blue drive control is turned down a little.

The contrast control

The standard CONTRAST control used in this circuit is a simple cathode-degeneration control, from the video output cathode to ground. This will be a small variable resistor, around 100 ohms. This control does NOT vary the cathode resistance; this would change the DC level and affect the brightness. Instead, its

slider is connected to a big electrolytic capacitor, 50-100 μ F or more. This can be moved from ground (maximum degeneration, lowest contrast) to the cathode (minimum degeneration, maximum contrast) without changing the DC bias. It affects only the *signal*. (Theoretically; actually, there will be a slight shift and an apparent increase in brightness in most cases.)

The BRIGHTNESS and CONTRAST controls in the typical set will show some interaction. You'll usually have to adjust

both controls to get the picture you want. Excessive contrast can actually cause blooming of some colors and even a false misconvergence. In many of the older sets, the best setting for the CONTRAST control is practically at minimum.

Signal polarity

In the common-cathode tube amplifier, there is a polarity inversion between input and output. The same polarity inversion exists in common-emitter transistor amplifiers. So, the designer must start at the

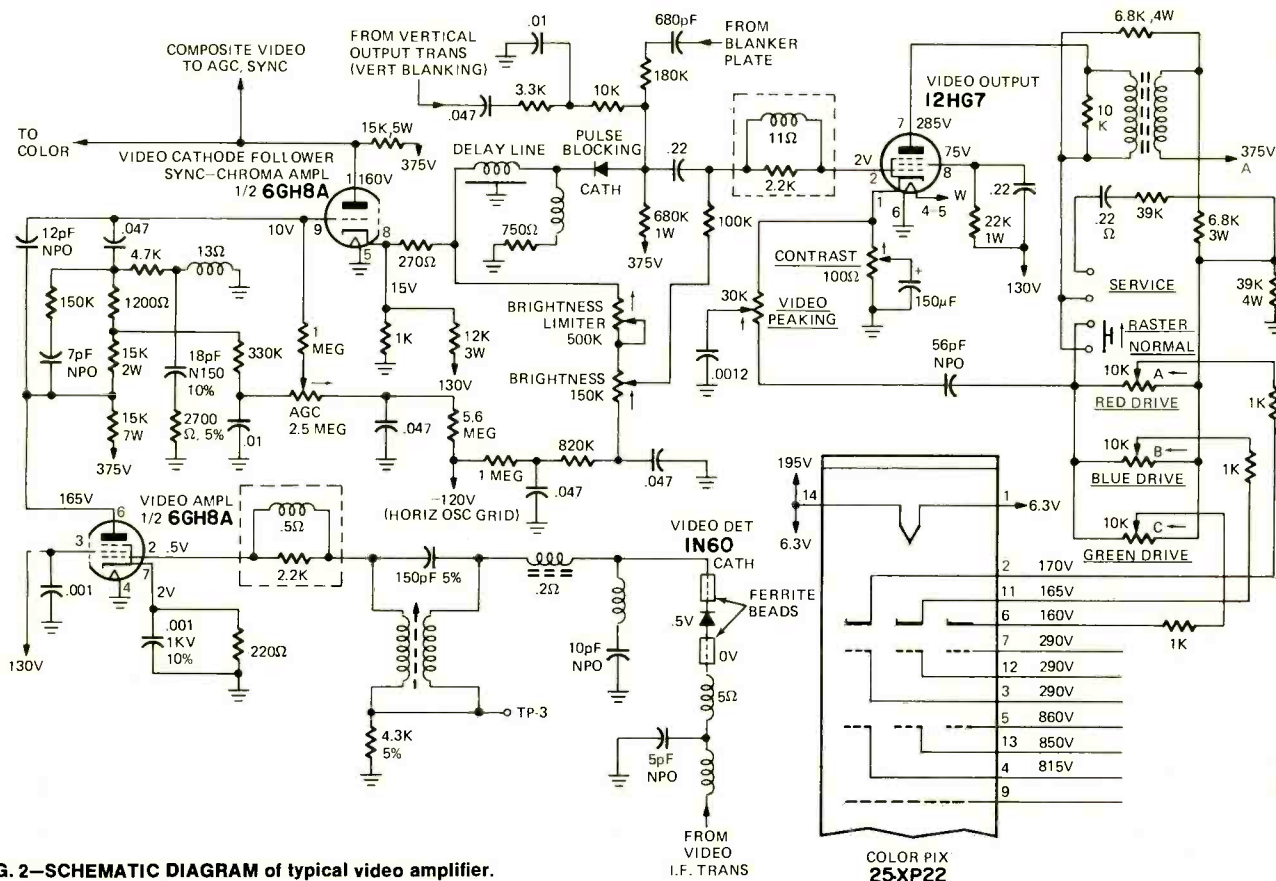


FIG. 2—SCHEMATIC DIAGRAM of typical video amplifier.

Step-by-step TV Troubleshooters Guide

A good color picture depends upon a good video signal. Check the video stages if the color isn't quite right.

by JACK DARR
SERVICE EDITOR

AFTER THE TV SIGNAL COMES OUT OF THE video detector in a color TV, it is divided into two parts. One is the color signal, and the other is the black and white. The black and white signal is called luminance, "Y," and so on, but I think most of us say "video," so that'll be it from now on. This signal is very important in making a good color picture. Since all colors are actually the color signal minus the video (That's why you see terms like "R-Y," etc.), if the video signal isn't right, your color picture is going to look very odd indeed.

How It Works

The signal from the video detector output is fed through a straight cascade amplifier. This amplifier may have two or three stages, but the signal comes out the same. We must have a signal voltage at the output of at least 100 volts p-p to drive the picture tube cathodes, with the sync positive-going. Normal output voltage of the video detector will be about 2 volts. So, our video stages must have an overall voltage gain of at least 50.

The signal polarity will be the same in either of the two basic circuits found in color TV sets; the old original circuit, where colors are fed to the grids and video to the cathodes, and the later "RGB" circuits. In the RGB circuits, the video is a part of the composite signal which is fed to the cathodes. Grids are tied together. So, we still need signals with positive-going sync.

Why? Very simple reason. All TV sets start out with a white raster. The signal must blackout the raster at certain places to make the picture. So, we must have a signal with enough amplitude to drive the picture tube to full cutoff, and it must have the right polarity. If the signal is fed to the grids, it would have to be negative-

going. (All vacuum tubes can be cut off by enough negative voltage on the grid.) Since we are feeding the cathodes, we need the opposite polarity, or positive going sync. If we place a high enough positive voltage on the cathode, this is the same as making the grid negative, and we get cutoff.

In the typical B/W pix tube, this will be about 50 volts; in color picture tubes, about 100 volts. We do not want the sync signal in the picture. So, the sync actually starts at what is called the "black level" in the picture and goes on into the "blacker-than-black" part. See Fig. 1. The sync pulses actually help to blank out retrace for both sweeps.

If the video amplifier loses gain, we'll have a washed-out picture without enough contrast. Blacks will be gray and colors will be pale and weak. This happens because the signal voltage is not high enough to drive the picture tube into full cutoff. Some beam current still flows.

Peaking

Video amplifiers are simple cascaded stages. However, we must "peak" them for a very good high-frequency response; ideally up to 5.0 MHz. In practical circuits it's not that wide, but it is wide enough to get all of the fine detail into the picture. This high-frequency peaking is done by adding small RF chokes in the input and output circuits of each amplifier stage. This increases the load impedance at higher frequencies. In the color video signal, there are a few things that we'd rather not have in the picture, the 4.5-MHz sound i.f. and the 3.58-MHz color subcarrier for example. So, these are reduced in amplitude by adding sharply tuned trap circuits. This will not greatly affect the overall frequency response of

the circuit.

The delay line

The final unusual thing found in color-TV video stages is the delay line. Video signals go straight through; the color signals must go through several more stages. Therefore, the video must be delayed very slightly (about 1.0 microsecond) so that both video and color signals will arrive at the picture tube at precisely the same time. You'll usually find this unit in either the input or output circuit of the final video amplifier, although it can turn up anywhere. The delay-line unit is simply a single-layer coil with foil wrapped around it.

Blanking

Blanking of the raster is needed during retrace time for both sweeps. This is often added to the video signal in the form of a pulse. The blanking pulse must be of the right polarity to cause cutoff when it gets to the picture tube. You'll find it added to the signal in some of the early video stages in many sets.

Brightness control

In the vast majority of color TV sets, the whole video circuit will be directly coupled all the way from the video detector to the picture tube. So, a small change in DC level at the input can cause a large change at the output. We control brightness by varying the DC voltages on the picture tube cathodes. Grid voltages can also be varied for this effect and you'll find it in a few sets.

You may find the BRIGHTNESS control at any point in the video amplifier! It will be hooked up so that it varies the DC level in the video signal-path. Possibly the most common location would be in the input circuit of the last video amplifier. It will be connected across a source of negative voltage at one end, and positive at the other. Here, it controls the grid bias on the video output amplifier.

Color drive controls

In many color sets, you will find variable resistors in the green and blue cathode circuits. The red cathode is usually fed straight through. These are called drive controls although you'll find them labelled BLUE GAIN, etc., in some sets. They are used for better black-and-white tracking of the picture at varying brightness levels, usually near the brightest point. They're adjusted to make the whites white.

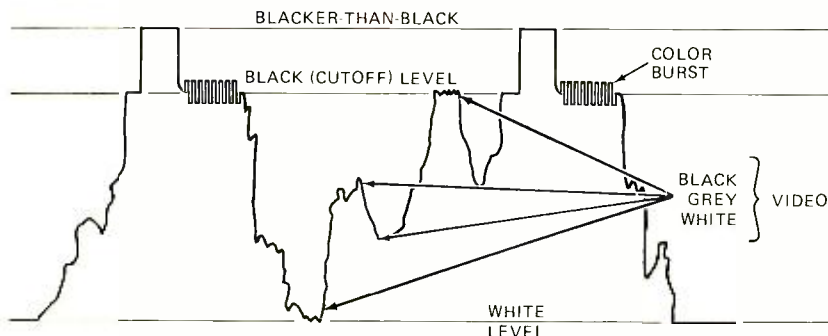


FIG. 1—STANDARD VIDEO signal shows the blacker-than-black level of the sync and the black, grey and white video signals.

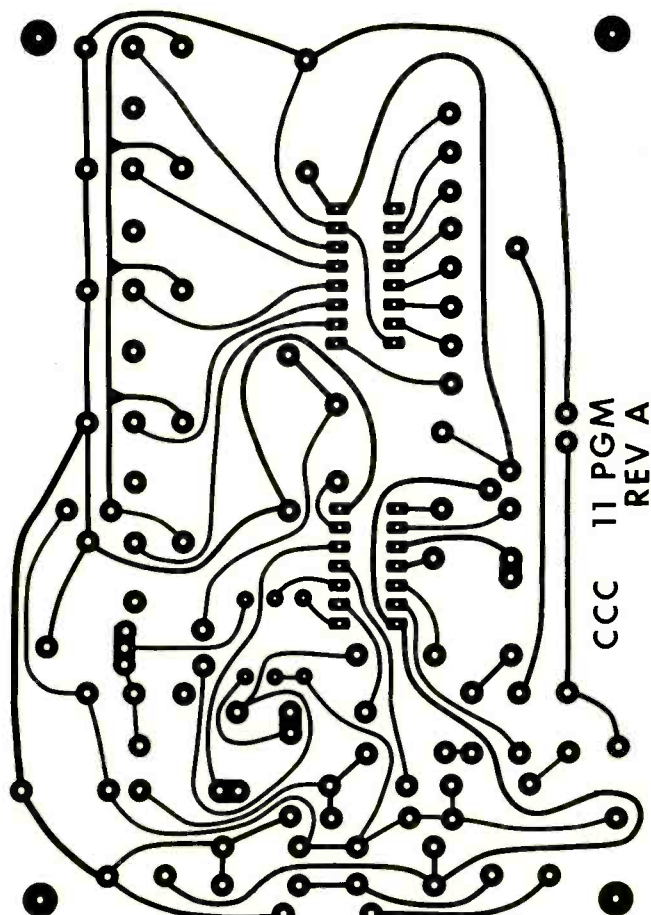


FIG. 4 (left)—PROM PROGRAMMER schematic diagram.

FIG. 5 (above)—FOIL PATTERN of printed circuit board for PROM Programmer.

FIG. 6 (right)—COMPONENT LAYOUT for the PROM programmer.

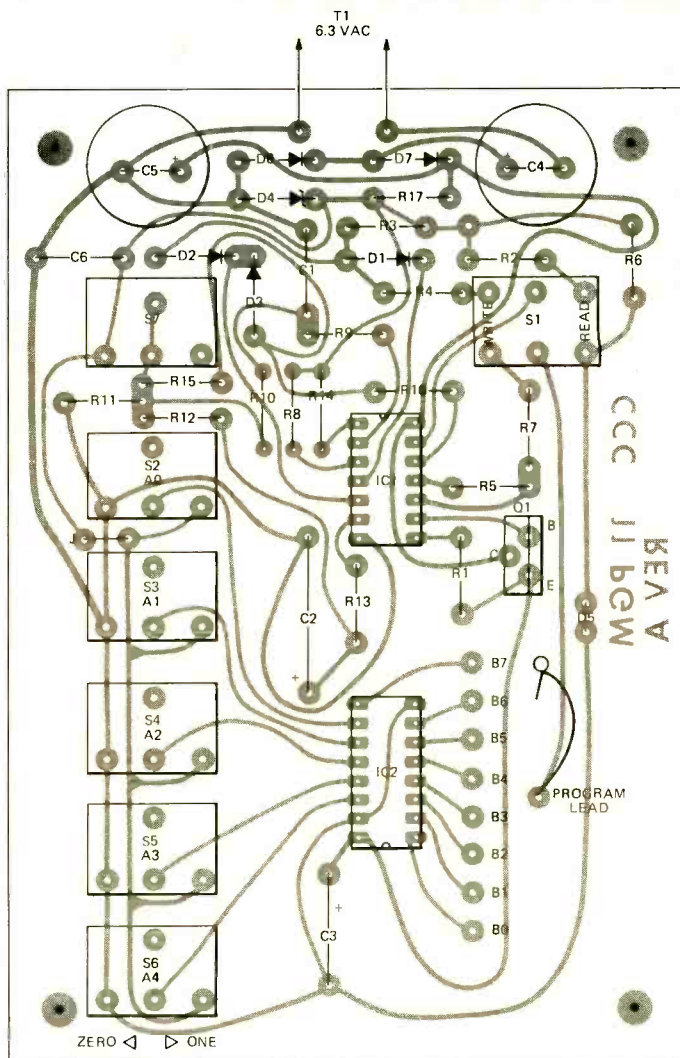


TABLE II

BINARY CODING FOR MUSICAL SCALE COVERING TWO OCTAVES

Musical Note	Binary word for each note					
	6*	5*	4*	3*	2*	1*
	B5	B4	B3	B2	B1	B0
E5	0	0	0	0	0	1
E5 \flat	0	0	0	0	1	1
D5	0	0	0	1	0	1
C5 \sharp	0	0	0	1	1	1
C5	0	0	1	0	0	1
B4	0	0	1	1	0	0
B4 \flat	0	0	1	1	1	0
A4	0	1	0	0	0	1
G4 \sharp	0	1	0	1	0	0
G4	0	1	0	1	1	1
F4 \sharp	0	1	1	0	1	1
F4	0	1	1	1	1	0
E4	1	0	0	0	0	1
E4 \flat	1	0	0	0	1	1
D4	1	0	0	1	0	1
C4 \sharp	1	0	0	1	1	1
C4	1	0	1	0	0	1
B3	1	0	1	1	0	0
B3 \flat	1	0	1	1	1	0
A3	1	1	0	0	0	1
G3 \sharp	1	1	0	1	0	0
G3	1	1	0	1	1	1
F3 \sharp	1	1	1	0	1	1
F3	1	1	1	1	1	0
mute	0	0	1	1	1	1

of capacitors and diodes. The Molex IC terminals provide a socket for the integrated circuit and a connector for plugging in the programming lead to select the bit position. For simplicity, the slide switches and push button are soldered directly to the circuit board.

Before plugging in the PROM for programming, the circuit should be checked as follows. Confirm that the power supply voltage is 17-19 volts measured across C5. With the mode switch in the READ position, measure the voltage on the emitter of Q1 which should be 4.75 to 5.25 volts. Place the mode switch in the PROGRAM position, and connect a temporary short across

C2. Pressing the pushbutton switch S7, measure the voltage at emitter Q1 and the programming lead. Both should measure between 12 and 13 volts which then drops to 1.5 volts or less when the short is removed from C2.

To illustrate a typical programming procedure, refer to the Table I. Start at program step #1. Set address switches A0, A1, A2, A3 and A4 all to "0" (ground). Place mode switch on READ. Connect the programming lead to B0 (IC pin 1). The LED should be off confirming that the B0 fuse has not been blown. Throw mode switch to PROGRAM. Note the LED will always light when the mode switch is in PROGRAM position. Since Table I shows B0 as a "1", the fuse for this bit position should be blown. Pressing the pushbutton switch S7 blows the fuse programming a "1". Verify the "1" by switching to the READ mode. It may be necessary to repeat the procedure if the fuse does not blow the first time. It is also advisable to check the "0" bit positions to confirm that the fuse has not been blown. Use great care in programming since it is not possible to change a "1" to "0".


R-E

TABLE III

PROGRAMMING THE BEATS PER NOTE

Beats Per Note	Bit Position	
	B7	B6
	9*	7*
1	0	0
2	0	1
3	1	0
4	1	1

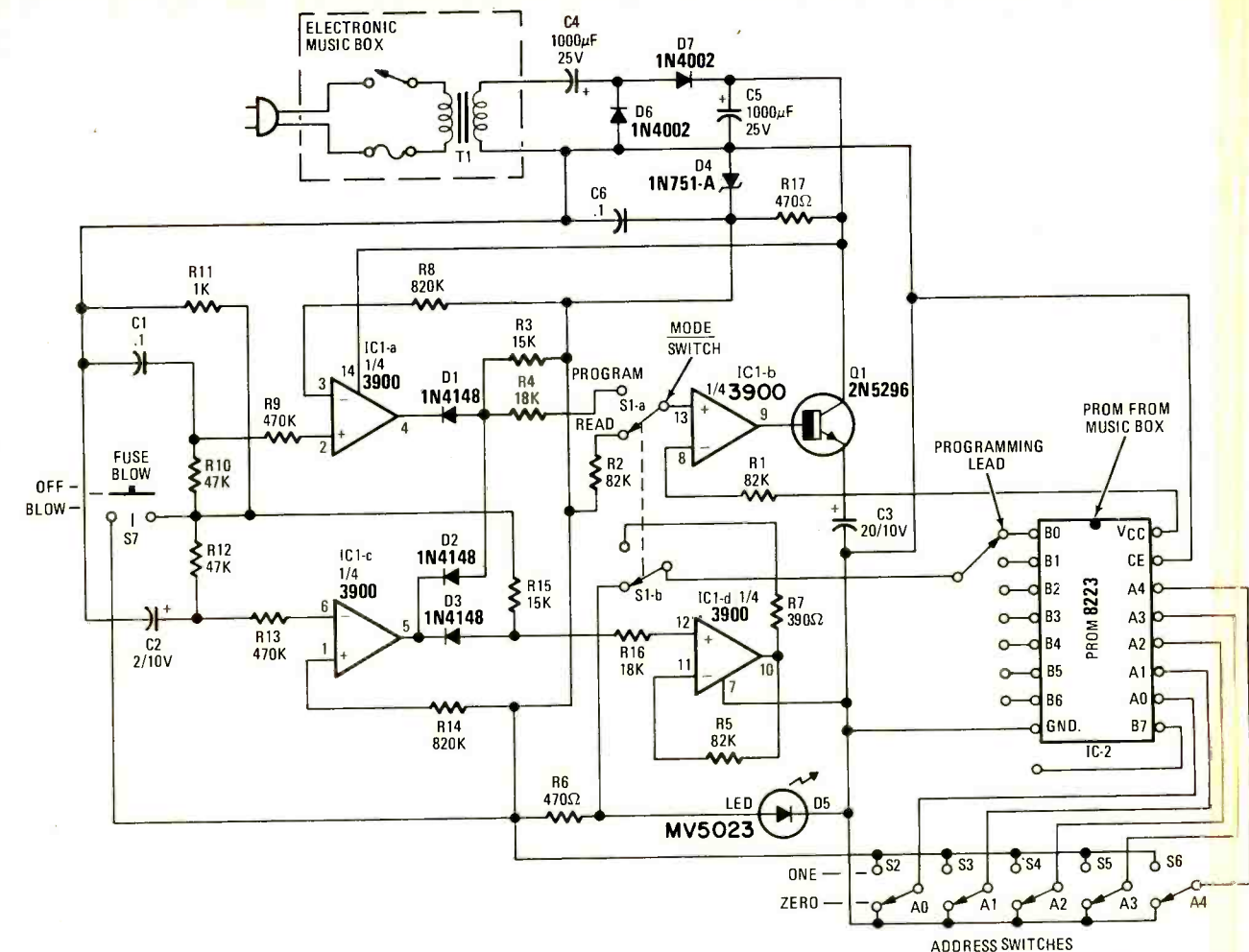*Number designates pin connection on IC6.



PROM PROGRAMMER PARTS LIST

All resistors are 1/4-watt, 10%, unless noted

R1, R2, R5—82,000 ohms, 5%
 R3, R15—15,000 ohms, 5%
 R4, R16—18,000 ohms, 5%
 R6, R17—470 ohms
 R7—390 ohms
 R8, R14—820,000 ohms
 R9, R13—470,000 ohms
 R10, R12—47,000 ohms
 R11—1,000 ohms
 C1, C6—.1 μ F polyester film
 C2—2 μ F, 10 volt electrolytic
 C3—20 μ F, 10 volt electrolytic
 C4, C5—1,000 μ F, 25 volt electrolytic
 IC1—3900 linear quad amplifier
 Q1—2N5296
 D1, D2, D3—1N4148
 D4—1N751A

D5—MV5023 LED
 D6, D7—1N4002
 S1—DPDT slide switch, PC board mount
 S2, S3, S4, S5, S6—SPDT slide switch, PC board mount
 S7—SPST normally open spring return slide switch, PC board mount
 T1—117 volt primary, 6.3 volt @ 0.6A secondary
 Misc.—Molex IC connectors, wire, solder, hardware.

The following parts may be ordered from Cousino Circuit Company, 3313 Brace Street, Burbank, CA 91504
 #K11-EMB—Kit of all items in Electronic Music Box parts list, except miscellaneous items, fuse and transformer. Includes

PC board and un-programmed PROM. \$36.95 postpaid within USA.

#KHS11-EMB—Same as #K11-EMB except PROM is pre-programmed with "Home Sweet Home" melody. \$39.95 postpaid within USA.

#11-EMB—Drilled glass epoxy printed circuit board for Electronic Music Box. \$6.95 postpaid within USA.

#K11-PGM—Kit of all parts in parts list for PROM Programmer except miscellaneous items. Includes printed circuit board and programming data for several melodies. \$21.95 postpaid within USA.

#11-PGM—Drilled glass epoxy printed circuit board for PROM Programmer. \$5.95 postpaid within USA. California residents add sales tax.

setting switches S2, S3, S4, S5 and S6 to the binary address being programmed. This address is designated as A0, A1, A2, A3, A4 in the programming Table 1. The bit positions for each word B0, B1, B2, B3, B4, B5, B6 and B7 are programmed "1" as designated in Table 1 by connecting the programming lead to each bit position being programmed. The mode switch S1 placed in the READ position shows the bit status. The LED is on when a "1" is programmed. With the LED off, a "0" is programmed which should be the case of an unprogrammed bit.

Changing the mode switch S1 to the PROGRAM position prepares the circuit for blowing the bit fuse.

Depressing pushbutton switch S7 for one second or more blows the bit fuse, thereby programming a "1". When S7 is depressed, 5 volts is applied to the two R-C networks and voltage regulator IC1-d. The R10-C1 network switches comparator IC1-a after a brief delay. This unclamps voltage regulator IC1-b applying 12.5 volts to V_{cc} of the PROM. At the same time, 12.5 volts is applied immediately by voltage regulator IC1-d to the bit position being


programmed. After an elapsed time determined by R12-C2, comparator IC1-c clamps both voltage regulators to ground reducing both 12.5 volt outputs to 1.5 volts or less. At this time, the bit fuse should be blown. It is confirmed by switching the mode switch to the READ position. The LED should light, confirming a "1".

The programming circuit can be constructed on a PC board, with the circuit layout shown in Fig. 5 and component location detailed in Fig. 6. All components should be soldered in place using care to observe polarities

IC Doorbell Plays Your Song

You can program your own tune into this device and connect it to your doorbell. It features a PROM with a 32-note capacity.

by RALPH E. COUSINO

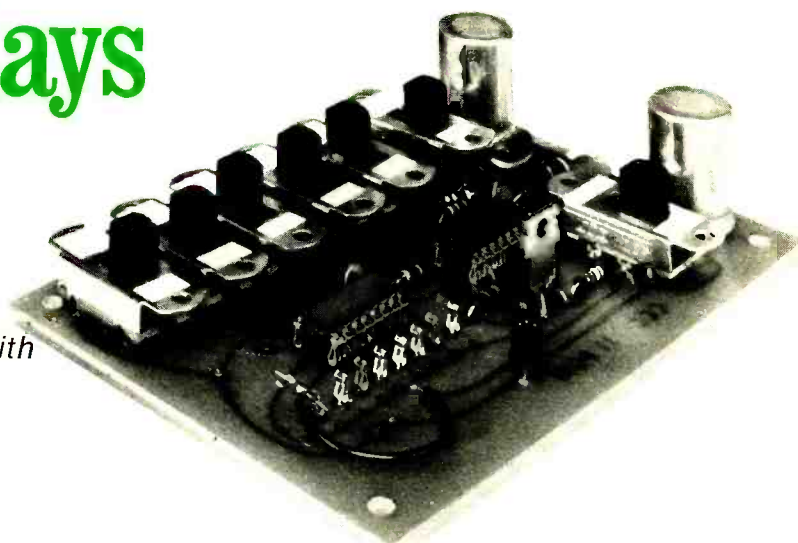

PART 1 OF THIS ARTICLE CONTAINED THE circuit description and construction details for this unusual doorbell.

This month, part 2 concludes this article with the circuit and programming details for the PROM.

Programming your melody

The electronic music box covers two octaves which provides the musical range to program most melodies. These two octaves begin at F below middle C or F3, when the master oscillator is set for 21560 HZ. Table I illustrates programming for the melody "Home Sweet Home." The notes of the melody are shown in the sequence in which they are played, beginning with program step one. The corresponding beats per note is also shown and designates the time the note will be held. The program word consists of eight bits B7 through B0. Refer to Tables II and III for the proper encoding of each note and beat. Since the melody requires only 28 steps, the remaining four steps are muted by making B3, B2, B1 and B0 all high. Where it is required to hold a note longer than four beats, step to the next word. Repeat the note and hold for the required additional beats. This is illustrated by steps #13 and #14, plus #27 and #28 where six beats are required.

The PROM can now be set up with your completed program. The address for each word should be noted as in Table I. Addressing all words of the PROM, blow the fuse to program each bit as shown for your melody. The program may be checked before programming the PROM. With the PROM IC6 and IC1 removed from their sockets, connect the poles of six SPDT switches to pins 1, 2, 3, 4, 5 and 6 of IC6. This corresponds to bit positions B0, B1, B2, B3, B4 and B5, respectively. One side of the switches should be tied to 5 volts—the other to ground. In the 5 volt

position, a "1" is programmed. In the ground position, a "0" is programmed. Set the switches for the note required which plays continuously. Using a tape recorder with pause control, record each note in the sequence it will be

memory that is programmed by means of built-in fuses. For each bit position, a "1" is programmed when the fuse is blown and "0" when not blown. The 8223 is supplied with all bit positions low or zero. The programming is ac-

TABLE I
PROGRAMMING FOR THE MELODY "HOME SWEET HOME"

Program Step	Program Steps Binary Address					Notes of Melody	Beats per Note	Binary Program for Note and Beat							
	14*	13*	12*	11*	10*			9*	7*	6*	5*	4*	3*	2*	1*
	A4	A3	A2	A1	A0			B7	B6	B5	B4	B3	B2	B1	B0
1	0	0	0	0	0	F4	1	0	0	0	1	1	1	1	0
2	0	0	0	0	1	G4	1	0	0	0	1	0	1	1	1
3	0	0	0	1	0	A4	4	1	1	0	1	0	0	0	1
4	0	0	0	1	1	B4 _J	2	0	1	0	0	1	1	1	0
5	0	0	1	0	0	D5	2	0	1	0	0	0	1	0	1
6	0	0	1	0	1	C5	4	1	1	0	0	1	0	0	1
7	0	0	1	1	0	A4	2	0	1	0	1	0	0	0	1
8	0	0	1	1	1	C5	2	0	1	0	0	1	0	0	1
9	0	1	0	0	0	B4 _J	3	1	0	0	0	1	1	1	0
10	0	1	0	0	1	A4	1	0	0	0	1	0	0	0	1
11	0	1	0	1	0	B4 _J	3	1	0	0	0	1	1	1	0
12	0	1	0	1	1	G4	1	0	0	0	1	0	1	1	1
13	0	1	1	0	0	A4	4	1	1	0	1	0	0	0	1
14	0	1	1	0	1	A4	2	0	1	0	1	0	0	0	1
15	0	1	1	1	0	F4	1	0	0	0	1	1	1	1	0
16	0	1	1	1	1	G4	1	0	0	0	1	0	1	1	1
17	1	0	0	0	0	A4	4	1	1	0	1	0	0	0	1
18	1	0	0	0	1	B4 _J	2	0	1	0	0	1	1	1	0
19	1	0	0	1	0	D5	2	0	1	0	0	0	1	0	1
20	1	0	0	1	1	C5	4	1	1	0	0	1	0	0	1
21	1	0	1	0	0	A4	2	0	1	0	0	1	0	0	1
22	1	0	1	0	1	C5	2	0	1	0	0	1	0	0	1
23	1	0	1	1	0	B4 _J	3	1	0	0	0	1	1	1	0
24	1	0	1	1	1	A4	1	0	0	0	1	0	0	0	1
25	1	1	0	0	0	B4 _J	2	0	1	0	0	1	1	1	0
26	1	1	0	0	1	G4	2	0	1	0	1	0	1	1	1
27	1	1	0	1	0	F4	4	1	1	0	1	1	1	1	0
28	1	1	0	1	1	F4	2	0	1	0	1	1	1	1	0
29	1	1	1	0	0	mute	1	0	0	0	0	1	1	1	1
30	1	1	1	0	1	mute	1	0	0	0	0	1	1	1	1
31	1	1	1	1	0	mute	1	0	0	0	0	1	1	1	1
32	1	1	1	1	1	mute	1	0	0	0	0	1	1	1	1

*Number designates pin connection on IC-6.

played for a period equal to the number of beats it is to be held. Playing back the tape you will hear the melody.

Programming the PROM

The PROM 8223 is a read-only

completed by addressing each word of eight bits and blowing those bit fuses that are required to be "1".

The circuit used for programming is shown in Fig. 4. The circuit operation consists of addressing each word by