

# Radio-<sup>IND</sup>Electronics

\$1.25 ■ AUG. 1979

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

## ADAPTIVE NOISE FILTER

Hi-fi add-on you build

## SATELLITE TV RECEPTION

A new DX craze

Build your own

## AC POLARITY CHECKER

Don't get zapped!

## TV ADD-ON GADGETS

Do they really work?

## WIRING SYSTEMS

Easy ways to build projects

Build this 4½-digit

## PRECISION DMM

with true RMS and temperature



**PLUS:**

- ★ New FM Tuner Circuits
- ★ 2 R.E.A.L. Lab Test Reports
- ★ Hobby Corner ★ Equipment Reports ★ Service Clinic

RETAILER: SEE PAGE 102 FOR  
SPECIAL DISPLAY ALLOWANCE PLAN



# Value where it counts.



Count up to 550 MHz or more, count down to \$69.95\*. Smaller size, lower prices and professional accuracy help make CSC portable frequency counters the best in the business.

**MAX-550** lets you count up to 550 MHz on your fingers! This amazing counter is as small as some pocket calculators, yet offers continuous six-digit readings from 30 KHz to 550 MHz, updated six times a second to speed your work. Battery powered, it's just \$149.95\*.

**MAX-100** measures down to the last Hertz from 20 Hz to past 100 MHz, displaying the count on eight big 0.6" LED digits. It's battery operated, portable, and perfect for professional precision applications—and just \$134.95\*.

**MAX-50** in its calculator-sized case lets you

grab ahold of 100 Hz to 50 MHz and displays the count on six bright LED digits. Its accessory mini-whip antenna even lets you pick up RF fields when a cable is inconvenient. And it's a speed reader, with six updates per second. All for just \$69.95\*.

**PS-500** is our very capable Buffered Prescaler, which extends the range of almost any frequency counter ten times, up to 500 MHz. Its buffered 400 mV output can drive even tired old counters reliably. And you can add this extra capability for just \$59.95\*.

We have a full line of accessories, too, including cables, battery charger/eliminators and more.

From audio to UHF, microprocessor to radio control, whatever your application, you can count on CSC frequency counters for performance—and value—where it counts.

70 Fulton Terr. New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227  
OTHER OFFICES: San Francisco (415) 421-8872, TWX 910-372-7992  
Europe: CSC UK LTD Phone Saffron-Walden 0799-21682, TLX 817477  
Canada: Len Finkler Ltd., Ontario

CONTINENTAL SPECIALTIES CORPORATION



Call toll-free for details  
**1-800-243-6077**

**Smarter tools for testing and design.**

\* Suggested U.S. resale. Available at selected local distributors. Prices, specifications subject to change without notice. © Copyright 1979 Continental Specialties Corporation

CIRCLE 12 ON FREE INFORMATION CARD



# Don't take our word for it.

"We can heartily recommend the Superboard II computer system for the beginner who wants to get into microcomputers with a minimum of cost. Moreover, this is a 'real' computer with full expandability."

*Popular Electronics March, 1979*

"(Their) new Challenger 1P weighs in at \$279 and provides a remarkable amount of computing for this incredible price."

*Kilobaud Microcomputing February, 1979*

"Over the past four years we have taken delivery on over 25 computer systems. Only two have worked totally glitch free and without adjustment as they came out of the carton: The Tektronic 4051 (at \$7,000 the most expensive computer we tested) and the Ohio Scientific Superboard II (at \$279 the least expensive) . . . The Superboard II and companion C1P deserve your serious consideration."

*Creative Computing January, 1979*

"The Superboard II and its fully dressed companion the Challenger 1P series incorporate all the fundamental necessities of a personal computer at a very attractive price. With the expansion capabilities provided, this series becomes a very formidable competitor in the home computer area."

*Interface Age April, 1979*

"The graphics available permit some really dramatic effects and are relatively simple to program . . . The fact that the system can be easily expanded to include a floppy means that while you are starting out with a low-cost minimal system, you don't have to throw it away when you are ready to go on to more complex computer functions. Everything is there that you need; you simply build on to what you already have. You don't have to worry about trading off existing equipment to get the system that will really do what you want it to do. At \$279, Superboard II is a tough act to follow."

*Radio Electronics June, 1979*

"The Superboard II is an excellent choice for the personal computer enthusiast on a budget."

*Byte May, 1979*



## **SUPERBOARD II** **\$279.00**

The world's first complete computer system on a board including full keyboard, video display, audio cassette interface, 8K BASIC-in-ROM and 4K RAM. Expandable. Requires +5V at 3 amp power supply.



## **C1P \$349.00**

Complete with enclosure and power supply. All features of Superboard II. Easy to expand to more memory and floppy disk.

## **C1P MF \$995.00**

The first floppy disk based computer system the world has ever seen for under \$1,000. 8K BASIC-in-ROM, 12K RAM. Expandable to 32K RAM.



# OHIO SCIENTIFIC

1333 S. CHILLICOTHE RD., AURORA, OHIO 44202 (216) 562-3101

See your Ohio Scientific dealer for full details.

CIRCLE 3 ON FREE INFORMATION CARD

# WHEN THE GOING GETS TOUGH, BECKMAN'S NEW DIGITAL MULTIMETERS KEEP GOING.



## Featuring new continuity function.

If you've ever been troubled by a faulty multimeter—or had to use one that wasn't quite up to the tougher jobs—your troubles are over. Now there's the Beckman line of digital multimeters. A new generation of 3½-digit models that combine superior reliability with highly versatile features.

Features like a unique continuity test function. With Beckman's new Insta-Ohms™ quick continuity indicator, you no longer need an analog VOM for fast, convenient continuity checks.

There's also 10-amp current ranges, in-circuit resistance measurement capability in all six-ohm ranges, a dedicated diode test function, and up to two years normal operation from a common 9V battery.

The Model TECH 310 with all these features,

7 functions, 29 ranges, and 0.25% Vdc accuracy is only \$130.

The Model TECH 300 with 0.5% Vdc accuracy, but without the continuity function or the 10-amp current ranges, is just \$100.

Whichever model you choose, you get a multimeter that won't let you down. There's exceptional overload and 6kV transient protection, plus ruggedness to take a 6-foot fall and to come up working.

So get the Beckman digital multimeter that performs and keeps on performing. No matter how tough the going gets. For information on the complete line and accessories, write or call your local distributor or the Advanced-Electro Products Division, Beckman Instruments, Inc., 2500 Harbor Boulevard, Fullerton, CA 92634, (714) 871-4848, ext. 3651.

# BECKMAN

CIRCLE 51 ON FREE INFORMATION CARD



# Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS  
Electronics publishers since 1908

AUGUST 1979 Vol. 50 No. 8

## BUILD ONE

- 37 **4½-Digit Precision DMM**  
Lab grade instrument with true-RMS and temperature.  
by Bill Owen
- 43 **Adaptive Noise Filter**  
Add-on for your hi-fi system reduces noise by 14-dB.  
by Tim Skormond and Gene Garrison
- 53 **AC Polarity Checker**  
Don't get zapped! Simple device checks AC outlet sockets for correct polarity and ground connections.  
by William D. Kraengel, Jr.

## VIDEO

- 47 **Home TV Reception Via Satellite**  
The TV satellite network—broadcasts and frequencies.  
by Robert Cooper
- 50 **TV Add-On Gadgets—Do They Really Work?**  
A look at ghost eliminators, interference filters, etc., and their effectiveness.  
by Robert B. Grove
- 72 **Service Clinic**  
Don't forget the filter capacitors.  
by Jack Darr
- 72 **Service Questions**  
R-E's Service Editor solves technician problems.

## AUDIO

- 57 **New FM Tuner Circuits**  
A look at the circuitry behind the super performance and features of today's FM tuners.  
by Len Feldman
- 60 **R.E.A.L. Sound Lab Tests Sony STR-V7 Receiver**  
Sony's most powerful receiver.
- 63 **R.E.A.L. Sound Lab Tests dbx Model 2BX Expander**  
2 band expander increases dynamic range.

## TECHNOLOGY

- 4 **Looking Ahead**  
Tomorrow's news today.  
by Dave Lachenbruch
- 54 **Wiring Systems For Projects**  
A look at the different ways you can wire your projects.  
by Earl "Doc" Savage, K4SDS
- 66 **Hobby Corner**  
How to modify an alarm clock for multiple alarms.  
by Earl "Doc" Savage, K4SDS
- 68 **Communications Corner**  
Are computerized CB's really computerized?  
by Herb Freidman
- 70 **Computer Corner**  
A look at the 8085 and how it compares to the 8080.  
by P. Rony, C. Titus, D. Larsen and J. Titus

## EQUIPMENT

- 24 **Sinclair Radionics Model DM350 DMM**
- 24 **PTS Model 8001 Component Analyzer**
- 26 **Apple Disk II Floppy Disc System**
- 33 **Realistic Model DX-300 Receiver**

## DEPARTMENTS


- |                           |                    |
|---------------------------|--------------------|
| 102 Advertising Index     | 12 Letters         |
| 6 Advertising Offices     | 82 Market Center   |
| 76 Communication Products | 81 New Books       |
| 75 Computer Products      | 74 Stereo Products |
| 6 Editorial               |                    |
| 103 Free Information Card |                    |
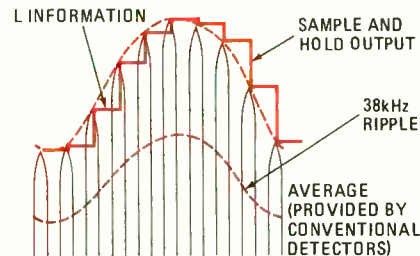
## ON THE COVER

Precision 4½-digit DMM has lab-grade performance and features, including true-RMS and temperature measurement. Basic DC accuracy is better than .05%. Internal rechargeable nickel-cadmium battery pack provides portability. Sounds interesting? Construction details start on page 37.



**SATELLITE RECEIVING ANTENNA** being mounted on posts in authors' backyard. To find out what's being broadcast and the frequencies, turn to page 47.



**SAMPLE-AND-HOLD STEREO DECODING** circuit is just one of the new circuits manufacturers are using for increased FM tuner performance. To find out what the circuits look like and how they work, turn to page 57.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Controlled Circulation Postage Paid at Concord, NH. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98. Other countries, \$14.98. Single copies \$1.25. © 1979 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A. (ISSN 0033-7862)

**Subscription Service:** Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

# looking ahead

**9-hour VCR?** Things have changed in just 30 days' time. Last month, the Beta group announced that they had finally overtaken the VHS group in recording time per cassette, by means of a third (slower) speed and a cassette containing more tape. This combination provides five hours, as compared with four hours for the longest recording per cassette with the VHS system.

The VHS camp lost no time in adding a third speed of its own, which it calls "super long play" or SLP. Like Beta's new speed, this is one-third slower than the previous slowest tape movement in this format. Thus, VHS recorders push recording duration to six hours on the same cassette that will record for two hours on the original speed and four hours on the LP speed. But one technique employed by the Beta group is yet to be tried by VHS—longer and thinner tape. This is currently under development, however, and could expand the recording time to nine hours per cassette.

The first super-long-play VHS recorder will be a Matsushita-built programmable machine to be offered by RCA, but the third speed is expected to be added eventually to all VHS brands. Among other new VCR's is a Betamax by Sony, and a similar unit from Zenith, that offer stop motion, visible rewind and visible fast-forward (the latter function valuable for speeding through commercials without missing any of the program), all controlled from a wired remote control panel.

**TV for the deaf:** A government-sponsored "closed-captioning" project is designed to make television more meaningful for America's 14 million hearing-impaired citizens. The system approved by the FCC uses one line of the vertical blanking interval, doesn't affect the picture seen by those viewing in the normal way, but superimposes a caption on the screen of those using special decoders. The Public Broadcasting System will supply 10 hours of programming weekly, ABC and NBC will supply five hours each to a new nonprofit National Captioning Institute that will encode the broadcast material for captions. The captioning decoders, using a Texas Instruments IC, initially will be manufactured by Sanyo Manufacturing Co. in Forrest City, AK. Decoders will be sold by Sears Roebuck next year at \$225 to \$250 and 19-inch color sets with built-in decoding capability will retail at about \$500. The National Captioning Institute will be supported by captioning fees paid by the networks and an eight-dollar royalty on each decoder or decoder-equipped TV set. CBS has declined to join the other networks in using the captioning system because it believes captioning should be but one of the features of a more all-inclusive teletext system. The other networks agree that teletext systems can accomplish more and conserve vertical-interval space, but say it could be many years before such services are available, while captioning can start early next year. They also argue that teletext decoders will be far more expensive than simple captioning attachments.

**Farewell to dots:** The phosphor dots and delta guns that were important parts of the first practical color TV tube, as

introduced by RCA 25 years ago, will fade into history before the end of this year. Tube makers are now phasing out the last of these tubes in favor of slot-mask tubes with in-line electron guns. In the latter, instead of phosphor dots there are strips of colored phosphors. Europe and Japan have already switched over, and in the U.S. the change is almost complete. Manufacture of delta-gun tubes will be confined to the replacement market.

Slot-mask in-line-gun tubes simplify the TV set manufacturing process and are more reliable because they eliminate most convergence adjustments. Until recently, their use was principally confined to small-screen tubes because of resolution problems involved in their use in larger tubes. But new electron gun designs have increased the resolution to the point where it is claimed to be better than that of delta-gun tubes. The new tubes in 19- and 25-inch sizes generally employ 100-degree deflection, which also helps increase resolution and makes the set about two inches slimmer from front to back. Most manufacturers are expected to change over their entire large-screen lines to 100-degree deflection.

**Computers & games:** Consumer logic and data-storage devices keep getting more sophisticated. Although computers as such have failed to catch on with the general non-sophisticated public, there's no doubt they will when somebody finds the correct formula. Mighty Texas Instruments is betting that it has that formula, although it hasn't yet announced what it is—only that it will have a home computer TV attachment for under \$500 with color graphics and a 16-bit MPU.

Semi-computers and video games *have* caught on, though, and their sophistication grows every day. Portable storage and retrieval devices—such as the language translators by Craig and Lexicon—are being snapped up almost as fast as they can be made. Now Texas Instruments has come up with its own version, a *talking* language translator which gets the accent right every time. It has combined a translator with a voice synthesizer. You merely punch in the word in English, and the translation comes out the loudspeaker while the proper spelling is displayed. The handheld unit accommodates modules containing 1,000-words, of which half the words can be pronounced by the unit, all of them displayed. English and Spanish modules (150 each) are scheduled for marketing in September, along with the under-\$500 translator, with French, German, Japanese and Chinese modules due later.

A video game that is programmed by cable TV is the new "Playcable" by Mattel and Jerrold, which will be tested by four CATV systems. Two-way cable systems aren't required. For \$50, an "emulator" cartridge is inserted into the standard Mattel video game, the user selecting the program he wishes from a catalog of 20 to 40 games stored in the cable system's head-end computer—for a monthly fee. After the initial games are tried, computer programs are expected to become available.


**DAVID LACHENBRUCH**  
CONTRIBUTING EDITOR



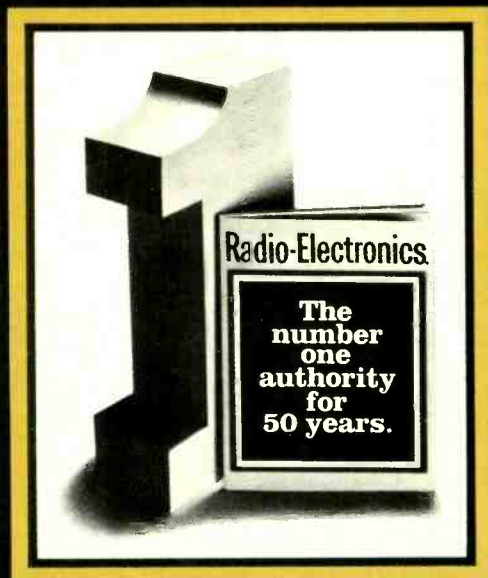**On your newsstand September 18...**

**the single most  
exciting issue of any  
electronics magazine  
in the  
Twentieth Century..**

**October 1979  
Radio-Electronics®  
50<sup>th</sup>  
Anniversary Issue**



From "Radio-Craft" in 1929 to Radio-Electronics today, and tomorrow, from the vacuum tube to the chip, from "wireless radio" to interplanetary communication—it's fifty years of history, experiments, and excitement from the pages of America's greatest newsstand electronics magazine, all in the most spectacular issue ever of any electronics magazine—October, 1979 Radio-Electronics.

Don't miss a word of this colorful, extra-special retrospective issue, bursting with all the excitement of all those years—or of our experts' fascinating projections and predictions for "The Next Fifty Years" of our lives.

It's October Radio-Electronics. On your newsstand September 18 ... but not for long. Don't miss it.

# editorial

## What's Special About Radio-Electronics?

I was asked that question recently by a prospective reader. It's a simple question; a good one and it requires much more than just a simple response.

The answer starts off simply enough—**Everything!**

But that's only the start. Let's look at the issue you are now reading. There are six major articles. They range from a full-blown detailed story on how you can build your own 4½-digit precision DMM, to a newsbreaking article on tuning in television satellites to a how-to story on wiring systems to use when building projects. There are also a variety of features including an article on new FM tuner circuits, two R.E.A.L. Sound reports and numerous columns, equipment reports and product previews.

All of the material in this issue was carefully selected with your specific interests in mind. There is a variety of material because you have a variety of interests. Sure, some will like one article more than another and all of you may find some particular story that doesn't appeal to you at all. But what has been done is to put together a package of information deliberately designed to keep you up to date on what is happening in our industry.

When the computer came along, Radio-Electronics presented the first article to ever tell readers how to build one for themselves. When the Videodisc was announced, Radio-Electronics presented a group of three articles to show how the player works. When flat-screen or 3-D color TV comes along we'll tell you about that too.

In this issue, our story on Satellite TV Reception is a first. The satellites have been there for quite some time. Now you will discover just what is being broadcast, how it is being broadcast; and in the next few months, how you can tune in on these broadcasts—direct from space to your home.

That's the kind of magic that makes Radio-Electronics special. That's how we have kept Radio-Electronics special and young and growing. That's why in October 1979 we will celebrate 50 years of publication; 50 years of new events and happenings; 50 years of excitement in a never-dull field. That's why we are special and that's why we will continue to be special.

We don't promise to make all of our readers happy all of the time. We do promise to deliver the best and most authoritative electronics magazine you can purchase.

  
**LARRY STECKLER**  
Editor

## Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, KTX-3644, CET, editor

Arthur Kleiman, KTZ-3288,  
managing editor

Robert F. Scott, CET, W2PWG,  
KXK-8533, technical editor

Jack Darr, CET service editor

Leonard Feldman  
contributing high-fidelity editor

Karl Savon, semiconductor editor

Herb Freidman, communications editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Ruby Yee, production manager

Robert A. W. Lowndes, production  
associate

Marie J. Stolli, production assistant

Gabriele Margules, circulation director

Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen  
Cover photo by Walter Herstatt

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.  
200 Park Ave. S., New York, NY 10003  
(212) 777-6400  
President: M. Harvey Gernsback  
Vice President: Larry Steckler  
Treasurer: Carol A. Gernsback  
Secretary: Bertina Baer

### ADVERTISING SALES

Paul McGinnis  
Director of Marketing

### EAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
(212) 777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
The Ralph Bergen Co.  
540 Frontage Road—Suite 361-A  
Northfield, Illinois 60093  
(312) 446-1444

### PACIFIC COAST Mountain States

Jay Eisenberg  
J.E. Publishers Representative Co.,  
8732 Sunset Blvd.,  
4th Floor,  
Los Angeles, CA 90069  
(213) 659-3810  
Sales Mart Building  
1485 Bayshore Blvd., Box 140  
San Francisco, CA 94124  
(415) 467-0125





# DATA PRECISION Model 935 DIGITAL MULTIMETER

## \$149



- **ACCURATE** — basic 0.1% DC accuracy — better than that of many bench/lab DMM's.

- **VERSATILE** — all the functions and ranges you need...29 in all: volts & amps, AC & DC switchable HI & Lo ohms.

- **ECONOMICAL** — operates up to 200 hours on a standard 9V alkaline battery.

- **TOUGH** — built to take rough everyday field usage and electrical overload... yet maintain its calibration.

- **HANDY** — easy to hold, to carry, to use, to read...

- **RELIABLE** — backed by a full 2-year warranty.

**ALSO AVAILABLE —**  
**Model 938**

**0.1 • 3½-digit CAPACITANCE METER,**  
**only \$149. Ask for details.**

**Order Toll-Free: Call 800-223-0474**

### BASIC SPECIFICATIONS

- 24 Measurement Ranges:
- 100μV—1000VDC, 5 ranges, ±0.1% Accuracy
- 100μV—700VAC, 5 ranges, ±0.5% Accuracy
- 1μA—2A DC, 4 ranges, ±0.5% Accuracy
- 1μA—2A AC, 4 ranges, ±0.75% Accuracy
- 100mΩ—20MΩ, 6 ranges, 0.1—0.3% Accuracy
- 3½-Digit, ½" Liquid-Crystal Readout
- Automatic Polarity Indication
- Automatic Overload Indication
- Automatic Low-Battery Indication
- Optional Battery Eliminator Available, for 120VAC ±10%, 50—60Hz line operation
- 6¼"L. x 3½"W. x 1½"H. Weighs 11 oz.

**CIRCLE 63 ON FREE INFORMATION CARD**

**ADVANCE  
ELECTRONICS**

54 W. 45th Street, New York, N.Y. 10036, (212) 687-2224

PLEASE SEND ME:

- ☐ Model 935 DMM @ \$149.00
- ☐ CS11 20-amp Current Shunt @ \$20.00
- ☐ CC35 Vinyl Carrying Case @ \$7.00
- ☐ BE9 Battery Eliminator (120VAC, 50—60Hz) @ \$15.00

Payment Enclosed ☐ Bill my: Master Charge ☐ Visa ☐  
Add \$3.00 to cover postage and handling. N.Y. residents add sales tax.

Account # \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City, State, Zip \_\_\_\_\_



RE-8

**New from NRI!**  
**25" color TV that tunes**  
DIAGONAL  
**by computer, programs**  
**an entire evening's**  
**entertainment.**

Just part of NRI's training in  
servicing TV, stereo systems, video  
tape and disc players, car  
and portable radios.





Only NRI home training prepares you so thoroughly for the next great leap forward in TV and audio...digital systems. Already, top-of-the-line TV's feature digital tuning, computer programming is appearing, and new digital audio recording equipment is about to go on the market.

NRI is the only home study school to give you the actual "hands-on" training you need to handle servicing problems on tomorrow's electronic equipment. Because only NRI includes this designed-for-learning, 25" diagonal color TV with electronic tuning, built-in digital clock, and computer programmer as part of your training. With this advanced feature, you can pre-program an entire evening's entertainment... even key lock it in to control children's viewing.

As you assemble it, you learn how digital tuning systems work, how to adjust and service them. You work with the same advanced features used in the new programmable TV's and video tape recorders. It's exclusive NRI training that keeps you up with the leading edge of technology.

### **Exclusive Designed-for- learning Concept**

The color TV you build as part of NRI's Master Course looks, operates, and performs like the very finest commercial sets. But behind that pretty picture is a unique designed-for-learning chassis...



the only such unit in the world. Rather than retrofit lessons to a hobby kit or an already-built commercial set, NRI instructor/engineers have designed this television so each step of construction is a learning experience.

As you build it, you perform meaningful experiments. You see what makes each circuit work, what it does, how it interacts with other circuits. You even introduce defects, troubleshoot and correct them as you would in actual practice. And you end up with a magnificent, big-picture TV with advanced features. One you can sell or use in your home.

### **Also Build Stereo, Test Instruments**

That's just a start. You demonstrate basic principles and circuits on the unique NRI Discovery Lab®, then apply them as you assemble a fine AM/FM stereo receiver, complete with speakers. You also get practical experience as you build your own test instruments, including a 5" triggered sweep oscilloscope, CMOS digital frequency counter, color bar generator, and transistorized volt-ohm meter. Use them for learning, use them for earning as a full- or part-time TV, audio, and video systems technician.

### **Complete, Effective Training Includes Video Systems**

Using NRI's exclusive methods, you learn far more than TV servicing. You'll be prepared to work with stereo systems, car radios, record and tape players, transistor radios, short-wave receivers, PA systems, musical instrument amplifiers, electronic TV games, even video tape recorders and tape or disc

video players. Your training covers just about every kind of electronic entertainment equipment available now or in the near future.

And because NRI has unmatched experience gained in over 60 years and a million students worth of training, your course is designed for ease of learning and practical utility. You need no previous experience of any kind. Starting with the basics, exclusive "bite-size" lessons cover subjects thoroughly, clearly, and concisely. "Hands-on" experiments reinforce theory for better comprehension and retention. And your personal NRI instructor is always available for consultation, ready with explanations, answers, and advice.

### **Send for Free Detailed Catalog... No Salesman Will Call**

Get all the facts on this exciting course and its potential for you by mailing the postage-paid card today. Our free 100-page catalog includes color photos of all kits and equipment, complete lesson plans, convenient time payment plans, and information on other electronics courses. You'll also find out about NRI's new Computer Technology Course that includes your personal



microcomputer. Or Complete Communications with 2-meter transceiver that gets you ready for opportunities in broadcasting, 2-way radio, microwave, and other growing fields. If card has been removed, write to:



**NRI Schools**  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Ave.  
Washington, D.C. 20016

# letters

## 3 UNIQUE PROJECTS

The "3 Unique Projects" article (April 1979 issue, page 48) has been a godsend.

We built two of the One-Station Intercoms and installed them in Sales and Engineering; communications between the two are now on an order of magnitude better than before! The next two we build will go to Production and Quality.

Our Engineering Director has been complaining that he doesn't get "hands-on" duties since his promotion, so we gave him the Solar-Powered Night Light to debug: A glitch you failed to notice is the unit's behavior in semidarkness—when the lamp light reflects from our receptionist's jewelry onto the solar cells, which in turn increases drive to the lamp, etc. This feedback ultimately results in broadband oscillations centered just below  $10^{15}$  Hz. Our Engineering Director solved the problem by replacing the lamp with one of National's Dark-Emitting Arsenide Diodes (DEAD's).

Finally, the Single-Shot Logic Indicator

with Memory ended our long search for a readout device for Signetics' 25120 Write-Only Memory (WOM). Due to the WOM's unique architecture (all inputs are wired-don't-care), we've had trouble remembering if we had loaded a given IC with the program, and if so, with *which* program. The Logic Indicator worked so well in this application, it's no exaggeration so say it left us with stars in our eyes.

DOUG PRUNER  
Genisco Technology  
Compton, CA

I have been a subscriber to **Radio-Electronics** since 1956. I received my April issue and, with trepidation derived from past experience, examined the index, and was immediately drawn to the construction articles on pages 48 and 49.

I think the authors of these articles should be admonished on two counts:

1. They failed to emphasize the main outstanding feature of the One Station In-

tercom—its portability over all other systems.

2. The Solar-Powered Night Light would be a great boon on polar expeditions. With suitable modifications to maintain orientation, it should operate at full brilliance for six months at zero degrees, north or south latitude. The cells should be oriented to the noon sun and the light 180 degrees away, illuminating the midnight area.

I will not construct the Logic Indicator as searching for logic in this day and age is an exercise in futility.

JOHN MOON  
Brossard, Canada

The Solar-Powered Night Light in the April 1979 article contains a philosophical error, which I figured out as soon as I built it. Those charlatans, Weinstein and Gartman, don't *really* care about energy conservation. That's why the lamp runs wastefully all the time even when it is not needed.

*continued on page 14*

# Now, an automotive computer plus cruise control at your fingertips!

This is CompuCruise! The first true computer for your car, truck or RV. It's the most effective and functional cruise control ever designed, PLUS complete trip computing, an efficient fuel management system, and a split-second-accuracy quartz time system.

CompuCruise is a cruise control with a memory. A unique seek-and-hold capability makes highway driving easier and more enjoyable. Fully electronic, making it more accurate and reliable.

CompuCruise is a true computer, constantly reacting via automatic sensors to changing conditions, updating vital data for you every second. Just look at what CompuCruise gives you:

- Time, E. T. Lap timing, Alarm
- Time, Distance, Fuel to arrival
- Time, Distance, Fuel to empty
- Time, Distance fuel on trip
- Current or average MPH, MPG, GPH
- Fuel used, Distance since fillup
- Inside, outside or coolant temp.
- Battery voltage
- English or Metric display

CompuCruise works on foreign or American cars (except Diesel and fuel-injected vehicles). It's priced for the budget-minded, and easily installable by you or your automotive outlet.

Only \$199.95 with Cruise Control, \$159.50 without. Fully warranted for 90 days from date of purchase. Delivered

complete with easy-to-follow installation guide. And backed by a 100% satisfaction guarantee. If not fully satisfied when you receive your unit, return it before installation and your money will be fully refunded without question.

For the name of your nearest dealer, call or write us right now: ZEMCO, 12907 Alcosta Blvd., San Ramon, CA 94583. Phone (415) 838-8060.

Do it today—for a better cruise control and more automotive information than you've ever had before.



## COMPUCRUISE





# Build better value with world-famous Heathkit Electronic Products

**SEND FOR YOUR NEW**

# FREE HEATHKIT® CATALOG

Read about the world's largest selection of fun-to-build, money-saving electronic kits – plus educational programs so effective they're guaranteed!

Every Heathkit product is quality designed and engineered, and gives you extra value because you build it yourself. Our world-famous instruction manuals take you step-by-step from unpacking the kit to final plug-in. They're marvels of technical accuracy and thoroughness. Find out about the pride, satisfaction and savings you can get by building your own electronic kits. Send for your catalog today!



**NEW! One-Button Dialer**  
Real convenience for any telephone.

**NEW! DC to 5MHz Oscilloscope**  
Low-priced scope great for TV service.

**NEW! Auto-Ranging Digital Multimeter**  
Automatically selects proper range for best measurements.

**NEW! All-In-One Computer System**  
Desktop computer with Terminal, Floppy Disk, and Keyboard in one compact unit.

**NEW! Deluxe Metal Locator**  
Adjustable discrimination for finding any kind of metal.

**NEW! Low-Priced Multimeter**  
Great for hobbyist or service bench.

**NEW! CW Transmitter**  
Deluxe transmitter with famous Heath value.

**NEW! X-Y Chart Recorder**  
Two channels for comparison plotting.

If coupon is missing, write:  
Heath Company, Dept. 020-560 Benton Harbor, MI 49022

Heathkit products are displayed, sold and serviced coast-to-coast at Heathkit Electronic Centers (Units of Schlumberger Products Corporation). See the white pages of your phone book.

Nearly 400 quality electronic kits including:

• Hobby and Business Computers • Color TV • Stereo Components • Test Instruments • Amateur Radio Gear • Metal Locators • Automotive Instruments • Marine Gear and Accessories • Aircraft Instrumentation • Home Convenience Items • Security • R/C Modeling Equipment • Clocks • Weather Instruments • Tools... and much more

**Send for it TODAY**

HEATH  
Schlumberger

Heath Company, Dept. 020-560  
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.  
I am not currently receiving catalogs.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

CL-708 Zip \_\_\_\_\_

**FREE  
CATALOG!**

CIRCLE 100 ON FREE INFORMATION CARD

## LETTERS

continued from page 12

So I added an ON-OFF switch in series with the circuit (at the risk of increasing circuit complexity and operating-procedure confusion). I refrained from the temptation to use a momentary-on pushbutton switch as that would increase the number of on-off surges and lead to short bulb life. This disadvantage would offset the automatic-off mode's advantages.

The ON-OFF switch is also essential in case of extreme positive feedback from the lamp output back to the cells, which could happen if you carried the night light into a well-mirrored bathroom, for example. Turning the switch promptly OFF can prevent the

familiar motorboating condition or the dread runaway situation.

By the way, I was able to increase the usefulness of the night light by simply connecting about 10,000 miles of twisted pair in the circuit. Just put the solar cells either east or west of the lamp location.

ROBERT A. PEASE  
Transtronics  
San Francisco, CA

## VIDEODISC SYSTEMS

Regarding the article that appeared in the April 1979 issue on the competing Magnavox and RCA videodisc systems, there are several points that should be made. No matter how biased my statements may sound, I am *not* professionally connected with any companies involved in

promoting either system, although I do own and enjoy a Magnavox optical videodisc player and an assortment of the programs.

The author makes the point that several Japanese manufacturers (Panasonic and JVC) have already joined RCA in promoting the capacitive format. This has not yet occurred; and the JVC Visc system has so many obvious advantages over RCA's approach that if there is to be any standardization between these three companies, it may well be that RCA will join them.

Also, while the article states that these companies are at least talking with RCA about standardization, no mention is made of the fact that there is presently a partnership between MCA and Pioneer Electronics (under the name of Universal-Pioneer) to market optical videodisc players, and that General Motors has already placed an order for a *minimum* of 7000 players from the new company.

Although the article points out that due to the laser scanning of the MCA discs there is no deterioration from repeated playing, it does not tell us that with the RCA capacitive design, the discs wear out after about 200 plays and that the stylus that tracks RCA's grooves must be replaced after (approximately) 300 hours of use.

The paragraph that states that MCA is supplying the discs for the optical system reads as if MCA is the only source of feature movies. It is true that MCA is the only manufacturer of the discs; however, the initial program catalog includes feature films licensed to MCA from other studios, including Paramount, Disney and Warner Brothers.

ALFRED W. MYERS  
White Plains, NY

## EXPERIMENTERS' GROUP

I am a longtime reader and subscriber to your magazine, and it goes without saying that I like it very much. The articles give a very rounded insight into many aspects of electronics.

Being an experimenter by nature, I have felt there was a need for an organization to bring amateur scientists together. Now that need has been filled—the Amateur Scientists Research Organization has been formed. Interested persons can find out more by writing to ASRO, P. O. Box 4, McMechen, WV 26040. The latest newsletter and bulletin will be sent free with no obligation.

RICHARD S. MEYER  
McMechen, WV

## ON-SCREEN DIGITAL CLOCK

This is in reply to J. G. Ash's letter in the March 1979 issue regarding construction of the on-screen digital clock (July 1977 issue).

It appears to me that if S1 is held down longer than the C9-R13 time constant, the clock will be permanently on. This is because when S1 is initially closed, a ground is applied not only to pins 4 and 5 of IC2-b, but also to the negative side of C8. This will cause C8 to charge more or less instantly to pin 3's level, which is now going low. After C9 charges (from 4 to 6 seconds), current ceases to flow through R13, causing pins 1 and 2 to go low and pin 3 to go high. At this point, if S1 is still depressed,

continued on page 16



# The DMM you've wanted: Quality and performance at a low, low cost

**A surprisingly low \$69.95.** Surprising because you get the type of performance you've wanted but expected to pay much more for.

## Quality, Performance and Accuracy

The 2010A offers you long-term accuracy with a laser-trimmed resistor network, a stable bandgap reference element, and single-chip LSI circuitry. With 31 ranges and 6 functions, you can measure AC or DC volts from 100  $\mu$ V to 1000V; AC and DC current from 0.1  $\mu$ A all the way to 10 A; resistance from 0.1  $\Omega$  to 20 M $\Omega$ . Typical DCV and Ohms accuracy is 0.1%  $\pm$  1 digit. Easy-to-read 3 1/2 digit LED's with 9mm numerals and automatic decimal point.

## Extra features for greater convenience and flexibility

- Unique X10 multiplier switch gives you convenient selection of the next higher decade. Hi-Low Power Ohms capability gives you three high-ohm ranges that supply enough voltage to turn on a semiconductor junction. You use the three low-ohm ranges for in-circuit resistance measurements.

- Wide Frequency Response: 40 Hz to 40 kHz bandwidth lets you measure audio through ultrasonic AC signals.

- Touch-and-Hold Capability (with optional probe) lets you hold readings as long as you wish so you can make measurements in hard-to-reach places without taking your eyes off the probe tip.

- And More: automatic polarity and zeroing; overrange indication; overload protection on all ranges.

This compact unit is powered by 4 "C" cells (not included) so that you can take your lab-quality benchtop unit anywhere with you.

## Kit or Factory-Assembled

Either is a tremendous value. Complete kit only \$69.95; assemble it yourself with our easy-to-follow instructions. Or, for only \$99.50, Sabtronics will ship your 2010A factory-assembled and calibrated.

Whether you're a professional or a hobbyist (or both!): When quality, accuracy, and price count, you should check out the 2010A DMM for yourself. Order one today for a full 10 days to inspect it; if you're not completely satisfied, merely return it in its original condition for a prompt and courteous refund of purchase price. Call with your Master Charge or Visa number or write the address below.

**2010A Kit: \$69.95 (plus \$4.00 S&H)**

**2010A Assembled: \$99.50 (plus \$4.00 S&H)**

**NC-115 Adaptor: \$7.50**

**NB-120 Nickel Cadmium Batteries: \$17.00**

**THP-20 Touch and Hold Probe: \$18.00**

Making Performance Affordable

**sabtronics**   
INTERNATIONAL INC.

13426 Floyd Circle M/S 35 Dallas, Texas 75243  
Telephone 214/783-0994




# Jim-pak<sup>®</sup>

electronic components

## One-Stop Component Center

### EXCITING NEW KITS!!

#### Regulated Power Supply

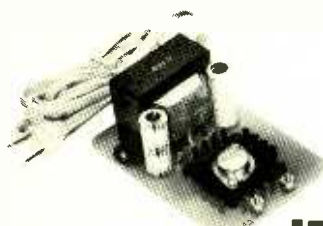

- ★ Uses LM 309K
- ★ Heat sink provided
- ★ P.C. board construction
- ★ Provides a solid 1 amp @ 5V
- ★ Includes components, hardware and instructions
- ★ Size: 3-1/2" x 5" x 2" high

**JE200 5v 1amp**

#### 4-Digit Clock Kit



**JE730**

- ★ Bright .357" ht. red display
- ★ Sequential flashing colon
- ★ 12 or 24 hour operation
- ★ Extruded aluminum case (black)
- ★ Pressure switches for hours, minutes and hold functions
- ★ Includes all components case and wall transformer
- ★ Size: 3-1/4" x 1-3/4" x 1-1/4"

#### Function Generator Kit



- ★ Provides 3 basic waveforms: sine, triangle & square wave
- ★ Frequency range from 1 Hz to 100K Hz
- ★ Output amplitude from 0-volts to over 6 volts (peak to peak)
- ★ Uses a 12V supply or a  $\pm 6V$  split supply
- ★ Includes chip, P.C. board, components and instructions.

**JE2206B**

#### NOW!!! OVER 300 AUTHORIZED DISTRIBUTORS... HERE'S JUST A SAMPLING:

ALABAMA Mobile ALASKA Anchorage ARIZONA Yuma CALIFORNIA Beaumont Berkeley Mission Viejo Monterey Oceanside Palo Alto Pasadena Sacramento San Carlos San Diego San Fernando San Francisco San Jose San Luis Obispo Santa Ana Santa Cruz Santa Maria Santa Monica Suisun City Sunnyvale Vallejo Walnut Creek COLORADO Aurora CONNECTICUT Bridgeport FLORIDA Ft. Lauderdale GEORGIA Atlanta HAWAII Honolulu IDAHO Idaho Falls ILLINOIS Evanston Evanston Groveland Mount Prospect	Lafayette Radio Electronics TV Mart Yuma Electronics Earl's Hobby Shop Al Lasher Electronics Tower Electronics Corp. Zackit Electronic Center Dow Radio Inc. Heathkit Electronic Center Zackit J & H Outlet Store Radio Shack A.S.C. Mira Mesa San Fernando Electronics Zack Electronics United Radio & TV Supply Mid-State Electronic Supply Quality Electronics Santa Cruz Electronics Caps Electronics Mission Control Byte Shop Sunnyvale Electronics Zackit Byte Shop of Walnut Creek Com Co Electronics Bridgeport Computer Computers For You Atlanta Computer Mart Integrated Circuit Supply Audiotronics Itty Bitty Machine Co. Tri-State Electronic Corp. Moyer Electronics Tri-State Electronic Corp.	ILLINOIS (Continued) Oak Park Rockford Schaumburg INDIANA East Chicago IOWA Indianola KANSAS Wichita KENTUCKY Lexington LOUISIANA Baton Rouge Houma Metairie MARYLAND Churchville Damascus La Vale Rockville Rockville Towson MASSACHUSETTS Pittsfield Waltham Worcester MICHIGAN Clawson Detroit Flint Lansing Midland Mt. Clemens Niles MINNESOTA Duluth Hopkins St. Paul MISSOURI El Dorado Springs MONTANA Billings BOZEMAN NEBRASKA Lincoln Lincoln	Specronics Inc. Imperial Computer Systems Data Domain Acro Electronics Corp. Electronix Limited Amateur Radio Equipment Company Radio-Electronic Equipment Co. Pelican Electronics Pelican Electronics Pelican Electronics Churchville Electronics Damascus CB J & M Electronics Computer Workshop Heathkit Electronic Center Bayview Electronics Inc. Heathkit Electronic Center Pittsfield Radio Co. Inc. Computer Mart Inc. RM Electronics Inc. Radio Supply & Engineering Heathkit Electronic Center Hobby Electronic Center Fulton Radio Supply Co. Computronix Corp. The Computer Store Niles Radio Supply Northwest Radio of Duluth Heathkit Electronic Center Heathkit Electronic Center Beckman Electronics Conley Radio Supply Electronic Service & Dist. Altair Computer Center Scott Electronic Supply Inc.	NEBRASKA (Continued) Omaha Omaha NEVADA Las Vegas NEW JERSEY Bricktown Cherry Hill Pompton Lake Ramsey NEW MEXICO Las Cruces NEW YORK Endwell Kingston New York Troy Ulva NORTH CAROLINA Boone Durham Greensboro Raleigh NORTH DAKOTA Fargo OHIO Bucyrus Cincinnati Columbus Dayton Reynoldsburg OKLAHOMA Oklahoma City OREGON Albany Coos Bay Portland Salem PENNSYLVANIA Hershey Pittsburgh RHODE ISLAND Cranston Pawtucket TENNESSEE Chattanooga Clarksville Cookeville	Heathkit Electronic Center Omaha Computer Store Century 23 Radio Shack Associate Store The Computer Emporium Computer Corner of New Jersey Typetronic Computer Store Mannie's Electronic Supply Computer Tree Inc. Greylock Electronics Computer Mart of New York Trojan Electronics Am-Com Electronics Alpha Digital Systems Futureworld Byte Shop Byte Shop of Raleigh The Computer Company Mead Electronics Heathkit Electronic Center Heathkit Electronic Center Altair Computer Center Universal Amateur Radio Bits, Bytes & Micros Oregon Ham Sales Herrick Electronics Portland Radio Supply Computer Pathways Microcomputer Systems Inc. Heathkit Electronic Center G.Y.C. Company Jabbour Electronics City Jabbour Electronics City William's Data Comp Div. Mastronics Wagon's Stereo Center	TENNESSEE (Continued) Knoxville Nashville TEXAS Amarillo Dallas Houston Houston Houston San Antonio UTAH Midvale Provo VIRGINIA Alexandria Alexandria Charlottesville Hampton Norfolk Richmond Roanoke Virginia Beach WASHINGTON Longview Moses Lake Pasco Seattle Seattle Seattle Spokane Tacoma WEST VIRGINIA Morgantown Wheeling WISCONSIN West Allis CANADA Alberta (Calgary) Ontario (Willowdale) Quebec (Montreal) ENGLAND Berkshire GUAM PANAMA Panama City SINGAPORE	Byte Shop Electra Distributing Co. Computer Encounters Inc. CompuShop Altair Computer Center CompuShop Interactive Computers Sherman Electronics Supply Inc. Heathkit Electronic Center Alpine Electronic Supply Co. Computer Hardware Store Heathkit Electronic Center Lafayette Radio Lafayette Radio Avec Electronics Corp. Avec Electronics Corp. The Computer Place Heathkit Electronic Center Progress Electronics Ron's Electronics Riverview Electronics Amateur Radio Supply C-Com Empire Electronics Personal Computers C & G Electronics Electro Distributing Co. Lafayette Radio Olson Electronics The Computer Shop Home Computer Centre Wang's Microcenter NewBear Computing Store Marianas Electronics Sonitel, S.A. Inter-trade (PTE) Ltd.
---	--	--	---	---	--	---	---

ASK YOUR ELECTRONICS STORE TO STOCK JIM-PAK<sup>®</sup> TODAY!!

JIM-PAK<sup>®</sup> • 1021 HOWARD AVENUE, SAN CARLOS, CALIFORNIA 94070 • (415) 592-8097

## LETTERS

continued from page 14

C8 will charge instantly to this new level and will stay there even if S1 is released. We now have a stable state and the clock will stay on indefinitely.

My solution was to place an SPST toggle switch in parallel with C9. Closing the switch and activating S1 will cause the clock to stay on indefinitely (for setting purposes). After the clock is set, open the switch and the display will turn off after 4 to 6 seconds. I call this switch "Display Hold" on my clock.

D. A. TABBUTT  
Las Vegas, NV

### BURGLAR ALARM FLAW

Several years ago I built and installed a burglar alarm from an article in **Radio-Electronics** ("Anti-Theft Devices," R.M. Marston, November, December 1976). The circuit was ingenious and worked well—so well that I later built several for friends. But recently I discovered a basic and serious flaw in this design that applies to any other circuits using CMOS gates as sensitive switches.

The circuit takes advantage of the very high input impedance of CMOS gates, in order to use the series loop of normally closed switches with very low standby current. The switches are in series with a 22-megohm resistor. If all switches are closed, the input to the gate is pulled high; if any switch opens, the 22-megohm resistor pulls

the input low, triggering the alarm.

The system I installed in my apartment uses conventional magnetic reed switches with exposed screw terminals. The apartment was painted recently by a sloppy housepainter using water-based latex paint. Several days afterward, quite by accident I discovered the alarm would not trigger if a particular door was opened.

A careful investigation revealed some paint had been slopped over the screw terminals of the reed switch. While the top surface of the paint was dry and measured infinite resistance, the underside of the peeled-off chip was evidently still damp and showed a series resistance of only 300K across the 1-inch span between terminals.

Since this 300K resistance was shunting the open switch, the alarm system interpreted it as a closed door. I don't know how long it would take for the paint to dry enough to increase its resistance to the 30 megohms or so that would be required to allow the circuit to function normally.

But this suggests a more serious problem. Any moisture across the screw terminals would shunt the open switch to the point where the circuit would not trigger! Readers who have installed alarms using this circuit should be warned to do one of two things:

1. Decrease the value of the pulldown resistor from 22 megohms to no more than 50K. Unfortunately, this will increase standby current to about 250  $\mu$ A, but it will prevent dampness and condensation from defeating the system. OR . . .

2. Paint, spray or otherwise completely insulate the terminals on all sensor switches with a non-water-based paint or lacquer to prevent them from being shunted by moisture.

ROBERT R. LEVINE  
New York, NY

### CB REPAIR INFO WANTED

Your Jack Darr service format is one of the finest columns in any electronics magazine. I have been using the column for years in my TV servicing and have found many service troubles, thanks to Mr. Darr.

Now I have branched off into CB repair, and the same type of service format would be very useful. You definitely don't have enough information (in some months, none at all) or articles regarding CB's. I would think there would be more readers interested in CB's than in microprocessors, etc. Please stick more with the items the consumer on the street is likely to have.

CHET WHEELER  
Bethlehem, PA

### FUTURE DEVICES

Your April 1979 editorial was a well-produced mini-history lesson that many have probably taken for granted. Concerning the last paragraph about future products, I would probably not be able to fill the bill on dreaming; however, since you did ask:

I have been visualizing the day when our energy problems could be reduced to perhaps 10% of what they are now. To help this

continued on page 22

## Exclusive Sheldahl FLEXSWITCH® kits

With scissors, modify the .030 thick, non-tactile panel into water/dust resistant switching module. Kit includes design guidelines, instructions, Sheldahl membrane switching panel, flexcircuit connector, press-on nomenclature and RFQ checklist. Production quantities cost less. Pressure sensitive back.

9 key kit (1x9)  
**\$9.00**

16 key kit (4x4)  
**\$10.00**

Please send me ☐ 16 key kit(s) ☐ short to ground  
at \$10.00 each. ☐ crosspoint  
☐ 9 key kit(s) ☐ short to ground  
at \$9.00 each. ☐ crosspoint

I enclose a check or money order for my FLEXSWITCH kit order.

Name \_\_\_\_\_ Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



**Sheldahl**

Mail to:  
Sheldahl Electrical  
Products Division  
P.O. Box 170, Northfield, MN 55057

## THE BIG PLUS + Graphic Equalizer

ASSEMBLED  
**\$189.95**

KIT  
**\$99.95**



**LOADED with Quality Features!**

- Stereo . . . Eleven Bands Per Channel • Extremely Low Noise & Distortion • LED Peak Indicators • Center Detent ("flat") sliders • Built-in "record" Switching • Line and Microphone Level Inputs/Outputs • Regulated Power Supply • Fully Guaranteed • Horizontal or Vertical Cabinets • Kit or Fully Assembled • Plus Much, Much More!

**Absolutely equals or exceeds overall performance and features of any graphic equalizer made today!**

AARON-GAVIN INSTRUMENTS, INC.

17231 Coria Avenue

Tustin, California 92680

Yes! I've enclosed \$\_\_\_\_; RUSH me: ☐ assembled equalizers at \$189.95, p.p.d. ☐ cabinet ☐ send brochure  
☐ unassembled equalizer kits at \$99.95, p.p.d. ☐ Horizontal (flat) ☐ Vertical (up-right)  
California residents include 6% sales tax

Visa & Master Charge orders accepted

Name \_\_\_\_\_ Card No. \_\_\_\_\_  
Address \_\_\_\_\_ Exp. Date \_\_\_\_\_ Bank \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_ No. \_\_\_\_\_

Dealer inquiries invited

**CIRCLE 10 ON FREE INFORMATION CARD**



# sophisticated soldering of space-age heat- & voltage-sensitive components

DEMANDS THE RELIABILITY OF

## Weller® controlled output irons and stations

Modern, ultra-sophisticated electronic technology calls for totally dependable soldered connections. This requires not only sensing the soldering tip temperature, but applying and removing wattage at precisely the right moment to control the selected operating range of the iron.

That, in a nutshell, is what the Weller family of Controlled Output Soldering Equipment is all about. And that explains how it can avoid defects in soldered connections and damage to heat- and voltage-sensitive components and substrates, as well as deteriorating over-exposure from needlessly long soldering contact. In other words, dependence on the human element is eliminated. But there are other significant benefits from the Weller controlled output soldering technique. Soldering tips last longer. Much longer. And power consumption is less than that of uncontrolled irons.

What's the secret of Weller's controlled output? It's really no longer a secret. Today it's a time-proved principle: Closed loop, low voltage circuitry and a ferromagnetic sensor control temperature at a pre-selected range. Sounds simple? It is. That's why it's totally reliable!

Ready to meet the whole Weller Temperature Controlled family? This way, please for a brief introduction to the members presented below.

### LINE VOLTAGE PORTABLE IRONS

**Models W60 and W100:** 60 and 100 watts. Operate from 120V outlet. Interchangeable 600, 700, and 800°F tips, grounded and non-grounded. Available in 9 sizes. Optional de-soldering adaptor and non-heat-sinking tool holders.

### COMPLETE SOLDERING AND DE-SOLDERING STATIONS

Include iron holder, tip-wiping sponge and receptacle, power on-off switch with indicator light, stepdown transformer dropping power to 24V in heating element, positive tip-grounding to prevent build-up of electrostatic charges that injure delicate components, non-burnable silicone rubber cord, and dozens of other Weller quality features.

**Model WTCPN:** Plug-in pencil soldering iron with comfort-cool heat shield, 17 available styles and sizes of interchangeable tips for 600, 700, and 800°F temperature control, integral tip storage tray. 120V, 60Hz, 60W. Optional de-soldering adaptor.

**Model MP:** For precision soldering of miniaturized electronics, especially PC work. Plug-in, true pencil shape 650 or 750°F iron with 1/8" diam. tips available in 8 sizes and styles. 120V, 60/40Hz, 22W.

**Model DS100:** De-soldering and re-soldering unit designed for PC board repair and re-work lines. Utilizes interchangeable 600, 700, and 800°F soldering tips and interchangeable 700 or 800°F de-soldering heads. Complete with footswitch, twin safety tool holder, vacuum adjustment gauge, and cleanable, replaceable see-thru solder collector. 8 de-soldering tiptlet sizes and 17 soldering tip styles (in 3 temps) available. Operates from factory air and line voltage.

Yes, of course, the entire family is UL listed and OSHA compliant. Now that you've been introduced, any leading electronic distributor will display the units and fill you in on all the features. For technical information and consultation, write the factory on your company letterhead.

CIRCLE 13 ON FREE INFORMATION CARD




**The Cooper Group**  
**Electronics Division**

WELLER® • WISS® • XCELITE®

P.O. BOX 728, APEX, NORTH CAROLINA 27502, 919/362-7511

# **You gotta shop around.**

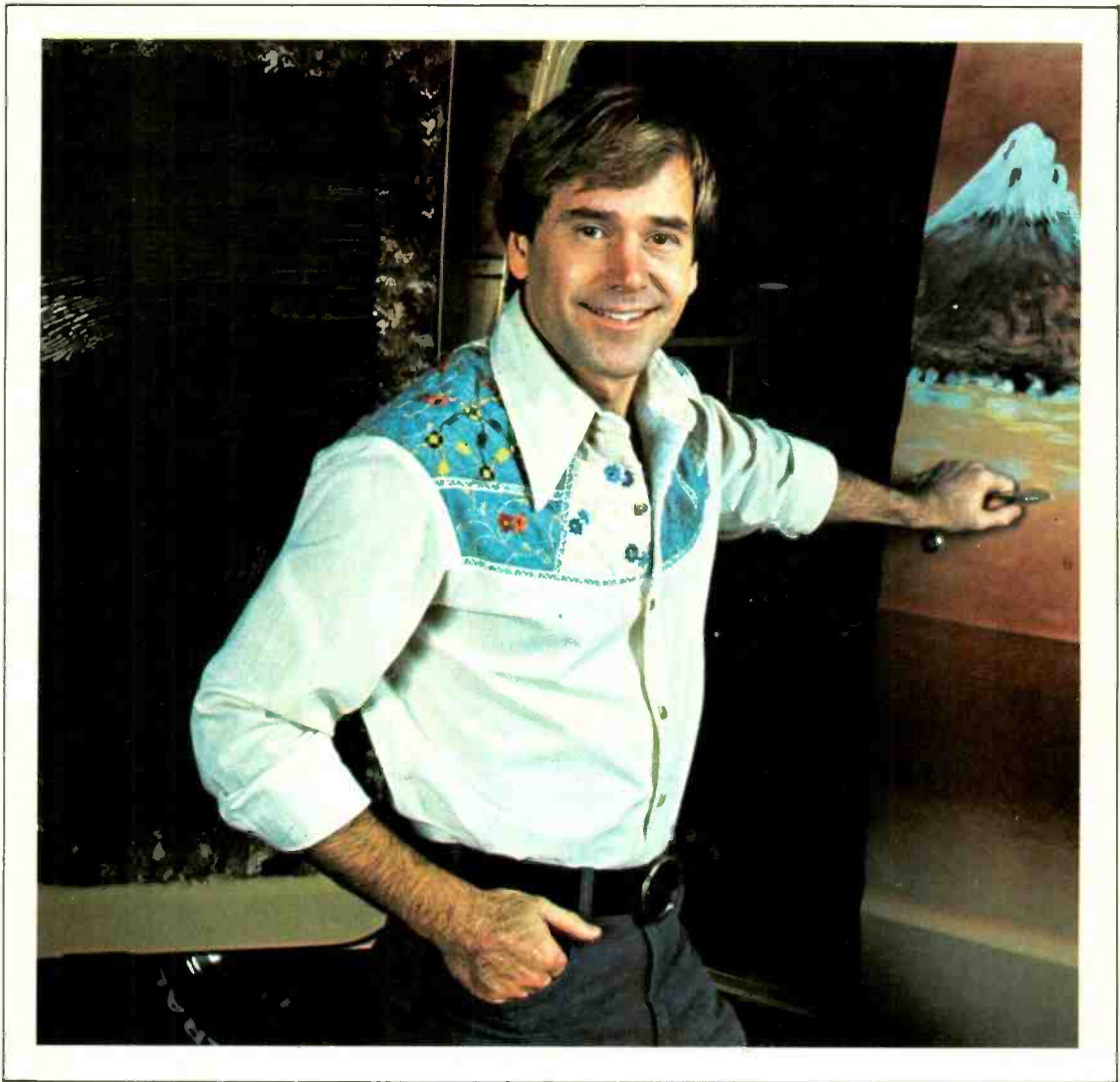

**When you do, you'll probably pick CIE.  
You can't afford to settle for  
less when it comes to something like  
electronics training that could  
affect your whole life.**



**W**hen you shop around for tires, you look for a bargain. After all, if it's the same brand, better price — why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

\* \* \*

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

### Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type — with serious career goals in electronics — take a close look at what we've planned for you at CIE.

### What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries — on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them — before you start using them!

### How practical is the training?

This is the next big important question. After all, your career will be built on what you can do — and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

**With CIE's Experimental Electronics Laboratory...**




you learn and review the basics — perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



**When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope** you take your first real professional step. You use it as a doctor uses an X-ray machine — to "read" waveform patterns... lock them in... study, understand and interpret them!

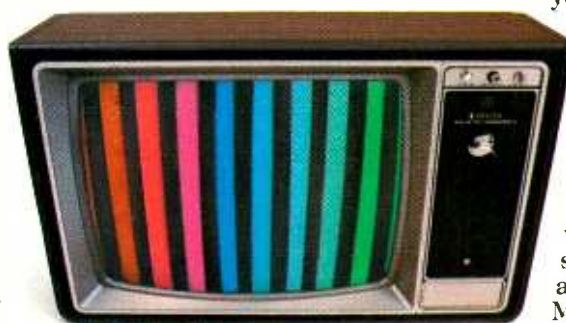**When you get your Zenith 19-inch Diagonal Solid-State Color TV** you



Pattern simulated.

apply your new skills to some real on-the-job-type troubleshooting! You learn to trace signal flow... locate malfunctions... restore perfect operating standards — just as with any sophisticated electronics equipment!



**When you work with a completely Solid-State Color Bar Generator** — actually a TV signal transmitter — you study up to ten different patterns on your TV screen... explore digital logic circuits... observe the action of a crystal-controlled oscillator!

Of course, CIE offers a more advanced training program, too. But the main point is

simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

### Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

For some troubleshooting jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of specific knowledge and skills!

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

### Shop around... but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon — or write: CIE, 1776 East 17th St., Cleveland, OH 44114.

## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

☐ **YES...** I'm shopping around for the **right** kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information! **RE-69**

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Phone \_\_\_\_\_ (area code)

Check box for G.I. Bill information:  
☐ Veteran ☐ Active Duty

**Mail today!**

## LETTERS

continued from page 16

become fact, a better system of transportation would be the chief ingredient—how about a transport system that operates over the phone lines. Sounds a little like "Star Trek," doesn't it? California to New York in two minutes? Remember, you said—dream!! If I get busy this week, maybe I'll have it in operation by, say, 2190. [The article on page 6 ("New & Timely") concerning the light-powered phone gave me the idea.]

And we just loved the Solar-Powered Night Light. As I see it, this should be the first practical perpetual motion machine.

Now, how about an LED on a giant scale

to be used for illumination? What a savings in power consumption for street lights, home lighting, etc. And then, how about a fiber-optic cable system to reduce power even more for street lights by putting one LED cluster in a 10-block sector and cabling to the immediately surrounding blocks?

DAVID HARTMAN  
Portsmouth, VA

### WIRE-WRAP TECHNIQUES

Thank you for an excellent presentation of my article "PC/Wire-Wrap—New Construction Technique" (*Radio-Electronics*, February, 1979).

However, while all basic principles of combined wire-wrap and PC board design of tri-level techniques have been included

in the article, your drawing of the 2102 PC board on page 54 (Fig. 1) does not make clear the breakpoints of the *data-in* and *data-out* pins. The top side of the PC board design shows clearly the breakpoints for 1K (18 IC's) enable lines, but the drawing will still have to show the breakpoints for each data input/output pin. A drawing of the bottom side of the PC board for the 2102 memory IC would have made this important detail clear.

Each 2102 IC must have an isolated wire-wrap foil pad. These pads are made by cutting the final etched PC line, just as the enable lines were separated. The final data lines are then connected for each input or output data bit by wire-wrap process. The data-bit 1 input requires eight wire-wrap connections, and the data-bit 1 output also requires eight wire-wrap connections.

Also the drawing of the edge connections in Fig. 1 for the wire-wrap circuits is misleading. The correct edge-connection pattern would have the following connecting points: 10 address lines, 1 positive line, 1 ground line, 8 enable lines for an 8K board by 1K increments, 8 Data Input Lines and 8 Data Output lines. The correct edge-connector pattern, then, is 36 individual connections for the wire-wrap points.

I hope this omission can be corrected since Fig. 1 only lacks the data line breakpoints of the bottom side of the PC board and the correct 36-line edge connections. Readers who use the drawing as shown will not have all the data that is needed to make this tri-level technique work; corrected drawings will help them beat the "wire-wrap jungle."

JAMES E. TEMPLE

### ELECTRONIC EQUATION

Mr. Ecklin's letter ("Letters," *Radio-Electronics*, April, 1979) about the "electronic equation" appears to correctly challenge the now-sacred law for the conservation of energy. Today's permanent magnets last for decades and off-the-shelf magnets easily lift 25 times their weight in iron, while most lodestones could not lift their own weight.

We now have tiny IC's for 16-bit computers with many thousands of active circuits on them that draw a total current in milliamperes. Even with this high efficiency, IBM is researching superconducting devices for even higher efficiency and speed. It is hard to guess how little power would be required to stop a magnetic field with a superconductor as Mr. Ecklin has suggested. It is also difficult to imagine a direct correlation between a 25-lb. magnet that could cause antigravity to over 600 lbs. of iron, and turning a superconductor on and off below the magnet's pole faces.

Maybe a magnet can store an unending supply of potential energy if we can divert or stop its magnetic field at will. So far we know of no way to stop or divert a gravitational field to create perpetual motion devices. One paragraph in a letter to *Radio-Electronics* may solve our energy crisis in spite of a well-proven law of science.

(By the way, Mr. Ecklin has informed me that the Doppler equation as shown in his letter was wrong; the last equal sign should have been a minus sign—i.e.,  $d = wf - c$ .)

DALE BERG  
Annapolis, MD

R-E

## When you're into electronics, Calctro is into whatever you need — whether it's ideas, instructions, or a complete supply of parts

Calctro has projects designed for you: a "Project of the Month", conceived by the Calctro engineering department, along with detailed instructions and a list of all the Calctro parts you need to build it!



Calctro has parts and accessories: printed circuit materials, tools, meters, testing devices, equipment boxes, sockets, switches, IC's, transistors, rectifiers, lugs, fuses, bulbs, wire, connectors, terminals, jacks, transformers, and lots more — everything you need to complete your project. And you'll find more of the parts you want at your Calctro store than anywhere else.



Calctro has literature: the Calctro Handbook — a valuable guide and product reference for the experimenter, hobbyist, audiophile, technician, and student; plus handbooks on semiconductors, circuits, and more! Coming soon: a new Calctro Handbook, a compendium of popular project ideas.

Whatever you need in electronics, your Calctro distributor is your surest, finest source!



### Calctro

Products of GC Electronics, Rockford, IL 61101



**TUNER SERVICE**



**CORPORATION**

**SAME DAY  
SERVICE**



**ONE YEAR  
GUARANTEE**

*The Company of Independent Professionals*

**Better Quality — Personal Attention — Faster Service**


TSC PROVIDES YOU WITH A COMPLETE  
SERVICE FOR ALL YOUR TELEVISION  
TUNER REQUIREMENTS



**TUNER REPAIRS**

**EXACT  
REPLACEMENT**

**UNIVERSAL  
REPLACEMENT**

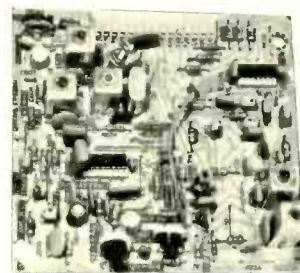

**SUBSTITUNER**

**MODULES**


HEADQUARTERS .....	BLOOMINGTON, INDIANA 47401 .....	537 South Walnut Street .....	Tel. 812/334-0411
ALABAMA .....	BIRMINGHAM, ALABAMA 35212 .....	5623 1st Avenue, North .....	Tel. 205/592-9150
ARKANSAS .....	LITTLE ROCK, ARKANSAS 72204 .....	4200-C Asher Ave. ....	Tel. 501/661-0393
CALIFORNIA .....	MODESTO, CALIF. 95351 .....	123 Phoenix Avenue .....	Tel. 209/521-8051
	NATIONAL CITY, CALIF. 92050 .....	117 East 8th Street .....	Tel. 714/477-8746
	NORTH HOLLYWOOD, CALIF. 91601 .....	10654 1/2 Magnolia Boulevard .....	Tel. 213/769-2720
	SAN MATEO, CALIF. 94402 .....	600 S. Amphlett Boulevard .....	Tel. 415/348-3292
FLORIDA .....	TAMPA, FLORIDA 33606 .....	1505 Cypress Street .....	Tel. 813/253-0324
	FT. LAUDERDALE, FLORIDA 33309 .....	3841 N.W. 9th Avenue .....	Tel. 305/566-4882
GEORGIA .....	ATLANTA, GEORGIA 30310 .....	646 Evans Street S.W. ....	Tel. 404/758-2232
ILLINOIS .....	URBANA, ILLINOIS 61801 .....	1005 Water St. ....	Tel. 217/384-2052
	SKOKIE, ILLINOIS 60076 .....	5110 West Brown Street .....	Tel. 312/675-0230
INDIANA .....	INDIANAPOLIS, INDIANA 46204 .....	112 West St. Clair Street .....	Tel. 317/632-3493
	SOUTH BEND, INDIANA 46628 .....	1709 Stocker Place .....	Tel. 219/288-8918
KENTUCKY .....	LOUISVILLE, KENTUCKY 40217 .....	#7 Dahlem Ctr. 826 Eastern Pkwy. ....	Tel. 502/452-1191
LOUISIANA .....	SHREVEPORT, LOUISIANA 71104 .....	2423 Southern Ave. ....	Tel. 318/221-3027
MASSACHUSETTS .....	SPRINGFIELD, MASSACHUSETTS 01109 .....	144 Boston Rd. ....	Tel. 413/788-8206
MISSOURI .....	ST. LOUIS, MISSOURI 63132 .....	9577 Page Avenue .....	Tel. 314/649-0633
NEVADA .....	LAS VEGAS, NEVADA 89102 .....	1114 South Casino Center Blvd. ....	Tel. 702/384-4235
NEW JERSEY .....	TRENTON, NEW JERSEY 08638 .....	1139 Pennsylvania Avenue .....	Tel. 609/393-0999
	JERSEY CITY, NEW JERSEY 07307 .....	454 Central Avenue .....	Tel. 201/792-3730
NEW YORK .....	ROCHESTER, NEW YORK 14606 .....	25 Howard Road .....	Tel. 716/647-9180
NORTH CAROLINA .....	GREENSBORO, N. CAROLINA 27405 .....	2914 East Market Street .....	Tel. 919/273-6276
OHIO .....	CLEVELAND, OHIO 44109 .....	4525 Pearl Road .....	Tel. 216/741-2314
OREGON .....	PORTLAND, OREGON 97210 .....	1732 N.W. 25th Ave., P.O. Box 10141 .....	Tel. 503/222-9059
PENNSYLVANIA .....	PITTSBURGH, PENNSYLVANIA 15209 .....	515 Grant Avenue .....	Tel. 412/821-4004
TEXAS .....	DALLAS, TEXAS 75218 .....	11540 Garland Road .....	Tel. 214/327-8413
CANADA .....	ST. LAURENT, QUEBEC H4N-2L7 .....	305 Decarie Boulevard .....	Tel. 514/748-8803
	CALGARY, ALBERTA T2H-1Y3 .....	P.O. Box 5823, Station "A" .....	Tel. 403/243-0971

If you want to branch out into the TV Tuner Repair Business write to the  
Bloomington Headquarters about a franchise.

CIRCLE 21 ON FREE INFORMATION CARD

# equipment reports

## Sinclair Radionics Model DM350 DMM

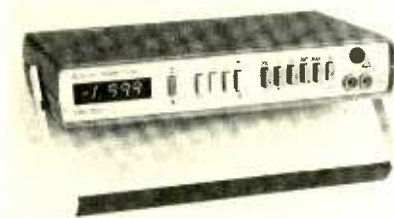

CIRCLE 101 ON FREE INFORMATION CARD

THE NAME OF SINCLAIR RADIONICS HAS BEEN familiar in England for quite a while. Now it's appearing in the U.S. The company is Sinclair Radionics, Inc., 66 Mt. Prospect Avenue, Clifton, NJ 07015.

The unit I tested was the *model DM350* bench digital multimeter (shown). This unit is one of a pair; the *model DM350* has a 3.5-digit display and the *model DM450* has a 4.5-digit display. Otherwise, the meters are identical, except for the greater resolution of the 4.5-digit model.

The meters measure AC or DC voltages from 200 mV up to 1200 volts DC or 750 volts AC in six ranges; AC or DC currents from 2.0  $\mu$ A to 10A. A separate input jack is included that can handle up to 20A for up to 10 seconds. Resistance can be measured from 200 ohms to 30 megohms on six ranges. Overrange is indicated by the display being blanked, except for the left-hand digit that displays a "1."

Some unusual switching is used. When you read "6 ranges" and then notice there are only five voltage pushbuttons on the range selector, you start wondering. Then you read the instructions, and the mystery clears up. A special 2000-mV range can be used that has a tremendously high input impedance—greater than 1000 megohms. To set up this range you press both the volts and milliampere buttons simultaneously, and then you release all the range pushbuttons. The display is in millivolts divided by 10.

On DC and AC current ranges, you do the same thing: the lowest range pushbutton is 200  $\mu$ A. A 2- $\mu$ A scale is produced by pressing the V and the mA pushbuttons in plus the 200- $\mu$ A pushbutton. For a 20- $\mu$ A scale, press the 20V pushbutton.

Autozeroing is used on all ranges. On the lowest resistance range, shorting the test leads displays the lead resistance—typically 0.3 ohm. For precise readings, subtract this value. Accuracy on the DC voltage ranges is 0.1% on the three lowest ranges and 0.25% on the higher ranges; for AC voltages, 0.25% on the low range and 0.4% on the higher ranges; and for AC or DC currents, accuracy is typically 0.2%. Ohmmeter accuracy is 0.2% on all ranges.

The *model DM350* provides overload protection up to 1200 volts DC on all ranges, and to 750 volts AC on the AC ranges. The ohmmeter withstands up to 400 volts peak AC.

Current ranges are protected by a 2A fuse (located in the back panel) except for the 10-amp range, which is not fuse protected.

The *model DM350* is housed in a small flat plastic case that measures 10 inches wide but is only 1.5-inches high. Despite the compactness of the DMM, the panel is easily accessible, and the pushbuttons are large enough and spaced far enough apart so that they are easy to hit. The displays are 7-segment LED's that are bright enough to read at any practical distance. The test leads (which are included) plug into three jacks at the far right of the panel, out of the way. A bail-type carrying handle doubles as a bench rest to hold the panel at the best viewing angle.

Power is provided by four built-in dry "C" batteries or from an AC adapter. The batteries are located under a sliding cover on the back of the unit. A selector switch on the back allows you to choose either disposable or rechargeable batteries. When the switch is in the disposable position, the internal batteries are disconnected when the AC adapter is plugged in. If rechargeable batteries are used, just set the switch to the rechargeable position, and the battery charge is maintained while the unit is plugged in. A low-battery condition is indicated by the whole display flashing; this means the batteries are down to 4.4 volts. However, accurate measurements can still be made for a few minutes before errors occur.

These DMM's are manufactured in England, and the workmanship looks good. Incidentally, if you misplace the manual, a label on the bottom of the case gives complete information on all ranges and functions. This is a very handy little instrument, at a reasonable price—\$139.

## PTS Model 8001 Component Analyzer



CIRCLE 102 ON FREE INFORMATION CARD

PTS ELECTRONICS, INC., (BOX 272, BLOOMINGTON, IN 47401) has added test equipment to its TV tuner repair and module rebuilding ser-

vices. There are several units. One of these is the *model 8001* Component Analyzer. It's a compact instrument that is easy to run. All you need is a scope (of any kind) and connect the *model 8001* to its vertical and external horizontal inputs and off you go. Calibration and setup are fast. Adjust the scope's vertical gain plus the horizontal calibration control on the analyzer and there you are.

The *model 8001* can be used for tests on all solid-state components, such as transistors, diodes, etc. On a good diode or transistor junction, the analyzer shows a sharp right-angle pattern. A rounding of the angle shows there is leakage. A straight vertical line indicates shorted parts; open circuits show up as a horizontal line. Here's a quick check before starting: short the test leads together, a vertical line shows. If the circuit's open, then a horizontal line appears.

The *model 8001* can be used for in-circuit transistor testing. The patterns will differ from the out-of-circuit patterns, but the characteristic sharp angle will be there. The patterns are distinctive enough to indicate whether the component is bad or good. Several manufacturers have adopted this testing method, and their service manuals show the typical patterns that are found in various stages.

A good resistor shows a straight diagonal line. The angle varies with the value of resistance. A good capacitor will show an oval or a round pattern. Large capacitors have very low impedance. The *model 8001* has a LOW-MED-HIGH range switch to check any size. Many low-frequency inductors, such as power transformers, vertical-output transformers, chokes, etc., can be checked for shorts. If the winding is good, the analyzer will show a definite ellipse or even a circle if the inductance is high enough. If the component has shorted turns, a straight vertical line appears, and you cannot get a loop at any range-switch setting. Check the analyzer on a few good parts and you'll discover what to look for.


This instrument is useful for making A-B comparisons between identical circuits. In a stereo amplifier with one bad channel (a common fault), the same stage and junctions can be cross-checked between the working channel and the bad one. Here again, check some working circuits and observe what the patterns look like.

The front panel of the *model 8001* contains all the controls. The scope is connected to the horizontal and vertical jacks, and the test leads (provided) go to two universal binding posts. These binding posts are colored red and black, but the *model 8001* has no polarity. Hook up the leads one way, the angle goes up and to the right; reverse the leads, the angle goes down and to the left; but the sharp angle remains. The scope's vertical-gain control sets the length of the vertical line; the horizontal calibration control on the *8001* front panel adjusts

*continued on page 26*


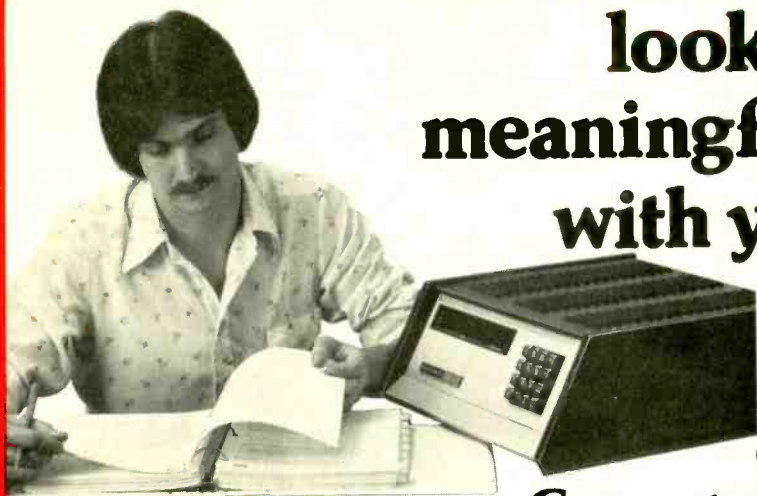
# looking for a more meaningful relationship with your computer?



Learn to speak its language with easy-to-use Heathkit® Computer Language Programs.

## Heathkit Self-Instruction Program for ASSEMBLY Language Programming.

- Use the full capacity of your computer.
- Execute programs faster.
- Store more in less space.

ASSEMBLY Language lets you do *everything* your computer is capable of doing. It's the most versatile, most powerful language you can use.

ASSEMBLY includes a mnemonic for every machine operation. No time is wasted interpreting, so programs run much faster.

ASSEMBLY makes more efficient use of memory. It stores in less space because codes are shorter, more explicit.

The Heathkit Self-Instruction Program teaches you to program your computer in ASSEMBLY Language. You learn

at your own pace through a special text designed for self-study. An exercise workbook provides hands-on experience with programming exercises performed by you on your computer. You learn in a way that's fast, fun and thorough.

The Heathkit Program is designed for computers using the popular 8080/8085/Z80 microprocessor series. This includes the Heathkit H8, H88 and H89 Computers. The concepts of the program, however, can be applied to any computer.

Now's the time to learn the language that puts you in total command of your computer's full potential. Send today for the Heathkit Self-Instruction Program for ASSEMBLY Language.

**Order No. EC-1108: \$49.95, plus shipping and handling.**

## Heathkit Self-Instruction Program for BASIC Language Programming.

- Easiest of all languages to use.
- Now easiest of all to learn.

More programs are written in BASIC than any other language. Because it uses English statements and commands, it's the easiest to learn and the easiest to use.

When you know BASIC you can adapt and run hundreds of existing programs. You can exchange programs with others. And you can write your own programs for your specific needs.

In 14 easy-to-follow segments, the Heathkit Program covers all formats, commands, statements and procedures. A special workbook provides programming instructions and experiments performed on your computer. You learn practical problem-solving techniques.

Until you know BASIC, you're missing the full selection of programs available to you. Send today for the Heathkit Self-Instruction Program for BASIC Language.

**Order No. EC-1100: \$39.95, plus shipping and handling.**

**Send Today or Phone for faster service on VISA and Master Charge. 616-982-3411**

Heath Company, Dept. 020-562, Benton Harbor, MI 49022

SHIP MY ORDER TO:

Name \_\_\_\_\_  
(please print)  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
Zip \_\_\_\_\_

HEATH

Schlumberger

Heath Company  
Dept. 020-562  
Benton Harbor, MI 49022

PLEASE RUSH ME:

- ☐ ASSEMBLY Language  
EC-1108 ..... \$49.95, plus \$2.60 shipping & handling.  
☐ BASIC Language  
EC-1100 ..... \$39.95, plus \$2.40 shipping & handling.  
Total price .....  
Michigan residents add  
4% sales tax .....  
Add shipping & handling .....  
Total enclosed .....

☐ check ☐ money order ☐ Heath Revolving Charge Or charge my ☐ VISA/BankAmericard  
☐ Master Charge

Account No. \_\_\_\_\_ Expiration Date \_\_\_\_\_

Signature x \_\_\_\_\_ (NECESSARY TO SEND MERCHANDISE)

Prices are mail order and subject to change without notice

ED-125

### MONEY-BACK GUARANTEE OF SATISFACTION

If you are not completely satisfied with the EC-1100 BASIC Program or the EC-1108 ASSEMBLY Program, simply return programs for a full refund of purchase price.

## EQUIPMENT REPORTS

continued from page 24

the length of the horizontal line. The pattern will get smaller as you switch from HI to LOW on the RANGE switch. If the pattern becomes too small, just reset the horizontal calibration and vertical gain controls. The size makes no difference.

This is a simple but handy instrument that can be very accurate when used properly. It doesn't take long to set up, and it is priced at \$54.95. **R-E**

## Apple Disk II Floppy Disc System



CIRCLE 103 ON FREE INFORMATION CARD

OWNERS OF THE APPLE II COMPUTER (Apple Computer, Inc., 10260 Bandley Drive, Cupertino, CA 95014) now have an alternate to their cassette tape system for saving programs and data. The Disk II system allows fast, reliable storage on standard 5¼-inch minifloppy dis-

kettes. Up to 14 disc drives can be connected to the Apple II for access to nearly 1.6M bytes of data. The DOS (Disc Operating System) is activated via a PROM-based bootstrap loader and master diskette supplied by Apple. The DOS adds the following commands: OPEN, CLOSE, READ, WRITE, SAVE, LOAD, EXEC, RUN, APPEND, RENAME, POSITION, VERIFY, CHAIN, LOCK, UNLOCK, DELETE, MON, NOMON, MAXFILES, CATALOG, INIT, BSAVE, BLOAD, BRUN, FP, and INT.

The Disk II consists of a controller card that plugs into one slot of the Apple II motherboard, a modified Shugart SA-400 disc drive, a system software diskette, a blank diskette and instructions. The packaging of the drive is excellent; the color-coordinated steel cabinet fits nicely on top of the computer. One controller card handles two drives; so up to a maximum of seven controllers can be used. Each drive is then referred to by its number, D, and by its controller's slot number, S (e.g., D1 and S6). Once a drive has been accessed, these values default to that drive until they are explicitly changed. Included on the software diskette is a game program, ANIMALS that demonstrates very nicely how the disc can be used to store data.

Using the Disk II is a breeze. Programs save and load by name, and about 10 times faster than by cassette. Thus, to store a program on the disc, you simply type SAVE <file name>, where <file name> is any name you select for the program. The DOS automatically keeps a directory of all files; these files can be seen by using the CATALOG command. The CATALOG command also shows the nature of the file (BASIC, Applesoft, machine code, or text),

whether the file is protected, and also gives you some indication of the file length. Using the LOCK command protects files from accidental change or deletion.

The command list gives a fairly good indication of the power of the disc system. Particularly noteworthy are the EXEC, FP and INT commands. The EXEC command is similar to a RUN command except that the indicated file may contain entries not normally allowed in a BASIC program; for example, the HIMEM command used to run many programs (i.e., the Apple Startrek game). Normally, such a program must be loaded into the computer and a HIMEM command issued to set memory pointers correctly before it is run. Using the EXEC command allows such a program to be run from the disc just like any other program.

Another good feature of the disc is that the floating-point BASIC (Applesoft) is always handy and can be loaded within 8 seconds. For convenience, the commands FP and INT are used to switch between BASIC's. When a program is loaded from the disc, the computer checks which BASIC it was written in, and then loads Applesoft (or selects the Applesoft firmware card when installed) if necessary. Incidentally, this Applesoft is actually Applesoft II, an improvement over the original version. The DOS also allows a program to begin executing immediately after booting for a turnkey type of operation.

The DOS however has two flaws; its inability to CHAIN Applesoft programs, and the lack of any password security for files. While this last feature is of little value to most home-computer hobbyists, it is very important in

continued on page 33



## Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

**Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long. **\$1.59**

**Kleps 20.** Same, but 7" long. **\$1.69**

**Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.99**

**Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. **\$2.89**

**Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. **\$1.09**

**Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. **\$ .99**

All in red or black - specify. (Add 50¢ postage and handling).

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

**RYE INDUSTRIES INC.**

130 Spencer Place, Mamaroneck, N.Y. 10543

130 Canada: Rye Industries (Canada) Ltd.

CIRCLE 27 ON FREE INFORMATION CARD



## Full Features ... Yet Portable

**\$850**

includes probes  
and front cover

Say "Hello" to an excitingly new 15 lb., 15 MHz 'scope. Smart looking and really convenient — only 5¼" high yet features a large, bright 10cm x 8cm rectangular CRT.

Check this capability: Versatile triggering in excess of 25MHz, 2mV sensitivity, differential mode, and much more.

Quality? You Bet! Backed by Exclusive Gould 2-yr. warranty.

It's a winner! Call us for the full story on the OS255.

For free brochure call: TOLL FREE NUMBER (800) 325-6400

In Missouri (800) 342-6600

Gould Inc., Instruments Division  
3631 Perkins Ave., Cleveland, OH 44114

**GOULD**  
An Electrical/Electronics Company

CIRCLE 54 ON FREE INFORMATION CARD



# TRI-COLOR

## WIRE CUTTING AND STRIPPING DISPENSER



Model No. **WD-30-TRI**  
Patent Pending

- 3 Rolls of wire in one convenient dispenser
- 3 Colors, Blue/White/Red, 50 ft. (15m) of each color
- AWG 30 (0.25mm) KYNAR® Insulated wire
- Built-in cutting plunger cuts wire to desired length
- Built-in stripper strips 1" of Insulation
- Easily refillable
- For wire-wrapping and other applications

WD-30-TRI	DISPENSER WITH WIRE	\$5.95
R-30-TRI	TRI-COLOR REPLACEMENT SPOOLS	\$3.95

Kynar® Patented

MINIMUM BILLING \$25.00/ ADD SHIPPING CHARGE \$1.00/ NEW YORK STATE RESIDENT ADD APPLICABLE TAX.



MACHINE & TOOL CORPORATION 3455 CONNER ST. BRONX, N.Y. 10475 (212) 994-6500/Telex 125031

CIRCLE 24 ON FREE INFORMATION CARD

# Train with NTS for the MicroComputers, digital the first name



## MicroComputers

The world of electronics is daily becoming more challenging. Technology is growing more specialized, and the importance of digital systems increases every day. Test instruments, home entertainment units and industrial control systems are all going digital. And now, NTS training programs include a wider choice of solid-state and digital equipment than ever before offered in any home study course: Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath microcomputer, digital test equipment, digital stereo receiver (70 watts per channel), NTS compu-trainer, plus much more state-of-the-art equipment to make your training exciting and relevant.

The equipment you receive with NTS training programs is selected to provide you with a solid

background in electronic systems. Kits and lessons are designed to work together to demonstrate electronic principles and applications. The kit-building not only shows you how electronic hardware functions, but how various circuit designs accomplish different purposes. Your lessons guide you through any number of experiments associated with many projects. This is the Project-Method, and it works. Step-by-step, you learn how and why digital electronics has become a part of our world, and the even bigger role it is sure to play in the future.

Whether you are looking for training in Consumer, Commercial, or Industrial electronics, NTS offers fourteen courses, some basic, many advanced, in several areas of electronics. An all-new full-color NTS catalog shows you what each course covers,



# electronics of the future.

systems and more...from  
in home study.

**Test Instruments**

**Basic Electronics**

**Digital Color TV**

*Simulated TV Reception*

*NTS Training Programs in Consumer and Industrial Electronics*

and every piece of equipment included.

Send for it today, and see for yourself what's really happening in electronics training technology at NTS. Find out how much has changed, and what new directions the field is taking. You'll probably want to be a part of it.

It's free. Just mail the card or coupon. Today.

**NO OBLIGATION. NO SALESMAN WILL CALL.  
APPROVED FOR VETERAN TRAINING.**

**NATIONAL TECHNICAL SCHOOLS**

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 South Figueroa St., Los Angeles, Calif. 90037

**NATIONAL TECHNICAL SCHOOLS** Dept. 206-089  
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- ☐ Color TV Servicing
- ☐ B & W TV and Radio Servicing
- ☐ FCC License Course
- ☐ Electronic Communications
- ☐ Electronics Technology
- ☐ Audio Electronics Servicing
- ☐ Digital Electronics
- ☐ MicroComputers/MicroProcessors

Name \_\_\_\_\_

Address \_\_\_\_\_

Apartment Number \_\_\_\_\_ Age \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_


☐ Check if interested in G.I. Bill information.

☐ Check if interested ONLY in classroom training in Los Angeles.



# NEW.

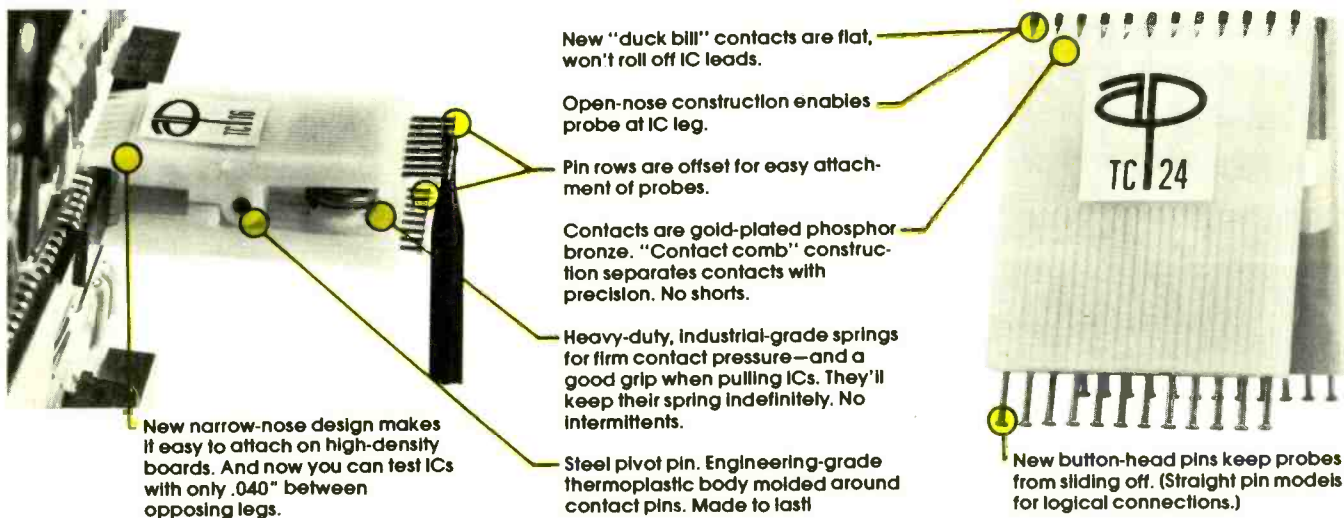**Meet Super Grip II, the great new test clip from A P Products.**



The new A P Super Grip II is, without question, the best way there is to troubleshoot DIP ICs.

You get positive contacts. No intermittents. No shorts. Ever.

So it's endlessly useful to you—and it's

built to stay useful indefinitely.

Try one. You'll find 8, 14, 16, 16 LSI, 18, 20,

22, 24, 28, 36 and 40-pin models at your nearby A P store. (Make sure it's your A P store.)

Need the address? Call (toll-free) 800-321-9668. And ask for our complete A P catalog, The Faster and Easier Book.



**A P PRODUCTS  
INCORPORATED**

Box 110B • 72 Corwin Drive  
Painesville, Ohio 44077  
Tel. 216/354-2101  
TWX: 810-425-2250

**Faster and Easier is what we're all about.**



## EQUIPMENT REPORTS

continued from page 26

multiuser systems such as schools or businesses (where many Apple II's are currently found). Without such file security, a programmer could inadvertently (or even purposely!) change or destroy another programmer's files. Since the DOS resides in RAM, undoubtedly Apple and other computer companies will supply improved versions in the near future.

Overall, the *Disk II* performed very well. I have transferred all my programs from tape to disc, which quickly filled up more than six diskettes (over 600K bytes), and the disc has operated flawlessly. Indeed, the *Disk II* appears to be up to the high standards that the company has shown in the Apple II computer.

The *Disk II* costs \$595, including the controller card. Additional drives (without controller) cost \$495. It should be noted that due to high demand, delivery may be quite slow for a while. **R-E**

## Realistic Model DX-300 Receiver



CIRCLE 104 ON FREE INFORMATION CARD

AFTER A PROLONGED PROMOTION PERIOD, Realistic (Radio Shack) has now made available its newest entry into the hobby listening market: the *model DX-300* general-coverage receiver.

This receiver is continuously tunable from 10 kHz through 30 MHz and features a large, bright digital-frequency display, a frequency synthesizer and triple conversion. Specifications include: a shortwave sensitivity better than 1 mV; an image ratio 70-80 dB down; AM/LSB/USB/CW detection modes; a selectivity of  $\pm 3$  kHz ( $-6$  dB) and ( $\pm 70$  dB); and less than 1-kHz drift after a one-hour warmup period.

The receiver's appearance is exceptionally attractive with a military black finish, aluminum knobs and colorfully illuminated dials.

Since we are aware that packaging is an important part of salesmanship, we were eager to test the receiver to see whether its looks were deceiving. Our first reaction was one of disappointment. The drift rate on the sample receiver we tested was very rapid; it was virtually unusable in the single-sideband or continuous-wave modes until after a lengthy warmup period (the specifications warn the user of this).

Proper adjustment for each frequency range (it tunes in 1-MHz increments) is cumbersome: After the frequency range to be tuned is selected, the megahertz dial ring must be tuned for best signal, and then the preselector must be tuned.

Although the importance of proper adjustment of the megahertz tuning knob is not emphasized in the manual, the setting of this knob is *crucial* to acceptable performance.

continued on page 34

NOW! For the first time . . . a clear, concise, understandable book on the Earth's most promising energy source.

# Solar Electricity

**Special Introductory Price!**  
**\$5.95 Ppd.**

## 140 EASY-TO-READ FACT FILLED PAGES

Loaded with charts, graphs, pictures of actual solar installations—by World's Foremost Authority SOLAREX

Most books and articles on Solar Energy are either jam packed with mind-boggling technical jargon, or they're so basic you can't find what you really want to know.

Here for the first time—is a definitive study of all the real (not blue sky) applications of solar, written by the world's leading experts but written in everyday language so you can understand and put to work the real, significant benefits of Solar electricity in scores of practical ways, both large and small. Most reading for everyone from the casual enthusiast right up to the trained solar professional.

**Nine Clear, Concise Chapters**  
Covers everything from a glossary of solar electric terms, how to use cells and practical solar electric generators, to the rapidly exploding variety of industrial,

educational, consumer, and military applications. It also includes solar electric projects, commercially available accessories the use of solar cells as light sensors rather than as power sources, and much, much more.


## Don't take our word for it!

Take your time. In fact—take two full weeks. Order the book. Read it. See if you don't completely agree that this is the best Solar electric summary you've ever read. If not—simply return the book and we'll refund your money by return mail.

Use handy coupon below or phone 301-948-0202. Dealers' inquiries invited.

STOCK NO. 37005E . . . \$5.95 Ppd.

Only \$5.95 Ppd

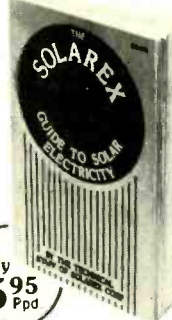

## COMPLETE AND ORDER TODAY

**SOLAREX CORP.** CPD-Dept. 100 E, 1335 Piccard Drive, Rockville, MD 20850

Please send me \_\_\_\_\_ copies of "Guide to Solar Electricity" (a \$5.95 each \$ \_\_\_\_\_)  
Shipping & Handling \_\_\_\_\_ 50¢  
TOTAL (Md. resident please add 5%) \_\_\_\_\_

☐ Enclosed is \_\_\_\_\_ check \_\_\_\_\_ M.O. in amount of \$ \_\_\_\_\_

Name \_\_\_\_\_ PLEASE PRINT

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



**SOLAREX Corporation**  
CPD-Dept. 100E  
1335 Piccard Drive,  
Rockville, MD 20850

CIRCLE 61 ON FREE INFORMATION CARD



Featuring

**RCA 1802 COSMAC**

Own a powerful home computer system, starting for just \$99.95—a price that gets you up and running the very first night with your TV set for video display. RCA 1802 8 bit microprocessor, addressable to 64K bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hex keyboard, two digit hex output display, stable crystal clock for timing purposes, RCA 1801 video IC to display your programs on any video monitor or TV screen and 5 pin plug in expansion bus (less connectors) to expand ELF II: BIER, DISASSEMBLER, VIDEO DISPLAY BOARD, and

## ELF II Explodes Into A Giant!

Master ELF II's \$99.95 capabilities, then expand with GIANT BOARD to record and play back programs, edit and debug programs, communicate with remote devices and make things happen in the outside world. KLUDGE BOARD to use ELF II as a controller: 4K RAM BOARDS, TINY BASIC, ASCII KEY BOARD, LIGHT PEN, ELF BUG MONITOR, COLOR GRAPHICS & MUSIC SYSTEM, TEXT EDITOR, ASSEMBLER, VIDEO DISPLAY BOARD, and

## More Breakthroughs Coming Soon!

Soon to be introduced: ELF II special application kits. PROM Programmer, A/D, D/A Converter, Controller Board, and more! So don't be trapped into buying a dinosaur that's already obsolete. An ongoing commitment to develop the RCA 1802 for home computer use by Netronics keeps you right on the outer fringe of today's home computer technology. Order your ELF II, direct from the factory, with the coupon below! Netronics guarantees your success!

**Netronics R&D Ltd., Dept RE-8**  
333 Litchfield Road, New Milford, CT 06776

Yes! I want my own computer! Please rush me—

- ☐ RCA COSMAC ELF II kit at \$99.95 plus \$3 postage and handling (includes 6 to 8 volt AC power supply).
- ☐ Power Supply (required) \$4.95 postpaid
- ☐ RCA 1802 User's Manual \$5 postpaid
- ☐ Tom Pittman's Short Course On Microprocessor & Computer Programming teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language it's a learning breakthrough for engineers and laymen alike \$5 postpaid
- ☐ Deluxe Metal Cabinet with plexiglas dust cover for ELF II \$29.95 plus \$2.50 p&h
- ☐ I am also enclosing payment (including postage & handling) for the items checked below:
- ☐ I want my ELF II wired and tested with power supply, RCA 1802 User's Manual and Short Course—all for just \$149.95 plus \$3 p&h

## ALSO AVAILABLE FOR ELF II

- ☐ **GIANT BOARD™** kit with cassette I/O, RS-232 C/TTY I/O, 8 pin P/V decoders, for 14 separate I/O instructions and a system monitor/editor. \$39.95 plus \$17.00 plus \$1 p&h
- ☐ **Kludge (Prototype) Board** accepts up to 16 IC's \$17.00 plus \$1 p&h
- ☐ **4K Static RAM kit**, Addressable to any 4K page to 64K \$89.95 plus \$3 p&h
- ☐ **Gold plated 85 pin connectors** (one required for each plug-in board) \$5.70 each, postpaid
- ☐ **Expansion Power Supply** (required when adding 4K RAM) \$34.95 plus \$7 p&h
- ☐ **Professional ASCII Keyboard kit** with 128 ASCII upper/lower case set, 96 printable characters, onboard regulator, parity logic selection and choice of 4 hand shaking signals to mate with almost any computer \$64.95 plus \$7 p&h
- ☐ **Deluxe metal cabinet for ASCII Keyboard**, \$19.95 plus \$2.50 p&h
- ☐ **Video Display Board kit** lets you generate a sharp professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor—manually improving your unexpanded \$99.95 ELF II (this inside ASCII Keyboard cabinet) \$89.95 plus \$2 p&h
- ☐ **ELF II Tiny BASIC** on cassette tape. Commands include SAVE, LOAD, ±, ×, ÷, !

- ☐ **26 variables A-Z LET IF/THEN INPUT PRINT GO TO GO SUB RETURN END REM CLEAR LIST RUN PLOT PEEK POKE**. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen with additional hardware. Also plays tic-tac-toe plus a drawing game that uses ELF II's hex keyboard as a joy stick. 4K memory required. \$14.95 postpaid
- ☐ **Tom Pittman's Short Course on Tiny BASIC** for ELF II \$5 postpaid
- ☐ **ELF-BUG™ Deluxe System Monitor** on cassette tape. Allows displaying the contents of all registers on your TV at any point in your program. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! \$14.95 postpaid
- ☐ **Text Editor** on cassette tape gives you the ability to insert, delete or edit lines and words from your programs while they are displayed on your video monitor. (Add printer and you can use ELF II to type error-free letters plus insert names and addresses from your mailing list) \$19.95 postpaid
- ☐ **Assembler** on cassette tape translates assembly language programs into hexadecimal machine code for ELF II use. Mnemonic abbreviations for instructions (rather than numerics) make programs easier to read and help prevent errors. \$19.95 postpaid
- ☐ **Disassembler** on cassette tape takes machine code

**PHONE ORDERS ACCEPTED!**  
Call (203) 354-9375

Total Enclosed \$ \_\_\_\_\_  
(Conn. res. add tax)

**CHARGE IT! Exp. Date**  
☐ Visa ☐ MasterCard  
(Bank # \_\_\_\_\_)

Account # \_\_\_\_\_

programs and produces assembly language source listings to help you understand and improve your programs \$19.95 on cassette tape  
**SAVE \$9.90**—Text Editor, Assembler & Disassembler purchased together, only \$49.95! (Require Video Display Board plus 4K memory.)  
☐ **ELF II Light Pen**, assembled & tested. \$7.95 plus \$1 p&h  
☐ **ELF II Color Graphics & Music System Board kit** \$49.95 plus \$2 p&h  
☐ ELF II connects directly to the video input of your TV set without additional hardware. To connect ELF II to your antenna terminals instead, order RF Modulator, \$8.95 postpaid.  
Coming Soon: A/D, D/A Converter, Controller Board and more!

Print Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 43 ON FREE INFORMATION CARD



## EQUIPMENT REPORTS

continued from page 33

Intermediate frequency feedthrough (i.e., the same interfering station is heard in the background, regardless of the setting of the tuning dial) is frequently present; this interference can be reduced by carefully adjusting the megahertz tuning knob and peaking the preselector. An external tuner or preselector would be very helpful here. "Birdies" (spurious signals generated by the synthesizer circuit) are present but no more troublesome than those found on similar receivers employing frequency synthesis.

Our particular sample receiver had a bad AC hum that could have resulted from shipping damage; also, the antenna screw-terminal was nonfunctional, as though it were disconnected internally. A subsequent inspection confirmed that a cold-soldered antenna-coupling capacitor was dangling loose in its solder pad.

Sensitivity was good above 150 kHz or so; below 150 kHz, the sensitivity became progressively worse. The receiver was virtually useless below approximately 70 kHz, even when using an external antenna tuner for optimum signal coupling. The VLF range was very unstable and full of oscillations.

Although the receiver can provide signal-copying capability without a tuner in the low-frequency range down to about 200 kHz, an external antenna-matching circuit is strongly recommended.

The IF selectivity is not adjustable, and some adjacent interference from the crowded frequency spectrum should be expected.

Make sure to read the instruction manual thoroughly while acquainting yourself with the receiver, or you may become very discouraged; with some practice, optimum tuning and adjustments will become automatic.

A company spokesman told us that the receiver is intended for general-purpose use; it is *not* a communications receiver. Now the receiver looks much better to us.

The reception on the AM band is excellent; the audio is crisp and a three-position tune control is provided for customizing the sound. The internal speaker works well without producing acoustic feedback at high volume. The ANL (Automatic Noise Limiter) circuit is highly effective; in a particularly noisy environment, the hash noise was virtually eliminated without degrading the desired audio signal.

The tuning has a particularly good feel; a spinner dial coupled with silicone damping gives a professional touch to the tuning mechanism. A three-way power supply allows 120 VAC, 12 VDC, or battery operation (self-contained; the batteries are optional).

For the international broadcast enthusiast, the *model DX-300* is excellent. When you dial up the proper frequency, you know that you are right on target (within 1 kHz). Single-sideband stations will be offset by several kHz (the manual indicates 3 kHz, but our sample receiver was off by 5 kHz).

The built-in code-practice oscillator could be considered a handy device by an aspiring ham, or just a gimmicky toy by a more serious listener; it depends upon your point of view!

The manual provides several helpful charts, including Morse Code, common radio terms

overheard on the air, and the "Q-signals" that are used to expedite communications over the air. The manual also contains a list of public safety "10-code" signals.

All in all, the receiver is a satisfactory addition to the casual hobby radio market. It is recommended for AM broadcast and short-wave listeners who would like to be able to occasionally copy continuous-wave and single-sideband signals.

We are certain that enterprising experimenters will devise improvements and modifications to increase the receiver's performance. The Realistic *model DX-300* costs \$379.95 and is available from Radio Shack, 1400 One Tandy Center, Fort Worth, TX 76102. (As of this writing, Radio Shack has informed us that several improvements have been made in the *model DX-300*, particularly in frequency stability. We advise our readers therefore to make sure they purchase the most recent model.—


Editor)

R-E



There's something wrong with this digital readout—it's nothing but a bunch of numbers.

# NEW!

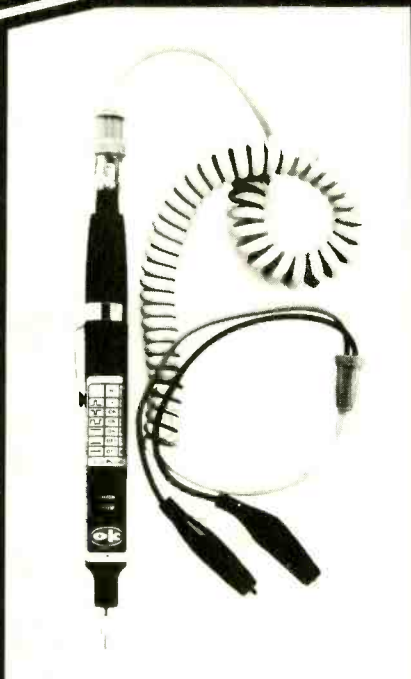

## PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL, CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

# \$36<sup>95</sup>\*

- DC to > 50 MHz
- 10 Nsec. pulse response
- 120 K  $\Omega$  impedance
- Automatic pulse stretching to 50 Msec.
- Automatic resetting memory
- Open circuit detection
- Automatic threshold resetting
- Compatible with all logic families 4-15 VDC
- Range extended to 15-25 VDC with optional PA-1 adapter
- Supply O.V.P. to  $\pm 70$  VDC
- No switches/no calibration


\* ADD \$2.00 FOR SHIPPING  
(N. Y. CITY AND STATE RESIDENTS ADD TAX)

OK MACHINE & TOOL CORPORATION

3455 Conner St., Bronx, N.Y. 10475 (212) 994-6600 / Telex 125091

CIRCLE 25 ON FREE INFORMATION CARD



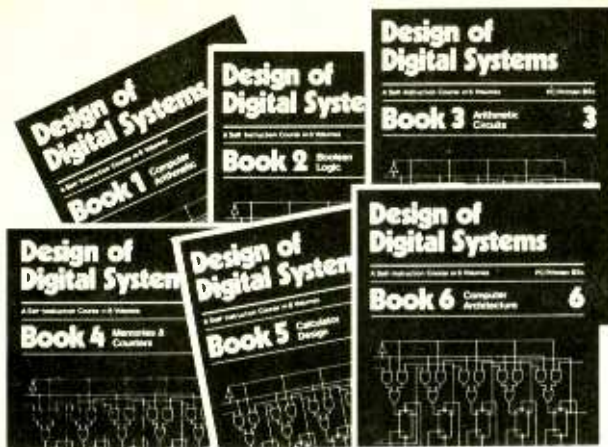

**Design of Digital Systems - six volumes**

# Designing Digital Systems

Two programmed learning courses:  
hardware and software; theory  
and application.

## ADVANCED COURSE DESIGN OF DIGITAL SYSTEMS

Six large-format volumes — each 11 1/4" x 8 1/4".

### CONTENTS

The contents of Design of Digital Systems include:

Book 1: Octal, hexadecimal and binary number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2: OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive - NOR functions; multiple input gates; truth tables; DeMorgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3: Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4: Flip-flops; shift registers; asynchronous counters; ring, Johnson and exclusive-OR feedback counter; random access memories (RAMs); read-only memories (ROMs).

Book 5: Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

Book 6: Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities programming; assemblers; executive programs, operating systems, and time-sharing.

### OUR CUSTOMERS

Design of Digital Systems has been bought by more than half the 50 largest corporations in America, and by Motorola, Intel, DEC, National Semiconductor, Fairchild, General Instrument, Hewlett-Packard, Heath Co., M.I.T., NASA, Smithsonian Institute, Bell Telephone Labs. And many, many more, as well as corporations and individuals in over 50 countries.

## BASIC COURSE



**Digital Computer Logic & Electronics**

### CONTENTS

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though you should have an aptitude for logical thought. It consists of 4 volumes — each 11 1/2" x 8 1/4" — and serves as an introduction to the subject of digital electronics.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; DeMorgan's Laws; design of logical circuits using NOR gates; R-S and J-K flip-flops; binary counters, shift registers and half-adders.

## NO RISK GUARANTEE

There's absolutely no risk to you. If you're not completely satisfied with your courses, simply return them to GFN within 30 days. We'll send you a full refund, plus return postage.

## TAX DEDUCTIBLE

In most cases, the full cost of GFN's courses can be a tax deductible expense.

## PHONE ORDERS - FREE

To order by phone, call (603) 224-5580 with your credit card information. It won't cost you a dime, because we'll deduct the cost of your call from the price of the courses you order.

## TO ORDER BY MAIL

You may use the order form below if you wish, but you don't need to. Just send your check or money order (payable to GFN Industries, Inc.) to the address below. If you don't use the order form, make sure your address is on your check or the envelope, and write "DDS" (Design of Digital Systems), "DCLE" (Digital Computer Logic & Electronics), or "both" (both courses) on your check.

There are no extras — no sales tax. And we pay all shipping costs.

We also accept company purchase orders.

## AIR MAIL

The prices shown include surface mail postage anywhere in the world. Air mail postage costs an extra \$10 for both courses (10 volumes).

## DISCOUNTS

Call or write for details of educational and quality discounts, and for dealer costs.

## SAVE \$5

If you order both courses, you save \$5. Order at no obligation today.



**GFN Industries, Inc.**  
Bldg. 7-20  
203 Loudon Road  
Concord  
NH 03301

- \* Order free by phone
- \* No sales tax
- \* No shipping charges
- \* Money-back guarantee
- \* Tax deductible
- \* Save \$5

Call (603) 224-5580 to  
order by phone - free.

7 days, 24 hours

**CIRCLE 60 ON FREE INFORMATION CARD**

To: GFN Industries, Inc., Bldg. 7-20, 203 Loudon Road, Concord, NH 03301

Please send me

\_\_\_ sets of Design of Digital Systems ..... \$19.95 \$\_\_\_\_\_  
\_\_\_ sets of Digital Computer Logic & Electronics ..... \$14.95 \_\_\_\_\_  
\_\_\_ sets of both courses ..... \$29.90 \_\_\_\_\_


Enclosed is check/money order (payable to GFN Industries, Inc.) for total \$\_\_\_\_\_

NAME .....

ADDRESS .....

CITY/STATE/ZIP .....

R8

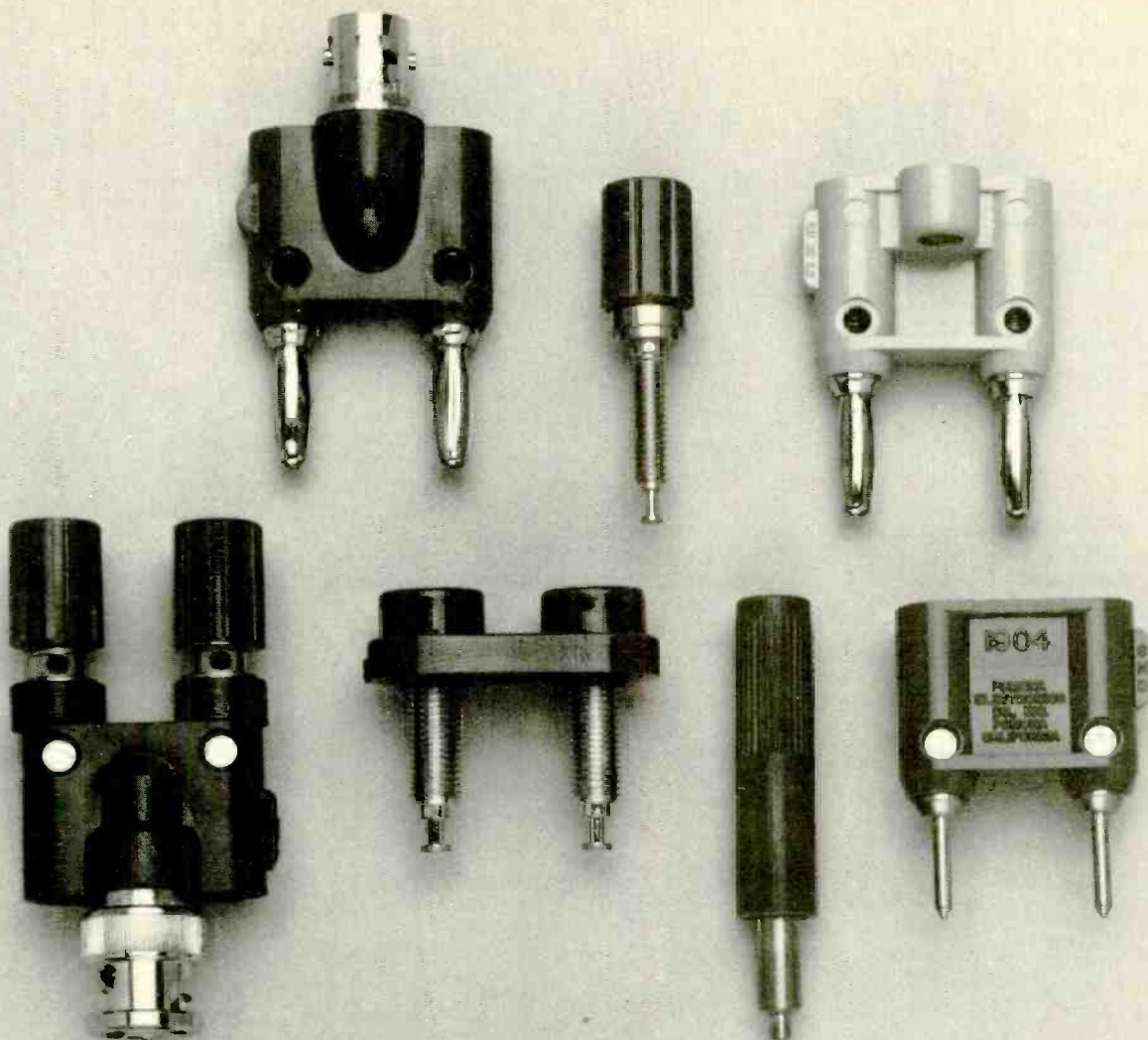

## THE OLDER WE GET THE MORE WE ADAPT.

When we started in 1951, we were sort of set in our ways. We lived, slept and ate nothing but banana plugs.

Then, our banana plug customers began asking us for other things. We listened, and adapted to meet their needs.

We've been adapting ever since 1951. Today, we manufacture and stock 180 different adapters to meet the changing needs of the industries we serve.

### FREE 1979 YEARBOOK CATALOG

Contains 100 pages of adapters, cable assemblies, jacks, plugs, boxes, sockets, connectors, jumpers, clips, probes, patch cords, wire, and much more. Yours free upon request. See our pages in EEM.



In fact, 25 pages of our new catalog are dedicated to adapters alone.

Get a copy for yourself, and get the whole story on the quality, value and specifications of Pomona Electronics adapters.

You'll also find nearly 640 other quality electronics products you know and trust.

Including, of course, banana plugs.

Although we've done a lot of adapting over the years, we've never stopped plugging away. ITT Pomona Electronics, 1500 East Ninth Street, Pomona, CA 91766 • Phone: (714) 623-3463 • TWX: 910-581-3822


AVAILABLE THROUGH YOUR FAVORITE  
ELECTRONIC PARTS DISTRIBUTOR

Pomona Electronics **ITT**

CIRCLE 38 ON FREE INFORMATION CARD



# BUILD THIS

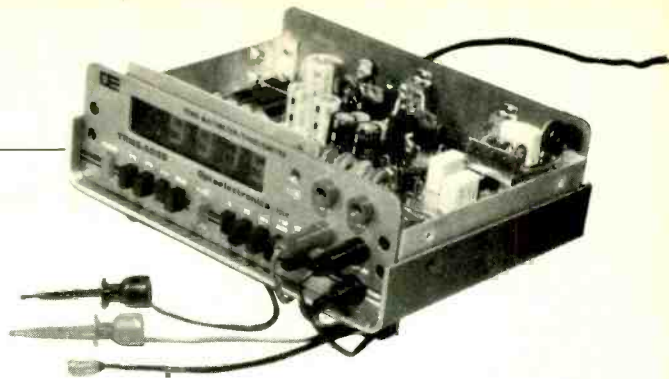

# 4<sup>1</sup>/<sub>2</sub> Digit Precision DMM

*This digital multimeter is ideal for the experimenter, engineer and service technician. Its basic accuracy is 0.05% and includes temperature and true-RMS capability.*

## BILL OWEN\*

THE TRMS-5000 IS A FULL-FUNCTION, state-of-the-art 4<sup>1</sup>/<sub>2</sub>-digit multimeter with many extra features that usually cost hundreds of dollars as options and accessories. In addition to the industry standard AC/DC amperes, AC/DC volts and resistance ranges, a precision temperature probe gives a switch selectable Celsius and Fahrenheit readout to .01°. A true-RMS-to-DC converter is used for accurate AC voltage and current measurements of complex waveforms from near DC to over 250 kHz. A 10-amp AC/DC current range is available through a separate protected input jack.

Lab bench multimeter features include jumbo 1/2-inch LED digits, uncluttered pushbutton controls and a rugged, yet attractive, aluminum case. Portability is maintained, however, by the convenient size and the optional rechargeable NiCad batteries. A precision band-gap Zener voltage reference and temperature tracking input attenuator network give better than .05% DC accuracy.

The heart of the multimeter is a new analog-to-digital converter IC set from Texas Instruments. The TL500C and TL502C 4<sup>1</sup>/<sub>2</sub>-digit converter features auto zero and true differential high-impedance inputs with autopolarity and overrange indication. A complete list of specifications appears in Table 1.

## Theory of operation

The heart of this digital multimeter is the analog-to-digital converter (ADC).

\*Product Engineer, Optoelectronics, Inc., Fort Lauderdale, Florida

TABLE 1—TRMS-5000 DMM / THERMOMETER SPECIFICATIONS

DC VOLTAGE				
Range		Max. Reading	Accuracy 18°–28°C, 1 Year	
2V		1.9999V	.04% ± 1d*	
20V		19.999V	.04% ± 2d	
200V		199.99V	.04 ± 2d	
1000V		1000.0V	.04 ± 2d	
Maximum Input Voltage: 1040V				
AC VOLTAGE				
		Accuracy 18°–28°C, 1 Year		
Range	Max. Reading	45 Hz–10 kHz	10 kHz–40 kHz	40 kHz–250 kHz
2V	1.9999V	.35% + 15d	.35% + 15d	3DB
20V	19.999V	.35% + 15d	1% + 15d	3DB
200V	199.99V	.35% + 15d	1% + 15d	3DB
1000V	1000.0V	.35% + 15d	2% + 15d	3DB
Crest Factor: 3				
Maximum Input Voltage: 1040V				
RESISTANCE				
		Accuracy 18°–28°C, 1 Year		
Range	Maximum Reading	High Ohms	Low Ohms	
2K ohm	1.9999K ohm	± .05% + 1d	± .10% + 15d	
20K ohm	19.999K ohm	± .05% + 1d	± .10% + 15d	
200K ohm	199.99K ohm	± .05% + 1d	± .10% + 15d	
2 megohm	1.9999 megohm	± .1% + 1d	± .15% + 15d	
20 megohm	19.999 megohm	± .3% + 2d	± .3% + 15d	
Maximum Voltage Output: High 1.5V Low .5V				
Maximum Input Voltage: 150V RMS				
Settling Time: 2 seconds to ± 1 digit of final reading except 10 seconds on megohm range.				

Specifications continued on page 39

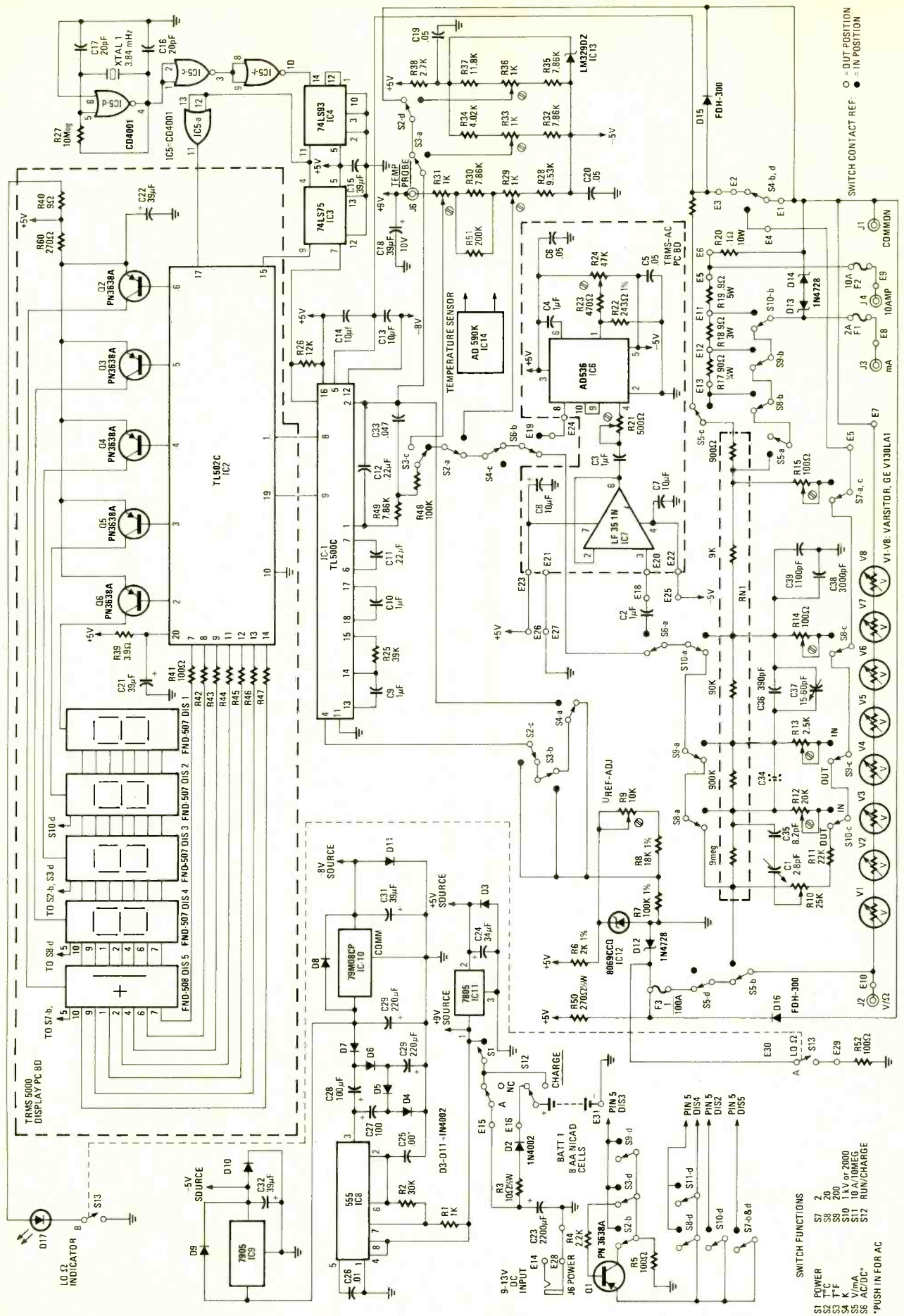


FIG. 1—SCHEMATIC DIAGRAM of the TRMS-5000 digital multimeter. One unusual feature is that on AC, it displays the true RMS value of any waveform, regardless of its complexity.



The ADC converts DC voltages between -2 and +2 volts applied to its input terminals into a digital count from -20,000 to +20,000. A display of 10,000 results from a one-volt input to the ADC.

The ADC employs the dual-slope method of conversion. The TL500C performs the analog processing while the companion TL502C digital processor provides the logic control signals for the TL500C as well as the counter and LED display drivers.

The entire conversion cycle timing is tied to the clock frequency generated by an external oscillator consisting of XTAL1, IC3, IC4 and IC5 (see Fig. 1). The 3.84-MHz crystal is divided down to 240 kHz by IC4. The resultant 240 kHz is a multiple of 60 Hz and is used to reject power-line-frequency interference. IC3 protects against false comparator triggering due to clock-frequency interference on the comparator input.

The precision voltage reference used is an Intersil 8069CCQ 1.2-volt band-gap Zener. Resistors R7, R8 and R9 form an adjustable divider to obtain 1.0000 volt for the reference input. Resistor R6 limits current through the reference to 2 mA.

#### Voltage measuring circuits

Because the ADC input is limited to +2 volts DC, additional signal-conditioning circuitry must be used for the extended multimeter functions and ranges. A voltage divider is used to extend the input voltage range up to  $\pm 1000.0$  volts while on any one range the ADC will see less than  $\pm 2$  volts.

The voltage divider consists of nine resistors connected in series across the multimeter's input terminals. Five are in the precision decade divider network RN1; the others are R17-R20. The total divider resistance is 10 megohms with each resistor having one-tenth the value of the resistor in series above it. When a voltage is applied to the multimeter's input terminals a current flows through the divider, producing a voltage across each resistor that is proportional to its resistance. Thus if 100 volts is applied across the divider, then 10 volts will be measured between the first and second resistors and 1 volt between the second and third and so on. Figure 2 shows the voltage divider with range switches to select the appropriate ratio; 1X for the 2-volt range, 10X for the 20-volt range and so on. A separate pole on each range switch is used to activate the appropriate decimal point in the LED display.

The multimeter's accuracy is dependent upon the ratio stability of the divider resistors. The first five decade resistors are contained in a thick-film network (RN1) in which the resistors track together to maintain their ratios over wide temperature variations. The bottom four discrete resistors plus the 900-ohm sec-

tion of RN1 are used as shunts in the current-measuring ranges.

For AC measurements, a converter circuit generates a DC voltage equal to the RMS (Root Mean Square) value of the applied AC voltage. Two poles of AC switch S6 are used to insert the converter in series with the ADC inputs. Most multimeter converter circuits simply compute the average rectified value of the input signal and are calibrated to display the equivalent sinewave RMS value. For other types of waveforms (square, triangle, pulse, complex, etc.) this type of conversion is inaccurate. The TRMS-5000 uses a true RMS converter that computes the RMS value of any complex waveform. This is a much more useful measurement because it is based upon the equivalent effective DC heating value of the AC voltage. The integrated circuit that performs this conversion is the Analog Devices AD536JH which actually solves the equation:

$$V_{rms} = \text{Avg.} \left[ \frac{V_{IN}^2}{V_{rms}} \right]$$

The AD536JH (IC6) measures AC signals from 10 Hz to over 100 kHz. This wide frequency range (many multimeters have only a few kilohertz of bandwidth) greatly enhances the usefulness of the

multimeter in making AC measurements at not only power line frequencies but throughout the audio frequency spectrum and beyond.

#### Current measurements

Both alternating and direct current measurements are made by placing a known resistor in the current path and measuring the voltage drop across it. The bottom five divider resistors shown in Fig. 2 are used for current measurements. A separate current input is used with the current-range switches. Because there is almost no current flowing into the ADC's analog inputs (input resistance is  $10^9$  ohms) the voltage across the current shunt resistors is seen through the 10 megohms in series with the inputs. The 10-AMP current range has a direct input, so that a 10-ampere current will not have to be switched. The power ratings of the current shunt resistors range from 3.6 milliwatts for the 900-ohm section to 10 watts for the 0.1-ohm resistor.

#### Resistance measurements

The TL500C ADC actually has two sets of analog inputs if the reference voltage and common inputs are considered. The ADC compares the unknown voltage at the input terminals to the known voltage at the reference input when making a

DC AND TRMS AC CURRENT				
		Accuracy 18°-28°C, 1 Year		
Range	Max. Reading	DC	45 Hz-10 kHz	10 kHz-40 kHz
2 mA	1.9999 mA	.6% + 2d	1% + 2d	1.5% + 2d
20 mA	19.999 mA	.6% + 2d	1% + 2d	1.5% + 2d
200 mA	199.99 mA	.6% + 2d	1% + 2d	1.5% + 2d
2000 mA	1999.9 mA	.6% + 2d	1% + 2d	1.5% + 2d
10 Amp	10.000A	.6% + 2d	1% + 2d	1.5% + 2d
Maximum Burden Voltage: 2V Crest Factor: 3				
TEMPERATURE				
	Celsius	Fahrenheit		
Range:	- 50.00° to + 150.00°	- 67.00° to + 199.99°		
Resolution:	.01°	.01°		
Accuracy:	± .5°	± .9°		
Voltage Standoff: Sensor tip to voltmeter common ± 200 volts				
GENERAL				
Display: Five 0.5" Red LED Digits Conversion Period: .1664 Sec Power Supply: Wall Plug Transformer-input 105-125 VAC; output 9 DVC @ 300 mA Dimensions: 3¼"H X 7¼"W X 6¾"D Weight: Approximately 2 pounds Input Impedance: 10 megohm shunted by less than 80 pF				
BATTERY OPTION				
Type: 8, AA NiCAD cells in holders, mounting inside the multimeter cabinet. Charge/operate switch mounts on rear of multimeter cabinet. Operation: 2 hours from full charge Charge Period: 12 hours				

\* ±% of reading + digits

measurement. This voltage ratio measuring ability of the converter is used in making resistance measurements. As shown in Fig. 3, a known reference resistor (one of the precision attenuator resistors) is placed in series with the unknown resistor at the input terminals. A precise 3.3 volts from Zener diode D12 is placed across the reference and unknown resistors and a current flows through them. The voltage drop across the known resistor is applied to the voltage reference and common inputs of the ADC while the voltage drop across the unknown resistor is applied to the analog + and - inputs. The meter's output then becomes the ratio between the reference resistor and the unknown resistor. For different ranges the reference resistor is changed from 1K up to 10 megohms.

### Temperature

The TRMS-5000 can measure temperature using an external sensor probe that plugs into a front panel jack (J6). The sensor is an Analog Devices AD590K temperature-dependent current source that generates 1  $\mu$ A-per-degree-Kelvin. The Kelvin temperature scale starts at absolute zero and has Celsius-sized degrees such that  $0^\circ\text{K} = -273.2^\circ\text{C}$ . The temperature sensor's current output is converted to a voltage, using scaling resistors R28, R29, R30 and R31. The output voltage (referenced to the -5-volt supply) from R29 is equal to 10 mV-per-degree-Kelvin while the output voltage from R31 is equal to 10 mV-per-degree Rankine (the Rankine temperature scale starts at absolute zero and has Fahrenheit-sized degrees). To generate Celsius and Fahrenheit output voltages, the Kelvin output must be offset by 2.732 volts and the Rankine output offset by 4.595

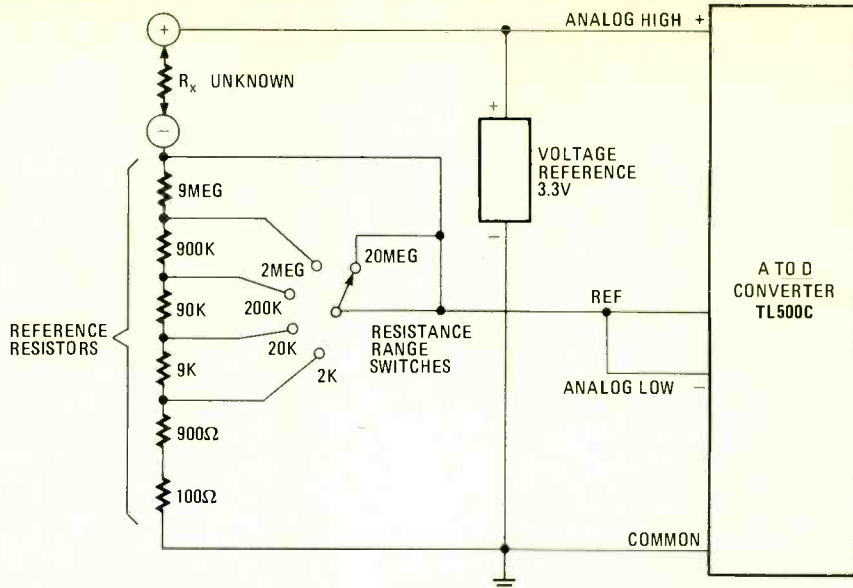


FIG. 3—WHEN MEASURING RESISTANCE, the unknown is in series with a selected known resistor across a precise reference voltage. The A/D converter determines the unknown value.

volts. IC13 is a 6.9-volt integrated circuit Zener reference. Its output is divided by R35, R36 and R37 to generate the Celsius offset and by R32, R33 and R34 to generate the Fahrenheit offset voltage.

When either the  $^\circ\text{C}$  or  $^\circ\text{F}$  switch is depressed, the ADC's analog inputs are switched to the correct temperature and reference voltage as shown in Fig. 4. A temperature range of  $-50.00^\circ\text{C}$  ( $-60.00^\circ\text{F}$ ) to  $199.99^\circ\text{C}$  or  $^\circ\text{F}$  is obtained with the  $4\frac{1}{2}$ -digit ADC. The sensor can be calibrated to within  $\pm 0.2^\circ\text{C}$  from  $0^\circ$  to  $100^\circ$  using trimmers R29 and R31. Because the AD590K sensor is a current source, it requires only a two-conductor cable and can be located over hundreds of feet away from the multimeter because it is not affected by voltage or noise pickup.

The multimeter (see complete schematic in Fig. 1) uses a 9-volt DC plug transformer/power supply to keep the 60-Hz line frequency outside of the instrument case. The circuit operates from three regulated power supplies, one positive and two negative. A 7805 voltage regulator (IC11) supplies +5 volts to the circuit, and because it supplies over 200 mA of current it is heat sunk to the cabinet's rear panel. A 555 timer (IC8) generates a 20-kHz squarewave that is AC-coupled and diode-clamped by a voltage doubler circuit to produce approximately -11 volts. A 79MO8CP regulator supplies -8 volts to the TL500C analog processor (IC1) and a 7905 regulator supplies -5 volts to the AD536 RMS-to-DC converter and the temperature circuit. An optional 10-volt NiCad battery pack consisting of eight size-AA cells is charged through R3 and automatically switched in on the absence of line power by D2. Diode D1 prevents battery discharge through the plug transformer.

The multimeter readout consists of four Fairchild FND507  $\frac{1}{2}$ -inch common-anode red 7-segment LED digits with one FND508  $\pm 1$  digit. The LED digits are multiplexed by the TL502C that directly drives the segments through current limiters R41 through R47 and drives the digits through external digit drive transistors Q2 through Q6.

### Overvoltage protection

A series string of eight metal-oxide varistors across the input divider will provide a short circuit path if 1040 volts or more is applied. Each varistor maintains a very high impedance until 130 volts is applied across it causing it to conduct. The varistors will pass 10 amps and fail as a short circuit if continuous overvoltage is applied.

Both the 2-amp (mA) and 10-AMP current inputs are fused and the 2-amp input

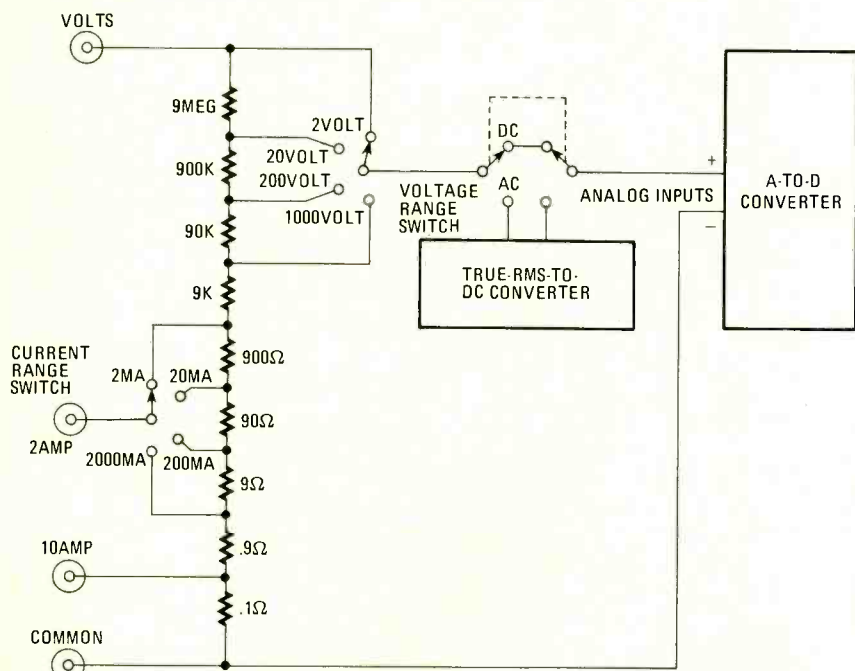


FIG. 2—VOLTAGE DIVIDER AND CURRENT SHUNTS. Resistor string is proportioned so maximum voltage applied to the A/D converter is 2 volts on any voltage or current range.



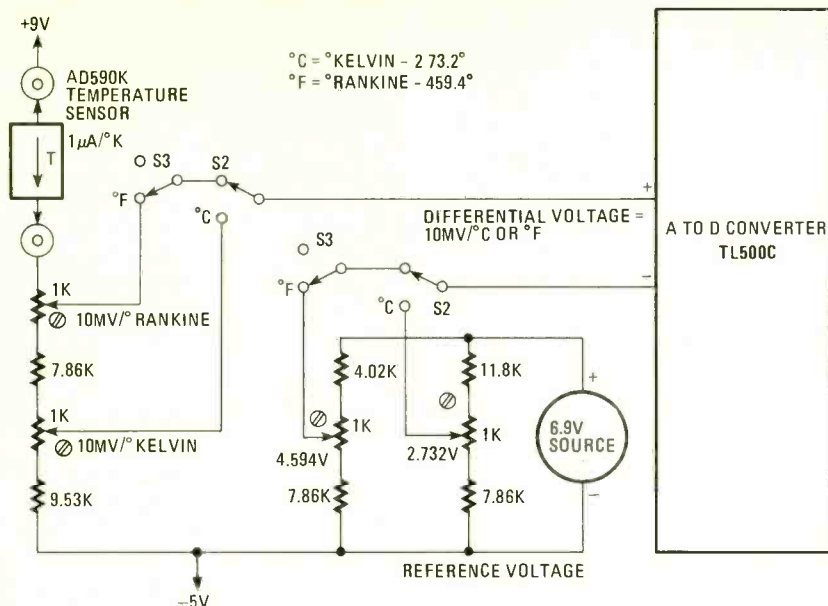


FIG. 4—BASIC DIAGRAM of circuit used for temperature measurement. The temperature sensor is a current source; passing 1  $\mu$ A-per-degree Kelvin. Readout is in  $^{\circ}$ C and  $^{\circ}$ F.

is diode clamped as well to blow the fuse if an overvoltage is applied to the low-current range shunts.

The ohmmeter circuit is fused for  $\frac{1}{100}$  ampere. Low-leakage diodes (D15, D16) steer currents around the reference resistor if a voltage is applied to the input terminals while measuring resistance.

### Making it work

The design of the multimeter's printed circuit board takes into account several factors that would otherwise seriously degrade performance. Ground paths are kept separate to prevent ground loops that cause offset errors that the ADC's autozero circuit cannot remove. Ground planes are used (where possible) to keep resistance in the ground returns as low as possible. The layout avoids putting supply or ground paths close enough to the high-impedance inputs or to the 10-megohm divider to allow leakage currents to cause offset errors. All insulation materials have extremely high resistance to prevent leakage paths. Digital and analog signal paths are kept apart and not parallel to each other on the PC board. The ADC's comparator output causes a problem if there is a path from it to any of the analog lines.

The multimeter's high-impedance input is susceptible to noise pickup, especially 60 hertz, which is almost universally present in our environment. The AC converter circuit's wide bandwidth makes it susceptible not only to 60-hertz pickup but to audio as well as RF frequencies. The TRMS-5000's heavy-gauge aluminum case provides shielding against noise pickup. There is also a filter on the analog inputs to the ADC, consisting of R48, R49, C12, and C33, that rejects 60-Hz voltages.

### Assembly

The TRMS-5000 multimeter is built

on three PC boards. The main board and the TRMS-to-DC converter board are double-sided. The foil patterns for the main board are in Figs. 5 and 6 and the parts layout is in Fig. 7. The two foil patterns for the TRMS board are in Figs. 8 and 9 and the parts are positioned as in Fig. 10. The four 7-segment displays and the polarity and overflow display are on a separate board. The foil pattern in Fig. 11 and the assembly diagram in Fig. 12 show how the readout goes together.

Begin assembly by soldering the components on the display, TRMS-AC and main printed circuit boards. Use the component placement drawings and the parts list to aid assembly. It is helpful to install jumper wires, diodes and resistors before the larger capacitors, trimmers, etc. The TRMS-AC PC board is double-sided but *not plated through, so component leads must be soldered to the foil on both sides wherever the foil comes right up to the lead*. The three PC boards are mated before the switches are installed. Assemble the front panel, rear panel and side

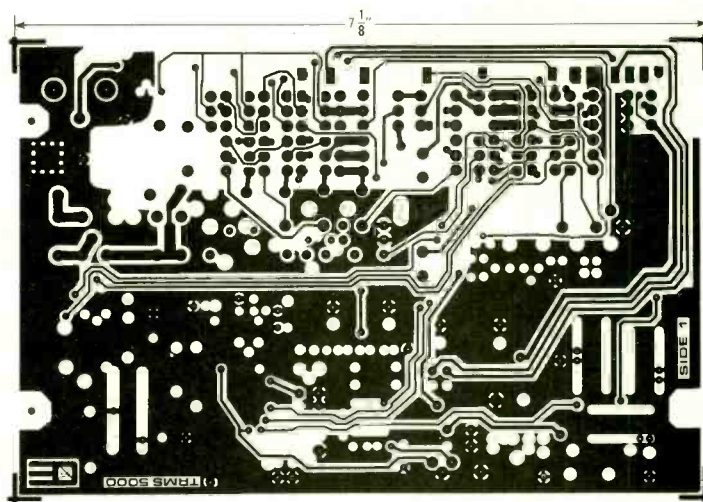


FIG. 5—FOIL PATTERN for Side 1, the top surface of the main board. Pattern is approximately one-half size. Enlarge to  $7\frac{1}{8}$  inches across.

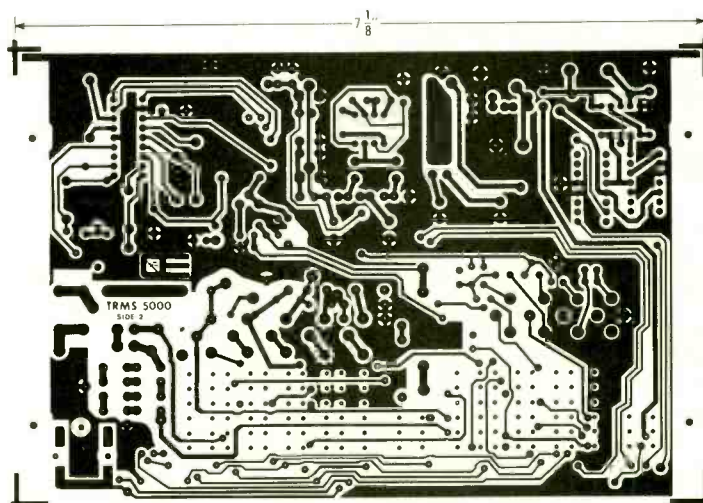


FIG. 6—PATTERN for the under side of the main PC board shown half-size. The pushbutton range and function switches are on this side.

## PARTS LIST

### Resistors, 1/4 watt, 5% unless noted

R1—1000 ohms  
 R2—30,000 ohms  
 R3—10 ohms  
 R4—2200 ohms  
 R5, R41—R47—100 ohms  
 R6—2000 ohms, 1%  
 R7, R48—100,000 ohms, 1%  
 R8—18,000 ohms, 1%  
 R9—10,000 ohms, 10-turn trimmer  
 R10—25,000 ohms, trimmer  
 R11—22,000 ohms  
 R12—20,000 ohms, trimmer  
 R13—2500 ohms, trimmer  
 R14, R15—100 ohms, trimmer  
 R16—100 ohms, 1%  
 R17—90 ohms, 1%, factory calibrated  
 R18—9 ohms, 1%, 3 watts, factory calibrated  
 R19—0.9 ohm, 1%, 5 watts, factory calibrated  
 R20—0.1 ohm, 1%, 10 watts, factory calibrated  
 R21—500 ohms, trimmer  
 R22—243 ohms, 1%  
 R23—470 ohms  
 R24—47,000 ohms, trimmer  
 R25—39,000 ohms, 1%  
 R26—12,000 ohms  
 R27—10 megohms  
 R28—9530 ohms, 1%  
 R29, R31, R33, R36—1000 ohms, trimmer  
 R30, R32, R35—7860 ohms, 1%  
 R34—4020 ohms, 1%  
 R37—11,800 ohms, 1%  
 R38—2700 ohms, 1%  
 R39—3.9 ohms  
 R40—9 ohms, 3 watts, 1%  
 R49—10,000 ohms  
 R50—270 ohms, 1/2 watt  
 RN-1—Temperature tracking precision resistor attenuator (Caddock 1776-231 7849)

### Capacitors

C1—2–8 pF, trimmer

C2, C3, C9, C10—1  $\mu$ F, Mylar  
 C4—4.7  $\mu$ F, tantalum  
 C5, C6, C19, C20, C26—.01  $\mu$ F, disc ceramic  
 C7, C8, C13, C14—10  $\mu$ F, 10 volts, tantalum  
 C11, C12—0.22  $\mu$ F, Mylar  
 C15, C18, C21, C22, C24, C31, C32—39  $\mu$ F, 10 volts, tantalum  
 C16, C17—20 pF, disc ceramic  
 C23—2200  $\mu$ F, 25 volts, electrolytic  
 C25—.001  $\mu$ F disc ceramic  
 C27, C28—100  $\mu$ F, 25 volts, electrolytic  
 C29, C30—220  $\mu$ F, 25 volts, electrolytic  
 C33—.047  $\mu$ F, polypropylene  
 C34—470 pF, disc ceramic  
 C35—8.2 pF  
 C36—390 pF  
 C37—15–60 pF, trimmer  
 C38—3000 pF  
 C39—1100 pF

### Semiconductors

Q1—Q6—PN3638A (National) or MPS 3638 (Motorola)  
 D1, D2—3-amp, 100 PIV diode  
 D3—D11—1N4002  
 D12—D14—1N4728, 3.3-volt Zener diode  
 D15, D16—FDH-300 low-leakage diode (Fairchild only)  
 D17—miniature red LED  
 V1—V8—V130LA1 varistor (GE)  
 DIS1—DIS4—FND570, 7-segment LED  
 DIS5—FND508, +1 LED display  
 IC1—TL500C analog processor (TI)  
 IC2—TL502C digital controller (TI)  
 IC3—74LS75 D-type flip-flop  
 IC4—74LS93 counter  
 IC5—CD4001—quad 2-input NAND gate  
 IC6—AD536JH—RMS-to-DC converter (Analog Devices)  
 IC7—LF351N bi-FET op-amp  
 IC8—555 timer  
 IC9—7905—5-volt regulator  
 IC10—79M08CP—8-volt regulator (National)

IC11—7805 5-volt regulator  
 IC12—ICL8069CCQ 1.22-volt reference  
 IC13—LM329DZ 6.9-volt reference (National only)  
 IC14—AD590KH temperature sensor (Analog Devices)

### Miscellaneous


S1, S6—2PDT pushbutton switch  
 S2—S5—4PDT pushbutton switch, interlocked  
 S7—S11—5PDT pushbutton switch, interlocked  
 S12, S13—D PDT miniature slide switch  
 J1—banana jack, black  
 J2—J4—banana jack, red  
 J5—pin-type DC power receptacle  
 J6—PC mount right-angle phono jack  
 XTAL1—3.84 MHz crystal  
 F1—2 ampere fuse  
 F2—10 ampere fuse  
 F3—1/100 ampere fuse  
 Thermometer test cable, power transformer—9 VDC, 300 mA plug type with hollow-pin plug. IC sockets: 2 8-pin, 2 16-pin, 1 18-pin, 1 20-pin, 1 14-pin. PC boards, cabinet and assorted hardware.

**Note: The following are available from Optoelectronics, 5821 N.E. 14th Ave., Ft. Lauderdale, FL 33334.**

**Factory-assembled multimeter with 1-year guarantee (TRMS-5000) \$279.95; complete kit (TRMS-5000K) \$199.00.**

**Set of three PC boards—all boards are glass epoxy, solder-plated with screened printed component layout—\$28.50. Set of all switches (13) \$20.00. TL500C and TL502C IC's \$16.95.**

**Include 5% for shipping, handling and insurance (to a maximum of \$10) with all orders. Florida residents add 4% sales tax.**

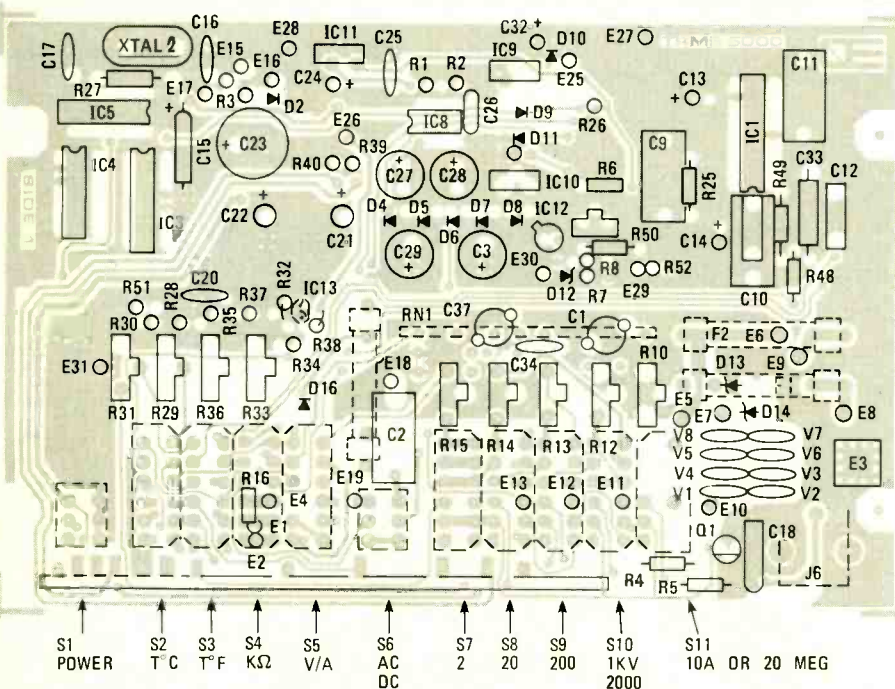

**FIG. 7—WHERE PARTS ARE PLACED on the main PC board. Most are on Side 1—the top side. Parts on the underside are outlined in dashed lines.**

rails, and then bolt the main PC board to the side rails. Align the foil fingers on the display board to the pads on the main PC board, and after checking alignment solder them together. The TRMS-AC PC board installs in the same way over the S6 switch area. Install the switches and then use No. 14 or No. 16 hookup wire to make the following connections:

From	To
J1	E1
J2	E10
J3	E8
J4	E9
E2	E3
E4	E5

Connect the following resistors between the points indicated below:

R20—0.1 ohm 10W—E1, E6  
 R19—0.9 ohm 5W—E11, E6  
 R18—9 ohm 3W—E12, E11  
 R17—90 ohm 1/4"W—E13, E12

Use hookup wire to connect the center pin of the power input jack to E10 and the bracket to E11.

Before applying power to the multimeter, check all parts for correct placement.  
*continued on page 79*



# Adaptive Noise Filter



**TIM SKORMOND AND  
GENE GARRISON**

*Simple to construct and operate, this dynamic variable-cutoff low-pass filter removes the snap crackle, and pop from your favorite records and tapes.*

MANY POPULAR NOISE-REDUCTION SYSTEMS are complementary in nature; i.e., the signal is processed by some compression technique prior to being recorded and then decoded by the equivalent expansion technique during playback. This leaves a large quantity of older recorded material, both disc and tape, unable to benefit from the noise-reduction circuits built into many hi-fi systems. Since many of us have treasured recordings that fall into this category, the need exists for a single-ended, add-on Adaptive Noise Filter that will permit us to enjoy these recordings at the same quality level we expect from encoded material.

A great deal of the noise in tape and FM sources is located in the frequency band from about 1 kHz to 7 kHz. This frequency band is also the area in which the human ears are most sensitive. Fortunately, when musical signals are also present in this same frequency band, at a few dB higher level, they effectively mask the noise. This makes it possible to use a variable-frequency low-pass filter in the audio channel to reduce the noise without audibly affecting the dynamics of the desired signal. If no signal is present, between musical passages for instance, a low-pass filter with a cutoff frequency of 800 Hz will substantially reduce the level of the audible noise. When music of sufficient amplitude is present at frequencies above 800 Hz, the filter opens to pass the music, and since the noise and music occupy the same spectral area, the noise is masked and the music faithfully reproduced.

## About the circuit

A block diagram of a suitable circuit is shown in Fig. 1. The circuit consists of

three major sections: a signal path, a control path and an LED bar-graph display.

The signal path is straightforward, consisting of two (one per channel) current-controlled low-pass filters with 6-dB-per-octave slopes. The two filters are designed to roll off at a corner frequency of 800 Hz with no input and at a corner frequency of 30 kHz when fully driven by the common control voltage.

Figure 2 gives a detailed look at the actual current-controlled filter circuits. Most existing variable filter designs use one or more field-effect transistors as voltage-controlled resistors in an active or passive filter configuration. This can lead to two troublesome problems. One is the need for some means of offsetting the difference in pinch-off voltages between individual FET's. A trimmer from each gate to a fixed bias voltage must be adjusted to calibrate each device. The second problem is the modulation of the drain-to-source resistance with moderately large input signals. This modulation quite often results in excessive distortion

at the filter output and, in some cases, will require another trimmer from each gate to minimize the effect.

Both of these pitfalls are successfully avoided in this circuit by using a new operational transconductance amplifier (OTA) as the controlled device. National Semiconductor has recently introduced the LM13600, a dual OTA with Darlington buffers and input linearizing diodes in a single 16-pin DIP package. The linearizing diodes compensate for the logarithmic characteristics of the input stage of the OTA, enabling it to pass relatively large signals with low distortion. (OTA circuits in the past have required very small input signals to obtain respectable distortion levels.)

The transconductance of the OTA's is set by the amplifier bias current (supplied to pins 1 and 16 in the case of the LM13600). The signal path of Fig. 2 uses this variable transconductance (conductance being the inverse of resistance) to implement a current-controlled filter (CCF).

The filter cutoff frequency is initially set at 800 Hz by the current through

**TABLE 1—SPECIFICATIONS (typical)**

<b>Attack time</b> (to within 10% of final value):	1 ms
<b>Decay time</b> (to within 10%)	50 ms
<b>Minimum bandwidth:</b>	800 Hz
<b>Maximum bandwidth:</b>	30 kHz
<b>THD</b> (1 kHz, 1 V <sub>RMS</sub> , max. sensitivity):	0.11%
<b>S/N ratio</b> re: 1 V <sub>RMS</sub> :	
800 Hz, BW, 20 Hz to 20 kHz:	—88 dBV
CCIR/ARM weighted:	—98 dBV
30 kHz, BW, 20 Hz to 20 kHz:	—85 dBV
CCIR/ARM weighted:	—87 dBV
<b>Effective noise reduction</b> (CCIR/ARM weighted cassette tape noise):	14 dB

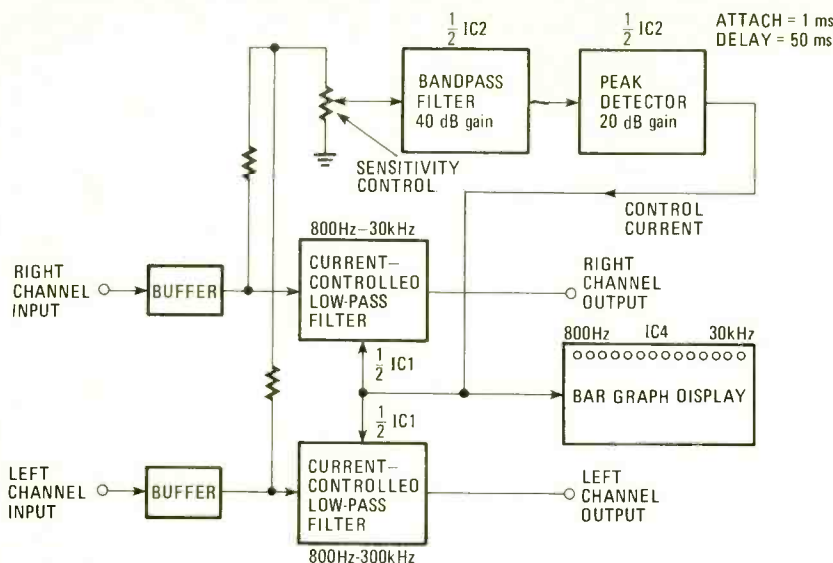


FIG. 1—BLOCK DIAGRAM of the adaptive noise filter. Audio signals are summed into the bandpass filter and then rectified to develop a control current that varies with noise in the signals.

R15. Additional current supplied through R16 by the control path circuitry

increases this —3-dB frequency to as high as 30 kHz, this bandwidth being

directly proportional to the applied current. Figure 3 shows the filter bandwidth vs. the amplitude of an 8-kHz input signal.

The control path consists of two basic stages: a bandpass filter with 40-dB gain and a specially configured peak detector with 20-dB gain. The LM387 operational amplifier was chosen because of its high-gain capability at 20 kHz and its high slew rate (required at the output of the peak detector).

The left and right input signals are summed together by resistors R17 and R18. Capacitor C7 provides a rolloff above 16 kHz, while a rolloff below 1.6 kHz is provided by C8. This low-level input signal is then amplified by the first half of IC2, whose gain is attenuated below 4.8 kHz by C10 with R20. R22, C11, C12, L1 and C13 couple the signal into the peak detector and provide additional frequency shaping, L1 being tuned to provide a filter notch at 19 kHz for use with FM stereo sources. Figure 4 shows the response of the control path.

## R-E TESTS IT

LEN FELDMAN

THE NR-2 NOISE FILTER WAS EVALUATED IN our laboratory, both for its measured characteristics and its performance as a single-ended noise reduction filter. Its principle of operation depends upon signals passing through variable-bandpass filters whose cutoff frequencies are made to vary between 800 Hz and 30 kHz, depending upon a control current derived from the original audio signal. While this is certainly not an original concept, the execution of the design is excellent. Attack time (confirmed as approximately 1 millisecond) and decay times (around 50 milliseconds) are ideally chosen so that, in use, the action of the filter is almost inaudible—except of course for the great audible improvement in noise. The NR-2 can be used to reduce noise in program sources such as records, weak FM signals and, most significantly, playback of cassette tapes that have not had the benefit of a two-sided noise reduction system such as Dolby or dbx encoding and decoding.

Figure 1 illustrates how different levels of swept signals (from 20 Hz to 20 kHz) affect overall response of the device. We see that when the device "senses" low-level signals

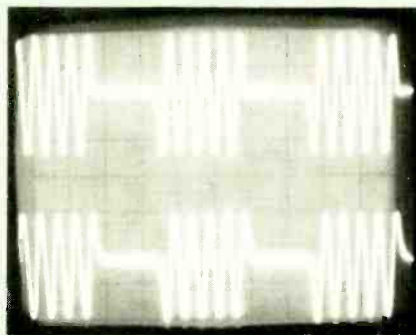


FIG. 2

(equivalent to noise) bandwidth is restricted. On the other hand, when high-amplitude signals, corresponding to musical sig-

nal content, are fed through the device, bandwidth is fully restored so that overall frequency response is virtually flat to 20 kHz.

Figure 2 illustrates the attack and decay times of the device. A tone burst, consisting of several cycles at 1 kHz, was fed through the filter. Upper trace is the input signal, while lower trace is the output signal. Note that the first cycle of each burst, whether negative going or positive going, is accurately reproduced at the output, while the last cycle in each burst is somewhat retarded in the output trace, indicating the slower but desired decay time of the device.

Table 1 summarizes our measured findings as compared with the author's claimed specifications.

TABLE 1

SPECIFICATIONS	DESIGNERS' CLAIM	MEASUREMENTS
Attack Time (ms)	1.0	0.8
Decay Time (ms)	50.0	40.0
Minimum Bandwidth (Hz)	800	800
Maximum Bandwidth (kHz)	30	30
THD (1V, Max. Sensitivity) (%)		
1 kHz	0.11	0.12
20 Hz	N/A	0.3
20 kHz	N/A	0.11
S/N (re: 1V)		
800 Hz B.W.	88 dB (98 Wt'd)*	90 dB (95 Wt'd)
30 kHz B.W.	85 dB (87 Wt'd)*	85 dB (90 Wt'd)
Effective Noise Reduction (tested with cassette tape)	14 dB (Wt'd)*	12 dB (Wt'd)*

\* Small differences in weighted results arise from the fact that the author used CCIR/ARM weighting whereas we used IHF "A" weighting, but, as can be seen, unweighted results are as good or better than claimed.



FIG. 1



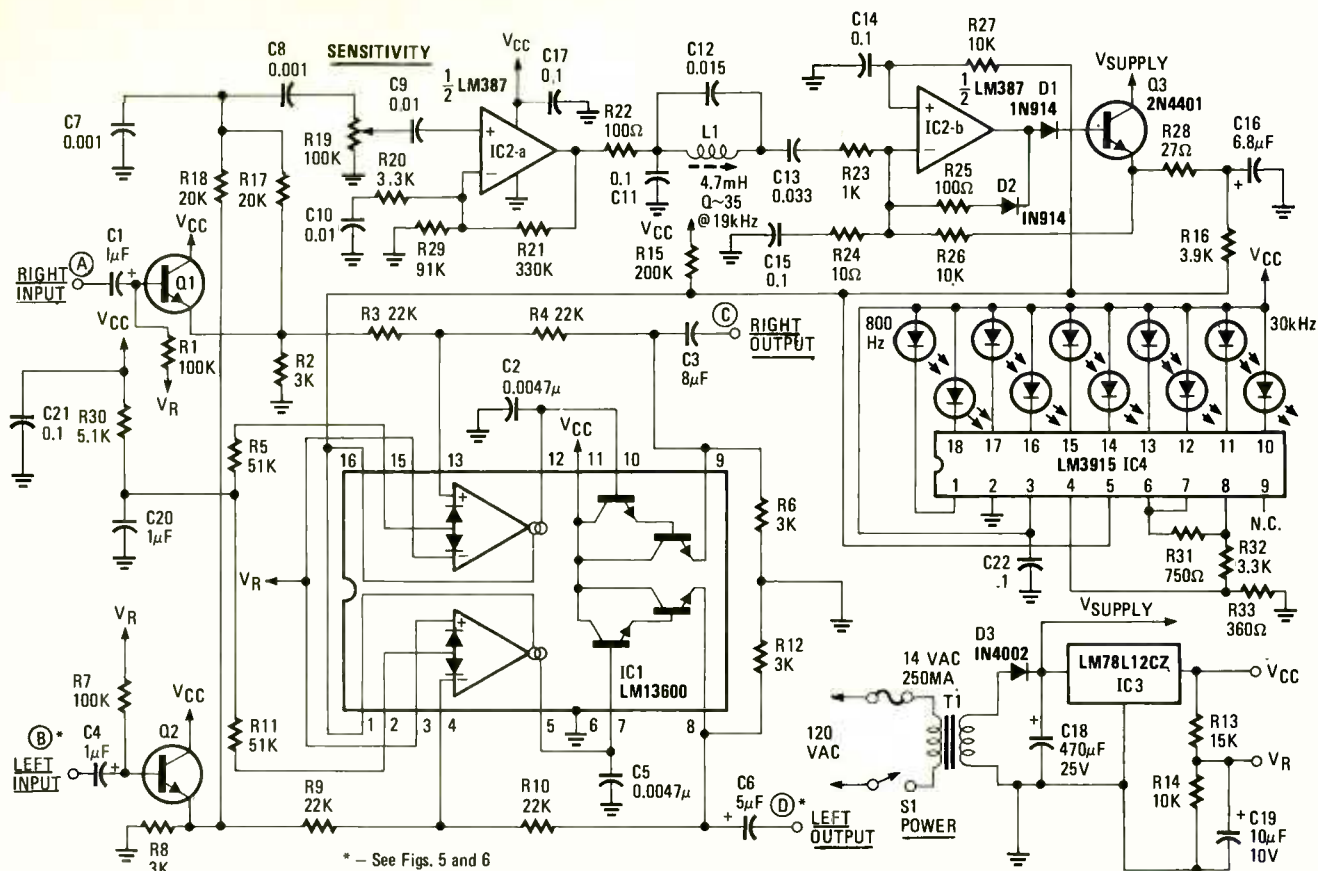


FIG. 2—SCHEMATIC DIAGRAM of the current-controlled variable-bandwidth low-pass filter circuits. Bandwidth is controlled by a current developed from the input signal.

The peak detector amplifies the AC output from the frequency-selective control amplifier and converts it into a DC voltage at the emitter of Q3. Resistor R28 sets the system attack time or charging rate into the peak-detector storage capacitor, C16. Capacitor C16 is discharged at a much slower rate (decay

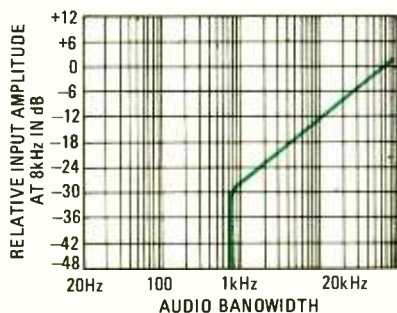


FIG. 3—FILTER BANDWIDTH and how it varies with the input of an 8-kHz signal.

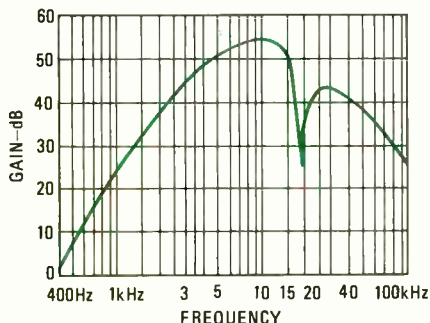


FIG. 4—RESPONSE of the final control path sensitivity vs. input frequency.

time) by the current drains of the two CCF's through resistor R16. Resistor R27 sets the initial no-signal DC level at the peak-detector output.

The attack and decay times and response characteristics were chosen with great care as they determine the subjective effects of the filter. An attack time of 1 ms was selected because it is fast enough to accommodate the response time of the human ear and yet slow enough to be relatively insensitive to "clicks" and "pops" on the record surface. The decay time was set at 50 ms so the filter could close quickly after the passing of high-frequency musical information and thus pass a minimum of noise. A shorter decay time would cut into the natural reverberation time of some program sources, making them sound "sterile" or flat.

The third section of the Adaptive Noise Filter is the bandwidth bar-graph display. A bar graph was used instead of a meter because of the millisecond response time of the control signal. The National LM3915 bar-graph display driver was chosen as it requires only a few external parts and contains all the necessary circuitry for a 10-point logarithmic bar-graph display. The common control voltage at the top of R16 has upper and lower limits of 9.3 VDC and 1.1 VDC, respectively. Therefore, the upper and lower limits of the LM3915 are set accordingly at pins 4 and 6 (internal logarithmic resis-

tor string between these two pins sets the DC levels at which each of the internal comparators drives its associated LED). The left-hand LED corresponds to an 800-Hz bandwidth and the right-hand LED corresponds to a 30-kHz cutoff. The LED's between these two extremes represent steps of approximately 1.5 times the frequency display by the preceding step.

A logarithmic display was selected because it was most indicative of the audible

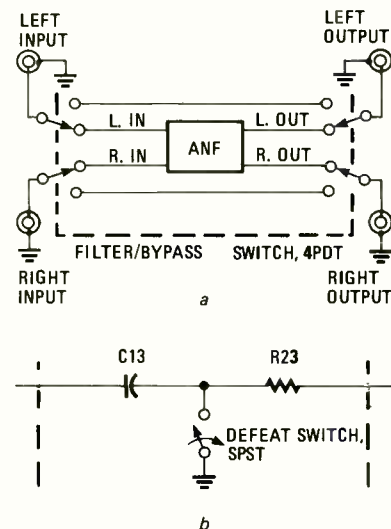


FIG. 5—CONTROL SWITCHING illustrating how the adaptive noise filter can be switched in and out of play-only circuit.

## PARTS LIST

All resistors 5%, 1/4 watt unless otherwise noted

R1, R7—100,000 ohms  
R2, R6, R8, R12—3000 ohms  
R3, R4, R9, R10—22,000 ohms  
R5, R11—51,000 ohms  
R13—15,000 ohms  
R14, R26, R27—10,000 ohms  
R15—200,000 ohms  
R16—3900 ohms  
R17, R18—20,000 ohms  
R19—100,000 ohms, miniature pot, audio taper (Clarostat 389 N 100K-Z)  
R20, R32—3300 ohms  
R21—330,000 ohms  
R22, R25—100 ohms  
R23—1000 ohms  
R24—10 ohms  
R28—27 ohms  
R29—91,000 ohms  
R30—5100 ohms  
R31—750 ohms  
R32—360 ohms

### Capacitors

C1, C4, C20—1  $\mu$ F, 16 volts electrolytic, radial leads  
C2, C5—.0047  $\mu$ F, 50 volts, Mylar, 10%  
C3, C6—5  $\mu$ F, 10 volts, electrolytic, radial leads  
C7, C8—.001  $\mu$ F, 50 volts, ceramic disc  
C9, C10—.01  $\mu$ F, 50 volts, ceramic disc  
C11, C14, C15, C17, C21, C22—0.1  $\mu$ F, 50 volts, Mylar  
C12—.015  $\mu$ F, 50 volts, Mylar, 5%  
C13—.033  $\mu$ F, 50 volts, Mylar  
C16—6.8  $\mu$ F, 25 volts, tantalum, 10%, radial leads  
C18—470  $\mu$ F, 25 volts, electrolytic, radial leads  
C19—10  $\mu$ F, 10 volts, electrolytic, radial leads

### Semiconductors

D1, D2—1N914  
D3—1N4002  
Q1, Q2, A3—2N4401  
IC1—LM13600 dual operational transconductance amplifier (National)  
IC2—LM387N dual low-noise preamplifier (National)  
IC3—LM78L12CZ (National)  
IC4—LM3915N logarithmic bar-graph display driver (National)  
LED1—LED10—NSL57124 rectangular LED for bar graph (National)

### Miscellaneous

S1—miniature SPST toggle switch  
S2, S3—miniature 4PDT toggle switch  
T1—power transformer, 14 VAC, 250 mA (Triad F-112X)  
L1—adjustable inductor, 4.7 mH, Q = 35 at 19 kHz (TOKO CLN20 740 HM)  
J1—J8—panel-mount RCA-type phono  
F1—1/4-amp slow-blow fuse  
Fuse holder, line cord, PC boards, control knobs, hardware


The following parts are available from Advanced Audio Systems, PO Box 24, Los Altos, CA 94022:

DX-244 (NR-2) complete kit including case—\$69.95

DX-245 (NR-2) main and display PC boards—\$19.95

DX-247 (NR-2) component kit; includes D1, D2, D3, IC1, IC2, IC3, IC4, Q1, Q2, Q3 and L1—\$27.50

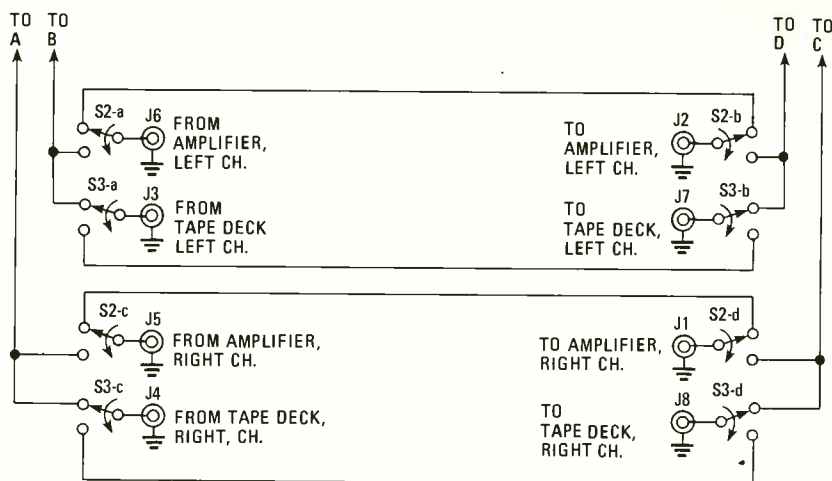
California residents add state and local taxes, as applicable.



SWITCH S2: PRE-TAPE/BYPASS  
SHOWN IN BYPASS POSITION

SWITCH S3: POST-TAPE/BYPASS  
SHOWN IN POST-TAPE POSITION

FIG. 6—IDEAL SWITCHING ARRANGEMENT is simple and flexible. User must be careful not to place both switches in non-bypass positions simultaneously.

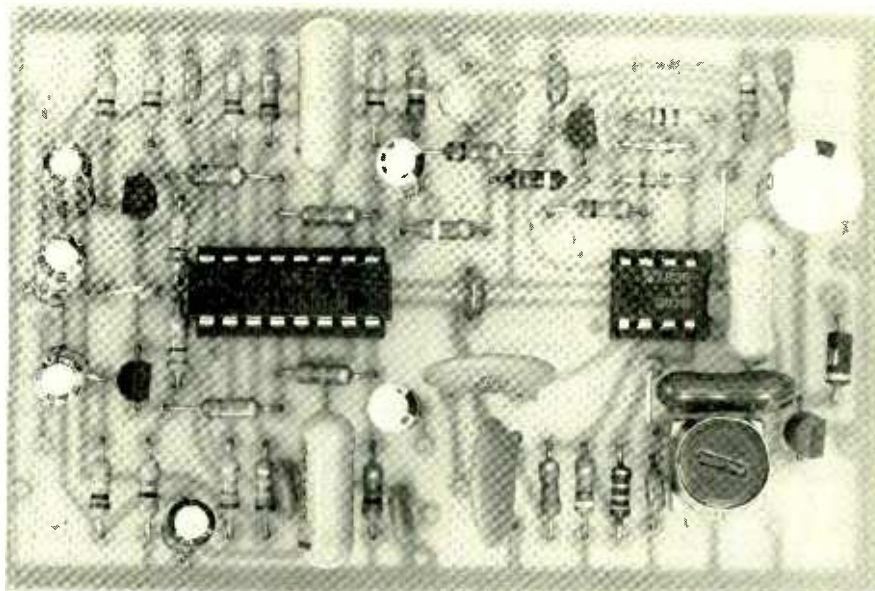

TOP VIEW OF THE PC BOARD shows the locations of most of the components. Parts not shown include the bar-graph display and power supply.

action of the filter. It should be noted that the LED bar graph does not indicate signal level, but rather the instantaneous bandwidth of the two filters and, as such, should not be used as a signal-level indicator.

If the Adaptive Noise Filter is used for only one source, such as for tape playback, then a BYPASS switch will be the only switching needed in addition to the power switch. Figure 5-a shows a suitable arrangement. Alternatively, the filter may be defeated by switching the junction of C13 and R23 (Fig. 2) to ground, as shown in Fig. 5-b, thereby forcing the filter to a constant 30-kHz bandwidth. This approach has the advantage of requiring only a single-pole switch as opposed to the four-pole switch and associated wiring required for the straight-wire bypassing.

A more flexible system, as used in the

prototype model, can be obtained by providing for insertion of the filter either before or after the tape deck (record or playback). The rather unusual switching scheme shown in Fig. 6 was selected for its relative simplicity. A setup having a PRE TAPE/POST TAPE and a FILTER/BYPASS switch would require one four-pole and one eight-pole switch. The scheme of Fig. 6 only requires two four-pole switches, but the user should be careful not to place both switches in the non-bypass positions simultaneously.

Printed-circuit construction techniques are used in the assembly of the prototype adaptive noise filter. Foil patterns for the printed-circuit boards used for the filter and associated display board will be published next month along with complete construction details and calibration and operating instructions.

*continued next month*



## Home Reception *via* SATELLITE



*An introduction to domestic satellite communications; with details on how those illusive TV signals are pulled from space*

**ROBERT B. COOPER, JR.**

YOU MAY BE TOO YOUNG TO HAVE BEEN A PART OF THE EXCITING 1946-1952 "dawn of television era." I was a youngster in upstate New York who spent his high school years souping up 630-type chassis, building cascade and cascode signal boosters with 6BQ7's and trying out every antenna I could lay my design hands on—from stacked 10-element Yagi arrays to 12 wave-length rhombic antennas.

Television happened for me at an infectious age. A paper route helped me maintain a library of that era's **Radio-Electronics** and a host of other valuable trade magazines that were documenting the fast changing world of television technology. Summer odd jobs and caddying at the golf course enabled me to buy a minimum tubing, wire, electronics parts and bargain-basement-priced 630 chassis. In later years I would sometimes wish that I had been born "only five or ten years sooner" so that I would have been old enough by 1950 to have really been in a position to participate fully in the television revolution. "But alas" I would say to myself "that's it for the television revolution. Now that it's established nothing will come along to change it 'that much' so I'll just have to find my niche someplace else."

And so it was until 1975 when I discovered a whole new television revolution just getting underway—satellite TV transmission and reception. And I have been tracking it, playing an active part in it and enjoying it ever since.

### Forget everything you know

If you are in the television business to make a living, you probably think you know all there is to know (or need to know) about reception techniques and equipment. You've tracked down ghosts and explained away weather-caused co-channel interference. You've doped out MATV systems and traced bad components. You've been stuck with an inventory full of "brand name" parts that overnight went off the market, and you own every Sams *Photofact* that they ever printed. Forget it all!

First, let me tell you a bit about the TV reception in my present home, some 20 miles outside of Oklahoma City. We have the usual three major networks as well as PBS (Public Broadcasting System). And like a good majority of the United States, that is all we have (or *had* until the fall of 1977).

In August 1977 I placed some 1 × 2 stakes in our sidelawn and backhoed enough clay to let me refill the holes with a few pieces of properly formed steel and around 4 yards of concrete. Then, in September 1977, I brought in a crew of friends and this funny-looking, 3000-lb., all-steel saucer-shaped apparatus, and in about eight hours we had the saucer mounted on a set of steel posts. (See Fig. 1.) The saucer pointed more or less south of us and up into the sky.

The same evening I sat down with a special receiver and watched the evening news live from Vancouver, British Columbia; a baseball game from Atlanta, GA; and a movie via some-





FIG. 1—SATELLITE RECEIVING ANTENNA as it is being installed on steel mounting posts.

thing called HBO (Home Box Office).

My home is located just 18 airline miles from our local network and PBS stations, and I had always been able to receive the best-looking TV pictures this side of a network monitor, up until that fabled September 1977 evening. Until you have had a high-quality color monitor plugged directly into the video output of a satellite TV receiver and observed 54-dB signal-to-noise-ratio video produced by people who really care about how good it looks when it leaves their studio, you simply have not seen how good NTSC color reception can really be!

Let me digress a bit and explain what satellite television is all about, how it works and why it works the way it does.

#### How it began

The first man-made satellite was Russia's SPUTNIK (1) in the fall of 1957. It shook a lot of people up as you may recall. The idea of a ton or so of steel and electronics going around and around the world and crossing our country beeping in Morse code and doing who knows what else spurred the U.S. into the space race. We responded by launching a U.S. Airforce satellite named SCORE in December 1958, and to one-up the Russians, we added a prerecorded message from the President of the United States who welcomed in the American space age and the Christmas season.

TABLE 1—INTELSAT GEOSTATIONARY satellites operating in the 3.7- to 4.2-GHz downlink frequency band are clustered in three separate areas.

Longitude (west)	Name	Year Launched	Service Status
1°	I-IV-F7	1973	Secondary
4°	I-IV-F2	1971	Reserve
19.5°	I-IVA-F4	1977	Reserve
24.5°	I-IVA-F1	1975	Primary
29.5°	I-IVA-F2	1976	Reserve
34.5°	I-IV-F3	1971	Secondary
181°	I-IV-F4	1972	Reserve
186°	I-IV-F8	1974	Primary
297°	I-IVA-F3	1978	Primary
298.6°	I-IV-F1	1975	Primary
300°	I-IV-F5	1972	Reserve
300°	I-IV-F6	1978	Reserve

SPUTNIK, SCORE and all the satellites that followed them through 1963 had one common fault. They were launched into a "low orbit" and (with reference to a point on earth) they were always moving. To receive messages from or transmit messages to these "low orbit birds" required that the stations working with the satellite know rather precisely its orbit path and the timing of that path, and then be prepared to track the satellite as it came over one horizon, moved in an arc through the sky and finally disappeared beyond the opposite horizon.

In 1963 space technology and rocket power progressed, and SYNCOM, designed and built by the Hughes Aircraft Corporation, was launched—the world's first geostationary (or geosynchronous) satellite. (A geostationary satellite has an orbit directly above the equator and an orbital velocity that matches the rotational velocity of the earth. (See Fig. 2.) In this way, the satellite appears to remain stationary in the sky with respect to a point on the earth.) SYNCOM was an experiment. It provided the capacity to relay either a *single* TV channel or 50 separate telephone conversations; from its orbit above the Equator between Africa

and South America, it interconnected North America and Europe with their first real-time (live) television transmissions. By 1965 the geostationary satellite looked like a winner, and 19 countries joined to form something called Intelsat, a consortium of nations that would fund the launching of a series of satellites.

#### The Intelsat world

With nearly 14 years to grow, the Intelsat system is relatively mature. Today, more than 100 nations belong to the system, which consists of 12 separate satellites located in three distinct "groups." Commercial Intelsat installations cost in the megabuck region, but amateur builders of backyard terminals have successfully tapped into the Intelsat circuit, using surplus-salvaged parabolic antennas as small as 8 feet in diameter and with investments well under \$500, as we'll discuss in some detail.

As mature as Intelsat is today, it is in a constant state of evolution. The present satellite series is generally of the so-called Number IV (or "4") class, indicating there have been three previous series. Table 1 lists where they are located; a sharp eye will spot the three "clusters" in operation: One is over the Equator in the Pacific Ocean; another over the Indian Ocean north of the Seychelles Islands; and a third between the tip of Africa and the tip of South America. Each location has as a minimum a "primary" and a "reserve" satellite, but heavy Atlantic and Indian Ocean traffic has resulted in additional satellites in these areas. In 1971 the Intelsat consortium agreed that identical-frequency satellites should be spaced over the equator in 4- to 5-degree increments. In this fashion the large parabolic ground-receiving antennas could intercept the desired satellite's signals without interference from adjacent-position satellites, even though both would be operating on the same frequency simultaneously. The present series IV satellites will begin to be replaced with a new, advanced family of satellites during 1979, the Intelsat V series. We'll look at these later on.

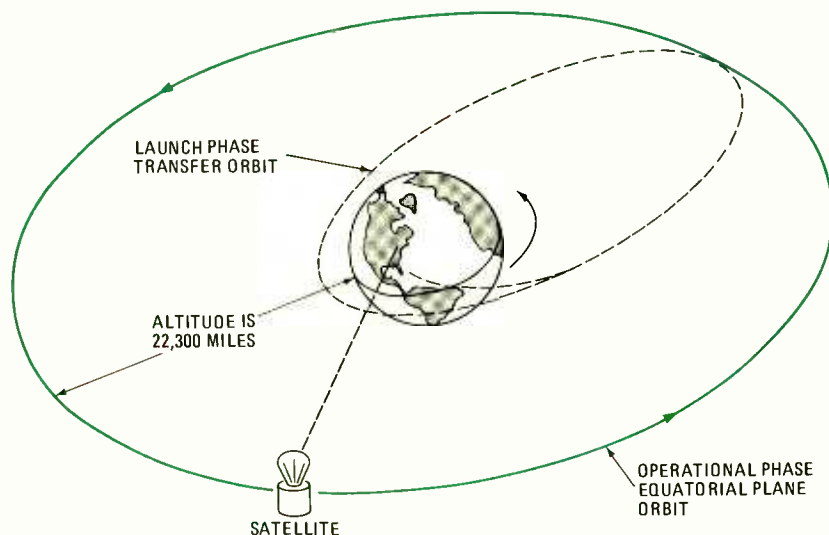


FIG. 2—GEOSYNCHRONOUS ORBIT is achieved by launching satellite into a highly elliptical orbit that is followed by a transfer to an equatorial plane orbit. Satellite's position over equator is typically maintained to  $\pm 0.1$  degree.



# GADGETS— EALLY WORK?

feedline for coupling had no effect. Interference bars were again apparent on several TV channels, with or without the CB filter attached. The trap circuitry is a series L-C filter, designed to short-circuit much of the 27-MHz CB signal, but it has no effect at TV frequencies. The schematic is shown in Fig. 3. Similar to the filter described above, it would be effective only in preventing front-end overload by a powerful 27-MHz CB signal. In fact, if an interference filter were designed to attenuate interfering signals on TV channels, it would also diminish the TV signals since they occupy the same frequencies.

## Ghost eliminator

Phantom borders that accompany the TV picture as a smear or additional outline alongside the primary image are due to phase delay—two identical picture signals arriving slightly apart in time. As a result, the sweep lines that draw the picture on your screen trace two sets of images; one is usually weaker because ghosts are caused by a reflection of the signal from nearby objects, arriving at the antenna both weaker and at a later time than the direct signal from the broadcasting station.

The ghost eliminator shown in Fig. 4 was installed and adjusted as directed; the ghosts were unaffected. Suspecting that the unit was labeled backwards, I reversed the leads, but the ghosts remained.

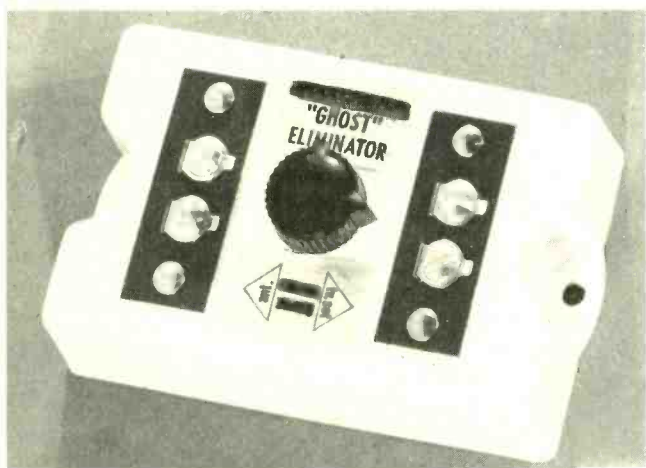


FIG. 4—GHOST ELIMINATOR is inserted in antenna lead-in and adjusted for best picture.

The ghost eliminator is an L-pad (see Fig. 5) consisting of carbon resistances that remain essentially noninductive throughout the VHF range; UHF performance is unpredictable. Because the device is a variable attenuator, it makes signals weaker; and weaker signals are more vulnerable to electrical



FIG. 5—GHOST ELIMINATOR is actually an L-pad attenuator as shown in a. Equivalent circuit when adjusted for minimum signal is shown in b. When adjusted for maximum signal, equivalent circuit is shown in c.

interference. Although it is stated on the eliminator's blister pack that the unit remains at a constant 300 ohms, it does not; the resistance of the device I tested varied from 300 to 7000 ohms at the TV terminals.

While it is dangerous to make generalizations, no inexpensive add-ons can take the place of a good antenna system; an outside antenna is always better than an inside antenna; interference is best eliminated at its source.

This article is not meant to be a blanket indictment of all TV accessories. High-quality picture-enhancing devices such as antenna preamplifiers, cavity wavetraps, etc., are available but at a substantially higher cost. However, the bottom line is: Use a good antenna and transmission line, and additional gadgets will rarely be necessary.

## TV/FM splitters

A splitter is a coupling device that permits you to hookup two sets to one antenna. Since most TV antennas are rather broadband in nature, they work quite well on the FM broadcast band as well as on TV channels; so why not use this feature for your benefit? Since most stereo receivers have a 300-ohm (two screws) antenna input, it is a simple matter to run a length of TV twin-lead from the receiver to the TV antenna splitter and enjoy greater quieting, stronger distant reception, and less flutter and fade. Of course, the FM reception is enhanced in the same direction as the TV antenna is pointed. The TV reception will be virtually unaffected, since splitter loss is minimal. Acceptable units are mass-produced for most retail outlets and large chain discount houses. They are all fairly identical (see Fig. 6) so shop for price; the average price for a typical two-set coupler is from \$3.50-\$4.00. (Be aware that some of the better TV antennas are designed to trap out FM signals—thus eliminating them as a source of interference.—*Editor*)

## Privacy earphone attachments

Although not all TV sets come with earphone jacks, many imported portable sets do. Make sure that the plug size is compatible with the jack on your set (most measure  $\frac{1}{8}$  inch, and adapters are available). If there's no earphone jack on your set, it is a relatively straightforward procedure to cut off the speaker



FIG. 6—TYPICAL TV/FM SIGNAL SPLITTER manufactured by the Finney Company.

lead inside the TV set and attach the adapter; before undertaking this minor surgery make sure instructions are included with the adapter. (Modern TV sets frequently do not have power transformers and, therefore, have a "hot" chassis. The audio output stages are similarly transformerless and the speaker leads can present a potentially dangerous shock hazard.—*Editor*)

Such units are sold for convenience, not hi-fi quality. They are available from the same sources as TV/FM splitters.

### Antenna boosters

These little preamplifiers make a weak signal stronger, and strong signals stronger. They improve a snowy picture. Outdoor antenna-mounted preamplifiers are recommended over indoor antenna boosters, since you want a stronger signal to come down the antenna transmission line and don't want to amplify the



FIG. 7—TYPICAL ANTENNA BOOSTER that is mounted on the antenna mast itself. Made by Channel Master.

interference picked up by the lead-in itself. A typical booster is shown in Fig. 7.

If you are plagued with weak-signal reception, a booster will probably help. Make sure that you purchase one that is weather-proof, with all-channel capability (if you watch UHF transmissions), and that you cover the terminals with a good lacquer or silicone rubber caulk to retard corrosion after you have installed and tested the booster. Unit prices vary from \$30 to \$70.

### Line-noise filters

Noise from motors, fluorescent lights and dimmers, and other sources of AC line interference constantly arrive at the TV line plug as voltage spikes. These interfering electrical pulses may not get filtered out by the TV set's power-supply circuitry and, as a result, show up as a tearing of the picture, or may be even heard through the speaker.

Inexpensive (\$1.50–\$6.00) filters usually consist of a plug and receptacle housing containing a capacitor or two. The TV line plug is inserted into the receptacle, and the unit is plugged into the wall. The line-noise filters are almost always either totally ineffective or inadequate because most electrical interference arrives through the antenna. An external ground should always

be present (and rarely is); more sophisticated (and more expensive) units containing inductor coils are more likely to provide some relief from power-line noise.

### Color purifiers

Color TV pictures are very sensitive to magnetic fields. Iron picture-tube envelopes, nearby steel hardware, etc., all may cause potential color distortion. If a TV set has been recently moved, transported for repair, exposed to strong electric motor fields, exposed to a nearby lightning strike or a host of other unexpected sources of magnetic energy, its components may have become magnetized and could degrade the purity of color distribution on the face of the picture tube. Color purifiers (also called *degaussers*) are simply multiturn loops of wire which, when plugged into the AC power line, produce a strong, fluctuating magnetic field capable of neutralizing the vestigial magnetism on the chassis parts.

At a cost of \$5 or \$6, this device is not a bad investment if it is properly designed and can deliver a strong enough demagnetizing field. Only a test of the unit will confirm this.

### Wall-plate terminals

Many houses are built with TV lead wire "stubbed in"—i.e., twin-lead is left dangling through a hole in the wall for connection. Alternately, a more cosmetic plastic cover plate is connected to the lead-in and affixed to the wall to cover the hole. Connections are then made to the TV set by a short length of twin-lead that is either attached to screw terminals or plugged into the wall plate.

The wall-plate terminals offer very little loss to the TV signals, and are relatively inexpensive. They are worthwhile if you want to give a finished look to the TV installation. Some wall plates contain internal splitters for FM reception as well.

### Wall-through tubes

There are many ways to bring a transmission line into a house from an external antenna: through a louvered vent, a hole under the eaves, or via a hole in the wall. But along with the hole comes another problem: How do you keep bugs, rain, or even temperate air from penetrating the house? The wall-through tube provides a seal. (See Fig. 8.) Consisting of a plastic tube with



FIG. 8—THROUGH-WALL TUBES serve a dual purpose—they protect the lead-in at the point of entry into the house, while covering the hole in the wall. Available from several sources.

finished and adjustable ends, the unit is used to line the hole drilled for the lead-in. Of course, a larger hole must be drilled than would be required for the wire alone, but the device provides isolation and insulation from both the wall and the outside. At a cost of \$2, it is a worthwhile investment.

### Lightning arresters

Solid-state TV sets are far more vulnerable to failure from high-voltage spikes than the old tube sets. Even a nearby lightning stroke can induce enough voltage in a TV antenna line to destroy tuner components. A lightning arrester probably won't protect your set from a direct hit, but it should guard it from nearby lightning during an electrical storm.

A variety of arresters are available for \$3–\$5. Make sure to follow directions to insure both TV protection and efficient signal transfer. A well-grounded antenna mast is mandatory in any TV installation! If your reception seems to be a little weaker than usual, check the lightning arrester, perhaps even replace after a stormy season.





# AC OUTLET CHECKER

*Is the ground grounded or ungrounded?  
Your life can depend on the answer!*


**WILLIAM D. KRAENGEL, JR.**

DO YOU KNOW IF YOUR 3-WIRE AC OUTLETS are functioning properly? If you accept the premise that the purpose of a 3-wire system is to provide an additional margin of safety (with a grounding conductor to which frames, cabinets, housings, etc., are separately grounded), it is necessary to be able to verify that the system is indeed working as designed; i.e., that the ground is really grounded.

How can this be done easily? You can use the Outlet Polarity Checker described in this article. With a little additional sleight-of-hand, the unit can be used to check 2-wire systems to determine if they can be used safely with a 2-to-3-wire adapter. (I don't like them—as shall be seen later, these can lead to a false sense of security!) And it can also be used to check an appliance that has a 3-blade plug.

The checker consists of three neon lights (see Fig. 1) wired so that they light in different combinations according to circuit conditions. Since only one combination of lights (the ones labeled "O" and "K") indicate a correctly wired outlet, the other combinations indicate various faults. Table 1 lists these possible light combinations and their causes. In most cases, but not always, any trouble will be due to an incorrectly wired outlet. However, the entire branch circuit can be incorrectly wired, especially if it has been installed by nonqualified personnel.

When 3-wire systems are working properly, they do provide an extra margin of safety. But what happens when a homeowner wants to use a new 3-wire appliance with an existing 2-wire system? He sometimes buys an adapter or uses the one that is conveniently furnished with many new 3-wire appliances. He hooks the adapter up according (sometimes) to

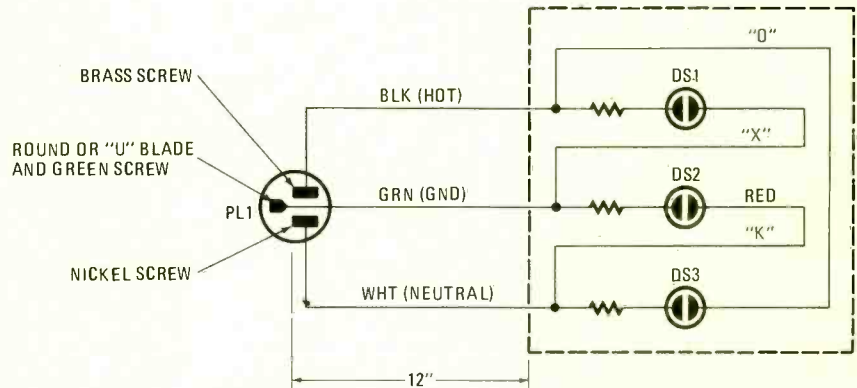

**FIGURE 1—OUTLET POLARITY CHECKER.** A simple and sure way of knowing if the outlet that you are about to plug into is functioning properly.

**TABLE 1—SIGNAL LIGHT COMBINATIONS**

LIGHTS ○ OFF    ● ON			CIRCUIT CONDITIONS
O	K	X	
○	○	○	OFF - FUSE OR CIRCUIT BREAKER OPEN
●	●	○	OK (SAFE!)
●	○	○	NEUTRAL OPEN - DANGER!
○	●	○	GROUND OPEN - DANGER!
○	○	●	HOT TERMINAL OPEN AND HOT ON NEUTRAL TERMINAL - DANGER!
●	○	●	HOT AND GROUND REVERSED - DANGER!
○	●	●	HOT AND NEUTRAL REVERSED - DANGER!
●	●	●	(NOT POSSIBLE)

## PARTS LIST

DS1, DS3—Amber neon lamp assembly (Lafayette No. 99A62259 or equal)  
DS2—Red neon lamp assembly (Lafayette 99A62267 or equal)  
P1—3-wire polarized plug and cord  
Misc.—Bakelite case (Lafayette No. 99E80780 or equal); grommet to fit cord.

the instructions (if any). He now blithely assumes that he has successfully converted his old 2-wire system into a safe, grounded 3-wire system—but has he? Unless he has actually grounded the green lead of the adapter, he hasn't! Just fastening the green lead under an outlet-plate mounting screw grounds the appli-

*continued on page 78*

# Wiring Syst For Proj

*A comparison look at four different ways you can wire your projects. Selecting the right one for your next construction project will make the task easier and more pleasurable.*

**EARL "DOC" SAVAGE, K4SDS**  
HOBBY EDITOR

NOT SO LONG AGO THERE WAS ONLY ONE WAY TO WIRE AN ELECTRONIC project; and too many people believe there is *still* only one way.

Today there are *four* major wiring systems from which to choose. If you are not familiar with these systems and their advantages and disadvantages, you are likely to spend too much time constructing and correspondingly less time designing and using your projects.

To avoid wasting time, a knowledge of available wiring systems is a *must*. Although it is equally important to be able to use all systems, first you must be able to choose which one is best for a given project. So let's examine and compare the four major wiring systems.

## CSH wiring

This wiring system has been in use for many years. It is conventional or traditional wiring, but many call it CSH (Cut/Strip/Hook). The name itself shows how slow and tedious it is.


We'll review the CSH wiring system, briefly, but, first, since every project must be built *on* something let's see what's available.

Figure 1 shows several types of perforated boards that are used with the CSH system. A plain perforated board is often chosen. Three types of universal PC boards are also shown. Depending upon the nature of the project circuit, a universal PC board can ease the wiring task.


The cut/strip/hook wiring method started when components projects were large. Even so, it is still used on modern small board-mounted projects. Figure 2 shows the tools and materials used in this system. It's the cutting, stripping and hooking that takes so much time; and the hooks must then be clamped to the joints. The final step is soldering, and, a very small iron tip is essential. Note that components can be wired directly or sockets can be used.

The overwhelming disadvantage of this wiring system is the great amount of time and effort it requires. This fact will become more apparent as we look into the following systems.

However, the other side of the coin is that there is no limit to the size wire you can use. When constructing high-current and/or high-voltage circuits, this can be an advantage. The CSH wiring method is generally used in constructing power supplies and high power amplifier stages. Of course, it is standard in tube circuits.

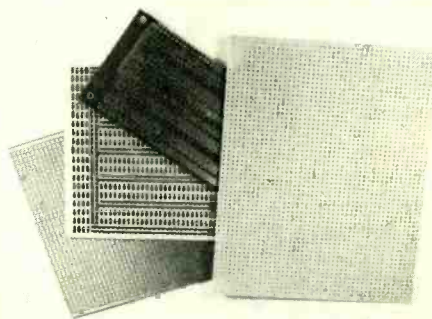

**FIG. 1—PERFORATED BOARDS** are used with the cut/strip/hook and wire-wrap wiring methods. Also shown is a universal-type printed-circuit board.

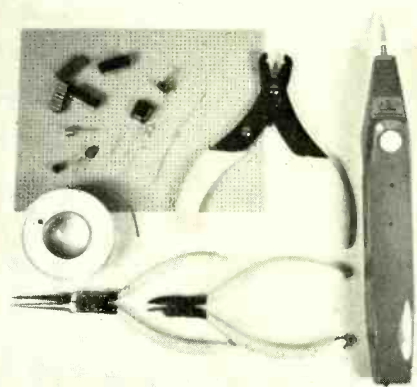

**FIG. 2—TOOLS AND MATERIALS** required for the cut/strip/hook wiring method.

## Pencil wiring system

Figure 3 shows the tools and materials used in the *pencil* (or *pen*) wiring system. This type of wiring is very much like drawing with a regular pencil. The pencil contains a roll of special wire at one end that passes down the shaft and is dispensed through a small metal point.

The wire is wrapped three or four times around a component lead or socket tail, then fed to the next component and so forth, daisy-chain fashion. At the end of the chain, you cut the wire by



A series of four 1/2-inch videotapes describing various aspects of satellite television communications are available from *Satellite Television Technology*, P.O. Box G, Arcadia, OK 73007:

Tape HTS-1, "How The Home Terminal works"

Tape HTS-2, "Private Terminals Today"

Tape HTS-3, "TV Terminal Technical Topics"

Tape HTS-4, "How The Bird Flies"

Tapes are 1/2-inch and run from 70 to 110 minutes and are in full color. Specify either VHS or Beta format when ordering and enclose payment with order. Price is \$50, each in Beta format; \$55, each in VHS format.

Also available is a "Satellite Study Package," including a 52-page booklet explaining private terminals, a 22 by 35 four-color wall chart showing all satellites in operation and how the receive terminal is designed and installed, and a copy of a recent issue of *CATV* (the worldwide monthly publication dealing with satellite terminal systems) is available for \$13 postpaid (\$16 outside the U.S.).

The first national seminar conference dealing with practical technology for building and operating your own private television receive satellite terminal will be held August 14, 15 and 16 in Oklahoma City.


This conference will feature worldwide experts in the field of private (low cost) satellite terminals demonstrating their equipment design and construction techniques. Numerous operating terminals from 6 to 20 feet in size will be on hand and several firms marketing equipment in this field will be on hand to explain their marketing approaches to home terminal installations. Firms interested in acting as area marketing, servicing and installation affiliates of the national suppliers in this field will have the opportunity to learn about the various products being offered in this field.

Among the systems to be demonstrated will be ten foot terminal systems operating without any LNA devices (utilizing new technology in the receiver area), various approaches to low cost privately built receivers and antenna sub-systems, and a series of sessions on the projected growth and activity in this fast moving area.

Attendance is by advance registration only; for full information contact *Satellite Television Technology*, P.O. Box G, Arcadia, OK 73007 (405) 396-2574

## Domestic satellites

As needed as the Intelsat-type satellites are, they cannot serve all the communications needs of all countries. Some nations, such as the U.S., Canada and Russia, have unique internal needs that in sheer

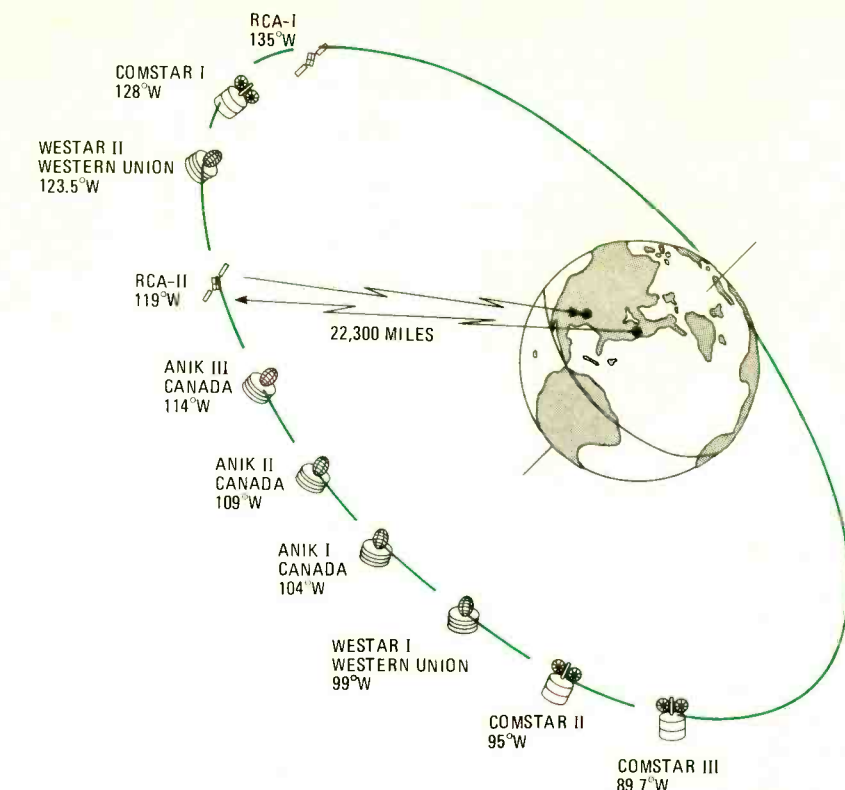

**FIG. 3—DOMESTIC SATELLITE "parking" spots. Ten domestic satellites are currently active—3 Canadian and 7 U. S. A. A third WESTAR satellite should have been launched by the time you read this and a third SATCOM is due for launch between October and December of this year.**

message volume (or circuits required), far outstrip Intelsat's services. For example, in the Atlantic Intelsat cluster five separate satellites have a total flat-out capacity of 100 separate "channels" or transponders. A single transponder can provide (typically) up to 900 voice or message circuits, or one TV channel circuit. Obviously, not all these circuits are used full time, so satellite communications planners take advantage of what are called "peak load times." They attempt to have enough circuits available to handle peak or maximum traffic-time loads. In the long haul, the average number of circuits in use would be somewhat less than 50% of the total capacity available.

Some smaller nations, such as Nigeria, Sudan, Uganda, etc., lease one or more transponder/channels full time from Intelsat to provide ground-to-satellite-to-ground communications for circuits wholly within their own countries (except for the satellite link). Other countries such as Spain, lease full-time circuits to maintain ground-to-satellite-to-ground communications with distant outposts of their nation, for example, television, telephone and data circuits with the Canary Islands.

In 1970-1971 individual countries with projected satellite circuit needs for exceeding Intelsat's capability persuaded other Intelsat nations to allow some portions of the equatorial orbit belt to be reserved for non-Intelsat geostationary satellites, or for domestic satellites. In the interim so-called Domestic Satellite Sys-

tems have been activated for Indonesia, Canada, Russia and the U.S. although actually the Russian system was first made operational back in 1965.

In North America the orbit parking region from 70 degrees west longitude (a point due south of New England) to around 135 degrees west (roughly due south of the Alaskan peninsula) is reserved for North American domestic satellites. (See Fig. 3.) Canada was the first to launch a domestic satellite into this region (ANIK I in 1972); and in seven years, 10 other Canadian or U.S. domestic satellites have joined ANIK I. An additional pair of U.S. domestic satellites will join the crowd before 1979 is over. There are 13 satellites in all, and all are parked between 70 degrees west and 135 degrees west.

On a transponder or channel-capacity basis, the North American satellites have the full-load capability to provide as many as 228 separate TV channels, or more than 200,000 telephone voice channels simultaneously—more than twice that available on the Intelsat system. With all that capacity available, you might suspect there is some extremely interesting, perhaps even downright enticing, "television" up there.

Indeed there is. There's a lot of good watching—more than 40 channels worth—to be had from those U.S. And Canadian domestic birds. Next month, we'll take you channel-by-channel, bird-by-bird as we scan programming available to TV viewers in other locations throughout North America.

R-E

# TV ADD-ONS DO THEY R

*As we strive for improved TV reception, we are offered innumerable gadgets that promise us a near-perfect picture. Not all work as well as the sellers claim that they do.*

ROBERT B. GROVE

WE ARE ALL TEMPTED—AT ONE TIME OR ANOTHER—BY THE quick-and-easy-remedy syndrome: Gas-tank additives, pill-popping medication, flea collars, spray deodorants. Even the family TV set is besieged with handy accessories that promise fantastic results for a minimum investment in time and money.

The TV gadget syndrome began soon after World War II, when small-screen black and white TV was just catching on, and families, friends and neighbors clustered for hours around the magic box, squinting at teeny-tiny pictures.

A few enterprising souls decided to capitalize on the small screen problem by selling attachable magnifiers: A clear, convex cell of mineral oil was braced in front of the tiny screen; if the viewer sat directly in front of the screen, he could view an enlarged (albeit blurry) picture. The hapless souls who had to view the magnified image from an angle were plagued by incredible distortion. The magnifiers finally went the way of the dinosaurs!

Another item that appeared was the color-filter adapter, an incredible hoax consisting of alternating horizontal bands of colored plastic film stuck to the face of the picture tube. True, your black and white TV set could then show color . . . if you didn't mind seeing Ed Sullivan with red eyes, green nose, blue lips and a yellow chin!

Accessory gadgets are still in popular demand, but do they really work? I decided to find out. A trip to my local electronic store provided several devices intended to improve TV picture quality. Interestingly enough, *none* carried a guarantee of any kind!

The devices were tested on two separate TV sets in two different locations, and the results were disturbing. Here's what I found:

## TV interference filters

These devices are advertised as being effective against neon signs, fluorescent lights, auto ignition noise, airplanes, appliances, amateur radio transmitters, medical and X-ray equipment, electric razors, and oil burners. I purchased the filter shown in Fig. 1 and tested it using a CB transceiver; the filter did not reduce the interference on either set. Further experiments using an RF signal generator radiating local interference on TV channels also resulted in no improvement with the filter attached. The filter was then tested for its effectiveness in

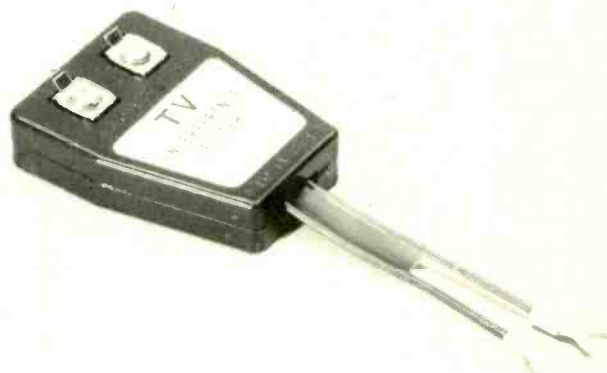


FIG. 1—TV INTERFERENCE FILTER is inserted in the antenna lead-in.

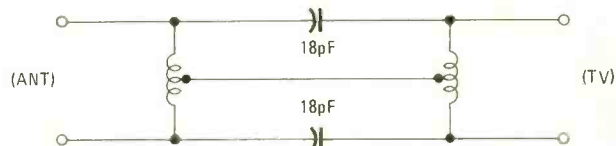


FIG. 2—INTERFERENCE FILTER is a high-pass filter that attenuates signals below 54 Hz.



FIG. 3—CB TRAP is a series filter that eliminates 27-MHz CB signals.

suppressing the spark-tearing of the picture caused by electrical appliances; again, no improvement.

Internally, the TV interference filter is a constant-k high-pass filter, attenuating all signals below 54 MHz (Channel 2). The schematic diagram is shown in Fig. 2. It should be effective in preventing front-end overload from signals below 54 MHz, but it has no effect on interfering signals in the TV frequency bands, which is where the majority of interference originates!

## CB interference trap

Turning the CB transceiver on transmit next to the antenna



# ems ects

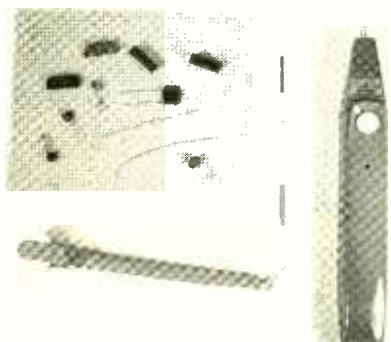
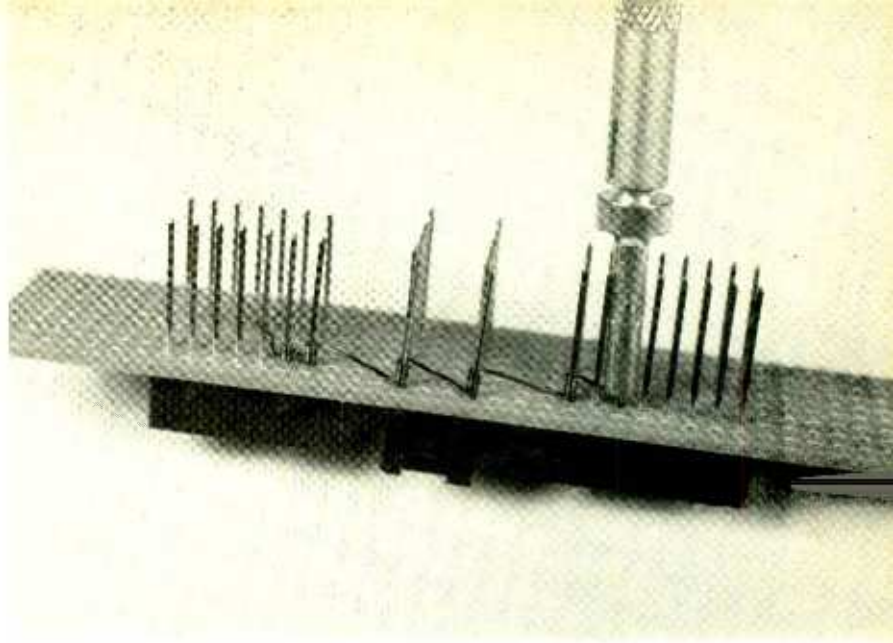


FIG. 3—PENCIL WIRING SYSTEM also requires perforated board and soldering iron.

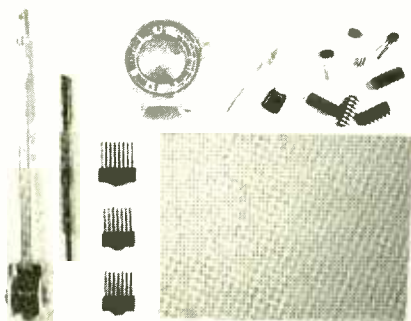


FIG. 4—TWO TECHNIQUES are available for wire-wrap construction. The tools and materials required for both techniques are shown.

pinching it against the board using a chisel-like tool or an *Xacto* knife or other type of blade.

So far, we have not mentioned stripping the wire. This is because the wire has a special insulation that *vaporizes* at a temperature of about 750°F, making wire-stripping unnecessary. You only have to touch the wire with a hot iron to melt the insulation so that solder can be applied.

Quite obviously, the great advantages to the pencil wiring method are its simplicity and speed. It is ideal for most modern

digital and analog circuits. As you might expect, the disadvantage is the limited wire size—gauges No. 32 through No. 38 are usually available. Therefore, pencil wiring would not be suitable for constructing a 2-amp power supply.

## Wire-wrapping

There are two wire-wrapping methods, and the tools and materials for both are shown in Fig. 4. One method (Type 1) resembles the CSH system, although it is much faster.

The first wire-wrapping method (Type 1) requires that the wire be cut and stripped. Fortunately, these operations are simplified by the wire dispenser and stripper shown in Fig. 5. OK Machine and Tool's refillable wire dispenser has a built-in cutter and stripper that saves a lot of time. The other device has a stripper built into the handle of the double-ended wrap/unwrap tool. Kits are also available containing various lengths of pre-cut and pre-stripped wire.

Wiring is performed by simply wrapping the wire around the terminal. In case of error or modification, the other end of the tool can be used to *unwrap* the connection.


The second wire-wrapping method (Type 2) is called slit-and-wrap wiring and is accomplished with a tool from Vector Electronics that resembles a wiring pencil. This wire is also contained in a spool mounted on one end of a hollow shaft through which the wire passes. The business end of the tool not only wraps the wire but *slits* the insulation as it does so, allowing contact to be made with the terminal.

The slit-and-wrap technique has two decided advantages over the Type 1 method. First, cutting and stripping are *not* required. Second, continuous daisy-chain connections can be made (see Fig. 6). These two factors greatly improve convenience and time-saving (and there are also motor-driven wrapping tools).

You will note that no mention has been made of soldering. The ultra-speed of the wire-wrapping system (the slit-and-wrap technique especially) results from the fact that there is *no soldering*. As strange as it may seem, a properly wrapped connection is *at least* as stable mechanically, and has as low a resistance as a soldered connection.

The wire-wrapping system is not a cure-all, however. It has some disadvantages: The wire is of limited size, although typically a little heavier than pencil wire (but, as previously noted, this is seldom a problem). What is more important is that connections must be made on special wrapping posts.

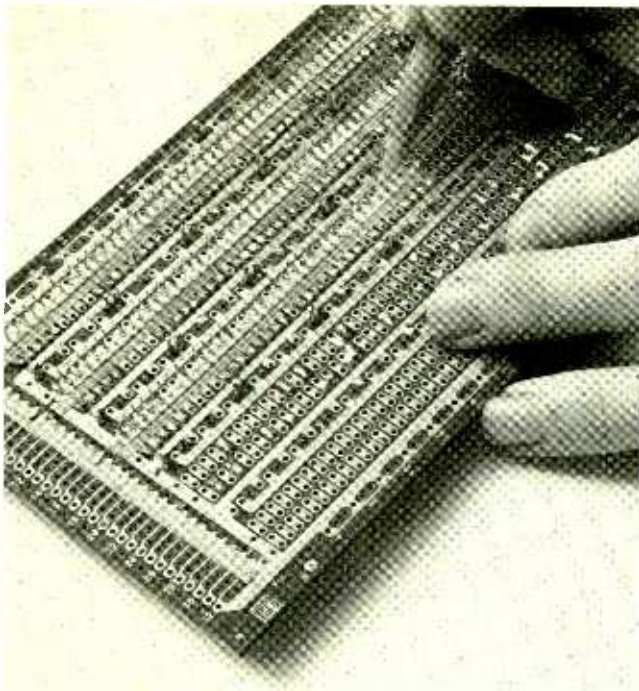Wire-wrapping *cannot* be performed on component leads. The wrapping posts must have sharp edges to dig into the



**UNIVERSAL PC BOARD and wiring pen manufactured by Vero Electronics, Inc.**

wrapped wire. This means using special wire-wrapping sockets and through-board posts for mounting discrete components.

#### Printed-circuit boards

There is some confusion about the meaning of the term PC board because both *universal* and *dedicated* boards can be called PC boards. In order to distinguish between the two types, the adjective "universal" is included for that type of board. (An unqualified PC board generally refers to a dedicated board—that is, one designed for use with a specific circuit.)

The PC board wiring technique is the simplest and quickest technique of all. It would win hands down over the others except for two factors: First, modifications are more difficult (although not impossible) to make on PC boards. It is just a matter of cutting the traces and substituting actual wires, and, with reasonable care, this procedure works quite well.

The more important difficulty is making the PC board itself. At the outset, the copper-clad board is plain and undrilled. Somehow the circuit must be placed on the board—either by drawing, transferring, pasting-up, or using a photosensitive process. Next, the unwanted copper must be removed—by etching, grinding, or even sawing. Finally, the PC board must be drilled for component mounting.


Several excellent methods have been devised for constructing PC boards. Everyone should become familiar with them in order to be able to select the correct one. However, there is *no* presently available *fast* method of doing the job.

Time can be saved only when a quantity of identical boards must be constructed, which is a rare situation for the individual builder. Even ordering a preconstructed board takes time. In spite of all this, time and effort are not always the most important considerations, so PC board wiring should not be overlooked.


#### Material sources

For your convenience, some of the manufacturers of tools and materials needed for the various wiring systems are listed in Table 1. Listed under each name are applicable tools, identification numbers and the latest prices (subject to change). Each manufacturer also produces materials and accessories, so request a catalog from each one.

You can sometimes find these items in many mail-order catalogs. There may also be sources in your own area, such as retail

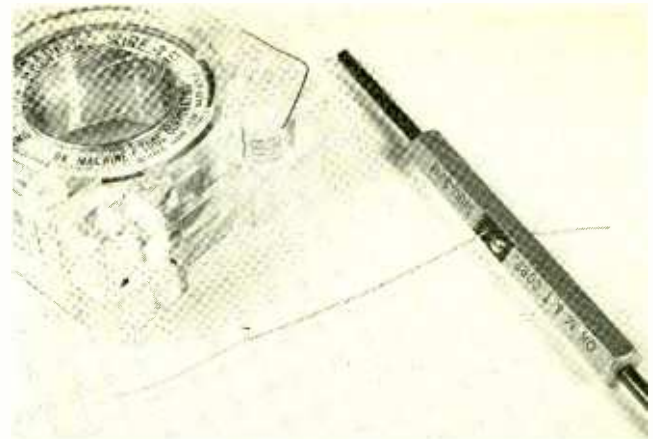

**FIG. 5—WIRE DISPENSER and wrap/unwrap tool available from OK Machine and Tool Corp.**

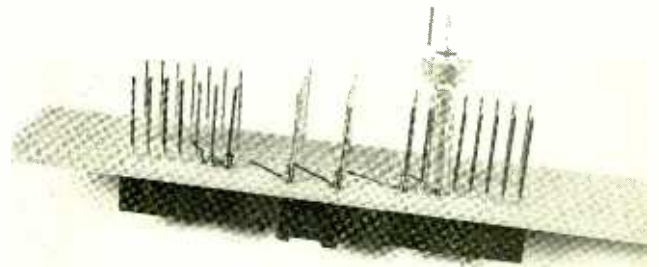

**FIG. 6—SLIT-N-WRAP tool from Vector Electronics has wire stripper built-in so the wire is automatically stripped as it is wrapped.**

**TABLE 1—MANUFACTURERS of tools and materials for various wiring systems**

<b>OK Machine &amp; Tool Corp., 3455 Conner St., Bronx, NY 10475:</b>	
<b>CIRCLE 148 ON FREE INFORMATION CARD</b>	
WSU-30—Wrap/unwrap tool, \$6.95, plus materials, accessories, boards.	
JWK-6—Just Wrap kit, \$24.95.	
<b>Vector Electronics Co., Inc., 12460 Gladstone Ave., Sylmar, CA 91342:</b>	
<b>CIRCLE 149 ON FREE INFORMATION CARD</b>	
P-178-1—Wiring pencil, \$7.95.	
P-183—Chisel knife and forming tool, \$1.95.	
P-180—Slit-N-Wrap tool, \$24.50, plus materials, accessories, boards, kits.	
<b>Vero Electronics, Inc., 171 Bridge Rd., Hauppauge, NY 11787:</b>	
<b>CIRCLE 150 ON FREE INFORMATION CARD</b>	
79-1732G—Wiring pen, \$8.00.	
58-2808J—Wrap tool, \$21.70, plus materials, accessories, boards, kits.	

stores and electronic supply distributors. If you cannot locate what you need, you can write the manufacturer.

#### Summary

Knowledge is, indeed, a powerful thing. You can save yourself much "fussin' an' cussin'" if you know enough about the four major wiring systems to pick the right one at the right time. Choosing the wrong one can result in anything from frustration to disaster. After all, old Murphy's Law says that something will go wrong anyway—you don't have to make it worse by selecting the wrong one from the start!

Every electronics hobbyist should not only read about, but *try out* each wiring system. That way, you *really* know. Don't take someone else's word—even mine—because we may have different expectations. Try all of them and then you can choose the system you need when you need it.

**R-E**



## New FM Tuner CIRCUITS

*During the last few years the sound quality developed by the FM detector and stereo decoder has improved noticeably. Here is a look at some state-of-the-art circuits that make this possible.*


**LEN FELDMAN**  
CONTRIBUTING HI-FI EDITOR

IT WASN'T VERY LONG AGO THAT AN FM tuner capable of delivering an audio signal with less than 1.0% total harmonic distortion at the output of its ratio detector or discriminator was considered to be a very high-quality product. Today, it is not uncommon to find FM tuners with distortion as low as 0.1%, even in the stereo FM mode. Despite such giant reductions in overall distortion of FM signal reception, some manufacturers continue to explore other innovative ways to improve FM reception.


For example, Kenwood Electronics (1315 E. Watsoncenter Rd., Carson, CA 90745) has developed a separate tuner, the *model KT-917*, that achieves a distortion rating of 0.05% in the monophonic mode and 0.09% in the stereophonic mode at any audio frequency from 50 Hz to 10 kHz. Several new and unusual circuits are responsible for this additional lowering of overall distortion; we'll examine four of these new circuits.

### Pulse-count detector

Conventional discriminators and ratio detectors, which have been in use since FM broadcasting began, use tuned circuits which first convert the FM signal into one that varies in amplitude. Non-linear devices (diodes) then rectify the frequency-dependent AM signal to recover the original audio modulation. Both steps in this process are inherently non-linear. The discriminator (or ratio-detector) S-curve, formed by transformer-coupled tuned circuits, is a continuous curve (see Fig. 1). It is this curve that converts frequency variations into varia-

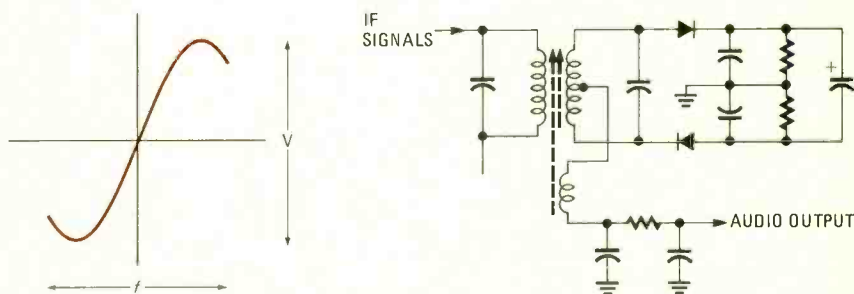

**FIG. 1—CONVENTIONAL DISCRIMINATOR** has a nonlinear S-curve characteristic to convert FM signals into AM signals.

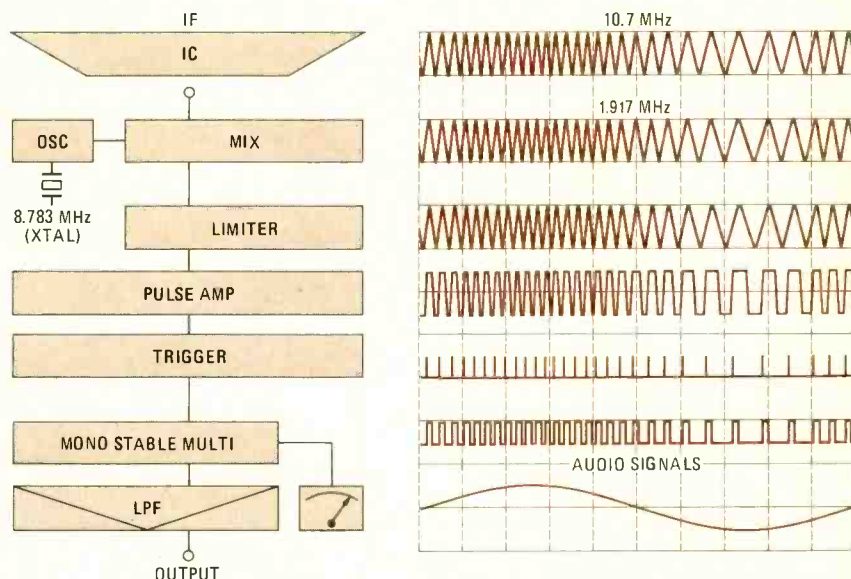

**BLOCK DIAGRAM OF PULSE COUNT DETECTOR**

**FIG. 2—PULSE COUNT DETECTOR** is a digital circuit that performs the function of a conventional discriminator but with much less distortion.

tions in amplitude. By restricting the FM deviation to a portion of this curve, linearity is approached but not fully realized. The second step in the demodulation process uses a diode's nonlinear characteristics for rectification. Here, with careful attention given to input-signal amplitude, linearity is again approached but not totally realized.

A pulse-count detector system, on the other hand, is theoretically linear. In this system each individual waveform (at the IF) is converted to a pulse of uniform amplitude and duration. An integrating circuit counts these pulses and averages the count over a given time interval; the output is proportional to the pulse count. A block diagram of the Kenwood pulse-count detector system is shown in Fig. 2. The pulse count rises as a linear function of frequency, and the counting process remains linear until there is no space left between pulses. This point of saturation occurs far beyond maximum deviation. The system uses no nonlinear analog elements. It is a digital system in that the precision-pulse formers use digital techniques. The pulse counter is a form of digital-to-analog converter.

In applying this technique to FM demodulation, Kenwood found that the best detector efficiency can be achieved when demodulation occurs at a frequency much lower than 10.7 MHz (the normal FM IF). Therefore, a second converter is incorporated to heterodyne the IF down to 1.96 MHz. This causes the deviation to be much greater compared with the center frequency, and suits the operating characteristics of the digital processors. Referring to Fig. 2, note the 1.96-MHz signal is shaped into narrow triggering spikes (one for each cycle) that drive a one-shot multivibrator. The multivibrator produces output pulses of uniform amplitude and duration. Only the frequency or density of pulses varies. A low-pass filter performs the pulse-counting function, producing an audio output that is determined solely and linearly by pulse count.

There is an additional performance advantage to this system. The multivibrator

is either off (zero volts) or on (supply voltage). In either state, no noise is produced, since the system is sensitive to noise only at the instant of triggering. This results in an important reduction in overall noise. Furthermore, since there are no tuned circuits the pulse-count detector never needs alignment and is not affected by temperature or humidity.

Figure 3 shows the differential gain for a conventional ratio detector and for a pulse-count detector. Note that ratio-detector gain varies as the frequency deviates farther and farther away from the center, while the pulse-count detector gain remains linear over a very wide frequency range.

### Distortion detection loop

With distortion caused by nonlinear detection virtually eliminated by the pulse-count detector, the one remaining possible source of distortion is the IF system of the FM tuner. In many FM tuners an indicator displaying center-tuning makes use of a balanced detector whose output voltage goes to zero when the converted signal is at the center of the detector's response. The drive from this circuit controls the deflection of the familiar zero-center tuning meter, or an AFC (Automatic Frequency Control) system, if one is used. This system works on the assumption that the IF response is perfectly symmetrical and has the same center frequency as that of the detector driving the tuning meter. Unfortunately, this is not always the case.

The DDL (Distortion Detection Loop) system developed by Kenwood examines distortion and adjusts local oscillator frequency to place the converted IF signal precisely where it should be for minimum distortion. The block diagram of Fig. 4 shows that the local oscillator is frequency-modulated by an internally generated 95-kHz signal that contains 10% positive and negative deviation components.

To avoid interference with the selected incoming channel, the 95-kHz signal was chosen to be five times the 19-kHz pilot-signal frequency. It is mixed with the selected carrier signal in order to place

frequency-modulated signals on the upper and lower skirts of the IF response curve. After FM detection, original test signals and any distortion (which appears as twice the 95-kHz signal) are extracted by a high-pass filter and applied to a synchronized detector where the original test signals and distortion components are compared. If an imbalance exists a DC error voltage is produced; this voltage is filtered and applied to the same varactor diode used to add the frequency-modulated injection signal to the local oscillator. This error voltage corrects the local oscillator's center frequency to balance the DDL phase detector. In this way the DDL system monitors the distortion by injecting test signals that accompany the selected channel through the IF system. It serves to balance the distortion and to place the selected channel at the precise mid-point of the IF passband.

To prevent interference with normal tuning, a logic-control circuit interrupts DDL control until manual tuning places a selected channel in the approximate center of the IF passband. Inputs to the control logic are a touch detector that is linked to the tuning knob, a noise detector that monitors IF output, and the output of the high-pass filter that delivers the recovered injection signals to the DDL phase detector. When the operator releases the tuning knob, the DDL system starts working, and a light is turned on to indicate that tuning for minimum distortion has occurred.

### Sample-and-hold decoding

In the conventional stereo FM decoding process, the (L-R) and -(L-R) audio information is recovered from the positive and negative excursions of the 38-kHz composite-signal envelope. In such switching systems the (L-R) and -(L-R) information is recovered in the form of averaged 38-kHz components. In the course of filtering the ripple components of the 38-kHz signal to reclaim the original modulation some sacrifice in stereo separation normally occurs.

In a newly developed sample-and-hold technique, the 38-kHz signal envelope is examined in short bursts at a rate that is determined by the 38-kHz signal produced by a phase-locked-loop (PLL) system. The recovered levels, in terms of modulation envelope voltage, are stored in a capacitor that is effectively disconnected from the sampling switch after the sampling burst has passed. This voltage value is retained by the capacitor until the next sampling burst arrives. The capacitor then charges or discharges to the new envelope voltage value. As a result the envelope is traced in the form of horizontal voltage steps, as shown in Fig. 5. This represents a more accurate reproduction of the modulation envelope voltage. The resultant ripple component is lower and little filtering is required.


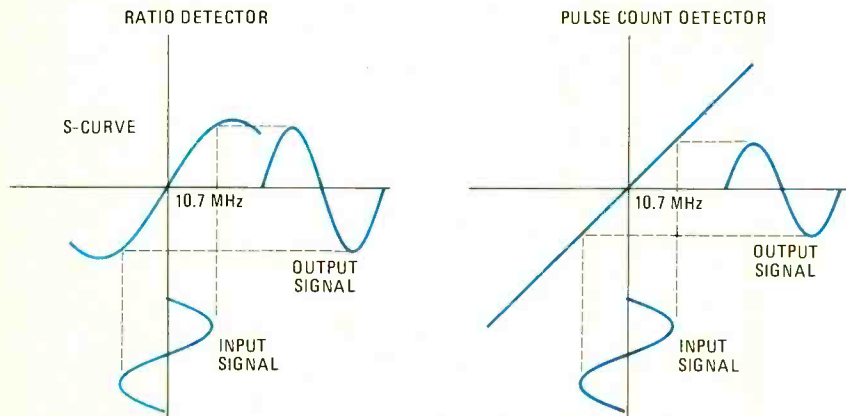


FIG. 3—TRANSFER CHARACTERISTICS for the conventional ratio detector and for the new pulse count detector.

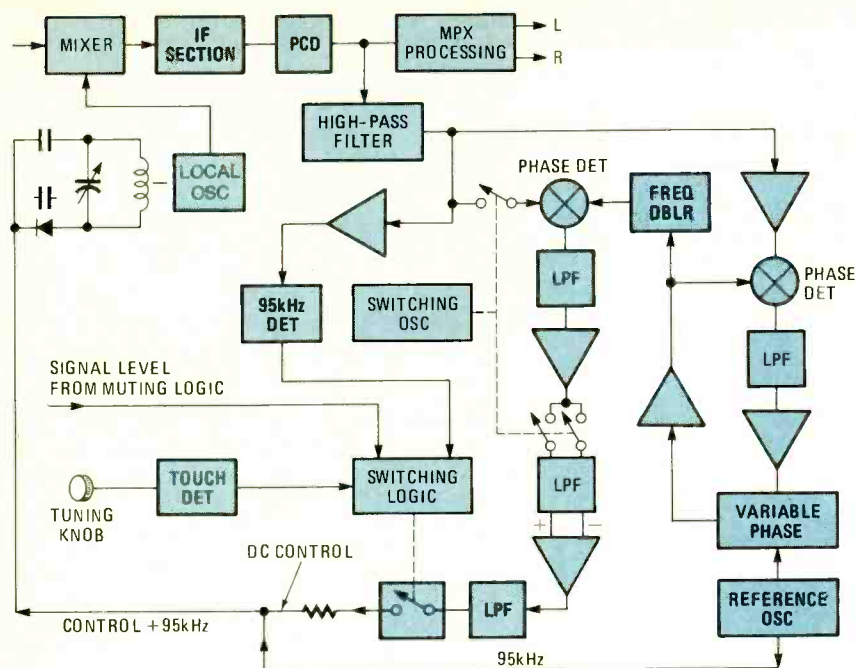



BLOCK DIAGRAM OF DISTORTION-DETECTION LOOP (DDL)

FIG. 4—DISTORTION DETECTION LOOP senses the distortion level at the output of the detector and adjusts the local oscillator frequency for minimum distortion.

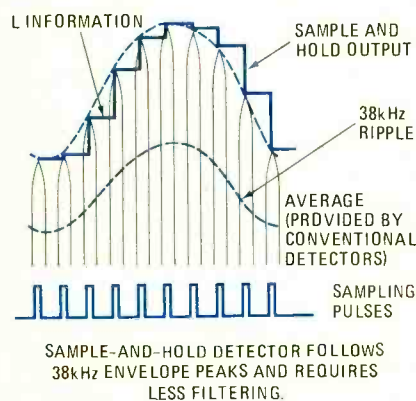


FIG. 5—SAMPLE-AND-HOLD stereo decoding circuit output follows the 38-kHz envelope and requires less filtering than conventional techniques.

### Two-speed phase-locked loop

Another form of distortion can be introduced into stereo decoding circuits that use a phase-locked loop circuit to regenerate the 19-kHz and 38-kHz carrier signals during decoding. Ideally, the regenerated 38-kHz subcarrier signal should be immune to noise-induced frequency jitter. To reduce such frequency jitter, some designers narrow the bandwidth of the phase-locked loop, 19-kHz capture range. This approach makes it more difficult for the PLL circuit to lock onto the incoming pilot-carrier signal. Opening the bandwidth to allow fast and reliable capture of the pilot signal, on the other hand, increases the possibility of pilot jitter; this normally peaks at around 200 Hz to produce high-order audible intermodulation. In the Kenwood stereo decoder (shown in the block diagram of Fig. 6) a dual time-constant filter is used in the PLL circuitry: a wide filter

for acquisition; followed by a narrow filter, which is inserted after lockup (of the pilot signal) to keep tight and jitter-free control of the regenerated pilot signal.

Figure 6 also demonstrates the way in which this PLL circuit eliminates any residual 19-kHz signals from the recovered audio outputs. Removal of this high-frequency signal is important because the presence of 19-kHz components in the output signals can produce beat frequencies during tape recordings (the 19-kHz harmonics can beat with the tape deck's bias oscillator); and can also cause improper tracking of built-in Dolby or other types of noise-reduction circuits. The conventional way of removing the 19-kHz pilot signal from the audio output signals is by using a simple low-pass filter. For the filter to be effective at 19 kHz, however, it must also rolloff response at

lower audio frequencies, beginning at around 10 kHz or 12 kHz. The decoding system shown in Fig. 6 does not use such simple filters. Instead, a sample of the regenerated 19-kHz signal from the two-speed phase-locked loop is applied to a subtractor circuit in the decoder input section. Here, the original pilot signal and the regenerated 19-kHz pilot signal are 180 degrees out-of-phase. By adjusting the out-of-phase 19-kHz signal so that it is equal in amplitude to the incoming 19-kHz signal (part of the overall detected composite stereo signal), the two 19-kHz components cancel each other out without affecting audio frequency response.

Manufacturers of high-fidelity FM equipment such as Kenwood and others seem to be able to develop more and more improved circuits to provide audibly better FM reception in the home. Unfortunately, only a few FM broadcast stations are able to transmit clean enough signals to allow state-of-the-art hi-fi FM tuners and receivers to perform optimally. The truth is that the performance of most FM receivers today is limited by the antiquated transmission equipment used by a majority of FM stations, not to mention the scratched recordings, worn styluses, and hum-and-noise in studio consoles and cables that many stations continue to transmit.

R-E

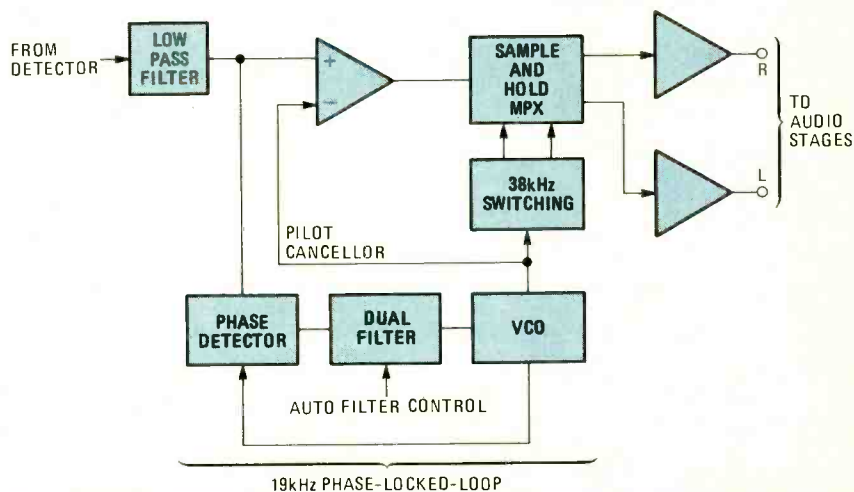


FIG. 6—BLOCK DIAGRAM of the Kenwood stereo decoder designed to eliminate pilot jitter. Two filters, one narrowband and the other wideband, provide a jitter-free regenerated pilot signal.

## Radio-Electronics Audio Lab Tests



CIRCLE 106 ON FREE INFORMATION CARD

## SONY STR-V7 AM/FM Receiver

LEONARD FELDMAN  
CONTRIBUTING HI-FI EDITOR

SONY CORPORATION HAS DEVELOPED ITS MOST powerful stereo receiver to date, the *model STR-V7* (see Fig. 1). This receiver's control layout has been carried over from earlier Sony models. The tuning knob and master volume control are conveniently placed in the upper right-hand side of the panel, and the POWER on/off pushbutton is located at the upper left-hand side. In between these controls are placed three meters—the center meter acts as either a signal-strength meter (when a pushbutton adjacent to the tuning knob is depressed) or, used with the meter on the left, as one of a pair of power-output meters directly calibrated in watts across an 8-ohm load. The third meter, next to the volume control, serves as a center-of-channel tuning indicator in the FM listening mode.

The FM dial scale is linearly calibrated with markings at every 200 kHz, while below it is a nominally calibrated AM scale. Above these scales are a series of indicator lights that denote program source as well as stereo FM reception. The remaining controls and switches are located along the bottom section of the panel. Adjacent to the usual headphone output jack at the extreme left is a SPEAKER selector

switch. Next to this control are three toggle switches for the low-cut and high-cut filters and for bypassing the BASS and TREBLE controls. Next come a rotary BALANCE control, LOUDNESS and MODE (stereo/mono) switches, TAPE switch and FUNCTION selector switch. The TAPE mode switch permits you to monitor either of two connected tape decks as well as to copy tape from one deck to another. The FUNCTION switch has two phono settings: for magnetic cartridges, or, alternatively, for moving-coil cartridges. Three additional toggle switches on the lower right-hand side of the panel are used for varying FM-IF selectivity (both normal and narrow bandwidths), for FM muting and for activating the built-in Dolby FM decoding circuitry.

The upper left of the rear panel contains antenna terminals for 300-ohm or 75-ohm coaxial FM transmission lines and for connecting to an external AM antenna. A useful addition is an antenna lead-in clamp that retains the antenna line and protects it from strain. Nearby are a built-in ferrite-bar AM antenna, pivotable in two planes, and a chassis ground terminal. Near the two pairs of phono inputs is a two-position slide switch that selects either

MM (Moving Magnet) or MC (Moving Coil) cartridge operation. The tape-input and tape-output jacks are located in the lower left of the rear panel. On the right-hand side are located two sets of spring-loaded, color-coded speaker-connection terminals, while just below are two AC receptacles (one switched and one unswitched). No external access to fuses is provided. A view of the rear panel is shown in Fig. 2.



The owner's manual contains virtually no information regarding the circuit design and no schematic diagram is provided. From a quick examination of the internal construction of the unit and an analysis of the block diagram (which is provided), we learned that the FM front-end uses a four-section tuning capacitor, and has separate filter systems for the normal and narrow bandwidth IF settings of the front-panel selectivity switch. The multiplex decoder comprises a phase-locked-loop circuit followed by low-pass filters to eliminate subcarrier products at the output. The AM circuit uses a single IC and a two-gang tuning capacitor. The Dolby FM decoding circuitry is also incorporated in a single IC. Power-output circuits are protected by electronic and mechanical-relay circuitry. The latter also serves to delay turn-on for a few seconds to prevent thumps and other noises from reaching the loudspeakers. Figure 3 is a diagram that shows how this receiver can be hooked up to associated components.

### FM measurements

Table 1 contains the measurements made for the FM tuner section of the *model STR-V7*. While usable sensitivity was poorer than claimed, the more important 50-dB quieting specification proved to be better than claimed, with readings of 2.3  $\mu$ V (12.4 dBf) in mono and 38  $\mu$ V (36.8 dBf) in stereo as opposed to the 2.8  $\mu$ V and 40  $\mu$ V claimed by Sony. On the other hand, the signal-to-noise ratio at strong signal levels failed to reach the manufacturer's specified levels. Even more surprising (and

### MANUFACTURER'S PUBLISHED SPECIFICATIONS:

#### FM TUNER SECTION:

**Usable Sensitivity:** 9.3 dBf (1.6  $\mu$ V) **50-dB Quieting:** mono, 14.2 dBf (2.8  $\mu$ V); stereo, 37.3 dBf (40  $\mu$ V). **S/N Ratio:** mono, 75 dB; stereo, 70 dB. **Frequency Response:** 30 Hz to 15 kHz,  $\pm 0$  dB. **Selectivity:** normal, 50 dB; narrow: 80 dB. **Capture Ratio:** 1.0 dB. **AM Suppression:** 60 dB. **Image Rejection:** 80 dB. **IF Rejection:** 100 dB. **Spurious Rejection:** 100 dB. **Muting Threshold:** 5  $\mu$ V (19.2 dBf). **Distortion, Mono:** normal, 0.08% at 100 Hz and 1 kHz, 0.1% at 10 kHz; narrow, 0.2% at 100 Hz, 1 kHz and 10 kHz. **Distortion, Stereo:** normal, 0.15% at 100 Hz and 1 kHz, 0.3% at 10 kHz; narrow, 0.4% at 100 Hz and 1 kHz, 0.6% at 10 kHz. **Stereo Separation:** normal, 40 dB at 100 Hz, 48 dB at 1 kHz, 43 dB at 10 kHz; narrow, 35 dB at 100 Hz, 40 dB at 1 kHz, 37 dB at 10 kHz.

#### AM TUNER SECTION:

**Usable Sensitivity:** 100  $\mu$ V (external antenna). **S/N Ratio:** 50 dB. **Harmonic Distortion:** 0.5%. **Selectivity:** 40 dB. **Image and IF Rejection:** 40 dB.


#### AMPLIFIER SECTION:

**Power Output:** 150 watts-per-channel, 8 ohms, 20 Hz to 20 kHz. **Rated THD:** 0.07%. **IM Distortion:** 0.07%. **Input Sensitivity:** phono, 2.5 mV and 0.25 mV; high level, 150 mV. **S/N Ratio (Phono, A-Weighted):** 80 dB and 65 dB (moving coil); high level, 100 dB. **Frequency Response:** phono, RIAA,  $\pm 0.5$  dB; high level, 5 Hz to 50 kHz,  $\pm 0$ ,  $-2$  dB. **Tone Control Ranges:**  $\pm 10$  dB at 100 Hz and 10 kHz. **Filter Cut-Off Frequencies:** 50 Hz and 9 kHz, 6 dB-per-octave.

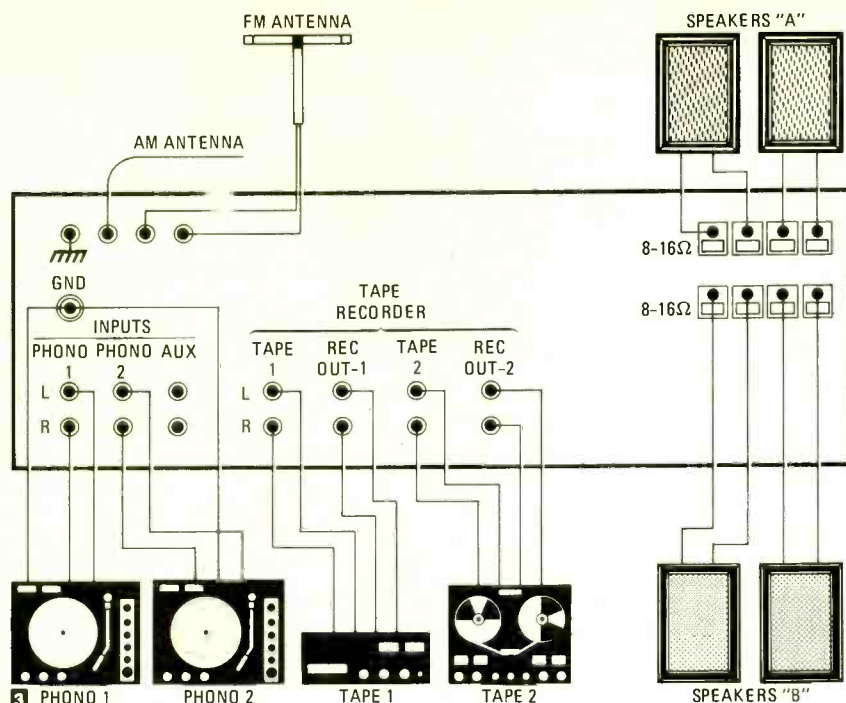
#### GENERAL SPECIFICATIONS:

**Dimensions:** 20½ W × 7½ H × 17¼ inches D. **Net Weight:** 48 lbs., 6 oz. **Power Requirements:** 120 volts, 60 Hz, 250 watts. **Suggested Retail Price:** \$820.





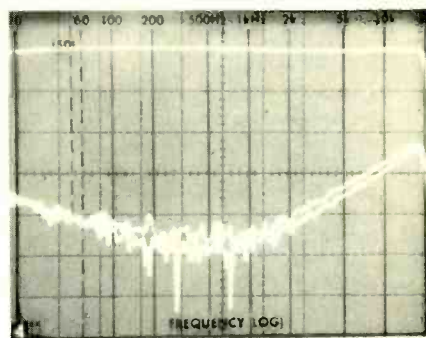watts-per-channel at mid-frequencies (and somewhat more than its rated power at high frequency), it was barely able to deliver its rated power at 20 Hz. Dynamic headroom



measured a moderate 1 dB. The manufacturer's specifications for S/N ratio and input sensitivity are reported by Sony in a manner that does not yet reflect the new IHF Measurement Standards for Audio Amplifiers. Therefore, you should not attempt to compare the input sensitivity values and signal-to-noise

disappointing) were the relatively small differences observed between distortion readings measured in the normal and narrow bandwidth modes. And, whereas we normally expect THD readings to be poorer in stereo than they are in mono, the opposite was true with this receiver. There is no easy way to determine whether this is the result of two types of distortion "tending to cancel each other out" or not. Stereo separation, while certainly adequate for all listening purposes, also fell short of published claims, both for the normal and narrow IF bandwidth settings; and, again, the differences were relatively small when shifting from one selectivity setting to the other.

Muting threshold and stereo-switching threshold (and, hence, usable stereo sensitivity) were all set a bit too high—at around 12  $\mu$ V (26.8 dBf). Sony specifications call for a 5- $\mu$ V threshold. The frequency response of the FM section was excellent, with deviations of no more than 0.5 dB from 30 Hz to 15,000 Hz, as shown in the top trace in Fig. 4. The lower trace in Fig. 4 shows the separation (or, more properly, the crosstalk) in stereo FM. Two scope sweeps were taken: one for the normal IF mode, the other for the narrow mode; and results agree fairly well with the static point-by-point measurements discussed above and shown in Table 1.

Figure 5 shows the built-in Dolby FM decoder action. At higher modulation levels (see the upper trace), frequency response is virtually flat, while at progressively lower modulation levels, the appropriate treble attenuation is introduced automatically by the Dolby circuitry.

Figure 6 shows only the frequency-response curve of the AM section. In this respect, the model STR-V7 is neither better nor worse than most competitive units. You should not expect anything resembling hi-fi performance from this minimal AM section.

## Amplifier measurements

Table 2 shows the results of measurements made on the amplifier/preamplifier control section. While the power-amplifier section delivered considerably more than its rated 150

TABLE 1

## R.E.A.L. SOUND PRODUCT TEST REPORT

Manufacturer: Sony Corporation

Model: STR-V7

## FM PERFORMANCE MEASUREMENTS

### SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE

IHF sensitivity, mono ( $\mu$ V) (dBf)	1.9 (10.8)
Sensitivity, stereo ( $\mu$ V) (dBf)	12.0 (26.8)
50-dB quieting signal, mono ( $\mu$ V) (dBf)	2.3 (12.4)
50-dB quieting signal, stereo ( $\mu$ V)	38 (36.8)
Maximum S/N ratio, mono (dB)	70
Maximum S/N ratio, stereo (dB)	68
Capture ratio (dB)	1.2
AM suppression (dB)	60
Image rejection (dB)	83
IF rejection (dB)	100+
Spurious rejection (dB)	100+
Alternate channel selectivity (dB)	80/48 (narrow)

R-E Measurement	R-E Evaluation
1.9 (10.8)	Good
12.0 (26.8)	Fair
2.3 (12.4)	Excellent
38 (36.8)	Fair
70	Good
68	Average
1.2	Very good
60	Excellent
83	Very good
100+	Superb
100+	Superb
80/48 (narrow)	Very good

### FIDELITY AND DISTORTION MEASUREMENTS

Frequency response, 50 Hz to 15 kHz ( $\pm$ dB)	0.5
Harmonic distortion, 1 kHz, mono (%)	0.22/0.2
Harmonic distortion, 1 kHz, stereo (%)	0.08/0.085
Harmonic distortion, 100 Hz, mono (%)	0.3/0.28
Harmonic distortion, 100 Hz, stereo (%)	0.14/0.10
Harmonic distortion, 6 kHz, mono (%)	0.16/0.25
Harmonic distortion, 6 kHz, stereo (%)	0.20/0.25
Distortion at 50-dB quieting, mono (%)	1.0/1.0
Distortion at 50-dB quieting, stereo (%)	0.3/0.3

### Narrow/broadband

0.5	Excellent
0.22/0.2	Fair
0.08/0.085	Excellent
0.3/0.28	Fair
0.14/0.10	Good
0.16/0.25	Good
0.20/0.25	Very good
1.0/1.0	Fair
0.3/0.3	Good

### STEREO PERFORMANCE MEASUREMENTS

Stereo threshold ( $\mu$ V) (dBf)	12.0 (26.8)
Separation, 1 kHz (dB)	45/45
Separation, 100 Hz (dB)	42/41
Separation, 10 kHz (dB)	25/27

### Narrow/broadband

12.0 (26.8)	Fair
45/45	Very good
42/41	Very good
25/27	Fair

### MISCELLANEOUS MEASUREMENTS

Muting threshold ( $\mu$ V) (dBf)	12.0 (26.8)
Dial calibration accuracy ( $\pm$ kHz at MHz)	75 at 108

12.0 (26.8)	Fair
75 at 108	Very good

### EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION




Control layout	Excellent
Ease of tuning	Excellent
Accuracy of meters or other tuning aids	Very good
Usefulness of other controls	Very good
Construction and internal layout	Excellent
Ease of servicing	Very good
Evaluation of extra features, if any	Very good

### OVERALL FM PERFORMANCE RATING

Good

values indicated in Table 2 with those shown by the manufacturer. The measured values should be judged on their own merits and compared with those obtained for other products that have been measured using the new IHF Standards. The RIAA equalization was as nearly perfect as we have ever measured, and phono overload was a much-more-than-adequate 230 mV (Sony's specification list makes no claims for this important parameter).

Tone controls operated fairly normally, with the pivot frequency of both the BASS and TREBLE control set at around 1 kHz, as shown in Fig. 7. (Note: In this and all other scope photos, one vertical division on the scope face equals 10-dB difference in amplitude.) Figure 8 is a scope photo of the high-cut and low-cut filter action. The high-cut filter has little audible effect upon hiss and scratch, while the low-cut filter, although it does help reduce turntable rumble, also considerably affects the lower bass frequencies in music programming. Both

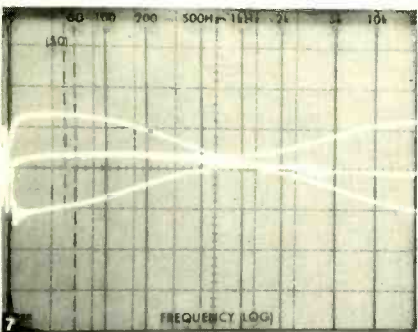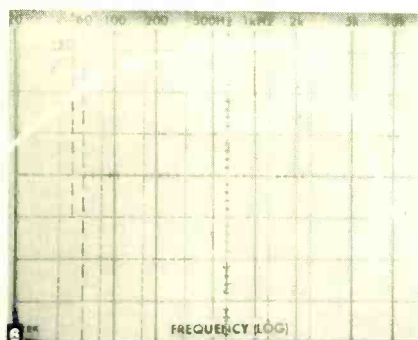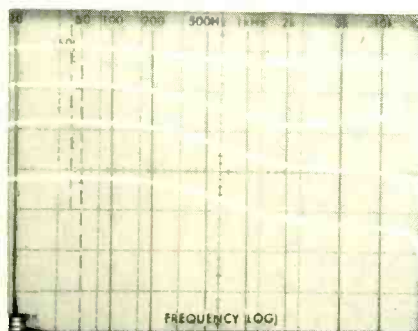

filter circuits use only a minimal 6 dB-per-octave roll-off slope. Figure 9 depicts the loudness-control circuit at various master volume-control settings (approximately 10-dB apart), in which both treble and bass frequencies are boosted as volume control settings are reduced. The treble accentuation has been kept at moderate levels compared with the bass boost.

**TABLE 2**  
**AMPLIFIER PERFORMANCE MEASUREMENTS**

	R-E Measurement	R-E Evaluation
<b>POWER OUTPUT CAPABILITY</b>		
RMS power/channel, 8-ohms, 1 kHz (watts)	164.7	Excellent
RMS power/channel, 8-ohms, 20 Hz (watts)	150.0	Fair
RMS power/channel, 8-ohms, 20 kHz (watts)	155.0	Good
RMS power/channel, 4-ohms, 1 kHz (watts)	N/A	N/A
RMS power/channel, 4-ohms, 20 Hz (watts)	N/A	N/A
RMS power/channel, 4-ohms, 20 kHz (watts)	N/A	N/A
Frequency limits for rated output (Hz-kHz)	20-20	Fair
Dynamic headroom (dB)	1.0	Good
<b>DISTORTION MEASUREMENTS</b>		
Harmonic distortion at rated output, 1 kHz (%)	0.058	Very good
Intermodulation distortion, rated output (%)	0.17	Good
Harmonic distortion at 1-watt output, 1 kHz (%)	0.055	Very good
Intermodulation distortion at 1-watt output (%)	0.04	Very good
<b>DAMPING FACTOR AT 8 OHMS, 50 Hz</b>	45	Very good
<b>PHONO PREAMPLIFIER MEASUREMENTS</b>		
Frequency response (RIAA $\pm$ dB)	0.1	Superb
Maximum input before overload (mV)	230	Excellent
Hum/noise, A-wt'd, referenced to 1-watt or 0.5-volt output, for 5-mV input (dB)	71	Good
<b>HIGH-LEVEL INPUT MEASUREMENTS</b>		
Frequency response (Hz-kHz, $\pm$ dB)	3.3-40	Excellent
Hum/noise A-wt'd, re: 0.5 or 1W out, 0.5V in (dB)	71	Very good
Residual noise, A-wt'd, minimum volume, re: 1w out (dB)	81	Very good
<b>TONAL COMPENSATION MEASUREMENTS</b>		
Action of bass and treble controls	See Fig. 7	Good
Action of secondary tone controls		N/A
Action of high- and low-cut filters	See Fig. 8	Fair/Good
<b>COMPONENT MATCHING MEASUREMENTS</b>		
Input sensitivity, phono 1/phono 2, re: 1w or 0.5v out (mV)	0.16/0.02	
Input sensitivity, high level, re: 1w or 0.5v out (mV)	9.8	
Output level, tape outputs, at rated output (mV)	9.8	
Output level, headphone jack, at rated output (mV or mW)	700 mV	
<b>EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN</b>		
Adequacy of program source and monitor switching		Excellent
Adequacy of input facilities		Excellent
Front panel layout		Superb
Action of controls and switches		Very good
Design and construction		Excellent
Ease of servicing		Good
<b>OVERALL AMPLIFIER PERFORMANCE RATING</b>		Good

**TABLE 3**  
**R.E.A.L. SOUND PRODUCT TEST REPORT**

Manufacturer: **Sony Corporation**

Model: **STR-V7**

**OVERALL PRODUCT ANALYSIS**


Retail price	<b>\$820</b>
Price category	<b>High</b>
Price/performance ratio	<b>Fair</b>
Styling and appearance	<b>Excellent</b>
Sound quality	<b>Good</b>
Mechanical performance	<b>Excellent</b>

**Comments:** Sony's top-powered receiver for 1979 left us with mixed emotions. On the one hand, the control and front-panel layout was excellent. Controls functioned smoothly and accurately, and although such top-of-the-line features as a subsonic filter and a mid-range tone control were missing, there were ample input and output facilities including built-in Dolby decoding for Dolby FM broadcasts (a feature which is worth about \$100.00).

What was disappointing was the tuner performance and, to a lesser degree, some of the measurements made on the amplifier section. Even after Sony went to the trouble of incorporating selectable IF bandwidth for the FM tuner, we found very little difference in distortion and separation capability between the two selectivity settings even though the readings themselves approached published specifications. The FM reception was not poor; it was, in fact, quite good, but no better than we have heard from receivers costing far less.

Table 2 shows that the amplifier just barely equaled its power-output specifications at the frequency extremes. We expect a certain degree of conservatism and reserve power in receivers selling for more than \$800. This is not to criticize the sound the receiver produces when driving even low-efficiency speakers. Nor can we overlook the incorporation of a built-in "head amp" or pre-preamplifier, which will appeal to audiophiles who prefer moving-coil cartridges. It seems that the rising value of the Japanese yen (and the sinking U.S. dollar) is at last causing Japanese hi-fi manufacturers to drive up the prices of their products to levels that no longer yield the superb price/performance ratios of a year or two ago.



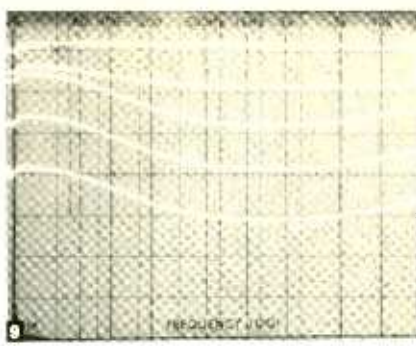

## Summary

Table 3 contains our overall product evaluation as well as summary comments regarding this Sony receiver. The *model STR-V7* is, in

many ways, an excellent instrument insofar as human engineering is concerned. Its controls are well placed and smooth operating. If it cost perhaps two hundred dollars less (or even one


hundred dollars less) we might be more enthusiastic about its performance. As it is, we do feel that the *model STR-V7* is priced too high for what it does. We do recognize that prices of all Japanese products have been skyrocketing owing to the drastic shifts in currency exchange rates; but, in most cases, technology has kept pace with rising costs and tends to offset them. We now seem to be reaching the point where costs are rising more rapidly than advances in circuitry are able to keep them down.

In summary, we believe that only the more innovative manufacturers are going to succeed in this changing audio market, and, the new Sony *model STR-V7* receiver, while certainly adequate in every sense, lacks the features and state of the art performance one would expect from a receiver in such a high price bracket.

R-E

# Radio-Electronics Audio Lab Tests

## dbx, Inc. Model 2BX Dynamic Expander

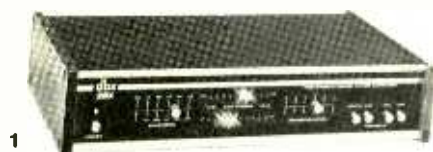

CIRCLE 107 ON FREE INFORMATION CARD

JUST ABOUT EVERY HIGH-FIDELITY PROGRAM source we listen to suffers from a lack of dynamic range. Tape recordings and even the very best discs cannot contain the wide range of audio levels that exists in a live musical performance. Such a dynamic range may well reach 80 dB or 90 dB—from the softest passages to the loudest—in any given performance. And since most of what we hear on FM radio originates from tapes or discs, the same holds true for that program source.

One way of combatting this problem is to add a dynamic expander to your stereo component system. An expander "senses" the sound level of program material and, in simple terms, makes the "louds" louder and the "softs" softer. In the past, expanders suffered from an effect described as "pumping and breathing." In other words, you could hear the expansion process taking place, as an effect in itself, over and above the actual improvement in dynamic range afforded to the reproduced sound of the musical program.

dbx, Inc. (71 Chapel Street, Newton, MA

02195) specializes in expanders and noise-reduction devices. The company's new two-band expander, the *model 2BX*, is shown in Fig. 1. The unit is intended for connection to a stereo component system via either the tape-input/tape-output jacks on a receiver or integrated amplifier, or by being interposed between a separate preamplifier/amplifier in separate-component systems.

The front panel of the *model 2BX*, which is finished in black and silver, has a POWER on/off switch and an indicator light on the left-hand side. A slide-control knob labelled EXPANSION to the right adjusts the degree of linear expansion—from 1.0 (no expansion) to 1.5 (50% expansion, in which every 2-dB change for input signals results in a 3-dB change at the output).

The most important innovation of this expander is its use of two separate frequency bands. Low frequencies are handled by one expansion circuit, while high frequencies are controlled by another circuit. (We'll discuss the importance of this feature later on in this

RADIO-ELECTRONICS AUDIO LAB

**R.E.A.L.  
SOUND**

RATES

DBX, INC. 2BX DYNAMIC EXPANDER

**EXCELLENT**


Copyright © Gernsback Publications Inc., 1979

article.) Two rows of LED's (five amber LED's and five red LED's per bank) indicate what is happening within each frequency band. The illumination of the amber lights in either row indicates that the signal frequencies are being *downward* expanded (i.e., low-level signals are lowered even more), while the illumination of the red LED's means that instantaneous signals are being expanded upward (loud signals are being made still louder).

The TRANSITION LEVEL control to the right of the rows of LED's determines the threshold or transition point between upward or downward expansion, and can be varied over a wide range to take care of a variety of program levels and types of music. Next to this control, two pushbuttons let you compare source and taped results, and two others let you select whether you want the expansion to occur *after* the tape outputs on the rear panel or ahead of them (for pre-expansion prior to taping).

The rear panel is shown in Fig. 2.

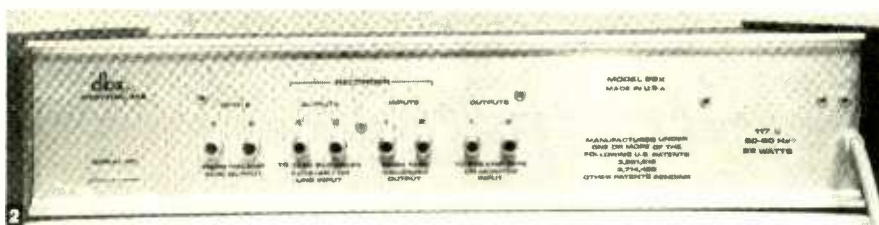Part of the reason why less-sophisticated expanders tend to breathe or pump audibly is due to their attack-and-release times. While a rapid attack-and-release time may be good for





## MANUFACTURER'S PUBLISHED SPECIFICATIONS:

**Expansion Ratio:** 1.0 to 1.5, linear, in dB. **Transition Level Range:** 30 mV to 3.0 volts. **Frequency Response (at 1.0:1.0 Expansion):** 20 Hz to 20 kHz,  $\pm 0.5$  dB. **Harmonic Distortion (at 1.0:1.0 Expansion):** 0.2% (20 Hz to 20 kHz). **IM Distortion (at 1.0:1.0 Expansion):** 0.15%. **Input Impedance:** 50,000 ohms. **Maximum Output Level:** 6.0 volts. **Power Requirements:** 117 volts, 50 to 60 Hz, 20 watts. **Dimensions:** 17 3/4" W  $\times$  3 3/4" H  $\times$  10 1/2" D. **Weight:** 8 lbs., 5 oz. **Suggested Retail Price:** \$450.

some types of music, different attack-and-release times may be desirable with other types of music. The *model 2BX*'s attack-and-release times actually follow the rate of change of the program envelope. In addition, attack-and-release times are scaled differently in each pair of frequency bands to provide an expansion characteristic that best suits the music.

As for the division of program material into two frequency bands, consider what would happen if in a given instant, a bass drum beat, or a series of beats, were to be sensed by a single-band expander. The level-detection circuits would momentarily increase the gain of the system, and, if other instruments or a vocalist's signal were also present, the entire program level would be expanded, resulting in an unnatural sort of heaving or breathing. By separating the lower frequencies from the mid-and high frequencies, the *model 2BX* does not allow the bass tones to influence vocals or mid-range instruments.

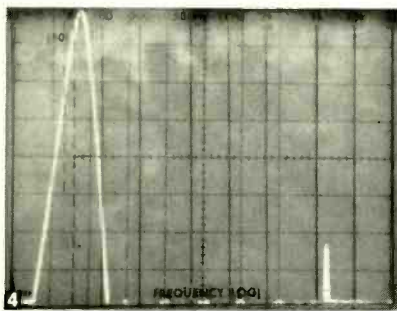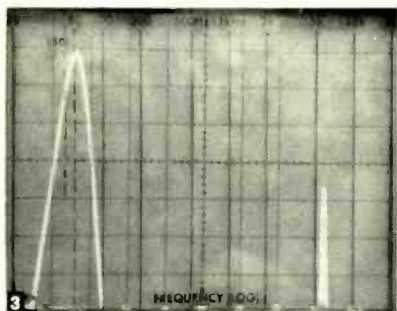To demonstrate how the expander is able to handle different frequencies differently, we fed in a mixture of 60 Hz and 7 kHz (readily available from our IM Distortion Analyzer).



With our spectrum analyzer set to its higher sensitivity mode (2 dB of amplitude per-vertical-division), we first examined the output with the expansion control set for 1.0 (no expansion). Figure 3 shows the response from 20 Hz to 20 kHz. Note that the 60-Hz component at the output is some 7-dB greater than the 7-kHz contribution to the overall signal.

Next, the threshold control was set so that the 60-Hz signal caused the first "upward-expansion" LED to light up. Since the high-frequency component was considerably lower in amplitude, amber lights in the high-frequency row of LED's lit up, indicating downward expansion. We advanced the expansion control to 1.5 (that is, to maximum expansion) and examined the output signal again, as shown in the scope photo of Fig. 4. Note that the low-frequency component has been expanded by some 2 dB (one vertical division). By contrast, the high-frequency component was actually downward-expanded by more than 3 dB. Thus,

TABLE 1

## R.E.A.L. SOUND PRODUCT TEST REPORT

Manufacturer: **dbx, Inc.**

Model: **2BX**

### EXPANDER PERFORMANCE MEASUREMENTS

SPECIFICATIONS	R-E Measurement	R-E Evaluation
Expansion ratio range (%)	0 to 50	Excellent
Transition level range (volts)	0.015-3.0	Excellent
Frequency response at 1:1 expansion (Hz-kHz, $\pm$ dB)	20-35, 0.5	Excellent
THD at 1:1 expansion (%)		
at 20 Hz	0.022	Excellent
at 1 kHz	0.02	Very good
at 20 kHz	0.02	Excellent
THD at maximum expansion (%)		
at 20 Hz	0.1	Very good
at 1 kHz	0.037	Excellent
at 20 kHz	0.045	Excellent
IM distortion, 1:1 expansion (%)	0.02	Excellent
IM distortion, maximum expansion (%)	0.18	Good
Maximum output level (volts)	7.0	Very good
<b>SUBJECTIVE EVALUATIONS</b>		
Attack time		Excellent
Decay time		Very good
Noise-reduction effect		Very good
Effectiveness of controls		Excellent
Ease of installation		Very good
Ease of use		Excellent
Additional features		Very good
<b>OVERALL EFFECTIVENESS OF EXPANDER</b>		<b>Excellent</b>

TABLE 2

### OVERALL PRODUCT ANALYSIS

Retail price	\$450
Price category	Medium/high
Price/performance ratio	Very good
Styling and appearance	Excellent
Sound quality	Excellent
Mechanical performance	Very good

Comments: The *model 2BX* expander goes a long way towards overcoming the chief objection many serious audiophiles have had against "add-on" dynamic expanders. It produces very little "breathing and pumping"—a rise and fall of the background noise level as the gain of variable-voltage-controlled amplifiers changes. Much of the improvement comes from the two-band design of the unit, and from its carefully programmed attack-and-delay times. The only expander that goes one step beyond this expander is dbx's *model 3BX*, which sells for \$200 more and divides the music frequency spectrum into three separate bands.

The effectiveness of the *model 2BX* will vary depending upon the type of music being reproduced. Obviously, not all program sources have been subjected to the same degree of compression and peak-limiting. It is important, therefore, to experiment with the *model 2BX* and to use its few front-panel controls to select the best overall effect for each type of musical program source. With FM radio programs, it was hardly ever necessary to alter the threshold setting once the unit was set up since FM modulation levels tend to remain fairly constant. With phonograph records, however, the average groove modulation can vary over a wide range from one disc to another, which is especially true in direct-to-disc records. The unit's secondary benefit—noise reduction—is clearly evident with all program material, but its chief virtue lies in its ability to restore missing dynamic range from just about any music program source. Once you experience the sound of music played through an expander such as this one, you may find not using it may make music sound extremely bland and unexciting.

the difference in levels between the two signal components is now around 12 dB. No single-band expander could have achieved these results.

### Lab measurements

The few lab measurements we made on the *model 2BX* are summarized in Table 1. It is clear that the distortion produced by the device is so low as to be inaudible, even when the maximum expansion is used. Frequency response is uniform over more than the audio spectrum, and therefore does not affect the tonality of reproduced program material.

The overall product analysis is shown in Table 2, along with our summary comments.

The *model 2BX* is easy to install and use. It covers an adequate adjustment range, and we

believe any expansion beyond 1.5:1 range would tend to make any reproduced music sound unnatural or artificial. A side benefit that should not be overlooked is the unit's ability to serve as a noise-reducing device. Since, with a properly adjusted threshold it provides both downward as well as upward expansion, residual noise levels (such as tape hiss or record-surface noise) that the detection circuits perceive as "low-level" signals are expanded downward and become less audible.

The *model 2BX* is a carefully engineered device that will appeal to serious music lovers who recognize the dynamic-range limitations of present-day program sources. Even though such devices may one day become obsolete, until that happens, the *model 2BX* provides the best alternative.

R-E



# LX303

## ALL THE MOST WANTED FEATURES AT A MOST WANTED PRICE...

**BIG ½" HIGH LCD DISPLAY**  
**USE INDOORS OR OUT**  
**200 HOUR 9V BATTERY LIFE**  
**AUTO ZERO, POLARITY,**  
**OVERRANGE INDICATION**  
**100 mV DC F.S. SENSITIVITY**  
**19 RANGES AND FUNCTIONS**



Removable cover stores test lead set furnished as part of the unit.



Available accessories include AC adapter, padded vinyl carrying case, 40KV DC probe, 10 Amp DC shunt.



X10 DCV probe adapter available for protecting input up to 10KV.



**ONLY \$74.95**  
**HICKOK**

THE HICKOK ELECTRICAL INSTRUMENT CO.  
 10514 Dupont Avenue • Cleveland, Ohio 44108  
 (216) 541-8060 • TWX: 810-421-8286

Here is the handfull of accuracy you've been waiting for. Hand-somely encased. Compact. Efficient. Only 12 ounces. Hickok's exciting, new LX 303, 3½ digit Mini-Multimeter with high quality components, one year guarantee and rugged Cyclo-lac® case offers features previously found only in expensive units... at a price under \$75.00! So why wait any longer? The amazing LX 303 is here, NOW! Another American made test equipment breakthrough from Hickok, The Value Innovator. Order today!

CIRCLE 48 ON FREE INFORMATION CARD

See your local Hickok distributor or order below

### SPECIFICATIONS:

**DC VOLTS (5 RANGES):** 0.1mV to 1000V; Accuracy  $\pm 0.5\%$  rdg  $\pm 0.5\%$  f.s.; Input impd: 10M $\Omega$ ; Max. input 1kV except 500V on 200mV range.

**AC VOLTS (40Hz to 5kHz):** 0.1V to 600V; Accuracy:  $\pm 1.0\%$  rdg  $\pm 0.5\%$  f.s. ( $-2\text{dB}$  max. at 5kHz); Max. input: 600V.

**RESISTANCE (6 LOW POWER RANGES):** 0.1 $\Omega$  to 20M $\Omega$ ; Accuracy:  $\pm 0.5\%$  rdg  $\pm 5\%$  f.s. ( $\pm 1.5\%$  rdg on 20M $\Omega$  range); input protected to 120VAC all ranges.

**DC CURRENT (6 RANGES):** 0.1 $\mu$ A to 100mA; Accuracy:  $\pm 1.0\%$  rdg  $\pm 0.5\%$  f.s.

**DIMENSIONS AND WEIGHT:** 5-7/8" x 3-3/8" x 1-3/4", 12 oz.; **POWER:** 9V batt. (not incl.) or Hickok AC adapter; **READ RATE:** 3/sec. **OPERATING TEMPERATURE:** 0°-50°C.

**ADVANCE ELECTRONICS**

TO ORDER CALL TOLL FREE  
 800-223-0474

54 West 45th Street, New York, NY 10036 212-687-2224

### PLEASE SEND ME

\_\_\_\_\_ Hickok LX303 Digital Multimeters ..... @ 74.95 ea.  
 \_\_\_\_\_ RC-3 AC Adapter, 115VAC (220VAC avail.) ..... @ 7.50 ea.  
 \_\_\_\_\_ CC-3 Deluxe Carrying Case ..... @ 7.50 ea.  
 \_\_\_\_\_ VP-10 X10 DCV Probe Adapter ..... @ 14.95 ea.  
 \_\_\_\_\_ CS-1 10A DC Current Shunt ..... @ 14.95 ea.  
 \_\_\_\_\_ VP-40 40 KV DC Probe ..... @ 35.00 ea.

Payment encl. ☐ Bill my: Master Charge ☐ VISA ☐

Account # \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Add \$3.00 Postage and Handling, N.Y. residents add sales tax.

RE-8

# HOBBY CORNER

## How to modify an alarm clock for multiple alarms and long-term alarms.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

IN A PREVIOUS ARTICLE WE DISCUSSED how to build a "slow" digital clock to measure weeks, months or years. I hope you have had an opportunity to build the recommended oscillator and experiment with your own slow clock. Now it is time (!) to add some refinements to it with a few additional simple circuits. Each of the circuits described here can be added to *either* a slow *or* a regular clock.

### Multiple alarm

A serious shortcoming of any alarm clock—slow or regular—is that it can be set to go off at one time only. Suppose, for example, you set your slow clock to go off at 10 am on the 18th of next month to remind you to have the car inspected. How then can you be reminded of your wife's birthday two weeks earlier and of your dental checkup three weeks later?

You *could* build several clocks, but a better solution would be to add more alarms to the one clock. Then, you could set each alarm for a different time. What you need is a way to build changeable *interfaces* between the clock IC output and an audio oscillator or LED's.

First, let's examine carefully the way a 7-segment readout creates the digits. The segments are designated by the letters shown in Fig. 1. Segments *b* and *c* are on to display a "1"; segments *a*, *b*, *g*, *e* and *d* display a "2" and so on. If you wrote all these letters and numbers down and studied the list, you would discover that there are certain short combinations that identify each digit exclusively.

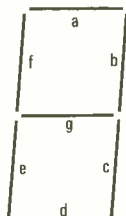


FIG. 1

For example, segments *a* and *f* are off (lo, 0) simultaneously *only* when digit 1 is being displayed. Segment *d* is on (hi, 1) while segment *f* is lo only when digit 3 is displayed. Such a short definitive pattern

TABLE 1

Digit	Segments	
	on/hi/1	off/lo/0
0	f	g
1		a,f
2		c,f
3	d	f
4	f	a,d
5		b,e
6		a,b
7	a	f,g
8	b,e,f,g	
9	a,f	d,e

exists for each digit, and some digits even have more than one pattern. One useful set of patterns is shown in Table 1; and the alarm circuits we'll describe are based on this set. Note that the hi and lo (1 and 0) states are for a clock using common cathode displays; just reverse these for common anode displays.

With the segment information shown in Table 1, you're halfway to building the circuit. All you need now are a few gates and an audio or visual indicator.

Let's build a circuit to remind yourself when the clock shows 7 hours and 20 minutes, whatever date or time that stands for. (You can use the same principles to set an alarm for any "time.")

The circuit in Fig. 2 lights the LED only when the hours digit is "7" and the 10's-of-minutes digit is "2." Trace out

the action of the gates to see how it accomplishes this. Of course, other gate combinations will produce the same result. Just use what is most convenient for you.

In Fig. 2, the 1's and 0's indicated in parentheses show the state of each line at 7:20. The LED requires no limiting resistor when it is used with CMOS gates unless the +V-supply is higher than 14 volts or so. The inset shows how to connect an LED that you want to light when the line goes high.

The input lines are connected to the digit drive pins of the clock IC. The top input line goes to segment *a* of the *hours* output, etc. If you have to use a segment connection on more than one alarm circuit, don't worry—you can add any practical number with no change in operation.

On a 12-hour clock you can use the AM/PM pin as a gate input to distinguish between 7:20 and 19:20, for example. On a 24-hour clock, you can use segments *b* and *g* as shown in Table 2.

TABLE 2

10's Hrs. Digit	Segments	
	hi	lo
Blank		b
1	c	
2	g	

Depending upon your clock's digital-drive circuit, you may find that the IC pin does not go high or low enough to switch the gate inputs. This may happen when there are current-limiting resistors between the pins and the digits. If you find this happens, simply replace the resistors with values up to 2K. The decrease in

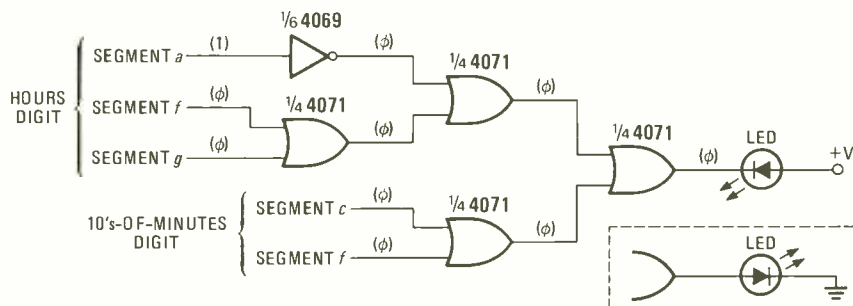


FIG. 2



digit brightness will be very little, but the changed load will allow the pin voltage to swing more.

I used LED's as alarm outputs on my clock. The LED's are arranged on a small panel next to labels on which is marked what each alarm is set for. You may want to use audible indicators with or without LED's to show which alarm is sounding off. A suitable audio oscillator can be made in many ways: by using transistors, unijunctions, 555's, etc. (See previous "Hobby Corners" and other articles if you need an oscillator circuit suitable for use as an alarm.)

Of course, you will have to change gate and clock IC connections whenever you wish to set an alarm for another "time." One approach is to use a bank of switches. Another method is to use a small section of solderless breadboard for cross-patching connections. Because changing alarm connections are made so seldom on a slow clock, I just tack-solder the connections as I need them.

A normal, real-time clock can be made into a multiple-alarm unit using the circuits described above for a slow clock. However, the inconvenience of resetting the alarms makes this of questionable value. With a normal clock, a more practical approach would be to use gates to pick off, say, 30-minute "ticks" that would drive counters, with the appropriate outputs being selectable through a switch or patch-cords.

#### Long-term alarm

Suppose you want to leave your digital clock *unmodified* so that it displays the time, yet also provides a reminder for next week or next year. This problem is relatively simple to solve using a few "external" components.

For example, suppose you want an alarm set at exactly 3 pm 43 days from now. First, if the clock has a built-in alarm circuit, disconnect the alarm from the clock IC output; then set the alarm for 3 pm.

Next, use the IC alarm pin to drive one or more counters. Finally, connect the counter output(s) to enable the original alarm circuit (or some other indicator) after 43 pulses (produced by 43 24-hour periods) have elapsed.

There is a wide variety of CMOS counters to choose from. There are standard counters, programmable counters, and even counters that can count up to 16,384 (for instance, the 4020 IC)! For proper functioning, you may have to invert the output of the IC alarm pin, depending upon your use of a positive-edge or negative-edge triggering counter, otherwise, the alarm may be 12 hours fast or slow when triggered on next month.

Note that you can use this same alarm technique with a slow clock (described last month) to count times of any desired length.

R-E




## fact: you can choose your microphone to enhance your individuality.

Shure makes microphones for every imaginable use.

Like musical instruments, each different type of Shure microphone has a distinctive "sound," or physical characteristic that optimizes it for particular applications, voices, or effects.

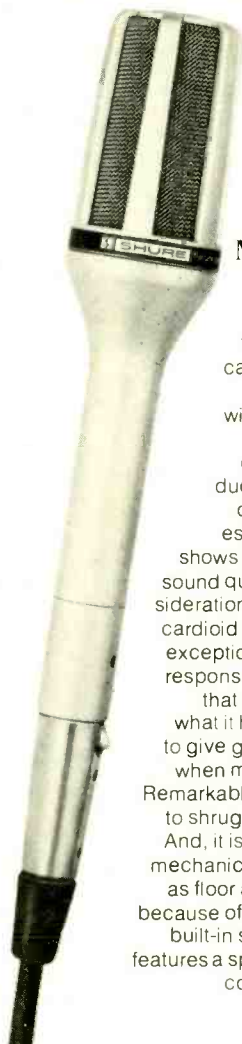Take, for example, the Shure SM58 and SM59 microphones:



### SM59 SM58

**Mellow, smooth,  
silent...**

The SM59 is a relatively new, dynamic cardioid microphone.


Yet it is already widely accepted as a standard for distinguished studio productions. In fact, you'll often see it on TV... especially on musical shows where perfection of sound quality is a major consideration. This revolutionary cardioid microphone has an exceptionally flat frequency response and neutral sound that reproduces exactly what it hears. It's designed to give good bass response when miking at a distance. Remarkably rugged—it's built to shrug off rough handling. And, it is superb in rejecting mechanical stand noise such as floor and desk vibrations because of a unique, patented built-in shock mount. It also features a special hum-bucking coil for superior noise reduction!




**Crisp, bright  
"abuse proof"**

Probably the most widely used on-stage, hand-held cardioid dynamic microphone. The SM58 dynamic microphone is preferred for its punch in live vocal applications... especially where close-up miking is important. It is THE world-standard professional stage microphone with the distinctive Shure upper midrange presence peak for an intelligible, lively sound. World-renowned for its ability to withstand the kind of abuse that would destroy many other microphones. Designed to minimize the boominess you'd expect from close miking. Rugged, efficient spherical windscreen eliminates pops. Lightweight (15 ounces!) hand-sized. The first choice among rock, pop, R & B, country, gospel, and jazz vocalists.

Some like it essentially flat...

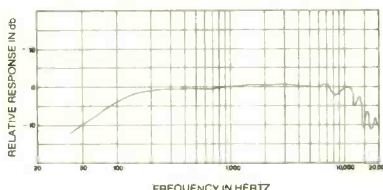

... some like a "presence" peak.

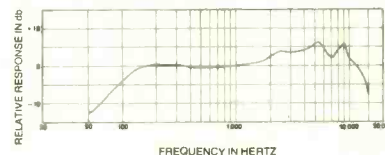

## professional microphones...by



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204, In Canada: A. C. Simmonds & Son Limited  
Manufacturers of high fidelity components, microphones, sound systems and related circuitry

CIRCLE 59 ON FREE INFORMATION CARD

# communications corner

## Are the new computerized CB's really computerized?

HERB FREIDMAN, COMMUNICATIONS EDITOR

AS EXPECTED, THE FIRST "COMPUTERIZED" CB transceivers—those incorporating a microprocessor—are the higher-priced, high-performance models. A natural question, however, is: "Does computerization improve communications?" (After all, communications is what CB is all about.)

The answer, unfortunately, is *no*. Computerization has essentially no effect on communications, at least not at the present time. At best, it is simply an operating aid or convenience. And, depending on your particular application, computerized CB can be a decided convenience or inconvenience.

The microprocessors—generally shown in schematics as a *box outline* with many connections protruding from each side—are basically user-programmable channel-selection (switching) circuits much as you might find in late-model VHF scanners before they also were computerized. At the touch of a button, the transceiver tunes through all 40 channels,



FIG. 1

stopping on busy or clear channels. The touch of another button lets you step through the channels one at a time; or by pressing a combination of pushbuttons, you can direct-access a particular channel. All this can be done (and has been done) with individual IC's; we don't really need the large-scale integration of a microprocessor. Although the use of a single IC does increase reliability.

The real difference between a comput-

erized CB and a scanning CB is in the *memory*. The microprocessor permits you to program a specific group of channels to be scanned in a specific order. As a general rule, most CB microprocessors contain from 5 to 10 channel memories. Some manufacturers chose to make one of the memories Channel 9, which actually means you have less user-selected channel memory. The advantage is that you can receive the emergency-only channel at the push of a button.

The microprocessor also features keyboard entry, whereby a keypad similar to those used on *Touch-Tone* telephones provides the means to select channels, program memories and to choose the various functions.

Most of the "computerized" transceivers use each keypad switch for two purposes, as if the designer couldn't stand to see a switch with a *single* numeral or function printed above or below. As you might expect, this produces complexity beyond what is generally needed, which tend to confuse the consumer.

One of the few manufacturers who opted to go "the other way" (i.e., using

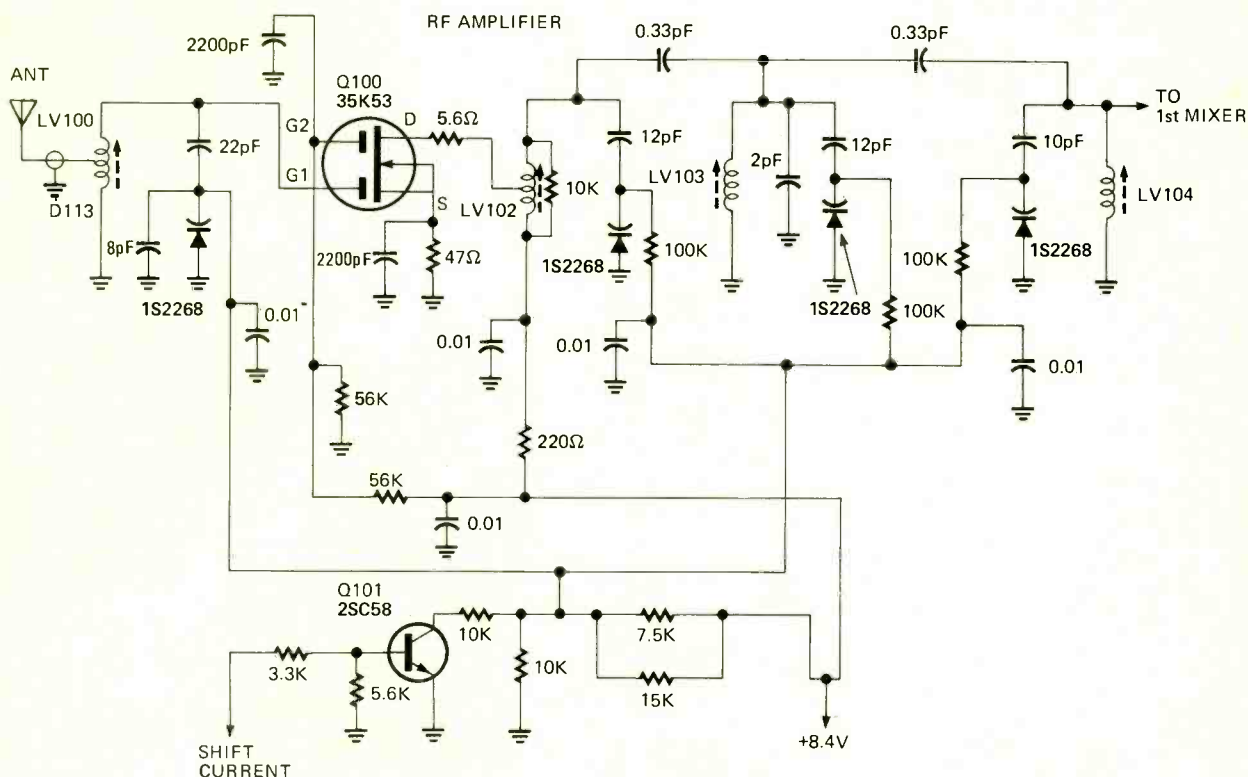


FIG. 2



the microprocessor for what many would consider the most important functions) is Robyn, whose uncluttered keypad from the model SB-540D AM/SSB Base Station is shown in Fig. 1. In this unit push-buttons M1-M5 handle the memories, which can be programmed in any sequence at any time. You can scan only the memory channels by pressing the MEMO SCAN switch, or you can directly tune to a memory by first pressing the MEMO RECALL switch that also permits you to reprogram any memory at any time. The SCAN DELAY switch *holds* the channel while it is in the scan mode so the tuning doesn't skip to the next memory or channel during the pause between transmissions. If there is no activity on the channel, the scan delay releases and the scanning resumes.

The Robyn keypad is presently the easiest to use and understand. It is almost self-explanatory, something that cannot necessarily be claimed of keypads of other computerized CB's.

But regardless of the complexity and sophistication of a microprocessor-controlled CB, the transceiver remains essentially the same in terms of reception and transmission as those of other CB's: Computerization has no effect on sensitivity, selectivity, RF output or modulation. Essentially, the microprocessor simply provides memory and scanning on a single IC, rather than on several. And if the microprocessor is simply a substitute for several IC's previously used in VHF receivers, and if it has no effect on communications specifications, do we in fact truly have computerized CB transceivers? Does computerization of only operating conveniences justify the term "computerized"? We'd like to hear your opinion—pro or con—so just drop us a short note. (Address all correspondence to: Communications Corner, Radio-Electronics, 200 Park Avenue South, New York, NY 10003.—Editor)

### Look Ma, no tuning capacitor!

If you ever had the need for relatively widely spaced VHF coverage (approximately 150 MHz–170 MHz) you know that you can generally peak the tuned circuits—such as the receiver's front end—for maximum performance to the low, middle or high side while experiencing reduced performance somewhere within the unit's frequency range. Generally, scanners are peaked for the center of the frequency band and you take whatever performance you can get at the frequency extremes.

While "letting the ends take care of themselves" is fine for hobbyist and semi-professional receivers, things should not take care of themselves if a life might depend on optimum performance. For instance, commercial VHF radios, such as those used on all kinds of ocean-going craft, optimize performance on *all* frequencies; it's handled very easily now that

the phase-locked-loop (PLL) digital-frequency synthesizer is almost universal in all multifrequency receivers. In fact, because the PLL digital synthesizer is so convenient and competitively priced, it's used in many hobby/professional scanners such as those manufactured by Regency, Electra and Radio Shack; and even a hobbyist can enjoy optimum sensitivity from one end of the frequency band to the other.

While the tuning of the synthesizer is electrical, it doesn't require variable tuning capacitors or even trimmers. And it's the lack of a tuning capacitor that makes it all possible.

The Fig. 2 schematic shows how this can be accomplished. The circuit shown represents the front end of a commercial ship-to-shore VHF radio. The four diodes with the parallel-line capacitor symbol at the cathode end are *varactors*—diodes whose anode/cathode capacitance can be precisely controlled by an applied DC voltage. The varactor capacitance represents only a small part of the total capacitance needed to tune each resonant circuit using adjustable coils LV100–LV104. A fixed capacitor in series with each varactor, in addition to stray capacitance, establishes the minimum circuit capacitance for the L–C network. Note that the DC supply for each varactor originates at a common source—the collector circuit of transistor Q101.

When the user sets the frequency selector(s) of the VHF radio, a *shift* current is applied to the base of Q101, which, in turn, changes the transistor's collector-emitter current that flows through R110–R111. This causes a variation in the voltage available at the junction of R110–R111 that is the "control" voltage for the varactors. The varactors' capacitance changes simultaneously, tuning each L–C network to the operating frequency.

While commercial radios apply a fixed-shift voltage so that the receiver tunes to one specific frequency, the same idea is used in the digitally controlled scanning monitors. As the scanning frequency sweeps within the chosen limits, the PLL circuits also provide a sawtooth (or sweeping) waveform (increasing or decreasing the DC voltage) to the front-end varactors, thereby tuning the front end precisely to the frequencies being tuned. When the radio is in the manual mode, the PLL circuit applies a fixed voltage to the varactor diodes, tuning the front end to whatever frequency you selected (or "punched in").

Essentially, the digital-frequency synthesizer allows you to tune precisely to the operating frequency, rather than settle for a broadband adjustment. It is one of the important differences between a broad-tuned crystal-controlled VHF monitor and continuously tuned digitally controlled VHF scanner.

R-E

## The Kit Project of a Lifetime...



## A Schober Electronic Organ

When an electronic project ends, we always seem to wish there were more to do. Well, here's the project where there really *is* more to do. It's the *ultimate* electronic kit, a Schober Electronic Organ.

We've had thousands of letters in our 24 years from enthusiasts all over the world who have had the time of their lives assembling Schober quality parts into fine musical instruments, guided by the famous crystal-clear, step-by-step Schober instructions. Many were family projects; even the little ones can sort resistor colors!

But when assembly is done, the fun is just beginning. You're ready to start a lifetime of musical enjoyment as a Schober course teaches you and your family to play.

A Schober Organ makes a wonderful gift for a music-loving wife or child—or for yourself. It *sounds great*—far more pleasing and authentic, with far greater musical resources than anything ready-built at a comparable price. In fact, you could easily pay twice as much and not get a better organ.

Basic Schober Organ Kits range from \$650 to \$3391—with five models to choose from. Each kit is complete with everything needed. The instructions are comprehensive, precise, and specific, giving you every bit of information you need, assuming no prior knowledge of organs—or even electronics.

There's optional equipment, too, which you can add any time later, new effects for more fun.

Send TODAY for the free color catalog. Enclose \$1 if you'd like the 12-inch demo record, so you can let your own ears tell you about Schober musical quality.

SCHOBER ORGAN CORP., Dept. RE-186  
43 West 61st St., New York NY, 10023  
Send Catalog. ☐ I enclose \$1 for record.

Name: \_\_\_\_\_

Address: \_\_\_\_\_

City, State, Zip: \_\_\_\_\_

CIRCLE 56 ON FREE INFORMATION CARD

# computer corner

## 8085 A look at the 8085 and how it compares to the 8080.

P. RONY, C. TITUS, D. LARSEN, J. TITUS\*

PAST COLUMNS HAVE LOOKED AT SOME applications of the 8085 central processing unit and some of IC's that are among the 8085 family. Now let's take a closer look at the 8085 and how it compares with the 8080.

One of the 8085's main features is that it is software-compatible with the 8080 machine codes. Thus, a 303 code is a jump (JMP) instruction in both systems. (The 8085 has two additional instructions to be discussed later.) Basic 8080 systems generally include a clock generator and a status latch circuit for external control. These functions are now provided for within the 8085. A simple R-C network or a crystal can be used directly with the 8085 to generate the necessary clock pulses. Many of the control signals required by external devices are now generated in the 8085 IC, further reducing the amount of external logic required.

There is a price to pay for this, though. The 8085 uses one set of eight lines to transmit both data and address information. In some systems, it may be necessary to latch the address bits (A7-A0) so that they are readily available for use. An Address Latch Enable signal (ALE) is output by the 8085 to control such a latch circuit. This type of bus multiplexing was also done in the 8008, the first general-purpose 8-bit microprocessor IC.

The 8085 provides the high-address bits (A15-A8) on eight output pins. These signals have no other purpose and they are not multiplexed. They are equivalent to the A15-A8 lines in an 8080-based computer. Some other 8085 input and output signals such as interrupt (INTR), interrupt acknowledge (INTA), RESET, HOLD, hold-acknowledge (HLDA), and READY operate as they do in 8080 systems. Two new 8085 outputs include CLOCK OUT, a TTL-compatible clock signal of one-half the system clock frequency, and RESET OUT, which can be used to reset other system components. The RESET OUT signal is derived from the reset input to the 8085.

\*This article is reprinted courtesy American Laboratories. Dr. Rony, Department of Chemical Engineering, and Mr. Larsen, Department of Chemistry, are with the Virginia Polytechnic Institute & State University. Both Dr. C. Titus and Mr. J. Titus are with Tychon, Inc.

Three control signals manage the flow of data to and from memories and the CPU, as well as to and from I/O devices and the CPU. These signals are:  $\overline{IO/M}$ ,  $\overline{RD}$  and  $\overline{WR}$ . The  $\overline{IO/M}$  signal is used to indicate what type of device the 8085 is attempting to communicate with: logic 1 = I/O devices and logic 0 = memories. The  $\overline{RD}$  and  $\overline{WR}$  signals coordinate the reading or writing of data, respectively. These three signals are used directly by the 8085-compatible memory and by I/O devices such as the 8155 and 8355. In other systems, you may have to use these signals to generate the  $\overline{MR}$ ,  $\overline{MW}$ ,  $\overline{IN}$  and  $\overline{OUT}$  signals that were discussed previously. Figure 1 shows the gating.

In almost all 8080-based systems, in-

like interrupt input. These interrupts have their vector addresses placed within the address space 000 000 to 000 100. Some of these addresses are placed between the usual 8080 vector addresses, leaving only four bytes of storage space between interrupt vector addresses. These new interrupts act in the same manner as the normal 8080-like interrupts, which means you still need a stack.

The 8085 also has a single input pin and a single output pin on the IC itself that can be controlled directly by software. Of course, the 256 addressable I/O port capability is still maintained. The two single I/O connections can be used for a single sense input and a single control output. Additionally, they could be used for serial I/O to a terminal or a teletypewriter, with the actual serialization being done by software.

Two new, single-byte instructions al-

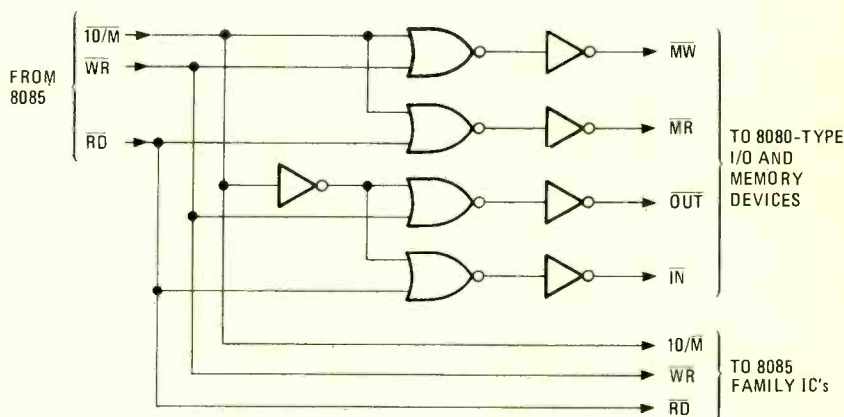


FIG. 1

errupts are implemented with an interrupt instruction port and restart instructions. The 8085 has four new interrupts that have been implemented. (See Table 1.) The overall priority of these interrupts from the highest to the lowest is as follows: TRAP, RST 7.5, RST 6.5, RST 5.5 and INT. The INT input is the usual 8080-

low you to manage the new interrupts and the two I/O lines, SID and SOD, (Serial Input Data and Serial Output Data). These instructions are: Set Interrupt Mask (SIM = 060) and Read Interrupt Mask (RIM = 040). The A-register is used as the source or the destination of the data bytes for each operation. R-E

TABLE 1—INTERNAL 8085 INTERRUPTS

Name	Restart Address	Characteristics
TRAP	000 044	Highest priority of all interrupts; nonmaskable, always "on"; both edge- and level-sensitive.
RST 5.5	000 054	Maskable, logic-1 sensitive
RST 6.5	000 064	Maskable, logic-1 sensitive
RST 7.5	000 074	Maskable, positive-edge sensitive



**PHILIPS****BK PRECISION****LEADER****FLUKE****TRIPLETT****VIZ** formerly **RCA****DATA PRECISION****Non-Linear Systems****DORIC****HICKOK****Simpson****FLUKE****DIGITAL MULTIMETERS****NEW 8022A**

- Extensive overload and transient protection
- Rugged construction
- Hi/Lo power ohms for in-circuit resistance and diode testing
- 10 MΩ input impedance doesn't load circuit
- 200 hour battery life — low battery indicator
- Large LCD readout — 2000 counts
- 1 year calibration cycle
- One-hand operation

**NOW \$129.****BASIC SPECIFICATIONS**


	DC Volts	AC Volts	DC Current	AC Current	Ohms
Range	0.2-1000V	0.2-750V	0.002-2A	0.002-2A	200Ω-20 MΩ
Resolution	100 μV	100 μV	1 μA	1 μA	0.1Ω
Accuracy*	(0.25 + 1)	(1 + 2)	(0.75 + 1)	(1.5 + 2)	(0.2 + 1)

**FLUKE****DIGITAL MULTIMETERS****8020A NOW 0.1% Basic dc accuracy**

- 26 Ranges—5 Functions plus New Conductance Function for up to 10,000 MΩ Leakage Measurements
- Extensive Overload and Transient Protection
- Rugged Construction—2 Year Warranty
- Hi/Lo Power Ohms for In-circuit Resistance and Diode Testing
- 10 MΩ AC/DC Input Impedance Doesn't Load Circuit
- 200 Hour, 9V-Battery Life—Low Battery Indicator
- Large LCD Readout—2000 Counts
- 0.1% Basic dc accuracy
- One Hand Operation
- Complete with Battery and Test Leads

The new Fluke 8020A continues the standard of excellence set by the highly successful 8000A multimeter family. Many features set the 8020A apart as a truly exceptional instrument. Twenty-four ranges and 5 functions include measuring capability up to 1000V dc, 750V ac, 2A ac/dc and 20 MΩ. Hi/Lo ohms are included for in-circuit resistance and diode test capability. In addition, a new Conductance function allows resistance and leakage measurements up to 10,000 MΩ, a must for circuit board work and component checking.


The 8020A has been designed with the user in mind and features exclusive one-hand operation. For harsh service environments, the 8020A has a ruggedized case and extensive overload/transient protection backed up by a 1-year warranty. Long term stability (1-year calibration cycle) is excellent with only three cal adjustments. Up to 200 hours of continuous operation can be expected from a single 9V alkaline battery.

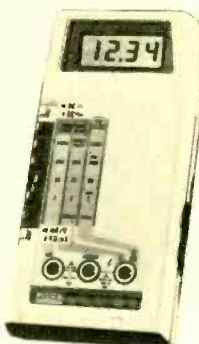**\$169.****FREE CASE WITH 8020A****New Portable Digital Capacitance Meter****BK PRECISION****MODEL 820**

- Measures capacitance from 0.1pF to 1 Farad
- Resolves to 0.1pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy
- Special lead insertion jacks or banana jacks
- Fuse protected
- Uses either rechargeable or disposable batteries
- Overrange indication

**\$149.95****REG \$180****LEADER Instruments Corp.****LTC-906 Transistor Checker**

- Automatically checks transistors, FET's, diodes, good/bad, in or out of circuit.
- Automatically identifies Germanium or Silicon.
- Automatically identifies emitter base and collector.
- LED display plus audible tone indication.
- Absolute meter readout of Hfe, Bve and Leakage current.

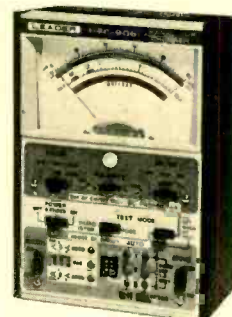**LBO-515 25MHz Dual Trace/Dual Time Base Scope with Variable Delay****LEADER Instruments Corp.****\$1175.****REG \$1395**

- Built-in variable delay circuitry — 1μ Sec to 5 Sec
- 5mV/Div Vertical Sensitivity.
- Rectangular, 8 x 10Div CRT with internal graticule
- Selectable synchronization, automatic, normal, single trace and reset modes.
- 14nSec rise time.
- Trigger CH-1 or CH-2.
- H.F. filter plus TV sync. assures stable displays.

**New Sweep/Function Generator****MODEL 3020 BK PRECISION**

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator
- Covers 0.02Hz-10MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs
- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel or externally programmable

MASTERCARD  
VISA**THE TEST EQUIPMENT SPECIALISTS****TOLL FREE HOT LINE  
800-223-0474**

54 West 45 Street, New York, N.Y. 10036 212-687-2224

**ADVANCE ELECTRONICS**

# service clinic

*If the symptom is a horizontal bar, suspect the filter capacitors.*

**JACK DARR, SERVICE EDITOR**

EVERY ONCE IN A WHILE, AN OLD FAMILIAR problem crops up again. Back in the "old days," we used to run into one particular symptom at quite frequent intervals. This symptom was the horizontal bar on the TV screen. It usually measured from  $\frac{1}{4}$ -inch to  $\frac{3}{4}$ -inch high, and crawled slowly up the screen. The bar could be lighter or darker than the picture, and it showed up mainly in less-expensive black-and-white TV sets.

The cause of this symptom was a voltage pulse getting into the video stages, where it caused partial blanking (a dark bar) or an increase in brightness (a light bar). Since there was only a single bar, this was obviously a 60-Hz line phenomenon. Many of the DC power supplies were full-wave supplies; so ripple would create two bars. In that case, where does the single bar come from?

It comes from the high-current pulse that is drawn by the vertical-output stage, once for each field. If this voltage isn't filtered out and gets into the video amplifiers, it causes the bar to appear. The bar crawls up the screen because of the very small difference between the vertical frequency of the picture and the local 60-Hz line ripple.

The major cause of this problem in the older sets was poor DC power supply filtering; that is, defective filter capacitors or poorly designed filter circuits. In some old TV sets, I have had to add as much as 100  $\mu$ F of capacitance in order to get rid of the bar. Now, the same symptom is showing up in late-model solid-state TV sets. The "Service Clinic" mailbag has received quite a few questions on this problem.

The basic cause is still apparently that voltage pulse from the vertical-output stage getting into the video stages, which happens because the pulse isn't being filtered out. There is one *new* cause, but the reason is the same (more on this later).

Here, the scope is the best tool to use for a quick test. You don't have to scope the video-stage signals because you know that pulse is there just from looking at the screen. Scope the DC supply to the vertical-output stage and look for the voltage pulse. If it appears there, check the large

filter capacitor that *should* be there. You can also go back to the filter output of the DC power supply and look at the ripple waveform. The amplitude of this waveform should be very low—typically, only 1.2 volt or so maximum. It should be stationary and usually looks like a sawtooth. If too much vertical signal is managing to get back into this, the waveform will slowly writhe and bend. Here again, this is due to the small phase difference between the 60-Hz frequency and the vertical frequency.

This usually means that one or more of the filter capacitors is not working properly. High power factor is a common cause; this reduces the filtering efficiency of the capacitor. One odd reaction occurs in these cases. If the defective capacitor does have high power factor, you can bridge it with a good one but it won't help! To make sure, unhook the original capacitor and put in a new one that's just as large or larger.

Now, here's the new wrinkle. In newer sets, particularly those with modules or separate circuit-board assemblies, the crawling bar can be caused by a very small difference in *ground potential* between the grounds on a board and the main chassis ground on the motherboard. In some sets, you can clear this up by adding a heavy jumper between board ground and the chassis, or by moving the ground-return point of a big capacitor from the board to the chassis. Check the service notes and modifications on the set; you may find this procedure is recommended.

Always examine all grounds very carefully. If they look suspicious, resolder them. I can vouch for this from recent bitter experience! My own antique model CTC-15 had exhibited an assortment of weird symptoms. I wasted quite a bit of time changing tubes, cleaning socket contacts, etc. One day, in desperation, I drew my trusty solder gun and resoldered all seven ground points on the color board. This cleaned up all the symptoms! So, if all else fails, try soldering grounds—you never can tell!

As I said before and repeat for emphasis, this pulse always appears in the video signal. All you have to do is find out the

cause and repair it. Changing filter capacitors is the answer in most cases; and fixing bad ground connections should take care of what's left! When replacing a capacitor, make sure that the replacement has an equal or higher voltage rating. **R-E**

## service questions

### DOUBLE TROUBLE

*Thanks for your letter concerning the problems I had in a General Electric chassis H-3. You confirmed my idea that the trouble was in the AGC. Checking out the AGC circuit completely, I found a 7-ohm short to ground on the AGC control itself. I took it off, took it apart and found . . . nothing! I put back after cleaning and it worked!*

*Now there was a picture, but it was weak and full of color blobs. This problem was due to a break in the +280-volt supply line, where focus resistor R554 goes to the +280-volt line. Apparently when the chassis was moved around, this resistor had been pushed over or moved enough to break the printed-circuit conductor to which it was soldered. Everything works fine now, and thanks for holding my hand!—W. McL., Phoenix, AZ.*

Glad to have been of some help!

### HALF A RASTER, BLOWN DIODES

*There are several problems in this Magnavox model T982. The scan board was a mess where D207, D208 and D209 are, and the three little chokes marked on the board had been replaced with small resistors, which were also burned up. I replaced the diodes with 2.5-amp diodes, and the resistors with 0.5-ohm types. When I turned the set on, only the top half of the raster showed with picture, color and sound all OK. Then I lost all the vertical sweep, and everything got hot.*

*Diode D208 had opened up again. I killed the -12.7-volt supply and checked capacitor C204 on the -12.7-volt supply; it was OK. Do you have any ideas?—M.D., APG, MD.*

A few. First, do not use stock diodes as substitutes for D207–D209. These diodes are fed from the flyback, and you *must* use fast-recovery diodes. The half-raster



problem is due to one of the transistors in the vertical-output stage (a complementary-symmetry circuit) being open or having lost the DC supply. One transistor is fed from the +16-volt line, the other transistor from the -12-volt line, and both these supplies come from the same area. Check for a possible shorted capacitor.

(Feedback: "Capacitor C203 was blown! That really helped!")

#### VOLTAGE OVERLOAD

*Please send help. This Zenith 25EC58 has a raster but no video. Resistor R355 is open. Replacing R355 blows the horizontal-output transistor and resistor R354 smokes. One side of diode CR221 reads +50 volts, the other side reads +250 volts. What's wrong!—A. C., Puerto Nuevo, PR.*

From the symptoms you describe, there's a short or an overload somewhere in the boost voltages, especially in the +240-volt supply that flows through R355. Check both boost diodes, CR221 and CR219. Make sure to use fast-recovery-type diodes for replacements in this and any other set using flyback-derived DC power supplies.

(Feedback: "Diode CR221 was very leaky. I replaced it, and changed CR219 just for luck. The set now works OK. Thanks a lot!")

R-E

**For  
faster  
service  
  
USE  
ZIP  
CODE  
  
on  
all  
mail**

INTERNATIONAL FM-2400CH

# FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability:  $\pm 0.0005\%$  from  $+50^\circ$  to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm 0.00025\%$  from  $+25^\circ$  to  $+125^\circ$  ( $0.00125\%$  special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	\$627.72
RF crystals (with temperature correction)	26.26 ea.
RF crystals (less temperature correction)	19.93 ea.
IF crystals	catalog price



INTERNATIONAL CRYSTAL MFG. CO., INC.  
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 58 ON FREE INFORMATION CARD

## A Classroom In Your Mailbox!

STUDY  
Two-Way Radio

THROUGH THE  
REVISED

**MTI**

Home Study Course

Send coupon below for free course outline

No obligation — No salesman will call

Professional Training in a Unique Career Field

Providing Training to the Industry Since 1960

## study FM two-way radio at home!

I am interested in learning more about professional FM two-way radio. Please send me full details on the MTI training program.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City/State/Zip \_\_\_\_\_

**MTI**

A3H

**Mobile Training Institute**

Box 735, Camp Hill, PA 17011-U.S.A.

CIRCLE 42 ON FREE INFORMATION CARD

THE GOVERNMENT  
CAN DO EVERYTHING  
THE UNITED WAY DOES  
ONLY THEY  
WRAP IT UP FOR YOU  
IN NICER RED RIBBON.  
MILES AND MILES OF IT.



One of the best things about United Way is not what it does, but what it doesn't do.

For instance, because United Way is run almost entirely by volunteers, it is able to return an amazing 89¢ of every dollar to people who need it. That means less than 11¢ goes for administrative costs. So it doesn't waste your money.

And because United Way is re-created each year with a combination of old and new volunteers, it doesn't become over encumbered with huge staffs of people who might actually get in the way of progress.

So it doesn't strangle you in red tape.

All of which means that because of what United Way doesn't do, it can do a much better job at what it does do.

Helping people.



Thanks to you it works for all of us.

© Public Service of the Magazine & The Advertising Council

AUGUST 1979

73



# BEST IN NEW ELECTRONICS BOOKS

- ☐ Design, Bld & Pgrm Yr Own Wkng Computer Sys 308 p. \$7.95
- ☐ Master Hdbk of 1001 MORE Practical Elect. Ckts 700 p. \$12.95
- ☐ Handbook of Electrical Noise: Msmnt & Technology 280 p. \$6.95
- ☐ Microprocessor Cookbook 266 p., 124 il. \$5.95
- ☐ How To Build Your Own Working Robot Pet 238 p., 86 il. \$6.95
- ☐ Practical Electrical-Installation, Repr & Rewiring 406 p. \$7.95
- ☐ Radio Control Handbook—4th Edition 420 p., 315 il. \$9.95
- ☐ The Giant Book of Amateur Radio Antennas 462 p., 255 il. \$8.95
- ☐ How to Build Your Own Working 16-Bit Microcomputer 96 p. \$3.95
- ☐ Electronic Designer's Handbook—3rd Edition 350 p., 278 il. \$9.95
- ☐ Electrical Hdbk for RVs, Campers, Vans, Boats & Trailers \$3.95
- ☐ Making and Using Electricity From the Sun 144 p., 85 il. \$5.95
- ☐ Lasers, the Light Fantastic 294 p., 158 il. \$6.95
- ☐ The Power Supply Handbook 420 p., 282 il. \$7.95
- ☐ The Complete Handbook of Robotics 364 p., 137 il. \$7.95
- ☐ Artificial Intelligence 252 p., 118 il. \$7.95
- ☐ Hdbk of Remote Control & Automation Tech. 294 p., 250 il. \$7.95
- ☐ Install Your Own Home or Mobile Electric Power Plant 252 p. \$5.95
- ☐ Build Your Own Working Robot 238 p., 117 il. \$5.95
- ☐ The "Compuator" Book 322 p., 224 il. \$7.95
- ☐ Miniprocessors: From Calculators to Computers 192 p., 67 il. \$5.95
- ☐ Master Transistor/IC Substitution Handbook 518 p., 165 il. \$7.95
- ☐ Cber's Handy Manual of Base Stations 96 p., 55 il. \$2.50
- ☐ Complete Hdbk of Public Address Sound Sys 272 p., 148 il. \$7.95
- ☐ Modern Transistor Radios 64 p., 112 il. \$2.50
- ☐ Modern Crystal Radios (Make and Use Series) 64 p., 101 il. \$2.50
- ☐ Home-Brew HF/VHF Antenna Handbook 210 p., 143 il. \$5.95
- ☐ Microwave Oven Service & Repair 420 p., 210 il. \$9.95
- ☐ IC Function Locator 224 p., 28 il. \$5.95
- ☐ Cber's Handy Manual of SSB 80 p., 42 il. \$2.25
- ☐ Beginner's Guide to Making Electronic Gadgets \$4.95
- ☐ Fire & Theft Security Systems—2nd Edition 192 p., 114 il. \$5.95
- ☐ Modern Digital Communications 308 p., 122 il. \$6.95
- ☐ Practical CB Radio T'shooting/Repair 2nd Ed. 406 p., 169 il. \$7.95
- ☐ Microprocessor Program. for Computer Hobbyists \$8.95
- ☐ Illus. Dict. of Broadcast-CATV-Telecommunications 420 p. \$8.95
- ☐ Hdbk of Marine Electronic & Electrical Sys 546 p., 338 il. \$9.95
- ☐ Linear IC Applications Handbook 280 p., 184 il. \$6.95
- ☐ Build-It Book of Optoelectronic Projects 238 p., 175 il. \$5.95
- ☐ Photo Guide to AM/FM Stereo Repair 288 p., 281 il. \$7.95
- ☐ Servicing Medical & Bioelectronic Equipment 350 p., 165 il. \$8.95
- ☐ Solid-State Motor Controls 322 p., 162 il. \$8.95
- ☐ How to Use AF & RF Signal Generators 238 p., 162 il. \$5.95
- ☐ Model Railroad Electronics 308 p., 224 il. \$5.95
- ☐ The ABC Book of Hi-Fi/Audio Projects 182 p., 131 il. \$4.95
- ☐ Repair Small Gasoline Engines, 2nd Ed 392 p., 251 il. \$6.95
- ☐ 88 Practical Op Amp Circuits You Can Build 140 p., 120 il. \$4.95
- ☐ Restoring and Collecting Antique Reed Organs 320 p., 124 il. \$8.95
- ☐ How to Build Metal/Treasure Locators 140 p., 58 il. \$3.95
- ☐ Build-It Book of Digital Electronic Timepieces 294 p., 209 il. \$6.95
- ☐ C.E.T. License Handbook, 2nd Edition 448 p., 381 il. \$9.95
- ☐ Third Class FCC License Study Guide 322 p., 88 il. \$6.95
- ☐ Practical Solid-State DC Power Supplies 196 p., 151 il. \$6.95
- ☐ 106 Easy Electronics Proj...Beyond the Transistor 244 p. \$5.95

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Clip entire ad to order. 100% guaranteed or your money refunded.

**TAB BOOKS** DEPT. RE-89  
BLUE RIDGE SUMMIT, PA. 17214

CIRCLE 9 ON FREE INFORMATION CARD



**Get A GNOME**  
the original micro-synthesizer

John Simonton's time-proven design provides two envelope generators VCA, VCO & VCF in a low cost, easy to use package.

Use alone with its built-in ribbon controller or modify to use with guitar, electronic piano, polytonic keyboards, etc.

The perfect introduction to electronic music and best of all, the Gnome is only \$59.95 in easy to assemble kit form. Is it any wonder why we've sold thousands?

( ) Send GNOME MICRO-SYNTHESIZER Kit (\$59.95 plus \$2.00 postage)  
( ) GNOME MICRO-SYNTHESIZER (Fully Assembled) \$100.00 plus \$2 postage  
( ) Send FREE CATALOG


name: \_\_\_\_\_  
address: \_\_\_\_\_  
city: \_\_\_\_\_ state: \_\_\_\_\_ zip: \_\_\_\_\_  
BAC/VISA MC card no. \_\_\_\_\_  
DEPT. 8R  
1020 W. WILSHIRE, OKLAHOMA CITY, OK 73116

CIRCLE 19 ON FREE INFORMATION CARD
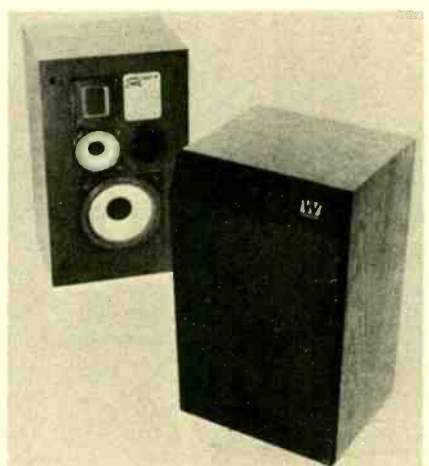
# stereo products

More information on stereo products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.


**HI-FI SPEAKER SYSTEM**, the *Wharfedale model Teesdale*, features an 8-inch woofer, a 4-inch mid-range cone and an isodynamic tweeter. Both the mid-range and tweeter were designed using laser beam holography techniques. The unit pro-



CIRCLE 131 ON FREE INFORMATION CARD

vides a frequency response from 40 Hz to 26 kHz  $\pm 3$  dB, and an 87-dB sound-pressure level for 1 watt at 1 meter. The *Teesdale* comes in walnut veneer, measures 23  $\times$  13  $\frac{1}{2}$   $\times$  11-inches, weighs 31 lb., and has a suggested retail price of \$270.—**Rank Hi-Fi, Inc.**, 20 Bushes Lane, Elmwood Park, NJ 07407.

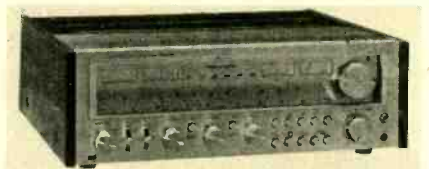**AM/FM STEREO RECEIVER**, *Realistic model STA-2100*, provides 120 watts-per-channel into 8 ohms from 20 Hz to 20 kHz, with no more than 0.1% THD. Its features include bass, mid-range and treble controls; 25- and 75- $\mu$ s de-emphasis; multiplex filter; dual tape monitors and dubbing;



CIRCLE 132 ON FREE INFORMATION CARD

DIN and phono tape-in/tape-out jacks; phono sensitivity switch; and high-cut and low-cut filters. The *model STA-2100* also includes built-in noise-reduction protection, plus AM signal-strength and FM center-channel meters and power meters.

The FM front end contains a MOSFET amplifier, ceramic filters and PLL circuitry. Specifications include: For the amplifier: Frequency response, 15 Hz—25 kHz  $\pm 2$  dB at 10 watts; IM distortion, 0.05% at 70 watts; S/N ratio, 70 dB

(phono); 75 dB (aux). For the FM section: IHF sensitivity, 1.6  $\mu$ V (10.1 dBf); capture ratio, 1.5 dB; alternate channel rejection, 75 dB; stereo separation, 52 dB at 1 kHz; THD, 0.1%, stereo, 0.05% mono. The *model STA-2100* measures 6  $\frac{1}{2}$   $\times$  20  $\frac{1}{2}$   $\times$  16  $\frac{1}{2}$  inches, and sells for \$599.95.—**Radio Shack**, 1400 One Tandy Center, Fort Worth, TX 76102.

**DIRECT-CONTROL TURNTABLES**, *Project 7 models AF977 and AF967*, are belt driven and use a phase-locked loop to control turntable speed. Selectable speeds are 33  $\frac{1}{3}$  RPM and 45 RPM. Speed variation is specified to be within  $\pm 0.002\%$ . The *model AF977* (shown) is an automatic single-play turntable with digital speed readout, and the *model AF967* is a semi-automat-



CIRCLE 133 ON FREE INFORMATION CARD

ic unit. Wow-and-flutter in both turntables is 0.02% WRMS. Suggested retail prices: *model AF977*, \$399; *model AF967*, \$349.—**Phillips High Fidelity Labs, Ltd.**, Box 2208, Fort Wayne, IN 46801.

**FM TUNER PREAMPLIFIER**, *model Beta III*, uses FET's in all its stages to provide low noise and low distortion. The first stage of the equalization amplifier section uses a single-cascade dual-FET input stage and the last stage uses a 3-parallel, regulated current load source follower. The tone-control amplifier uses attenuators in the I/O stages for lowest S/N ratio.

Specifications include: For phono 1 and 2: frequency response, 30 Hz—15 kHz  $\pm 0.2$  dB; input sensitivity, 2.0 mV; input impedance,



CIRCLE 134 ON FREE INFORMATION CARD


22,000, 47,000 and 100,000 ohms; S/N ratio, 81 dB (at input reference level of 2 mV); and THD, less than 0.004%. The unit is rack-mountable and comes with matte black front panel. The *model Beta III* measures 19  $\times$  2  $\frac{1}{2}$   $\times$  13 inches and weighs 13 lbs. \$399.—**Nikko Audio**, 16270 Raymer St., Van Nuys, CA 91406. R-E


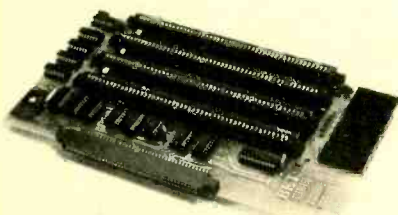
# computer products

More information on computer products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.

**INTERFACE/MOTHERBOARD, Betsi**, comes as a kit or assembled. Attaches to any PET computer to provide, on a single board, both interface and S-100 motherboard with four slots. Unit allows most S-100 compatible boards to be plug-compatible with PET. The board features a dynamic memory controller that allows use of Expandoram board for expansion to 32K of



## CIRCLE 121 ON FREE INFORMATION CARD

memory, plus sockets and address decoding for 8K of PROM (Intel 2716).

Kit includes single-sided board, owner's manual, plus all components and one 100-pin connector. Assembled, the *Betsi* comes with four 100-pin connectors and manual. Price: kit, \$119; assembled, \$165.—**Forethought Products, P.O.** Box 8066, Coburg, OR 97401.

**LOGIC ANALYZER KIT, model LTC-2**, contains three high-speed (10-ns) digital troubleshooting tools—the *model LP-3* logic probe, the *model DP-1* digital pulser and the *model DM-1* logic monitor. The *model LP-3* probe features 0.5-megohm input impedance, switch-selectable TTL/DTL and CMOS/HTL thresholds, LED indicators, built-in pulse stretcher and memory switch. The *model DP-1* provides single-pulse or



## CIRCLE 122 ON FREE INFORMATION CARD

100-hz-pulse operation and a TTL/CMOS mode switch. The *model LM-1* monitor clips onto standard 14- or 16-pin DIP IC's; LED's show pin state.

Accessories include probe tips, adapters, ground leads, operator's manuals and guides—all housed in rugged plastic case. Suggested retail price: \$235.05.—**Continental Specialties Corp.**, 70 Fulton Terrace, New Haven, CT 06509.

**DATA ACQUISITION/PROCESS CONTROL SYSTEM, Real World Interface System** (available as kit or assembled) is designed for use with both mini- and microcomputers, with typical applications in environmental control, robotics and automated assembly-line testing. The system cabinet contains a power supply, card cage and motherboard for up to 12 plug-in modules, including A/D



## CIRCLE 123 ON FREE INFORMATION CARD

and D/A converters and a computer interface card. Plug-in modules contain from 8 to 32 I/O channels (the *Current Probe* has 4 I/O channels). Plug-in module price range: kits, \$65—\$125; assembled, \$79.50—\$150. Cabinet with power supply, motherboard and parallel CPU interface, \$299 for the kit; \$360, assembled.—**General Computer Technology**, 400 S. Lipan, Denver, CO 80223.

**DISC SOFTWARE, model SL80-10F** text editing system, *model SL80-11F* text processing system and *model SL80-12F* mnemonic assembler, are designed for the 8080 microcomputer and operate under the CP/M disc operating system. The text editor features block move and copy, tabs, overlays, append and restrictive column searches. The text processor provides over 50 commands covering pagination, margin/indent settings, spacing, titling, centering and justification. New instructions can be implemented with conditional commands, number registers, terminal prompts and a loop command. A separate data file can be read for information required by the text file. The mnemonic assembler supports standard pseudo op-codes, plus paging, titling, hex or octal listings, line numbers, etc. All programs include user's manual, source listing and an 8-inch disc. Prices: *model SL80-10F* editor, \$40; *model SL80-11F* processor, \$50; *model SL80-12F* assembler, \$40.—**Technical Systems Consultants, Inc.**, P.O. Box 2574, West Lafayette, IN 47906.

## CIRCLE 124 ON FREE INFORMATION CARD

# Three supplies in one the auto-tracking B&K-PRECISION 1650



## Model 1650 \$275

- Functions as three separate power supplies
- 5V DC, 5A fixed output
- Two separate (A and B) 0 to 25VDC outputs at 0.5A
- B supply can be set to track A supply directly or in any ratio from 0 to 100%
- All terminals are fully isolated in all modes
- Outputs may be connected in series or parallel
- Fully automatic, current limited overload protection

The B&K-PRECISION 1650 was designed to fill your bench power needs for both linear and digital circuitry. The exclusive opto-isolator controlled automatic tracking circuit allows the B output to precisely track voltage changes of the A supply, while maintaining complete electrical isolation.

Available for immediate delivery at your local B&K-PRECISION distributor.

**BK PRECISION**  
**DYNASCAN**  
**CORPORATION**

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics Ontario  
Int'l. Sys. Empire Exp., 270 Newtown Rd., Plainville, L.I. NY 11803

## CIRCLE 57 ON FREE INFORMATION CARD



# communications products

More information on communications products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.

**MOBILE CB TRANSCEIVERS**, the *McKinley*, *Thomas J.*, and *Andrew J.*, all provide a 4-watt AM power output (the *McKinley* has a 12-watt



CIRCLE 111 ON FREE INFORMATION CARD

SSB output) and -60 dB spurious rejection. Both the *Thomas J.* and *Andrew J.* transceivers have 100% modulation. The *McKinley* unit (shown) features standard controls plus a clarifier. The *Thomas J.* unit has standard controls, plus a

Channel 9 priority switch and an SWR meter. The *Andrew J.* unit contains a combination transmit/receive light and variable RF gain control. Prices: the *McKinley*, \$269.95; the *Thomas J.*, \$159.95; the *Andrew J.*, \$119.95.—**President Electronics, Inc.**, 16691 Hale Ave., Irvine, CA 92714.

**MORSE CODE COPIER**, model *DE-150*, is designed to operate with communications receivers and transceivers and features a built-in 100-Hz bandpass filter with 800-Hz center frequency. Other features include an 8-character 5 × 7 dot



CIRCLE 112 ON FREE INFORMATION CARD

matrix LED display and 50- to 60-word-per-minute copying capability. Comes with built-in 115-VAC power supply, patch cord and output monitor jack and measures 2 × 10 × 4 inches. Suggested retail price: \$425.—**Dynamic Electronics, Inc.**, Box 896, Hartselle, AL 35640.

**MARINE TRANSCEIVER**, model *T1 2100*, is a fully synthesized solid-state VHF/FM unit with programmable scan feature that enables simulta-



CIRCLE 113 ON FREE INFORMATION CARD

neous channel monitoring. The unit also provides 55-channel transmit and 76-channel receive capabilities (includes 4 weather stations) and operates on all USA and international channels. Keyboard automatically selects simplex, duplex, 1-

## THIS VISE IS CATCHING.

Catch PanaVise. It tilts, turns and rotates your work exactly where you want. Add our new Tray! It catches small parts you drop, separates tools, and keeps parts sorted. The Tray's wide 8 1/4" diameter of cast metal gives 'no-tip' stability, and has 6 slip resistant neoprene feet. Catch all the PanaVise combinations at your distributors now. Write for FREE brochure and distributor list.

**PANA VISE®**

Dept. CE 11  
2850 29th St.  
Long Beach, CA 90806

Shown:  
#315 Circuit Board  
Holder, #300  
Base, #312  
Tray Base Mount.



CIRCLE 38 ON FREE INFORMATION CARD

## 9 reasons why the real pros prefer Endeco desoldering irons

1. Operates at 120v, 40w. Idles at 20w for longer tip life
2. Flexible, burn resistant Neoprene cord set
3. Cool, unbreakable polycarbonate handle
4. Exclusive bracket insures alignment, prevents damage
5. Safety light in handle tells when it's on
6. Stainless steel construction
7. Temperature control, Low, high or off.
8. Eight tip sizes. Comes with .063 I.D.
9. Converts to soldering iron with 1/4" shank type tip

See your distributor or write . . .

**Enterprise Development Corp.**

5127 E. 65th St. • Indianapolis IN 46220  
PHONE (317) 251-1231

CIRCLE 53 ON FREE INFORMATION CARD



watt or receive-only operation. Other features include high-visibility displays, squelch and remote control. Suggested retail price: \$795.—**Texas Instruments, Inc.**, P.O. Box 226080, Dallas TX 75266.

**AM/FM CUSTOM ANTENNAS**, models KL-16F, NL-15-B, PM-95H, PM-21D, PM-30, PM-58, is a complete line of OEM-styled customized antennas for imported autos. The antennas are in-



**CIRCLE 114 ON FREE INFORMATION CARD**

tended for BMW, Datsun, Fiat, Mazda, Saab, Honda, Subaru, Toyota and VW. All models (model PM-95H designed for the Honda Accord is shown) feature stainless steel masts, shielded bodies and cables, and heavy chrome-plated hardware. Suggested retail price range: \$5-\$7.50.—**Harada Industry of America, Dept. P**, 145 E. Albertoni St., CA 90746. **R-E**

## Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through HOME STUDY

### Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.T. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. (We are located at 2500 S. LaCienega Bl., Los Angeles, Calif.) Write to our mailing address shown below for Bulletin R-79.

**Grantham College of Engineering**  
P. O. Box 35499  
Los Angeles, California 90035

Worldwide Career Training thru Home Study  
**CIRCLE 36 ON FREE INFORMATION CARD**

## Build The World's Most Powerful 8-Bit Computer

### Featuring The Famous Intel 8085!

## Explorer/85™

Starting for just \$129.95 you can now build yourself a sophisticated, state-of-the-art computer that can be expanded to a level suitable for industrial, business and commercial use. You learn as you go... in small, easy-to-understand, inexpensive levels!

- Features Intel 8085 cpu/100% compatible with 8080A software!
- Onboard S-100 bus (up to 6 slots)!
- Onboard RAM and ROM expansion!
- Built-in deluxe 2K Monitor/Operating ROM!
- Cassette/RS 232 or 20 ma J4-1/2 8-bit parallel I/O and timer all on beginner's Level "A" system!

EXPLORER/85 gives you "big computer" features immediately, without turning you into an appliance operator, doomed to run pre-developed software for life. Simply connect EXPLORER to a terminal, video monitor or TV set and 8 volt power supply and start running programs, the very first night! Level "A" teaches you machine language and computer fundamentals. It lets you run exercise programs including programs to examine the cpu registers, examine memory, move memory and make up games. You can load and play back these programs on an ordinary tape cassette—and display your efforts on any TV screen, video monitor or printer. (\$8.95 RF modulator required for TV use.) The simplified architecture of the Intel 8085 makes EXPLORER far easier to understand than computers using the older, more complex but less powerful 8080A. Then when you're ready, EXPLORER can be expanded—by you—to rival the power of any 8-bit computer on earth. Or you can customize it to perform a dedicated task, thanks to onboard prototyping, RAM and ROM expansion capabilities.

#### LEVEL "A" SPECIFICATIONS

EXPLORER's Level "A" system features an advanced Intel 8085 cpu, which is 50% faster than its 8080A predecessor, yet 100% compatible with 8080A software which, you'll discover, exists by the ton. "Big computer" features include an 8355 ROM with 2K deluxe monitor/operating system which has two programmable 8-bit bi-directional parallel I/O ports, built-in cassette interface with tape control circuitry to allow labeling cassette files, and commands which include "display contents of memory," "run at user location (go to)," "insert data," "move contents of memory," "examine registers individually or all," "fill command (to fill the contents of memory with any variable), automatic baud rate selection, programmable characters per line display output format, and more! An 8155 RAM—I/O chip contains 256 bytes of RAM, two programmable 8-bit bi-directional and one programmable 6-bit bi-directional I/O ports plus programmable 14-bit binary counter/timer, user interrupt and reset switches. Onboard expansion provisions exist for up to six S-100 boards, 4K of RAM and 8K of ROM, PROM or EPROM.

**Netronics R&D Ltd., Dept RE-8, 333 Litchfield Road, New Milford, CT 06676**

- |   |   |
|---|---|
| <input type="checkbox"/> Level "A" EXPLORER/85 kit (specify <input type="checkbox"/> terminal or <input type="checkbox"/> hex keypad input). \$129.95 plus \$3 p&h. | <input type="checkbox"/> Deluxe Steel Cabinet for EXPLORER/85. \$39.95 plus \$3 p&h.                |
| <input type="checkbox"/> Power Supply kit. 5 amp ±8 volt. \$34.95 plus \$2 p&h.   | <input type="checkbox"/> Deluxe Steel Cabinet for Keyboard/Video Terminal. \$19.95 plus \$2.50 p&h. |
| <input type="checkbox"/> Intel 8085 User's Manual. \$7.50 ppd.  | <input type="checkbox"/> RF Modulator kit. \$8.95 ppd.  |
| <input type="checkbox"/> ASCII Keyboard/Video Terminal kit. \$149.95 plus \$3 p&h.  | <input type="checkbox"/> Total Enclosed (Conn. res. add tax) \$_____                                |
| <input type="checkbox"/> Hex Keypad kit for hex version. \$69.95 plus \$2 p&h.  | Account # _____   |
| <input type="checkbox"/> Level "B" S-100/Onboard RAM/ROM Decoder kit (less S-100 connectors). \$49.95 plus \$2 p&h.   | <b>PHONE ORDERS CALL (203) 354-9375</b>   |
| <input type="checkbox"/> Level "C" S-100 5-Card Expander kit (less connectors). \$39.95 plus \$2 p&h.   | Print Name _____  |
| <input type="checkbox"/> S-100 Bus Connectors (gold). \$4.85 each.  | Address _____   |
| <input type="checkbox"/> Level "D" 4K Onboard RAM kit. \$69.95 plus \$2 p&h.  | City _____  |
|   | State _____ Zip _____   |

**CIRCLE 44 ON FREE INFORMATION CARD**

## PTS...the NEW name you need to know for semiconductors!

Transistors...SCRs...  
ICs...diodes...rectifiers...  
zeners...the same components we use for our module and tuner rebuilding. A high quality line of profit-builders for the servicing technician/dealer! Ask for a complete price list at any PTS tuner/module servicer.



**PTS ELECTRONICS, INC.**  
The Only Name You Need To Know

**CIRCLE 23 ON FREE INFORMATION CARD**



# FREE

## CATALOG

Audio—Computers  
Instruments  
Kits & Assembled

COMPUTER  
PRODUCTS  
CATALOGUE



Southwest Technical Products Corporation  
219 W. RHAPSODY  
SAN ANTONIO, TEXAS 78216

CIRCLE 55 ON FREE INFORMATION CARD

## Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

**WERSI**



Wersi Electronics, Inc.  
Dept. 42,  
1720 Hempstead Road  
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 28 ON FREE INFORMATION CARD

## AC OUTLET CHECKER

continued from page 53

ance only if the outlet box itself is grounded.

What happens all too often is that the adapter gives the user a false sense of

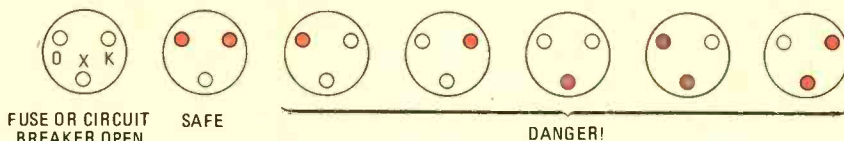


FIG. 2—HOW THE LIGHTS INDICATE different conditions. Indications are same as in Table 1.

security and he tends to forget the safety precautions he once observed. Unwittingly, he has created a system that can potentially be even more dangerous than the original.

How then do you know when the system is safe? It's simple; just hook the adapter up as it will be used, then plug the Outlet Polarity Checker into it. If the adapter checks out OK, all is well and it can be used with confidence. If not, the best remedy is to rewire the outlet to the proper 3-wire configuration. Figure 2 shows the various combinations of lights.

The same method can be used to check that the neutral (white) wire in a 2-wire system is grounded. Connect the green lead of the adapter to a known ground and then test it. If it checks out OK, then the ground is grounded. If not, you will get a "no ground" indication.

The Outlet Polarity Checker is a one-evening project. In most cases it can be made entirely from junk-box parts. For DS1, DS2 and DS3 you can use neon lamp assemblies with built-in current-limiting resistors. It is recommended that DS1 ("O") and DS3 ("K") have amber or clear lenses, and that DS2 ("X") have a red lens. The plug and cable can be cut from any 3-wire polarized (grounding) cord. The completed checker is housed in a small Bakelite case. You can use transfer lettering to label the panel for a professional appearance. **R-E**

**Make America smarter.  
Give to the college of your choice.**

# YOU DESERVE IT!

## GET IT EVERY MONTH!



Come on, treat yourself—and save money, too. Subscribe to Radio-Electronics today, and make sure you get all of the most interesting, most exciting and authoritative electronics reporting in any magazine, month after month. Don't miss a single one of the upcoming issues jam-packed with new-equipment test reports, projects to build, servicing ideas, and news of solid state, computers, hi-fi, hobbies and everything electronic. Save money, too—as much as \$11 off the newsstand price when you subscribe to Radio-Electronics. Come on, you deserve it—check off the money-saving offer you prefer on the handy coupon, and start enjoying Radio-Electronics every month.

Mail to: **Radio-Electronics**  
SUBSCRIPTION DEPT., P.O. BOX 2520 BOULDER, COLO. 80322

Name (Please print) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip Code \_\_\_\_\_

Indicate the offer you prefer:

☐ 1 Year—12 issues ONLY \$9.98  
(You save \$5.02 off newsstand price.)

☐ Payment enclosed (send one extra issue)

☐ Bill me

☐ 2 Years—24 issues ONLY \$19.00  
(Save More! \$11.00 off newsstand price.)

☐ Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

40H9



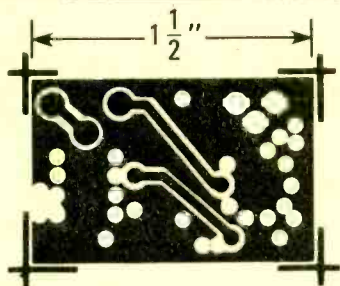


FIG. 8—TOP SIDE of the board for the true-RMS converter.

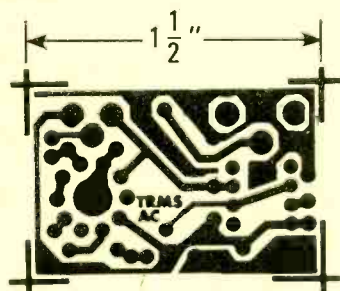


FIG. 9—PATTERN for the bottom side of the TRMS converter board.

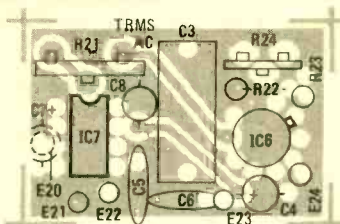


FIG. 10—HOW PARTS ARE POSITIONED on the TRMS converter board.

ment and check all solder connections for cold joints and possible bridges. Plug in the instrument, apply power and check for +5V, -5V and -8 volts at the output pins of the three voltage regulators.

If the correct supply voltages are obtained, then remove power from the instrument and install all remaining IC's in their sockets taking care to observe proper pin orientation.

### Calibration

Table 2 shows the calibration sequence for the multimeter. The ADC voltage reference is calibrated by allowing the meter to read a known voltage between 1 and 2 volts and adjusting R9 until the known value is obtained. (Use the 2-volt range.) The known voltage can be from a voltage reference source or a standard cell, or a stable voltage calibrated by another digital voltmeter or a fresh mercury cell (1.35 volts). The temperature references must be calibrated by another voltmeter, measuring between the test point indicated in Table 2 and the -5-volt supply. Known resistors are supplied with the kit of parts (see parts list) to calibrate the resistance ranges.

There are two adjustments for the AC converter calibration. Trimmer R24 is

continued on page 80

For  
faster  
service

USE  
ZIP  
CODE

on  
all  
mail

THE GOVERNMENT  
CAN DO EVERYTHING  
THE UNITED WAY DOES.  
ONLY THEY  
WRAP IT UP FOR YOU  
IN NICE RED RIBBON.  
MILES AND MILES OF IT.



One of the best things about United Way is not what it does, but what it *doesn't* do. For instance, because United Way is run almost entirely by volunteers, it is able to return an amazing 89% of every dollar to people who need it. That means less than 11% goes for administrative costs. So it doesn't waste your money. And because United Way is re-created each year with a combination of old and new volunteers, it doesn't become over encumbered with huge staffs of people who might actually get in the way of progress. So it doesn't strangle you in red tape. All of which means that because of what United Way *doesn't* do, it can do a much better job at what it *does* do. Helping people.



Thanks to you it works for all of us.

A Public Service of The Waynes & The Marketing Company

# MEET THE PRO:



The personal computer keyboard with industrial quality and features. From the PROfessionals who know keyboards best... (CHERRY)

Versatile. Reliable. Ideal for personal computer and small business applications. Modifiable to add total obsolescence protection. Versatile, expandable to grow as your system grows.

These unique standard features: • Complete and ready to use...with full customizing instructions. • Easily modified by hard wiring. • Full 67 key array. • Five user-definable spare keys with keycaps that have "quick change" clear plastic tops. • Only one power supply voltage required: +5 volts at 325 ma. max. • TTL and DTL compatible output circuitry. • Positive logic with outputs resting low. • Four modes: Lower case, upper case, control case and teletype-writer alpha lock configuration. • Piggyback a "daughter" board instantly. • Standard 22-pin dual card connector on .156" center.

PLUS: These on-the-spot customizing special features (fully explained in 8 page brochure PRO-977-2 containing specifications and instructions):

• Negative logic • Tri state—positive logic • High voltage output—CMOS compatible • Non encoded outputs • Encoded outputs • Flexible key assignments • Automatic repeat • and MORE.

## BUY THE PRO:

Special introductory price: \$115.00 postpaid

A full \$20 discount off the usual \$135 price if you order now.

MAIL TODAY...AND SAVE

☐ Ship me \_\_\_\_\_ Cherry PRO keyboards at \$115.00 each, postpaid. Total enclosed: \$\_\_\_\_\_ (check or money order). Illinois residents add 5% Sales Tax.

☐ Charge to my Master Charge

Card Number \_\_\_\_\_

Expiration date \_\_\_\_\_

Signature \_\_\_\_\_

☐ I'd like more information. Please mail 8 page brochure PRO-977-2.

Please type or print clearly.

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

# CHERRY


CHERRY ELECTRICAL PRODUCTS CORP.

3600 Sunset Avenue, Waukegan, IL 60085

Dealer inquiries invited.

# HEAR YE! HEAR YE!

## AMELECT CHIMES

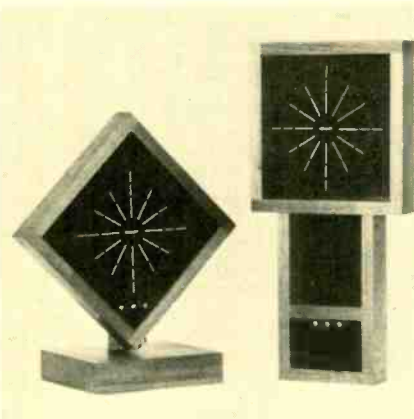

AMELECT Clock Models CL7401A and CL7402 are available with complete sound.

### FEATURING:

1. A realistic tic-toc sound: hear the seconds go by.
2. Beautiful, modified Westminster chimes have synthesized sounds composed of six frequencies. Four notes are provided on the quarter hour, eight notes on the half hour, twelve notes on the three quarter hour, and sixteen notes on the hour.
3. Following on the hour chimes, the hour displayed on the clock is counted out using the lowest chime note.
4. Chime volume, tic-toc volume, pitch and decay are adjustable.

Available assembled or in kit form. Can easily be added to any Amelect Clock.

	Silent Models		
	Kit	Assembled	With Base
CH 7401A	\$55.00	\$75.00	\$85.00
CL 7402	\$71.50	\$95.00	

	Chimes Models		
CL 7401A	\$94.00	\$114.00	
CL 7402	\$110.50	\$140.00	(3)

Indiana residents include 4% sales tax.  
Shipping and Handling \$3.50  
To order write or call 1-219-297-3320

## AMELECT

INCORPORATED

P.O. Box 367—106 S. Newton St.  
GOODLAND, INDIANA 47948

Allow 3-4 weeks for Del.

CIRCLE 62 ON FREE INFORMATION CARD

### PRECISION DMM

continued from page 79

TABLE 2—MULTIMETER CALIBRATION SEQUENCE

Step No.	Calibrate	Pot No.	Switches	Display
1	ADC Reference	R9	S5, S7	Known input voltage between 1 and 2 volts DC or 1.35 volts from a fresh mercury battery cell.
2	Celsius Reference	R36	S2	2.732 volts measured from arm of R36 to —5-volt supply using an external voltmeter.
3	Fahrenheit Reference	R33	S3	4.594 volts measured from arm of R33 to —5-volt supply using an external voltmeter.
4	Celsius Range	R29	S2	.0000° (ice water bath) 100.00° (boiling water)
5	Fahrenheit Range	R31	S3	Adjust R31 to equal Celsius range using conversion equation.*
6	2000-ohm Range	R15	S4, S7	Adjust to equal known resistance.
7	20,000-ohm Range	R14	S4, S8	Adjust to equal known resistance.
8	200,000-ohm Range	R13	S4, S9	Adjust to equal known resistance.
9	2-megohm Range	R12	S4, S11	Adjust to equal known resistance.
10	20-megohm Range	R10	S4, S11	Adjust to equal known resistance.
11	AC Offset	R24	S5, S6, S7	0.0000V with input shorted or with pins 2 and 4 of IC6 shorted.
12	AC Calibration	R25	S5, S6, S7	Adjust to equal known AC input voltage (RMS value, not peak).

\* °C = 5/9 (°F - 32)

°F = (9/5 × °C) + 32

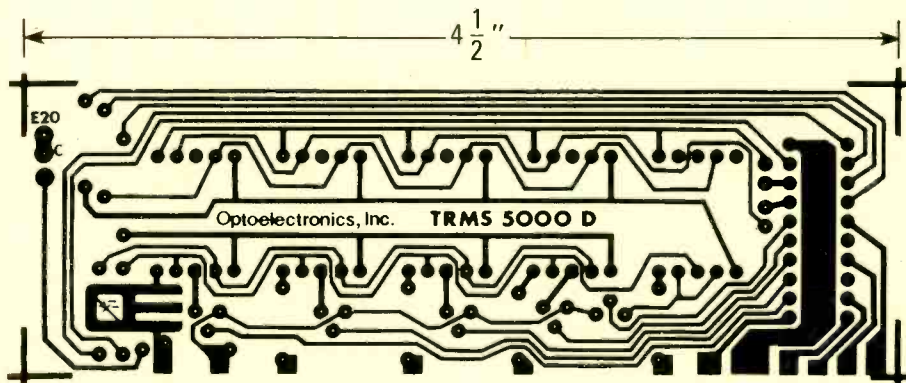


FIG. 11—FULL-SIZE PATTERN for the display board. All components are mounted on the front surface.

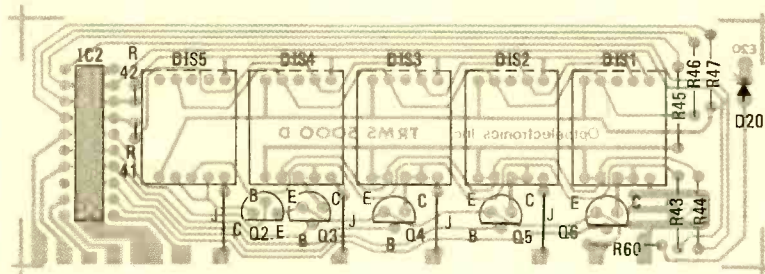


FIG. 12—DISPLAY BOARD parts placement. The IC is the display segment driver. The transistors are used in digit multiplexing.

the offset or zero trim, which is adjusted with the input shorted. There is a possibility of significant noise pickup due to the high input impedance of buffer IC7, so it may be necessary to short the input pin to IC6 by shorting pin 4 to pin 2 while

adjusting the offset to zero. Trimmer R25 is used to fine adjust the AC calibration with a known RMS value AC voltage applied to the input. If a calibrated AC voltage is not available, the pot should be centered for accuracy.

R-E



# books

**UNDERSTANDING DIGITAL ELECTRONICS**, Texas Instruments Learning Center. Texas Instruments, Inc., Box 3640, M.S. 84, Dallas, TX 75285. 265 pp. 5 1/4 x 8 1/4 in. Softcover \$3.95.

Finding out how digital electronics work by using a handheld calculator is the goal of this book, and a step-by-step approach explains circuits, from the most basic to the very sophisticated. Because it is really a self-teaching course, the book should be read chapter by chapter; self quizzes are provided at the end of each chapter (with the answers in the back of the book); and a glossary of special terms and a bibliography are also provided.

**THE INCREDIBLE SECRET MONEY MACHINE**, by Don Lancaster. Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, IN 46268. 159 pp. 5 1/4 x 8 1/4 in. Softcover \$5.95.

This is not a "get-rich-quick" book, but rather a "cookbook" and guide on how to turn your own full-time small-scale computer, technical or craft business into a successful enterprise. Written in tongue-in-cheek yet down-to-earth style, the book contains helpful hints on how to reduce your taxes, not pay a utility bill, get totally free insurance, and many other necessary adjuncts to running a successful "secret money machine."

**HOW TO BUILD YOUR OWN STEREO SPEAKERS: CONSTRUCTION, APPLICATIONS, CIRCUITS AND CHARACTERISTICS**, by Christopher Robin. Reston Publishing Co., Div. of Prentice-Hall Co., Reston, VA 22090. 193 pp. 6 1/4 x 9 1/4 in. Hardcover \$15.95.

The title of this book says it all—it is a "how-to" guide for hobbyists and professional engineers who want simple step-by-stop instructions on constructing a state-of-the-art speaker enclosure. The book also includes data on acoustics, planning and designing speaker crossover networks, and basic woodworking. Dimensional drawings and photographs accompany the text; and the back of the book contains several appendixes and a complete glossary of terms.

**TAPED EDITING**, by Joel Tall. Elpa Marketing Industries, Inc., Thorens & Atlantic Aves., New Hyde Park, NY 11040. 32 pp. 5 1/4 x 8 1/4 in. Softcover \$2.

This little book explains in detail all the ins and outs of audio and video tape splicing. It also gives you helpful tape editing hints such as how to run the tape backward in order to recognize speech sounds. Other chapter topics deal with splicing and editing procedures, speech characteristics and how to work within the limits of hearing sensitivity.

**BASIC FOR HOME COMPUTERS**, by Bob Albrecht, LeRoy Finkel and Gerald R. Brown. John Wiley & Sons, Inc., 605 Third Ave., New York, NY 10016. 336 pp. 6 1/4 x 10 in. Softcover \$5.95.

This book is a self-instruction course in the BASIC programming language for home computer applications; it does not require access to an actual computer. The version of BASIC used is *Microsoft BASIC* developed for the Altair MITS. Some of the topics covered are assigned statements, stored programs and branching; subscripted variables, double subscripts; string variables and functions; and subroutines. Each chapter contains a self-test section, and there is a final self-test in the back, together with appendixes containing lists of computing periodicals, BASIC functions and ASCII character codes.

**S S I MICROCOMPUTER SOFTWARE GUIDE**. S S I Publications, 4327 East Grove St., Phoenix, AZ 85040. 140 pp. 5 1/4 x 8 1/4 in. Softcover \$7.95 (also available on mini-floppy disc).

This book is a must for anyone planning a microcomputer system for business, home or education applications. It consists of a listing of over 2200 software programs, alphabetically arranged from ASCII (codes, displays, etc.) to Zip Code (mail-code sorting & printing). The 236 classifications are drawn from discs, cassettes, books, paper tapes, listings, pamphlets and magazines; and the back of the book contains a list of 130 microcomputer software sources and addresses.

**BUGBOOK VIII, 8080/8085 SOFTWARE DESIGN WITH 190 SOFTWARE SOLUTIONS**, by Christopher A. Titus. E&L Instruments, Inc., 61 First St., Derby, CT 06418. 288 pp. 6 x 9 in. Softcover \$9.


This detailed treatment of assembly language programming for 8080- and 8085-based computers contains many elementary and advanced instructions. It analyzes and discusses programming techniques for mathematical routines, number system conversions, command decoders, arrays and tables, interrupt programming, etc. Many complete and tested programs in standard mnemonics are included. **R-E**

# Nobody does it better than VIZ

ISOTAP® Isolation Transformers
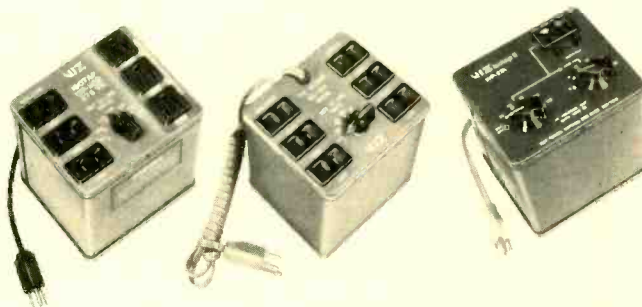
## MINIMIZE SHOCK HAZARDS

Here's new safety for service technicians. Protection for test instruments. ISOTAP provides AC output voltages isolated from AC power lines. You need an ISOTAP for servicing any transformerless equipment. Absolutely necessary for today's solid state TVs and stereos. Essential for safe servicing in the industrial plant, laboratory or technician training school.



### WP-25A

275 VA isolated, 500 VA direct. Outputs at 105, 115 and 130 V. \$49

### WP-26A

400 VA isolated, 500 VA direct. Outputs at 105, 115 and 130 V. \$58

### WP-27A ISOTAP II

400 VA isolated only. Outputs 25 to 150 Vac in 5V steps. \$68



## NEW Porta-Isotap WP-28 \$44.95

Compact, lightweight unit. Ideal for TV servicing. Easily carried for house calls. Has two fused outlets: (1) Isolated, 150 VA continuous for solid state TV; (2) Direct, 500 VA, a convenient power source for service instruments. Comes with accessory cords to take power from TV set back. No need to hunt for wall outlet. Weight 8 lb. Dimensions 3 3/4 x 3 3/8 x 5 3/8 in.

See your local VIZ distributor.

## VIZ Test Instruments Group

335 E. Price St., Philadelphia, PA 19144  
The VoltOhmyst company

# market center

**CLASSIFIED COMMERCIAL RATE** (for firms or individuals offering commercial products or services). \$1.50 per word (no charge for zip code) . . . minimum 15 words.

**NONCOMMERCIAL RATE** (for individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

**ONLY FIRST WORD AND NAME** set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

## FOR SALE

**FREE** catalog (anglais). IC's, semi's. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada, H3C 1H8. US inquiries.

**RADIO & TV** tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, Calif. 92105

**TEST** equipment catalog listing used Tektronix, HP and GR equipment at bargain prices. Price \$1.00 refundable with first order. **PTI**, Box 8699, White Bear Lake, MN 55110

**NAME** brand test equipment. Guaranteed discounts up to 50%. Free catalog. **SALEN ELECTRONICS**, Box 82-M, Skokie, IL 60077

**PRINTED-circuit boards**, reasonable. Also, artwork, prototypes, designs, fabrication and testing. **MICROCON INC.**, Box 43, Glenview, IL 60025

**RCA**, Zenith original TV parts. Dealer prices, fast service. Send part and model numbers. **LI. ELECTRONICS**, 981 Sunrise Hwy., Bayshore, NY 11706, 516-666-7360

**TEKTRONIX** 5440 Opt. 1 60-MHz scope, 5A48, 5B42 \$1750. Tektronix DM501 with temp. and probes, TM504 mainframe, 2 blank plug-ins, flexible extender cable \$550. H-P 5326A systems counter \$550. Wavetek 142 function generator \$400. All excellent with manuals. Call **518-489-4946** after 6 P.M. Eastern Time.

**VIDEO** recorders, cameras, blank tapes, prerecorded movies at low discount prices. **MIDWEST VIDEO**, Box 3233, Dayton, OH 45431, 513-227-7609

**NEW. Meter solid-state isolated relay.** Control 5 millivolts 5 microamperes 1000 ohms DC. Lead circuit 3 amperes 125 VAC. Write today for facts. **EGYD ELECTRONICS**, Box 92, Huntingdon Valley, PA 19006

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

**Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003**

### ORDER FORM

**PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.**

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( )

**Special Category: \$10**

**(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

## Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

**New ITEMS . . . New BARGAINS!**

**FREE UPON REQUEST!**

Send today for FREE copy of  
NEW CATALOG WS-79. Address Dept. RE

**FAIR RADIO SALES**

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

**SENSITIVE** converter 1.7-2.4 GHz \$99.95 postpaid. Details for stamp. **GW ELECTRONICS**, POB 688, Greenwood, IN 46142

**PARTS** priced to sell—bought at bankruptcy. All new parts. Guaranteed satisfaction. Send two 15¢ stamps for list. **MARCRUM**, 513 Pontiac Ct., Madison, TN 37115 (615) 865-7078

**SAM'S** photofacts original folders numbers 1 to 568 order your needs, will confirm. **RINEHART**, 241 South West 2nd Street, Richmond, IN 47374

**RECORDSAVER**, poly-lined inner sleeves, ten cents each, postpaid, minimum 100. **DEO INC.**, Box 452J, Glenview, IL 60025

## Burglar • Fire • Smoke Alarm Catalog

• Billions of dollars lost annually due to lack of protective warning alarms.

**FREE CATALOG** Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.



**Burdex Security Co.**

Box 82802 RE-089 Lincoln, Ne. 68501



### BIG SCREEN OSCILLOSCOPE

Converted from ANY Size TV Set...

Hams, Technicians, Hobbyists, Broadcasters: Minor, inexpensive changes convert TV set to super-sensitive testing device. No electronic experience needed. Follow clear cut plans. Fully illustrated. Use in workshop, lab, school, etc. Any size screen . . . Any size TV set . . .

**Complete Set of Plans . . . \$4.**

(INCL. 50¢ FOR POST & HANDLING)

**MILLCO IND.**, DEPT. OP-03, BOX 91, KOSSE, TX 76653

## PASS FCC EXAMS

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second class Radiotelephone licenses. Newly revised multiple-choice exams cover all areas tested on the actual FCC exam. Plus "Self-Study" Ability Test. Proven! \$9.95 postpaid. Moneyback Guarantee.



**COMMAND PRODUCTIONS**

Radio Engineering Division

P.O. Box 26348 • E

San Francisco, CA 94126



AVAILABLE NOW!

ONLY \$3.95  
Add \$1.00 for shipping  
JAPANESE TRANSISTOR SUBSTITUTION MANUAL



An invaluable Japanese to Japanese substitution guide for approximately 3000 transistors.

- \* Covers the 2SA, 2SD, 2SC and 2SD series.
- \* Introduction includes a guide to understanding Japanese transistors.
- \* A 90 page 8 1/2 by 11 soft cover book.

## PARTS PROCUREMENT PROBLEMS

**FUJI-SVEA Has the Largest Inventory of Original Japanese Parts Anywhere**

**Seeking Original Japanese Replacement Parts for CB, TV and Stereo Repair Use?**

TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9
2SA 473	45	55	60	2SB 346	30	35	40	2SC 693F	20	27	30	2SC 1226A	50	55	60	2SD 234	60	70	80
2SA 483	2.00	2.20	2.50	2SB 367	1.10	1.25	1.40	2SC 696	1.00	1.20	1.30	2SC 1237	1.80	2.00	2.25	2SD 235	60	70	80
2SA 484	1.50	1.75	1.95	2SB 368B	1.80	2.00	2.25	2SC 708	1.30	1.45	1.60	2SC 1239	2.20	2.70	2.90	2SD 261	35	40	45
2SA 485	1.40	1.60	1.80	2SB 379	70	80	90	2SC 710	20	27	30	2SC 1279	50	55	60	2SD 287	2.50	2.70	2.90
2SA 489	1.10	1.25	1.40	2SB 381	30	35	40	2SC 711	20	27	30	2SC 1306	1.30	1.45	1.60	2SD 300	4.50	5.00	5.60
2SA 490	70	80	90	2SB 400	30	35	40	2SC 712	20	27	30	2SC 1307	1.90	2.10	2.40	2SD 313	60	70	80
2SA 493	45	53	59	2SB 405	30	35	40	2SC 715	30	35	40	2SC 1310	20	27	30	2SD 315	60	70	80
2SA 495	30	35	40	2SB 407	80	90	100	2SC 717	35	40	45	2SC 1312	20	27	30	2SD 325	60	70	80
2SA 496	50	64	70	2SB 415	30	35	40	2SC 727	1.00	1.20	1.30	2SC 1313G	20	27	30	2SD 330	60	70	80
2SA 497	1.00	1.20	1.30	2SB 434	80	90	100	2SC 730	3.00	3.20	3.40	2SC 1316	4.20	4.40	4.90	2SD 350	3.80	4.00	4.40
2SA 505	50	64	70	2SC 435	90	110	120	2SC 731	2.50	2.70	2.90	2SC 1317	20	27	30	2SD 380	5.20	5.40	5.95
2SA 509	30	35	40	2SC 440	40	53	59	2SC 732	20	27	30	2SC 1318	35	40	45	2SD 381	85	100	1.10
2SA 525	50	64	70	2SB 449	1.30	1.45	1.60	2SC 733	20	27	30	2SC 1325A	6.50	6.90	7.60	2SD 424	3.80	4.00	4.40
2SA 530	1.50	1.70	1.90	2SB 461	90	110	120	2SC 734	20	27	30	2SC 1327	20	27	30	2SD 425	2.90	3.20	3.40
2SA 537A	1.50	1.70	1.90	2SB 463	90	110	120	2SC 735	20	27	30	2SC 1330	50	55	60	2SD 426	3.10	3.30	3.60
2SA 539	40	45	50	2SB 471	1.10	1.25	1.40	2SC 738	20	27	30	2SC 1335	50	55	60	2SD 427	1.80	2.00	2.25
2SA 545	45	53	59	2SC 472	2.10	2.50	2.80	2SC 756	1.50	1.80	2.00	2SC 1342	45	53	59	2SD 525	90	110	1.10
2SA 561	30	35	40	2SB 473	80	90	100	2SC 756A	1.50	1.80	2.00	2SC 1344	45	53	59	2SD 526	60	70	80
2SA 562	30	35	40	2SB 474	70	80	90	2SC 763	35	40	45	2SC 1358	4.20	4.40	4.90	2SK 19BL	50	55	60
2SA 564A	20	27	30	2SB 481	90	110	120	2SC 772	30	35	40	2SC 1359	30	35	40	3SK 22Y	1.40	1.60	1.80
2SA 565	70	80	90	2SB 492	60	70	80	2SC 773	35	40	45	2SC 1360	50	55	60	3SK 39	90	110	1.20
2SA 566	2.50	2.70	3.00	2SB 507	80	90	100	2SC 774	1.00	1.20	1.30	2SC 1362	35	40	45	3SK 40	90	110	1.20
2SA 568	1.00	1.20	1.30	2SB 509	1.10	1.20	1.30	2SC 775	1.40	1.60	1.80	2SC 1364	35	40	45	3SK 41	90	110	1.20
2SA 607	1.10	1.25	1.40	2SB 511	70	80	90	2SC 776	2.00	2.20	2.50	2SC 1377	3.20	3.40	3.70	3SK 45	1.30	1.45	1.60
2SA 624	70	80	90	2SB 514	70	80	90	2SC 777	3.00	3.25	3.50	2SC 1383	30	35	40	AN 203	1.40	1.60	1.80
2SA 627	3.10	3.30	3.60	2SB 523	70	80	90	2SC 778	2.90	3.20	3.40	2SC 1384	35	40	45	AN 214Q	1.50	1.70	1.90
2SA 628	30	35	40	2SB 526C	70	80	90	2SC 781	1.80	2.10	2.40	2SC 1396	45	53	59	AN 239	4.20	4.40	4.90
2SA 634	40	45	50	2SB 527	90	110	120	2SC 783	2.10	2.50	2.80	2SC 1398	70	80	90	AN 247	2.50	2.70	3.00
2SA 640	30	35	40	2SB 528	70	80	90	2SC 784	30	35	40	2SC 1400	35	40	45	AN 274	1.50	1.75	1.95
2SA 642	30	35	40	2SB 529	70	80	90	2SC 785	35	40	45	2SC 1402	3.00	3.20	3.40	AN 313	3.00	3.20	3.40
2SA 643	30	40	45	2SB 530	3.20	3.40	3.70	2SC 789	80	90	100	2SC 1403	3.20	3.40	3.70	AN 315	1.80	2.00	2.25
2SA 653	1.90	2.10	2.40	2SB 531	1.80	2.00	2.25	2SC 790	80	90	100	2SC 1407	50	55	60	BA 511A	1.80	2.00	2.25
2SA 659	35	40	45	2SB 536	1.00	1.20	1.30	2SC 793	2.00	2.20	2.50	2SC 1419	60	70	80	BA 521	1.90	2.10	2.40
2SA 661	50	64	70	2SB 537	1.00	1.20	1.30	2SC 799	2.00	2.20	2.50	2SC 1444	1.60	1.80	2.00	HA 1151	1.90	2.10	2.40
2SA 663	3.65	3.80	4.20	2SB 538	3.20	3.40	3.70	2SC 828	20	27	30	2SC 1445	2.50	2.70	2.90	HA 1156W	1.60	1.80	2.00
2SA 666	35	40	45	2SB 541	3.20	3.40	3.70	2SC 829	20	27	30	2SC 1447	70	80	90	HA 1306W	2.00	2.20	2.50
2SA 671	80	90	100	2SB 544	3.00	3.00	6.60	2SC 830H	2.50	2.70	3.00	2SC 1448	70	80	90	HA 1339	2.50	2.70	3.00
2SA 672	30	35	40	2SB 556	3.20	3.40	3.70	2SC 838	35	40	45	2SC 1449	60	70	80	HA 1339A	2.50	2.70	3.00
2SA 673	35	40	45	2SB 557	2.10	2.50	2.80	2SC 839	30	35	40	2SC 1451	1.00	1.10	1.20	HA 1342A	2.50	2.70	3.00
2SA 678	35	40	45	2SB 561B	35	40	45	2SC 853	70	80	90	2SC 1454	3.20	3.40	3.70	HA 1366W	2.50	2.70	3.00
2SA 679	4.20	4.40	4.90	2SB 564	40	53	59	2SC 867	3.20	3.40	3.70	2SC 1475	80	90	100	LA 1366WR	2.50	2.70	3.00
2SA 680	4.20	4.40	4.90	2SB 565	1.10	1.40	1.50	2SC 867A	3.20	3.40	3.70	2SC 1509	50	55	60	LA 1380	2.50	2.70	3.00
2SA 682	80	90	100	2SB 595	1.10	1.40	1.50	2SC 870	35	40	45	2SC 1567	60	70	80	LA 4032P	1.80	2.00	2.25
2SA 683	30	35	40	2SB 596	1.10	1.40	1.50	2SC 871	35	40	45	2SC 1567	60	70	80	LA 4051P	1.80	2.00	2.25
2SA 684	35	40	45	2SC 183	40	53	59	2SC 895	4.20	4.40	4.90	2SC 1587A	60	70	80	LA 4400	1.90	2.10	2.40
2SA 685	35	40	45	2SC 184	40	53	59	2SC 897	2.00	2.20	2.50	2SC 1584	6.00	6.30	7.00	LA 4400Y	2.00	2.20	2.50
2SA 695	40	53	59	2SC 281	30	35	40	2SC 898	2.50	2.70	3.00	2SC 1586	6.50	6.90	7.60	LA 4420	2.00	2.20	2.50
2SA 697	40	53	59	2SC 284	80	90	100	2SC 900	20	27	30	2SC 1624	60	70	80	LD 3001	2.00	2.20	2.50
2SA 699A	50	64	70	2SC 284	80	90	100	2SC 927	20	27	30	2SC 1626	60	70	80	M5 1513L	2.00	2.20	2.50
2SA 705	40	53	59	2SC 317	40	53	59	2SC 929	20	27	30	2SC 1628	60	70	80	STK 011	3.80	4.00	4.40
2SA 706	85	100	1.10	2SC 352A	2.00	2.20	2.50	2SC 930	20	27	30	2SC 1647	70	80	90	STK 013	7.60	8.00	8.80
2SA 715	60	70	80	2SC 353A	1.40	1.60	1.80	2SC 941	20	27	30	2SC 1657	3.00	3.20	3.40	STK 015	4.20	4.40	4.90
2SA 719	30	35	40	2SC 367	60	70	80	2SC 943	35	40	45	2SC 1669	90	100	1.10	STK 435	4.50	5.00	5.60
2SA 720	30	35	40	2SC 369	30	35	40	2SC 945	20	27	30	2SC 1674	30	35	40	STK 439	7.90	9.00	9.90
2SA 721	30	35	40	2SC 370	20	27	30	2SC 959	1.00	1.20	1.30	2SC 1675	20	27	30	TA 7045M	2.00	2.20	2.50
2SA 725	30	35	40	2SC 371	30	35	40	2SC 971	70	80	90	2SC 1678	1.10	1.25	1.40	TA 7055P	2.00	2.20	2.50
2SA 726	30	35	40	2SC 372	20	27	30	2SC 982	70	80	90	2SC 1679	3.00	3.20	3.40	TA 7061AP	90	110	1.20
2SA 727	30	35	40	2SC 373	20	27	30	2SC 983	50	64	70	2SC 1681	30	35	40	TA 7062P	1.10	1.25	1.40
2SA 733	20	27	30	2SC 374	30	35	40	2SC 1000	35	40	45	2SC 1682	30	35	40	TA 7203P	2.50	2.70	2.90
2SA 738	40	53	59	2SC 375	30	35	40	2SC 1012	1.20	1.40	1.50	2SC 1684	30	35	40	TA 7204P	2.00	2.20	2.50
2SA 740																			



# SpeakerCuts.

The absolute latest in advanced speaker technology. Wave Aperture™ Drivers, the Patented Nestroic Woofer System, raw speaker components selected for their excellence. Horns, crossovers, subwoofers, woofers, midranges, horn and dome tweeters. Over 30 in all. Build your own speaker system and we'll provide top quality speakers and design information. Send for FREE 48 page color catalog from the largest, most experienced speaker kit manufacturer in the world. **DON'T DELAY. Write today!**



Dept. 8-RE, 735 N. Northlake Way  
Seattle, Washington 98103

## PLANS & KITS

**SCANNER** users—build many useful accessories. Free kit catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

**PRINTED** circuit boards from your sketch or artwork. Affordable prices. Also fun kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

**FREE** schematic. Touchlite electronic switch and dimmer. Send stamp: **TOUCLITE**, Box 161, Plainville, NY 13137

**ALUMINUM** panels 19 X 6 X 1/4. Perfect for rack or custom installations. \$6.50 each. **RJP SALES**, 2360 Rockymont, St. Louis, MO 63136

**CONSTRUCTION** plans for profitable business ideas. Catalog \$1.00. **GARLING**, 438 N. Garfield Street, Lombard, IL 60148

**ELECTRONICS** "Gas" detector plans including IC amplifier. Detects carbon monoxide, propane, natural gas, smoke, etc. Ideal for Home, Vans, Autos, RV's, Boat Bilges or for controlling Vent Fans, Garage Door Openers, etc. \$2.75. **JR INDUSTRIES**, 5834-B Swancreek, Toledo, OH 43614

**NEW** modern design specialties for hobbyists and kit builders never been on US market, featuring professional quality PC boards and components for outstanding performance at economy prices. Write for free catalog. **LORS ASSOCIATES**, Box 518, Berwyn, IL 60402

**CHARGE!** Build your own negative ion generator and save. Plans \$5.00. **LUNATRIX**, P.O. 891, Yucaipa, CA 92399

## GRAPHIC EQUALIZER

**TWELVE** bands/channel \$100 kit still available: See May 1978 cover story. Complete instructions, reprint review \$2.50. Free information. **SYMMETRIC SOUND SYSTEMS**, 1608 South Douglas, Loveland, CO 80537

## EDUCATION & INSTRUCTION

**TELEPHONE** bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

**UNIVERSITY** degrees by mail! Bachelors, Masters, Ph.D's... Free revealing details. **COUNSELING**, Box 317-RE8, Tustin, CA 92680

**UNDERSTAND** digital electronics. Programmed learning courses. Design of Digital Systems, 6 volumes, only \$19.95. Digital Computer Logic, 4 volumes, \$14.95. Both \$29.95. Free details. **GFN INDUSTRIES**, Bldg. 7-20, 203 Loudon Road, Concord, NH 03301

**FORTUNES** made in Real Estate. Book tells secret guidelines. \$3.00 plus 30¢ postage. **DEBLEN'S SPECIALTIES**, Dept. RE8, 2300 W. Pleasant Valley, Parma, OH 44134

**EARN** high school diploma, spare time. College-recognized. Credits given for previous courses, job experience. Low tuition. Exams repeated free. Individual counseling. State registered. **CAMBRIDGE ACADEMY**, Dept. RE-1, 409 E. Osceola, Stuart, FL 33494. Toll-free 1-800-327-8103.

## BUSINESS OPPORTUNITIES

**MECHANICALLY** inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

**LEARN** to repair PLL or crystal synthesis CB for profit, 30 PLL's covered. Send \$12.95 for instruction book. **A.P. SYSTEMS**, PO Box 488, Milford, PA 18337, Dept. RE

## WANTED

**ELECTRONICS** technician to repair musical electronic equipment (amplifiers, synthesizers, etc.). Salary commensurate with ability. Send resume to: **ACE MUSIC**, 13630 W. Dixie, N. Miami, FL 33161

**RADIO** and TV tubes 1938 to 1978 \$1.00 ea. **PRELLER TV**, Augusta, AR 72006. (501) 347-2281.

**HIGHLY PROFITABLE**

## ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-T, Box 248, Walnut Creek, CA 94597.**

BREATHE REFRESHING "VITAMINS OF THE AIR" with an amazing **NEGATIVE ION GENERATOR**

ROOM-PORTABLE-CAR UNITS, TESTERS AND ACCESSORIES (Dealers Wanted)

**\$129.00**

Or Send \$1.00 for fascinating details to **GOLDEN ENTERPRISES, INC.** P.O. Box 1282-RE Glendale, Arizona 85311

## CHRISTMAS IN AUGUST

DELTA'S FIRST-TIME-EVER SALE! We bring you Christmas Savings now so you can get more for your money than ever before!

OUR ORIGINAL PRICES  
**1/2 OFF**  
GOOD TILL SEP. 30

**1/2 OFF!**

**TV Game Boards!**

**FANTASTIC TREASURE OF PARTS!!**

Without Joysticks No. 6939R **\$2.95**

With Joysticks. No. 6938R **\$5.95**

These TV game boards are a fantastic source of parts as you can see by the parts listed below. Included with ea. board is step-by-step instructions for the removal of all these parts.

- |   |                     |
|---|---------------------|
| 4001-3 pcs.—Quad 2-Input NOR gate.                    | <b>C-MOS</b>        |
| 4008-1 pc.—4 bit Full adder.                          |                     |
| 4011-3 pcs.—Quad 2-Input NAND gate.                   |                     |
| 4013-2 pcs.—Dual D Flip Flop.                         |                     |
| 4016-2 pcs.—Quad Analog switch/Quad Multiplexer.      |                     |
| 4022-1 pc.—Triple 3-Input NAND Gate.                  |                     |
| 4071-1 pc.—Quad 2-Input OR gate.                      |                     |
| 4511-1 pc.—BCD-to-7 segment latch/decoder/divider.    |                     |
| 4519-2 pcs.—4-Bit AND/OR selector.                    |                     |
| 4520-1 pc.—Dual Binary UP counter.                    |                     |
| 4528-1 pc.—Dual Monostable Multivibrator.             | <b>WORTH OF ICS</b> |
| 3401-2 pcs.—Quad Operational Amplifier.               |                     |
| LM339-5 pcs.—Quad Differential Comparators.           |                     |
| LM301A-1 pc.—High-performance operational amplifiers. |                     |
| NE555-2 pcs.—NPN high speed switching transistor.     |                     |
| 2N3904-2 pcs.—timer.                                  |                     |
| 2N3906-1 pc.—PNP high speed switching transistor.     |                     |
- Also included are two 10K Joysticks (which we sell for \$3.95), many capacitors, resistors, trimmers & diodes.

**1/2 OFF!**

**SWITCHCRAFT**

**\$3.50**

Delta's original \$6.95 ea.

**Push Button Assemblies!**

No. 6408R

This is the top-of-the-line SWITCHCRAFT multi-gang switch. It has SIX push buttons. Button 1 is SPST, momentary switch; and releases any button that has been depressed. Switches 2 and 3 lock when depressed and release when switches 1—4—5 or 6 is depressed. Switches 4—5 & 6 are interlocked, depress any one of them releases the others. Switch 2 is SPST normally open. Switch 3 is SPDT & SPST normally open. Switch 4 is DPDT. Switch 5 is DPDT & 3 SPST normally open switches. Switch 6 is DPDT & SPST normally open. A fantastic feature of this switch is that any of the switch sections may be removed from its initial position and placed on another push button; and ganged so that more combinations are possible on any of the push buttons. This switch has the special SWITCHCRAFT LOCKOUT feature which prevents operation of more than one push button at a time. Switchcraft catalog price (in 1976) was \$29.48. Delta's original price \$6.95.

## 1/2 OFF! Momentary Push Button Switches

Delta's This switch is the same physical shape as the one shown above, except this momentary switch has only TWO switches. Compact, low-silhouette design. Only 1 1/4" H. & 3 5/8" behind panel. Plunger on 5/8" centers. Features 2 momentary switches. The first is a momentary on-off switch. Second has 4 functions, the 1st is a momentary on-off, the 2nd is a SPDT, the 3rd & 4th section are DPDT momentary. The catalog price is \$9 ea. No. 6412R

**\$1** Each

**1/2 OFF!**

**BEAM-X Counters!**

Delta's original price \$13.95 **\$6.95**

2 for \$12

**With 3 Nixie Tubes!**

This counter was originally used by a large mfg. of copying machines. Function: the number of copies desired was preset by dials & the machine then made this number of copies—displaying the count on the NIXIE tubes. When the preset number was reached, the counter stopped the machine. These counters were removed from the copiers & replaced by new models. Input: 115VAC and uses 24V logic. This unit contains 5 BEAM-X switching tubes, its own power supply, plus a 200 VDC & 6.3 VAC supply. It contains 3 Burroughs NIXIE tubes, type B5092A which currently sells for \$1.7 each. We supply diagram of BEAM-X tubes, operating instructions and some application data. We are selling these counters at this low price because of the minor defects that some of these counters have. Unfortunately we do not have the time to test or make the minor repairs needed to make the counters operational. 6 1/2 x 6 1/2 x 11 1/2". Wt. 7 lbs. Beam X Tubes worth \$50. apiece if you can find 'em.

**40 FOR \$6.**

**1/2 OFF! GANGED 18 Assorted Pots \$3**

No. 8902R

**1/2 OFF! GANGED 18 Assorted Pots \$3**

**POT Bonanza**

No. 8902R

We have acquired the entire inventory (2 million pieces) of ganged pots from one of the largest makers of automobile radios in the country. There are 2-gang, 3-gang, 4-gang, 5-gang, and 6-gang pots; almost all also include line switch. These are made by C-T-S (American made). All the popular resistance values, tapers and many of the pots are tapped. Any one of these pots would cost you more than the whole package of 18 pieces.

**Wow! Less Than 17¢ Each!**

## CopperClad PC Boards!

- No. 5721R...9 1/2x18", single-sided copper clad with phenolic board on reverse side: (With holes). Original Delta price \$2 ea. **\$1.**
- No. 5672R...12x18", single-sided, copper clad with approx. 1-oz. of copper. Reverse side 1/16" G-10 glass epoxy board. (With holes). Original Delta price \$3 ea. **1.50**
- DOUBLE SIDED**
- No. 5712R...12x18", double-sided copper clad, with approx. 1-oz. of copper each side, over 1/16" G-10 glass epoxy board. (No holes). Original Delta price \$5 ea. **2.50**
- No. 5711R...16x17", double-sided copper clad, with approx. 1-oz. of copper each side, over 1/16" G-10 glass epoxy board. (No holes). Original Delta price \$6 ea. **\$3.**

## NEW MAIL-ORDER ADDRESS

**FREE 120-PG. 'SURPLUS' CATALOG**

**DELTA ELECTRONICS**

176 SECOND AVE. WALTHAM, MASS. 02154

**TEL. (617) 388-4705**

When in our area, northeastern Mass. or southern N.H. visit our retail at 7 Oakland St., Amesbury, Mass.

CIRCLE 8 ON FREE INFORMATION CARD







<p>7400 TTL .16</p> <p>7404 .18</p> <p>7408 .19</p> <p>7410 .16</p> <p>7412 .25</p> <p>7413 .40</p> <p>7416 .25</p> <p>7420 .16</p> <p>7425 .28</p> <p>7426 .28</p> <p>7427 .25</p> <p>7430 .25</p> <p>7437 .24</p> <p>7438 .24</p> <p>7440 .16</p> <p>7445 .75</p> <p>7451 .16</p> <p>7454 .16</p> <p>7474 .35</p> <p>7475 .49</p> <p>7483 .58</p> <p>7485 .78</p> <p>7486 .35</p> <p>7489 .1.80</p> <p>7490 .43</p> <p>7492 .42</p> <p>7493 .42</p> <p>7495 .65</p> <p>74107 .35</p> <p>74123 .35</p> <p>74141 .78</p> <p>74151 .58</p> <p>74155 .75</p> <p>74160 .86</p> <p>74165 .86</p> <p>74175 .75</p> <p>74180 .75</p> <p>74181 .1.85</p> <p>74195 .65</p> <p>MISC TTL</p> <p>74S04 .35</p> <p>74S05 .35</p> <p>74S50 .35</p> <p>74S153 1.95</p> <p>74S181 2.75</p>	<p><b>P1103A</b></p> <p>1024 X1 Dynamic RAM</p> <p>42c</p> <p><b>741PC</b></p> <p>MINI-DIP DP AMP</p> <p>.29c</p> <p><b>LM300H</b></p> <p>VOLTAGE REGULATOR</p> <p>\$1.00</p> <p><b>82S115</b></p> <p>512 X8 PROM 60ns</p> <p>OTYS LIMITED</p> <p>\$4.75</p> <p><b>LM305H</b></p> <p>VOLTAGE REGULATOR</p> <p>T0-99</p> <p>75c</p> <p><b>74S201</b></p> <p>256 X1 Static RAM</p> <p>50ns</p> <p>\$1.95</p> <p><b>2716</b></p> <p>16K EPROM</p> <p>\$38.50</p> <p><b>MC1458P</b></p> <p>Dual Op-Amp</p> <p>24c</p>	<p><b>S-10016K BOARD</b></p> <p>ASSEMBLED &amp; TESTED</p> <p>\$279.00</p> <p><b>7114A APPLE II™ PROM MODULE</b></p> <p>PERMITS THE ADDITION OR REPLACEMENT OF APPLE FIRMWARE WITHOUT PHYSICAL REMOVAL OF THE APPLE ROMS.</p> <p>•NEW•</p> <p>LESS PROMS</p> <p>\$79.95</p> <p><b>7811A ARITHMETIC PROCESSOR</b></p> <p>• BASED ON AMD'S AM9511</p> <p>• ADD • SUBTRACT • MULTIPLY • DIVIDE</p> <p>TRIG • ROOTS • LOGS</p> <p>\$400.00</p> <p><b>Calculator</b></p> <p>CREDIT CARD SIZE</p> <p>W/MEMORY</p> <p>AUTOMATIC SHUT-OFF</p> <p>\$19.95</p>	<p><b>NIXIE TUBE</b></p> <p>BURROUGHS</p> <p>\$1.25</p> <p><b>8038C</b></p> <p>VCO Waveform Gen w/sine</p> <p>\$2.75</p> <p><b>2708</b></p> <p>1024 X8 EPROM</p> <p>250ns</p> <p>\$8.50</p> <p><b>555</b></p> <p>TIMER</p> <p>28c</p> <p><b>3HT1</b></p> <p>3 AMP</p> <p>100 VOLT</p> <p>FULL WAVE BRIDGE</p> <p>.50c</p> <p><b>1702A</b></p> <p>256 X8 EPROM</p> <p>\$3.95</p> <p><b>ULN2001</b></p> <p>High-current Drivers</p> <p>Darlington</p> <p>75c</p> <p><b>74LS240 IN 74LS244</b></p> <p><b>74LS245 STOCK 74LS373</b></p> <p><b>74LS374</b></p> <p>LIMIT 10 EACH</p> <p>\$2.45</p> <p><b>2505K</b></p> <p>512 X1 DYNAMIC SHIFT REGISTER</p> <p>95c</p>	<p>LINEAR</p> <p>LM300H .78</p> <p>LM301N .35</p> <p>LM305H .60</p> <p>LM306H/N 1.50</p> <p>LM307H/N .35</p> <p>LM308N .95</p> <p>LM309K 1.25</p> <p>LM310N 1.10</p> <p>LM311N .85</p> <p>LM320T5 1.25</p> <p>LM320T12 1.25</p> <p>LM320T15 1.25</p> <p>LM322N 1.75</p> <p>LM323K 5.75</p> <p>LM340T5 1.25</p> <p>LM340T12 1.25</p> <p>LM340T15 1.25</p> <p>LM556 .89</p> <p>LM566 1.65</p> <p>LM711N/H .39</p> <p>LM723N .55</p> <p>LM725H 1.75</p> <p>LM733N .95</p> <p>LM741N/H .35</p> <p>LM747N .78</p> <p>LM749N .85</p> <p>LM9300 .46</p> <p>781105 6.95</p> <p>SG4501 1.95</p> <p>TRANSISTORS</p> <p>2N2222A 5/1.00</p> <p>2N2907A 5/1.00</p> <p>2N3055 .85</p> <p>2N3904 6/1.00</p> <p>2N3906 6/1.00</p> <p>2N4401 6/1.00</p> <p>2N4403 6/1.00</p> <p>MJE2955 1.20</p> <p>MJE3055 1.00</p> <p>DIODES</p> <p>1N914 20/1.00</p> <p>1N4003 15/1.00</p> <p>1N4005 12/1.00</p> <p>1N4007 10/1.00</p> <p>1N4148 20/1.00</p>	
<p><b>6301-1J</b></p> <p>256X4 PROM</p> <p>\$165</p>	<p><b>20,000 VOLT RECTIFIER</b></p> <p>25 ma</p> <p>\$1.65</p>	<p><b>CONCORD COMPUTER COMPONENTS</b></p> <p>1971 South State College-Anaheim, Calif. 92806</p> <p>Visa- Master Charge</p> <p>Check or M.O.</p> <p>No COD</p> <p>(714) 937-0641</p> <p>Minimum Order-10.00</p> <p>Add 1.00 for Frt.</p> <p>Cal. Res. add 6%</p>		<p><b>78H05</b></p> <p>5 AMP 5VOLT REGULATOR</p> <p>IN TQ-3 PKG</p> <p>\$4.95</p>	<p><b>8AMP SCR</b></p> <p>2N4442</p> <p>200 V</p> <p>.50</p>

CIRCLE 31 ON FREE INFORMATION CARD

**HOBBY WORLD**

CALL TOLL FREE: (800) 423-5387

CA, HI, AK: (213) 886-9200

Your No.1 Source for Computer Electronics

**FINALLY! PANAVISE at a Discount**

<p><b>LOW PROFILE BASE</b></p> <p>Cat No. PV305</p> <p>\$10.50</p>	<p><b>STANDARD BASE</b></p> <p>Cat No. PV300</p> <p>\$10.50</p>
<p><b>VACUUM BASE</b></p> <p>Cat No. PV380</p> <p>\$14.50</p>	<p><b>STANDARD VISE HEAD</b></p> <p>Cat No. PV303</p> <p>\$11.25</p>
<p><b>BASE TRAY</b></p> <p>Cat No. PV312</p> <p>\$8.50</p>	<p><b>WIDE OPENING VISE HEAD</b></p> <p>Cat No. PV366</p> <p>\$11.25</p>
<p><b>BASE MOUNTING CLAMP</b></p> <p>Cat No. PV311</p> <p>\$10.00</p>	<p><b>PC BOARD VISES</b></p> <p>Cat No. PV315 Standard, \$10.98</p> <p>Cat No. PV315 S-100 \$16.75</p>
<p><b>HORIZONTAL VISE HEAD</b></p> <p>Cat No. PV304</p> <p>\$12.00</p>	

**IC Sockets Penny-A-Pin**

- Texas Instruments
- Solder tail
- Package quantities only
- Order by Cat No. 1117 and pins

8 pin	20 for \$1.60
14 pin	10 for \$1.40
16 pin	10 for \$1.60
18 pin	8 for \$1.44
20 pin	8 for \$1.60
22 pin	8 for \$1.76
24 pin	3 for .72
28 pin	3 for .84
40 pin	2 for .80

**19355 Business Center Dr. Northridge CA 91324 6R8**

Pay by check, COD, Visa, or Mastercharge. Order by phone or mail. Please include phone number and magazine issue you are ordering from. USA: add \$2 for shipping/handling. \$3 for air. Foreign: add \$3 for surface, \$6 for air. COD's also add \$1. Guaranteed satisfaction for 120 days or your money back!

Send for FREE CATALOG Featuring

The best selection of computer accessories add-ons, factory fresh IC's, led's, semi's, software, PC aids, prototyping aids, books, test equipment, and more! Always updated! Dozens of new products every issue!

CIRCLE 26 ON FREE INFORMATION CARD

**Electricity from the sun.**

5 Volt panel 1/4 amp \$50 2.5 Volt panel 1/2 amp \$40

**GIANT 3 1/2 inch cell, delivers 1 amp \$8.50**

Above cell with special motor & prop, runs in sun \$10.25

**LOGIC power supplies, unused, solid state construction.**

5 Volt 4 amp \$35 5 Volt 15 amp \$45 5 Volt 25 amp \$45

5 volt 35 amp \$50 12 Volt 15 amp \$40

**Govt surplus walky talky, used cond.**

47-55.4 mc range.

Ant. \$5 each extra.

With data.

\$25 ea 2 for \$45

**AN/PRC-6**

**SEE IN THE DARKNESS**

IR viewer, portable, new with choice of one lens...close up, telephoto or gen. purpose.

Requires 6 volt DC btry.

\$250

Shipping extra on all merchandise

**Meshna Inc., PO Box 62, E. Lynn, Mass. 01904**

CIRCLE 47 ON FREE INFORMATION CARD



# DIGI-KEY CORPORATION

## TOLL FREE 1-800-346-5444

Quality Electronic Components

MN., AK., HI. RESIDENTS

218-681-6674



**DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES**

**I.C.'S • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES • CLOCK MODULES • OPTOELECTRONICS • BREADBOARDING & TESTING DEVICES • DRAFTING SUPPLIES • DATA BOOKS • HEAT SINKS • WIRE • TOOLS • AND MORE... WRITE FOR FREE CATALOG**

### I.C. Socket Prices Slashed

**BOTH SOLIDSTATE AND WIRE WRAP ARE IN STOCK**  
**SOLIDSTATE SOCKETS ARE LOW PROFILE**  
**WIRE WRAP SOCKETS ARE STANDARD PROFILE/LEVEL 3**

Part No.	Description	1	10	100
4-5T	8 Pin Solid State	0.8	8.0	8.00
4-5T	14 Pin Solid State	1.4	14.0	14.00
4-5T	16 Pin Solid State	1.6	16.0	16.00
4-5T	18 Pin Solid State	1.8	18.0	18.00
4-5T	20 Pin Solid State	2.0	20.0	20.00
9-5T	22 Pin Solid State	2.2	22.0	22.00
9-5T	24 Pin Solid State	2.4	24.0	24.00
9-5T	26 Pin Solid State	2.6	26.0	26.00
9-5T	28 Pin Solid State	2.8	28.0	28.00
9-5T	30 Pin Solid State	3.0	30.0	30.00
9-5T	32 Pin Solid State	3.2	32.0	32.00
9-5T	34 Pin Solid State	3.4	34.0	34.00
9-5T	36 Pin Solid State	3.6	36.0	36.00
9-5T	38 Pin Solid State	3.8	38.0	38.00
9-5T	40 Pin Solid State	4.0	40.0	40.00
9-5T	42 Pin Solid State	4.2	42.0	42.00
9-5T	44 Pin Solid State	4.4	44.0	44.00
9-5T	46 Pin Solid State	4.6	46.0	46.00
9-5T	48 Pin Solid State	4.8	48.0	48.00
9-5T	50 Pin Solid State	5.0	50.0	50.00
9-5T	52 Pin Solid State	5.2	52.0	52.00
9-5T	54 Pin Solid State	5.4	54.0	54.00
9-5T	56 Pin Solid State	5.6	56.0	56.00
9-5T	58 Pin Solid State	5.8	58.0	58.00
9-5T	60 Pin Solid State	6.0	60.0	60.00
9-5T	62 Pin Solid State	6.2	62.0	62.00
9-5T	64 Pin Solid State	6.4	64.0	64.00
9-5T	66 Pin Solid State	6.6	66.0	66.00
9-5T	68 Pin Solid State	6.8	68.0	68.00
9-5T	70 Pin Solid State	7.0	70.0	70.00
9-5T	72 Pin Solid State	7.2	72.0	72.00
9-5T	74 Pin Solid State	7.4	74.0	74.00
9-5T	76 Pin Solid State	7.6	76.0	76.00
9-5T	78 Pin Solid State	7.8	78.0	78.00
9-5T	80 Pin Solid State	8.0	80.0	80.00
9-5T	82 Pin Solid State	8.2	82.0	82.00
9-5T	84 Pin Solid State	8.4	84.0	84.00
9-5T	86 Pin Solid State	8.6	86.0	86.00
9-5T	88 Pin Solid State	8.8	88.0	88.00
9-5T	90 Pin Solid State	9.0	90.0	90.00
9-5T	92 Pin Solid State	9.2	92.0	92.00
9-5T	94 Pin Solid State	9.4	94.0	94.00
9-5T	96 Pin Solid State	9.6	96.0	96.00
9-5T	98 Pin Solid State	9.8	98.0	98.00
9-5T	100 Pin Solid State	10.0	100.0	100.00

### MOLEX I.C. SOCKET PINS

**INTEGRATED CIRCUITS**

Part No.	Description	1	10	100
4-5T	8 Pin Solid State	0.8	8.0	8.00
4-5T	14 Pin Solid State	1.4	14.0	14.00
4-5T	16 Pin Solid State	1.6	16.0	16.00
4-5T	18 Pin Solid State	1.8	18.0	18.00
4-5T	20 Pin Solid State	2.0	20.0	20.00
9-5T	22 Pin Solid State	2.2	22.0	22.00
9-5T	24 Pin Solid State	2.4	24.0	24.00
9-5T	26 Pin Solid State	2.6	26.0	26.00
9-5T	28 Pin Solid State	2.8	28.0	28.00
9-5T	30 Pin Solid State	3.0	30.0	30.00
9-5T	32 Pin Solid State	3.2	32.0	32.00
9-5T	34 Pin Solid State	3.4	34.0	34.00
9-5T	36 Pin Solid State	3.6	36.0	36.00
9-5T	38 Pin Solid State	3.8	38.0	38.00
9-5T	40 Pin Solid State	4.0	40.0	40.00
9-5T	42 Pin Solid State	4.2	42.0	42.00
9-5T	44 Pin Solid State	4.4	44.0	44.00
9-5T	46 Pin Solid State	4.6	46.0	46.00
9-5T	48 Pin Solid State	4.8	48.0	48.00
9-5T	50 Pin Solid State	5.0	50.0	50.00
9-5T	52 Pin Solid State	5.2	52.0	52.00
9-5T	54 Pin Solid State	5.4	54.0	54.00
9-5T	56 Pin Solid State	5.6	56.0	56.00
9-5T	58 Pin Solid State	5.8	58.0	58.00
9-5T	60 Pin Solid State	6.0	60.0	60.00
9-5T	62 Pin Solid State	6.2	62.0	62.00
9-5T	64 Pin Solid State	6.4	64.0	64.00
9-5T	66 Pin Solid State	6.6	66.0	66.00
9-5T	68 Pin Solid State	6.8	68.0	68.00
9-5T	70 Pin Solid State	7.0	70.0	70.00
9-5T	72 Pin Solid State	7.2	72.0	72.00
9-5T	74 Pin Solid State	7.4	74.0	74.00
9-5T	76 Pin Solid State	7.6	76.0	76.00
9-5T	78 Pin Solid State	7.8	78.0	78.00
9-5T	80 Pin Solid State	8.0	80.0	80.00
9-5T	82 Pin Solid State	8.2	82.0	82.00
9-5T	84 Pin Solid State	8.4	84.0	84.00
9-5T	86 Pin Solid State	8.6	86.0	86.00
9-5T	88 Pin Solid State	8.8	88.0	88.00
9-5T	90 Pin Solid State	9.0	90.0	90.00
9-5T	92 Pin Solid State	9.2	92.0	92.00
9-5T	94 Pin Solid State	9.4	94.0	94.00
9-5T	96 Pin Solid State	9.6	96.0	96.00
9-5T	98 Pin Solid State	9.8	98.0	98.00
9-5T	100 Pin Solid State	10.0	100.0	100.00

### TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS

Part No.	Description	1	10	100
4-5T	8 Pin Solid State	0.8	8.0	8.00
4-5T	14 Pin Solid State	1.4	14.0	14.00
4-5T	16 Pin Solid State	1.6	16.0	16.00
4-5T	18 Pin Solid State	1.8	18.0	18.00
4-5T	20 Pin Solid State	2.0	20.0	20.00
9-5T	22 Pin Solid State	2.2	22.0	22.00
9-5T	24 Pin Solid State	2.4	24.0	24.00
9-5T	26 Pin Solid State	2.6	26.0	26.00
9-5T	28 Pin Solid State	2.8	28.0	28.00
9-5T	30 Pin Solid State	3.0	30.0	30.00
9-5T	32 Pin Solid State	3.2	32.0	32.00
9-5T	34 Pin Solid State	3.4	34.0	34.00
9-5T	36 Pin Solid State	3.6	36.0	36.00
9-5T	38 Pin Solid State	3.8	38.0	38.00
9-5T	40 Pin Solid State	4.0	40.0	40.00
9-5T	42 Pin Solid State	4.2	42.0	42.00
9-5T	44 Pin Solid State	4.4	44.0	44.00
9-5T	46 Pin Solid State	4.6	46.0	46.00
9-5T	48 Pin Solid State	4.8	48.0	48.00
9-5T	50 Pin Solid State	5.0	50.0	50.00
9-5T	52 Pin Solid State	5.2	52.0	52.00
9-5T	54 Pin Solid State	5.4	54.0	54.00
9-5T	56 Pin Solid State	5.6	56.0	56.00
9-5T	58 Pin Solid State	5.8	58.0	58.00
9-5T	60 Pin Solid State	6.0	60.0	60.00
9-5T	62 Pin Solid State	6.2	62.0	62.00
9-5T	64 Pin Solid State	6.4	64.0	64.00
9-5T	66 Pin Solid State	6.6	66.0	66.00
9-5T	68 Pin Solid State	6.8	68.0	68.00
9-5T	70 Pin Solid State	7.0	70.0	70.00
9-5T	72 Pin Solid State	7.2	72.0	72.00
9-5T	74 Pin Solid State	7.4	74.0	74.00
9-5T	76 Pin Solid State	7.6	76.0	76.00
9-5T	78 Pin Solid State	7.8	78.0	78.00
9-5T	80 Pin Solid State	8.0	80.0	80.00
9-5T	82 Pin Solid State	8.2	82.0	82.00
9-5T	84 Pin Solid State	8.4	84.0	84.00
9-5T	86 Pin Solid State	8.6	86.0	86.00
9-5T	88 Pin Solid State	8.8	88.0	88.00
9-5T	90 Pin Solid State	9.0	90.0	90.00
9-5T	92 Pin Solid State	9.2	92.0	92.00
9-5T	94 Pin Solid State	9.4	94.0	94.00
9-5T	96 Pin Solid State	9.6	96.0	96.00
9-5T	98 Pin Solid State	9.8	98.0	98.00
9-5T	100 Pin Solid State	10.0	100.0	100.00

### Panasonic DISC CAPACITOR KIT

Part No.	Description	1	10	100
4-5T	8 Pin Solid State	0.8	8.0	8.00
4-5T	14 Pin Solid State	1.4	14.0	14.00
4-5T	16 Pin Solid State	1.6	16.0	16.00
4-5T	18 Pin Solid State	1.8	18.0	18.00
4-5T	20 Pin Solid State	2.0	20.0	20.00
9-5T	22 Pin Solid State	2.2	22.0	22.00
9-5T	24 Pin Solid State	2.4	24.0	24.00
9-5T	26 Pin Solid State	2.6	26.0	26.00
9-5T	28 Pin Solid State	2.8	28.0	28.00
9-5T	30 Pin Solid State	3.0	30.0	30.00
9-5T	32 Pin Solid State	3.2	32.0	32.00
9-5T	34 Pin Solid State	3.4	34.0	34.00
9-5T	36 Pin Solid State	3.6	36.0	36.00
9-5T	38 Pin Solid State	3.8	38.0	38.00
9-5T	40 Pin Solid State	4.0	40.0	40.00
9-5T	42 Pin Solid State	4.2	42.0	42.00
9-5T	44 Pin Solid State	4.4	44.0	44.00
9-5T	46 Pin Solid State	4.6	46.0	46.00
9-5T	48 Pin Solid State	4.8	48.0	48.00
9-5T	50 Pin Solid State	5.0	50.0	50.00
9-5T	52 Pin Solid State	5.2	52.0	52.00
9-5T	54 Pin Solid State	5.4	54.0	54.00
9-5T	56 Pin Solid State	5.6	56.0	56.00
9-5T	58 Pin Solid State	5.8	58.0	58.00
9-5T	60 Pin Solid State	6.0	60.0	60.00
9-5T	62 Pin Solid State	6.2	62.0	62.00
9-5T	64 Pin Solid State	6.4	64.0	64.00
9-5T	66 Pin Solid State	6.6	66.0	66.00
9-5T	68 Pin Solid State	6.8	68.0	68.00
9-5T	70 Pin Solid State	7.0	70.0	70.00
9-5T	72 Pin Solid State	7.2	72.0	72.00
9-5T	74 Pin Solid State	7.4	74.0	74.00
9-5T	76 Pin Solid State	7.6	76.0	76.00
9-5T	78 Pin Solid State	7.8	78.0	78.00
9-5T	80 Pin Solid State	8.0	80.0	80.00
9-5T	82 Pin Solid State	8.2	82.0	82.00
9-5T	84 Pin Solid State	8.4	84.0	84.00
9-5T	86 Pin Solid State	8.6	86.0	86.00
9-5T	88 Pin Solid State	8.8	88.0	88.00
9-5T	90 Pin Solid State	9.0	90.0	90.00
9-5T	92 Pin Solid State	9.2	92.0	92.00
9-5T	94 Pin Solid State	9.4	94.0	94.00
9-5T	96 Pin Solid State	9.6	96.0	96.00
9-5T	98 Pin Solid State	9.8	98.0	98.00
9-5T	100 Pin Solid State	10.0	100.0	100.00

### THE MA1023 by NATIONAL SEMICONDUCTOR

Part No.	Description	1	10	100
4-5T	8 Pin Solid State	0.8	8.0	8.00
4-5T	14 Pin Solid State	1.4	14.0	14.00
4-5T	16 Pin Solid State	1.6	16.0	16.00
4-5T	18 Pin Solid State	1.8	18.0	18.00
4-5T	20 Pin Solid State	2.0	20.0	20.00
9-5T	22 Pin Solid State	2.2	22.0	22.00
9-5T	24 Pin Solid State	2.4	24.0	24.00
9-5T	26 Pin Solid State	2.6	26.0	26.00
9-5T	28 Pin Solid State	2.8	28.0	28.00
9-5T	30 Pin Solid State	3.0	30.0	30.00
9-5T	32 Pin Solid State	3.2	32.0	32.00
9-5T	34 Pin Solid State	3.4	34.0	34.00
9-5T	36 Pin Solid State	3.6	36.0	3



7400 TTL			
SN7400N	16	SN7470N	29
SN7401N	18	SN7471N	29
SN7402N	18	SN7472N	35
SN7403N	18	SN7473N	35
SN7404N	18	SN7474N	35
SN7405N	18	SN7475N	35
SN7406N	18	SN7476N	35
SN7407N	29	SN7477N	35
SN7408N	29	SN7478N	35
SN7409N	29	SN7479N	35
SN7410N	29	SN7480N	50
SN7411N	25	SN7481N	50
SN7412N	25	SN7482N	50
SN7413N	25	SN7483N	50
SN7414N	25	SN7484N	50
SN7415N	25	SN7485N	50
SN7416N	25	SN7486N	50
SN7417N	25	SN7487N	50
SN7418N	25	SN7488N	50
SN7419N	25	SN7489N	50
SN7420N	29	SN7490N	50
SN7421N	29	SN7491N	50
SN7422N	29	SN7492N	50
SN7423N	29	SN7493N	50
SN7424N	29	SN7494N	50
SN7425N	29	SN7495N	50
SN7426N	29	SN7496N	50
SN7427N	29	SN7497N	50
SN7428N	29	SN7498N	50
SN7429N	29	SN7499N	50
SN7430N	29	SN7500N	50
SN7431N	29	SN7501N	50
SN7432N	29	SN7502N	50
SN7433N	29	SN7503N	50
SN7434N	29	SN7504N	50
SN7435N	29	SN7505N	50
SN7436N	29	SN7506N	50
SN7437N	29	SN7507N	50
SN7438N	29	SN7508N	50
SN7439N	29	SN7509N	50
SN7440N	29	SN7510N	50
SN7441N	29	SN7511N	50
SN7442N	29	SN7512N	50
SN7443N	29	SN7513N	50
SN7444N	29	SN7514N	50
SN7445N	29	SN7515N	50
SN7446N	29	SN7516N	50
SN7447N	29	SN7517N	50
SN7448N	29	SN7518N	50
SN7449N	29	SN7519N	50
SN7450N	29	SN7520N	50
SN7451N	29	SN7521N	50
SN7452N	29	SN7522N	50
SN7453N	29	SN7523N	50
SN7454N	29	SN7524N	50
SN7455N	29	SN7525N	50
SN7456N	29	SN7526N	50
SN7457N	29	SN7527N	50
SN7458N	29	SN7528N	50
SN7459N	29	SN7529N	50
SN7460N	29	SN7530N	50
SN7461N	29	SN7531N	50
SN7462N	29	SN7532N	50
SN7463N	29	SN7533N	50
SN7464N	29	SN7534N	50
SN7465N	29	SN7535N	50
SN7466N	29	SN7536N	50
SN7467N	29	SN7537N	50
SN7468N	29	SN7538N	50
SN7469N	29	SN7539N	50
SN7470N	29	SN7540N	50
SN7471N	29	SN7541N	50
SN7472N	35	SN7542N	50
SN7473N	35	SN7543N	50
SN7474N	35	SN7544N	50
SN7475N	35	SN7545N	50
SN7476N	35	SN7546N	50
SN7477N	35	SN7547N	50
SN7478N	35	SN7548N	50
SN7479N	35	SN7549N	50
SN7480N	50	SN7550N	50
SN7481N	50	SN7551N	50
SN7482N	50	SN7552N	50
SN7708N	50	SN7778N	50
SN			

CD4000	23	C/MOS	CD4070	55
CD4001	23	CD4001	CD4071	23
CD4002	23	CD4026	89	
CD4006	1.19	CD4029	1.19	
CD4007	25	CD4030	49	
CD4009	49	CD4035	99	
CD4010	49	CD4040	1.19	
CD4013	23	CD4041	1.25	
CD4012	25	CD4042	99	
CD4013	39	CD4043	89	
CD4014	1.39	CD4044	89	
CD4015	1.19	CD4046	1.79	
CD4016	49	CD4047	2.50	
CD4017	1.19	CD4048	1.35	
CD4018	99	CD4049	49	
CD4019	49	CD4050	49	
CD4020	1.19	CD4051	1.19	
CD4021	1.39	CD4052	1.19	
CD4022	1.19	CD4055	2.95	
CD4023	23	CD4059	9.95	
CD4024	79	CD4060	1.49	
CD4025	23	CD4066	79	
CD4026	2.25	CD4068	39	
CD4027	69	CD4069	45	
		CD4070	55	
		CD4071	23	
		CD4072	23	
		CD4073	1.39	
		CD4074	1.39	
		CD4075	1.39	
		CD4076	1.39	
		CD4077	1.39	
		CD4078	1.39	
		CD4079	1.39	
		CD4080	1.39	
		CD4081	23	
		CD4082	23	
		CD4083	99	
		CD4084	249	
		CD4085	14.95	
		CD4086	14.95	
		CD4087	14.95	
		CD4426	14.95	
		CD4427		

74C00		
74C00	39	74C183 2.49
74C01	39	74C184 2.49
74C02	39	74C185 2.60
74C03	39	74C186 2.49
74C04	39	74C187 2.49
74C05	39	74C188 2.49
74C06	39	74C189 2.49
74C07	39	74C190 2.49
74C08	39	74C191 2.49
74C09	39	74C192 2.49
74C10	39	74C193 2.49
74C11	39	74C194 2.49
74C12	39	74C195 2.49
74C327	39	74C510 2.49



## Transistor Checker



— Completely Assembled —  
— Battery Operated —

The ASI Transistor Checker is capable of checking a wide range of transistor types, either "in circuit" or out of circuit. To operate, simply plug the transistor to be checked into the front panel socket, or connect it with the alligator clip test leads provided. The unit safely and automatically identifies low, medium and high-power PNP and NPN transistors. Size: 3 1/2" x 6 1/4" x 2 1/2". "C" cell battery not included.

Trans-Check \$29.95 ea.

## Custom Cables & Jumpers



### DB 25 Series Cables

Part No.	Cable Length	Connectors	Price
DB25P-4-P	4 ft.	2-DP25P	\$15.95 ea.
DB25P-4-S	4 ft.	1-DP25P/1-25S	\$16.95 ea.
DB25S-4-S	4 ft.	2-DP25S	\$17.95 ea.

### Dip Jumpers

Part No.	Cable Length	Connectors	Price
DJ14-1	1 ft.	1-14 Pin	\$1.59 ea.
DJ16-1	1 ft.	1-16 Pin	1.79 ea.
DJ24-1	1 ft.	1-24 Pin	2.79 ea.
DJ14-1-14	1 ft.	2-14 Pin	2.79 ea.
DJ16-1-16	1 ft.	2-16 Pin	3.19 ea.
DJ24-1-24	1 ft.	2-24 Pin	4.95 ea.

For Custom Cables & Jumpers, See JAMECO 1979 Catalog for Pricing

## CONNECTORS

### 25 Pin-D Subminiature

DB25P (as pictured)	PLUG (Meets RS232)	\$2.95
DB25S	SOCKET (Meets RS232)	\$3.50
DB51226-1	Cable Cover for DB25P or DB25S	\$1.75

### PRINTED CIRCUIT EDGE-CARD

156 Spacing - 1 in. Double Row Out — Brackets Contacts — Pins .054 to .070 P.C. Cards	
15/30	PINS (Solder Eyelet) \$1.95
18/36	PINS (Solder Eyelet) \$2.49
22/44	PINS (Solder Eyelet) \$2.95
50/100 (.100 Spacing)	PINS (Wire Wrap) \$6.95
50/100 (.125 Spacing)	PINS (Wire Wrap) R681-1 \$6.95

## 4-Digit Clock Kit

- Bright .35" ht. red display
- Sequential flashing colon
- 12 or 24 hour operation
- Extruded aluminum case (black)
- Pressure switches for hours, minutes & hold functions
- Includes all components, case and wall transformer
- Size: 3 1/4 x 1 1/4 x 1 1/4

JE730 \$14.95

## Jumbo 6-Digit Clock Kit

- Four .63" ht. and two .30" ht. common anode displays
- Uses MM5314 clock chip
- Switches for hours, minutes and hold functions
- Hours easily viewable to 30 feet
- Simulated walnut case
- 115 VAC operation
- 12 or 24 hour operation
- Includes all components, case and wall transformer
- Size: 6 1/4 x 3 1/4 x 1 1/4

JE747 \$29.95

## JE701

### 6-Digit Clock Kit \$19.95

## REMOTE CONTROL TRANSMITTER & RECEIVER



- Can be used as remote control for TV
- Use 1 for your own channel, other for TV
- Transmitter & Receiver 30 ft. range
- Thousands of uses for remote control applications
- Transmitter uses a 1.5V battery
- Battery included

\$19.95

## Digital Stopwatch Kit

- Use Intersil 7206 Chip
- Plated thru double-sided P.C. Board
- LED display (red)
- Times to 99 min. 59.99 sec. with auto reset
- Quartz crystal controlled
- Three stopwatches in one: single event, split (cumulative) & Taylor (sequential timing)
- Uses 3 penlite batteries
- Size: 4.5" x 2.15" x .90"

JE900 \$39.95

## MICROPROCESSOR COMPONENTS

8080A/8080A SUPPORT DEVICES		MICROPROCESSOR MANUALS	
8080A	CPU	M-280	User Manual \$7.50
8212	8-Bit Input/Output	M-CDP1802	User Manual 7.50
8214	Priority Interrupt Control	M-2650	User Manual 5.00
8216	8-Directional Bus Driver		
8224	Control Generator/Driver		
8226	Bus Driver		
8228	System Controller/Bus Driver		
8230	System Controller		
8231	Prog. Comm. 1/0 (USART)	2513(2140)	Character Generator (upper case) \$9.95
8253	Prog. Interval Timer	2513(3021)	Character Generator (lower case) 9.95
8255	Prog. Periph. 1/0 (PPI)	2516	Character Generator 10.95
8257	Prog. DMA Control	MMS230N	2048-Bit Read Only Memory 1.95
8259	Prog. Interrupt Control		
8800/6800 SUPPORT DEVICES		ROM'S	
MC6800	MPU	1101	256X1 Static \$1.49
MC6802CP	MPU with Clock and Ram	1103	1024X1 Dynamic 1.99
MC6810API	128KB Static Ram	2101(8101)	256X4 Static 3.95
MC6821	Periph. Inter. Adapt (MC6820)	2102	1024X1 Static 1.75
MC6828	Priority Interrupt Controller	2102	1024X1 Static 1.95
MC6830L8	1024X8 Bit ROM (MC68A30-8)	2112	256X4 Static MOS 4.95
MC6850	Asynchronous Comm. Adapter	2112	1024X4 Static 450ns 9.95
MC6852	Synchronous Serial Data Adapt.	2114	1024X4 Static 450ns low power 10.95
MC6860	0-600 bps Digital MODEM	2114-3	1024X4 Static 300ns low power 11.95
MC6862	2400 bps Modulator	5101	256X4 Static 7.95
MC6880A	Quad 3-State Bus Trans. (MC68T86)	5280/2107	4096X1 Dynamic 4.95
		7489	16X4 Static 1.75
MICROPROCESSOR CHIPS—MISCELLANEOUS		745200	256X1 Static Tristate 4.95
2801(7801)	CPU	93421	256X1 Static 2.95
CDP1802	CPU	UPD414	4K Dynamic 15 pin 4.95
2650	MPU	(MX4027)	
6502	CPU	UPD416	16K Dynamic 16 pin 9.95
8035	8-Bit MPU w/clock, RAM, 1/0 lines	(MX4116)	
8085	8-Bit MPU	TMS1044	4K Static 14.95
TMS9900UL	16-Bit MPU w/hardware, multiply & divide	45N1	
		TMS4045	1024X4 Static 14.95
		2117	16,384X1 Dynamic 350ns (house marked) 9.95
		MMS262	2KX1 Dynamic 471.00
SHIFT REGISTERS		PROM'S	
MM500H	Dual 25 Bit Dynamic	1702A	2048 FAMOS \$5.95
MM503H	Dual 50 Bit Dynamic	21761NTEL	16K* EPROM 59.95
MM504H	Dual 16 Bit Static	TMS2516	16K* EPROM 49.95
MM506H	Dual 100 Bit Static	(2716)	*Requires single +5V power supply
MM510H	Dual 54 Bit Accumulator	48X8	EPROM 89.95
MM5010H	500/512 Bit Dynamic	2708	8K EPROM 29.95
2504T	1024 Dynamic	2716 T.1	16K* EPROM 29.95
2518	Hex 32 Bit Static		*Requires 3 voltages: -5V, +5V, +12V
2522	Dual 132 Bit Static	5203	2048 FAMOS 14.95
2524	512 Static	6301/17611	1024 Tristate Bipolar 3.49
2526	1024 Dynamic	6301/17602	256 Open C. Bipolar 2.95
2527	Dual 256 Bit Static	82523	32X8 Open Collector 3.95
2528	Dual 250 Static	82S115	4096 Bipolar 19.95
2529	Dual 240 Bit Static	82S123	32X8 Bipolar 3.95
2532	Quad 80 Bit Static	74186	512 TTL Open Collector 9.95
2533	1024 Static	74188	512 TTL Open Collector 3.95
3341	Cable Register File (TTL static)	74188	256 TTL Open Collector 2.95
74LS570	4X4 Register File (TTL static)	74S287	1024 Static 3.95
A-Y-5-1013	30K BAUD UART'S		


## CONTINENTAL SPECIALTIES

### Proto Board 203




Model Number	L x W x H (Inches)	Price
PB-5	6.0 x 4.5 x 1.4	\$15.95
PB-100	6.0 x 4.5 x 1.4	\$19.95
PB-101	6.0 x 4.5 x 1.4	\$22.95

### Proto Board 203A

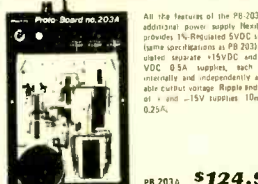

Model Number	L x W x H (Inches)	Price
PB-102	7.0 x 4.5 x 1.4	\$26.95
PB-103	9.0 x 6.0 x 1.4	\$44.95
PB-104	9.8 x 8.0 x 1.4	\$54.95

## THE SINCLAIR PDM35

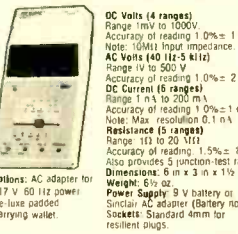

PDM35: Digital Multimeter (completely assembled)	\$59.95
PDM-AC: 117V AC Adapter	6.95
PDM-DP: Deluxe padded carrying case	6.95

## 100 MHz 8-Digit Counter



ACCESSORIES FOR MAX 100:	
Mobile Charger/Eliminator	Model 100 — CLA \$3.95
Charger/Eliminator	Model 100 — CAI \$9.95

## REGULATED POWER SUPPLY

### JE200 5V-1 AMP POWER SUPPLY

- Uses LM309K
- Heat sink provided
- PC Board construction
- Provides a solid 1 amp @ 5 volts
- Can supply up to ±5V, ±9V and ±12V with JE205 Adapter
- Includes components, hardware & instructions
- Size: 3 1/2" x 5" x 2 1/2"

JE200 \$14.95

### JE205 ADAPTER BOARD

- Adapts to JE200 — ±5V, ±9V and ±12V
- DC/DC converter w/ +5V input
- Toroidal hi-speed switching XFMR
- Short circ. protection
- PC Brd. construction
- Piggy-back to JE200 board
- Size: 3 1/2" x 2" x 9/16" h

JE205 \$12.95

\$10.00 Min. Order — U.S. Funds Only  
Calif. Residents Add 6% Sales Tax  
Postage — Add 5% plus \$1 Insurance (if desired)



MAIL ORDER ELECTRONICS — WORLDWIDE  
1021 HOWARD AVENUE, SAN CARLOS, CA 94070  
ADVERTISED PRICES GOOD THRU AUGUST

CIRCLE 5 ON FREE INFORMATION CARD

## The Incredible

### "Pennywhistle 103"



\$139.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modern and terminal for telephone "hamming" and communications. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

- Data Transmission Method: Frequency-Shift Keying, full-duplex (half-duplex selectable)
- Maximum Data Rate: 300 Baud
- Data Format: Asynchronous Serial (return to mark level required)
- Receive Channel Frequencies: 2025 Hz for space; 2225 Hz for mark; 1270 mark, High = 025 space; 2225 mark
- Transmit Channel Frequencies: Switch selectable: Low (normal) = 1070 space, 1270 mark, High = 025 space; 2225 mark
- Receive Sensitivity: -46 dbm acoustically coupled
- Transmit Level: 15 dbm nominal, Adjustable from -6 dbm to -20 dbm
- Receive Frequency Tolerance: Frequency reference automatically adjusts to allow for operation between 1500 Hz and 2400 Hz (EIA RS-232C or 20 mA current loop receiver is optional and non-polar)
- Digital Data Interface: 120 VAC, single phase, 10 Watts
- Physical: All components mount on a single 5" by 9" printed circuit board. All components equipped, is optoisolated and non-polar

Requires a VOM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align.

## TRS-80 16K Conversion Kit


Expand your 4K TRS-80 System to 16K. Kit comes complete with:

- \* 8 each UPD416-1 (16K Dynamic Rams) 250NS
- \* Documentation for conversion

TRS-16K \$75.00
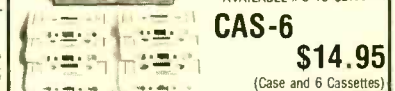
## COMPUTER CASSETTES

- \* 6 EACH 15 MINUTE HIGH QUALITY C-15 CASSETTES
- \* PLASTIC CASE INCLUDED
- \* 12 CASSETTE CAPACITY
- \* ADDITIONAL CASSETTES AVAILABLE #C-15-\$2.95 ea



## CAS-6

\$14.95 (Case and 6 Cassettes)

## SUP 'R' MOD II

- UHF Channel 33 TV Interface Unit Kit
- Wide Band B/W or Color System
- \* Converts TV to Video Display for home computers. CCTV camera, Apple II, works with Cromeco Dazier, SOL-20, IRS-80, Challenger, etc.
- MOD II is pretuned to Channel 33 (UHF).
- \* Includes coaxial cable and antenna transformer.

MOD II \$29.95 Kit

## Function Generator Kit

- \* Provides 3 basic waveforms: sine, triangle & square wave
- \* Frequency range from 1 Hz to 100K Hz
- \* Output amplitude from 0-volts to over 6 volts (peak to peak)
- \* Uses a 12V supply or a ±6V split supply
- \* Incl. chip, P.C. board, components and instructions.

JE2206B \$19.95

## IDEAL FOR TRS 80

- \* "Plug/Jack interface to any computer system requiring remote control of cassette functions"
- The CC100 controls cassette motor functions, monitors tape location with its internal speaker and requires no power. Eliminates the plugging and unplugging of cables during computer loading operation from cassette.



#CC-100 \$29.50

- 63-Key Unencoded Keyboard
- This is a 63-key, terminal keyboard newly manufactured by a large computer manufacturer. It is unencoded with SPST keys, unattached to any kind of P.C. board. A very solid molded plastic 13 x 4" base suits most application. IN STOCK \$29.95/each

Hexadecimal Unencoded Keypad

19-key pad includes 1-10 keys, ABCDEF and 2 optional keys and a shift key \$10.95/each



# Poly Paks'<sup>®</sup>

## ECONOMY MINDED INFLATION FIGHTING



**\$9.99**  
Cat. No. 92CU5653  
**DIAL  
DESK  
TELEPHONE**  
Guaranteed Satisfaction

### 12VDC 10 AMP POWER SUPPLY



**\$49.95**  
• Wired  
• Regulated

Converts 115VAC to 12VDC at 10 Amps fully regulated. Supplies up to 15 Amp surge. Dual transistor regulation with Motorola 2N3055 and 2N3773 for maximum dependability. Less than 100mV ripple, regulation better than 5%. Extra large heat sink for ULTRA COOL operation. Front panel on/off switch, fuse, and indicator lamp for fingertip control. 8 1/2" x 6 1/2" x 4 high. Wt. 9 lbs. Cat. No. 92CU5641



**HANDY COMPUTER  
MULTIMETER**  
• 1000 ohms per volt  
• 1% precision, movement  
diode protected against  
burnout. Measures DC volts  
0-15-150-1000; AC volts  
0-15-150-1000; DC current  
0-150ma; resistance X1000.  
Sensitivity 1000 ohms/volt.  
AC-DC. Uses penlite cell,  
not included. Size 2 1/2" x  
3 1/2" x 1 3/4". Wt. 5 ozs.  
Cat. No. 3921



**40 CHANNEL  
CB BOARD**  
Only **\$9.99**

Poly Paks buys up factory close-out from Hy-gain. "You gain!" Boards have: Heatsinked 9 Watt Amp Chip, RF and Mod. Transistors, and National Semi. MM series P.L.L. May be used for 10 meter conversion. (see 6 month series "CB to 10" in 73 Mag.) The parts alone make it an offer you can't refuse. Cat. No. 92CU5660


**1N4000 Epoxy Rectifiers**

Cat. No.	Type	Volts	Size	Price
2377	1N4001	50	10 for	\$ .75
2378	1N4002	100	10 for	.85
2379	1N4003	200	10 for	.95
2380	1N4004	400	10 for	1.19
2381	1N4005	600	10 for	1.39
2382	1N4006	800	10 for	1.49
2383	1N4007	1000	10 for	1.59

**2000 DEGREE SOLAR  
FURNACE** Only **\$595**

**Giant Fresnel Flat Magnifying Lens**  
It's different! It's unusual! Magnifies like a lens, yet it's flat! A series of small concentric grooves extend from the center to the edge of the lens, acting like a giant prism! Each groove bends the light waves that hit it, acting like a conventional convex lens. Lightweight, inexpensive, and extremely short focal length of 12". Harnesses the sun's energy with the fresnel lens and a simple wooden frame! Focus the sun on any flammable object and watch it burst into flames within seconds! Size 11" square, 3/32" thick. Optically perfect. Wt. 1 lb. Cat. No. 92CU5339

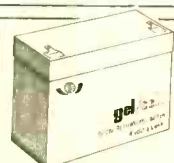**HOW TO ORDER**  
When ordering, always use catalog number, type no., the name of the magazine you are ordering from and the month.



**It's Stacked Energy!  
4V RECHARGEABLE**

### GEL/SEL ENERGY PAKS

Portable Power at Poly Paks Prices! Brand New, 4V @ 2.6 Amp. Hr. Gel Cell storage battery. Units consist of gelled electrolyte, enclosed in hermetically sealed plastic, for years of dependable service. Compact, (only 3 1/2" x 2 3/8" x 1 5/16" in size). Stack 'em to produce 8V, 12V, 24V... or increase the amperage up and away. Use 'em for Burglar Alarms, Intrusion Detectors, Ham, Mobile, or Solar Storage Applications. Cat. No. 92CU5788

### HY GAIN LED CLOCK KIT\*

• Panel or case design • 3 PC set

\*Kit consists of a 3 pc set, transformer, function switches on a board, and a National WA1012 12A digital clock module with all parts and IC chip mounted on a 3" x 1 3/8" G-10 pc board. The RED filtered module measures 3" x 3/4" x 3/16". The PC board-module is mounted in a bakelite frame 3 7/8" x 1 3/4" x 1/8" with 2 holes for easy panel mounting. (3/16" on centers).



**\$9.95**  
Cat. No. 92CU5663




### Only \$9.95 40 channel CB ONE ARM BANDIT BY hy-gain

• Single-Handed Operation Leaves "One For The Road"

• All Controls Contained In The Mike  
Now, take one hand command of all 40 ch's with the One Arm Bandit, the set with the works in the mike. All the controls you need to fumble for on the dash, are planted in the Palm of Your Hand. OFF-ON, VOLUME, SQUELCH, CHANNEL SELECTOR, and DISPLAY, as well as the SPEAKER itself are all conveniently located where your fingers do the talking. Cat. No. 92CU5666
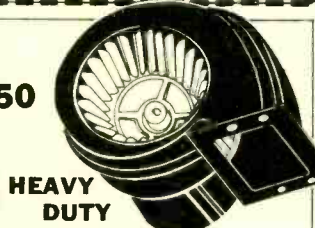
### HIGH POWER 300 CFM BLOWER

Imagine a 300 CFM blower worth \$33.00 at a special purchase for economy savings. Powerful, dynamically balanced. Motor specs 115vac 22 Amps. Housing: Wheel 5 1/2" diameter, 2 1/2" deep; housing diameter 7 1/4" x 3 1/2" deep; FLANGE 4 1/4" square; INLET 3 5/16" x 2 1/2". All black steel construction. 14" long, 115vac wire with lugs. Use for home, shop and industry. Wt. 12 lbs. Removed from equipment. Cat. No. 92CU5165



**\$2.95 Ea**  
**3 ELEMENT  
120 VAC HOTPLATE**  
2 for \$5

This Top Quality, Multi-Purpose Hotplate features: Built-In Thermostat, Neon "Red" AC Indicator Lamp, and 1/8" Textured Glass Surface for even heat distribution. Generates up to 150° C. 120 watts! Use for photographic applications, laboratory work, aquarium heater, plants, etc. Size: 10 3/8" x 5 3/8" x 1/8". Wt. 1 lb. 2 oz. Cat. No. 92CU5723



### ULTRASONIC TRANSDUCER

Perfect for dozens of projects, including remote control alarms, etc. Sends and receives 1" diameter, 1/4" deep, with standard RCA type phono jack. Wt. 2 oz. Cat. No. 92CU5375

**"TIE-PIN"  
CONDENSER MIKE**  
Only **\$2.50**  
It's a little giant in sound quality. Metal encased, and omnidirectional. Frequency response 20-20,000 Hz. Uses tie pin or lapel clip. 600 ohm impedance, 1.5 VDC. Cat. No. 5730


**"BEEM-O-LIGHT"  
LASER DIODES**  
Rated 5-9 Watts  
Wavelength 904 nm. **\$5.99**  
Cat. No. 92CU3508

**"INCHER" READOUT**  
only **\$1**  
To be exact 0.8" of an inch. COMMON CATHODE, direct replacement for Litronics 747, Left decimal. 6V @ 8 mils per segment. Red. Cat. No. 92CU3327

**DIP  
SWITCHES**  
Cat. No. Switches Sale  
3668 2 .77  
3669 3 .88  
3021 4 .99  
3670 5 1.19  
3164 8 1.95  
3672 10 2.50
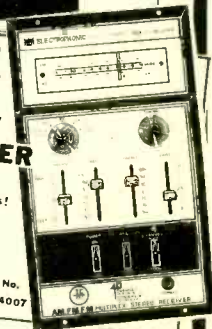
### STEREO AM-FM- MPX TUNER/ AMPLIFIER

Slide volume, bass, treble, balance controls! 2 & 4 speaker systems!  
**\$39.95**  
Cat. No. 92CU4007



### PARALLEL ENTRY DIGITAL PRINTER

**\$14.88**

These unique printers feature precision Swiss construction. 18 key columns are divided into 16 for numerals, and 2 for alphabetical and trig figures, and mathematical functions. Each wheel is 12 position. Utilizes 275' wide adding machine tape, and dual color ribbon. Printing technique: parallel pressure printing, multiple copies. Print Rate: 3 lines per second. Operating voltage: 22 to 28 VDC. Comes in original pecking w/roll of tape. Size: 6 1/2" x 3 1/8" x 5 3/8". Wt. 7 lbs. Cat. No. 92CU5545

### "CRIMP-ON" PL-259 COAX PLUG 4 for \$1.29

Quick, Easy plier crimping. No Soldering! Strip insulation, squeeze. Mates to SO-239. For RG58/U - 59/U.

### MINI LECTROS

MFD.	VOLTS	LEADS	SALE
25	15	Axial	.14
25	25	Axial	.17
50	15	Axial	.17
50	25	Axial	.19
50	100	Axial	.21
100	15	Axial	.23
100	50	Axial	.35
220	25	P.C.	.32
300	25	P.C.	.33
500	15	P.C.	.33
500	25	P.C.	.36
1000	15	P.C.	.55
1000	25	Axial	.69

### "SKINNY-TRIMS" POTENTIOMETERS

3/8" square! Single turn style. Screw driver adjust. 20% tolerance. 0.5 Watt ratings, cermet construction. PC leads. ORDER BY CAT. NO. AND VALUE  
Type-63  
SINGLE TURN FLAT  
6 for **\$2.49**  
Cat. No. 92CU3866

**LED  
WATCH GUTS**  
**\$1.49**  
Cat. No. 92CU5158

**POLY PAKS<sup>®</sup>**  
COD-MAY BE PHONED  
P.O. BOX 942-R8  
SO. LYNNFIELD, MA 01940  
Terms: Add Postage  
Phone: (617) 245-3828  
Retail: 16-18 Del Carmine St.  
MINIMUM ORDER: \$8 Wakefield, MA







## FAIRCHILD RED LED LAMPS

#FLV5057 Medium Size Clear Case RED-EMITTING These are not retested off-spec units as sold by some of our competition. These are factory prime, first quality, new units.



10 FOR \$1.19

50 FOR \$4.95

"WE BOUGHT 250,000 PCS."

"THE COLOSSUS"

### FAIRCHILD SUPER JUMBO LED READOUT

A full .80 inch character. The biggest readout we have ever sold! Super efficient. Compare at up to \$2.95 each from others!

YOUR CHOICE \$1.49 EA

FND 847 Common Anode

FND 850 Common Cathode

(6 for \$6.95)

## NATIONAL SEMICONDUCTOR

## JUMBO CLOCK MODULE

ASSEMBLED,  
NOT A KIT!



\$4.95

\$7.95

REG. \$9.95

ADD \$1.95 FOR  
AC XFMR

**ZULU**

50% OFF SALE!

PERFECT FOR USE  
WITH A TIMEBASE.

MILITARY TIME FORMAT!

MA1008D

BRAND NEW!

### FEATURES:

- FOUR JUMBO 1/2 INCH LED DISPLAYS
- 24 HR REAL TIME FORMAT
- 24 HR ALARM SIGNAL OUTPUT
- 50 OR 60 HZ OPERATION
- LED BRIGHTNESS CONTROL
- POWER FAILURE INDICATOR
- SLEEP & SNOOZE TIMERS
- DIRECT LED DRIVE (LOW RF)
- COMES WITH FULL DATA

COMPARE AT UP TO TWICE  
OUR PRICE!

MANUFACTURER'S CLOSEOUT!

## 16K DYNAMIC RAM CHIP

WORKS IN TRS-80 OR APPLE II

16K X 1 Bits. 16 Pin Package. Same as Mostek 4116-4. 250 NS access. 410 NS cycle time. Our best price yet for this state of the art RAM. 32K and 64K RAM boards using this chip are readily available. These are new, fully guaranteed devices by a major mfg.

VERY LIMITED STOCK!

"MAGAZINE SPECIAL" — 8 For \$79.50

### FAIRCHILD PNP

"SUPER TRANSISTOR"

2N4402 TO-92 Plastic Silicon PNP Driver High Current VCEO-40 HFE-50 to 150 at 150 MA FT-150 MHZ A super BEEFED-UP Version of the 2N3906

8 FOR \$1

### G.I. FULL

WAVE BRIDGE

4 AMP 600 PIV

3/4 In. Square

With Lugs, #LM-1

75¢ ea. 3 For \$2

### MOTOROLA POWER

TRIAC

TO-220 CASE

15 AMP 400 PRV

SPECIAL: 89¢ each

5 FOR \$3.95

### EXPERIMENTER'S CRYSTAL



262.144KHZ This frequency is 2 to the 18th power. Easily divided down to any power of 2, and even to 1HZ. New by CTS-Knight A \$5 value:

\$1.25 each

4.00 MHZ — \$1.75

### TOSHIBA POWER AUDIO AMP

5.8 Watt RMS Typical Output. 50 to 30,000 HZ  $\pm$  3 DB. For CB's, tape decks, PA's, etc. Works off of a single supply voltage from 10.5 to 18 VDC. 10 Pin plastic DIP with special built in heat sink tab. Perfect for use on 12VDC. With Data.

### COMPLEMENTARY POWER TRANSISTORS

SILICON NPN AND PNP. TO-220 CASE.

VCEO - 40V PD - 30 WATTS


FOR AUDIO POWER AMPS, ETC.

TIP29 - NPN

TIP30 - PNP

YOUR CHOICE

3 FOR \$1

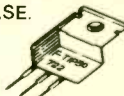

### ANNOUNCEMENT:

To better serve our customers we are splitting Digital Research Corp of Texas into two operating sections: PARTS AND COMPUTERS. We feel this change will allow us to offer you lower prices, better service, and many more new products. Continue to order parts, clock modules, etc. from DRP P.O. Box 401247 Garland, TX 75040. To order computer parts and computer kits order from Digital Research: Computers P.O. Box 401565 Garland, TX 75040.

TERMS: Add 50¢ postage, we pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa, MasterCard, and American Express cards. Tex. Res. add 5% Tax. Foreign orders (except Canada) add 20% P & H. 90 Day Money Back Guarantee on all items.

## Digital Research: Parts

(OF TEXAS)

P. O. BOX 401247 GARLAND, TEXAS 75040 • (214) 271-2461

# SUBSCRIBE AND SAVE!



Get every excitement-packed issue of Radio-Electronics delivered to your door. And save money, too—up to \$9 off newsstand prices! Use the handy coupon and subscribe today!

Mail to: **Radio-Electronics**  
SUBSCRIPTION DEPT., P.O. BOX 2520,  
BOULDER, COLO. 80322 (please print)

Name		
Address		
City	State	Zip Code

Indicate the offer you prefer:

- ☐ 1 Year—12 Issues ONLY \$9.96 (You save \$2.02 off newsstand price.)
- ☐ 2 Years—24 Issues ONLY \$19.00 (Save More! \$5.00 off newsstand price.)

- ☐ Payment enclosed ☐ Bill me
- ☐ Check here if this is a new subscription.
- ☐ Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year. 41H9



### HOUSE MARKED SPECIAL DARLINGTON POWER TRANSISTOR

16 Amps 60 Volts 150 Watts  
Similar to: MJ4030 PNP  
MJ4033 NPN

\$1.50 each  
Specify NPN or PNP

### HEAVY DUTY 12 VOLT RELAY

- Clear Plastic Enclosed
- 3 PNT
- 12 Amp Contacts

\$3.00 each

### 10 MEG POTS

- Standard 1/4 Watt Size
- 3/8" Long Shaft

4 for \$1.00

### SPRITE COOLING FAN

- Used But Fully Tested
- 115 vac 9 watts
- 3 1/8" x 3 1/8" x 1 5/8"

\$8.00 each

### MAGNETICALLY ACTUATED SWITCH

- N.O. W/Magnet Engaged
- Installs in 1/4" Hole
- Magnet Included

75¢ each

### ALCO MINIATURE SWITCH

- S.P.D.T.
- 6 amps @ 125 volts

\$1.15 each

### ALLIED CONTROL

- Miniature P.C. Relay
- MPC-4C00—12VDC
- 4PDT
- 12 VDC @ 960 MW
- 150 ohms

\$2.50 each

### P.N.P. GER. TRANSISTOR

- 2N1038 TO—39
- 40 volts 8 amps 20 watts

\$1.00 each

### N.P.N. SI. TRANSISTOR

- 2N6307 TO—3
- 300 volts 8 amps 125 watts

\$2.00 each

### RHEOSTATS

- 4 ohms 100 watts \$2.00 each
- 25 ohms 25 watts \$1.00 each
- 1K ohm 25 watts \$1.00 each

\$1.00 each

### MALLORY COMPUTER GRADE 150,000 MFD 15 VDC

- 3" Dia. 5" High
- 18V Surge

\$3.50 each

## ALL ELECTRONICS CORP.

SEND FOR OUR FREE FLIER

905 S. Vermont Ave.  
Los Angeles, CA 90006  
(213) 380-8000

Store & Warehouse Hours  
9 AM - 5 PM  
Monday thru Friday

- Quantities Limited
- Min. Order \$5.00
- Add \$1.50 Shipping USA
- Calif. Res. Add 6%
- Same Day Shipping with Cert. Check or M/O

## SEND FOR YOUR FREE TEK-EL CATALOG

Complete listings of IC, Transistors, Capacitors, Resistors and readouts along with mfgs. closeouts and surplus material.

• Hobbyist • Experimenter • Wholesale & Dealer inquiries invited.

Our device is a "MOTION DETECTOR" in the true sense of the word. It detects motion for a distance of 8 feet (minimum), in a cone with a base of 2 ft. The secret is in the ultra complex LSI chip. The device is completely self contained in a case 6" x 3 1/2" x 2" and is powered by 4 "AA" Nicad cells. NOTHING ELSE is needed for the device to perform its basic function.

There are 2 operating modes. Mode 1 is audible. When the device is triggered, an audible "whoop" alarm is sounded. In the silent mode, any motion activates a time delay (adjustable), which then can activate any kind of alarm, such as remote siren, noise maker, telephone dialer, tape recorder etc.

Miniature "MOTION DETECTOR". Complete and operating, includes batteries and charger, but does not contain the silent-remote feature in above 2 versions. 2 1/4" x 3 1/2" x 1". Cigarette pack size.

MODEL 1K "MOTION DETECTOR" kit with data \$24.50

MODEL 1 Completely assembled "MOTION DETECTOR" with batteries and charger \$69.50

MODEL 2 Complete Miniature MOTION DETECTOR with batteries and charger \$39.50

M1137 "MOTION DETECTOR" on board with capacitors \$7.95

ACCY. 1 Set of 4 Nicad batteries \$4.50

ACCY. 2 Charger for 4 Nicad batteries \$5.95

COD'S MAY BE PHONED!  
TERMS: Add Postage  
RATED: Net 30  
PHONE: (617) 631-7434 9:00 A.M. to 4:30 P.M.  
MINIMUM ORDER: \$10  
Mastercharge and Visa accepted.  
When ordering, always use catalog number, type no., the name of the magazine you are ordering from and the month.

TEK-EL Corp.  
P.O. Box 761R  
Marblehead, Mass.  
01945

CIRCLE 37 ON FREE INFORMATION CARD

CIRCLE 45 ON FREE INFORMATION CARD





## FREQUENCY COUNTER KIT

Outstanding Performance

Incredible Price **\$89<sup>95</sup>**

**CT-50**

The CT-50 is a versatile and precision frequency counter which will measure frequencies to 60 MHz and up to 600 MHz with the CT-600 option. Large Scale Integration, CMOS circuitry and solid state display technology have enabled this counter to match performance found in units selling for over three times as much. Low power consumption (typically 300-400 ma) makes the CT-50 ideal for portable battery operation. Features of the CT-50 include: large 8 digit LED display, RF shielded all metal case, easy pushbutton operation, automatic decimal point, fully socketed IC chips and input protection to 50 volts to insure against accidental burnout or overload. And, the best feature of all is the easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on. **Order your today!**

CT-50, 60 MHz counter kit  
CT-50WT, 60 MHz counter, wired and tested  
CT-600, 600 MHz scaler option, add

**\$89.95**

**\$159.95**

**\$29.95**

CB-1, Color TV calibrator-stabilizer

DP-1, DC probe, general purpose probe

HP-1, High Impedance probe, non-loadin

**\$149.95**

**\$12.95**

**\$15.95**

### SPECIFICATIONS:

Frequency range: 6 Hz to 65 MHz, 600 MHz with CT-600  
Resolution: 10 Hz @ 0.1 sec gate, 1 Hz @ 1 sec gate  
Readout: 8 digit, 0.4" high LED, direct readout in mHz  
Accuracy: adjustable to 0.5 ppm  
Stability: 2.0 ppm over 10" to 40" C. temperature compensated  
Input: BNC, 1 megohm/20 pF direct, 50 ohm with CT-600  
Overload: 50VAC maximum, all modes  
Sensitivity: less than 25 mV to 65 MHz, 50-150 mV to 630 mHz  
Power: 110 VAC 5 Watts or 12 VDC @ 400 ma  
Size: 6" x 4" x 2", high quality aluminum case, 2 lbs  
ICS: 13 units, all socketed

## CAR CLOCK

The UN-KIT, only 5 solder connections

Here's a super looking rugged and accurate auto clock which is a snap to build and install. Clock movement is completely assembled—you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell—assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify).

DC-3 kit, 12 hour format **\$22.95**  
DC-3 wired and tested **\$29.95**  
110V AC adapter **\$5.95**

## Under dash car clock

12 24 hour clock in a beautiful plastic case features 6 jumbo RED LEDs, high accuracy (1 min./mo.), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level.

DC-11 clock with mfg. bracket **\$27.95**  
DM-1 dimmer adapter **2.50**

## PRESCALER

Extend the range of your counter to 600 MHz. Works with any counter. Includes 2 transistor pre-amp to give super sens., typically 20 mV at 150 MHz. Specify +10 or +100 ratio.

PS-1B, 600 MHz prescaler **\$59.95**  
PS-1BK, 600 MHz orescaler kit **49.95**

## OP-AMP SPECIAL

741 mini dip **12/\$2.00**  
B1-FET, mini dip, 741 type **10/\$2.00**

## VIDEO TERMINAL

A completely self-contained, stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply, XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor, Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 3216 is 32 char. by 16 lines, 2 pages with memory dump feature. The 6416 is 64 char. by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.

RE 3216, terminal card **\$149.95**  
RE 6416, terminal card **189.95**  
Lower Case option, 6416 only **13.95**  
Power Supply Kit **14.95**  
Video/RF Modulator, VD-1 **6.95**  
Assembled, tested units, add **60.00**

## CALENDAR ALARM CLOCK

The clock that's got it all. 6-5" LEDs, 12 24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size 5x4x2 inches.

Complete kit, less case (not available) **\$34.95**  
DC-9

## 30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out. Max. output of 35 W, incredible value, complete with all parts, less case and T-R relay.

PA-1, 30 W pwr amp kit **\$22.95**  
TR-1, RF sensed T-R relay kit **6.95**

## FM MINI MIKE KIT

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna battery and super instructions. This is the finest unit available.

FM-3 kit **\$12.95**  
FM-3 wired and tested **16.95**

## CLOCK KITS

our Best Seller  
your Best Deal



Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six 4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, bronze, black, blue (specify).  
Clock kit, 12/24 hour, DC-5 **\$22.95**  
Clock with 10 min. ID timer, 12 24 hour, DC-10 **27.95**  
Alarm clock, 12 hour only, DC-8 **24.95**  
12V DC car clock, DC-7 **27.95**  
For wired and tested clocks add \$10.00 to kit price.

## Hard to find PARTS

LINEAR ICs		REGULATORS	
301	\$ .35	78MG	\$1.25
324	1.50	723	.50
380	1.25	309K	.85
380-8	.75	7805	.85
555	.45	78L05	.25
556	.85	7905	1.25
566	1.15	7812	.85
567	1.25	7912	1.25
1458	.50	7815	.85
3900	.50	TTL ICs	
4011	.20	74500	.35
4013	.35	7447	.65
4046	1.85	7475	.50
4049	.40	7490	.50
4518	1.25	74196T1	1.35
5369	1.75	SPECIAL ICs	
2N3904 type	10/1.00	11C50	13.50
2N3906 type	10/1.00	10116	1.25
NPN 30W Pwr	3/1.00	4511	2.00
PNP 30W Pwr	3/1.00	5314	2.95
2N3055	.60	5375AB	2.95
UJT 2N2646 type	3/2.00	7001	6.50
FET MPF102 type	3/2.00	4059 + N	9.00
UMF 2N5179 type	3/2.00	7208	17.95
MRF-238 RF	11.95	LEDs	
SOCKETS		Jumbo red	8/1.00
8 pin	10/2.00	Jumbo green	6/1.00
14 pin	10/2.00	Jumbo yellow	6/1.00
16 pin	10/2.00	Mini red	8/1.00
24 pin	4/2.00	Micro red	8/1.00
28 pin	4/2.00	BiPoar	.75
40 pin	3/2.00	FERRITE BEADS	
		With info, specs	15/1.00
		6 hole balun	5/1.00

## Ramsey's famous MINI-KITS

### FM WIRELESS MIKE KIT

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage.  
FM-1 kit **\$2.95** FM-2 kit **\$4.95**

### COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300W. Great for parties, band music, nite clubs and more.  
Complete kit, ML-1 **\$7.95**

### LED BLINKY KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts.  
Complete kit, BL-1 **\$2.95**

### VIDEO MODULATOR KIT

Converts any TV to video monitor. Super stable, tunable over ch 4-6. Runs on 5-15V, accepts std video signal. Best unit on the market!  
Complete kit, VD-1 **\$6.95**

### TONE DECODER

A complete tone decoder on a single PC board. Features 400-5000 Hz adjustable range via 20 turn pot. voltage regulation. 567 IC. Useful for touch-tone decoding, tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts.  
Complete kit, TD-1 **\$5.95**

### WHISPER LIGHT KIT

An interesting kit. Small mike picks up sounds and converts them to light. The louder the sound the brighter the light. Completely self-contained, includes mike, runs on 110VAC, controls up to 300 watts.  
Complete kit, WL-1 **\$6.95**

### SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker.  
Complete kit, BN-9 **\$5.95**

### POWER SUPPLY KIT

Complete triple regulated power supply provides variable -6 to 18 volts at 200 ma and +5V at 1 A. Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3V @ 1 A and 24 VCT.  
Complete kit, PS-3LT **\$6.95**

### SIREN KIT

Produces upward and downward wail characteristic of a police siren. 5W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker.  
Complete kit, SM-3 **\$2.95**

**ramsey electronics**

BOX 4072, ROCHESTER, N.Y. 14610

PHONE ORDERS CALL

(716) 271-6487




TERMS: Satisfaction guaranteed or money refunded. COD, add \$1.50. Minimum order, \$6.00. Orders under \$10.00, add \$7.50. Add 5% for postage, insurance, handling. Overseas, add 15% NY residents, add 7% tax.



# BULLET ELECTRONICS

P. O. BOX 401244R  
GARLAND, TX 75040  
214/278-3553

## SE-01 SOUND EFFECTS KIT

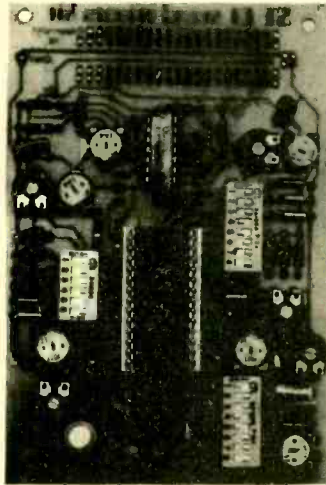

- ALL PARTS
- COMPLETE INSTRUCTIONS
- QUALITY PLATED & DRILLED BOARD
- IC SPECS INCLUDED
- RUNS ON ONE 9-VOLT BATTERY
- SMALL 3 1/2" x 5"
- **\$16.95** LESS SPEAKER & BATTERY
- 76477 CHIP IS INCLUDED. EXTRA CHIPS \$2.95 EACH

OTHERS WILL SELL YOU THE CHIP. BUT ONLY BULLET CAN FURNISH YOU A COMPLETE KIT OF ALL THE PARTS YOU NEED TO PUT THE T.I. 76477 SOUND CHIP THROUGH ITS PACES! WE INCLUDE SPECS AND PROGRAMMING CHARTS. YOU WILL BE AMAZED AT THE THOUSANDS OF SOUND EFFECTS YOU CAN PRODUCE WITH OUR KIT! MAKE PHASOR GUN, STEAM TRAIN, GUNSHOT AND OTHER SOUNDS. BOARD HAS AUXILIARY PULSE GENERATOR, COMPARATOR AND MULTIPLEX OSC FOR EVEN MORE VERSATILITY.

NEW!

## 7 WATT AUDIO AMP KIT

SMALL. SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12 VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THO @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.

**\$5.95**

## 6 DIGIT AUTO/VAN CLOCK

- LARGE 1/2" CHARACTERS (LED)
- QUARTZ XTAL TIMEBASE
- ALARM & SNOOZE OPTIONS
- NOISE FILTERING
- EASY TO ASSEMBLE
- 4 5/8" x 3" x 1 1/2"
- DRILLED & PLATED PC BOARDS

COMPLETE KIT  
12 VDC

**\$16.95**

## ULTRASONIC RELAY KIT

INVISIBLE BEAM. WORKS LIKE A PHOTO ELECTRIC EYE. USE UP TO 25 FT. APART. COMPLETE KIT. ALL PARTS & PC BOARDS.

**\$21.50**

- NO COD'S
- SEND CHECK, M.O., M.C. OR VISA \*
- ADD 5% FOR SHIPPING
- CATALOG FREE UPON REQUEST
- ORDERS UNDER \$10 ADD 75c
- TEX. RESIDENTS ADD 5% SALES TAX
- FOREIGN ADD 10%

## PARTS

301 OP AMP 8 LEAD CAN	3/1.00
723 VOLT REG. 10 LEAD CAN	.50
*13741 FET INPUT 741 MINI DIP	3/1.10
30.000 @ 15V COMPUTER GRADE	2.10
2N4400 NPN GEN. PURPOSE	8/1.00
2N4402 PNP COMPLIMENT	8/1.00
2N6028 P.U.T. W/SPECS	.50
LM380 2W AUDIO IC W/SPECS	1.09
LM377 DUAL LM380 W/SPECS	2.50
*7815 VOLT REG. 1A 15V	.69
*725 LOW NOISE OP AMP	.99
IL-1 OPTO ISOLATOR MINI DIP	.60
*MEM 631 QUAL GATE MOSFET.	
DIOOE PROTECTED. SIMILAR TO 40673	.50
MV1624 VARICAP DIODE 10 PFD	.49
1N4003 1A 200V DIODE	15/1.00
TIP30 TAB PNP POWER	3/1.00
*MC1351P FM IF. DISC IC	.50


\*INDICATES ITEM IS "HOUSE NUMBERED"

## LED'S

JUMBO GREEN	4/.89
JUMBO RED	5/.89
MEDIUM RED (1/8")	.15
MEDIUM GRN OR YELLOW	.16
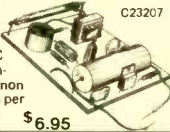
## Electronic Warning Flasher Kit


This battery operated device continuously emits bursts of intense light. Great for bicyclists, skiers, boaters & campers. Comes with all parts, quality PC board and easy-to-understand instructions. Uses high-output xenon flash tube which flashes 2 times per second when batteries are fresh.



**\$6.95**
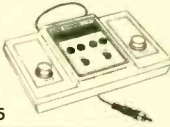
## T.V. Game Special


Reject "Video Olympiad" TV game units. Play 3 exciting color TV games, with on-screen digital scoring and realistic sound effects. You repair and save!



**\$8.95**
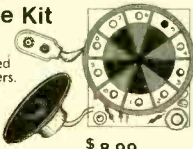
## Wheel of Fortune Kit

Popular game device uses LED's, transistors & IC to give the effect of a bright red ball spinning around numbers. Unit emits a clicking sound as ball spins and finally stops on a number. Incl. all parts, faceplate & P-C board.



**\$8.99**

## Strobe Kit

Complete variable rate strobe light kit. Contains all parts, line cord, PC board and instructions. 117V.

## 6KV Trigger

COIL. To fire xenon flash tubes.

## Strobe Tube Assortment

Brand new factory prime strobe tubes. 5 tubes, w/ schematics.

## Reject Earadio

Rejected for various reasons. We are offering these sets "as-is" at tremendous savings. We send a block diagram of the radio IC with the reject set. W/O batteries.

## Tube Special

6SN7 C23696  
7AK7 C23697  
12AU7 C23698  
12AH7 C23699  
12AT7 C23700

YOUR CHOICE:

2 for \$1.00

- Minimum order: \$5.00
- Please include \$1.00 for postage
- Visa, MC and COD accepted
- Phone orders are welcome

CHANEY electronics inc.

P.O. BOX 27038, DENVER, CO. 80227 (303) 781-5750  
Send for our free giant catalog of unique items!!!

## FREE KIT Catalog

AUTORANGE DIGITAL CAP-METER KIT. Still the best for only \$74.95  
Phone 415-447-3433  
Write or Phone for FREE CATALOG. Average 1 minute Saturday call is 21c.

DAGE SCIENTIFIC INSTRUMENTS BOX 1054R LIVERMORE CA 94550

## YOUR PHONE CALLS ON TAPE

Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up, making a permanent record. Easily installed. No extra monthly phone charges. FCC APPROVED 2-1/4 x 1-3/4 x 3/4 **\$24.50\***

## VOX VOICE ACTIVATED CONTROL SWITCH

2-1/4 x 3/4 x 1-1/2"  
Self contained solid state. Excellent adjustable sensitivity. Recorder activated by voices or other sounds. Uses recorder mike or remote mike. Great for home, business, etc. **\$24.95\***

## AMAZING ELECTRONIC MICRO MINI MIKE

FCC APPROVED  
Among world's smallest, solid state, self contained WIRELESS MIKE. Mercury Bat. turn. Picks up most sounds and transmits without wires up to 300 ft. thru FM Radio. Tuneable. Use as mike, ampl., alarm & alert system, baby sitter, not line, etc. ("Plus \$1.00 Pstg. & Hdg.) Money back guarantee. California residents add tax. Free data. Mail order, Visa, M/C, Cod's o.k. Quantity discount available. AMC Sales, Dept. 19, 9335 Lubec St., Box 928, Downey, Calif. 90241 Phone (213) 869-8519  
**\$18.95\***  
2-1/4 x 3/4 x 1/2"

## SATELLITE TV GET 50 CHANNELS!

It's all true! No matter where you live receive movies, sports, pay television, sports from around the world! 24-hour programming! Crystal clear reception! For complete information sources and design information, send \$7.95.  
SPACECOAST RESEARCH  
Dept. B, P.O. Box 442, Altamonte Springs, FL 32701  
New Technology!

## YOU'RE UNDER SURVEILLANCE!!

A HOST OF PEOPLE, AGENCIES, AND COMPUTERS ARE BUSY SPYING ON YOU AND YOUR BUSINESS EVERY DAY, OFTEN ILLEGALLY. . . .

HOW TO STOP IT OR DO IT BACK!

# THE BIG BROTHER GAME

A Large Format (8 1/2" x 11") Quality Paperback, 240 Pages

BUGGING  
WIRETAPPING  
TAILING  
OPTICAL AND  
ELECTRONIC SURVEILLANCE  
SURREPTITIOUS ENTRY  
DETECTIVE TECHNIQUES  
WEAPONS  
COUNTERMEASURES

**\$11.95** POSTPAID  
"A VIRTUAL ENCYCLOPEDIA ON SURVEILLANCE . . . EVERYTHING YOU'VE ALWAYS WANTED TO KNOW ABOUT SPYING."  
PLAYBOY MAGAZINE

With this order  
FREE SHOPLIFTING BOOKLET FOR DETECTIVES—plus other  
Investigative materials.

QUIMTRONIX  
Postpaid—P.O. Box 548-RE  
Seattle, Washington 98111  
CIRCLE 11 ON FREE INFORMATION CARD



# HICKOK TEST INSTRUMENTS

## HICKOK New Digital Mini-Multimeter

**Lowest  
Price**

MODEL LX303

- Big 1 1/2" high LCD display
- Use indoors or out
- 200 hour 9V battery life
- Auto zero, Polarity, Overrange Indication
- 100 mV DC F.S. sensitivity
- 19 ranges and functions



**Call TOLL FREE  
(800) 645-9518**

In N.Y. State call (516) 752-0050

**"We Will Beat Any  
Advertised Price"**



## Oscilloscopes

**30 MHz Dual Trace**

MODEL 532

Reg. \$995.00

Our Price **\$845.75** incl. probes

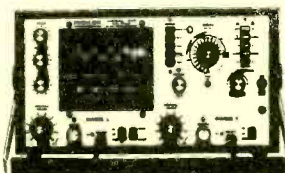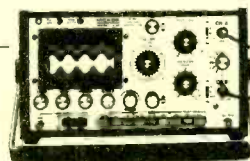

**15 MHz Dual Trace**

MODEL 517

Reg. \$695.00


Our Price **\$590.00** incl. probes

**15 MHz  
Triggered Sweep**

MODEL 515

Reg. \$495.00

Our Price **\$425.75** incl. probes

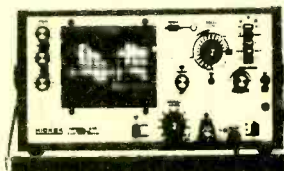

**Before you buy, check our prices...**

**FORDHAM**

YOUR ONE STOP DISCOUNT CENTER

Master Charge, Bank Americard, Visa, C.O.D.'s accepted.

**FREE**

Send for new 1979 catalog of over 3,000 items ... 164 pages of test equipment, CB tools, tubes, components and electronic supplies.

RADIO SUPPLY CO., INC.  
855R Conklin St.  
Farmingdale, N.Y. 11735



ADD \$3.00 TO COVER  
SHIPPING, HANDLING  
& INSURANCE. N.Y.  
Res. add approx.  
sales tax.

**Sinclair  
PDM35 digital MultiMeter**

- 3 1/2 digit resolution
- Sharp, bright LED display
- Automatic polarity selection
- All purpose versatility

Reg. \$59.95 **\$52.95**



**BK PRECISION 3 1/2-Digit  
Portable DMM**

- Overhead Protected • Battery or AC operation • 3 1/2 high LED Display
- Auto Zeroing

Model 2800 **\$85**  
comes complete with test leads, operating manual and spare fuses.  
Model 2810 **\$110.50**



**Ungar  
Heat Gun**  
Reg. \$65.00  
**\$46.50**

**SENCORE  
TV-VTR-MATV  
and Video Analyzer**



Model VA48  
Reg. \$875.00  
Reg. \$975.00

**CONTINENTAL SPECIALTIES**

**100 MHz 8-Digit Counter \$119.00**

- 20 Hz 100 MHz Range • 6 LED Display • Fully Automatic
- Includes 100 IPC circuit board test cable manual

Now Available **PS500 500MHz Prescaler \$52.95**




**BK PRECISION Digital  
Capacitance Meter**



Reg. \$130.00  
**\$110.50** Model 820

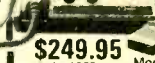**CODE-A-PHONE  
Telephone  
Answering  
Devices**



**\$249.95**  
Model 1500 Model 1400 \$199.95

**BSR Changer  
Accessories**



**\$29.95**  
Model BSR-129

**NLS  
15 MHz Mini  
Oscilloscope**  
Model MS 15



Reg. \$318.00  
**\$269.95**  
• Battery or line operation  
• Automatic and line sync modes  
• Power consumption less than 15 W  
NOW AVAILABLE

**Weller Xcelite**




**Service Master  
Tool Kit**  
Model 99SM  
**\$42.95**

**Tool Cases**  
MODEL TC 100/ST  
Reg. \$783.00  
**\$269.95**



**Roll Kit**  
Model 99PR  
**\$15.95**

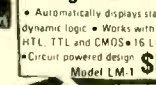


**Logic Monitor**



• Automatically displays static and dynamic logic • Works with DTL, HTL, TTL and CMOS • 16 LED display  
• Circuit powered design  
Model LM-1 **\$52.95** complete

**WAHL  
NEW ISO-TIP  
"Quick Charge"**

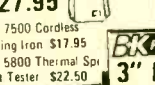

12 units  
**\$27.95**  
Model 7500 Cordless Soldering Iron \$17.95  
Model 5800 Thermal Spi Circuit Tester \$22.50

**6" x 9" 3-Way  
Speaker**



20 oz. ceramic magnet  
**\$14.95**

**Logic Probe**  
Model LP-1  
• Compact, circuit powered  
• Detects pulses as short as 50 nSec  
• Multi family compatibility DTL/TTL/HTL/CMOS  
complete  
**\$40.00**

**20 MHz.  
Dual Trace**  
• Auto. subtract modes on CH 1 & CH 2  
• Front panel X-Y operation  
• 17.5 nSec rise time  
Reg. \$769.95  
**\$654.50**  
with accessories



**SUPER  
SPECIAL**  
Model 1827



**In-Dash  
AM/FM 8 Track  
Stereo**  
Model 600T  
Reg. \$89.00  
**\$65.00**

**HICKOK  
Function  
Generator**  
Model 270  
**\$169.15**

**Weller  
Controlled  
Output  
Soldering  
Station**  
Model 1432P  
Reg. \$780.00  
**\$663.**  
with probes

**15MHz  
3" Dual Portable  
Trace  
Scope**  
Model 1432P  
Reg. \$780.00  
**\$663.**  
with probes

**SENCORE  
POCKET CRICKET  
TRANSISTOR/FET TESTER**  
Reg. \$125.00  
**\$99.95**  
TF 40

**Magnifier  
LAMP**  
Model MG 10A  
**\$49.50**

**700 Series**  
Precision ground and polished magnification lens. Uses 22W T-8 Circine fluorescent.  
Model MG 10A  
**\$49.50**

**30MHz  
Portable  
Frequency  
Counter**  
Reg. \$120.00  
**\$59.95**

**AM/FM  
Cassette  
Stereo**  
CAS 888  
**\$57.50**

**Sub-  
stitution  
Box \$51**  
Model 2910

**Call TOLL FREE  
(800) 645-9518**

**FREE  
1979  
Catalog**

**Auto Stereo 40 Watt  
Power Booster  
POW-40** Reg. \$39.95 **\$24.95**

**VOM Multimeters**  
**20K ohm/v \$19.95**  
with mirrored scale.

**1K ohm/v \$9.95**

**"We Will Beat Any  
Advertised Price"**

**FORDHAM**

855R Conklin St. Farmingdale, N.Y. 11735

For N.Y. State call (516) 752-0050  
MasterCharge • Bank-Americard  
• COD • Check • Money Order  
Add \$3.00 for shipping and insurance  
C.O.D.'s Extra New York State  
residents add, approx sales tax

**FREE  
1979  
Catalog**



## DIGITAL AUTO SECURITY SYSTEM

4 DIGITS  
PERSONAL CODE!!

- proximity triggered
- voltage triggered
- mechanically triggered



### 3-WAY PROTECTION!

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

**SPECIAL \$19.95**


ALL UNITS FACTORY ASSEMBLED AND TESTED—NOT A KIT!

## 100 W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

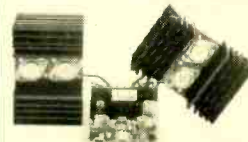- \*Output power : 100W RMS into 8-ohm  
125W RMS into 4-ohm
- \*Frequency response: 10Hz - 100 KHz
- \*T.H.D.: less than 0.008%
- \*S/N ratio: better than 80dB
- \*Input sensitivity: 1V max.
- \*Power supply:  $\pm 40V$  @ 5amp



TA-1000 KIT  
\$51.95  
Power  
transformer  
\$15.00 each

## LOW TIM DC STEREO PRE-AMP KIT TA-10-20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz - 100KHz  $\pm 0.5dB$ ! Added features like tone defeat and loudness control let you tailor your own frequency response. Independent I.C. regulated power supplies to eliminate power fluctuation! Specifications: \*T.H.D. less than .005% \*T.I.M. less than .005% \*Frequency response: DC to 100KHz  $\pm 0.5dB$  \*RIAA deviation:  $\pm 0.2dB$  \*S/N ratio: better than 70dB \*Sensitivity: Phono 2MV 47K/Aux. 100mV 100K \*Output level: 1.3V \*Max output: 15V \*Tone control: bass  $\pm 10dB$  @ 50Hz/treble  $\pm 10dB$  @ 15Hz \*Power supply:  $\pm 24 D.C.$  @ 0.5A

Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A

ONLY \$44.50

X\*FORMER  
\$4.50



## THE MOST ADVANCED TIMEPIECE OF ITS KIND IN THE WORLD!

LCD Quartz Alarm Chronograph with calendar and dual time zone!! Watch is the same as Seiko but you pay a lot more for the name! Features:

- \* 24 hour alarm
- \* Chronograph counts up to 12 hrs. 59 mins 59.9 sec.
- \* Precision of chrono up to 1/10 sec indicated by 10 moving arrows!!
- \* Lap time (with chrono running uninterrupted)
- \* Time displays by LCD for hour, min, sec, day, date of the week and AM/PM.
- \* Calendar gives out date-day
- \* Dual time zone for any two cities of the world at your own choice.
- \* With light switch to allow you to see the time in the dark!



\$65.50

ONE YEAR FULL WARRANTY!

## PROFESSIONAL FM WIRELESS MICROPHONE

TECT model WEM-16 is a factory assembled FM wireless microphone powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric condenser. Element built-in plastic tube type case; mike is 6 1/4" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good. \$16.50



### sanwa

- COMPACT —
- LIGHTWEIGHT —
- ULTRASLIM —
- BATTERY CHECKER
- LED TESTER —

T-55D (w/o temp probe)

\$44.50

T-55THD (temp probe)

\$66.50



### SPECIFICATIONS:

Ranges: 150mV, 500mV, 1.5V, 5V  
DC Voltage: 15V, 50V, 250V, 1kV (AII 20k  $\Omega$  /V)  
25kV (Using HV probe)  
DC Current: 50 $\mu$ A, 2.5mA, 25mA, 250mA (500mV drop)  
AC Voltage: 15V, 50V, 500V 19k  $\Omega$  /V  
AC Current: 6mA, 60mA (2V and 55mV drop)  
Resistance: 10k  $\Omega$ , 100k  $\Omega$ , 1M  $\Omega$ , 5M  $\Omega$  (max. cabinet)  
100k  $\Omega$ , 1k  $\Omega$ , 10k  $\Omega$ , 50k  $\Omega$  (mid scale)  
Load Current: 30mA, 3mA, 300mA  
Load Voltage: 3V, 3V, 3V  
Decibels: -10 to +55dB  
Batt Check: 0.9 to 1.5V (10  $\Omega$  load) (available)  
Temperature: -50 to +100°C and 0 to +200°C (Probe not supplied with T-55D)

Accuracy: DC Voltage:  $\pm 2.5\%$  f.s.d.  
DC Current:  $\pm 2.5\%$  f.s.d.  
Batt Check:  $\pm 2.5\%$  f.s.d.  
AC Voltage/Power on 1.5V range:  $\pm 5\%$  f.s.d.  
AC Voltage/Power above 1.5V range:  $\pm 3.5\%$  f.s.d.  
AC Current:  $\pm 5\%$  f.s.d.  
Resistance/Temperature:  $\pm 3\%$  of arc  
Dimensions: 146 x 97 x 28 mm thick  
Weight: 240g  
Instrument supplied with Batteries 1.5V (UM 3 or R6) x2  
Fuse & Spare: 500mA, 250V  
Temperature Probe (T-55THD only)

## HICKOK LX303 DIGITAL LCD MULTIMETER

- 3 1/2 digits display
- 200 hours 9V battery life
- Auto zero; polarity; overrange indication
- 100mV DC F.S. sensitivity
- 19 ranges and functions
- D.C. volt: 0.1 MV to 1000 V
- A.C. volt: 0.1 V to 600 V
- Resistance: 0.1  $\Omega$  to 20 M  $\Omega$
- D.C. current: 0.01  $\Omega$  A to 100 MA

CALL FOR OUR DISCOUNTED PRICE



### 60W + 60W



### COMPLETED UNIT—NOT A KIT!

OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8  $\Omega$ . Power supply is 24 - 36V AC or DC. Complete unit

Assembled \$49.50 ea.

\$ 8.50 ea.

Power transformer



POWER TRANSFORMER \$6.50 EACH

## 30W 30W STEREO HYBRID AMPLIFIER KIT

It works in 12V D.C. as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mz and 10KHz. \$32.50 PER KIT

## MARK IV 18 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (18 per channel) to indicate the sound level output of your amplifier from -36dB ~ +3dB. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6 ~ 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!

Kit includes 70 pcs. driver transistors, 36 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



MARK IV KIT \$31.50

## JUMBO 1" LED ALARM CLOCK MODULE

- Assembled - not a kit!
- Features:
- \* 1" 4 digits red LED display
  - \* 12 hours real time format
  - \* 24 hours alarm audio output (just add speaker)
  - \* Power failure indicator
  - \* Count down timer 59 mins.
  - \* 12-16V AC 50/60 Hz input
  - \* 10 min. snooze control



Red Display \$8.50 each  
Green Display \$10.50 each

Transformer \$1.75

## ELECTRONIC DUAL SPEAKER PROTECTOR

Cut off when circuit is shorted or overload to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM

\$8.75 EA.



## FM WIRELESS MIC KIT

It is not a pack of cigarettes. It is a new FM wireless mic kit! New design PC board fits into a plastic cigarette box (case included). Uses a condenser microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft.! With an LED indicator to signal the unit is on.

KIT FORM \$7.95





## SUPER 15 WATT AUDIO AMP KIT



**ONLY \$23.50 each**

Uses STK-015 Hybrid Power Amp

Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power 1/2dB response from 20-100,000 Hz. This amplifier has QUASI-Complementary class B output. Output max is watt (10 watt RMS) at 4Ω.

**REGULATED DUAL VOLTAGE SUPPLY KIT**  
±4 ~ 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C., heat sinks and P.C. board.

**\$12.50 PER KIT**

### MANY SOUND DECISIONS!




\$3.60 EACH

Solid state sound indicator operating voltage 6V DC 30mA. Small size approximately 1/2" x 1 1/4".


Model EB2116 (Continuous)  
Model EB2126 (Slow Pulse)  
Model EB2136 (Fast Pulse)



Continuous

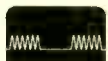

Slow pulse

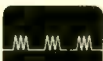

Fast pulse

### 1Watt AUDIO AMP

All parts are pre assembled on a mini PC Board. Supply Voltage 6 ~ 9V D.C. SPECIAL PRICE \$1.95 ea.

### "FISHER" 30 WATT STEREO AMP

MAIN AMP (15W X 2)

Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board, Power supply ± 16V DC (not included). Power band with (KF 1% ± 3dB). Voltage gain 33dB. 20Hz ~ 20KHz.

Super Buy Only \$18.50

### 5W AUDIO AMP KIT

2 LM 380 with Volume Control. Power Supply 6 ~ 18V DC. ONLY \$6.00 EACH

### WE FOUND THE CASE FOR THE FM MIC!

Small nice looking aluminum case size like a pack of cigarettes. It is an intercom Audio amp inside with a mic jack, a mini toggle switch on top, can be used for many projects. We give you the circuit data as well.

VERY SPECIAL PRICE 2 for \$4.99

### Sub-Mini Size CONDENSER MICROPHONE

FET Transistor Built-in \$2.50 each

### ELECTRONIC ALARM SIREN

COMPLETE UNIT

Ideal for use as an Alarm Unit or hookup to your car back up to make a reverse indicator. Light Output up to 130dB. Voltage Supply 6 ~ 12V \$7.50

### SOUND ACTIVATED SWITCH

All parts completed on a PC Board. SCR will turn on relay, buzzer or trigger other circuit for 2 ~ 10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V ~ 3V D.C. \$1.75 ea/2 for \$3.00

### LINEAR SLIDE POT

500KΩ SINGLE Metal Case 3" Long 2 FOR \$1.20

Rechargeable NI-CD Batteries Pak 6AA NI-CD in a flat pack gives you a total of 7.2V 450MA output \$5.25 PER PACK

### BATTERY POWERED FLUORESCENT LANTERN

#### FEATURES

- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6V cool/daylight miniature fluorescent tube.
- 8 x 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing illumination of the lantern.

\$10.50 EACH MODEL 888 R

### PROFESSIONAL CASE



for our 0-30V Power Supply. It is a nice looking metal cast case with giant 4" volt/amp meter; output blinding post and fuse holder, on/off switch and line cord!

ONLY \$21.50 EA.

CASE 030

### POWER SUPPLY KIT

0-30V D.C. REGULATED



Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts.

0-30 POWER SUPPLY \$10.50 each

Transformer for Power Supply, 2AMP 24V x 2 \$8.50

### 12V DC MINI RELAY

6V SPDT 2AMP 1.30  
12V SPDT 3AMP 1.60  
12V DPDT 2AMP 2.50  
12V 4PDT 3AMP 3.50




### SUB-MINI SIZE SPDT RELAY

Ideal for use in mini circuits, contact rated at 1amp 125V AC. Coil resistance 300Ω, standard 0.1" lead spacing allows it to plug into a 14 pin I.C. socket!



12V DC type \$2.50 ea.  
5V DC type \$3.50 ea.


### ULTRA SONIC SWITCH KIT

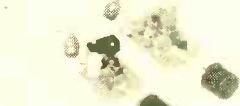

Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operated by 9-12 DC.

\$15.50

### LCD CLOCK MODULE!

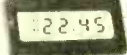

- 0.4" LCD 4 digits display
- X'tal controlled circuits
- D.C. powered (1.5V battery)
- 12 hr. or 24 hr. display
- 24 hr. alarm set
- 60 min. countdown timer
- Dual time zone display
- Stop watch function

NIC1200 \$24.50 EA.

### I.C. TEST CLIPS

Same as the E Z clips With 20 Long Leads in Black and Red Colors \$2.75 per pair



### BECKMAN FET

### LIQUID CRYSTAL DISPLAY

Overall size 2" x 1.2" 0-5" characters reflective type



737-01



739-04



739-03

Model 737-01 - for clock 4 digits with PM, alarm, snooze, colon indicators.

Model 739-04 - for panel meter 4 digits.

Model 739-03 - for panel meter 3 1/2 digits with ± sign and over range indicator.

All displays include zeber connectors and front bezel. With data sheets. Your choice—any model \$7.50 EACH

### FLUORESCENT LIGHT DRIVER KIT

12V DC POWERED

Lights up 8 ~ 15 Watt Fluorescent Light Tubes Ideal for camper, outdoor Auto or Boat



Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included! WITH CASE ONLY \$6.50 PER KIT

### MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches! Receives all AM stations Batteries and ear phone included

Only \$10.50



### SOUND GENERATOR I.C.

T176477

Creates almost any type of sound—gun shot, explosion, train, car crash, star war, birds, organ ext. A built-in audio amplifier provides high level output. Operates from one 9V battery, 28 pin dip; we supply the datas. \$2.90 EACH

### Sub Mini Size PANEL METER

500 U.A. ONLY \$1.20 ea



### ELECTRONIC SWITCH KIT CONDENSER TYPE

Touch On Touch Off uses 7473 I.C. and 12V relay \$5.50 each



### TRANSFORMERS

ALL 117-VOLT INPUT



30V 4AMP \$7.50 EA.  
36V CT 3AMP \$8.50 EA.  
48V CT 3AMP \$8.50 EA.  
24V CT 3AMP \$8.50 EA.  
24V CT 0.5AMP \$1.80 EA.  
12V CT 0.5AMP \$1.80 EA.  
12V CT 120MA \$1.25 EA.

### AC POWER SUPPLY

Wall Type Transformer



12V AC Output 200MA \$2.75 EA.  
16V CT AC Output 100MA \$2.10 EA.  
6V DC Output 120MA \$1.90 EA.  
12V DC Output 100MA \$1.90 EA.

### PROFESSIONAL PANEL METERS



A. 0-50UA 8.50 ea  
B. 0-30VDC 8.50 ea  
C. 0-50VDC 8.50 ea  
D. 0-3ADC 9.00 ea  
E. 0-100VDC 9.00 ea



TYPE MU-52E ALL METERS WHITE FACE WITH BLACK SCALES. PLASTIC COVER.

### HEAVY DUTY CLIP LEADS

10 pairs - 5 colors Alligator clips on a 22" long lead. Ideal \$2.20/pack for any testing.



### UNIVERSAL PROTOBOARDS "CIRCUIT FIT"

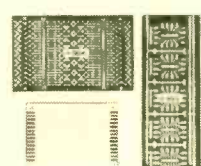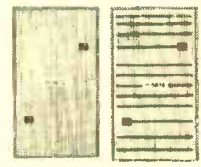


All Boards are made of High Quality G10 Fiber-glass and Phenolic. Pre-drilled in .042" diameter holes on 0.1" centers with tin plated copper eyelet and finger edge connectors (single sided) to allow any kind of standard components to fit board.

H-5612 3 1/2" x 6" 1.70  
H-5616 3 1/2" x 6" 1.70  
H-5606 3 1/2" x 6" 1.50  
H-5602 2 1/2" x 6" 1.50
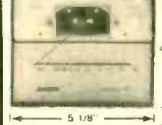
### GIANT SIZE VU METER

1MA movement 3 1/2" scale length. Scale in VU -20db to +3db. Meter face 5 1/8" x 2 3/8" with a "smoke" plastic cover.



SPECIAL

\$8.50 Each

### PUSH-BUTTON SWITCH

N/Open Contact Color: Red, White, Blue, Green, Black 3/\$1.00 N/Close also 50¢ ea. LARGE QTY. AVAILABLE



## FORMULA INTERNATIONAL INC.

8/79

	SHIPPING AND HANDLING CHARGES	
	Under \$50.00 purchase	Over \$50.00 purchase
Inside California	10%	5%
Outside Calif. (includes Mexico & Canada)	15%	10%
Overseas	25%	20%

Minimum Order \$10.00/Calif. Residents Add 6% Sales Tax

Phone Orders Accepted on Visa or MC ONLY, NO C.O.D./Store Hours 10-7 Mon. thru Sat.

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250  
PHONE: (213) 973-1921 • (213) 679-5162

Send \$1.00 For Detailed Catalogue

1984



C/MOS (DIODE CLAMPED)									
4001	- 22	4023	- 22	4089	45	74C93	95		
4002	- 22	4024	- 22	4071	20	74C151	1.75		
4007	- 22	4025	- 22	4072	38	74C157	1.75		
4009	- 45	4027	- 45	4518	1.00	74C160	1.20		
4010	- 45	4028	- 80	4520	1.00	74C165	1.25		
4011	- 22	4029	- 95	74C05	27	74C171	1.30		
4012	- 22	4030	- 35	74C02	27	74C174	1.20		
4014	1.20	4035	97	74C08	30	74C175	1.20		
4015	- 1.00	4042	85	74C10	27	74C193	1.40		
4016	45	4044	85	74C06	27	74C197	1.40		
4017	- 1.00	4049	75	74C42	90	74C202	50		
4018	- 90	4050	45	74C73	37	74C214	1.90		
4019	- 45	4051	1.10	74C74	50				
4020	- 1.10	4053	1.10	74C83	1.30				
4021	- 1.10	4055	1.25	74C86	50				
4022	- 1.00	4066	70	74C90	95				

1488 RS232 INTERFACE	\$1.40	UPD101-4K STAT RAM	9.95
1489 RS232 INTERFACE	1.25	1116	9.95
2509 TRI STATE STAT. SR	1.35	5280/21078 4K DYN RAM	3.40
2513 CHANAL GEN. UP	8.75	7M54050	1.99
2518 HXK 32 BIT SR	2.20	5008-HK PROM	5.00
2522 STAT SHIFTRIG	1.95	82523	1.95
2708 BK EPROM 4M10	12.95	825129	3.25
740309 HC 80175 DYN SR	1.35	AVS 103 VARY	5.25
7181-IT1	35.95	TR1 8028	4.98
21021 1480 Hz	.99	8030C TELETYPE 8 BIT AD	
21021 1480 Hz	1.25	CONVERT	9.95
MW5210 4K 1 DYN	3.48	PT 1482 PSAT	6.95
KC4020P	1.95	80564	1.75
2101 1.254 + 4 STAT	2.45	82512	2.75
2111 1.256 + 4 STAT	3.45	82516	2.75
2101 1.256 + 4 STAT	2.75	82228	4.95
211446 STAT RAM 160 nH	8.50	82565	16.00
211716K DYN RAM	7.95	8251	12.50

ICRYSTALS \$3.45 ea.		RIBBON CABLE	
2.000 MHz 6.144 MHz		FLAT (COLOR CODED)	
4.000 MHz 8.000 MHz		#30 WIRE	
3.57 MHz 10.000 MHz		26 cond. .50/ft	
5.000 MHz 20.000 MHz		40 cond. .75/ft	
6.000 MHz		50 cond. .90/ft	

CTS 206-8 eight position dip switch	\$1.60
CTS 206-4 four position dip switch	\$1.45
LIGHT ACTIVATED SCR's to 18, 200V 1A.	\$7.70

SILICON SOLAR CELLS	
4" diameter 4V at 1 AMP	\$10.00

FND 359 C.C. 4" \$6.00	LED READOUTS
FCS 8024 4 digit	DL-704 C.A. 3" \$7.75
C.C. 8" display	DL 747 C.A. 6" \$15.00
FND 503 C.C. 5" \$5.85	HP3400 8" CC \$19.95
FND 510 C.A. 5" \$5.85	HP3405 8" CA \$19.95
DL 704 3" C.C. \$5.85	

Terms: FOB Cambridge, Mass. Send 25¢ for our catalog featuring Transistors and Rectifiers. Send Check or Money Order. Include Postage, Minimum Order \$5.00, COD's \$20.00.

PRINTED CIRCUIT BOARD	
4" x 8" DOUBLE SIDED EPOXY BOARD 1/16" thick	\$52/60
7 WATT LD-65 LASER DIODE 1R	\$8.95
2N 3820 P FET	\$4.45
2N 6457 N FET	\$4.45
2N2646 UJT	\$4.45
ER 930 TRIGGER DIODES	\$4.00
2N 6078 PHOC UJT	\$5.65
MINIATURE MULTI-TURN TRIM POTS	
100, 1K, 2K, 5K, 10K, 20K, 50K, 200K, 1Meg, 2Meg, 5.75 each 3/\$2.00	

25 watt Infra Red Pulse Laser Diode (Spec sheet included)	\$24.95
VERIPAX PC BOARD	\$12.95
Our new Prototyping is a hi density 4" x 6" single sided 1/16" epoxy board. It will hold 40, 24, 16 (34 units), 14 + 8 pin IC's. There are three buses, +5V, ground and a floating bus. There is a pad for a TO-220 regulator. There is a 22 pin edge connector with .156" spacing.	
FP 100 PHOTO TRANS	\$5.50
RED YELLOW GREEN LARGE LED's 2"	6/\$1.00
TIL 118 OPTO-ISOLATOR	\$7.75
MCT-6 OPTO ISOLATOR	\$8.80
1 WATT ZENERS: 3.3, 4.7, 5.1, 5.6, 9.1, 10, 12, 15, 18, or 22V	6/\$1.00
MCM 6571A 7 x 9 character gen	\$10.75

UNIVERSAL 4Kx8 MEMORY BOARD KIT	\$9.95
32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin bus, may be used with F-8 & KIM	

Silicon Power Rectifiers									
PRV	1A	3A	12A	50A	125A	250A			
100	06	14	35	90	370	5.00			
200	07	20	40	130	425	6.50			
400	09	25	65	150	650	9.50			
600	11	30	80	200	850	12.50			
800	15	35	100	250	1050	16.50			
1000	20	45	125	300	1250	20.00			

SAD 1024 a REDICION 1024 stage analog "Bucket Brigade" shift register.	\$14.95
--	---------

IN 4148 (IN914)	15/\$1.00
1 ul 25V ceramic caps	16/\$1.00, \$5.00/100

RS232 CONNECTORS	
DB 25P male	\$2.95
DB 25F female	\$3.50
HOODS	\$1.50

REGULATORS	
323K - 5V 3A	\$5.75
309K	\$1.60
7203	\$5.50
340K - 12, 15 or 24 V	\$1.50
340T - 5, 6, 8, 12, 15, 18 or 24VS	1.40
5, 12, or 15 V	78 MG \$1.35
	79 MG \$1.35

TRANSISTOR SPECIALS	
2N6233 NPN SWITCHING POWER	\$1.95
MRF-8004 a CB RF Transistor NPN	\$7.75
2N3772 NPN Si TO 3	\$1.00
2N1546 PNP GE TO 3	\$7.75
2N4908 PNP Si TO 3	\$1.00
2N5086 PNP Si TO 92	4 \$1.00
2N3137 NPN Si RF	\$5.95
2N3919 NPN Si TO 3 RF	\$1.50
2N1420 NPN Si TO 5	3/\$1.00
2N3761 NPN Si TO 66	\$7.70
2N2222 NPN Si TO 18	5 \$1.00
2N3055 NPN Si TO 3	\$5.50
2N3904 NPN Si TO 92	6/\$1.00
2N3906 PNP Si TO 92	6/\$1.00
2N5296 NPN Si TO 220	\$5.50
2N6109 PNP Si TO 220	\$5.55
2N3138 PNP Si TO 5	5 \$1.00
MPSA 13 NPN Si	4/\$1.00

TTL IC SERIES									
7400	- 32	7430	- 27	75491	- 105				
7401	- 32	7412	- 47	75492	- 105				
7402	- 32	7413	- 42	75154	- 141				
7403	- 32	7414	- 42	74155	87				
7404	- 32	7415	- 67	74157	87				
7405	- 32	7416	- 65	74161	87				
7406	- 32	7480	45	74162	120				
7408	- 32	7483	87	74163	87				
7409	- 32	7485	139	74164	127				
7410	- 32	7486	42	74165	142				
7411	- 32	7489	187	74173	180				
7412	- 32	7490	83	74174	142				
7413	- 32	7491	87	74175	127				
7414	- 32	7492	64	74176	112				
7415	- 32	7493	64	74177	112				
7416	- 32	7494	87	74180	87				
7417	- 32	7495	87	74181	285				
7418	- 32	7496	87	74190	150				
7419	- 32	7497	42	74191	127				
7420	- 32	74121	45	74192	118				
7421	- 32	74122	60	74193	118				
7422	- 32	74123	67	74194	130				
7423	- 32	74125	60	74195	75				
7424	- 32	74126	60	74196	129				
7425	- 32	74145	97	74197	120				
7426	- 32	74148	185	74270	87				
7427	- 32	74150	150	74298	135				
7428	- 32	74151	97	74298	83				
7429	- 32	74153	97	74293	187				
7430	- 32	75322	225	74325	225				

DATA CASSETTES 1/2 HR	\$5.95
14 pin headers	3/\$1.00

MMS387AA	CLOCK CHIPS	\$5.95
M7001		\$7.50
MMS369		\$3.75

NO. 30 WIRE WRAP WIRE SINGLE STRAND	100' \$1.40
-------------------------------------	-------------

ALCO MINATURE TOGGLE SWITCHES	
MTA 106 SPDT	\$ .95
MTA 206 DPDT	\$ 1.70
MTA 206 P-DPDT CENTER OFF	\$ 1.85
MSB 206 P-DPDT CENTER OFF LEVER SWITCH	\$ 1.85

Full Wave Bridges			
PRV	2A	6A	25A
100	22	1.37	1.43
200	82	1.37	2.20
400	1.04	1.65	3.30
600	1.32	1.92	4.40

SANKEN AUDIO POWER AMPS	
\$1010 G 10 WATTS	\$7.90
\$1020 G 20 WATTS	\$15.70
\$1050 G 50 WATTS	\$28.50

TANTULUM CAPACITORS			
.22UF 35V 5/51.00	6.8UF 35V 4/51.00		
47UF 35V 5/51.00	10UF 10V \$2.25		
.68UF 35V 5/51.00	22UF 25V \$4.40		
1UF 35V 5/51.00	15UF 35V \$31.00		
3.2UF 20V 4/51.00	30UF 6V 5/51.00		
4.7UF 15V 5/51.00	150UF 10V \$9.95		
	47UF 20V \$3.35		
	68UF 15V \$5.00		

74LS SERIES		LINEAR CIRCUIT	
74LS00	74LS138	LM 201	-75
74LS01	74LS139	LM 202	25
74LS02	74LS151	LM 307	30
74LS03	74LS153	LM 308	30
74LS04	74LS155	LM 311	75
74LS05	74LS156	LM 318	-75
74LS06	74LS157	LM 324	-90
74LS07	74LS158	LM 339	-110
74LS08	74LS159	LM 339	-70
74LS09	74LS160	LM 370	-15
74LS10	74LS161	LM 377	-160
74LS11	74LS162	LM 377	95
74LS12	74LS163	LM 387	-25
74LS13	74LS164	LM386	80
74LS14	74LS165	LM 390	125
74LS15	74LS166	LM 1800	155
74LS16	74LS167	CA 3080	95
74LS17	74LS168	LM 390	250
74LS18	74LS169	LM 553	250
74LS19	74LS170	LM 555	49
74LS20	74LS171	LM 555	85
74LS21	74LS172	LM 555	200
74LS22	74LS173	LM 555	95
74LS23	74LS174	LM 555	110
74LS24	74LS175	LM 555	110
74LS25	74LS176	LM 555	110
74LS99	74LS250	LM 555	110



# Active Electronic Sales Corp.

## EPROM'S

### Special of the Month

1702A-6	\$6.95	\$4.45
256 x 8 1.5 uS		
2708		\$9.95
1K x 8 450 NS		

## MICROCOMPUTER BOARDS

### SYM-1 MICROCOMPUTER BOARD

- Hardware compatibility with KIM-1
- Standard interfaces include audio cassette with remote control, both 8 bytes second (KIM) and 185 bytes second (SYM-1) cassette formats, TVT and RS232 system expansion bus, 1V KB expansion board interface, four I/O buffers, and an oscilloscope single line display.
- Single +5V power requirements.

SYM-1 \$329.00

### NEC MICROCOMPUTER TK-80A

- The TK-80A is a complete microcomputer on a board based on the industry standard 8080A. The board has both 1K RAM and 1K Electrically Erasable PROM expandable to 8K x 8 and 8K x 8 respectively. It also features 300 to 1200 baud cassette interface, the Kansas City type, and three 8 Bit Programmable I/O Ports (2 I/O lines). Keyboard with 20 trackings, built-in calculator keypad and 8 digit bright 7 digit display are also included.

TK-80A \$299.00



Rockwell International  
AIM65

AIM 65 features on-board thermal printer and alphanumeric display, and a terminal style keyboard. It has an addressing capability up to 65K bytes, and comes with a user dedicated 1K RAM. Two installed 4K ROMs hold a powerful Advanced Interface Monitor program and three spare sockets are included to expand on-board ROM or PROM up to 20K bytes. An application Connector provides for attaching a TVT and one or two audio cassette recorders, and gives external access to the user-dedicated general purpose I/O lines. Also included as standard are a comprehensive AIM65 User's Manual, a handy pocket reference card, an RS500 Hardware Manual, an RS500 Programming Manual and an AIM 65 schematic. AIM 65 is packaged on two compact modules. The circuit module is 12 inches wide and 10 inches long. The keyboard module is 12 inches wide and 4 inches long. They are connected by a detachable cable.

AIM65 \$375.00



MULTIBUS MEMORY  
LARGE SCALE MULTIBUS MEMORY  
MEMORY ONLY

SIZE (BYTES)	MUPRO PRODUCT NUMBER	INTEL EQUIV PART NUMBER	PRICE
16K	MBC-016-8	SBC-016	\$ 715
32K	MBC-032-8	SBC-032	1125
48K	MBC-048-8	SBC-048	1475
64K	MBC-064-8	SBC-064	1795
32K	MBC-032-16	SBC-032	1125
64K	MBC-064-16	SBC-064	1795

## MICROPROCESSOR CHIPS

### CPU's

Part No.	Price
8080A	5.50
8085	12.95
6800	7.95

## INTERFACE SUPPORT CIRCUITS

Part No.	Price	Part No.	Price
8212	1.98	8255	4.95
8214	3.95	8257	10.95
8216	1.98	8259	14.95
8224	2.75		
8226	1.98	6810	3.95
8228	3.98	6820	3.95
8238	3.98	6821	3.95
8251	5.50	6850	4.95
8253	14.95	6852	4.95



Zilog

Z80 CTC	\$10.90	Z80 DMA	\$32.20
Z80A CTC	\$13.10		
		Z80 SIO/0	\$45.00
Z80 CPU	\$13.60	Z80A SIO/0	\$50.00
Z80A CPU	\$16.20		
		Z80 SIO/1	\$45.00
Z80 PIO	\$10.90	Z80A SIO/1	\$50.00
Z80A PIO	\$13.10		
		Z80 SIO/2	\$45.00
		Z80A SIO/2	\$50.00

## Features.....

### BRAND NEW!

1979  
IC MASTER 2500 pages

Complete integrated circuit data selector. Master guide to the latest I.C.'s including microprocessors and consumer circuits.

Free Quarterly Updates

\$39.95




## Texas Instruments Low Profile Sockets

Finest Quality Socket available in the world. Nobody can match Texas Instruments quality — a unique combination of I.C. technology and multi-metal expertise.

Over one million pieces in stock.

Contacts	Price	Contacts	Price
8 PIN	.08	22 PIN	.22
14 PIN	.12	24 PIN	.24
16 PIN	.14	28 PIN	.28
18 PIN	.18	40 PIN	.40
20 PIN	.20		

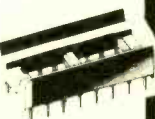

## MOS Static RAM's

Part No. Price

2101	\$2.45	\$2.39
1K 22 PIN		
2102LFPC	\$1.49	\$1.14
1K 350NS (Low Power)		
2102-1PC	\$99	0.94
1K 450NS		
2114	\$6.99	\$6.75
4K (1K x 4) 300NS		
2114	\$6.50	
4K (1K x 4) 450NS		

## MOS Dynamic RAM's

Part No. Price

4K 4027	\$2.95
4K (4K x 1) 300NS 16 PIN	
16K 416-3	\$9.95
16K (16Kx1) 200NS 16PIN	
16K 416-5	\$7.95
16K (16Kx1) 300NS 16PIN	

## UART's

Part No. Price

AY5-1013A	\$4.50	\$4.25
AY3-1015	\$5.50	\$5.25


## 1K CMOS RAM

Part No. Price

5101	\$4.95	\$4.50
450NS (Low Power)		

## L.E.D. LAMPS

LED209	T-1 3mm Red	.09
LED211	T-1 3mm Green	.14
LED212	T-1 3mm Yellow	.13
LED220	T-1 3/4 5mm Red	.11
LED222	T-1 3/4 5mm Green	.15
LED224	T-1 3/4 5mm Yellow	.14

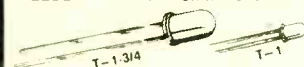

## DISPLAYS

FND357	375	Common Cathode	\$1.45	\$1.09
FND500	500	Common Cathode	\$1.80	\$1.09
FND507	500	Common Anode	\$1.80	\$1.09
FND567	500	Common Anode	\$1.40	\$1.29
DL747	630	Common Anode	\$2.95	\$1.49
DL704	300	Common Cathode	\$1.80	\$1.29
DL707	300	Common Anode	\$1.80	\$1.29

## ISOLATORS

TIL112	Opto Isolator 1500V	\$0.95	\$0.49
MCT6	Dual Opto Isolator 1500V	\$2.95	\$1.29

## LINEAR I.C.'S

LM324N	.49	Quad Op Amp		
LM339N	.49	Quad Comparator		
LM555N-8	.29	Timer		
LM556N-14	.59	Dual Timer		
LM723CN	.36	Voltage Regulator		
LM723CH	.39	Voltage Regulator		
LM741CH	.37	Op Amp		
LM741CN-8	.24	Op Amp		
LM1458N-8	.49	Dual Op Amp		
RC4558N-8	.45	Dual Op Amp		



Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over-the-counter sales,  
12 Mercer Rd., Natick, Mass 01760  
Behind Zayres on Rte. 9  
Telephone Orders & Enquiries (617) 879-0077

### IN CANADA

5651 FERRIER ST.  
MONTREAL, QUEBEC  
H4P 2K5  
Tel: (514) 735-6425

4800 DUFFERIN ST.  
DOWNSVIEW, ONTARIO  
M3H 5S9  
Tel: (416) 661-1115

MINIMUM ORDER \$10.00 • ADD \$2.00 TO COVER POSTAGE & HANDLING

Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.

BAKTER CENTRE  
1050 BAKTER ROAD  
OTTAWA, ONTARIO  
K2C 3P2  
Tel: (613) 820-9471

3070 KINGSWAY  
VANCOUVER, B.C.  
V5R 5J7  
Tel: (604) 438-3321







## SURPLUS OFFER:

### IBM Selectric PRINTER

Removed from equipment. Features x-y servos for graphics, etc. Includes edge connector pin-out drawing plus all circuit diagrams. These terrific Selectric-based printers were part of an electronic word processor system and may be used as an electronic word processor / typewriter or even a terminal. Features independent keyboard.



Printer with schematics: **\$335.00**

Limited Supply, Call now to reserve your printer. Price does not include shipping.

**UNIVERSAL ACTIVE FILTER HYBRID:** Identical to Nat'l AF-100-ICJ. State-variable filter hybrid w/4 on-board op amps, capacitors, etc. A complete active filter with hipass, bandpass, lopass, and notch outputs. Makes simple, low disto sine-wave oscillator. Easily tuned with 2 ext'l resistors or pots. Range DC-10kHz. With Data. **\$6.95 ea.**

### EXCLUSIVE OFFER!!!!

**Audio Comb Filter, Flanger-phase delay kit.** Creates incredible audio effects not available from any other device of a similar nature. So unique we offer a demo "sound-sheet" record (33 1/3 RPM) for 99¢. It's called the **PIPE**. Sounds like a variable pipe with adjustable resonance from a wooden pipe to one of silver. Features 10 notch variable comb filter response. 10 V P-P input/output levels (ideal for synthesizers). Needs  $\pm 15$  volts at 30 mA. Includes all components, PC board, instructions, etc. Nothing even touches it!!!

The PIPE Kit. **\$99.00 ea.**



**RS-232C CONNECTORS:** Removed from equipment, otherwise like new. Specify male or female type. **ONLY \$2.59 Ea.; 2/\$5.00**

### ★ ★ ★ OP AMP SPECIALS ★ ★ ★

NE 531 minidip.....	79¢ ea.	CA 3401 quad dip.....	49¢ ea.
BB 3500 minidip.....	95¢ ea.	SG 14367, TO-99, HiV.....	99¢ ea.
CA 3140 minidip, BiMos.....	66¢ ea.	LM 733 dip.....	35¢ ea.
HA 911, fast, to noise, TO-99.....			\$3.40 ea.
CA 3080 TO-99.....			55¢ ea. 2/\$1.00

• Minimum order \$10.00 • Add \$2.00 for shipping  
• MC, VISA, & C.O.D. accepted • Phone orders are welcome  
**SATISFACTION GUARANTEED**  
**(603)382-5179**

We have many unusual and unique bargains in our CATALOG. Send a stamp or 25¢ (for postage) for a FREE COPY, and get on our mailing list.

**CIRCLE 64 ON FREE INFORMATION CARD**

**PICTURE TUBE MACHINE**  
We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFGR.

For complete details send name, address, zip to:

**LAKEVIEW INDUSTRIES**  
4071 N. Eiston Avenue  
Chicago, Ill. 60618  
Phone: 312-583-6565



### MECHANICALLY INCLINED INDIVIDUALS

Assemble electronic devices in your home. Investment, knowledge, or experience not necessary. Get started in spare time. Above average profits. \$300-\$600/wk. possible. Sales handled by others. Write for free details.

**ELECTRONIC DEVELOPMENT LAB**  
Box 1560R, Pinellas Park, FL 33565

### AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning, Cutting, Rifle, Pistol. Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying. Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE Catalog \$1. Information Unlimited, Dept. R8 Box 716 Amherst, N.H. 03031.

## Give to the college of your choice.



## save on gas!

Enjoy the benefits of 20% better gas mileage, quicker starting, elimination of tune-ups, reduced pollution, and 50,000 miles on plugs and points.

Update your car with a **TIGER** solid state electronic ignition system. Easily installed in 30 minutes . . . even on new cars.

**Tiger 500 CD**  
Assembled . . . . . \$49.95  
Simplikit . . . . . \$29.95

Postpaid USA.

Master Charge & BankAmericard accepted.

### Tri-Star Corporation

Phone (303) 243-5200


P.O. Box 1727

Grand Junction, Colorado 81501

**CIRCLE 20 ON FREE INFORMATION CARD**

# LEADER Test Instruments


## OSCILLOSCOPES

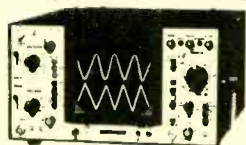

### The 30 MHz Dual Trace Oscilloscope with Delay

- 5mV sensitivity.
- Built-in delay line.
- Single shot trigger (CH-1, CH-2).
- 5" P-D-A CRT assures brighter, sharper trace.
- 20 nS/cm sweep capability plus 11.7 nSec rise time.

LIST PRICE: \$1050 OUR PRICE: **\$888**

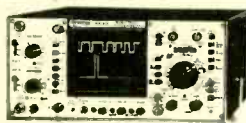

### 25 MHz Dual Trace, Oscilloscope Delayed Sweep

- Sweep delay, continuously variable from 1 uSec to 5 Sec.
- 5 mV/Div. Vertical Sensitivity with  $\pm 3\%$  acc.
- Rectangular CRT with internal graticule.
- 14 nSec rise time.
- CH-1 or 2 trigger; HF filter; and TV sync.


LIST PRICE: \$1395 OUR PRICE: **\$1180**



### The 20 MHz Dual Trace Oscilloscope

- Add & subtract modes (with CH-2 invert).
- Front panel X-Y operation.
- 17.5 nanosec rise time.
- Automatic trigger from either channel, including TV sync.
- 10 mV sensitivity.

LIST PRICE \$769 •OUR PRICE: **\$635**

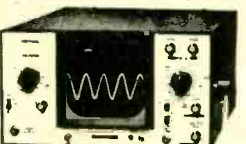

### The 20 MHz Single Trace Triggered Oscilloscope

- Outstanding trigger sensitivity over entire operational range.
- 10 mV sensitivity and 17.4 nSec rise time.
- X5 magnification ( $\pm 5\%$ ) delivers 100 nS/cm maximum speed for easy, precise readings.

LIST PRICE: \$549 OUR PRICE: **\$455**



## NEW DIGITAL MULTIMETERS



8022A

- 10,000 M $\Omega$  resistance meas with conductance function
- Extensive overload and transient protection
- Rugged construction — MIL-T-28800
- Hi/Lo power ohms for in-circuit resistance and diode testing
- 10 M $\Omega$  input impedance doesn't load circuit
- 200 hour battery life — low battery indicator
- Large LCD readout — 2000 counts
- 1 year calibration cycle — only 3 adjustments
- One-hand operation

OUR PRICE: **\$129**



8010A

OUR PRICE **\$239**

8012A

OUR PRICE **\$299**

- Large 3 1/2-Digit LCD's - view in any light
- Conductance function - resistance to 10,000 M $\Omega$
- AC measurements to 50 kHz and higher
- True RMS for ac accuracy
- Touch-Hold probe for tricky places (Y8008)
- Diode test and low power ohms
- One year accuracy reduces calibration costs
- COMMON floatable to 500V
- Recessed jacks reduce shock hazard
- Current mode fuse protection to 600V
- Voltage mode transient protection to 6 kV
- Autozero and autopolarity
- AC or dc current to 10 amps with 8010A
- Resistance resolution to 0.001 $\Omega$  with 8012A
- Built-in batteries and charger (Option -01)
- Rugged enough for field or bench

SEND FOR OUR CATALOG

Call TOLL FREE:

(800)526-2514 • (201)227-7720

### AMPOWER INST., INC.

26 JUST ROAD, FAIRFIELD, N. J. 07006

THE MEASUREMENT SPECIALISTS  
"WE SERVICE WHAT WE SELL"



**FREE**  
TEST LEADS  
WITH EVERY  
ORDER

CALL  
TODAY

Mastercharge  
BankAmericard  
and  
COD Accepted  
add \$3.00 to  
cover shipping  
handling insurance  
N.J. res. add  
5% tax.

**CIRCLE 46 ON FREE INFORMATION CARD**



# Radio Shack: No. 1 Parts Place

## Low Prices and New Items Everyday!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Always count on Radio Shack for the finest quality electronic parts!

### TTL and CMOS Logic ICs

Full-Spec Devices  
Direct from  
Motorola and  
National Semiconductor



Type	Cat. No.	ONLY
7400	276-1801	49¢
7402	276-1811	49¢
7404	276-1802	49¢
7441	276-1804	99¢
7447	276-1805	99¢
7448	276-1816	99¢
7473	276-1803	49¢
7474	276-1818	59¢
7475	276-1806	89¢
7476	276-1813	59¢
7490	276-1808	89¢
7492	276-1819	89¢
74154	276-1834	1.39
74192	276-1831	1.19
74193	276-1820	1.19
4001	276-2401	69¢
4011	276-2411	69¢
4012	276-2412	79¢
4013	276-2413	99¢
4017	276-2417	1.69
4020	276-2420	1.69
4021	276-2421	1.69
4023	276-2423	69¢
4027	276-2427	99¢
4028	276-2428	1.29
4046	276-2446	1.69
4049	276-2449	79¢
4050	276-2450	79¢
4051	276-2451	1.49
4066	276-2466	1.39
4070	276-2470	79¢
4511	276-2447	1.69
4518	276-2490	1.49
4543	276-2491	1.99

### SN-76477 Sound/Music Synthesizer IC

**299**

Featured in Oct.  
Popular Electronics

Creates almost any type of sound — music to "gunshots"! Built-in audio amp. Includes 2 VCO's, LF osc., noise gen., filter, 2 mixers, envelope modulator, logic circuit. 28-pin DIP. With data/applications circuits. 276-1765 ..... 2.99

### Mercury Tilt Switch

- Hermetically Sealed
- Perfect for Alarm Circuits

**89¢**

Actual Size!

Subminiature position-detecting switch for use in projects or special applications. Switch is normally closed when upright, opens when tilted more than 45°. Rated 100mA at 24VDC. 275-025 ..... 89¢




### 15 Ceramic Trimmers

**198**

Assorted low-loss RF trimmer capacitors. May include both compression and piston types rated up to 500VDC with maximum capacity values of 3 to 100 pF. 272-805 ..... Pkg. of 15/1.98

### Top-Quality IC and PCB Accessories

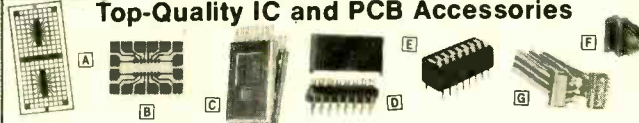

- A PC Board. Mounts two 14 or 16-pin ICs or sockets for bread boarding. Copper clad. 2 1/2 x 5 x 1 1/8". 276-151 ..... 2.99
- B PC Board. Mounts single 14 or 16-pin IC or socket. 276-024 ..... Pkg. of 2/99¢ Sale 2.89
- C 16-Pin IC Test Clip. 276-1951 ..... 1.29
- D 16-Pin DIP Header. With snap-on cover. 276-1980 ..... 1.99
- E 8-Position DIP Switch. 275-1301 ..... 1.99
- F 4-Position DIP Switch. (Not shown.) 275-1304 ..... 1.49
- G Vertical 16-pin Socket. For LED displays. 276-1986 ..... 1.49
- H 16-Pin DIP Jumper Cable. 18" long. 276-1976 ..... 3.99

### DPDT Dual Inline Relay

**449**

Fits Std. 14-Pin IC Socket



Subminiature relay is designed for use with TTL or CMOS circuitry. Contacts rated 1A at 125VAC. Coil requires 5VDC. Coil resistance, 50 ohms. 275-215 ..... 4.49

### MC14553 3-Digit BCD Counter IC

For Low-Cost Digital Readout

CMOS chip replaces over 8 separate IC's in a digital display circuit. Input pulse shaping. Master reset pin. 16-pin DIP. 276-2498 ..... 3.49

### RAM Memory ICs

Under 450 nS Access Time

2102 1024 x 1 Array. Low-cost static memory chip. 16-pin DIP. Buy 8 and save! 276-2501 ..... 2.49 Ea. or 8/14.95  
2114L 1024 x 4 Array. NMOS static RAM. 18-pin DIP. 276-2504 ..... New Low Price 10.99

### Handheld 6-Digit Frequency Counter

Reg. 99.95

**49.95**

- Lead Zero Blanking
- 100 Hz Up to 45 MHz
- kHz and MHz Decimals

Accuracy is 3 ppm at 25°C or less than 30 Hz at 10 MHz. Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. 3x4 1/2". With mini-rod antenna, leads, case, instructions. Requires 9V battery. 22-951 ..... Sale 49.95  
AC Adapter. U.L. listed. 65-731 ..... 4.95



### Digital IC Logic Probe

**24.95**

Multi-Logic Family  
Compatibility  
from 5-15VDC

Detects one-shot low repetition rate, narrow pulses scopes miss. Combines level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high-frequency signals (up to 1.5 MHz). With cables. 22-300 ..... 24.95



### Custom Printed Circuit Board Kit



Everything you need for making high-quality custom PC boards. 276-1576 ..... 7.95  
Extra Resist Pen. 276-1530 ..... 1.29  
Extra Etching Solution. 276-1535 ..... 2.19

### Computer Data Manuals & Semiconductor Handbook


- A Intel 8080/8085 Programming Manual. Handy reference for programming with Intel's assembly language. 62-1377 ..... 3.95
- B Intel Memory Design Handbook. Explains use of Intel's memory components and support circuits in systems. 62-1378 ..... 3.95
- C Intel Data Catalog. 928 pages of specifications on most of Intel's standard microcomputer-related products. 62-1379 ..... 4.95
- D Semiconductor Reference and Application Handbook. Complete specs and applications for popular IC transistors, diodes. 276-4002 ..... Sale 99¢
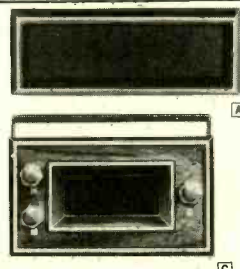
### NEW LEDs

- Tri-Color
- Red Flasher




A Displays red, green, yellow. Uniform light output of 0.6 mcd. Forward voltage: 2.2VDC. Max. current: 25mA. T1-3/4 case style. 276-036 ..... 1.39  
B Operates directly from 5VDC power source. Pulse rate: 3Hz. Max. current: 20mA at 5VDC. 276-038 ..... 1.29



### Digital Project Accessories

- A Bezel with Lens. High-contrast filter for LED displays. 3 3/4" x 1" lens opening. 270-301 ..... 3.95
- B Deluxe Molded Display Case. Red lens. Mount up to four 0.6" or eight 0.3" LED digits. With brackets. 1 1/2" x 3 1/2" x 1 1/2". 270-295 ..... 3.95
- C MA 1003 Clock Case. For car clock modules. Accepts 3 pushbutton switches (not inc.). With brackets, blue lens. 3 1/2" x 2 1/2" x 2". 270-303 ..... 5.95

### Molded Connectors

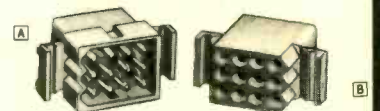

Rated 8A @ 250V. Standard .093" pin diameter.

Fig	Pins	Type	Cat. No.	Each	Fig	Pins	Type	Cat. No.	Each
A	4	Male	274-224	99¢	B	4	Female	274-234	99¢
A	6	Male	274-226	1.19	B	6	Female	274-236	1.19
A	9	Male	274-229	1.39	B	9	Female	274-239	1.39
A	12	Male	274-232	1.49	B	12	Female	274-242	1.49

2-Pin Male & Female. (Not shown) 274-222 ..... Pair 89¢

**WHY WAIT FOR MAIL ORDER DELIVERY?  
IN STOCK NOW AT OUR STORE NEAR YOU!**

Prices may vary at individual stores and dealers

# Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102  
OVER 7000 LOCATIONS IN NINE COUNTRIES

CIRCLE 65 ON FREE INFORMATION CARD



# CARBON FILM 1/4W-5% Resistors

OHMS	OHMS	OHMS	OHMS	OHMS	OHMS	OHMS	OHMS	OHMS
2.7	11	47	200	820	3600	15K	62K	270K
3.0	12	51	220	910	3900	16K	68K	300K
3.3	13	56	240	1000	4300	18K	75K	330K
3.6	15	62	270	1100	4700	20K	82K	360K
3.9	16	68	300	1200	5100	22K	91K	390K
4.3	18	75	330	1300	5600	24K	100K	430K
4.7	20	82	360	1500	6200	27K	110K	470K
5.1	22	91	390	1600	6800	30K	120K	510K
5.6	24	100	430	1800	7500	33K	130K	560K
6.2	27	110	470	2000	8200	36K	150K	620K
6.8	30	120	510	2200	9100	39K	160K	680K
7.5	33	130	560	2400	10K	43K	180K	750K
8.2	36	150	620	2700	11K	47K	200K	820K
9.1	39	160	680	3000	12K	51K	220K	910K
10	43	180	750	3300	13K	56K	240K	1.0M

# HIGH QUALITY... LOW O.E.M. PRICE

5 for .25 10 for .40 100-\$1.60-1000  
one one at \$14.  
value value 100 per value

**CMOS BOARD \$2.95**  
CONTAINS:  
4553 3 digit decade counter  
4511 4bit latch 7 seg. decoder  
driver for LED display  
4060 oscillator w/4 stage binary counter.  
4011 CMOS gate  
2 switches, resistors, capacitors.  
HP 2 digit LED display

# RCA to220 8A, 600V TRIAC ea. 99¢ ten-\$9.50 \$89/c

**BISTABLE RELAY** SPDT 50VDC 700 ohm coils  
1 amp, 20 volt AC contacts  
Long life (10,000+ ops)  
High speed (100 Hz)  
Non-mechanically sealed  
3/8x3/8x3/4" \$2.95 ea.  
**OPTO ISOLATOR** FC0820 6pin DIP  
WILL DRIVE A TTL GATE  
WITH TEN MA LED CURRENT  
69¢ ea ten \$6  
**Ge or Si SIGNAL DIODES** High quality, marked  
colorful grade signal  
diodes. Leads trimmed  
for PCB mounting...  
1/8" mounting center  
40 for \$2

**VOICE ACTUATED SWITCH 95¢ ea**  
COMPLETELY ASSEMBLED ON CIRCUIT BOARD AS SHOWN  
CONTAINS: CRYSTAL MICROPHONE, OPA101 OPAMP,  
TRANSISTOR DRIVER AND 4 AMP SW. WHICH IS TURNED  
ON BY AUDIO FROM MICROPHONE. FEATURES 5-15  
VDC PWR. REQUIREMENTS.  
MICROPHONE CAN BE REPLACED BY COIL PHOTOCELL  
FOR LIGHT ACTUATION.  
40¢ ea. \$3.10

# TRANSISTOR BONANZA!

PRIME TO-92 PLASTIC TRANSISTORS FROM A  
MAJOR SEMI CONDUCTOR MANUFACTURER. THESE  
ARE FIRST QUALITY DEVICES MADE FOR A COM-  
PUTER FIRM. THE NPN'S HAVE CUT AND FORMED  
LEADS (TO-5 SHAPE), AND THE PNP ARE FULL  
LENGTH LEADS. SPECIFY NPN OR PNP. 50 PER  
TYPE MINIMUM.  
\$6 for 100 \$50-k

**SUPER SAVER**  
DIGITAL IC's  
2504T 1024 bit shift register TO-99 \$1.80  
C0402S CMOS 3 input NOR gate DIP .19  
C0401S CMOS 2 input NAND gate .10  
M4015 TTL quad latch MONITORA 1.00  
75451 dual peripheral driver .30  
M0508 1024 bit static shift reg. (8) 1.50  
7402N quad 2 input NOR TTL gate .12  
7430M 8 input NAND gate .30  
7482N divide by 12 TTL counter .30  
SP380 (M0383) NOR BUS receiver 1.00  
PM051 quad MOS interface IC .50  
8424 10/μm dual SR flip flop .25  
5270 pfn compatible w/7400 .30  
7417B (8270) 4 bit sh. reg. .30  
LU321 dual JK flip flop S1C. .25

**LINEAR IC's**  
741 dual 741 op-amp .125  
7706BP 5k audio out w/hat s/n 1.25  
AMP-1 (MC6807) 1W out audio (8) .40  
LU300 precision regulator TO-99 .30  
LM007 op-amp (improved 741) .30  
LM308AH micropwr op-amp 1.00  
uA715 1/4 speed 100V/100kV op-amp  
available in DIP(DIL) or TO99 2.00  
LM1303 Motorola stereo amplifier DIP 2.00  
uA716 programmable op-amp 1.00  
LM309 +5V-1 AMP REGULATOR TO-3 .75  
7812K +12-1 AMP REGULATOR TO-3 1.00  
LS1412 LANCOS +12-3 AMP REGULATOR TO-3  
(removed from sockets full  
specifications guaranteed) 3.95  
63079 zero crossing switch DIL .60  
uA703 VMC transistor array/copy TO99 .30

**ZERO CROSSING SWITCH**  
8.2, lowered 14 pin DIP  
"C" used to trigger timer  
devices - RCA CA3070  
60¢ ea \$5-ten

**DIP TRIMMER**  
12 TURN 1/4" x 1/4" x 1/4"  
5K or 200K only  
mfg. DALE  
\$5.00 TEN FOR \$4

**1/2 WATT RESISTORS**  
10 ea. -390, 1.8K, 3.9K, 6.8K, 11K  
43K, 68K, 240K - 5 percent tol.  
80 FOR \$4

**POTTER BRUMFIELD**  
TYPE KHP RELAY  
4PDT 3AMP  
24VDC 650 ohms  
or  
120VAC 10.5MA  
please specify  
coil required. \$1.75

**Numeric Display**  
1/4" Single Digit  
GaAsP LED  
COMMON CATHODE WITH RIGHT HAND DECIMAL  
POINT. 10 TO 100 DIGITS IN 2.5mm PITCH. MOUNT  
VIBRA L (LEAD-HEAT) RED "C" CHARACTER  
VISIBLE. READ WITH 10X DOWNS. A WIDE  
VIEWING ANGLE-120° PER DIGIT AT TYPICAL  
DISTANCE LEVELS.  
65¢ each - 10 for \$5.95

**VARO SEMICONDUCTOR**  
SAFARI  
EXOTIC BRIDGE RECTIFIERS  
10 AMP 50V V104S  
90 ea. 10 for \$7.50 100-\$65

**PO BOX 41778 SEND FOR FREE FLYER TODAY**  
Sacramento  
California  
95841  
\$5 minimum order, add \$1 handling charge to orders  
less than \$10. We pay post or UPS on domestic orders  
over \$10. BAC MC and VISA accepted. \$15 minimum  
and shipping is added. open accounts accepted from  
government entities and large retail firms.  
SAME DAY SHIPMENT - telephone (916) 334-2161  
4811 Myrtle Avenue, Sacramento, CA 95841

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume  
any responsibility for errors that may  
appear in the index below.

## Free Information Number Page

—	AMC Sales	94
52	A P Products, Inc.	32
10	Aaron-Gavin Instruments	16
17	Active Electronics	99
63	Advance Electronics	7, 71
2	Advanced Computer Products	91
37	All Electronics	92
62	Amelect, Inc.	80
30	American Antenna	Cov. 4
46	Ampower	100
57	B & K Precision Dynascan Co.	75
32	Babylon Electronics	102
—	Karel Barta	84
51	Beckman Instruments	2
—	Bullet Electronics	94
—	Burdex Security Co.	82
64	C F R Associates.	100
—	Chaney Electronics	94
—	Cherry Electronics	79
—	C I E—Cleveland Institute of Electronics	18-21
—	Command Productions	82
31	Concord—Computer Components	86
12	Continental Specialties	Cov. 2
13	The Cooper Group—Electronics Div.	17
—	Dage Scientific	94
8	Delta Electronics	84
29	Digi-Key	87
—	Digital Research Corporation	92
—	Electronic Development Lab	100
41	Electronic Supermarket	98
53	Enterprise Development	76
—	Fair Radio Sales	82
49	Fordham Radio Supply	95
33 & 34	Formula International	96 & 97
—	Fuji-Svea	83
—	G C Electronics	22
60	GFN Industries	35
35	Godbout Electronics	98
—	Golden Enterprises	84
54	Gould, Inc.—Instruments Div.	26
36	Graham College of Engineering	77
100	Heath	13, 25
48	Hickok Electrical Instruments	65
26	Hobby World	86
—	Information Unlimited	100
58	International Crystal Mfg. Co.	73
4 & 5	Jameco Electronics	88-89
7	Jim-Pak	15
—	Lakeside Industries	100
47	Meshna	86
42	Milco Industries	82
—	MTI—Mobile Training Institute	73
—	National Radio Institute (NRI) Div. of McGraw-Hill	8-11
—	National Technical Schools	28-31
43, 44	Netronics	33, 77
24, 25	O.K. Machine & Tool	27, 34
3	Ohio Scientific	1
16	Optoelectronics	Cov. 3
19	P A I A	74
23	PTS Electronics	77
38	Panavise	76
15	Polym Paks	90
39	Pomona Electronics	36
18	Quest	85

11	Quimtronix	94
65	Radio Shack	101
47	Ramsey Electronics	93
20	Rye Industries	26
—	Sabtronics	14
56	Schober Organ	69
—	Sheldahl	16
59	Shure Brothers	67
61	Solarex	33
6	Solid State Sales	98
55	Southwest Technical Products	78
—	Spacecoast Research	94
—	Speakerlab, Inc.	84
9	Tab Books—Electronic Book Club	74
45	Tek-El Corp.	92
20	Tri-Star	100
21	Tuner Service	23
—	V.I.Z. Mfg.	81
28	Wersi Electronics	78
14	Zemco	12

Independent News Company, Inc. is pleased  
to announce a Retail Display Plan available  
to all retailers interested in earning a display  
allowance on Radio-Electronics magazine  
and who purchase the magazines from sup-  
pliers other than Independent News Co.,  
Inc., or the publisher.

To obtain details and a copy of the formal  
contract please write to **Director, Retail Sales  
Division, Independent News Co., Inc., 75  
Rockefeller Plaza, New York, N.Y. 10019.**  
Under the display plan in consideration of your  
acceptance and fulfillment of the terms of  
formal contract to be sent to you upon your  
request you will receive a display allowance of  
10% of the cover price per copy sold by you.  
This plan will become effective with all issues of  
Radio-Electronics delivered to you subsequent  
to the date your written acceptance of the  
formal Independent News Co., Inc. Retail  
Agreement is received and accepted by our  
Company.

## MOVING?

Don't miss a  
single copy of  
**Radio-Elec-  
tronics.** Give  
us:  
Six weeks' no-  
tice

Your old ad-  
dress and zip  
code

Your new ad-  
dress and zip  
code

ATTACH  
LABEL  
HERE

name (please print) \_\_\_\_\_  
address \_\_\_\_\_  
city state zip code \_\_\_\_\_

Mail to: Radio-Electronics,  
SUBSCRIPTION DEPT., P.O. BOX 2520,  
BOULDER, COLO. 80322

**ORDER NOW!**  
CIRCLE 32 ON FREE INFORMATION CARD



# ALL NEW

# Real-State-of-the-Art

## TWO NEW AC•DC•BATTERY PORTABLE COUNTERS

### OPTO-8000 .1A 10Hz to 600 MHz — FREQUENCY COUNTER

- Precision TCXO time base 0.1 PPM Stability 17-40°C
- Super Sensitivity with preamps in both HI-Z & 50 Ohm inputs <10mV to 50MHz, 25 mV @ 150 MHz <50mV to 600MHz
- Auto Decimal Point • Aluminum Case • Socketed IC's
- Three position attenuator: X1, X10, X100 (avoids false counting)

#OPTO-8000.1A	Factory Assembled	.....	\$329.95
#OPTO-8000.1AK	Kit Form	.....	\$279.95
#NI-CAD-80	NI-CAD Battery Pack	.....	\$ 19.95

### OPTO-7000 10 Hz to 600 MHz MINIATURE COUNTER

- XTAL (TCXO) Time Base  $\pm .08$ PPM/°C
  - Aluminum Case • HI-Z & 50 Ohm inputs
  - 1 Sec. & 1/10 Sec. Gate times • Auto Dec. Pt.
  - Built-in Prescaler and Preamps Standard
- |             |                                 |       |          |
|-------------|---------------------------------|-------|----------|
| #OPTO-7000  | Factory Assembled - 1 Year-Guar | ..    | \$139.95 |
| #OPTO-7000K | Kit Form                        | ..... | 99.95    |
| #AC-70      | AC Power Pack                   | ..... | 4.95     |
| #NI-CAD-70  | NI-CAD Battery Pack             | ..... | 19.95    |
| #TCXO-70    | Precision TCXO Time Base        |       |          |
|             | <0.1PPM, 17-40°C                | ..... | 79.95    |

### ACCESSORIES

#### PROBES:

#P-100	50 Ohm, 1X	.....	\$13.95
#P-101	Lo-Pass	.....	16.95
#P-102	H1-Z, 2X	.....	16.95
# AP- 8015	UHF Counter Preamp 20 MHz to 600 MHz 15-50 DB Gain		
	(Not Shown) ..	\$49.95/Kit	\$39.95



#### #D-450 Antenna

Rubber Duck RF Pick-up 450 MHz ... \$12.50

#### #D-146 Same as above

146.5MHz..... \$12.50
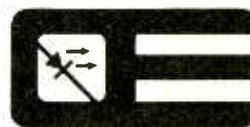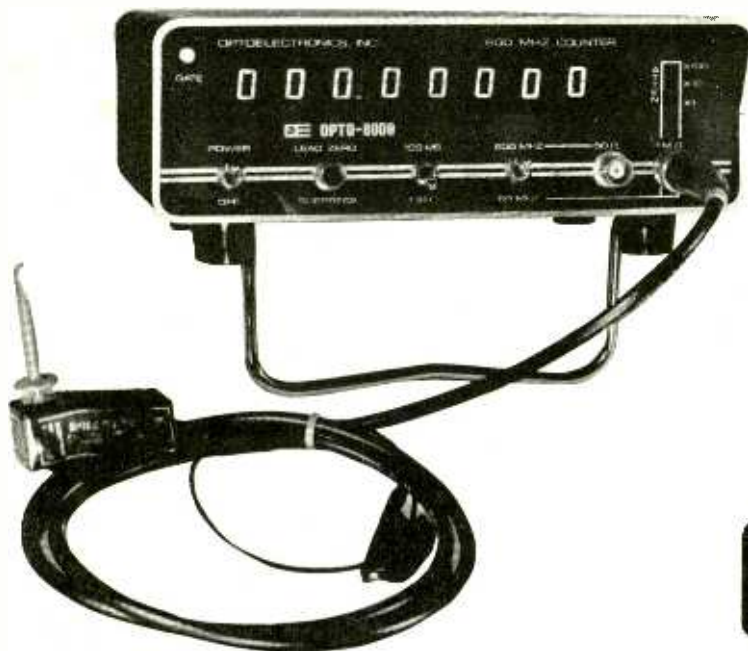
#RA-BNC Right-Angle BNC Adapter for above Antenna ..... 2.95



**OPTOELECTRONICS, INC.**

5821 NE 14 Avenue  
Ft. Lauderdale, FL 33334  
Phones: (305) 771-2050 771-2051

Phone orders accepted

### ORDER FACTORY DIRECT — PHONE OR MAIL

**TERMS:** Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: \$1.00. Personal checks must clear before merchandise is shipped.

# THE K40 SPEECH PROCESSOR

**The K40  
Speech Processor.**  
**So unique it's patented.**  
**So good its guaranteed**  
**to out-perform any**  
**microphone on any radio.**

## **CLIPS ANYWHERE WITHOUT A CLIP!**

Molded four-pole internal magnet clamps instantly to any steel surface. Steering column, metal dash, roof top, or the side of your CB radio. No groping for your mounting clip.

## **PROCESSES SPEECH WITH A COMPUTER CIRCUIT!**

It's its own computer—it automatically monitors your speech and adjusts it in micro-second increments pumping so much db gain into your speech that you get 400% more power than a standard mike.

## **Double Guarantee**

### **GUARANTEE I:**

The K40 Speech Processor is guaranteed to outperform any microphone it replaces or return it for a complete and full refund within 7 days from the K40 Dealer that installed and tuned it.

### **GUARANTEE II:**

Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping, or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. No exclusions. No gimmicks. For a full 12 months.

## **SOUND SENSITIVE 2 INCHES OR 2 FEET!**

A microphone so sensitive it will select your voice and process your speech no matter how close or far you are from the microphone.

## **TWO MICS WITH ONE SWITCH!**

Switch up for a high-pitched transmission for cutting congested city traffic. Switch down for a mellow base in open, uncluttered rural areas.

## **NOISE CANCELLING**

Pull the Processor directly to your mouth and speak directly into the mic. The Processor adjusts to your voice—and blanks out *all* the cab noise while you're speaking. Automatically.

## **FRESH CHARGE WITH NO BATTERIES!**

Patented electronic storage system recharges while you listen to the radio. It provides a fresh electrical charge every time you squeeze the trigger. You never replace batteries.

# **\$42.50\***

American Antenna Elgin, IL 60120

\*suggested retail.

CIRCLE 30 ON FREE INFORMATION CARD

SOLD AND SERVICED EXCLUSIVELY BY 3,500 REGISTERED K40 DEALERS THROUGHOUT THE U.S. AND CANADA